



@ $t = \frac{T}{2}^+$

$$V_{in} = -14V$$

D_1 and D_2 both are off

$$V_o\left(\frac{T}{2}^+\right) = -20.5V$$



$$V_o(s.s.) = 0V, V_c(s.s.) = -14V$$

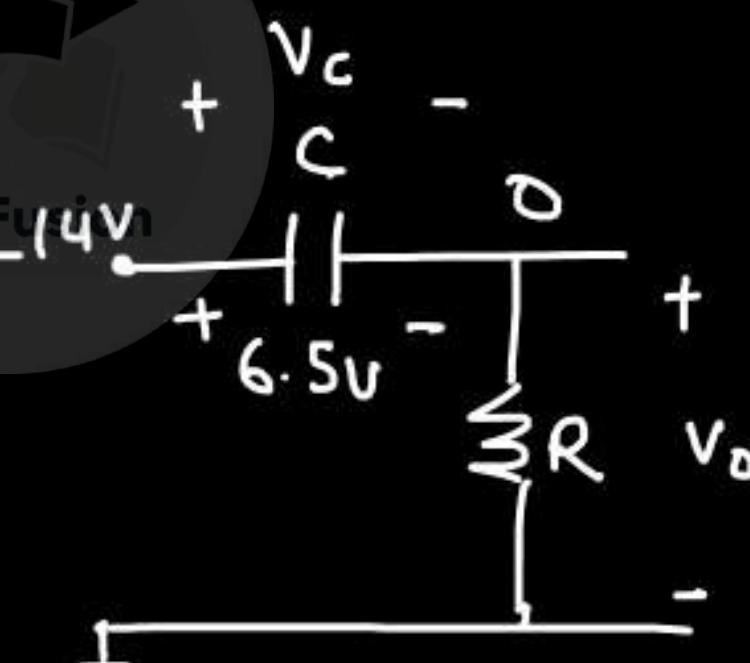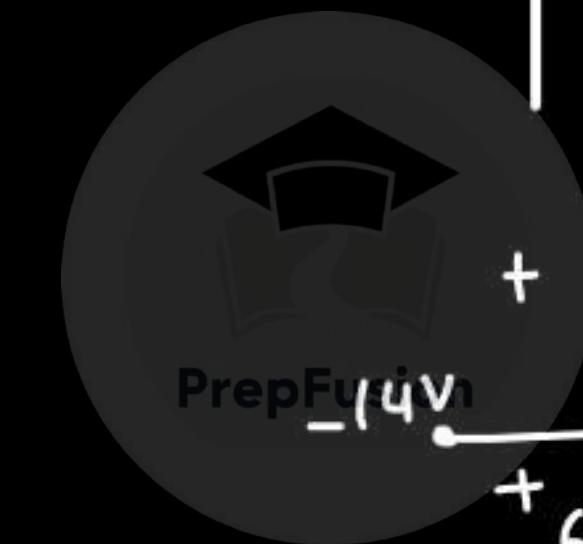



$\frac{1}{RC}$

$$RC \ll \ll T$$


You have
enough time
to reach 8.5

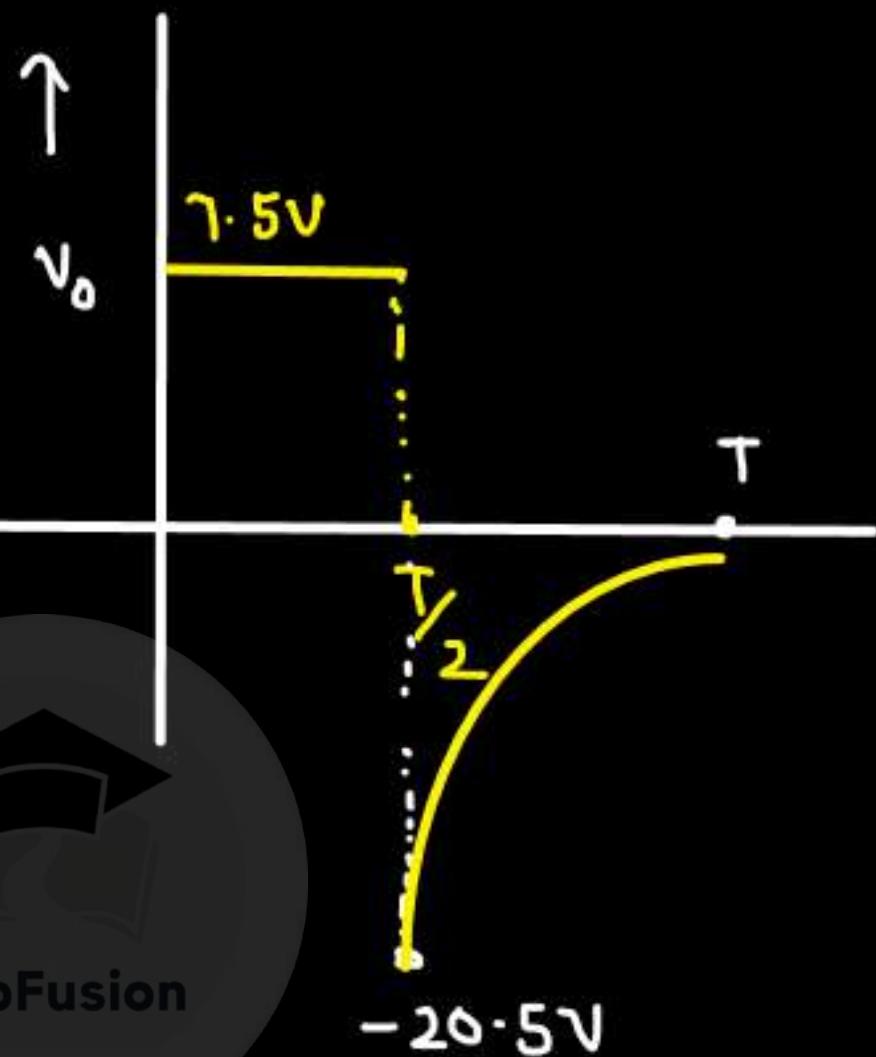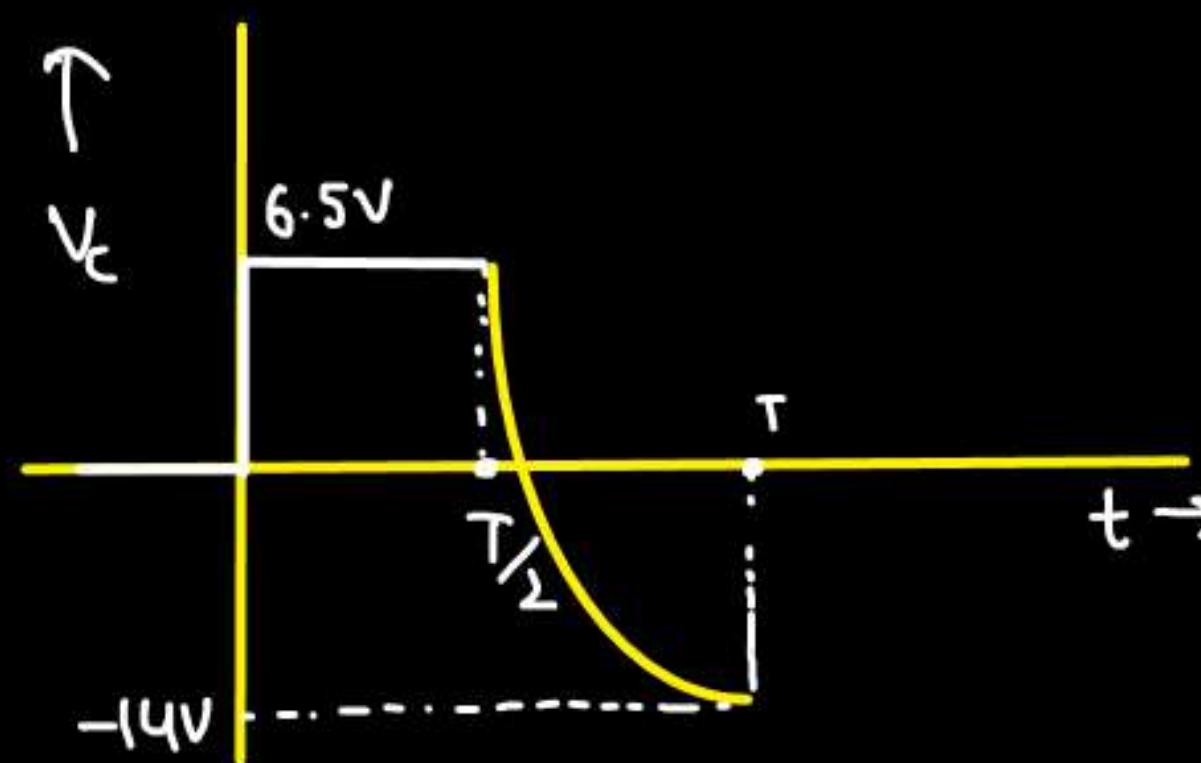

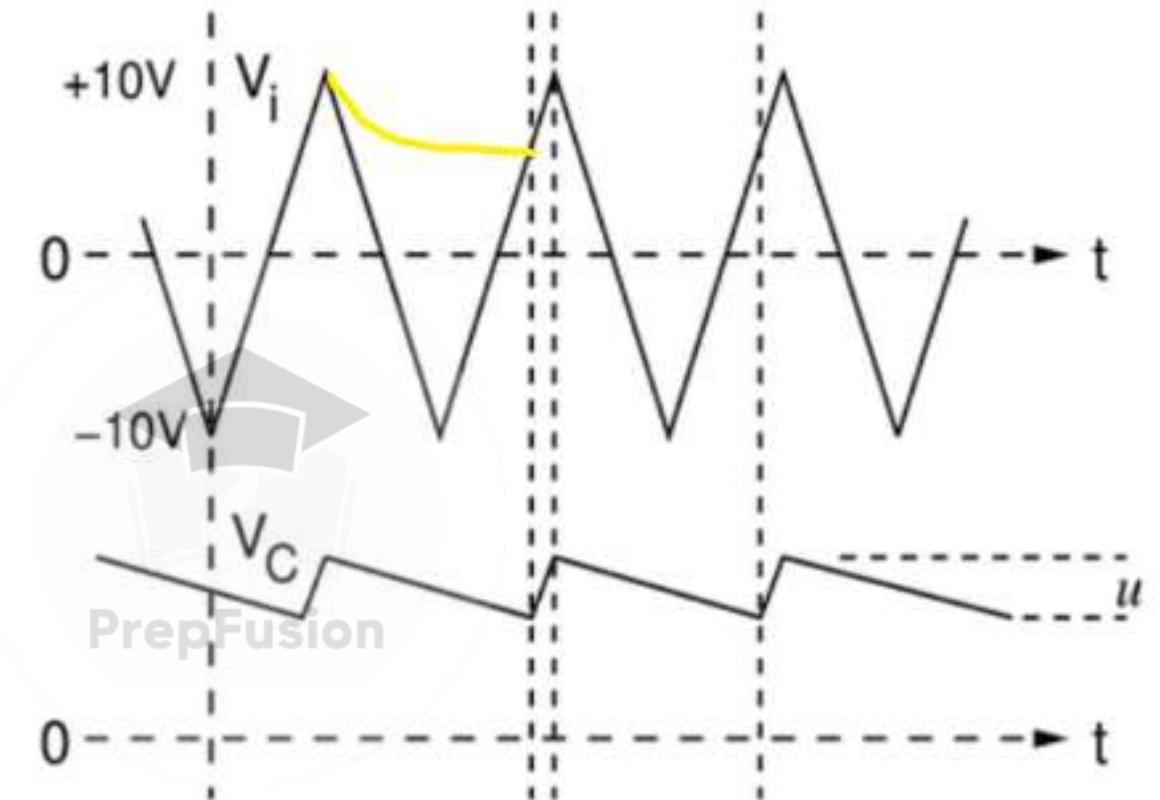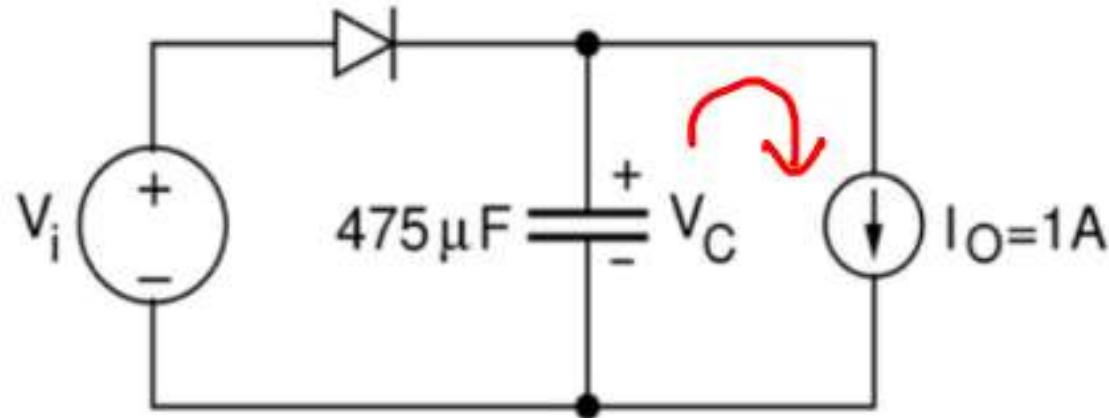The figure shows a half-wave rectifier with a $475 \mu\text{F}$ filter capacitor. The load draws a constant current $I_O = 1 \text{ A}$ from the rectifier. The figure also shows the input voltage V_i , the output voltage V_C and the peak-to-peak voltage ripple u on V_C . The input voltage V_i is a triangle-wave with an amplitude of 10 V and a period of 1 ms.



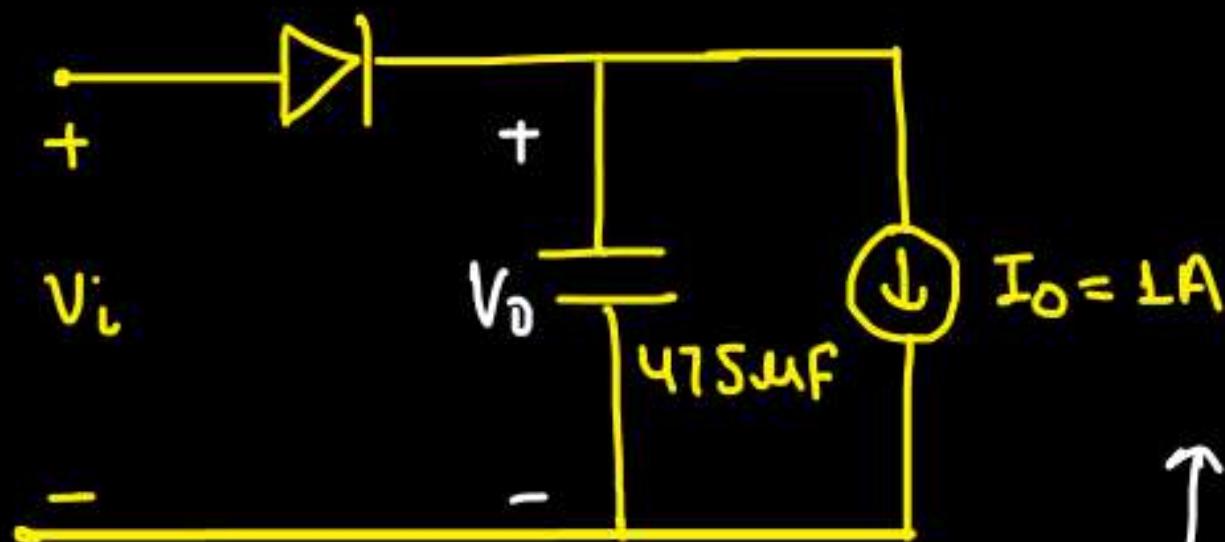
The value of the ripple u (in volts) is _____




$$V_i = +ve \quad (@ t=0^+)$$

diode on
 @ $t = \frac{T}{4}^+$
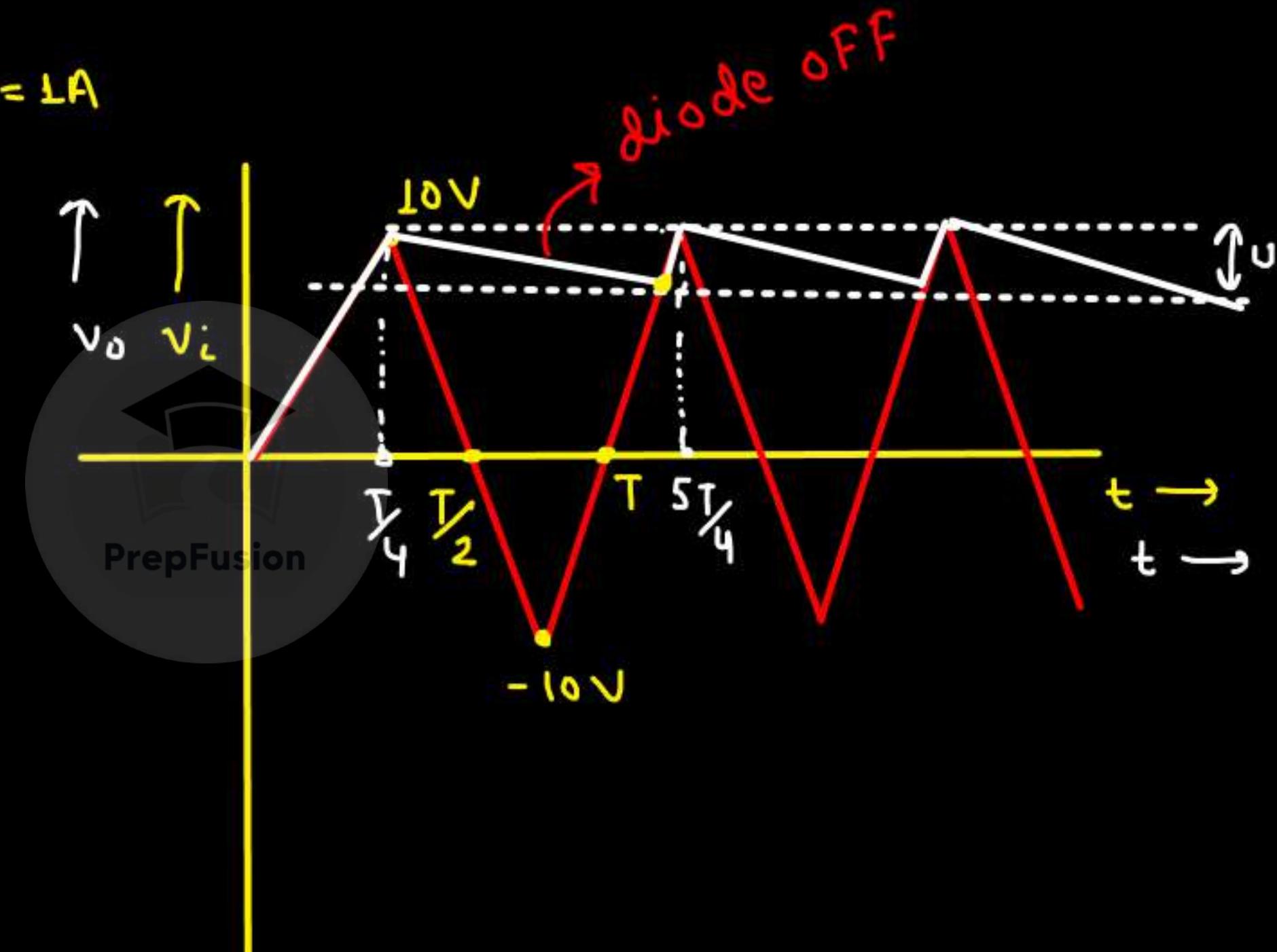
$$V_i = 9.9, \quad V_o = 10 \\ (\text{at}) \quad \Rightarrow \text{diode off}$$



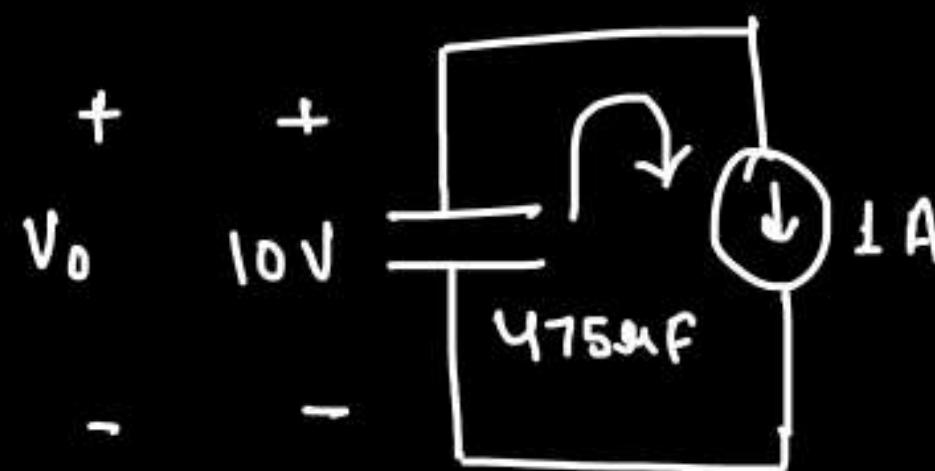

$$v_o(t) = 10 - \frac{t - T_0}{475\mu}$$

$$v_o(\text{s}^{-1}) = 10 - \frac{T}{475\mu}$$

$$= 10 - \frac{1000\mu}{475\mu}$$



$$= 10 - 2.1$$

$$v_o(\text{s}^{-1}) = 7.9 \text{ V}$$

$$i = C \frac{dV_C}{dt}$$



$$V_C = \frac{1}{C} \int_{-\infty}^t i_C \cdot dt$$

$$V_C = \frac{i_C(t)}{C}$$

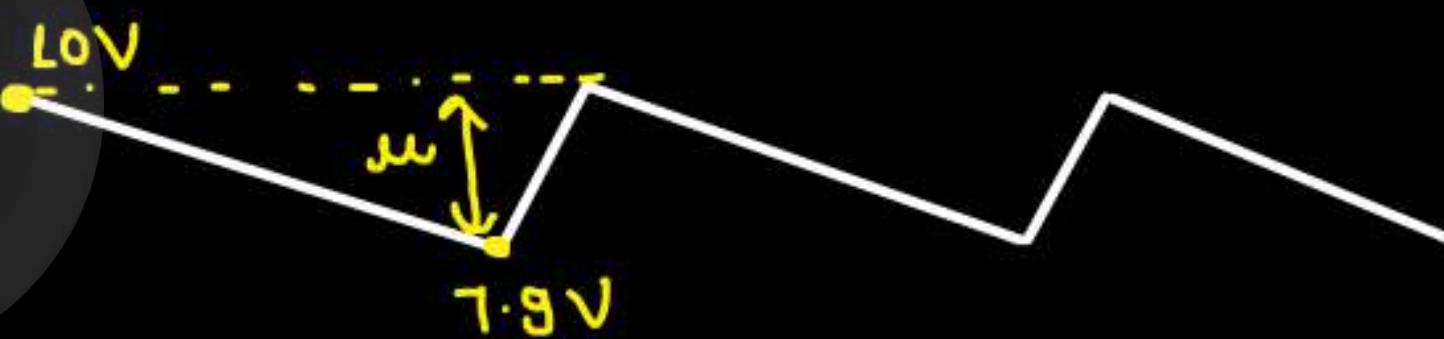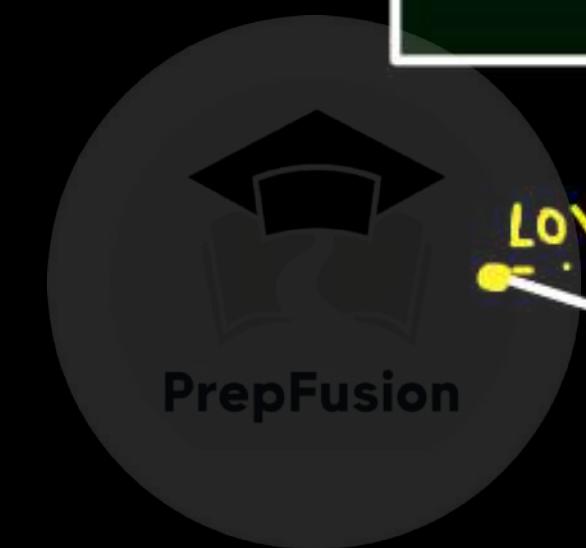

$$\mu = Q \cdot 1 \text{ V}$$

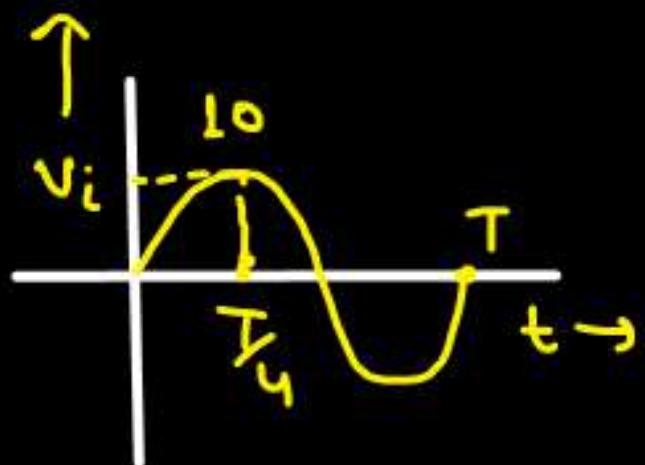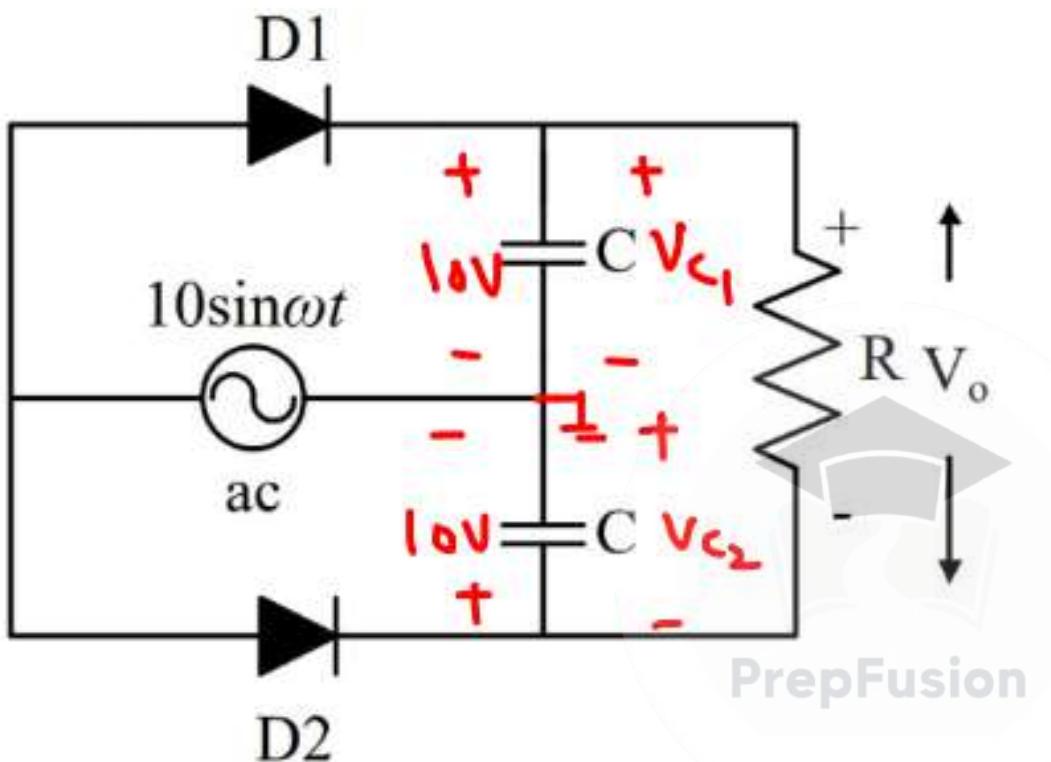The diodes D1 and D2 in the figure are ideal and the capacitors are identical. The product RC is very large compared to the time period of the ac voltage. Assuming that the diodes do not breakdown in the reverse bias, the output voltage V_o (in volt) at the steady state is _____



$$0 < t < \frac{T}{4}$$

$v_i = +ve$, D_1 and D_2 are ON

$$V_{c_1} \left(\frac{T}{4} \right) = 10V$$

$$V_{c_2} \left(\frac{T}{4} \right) = -10V$$



$$@ \quad t = \frac{\tau}{4}^+$$

$$V_i = g \cdot g \{ \text{Let} \} \quad V_{C_1} = 10V, \quad V_{C_2} = -10V$$

D_1 and D_2 are off.

{ To turn on D_1 and D_2 }

$V_i > 10V$



NOT POSSIBLE

\Rightarrow steady state reached

$$V_{C_1} = 10V, \quad V_{C_2} = -10V$$

$$V_o = V_{C_1} + V_{C_2} = 0V$$

ANALOG ELECTRONICS

BASIC SEMICONDUCTOR PHYSICS


LECTURE-1

GATE 2025-26 (EC/EE/IN)

Watch on YouTube

AIR 27 (ECE)
AIR 45 (IN)

Q.

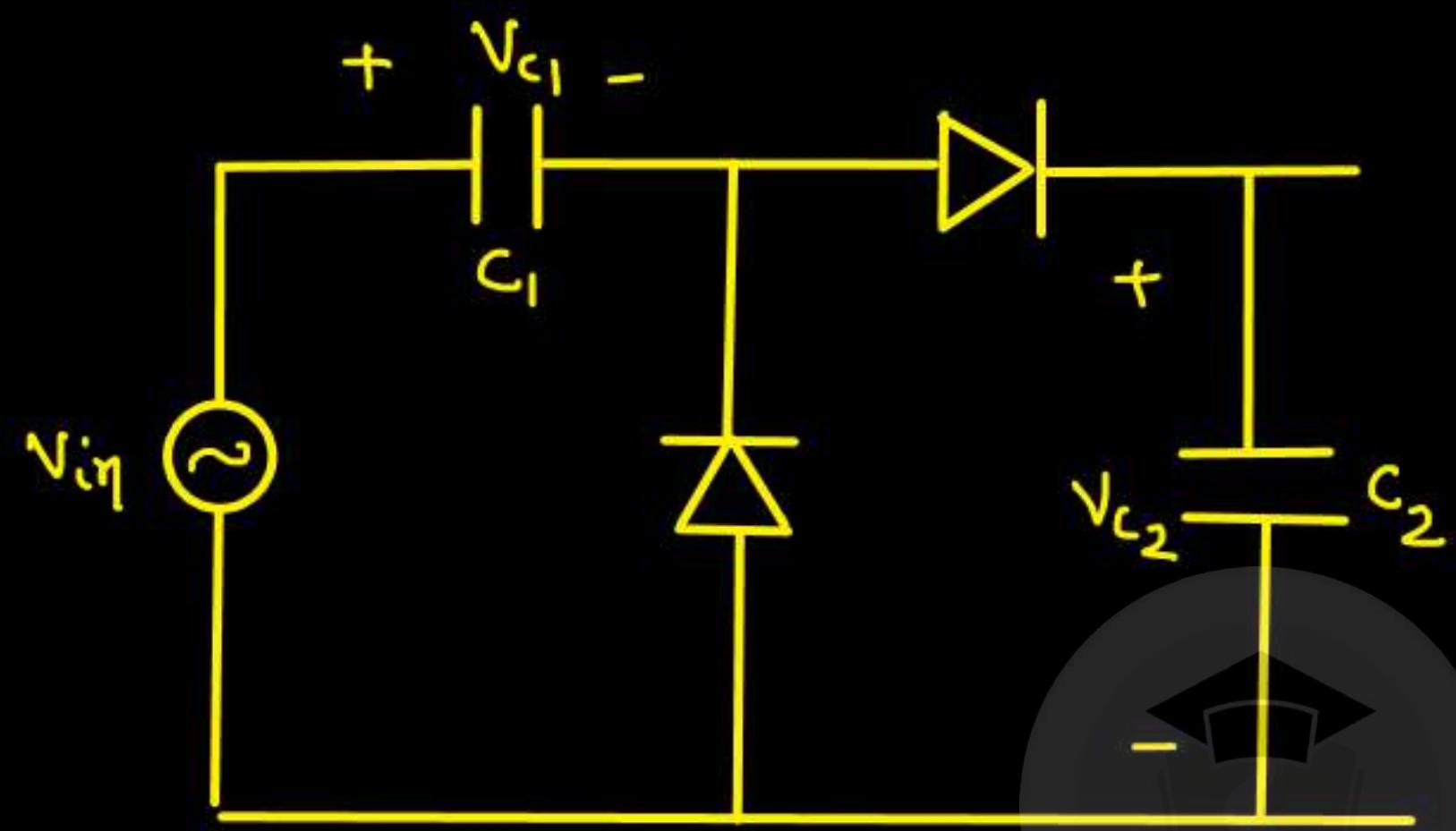



$$V_{in} = V_m \sin \omega t$$

$$C_1 = C_2 = C$$


Find V_{c_1} and V_{c_2} @ $t = T$
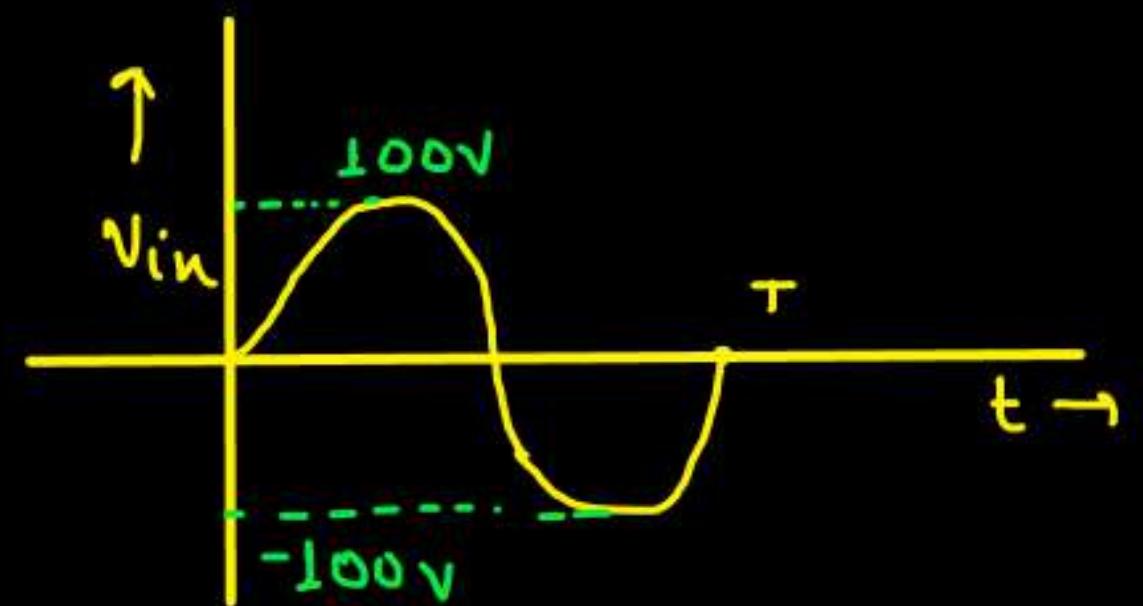
$$\rightarrow V_{c_1}(T) = -V_m , V_{c_2}(T) = 2V_m \quad \times \Rightarrow \text{This is steady state. (NOT after one cycle)}$$



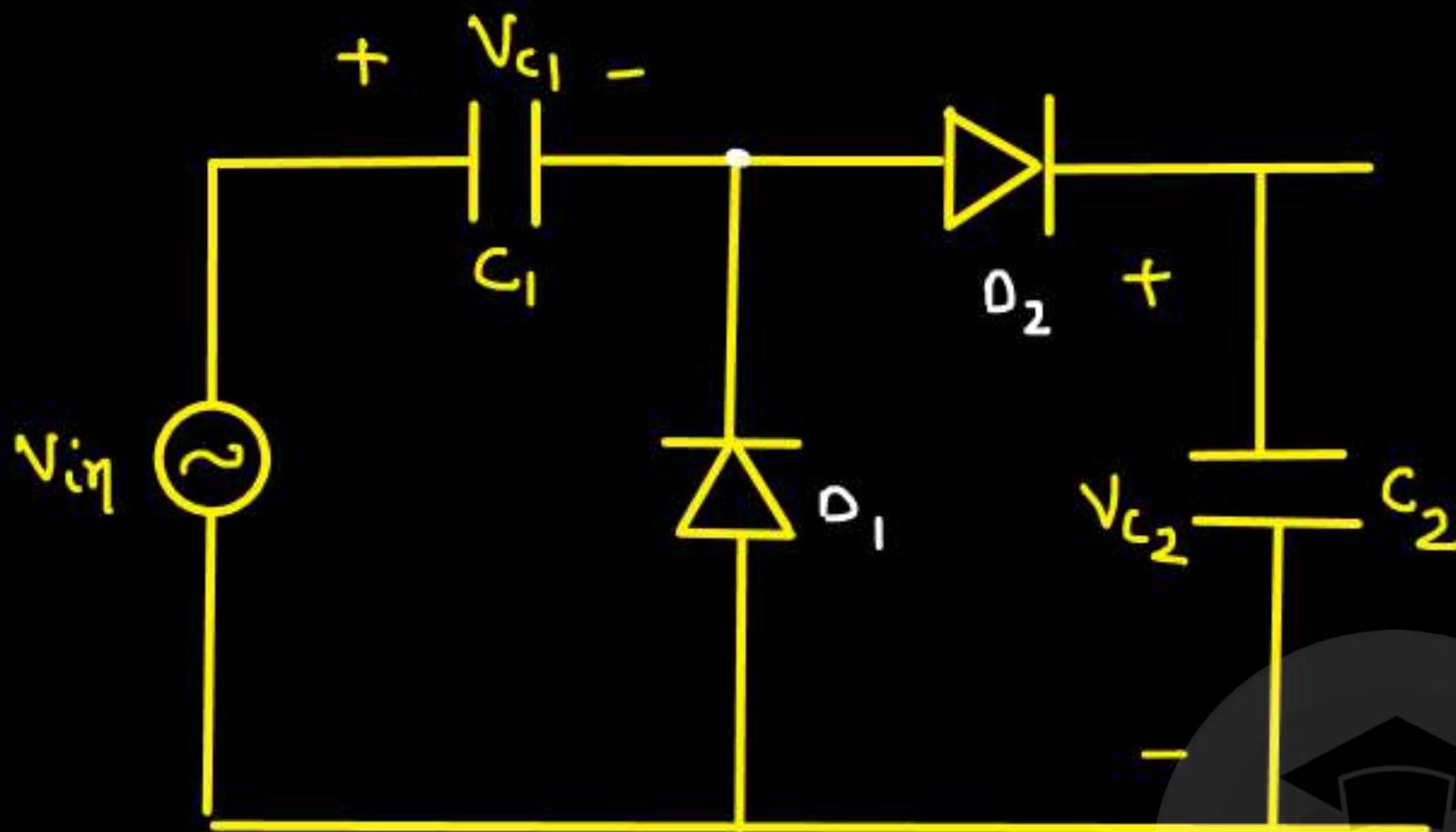

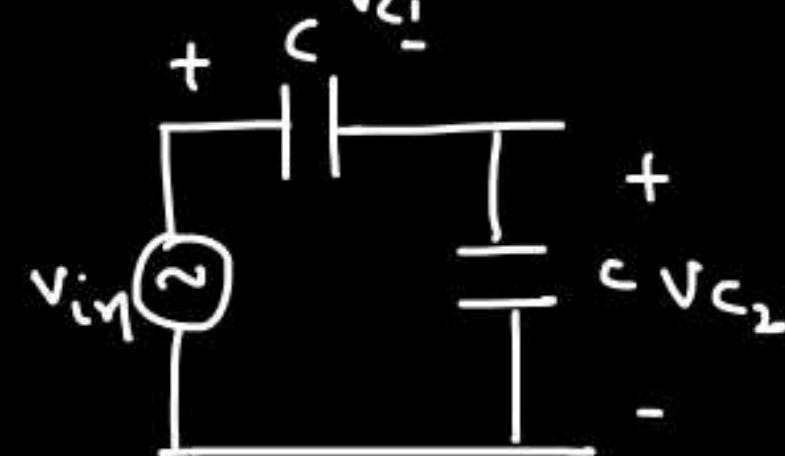
@ $t=0^+$ $\Rightarrow v_{in} = +ve \Rightarrow D_1 \text{ OFF}, D_2 \text{ ON}$



$0 < t < T/4 \Rightarrow v_{in} \Rightarrow [0 \rightarrow 100V]$

$$v_{c1} \Rightarrow [0 \rightarrow 50V]$$
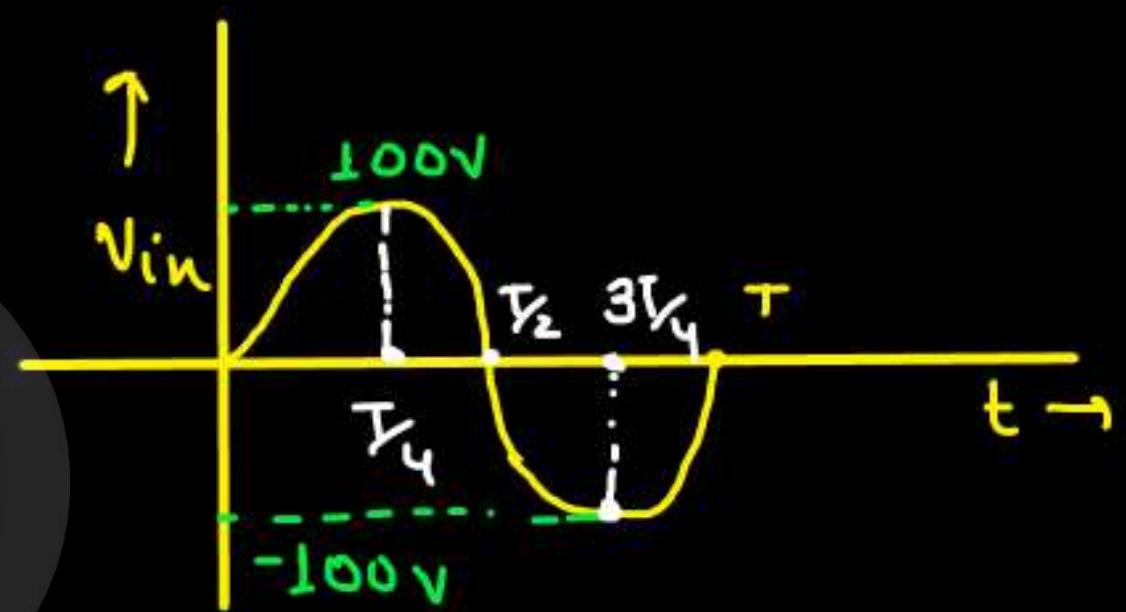
$$v_{c2} \Rightarrow [0 \rightarrow 50V]$$





@ $t = \frac{T_4}{4}^+$

$$V_i = 99V \{ \text{let} \} \quad V_{C_1} = V_{C_2} = 50V$$

D_1 and D_2 both are off


Both C_1 and C_2 will retain their voltages.
{ But till what time? }

when $V_i - 50 < 0 \Rightarrow D_1$ turns ON, D_2 still remains off

until $V_i < 50V$, both D_1 and D_2 are off.

Now

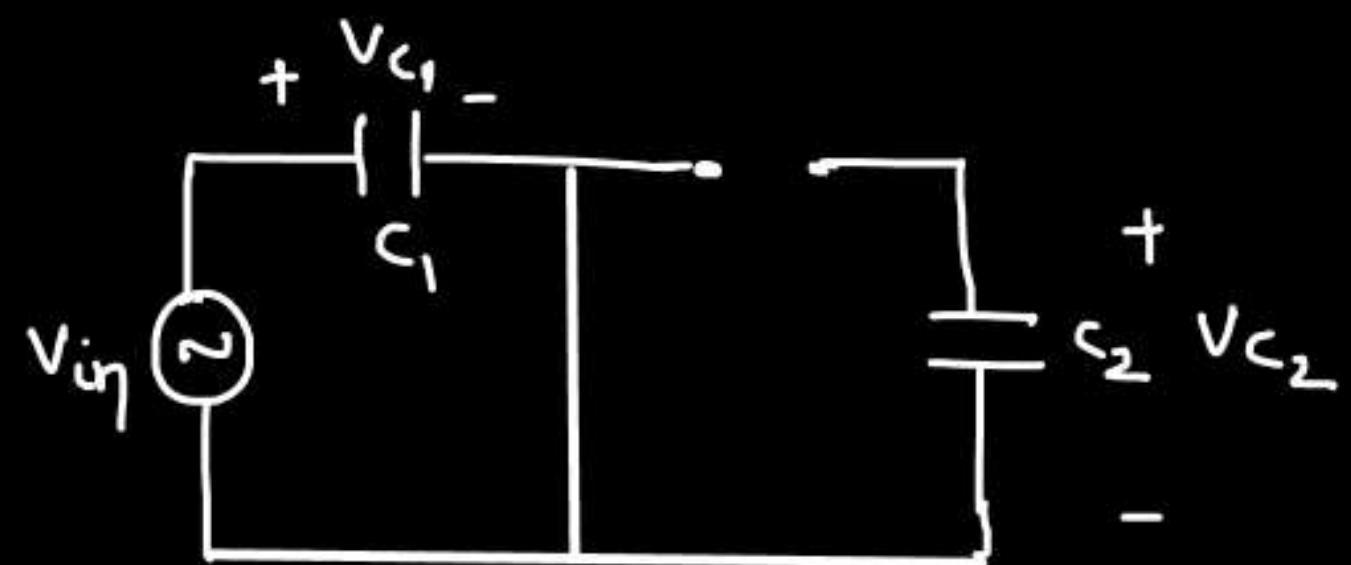@ $t = \frac{5T}{12}^+$ $V_i = 49V \{ \text{let} \} \Rightarrow D_1$ turning ON, D_2 still off



C_1 will follow the i/p

C_2 will retain its voltage

$$@ t = \frac{3\pi}{4}^+ \quad V_i = -99V \quad \left\{ \text{let} \right\} \quad V_{C1} = -100V, \quad V_{C2} = 50V$$

D_1 turns OFF, D_2 still OFF

How D_2 will turn ON?

$$V_{in} + 100 > 50 \Rightarrow V_{in} > -50$$

Until $V_i > -50V$, both D_1 and D_2 are off


Both C_1 & C_2 are retaining their voltage.

$$@ t = \frac{LT}{12} ; V_{in} = -49V \{ \text{let} \}$$

$$V_{C_1} = -100V \quad V_{C_2} = 50V$$


D_1 is OFF, D_2 turns OFF

PrepFusion

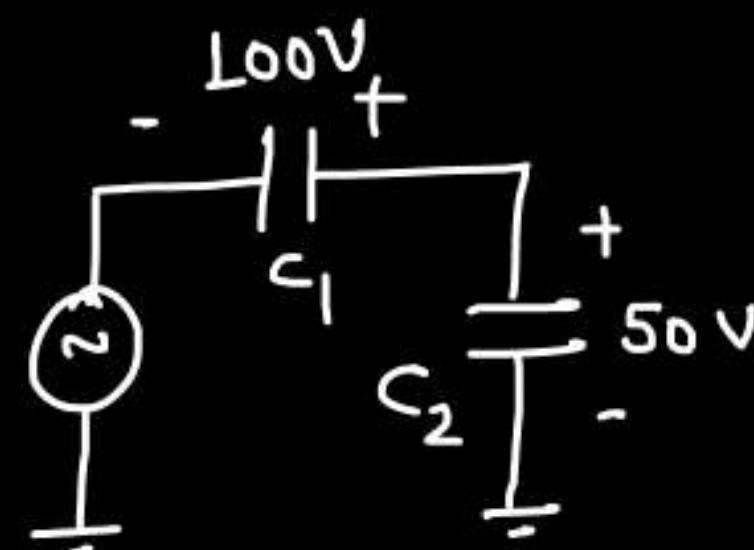

$$V_{in} \Rightarrow [-50 \rightarrow 0] \Rightarrow \text{increased by } 50V$$

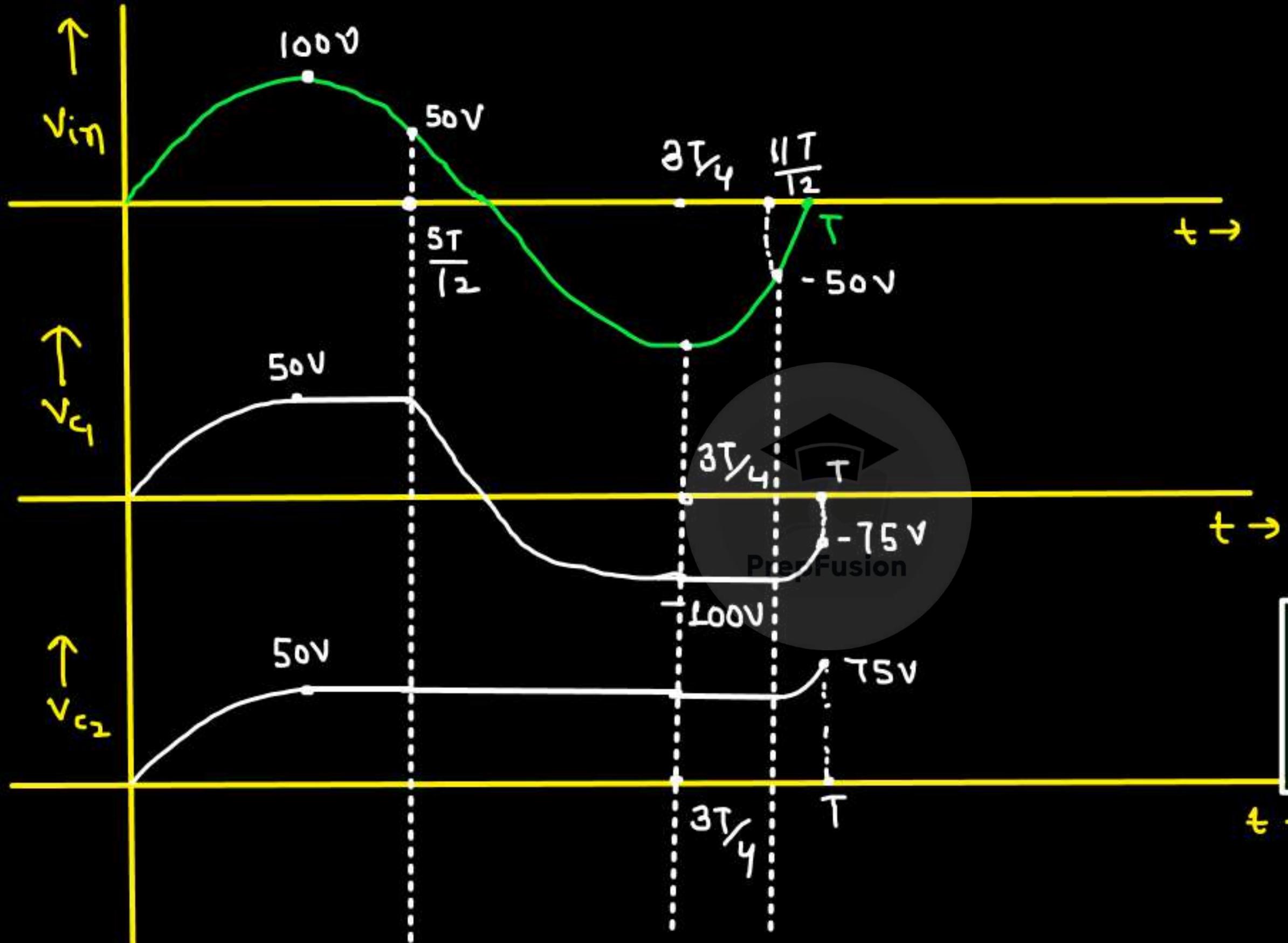V_{C_1} and V_{C_2} will also increase by 25V each.




$$V_{c_1}(T) = -75 \text{ V}$$


$$V_{c_2}(T) = 75 \text{ V}$$



Q.

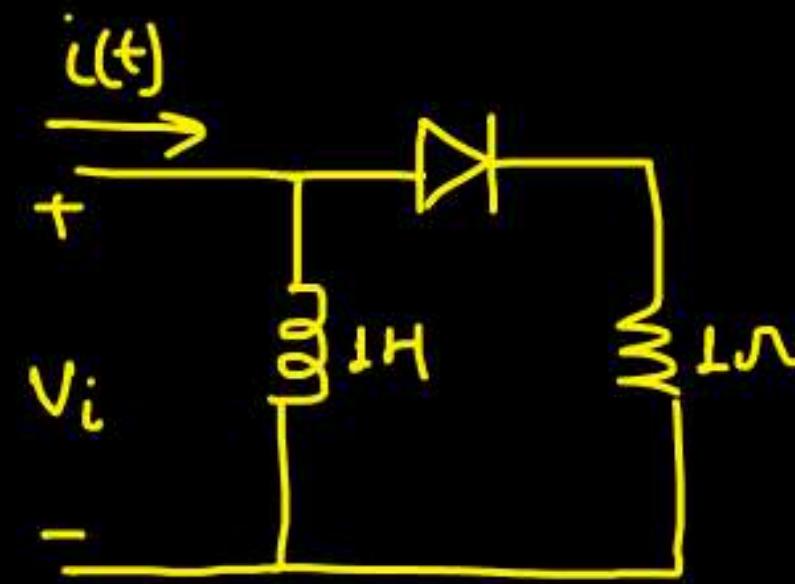


plot $i(t) = ?$

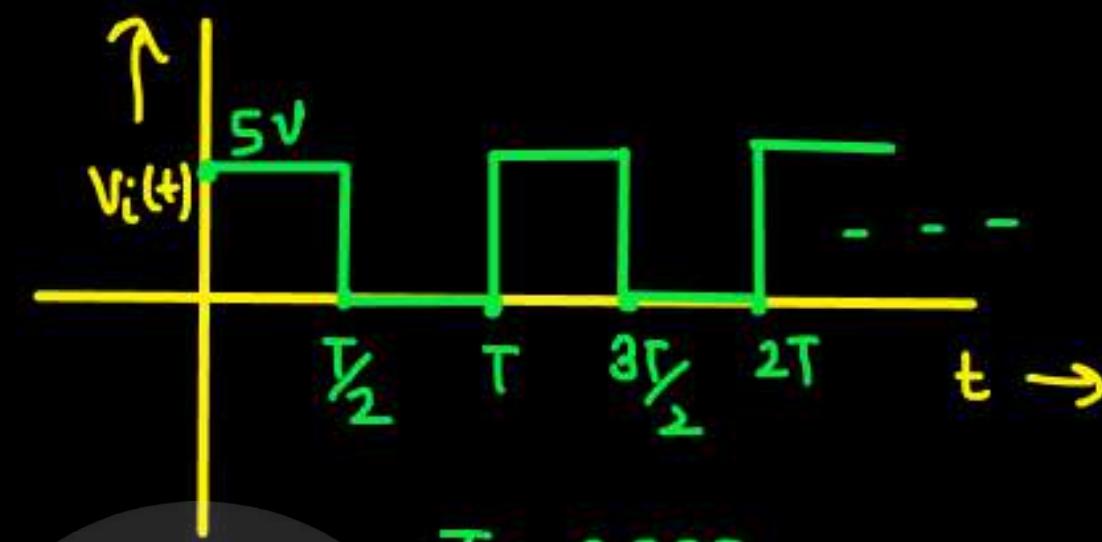

$$T = 25 \text{ sec} =$$

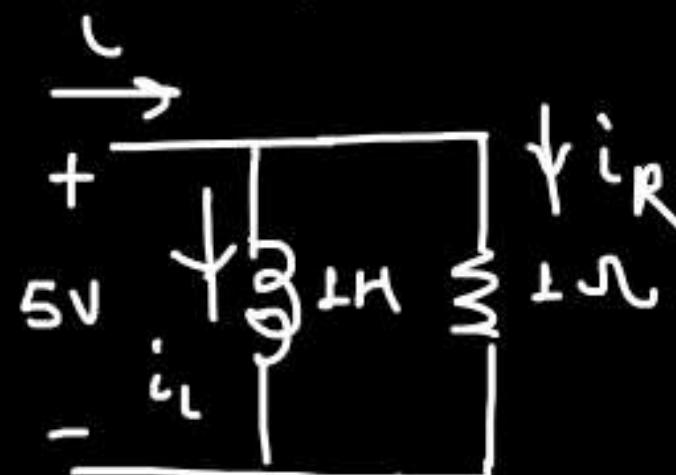
$0 < t < T/2 ; V_i = 5V \Rightarrow \text{diode ON}$




$$i(t) = i_L(t) + i_R(t)$$

$$i(t) = 5t + 5 \quad \left\{ 0 < t < \frac{T}{2} \right\}$$
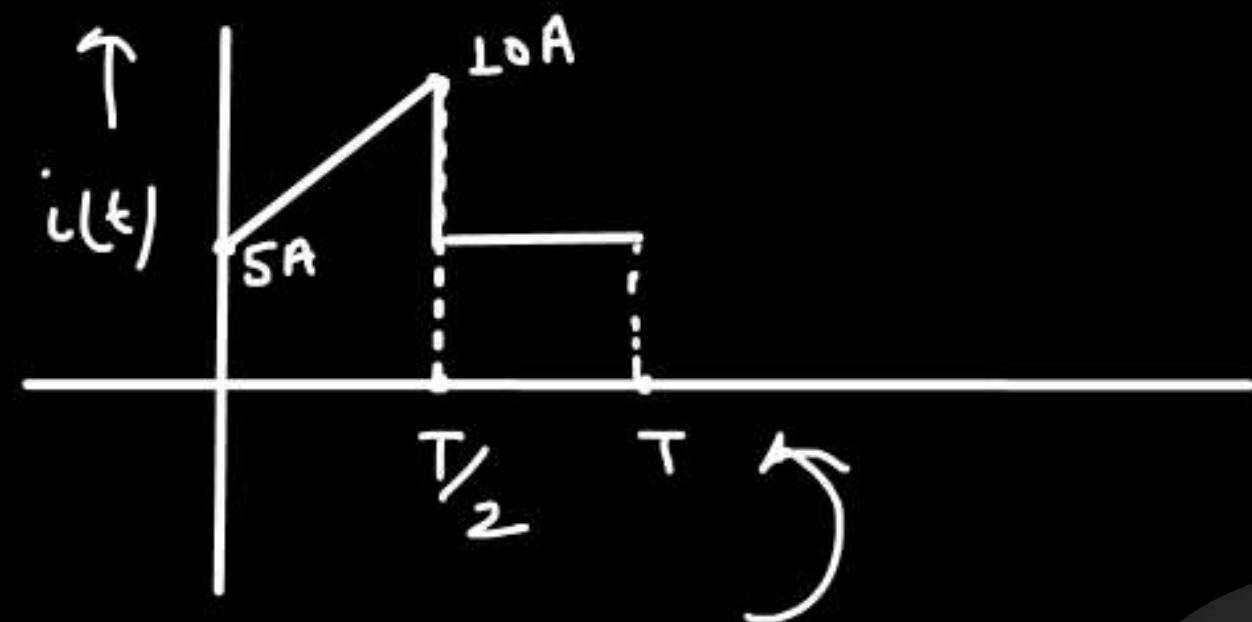
$$i\left(\frac{T}{2}\right) = 5 + 5 = 10 \text{ Amp.} =$$



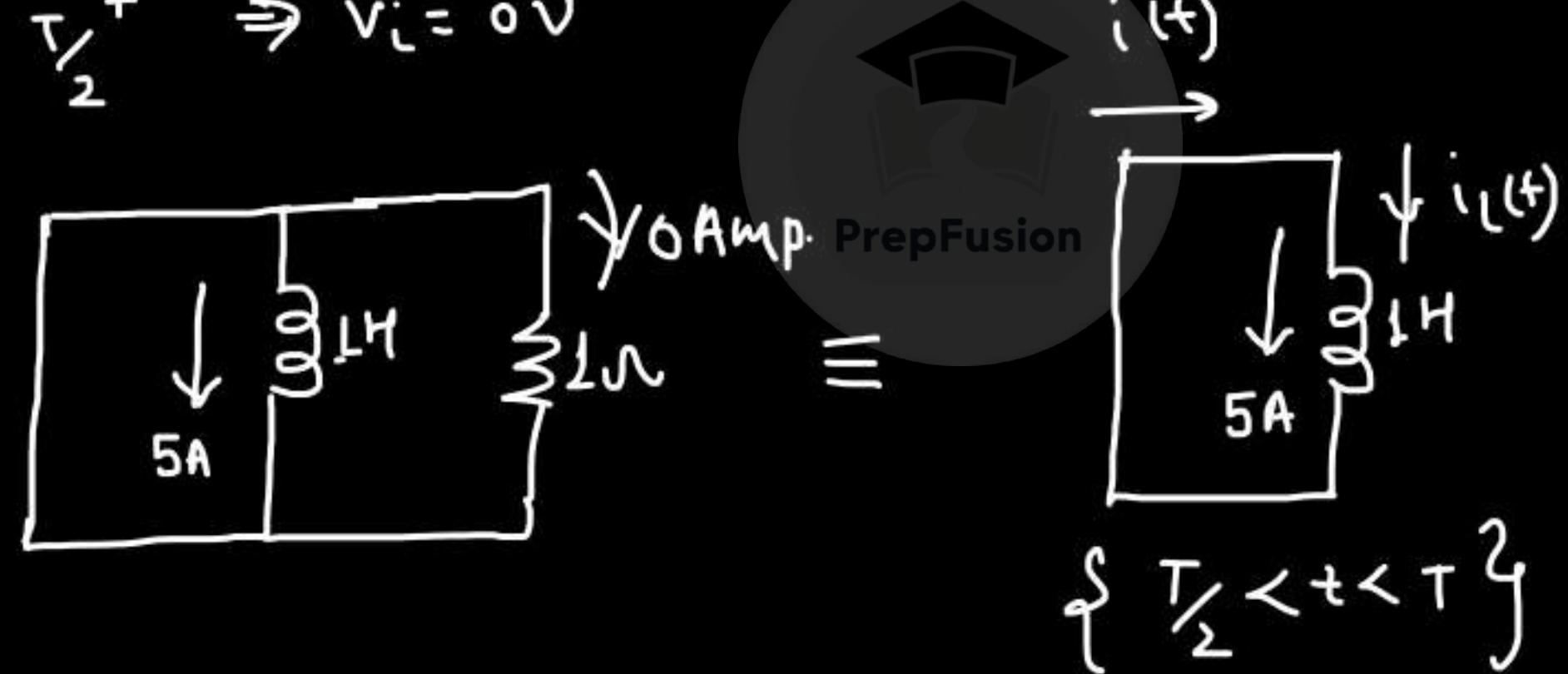
$$@ t = \frac{T}{2}^+ \Rightarrow V_L = 0V$$




@ $t = T^+$

$$V_L = 5V$$

$\rightarrow i(t)$

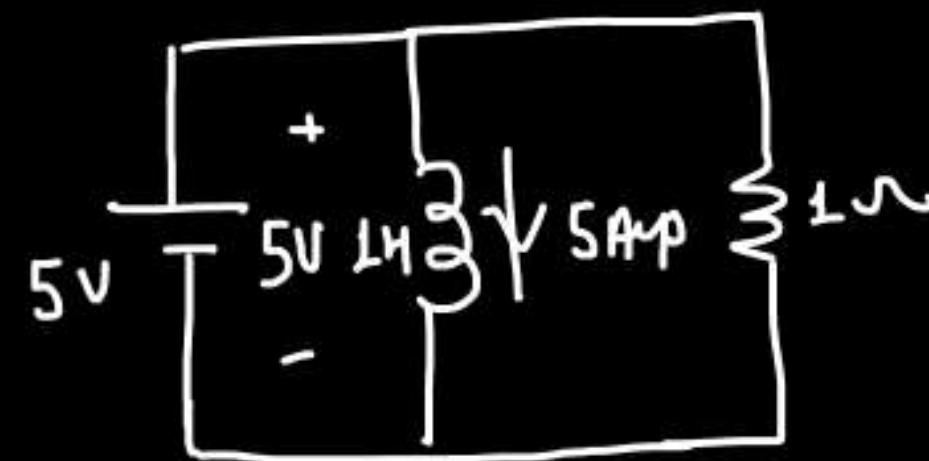

@ $3T/2^+$

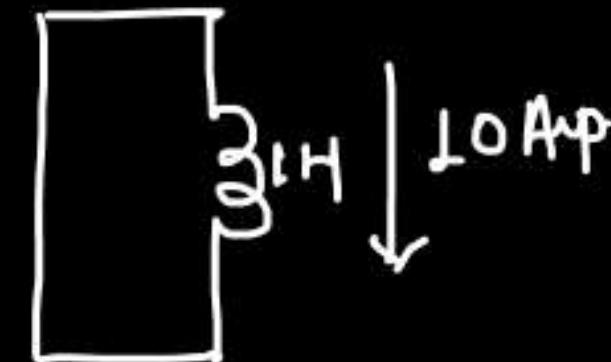

Inductor Resistor



$$i(t) = 5A + 5(t - T) + 5A$$

$$i\left(\frac{3T}{2}\right) = 5A + 5A + 5A$$


$$= 15A$$

@ $t = 2T^+$


$$i(t) = 10A + 5(t - 2T) + 5A$$

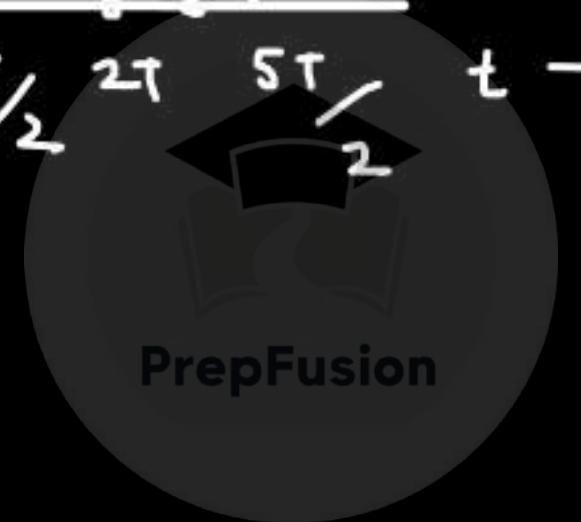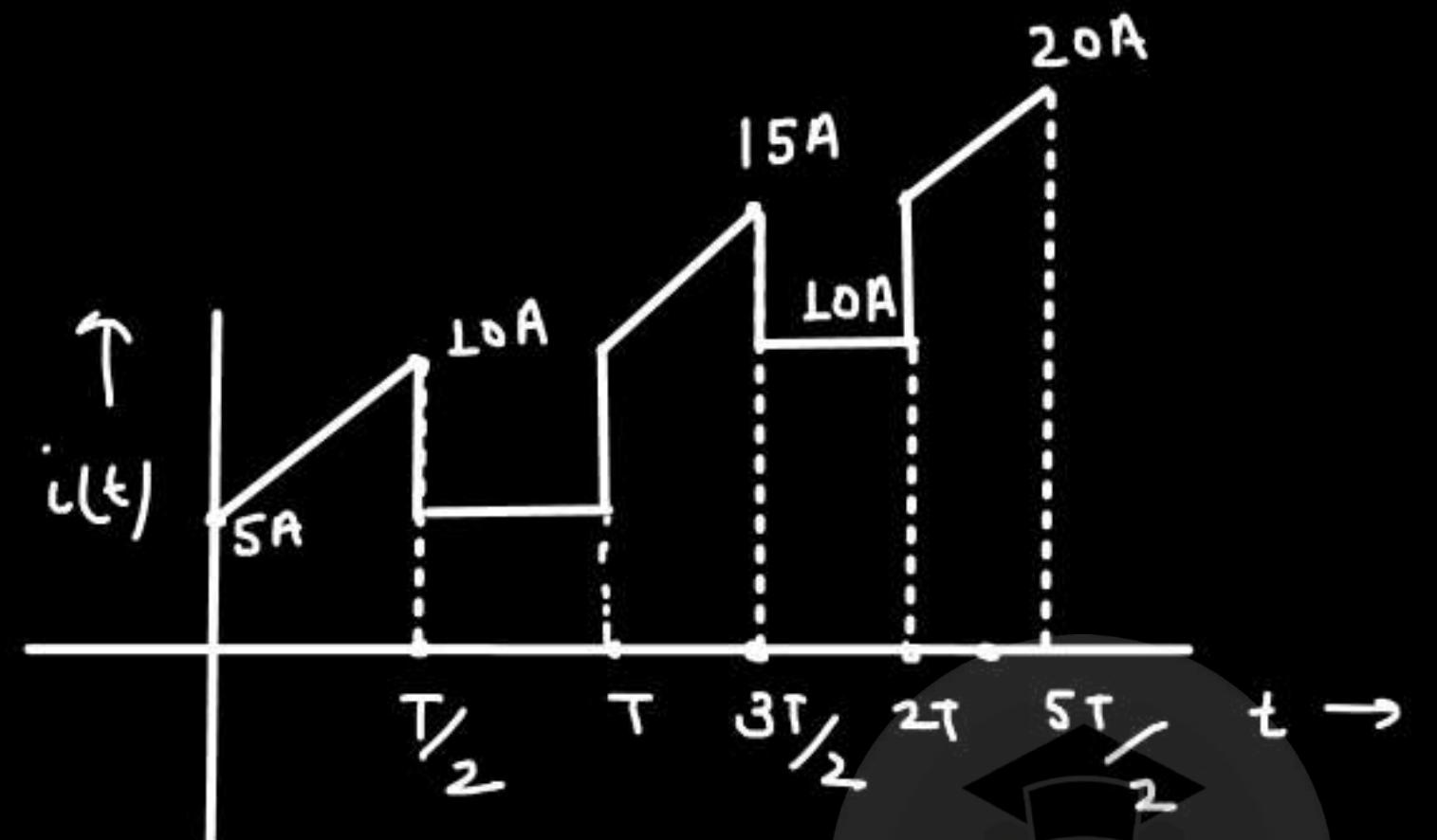

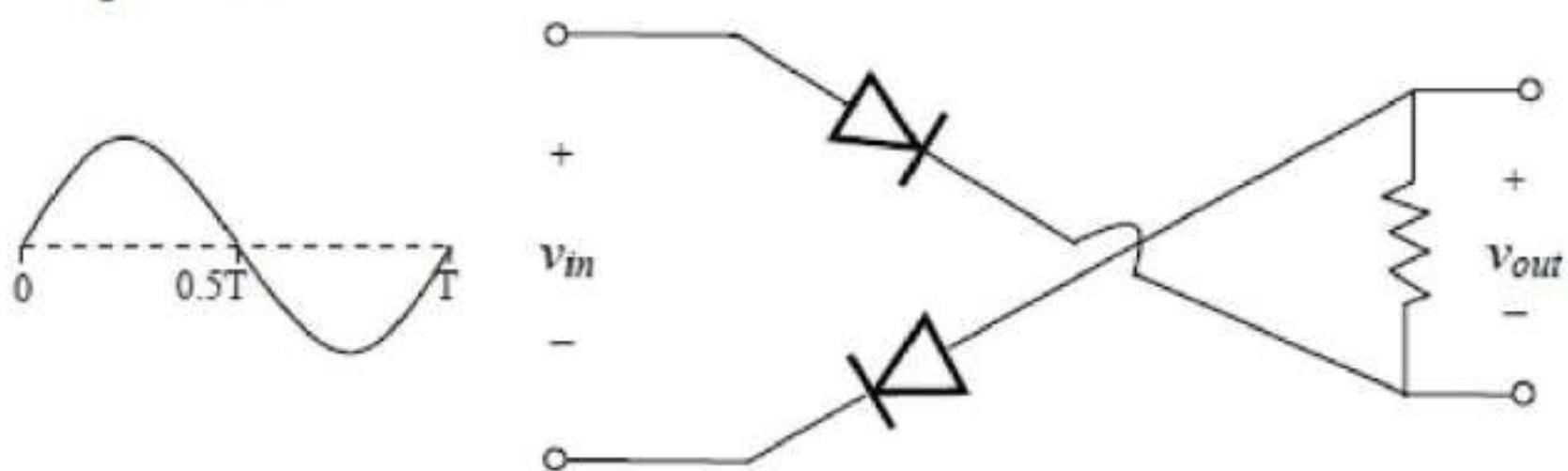
For the circuit with ideal diodes shown in the figure, the shape of the output (v_{out}) for the given sine wave input (v_{in}) will be




(A)

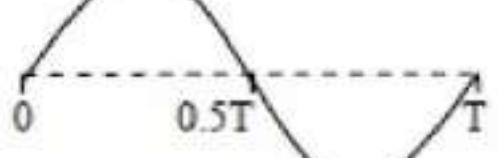


(B)

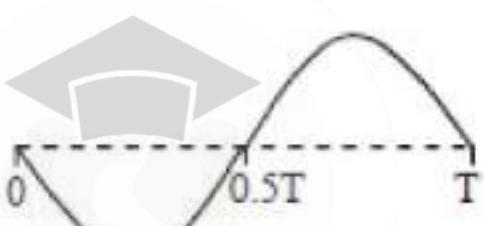

(C)

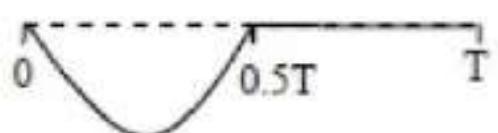

(D)

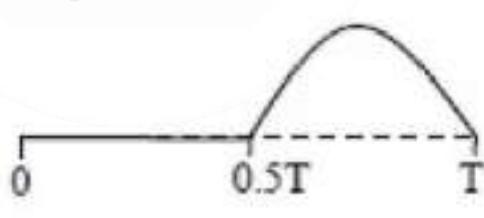

$$V_{in} = +ve$$

$$V_o = -V_{in}$$

$$V_{in} = -ve$$

$$V_o = 0V$$


* What we have studied ?


⇒ Diode → Two terminal device → 

* What did we get from diode ?


- ① Clipper → clips off undesired part.
- ② Clamper → Sets a new dc value of the i/p.
- ③ Peak detector → detects peak value of i/p and gives dc o/p.
PrepFusion
- ④ Voltage Multipliers → gives the o/p more than the max value of i/p signal (dc o/p)

⑤ Small signal Analysis :-

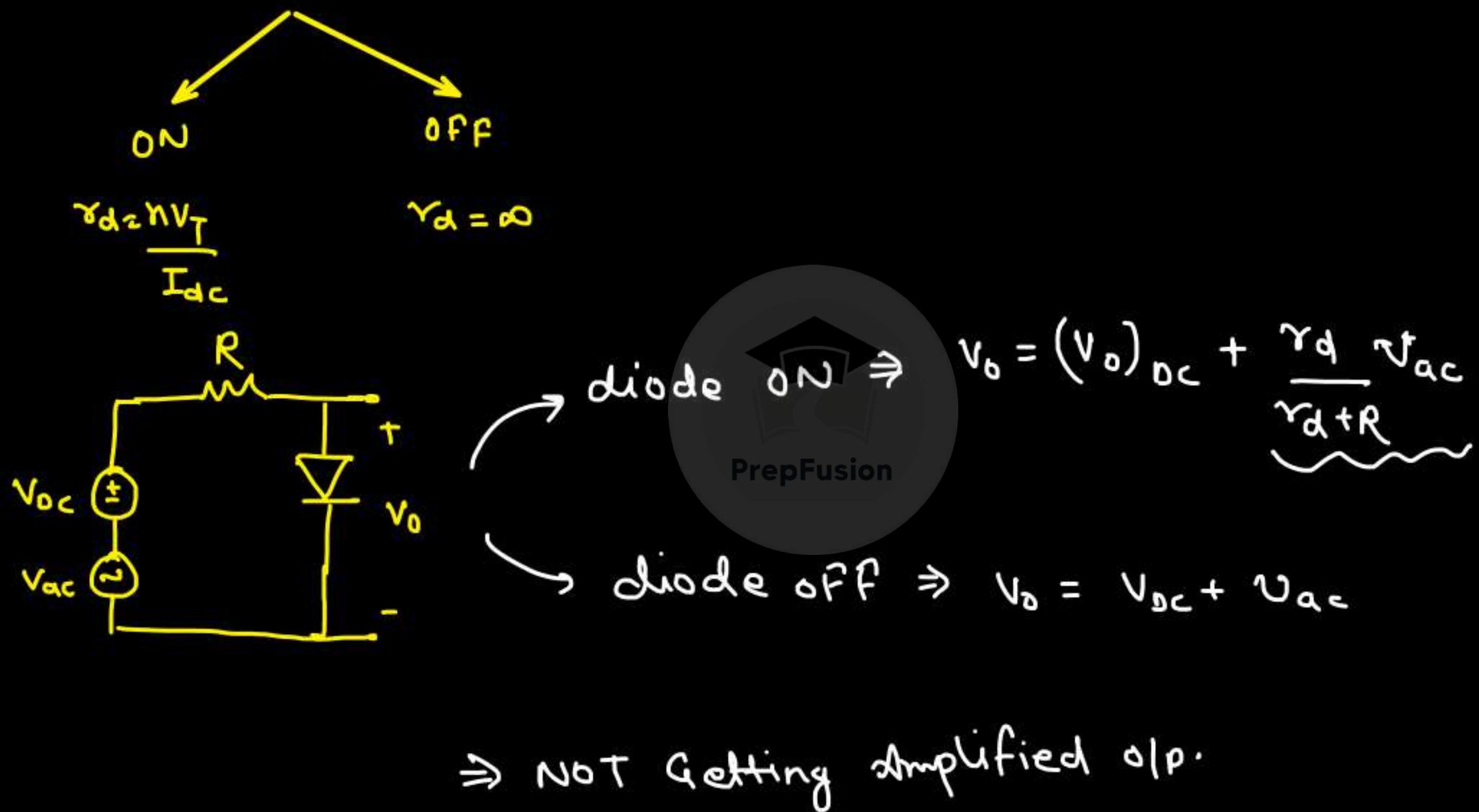


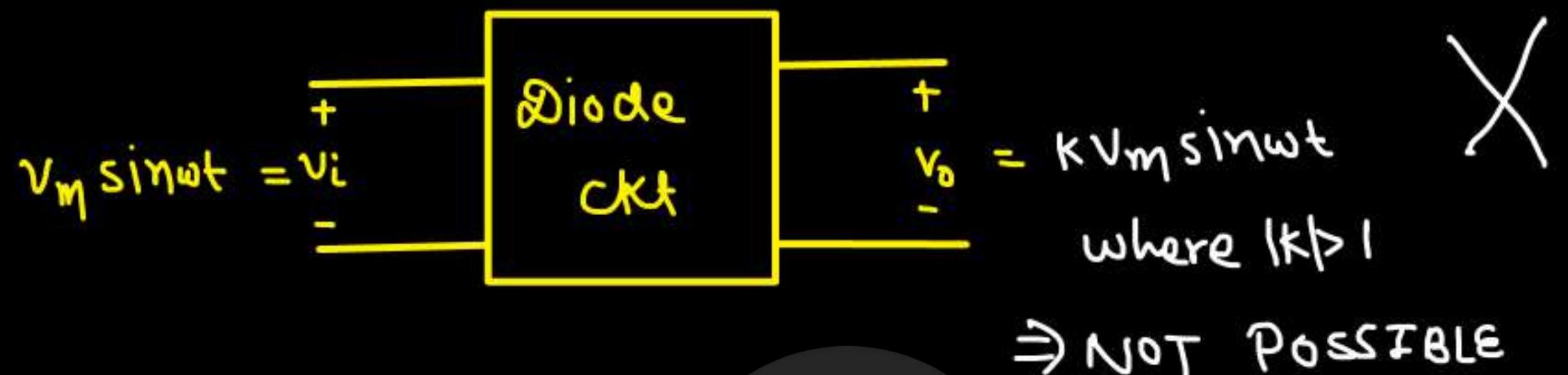

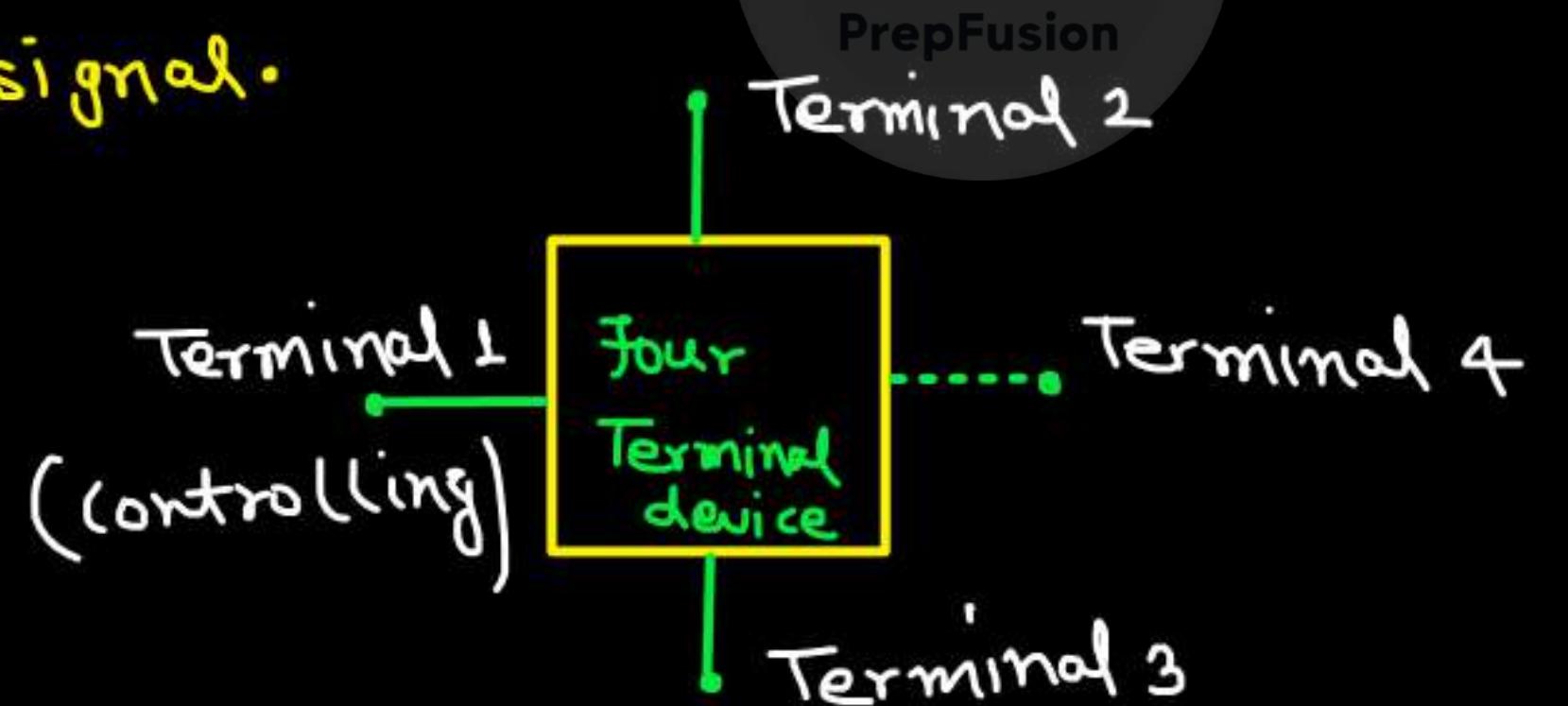⇒ You need some three / four terminal device for amplification of i/p ac signal.



A Basic Amplifier :-

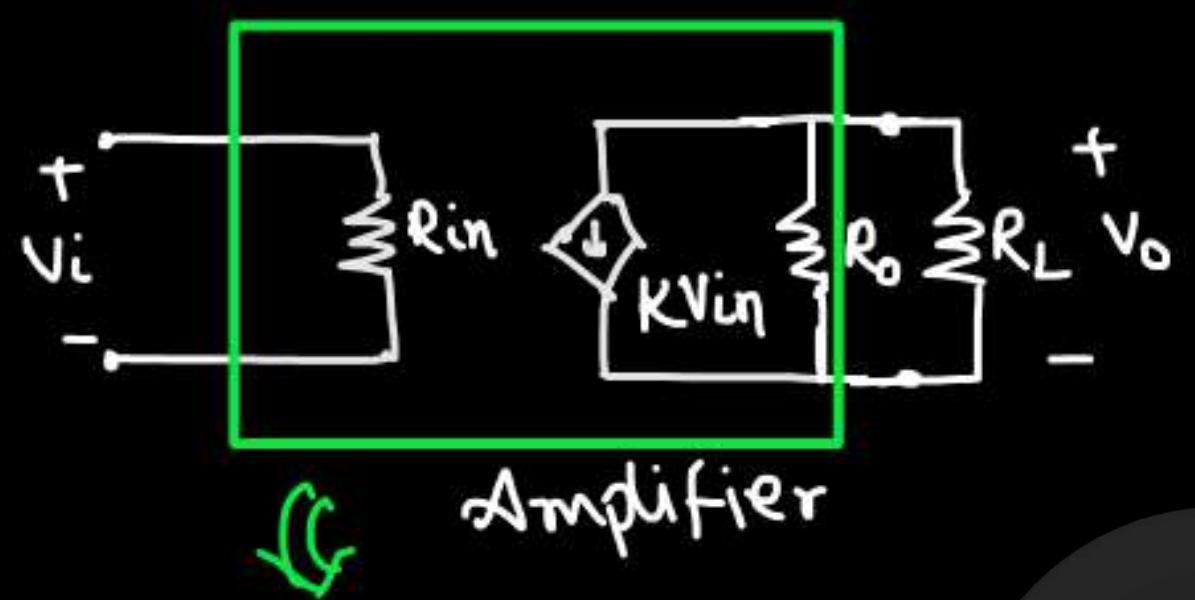

$$V_o = -K R_L V_{in}$$

↓
Amplification =

Gives Rise to Transistors





Field Effect Transistors (FET)

MosFETs
(Metal oxide Semiconductor)

PrepFusion



Depletion Type

n-channel P-channel

Enhancement type

n-channel p-channel

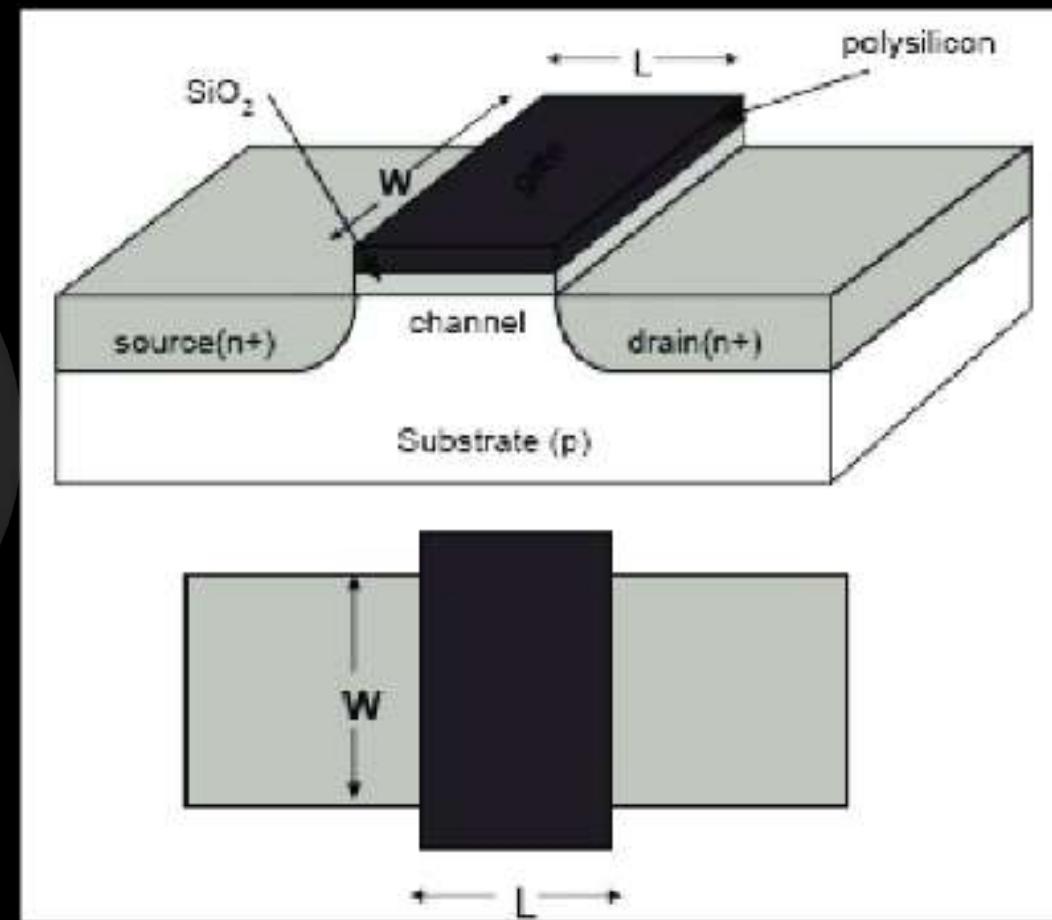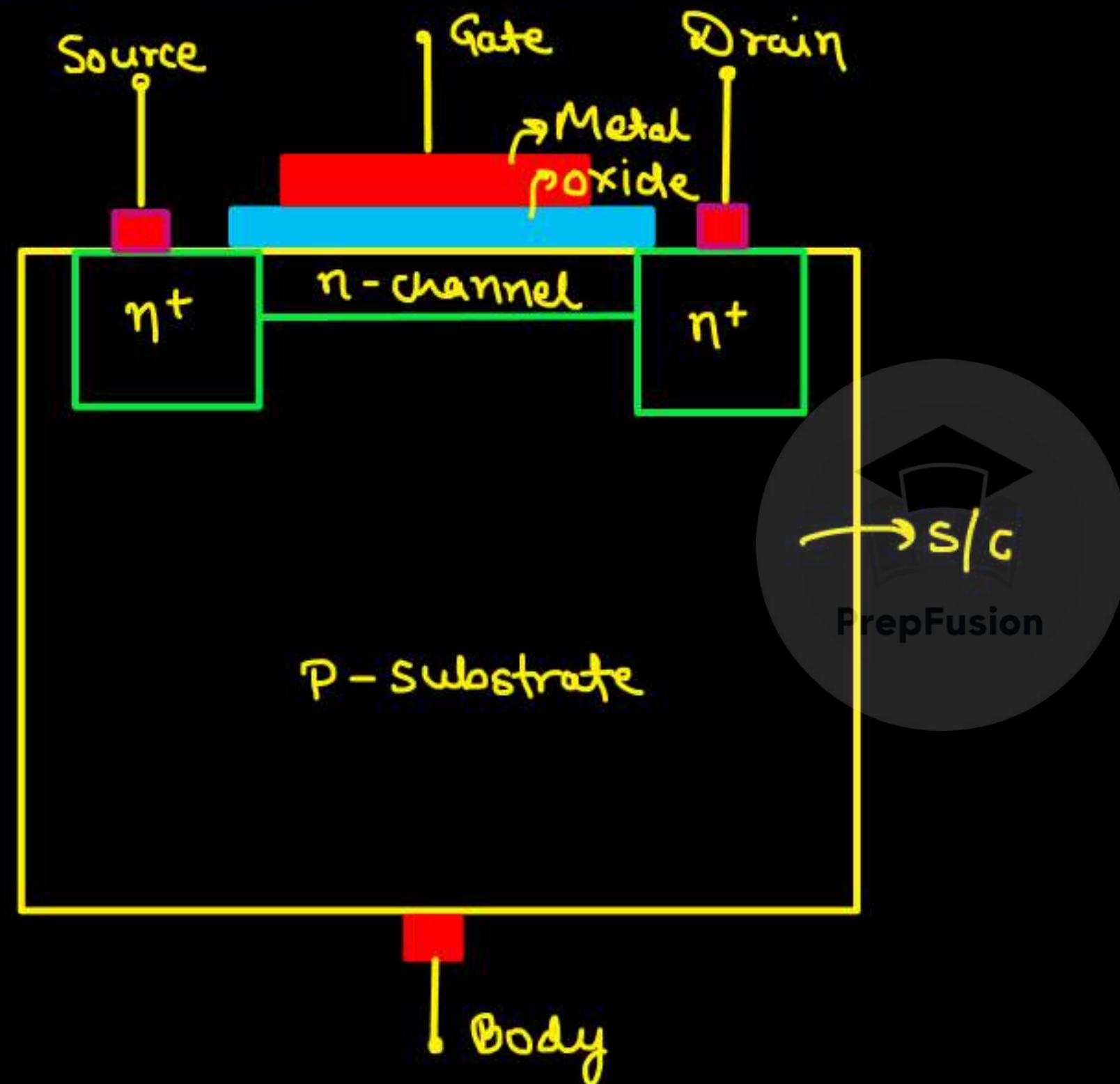① n-type depletion MOSFETs:- [channel is already +nt]




[Photo from ResearchGate]

MOS \rightarrow 4 terminal device
(Gate, Source, Drain, Body)

- ① Source :- Supplies the charge carrier to the channel.
- ② Drain :- Collects the charge carrier from the channel.
- ③ Gate :- Controls the flow of charge carriers.
- ④ channel :- The path b/w drain and source from where the charge carrier travels.
- ⑤ JET (Field Effect Transistor) :- The flow of current is modulated by applied voltage or electric field.

Analogy :-

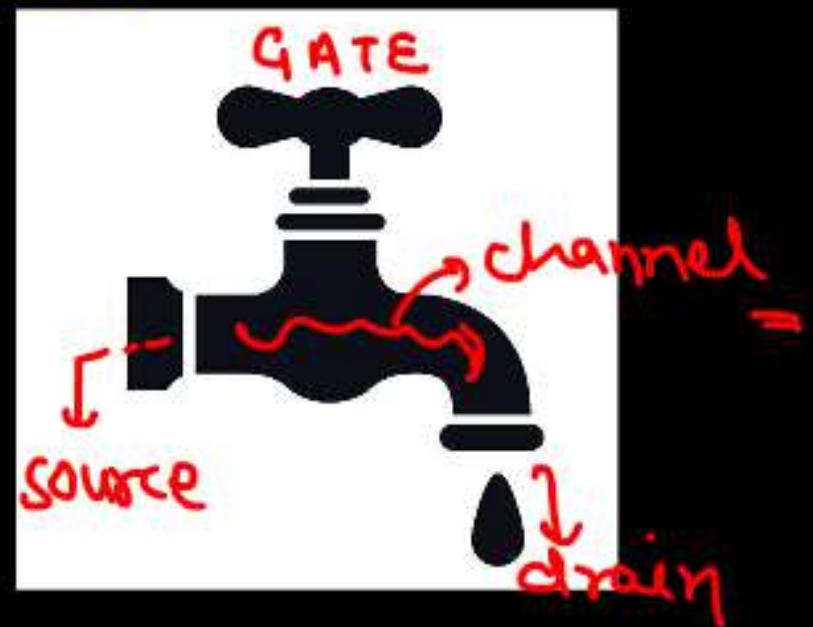


For n-channel depletion type MOSFET :-

Codⁿ 1:-



(i) $V_{GS} = 0V$

(ii) $V_{DS} = +ve$

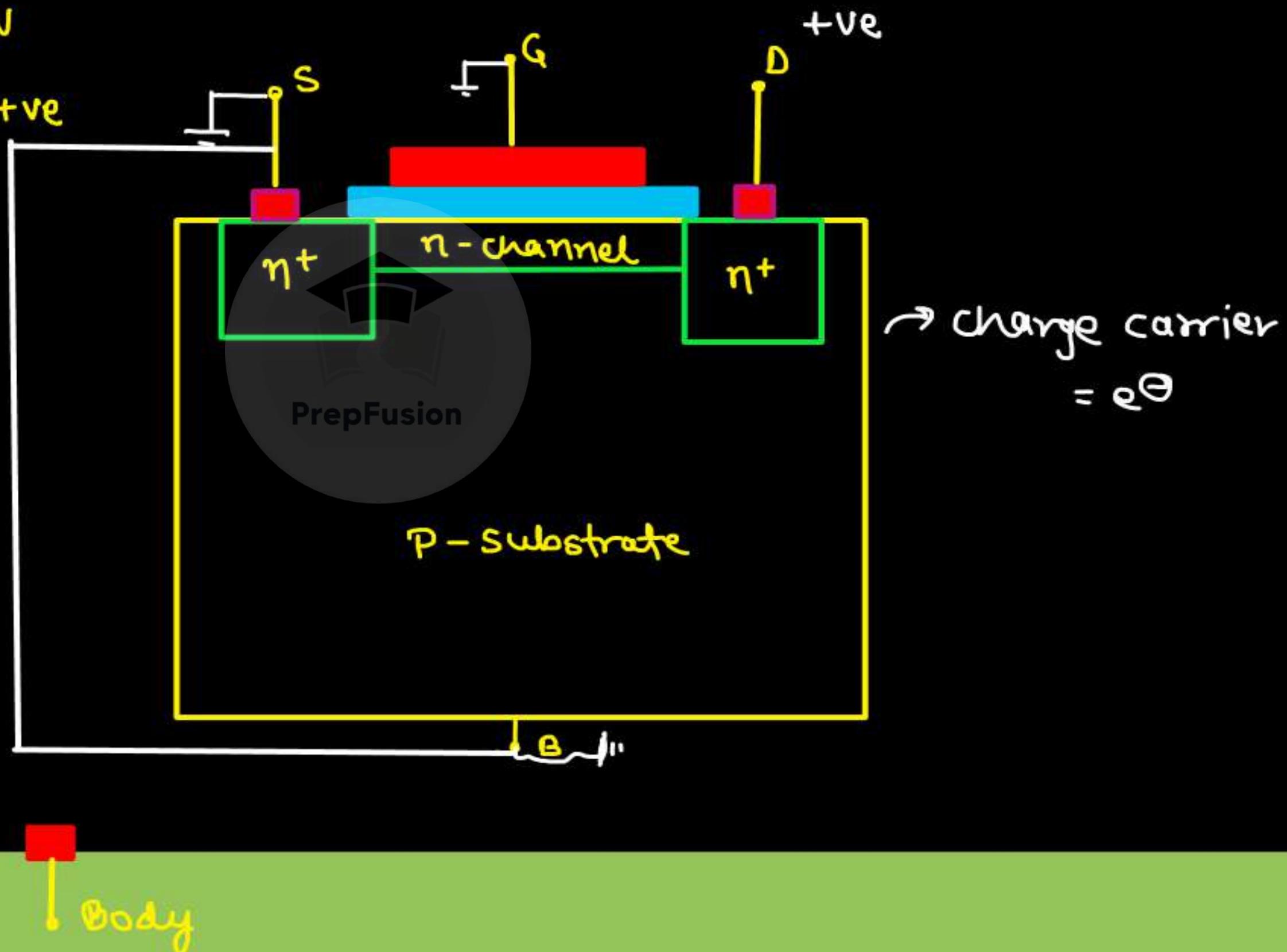

n^+ → Highly doped → more conductivity
↓
less resistance

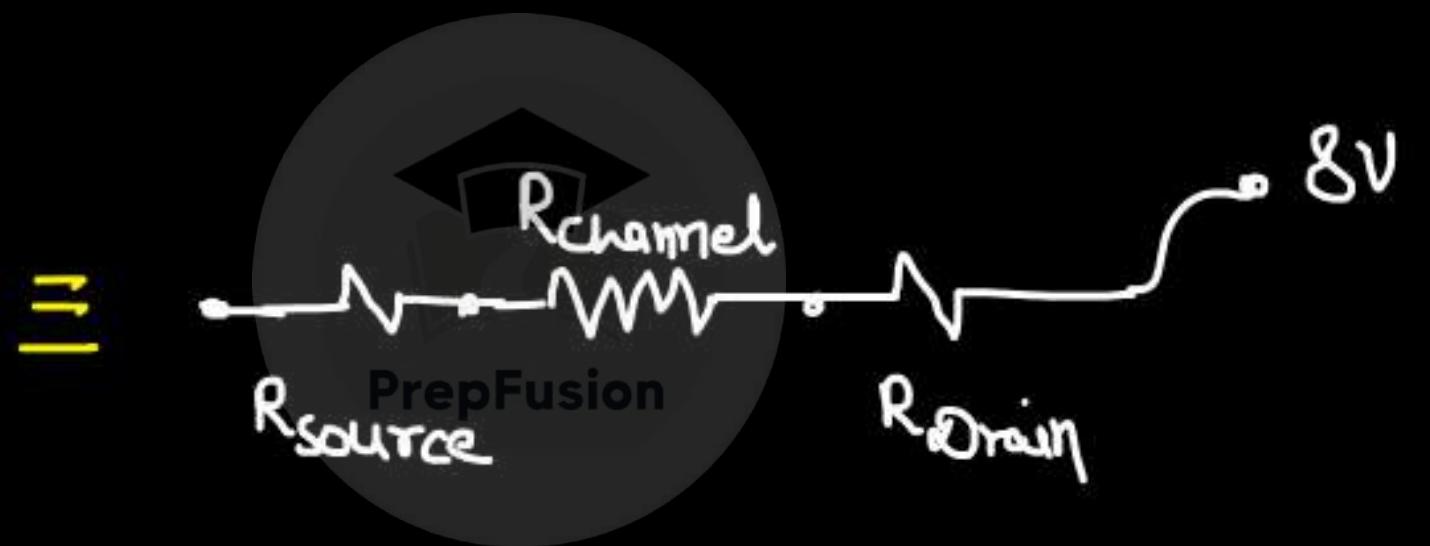
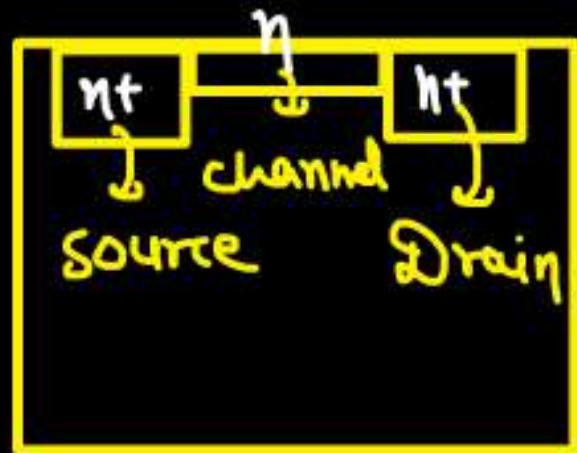
n → Lightly doped → less conductivity
↑
More resistance




Assumption

$$R_{\text{ch}} = 2R_D = 2R_S$$
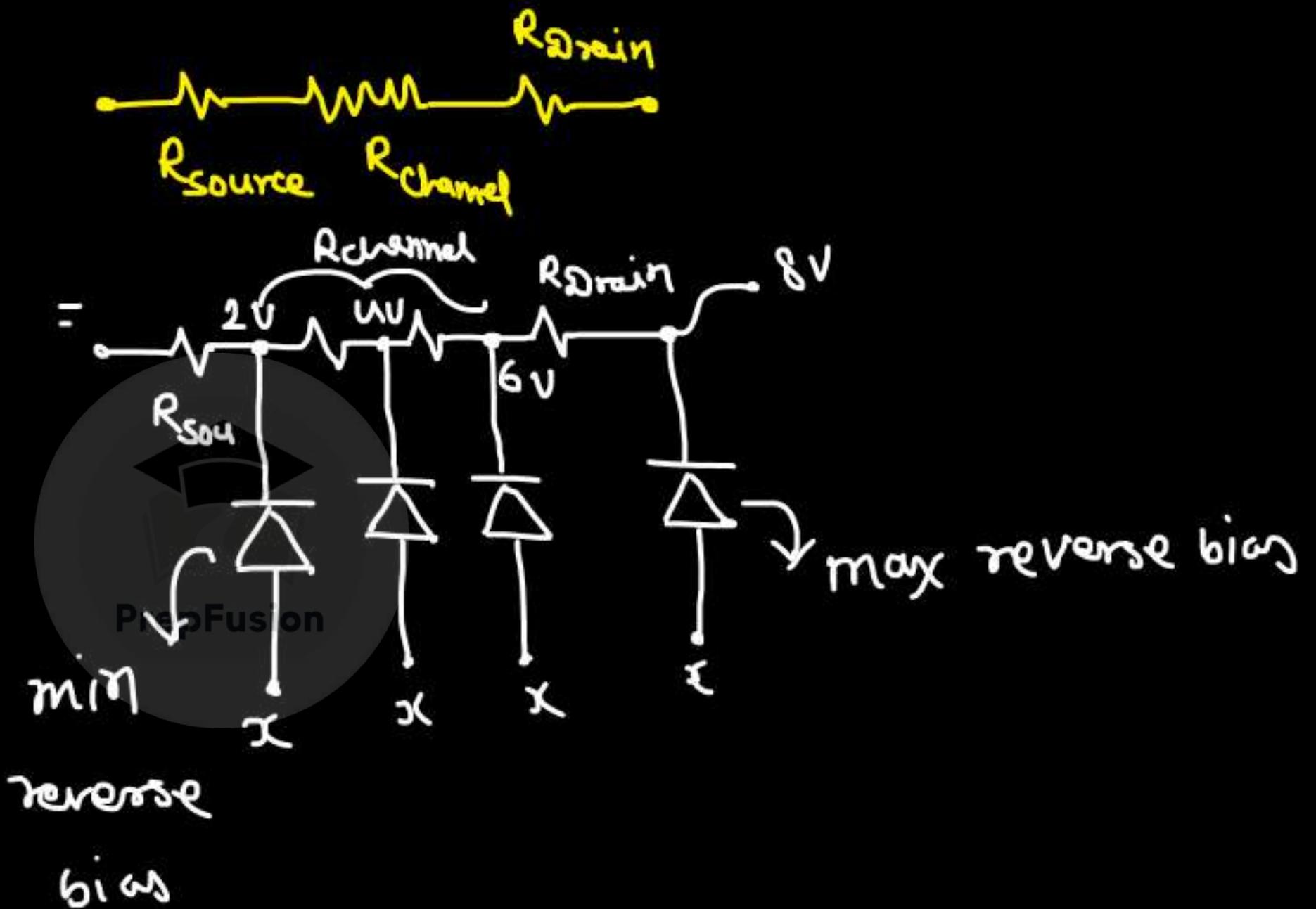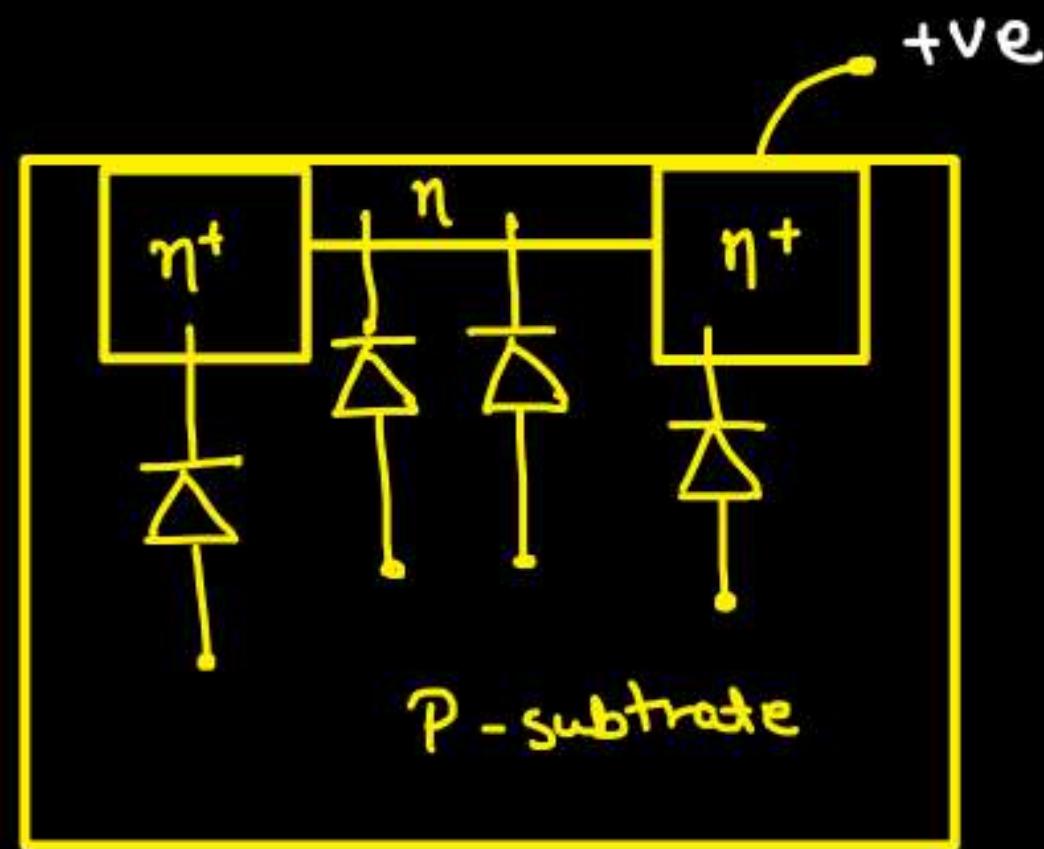
$$R_{\text{channel}} > R_{\text{Drain}}, R_{\text{Source}}$$



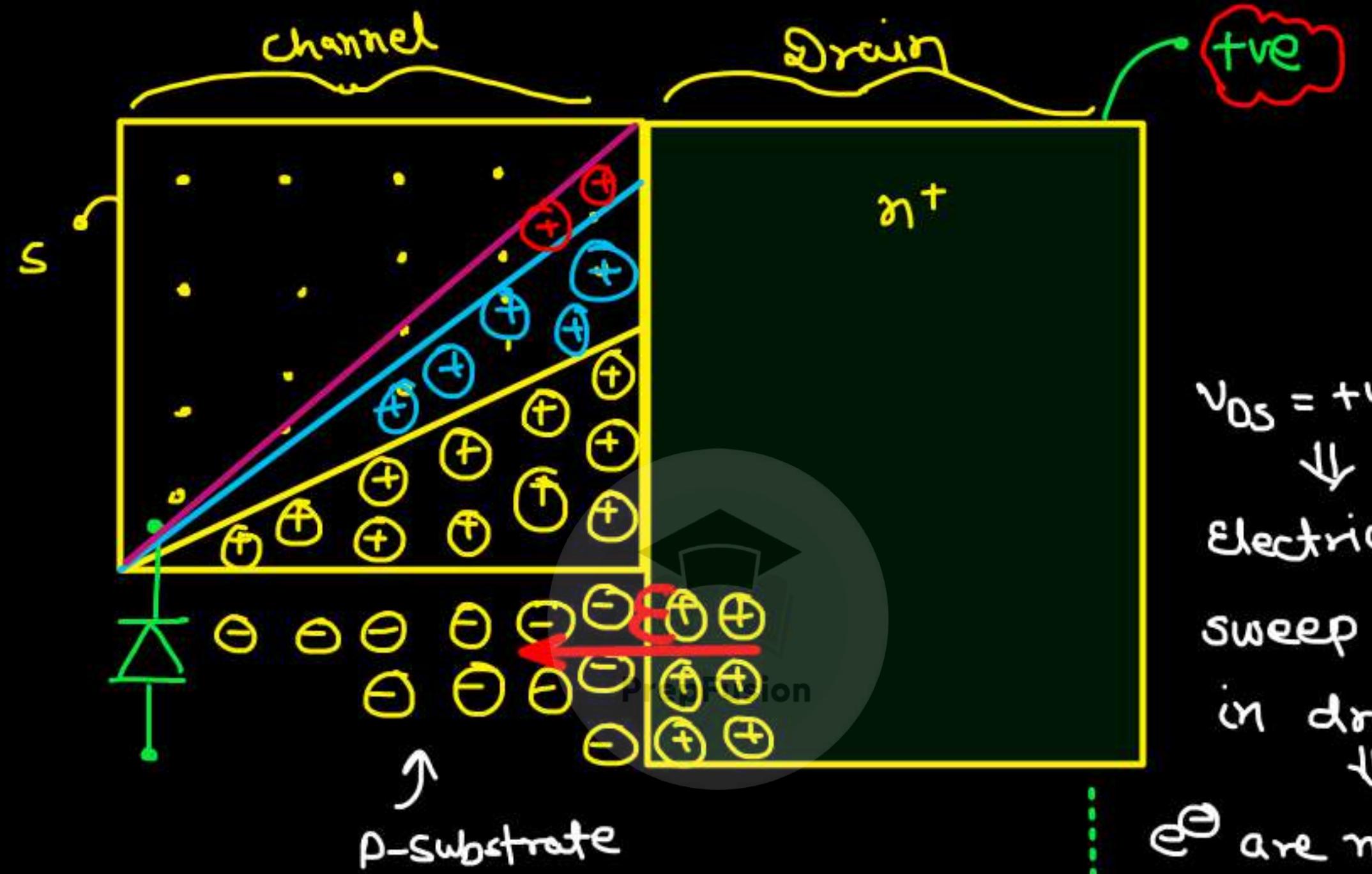
From drain to source, Reverse bias $\downarrow \Rightarrow$ depletion width \downarrow



What if $V_{DS} \uparrow \uparrow \Rightarrow "e^{-}"$ will be strong $\Rightarrow e^{-}$ will travel fast \Rightarrow current \uparrow

$V_{DS} = +ve$
 \downarrow
 Electric field E will sweep away the e^{-} in drain terminal
 \downarrow

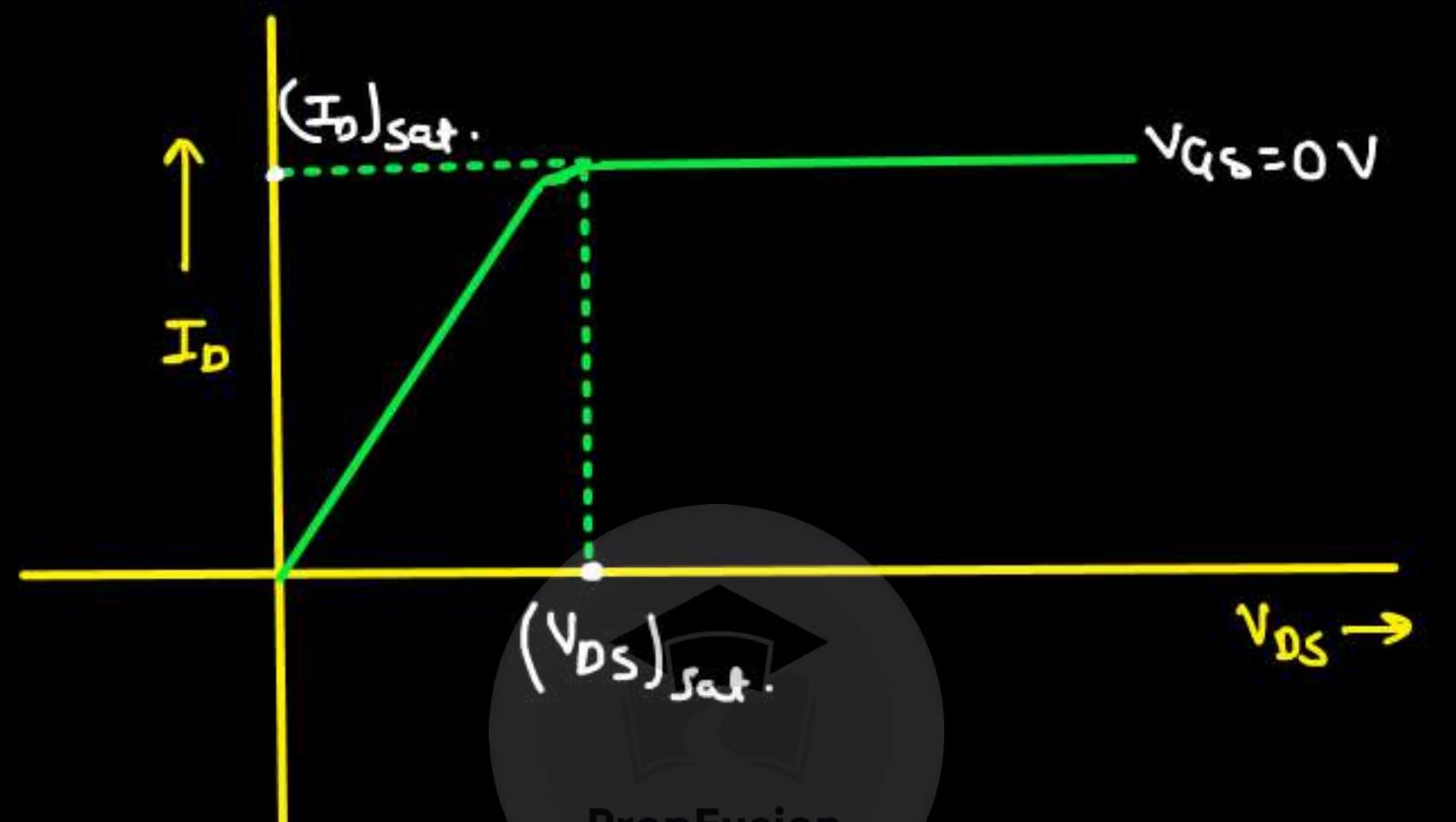e^{-} are moving from source to drain
 \downarrow
 current will flow from Drain to source.




But @ a certain value of V_{DS} , the channel will start having very less charge carriers. Although the "E" field is strong but the charge carriers are less and because of that current saturates.

Condⁿ 2:-

$V_{DS} = +ve \{ \text{Fixed} \}$

$V_{GS} = \text{varying } [-ve \rightarrow +ve]$

① $V_{GS} = -ve$

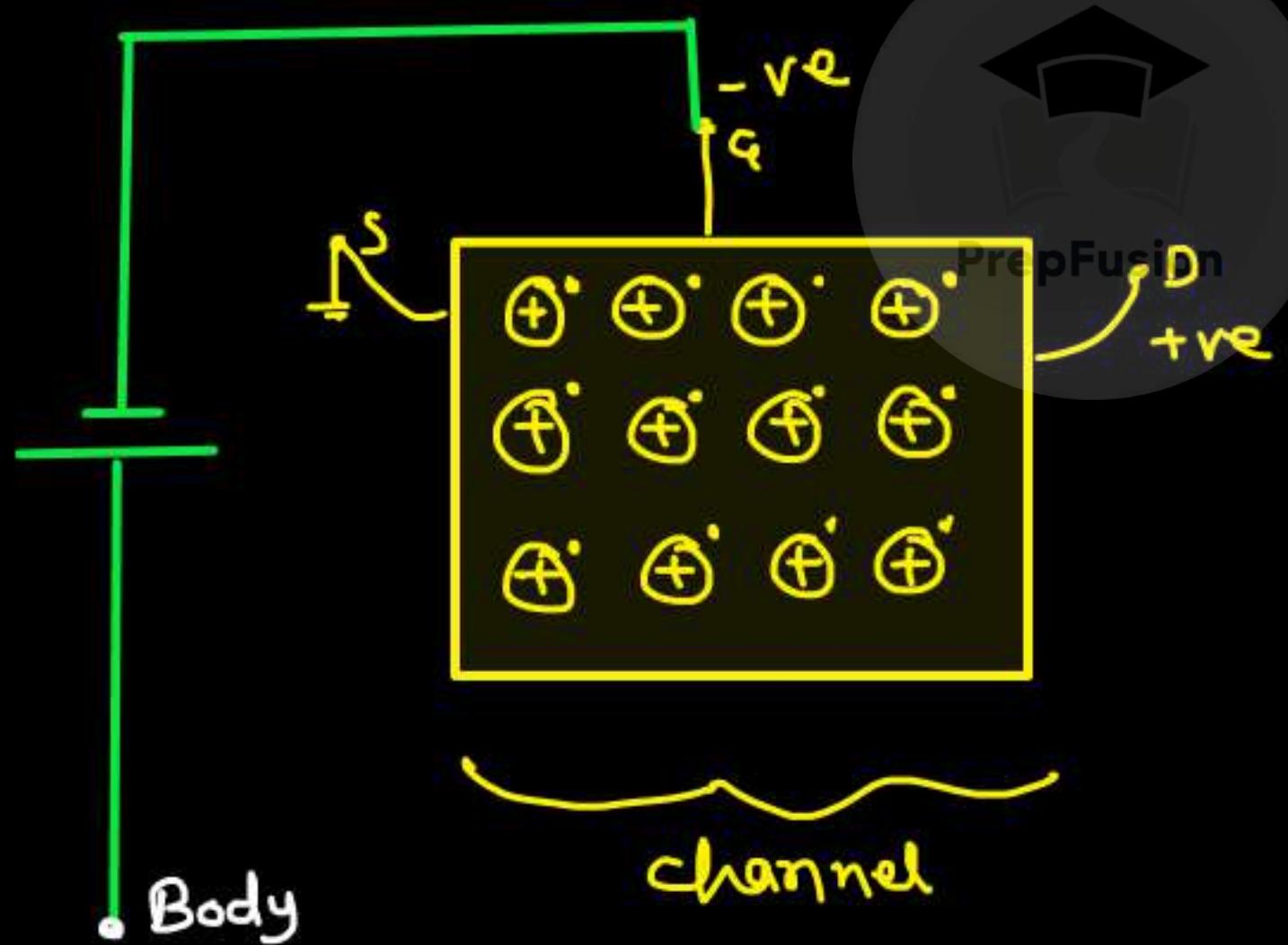


V_G is increasing in negative dirⁿ

↓
channel is getting depleted of charge carrier

↓
Current is decreasing


if we keep on decreasing V_{GS} value, then

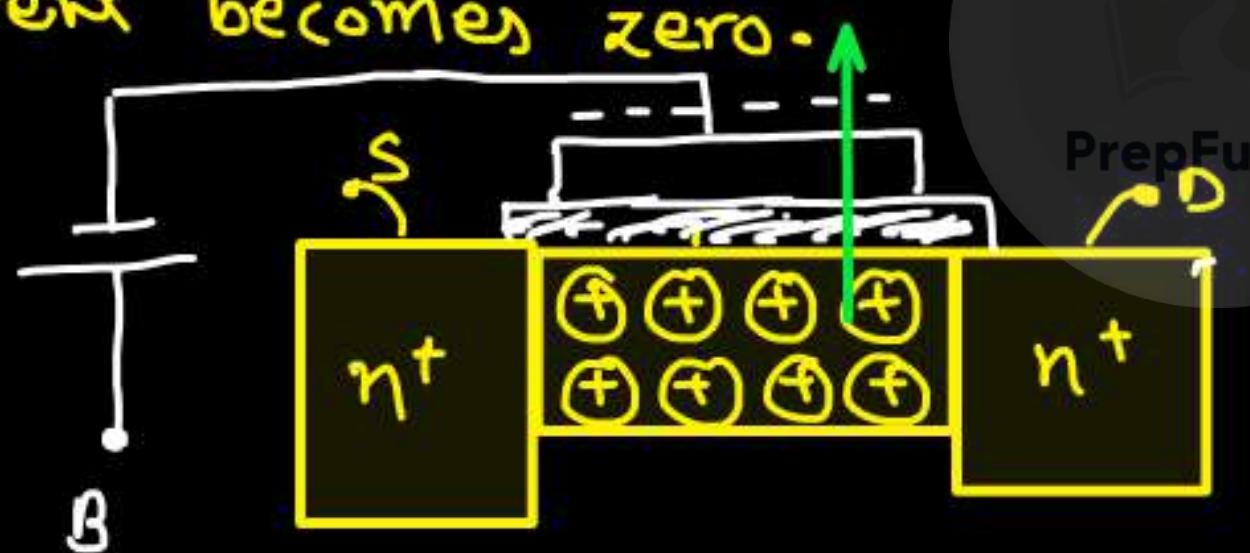@ Some -ve V_{GS} value, the channel will be depleted of charge carrier and the electric field in vertical direction will be so strong that the e Θ from source side will not be reaching the drain side and the current becomes zero.



⇒ Negative potential is known as pinch-off voltage.

② $V_{GS} = +ve$

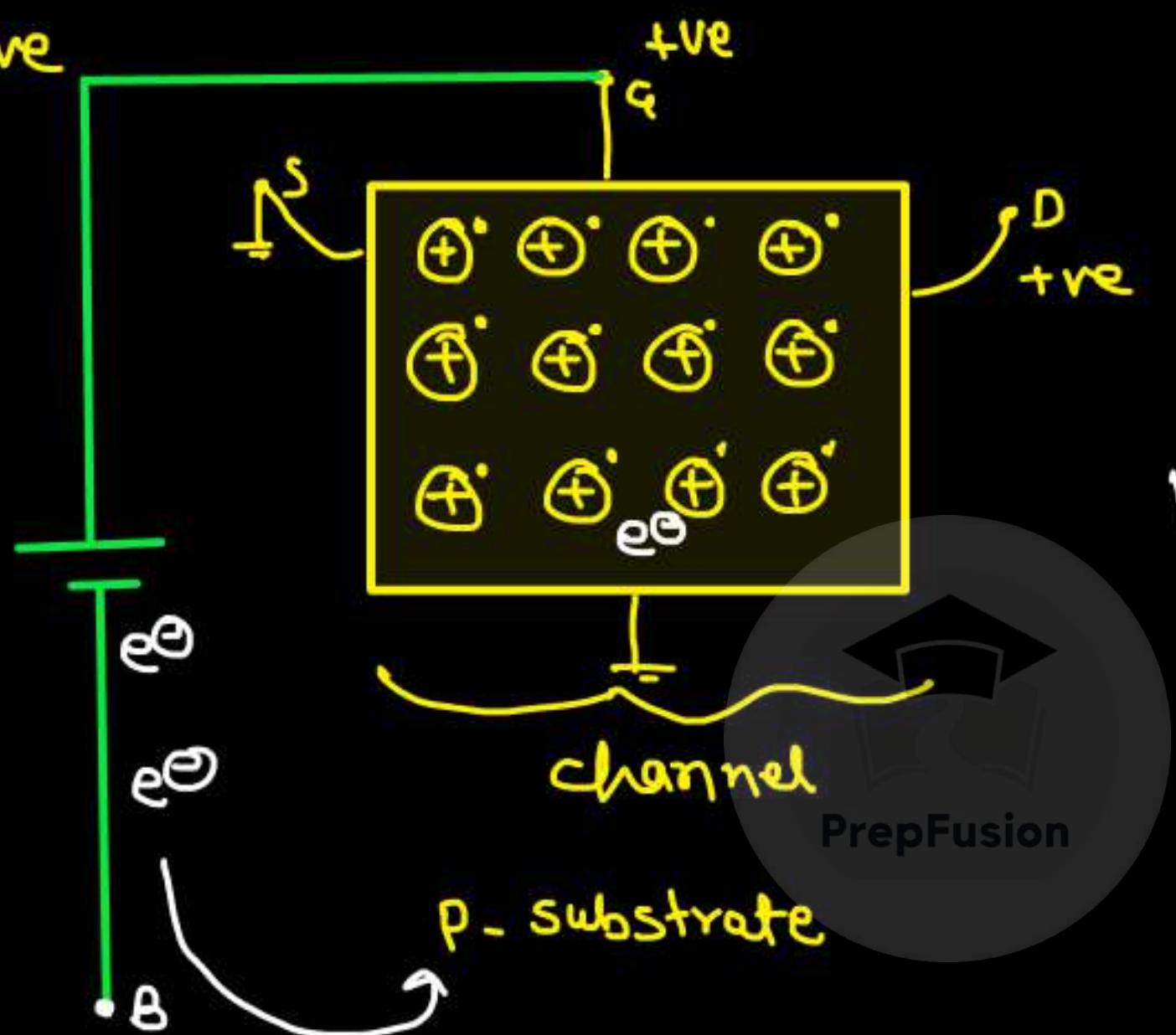


$V_G \uparrow \Rightarrow$ more e^- in channel



$I_D \uparrow$


I_D v/s V_{DS} curve:-

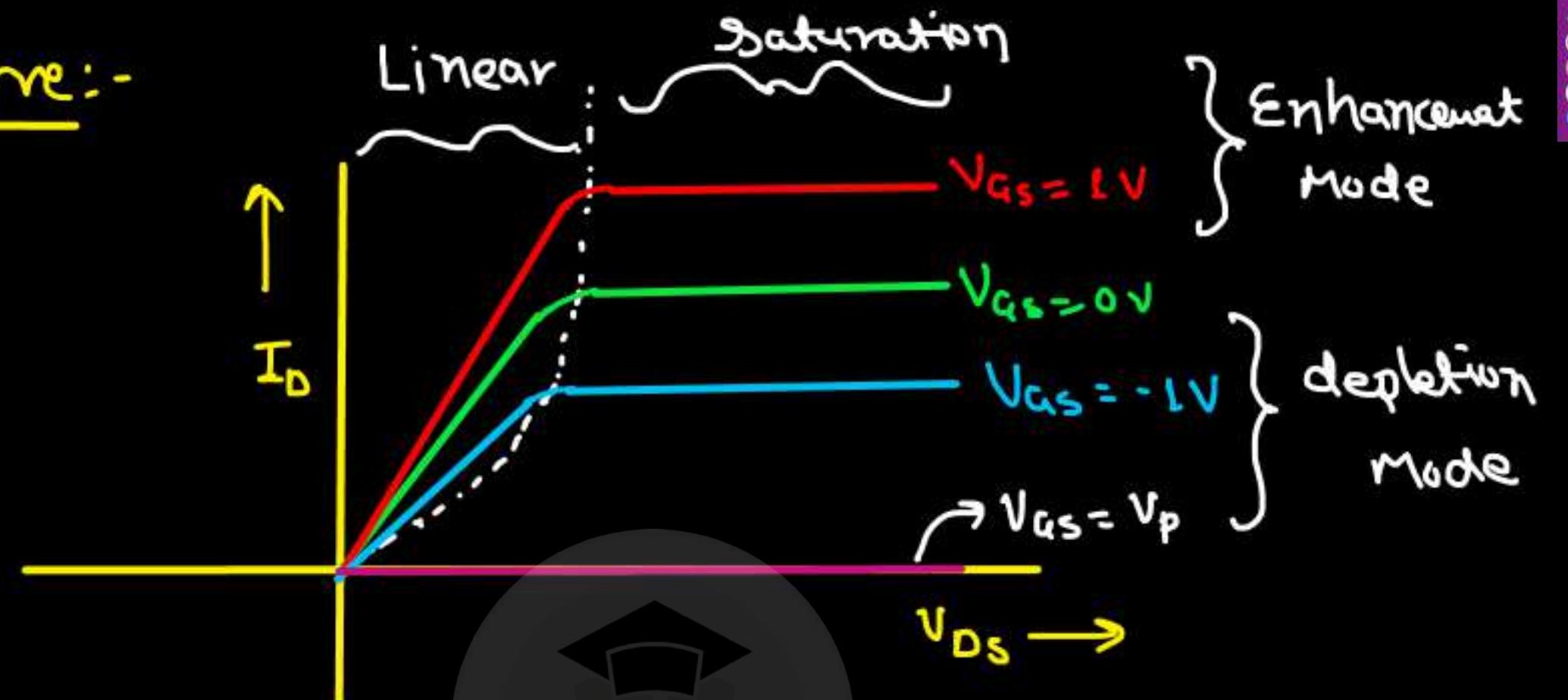


I_D v/s V_{GS} curve:-



P-channel depletion type MOSFET :-

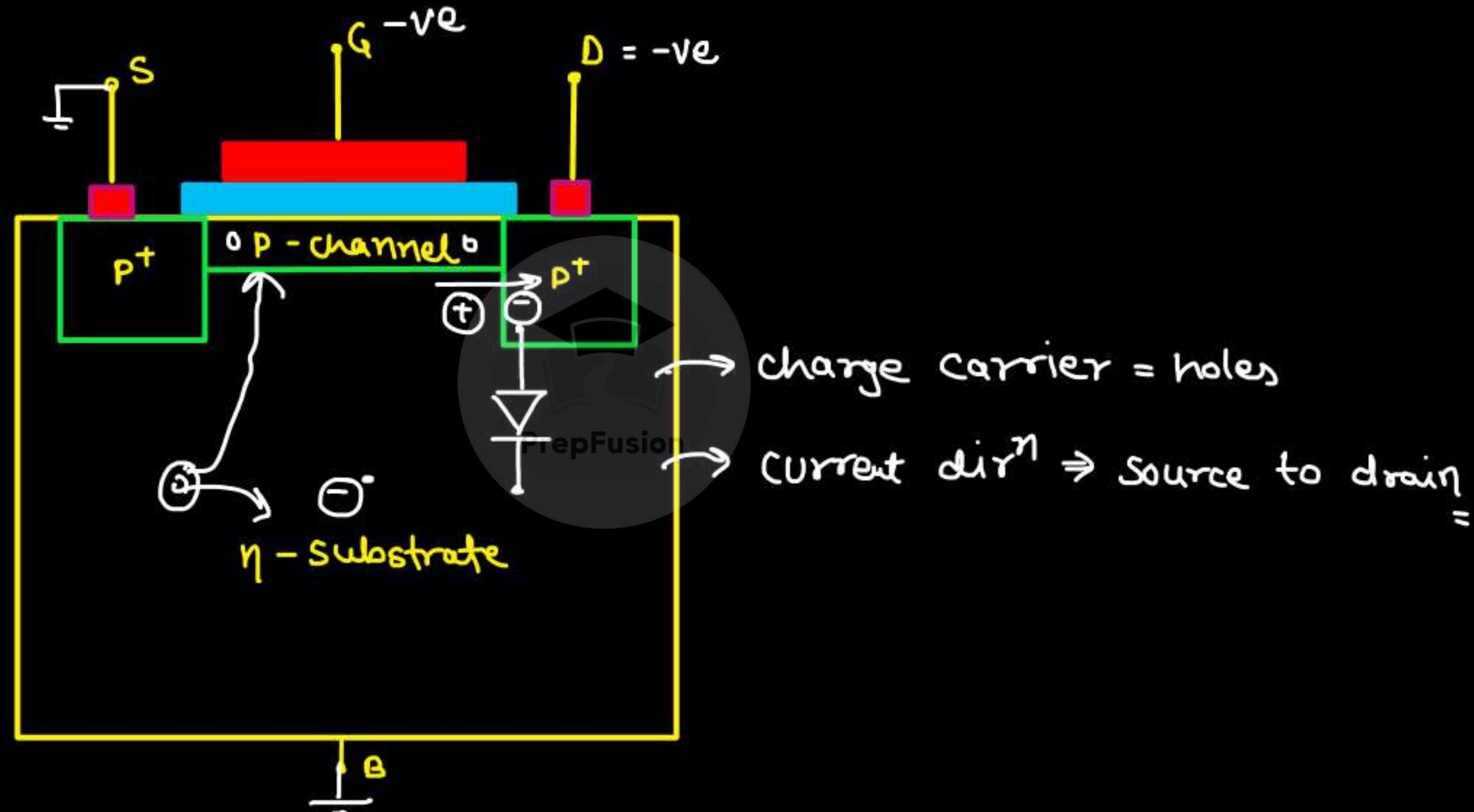


I_D v/s V_{DS} curve :-

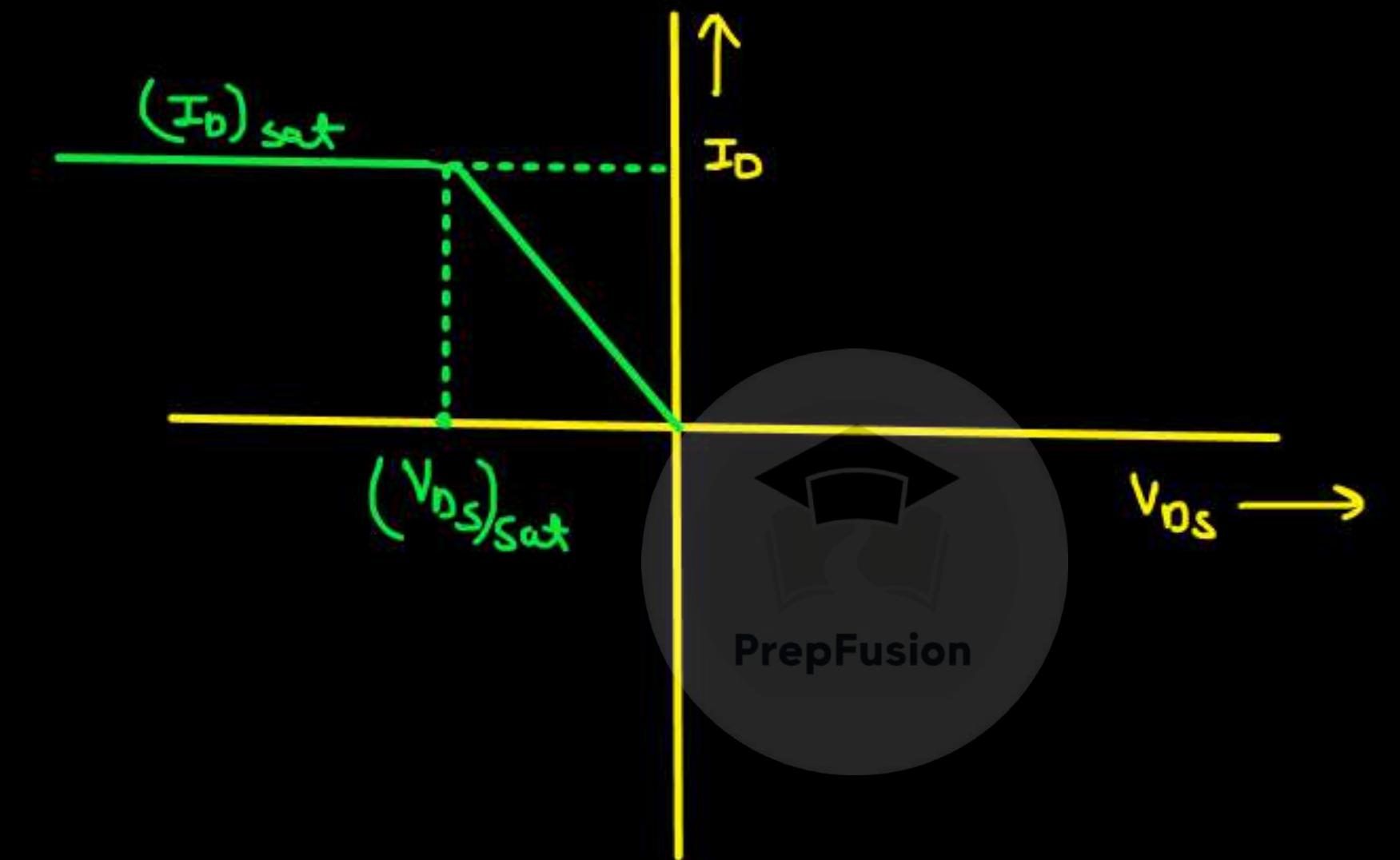

I_D direction \Rightarrow Source to drain


I_D v/s V_{GS} curve :-

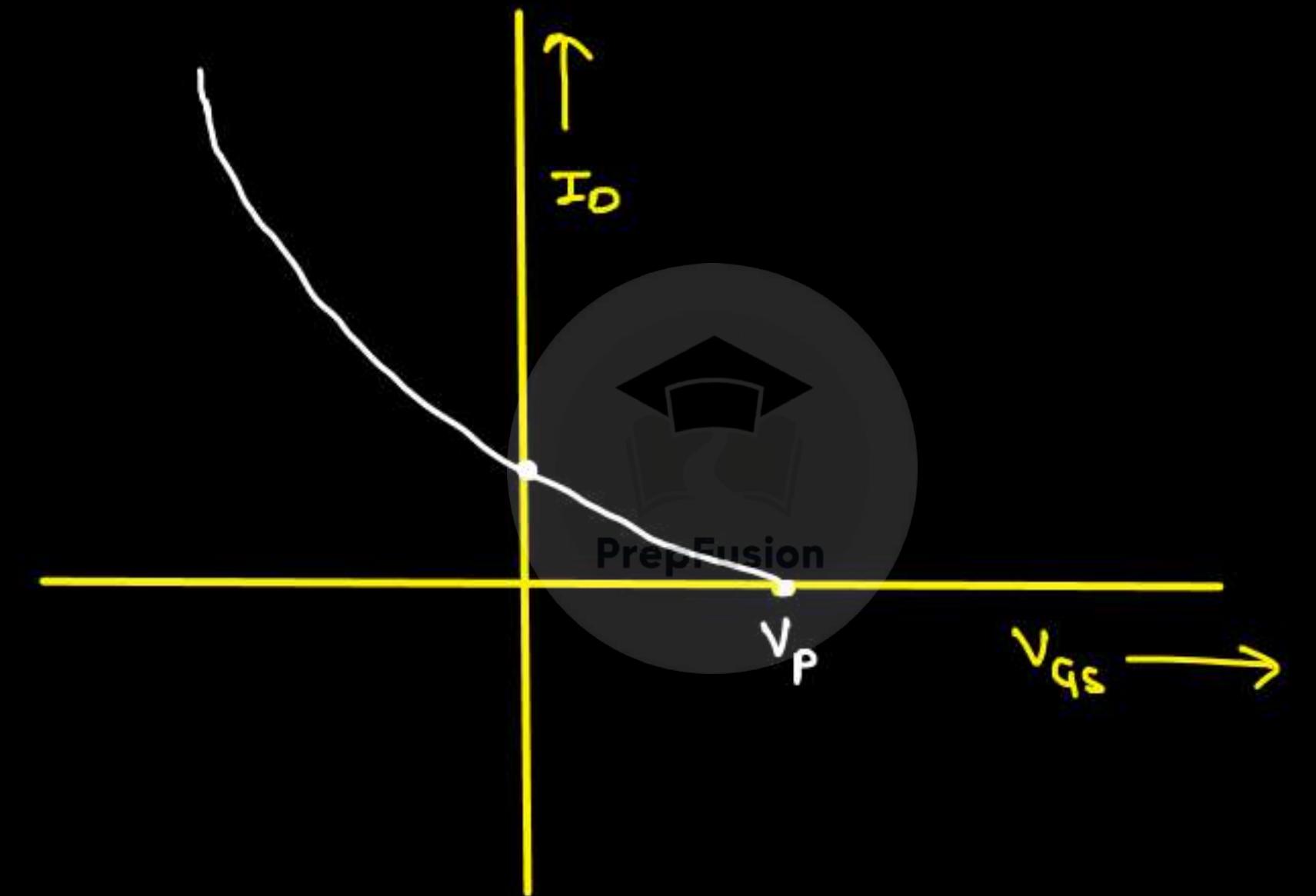

N.B. - In depletion type MOSFET, the channel (P or n) was already present. Even if you don't apply any controlling voltage @ Gate terminal ($V_{GS} = 0V$), still there will be some current flowing in the MOS and you will have some o/p @ the load.

For amplifier design, we need a input controlled energy source. That's why we can't use depletion type MOSFET for amplifiers.

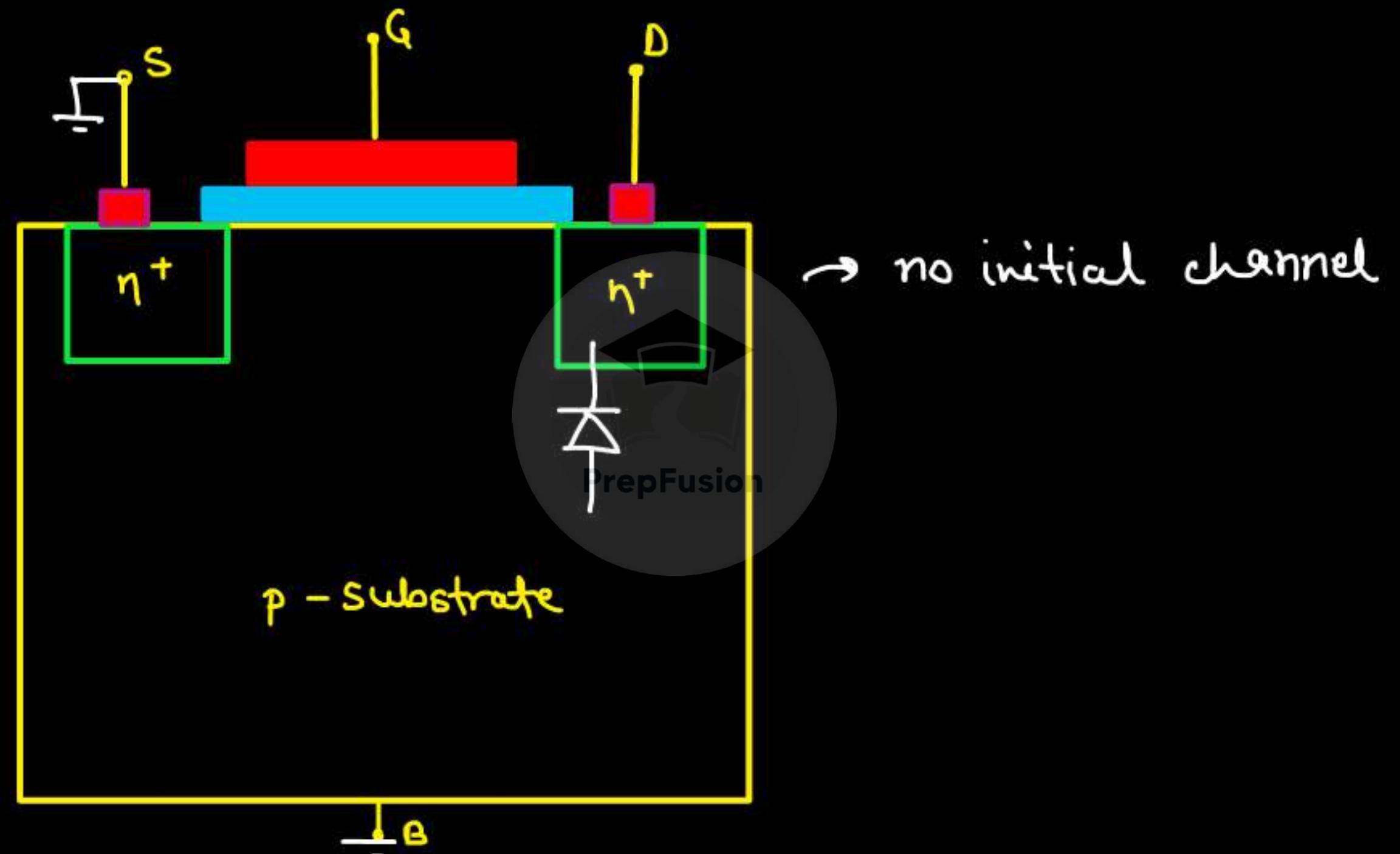* n-channel enhancement type MOSFET :- (NMOS)



Codⁿ-1

$$V_{GS} = 0 \text{ V} \Rightarrow I_D = 0 \text{ Amp}$$

$$V_{DS} = 0 \text{ V}$$

Codⁿ-2

$$V_{GS} = 0 \text{ V} \Rightarrow I_D = 0 \text{ Amp}$$

$$V_{DS} = -\text{ve}$$

Codⁿ-3

$$V_{GS} = 0 \text{ V} \Rightarrow I_D = 0 \text{ Amp}$$


$$V_{DS} = +\text{ve}$$



Codⁿ-4

$V_{GS} = +ve \{ \text{very less} \}$

$V_{DS} = +ve$

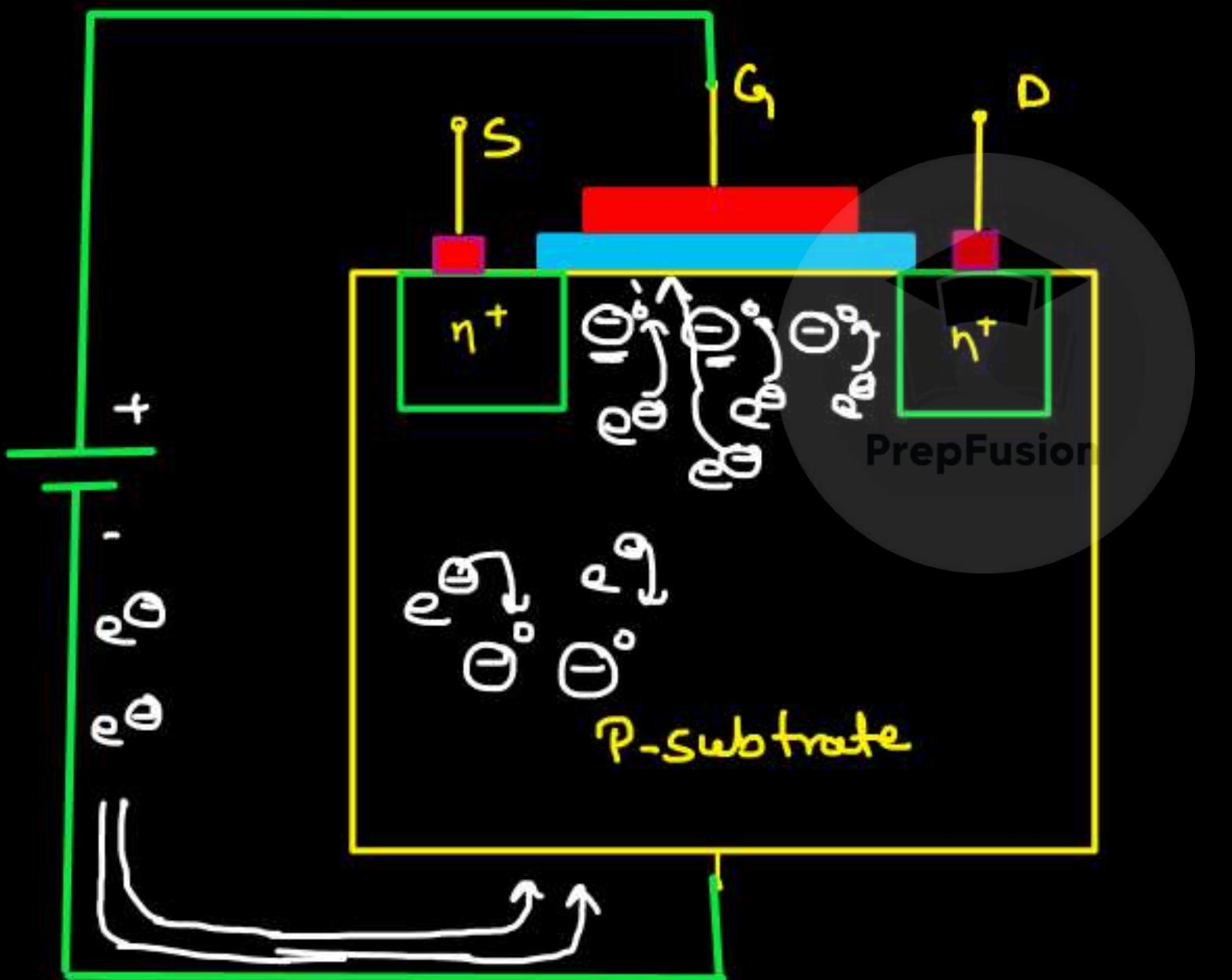

$V_G \uparrow \Rightarrow$ electron will come into substrate & recombine with hole




can't conduct current

still $I_D = 0 \text{ Amp}$



I have to increase V_G potential

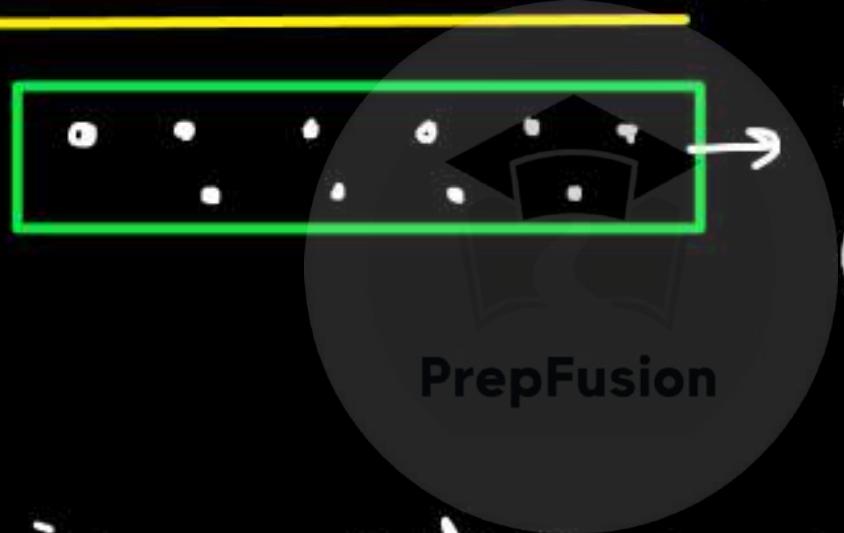@ some positive potential of V_G , the channel will be framed



Inversion layer
(P-substrate, we have framed
n-channel)

since, the channel is present now, so the current I_D flows.
direction of current is from drain to source.


* The value of V_G at which the current flows, is known as threshold voltage (V_T).

CodN - 5

$$V_{DS} = +ve$$


$$V_{GS} > V_T$$

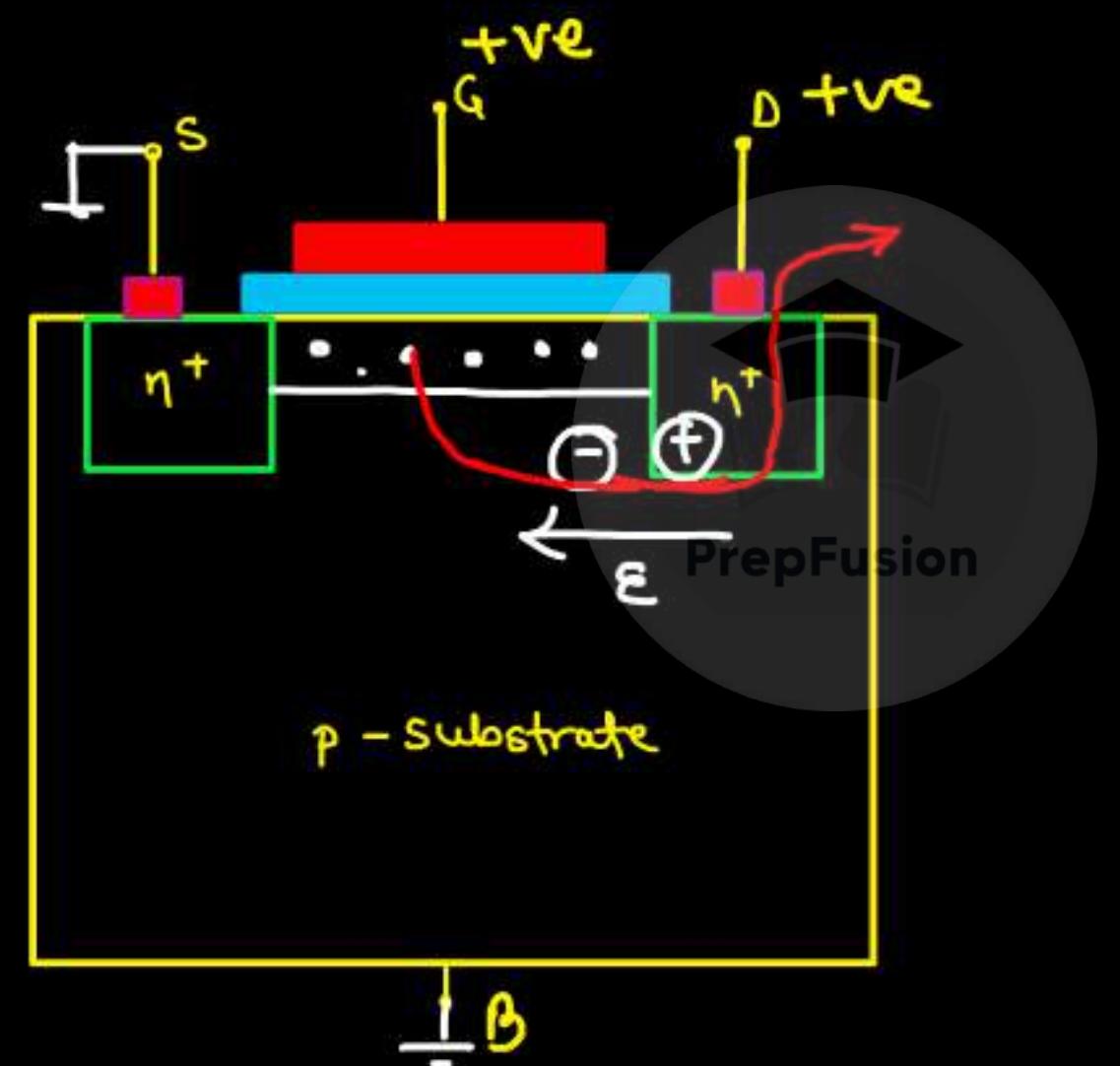$\Rightarrow I_D$ flows from drain to source.



After V_{TH} , Increasing $V_{GS} \uparrow \Rightarrow$ more e^- in channel


* * *
 I_D v/s V_{GS} Curve :-

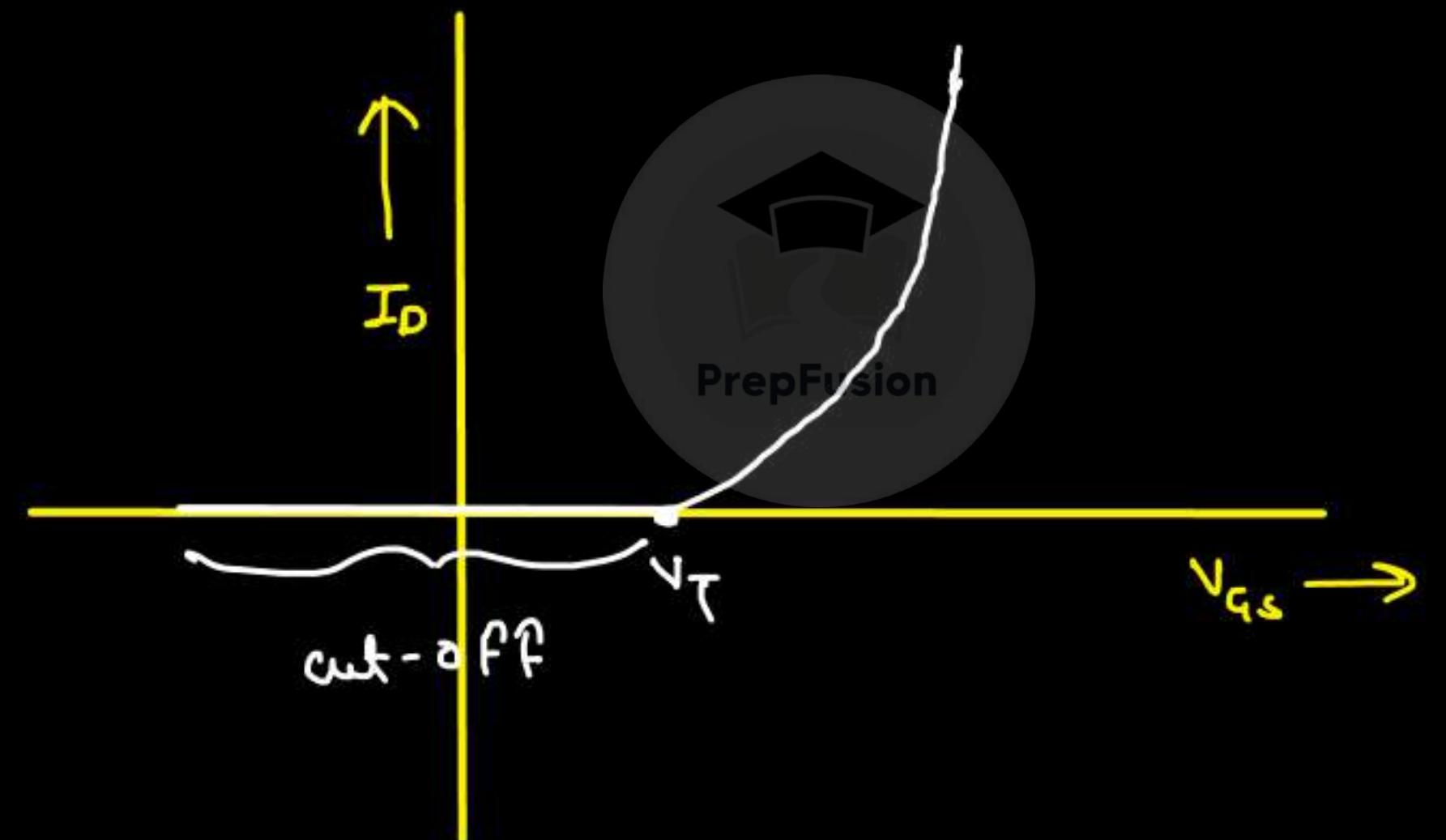

Codⁿ-6

$$V_{GS} > V_T \{ \text{fixed} \}$$


$$V_{DS} = +ve \{ \text{Increasing} \}$$

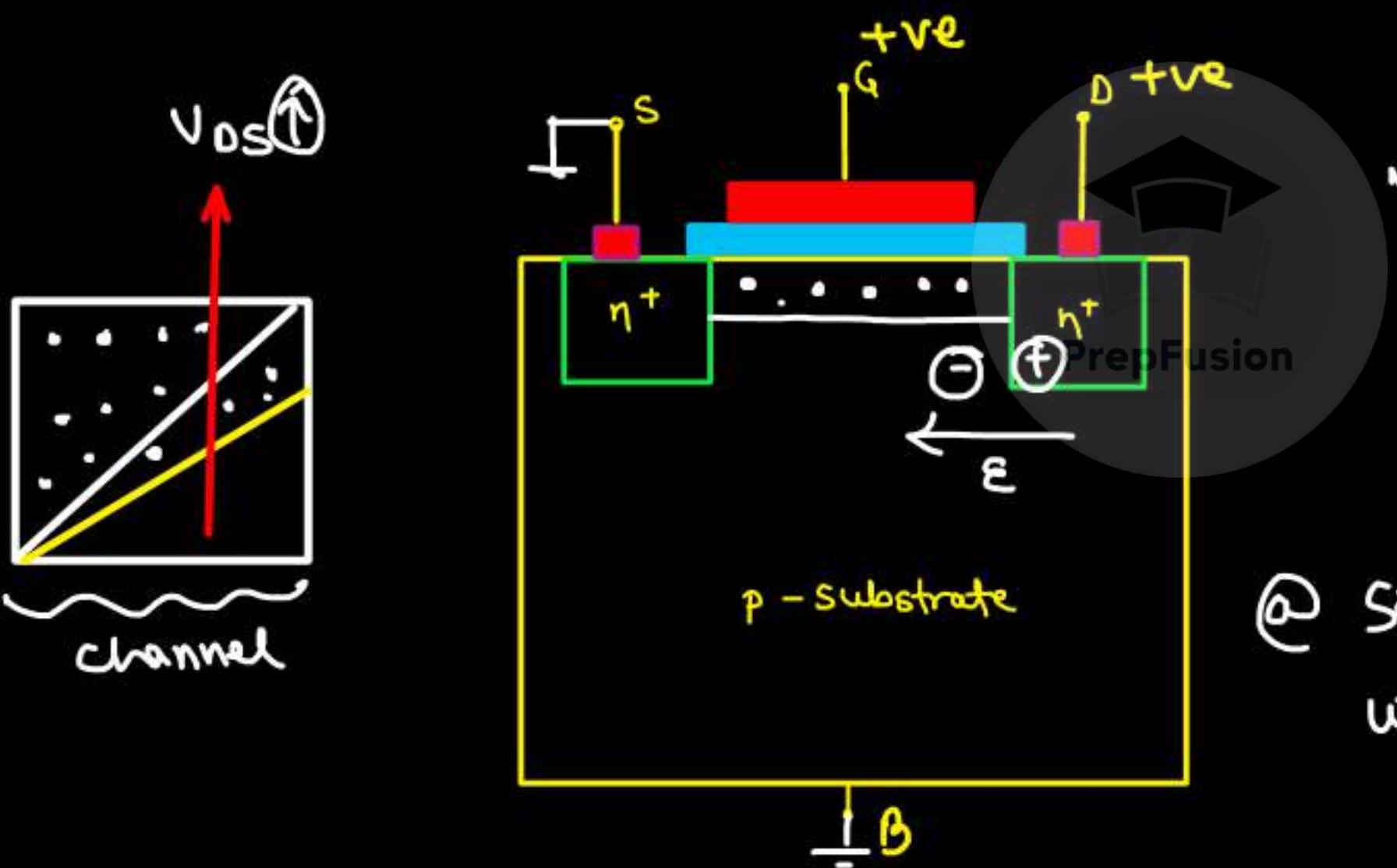

$V_{DS} \uparrow \Rightarrow \epsilon \uparrow \Rightarrow e^\Theta \text{ gets more force} \downarrow \text{more current}$

@ some value of V_{DS} , the current will saturate.

I_D v/s V_{DS} curve :-

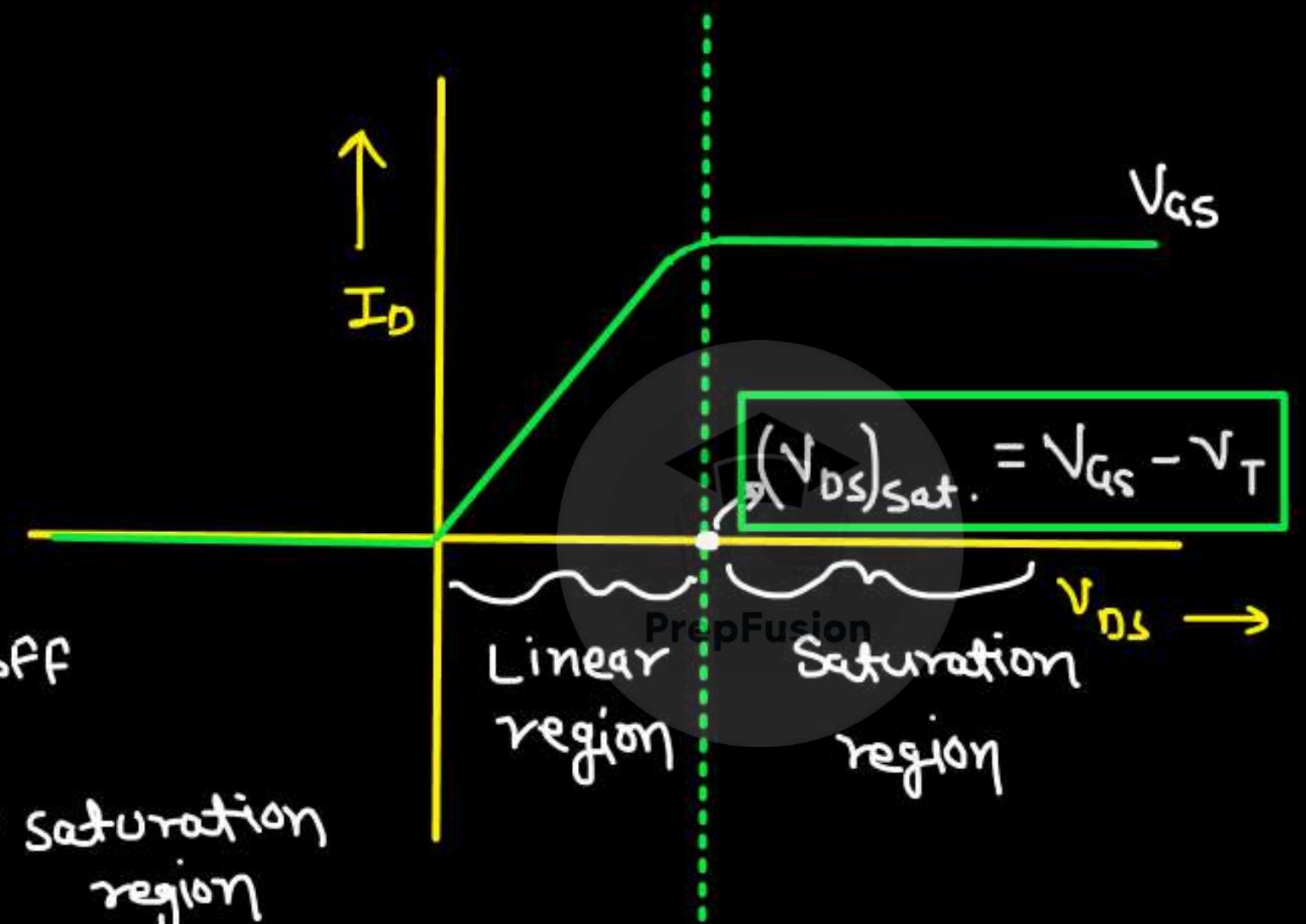


$V_{DS} < 0 \Rightarrow$ cut off

$V_{DS} > V_{GS} - V_T \Rightarrow$ saturation region

$V_{DS} < V_{GS} - V_T \Rightarrow$ linear

I_D v/s V_{GS}

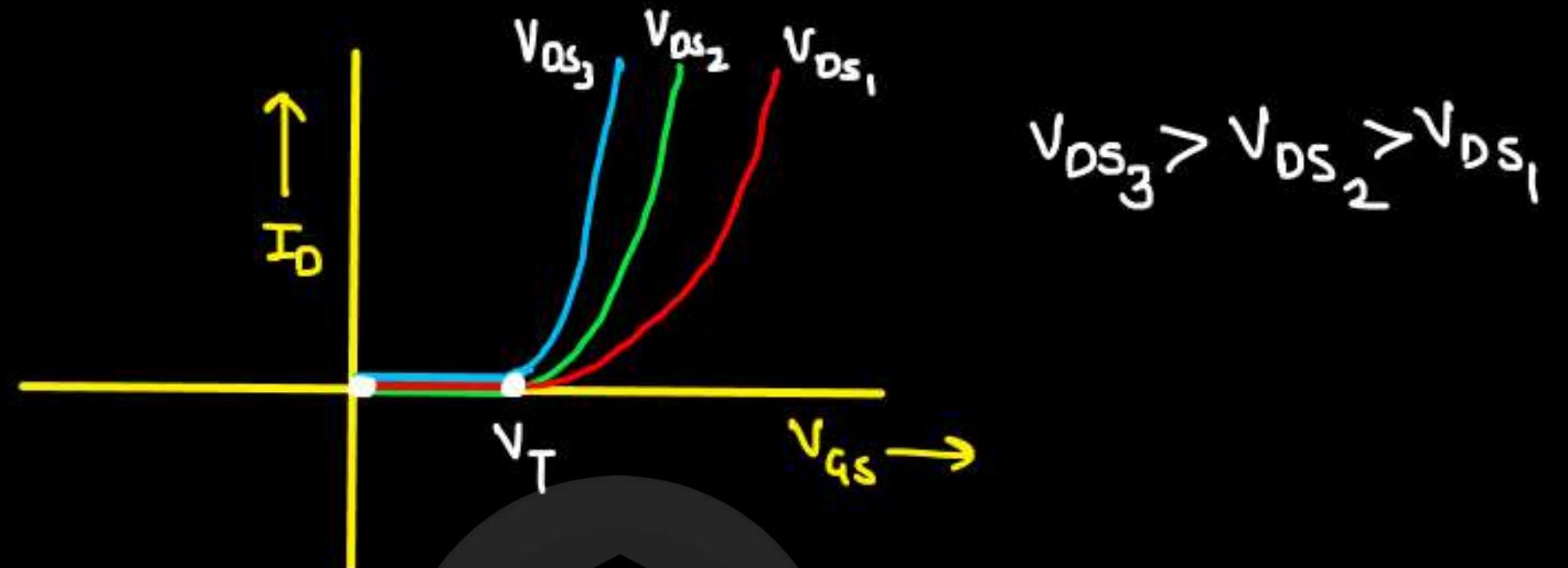


I_D v/s V_{DS}

Sat. voltage



$$V_{DS_1} = V_{GS_1} - V_T$$

$$V_{DS_2} = V_{GS_2} - V_T$$

$$V_{DS_3} = V_{GS_3} - V_T$$

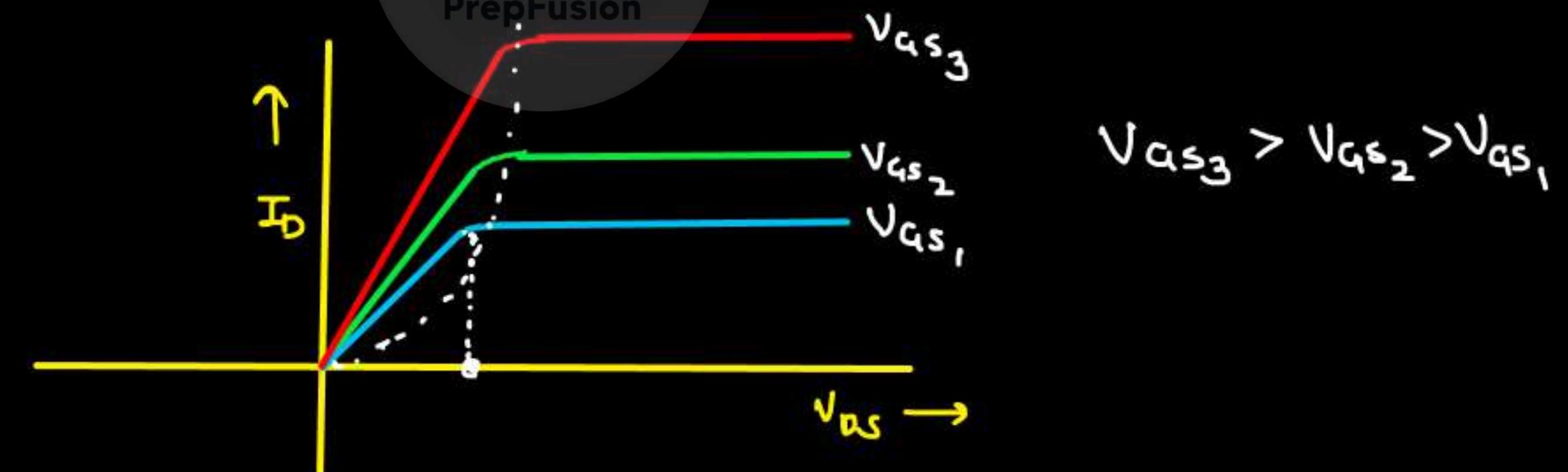

MOSFET Current Equation (N MOS) :-

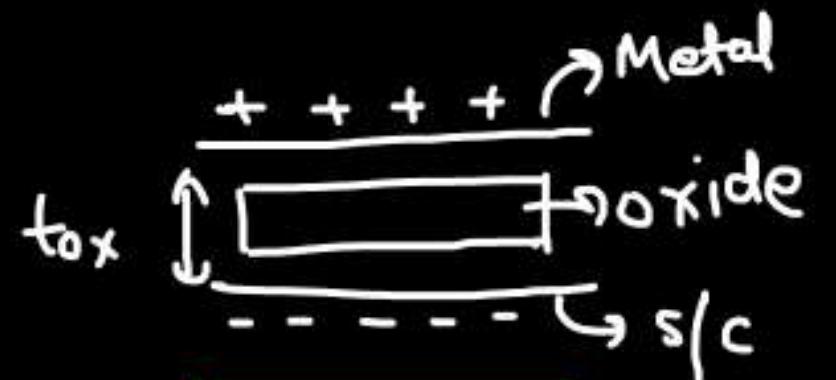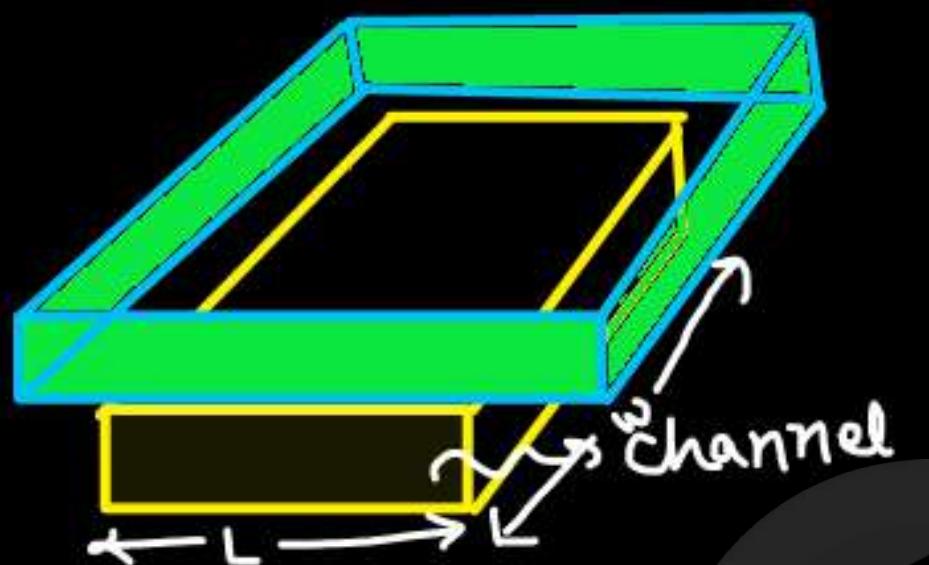

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \rightarrow \text{permittivity of oxide layer}$$

Current in Linear region :- [V_{DS} < V_{GS} - V_T]

PrepFusion





$$I_D = \frac{\mu_n C_{ox} W}{L} \left[(V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

μ_n → mobility of eθ

L → channel length

W → channel width

V_{Tn} → Threshold voltage

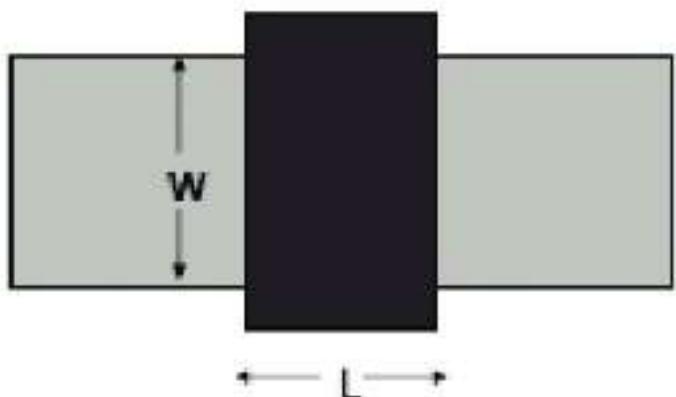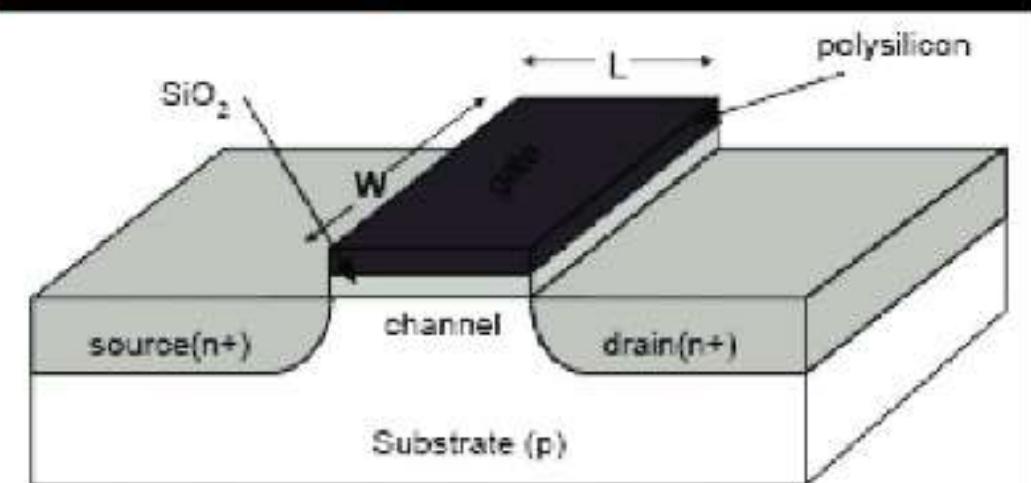


Current in saturation region:- [$V_{DS} \geq V_{GS} - V_T$]

$$(I_D)_{Sat.} = \frac{\mu_n C_{OX} W}{2L} (V_{GS} - V_{Tn})^2$$

N.B. - In case NMOS ; Higher potential node \Rightarrow drain
 lower potential node \Rightarrow source
 Current flow \Rightarrow drain to source

* P-channel enhancement type MOSFET :-

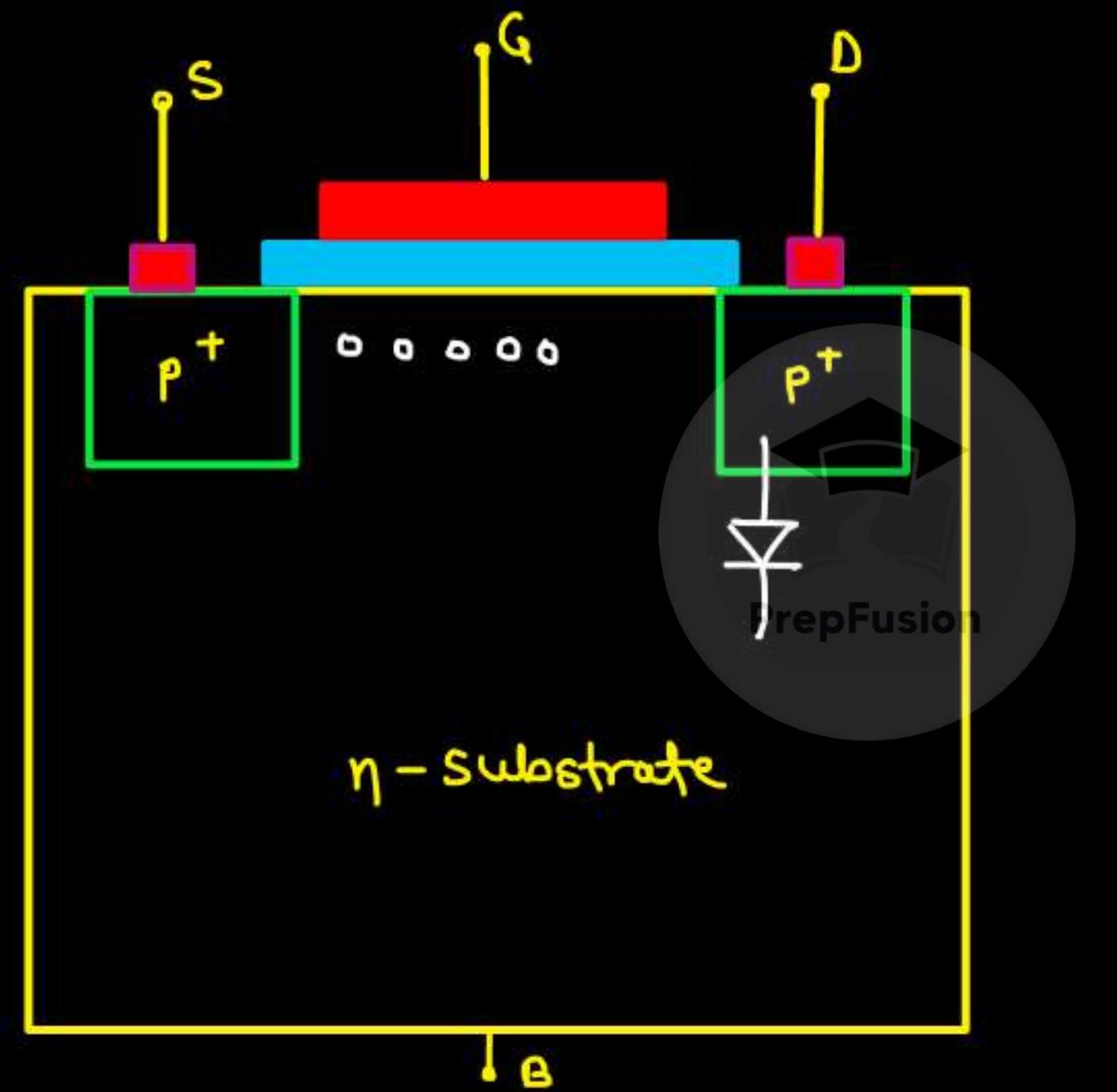

Condⁿ 1:-

$$V_{GS} = 0 = V_{DS} \Rightarrow I_D = 0$$

Condⁿ 2:-

$$V_{GS} = 0, V_{DS} = +ve \Rightarrow I_D = 0$$

Condⁿ 3:-

$$V_{GS} = 0, V_{DS} = -ve \xrightarrow{\text{ProFusion}} I_D = 0$$

Condⁿ 4 :-


$V_{GS} = -ve$ (very less)

$V_{DS} = -ve$

⇒ channel is not framed



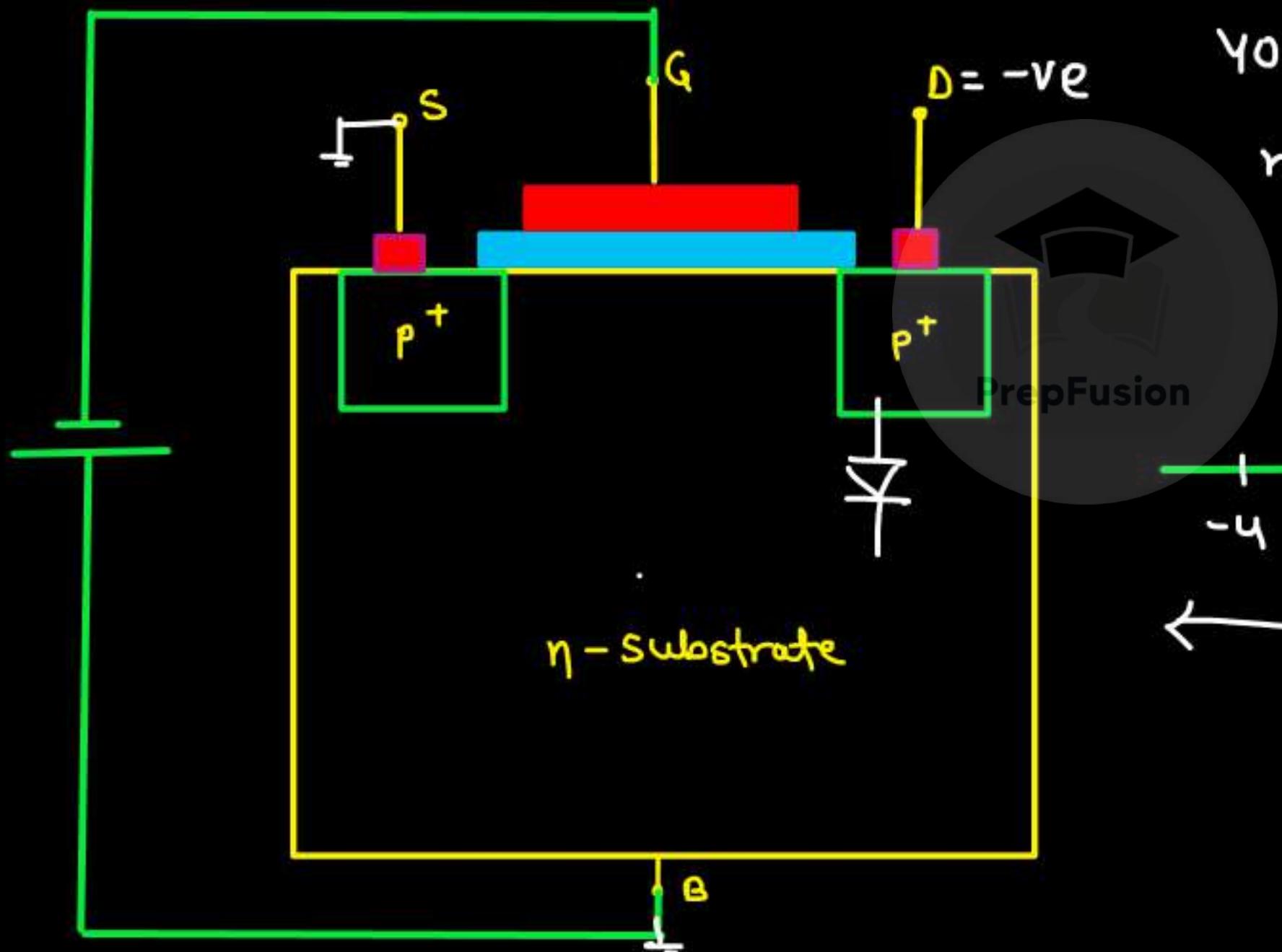You have to apply more negative potential.




$$V_{GS} < V_{TP}$$

$\leftarrow V_G$

↓
Current flows

when $V_{GS} < V_{TP}$

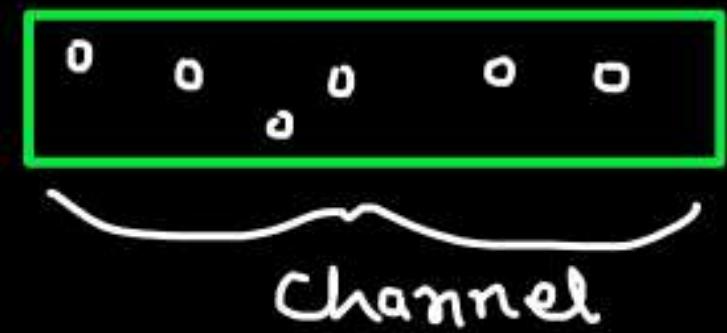


NMOS \rightarrow PMOS :-

$$V_{GS} \rightarrow V_{SG}$$

$$V_{DS} \rightarrow V_{SD}$$

$$V_{Tn} \rightarrow |V_{Tp}|$$

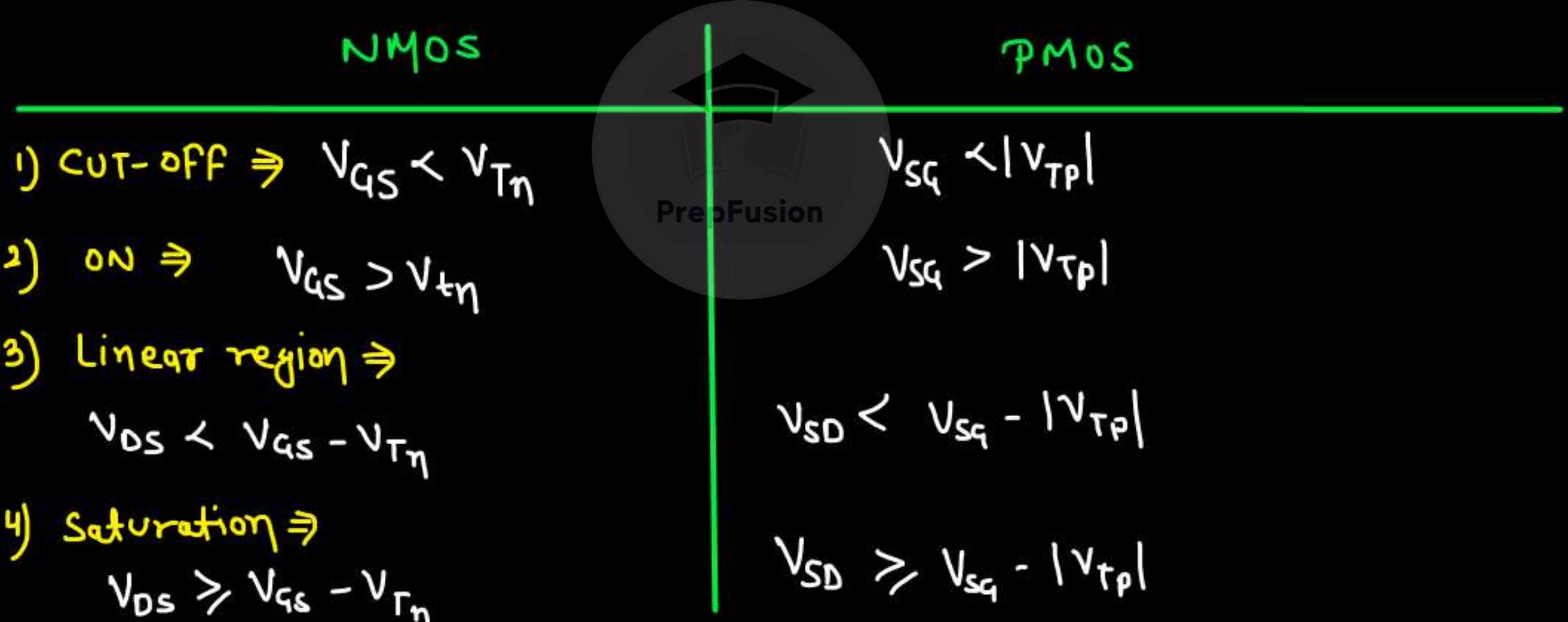


Condⁿ 5: -

$$\begin{aligned} \text{(i) } V_{GS} &< V_{TP} & \text{OR} & \quad V_{SG} > |V_{TP}| \\ \text{(ii) } V_{DS} &= -\text{ve} & \text{OR} & \quad V_{SD} = +\text{ve} \end{aligned} \Rightarrow I_D \text{ flows}$$




Source to drain

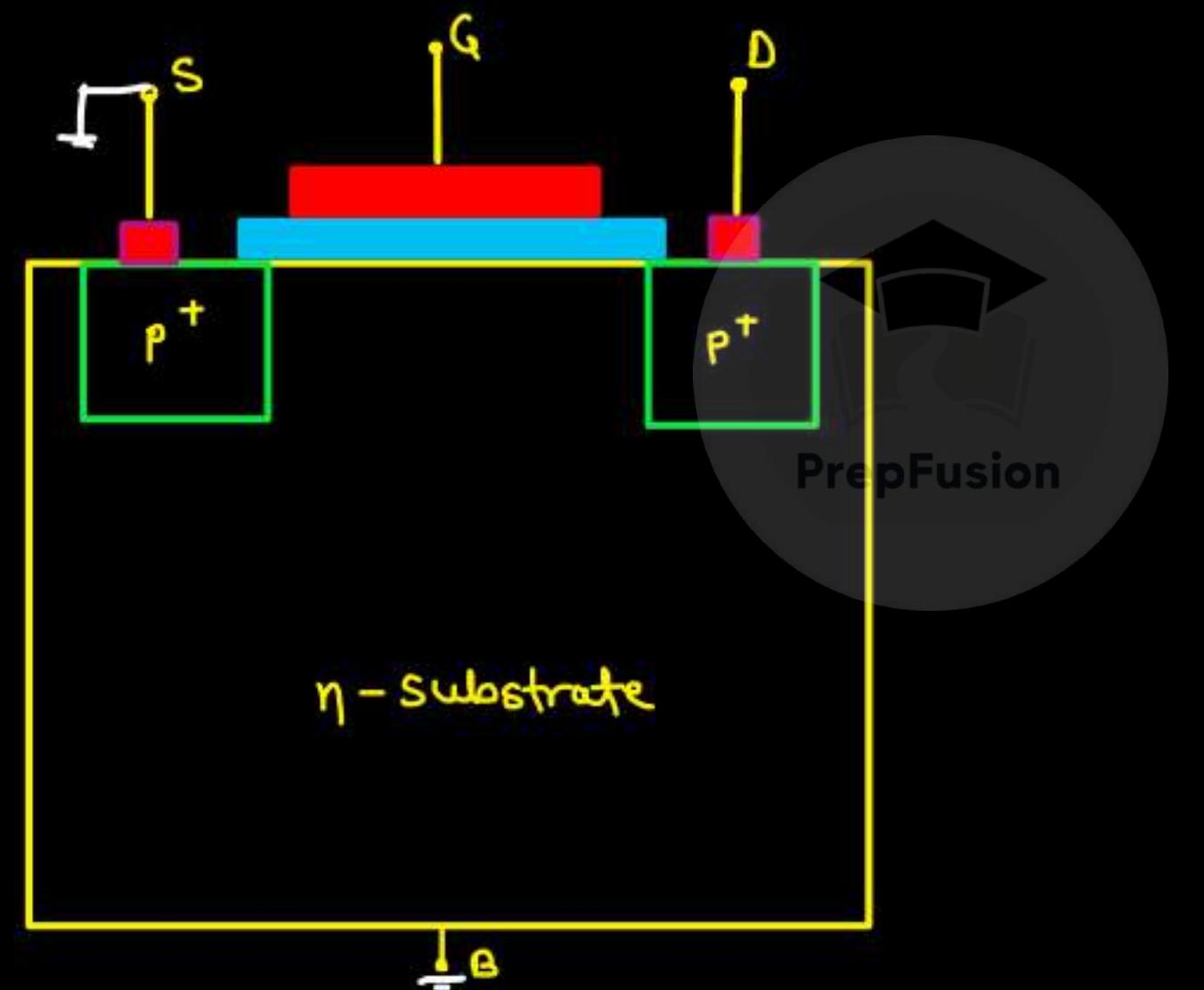

n - Substrate


I_D v/s V_{GS} curve :-

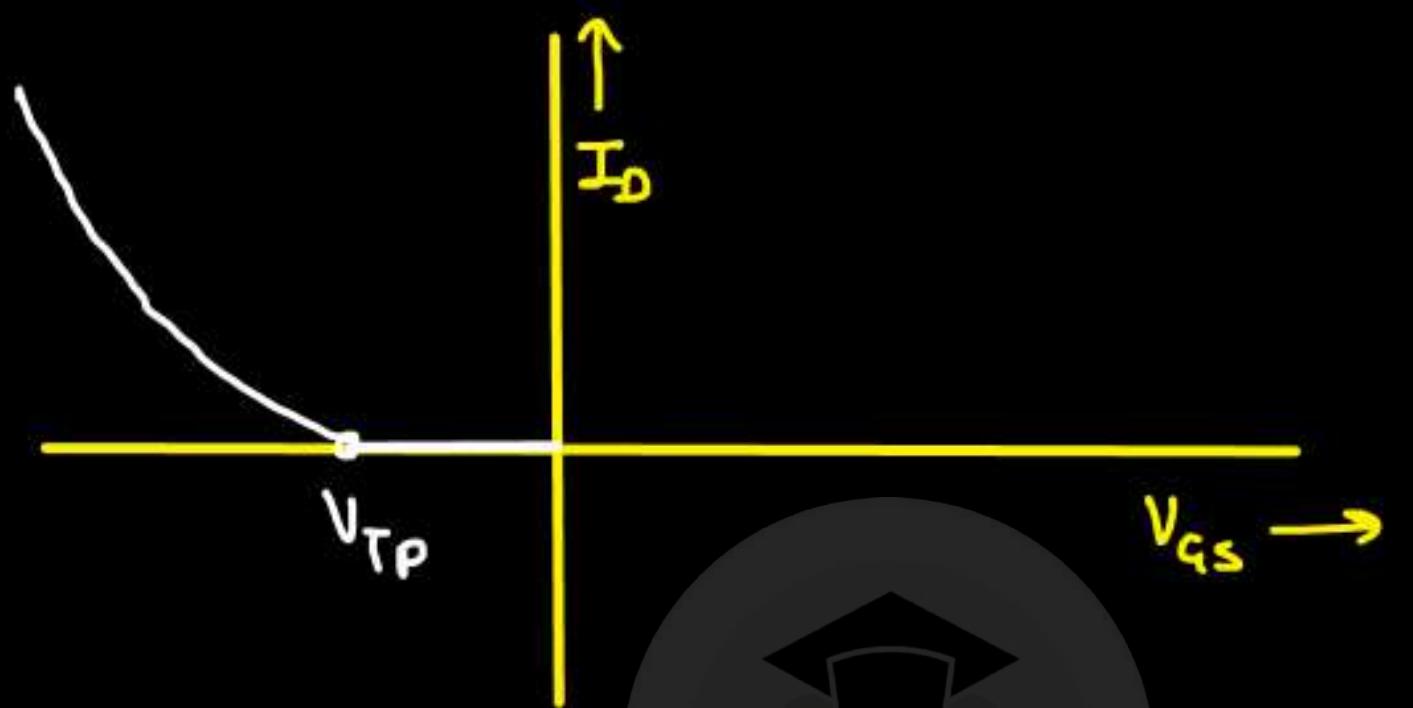

current dirⁿ :-

source to
drain

I_D v/s V_{SG} curve:-

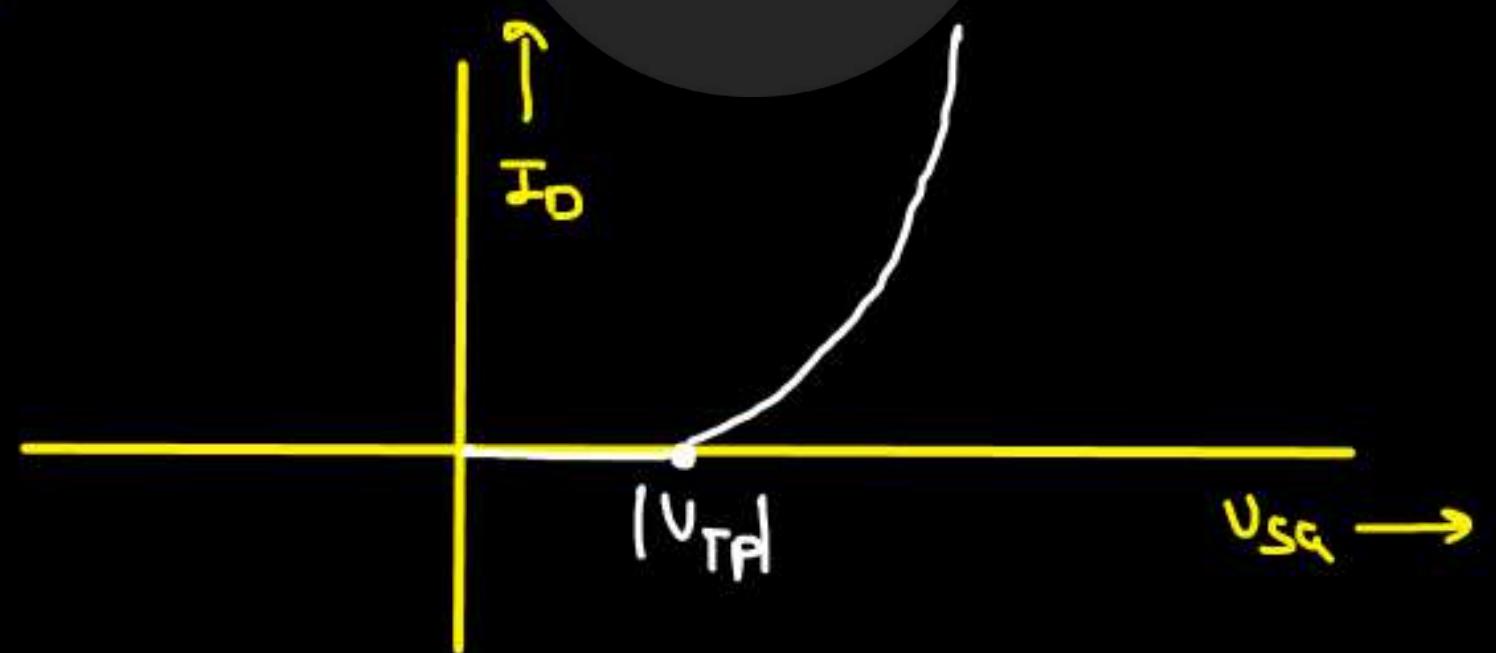

$$V_{SG} > |V_{TP}|$$

Cool 6:-

$V_{GS} < V_T$ { fixed }


$V_{DS} = -ve$ { negative supply increasing }




Current initially increases linearly
and then **saturates**.

PrepFusion

I_D v/s V_{DS} Curve

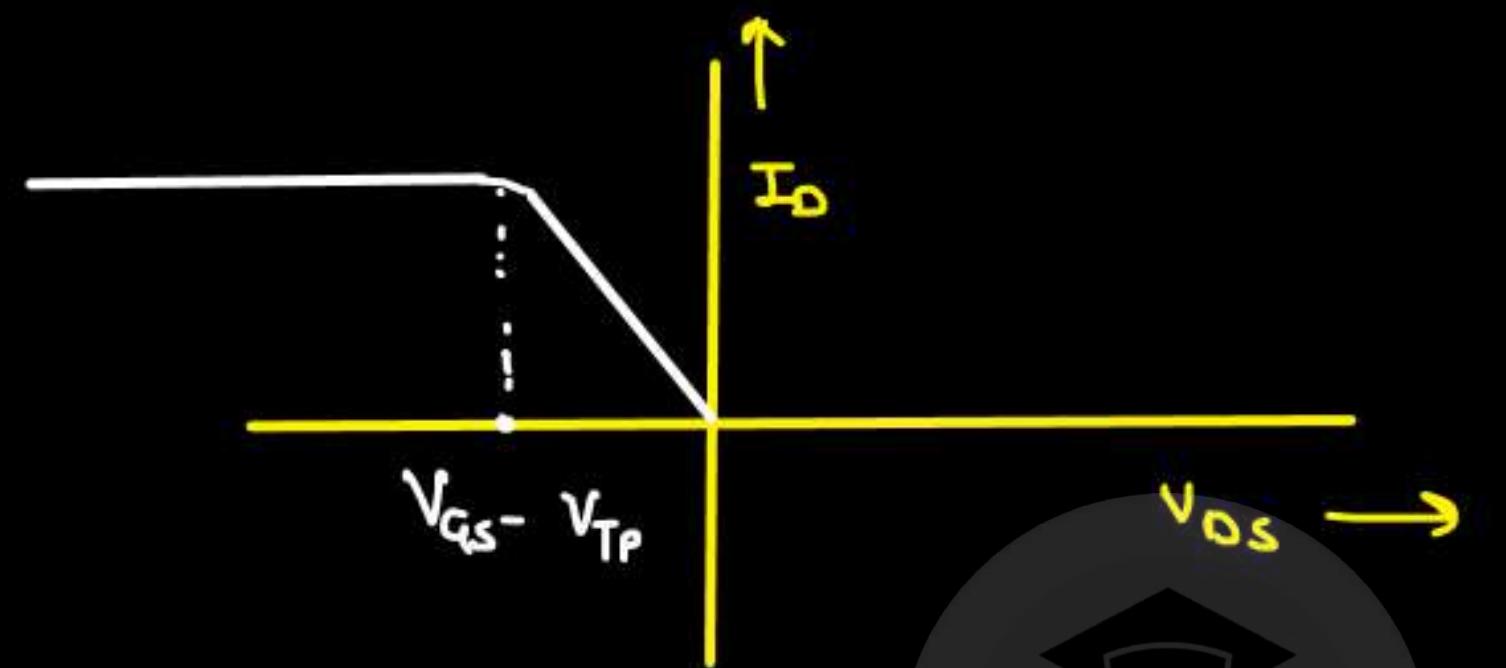


I_D v/s V_{SD} Curve:-

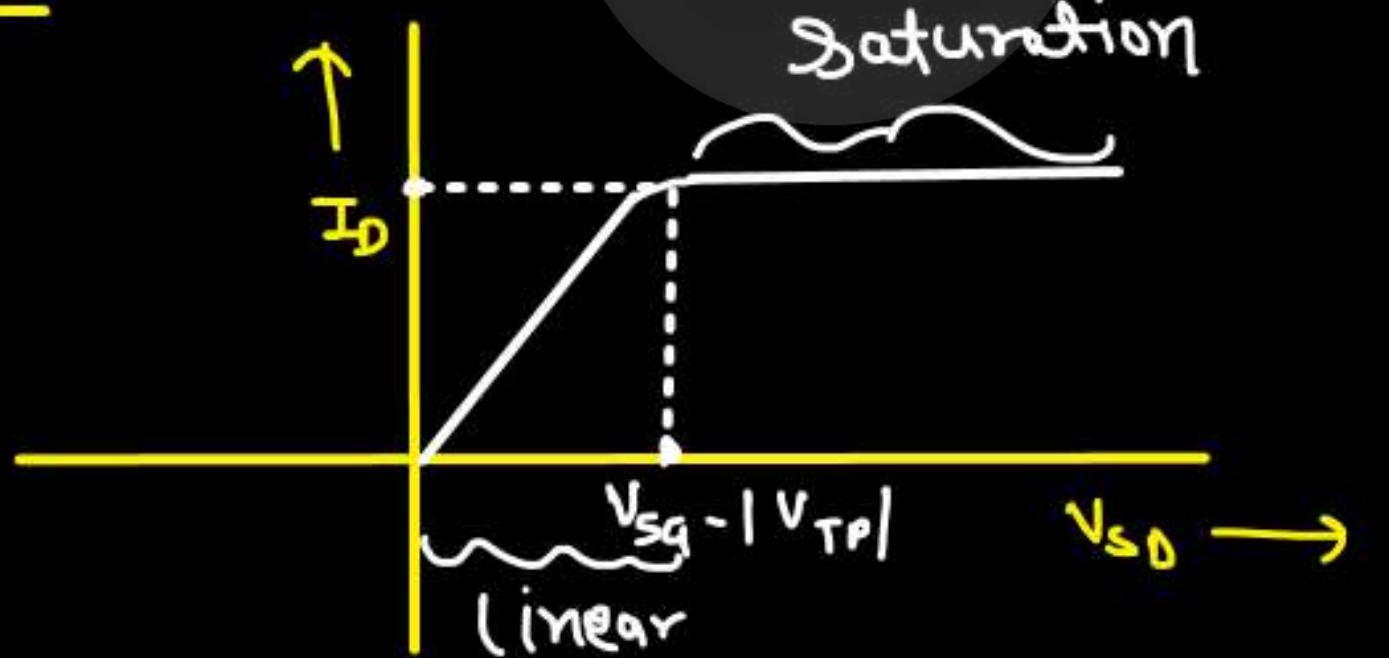


$$(V_{SD})_{sat} = V_{SG} - |V_{TP}|$$

I_D v/s V_{SG} CURVE:-

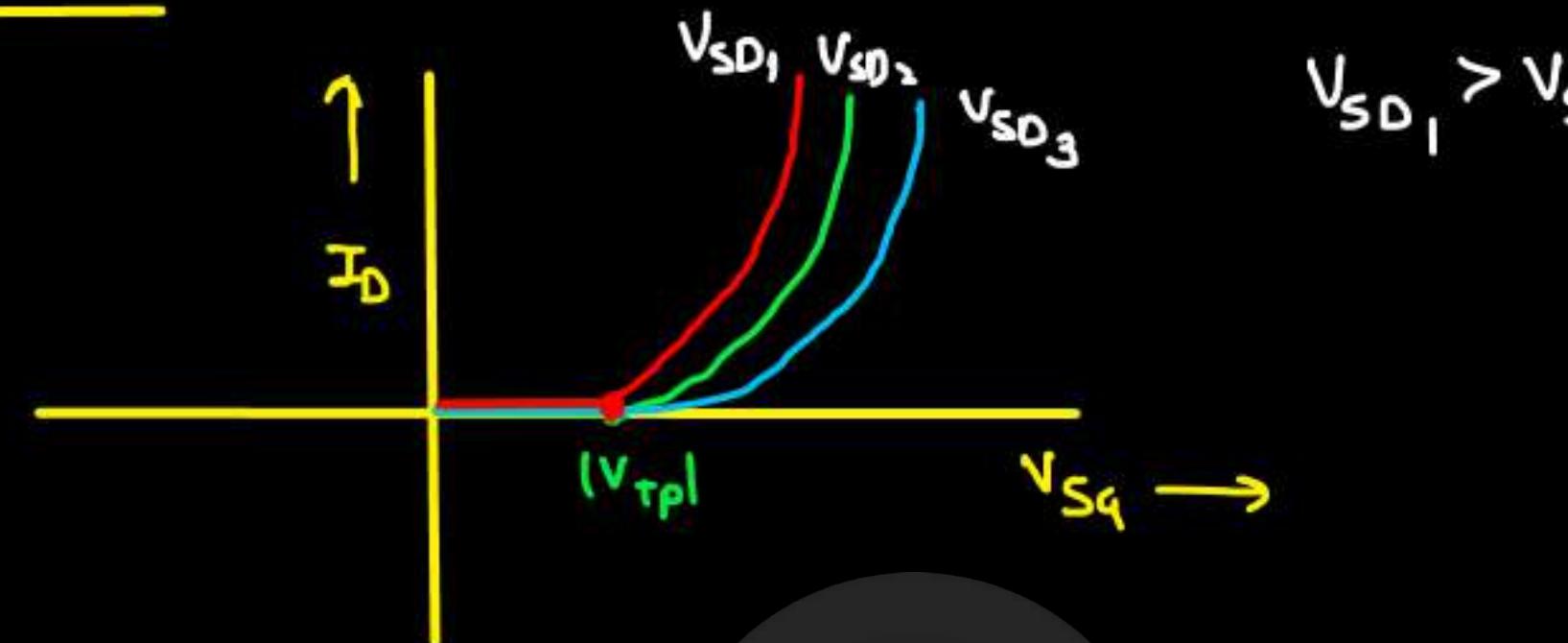


$$V_{SD_1} > V_{SD_2} > V_{SD_3}$$

I_D v/s V_{SD} CURVE:-

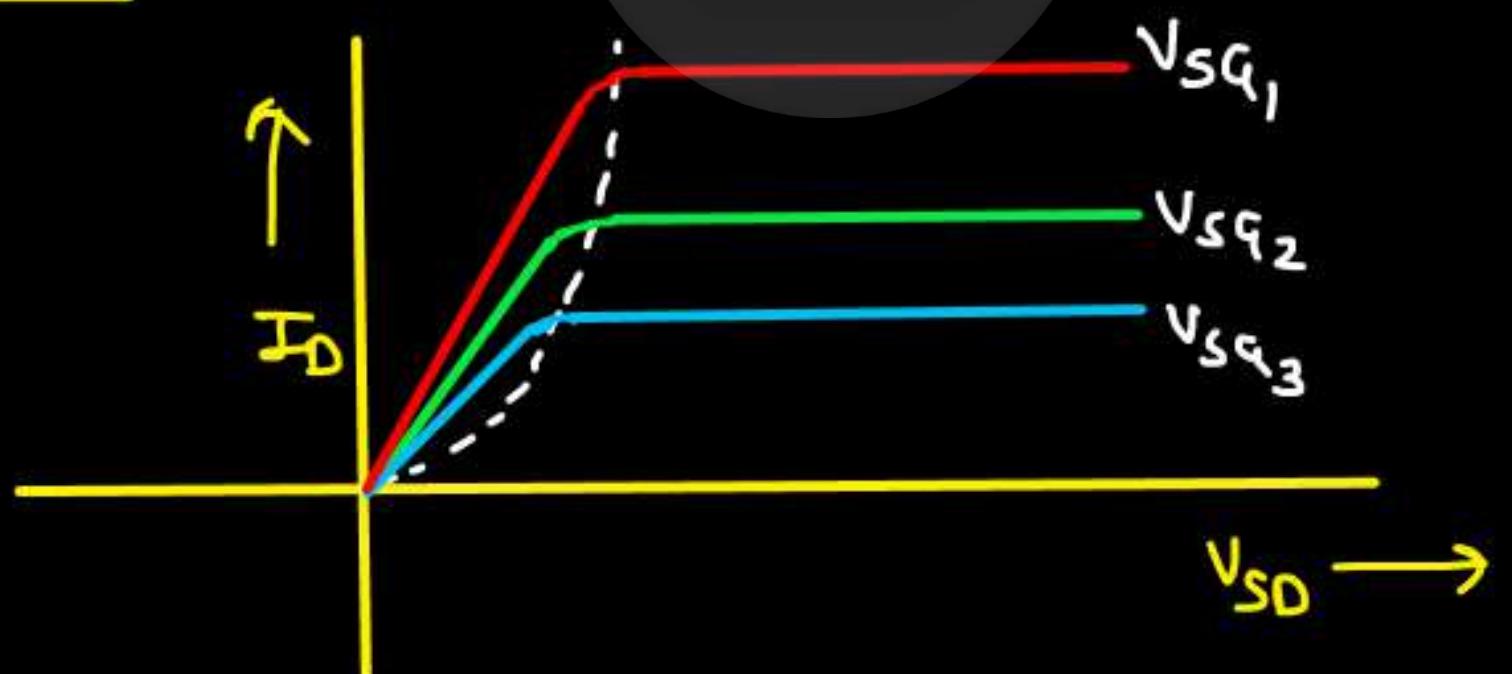

$$V_{SG_1} > V_{SG_2} > V_{SG_3}$$

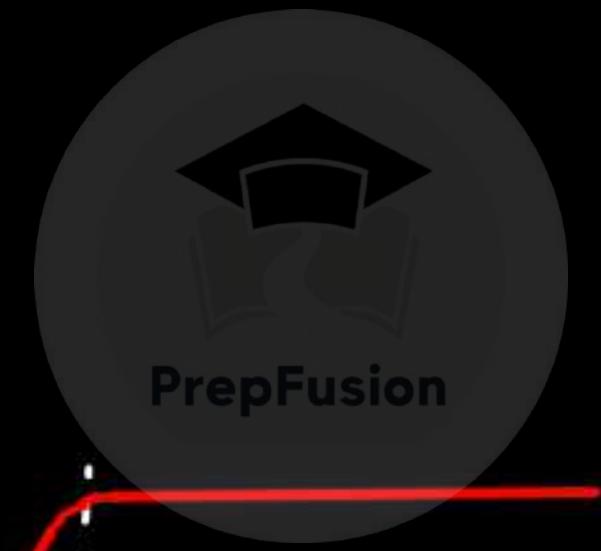

Current equation:- (PMOS)

NMOS \rightarrow PMOS

$$V_{GS} \rightarrow V_{SG}$$

$$V_{DS} \rightarrow V_{SD}$$

$$V_{Tn} \rightarrow |V_{TP}|$$

① Linear region :- $[V_{SD} < V_{SG} - |V_{TP}|]$

$$I_D = \frac{\mu_p C_{ox} W}{L} \left[(V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

② Saturation region :- $[V_{SD} \geq V_{SG} - |V_{TP}|]$

$$I_D = \frac{\mu_p C_{ox} W}{2L} (V_{SG} - |V_{TP}|)^2$$

N.B. -
=

IN PMOS,

Higher potential = Source

lower potential = Drain

dirn of current = Source to Drain

IN NMOS,

Higher potential = Drain

PrepFusion

lower potential = Source





dirn of current = Drain to Source

* MOSFET Circuit Symbol:-

H.P. → Higher potential
L.P. → Lower potential

Depletion type	Enhancement type	common for both
<p>n-channel → (NMOS)</p>	<p>Dashed D ~ H.P. S ~ L.P.</p> <p>PreFusion</p>	<p>D ~ H.P. S ~ L.P.</p>
<p>p-channel → (PMOS)</p>	<p>S ~ H.P. D ~ L.P.</p>	<p>S ~ H.P. D ~ L.P.</p>

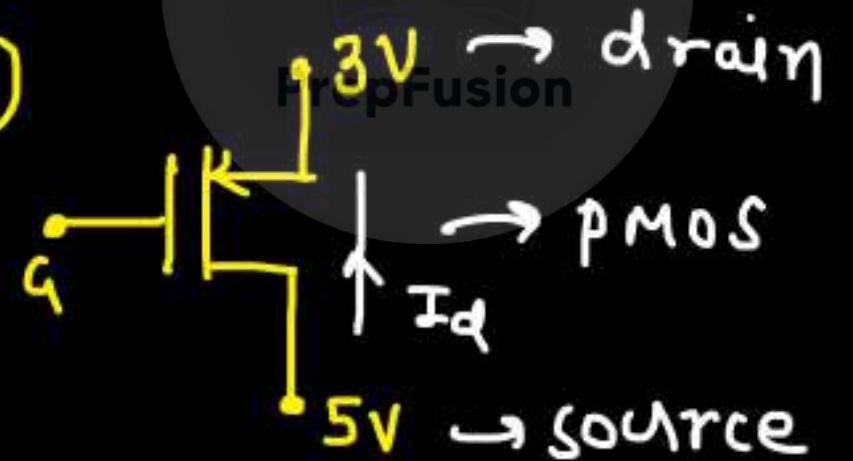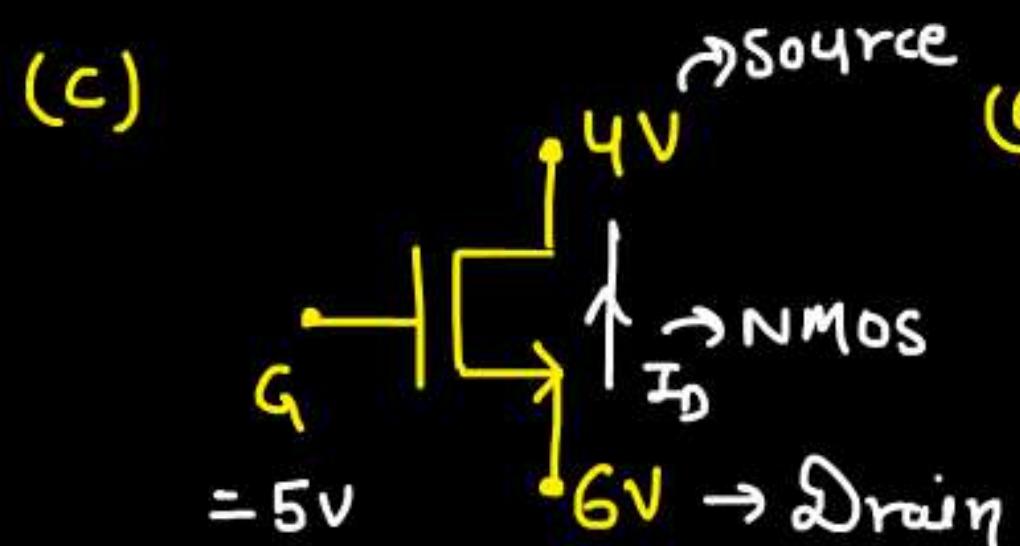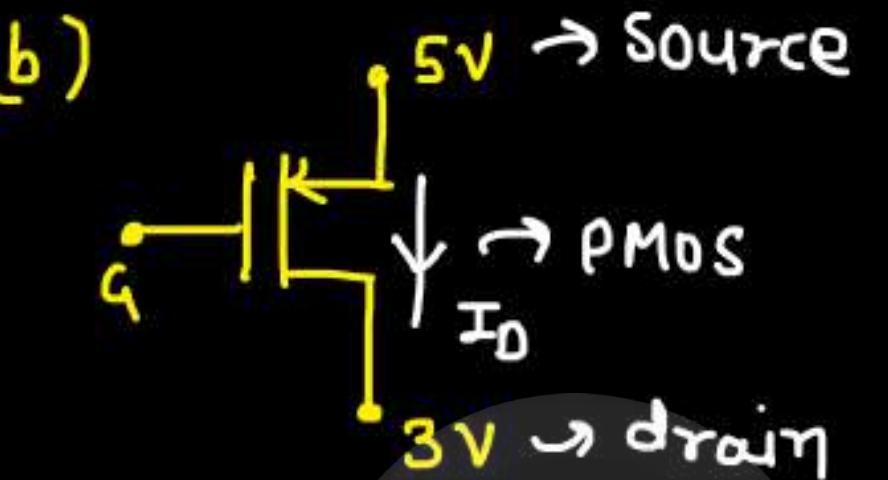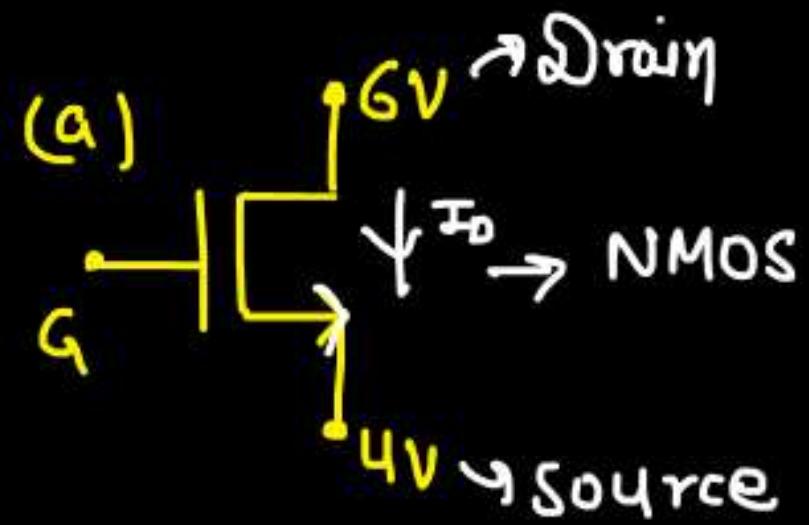Q. Mark Source and drain and the current dir'.



Q. Given $\mu_p = 0.4 \mu_n$ -

What must be the relative width of n-channel and p-channel devices if they are to have equal drain currents when operated in the saturation mode with overdrive voltage of the same magnitude.

→ Overdrive voltage

$$V_{ov} = V_{GS} - V_{Tn}$$

↓
PropFusion
NMOS

$$V_{ov} = V_{SG} - |V_{Tp}|$$

↓
PMOS

$$(I_D)_p = (I_D)_n$$

$$\frac{\mu_p C_f \left(\frac{W}{L}\right)_p (V_{SG} - |V_{Tp}|)^2}{2} = \frac{\mu_n C_f \left(\frac{W}{L}\right)_n (V_{GS} - V_{Tn})^2}{2}$$

$$\mu_p \left(\frac{\omega}{L} \right)_p = \mu_n \left(\frac{\omega}{L} \right)_n$$

$$0.4 \left(\frac{\omega}{L} \right)_p = \left(\frac{\omega}{L} \right)_n$$

$$\left(\frac{\omega}{L} \right)_p = 0.5 \left(\frac{\omega}{L} \right)_n$$

PrepFusion

Q. For n-channel MOSFET, if conduction parameter (k_n) is 0.249 mA/V^2 , Gate to Source voltage is $2V_T$.

where $V_T = 0.75$, $V_{DS} = 0.4V$. Find drain current. Given:-



$$\left\{ k_n = \frac{\mu_n C_{ox} W}{2L} \right\}$$

$$\frac{\mu_n C_{ox} W}{2L} = 0.249 \text{ mA/V}^2$$

$$V_{GS} = 2V_T = 1.5V$$

$$V_T = 0.75V$$

$$V_{DS} = 0.4V$$

Drain current = ? → Sat. ?
 → Linear. ?



$$V_{ov} = V_{GS} - V_T = 0.75V$$

$$V_{DS} = 0.4V$$

$$V_{DS} < V_{ov} \text{ OR } V_{DS} < V_{GS} - V_T$$

↓

Linear region =

MOS is working in Linear region

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$= 2 \times 0.249 \left[\frac{mA}{V^2} \right] \left[0.75 \times 0.4 - \frac{(0.4)^2}{2} \right] \times V^2$$

$$I_D = 0.109mA$$




Q. How many charge carriers are there in a MOS?

- One one. PMOS → Holes
NMOS → Electrons


Q. What is the need of oxide layer in MOS.

-

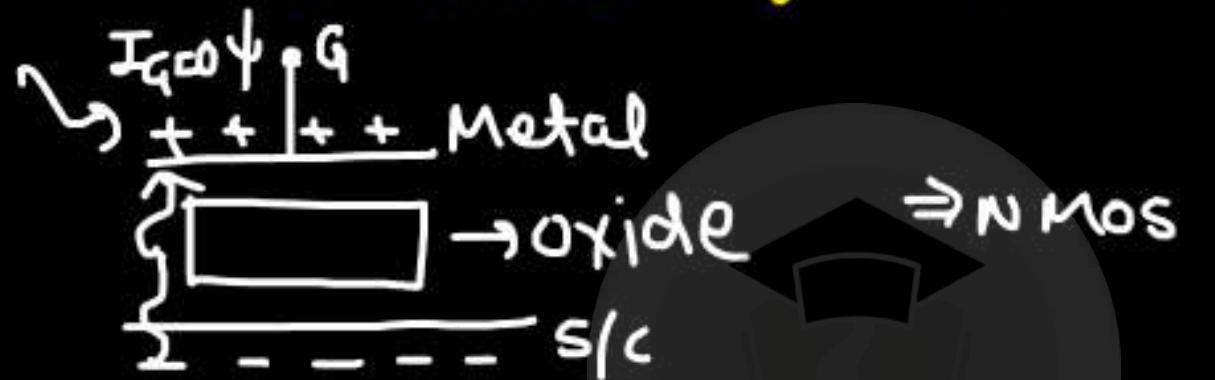


PrepFusion

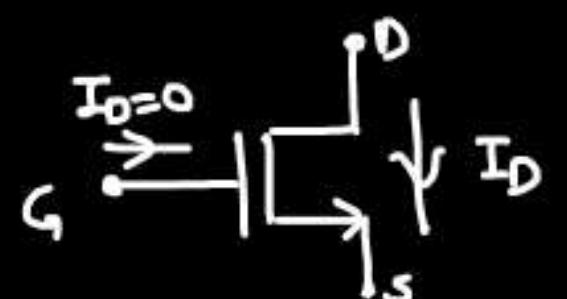Because of this oxide layer only, the e^- or the negative charge near the S/C is not reaching to the metal and we are able to frame the channel and this channel helps in generating drain current.



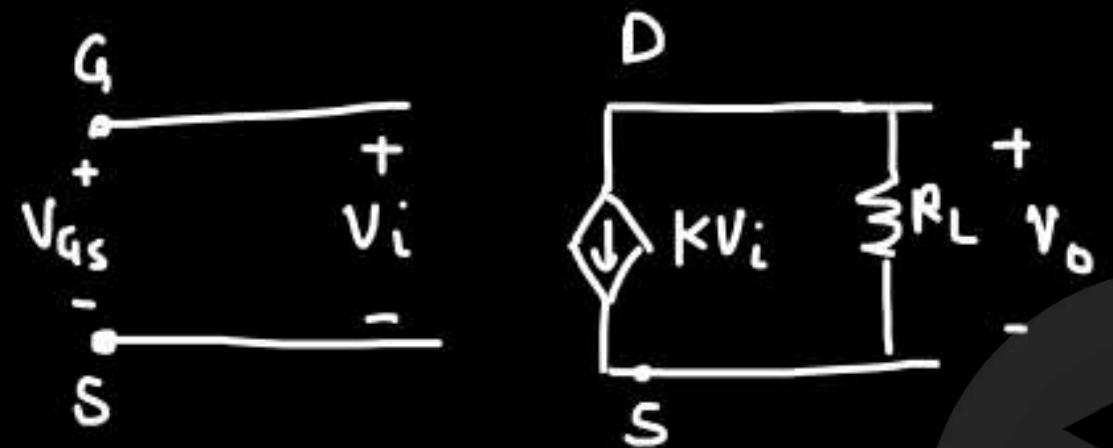Q. Why do we use MOSFET in enhancement mode for amplification?



Enhancement type MOSFETs doesn't conduct for zero i/p voltage.

PrepFusion


For conduction, $V_{gs} > V_T$

And the drain current depends on the applied i/p voltage.


Channel length Modulation (CLM) :-

Ideally, for $V_{DS} > (V_{DS})_{sat}$ \Rightarrow Current saturates

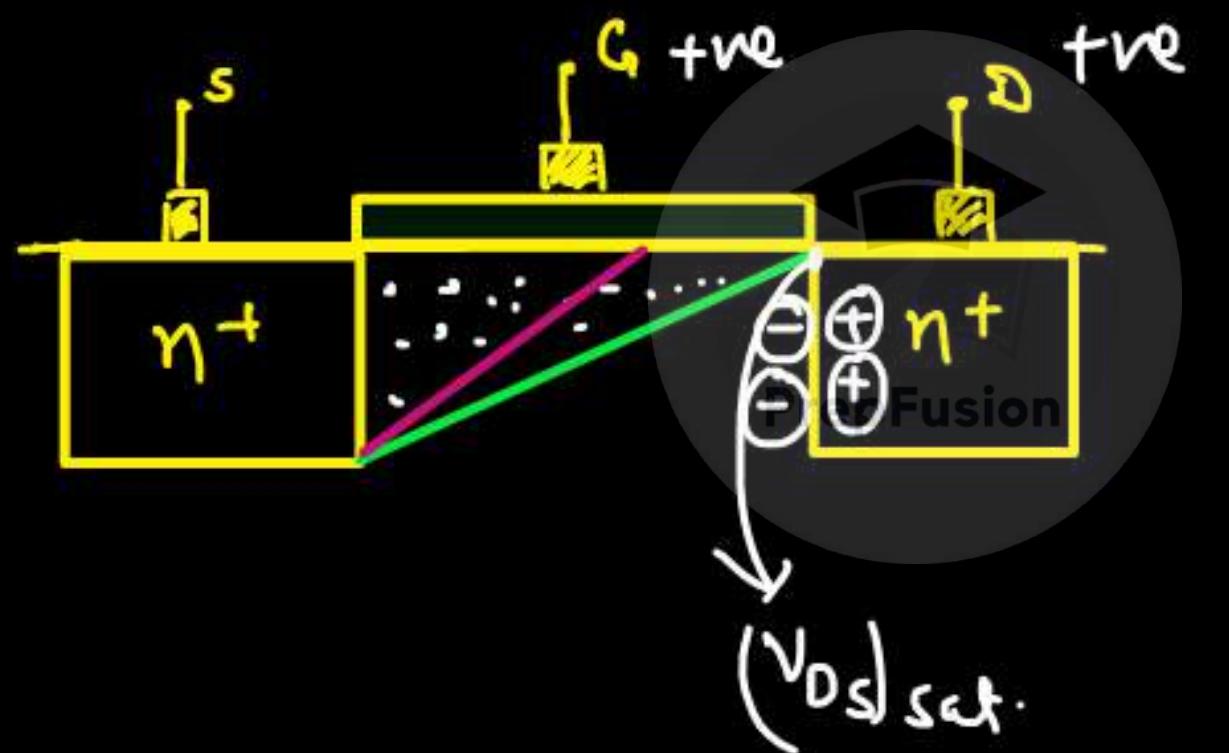Practically, for $V_{DS} > (V_{DS})_{sat}$ \Rightarrow Current rises slightly



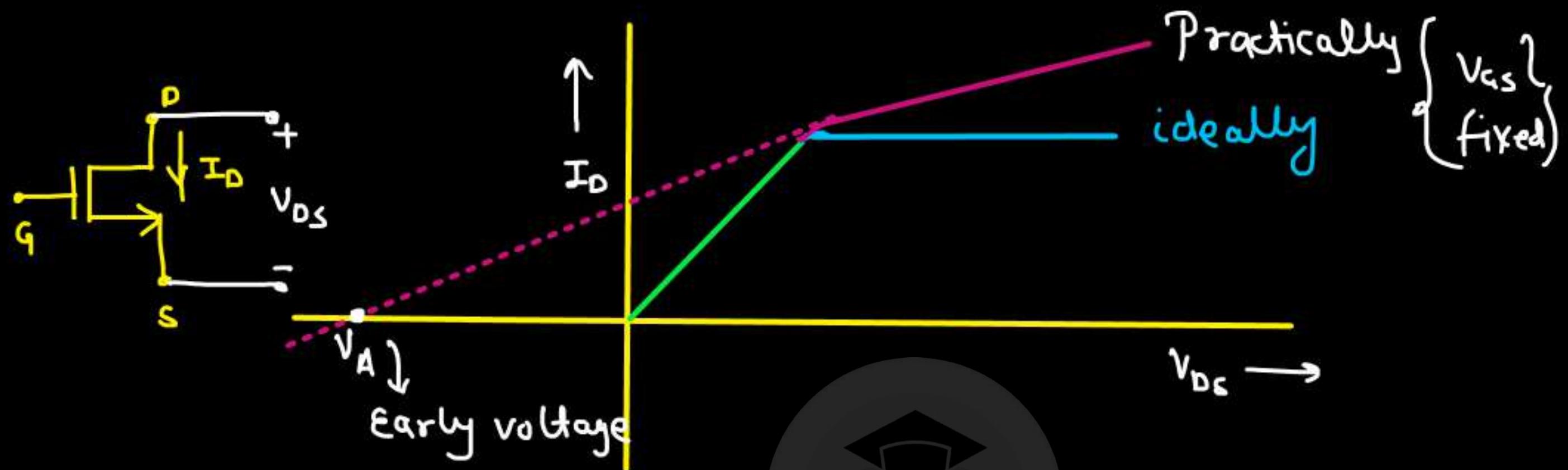$V_{DS} > (V_{DS})_{sat}$ \Rightarrow depletion width \uparrow \Rightarrow strong electric field \Rightarrow increases the current slightly.




Ideal Case:- (Saturation)


$$(I_D)_{\text{sat}} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 \rightarrow \text{constant for fixed } V_{GS} \\ (\text{Independent of } V_{DS})$$

Drain-Source ON Resistance:- (Saturation)

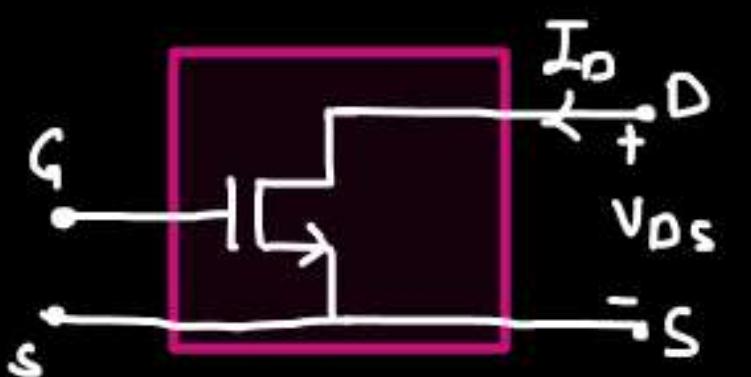
$$\frac{1}{r_{ds}} = \frac{\partial I_D}{\partial V_{DS}} = 0 \Rightarrow r_{ds} = \infty$$



Practically:-

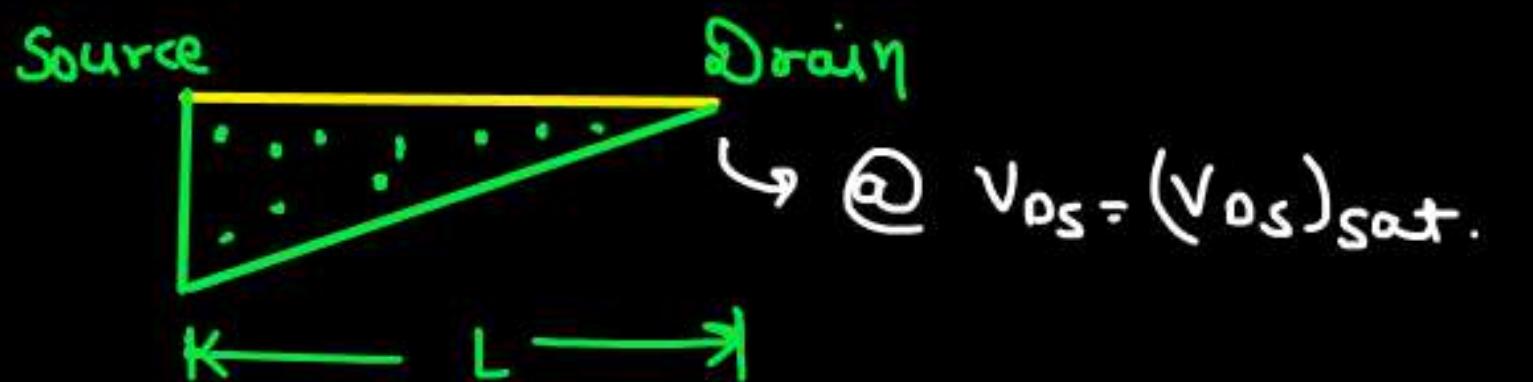

Further increasing V_{DS} :-

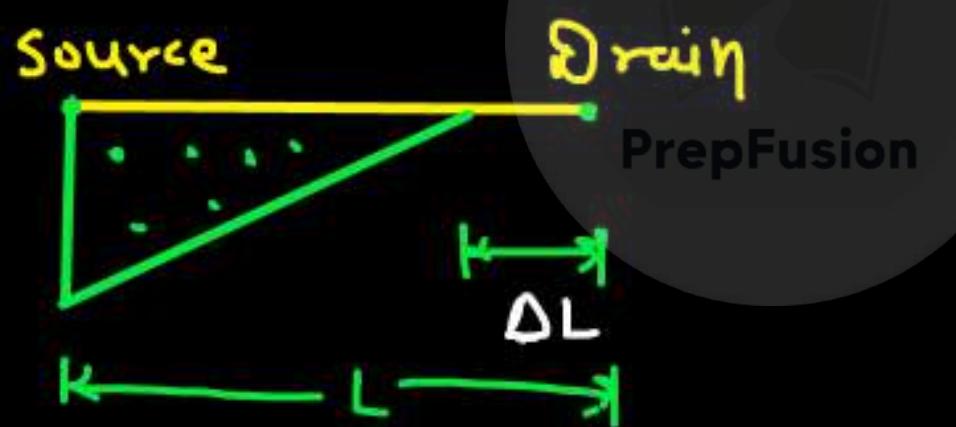

$$(I_D)_{Sat} = \frac{\mu_n C_{ox} W}{2(L - \Delta L)} (V_{GS} - V_T)^2$$

$$(I_D)_{sat} = \frac{\mu_n C_{ox} W}{2(L - \Delta L)} (V_{GS} - V_T)^2$$

$$= \frac{\mu_n C_{ox} W}{2L \left[1 - \frac{\Delta L}{L} \right]} (V_{GS} - V_T)^2$$

$$= \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 \left[1 - \frac{\Delta L}{L} \right]^{-1}$$

PrepFusion

$$\left[(I_D)_{sat} \right]_{CLM} \sim \left[(I_D)_{sat} \right]_{ideal} \left[1 + \frac{\Delta L}{L} \right] - \textcircled{2} \quad \left\{ \begin{array}{l} (1-x)^{-1} \\ = 1+x \end{array} \right\}$$

$$\Rightarrow \frac{\Delta L}{L} \propto V_{DS}$$

$$\Rightarrow \frac{\Delta L}{L} = \lambda V_{DS} \quad - \textcircled{2}$$



$$[(I_D)_{sat.}]_{CLM} = \underbrace{[(I_D)_{sat.}]_{ideal}}_{\lambda} [1 + \lambda V_{DS}]$$

$\lambda \rightarrow$ process technology
parameter
(V⁻¹)

Drain - Source ON resistance [Saturation] [CLM is present] :-

PreFusion

$$r_{ds} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda [(I_D)_{sat.}]_{ideal}}$$

if $\lambda = 0 \Rightarrow$ NO CLM $\Rightarrow r_0 = \infty$
ideal case

Early voltage -

$$[(I_D)_{sat}]_{CLM} = [(I_D)_{sat}]_{ideal} [1 + \lambda V_{DS}]$$

$$= 0$$

$$\Rightarrow 1 + \lambda V_{DS} = 0$$

$$V_{DS} = -\frac{1}{\lambda}$$

PrepFusion

⇒ The value of V_{DS} @ which the drain current becomes zero,
That is known as early voltage.


$$V_A = \frac{1}{\lambda}$$



Body Effect:-

Threshold voltage
of NMOS
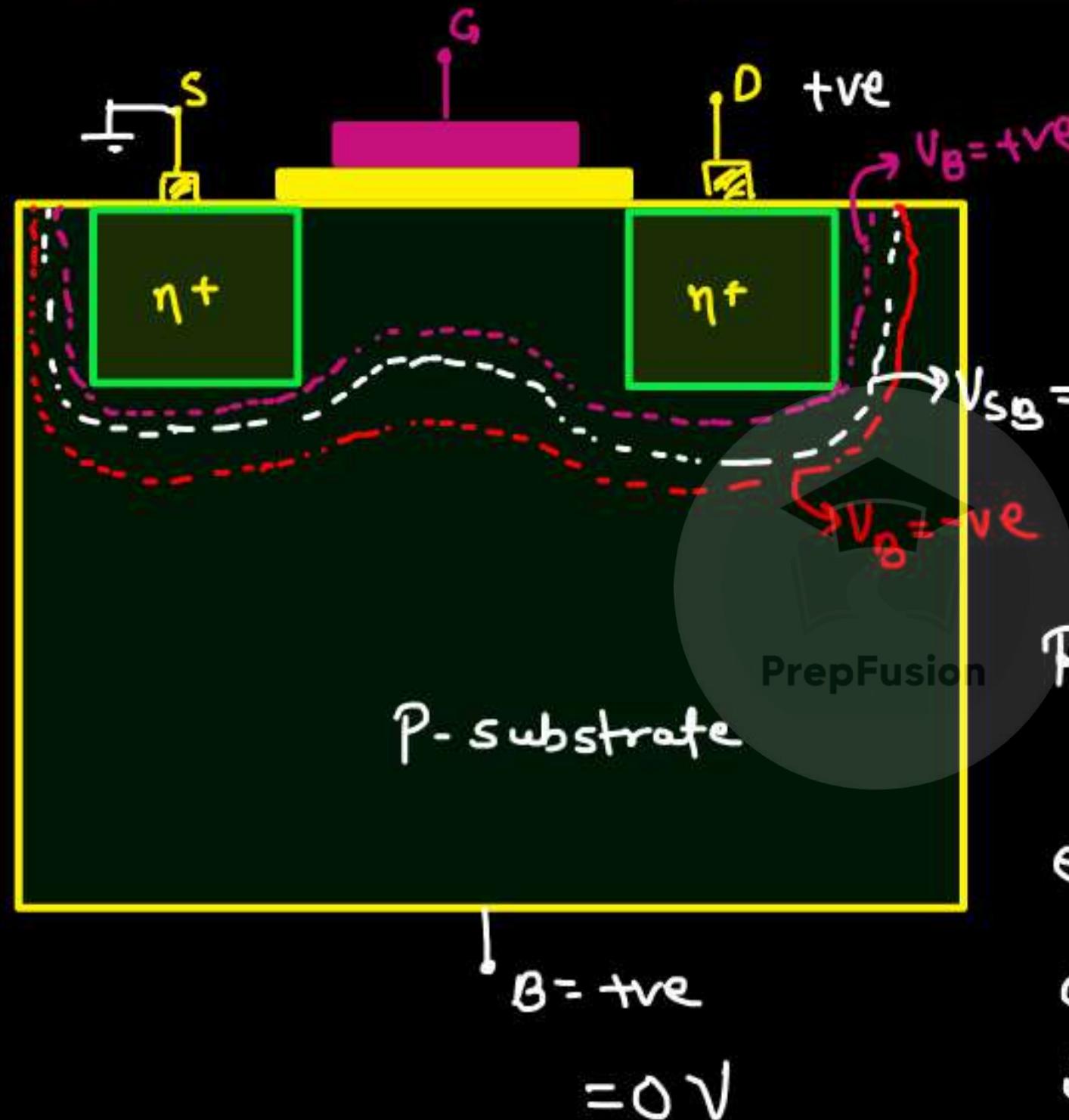
$$V_T = V_{TO} + \gamma [\sqrt{2\Phi_f + V_{SG}} - \sqrt{2\Phi_f}]$$



① $V_{SB} = 0$

⇒ NO change in
Threshold voltage.

② $V_{SB} = +ve ; V_B = -ve$

Reverse bias @ source side ①



e^- from source will feel High
electric field pushing them back
into the source terminal



Higher V_G required $\Rightarrow V_T \uparrow$

$$③ V_{SB} = -ve, \quad V_B = +ve$$




Forward bias Towards source side ↑



Source can supply more electrons @ lower V_G



$$V_T \downarrow$$

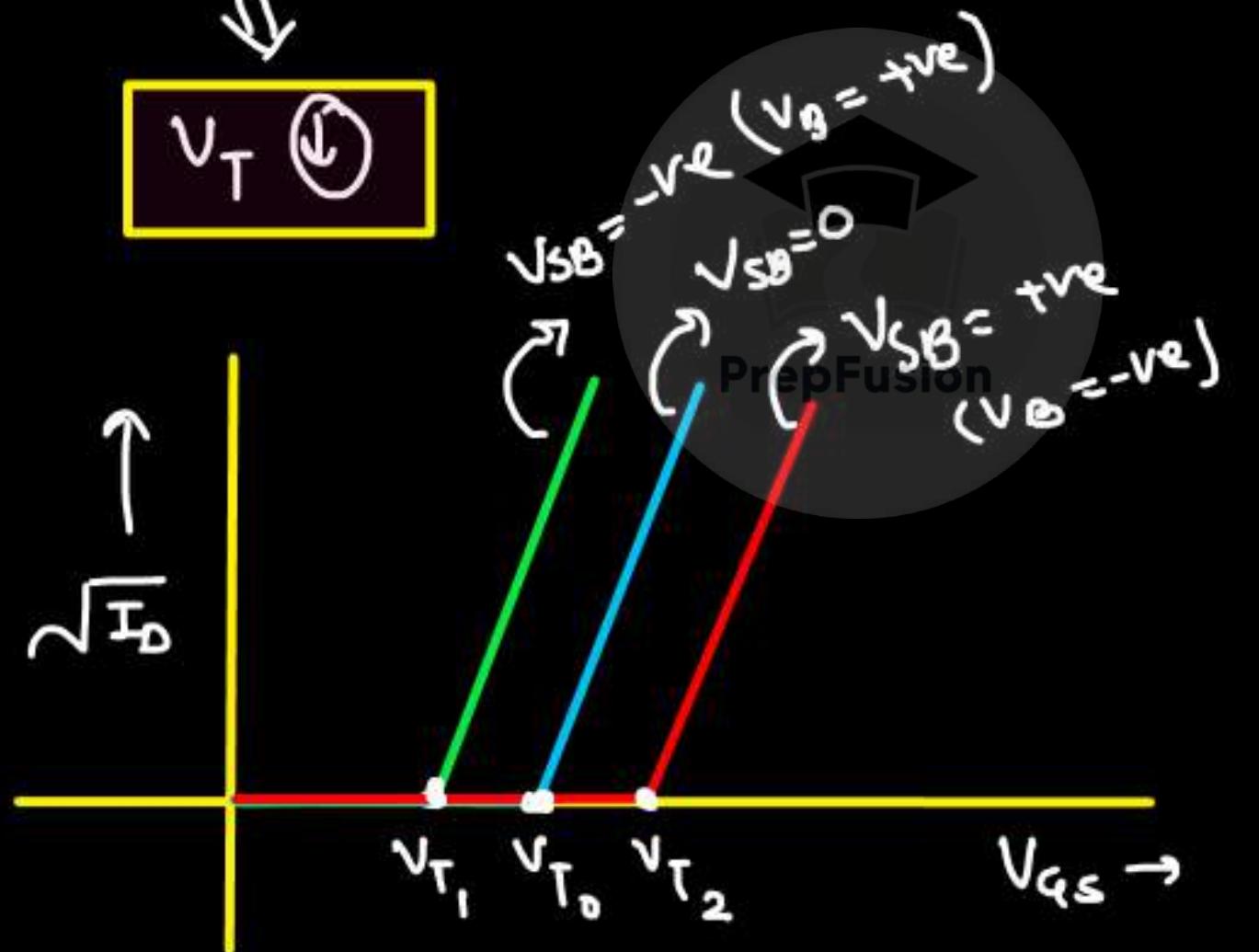

(i) $V_{SG} = +ve, V_B = -ve \Rightarrow V_T \uparrow$ (NOT Desirable)

(ii) $V_{SG} = -ve, V_B = +ve \Rightarrow$ Unwanted power consumption
(NOT Desirable)




⇒ We always try to keep $V_{SG}=0V$; Source- Body shorted

{ or at least source to body }
diode should be reverse
biased

Assignment - 4

Q.

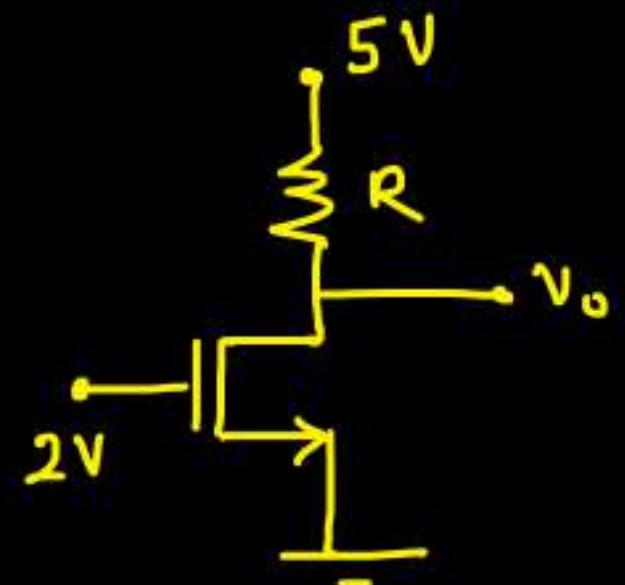

$$w/L = 10$$


$$\mu_n C_{ox} = 200 \mu A/V^2$$

$$V_T = 1V$$

PrepFusion
Find $v_o = ?$

(i) $R = 1K\Omega$

(ii) $R = 4.5K\Omega$

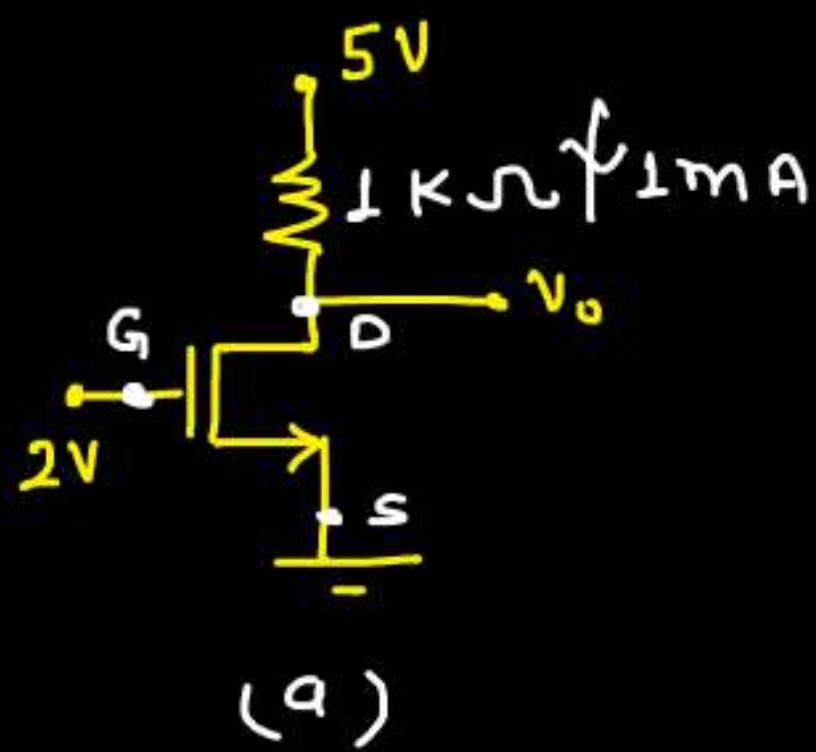

$$V_{GS} = 2 \text{ V}$$

$$V_{DS} = V_0$$

$$V_T = 1 \text{ V}$$

het, Mos is working in sat. region

$$I_D = \frac{\mu_n C_o x W}{2L} (V_{GS} - V_T)^2$$

PrepFusion
 $= \frac{200 \mu \times 10}{2} (2 - 1)^2$

$I_D = 1 \text{ mA}$

$V_0 = 5 - 1 \text{ k} (1 \text{ m}) = 5 - 1 = 4 \text{ V}$

$$V_{GS} = 2V, \quad V_T = 1V, \quad V_{DS} = V_{GS} - V_T \\ = 2 - 1 = 1V$$

$$V_{DS} = 4V$$

Here, $V_{DS} > V_{GS} - V_T$

OR


$$V_{DS} > V_{OV} \Rightarrow \text{MOS is in sat.}$$

PrepFusion

Assumption correct ✓



$$V_o = 4V$$

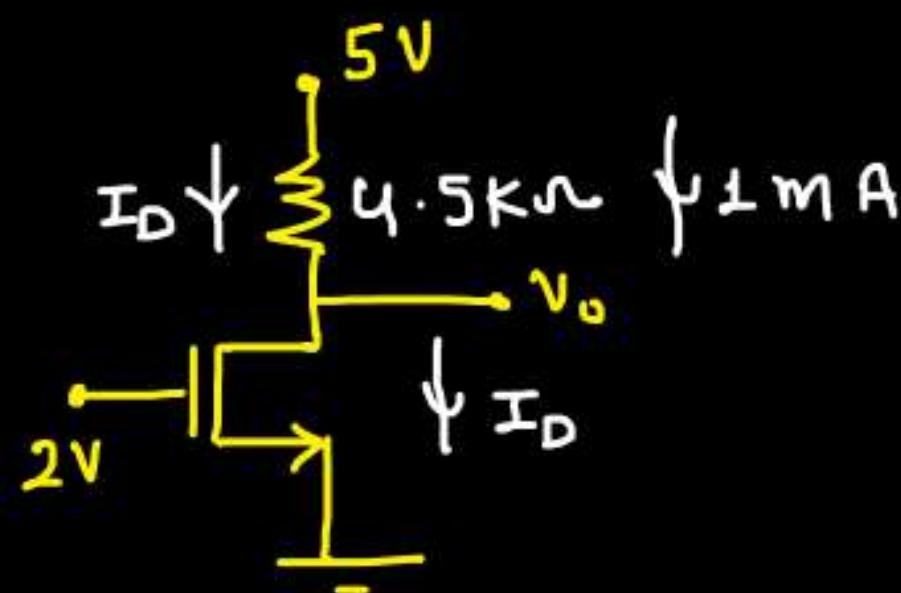

Assuming, Sat. region

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$= \frac{200 \mu \times 20}{2} (2 - 1)^2$$

$I_D = 1 \text{ mA}$



$V_o = 5 - 4.5 \text{ k}(\text{lm})$

$V_o = 0.5 \text{ V}$



Now, $V_{DS} = V_o = 0.5 \text{ V}$

$V_{GS} - V_T = 2 - 1 = 1 \text{ V}$

Here, $V_{DS} < V_{GS} - V_T \rightarrow$ linear region

Assumption wrong

Assuming, linear region;

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{5 - V_D}{4.5K} = \underbrace{200 \mu A \times 10}_{2m} \left[1 \times V_D - \frac{V_D^2}{2} \right]$$

$$5 - V_D = 2 \left[V_D - \frac{V_D^2}{2} \right]$$

$$4.5V_D^2 - 10V_D + 5 = 0$$

$$V_D = \frac{10 \pm \sqrt{100 - 90}}{9}$$

$$\swarrow \searrow$$

$$1.46V \quad 0.76V$$

$$V_D \rightarrow 1.46 V$$

$$V_D \rightarrow 0.76 V$$

Let, $V_D = 1.4 V = V_{DS}$

$$V_{GS} - V_T = 1 V$$

Here $V_{DS} > V_{GS} - V_T$

\Rightarrow Sat.



$$V_D = 0.76 V = V_{DS}$$


$$V_{GS} - V_T = 1 V$$

$$V_{DS} < V_{GS} - V_T$$

\Rightarrow Linear



Assumption correct

$V_D = 0.76 V$

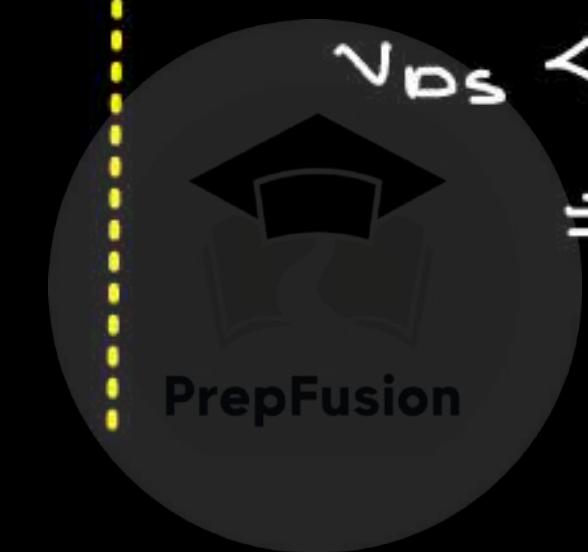


Q. Given, $\mu_n C_{ox} = 100 \mu A/V^2$, $w/l = 1$, $V_T = 1V$

Find region of operation.

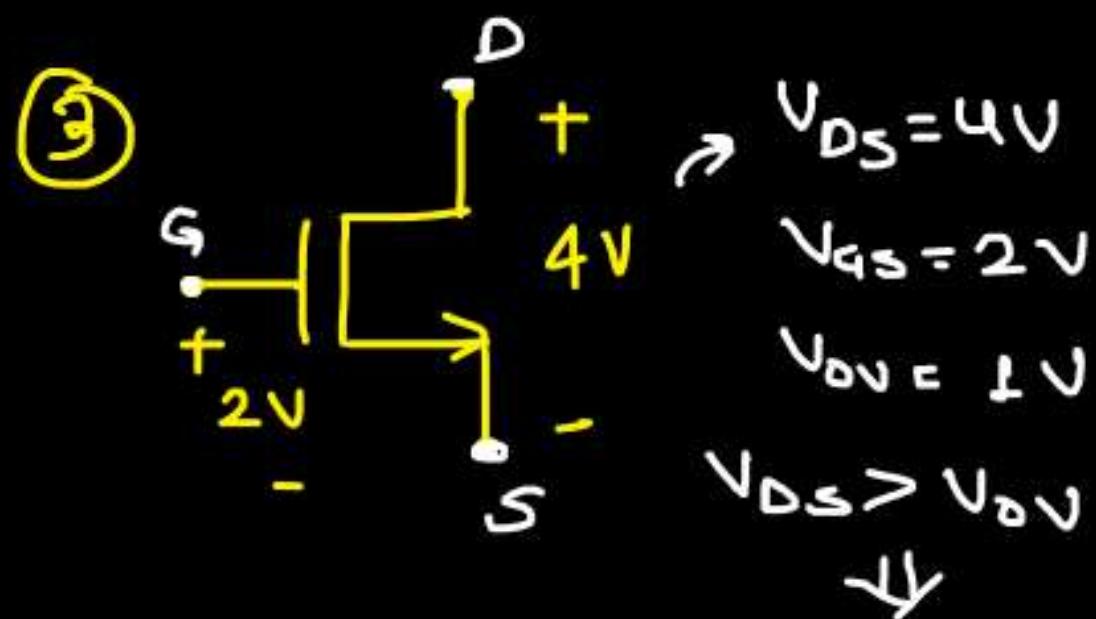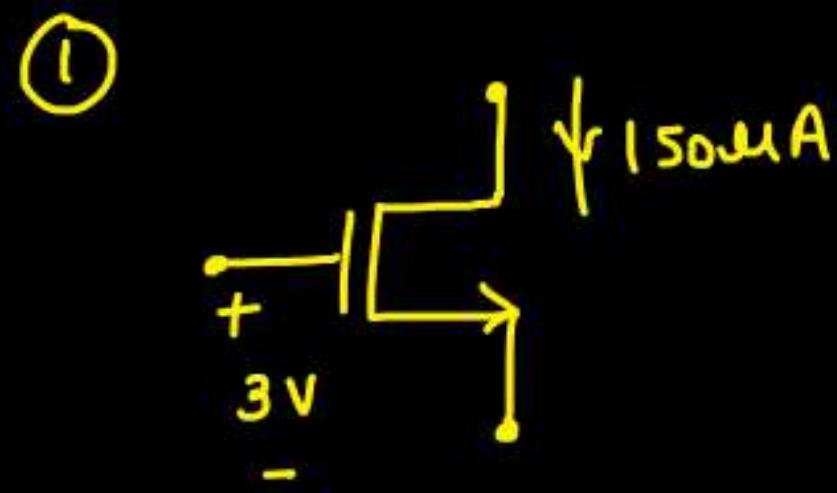


Sat. region

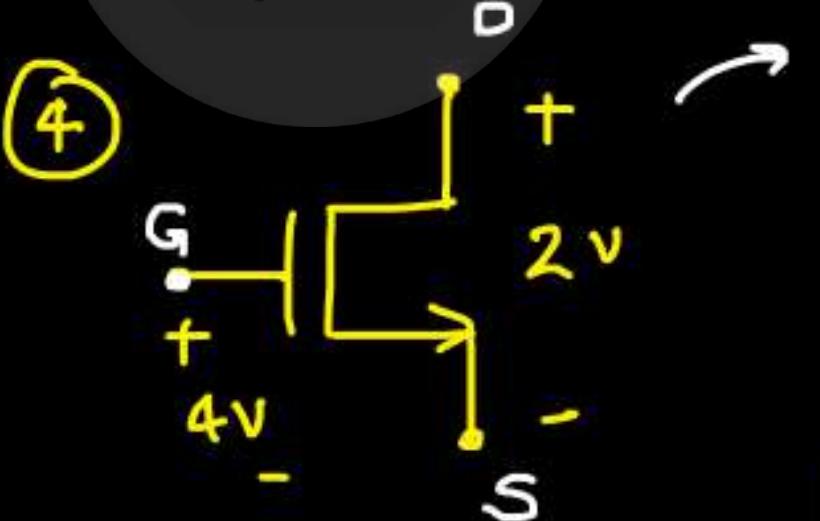


$V_{DS} = 2V$
 $V_{OV} = 3V$
 $V_{DS} < V_{OV}$

Linear region

5

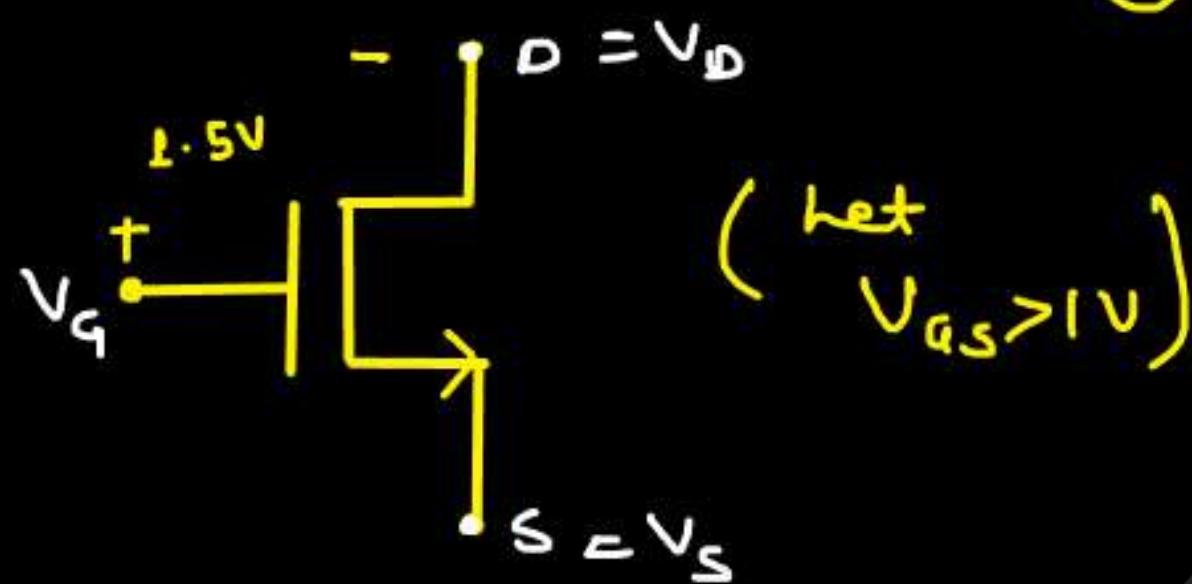

6

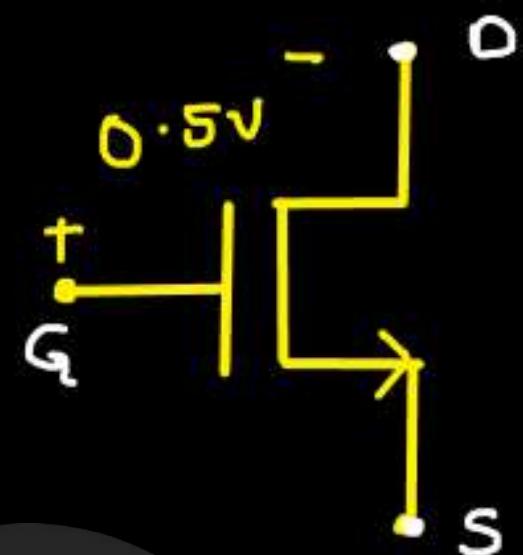

$$V_{DS} = V_D - V_S$$

$$V_{GS} = V_G - V_S$$

$$= V_D + 1.5 - V_S$$

$$V_{GS} = 1.5 + V_{DS}$$

$$V_T = 1V$$

$$V_{OV} = 0.5 + V_{DS}$$

$V_{DS} < V_{OV}$ \Rightarrow linear region



$$V_{DS} = V_D - V_S$$


$$V_{GS} = V_D + 0.5 - V_S$$

$$V_{GS} = V_{DS} + 0.5$$

$$V_T = 1V$$

$$V_{OV} = V_{DS} - 0.5$$

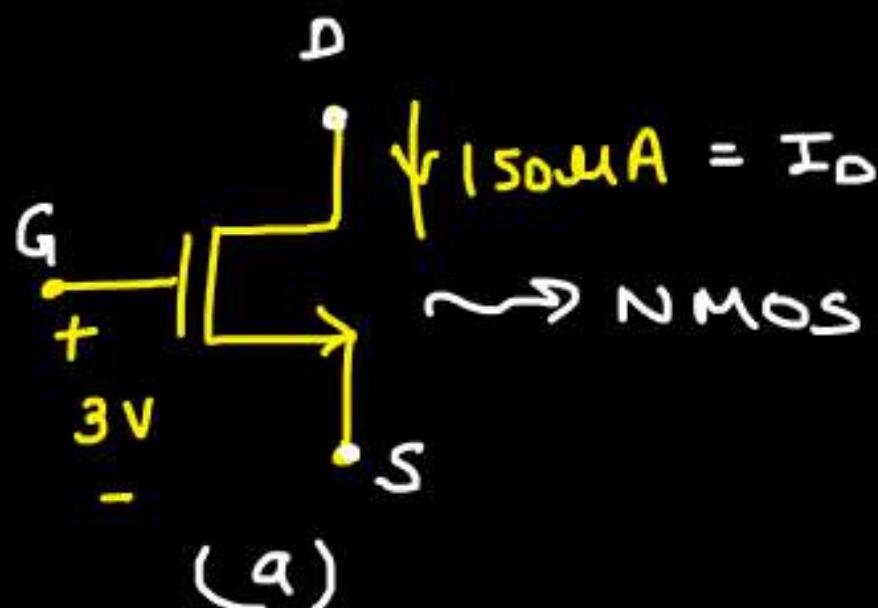$V_{DS} > V_{OV} \Rightarrow$ Sat. region =




$$V_{GS} = 3 \text{ V}$$

$$V_T = 1 \text{ V}$$

$$I_D = 150 \mu\text{Amp.}$$

het MOS is in sat. region

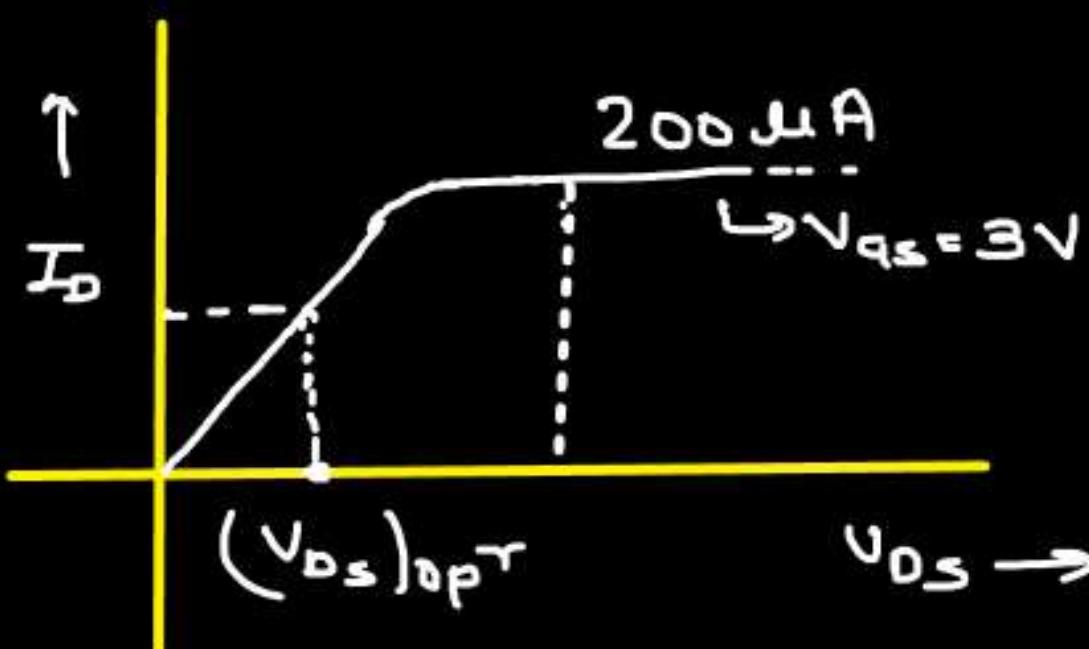


$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

PrepFusion

$$= \frac{150 \mu\text{A} \times 10}{2} (3 - 1)^2$$

$$I_D = 200 \mu\text{A}$$

↙
MOS is not in sat. but in **linear**

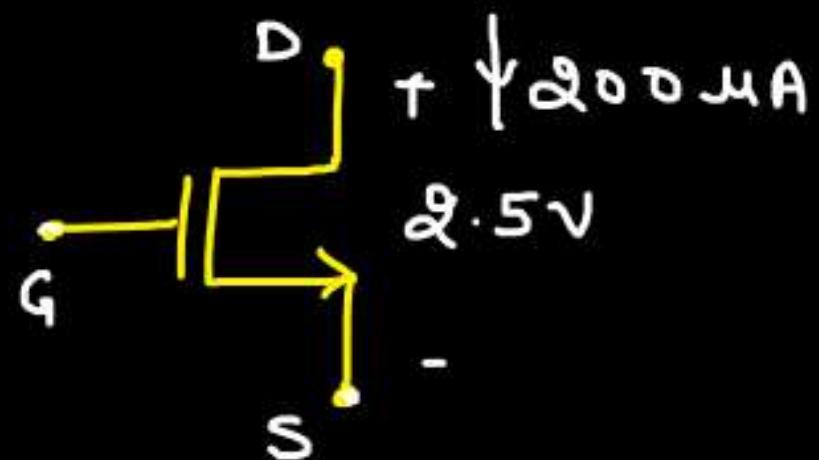

het, sat. region

$$I_D = \frac{4nC_{ox}W}{2L} (V_{GS} - V_T)^2$$

$$200\mu A = \frac{100\mu A \times 1}{2} (V_{GS} - 1)^2$$


Prepuision
 $V_{GS} = 3 V$

$$V_{DS} = 2.5 V$$

$$V_{OV} = 3 - 1 = 2 V$$

Here $V_{DS} > V_{OV} \Rightarrow$ sat. region \Rightarrow Assumption ~~✓~~

Q.

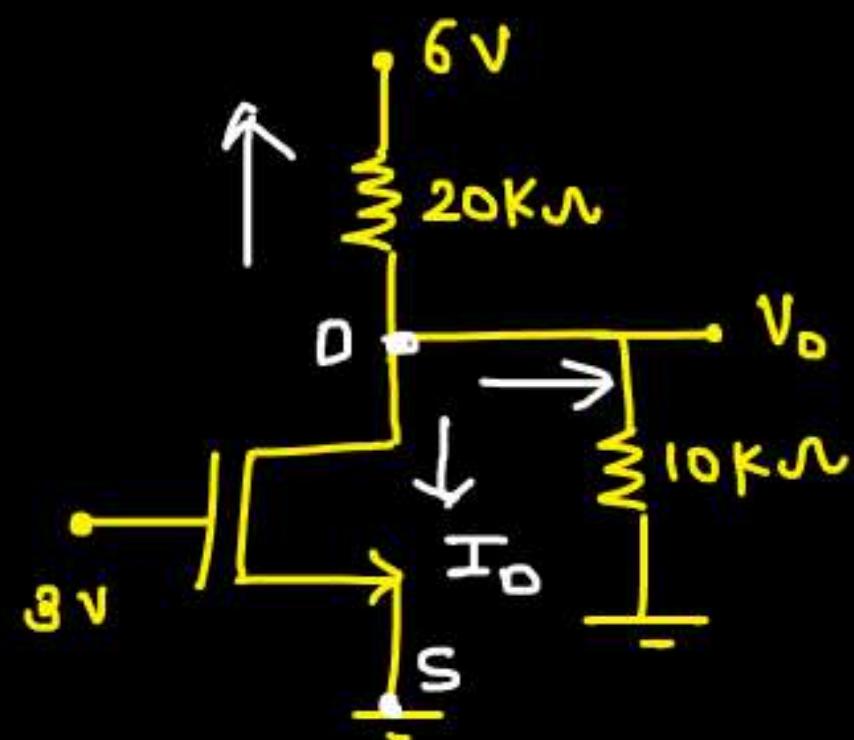

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$w/l = 1$$

$$V_T = 1V$$

find $V_o = ?$

$$V_{DS} = V_o$$

find drain current of MOS.

KCL @ node V_o



$$I_D + \frac{V_o}{10k} + \frac{V_o - 6}{20k} = 0$$

PrepFusion

$$I_D = \frac{6 - V_o}{20k} - \frac{V_o}{10k} \rightarrow \textcircled{1}$$

Let, MOS is in sat.

$$I_D = \frac{100 \mu}{2} (3-1)^2$$

$$I_D = 200 \mu A$$



$$200 \mu = \frac{6 - V_o}{20k} - \frac{V_o}{10k}$$



$$4 = 6 - V_o - 2V_o$$

$$V_o = \frac{2}{3} = 0.67V$$



$$V_{DS} = V_{GS} - V_T = 2V$$

$V_o = V_{DS} < V_{DS} \Rightarrow$ linear region \Rightarrow assumption X

Assuming, MOS in linear region

$$I_D = \frac{\mu_n C_{ox} w}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{6 - V_o}{20k} - \frac{V_o}{10k} = 100 \times 1 \left[2V_o - \frac{V_o^2}{2} \right]$$

$$6 - V_o - 2V_o = 2 \left[2V_o - \frac{V_o^2}{2} \right]$$

$$6 - 3V_o = 4V_o - V_o^2$$

$$V_o^2 - 7V_o + 6 = 0$$

$$\Rightarrow V_o \rightarrow 1V$$

$$\Rightarrow V_o \rightarrow 6V$$

if $V_o = 1V$

$$V_{DS} = 2V$$

$$V_{DS} < V_{DS}$$

\Rightarrow Linear region

$$\boxed{V_o = 1V}$$

if $V_o = 6V$

$$V_{DS} = 2V$$


$$V_{DS} > V_{DS}$$

\downarrow

Sat.

\times

Q.

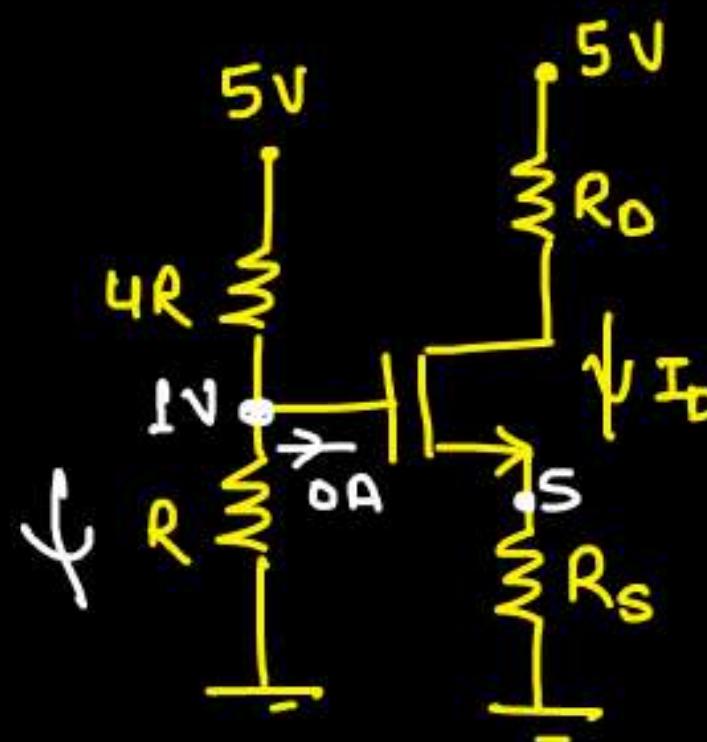

find R_S such that MOS works in saturation region.

Given

$$I_D = 119 \mu A \text{mp} , V_T = 0.5V$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = 4.12 \text{ ms/V}$$

$$V_G = 1V$$

$$V_S = I_D R_S$$

$$V_{GS} = 1 - I_D R_S$$

$$V_T = 0.5V$$


$$I_D = K_n (V_{GS} - V_T)^2$$

$$119\mu = 4.12m (1 - 119\mu \times R_S - 0.5)^2$$

$$0.17 = 0.5 - 119\mu \times R_S$$

$$\Rightarrow R_S = 2.71 \text{ k}\Omega$$

Q.

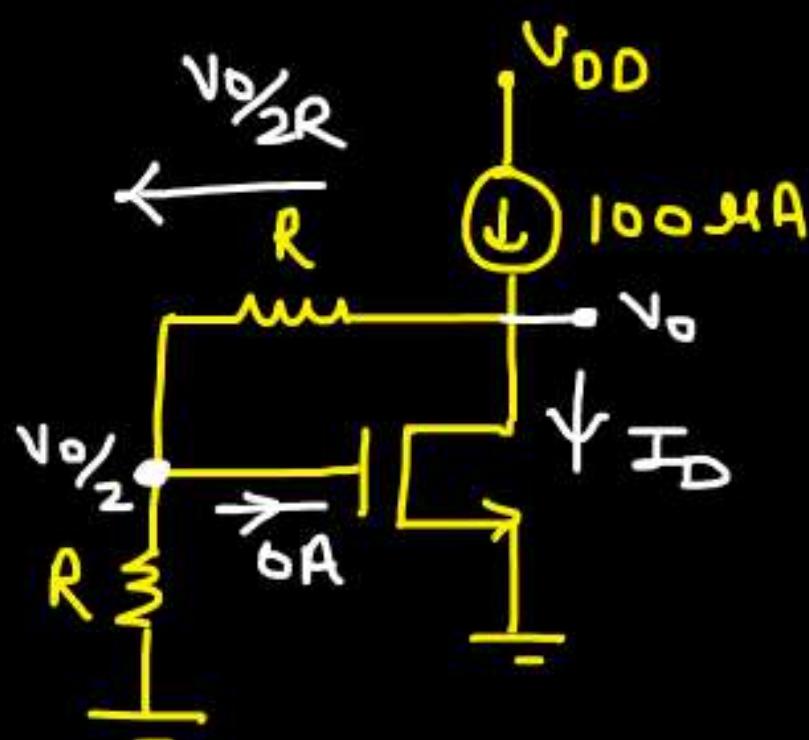

$$\frac{m_{nCOX} W}{L} = 100 \mu\text{s}/\text{V}$$

$$V_T = 1\text{V}, R = 40\text{k}\Omega$$

Find bias current in Transistor.

$$V_{DS} = V_D$$

$$V_{GS} = V_D/2$$

$$V_T = 1\text{V}$$

PrepFusion

$$100\mu\text{A} = \frac{V_D}{2R} + I_D$$

$$I_D = 100\mu\text{A} - \frac{V_D}{80\text{k}}$$

$$I_D = 100\mu\text{A} - \frac{1000}{80} V_D \times \mu$$

$$I_D = 100\mu - 12.5V_o \mu \text{ A}$$

Let, MOS in sat,

$$I_D = \frac{100\mu}{2} \left(\frac{V_o}{2} - 1 \right)^2$$

$$100\mu - 12.5\mu V_o = 50\mu \left(\frac{V_o}{2} - 1 \right)^2$$

$$100 - 12.5V_o = 50 \left(\frac{V_o^2}{4} + 1 - V_o \right)$$

$$100 - 12.5V_o = 12.5V_o^2 + 50 - 50V_o$$

$$12.5V_o^2 - 37.5V_o - 50 = 0$$

$$V_o^2 - 3V_o - 4 = 0$$

$$\begin{aligned} &\rightarrow V_o = 4V \\ &\rightarrow V_o = -1V \end{aligned}$$

Let $V_D = -V_U = V_{DS} \Rightarrow$ MOS goes into cut-off

Check:-


MOS cut-off

$$I_D = 0 \text{ Amp.}$$

$$\frac{V_o}{2R} = 100 \text{ mV}$$

$$V_D = 8V, V_{GS} = 4V$$

$$V_{DV} = \frac{V_D}{2} - V_T = 3V$$

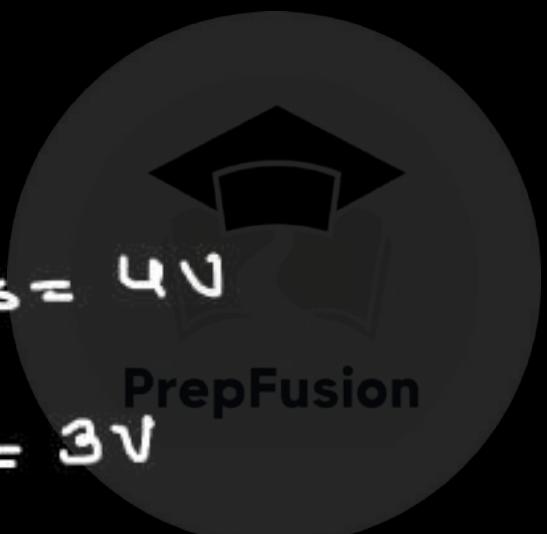

$V_D > V_{DV}$
also $V_{GS} > V_T$
also $V_{DS} > 0V$

$\left. \begin{array}{l} \\ \\ \end{array} \right\} \Rightarrow$ MOS goes into sat.
(Can't be cut-off)

if $V_D = 4V$

$$V_{DS} = 4V$$

$$V_{GS} = 2V$$

$$V_T = 1V$$

$$V_{OV} \approx 1V$$

$\Rightarrow V_{DS} > V_{OV} \Rightarrow$ Sat. region \Rightarrow Assumption ✓


$V_D = 4V$ PrepFusion

$$I_D = 100\mu A = 12.5\mu A \times 4$$

∴ $I_D = 50\mu A$

Biasing:-

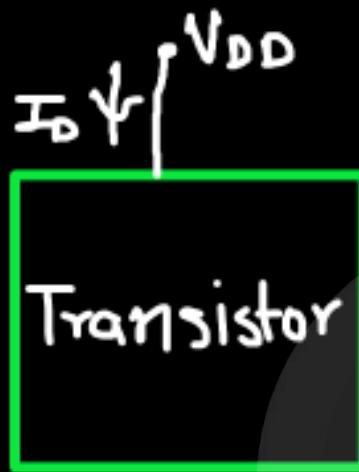The process of setting a transistors DC operating voltage or current conditions to the correct level so that any AC input signal can be amplified correctly by the transistor.



Why biasing is required ?

↳ Why we needed MOSFET:-




* Let I don't apply an dc bias to my Amplifier
and directly give small signal ac voltage.



$$\text{max} = 20\text{mV}$$

$$\text{min} = -20\text{mV}$$

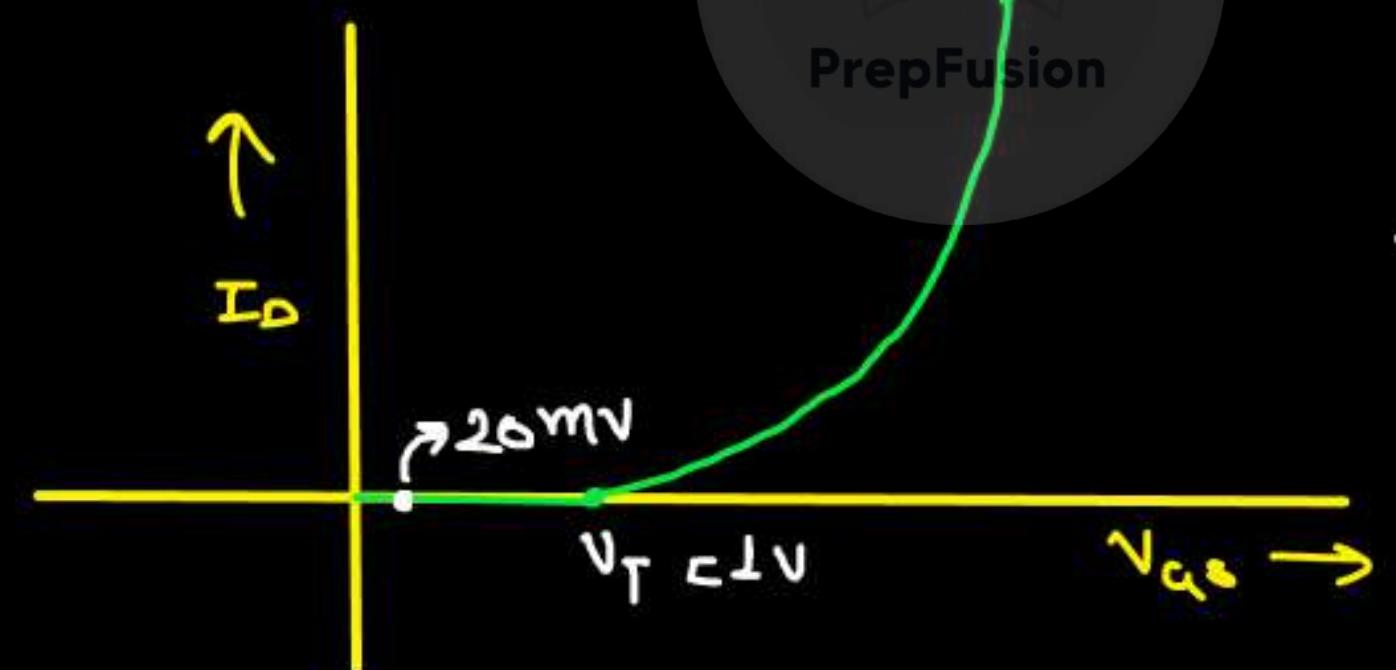


\Rightarrow Transistor doesn't even turn on.

So, to make sure that the transistor is always in "ON condition", we give some dc bias to the MOS and apply small signal voltage (20mV, 10mV, 40mV) on it.

$$\Rightarrow V_{GS} = V_{GG} + V_i$$


$$V_{GS} = 2V + 20mV \sin \omega t$$

PrepFusion

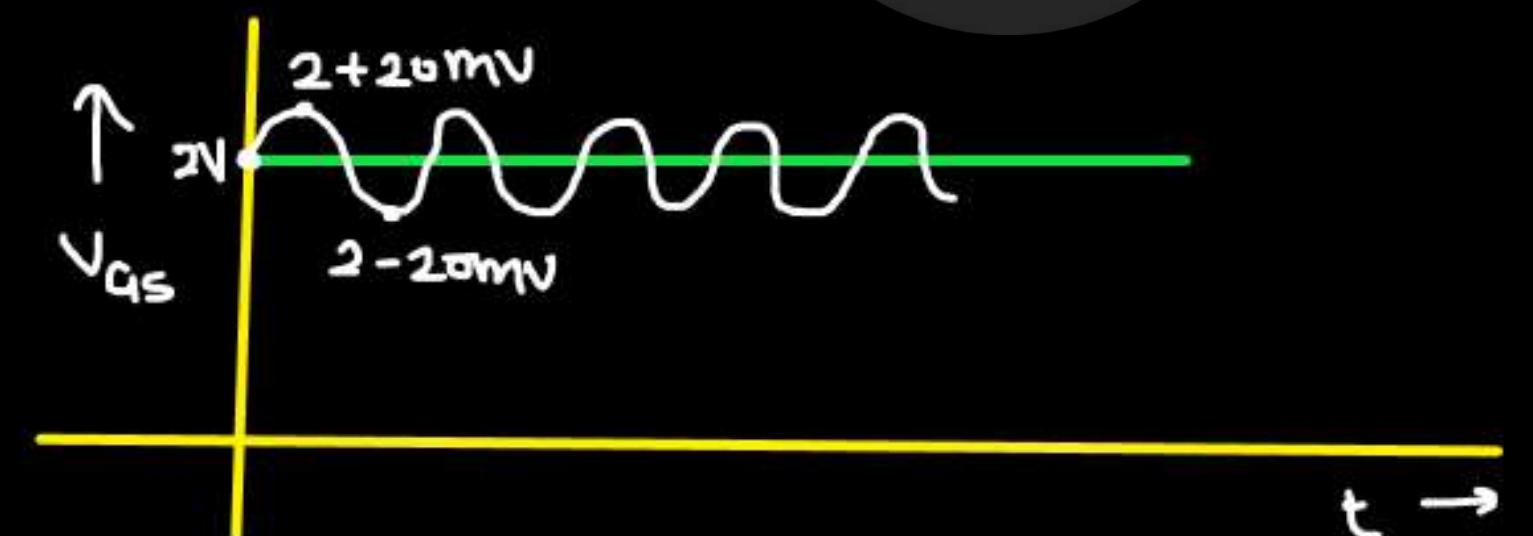

Transfer Characteristics:-

$V_{DS} < V_{DS(on)}$

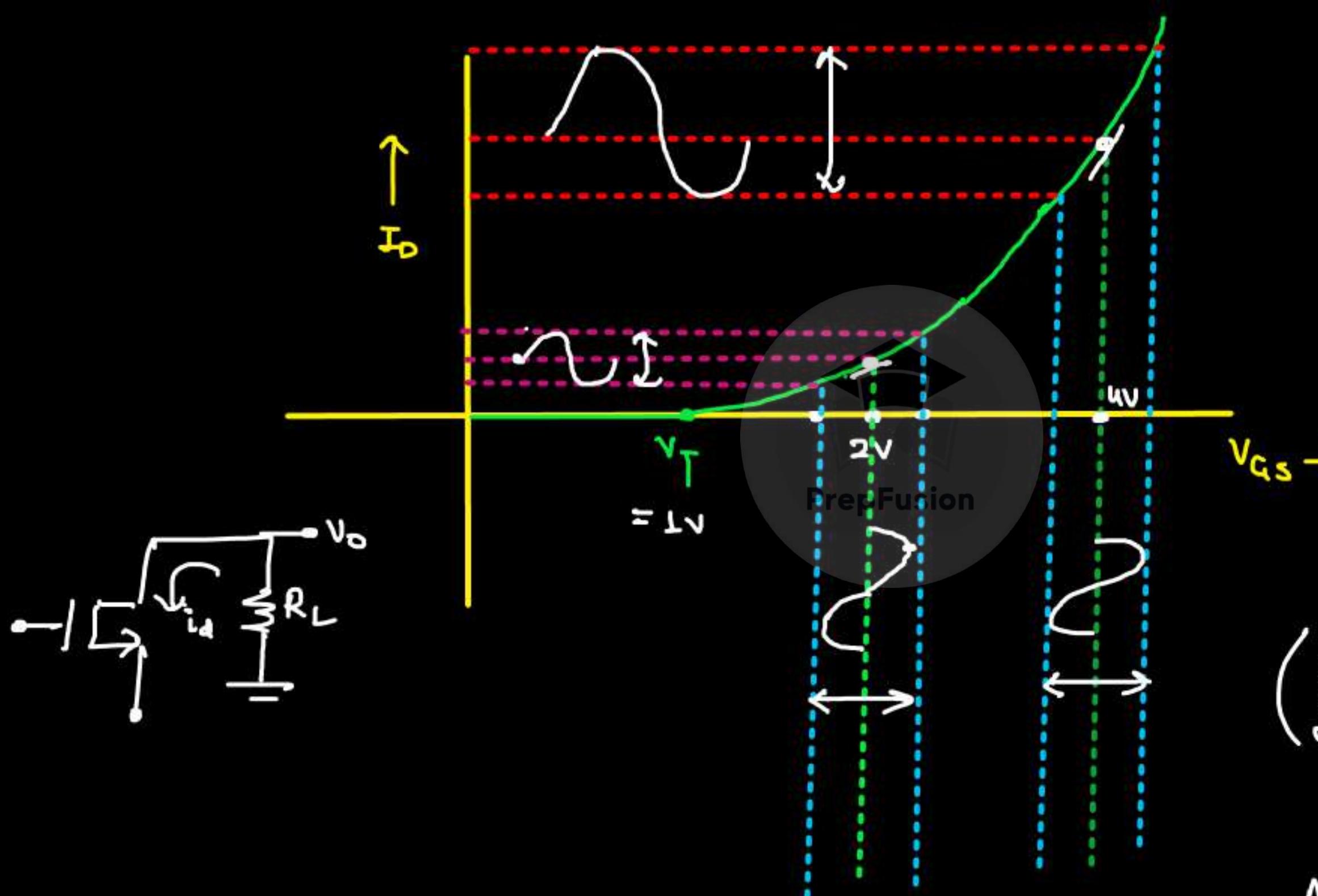

$$V_{GS_1} = 2 + V_i$$

$$V_{GS_2} = 4 + V_i$$

$$\left(\frac{\partial I_D}{\partial V_{GS}} \right)_{V_{GS_2}} > \left(\frac{\partial I_D}{\partial V_{GS}} \right)_{V_{GS_1}}$$

↓
MORE GAIN

@ Higher V_{GS} , you get Higher value of $\frac{\partial I_D}{\partial V_{GS}}$

and that eventually gives more gain.

But, while using MOS as an amplifier, you can't keep V_{GS} (dc) value to be very High. Why?

- (i) More power consumption
- (ii) MOS will fall out of saturation.


Concept of Transconductance :- (g_m)



$$g_m = \frac{\partial i_{out}}{\partial V_{in}}$$

PrepFusion

considering NMOS:-

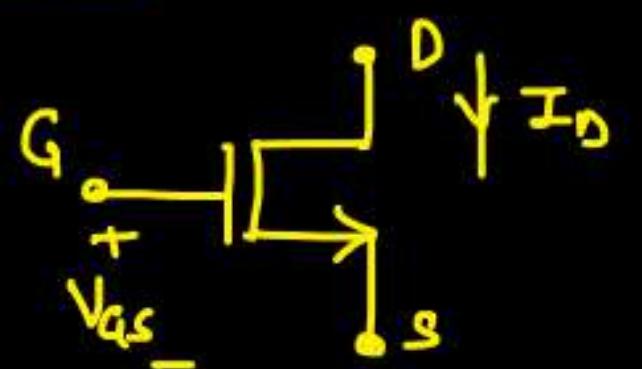

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

Transconductance for Triode region:-

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\mu_n C_{ox} W}{L} [V_{DS} - 0]$$

$$(g_m)_{\text{Triode}} = \frac{\mu_n C_{ox} W}{L} \times V_{DS}$$

Transconductance for Saturation region :-

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 \quad \text{--- (1)}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)$$

PrepFusion

→ (2)

From eqn (1)

$$\frac{\frac{\partial I_D}{\partial V_{GS}}}{V_{GS} - V_T} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T) = g_m$$

*
$$g_m = \frac{2 I_D}{V_{GS} - V_T} \quad \text{--- (3)}$$


$$I_D = \frac{\mu_n C_{ox} \omega}{2L} (V_{GS} - V_T)^2$$

2 $\frac{\mu_n C_{ox} \omega}{L} I_D = \left(\frac{\mu_n C_{ox} \omega}{L} \right)^2 (V_{GS} - V_T)^2$


$\sqrt{2 \frac{\mu_n C_{ox} \omega}{L} I_D} = \frac{\mu_n C_{ox} \omega}{L} (V_{GS} - V_T) = g_m$

$$g_m = \sqrt{2 \times \frac{\mu_n C_{ox} \omega}{L} I_D} \quad \text{--- (3)}$$

Saturation region :-

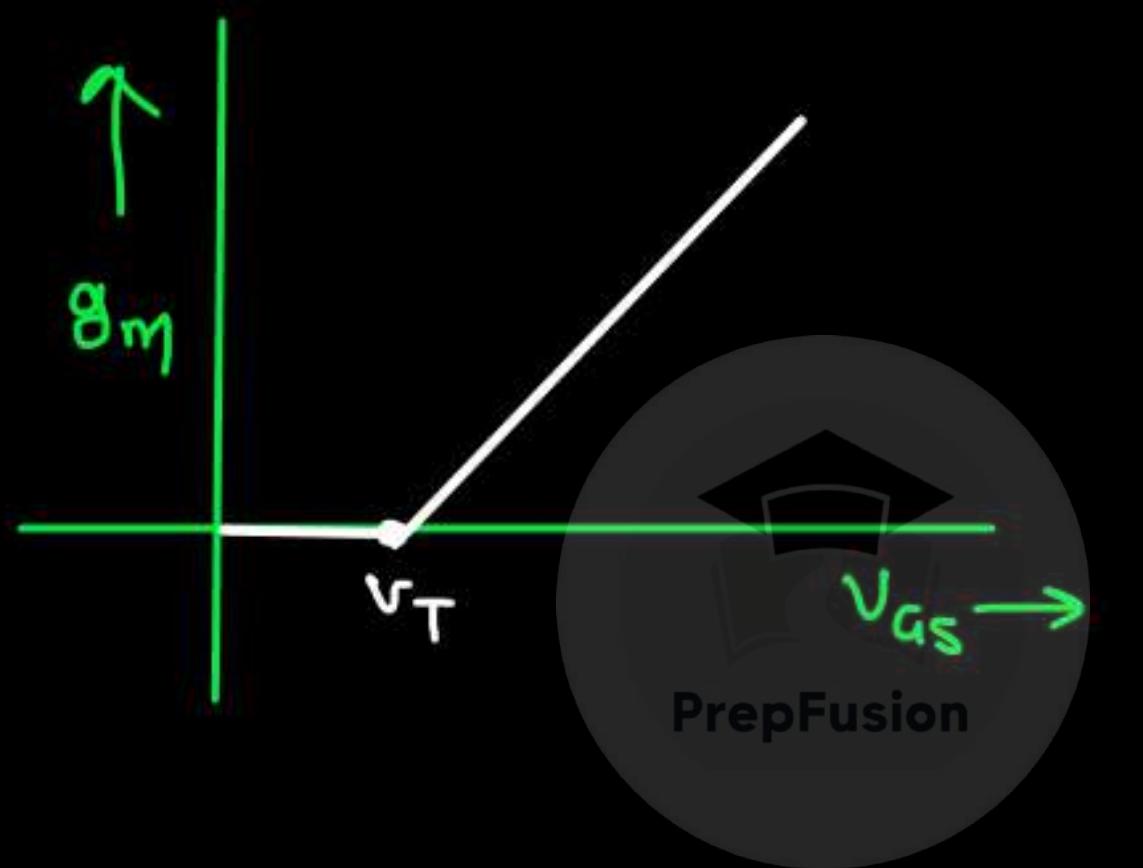

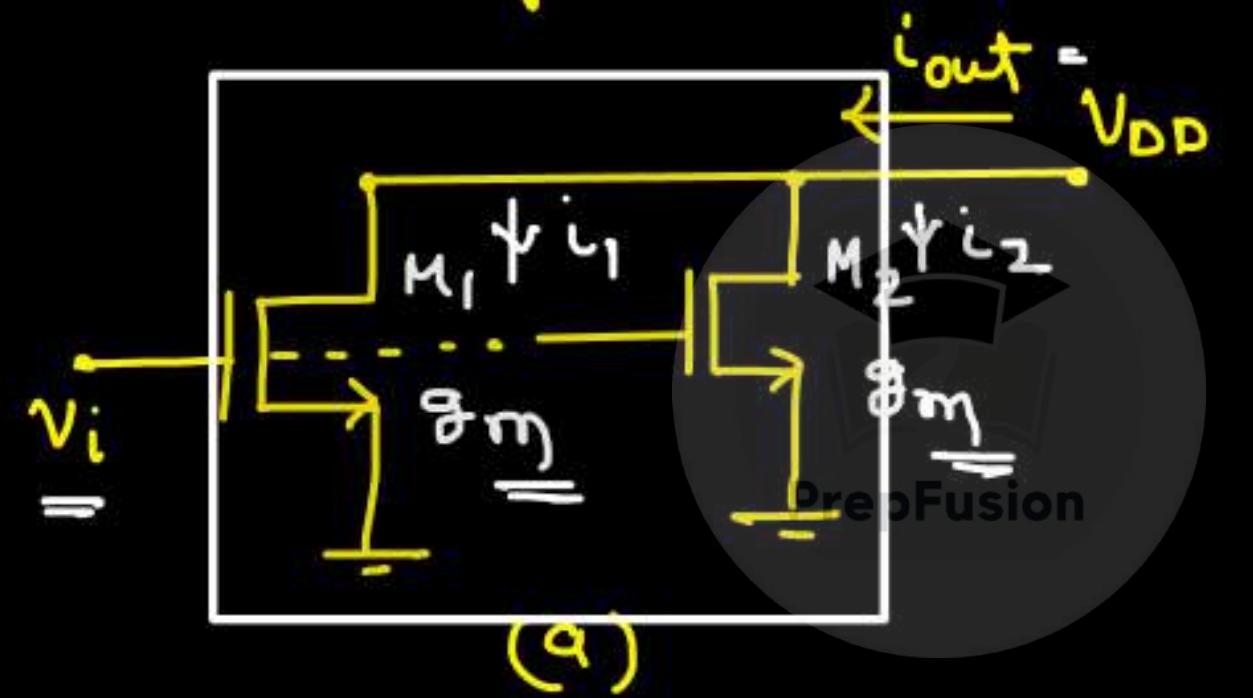- ① Find the overall Transconductance of the given fig. M_1 and M_2 are identical MOS with Transconductance g_m .



$$\Rightarrow \text{Overall Transconductance } G_m = \frac{\partial i_{out}}{\partial v_{in}}$$

For M₁,

$$g_m = \frac{\partial i_1}{\partial v_{in}}$$

For M₂

$$g_m = \frac{\partial i_2}{\partial v_{in}}$$


$$G_m = \frac{\partial i_{out}}{\partial v_{in}}$$

$$i_{out} = i_1 + i_2$$

$$G_m = \frac{\partial (i_1 + i_2)}{\partial v_{in}}$$

$$G_m = \frac{\partial i_1}{\partial v_{in}} + \frac{\partial i_2}{\partial v_{in}}$$

$G_m = 2g_m$

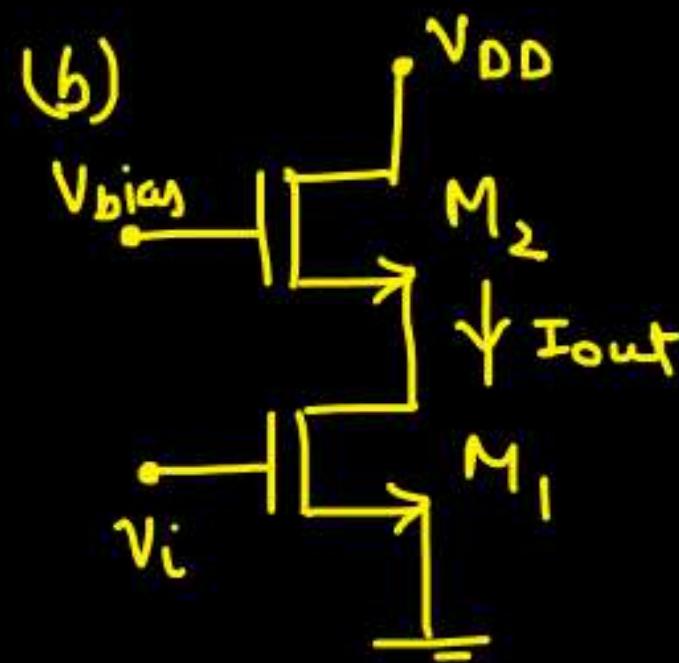

Transconductance of M_1 and M_2 is g_{m_1} and g_{m_2} respectively.



Find overall Transconductance of given ckt.

→ Overall Transconductance = $\frac{\partial I_{out}}{\partial V_{in}} = G_m$

$$g_{m_1} = \frac{\partial I_{out}}{\partial V_{in}} = G_m$$

$$G_m = g_{m_1}$$

★ O/P characteristics of MOS:-

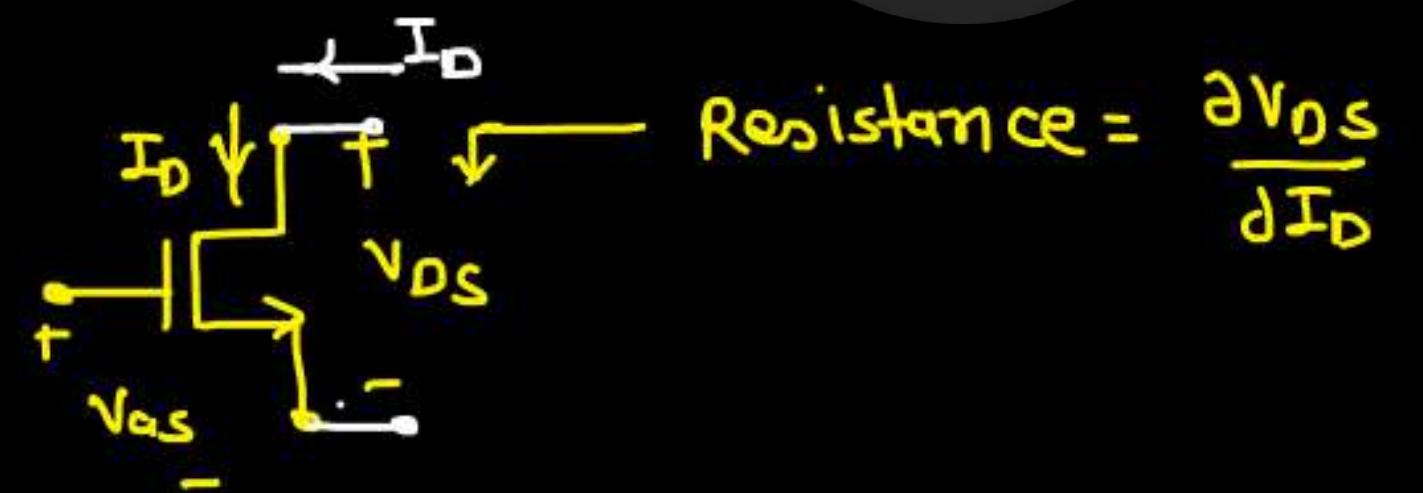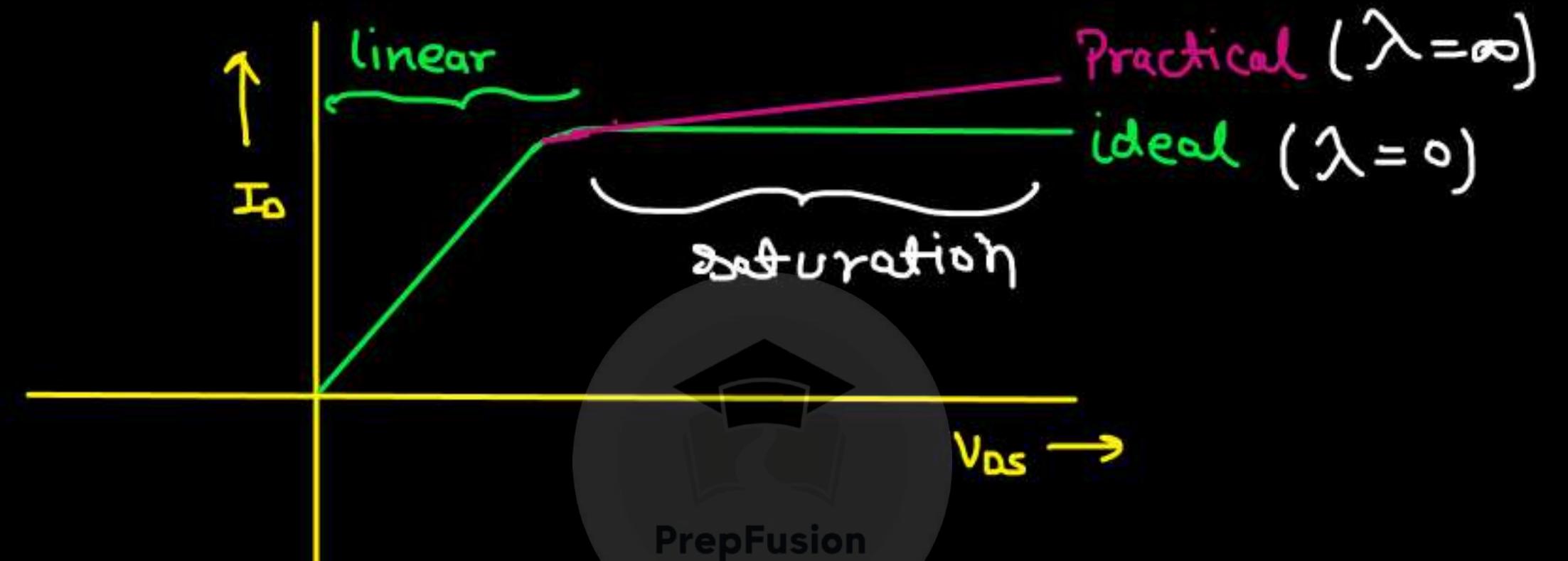

$$\text{Resistance} = \frac{\partial V_{DS}}{\partial I_D}$$

$$\downarrow \quad (I_D)_{\text{sat.}} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$(I_D)_{\text{linear}} = \frac{\mu_n C_{ox} W}{L} [(V_{GS} - V_T) V_{DS} - V_{DS}^2 / 2]$$

For saturation region:-

$$\gamma_{DS} = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}}$$




Practical
ideal

$$\gamma_{DS} = \frac{1}{\lambda [I_D]_{\text{sat-ideal}}}$$

$$\gamma_{DS} = \infty$$

MOS in saturation region:-

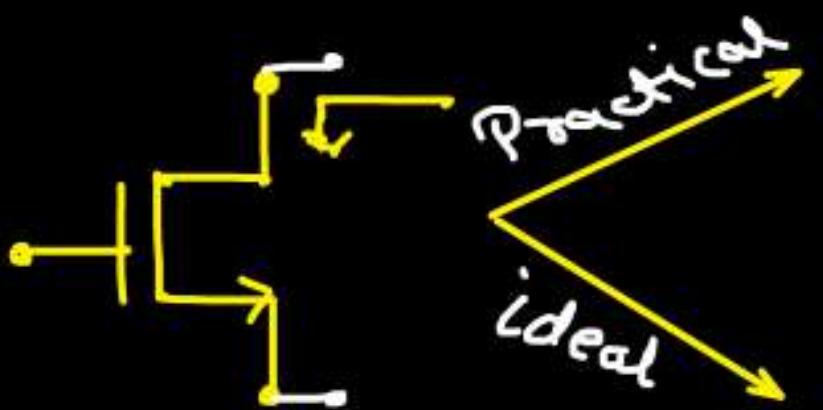

$$r_{ds} = \frac{1}{\lambda(I_D)_{sat-ideal}}$$



$$I = f(V_{GS})$$



For Triode region :-

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

for deep Triode region:-

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[(V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


$$R_{ON} = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}}$$

For deep Triode region,

V_{DS} is very small

$$\left[V_{DS} < \frac{(V_{GS} - V_T)}{2} \right]$$

$$V_{DS} \approx 0$$

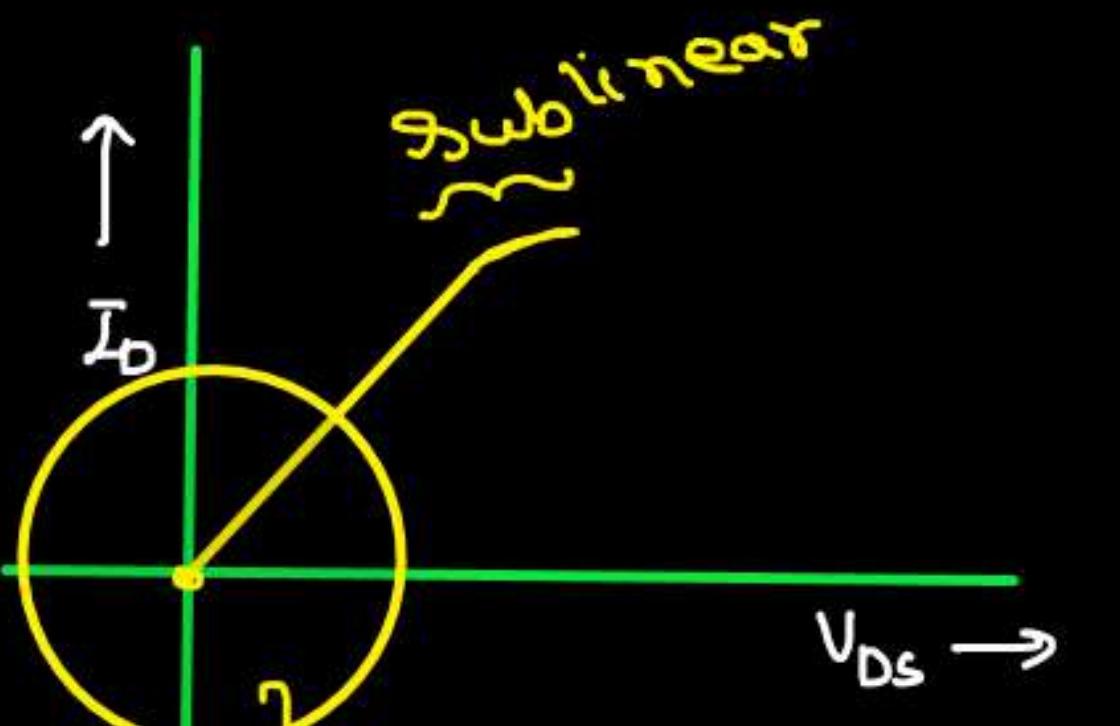

deep Triode region

$$I_D = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T) V_{DS}$$

$$\frac{\partial I_D}{\partial V_{DS}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)$$

$$R_{on} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)}$$

PrepFusion

deep
MOS in Triode region




Assignment - 5 (Fusion-Special)

Q. 1 V_x is varying from 0 to 3V.

Take $V_{T\eta} = 0.7V = |V_{Tp}|$


Plot I_x v/s V_x and g_m v/s V_x .

(a)

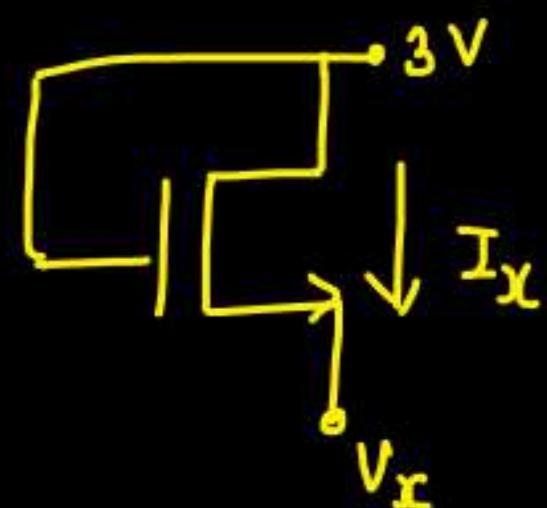

$$\text{where } g_m = \frac{\partial I_D}{\partial V_{GS}}, \quad g_m = \frac{\partial I_D}{\partial V_{SG}}$$

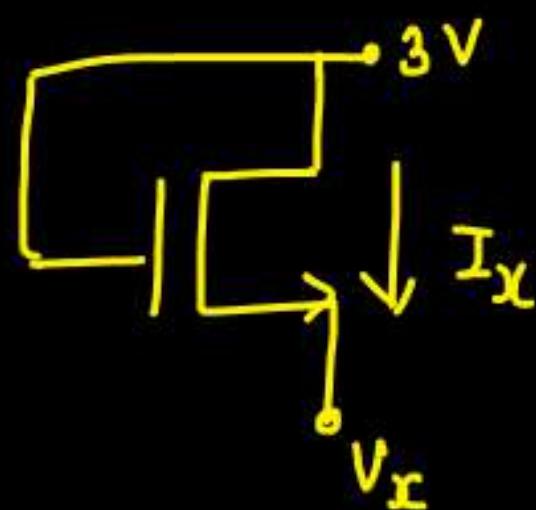$I_D \rightarrow$ Current from D to S (NMOS)
 \rightarrow Current from S to D (PMOS)



(q)

$$V_{DS} = 3 - V_x \quad \text{---}$$

$$V_{GS} = 3 - V_x$$

$$V_T = 0.7$$

$$V_{OV} = V_{GS} - V_T = 2.3 - V_x \quad \text{---}$$

$V_{DS} > V_{OV} \Rightarrow$ always \Rightarrow sat.

$$I_x = k (2.3 - V_x)^2 \quad \text{---} \quad \text{Pre fusion}$$



If Gate and Drain are shorted, the MOS will always be in sat.

for cut off :-


$$V_{GS} < V_T$$

$$3 - V_x < 0.7$$
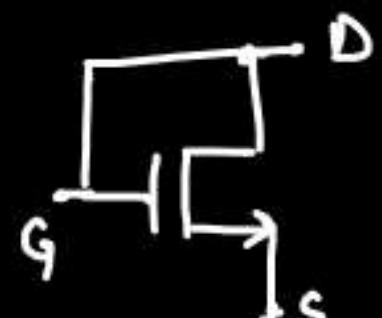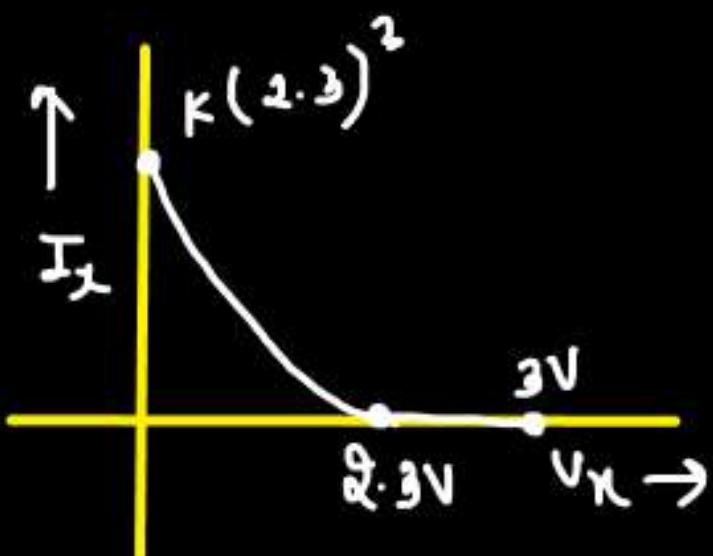
$$\begin{aligned} V_x &> 2.3V \\ \Rightarrow I_x &= 0 \text{ Amp} \end{aligned}$$



$$V_{DS} > V_{GS} - V_T$$

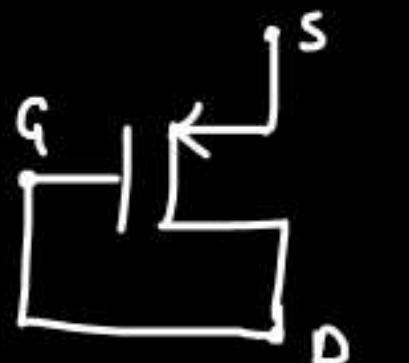

$$V_{SD} > V_{GS} - V_T$$

Talking about g_m :


MOS is always in sat. $\{ 0 < v_x < 2 \cdot 3 \}$

$$(g_m)_{\text{sat}} = K' (v_{GS} - v_T)$$


$$g_m = K' (2 \cdot 3 - v_x)$$

when $v_x \geq 2 \cdot 3V \Rightarrow I_x = 0 \Rightarrow g_m = 0$

PrepFusion

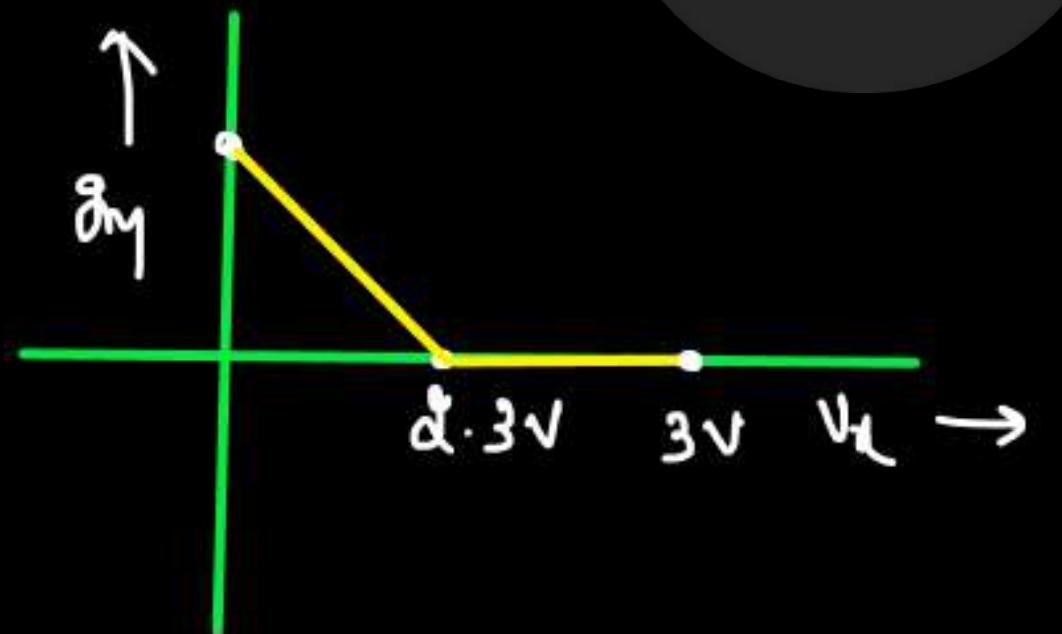

(b)


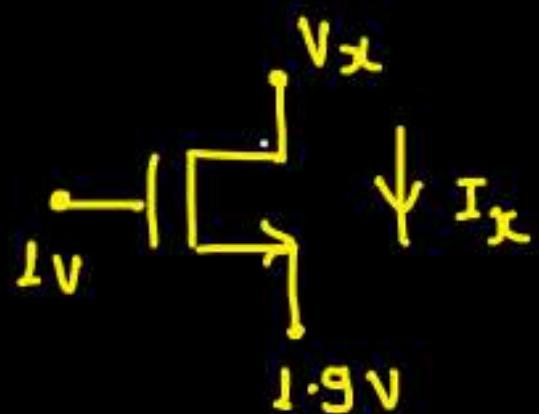


$$V_X = 0 \rightarrow 3V$$

$$V_T = 0.7V$$

→ \$V_{GS} = 1 - 1.9V = -0.9V < V_T \Rightarrow I_X = 0 \text{Amp.}\$ X X

\$0 < V_X < 1.9V\$

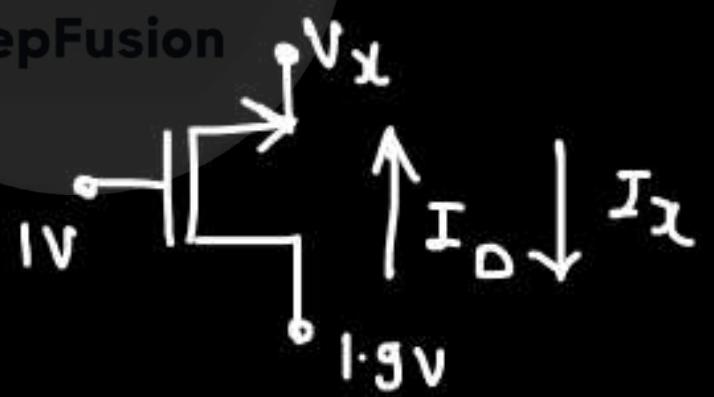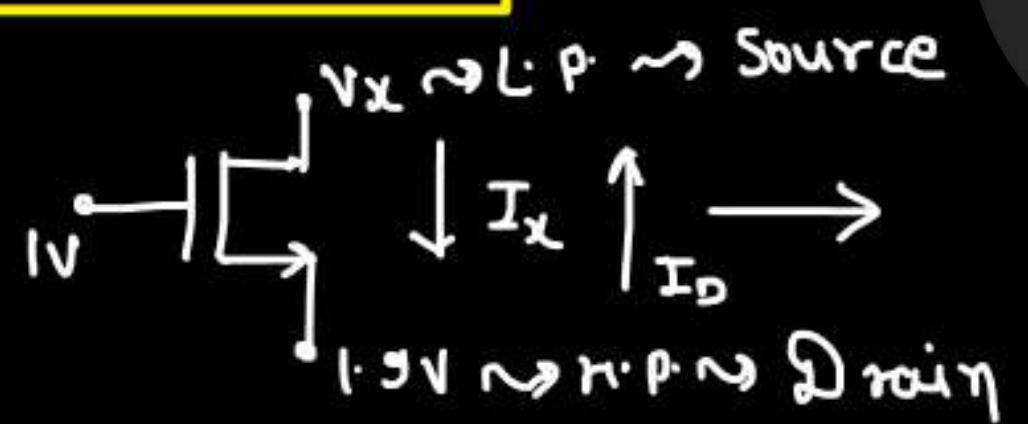

$$V_{DS} = 1.9 - V_X$$

$$V_{GS} = 1 - V_X$$

$$V_T = 0.7V$$

$$V_{OV} = 0.3 - V_X$$

For cut off $\Rightarrow V_{GS} < V_T \Rightarrow V_{OV} < 0$

$$V_L > 0.3V$$

$\Rightarrow V_{DS} > V_{GS} - V_T \Rightarrow Sat.$

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

$0 < v_x < 0.3 \Rightarrow \text{Sat.}$

$$I_D = k (v_{GS} - v_T)^2$$

$$I_D = k (0.3 - v_x)^2$$

$$I_X = -k (0.3 - v_x)^2$$



$0.3 < v_x < 1.9V \Rightarrow \text{cut-off}$

$$I_X = 0 \text{ Amp.}$$


$$\delta v = 0$$

$$\delta v = k' (v_{GS} - v_T)$$

$$\delta v = k' (0.3 - v_x)$$

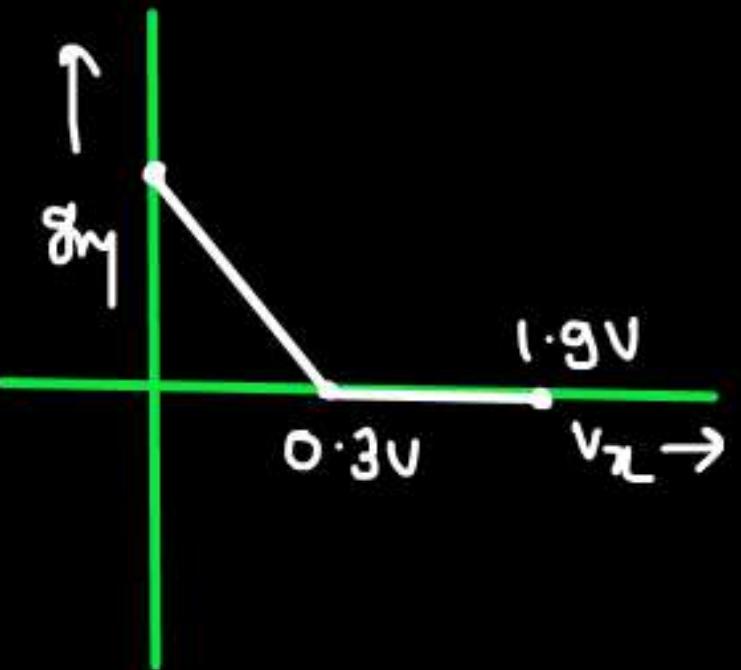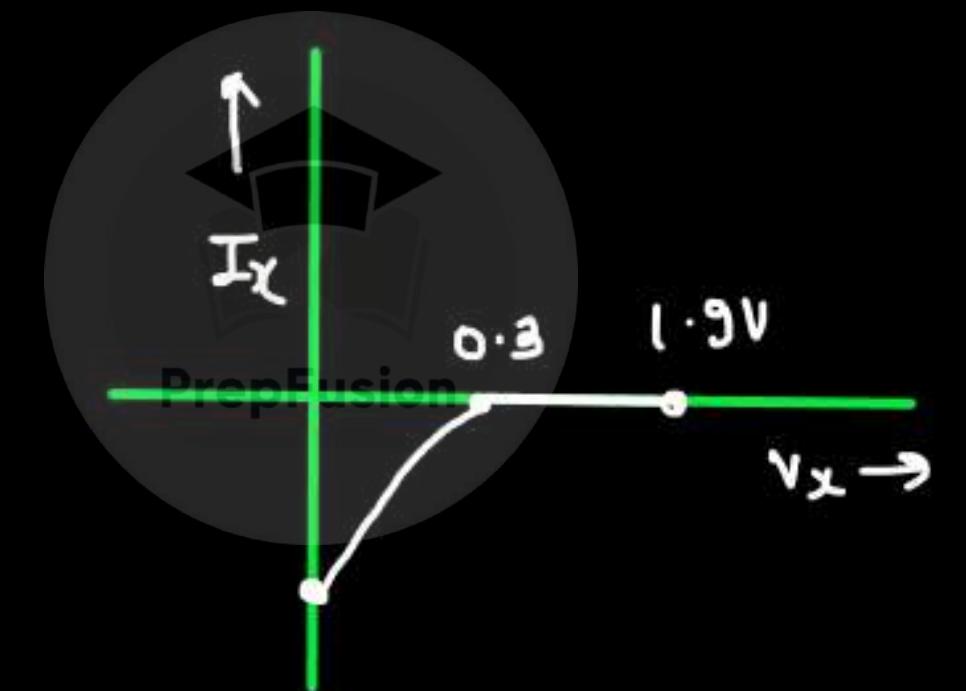



for $V_x > 1.9V$

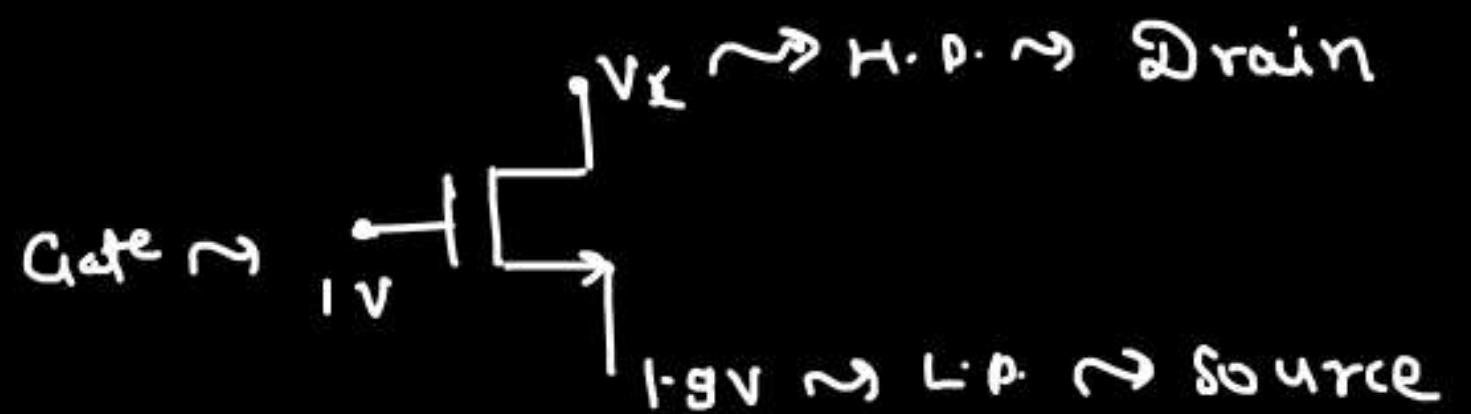


$V_{ds} = 1 - 1.9 = -0.9 < V_T \Rightarrow \text{MOS is off}$

$I_x = 0 \text{ Amp.}$ $g_m = 0$

PrepFusion

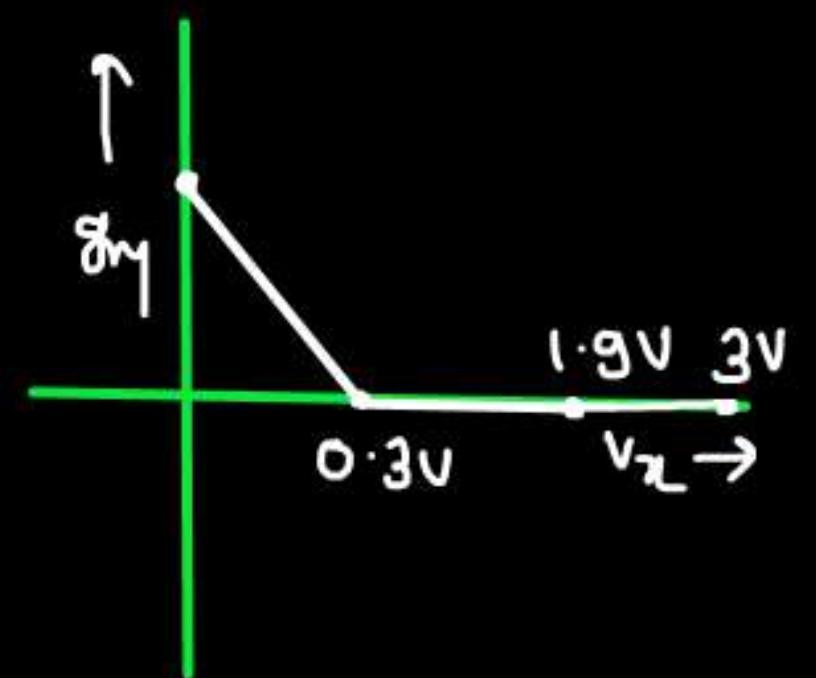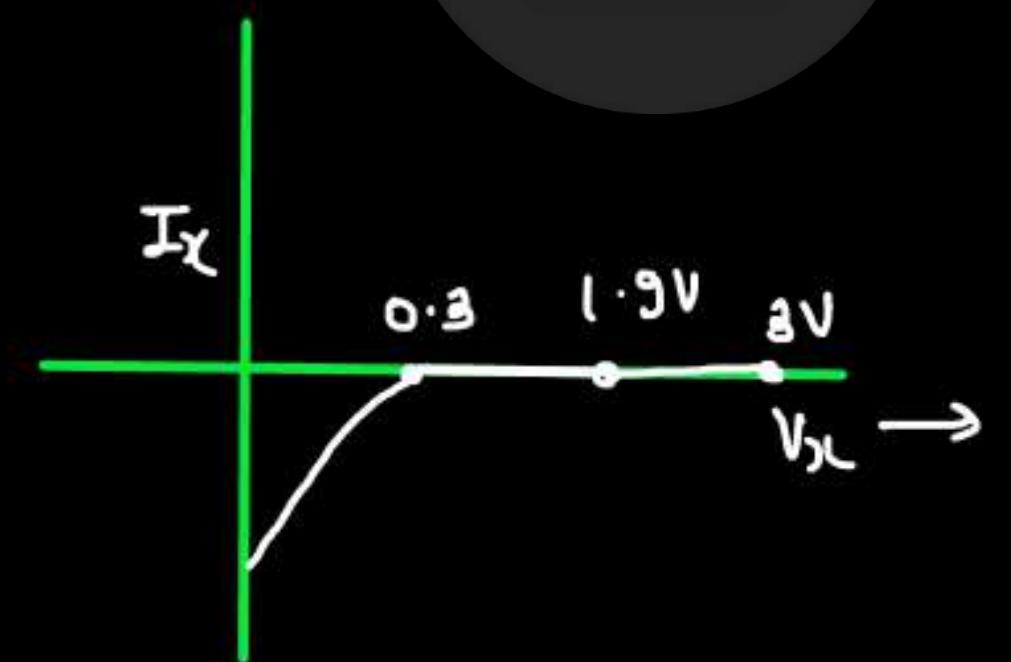

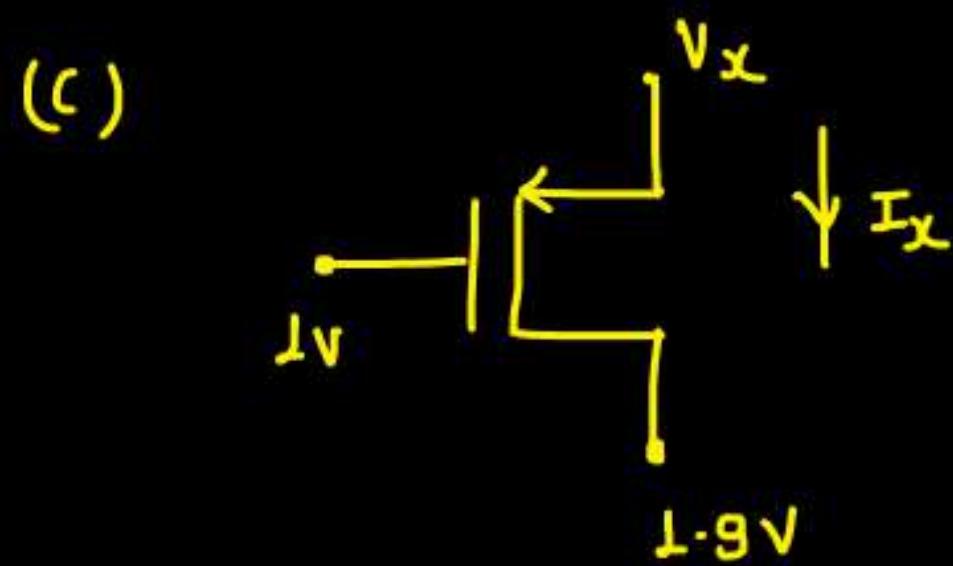

$$V_x \equiv 0 \rightarrow 3V$$

$$|V_{TP}| = 0.7V$$

→ $0 < V_x < 1.9V$



$$V_{SG} = 0.9V$$

$$V_{SD} = 1.9 - V_x$$

$$V_{DS} = 0.9 - 0.7 = 0.2V \rightarrow \text{MOS is ON}$$

for sat.

$$V_{SD} > V_{DS}$$

$$1.9 - V_x > 0.2V$$

$V_x < 1.7V$

$$\Rightarrow V_x < 1.7 \Rightarrow \text{Sat.}$$

$$1.9 > V_x > 1.7 \Rightarrow \text{linear}$$

$$V_X < 1.7V : -$$

$$I_D = k' (V_{SG} - V_T)^2$$

$$I_D = k' (0.2)^2$$

$$I_L = -I_D$$

$$I_L = -k' (0.2)^2 \sim \text{constant}$$

$$g_m = k (V_{SG} - V_T)$$

$$g_m = k (0.2) \sim \text{const.}$$

$$1.9V < V_X < 1.7V : -$$



$$I_D = k'' \left[(V_{SG} - V_T) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$I_L = -k'' \left[0.2 (1.9 - V_X) - \frac{(1.9 - V_X)^2}{2} \right]$$




$$(g_m)_{\text{lineq}} = k''' \times V_{SD}$$

$$g_m = k''' \times (1.9 - V_X)$$

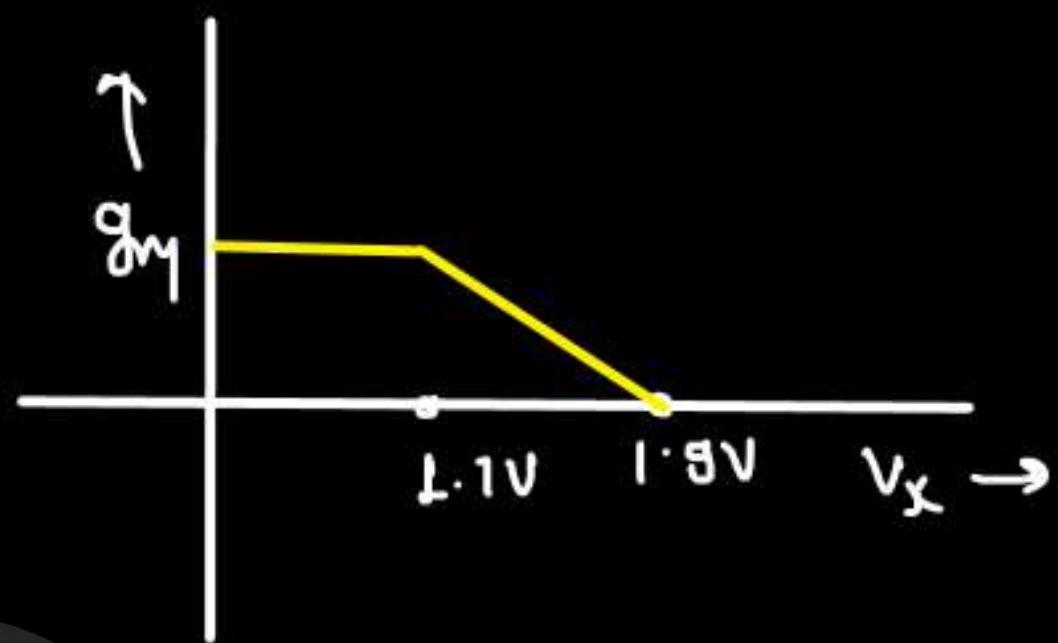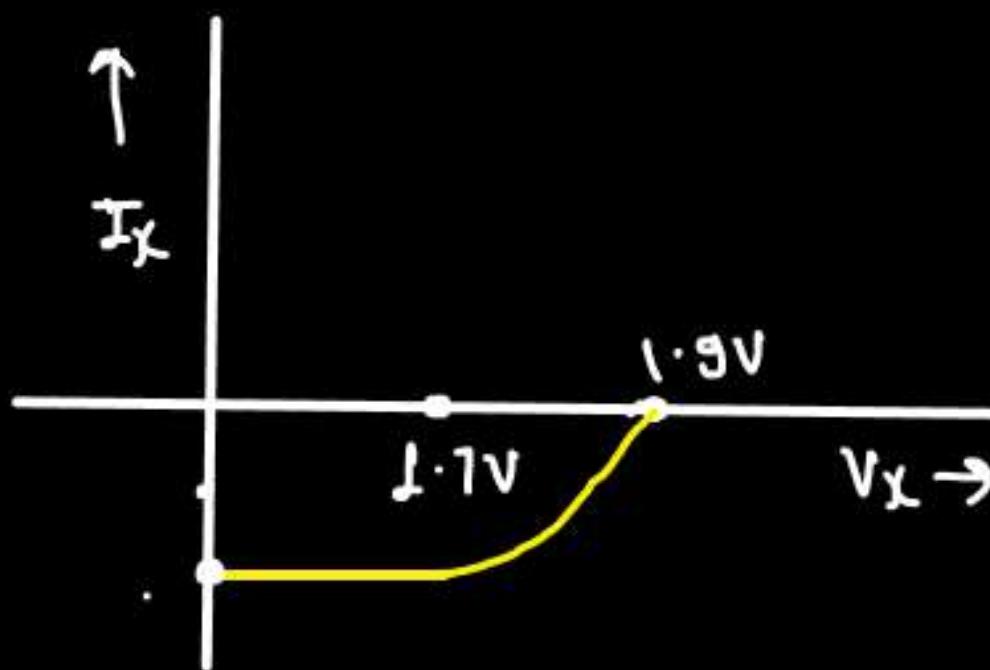

For $V_x > 1.5V$

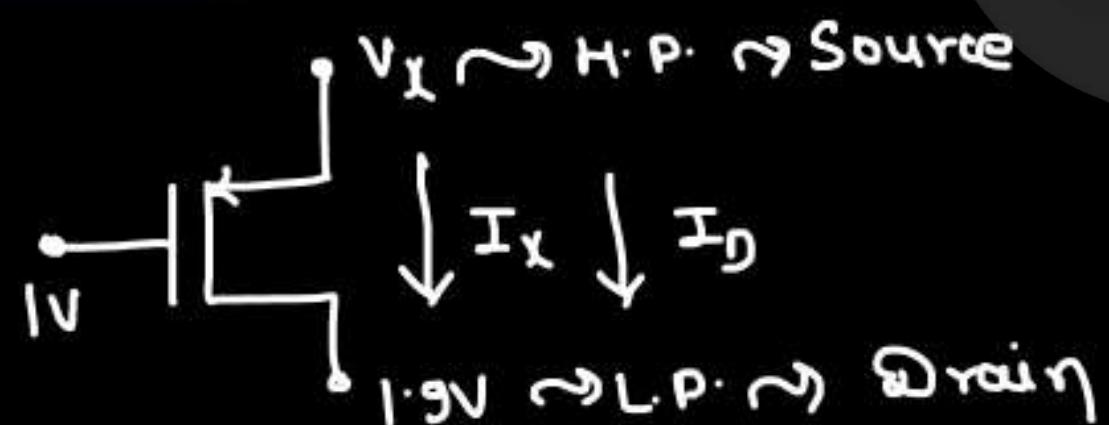

$$V_{SD} = V_x - 1.5V$$

$$V_{SG} = V_x - 1$$

$$V_T = 0.7V$$

$$V_{DS} = V_x - 1.1V$$



$\Rightarrow V_{SD} < V_{DS} \Rightarrow$ linear region

$$I_D = K \left[(V_{SG} - V_T) V_{SD} - \frac{V_{SD}^2}{2} \right]$$


$$I_D = I_X = K \left[(V_X - 1.1) (V_X - 1.9) - \frac{(V_X - 1.9)^2}{2} \right]$$

$$\delta V = K' [V_X - 1.9]$$



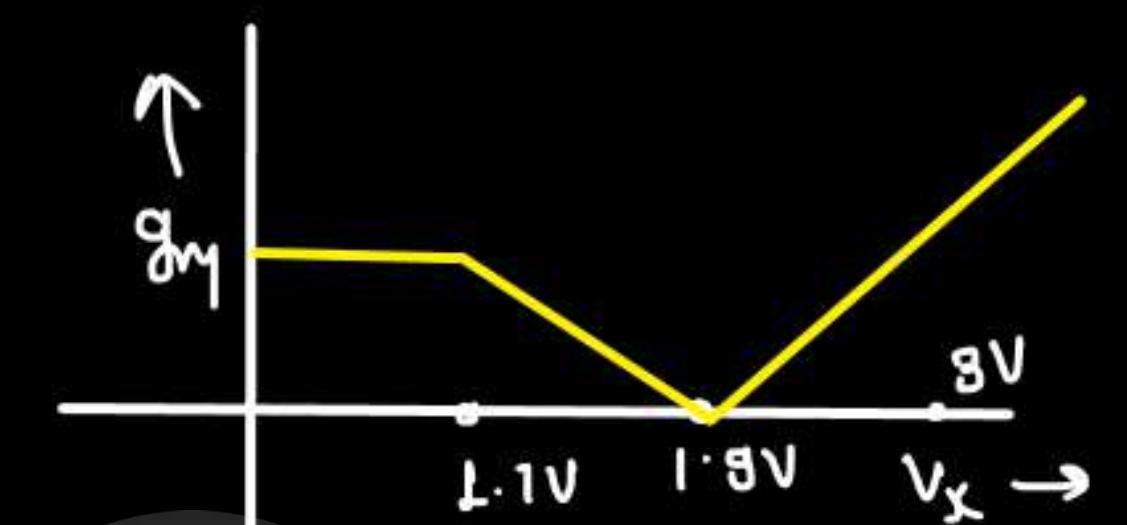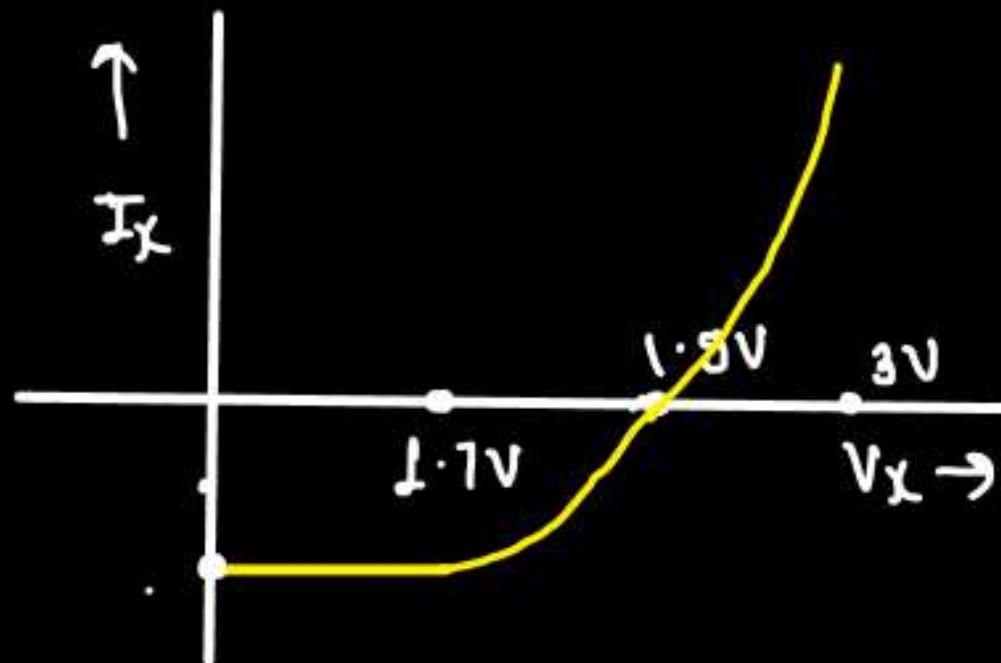

Q.

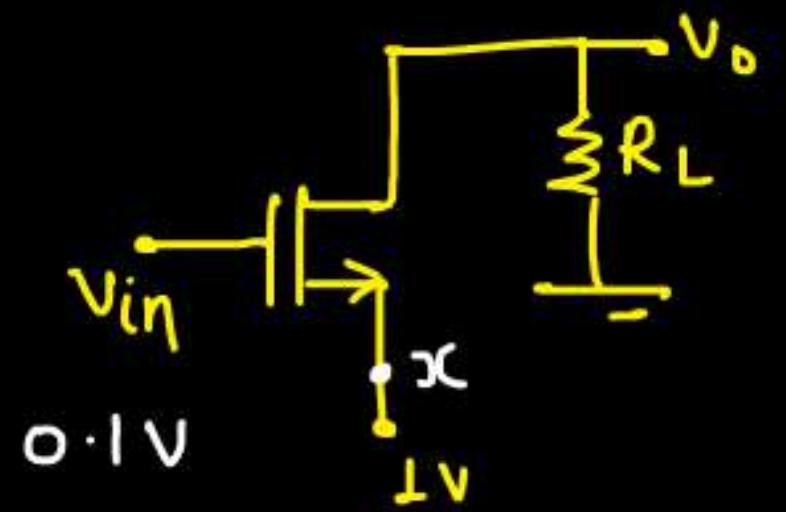

$$V_{in} \equiv 0 \rightarrow 3V$$

$$V_T = 0.7V$$

Plot V_d v/s V_{in} .

Given $R_L \rightarrow \text{very low}$

Find max value of V_d .

PrepFusion


For $V_i < 1.7V \Rightarrow \text{MOS off} \quad XX$

initially, Mos current = 0 A $\Rightarrow V_d = 0V$

$\Rightarrow V_d \rightarrow \text{Source}$

$V_x \rightarrow \text{Drain}$

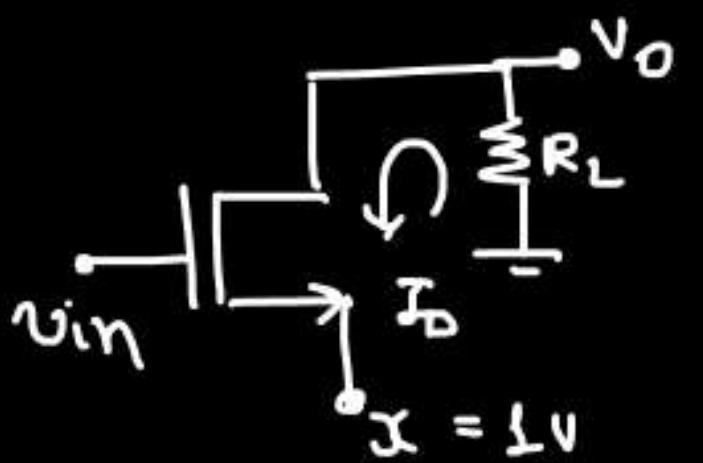Let's assume, potential x is source $\Rightarrow V_0 = -ve$



↓


$$\text{But } V_S = V_x = LV$$


$$\text{and } V_0 = V_D = -ve$$

↓

NOT POSSIBLE

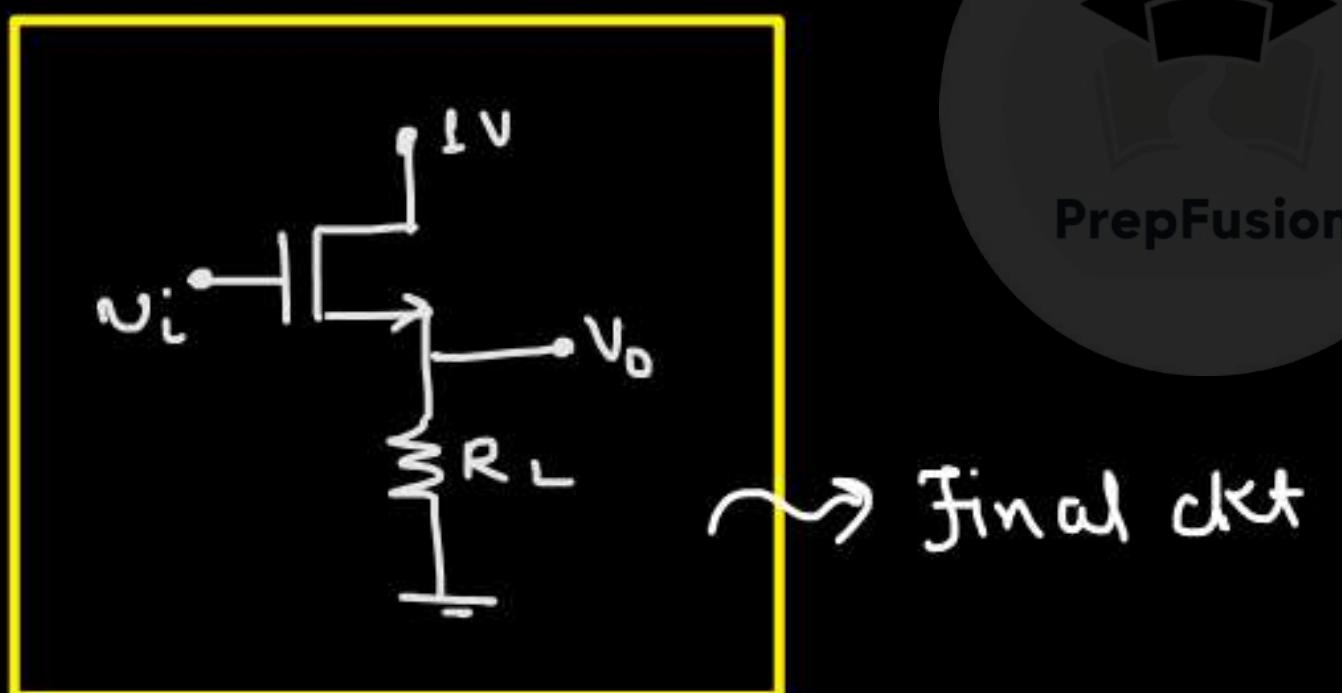$\Rightarrow x$ will always be drain
 V_0 will always be source



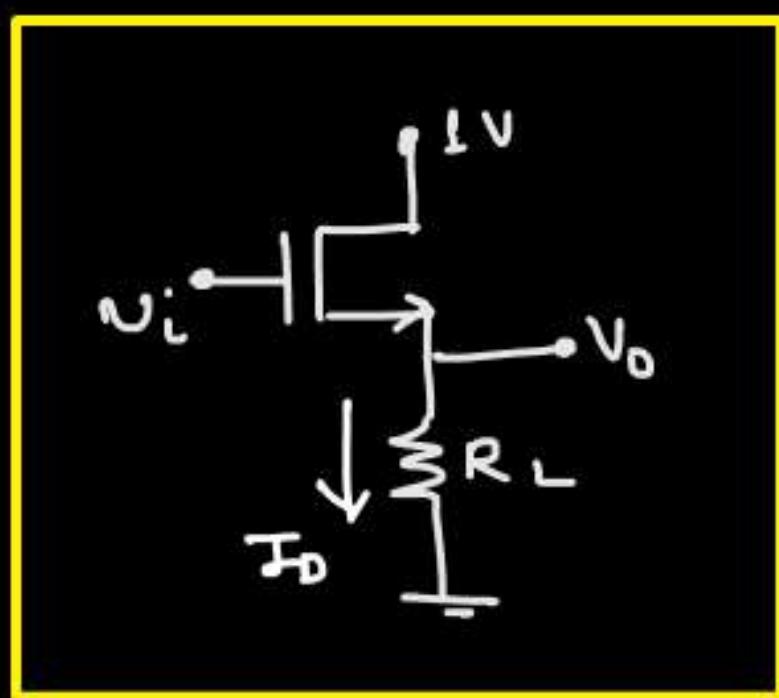

$$V_o = I_D R_L$$

initially, $V_o = 0V$

$V_{in} < V_T \Rightarrow V_{in} < 0.7V \Rightarrow \text{MOS OFF}$
 $[V_{GS} < V_T]$

when $V_{in} = 0.7V$

$\Rightarrow \text{MOS is ON}$

when MOS just turns on $\Rightarrow I_D$ is very small
 $V_o = I_D R_L = \text{very small}$

$$V_{DS} = 1 - V_o$$

$$V_{GS} = V_i - V_o$$

$$V_{DS} = V_i - 0.7 - V_o$$

\Rightarrow for sat.

$$1 - V_o > V_i - 0.7 - V_o$$

$$V_i < 1.7V \Rightarrow \text{sat.}$$

$$V_i > 1.7V \Rightarrow \text{linear}$$

for $0 < V_i < 1.7V$


$$I_D = K [V_i - 0.7 - V_0]^2$$

$$V_o = I_D R_L$$

$$V_o = K [V_i - 0.7 - V_0]^2 R_L$$

if we increase $V_i \Rightarrow I \uparrow \Rightarrow V_o \uparrow$


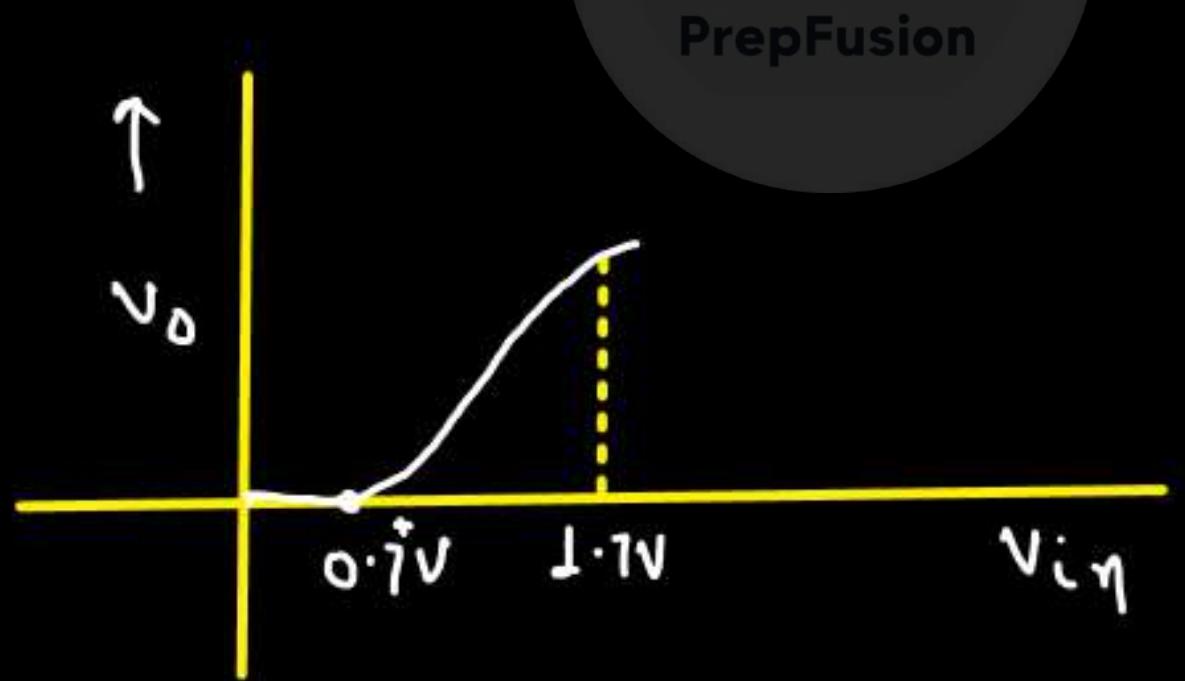
But V_o will not increase as much as V_i .




For $V_i > 1.7V \Rightarrow$ diode Triode

$$I_D = K \left[(V_i - 0.7 - V_0)(1 - V_0) - \frac{(1 - V_0)^2}{2} \right]$$

$$V_0 = I_D R_L$$

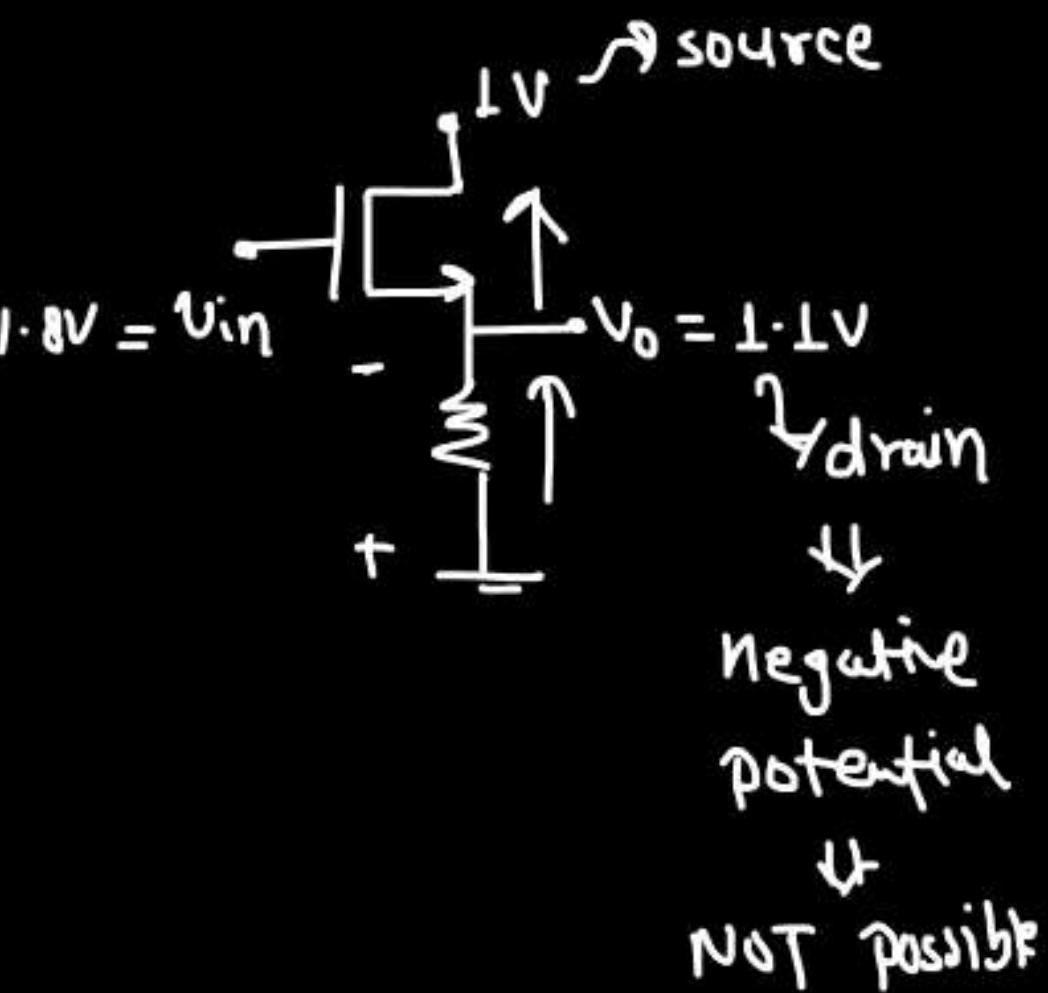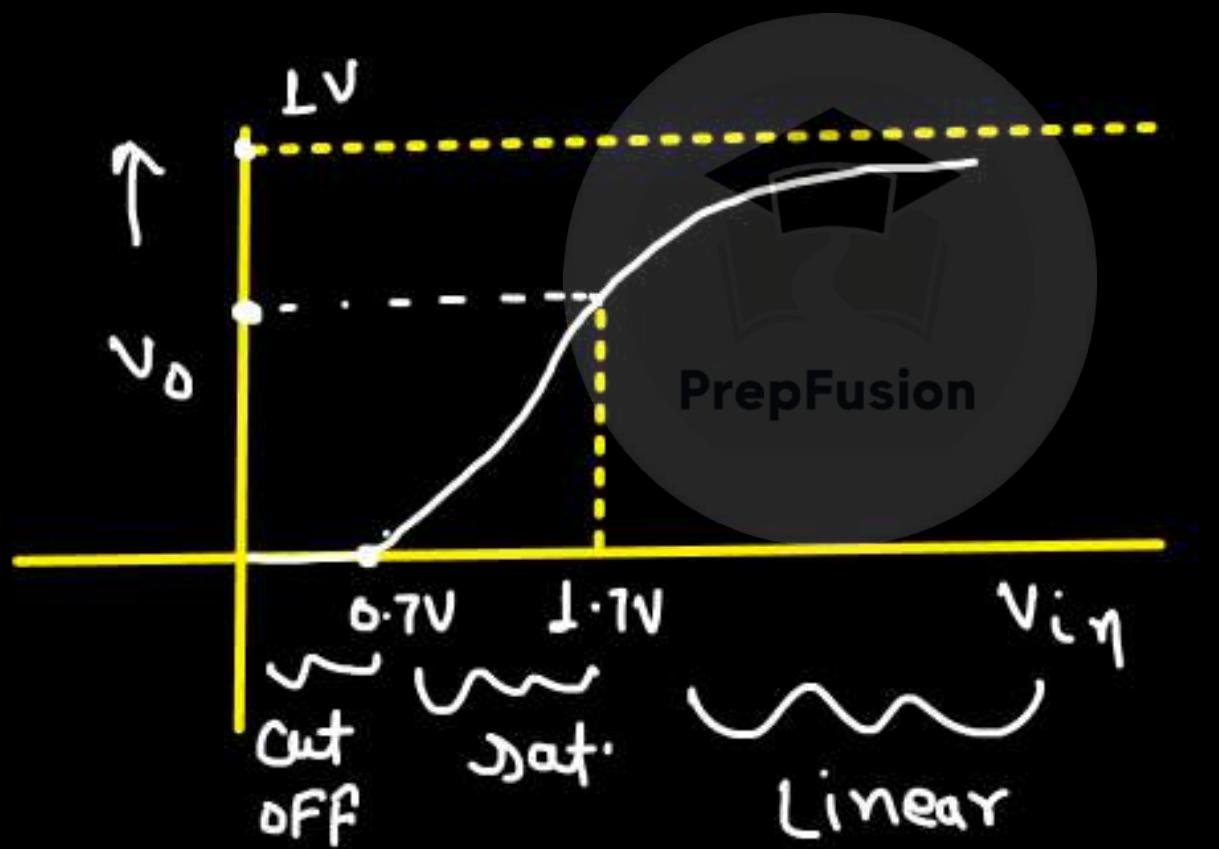

Q.

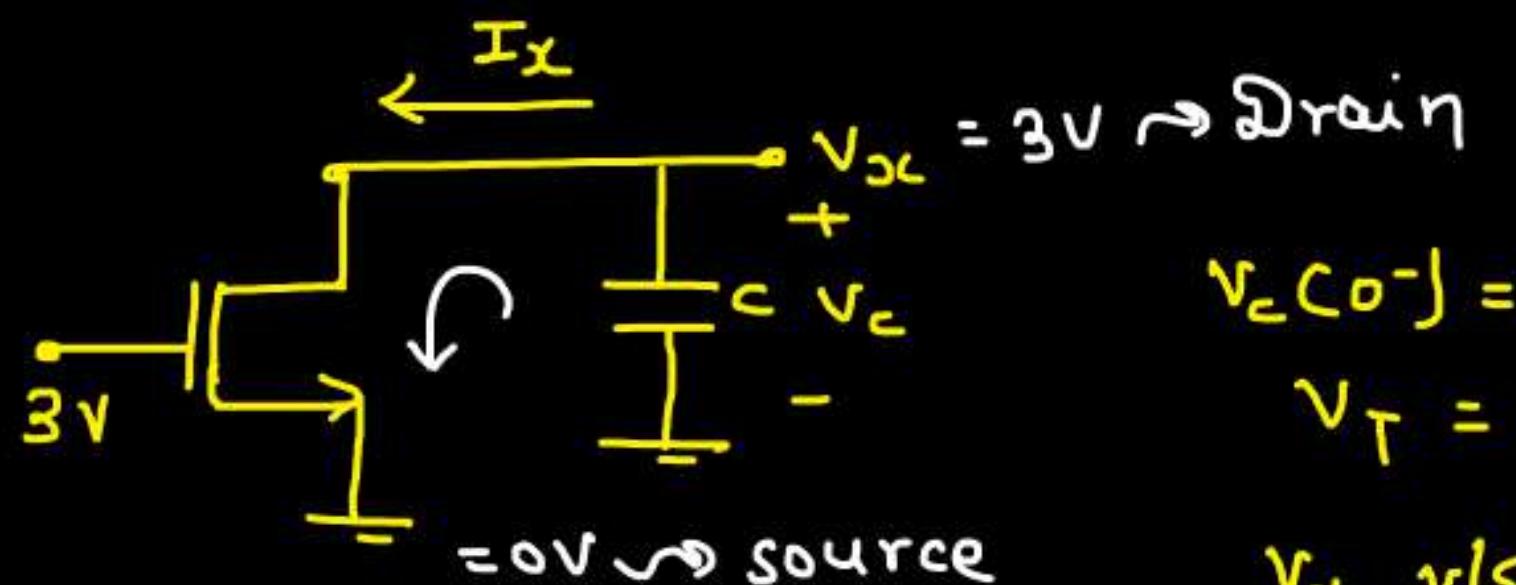

$$V_C(0^-) = 3V$$

$$V_T = 1V$$

$$V_{Dc} \text{ v/s } t = ?$$

$$I_D \text{ v/s } t = ?$$

→

$$V_{QS} = 3V, \quad V_{DS} = V_I = V_C$$

$$V_T = 1V$$

$$V_{OV} = 2V$$

@ $t=0^+$


$$V_{DS} = 3$$

@ $t=0^+$, $V_{DS} > V_{OV} \Rightarrow \text{sat. region}$

$$I_D = K [2]^2$$





@ $t = 0^+$

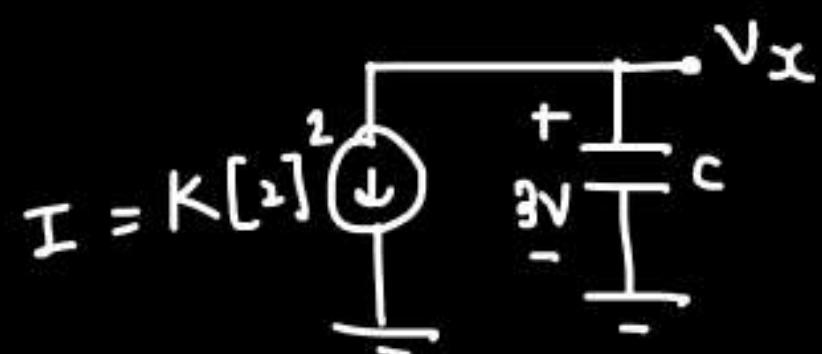

⇒ cap. will start discharging linearly.

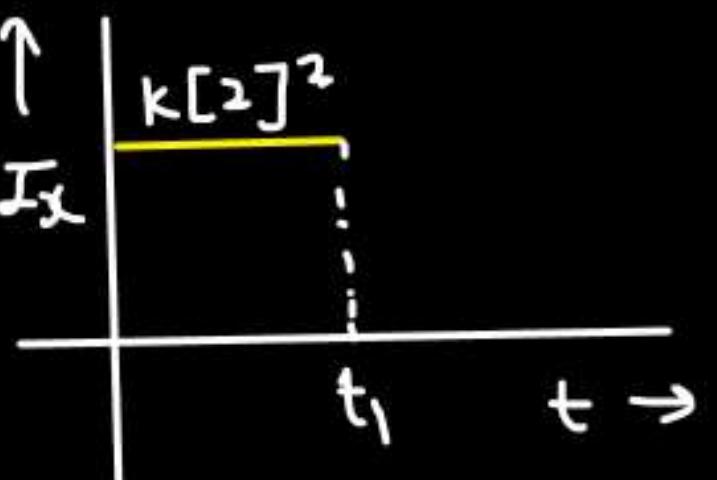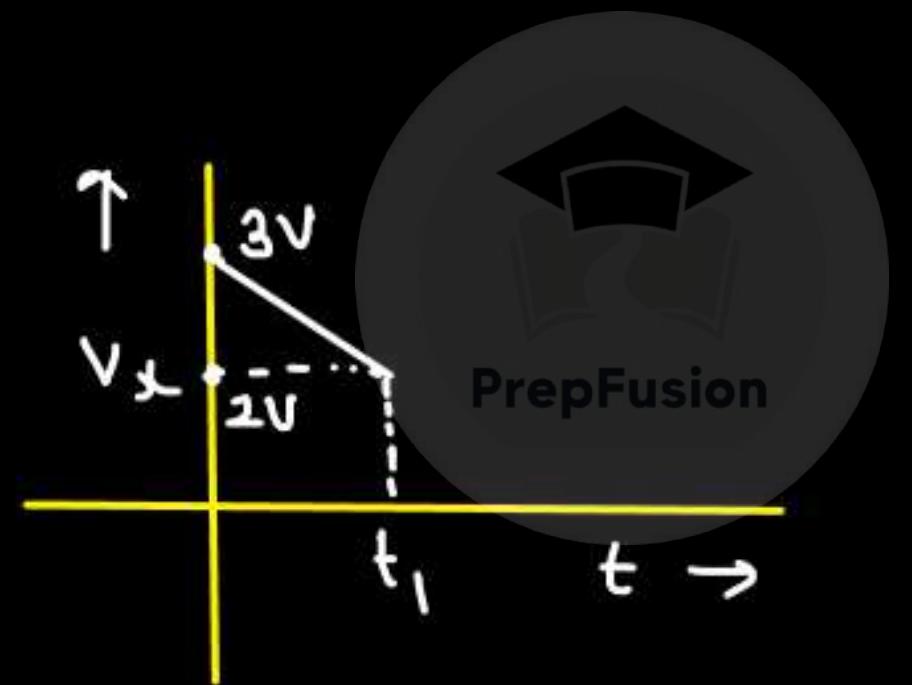
$$V_X = V_C(t) = 3 - \frac{1}{C} \int I \cdot dt \\ = 3 - \frac{I}{C} t$$



When V_{DS} or $V_X < 2$

$\Rightarrow V_{DS} < V_{DSV} \Rightarrow$ MOS will go into Triode \Rightarrow MOS acts as resistance

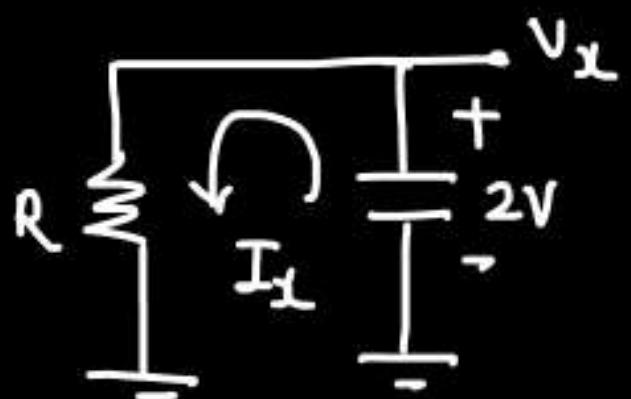For $t > t_1 \Rightarrow$ MOS goes into linear region.





$$V_x = \frac{R_{DN}}{R} = R$$


$$I_x = K \left[2 \cdot V_x - \frac{V_x^2}{2} \right]$$

\Rightarrow Both V_x and I_x will go down to zero

PrepFusion

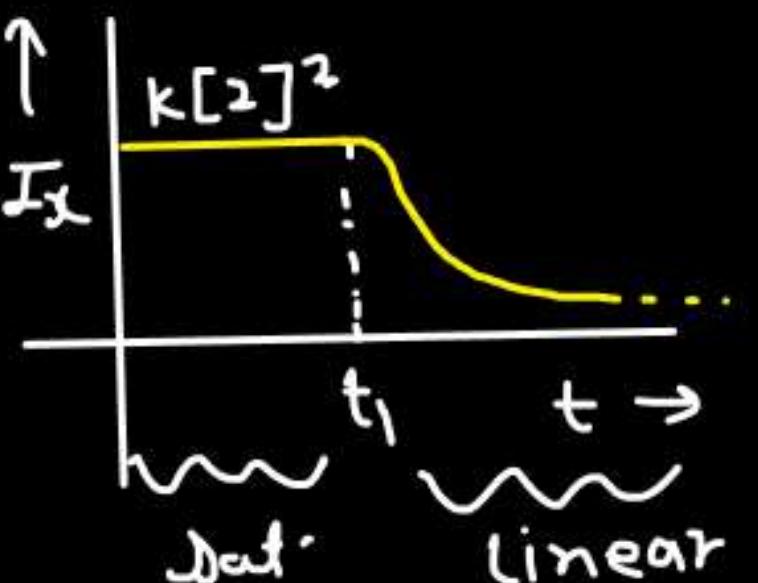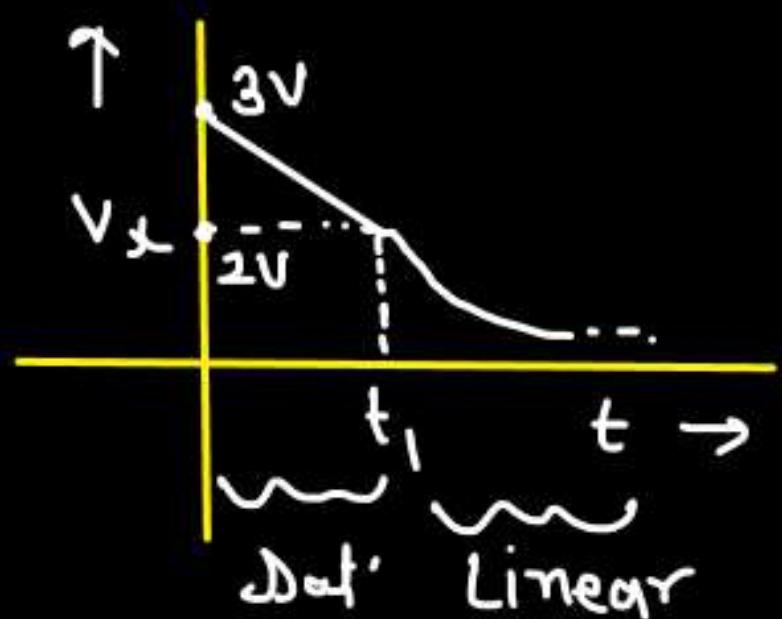

Q.
★

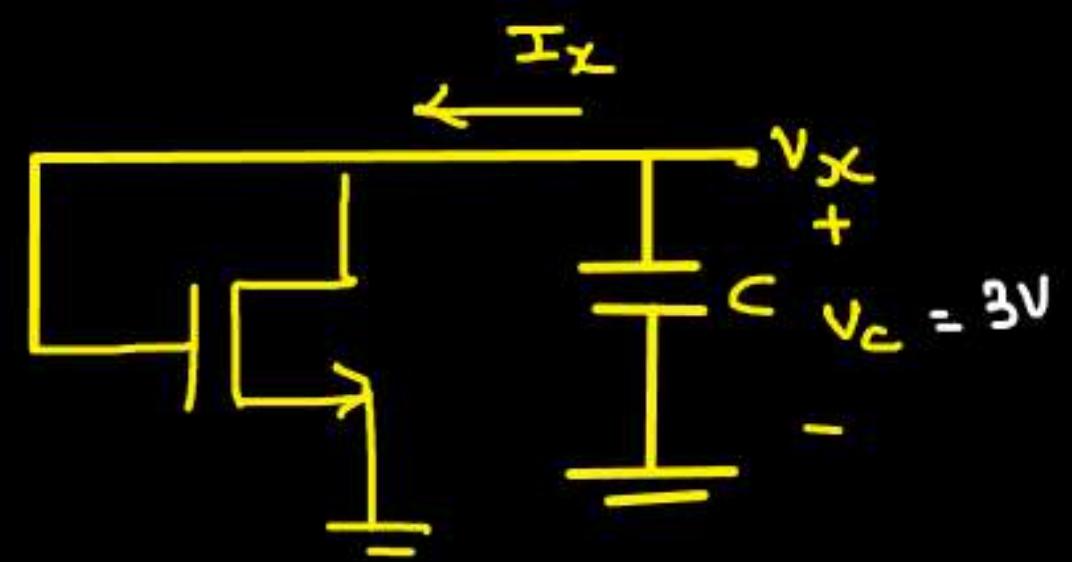

$$V_T = 1V$$

$$V_C(0) = 3V$$

$$V_x \text{ v/s } t = ?$$

$$I_x \text{ v/s } t = ?$$

Find min. value of V_x

→ D and G are shorted \Rightarrow MOS always be in sat.


PrepFusion

$$V_{GS} = V_x$$

$$V_{DS} = V_x \quad \Rightarrow \text{Sat.}$$

$$V_{DV} = V_x - 1$$

$$I_x = k [V_x - 1]^2$$

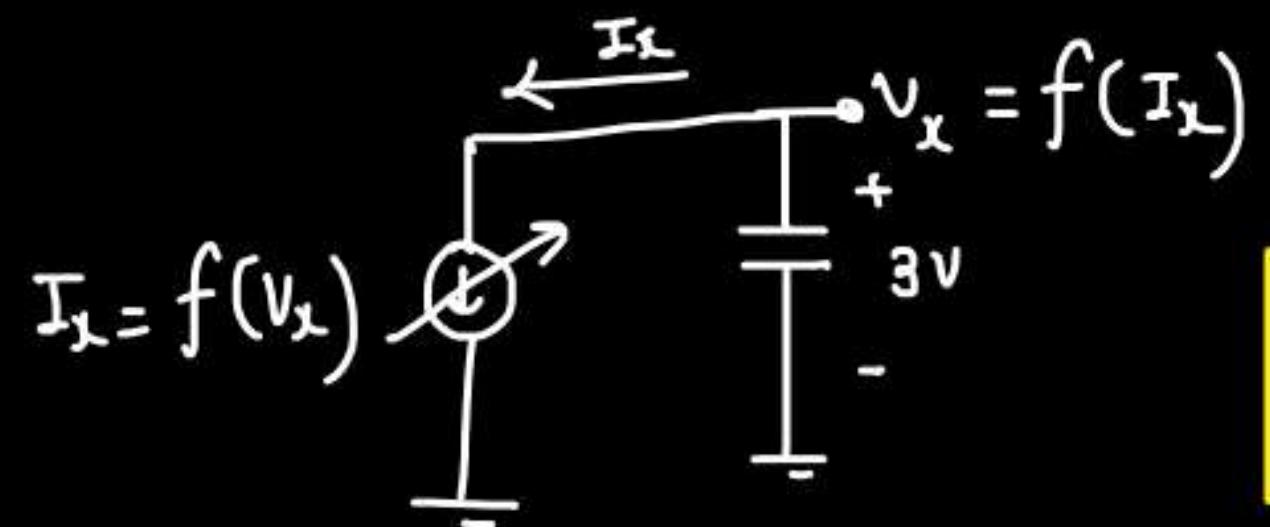




$$V_x = 3 - \frac{1}{C} \int |I_x(t)| dt$$

Here, V_x is going down. When $V_{GS} < V_T \Rightarrow$ MOS will be off


$$V_x < 1$$

PrepFusion

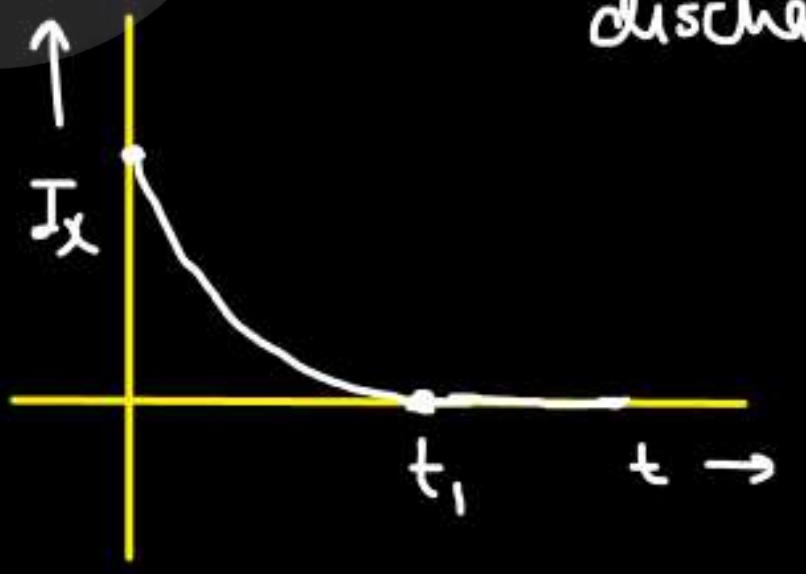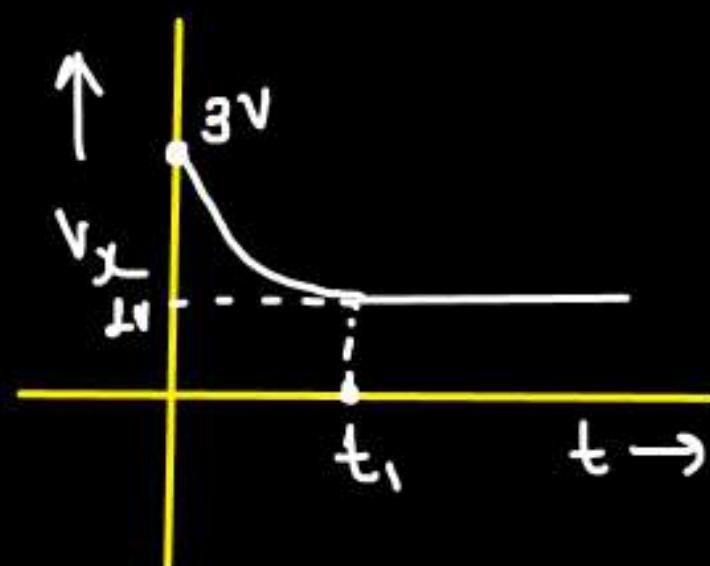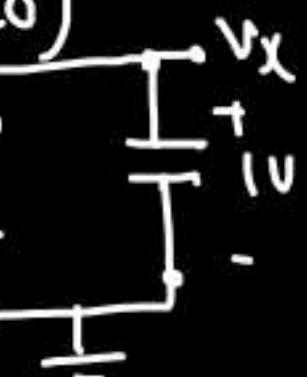\Rightarrow No current ($I_x=0$)
↓
No further discharging



Q.

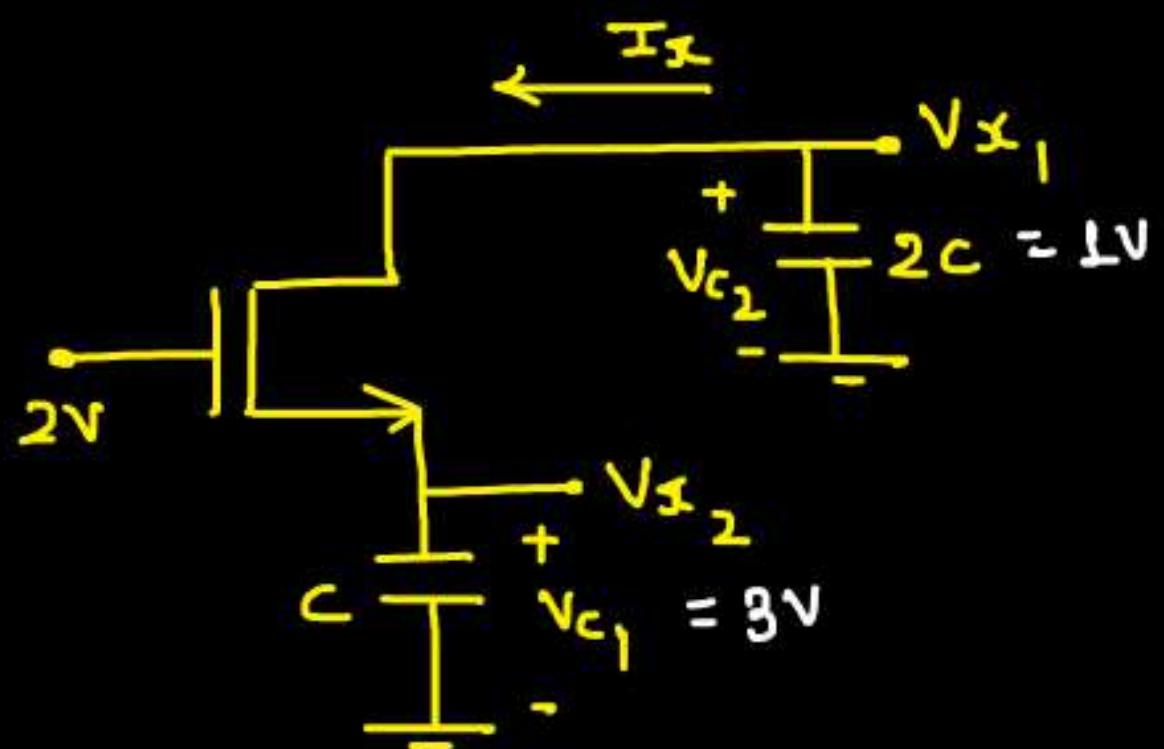

@ $t=0^+$


$$V_{x_2} = 3V, \quad V_{x_1} = 1V$$


\downarrow \downarrow

H.P. L.P.

\downarrow \downarrow

Drain Source

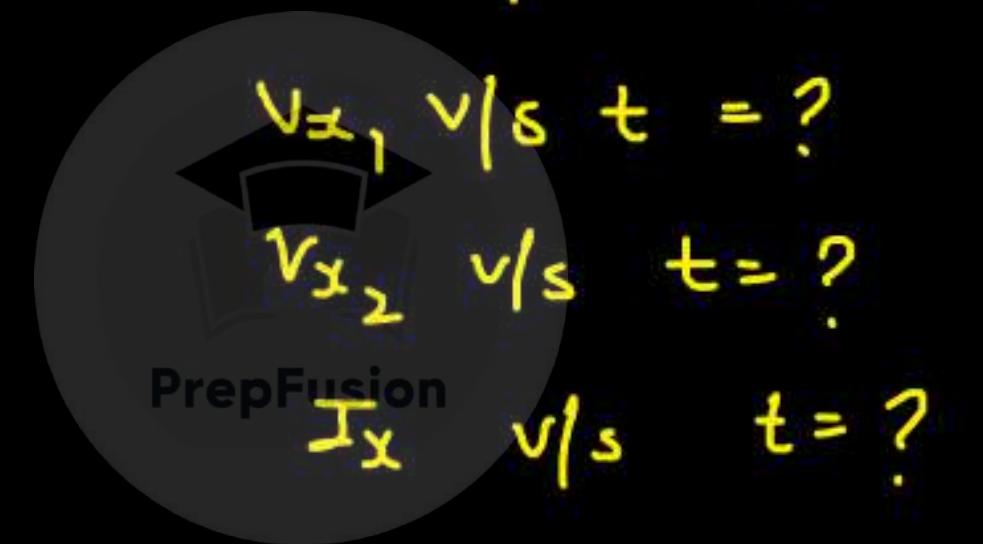

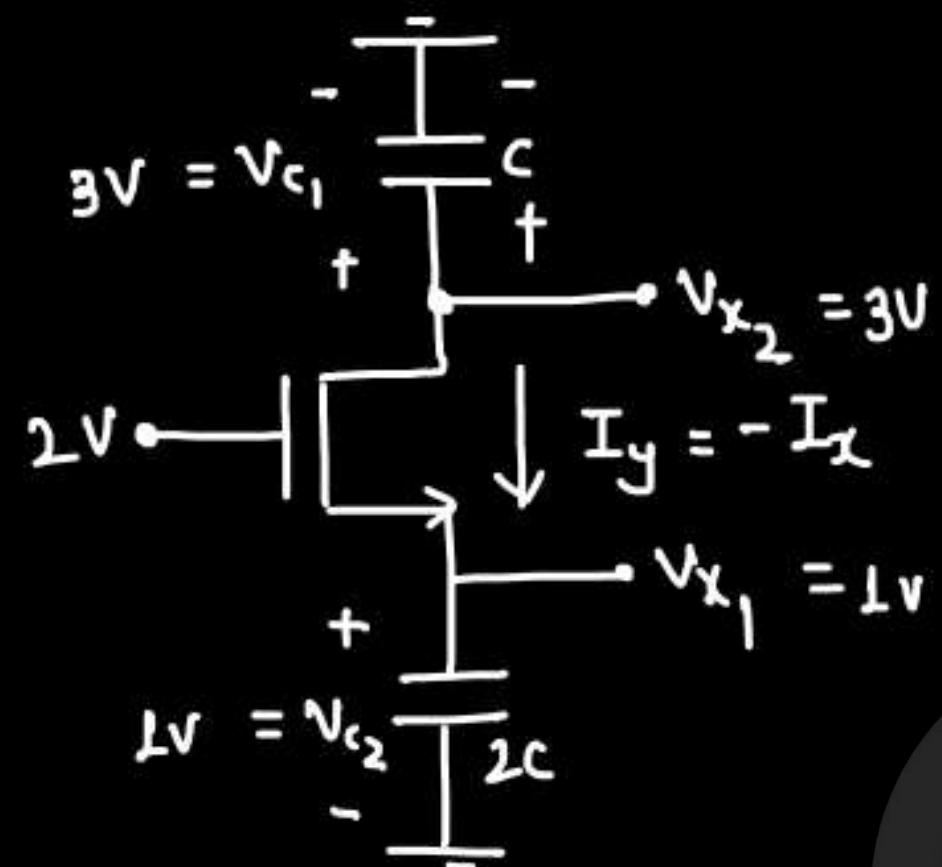

$C \rightarrow$ discharged

$2C \rightarrow$ charged

$$V_{DS} = 1V \Rightarrow V_{DS} = 0.3$$

$$V_T = 0.7V$$

$$V_{DS} = 2V$$

$$\Rightarrow V_{DS} > V_{DS} \Rightarrow \text{sat.}$$

$$I_y = f(V_{x_1})$$

\Rightarrow Cap. $2C$ can charge upto $1.3V$ only.

Because, if $2C$ charges above $1.3V \Rightarrow$ MOS will be off

$$V_{x_1} (\text{ss}) = 1.3V$$

When V_{x_1} was increasing from 1V to 1.3V

↳

There was I_y current flowing out
of cap. C

Both cap. C and $2C$ are having same current

$$I_C = I_{2C}$$

$$\frac{\Delta Q_C}{\Delta t} = \frac{\Delta Q_{2C}}{\Delta t}$$

PrepFusion

$$\Delta Q_C = \Delta Q_{2C}$$

$$C(\Delta V_C) = 2C(1.3 - 1)$$




$$\boxed{\Delta V_C = 0.6V}$$

⇒ change in capacitor C voltage would be 0.6V


Cap. C will discharge from 3V to 2.4V

V_{x_2} will decay down from 3V to 2.4V


$$V_{C_1} (\text{ss.}) = 2.4V$$

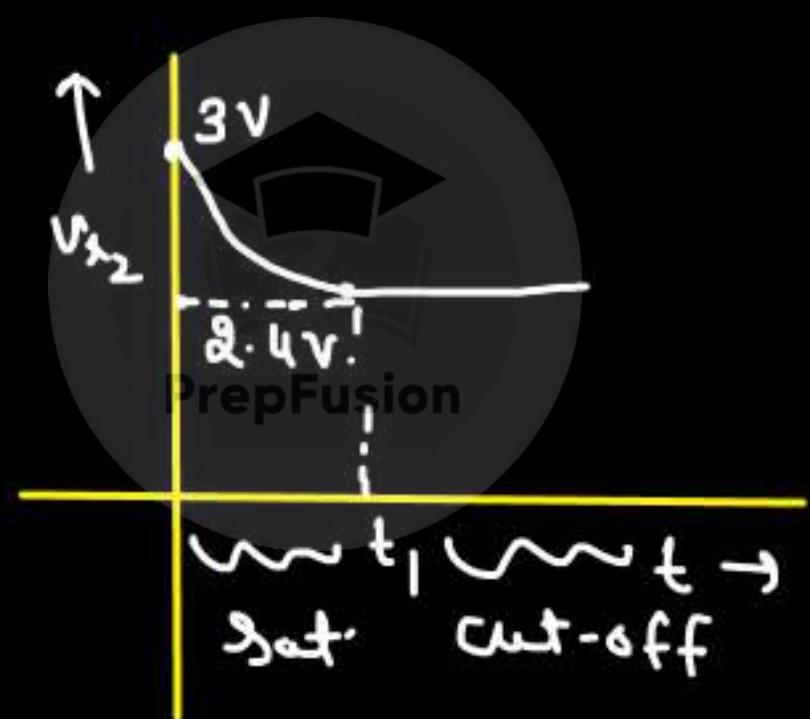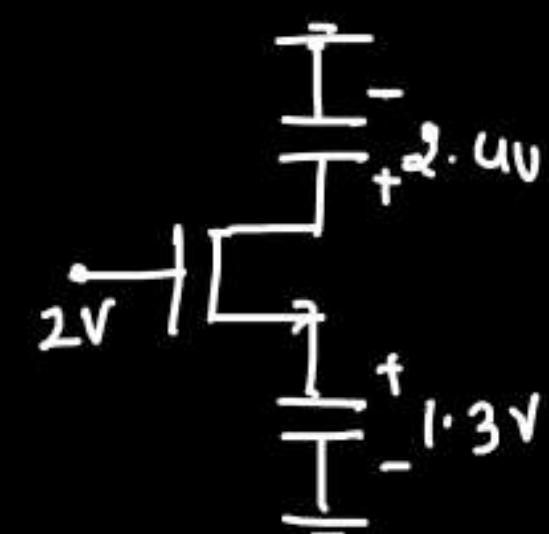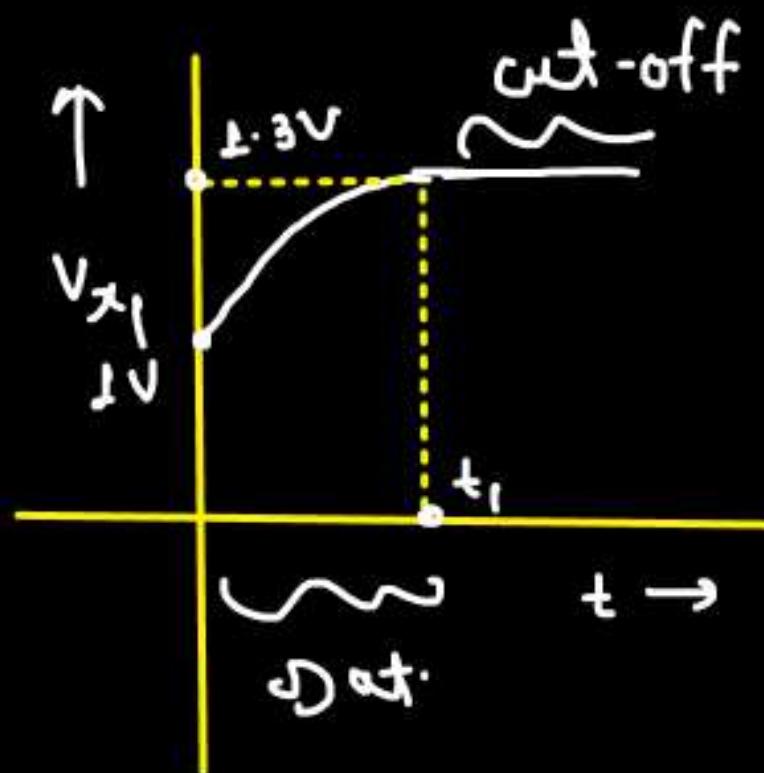
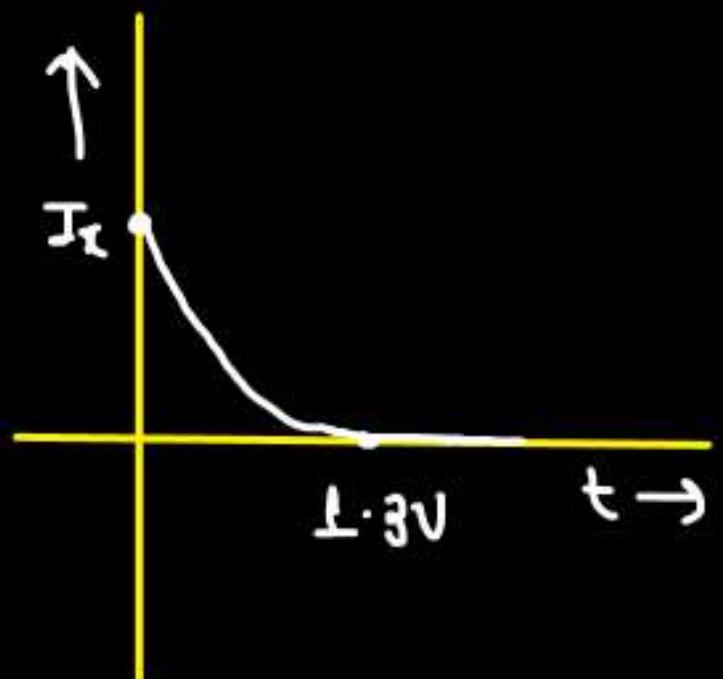
$$\begin{aligned} V_{DS} &= 1.1V \\ V_{GS} &= 0.7V \\ V_{OV} &= 0 \end{aligned} \quad \boxed{V_{DS} > 0V} \quad \Rightarrow \text{sat.}$$



Q.

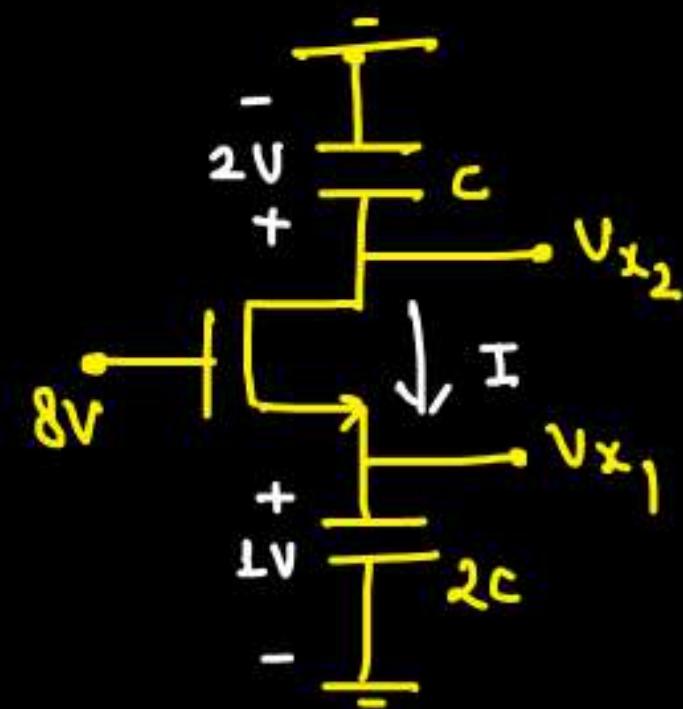

$$V_{x_1}(s.s) = 7V \quad \{ L \rightarrow 7 \}$$

$$\partial C(6V) = C(\Delta V_C)$$

$$\Delta V_C = 12V$$

C is discharging

$$V_{x_2}(s.s) = 2 - 12 = -10V$$

$$V_{x_2}(t=0^-) = 2V$$


$$V_{x_1}(t=0^-) = LV$$

$$V_T = LV$$

Find s.s. V_{x_1} and $V_{x_2} = ?$



$$V_{DS} = -10 - 7 = -17V \quad X$$

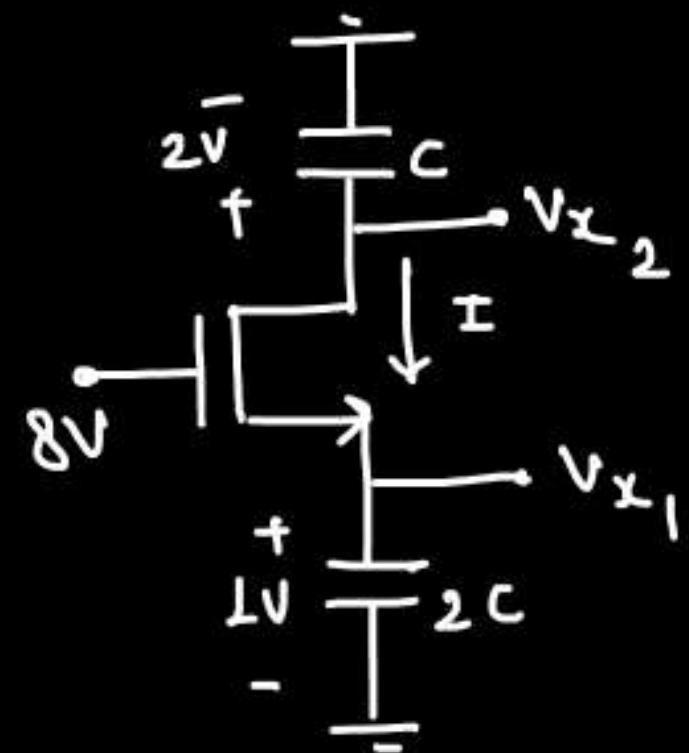

$C \rightarrow$ discharging
 $2C \rightarrow$ charging

$$I_{2C} = I_C$$

$$\Delta Q_{2C} = \Delta Q_C$$

$$2C (\Delta V_{2C}) = C (\Delta V_C)$$

$$\Delta V_C = 2 \Delta V_{2C}$$

Let $\Delta V_{2C} = x \Rightarrow 2C$ is gaining x voltage

$$V_{x1} (\text{ss}) = 1 + x$$

if 2c gains x voltage \Rightarrow c loses $2x$ voltage

$$V_{X_2}(\text{S.S.}) = 2 - 2x$$

@ S.S. $\Rightarrow V_{DS} = 0 \quad \{ I = 0 \}$

$$V_{X_2} - V_{X_1} = 0$$

$$V_{X_2} = V_{X_1}$$

$$2 - 2x = 1 + x$$


$$x = \frac{1}{3}V$$

$$V_{X_1}(\text{S.S.}) = 1.33V$$

$$V_{X_2}(\text{S.S.}) = 1.33V$$



Q.



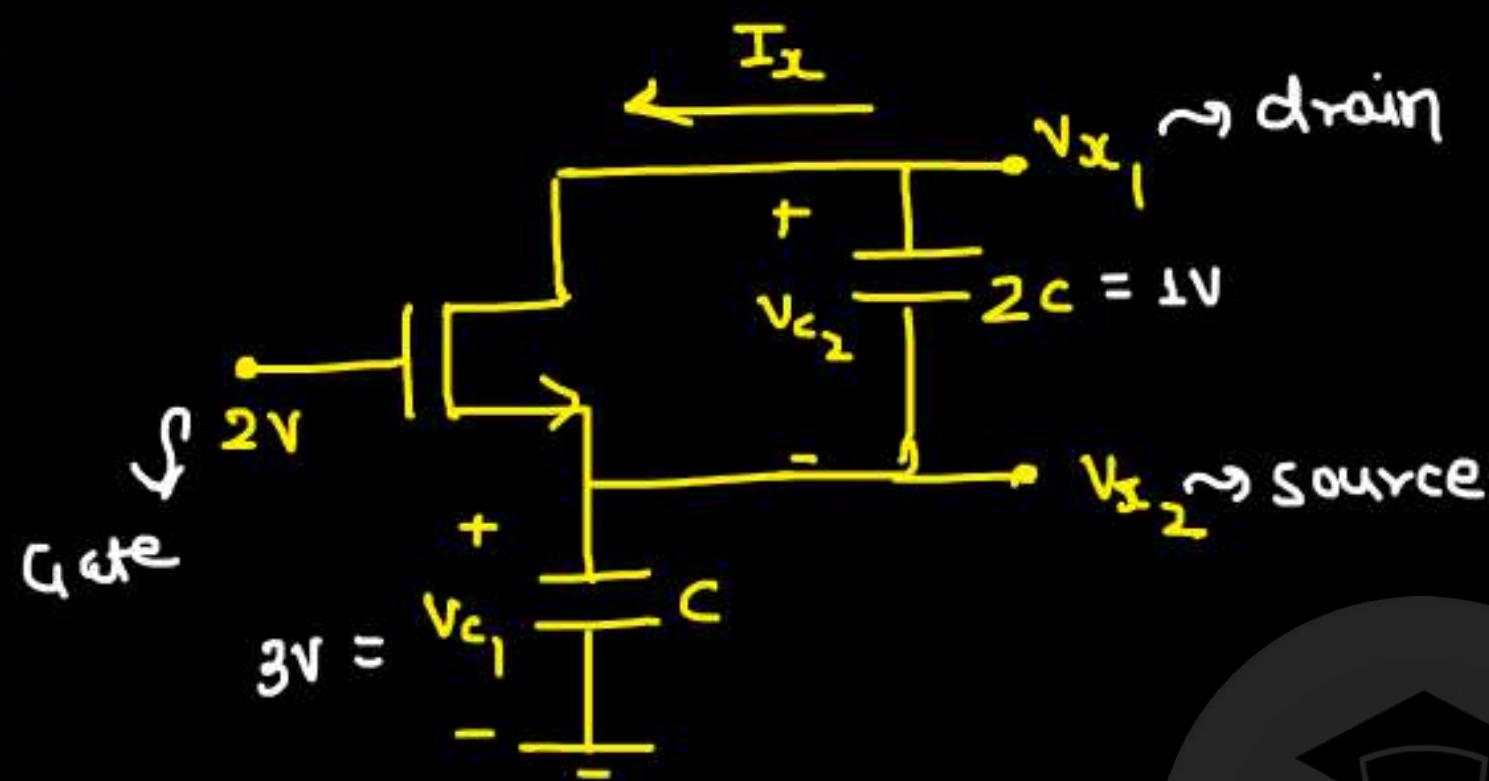


$$V_{x_1}(t=0^+) = 4V \sim \text{Drain}$$


$$V_{x_2}(t=0^+) = 3V \sim \text{source}$$

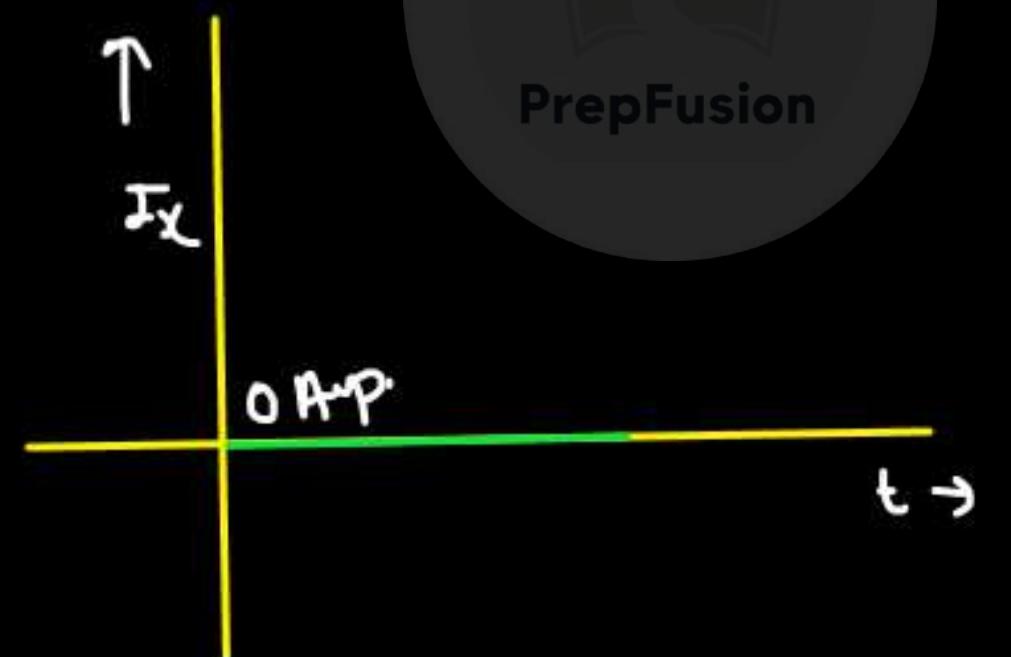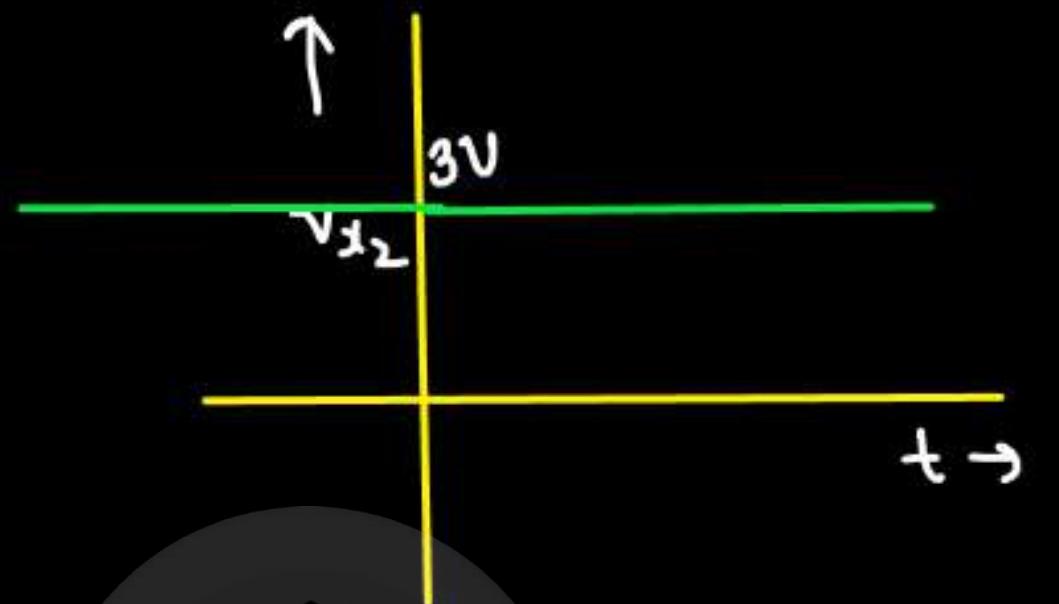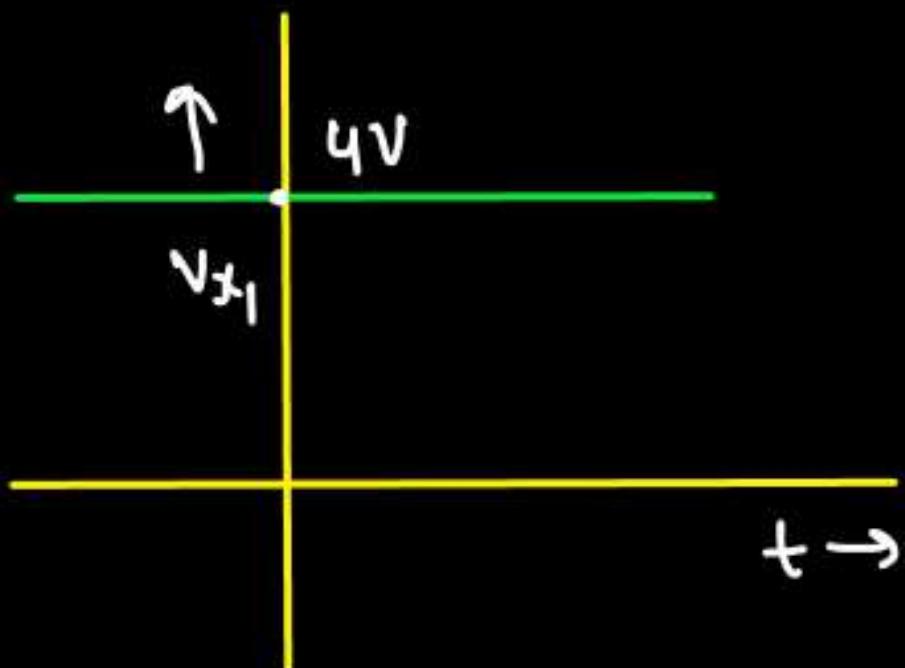$V_{GS} = 2 - 3 = -1V < V_T \Rightarrow \text{MOS doesn't even turn ON} \Rightarrow I_x = 0 \Rightarrow \text{ss.}$





Q.

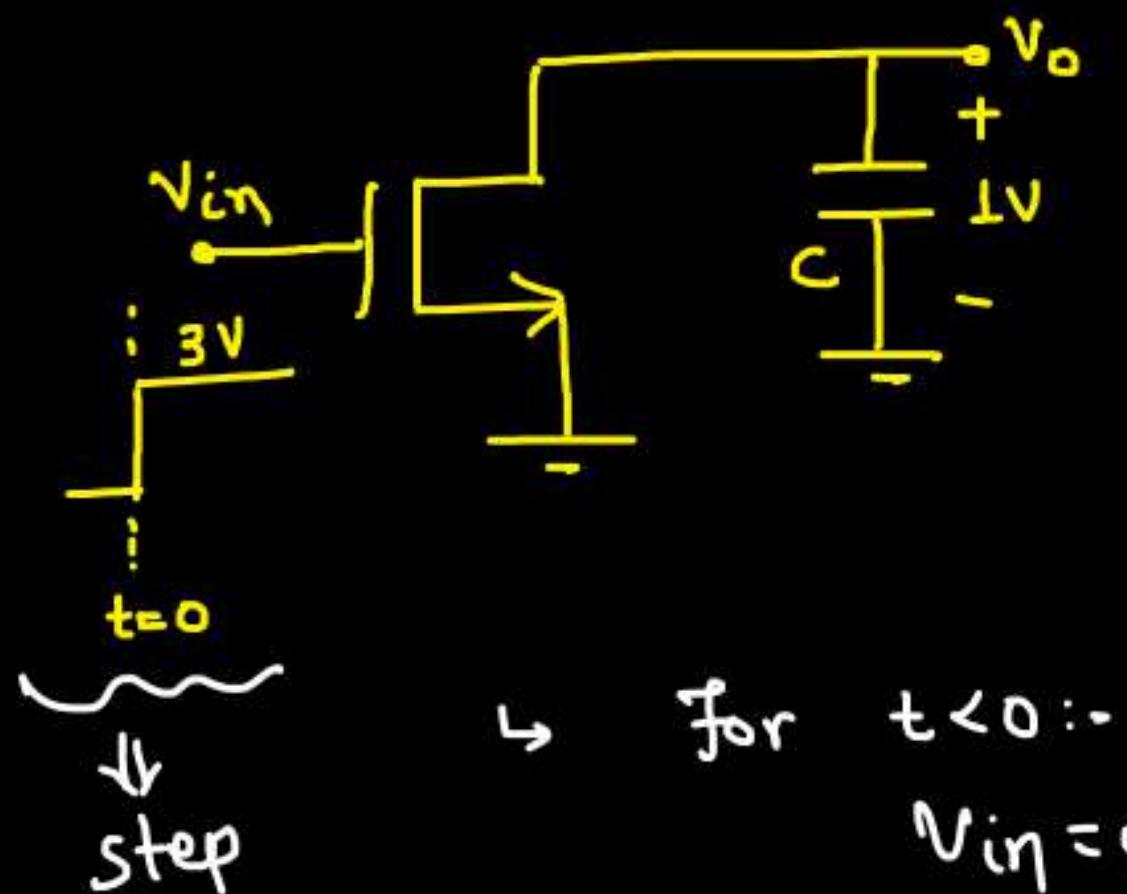

V_o v/s $t = ?$

$$V_T = 1V$$

↳ for $t < 0$:-

$$V_{in} = 0V$$

$$V_{qs} = 0V$$


PrepFusion
⇒ NO current

$$V_o(t=0^-) = V_c(t=0^-) = 1V$$

for $t > 0$:-

@ $t=0^+$

$$V_{in} = 3V$$

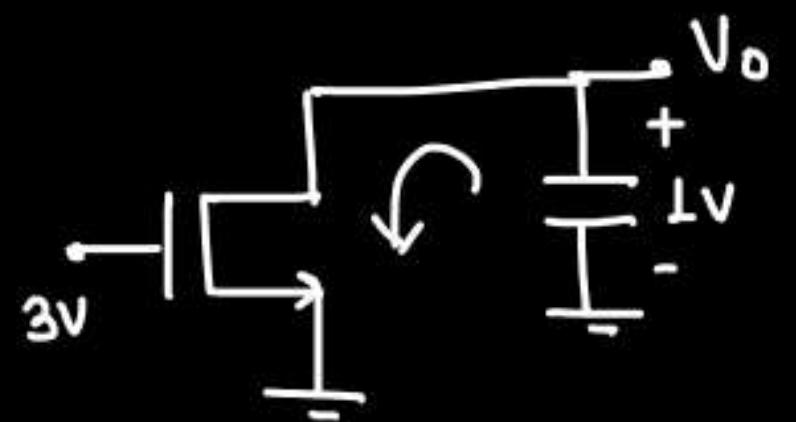

@ $t=0^+$



$$V_{DS} = V_O = 1V$$

$$V_{GS} = 3V \rightarrow$$


$$V_T = 1V$$

$$V_{OV} = 2V$$

⇒ linear region

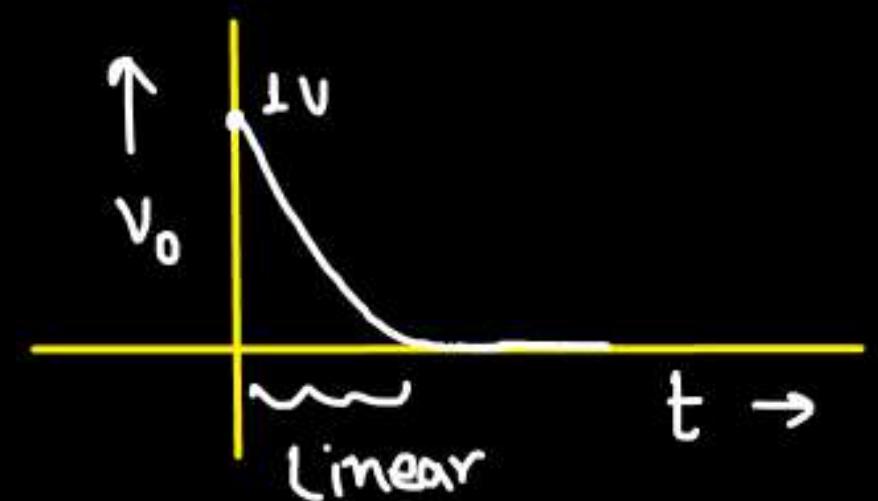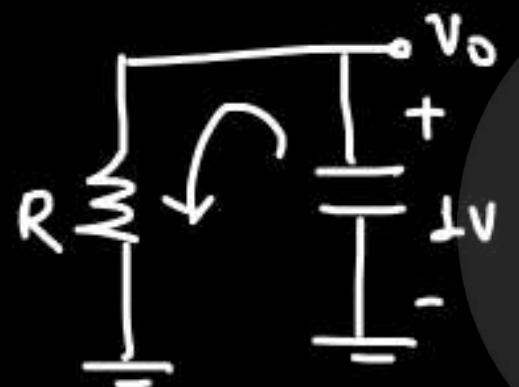



Q.

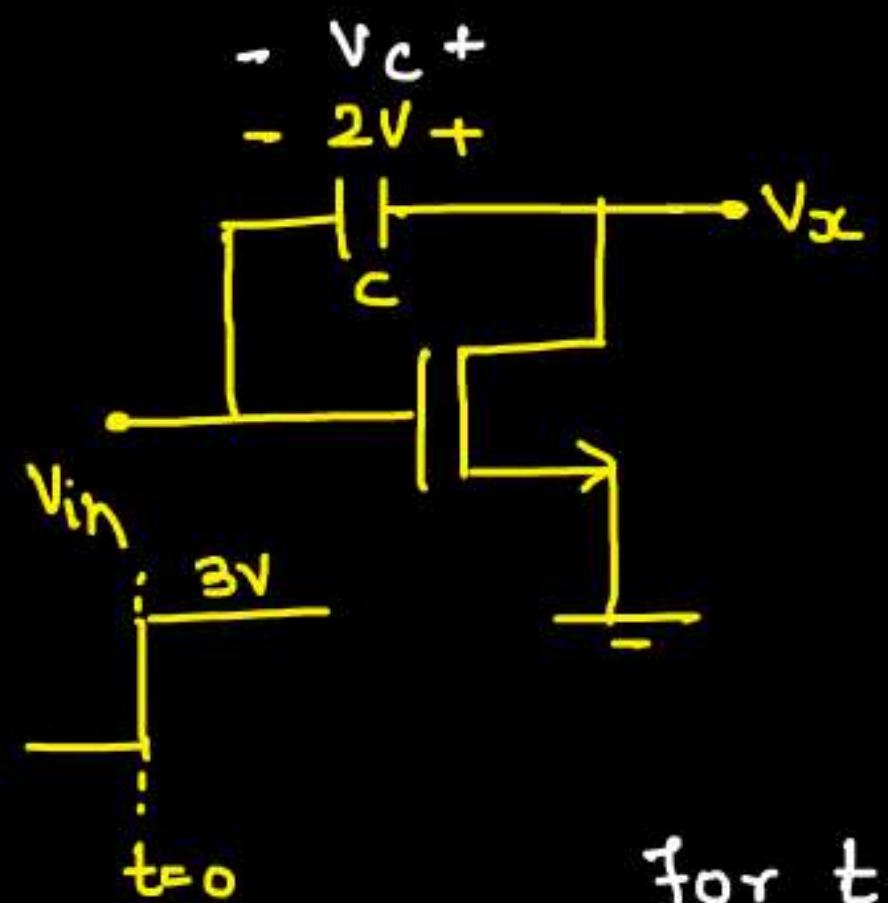

$$V_T = 1V$$

$$V_x \propto e^{-t/\tau} = ?$$

for $t < 0$:

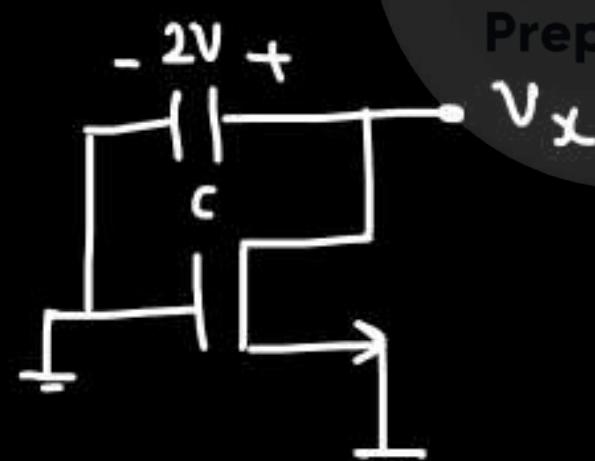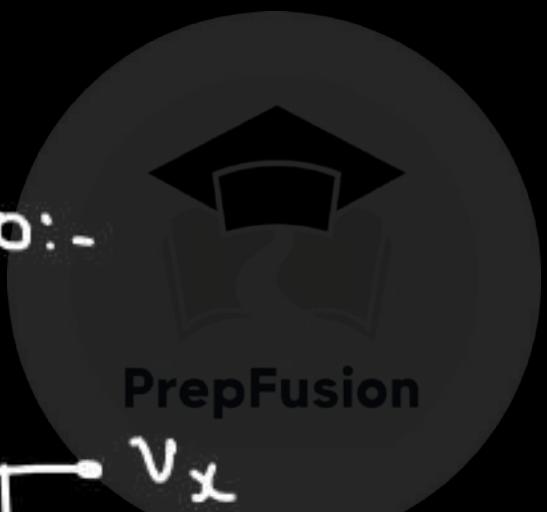

$$V_{GS} = 0V$$


$$\Rightarrow I_D = 0$$

S.C.

$$V_c(t=0^-) = 2V = V_c(t=0^+)$$

$$V_x(t=0^-) = 2V$$

for $t > 0$

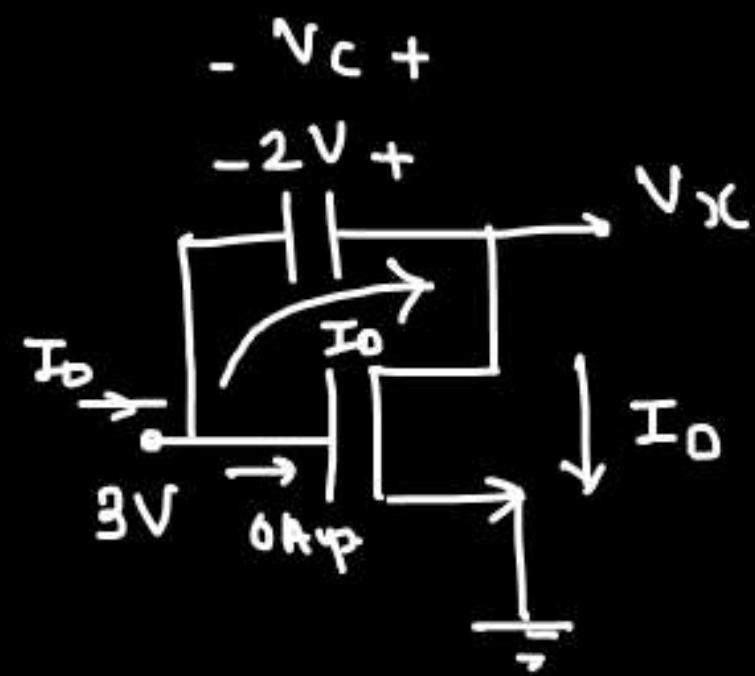

$$V_x(t=0^+) = 5V$$

$$V_{GS} = 3V, V_T = 1V \Rightarrow ON$$


$$V_{DS} = 5V$$

$$V_{OV} = 2V$$

$$V_{DS} > V_{OV} \Rightarrow Sat.$$

PrepFusion

$$(I_0) \propto K [2]^2$$

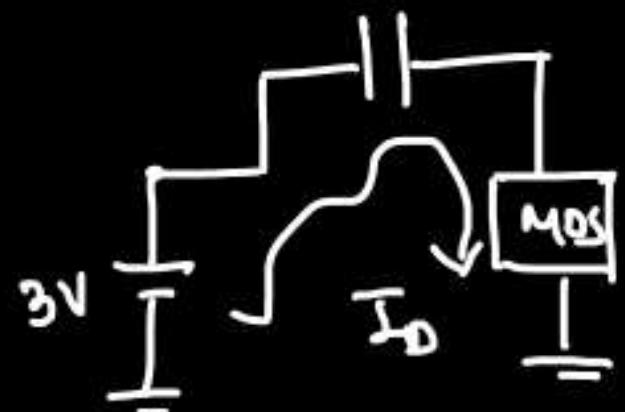

Cap. is getting charged in opposite direction.

V_C value will decrease.

$$V_x = 3 + V_c \Rightarrow V_x \text{ goes down}$$



$$V_C = Q - \frac{1}{C} \int I \cdot dt$$

$$V_C = Q - \frac{I}{C} t$$

$$V_{DS} = V_X$$


$$V_{DS} = 2$$

$V_X < 2V \Rightarrow$ Linear
region

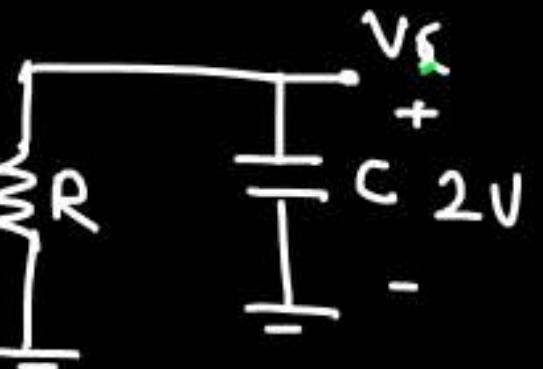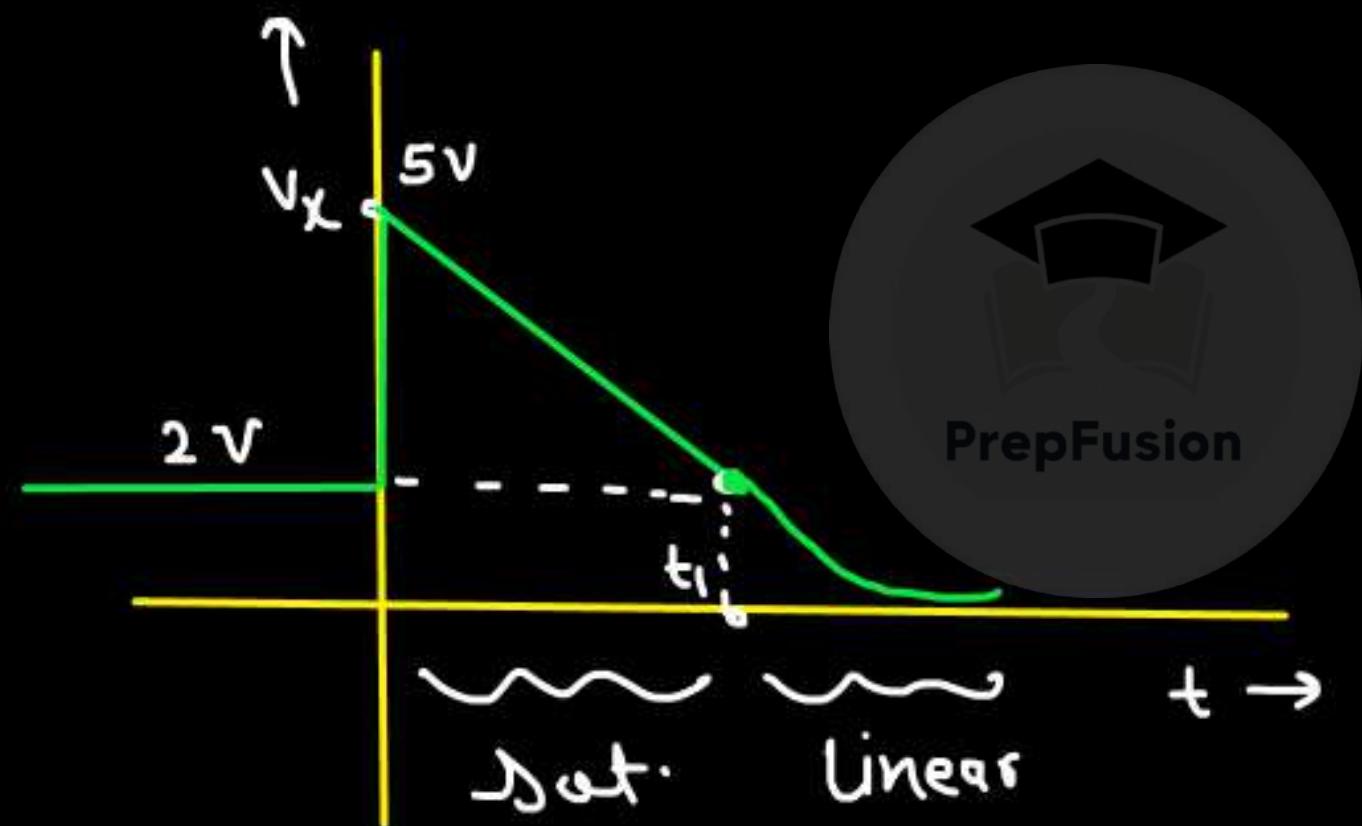

$$V_C(s \cdot s^-) = -3V$$

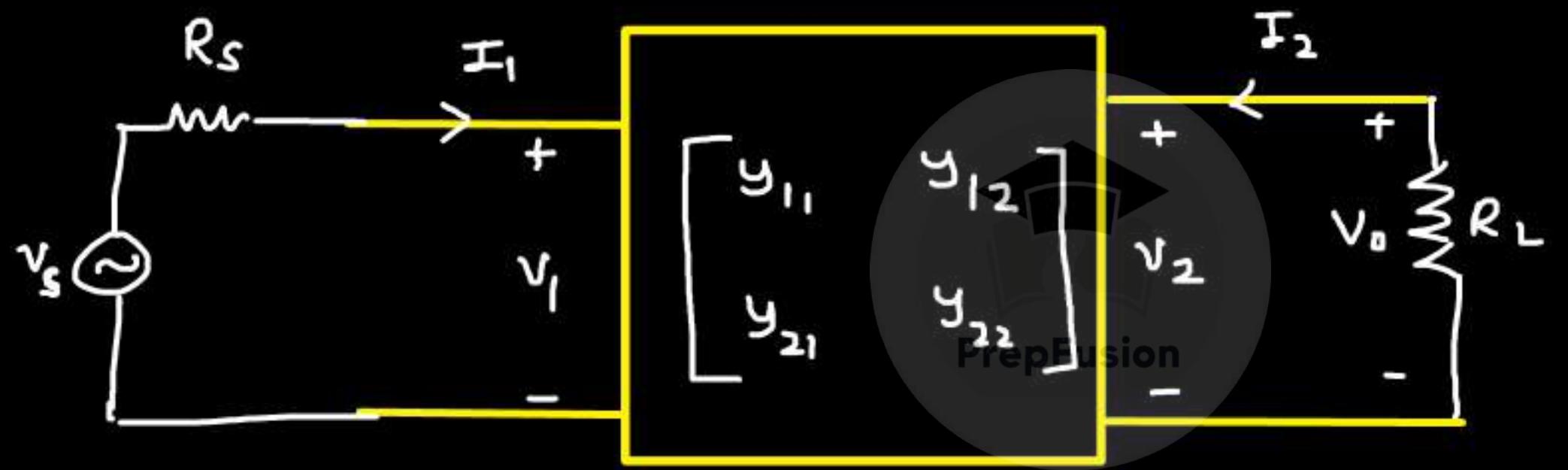
Q. In a two port N/w, find the cond'n on Y-parameter for which the voltage gain is maximum.



$\frac{V_o}{V_s} \rightarrow \text{maximize}$

$$\rightarrow I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (1)}$$
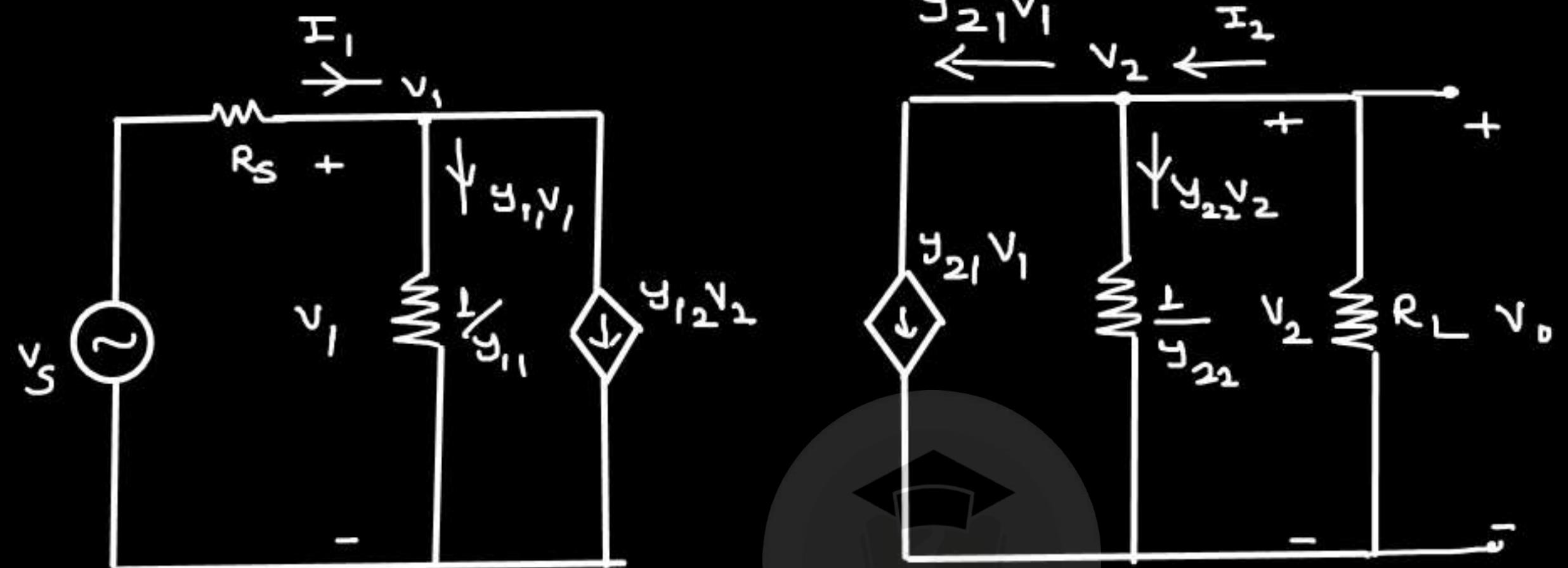
$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (2)}$$




PrepFusion

$\frac{V_o}{V_s} \rightarrow \text{maximize}$

$$I_1 = Y_{11}v_1 + Y_{12}v_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21}v_1 + Y_{22}v_2 \quad \text{--- (2)}$$

1. maximize V_1

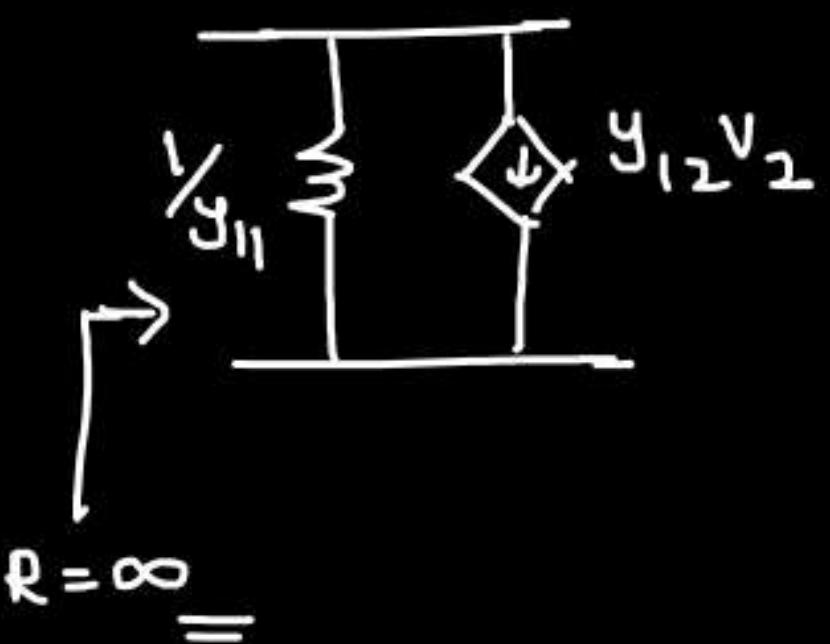

if $R = \infty$

$$V_1 = V_S$$

$$Y_{11} = 0, Y_{12} = 0$$

$$Y_{11} = \min, Y_{12} = \min$$

PrepFusion

2. maximize V_o / minimize $Y_{22}V_2$

$$\Rightarrow Y_{22} = 0$$

$$Y_{22} = \min$$

$$V_o = -Y_{21} V_i R_L \quad \text{--- (1)}$$

$$V_i = V_s$$

$$\frac{V_o}{V_s} = -Y_{21} R_L$$

★★


To have \max^m gain

$$Y_{21} = \max^m$$

⇒ $Y_{11} = \min, Y_{12} = \min, Y_{22} = \min, Y_{21} = \max^m$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (2)}$$
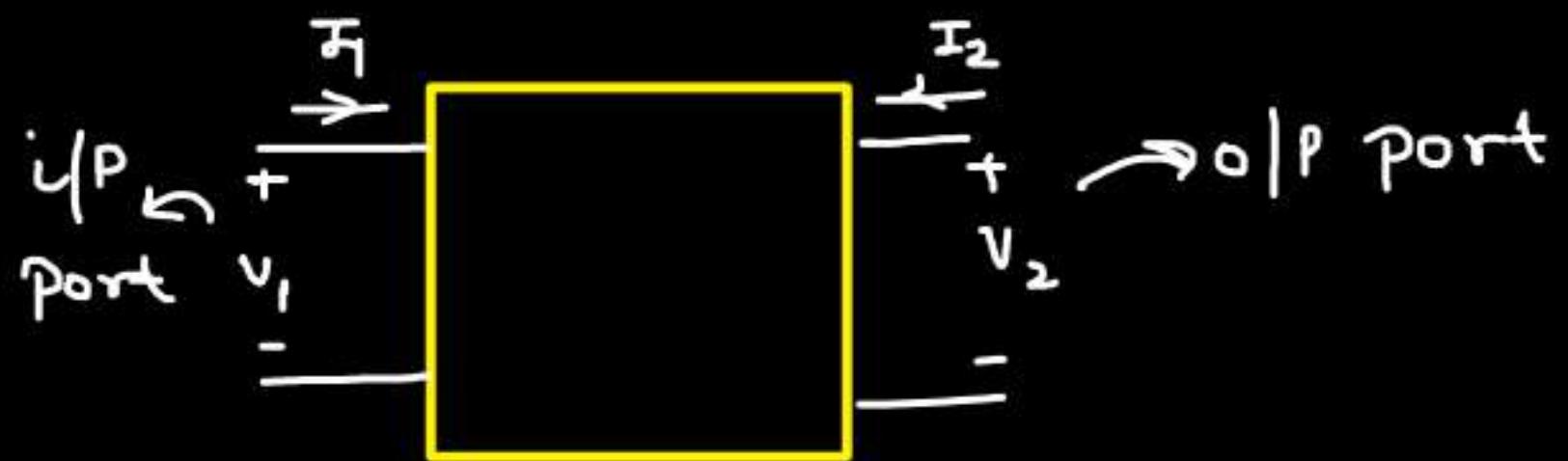
$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$



$$Y_{11} = \frac{\partial i_1}{\partial v_1} \Big|_{v_2=\text{const.}}$$


$$Y_{12} = \frac{\partial i_1}{\partial v_2} \Big|_{v_1=\text{const.}}$$



$$Y_{21} = \frac{\partial i_2}{\partial v_1} \Big|_{v_2=\text{const.}} = g_m = \text{large}$$

$$Y_{22} = \frac{\partial i_2}{\partial v_2} \Big|_{v_1=\text{const.}} = \frac{1}{\text{o/p resistance}} = \text{low}$$

Consider a MOS :-

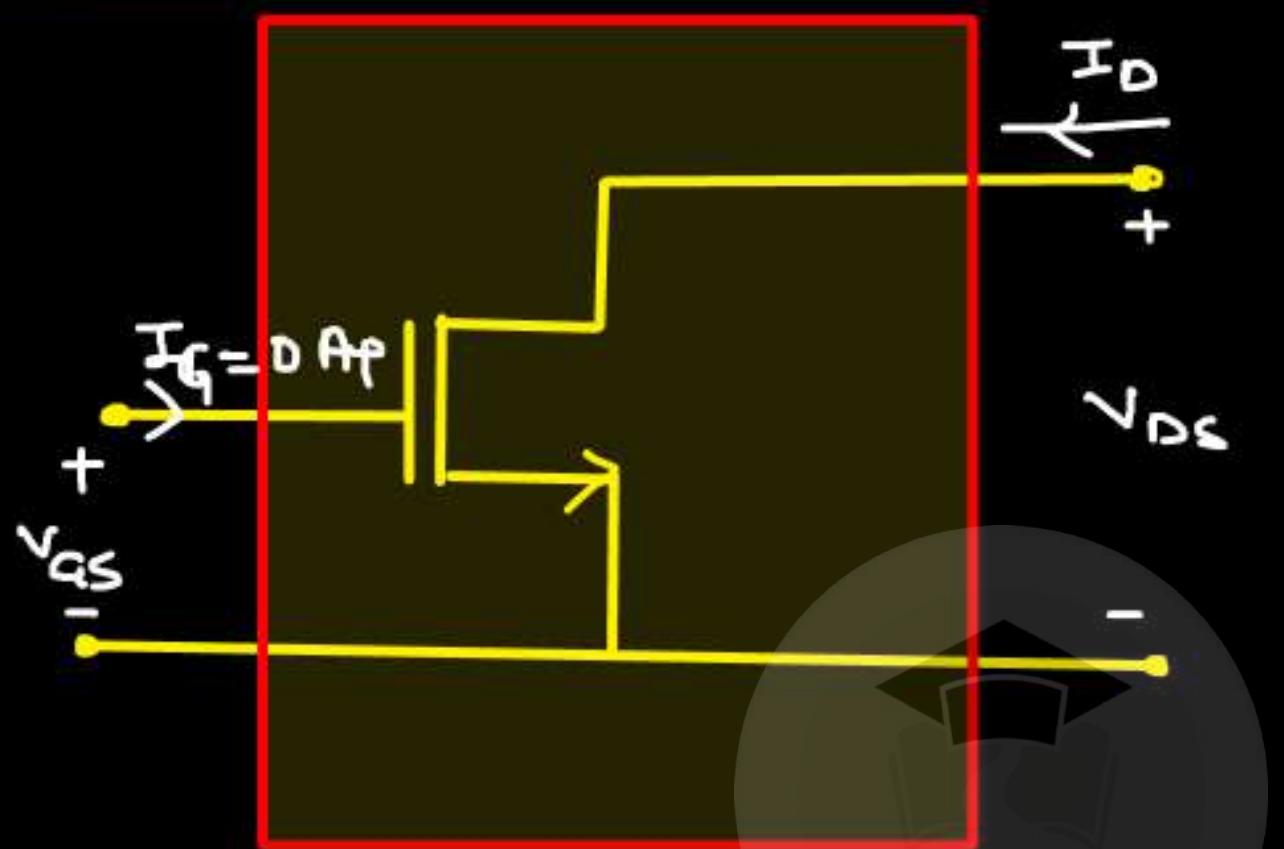

For both Triode and Sat. region

$$\frac{\partial I_G}{\partial V_{GS}} = g_{11} = D \quad \text{--- (1)}$$

$$\frac{\partial I_G}{\partial V_{DS}} = g_{12} = D \quad \text{--- (2)}$$

$\frac{\partial I_D}{\partial V_{GS}}$ for sat. and Triode

$$(g_m)_{\text{Triode}} = \frac{4\pi C_0 \times w}{L} (V_{DS})$$

In case of Triode region, $V_{DS} \ll V_{GS} - V_T$

$\Rightarrow V_{DS}$ is ~~Pre Junction~~ very low

g_m will be very low in Triode region


$$(\partial m)_{\text{Sat.}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)$$

$$(I_D)_{\text{Sat.}} = \frac{\mu_n C_{ox} W}{2L} \left[(V_{GS} - V_T)^2 \right]$$

I_D and V_{GS} follow square law relation \Rightarrow slope $\frac{\partial I_D}{\partial V_{GS}}$ will be High

★*

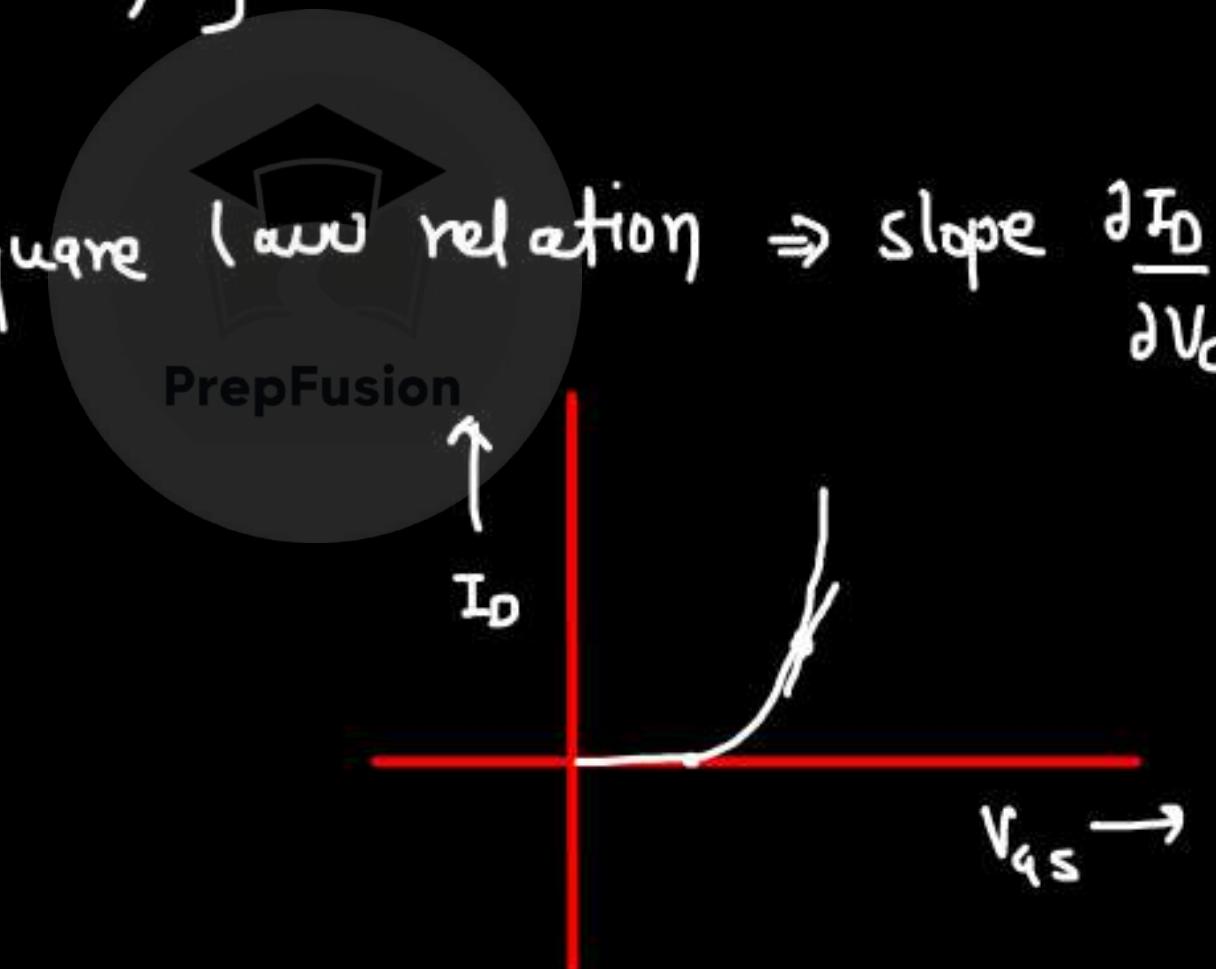
$$(\partial m)_{\text{Sat.}} > (\partial m)_{\text{Triode}}$$



$\frac{\partial I_D}{\partial V_{DS}}$ for linear and sat. region :-

$$\left(\frac{\partial I_D}{\partial V_{DS}} \right)_{\text{deep-linear}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)$$
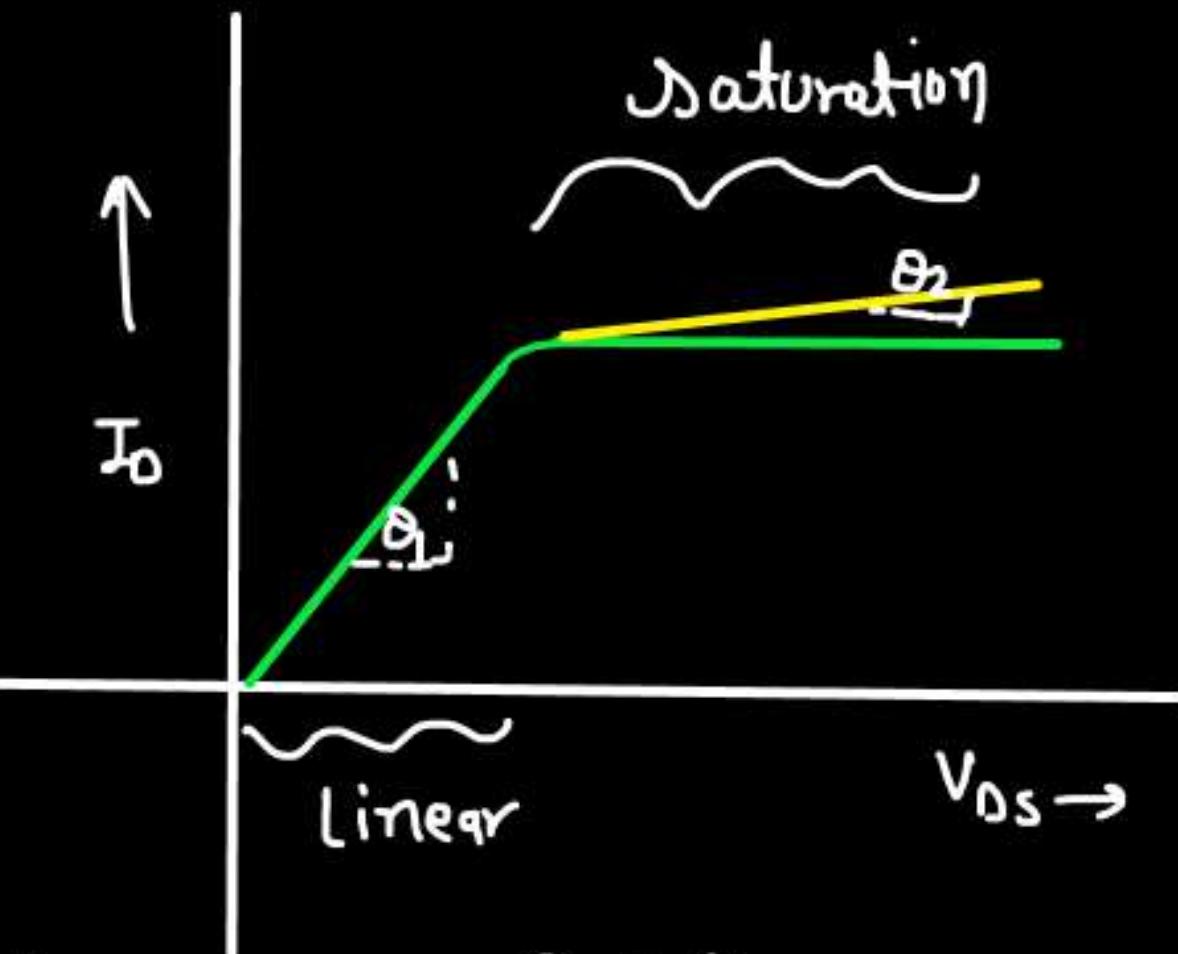
$$\left(\frac{\partial I_D}{\partial V_{DS}} \right)_{\text{sat.}} \begin{cases} \frac{1}{\lambda(I_D)} & (\lambda \neq 0) \\ \infty & (\lambda = 0) \end{cases}$$



For sat. $\frac{\partial I_D}{\partial V_{DS}} \rightarrow \text{less} \Rightarrow \frac{\partial V_{DS}}{\partial I_D} \rightarrow \text{high}$

$$\theta_1 > \theta_2$$

For Sat. region ,

O/P resistance is High



⇒ Why we use MOSFET in sat. region for Amplification ?

- Because , in sat. region , we get Higher g_m and Higher O/P resistance that maximizes our voltage gain .

PrepFusion

⇒ How to bias a MOS for amplification?

Try-1

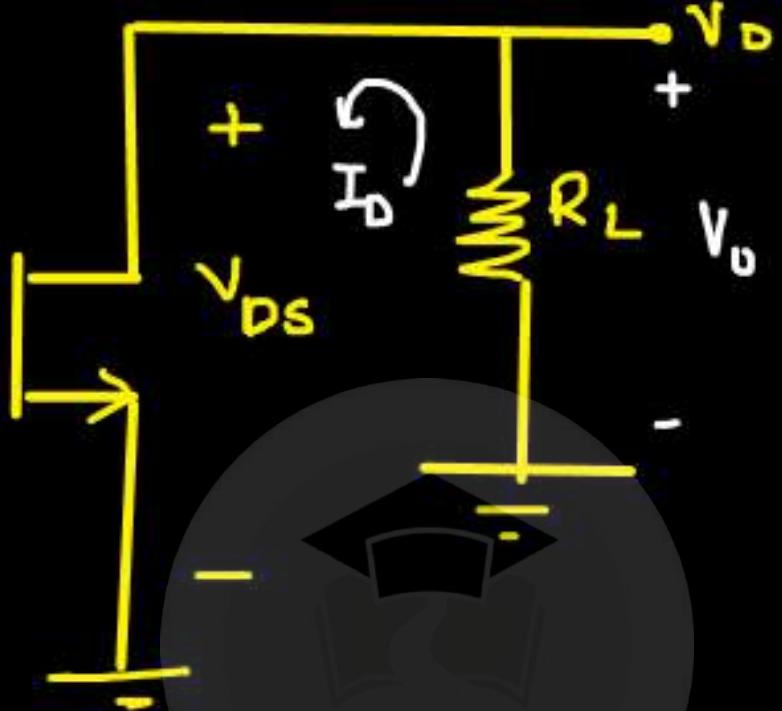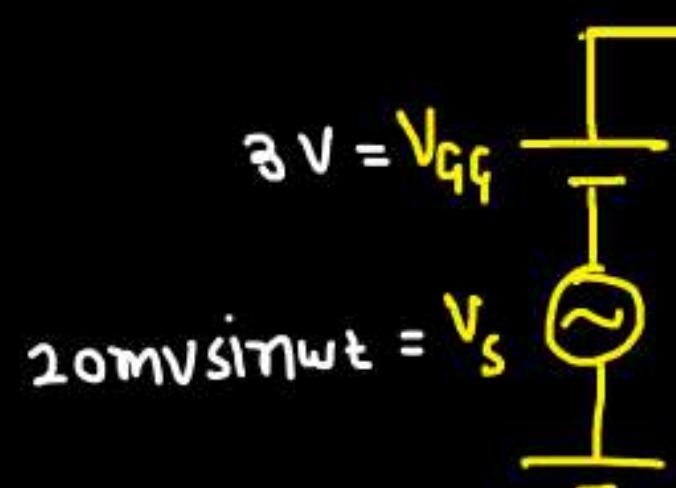

for sat. →

$$V_{DS} > V_{GS} - V_T$$

$$V_{DS} > 3 + 20mV \sin \omega t - 1$$

$$V_{DS} > 2V$$

$$V_{DS} = - I_D R_L$$

$$= \text{negative}$$




NOT DESIRED

[MOS will be in CUT-OFF]

Try-2

Fixing V_{DS}

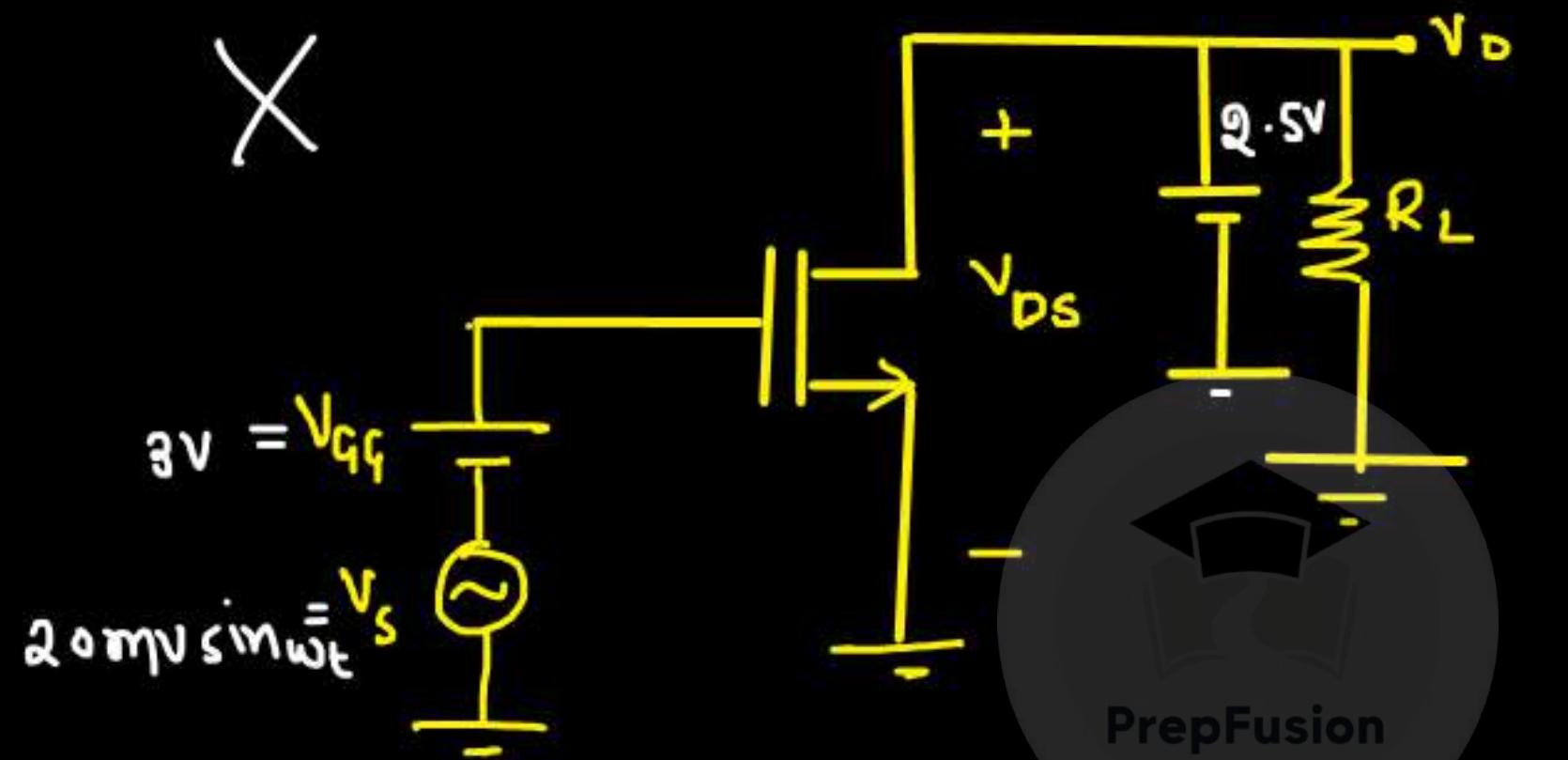

PrepFusion

$$V_D = 2.5V \rightarrow \text{fixed}$$





NOT working as
an amplifier =


Here ,

$$V_{DS} > V_{QS} - V_T \Rightarrow \text{sat. V'}$$

Try-3

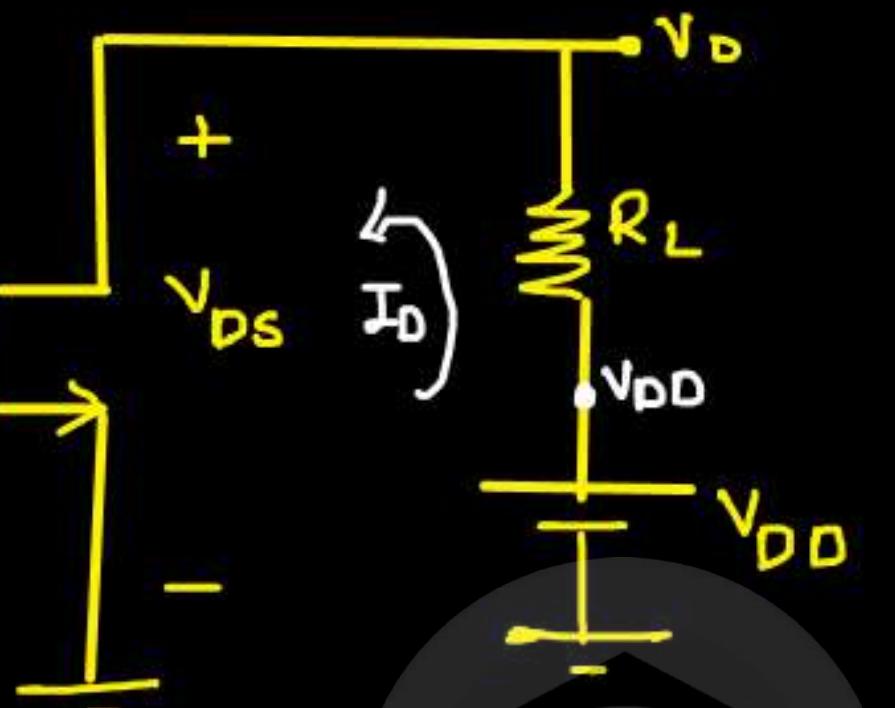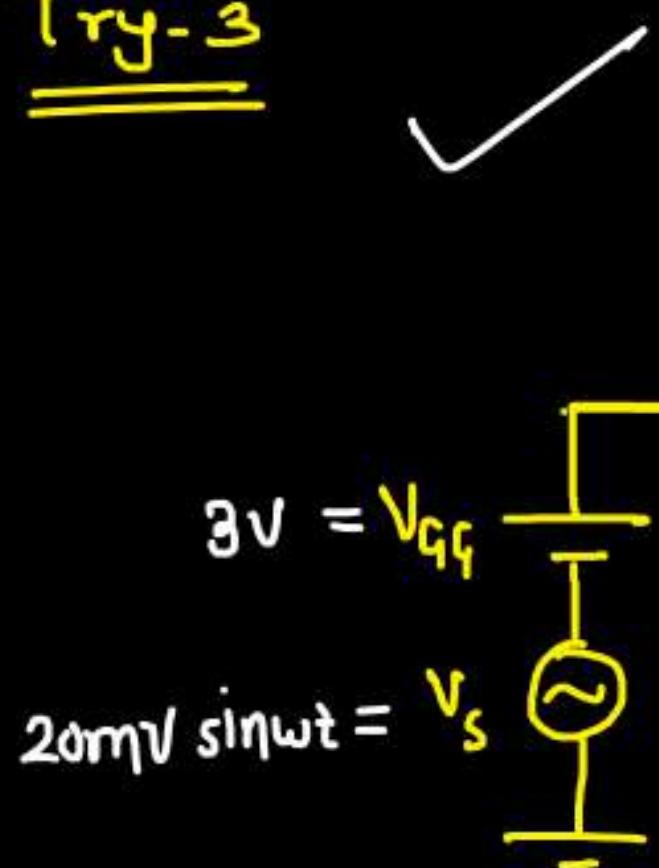

$$V_T = 1V$$

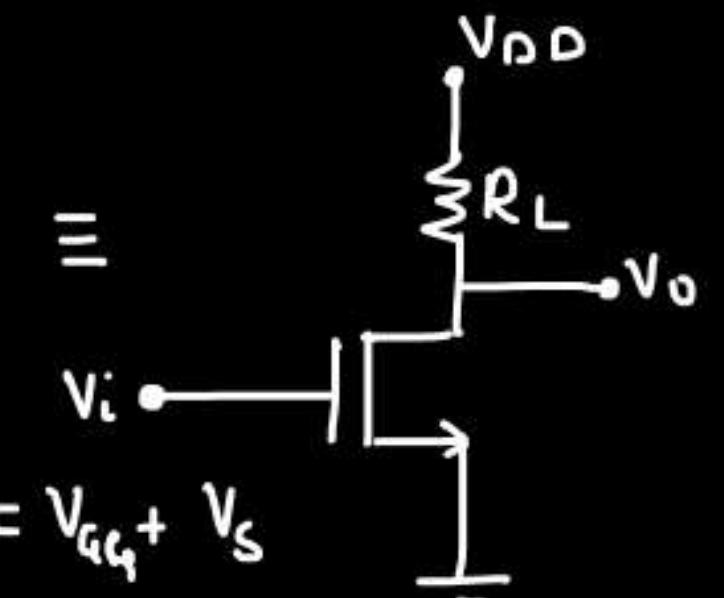


$V_{DS} = V_{DD} - I_D R_L$

You can adjust V_{DD} such that your MOS works in saturation region.

also, O/P is NOT fixed.

Small Signal Analysis of MOS Amplifiers :-

MOS in saturation

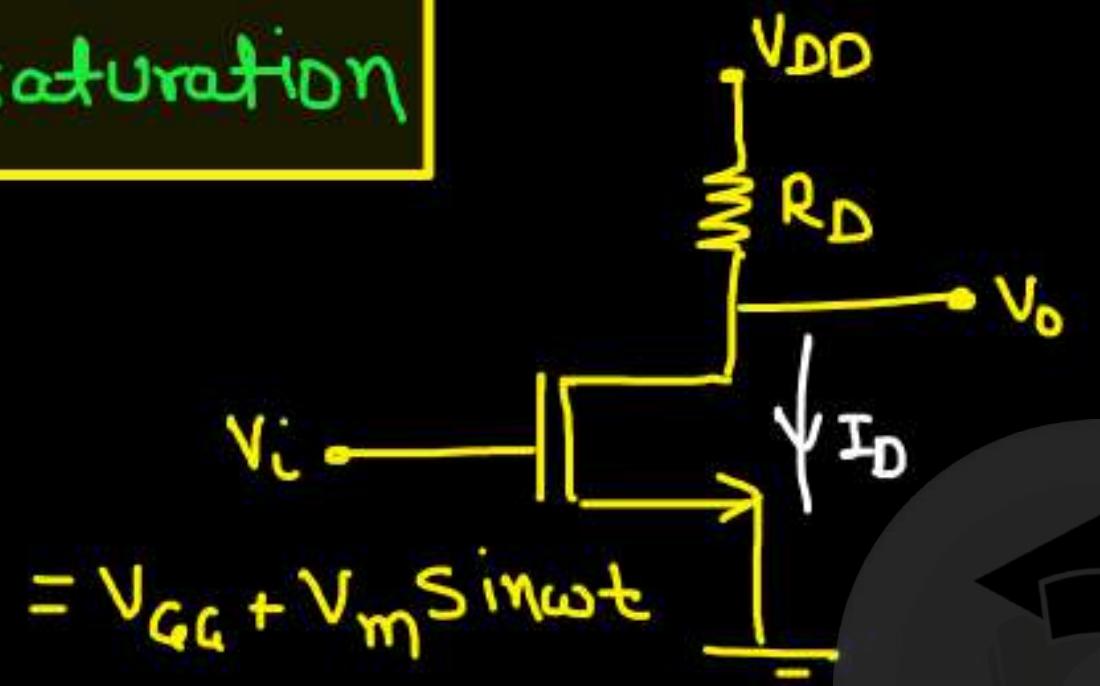

$$V_i = V_{GG} + V_m \sin \omega t$$

(dc) (ac) (V_{gs})

$V_{gs} = V_m \sin \omega t \rightarrow$ small signal ac input

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T]^2$$

$$= \frac{\mu_n C_{ox} W}{2L} [V_{GK} + V_m \sin \omega t - V_T]^2$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T + V_m \sin \omega t]^2$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T]^2 \left[1 + \frac{V_m \sin \omega t}{V_{GS} - V_T} \right]^2$$

↓
small $\left\{ (1+x)^2 \approx 1+2x \right\}$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T]^2 \left[1 + \frac{2V_m \sin \omega t}{V_{GS} - V_T} \right]$$

$$I_D = I_{DC} \left[1 + \frac{2V_m \sin \omega t}{V_{GS} - V_T} \right]$$

↓
Current if only V_{GS} (dc) was applied

$$I_D = I_{Dc} + \frac{2I_{Dc}}{V_{Gg} - V_T} V_m \sin \omega t$$

$$I_D = I_{Dc} + g_m V_{gs}$$

dc component
component

$\left\{ \begin{array}{l} V_{gs} = V_m \sin \omega t \\ = \text{small signal ac} \end{array} \right.$
i(p)


$$\begin{aligned} V_o &= V_{DD} - I_D R_D \\ &= V_{DD} - [I_{Dc} + g_m V_{gs}] R_D \end{aligned}$$

$$V_o = V_{DD} - I_{Dc} R_D - g_m V_{gs} R_D$$




DC AC

~~(I_D)_{ac} = $\underline{g_m V_{gs}} = i_d$~~ $\neq f(V_{DD}, V_{Gc})$
 $(V_o)_{ac} = -g_m V_{gs} R_D$


Method 2 (Understanding by Graph) :-

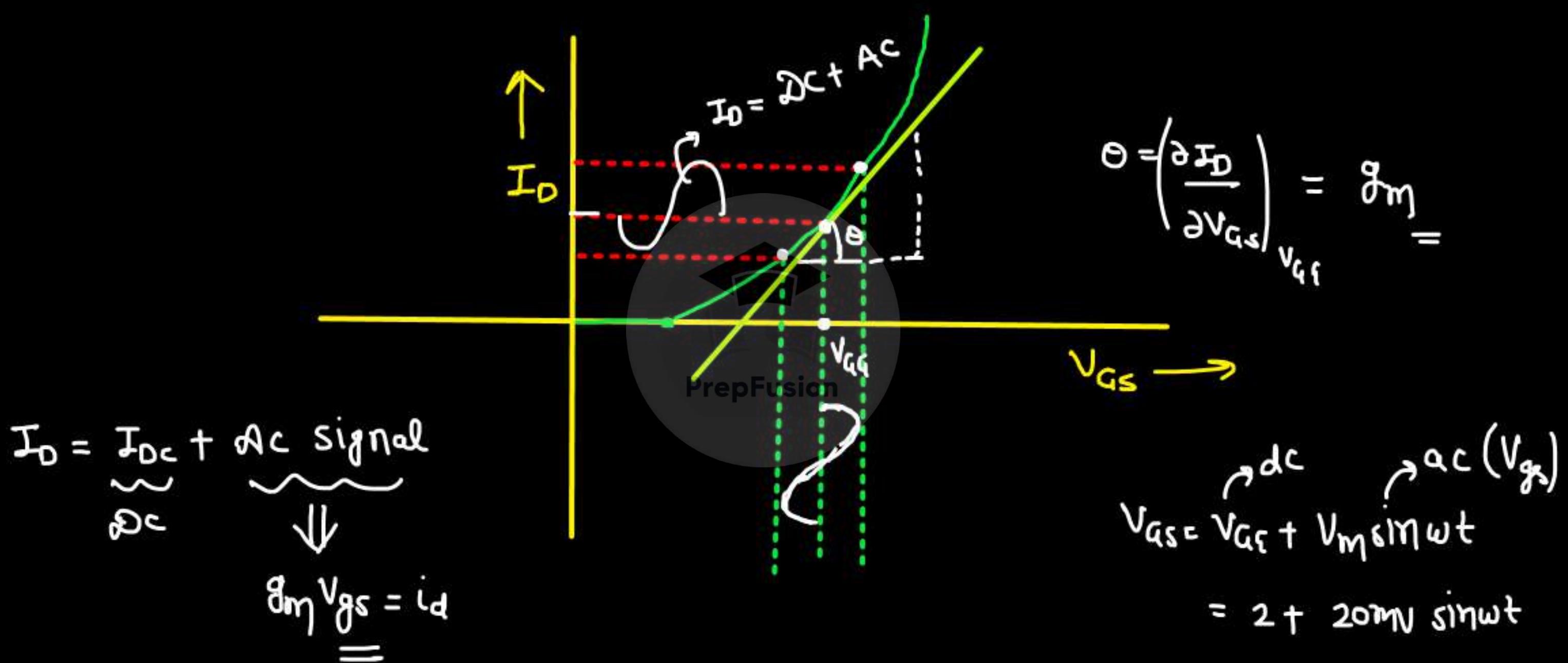

for Analysis Purpose :-

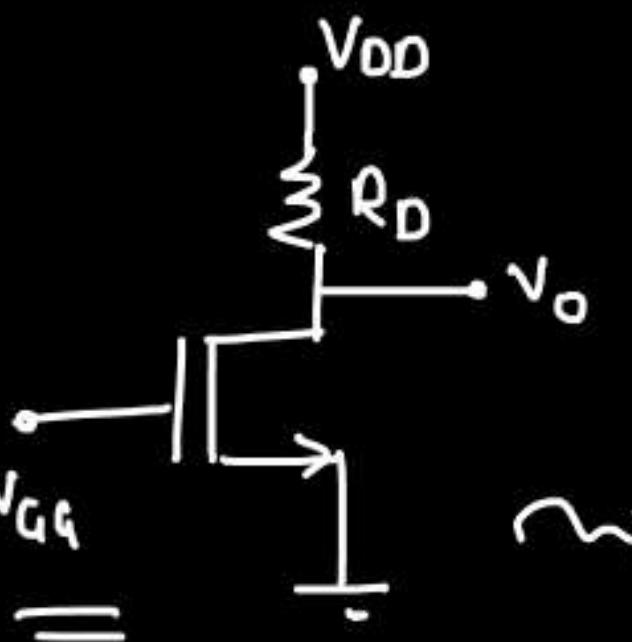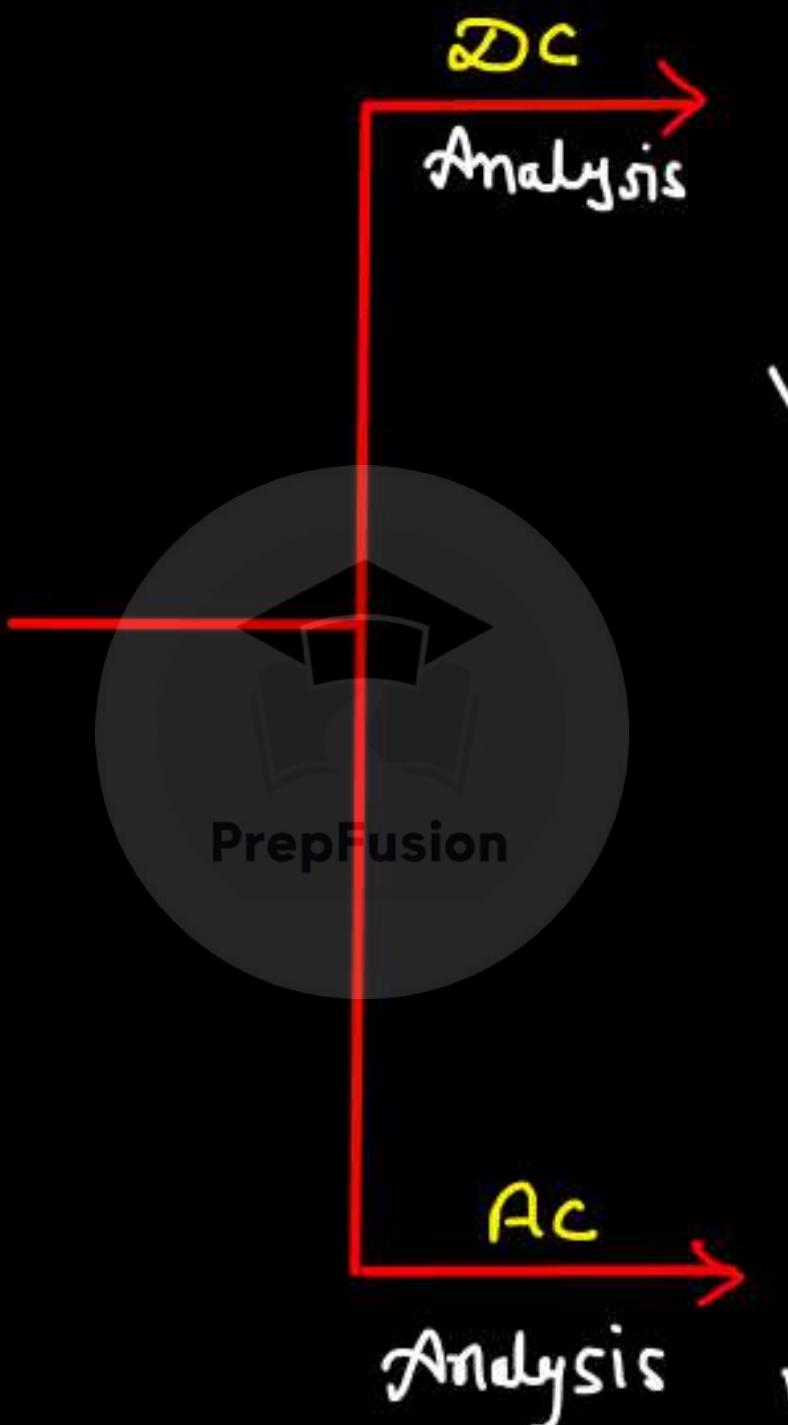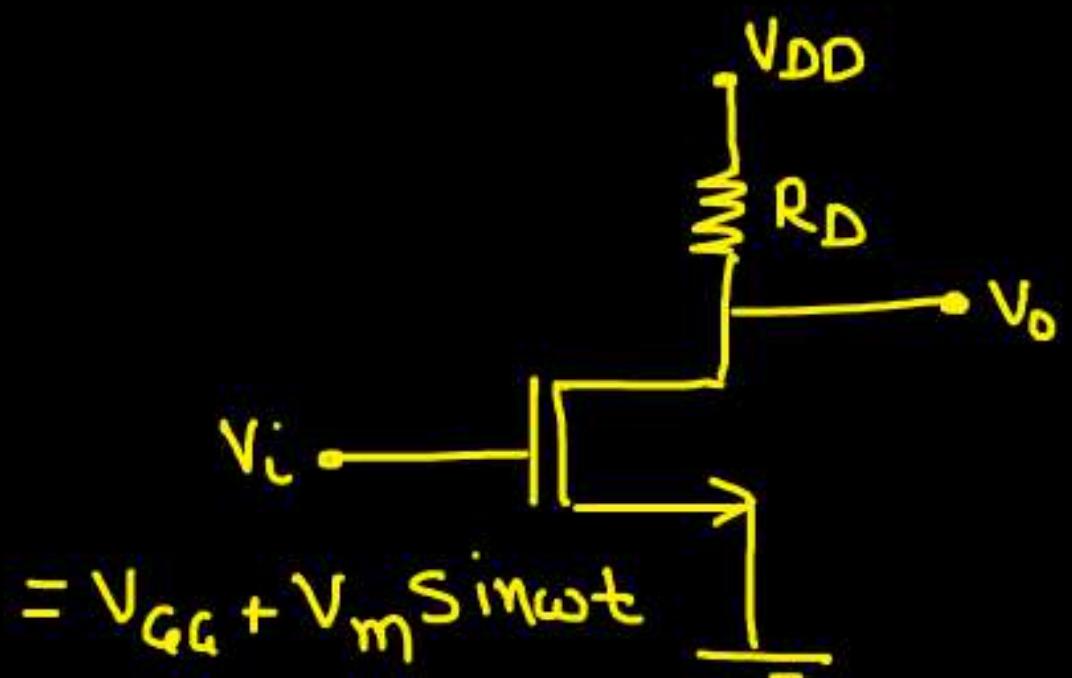
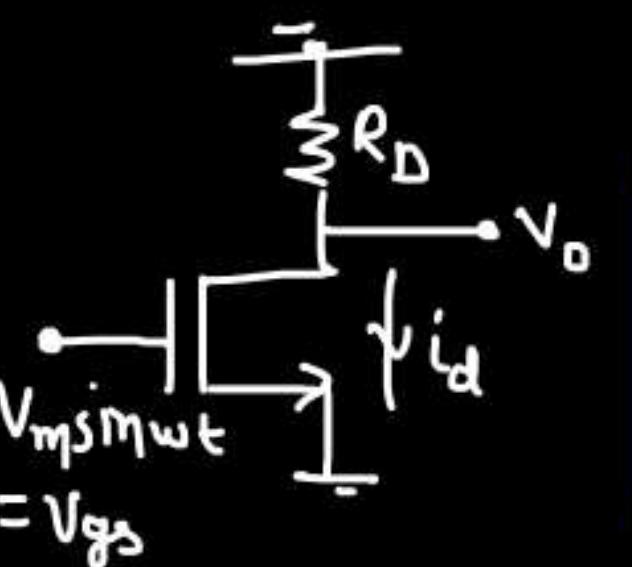
$$\approx g_m = \frac{2I_{DC}}{V_{GS} - V_T}$$




$$V_o = -i_d R_D$$

$$V_o = -g_m V_{GS} R_D$$


Small Signal Model of MOSFET:-

* AC Analysis:-

① Nullify all the dc sources.

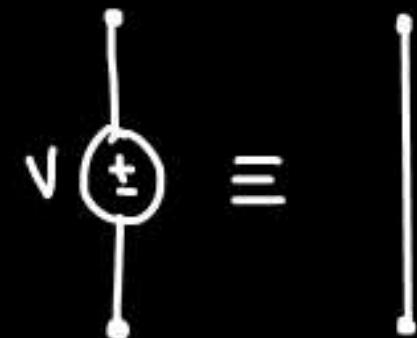

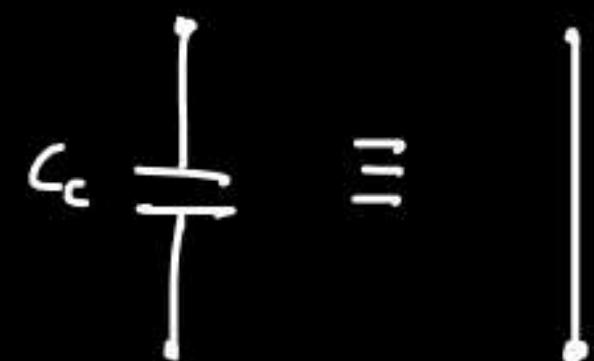② Coupling Cap. will be shorted. (Generally)




DC Analysis:-

- ① Nullify all the ac sources.
- ② Coupling cap. will be open circuited.


$$C_c \frac{1}{I} = I$$






NMOS: - (Small Signal Model)

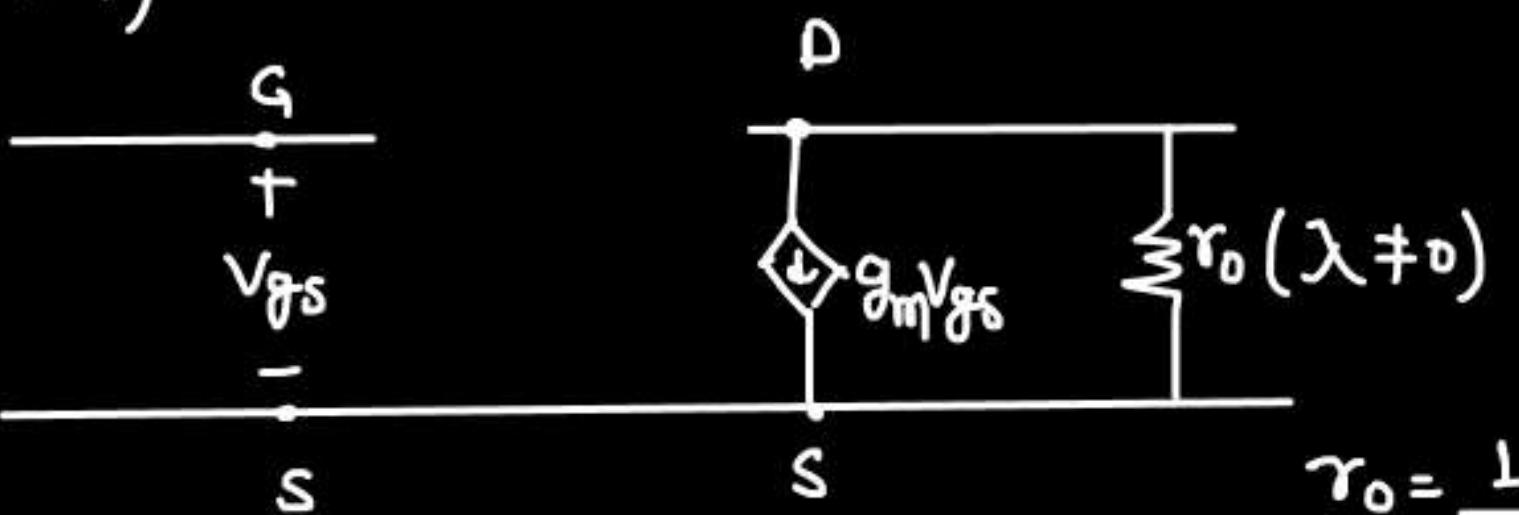




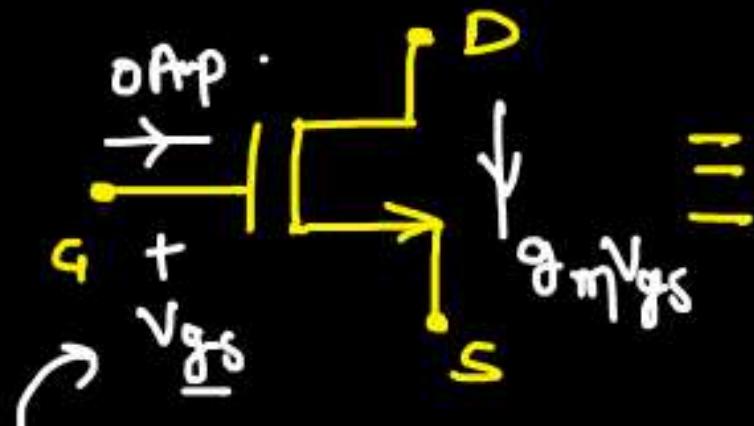
$$r_o = \frac{1}{\lambda(I_D)}_{\text{Sat. - ideal}}$$




Small signal voltage

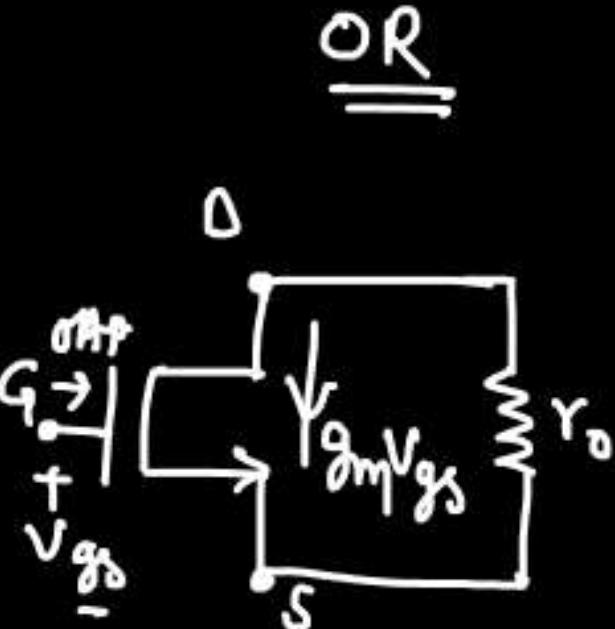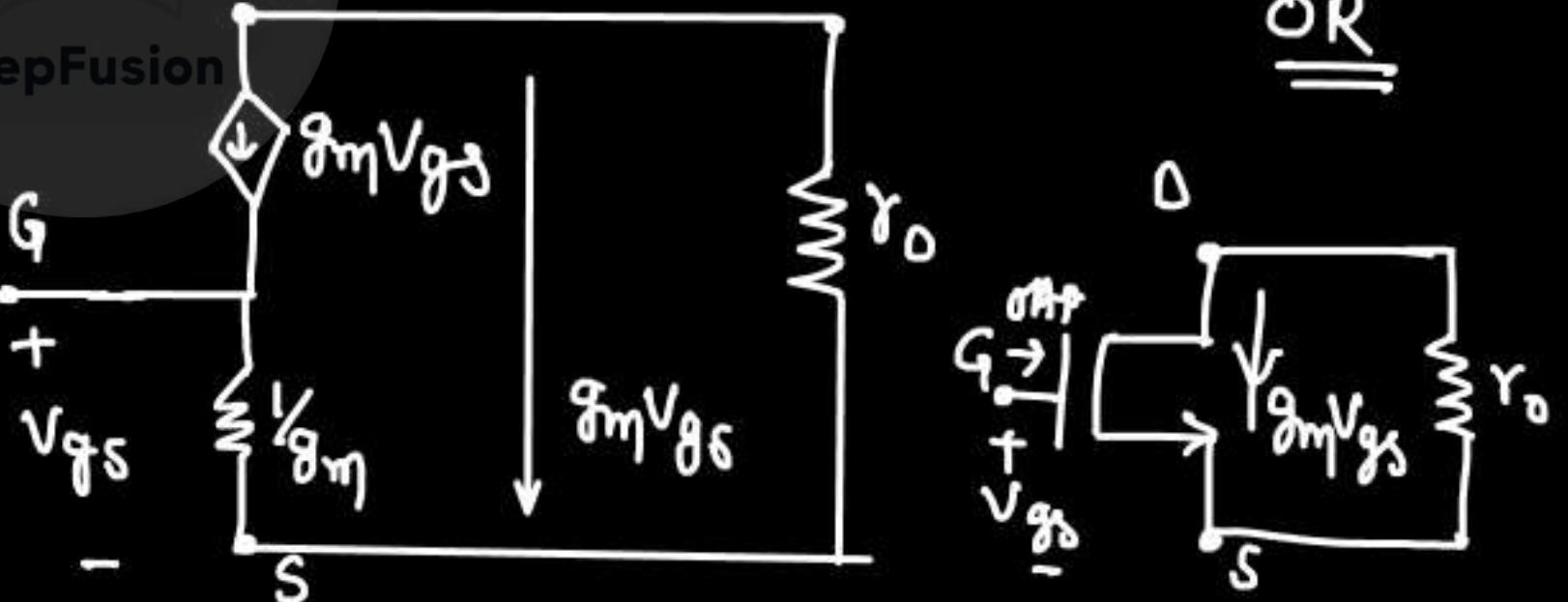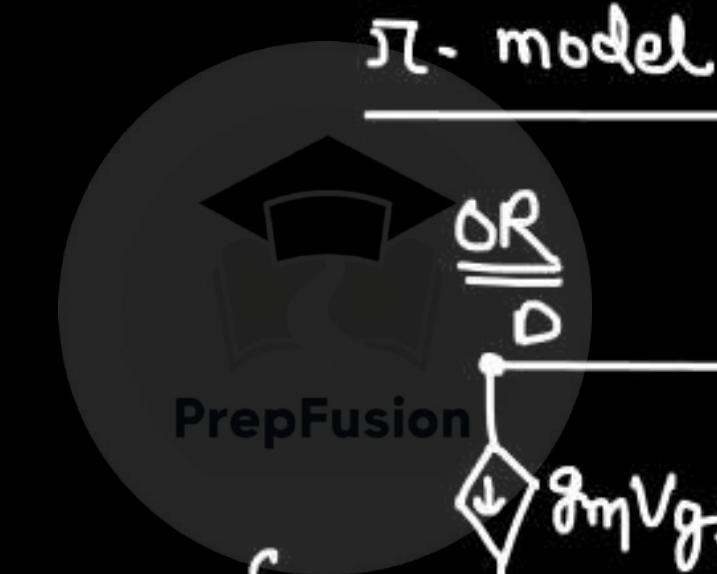

PMOS:-

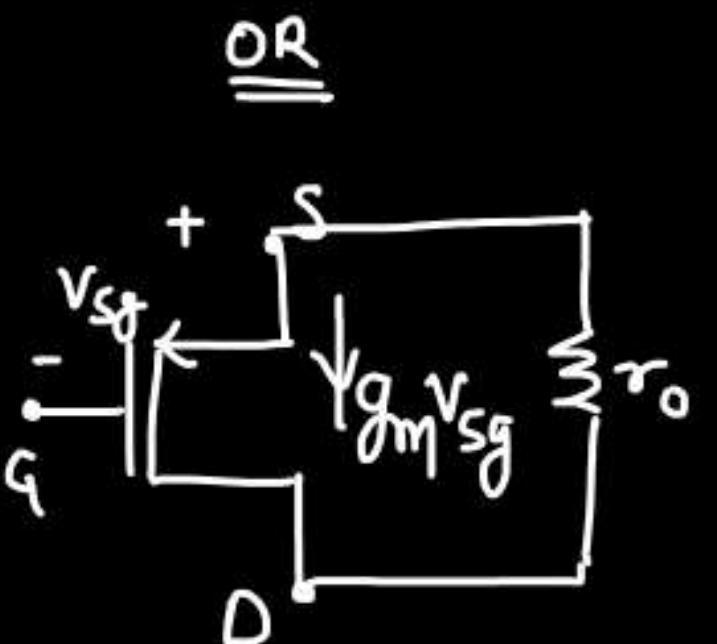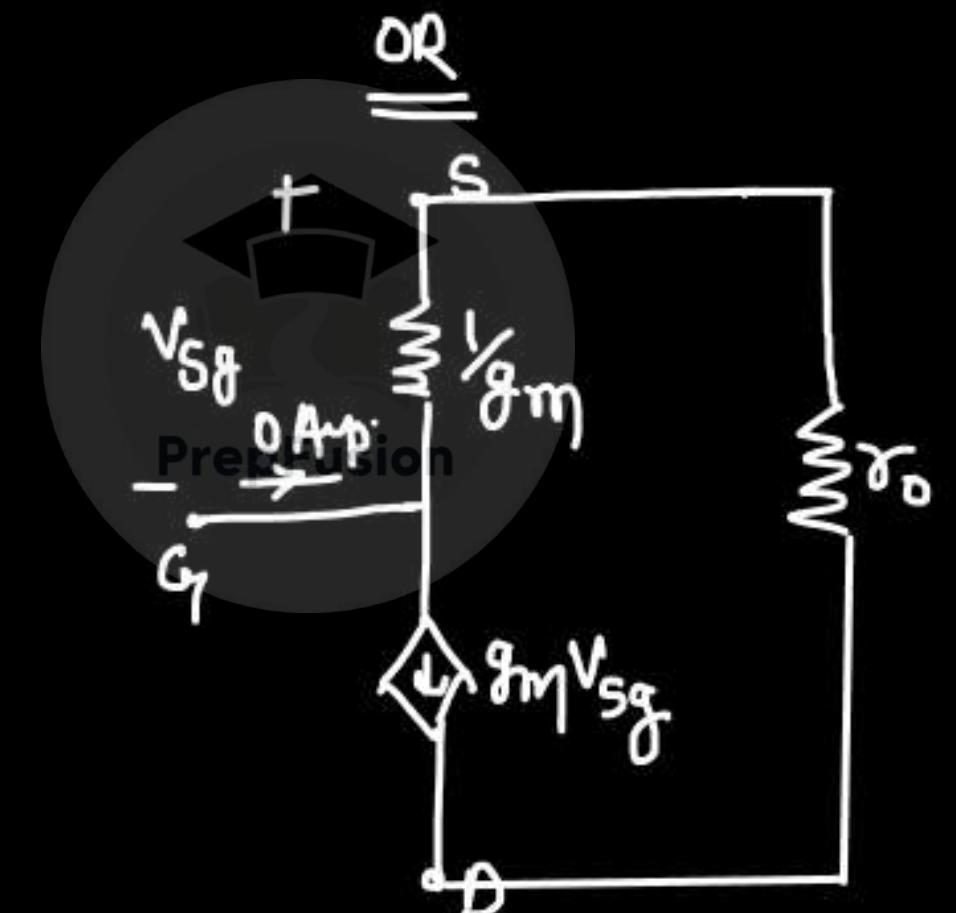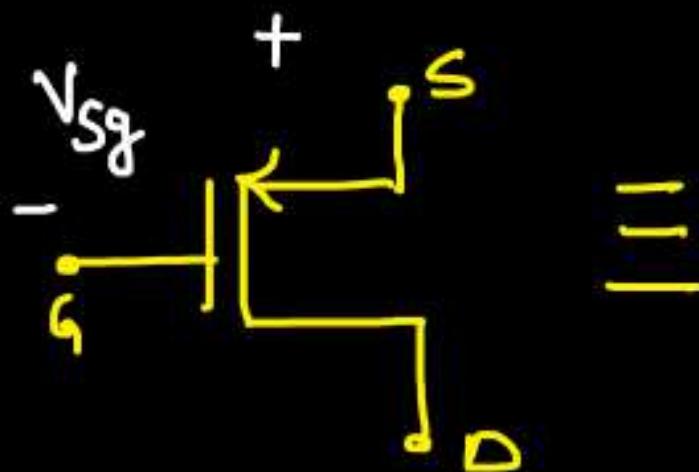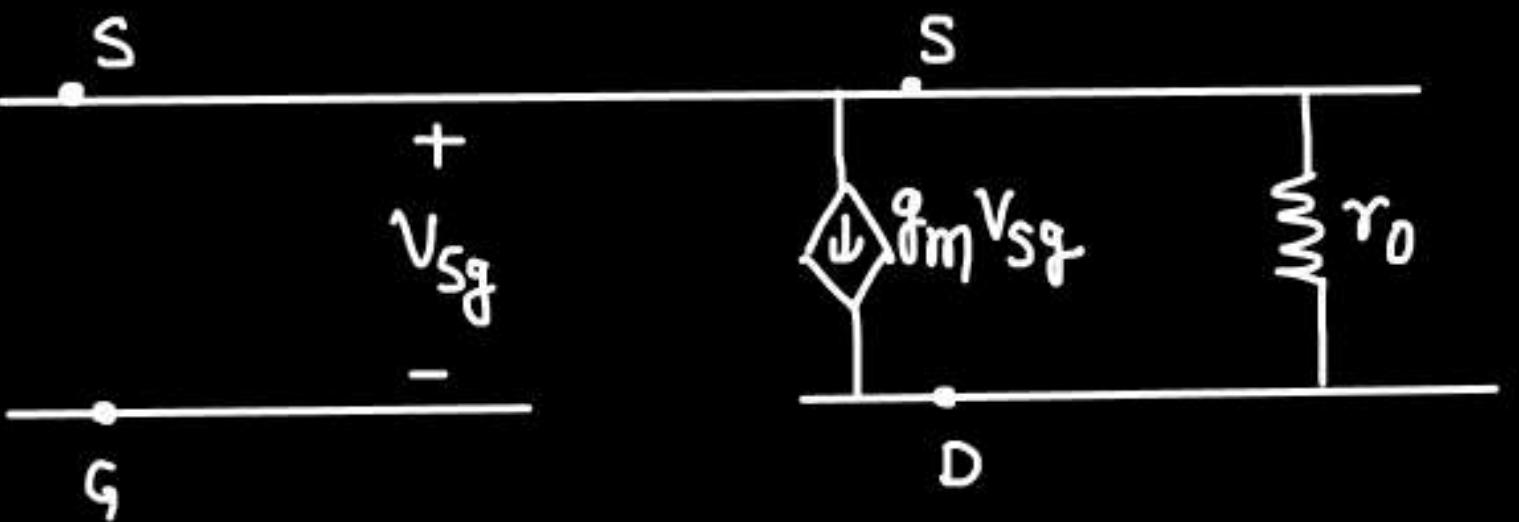

Concept of port impedance :-

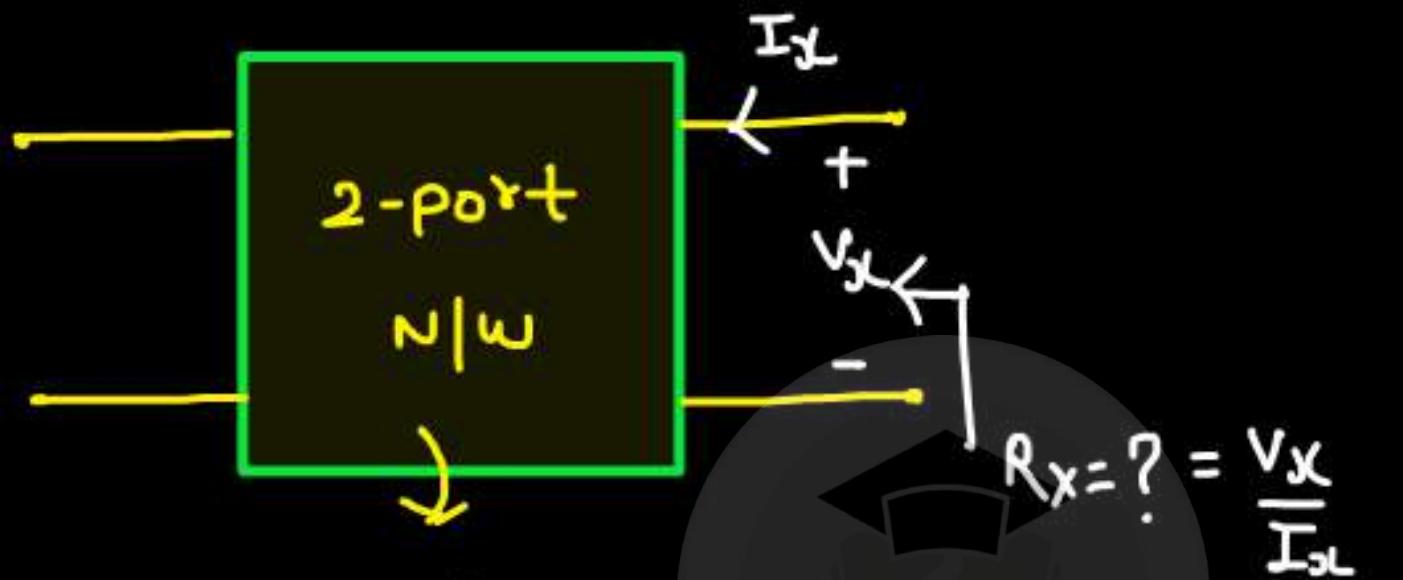

(i) All independent source = 0


PrepFusion

(ii) Apply V_x and get I_x out of it, @ the port where you need to find the impedance.


$$(iii) R_x = \frac{V_x}{I_x}$$

Eg. →

①


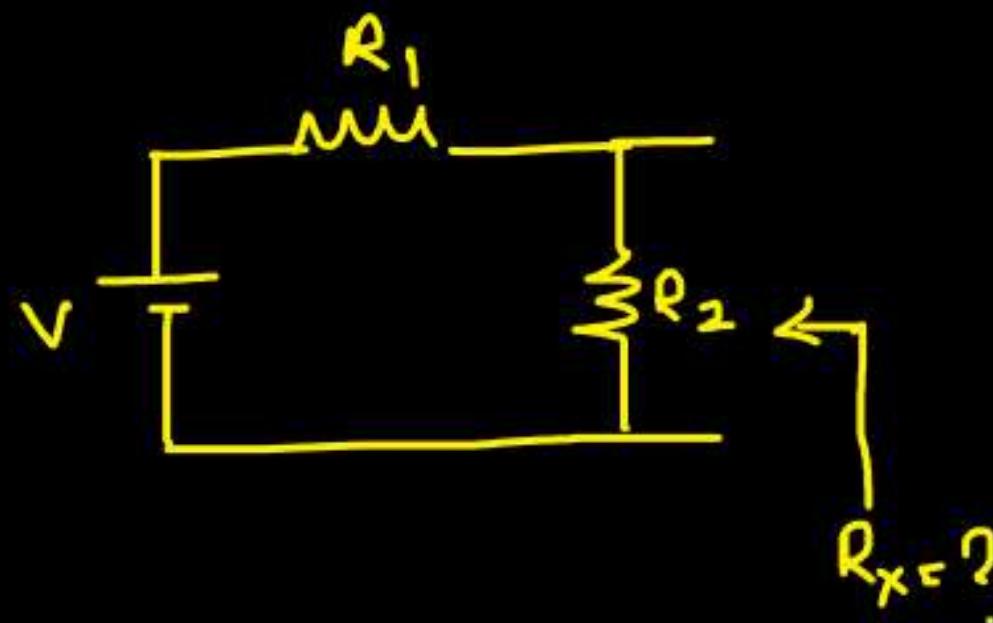


⇒

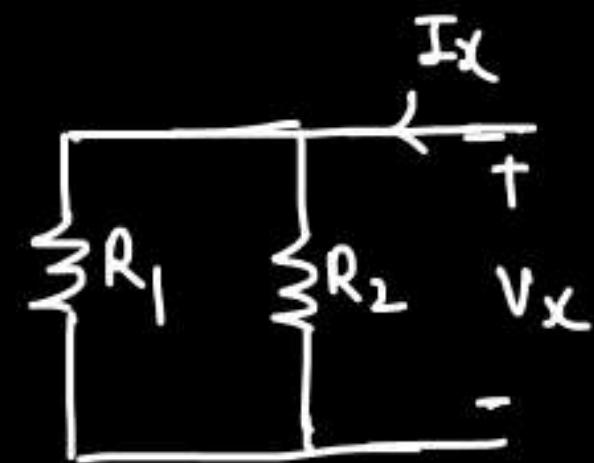

$$\frac{V_x}{I_x} = R_x = R_1 \parallel R_2$$

②

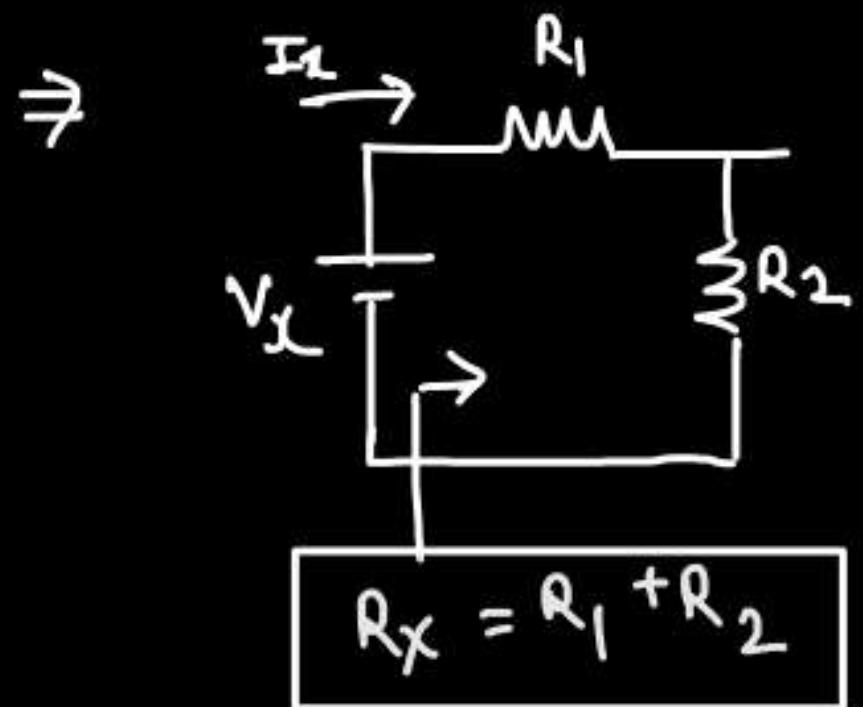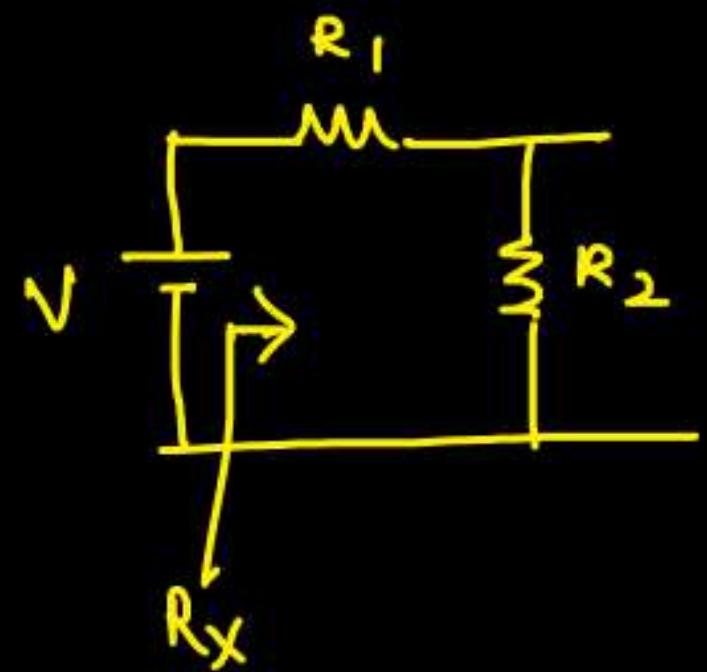


$$R_X = R_1 + R_2$$







3

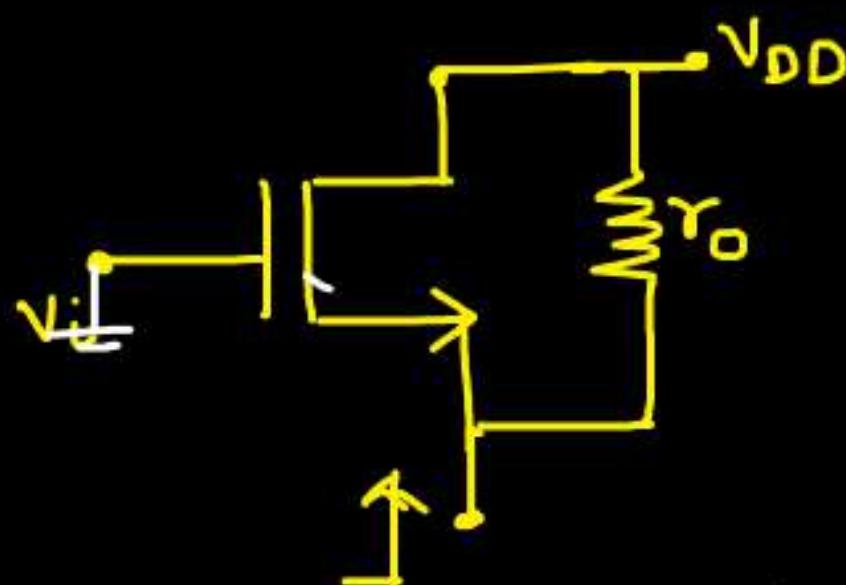

r_x (Small signal resistance)

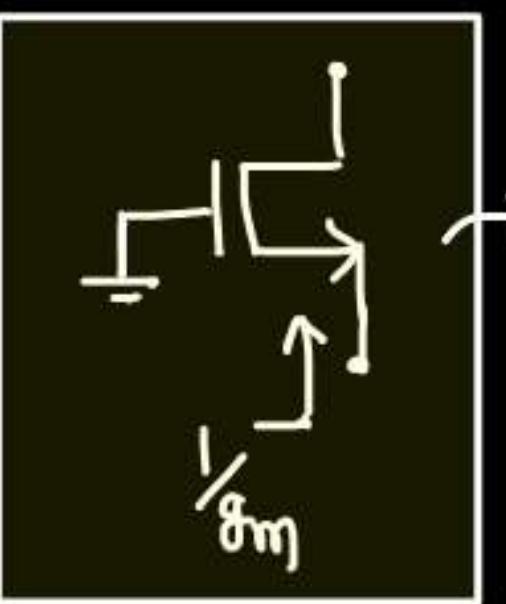

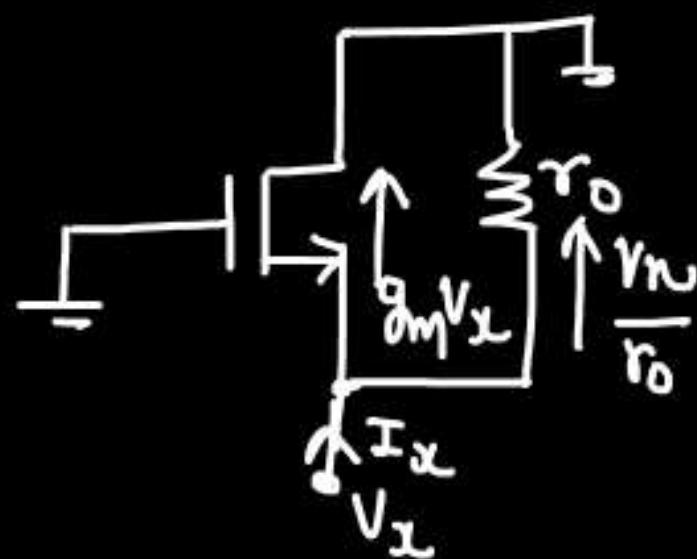From source to ground, I see $\frac{1}{gm}$



Nodal @ V_x

$$\frac{V_x}{r_o} + g_m V_x = I_x$$

$$V_x \left[1 + \frac{g_m r_o}{r_o} \right] = I_x$$





★ ★

$$R_x = \frac{1}{gm} || r_o$$

$$R_x = \frac{r_o}{1 + g_m r_o}$$

4

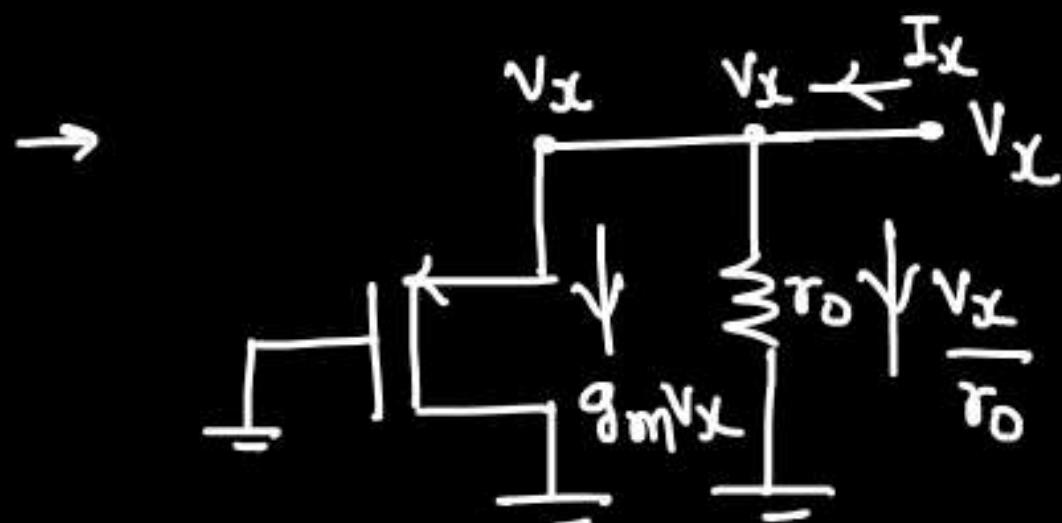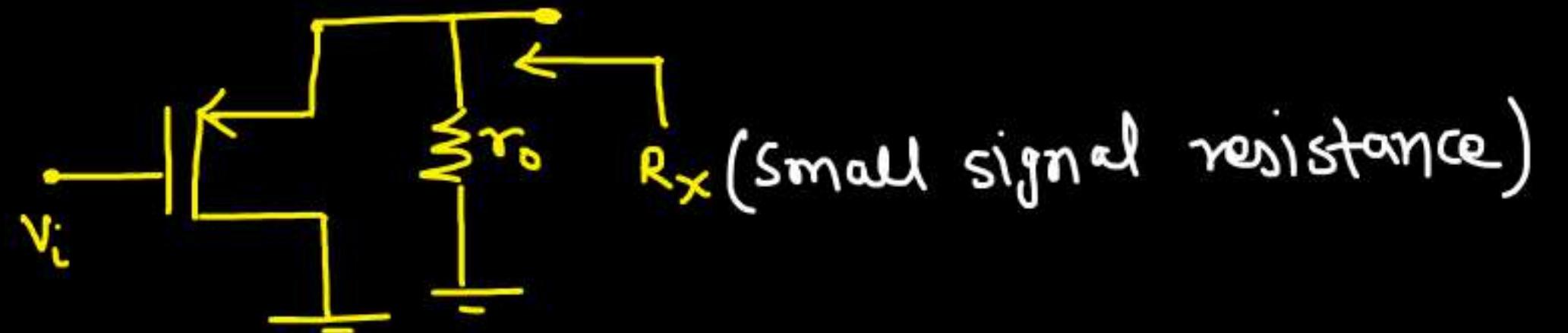


PrepFusion


$$g_m V_L + \frac{V_x}{r_o} = I_x$$

4

$$R_x = \frac{1}{g_m} \parallel r_o$$

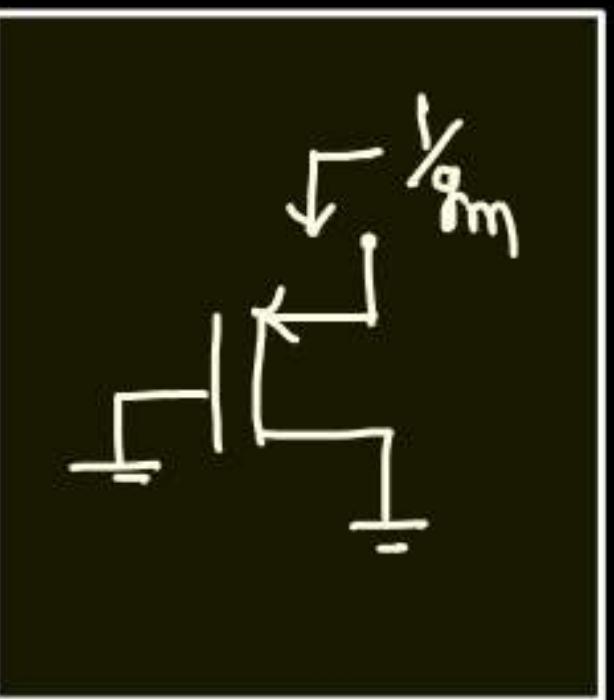

Q.

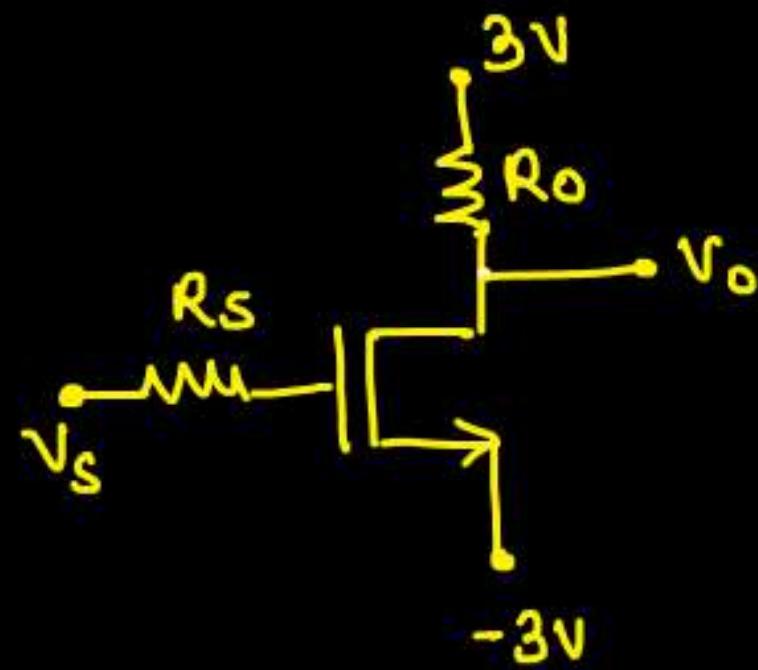

$$m_n C_{ox} = 100 \mu A/V^2$$

$$w/l = 1$$

$$V_T = 1V$$


$v_s \rightarrow$ small signal source (ac)

① Find R_o such that quiescent drain voltage is zero. (dc)

② Find small signal voltage gain. ($\frac{v_o}{v_s}$)

DC Analysis

Target $V_D = 0V$

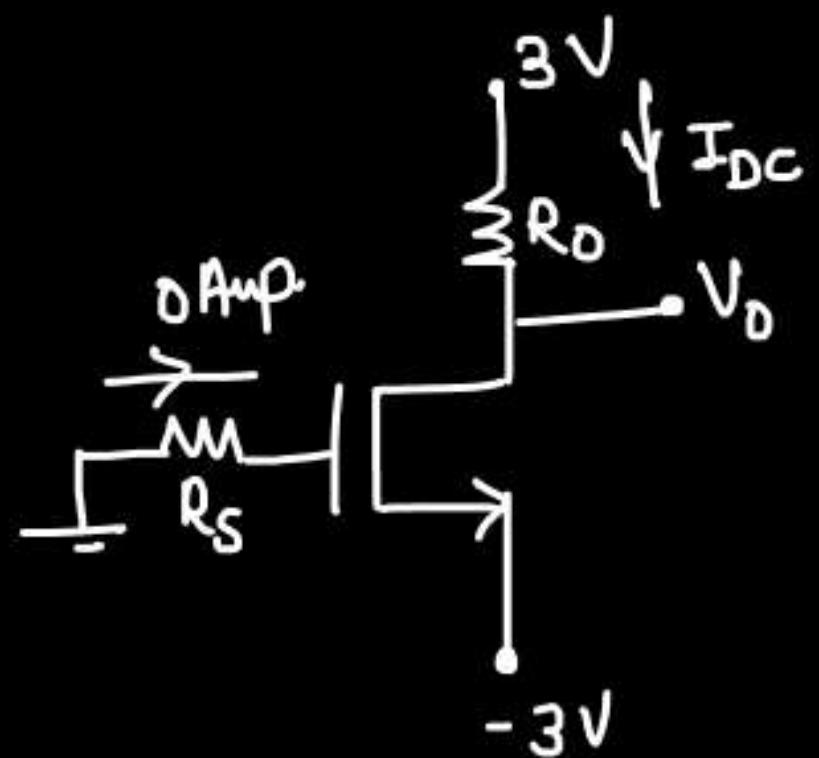

$$I_{DC} = \frac{m n C_o k \omega}{2L} (V_{GS} - V_T)^2$$

$$I_{DC} = \frac{100\mu}{2} (3-1)^2$$

$I_{DC} \approx 200 \mu \text{Amp}$

$$V_{DS} = 3V$$

$$V_{GS} = 3V$$

$$V_T = 1V$$

$$V_{OV} = 2V$$


$$V_{DS} > V_{OV} \Rightarrow \text{Sat.}$$

$$V_D = 3 - I_{DC} R_D = 0$$

$$I_{DC} R_D = 3$$

$$R_D = \frac{3}{200\mu} \Rightarrow R_D = 15k\Omega$$

AC Analysis:-

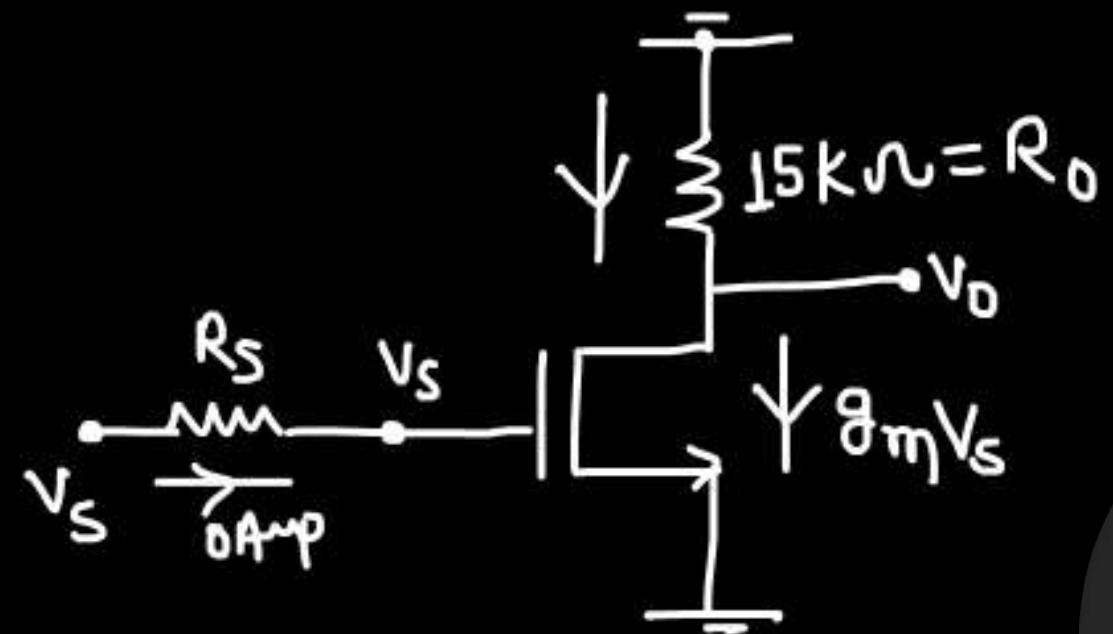

$$\frac{V_o}{V_s} = ?$$

$$V_o = -g_m V_s \times R_o$$

$$\boxed{\frac{V_o}{V_s} = -g_m R_o}$$

$$R_o \checkmark = 15 \text{ k}\Omega$$

g_m ?

$$g_m = \frac{m_n C_o \times W}{L} (V_{GS} - V_T)$$

$$= 100 \mu (3-1)$$

$$\boxed{g_m = 200 \mu \text{A}}$$

$$\frac{V_o}{V_s} = -200 \times 10^{-6} \times 1.5 \times 10^4$$

$$\boxed{\frac{V_o}{V_s} = -3 \text{ V/V}}$$




$$g_m = \sqrt{2 \mu_n C_{ox} W \frac{I_D}{L}} = \sqrt{2 \times 100 \mu \times 200 \mu} = 200 \mu V$$



$$g_m = \frac{2 I_{DC}}{V_{GS} - V_T} = \frac{2 \times 200 \mu}{2} = 200 \mu V$$

PrepFusion

Common Source Amplifiers:-

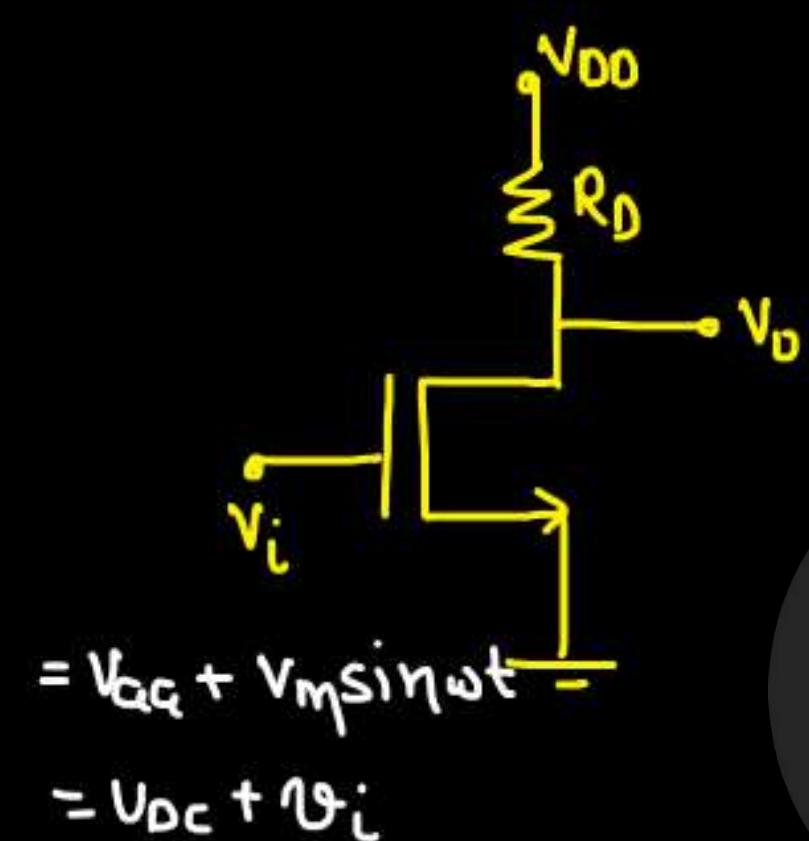


MOS is biased such that it's working in sat. region.

Common source amplifier →
Input → Gate , o/p → Drain

PrepFusion

Small signal analysis (ac) :-

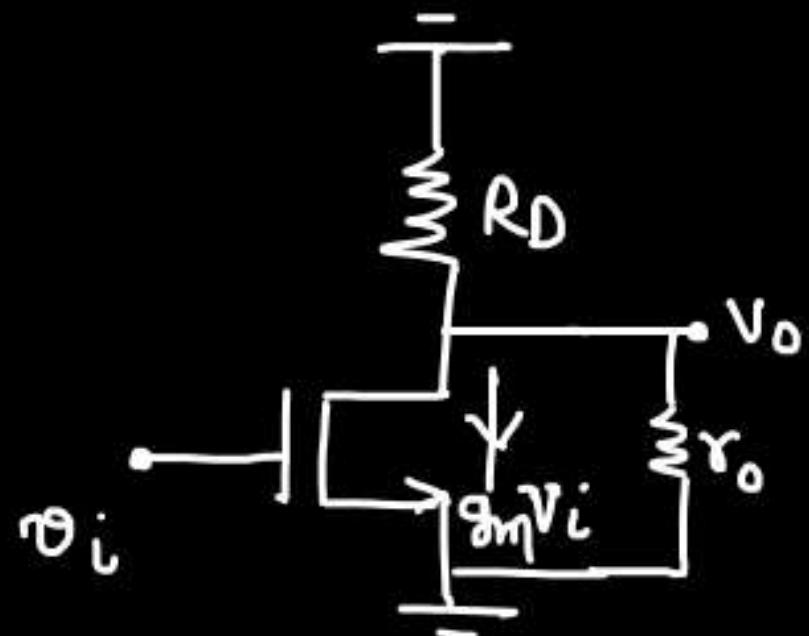


PrepFusion $V_o = -g_m V_i [R_D || r_o]$

$$\frac{V_o}{V_i} = -g_m [R_D || r_o]$$


→ small signal gain

② Small Signal o/p resistance (R_o): -

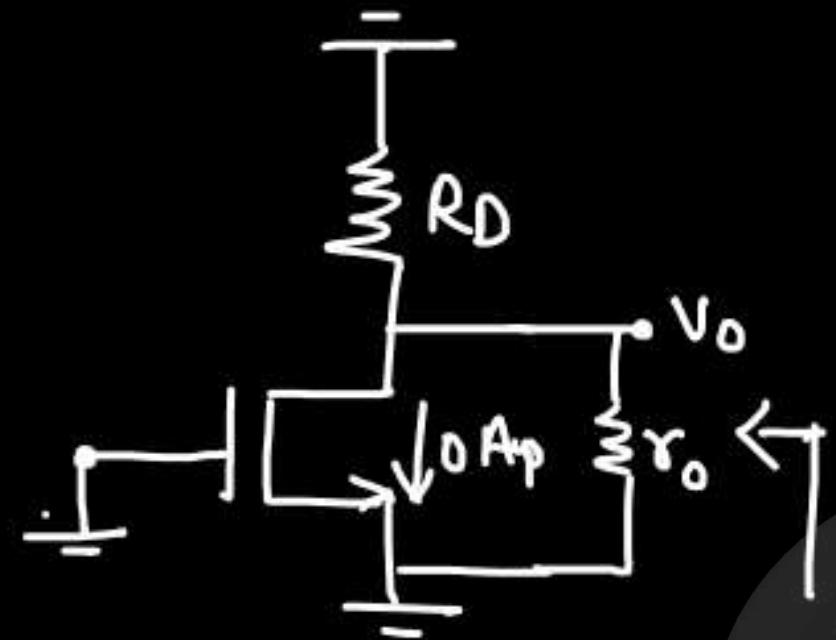


PrepFusion

$$R_o = R_D \parallel r_o$$

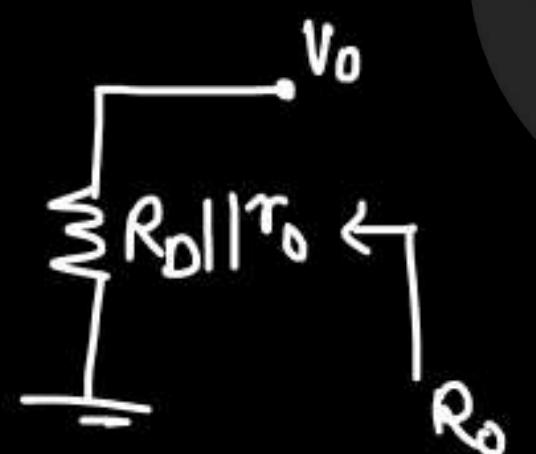


③ Small Signal Current gain :-

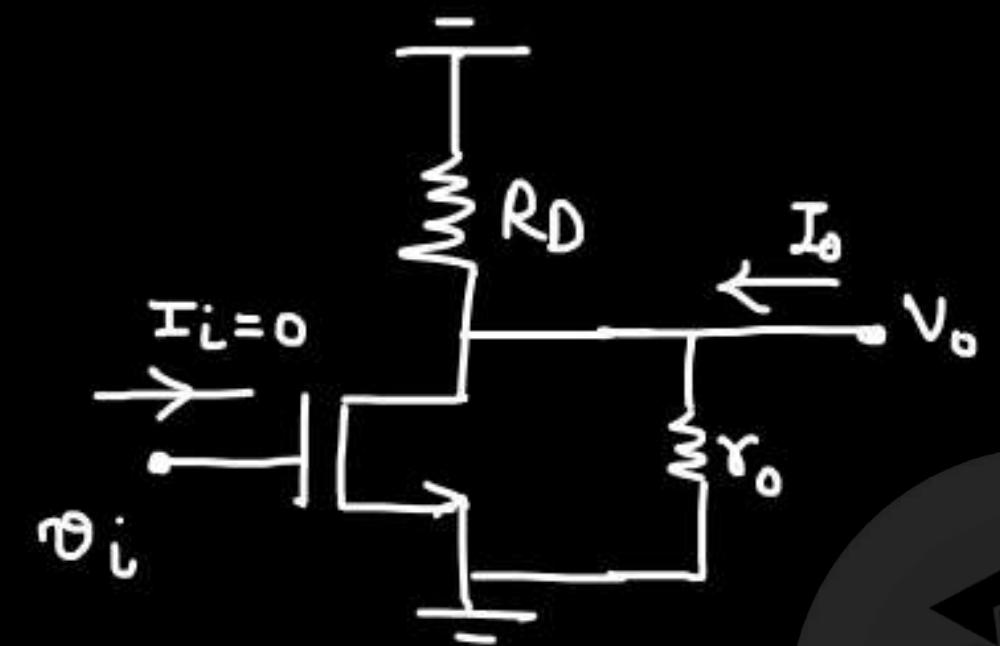

$$\text{Current gain} = \frac{v_o}{v_i} = \frac{I_o}{I_i}$$

$$A_I = \infty$$

④ Small signal i/p resistance :-

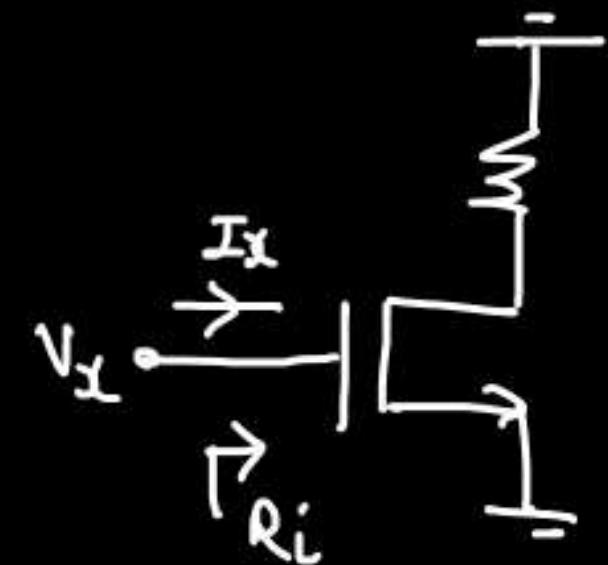

$$R_i = \frac{v_i}{I_i} = \frac{v_i}{0} = \infty$$

$$R_i = \infty$$

Problem with common source amplifier:-

$$A_V = -g_m R_D \quad [\lambda = 0, \gamma_0 = \infty]$$

$$A_V = -\sqrt{\frac{2\mu_n C_{ox} \omega}{L}} I_D \times R_D$$

$$T \uparrow \Rightarrow I_D \uparrow$$

$$A_V = f(I_D)$$


$$I_D = g(T)$$

$$A_V = h(T)$$

Because of Temp change, the gain can change \Rightarrow NOT Desirable

Using diode connected load in common Source Amplifier:-

Amplifier:-

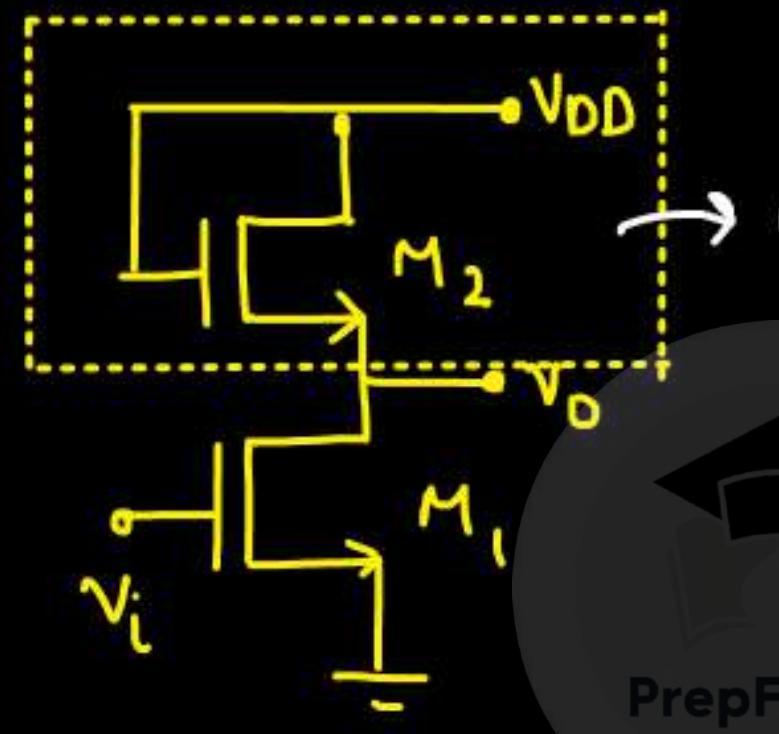


→ diode connected load.



Small Signal Analysis:-

Assuming [$\lambda = 0$]

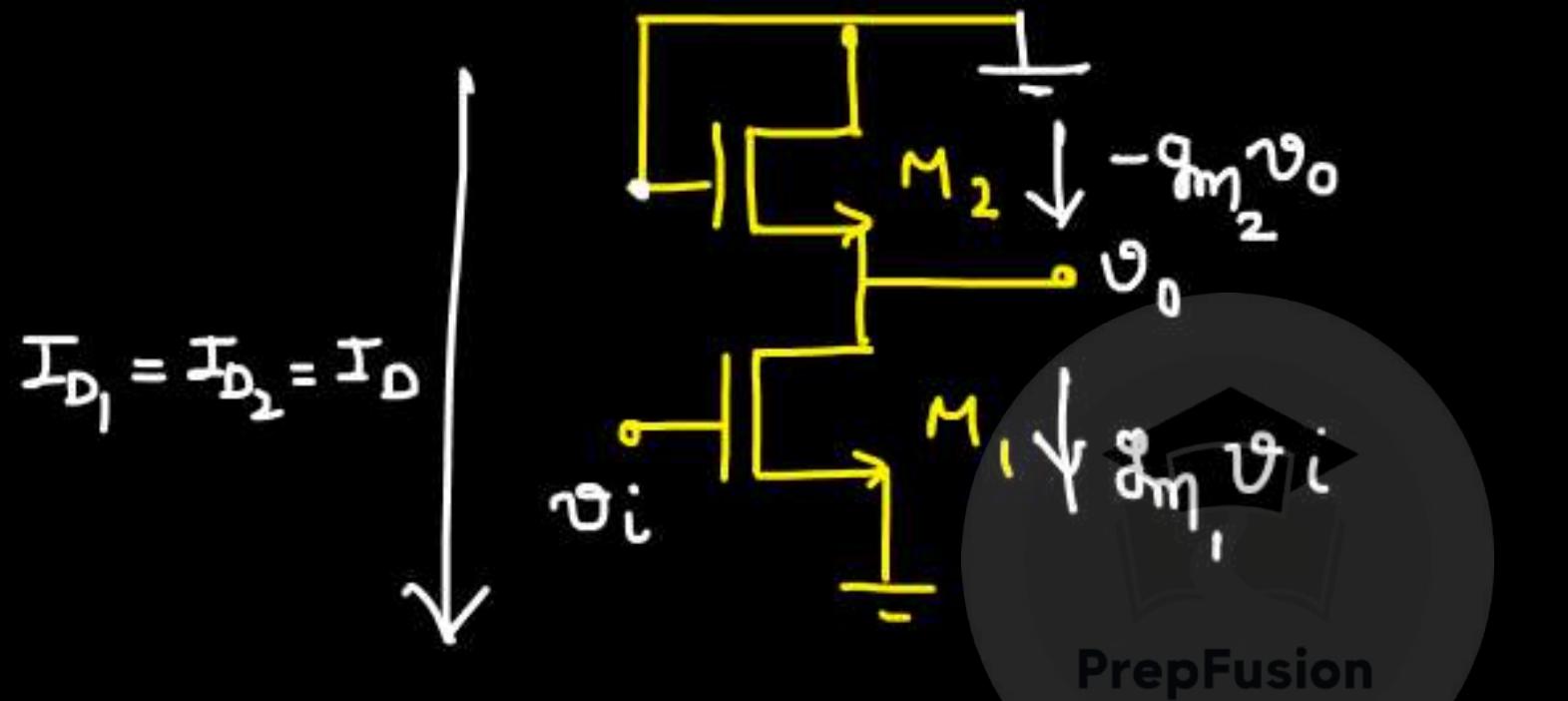

$$(V_{GS})_{M_1} = 0 - V_o$$

$$g_m v_i = - g_m v_o$$

$$\frac{v_o}{v_i} = - \frac{g_m}{g_m}$$

→ Small signal gain

$$A_V = - \frac{\delta m_1}{\delta m_2}$$

$$A_V = \frac{\sqrt{2(\mu_n C_{ox} \omega)} I_{D1}}{\sqrt{2(\mu_n C_{ox} \omega)} I_{D2}}$$


PrepFusion

Here $I_{D1} = I_{D2} = I_D$

$$A_V = \frac{\sqrt{(\omega_L)_1}}{\sqrt{(\omega_L)_2}} \rightarrow \text{constant gain}$$

$\frac{\omega}{L} \neq f(\tau)$

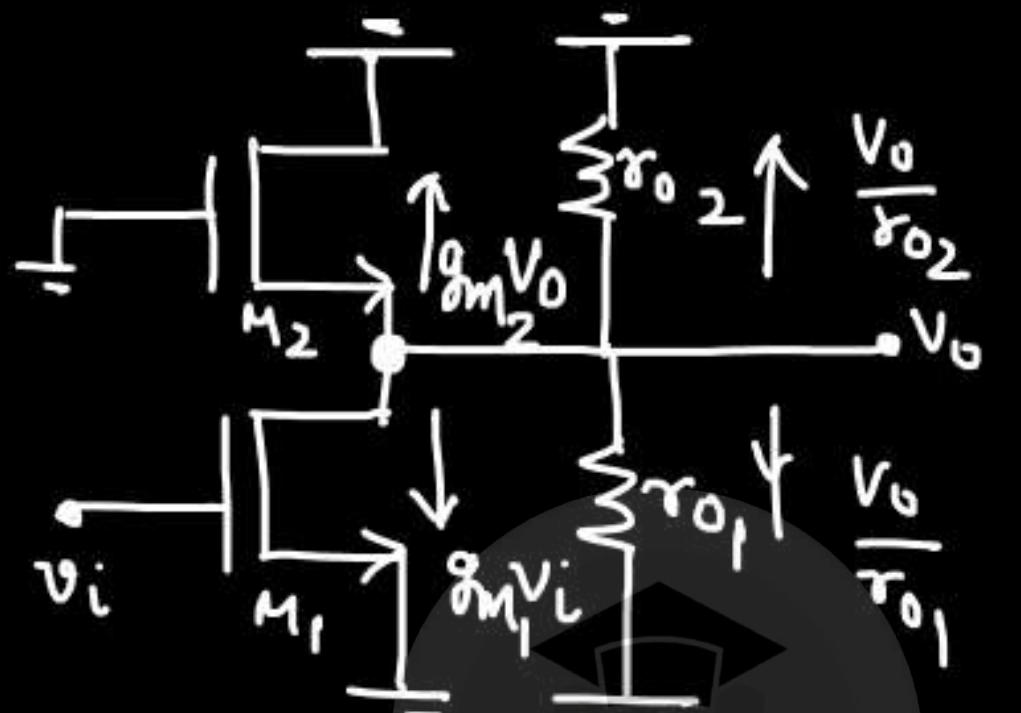⇒ Small signal gain considering $\lambda \neq 0$



KCL @ v_o :-

$$g_{m_2}v_o + g_{m_1}v_i + \frac{v_o}{r_{o_2}} + \frac{v_o}{r_{o_1}} = 0$$

$$v_o \left[g_{m_2} + \frac{1}{r_{o_2}} + \frac{1}{r_{o_1}} \right] = -g_{m_1}v_i$$

$$\left[\frac{1}{g_{m_2}} || r_{o_1} || r_{o_2} \right] = -g_{m_1}v_i$$

$$\frac{V_o}{V_i} = -g_m \left[\frac{1}{g_m} || r_{o1} || r_{o2} \right]$$


→ small signal
gain

if $r_{o1} = r_{o2} = \infty$

$$\frac{V_o}{V_i} = -\frac{g_m}{g_m}$$




M-II

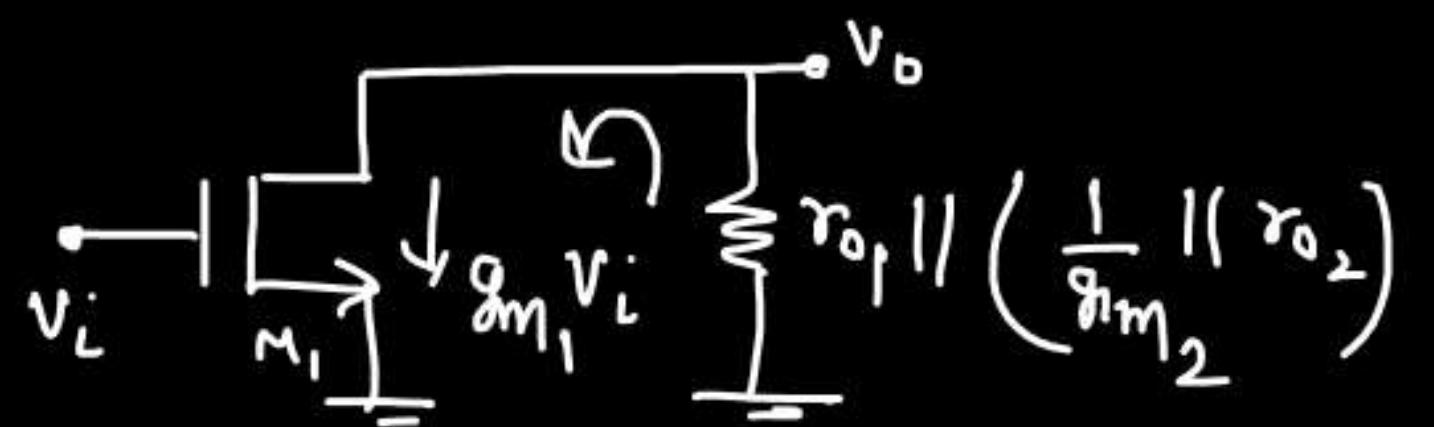

$$V_o = -g_m \left[r_{o1} || \frac{1}{g_m} || r_{o2} \right] V_i$$

$$\frac{V_o}{V_i} = -g_m \left[r_{o1} || r_{o2} || \frac{1}{g_m} \right]$$

O/P resistance :-

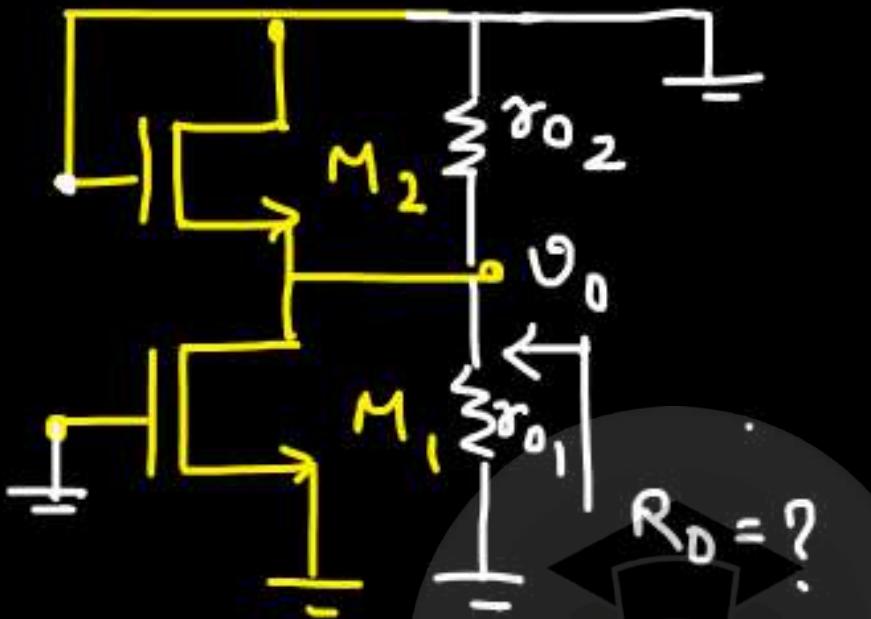


Preposition

$$R_o = r_{o1} || r_{o2} || \frac{1}{g_m2}$$


if $\lambda = 0 \Rightarrow r_{o1} = r_{o2} = \infty$

$$R_o = \frac{1}{g_m2}$$

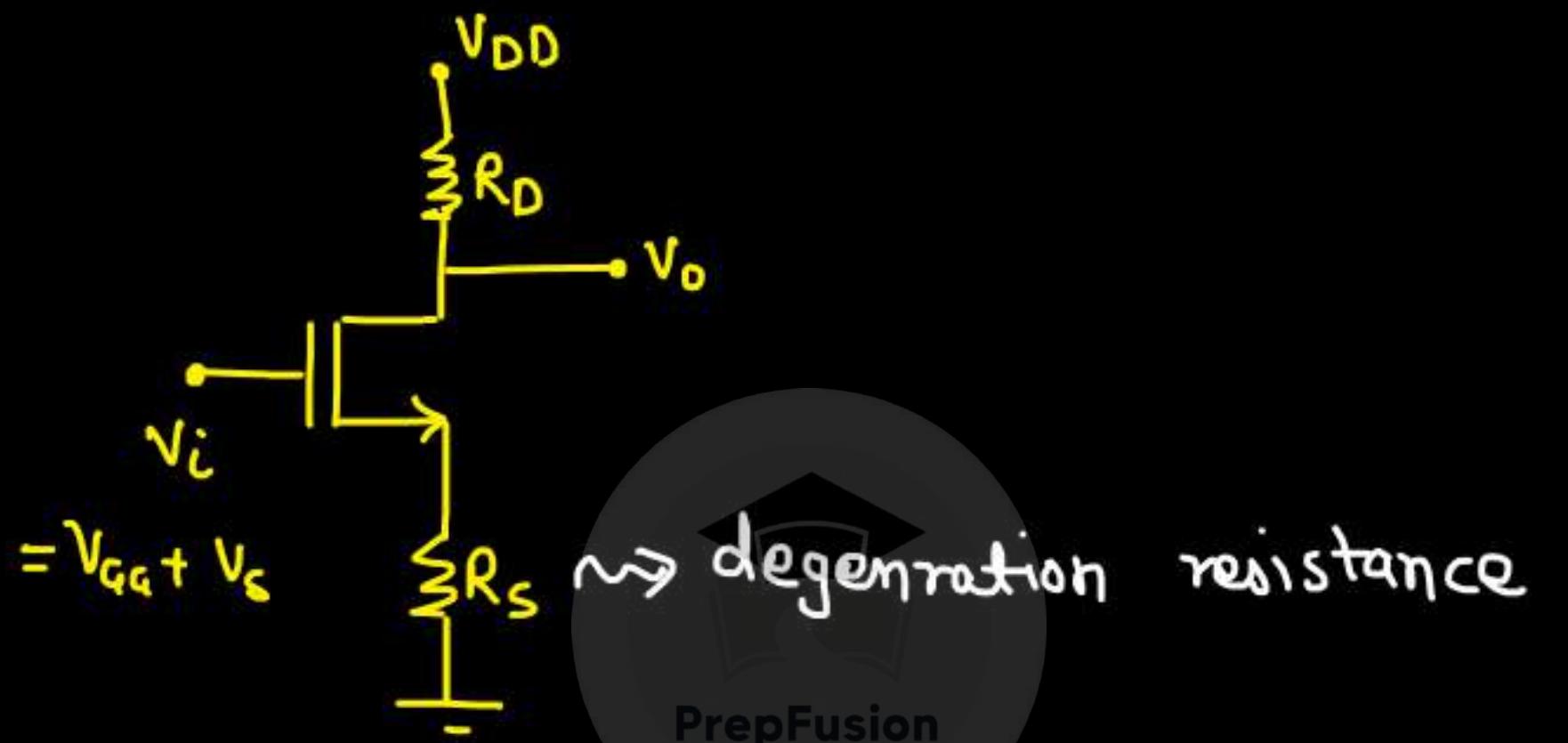Common source Amplifier with degeneration:-



DC Analysis:-

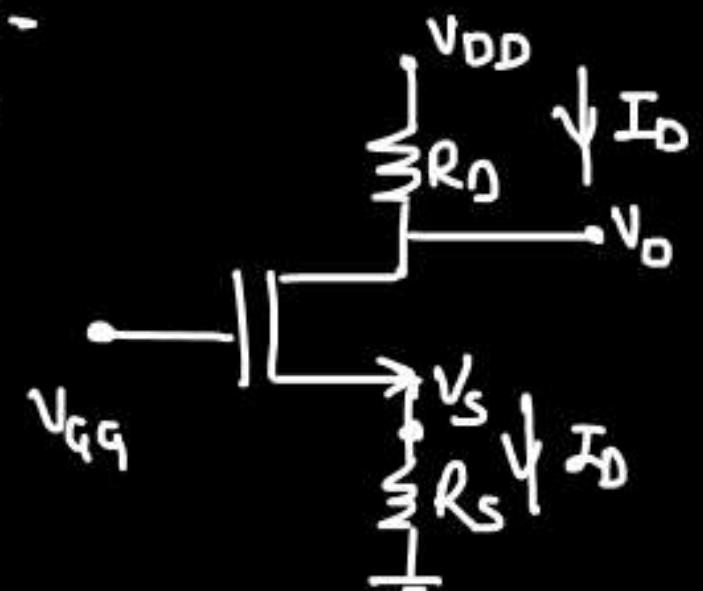


Let's assume, Because of Temp. $I_D \uparrow$

$I_D \uparrow \Rightarrow V_S \uparrow \Rightarrow V_{GS} \downarrow \Rightarrow I_D \downarrow$

\Rightarrow Stability achieved

Small Signal Analysis:-

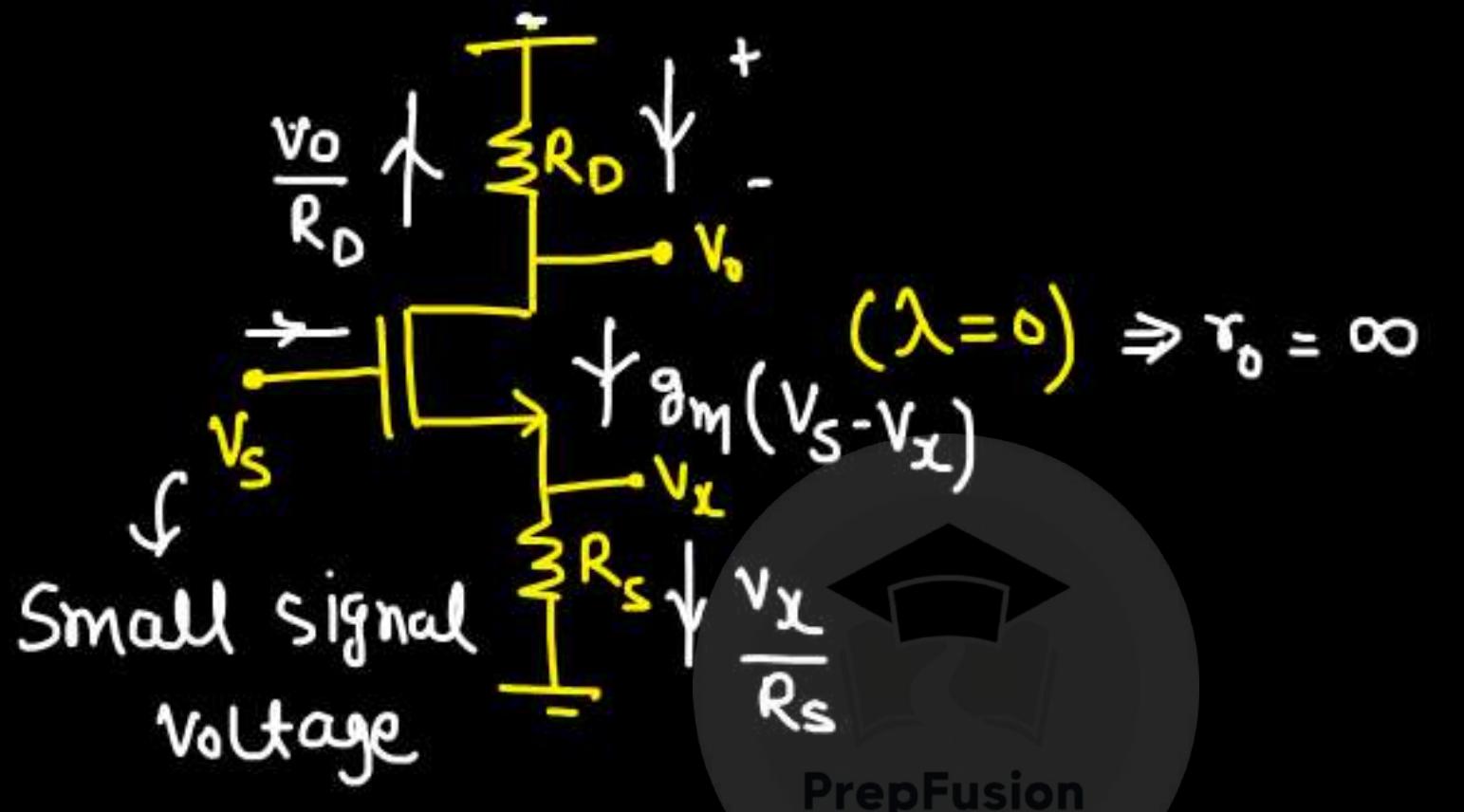

$$V_o = -g_m (V_s - V_x) \times R_D$$

$$V_o = -g_m R_D (V_s - V_x) - \textcircled{1}$$

$$\frac{V_o}{R_D} = -\frac{V_x}{R_S} \Rightarrow V_x = -\frac{R_S}{R_D} V_o - \textcircled{2}$$

By eqn ① and ②

$$V_o = -g_m R_D \left[V_s + \frac{R_S}{R_D} V_o \right]$$

$$V_o = -g_m R_D V_s - g_m R_S V_o$$

$$V_o [1 + g_m R_S] = -g_m R_D V_s$$

$$\frac{V_o}{V_s} = \frac{-g_m R_D}{1 + g_m R_S}$$

PrepFusion → Small signal voltage gain =


Current gain:-

$$\alpha_I = \frac{I_o}{I_i} = \frac{I_o}{0} = \infty$$

Input Resistance:-

$$R_{in} = \frac{V_i}{I_i} = \frac{V_i}{0} = \infty$$

Voltage gain considering r_o :-

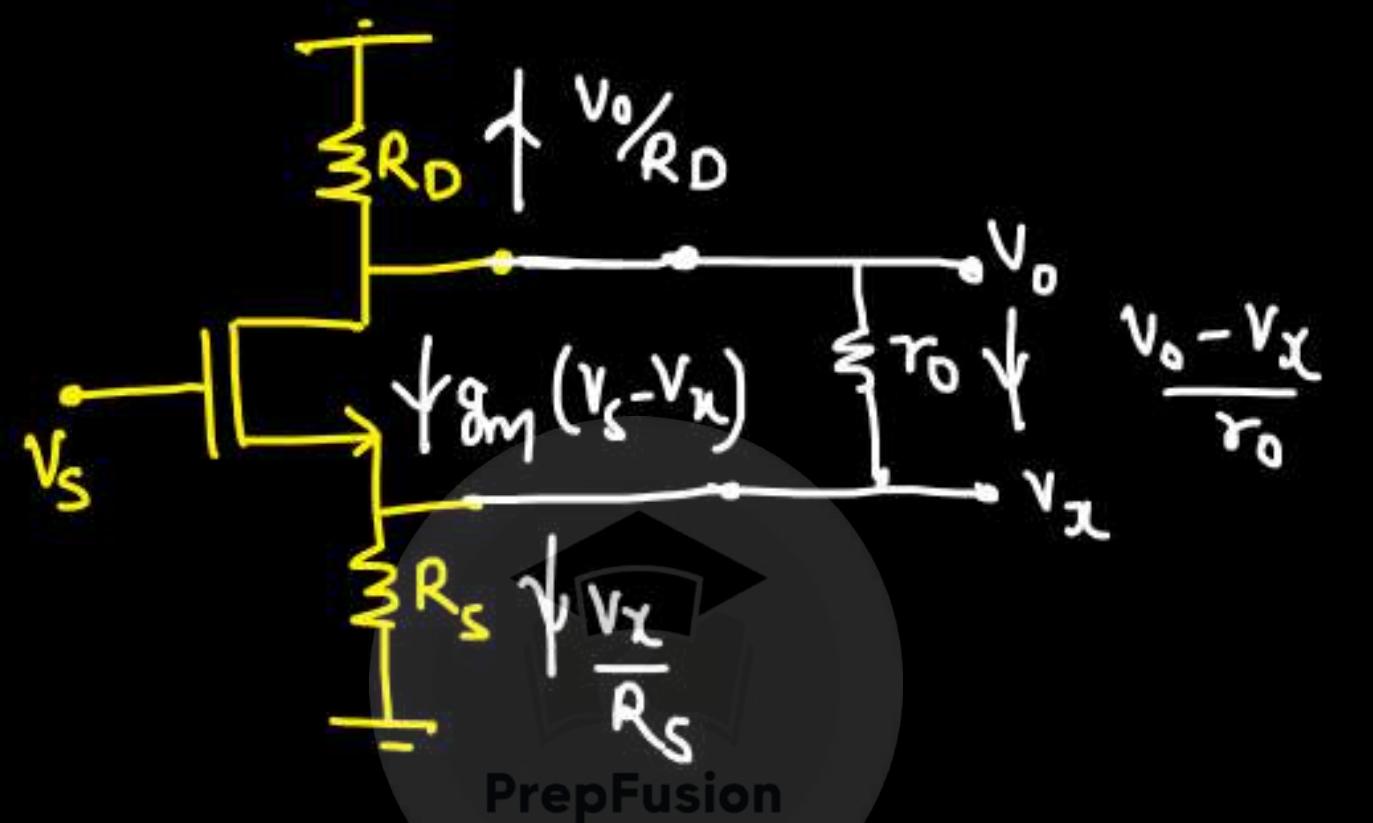

KCL @ V_0

$$g_M (V_S - V_x) + \frac{V_0}{R_D} + \frac{V_0 - V_x}{r_o} = 0 \rightarrow \textcircled{1}$$

$$\frac{V_0}{R_D} = -\frac{V_x}{R_S} \Rightarrow V_x = -\frac{R_S}{R_D} V_0 \rightarrow \textcircled{2}$$

By eqⁿ ① and ②

$$g_m \left(V_S + \frac{R_S}{R_D} V_o \right) + \frac{V_o}{R_D} + \frac{V_o}{r_o} \left[1 + \frac{R_S}{R_D} \right] = 0$$

$$g_m V_S + V_o \left[\frac{g_m R_S}{R_D} + \frac{1}{R_D} + \frac{1}{r_o} + \frac{R_S}{r_o R_D} \right] = 0$$

$$g_m V_S = - V_o \left[\frac{g_m r_o R_S + r_o + R_D + R_S}{r_o R_D} \right]$$

PropFusion

$$\frac{V_o}{V_S} = - g_m R_D \left[\frac{r_o}{g_m r_o R_S + r_o + R_D + R_S} \right]$$


if $r_o = \infty$ [very large]

$$\frac{V_o}{V_s} = -g_m R_D \left[\frac{r_o}{g_m r_o R_S + r_o} \right]$$


$$\frac{V_o}{V_s} = -\frac{g_m R_D}{1 + g_m R_S}$$

PrepFusion

O/P resistance :-

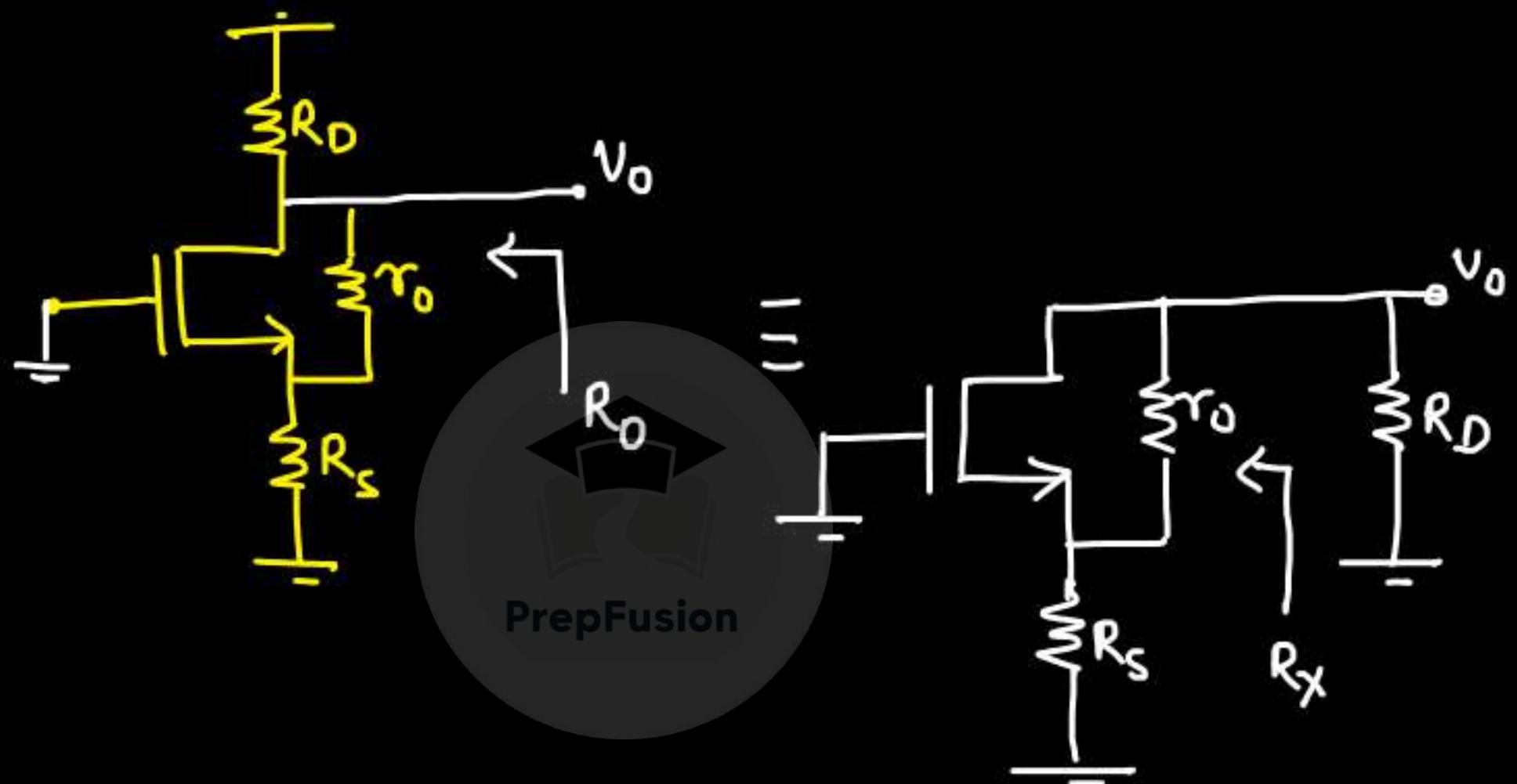

$$R_o = R_D || R_x$$

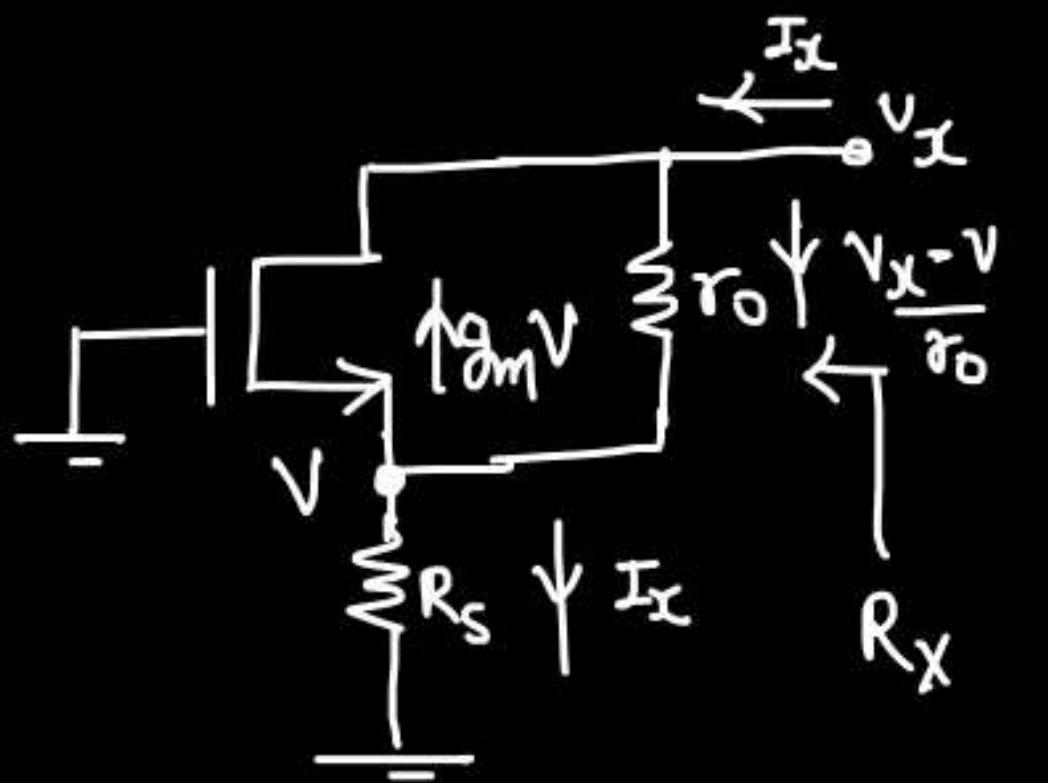

$$R_x = \frac{V_x}{I_x}$$

Nodal @ V_x :-

$$I_x + g_m V = \frac{V_x - V}{r_0}$$

$$I_x r_0 + g_m r_0 V = V_x - V \quad \text{--- (1)}$$

$$V = I_x R_s \quad \text{--- (2)}$$

By eqn ① and ②

$$I_x r_o + g_m r_o [I_x R_S] = V_x - I_x R_S$$


$$I_x [r_o + g_m r_o R_S + R_S] = V_x$$

$$R_x = \frac{V_x}{I_x} = R_S + r_o + g_m r_o R_S \approx g_m r_o R_S \quad \left\{ g_m r_o R_S \gg R_S + r_o \right\}$$

$$R_x = R_S + (1 + g_m R_S) r_o$$

$$R_x = r_o + (1 + g_m r_o) R_S$$

To REMEMBER:-

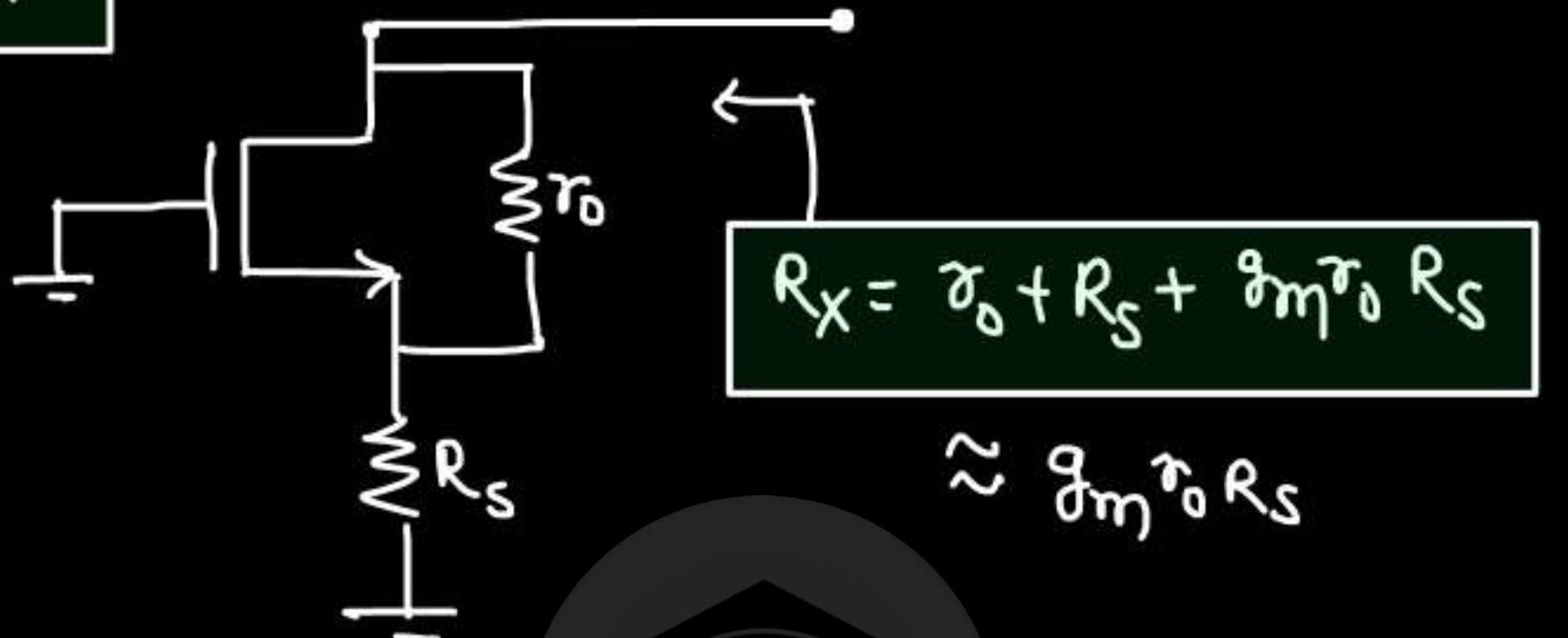


O/P resistance:-


$$R_o = R_D \parallel R_X$$

$$R_o = \underbrace{R_D}_{\approx r_o} \parallel (r_o + R_S + g_m r_o R_S)$$



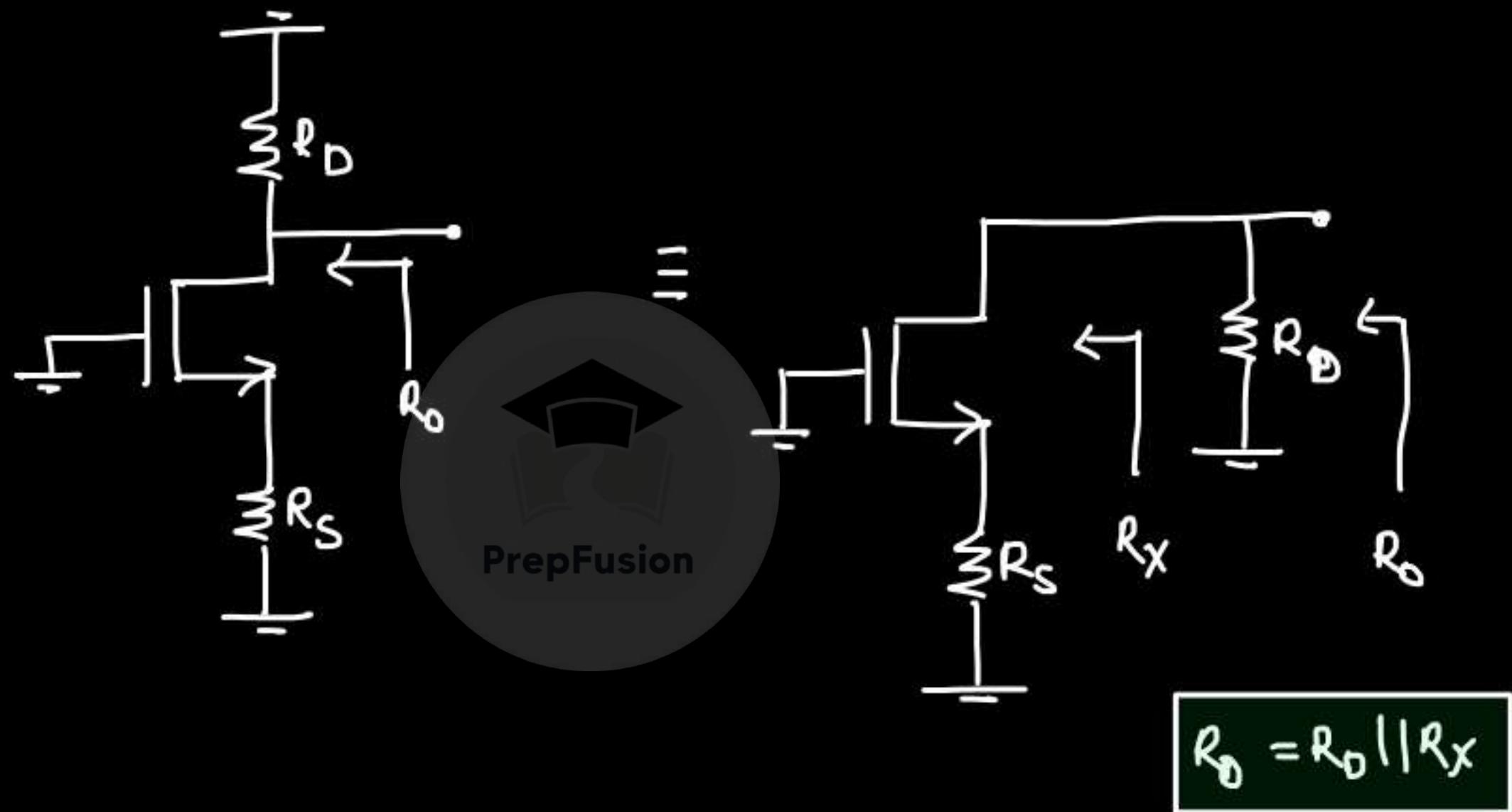* o/p resistance of common source with degeneration ($\lambda=0$)



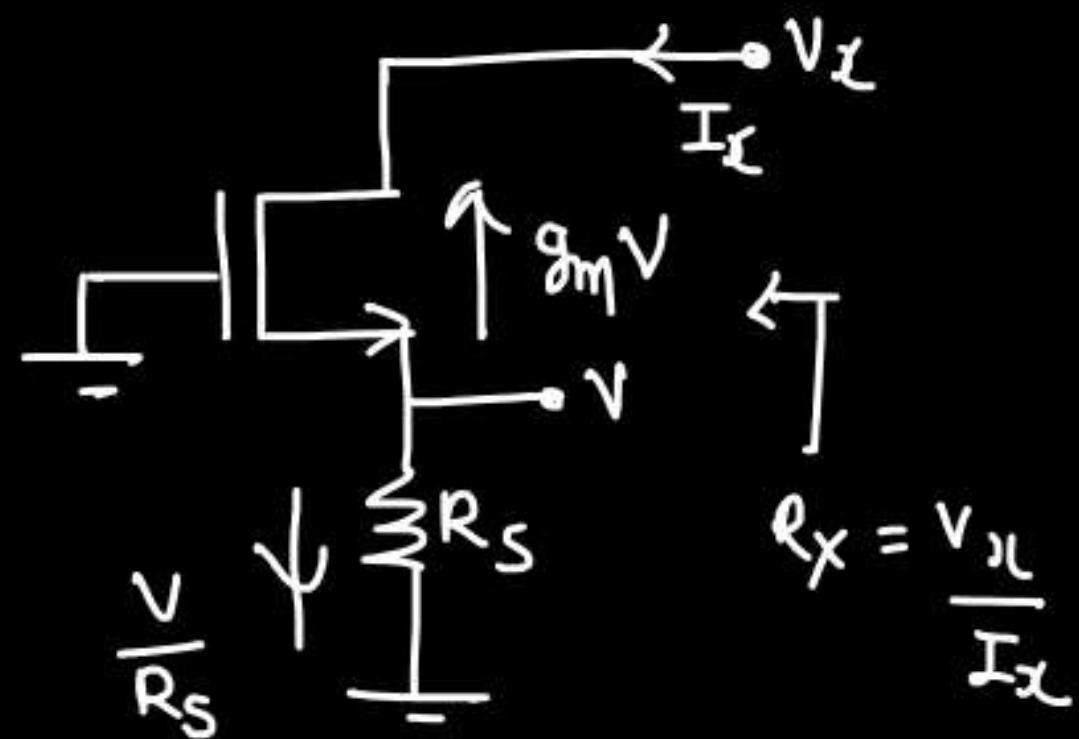

$$g_m V = -I_L \quad \textcircled{1}$$

$$\frac{V}{R_S} = I_L \quad \textcircled{2}$$

By eqⁿ ① and ②

$$g_m I_L R_S = -I_L$$

PrepFusion

$$I_L [g_m R_S + 1] = 0$$

$$I_L = 0$$

$$\Rightarrow R_o = \frac{V_L}{0} = \infty$$


$$R_o = R_D \parallel R_L$$

$$R_o = R_D \parallel \infty$$


∴ $R_o = R_D$

Common Source Amplifier:-

without degeneration

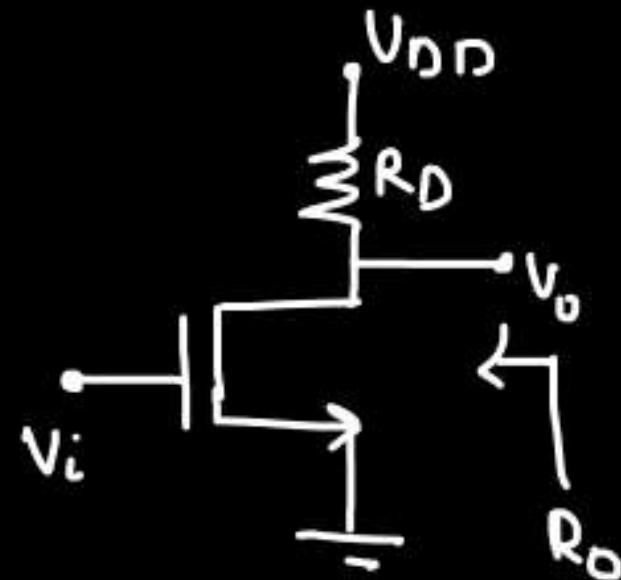

with degeneration

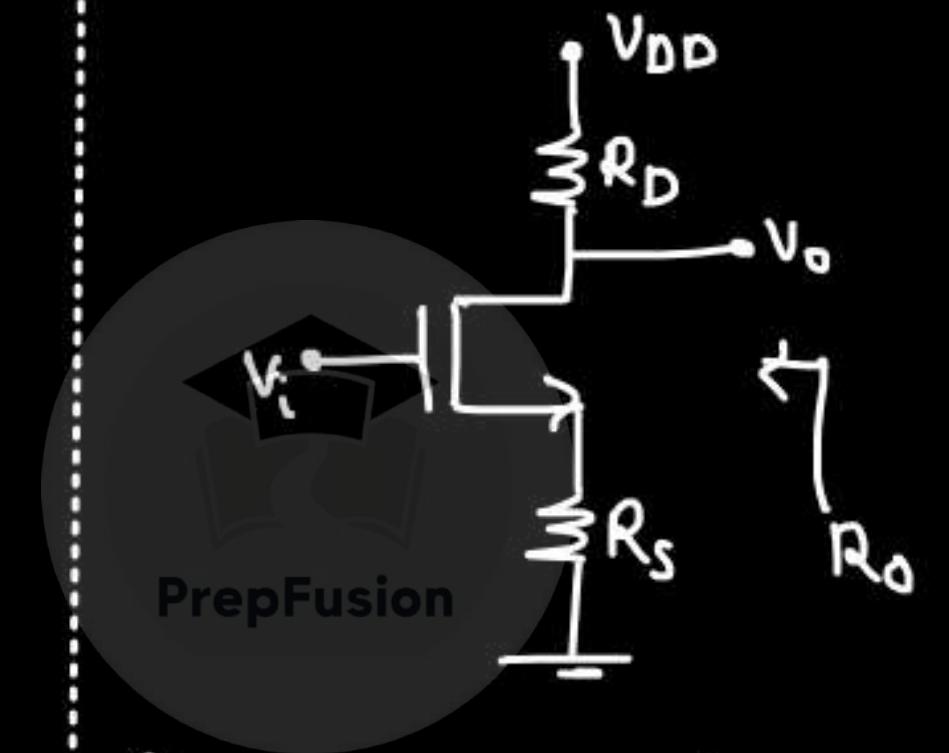


- ① less stability
- ② $\frac{V_o}{V_i} = -g_m R_D \rightarrow$ more gain
- ③ $R_{out} = R_D \parallel r_o$

- ① Better stability
- ② $\frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} \rightarrow$ less gain
- ③ $R_{out} = R_D \parallel (R_S + r_o + g_m R_S r_o)$

Best way of biasing a Common Source Amplifier:-

* Previous biasing:-

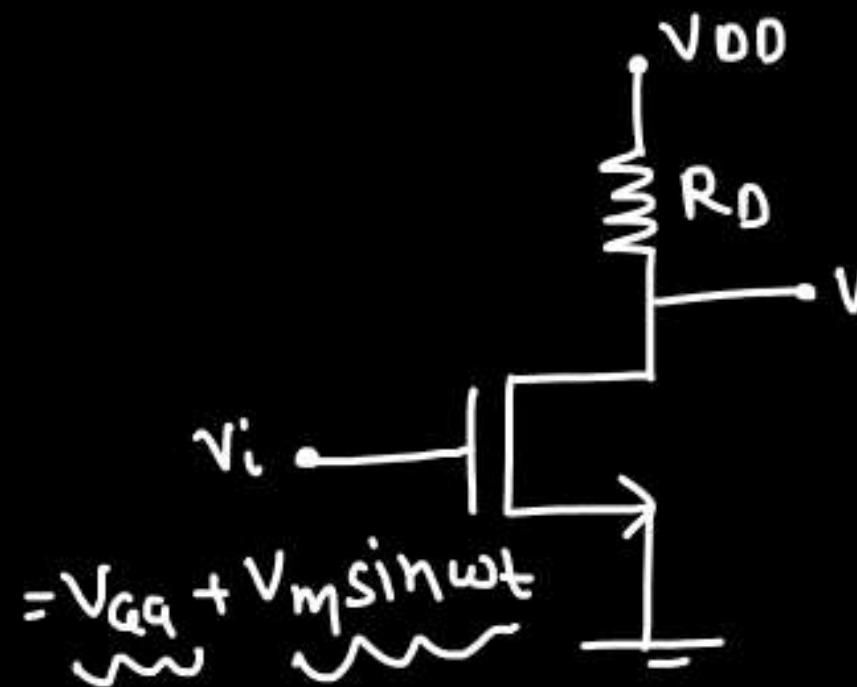


Here, for giving the dc bias, you need
to use two supplies V_{DD} and V_{GG}

NOT DESIRABLE


⇒ I will use only one supply.

New way of biasing:-

①

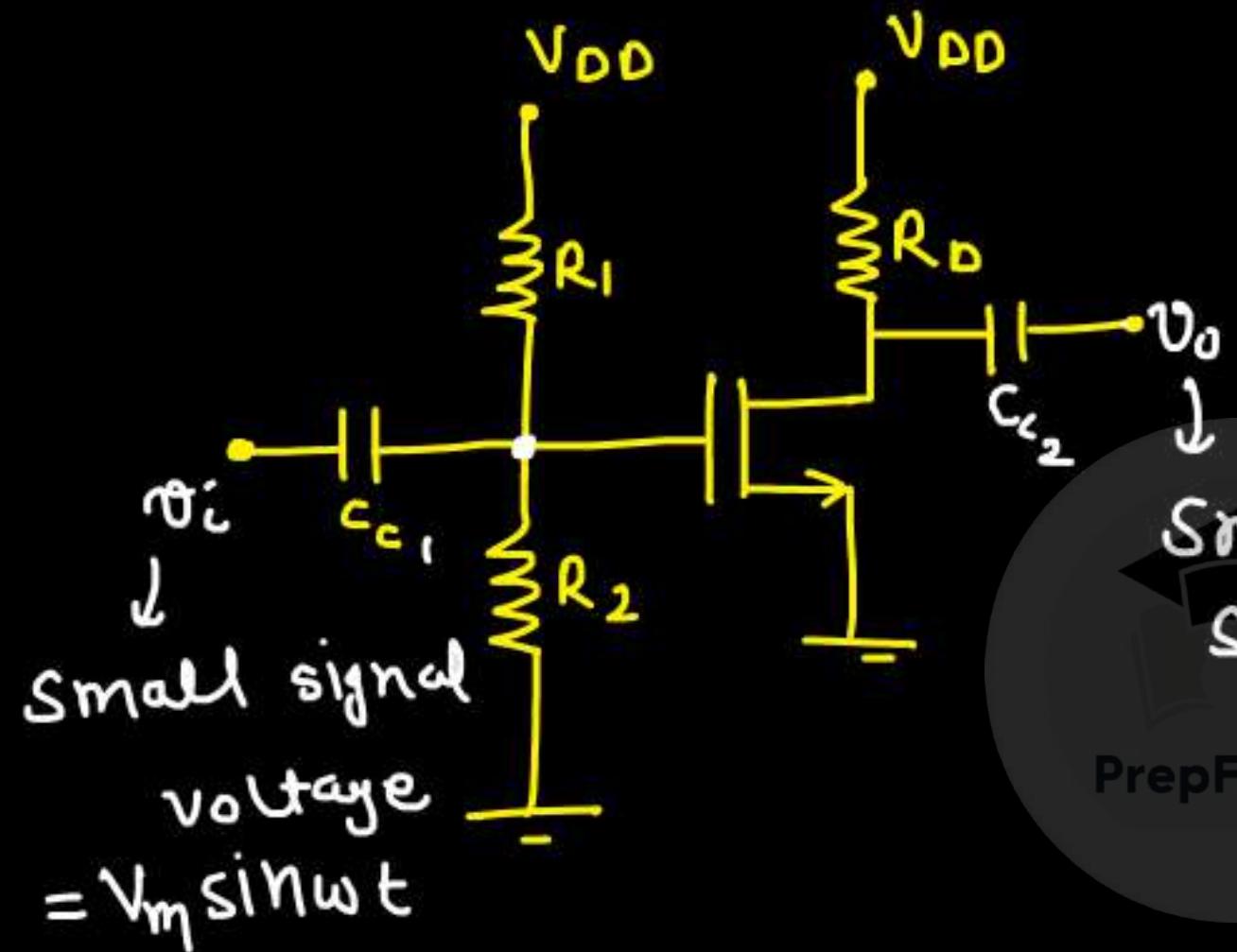

DC Analysis:-

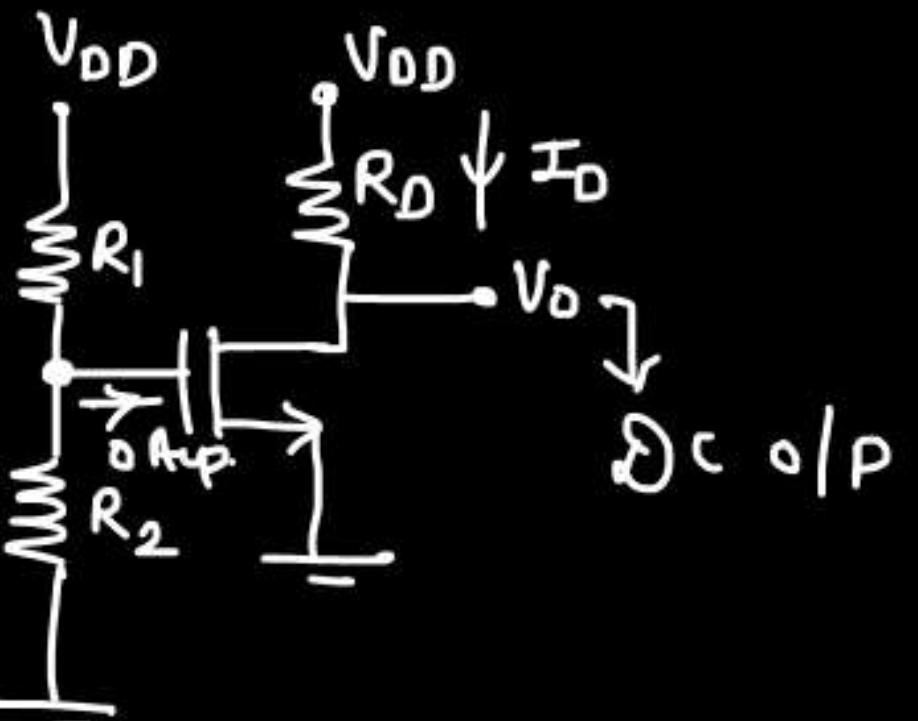

① Set R_1 and R_2 ; such that $V_{GS} > V_T$

$$\frac{V_{DD} \times R_2}{R_2 + R_1} > V_T$$



$$V_{GS} = \frac{V_{DD} R_2}{R_2 + R_1}$$

$$\Rightarrow V_o = V_{DD} - I_D R_D$$


$$I_D = \frac{4\pi \epsilon_0 \omega}{2L} (V_{GS} - V_T)^2$$

② Set R_2 , R_1 and R_D such that $V_{DS} > V_{GS} - V_T \rightarrow$ Ensuring Sat. region

AC Analysis:-

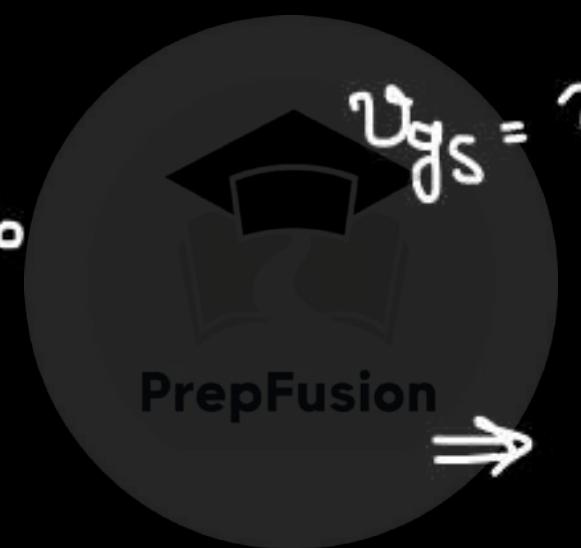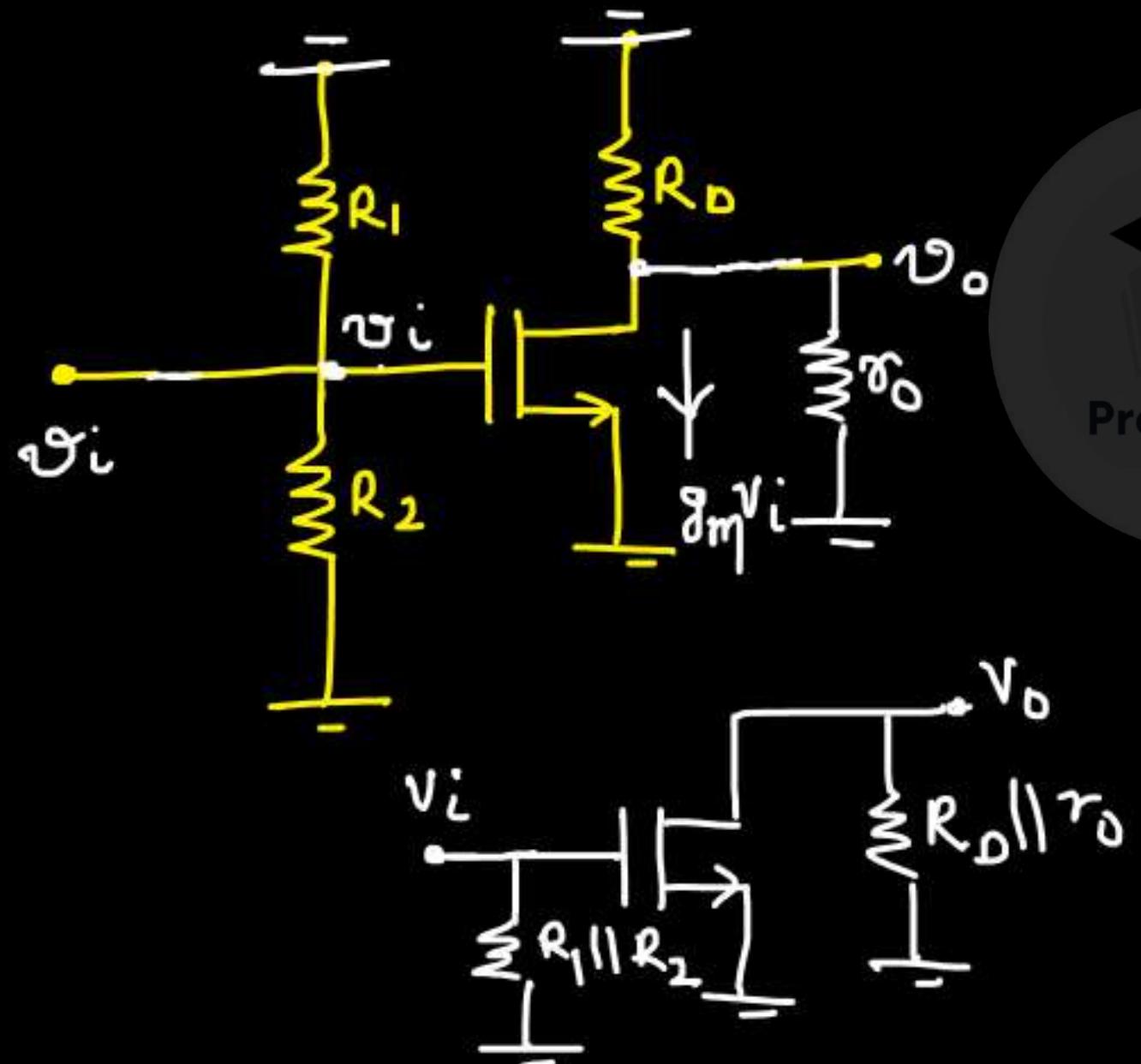


$$V_{GS} = V_i$$

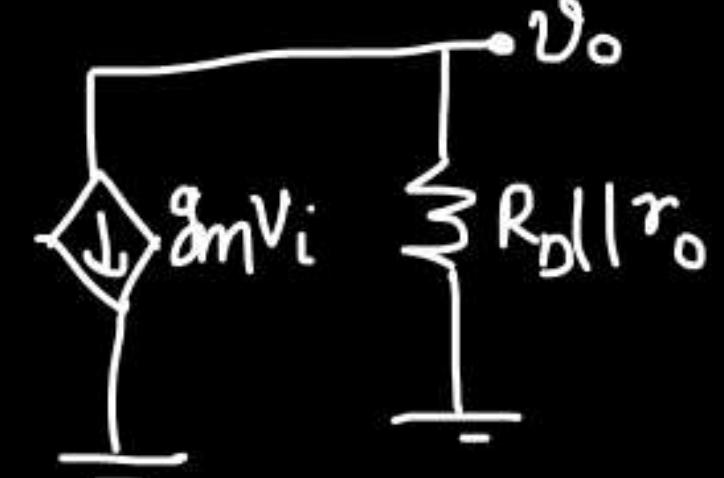

$$\frac{V_o}{V_i} = -g_m (R_D || r_o) \rightarrow \text{Voltage gain} =$$

Small Signal i/p resistance:-

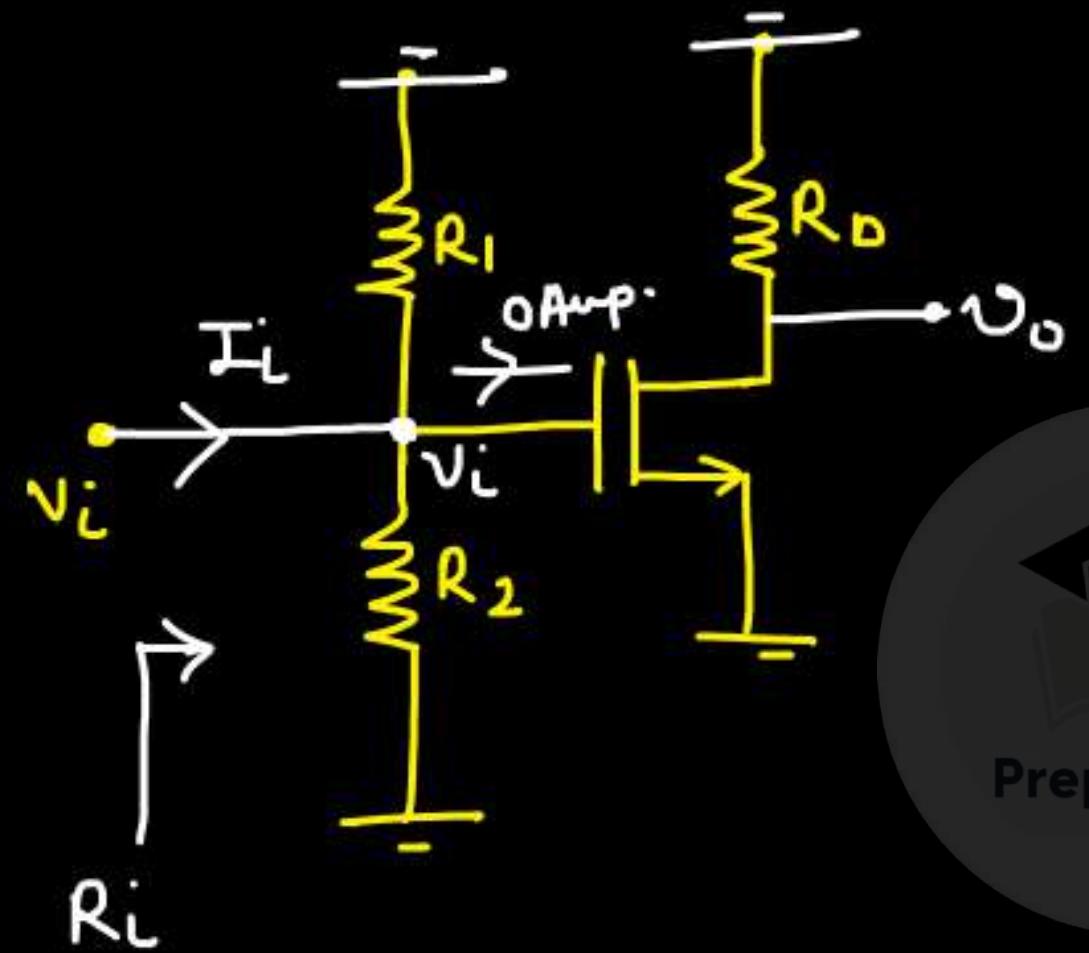

$$R_i = \frac{V_i}{I_i}$$

Nodal @ V_i


$$\frac{V_i}{R_1} + \frac{V_i}{R_2} = I_i$$

$$\frac{V_i}{I_i} = R_1 \parallel R_2$$

$$R_i = R_1 \parallel R_2$$




O/P resistance:-

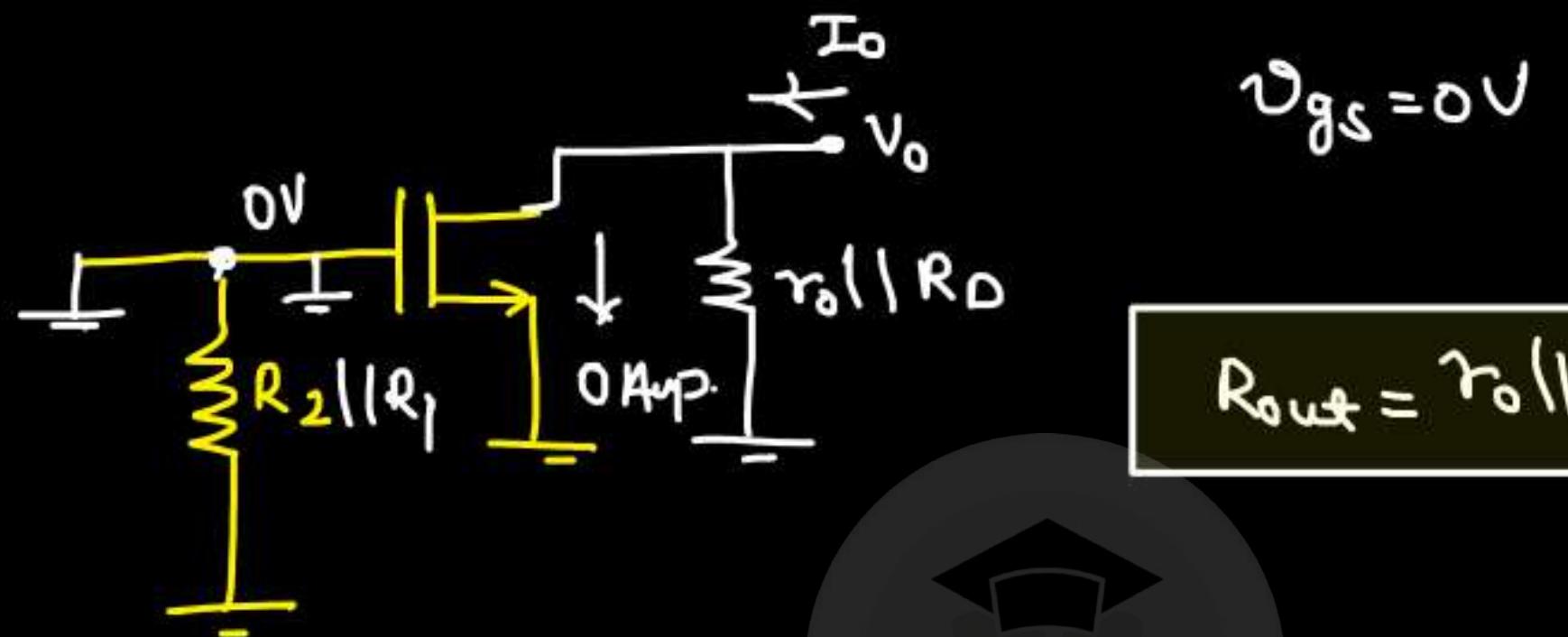


Why we use coupling capacitor (C_c) ?

- ① Helps in isolating the dc bias setting.
- ② If you are cascading two or more stages, then only ac signal from the 1st stage will pass to the next stage while dc is blocked.

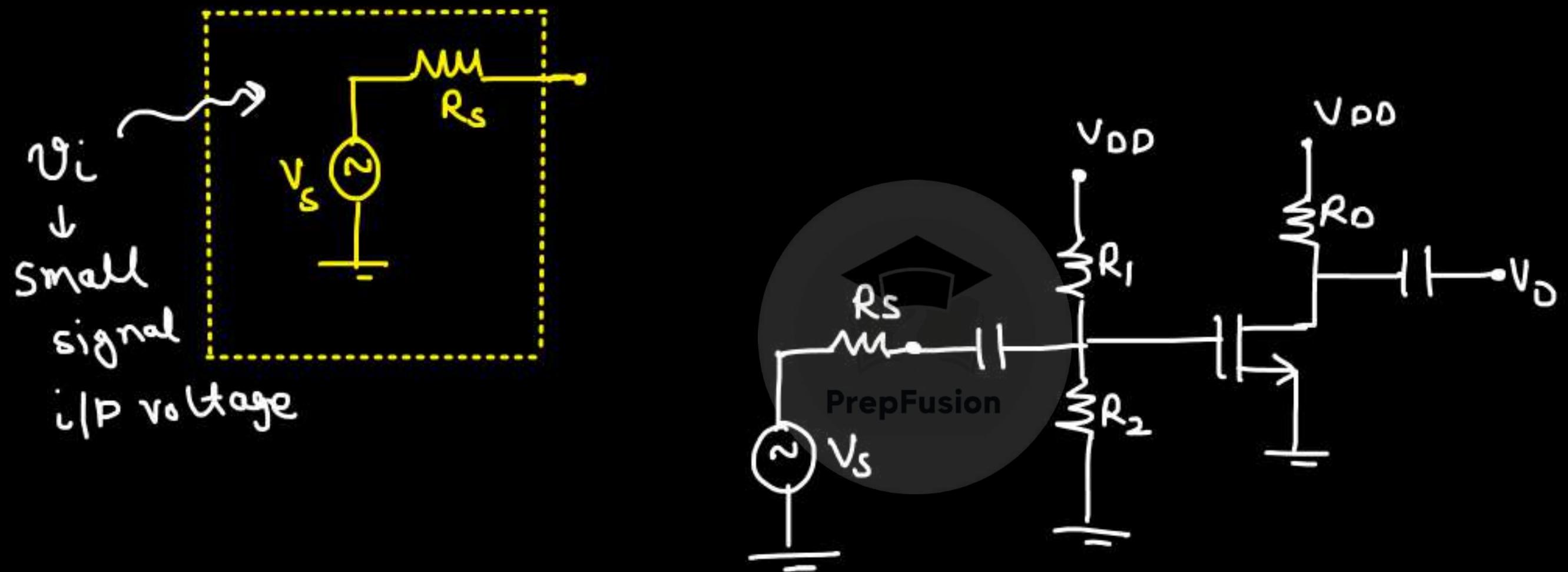If small signal input source has some
Resistance R_s .



Small Signal Analysis:-

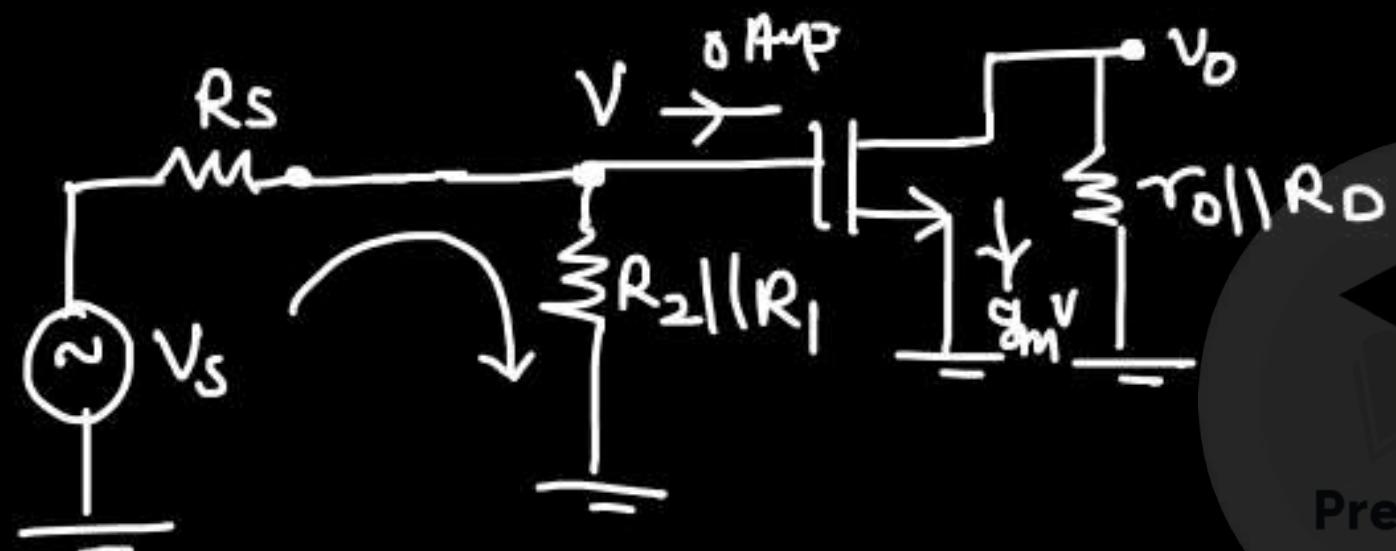

$$V_o = -g_m V [R_D || r_o]$$


$$V_o = -g_m [r_o || r_o] V = 0 \quad \text{--- (1)}$$

$$V = \frac{R_2 || R_1}{(R_2 || R_1) + R_s} \times V_s \quad \text{--- (2)}$$

PrepFusion


$$\text{Voltage gain} \quad g_m = \frac{V_o}{V_s} = -g_m [r_o || r_o] \times \frac{[R_2 || R_1]}{[R_2 || R_1] + R_s}$$

input resistance :-

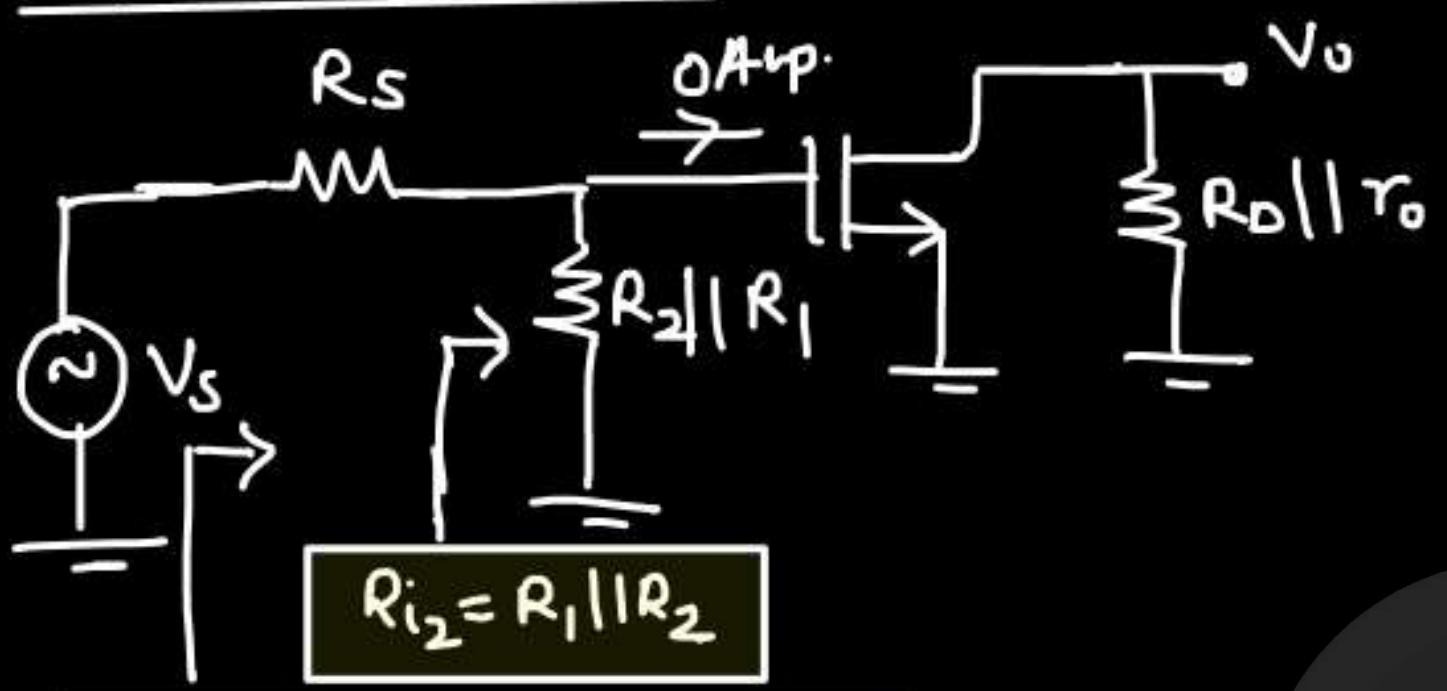


$$R_{i_1} = R_s + R_1 \parallel R_2$$

output resistance:-

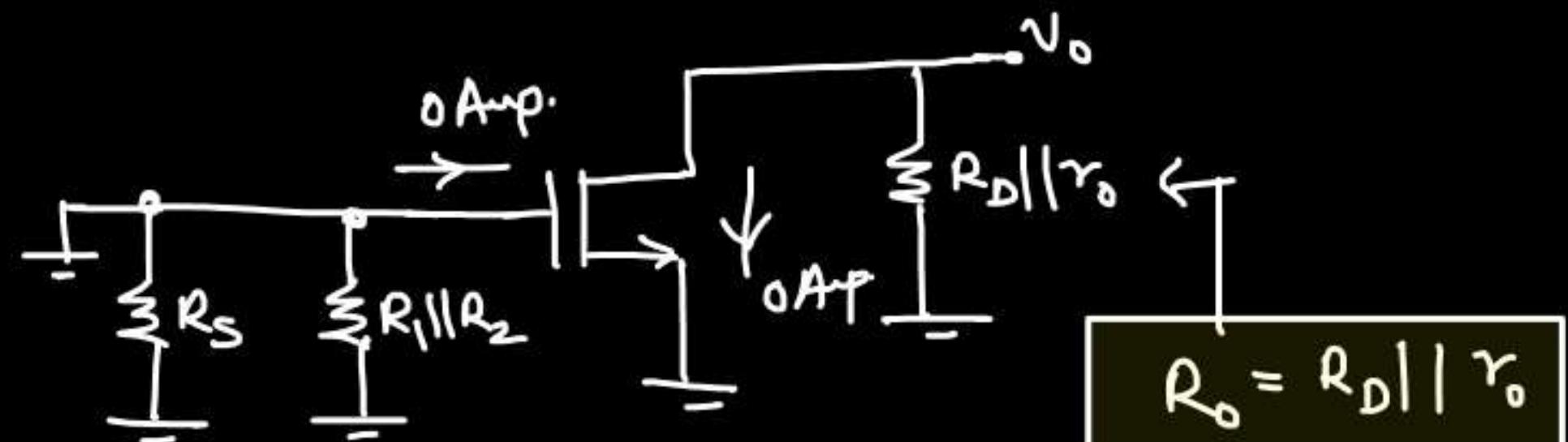


Miller's Theorem :-

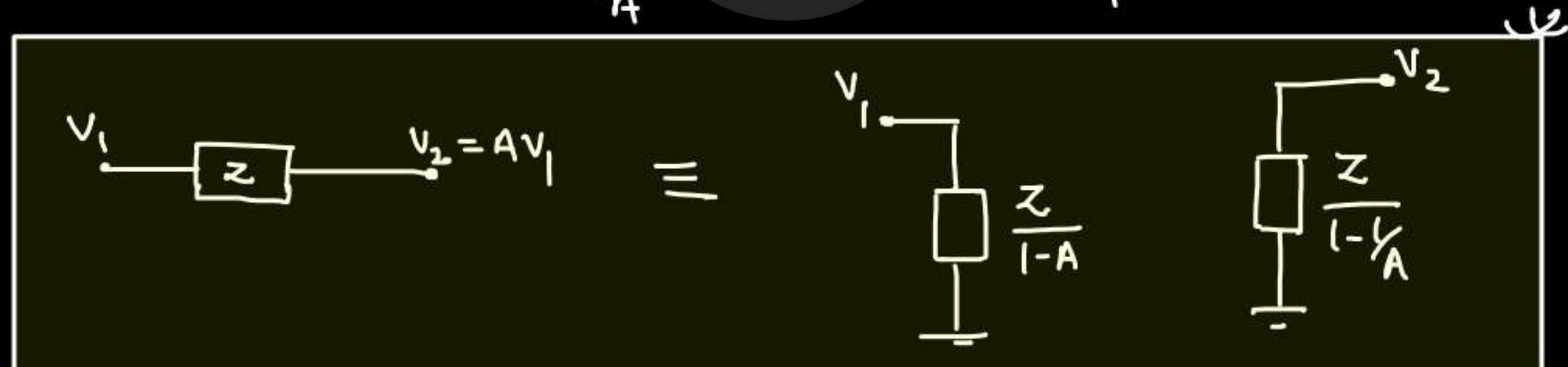
In a linear ckt, if there exist a branch with impedance z , connecting two nodes with nodal voltage v_1 and v_2 . We can replace this branch by two branches connecting the corresponding to ground by impedance respectively $\frac{z}{1-A}$ and $\frac{z}{1-\frac{1}{A}}$; where $A = v_2/v_1$



Derivation:-

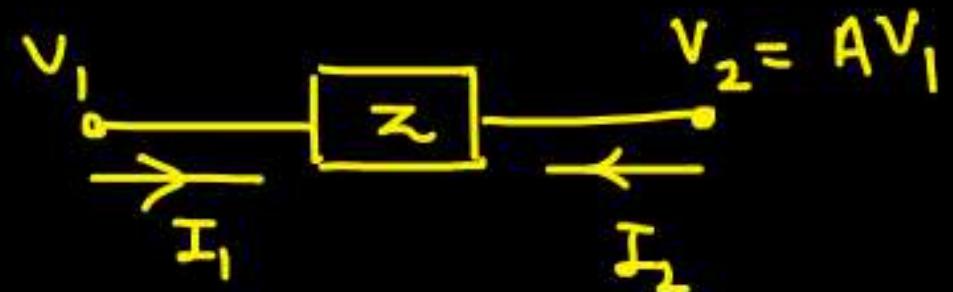

$$I_1 = -I_2$$

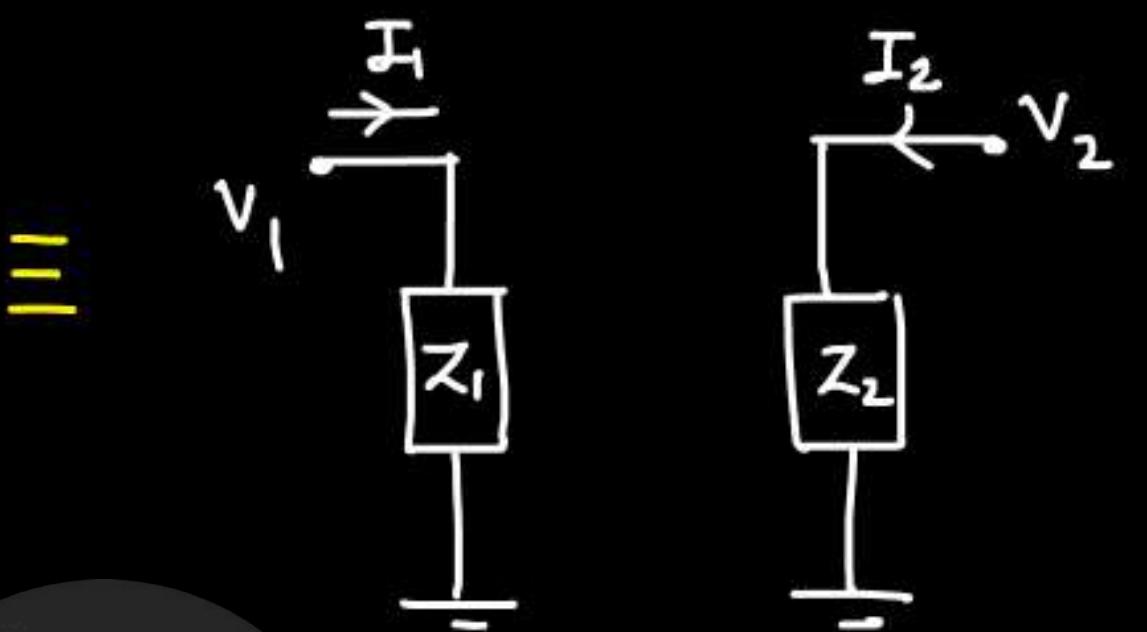

$$Z_1 = \frac{V_1}{I_1}$$

$$\frac{V_1 - V_2}{Z} = I_1$$

PrepFusion

$$Z_2 = \frac{V_2}{I_2}$$


$$\frac{V_2 - V_1}{Z} = I_2$$

$$\frac{V_1 - AV_1}{Z} = I_1$$


$$\frac{V_1}{I_1} = \frac{Z}{1-A} = Z_1$$

$$\frac{V_2 - V_1}{Z} = I_2$$
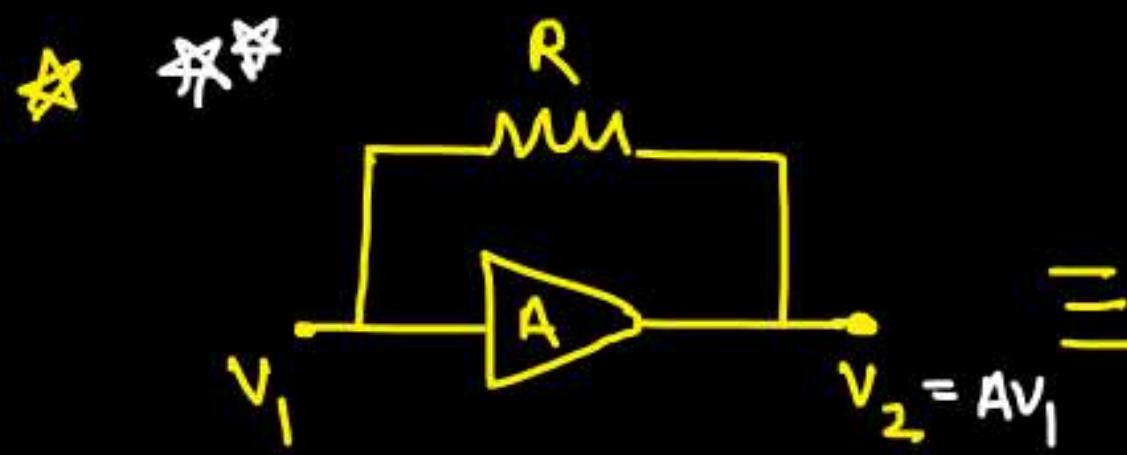
$$\frac{V_2}{I_2} = \frac{Z}{1-A} = Z_2$$



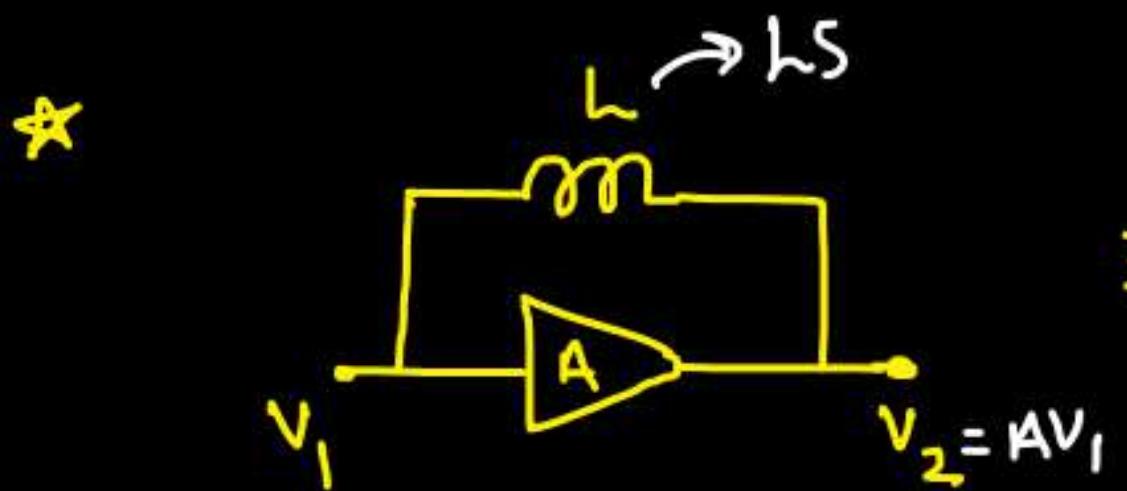
$$V_1 \left[\frac{R}{1-A} \right] \frac{V_2}{\frac{R}{(1-A)}} = V_1$$





PrexFusion
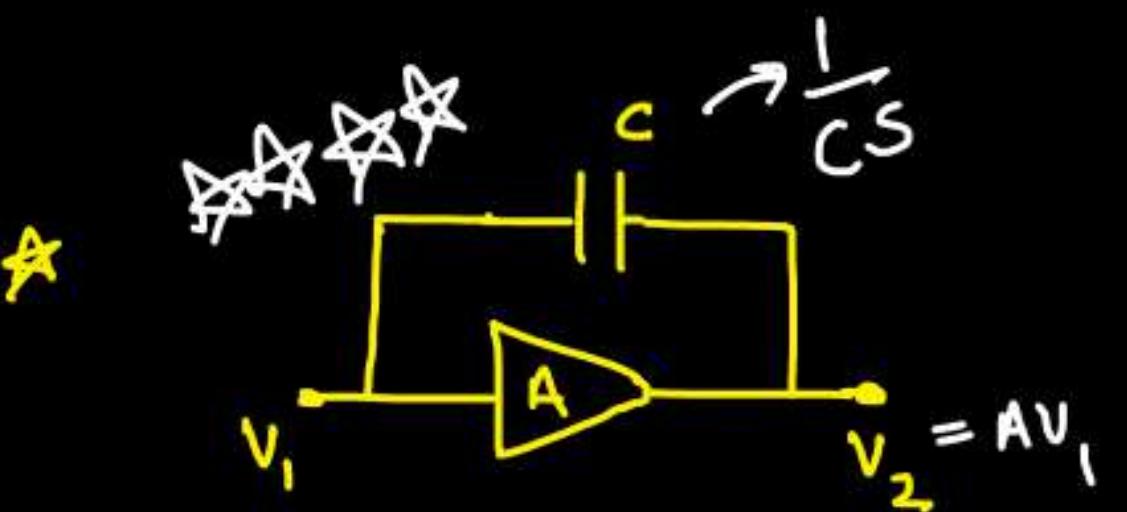
$$V_1 \left[\frac{L}{1-A} \right] \frac{V_2}{\frac{L}{1-A}} = V_1$$



$$V_1 \left[\frac{1}{1-C(1-A)} \right] \frac{V_2}{\frac{1}{1-C(1-A)}} = V_1$$

Eg.

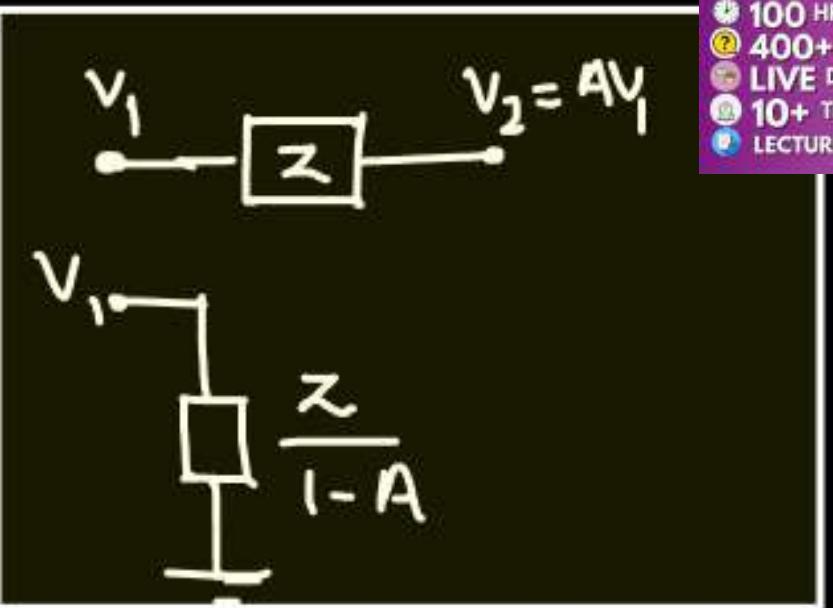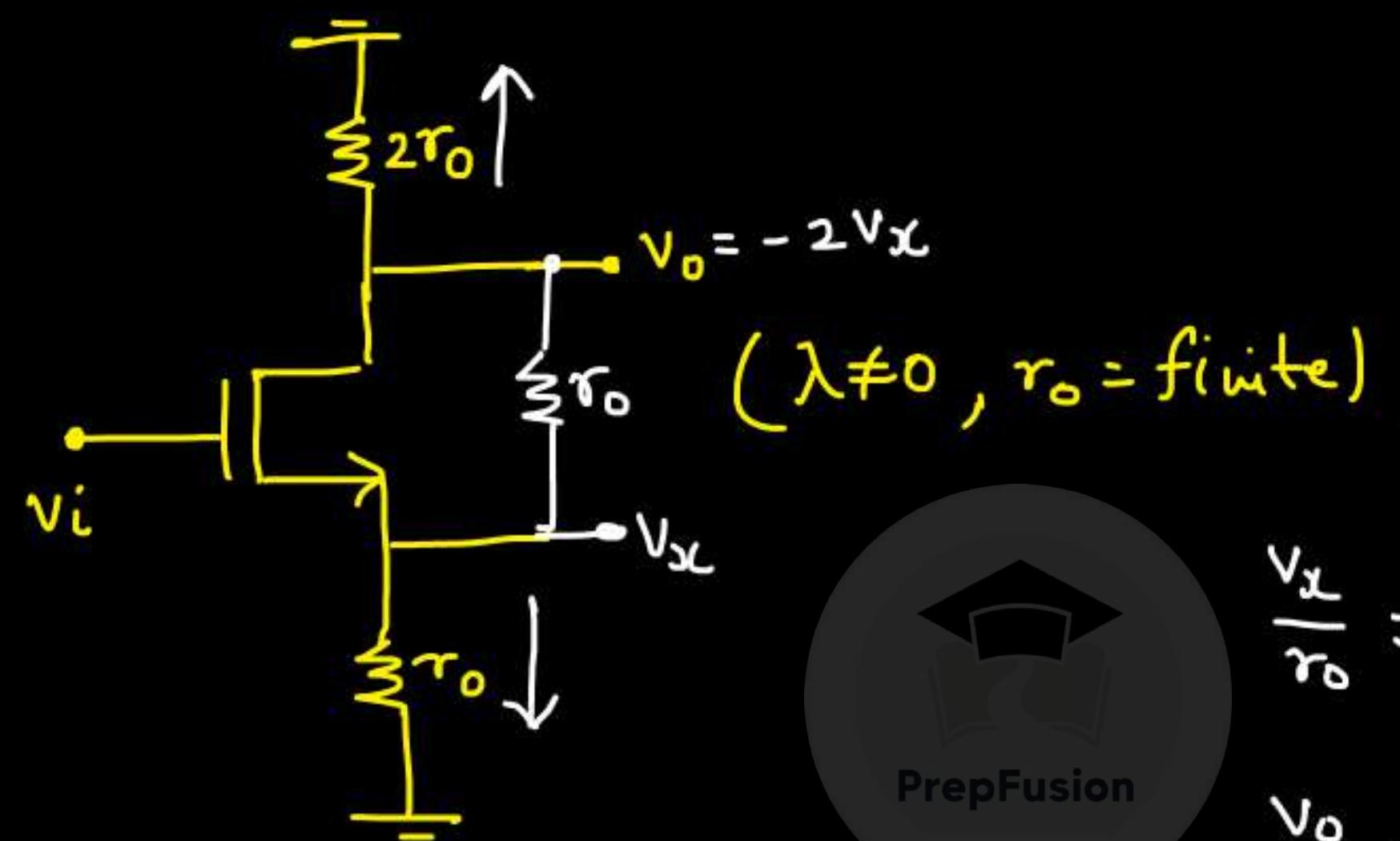

$$\frac{V_x}{r_o} = -\frac{V_o}{2r_o}$$


$$\frac{V_o}{V_x} = -2 \Rightarrow V_o = -2V_x$$

$$A = -2$$

$$\frac{V_x}{\frac{r_o}{1+2}} = \frac{r_o}{3}$$
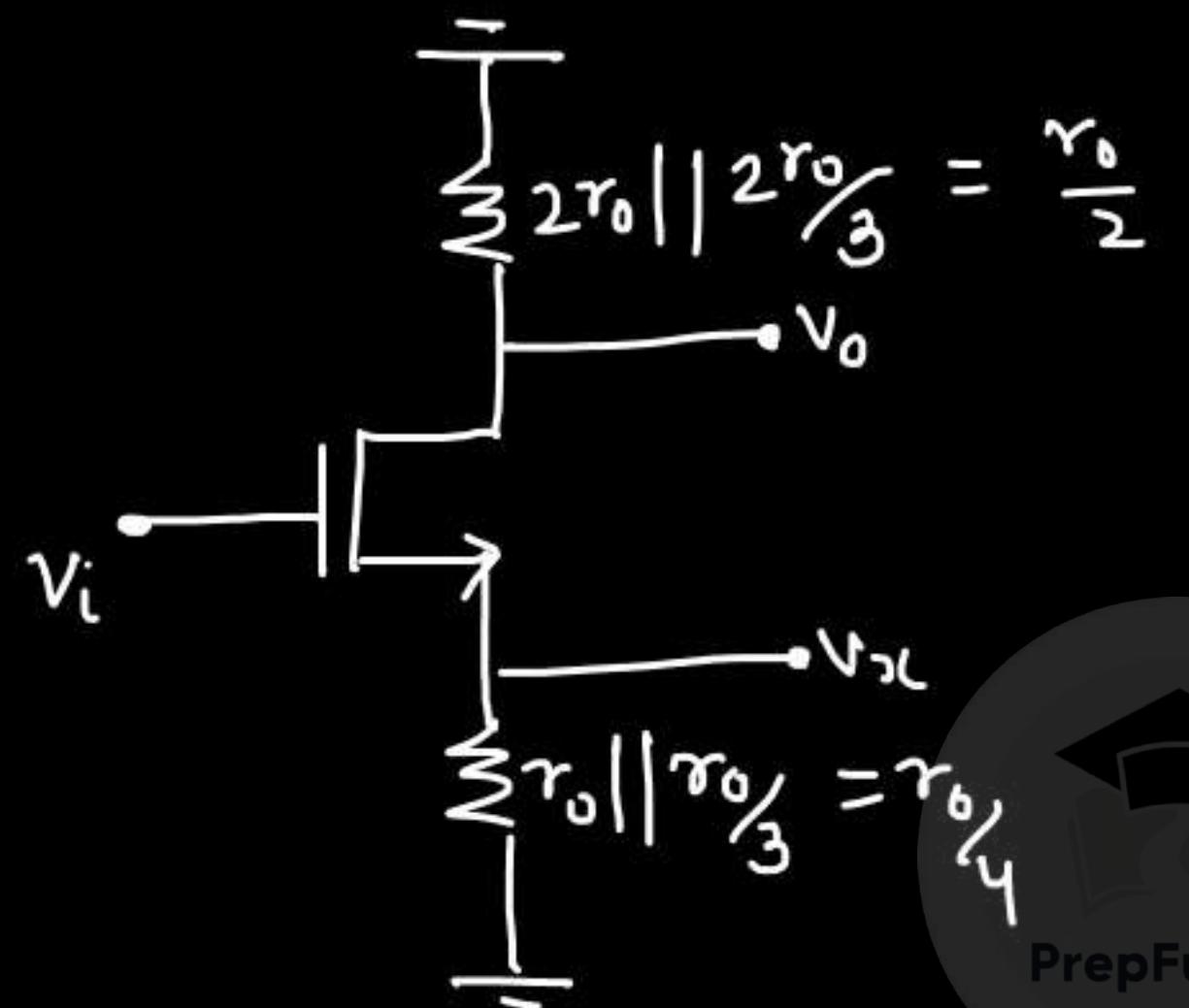
$$\frac{V_o}{\frac{r_o}{1+\frac{V_x}{2}}} = \frac{2r_o}{3}$$






$$\frac{V_0}{V_i} = - \frac{g_m \left[\frac{r_o}{2} \right]}{1 + g_m \left[\frac{r_o}{4} \right]}$$

$$= - \frac{g_m r_o / 2}{4 + g_m r_o}$$


$$\frac{V_0}{V_i} = - \frac{2 g_m r_o}{4 + g_m r_o}$$



② Self bias stage:-

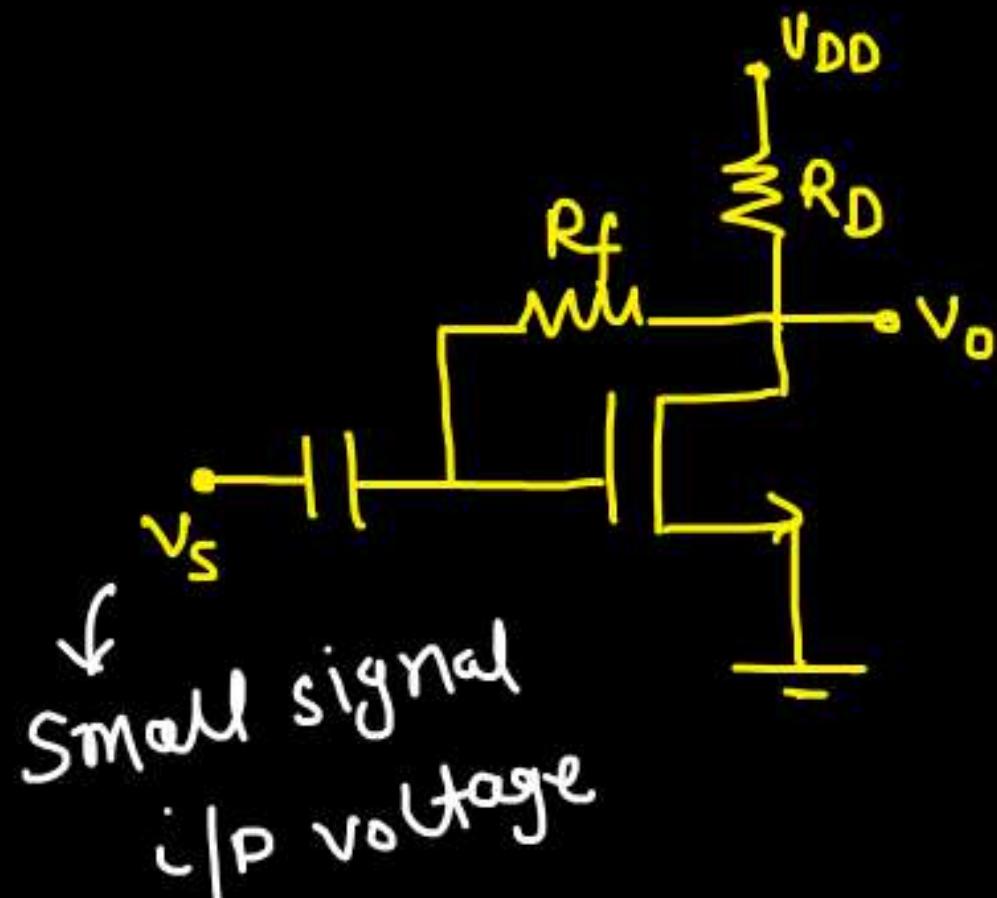

DC Analysis:-

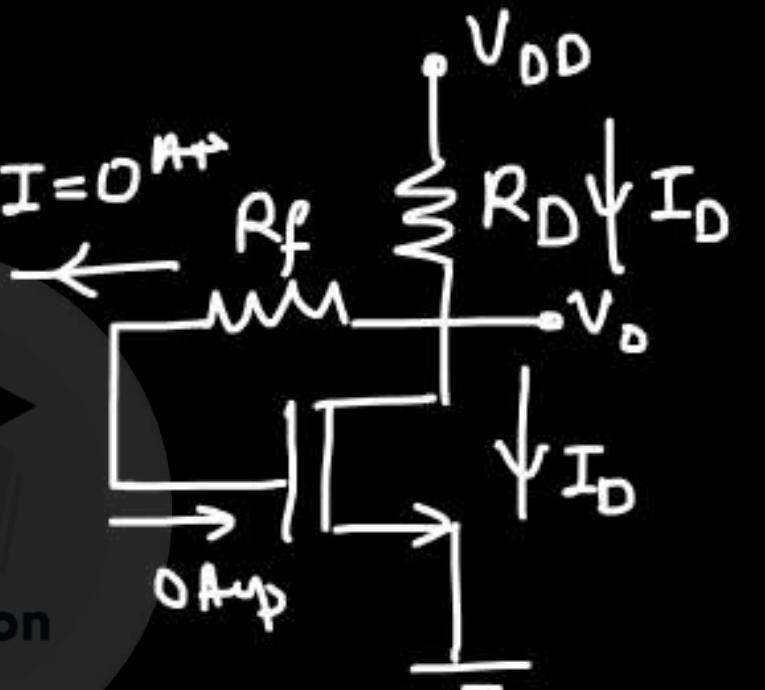

$$V_{GS} = V_o$$

$$V_{DS} = V_o$$

$$V_{OV} = V_o - V_T$$

$\Rightarrow V_{DS} > V_{OV} \Rightarrow$ Always in Sat.
=




① Make sure that

$$V_{DD} - I_D R_D > V_T$$

ensuring
MOS is ON



AC Analysis:-

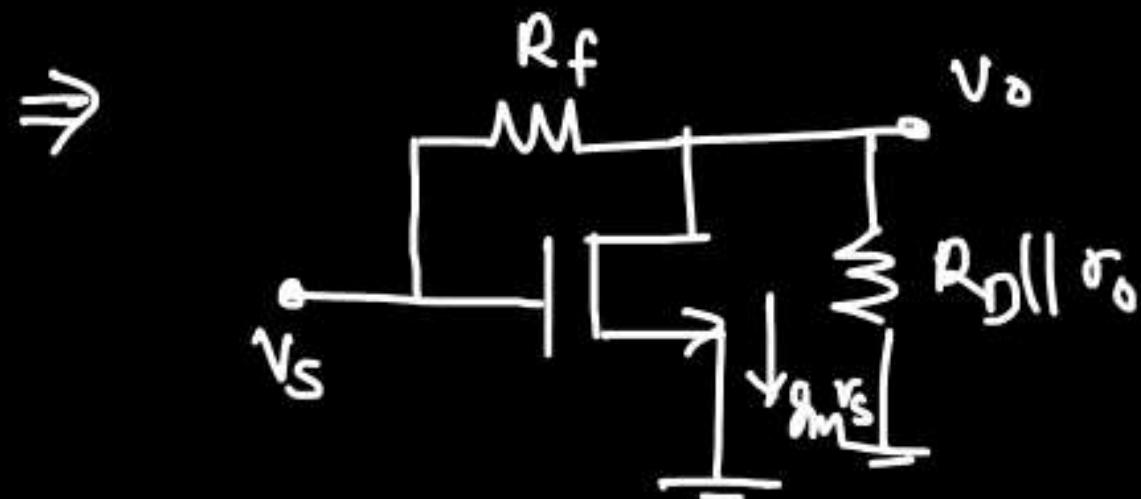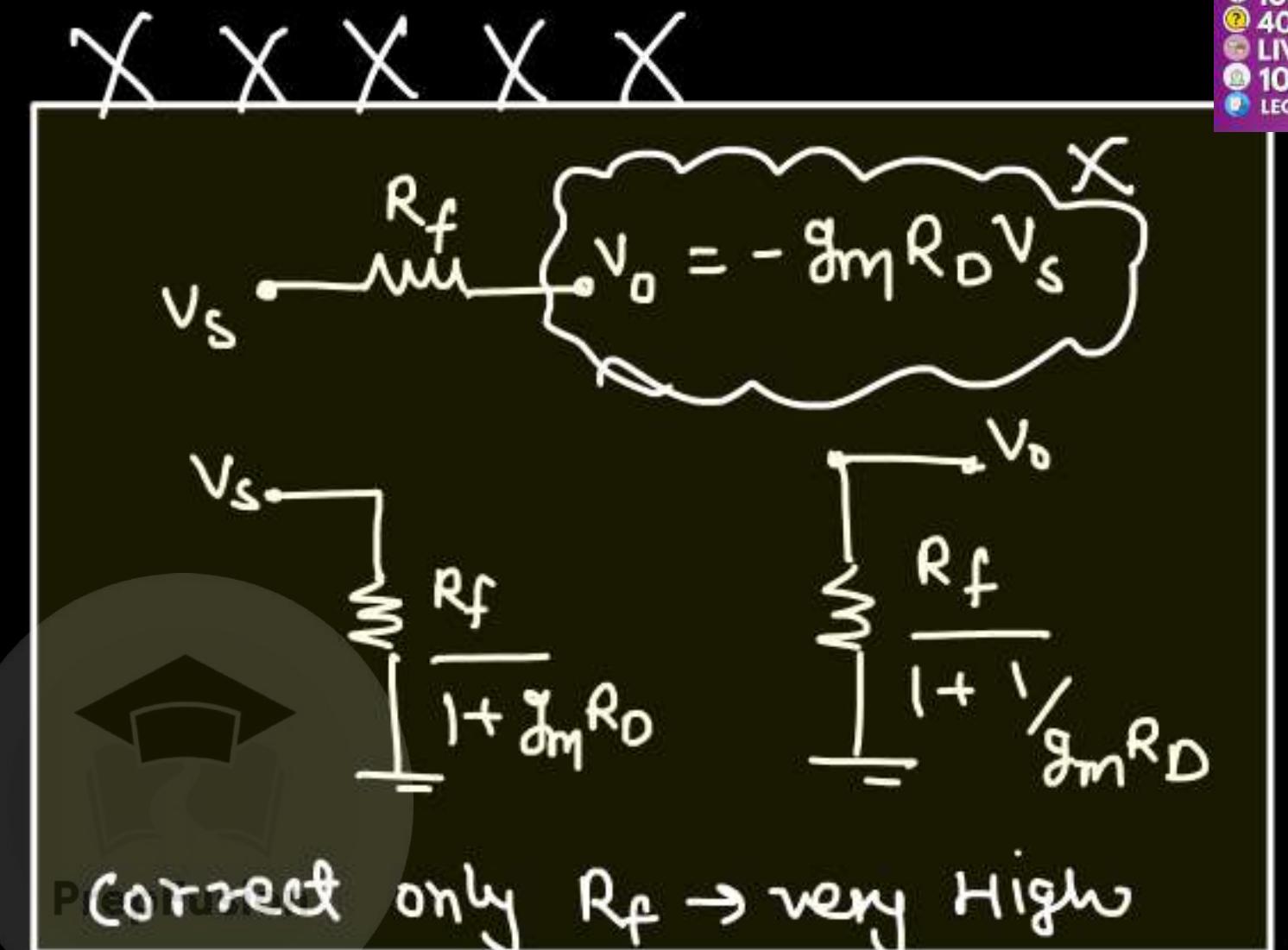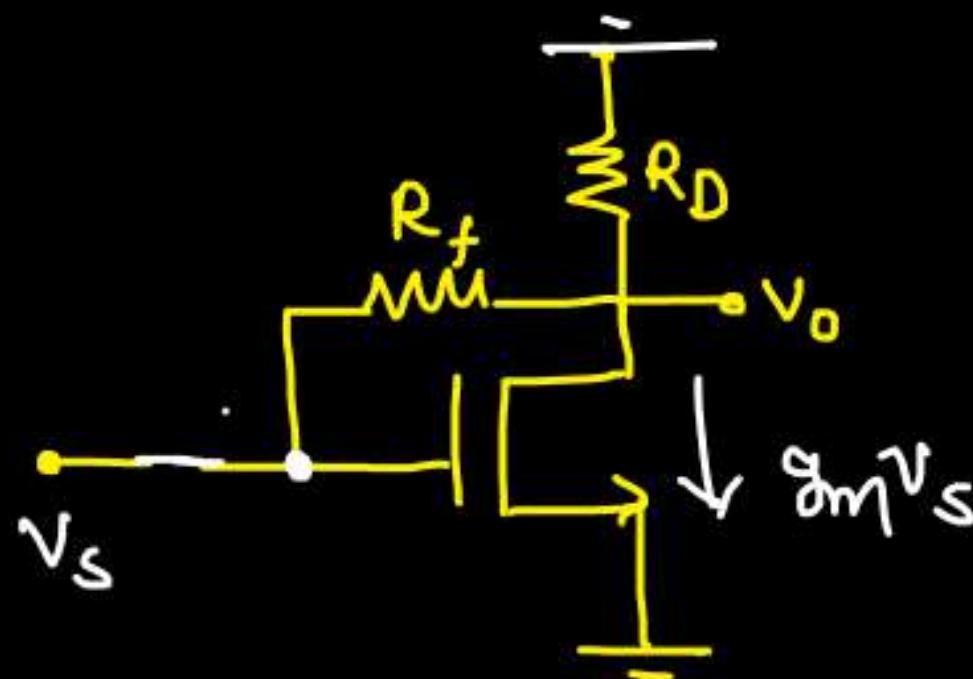

nodal @ V_o

$$\frac{V_o}{R_{D||r_s}} + g_m V_s + \frac{V_o - V_s}{R_f} = 0$$


$$\frac{V_o}{R_D \parallel r_o} + \frac{V_o}{R_f} = \frac{V_s}{R_f} - g_m V_s$$

$$\frac{V_o}{R_f \parallel R_D \parallel r_o} = \frac{V_s}{(-g_m \parallel R_f)}$$

$$\boxed{\frac{V_o}{V_s} = \frac{R_f \parallel R_D \parallel r_o}{-g_m \parallel R_f}}$$




M - II :-

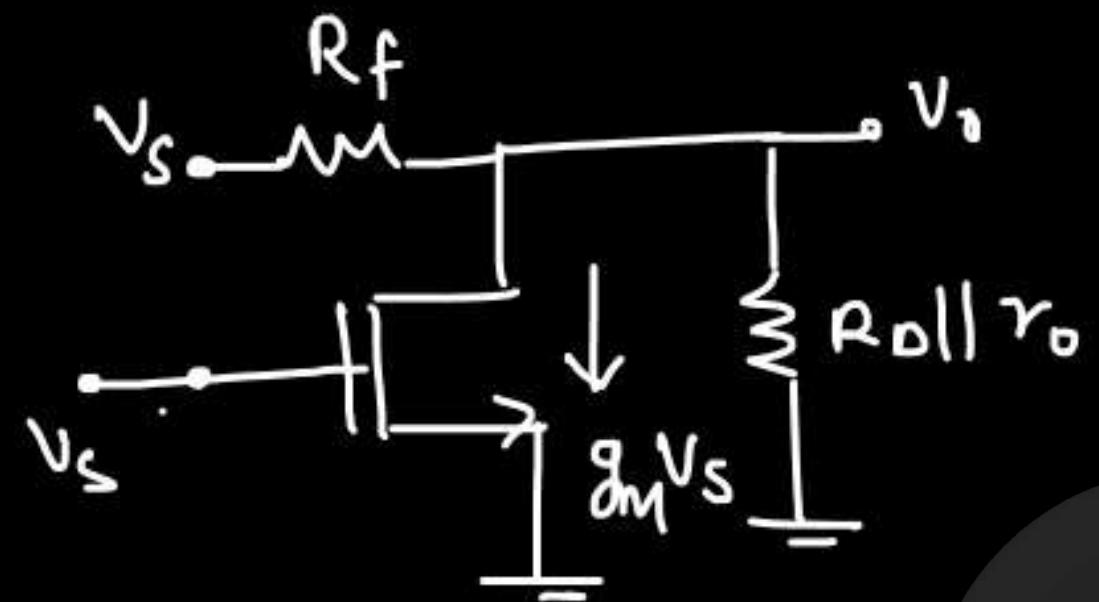


$$V_o = -g_m [R_D \parallel r_o \parallel R_f] V_s + \left[\frac{R_D \parallel r_o}{R_f + (R_D \parallel r_o)} \right] V_s$$

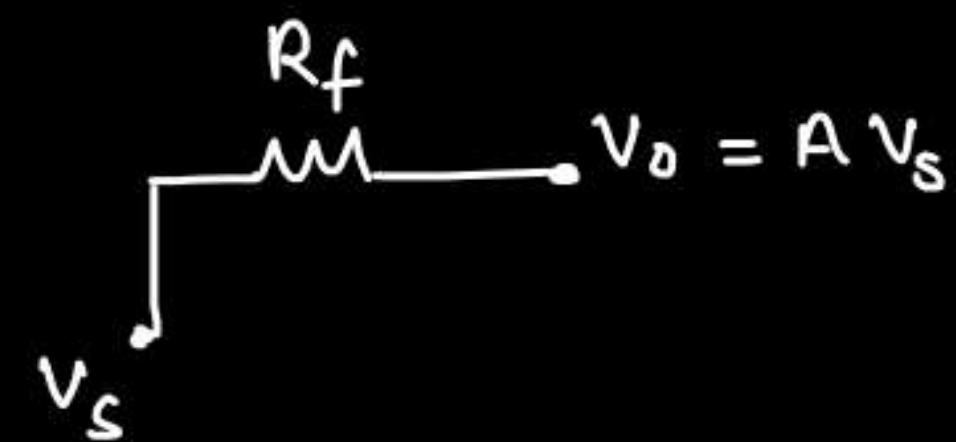
$$\frac{V_o}{V_s} = -g_m [R_D \parallel r_o \parallel R_f] + \frac{R_D \parallel r_o}{R_f + (R_D \parallel r_o)} = A$$



$$A = -\frac{R_f || r_o || R_f}{R_f + (R_f || r_o)}$$

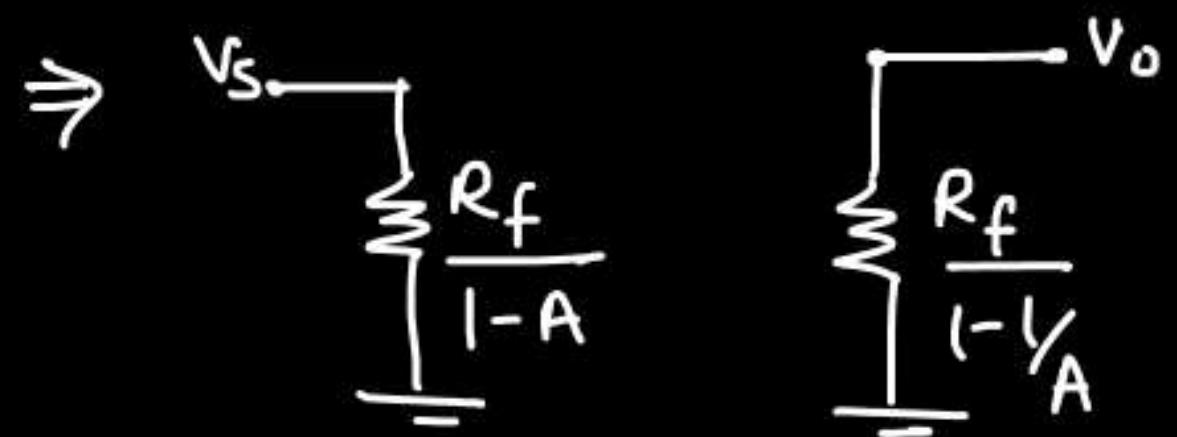

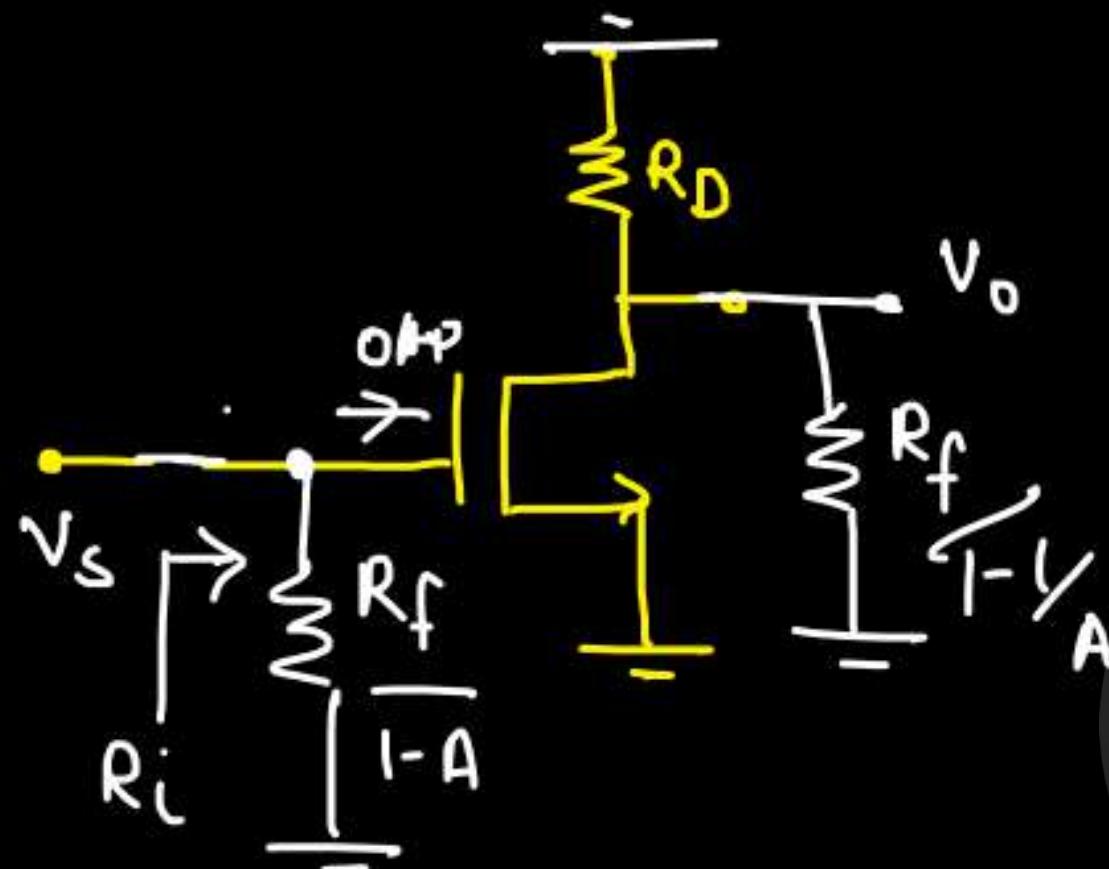input resistance :- / Output resistance :-




$$R_L = \frac{R_f}{1 - A}$$

$$R_o = R_D \parallel r_o \parallel \frac{R_f}{1 - A}$$

$$A = -g_m [R_D \parallel R_f \parallel r_o] + \frac{R_D \parallel r_o}{(R_D \parallel r_o) + R_f}$$

Assignment - 6

Q.

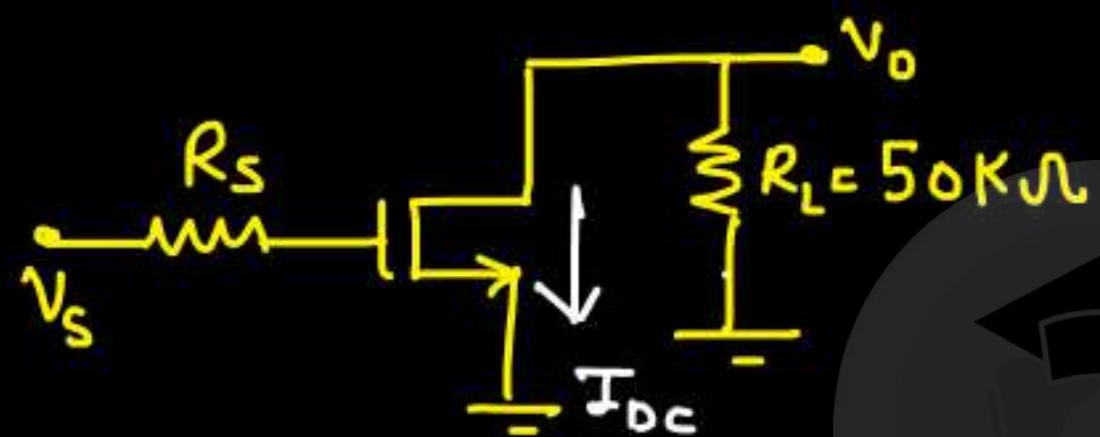

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$w/l = L$$

$$V_T = 1V, \lambda = 0$$

Small signal model is drawn. The gain magnitude is 8.

Determine the bias current flowing through the MOS.

$$\rightarrow |-g_m R_L| = 8 \Rightarrow g_m \times 50k = 8$$

$$g_m = 0.16mS$$


$$d\eta = \sqrt{\frac{2 \mu n C_o \times \omega}{L}} I_{Dc} = 0.16 \text{ m}$$

$$\sqrt{2 \times 100 \mu \times I_{Dc}} = 16 \times 10^{-5}$$

$$2 \times 10^{-4} \times I_{Dc} = 2.56 \times 10^{-10}$$

PreFision $I_{Dc} = 128 \text{ microAmp.}$ ↵

Q. 2

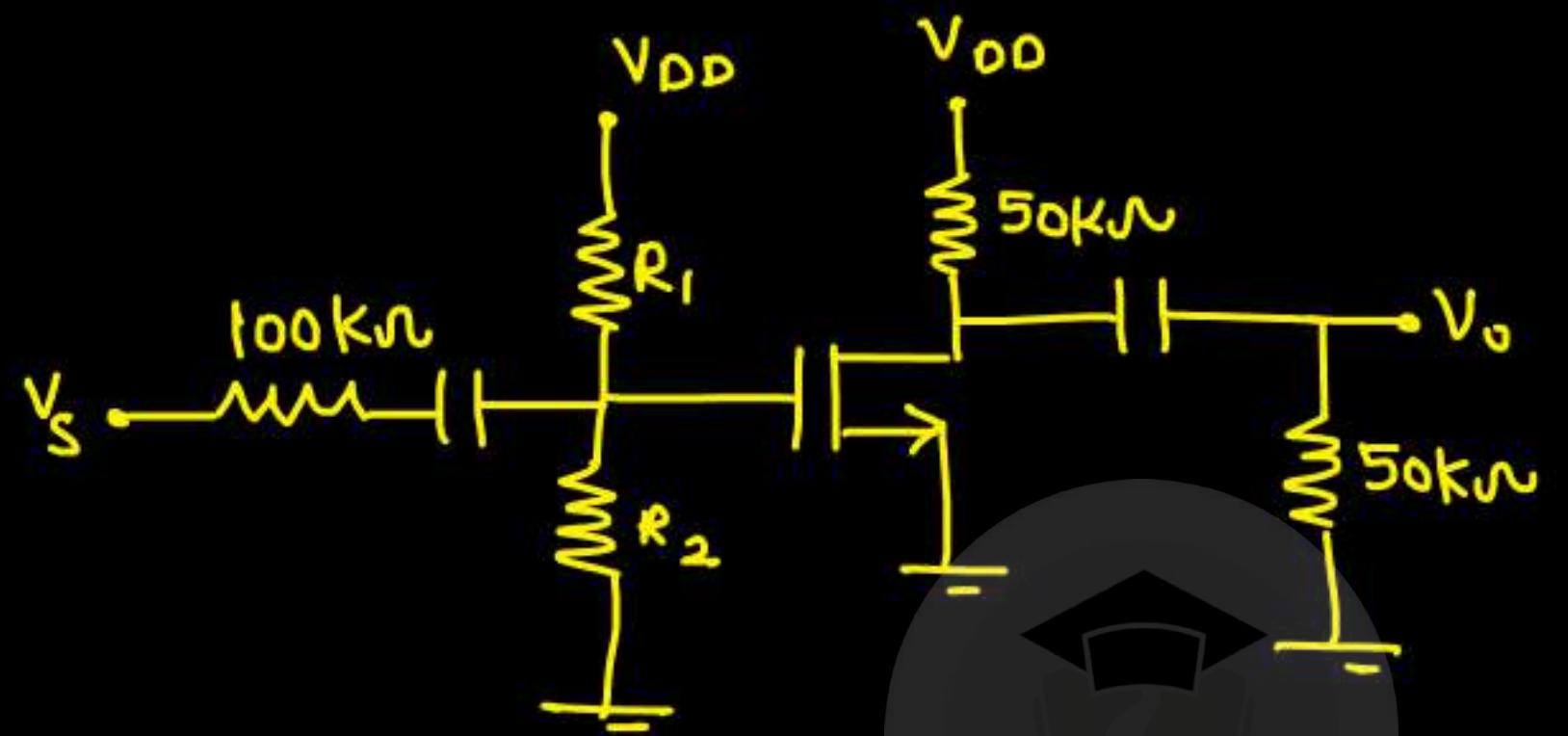


$\mu_{nCOX} = 100 \text{ mA/V}^2$, $w_L = 1$, $V_T = 1\text{V}$. The transistor is biased @ 128mA.

At operation point; $V_{DS} = V_{GS} + 1$

The bias current flowing through $R_{1,2}$ is 10mA.

- ① Determine V_{DD} .
- ② Determine R_1 & R_2 .
- ③ Determine small signal gain $\frac{V_o}{V_s}$.

① DC Analysis :-

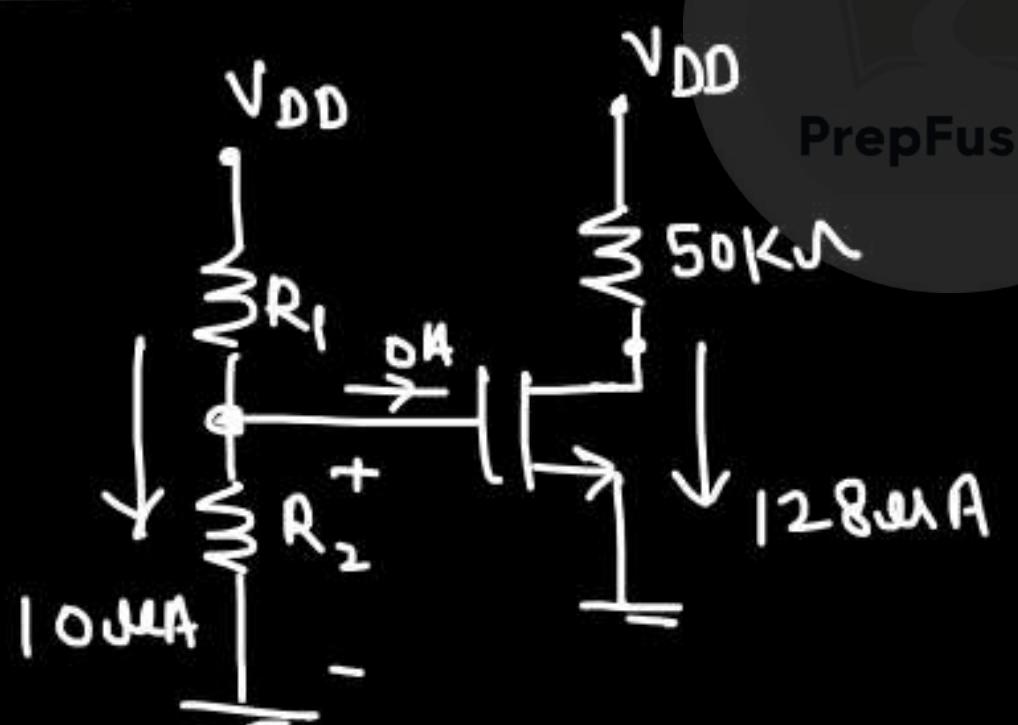

$$V_{DS} = V_{GS} + I \quad [\text{Given}]$$

$$V_{OV} = V_{GS} - V_T = V_{GS} - I$$

$V_{DS} > V_{OV} \Rightarrow$ Sat. region =

$$\Rightarrow V_{DS} = V_{DD} - 50K \times 128\mu$$

$V_{DS} = V_{DD} - 6.4$

— ①

$$I_D = 128 \mu A \quad [\text{Given}]$$

$$\frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 = 128 \mu$$

$$\frac{100\mu}{2} (V_{GS} - 1)^2 = 128 \mu$$

$$V_{GS} - 1 = \sqrt{2.56}$$

$V_{GS} = 2.6 \text{ V}$
PrepFusion

— ②

$$V_{DS} = V_{GS} + 1 \quad [\text{Given}]$$

$$V_{DD} - 6.4 = 2.6 + 1$$

$V_{DD} = 10 \text{ V}$

Ans.

② $R_1 = ?$, $R_2 = ?$

Given, $\frac{V_{DD}}{R_1 + R_2} = 10 \mu A$

$$\frac{10}{R_1 + R_2} = 10 \mu A$$

$$R_1 + R_2 = 1 M\Omega = 1000 k\Omega$$



Here, $V_{GS} = 10 \mu A \times R_2 = 2.5$



$$R_2 = 250 k\Omega$$

$$R_1 = 750 k\Omega$$

Ans.

Ans.

③ Small signal voltage gain :-

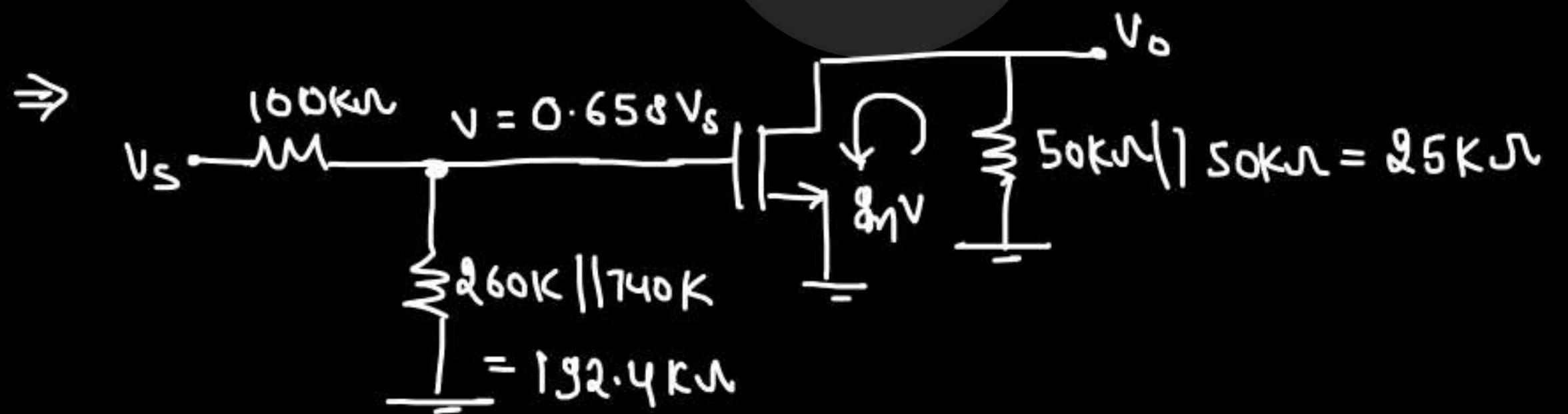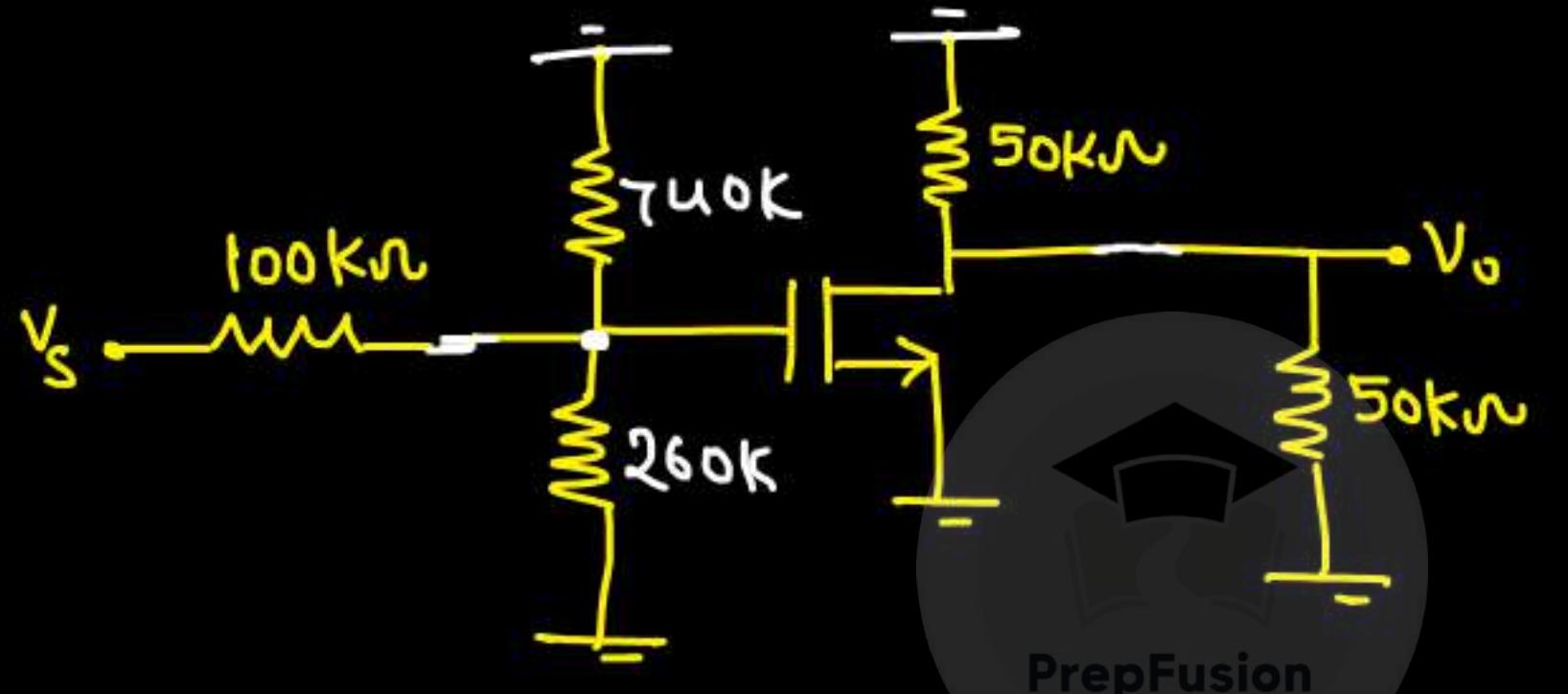

$$V_o = -g_m [25 \text{ k}\Omega] \times 0.658 V_s$$

$g_m = ?$

$$g_m = \frac{2 I_{DC}}{(V_{GS} - V_T)} = \frac{2 \times 128 \mu}{1.6} = 160 \mu S$$


$$V_o = -160 \times 10^{-6} \times 2.5 \times 10^3 \times 0.658 V_s$$



Preparation

$$\frac{V_o}{V_s} = -2.63 \text{ V/V}$$

Q.

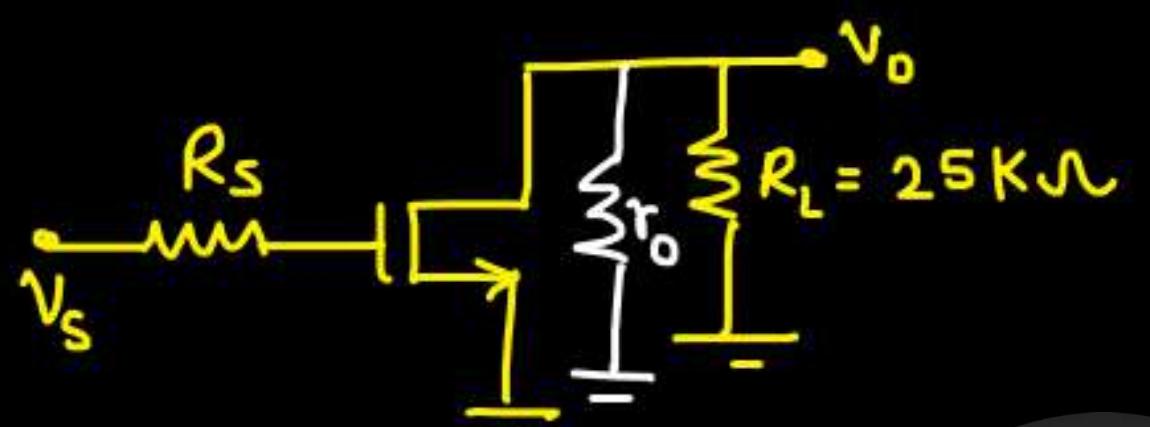

$$\mu_{nCOX} = 100 \mu\text{A}/\text{V}^2$$

$$w/L = 1$$

$$V_T = 1 \text{ V}$$

considering $\lambda=0$, you calculated the gain to be -4.

PrepFusion

Later, you realised that $\lambda = 0.0625 \text{ V}^{-1}$.

Find the actual small signal gain.

$$\rightarrow -g_m \times 25k\Omega = -4$$

$$g_m = \frac{4}{25k\Omega} = 0.16 \text{ mS}$$

$$\text{Actual gain} = -g_m [\gamma_0 \parallel 25\text{k}\Omega] \quad \textcircled{1}$$

$$\gamma_0 = ?$$

$$\gamma_0 = \frac{1}{\lambda [I_D]}_{\text{Sat. - ideal}}$$

$$g_m = 0.16 \text{ mS}$$

$$\sqrt{2 \times 100 \mu \times I_D} = 0.16$$

$I_D = 128 \mu\text{A}$



$$\Rightarrow \gamma_0 = \frac{1}{0.0625 \times 128 \mu}$$

$$\gamma_0 = \frac{10^6}{8}$$

$\gamma_0 = 125 \text{k}\Omega$

$$\text{Actual gain} = -0.16 \times 10^{-3} [125 || 25] \times 10^3$$

$$A_V = -3.33$$

Ans

N.B. -

Usually, we consider same g_m value for both of the cases

$$\lambda=0 \text{ & } \lambda \neq 0$$

$$[g_m]_{\lambda=0} = \frac{\mu_n C_{ox} \omega}{L} (V_{GS} - V_T)^2$$

$$[g_m]_{\lambda \neq 0} = \frac{\mu_n C_{ox} \omega}{L} (V_{GS} - V_T)^2 [1 + \lambda V_{DS}]$$


Since λ = very small $\Rightarrow [g_m]_{\lambda=0} = [g_m]_{\lambda \neq 0}$

Q. All the transistors are identical with


$$\frac{MnC_oxW}{L} = 100 \mu\text{A}/\text{V}^2, V_T = 1\text{V}, \lambda = 0$$

(biased in sat. region)

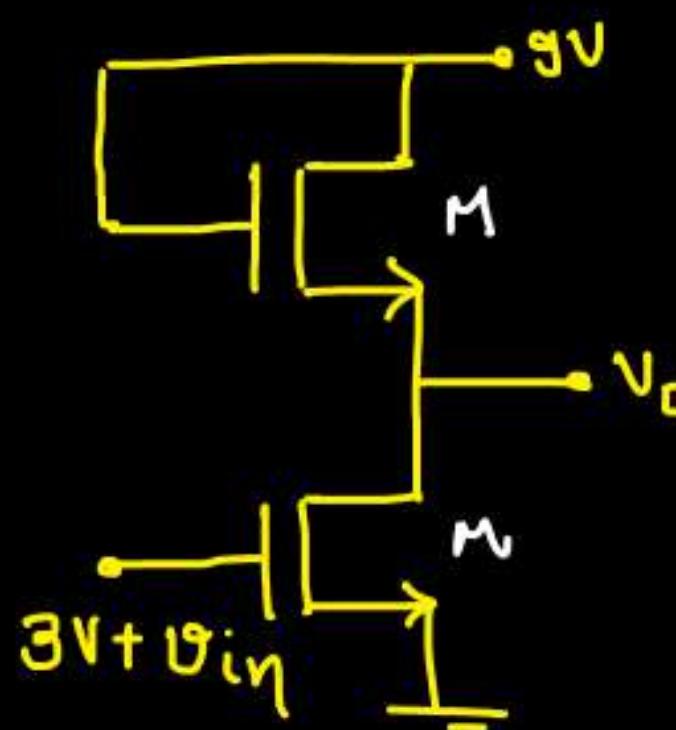Determine small signal voltage gain for (a) & (b).




(a)

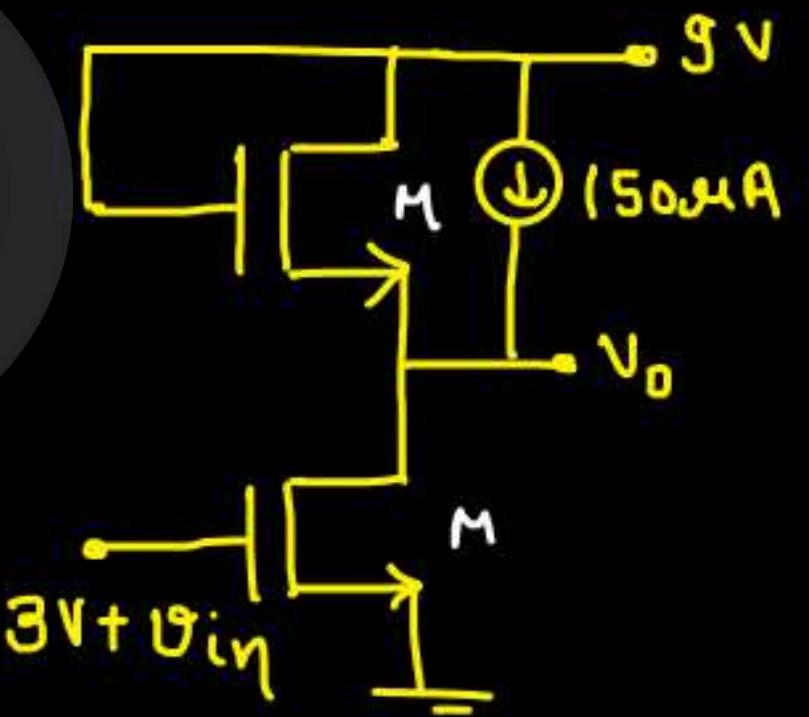

(b)




(i)

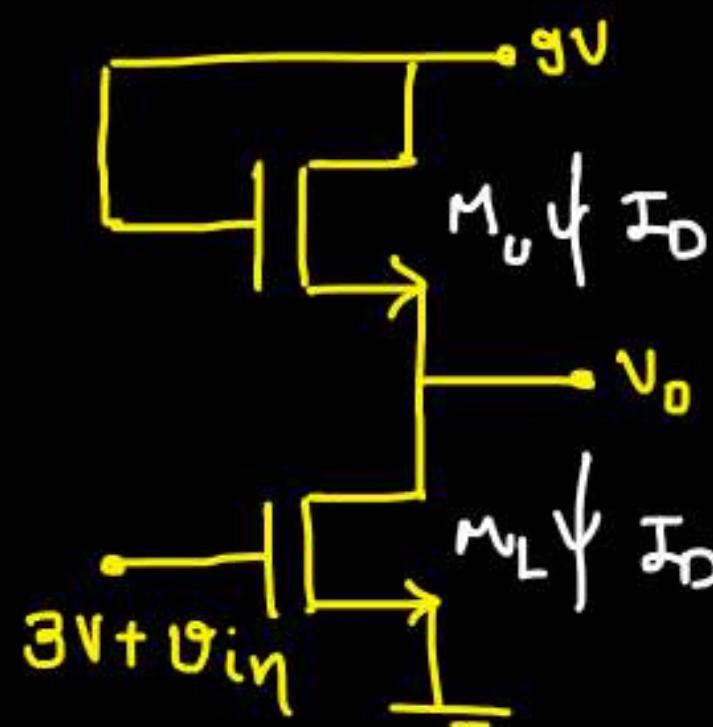

(a)

⇒

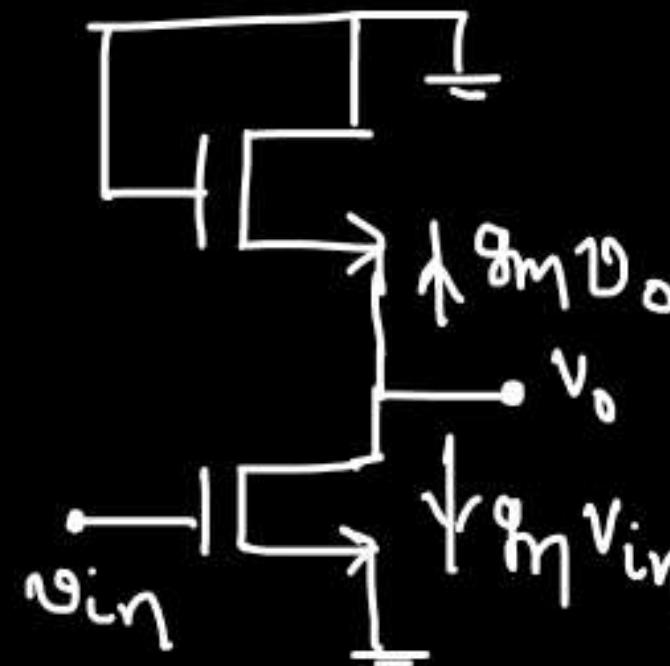


Both M_U and M_L will have same
 g_m value.

$$\left[g_m = \sqrt{2 \mu_n C_{ox} W \frac{I_D}{L}} \right]$$



$$g_m V_{in} = -g_m V_o$$

$$\frac{V_o}{V_{in}} = -1$$

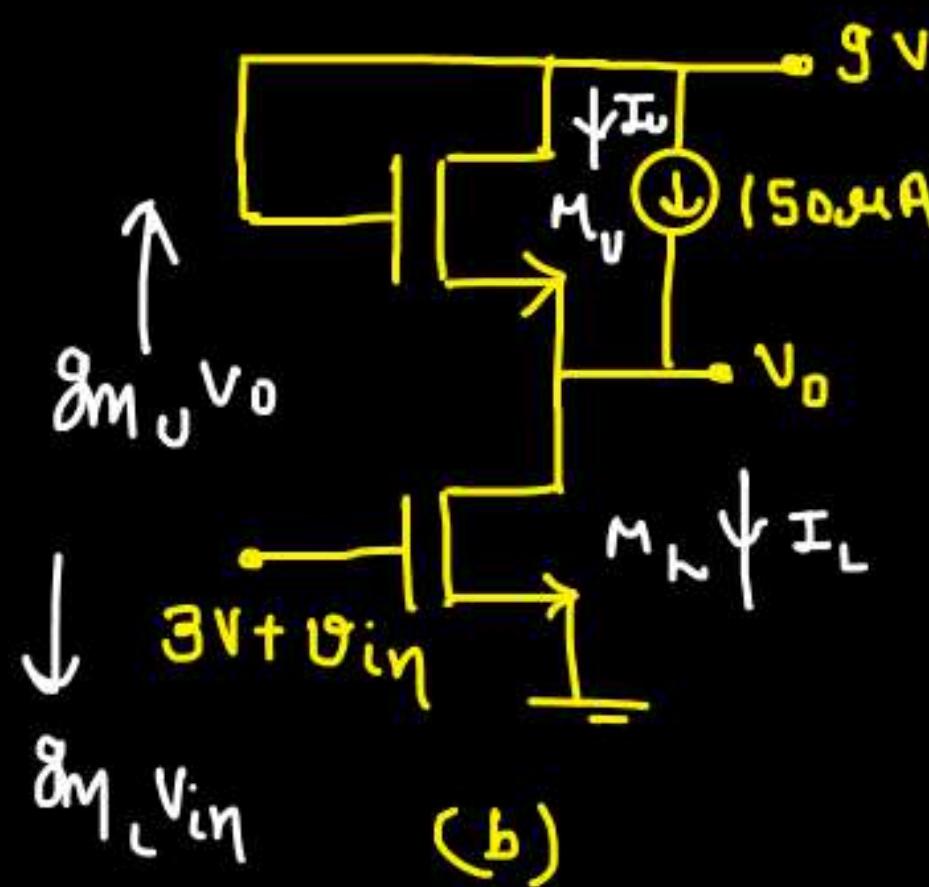

Small signal gain

$$A_V = -\frac{g_m L}{g_m U} \quad (2)$$

$$I_U = 150\mu A - I_L$$

Here the dc current is not same in both transistors, so g_m will be different.

$$I_L = \frac{100\mu A}{2} (3-1)^2$$

PrepFusion

$$\begin{aligned} I_L &= 200\mu A \rightarrow g_m L \\ I_U &= 50\mu A \rightarrow g_m U \end{aligned}$$

$$g_m = \sqrt{\frac{2\mu n C_{ox} W}{L}} I_D$$

$$\Rightarrow g_m \propto \sqrt{I_D}$$

$$\frac{g_m L}{g_m U} = \frac{\sqrt{I_{D_L}}}{\sqrt{I_{D_U}}}$$

$$\frac{g_m L}{g_m U} = \frac{\sqrt{200 \mu}}{\sqrt{50 \mu}}$$


$$\frac{g_m L}{g_m U} = 2$$

⇒

$$m_v = -2$$



Q.

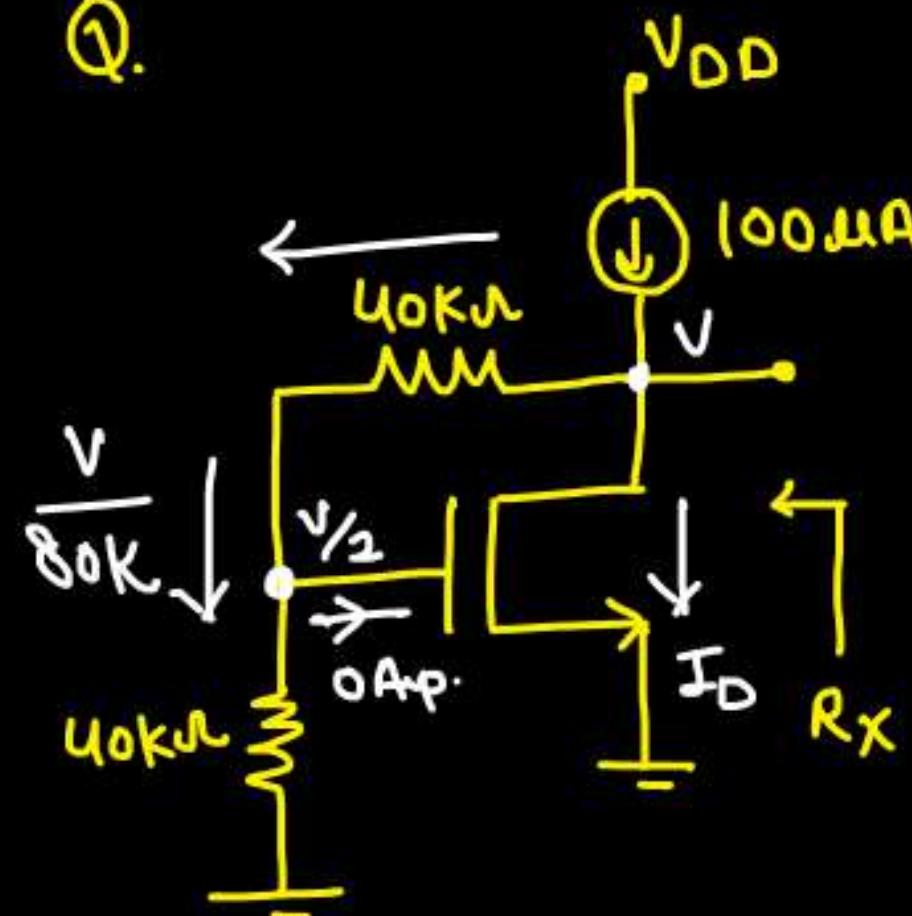

$$\frac{\mu n C_{ox} W}{L} = 100 \mu A / V_2, V_T = 1V, \lambda = 0$$

- ① Determine the bias current in the transistor.
- ② find small signal resistance R_X .

$$① V_{DS} = V$$

$$V_{GS} = V_2$$

$$V_{OV} = V_2 - 1$$

$$\Rightarrow V_{DS} > V_{OV} \Rightarrow \text{Sat.}$$

PrepFusion

$$100 \mu A = \frac{V}{80k} + I_D$$

⑨

$$I_D = \frac{100 \mu A}{2} (V_2 - 1)^2 \quad \text{--- (D)}$$

$$100\mu = \frac{V}{0.08} \times \mu + 50\mu \left(\frac{V}{2} - 1 \right)^2$$

$$100 = 12.5V + 50 \left(\frac{V^2}{4} + 1 - V \right)$$

$$100 = 12.5V + 12.5V^2 + 50 - 50V$$

$$12.5V^2 - 37.5V - 50 = 0$$

$$V^2 - 3V - 4 = 0$$

$$V^2 - 4V + V - 4 = 0$$

$$\begin{matrix} V & \rightarrow & -1 \\ & \searrow & \swarrow \\ & 4 & \end{matrix}$$


$$\Rightarrow V = 4V$$

$$V_{DS} = 4V, V_{GS} = 2V$$

$$I_D = \frac{100\mu}{2} (2-1)^2$$

$$I_D = 50\mu\text{Amp}$$

Small Signal Analysis:-

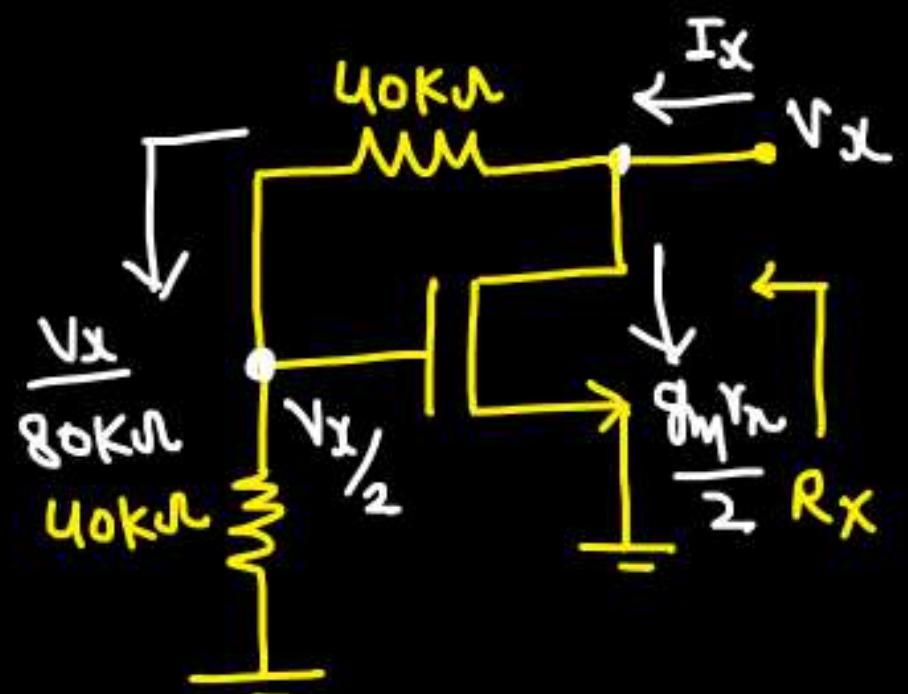

$$R_x = \frac{V_L}{I_x}$$

Preposition

$$\frac{V_x}{80K} + \frac{g_m V_x}{2} = I_x$$

$$R_x = 80K \parallel \frac{1}{g_m}$$

$$g_m = ?$$

$$g_m = \sqrt{2 \mu n C_{ox} W I_D / L}$$

$$= \sqrt{2 \times 100 \mu \text{A} \times 50 \mu \text{s}}$$

$$g_m = 100 \mu\text{s}$$

$$R_x = 80K \parallel \frac{2}{10^{-4}}$$


$$R_x = 80K \parallel 20K$$

$$R_x = 16K\Omega$$

ANS.
=




Common Gate Amplifier:-

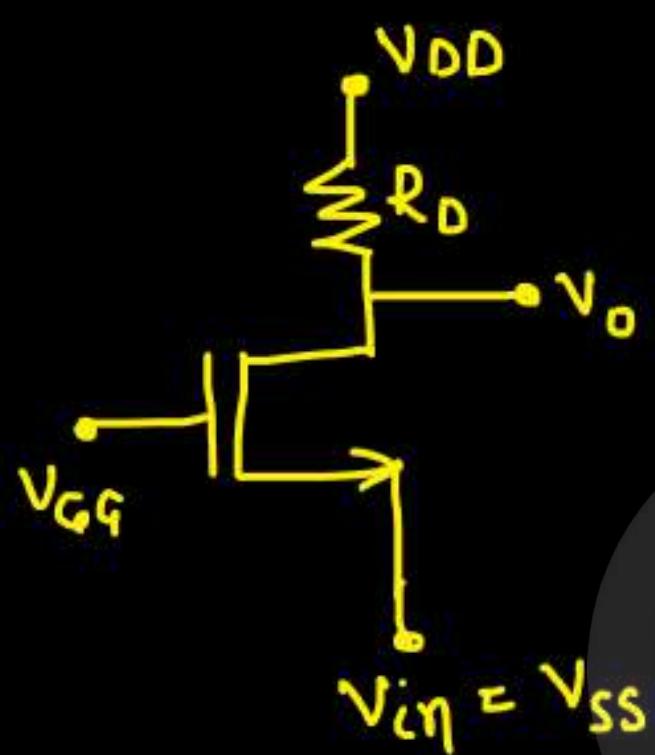

Small signal i/p \rightarrow source
" " o/p \rightarrow drain


PrepFusion

small signal model:-

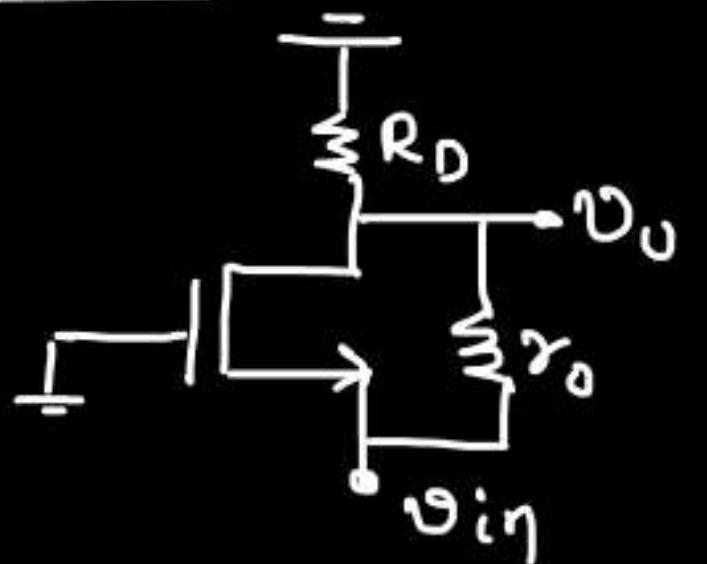

⇒ Voltage gain :-

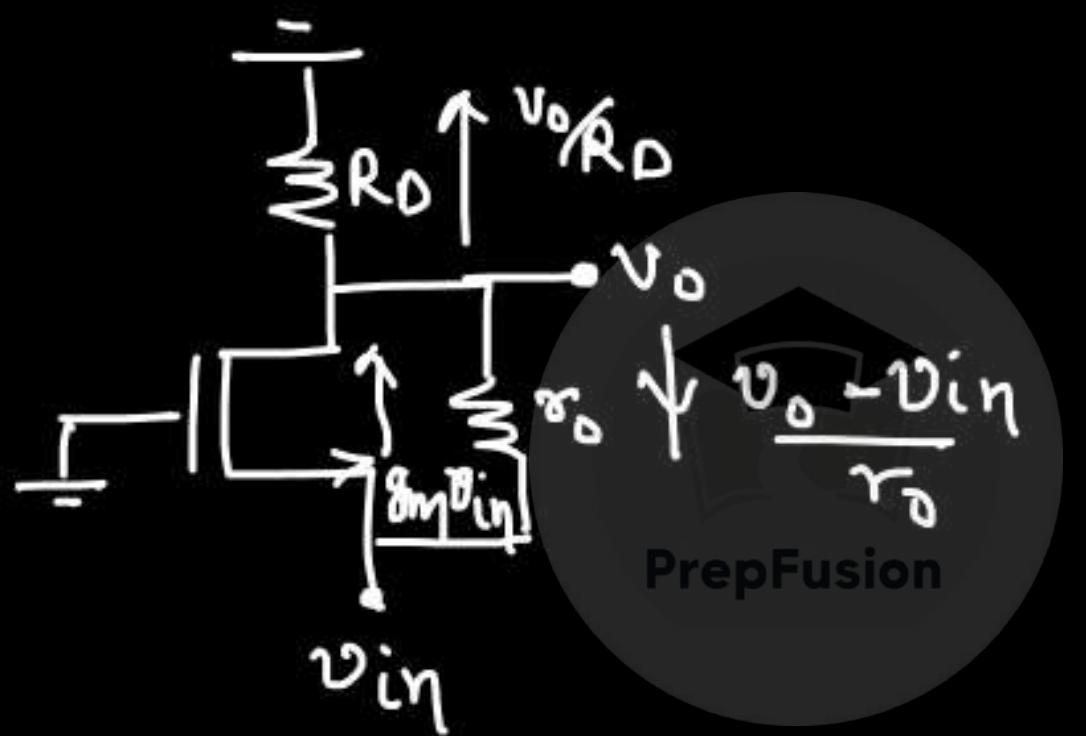$(\lambda \neq 0) \quad r_o = \text{finite}$




$$\delta_m v_{in} = \frac{v_o}{R_D} + \frac{v_o - v_{in}}{r_o}$$

$$v_{in} \left[\delta_m + \frac{1}{r_o} \right] = v_o \left[\frac{1}{R_D} + \frac{1}{r_o} \right]$$

$$v_{in} \left[\frac{\delta_m r_o + 1}{r_o} \right] = v_o \left[\frac{r_o + R_D}{R_D r_o} \right]$$

$$\frac{v_o}{v_{in}} = \frac{R_D [\delta_m r_o + 1]}{r_o + R_D}$$

Voltage gain ($\lambda=0$):-

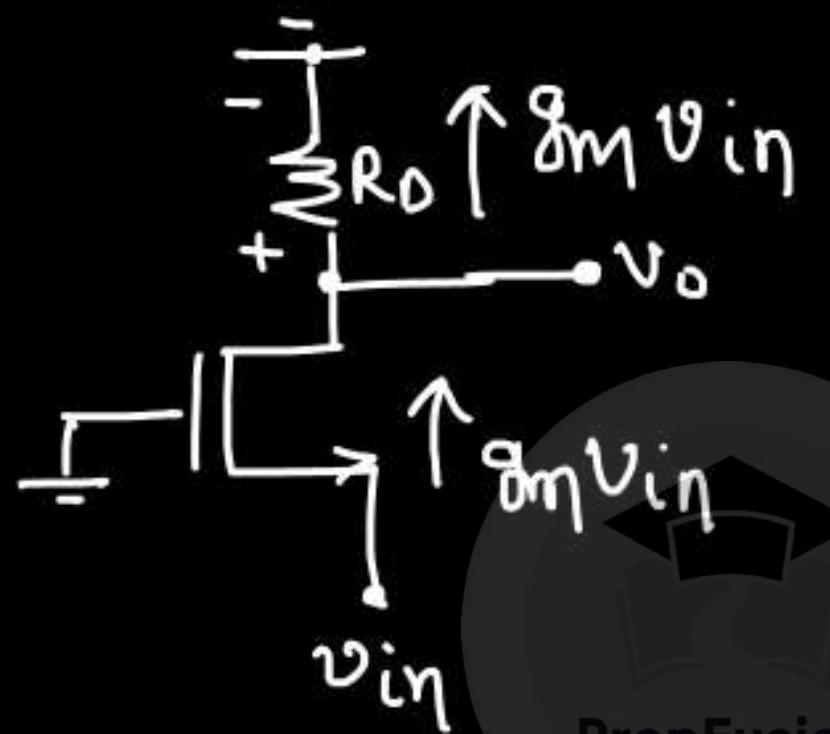


$$V_0 = (g_m V_{in}) R_D$$

$$\frac{V_0}{V_{in}} = g_m R_D \quad \underline{\underline{=}}$$

B/w o/p and i/p there is 0° phase shift.

③ Input Impedance :-

($\lambda \neq 0$)

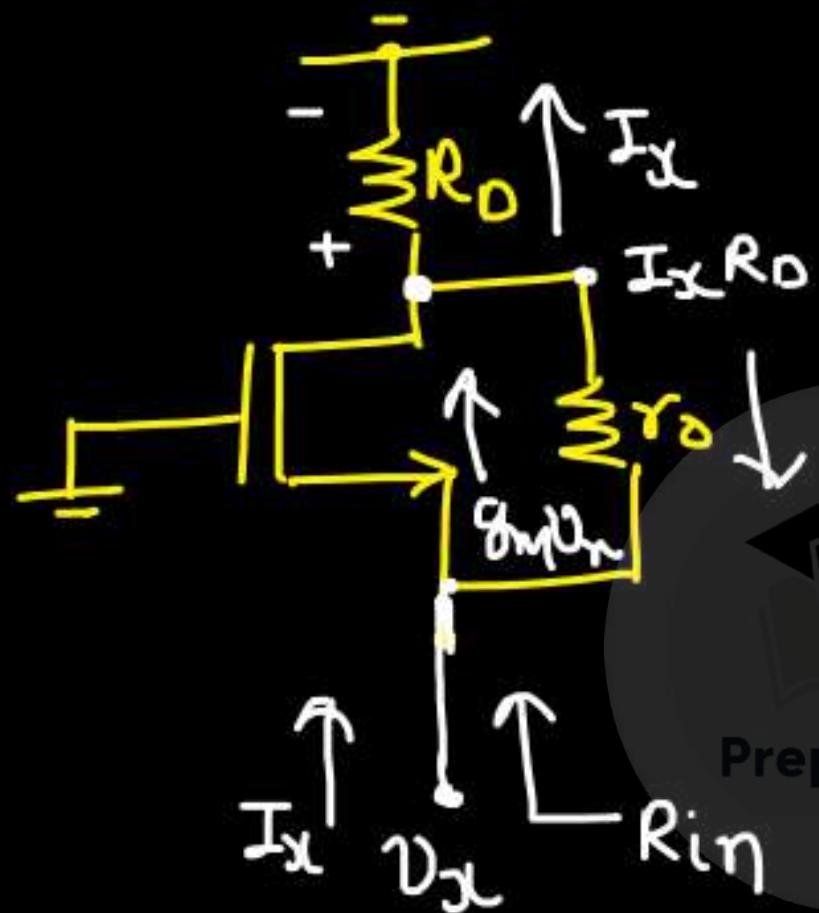

Nodal @ $I_x R_D$:-



$$I_x + \frac{I_x R_D - V_x}{r_o} = g_m V_x$$

$$I_x \left[\frac{r_o + R_D}{r_o} \right] = V_x \left[g_m + \frac{1}{r_o} \right]$$


$$I_x [r_o + R_D] = V_x [g_m r_o + 1]$$

$$R_{in} = \frac{V_x}{I_x} = \frac{r_o + R_D}{1 + g_m r_o}$$

TO REMEMBER :-

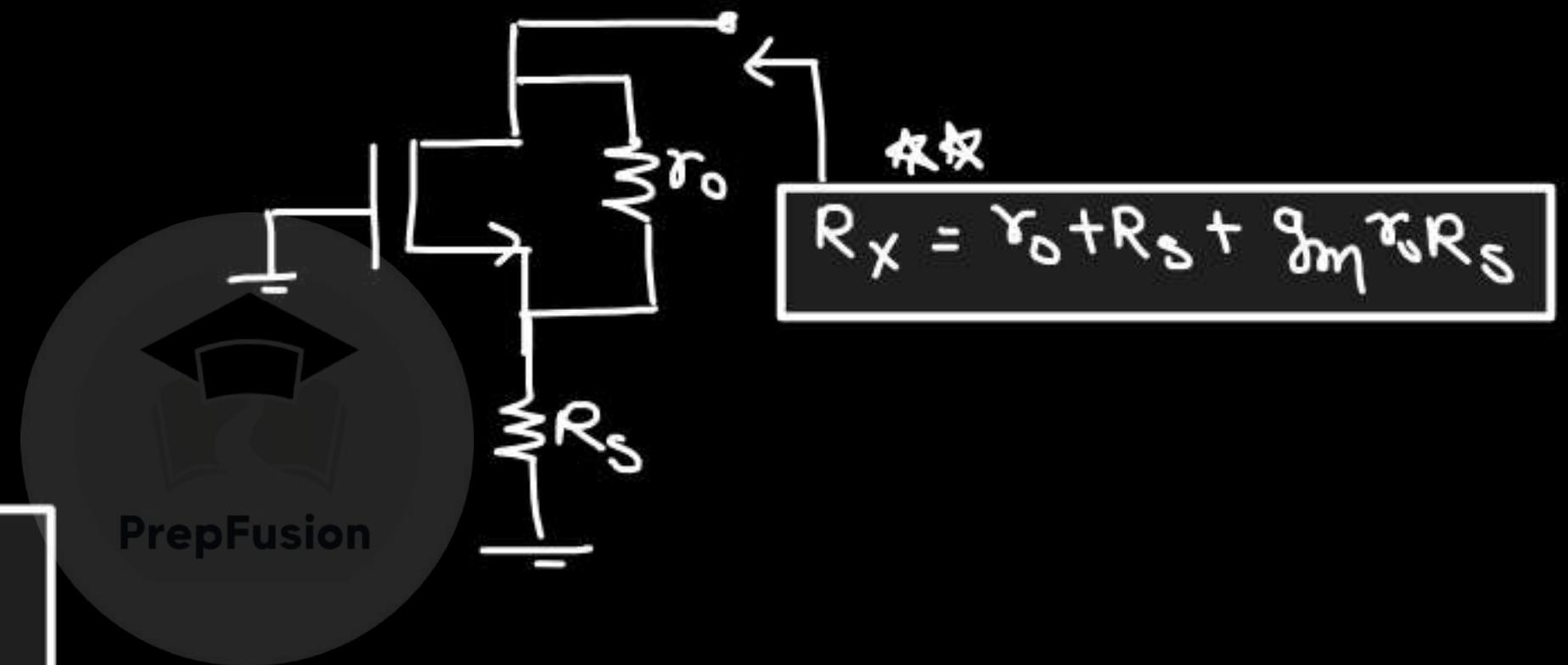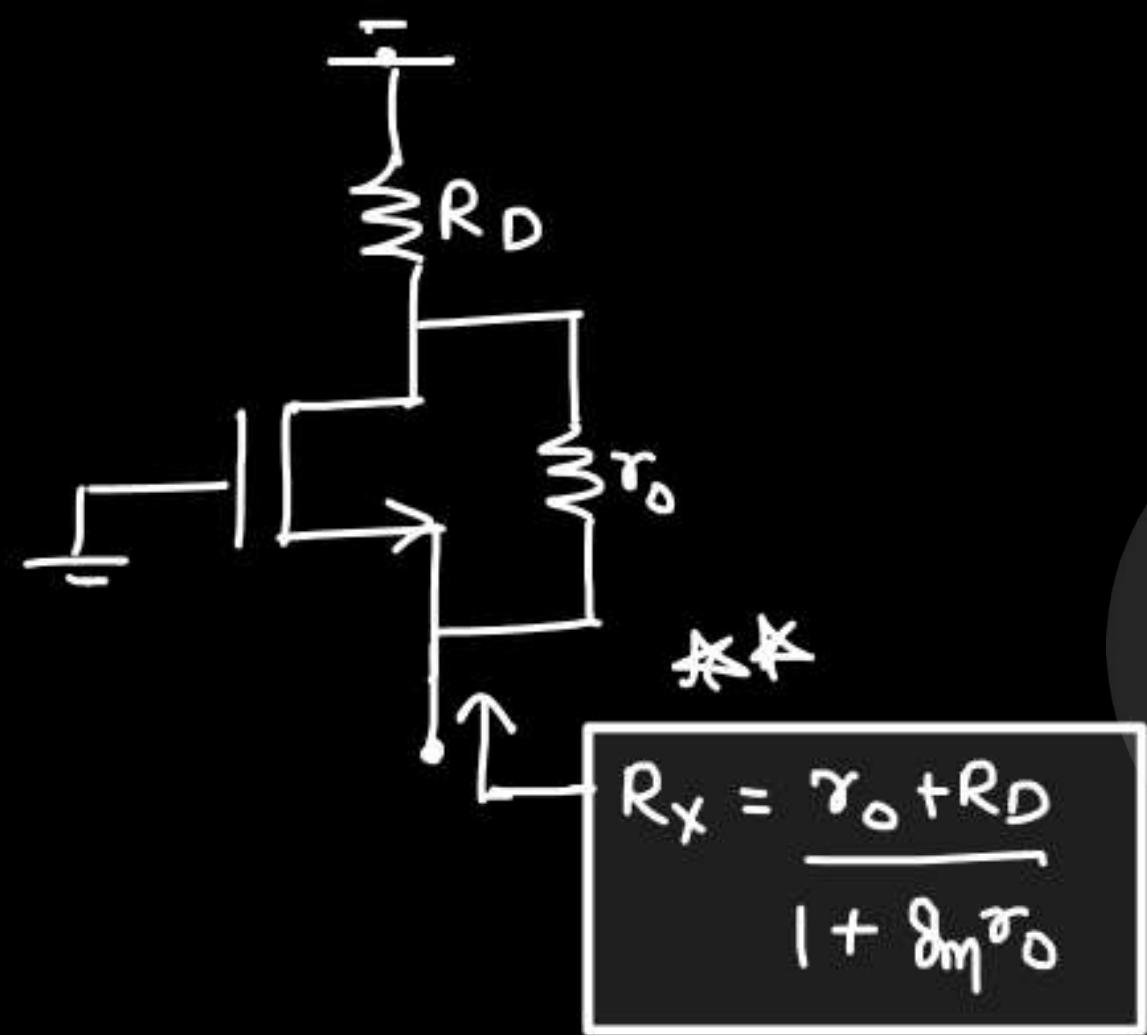

input impedance ($\lambda=0$) :-

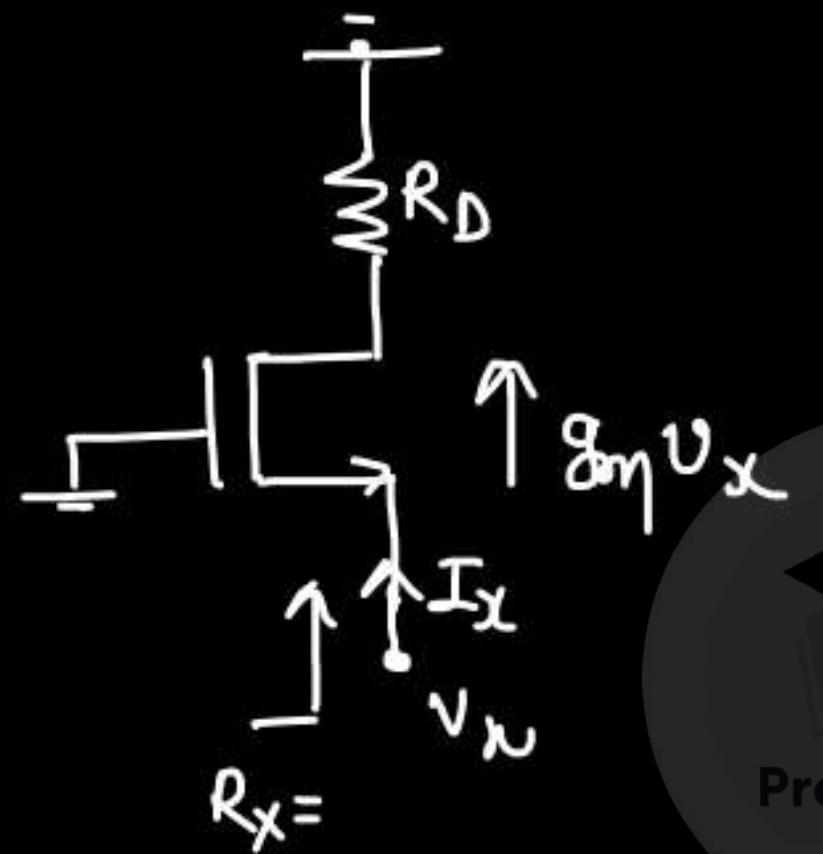



$$g_m v_x = I_x$$

$$R_x = \frac{V_x}{I_x} = \frac{1}{g_m}$$



Output impedance:-

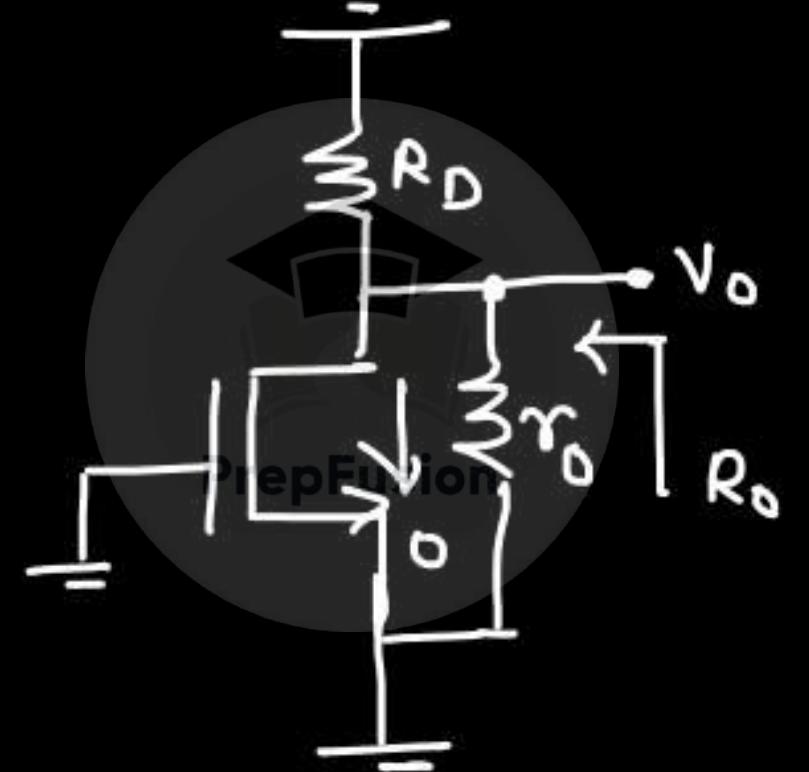
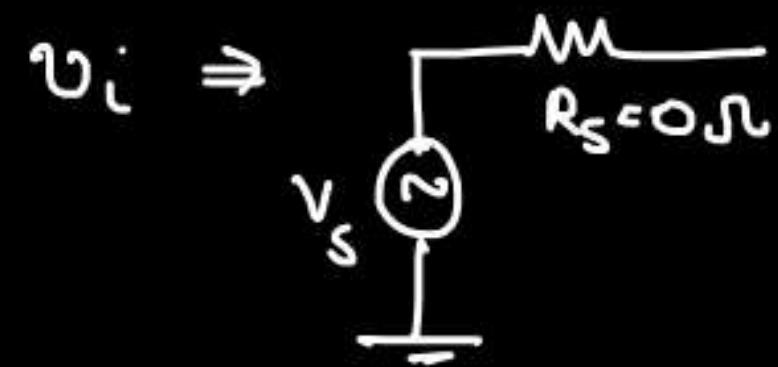
(input source doesn't have any internal resistance)



$$R_o = R_D \parallel r_o$$

Output resistance :-

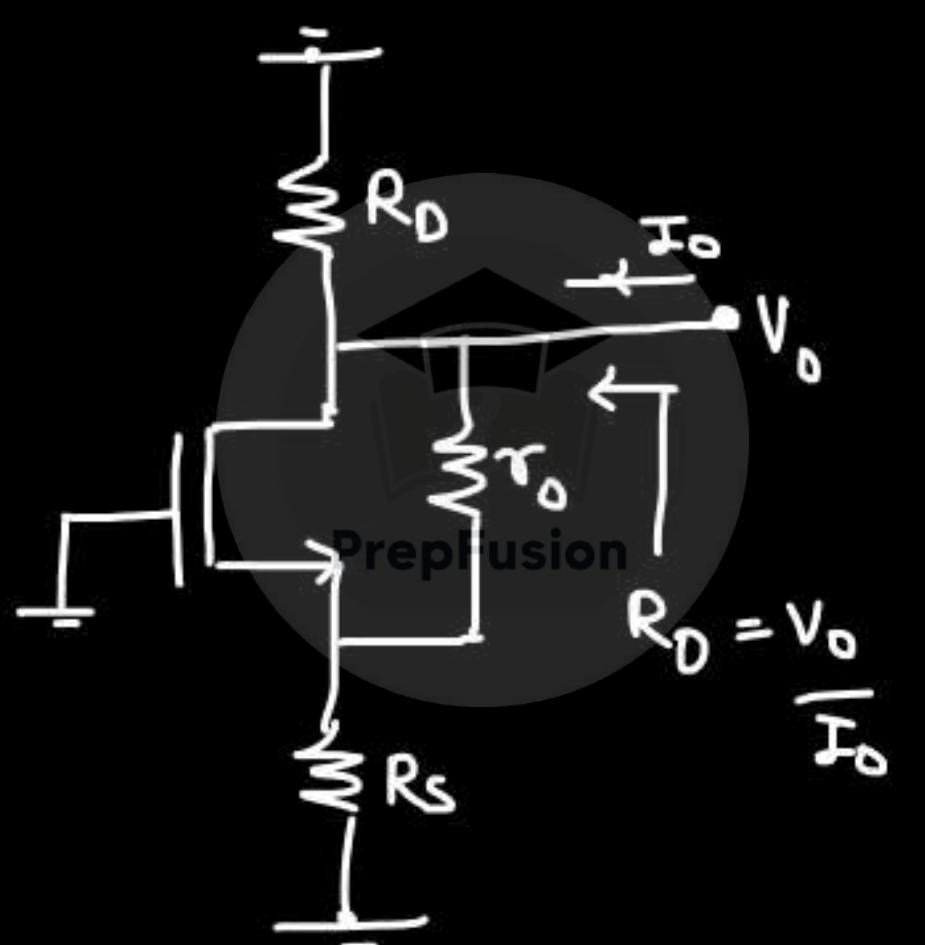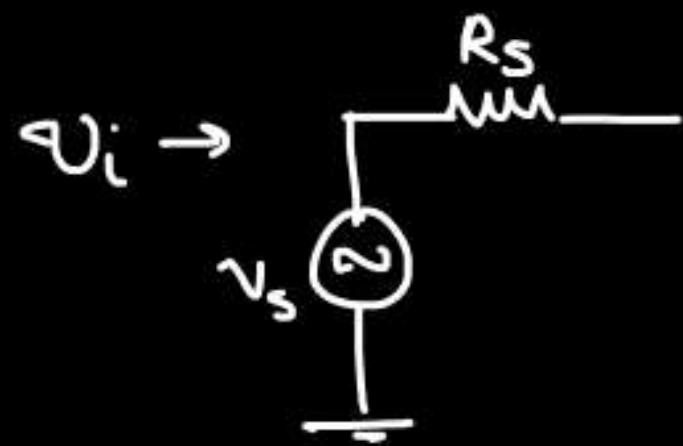
(input source has some internal resistance)



$$R_o = R_D \parallel (r_o + R_s + g_m r_o R_s)$$

$$R_D = \frac{V_o}{I_o}$$

Current - gain :-

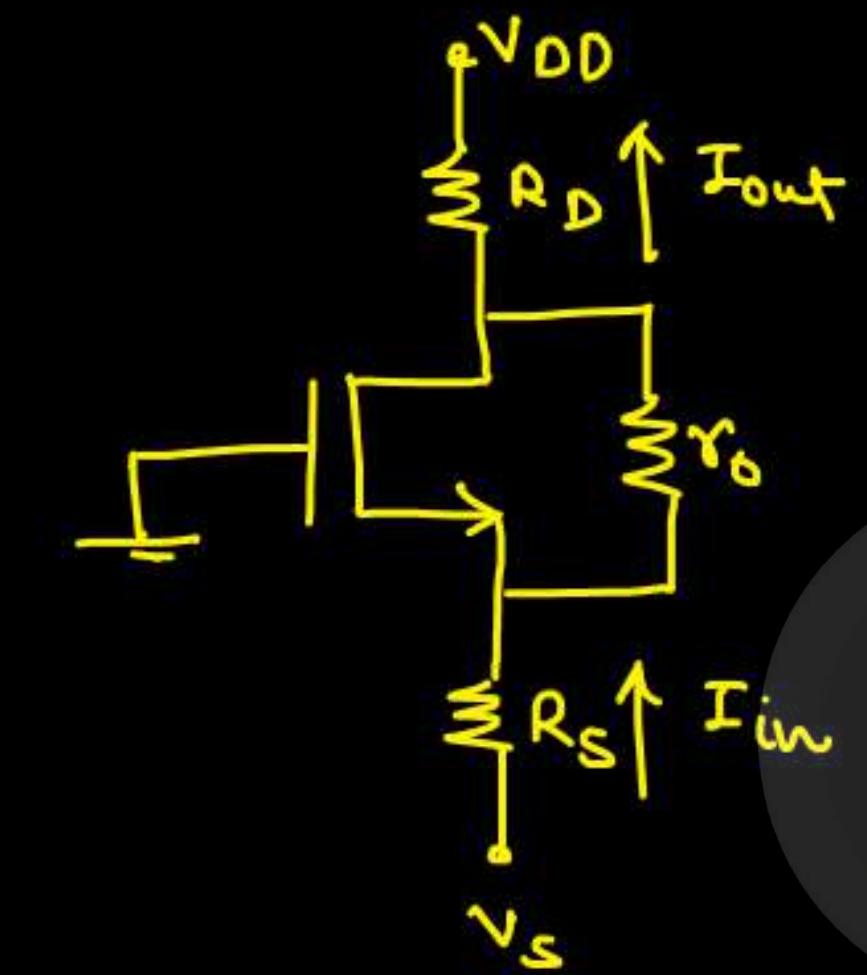

$$I_{in} = I_{out}$$


$$\frac{I_{out}}{I_{in}} = 1$$

⇒ CURRENT
- BUFFER



COMMON GATE AMPLIFIER = C - BUFFER


★ Common - drain amplifier :-

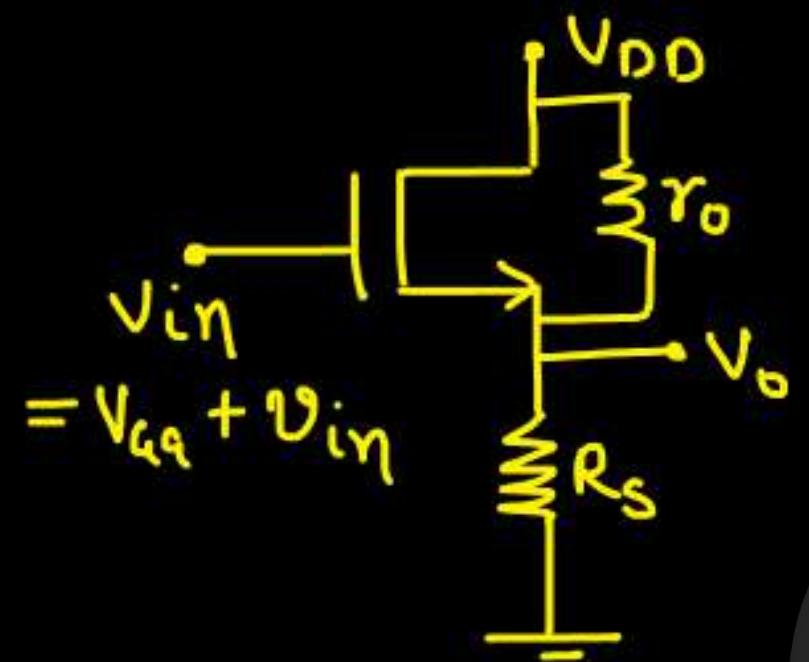

Small signal i/p \rightarrow Gate
" " o/p \rightarrow Source




small signal Model :-

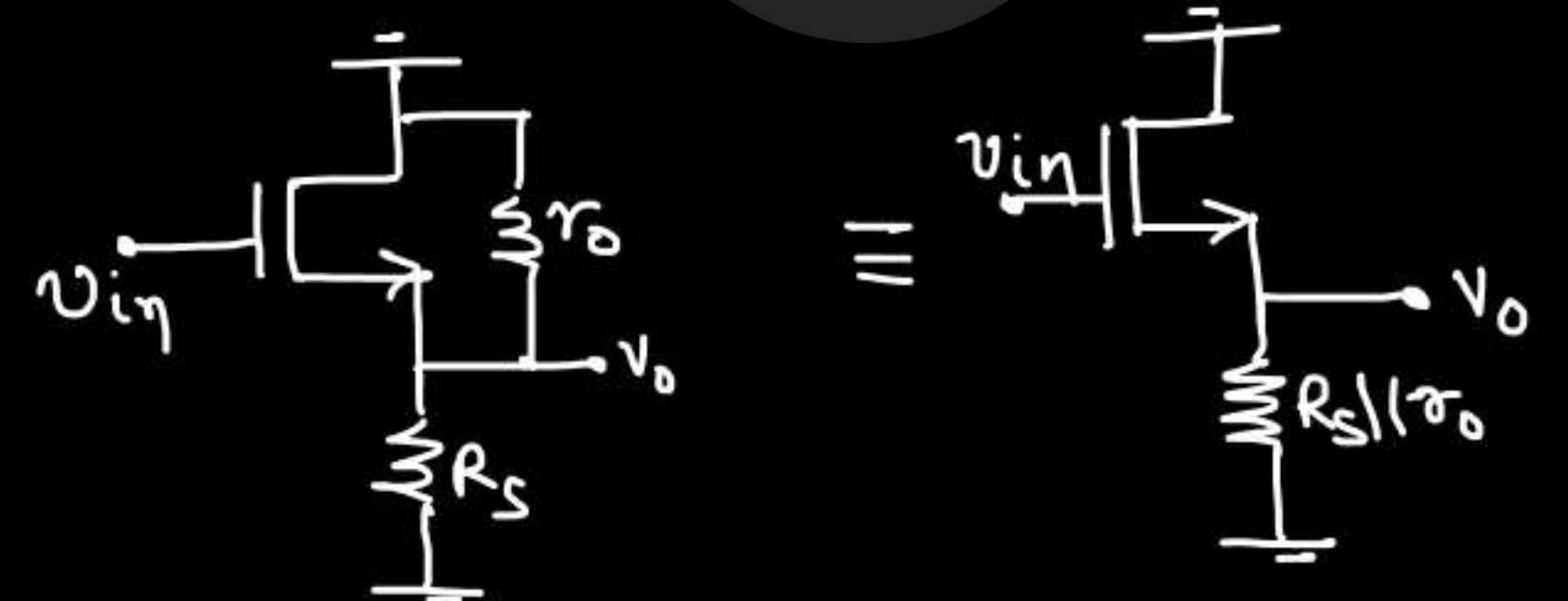

Voltage gain:-

M-I

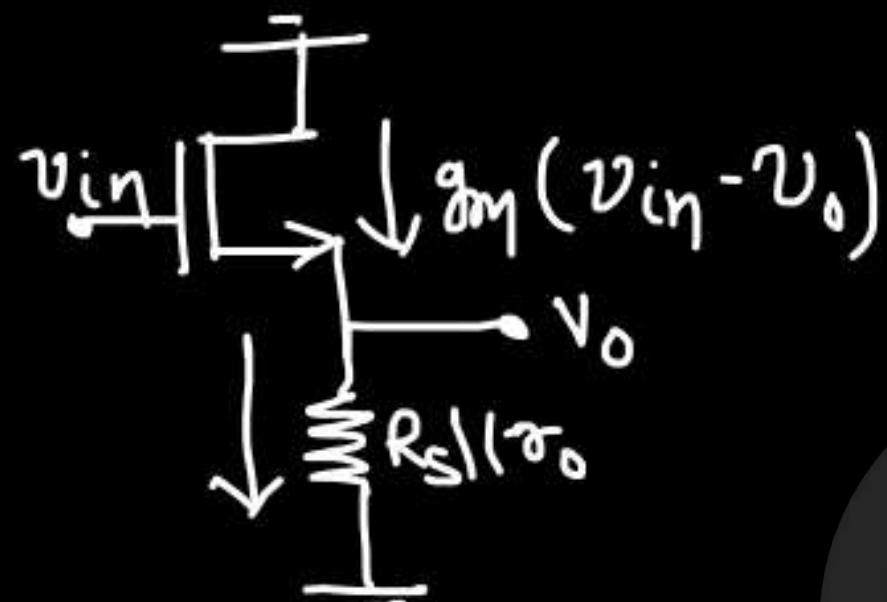

$$g_m(v_{in} - v_o) \times (R_s || r_o) = v_o$$

$$g_m(R_s || r_o) v_{in} = [L + g_m(R_s || r_o)] v_o$$

$$\frac{v_o}{v_{in}} = \frac{g_m(R_s || r_o)}{1 + g_m(R_s || r_o)}$$



★★

common - drain \equiv Source - follower

$$g_m(R_s || r_o) \gg > 1$$

$$\frac{v_o}{v_{in}} = 1 \rightarrow \text{Source-follower} =$$

M - II :-

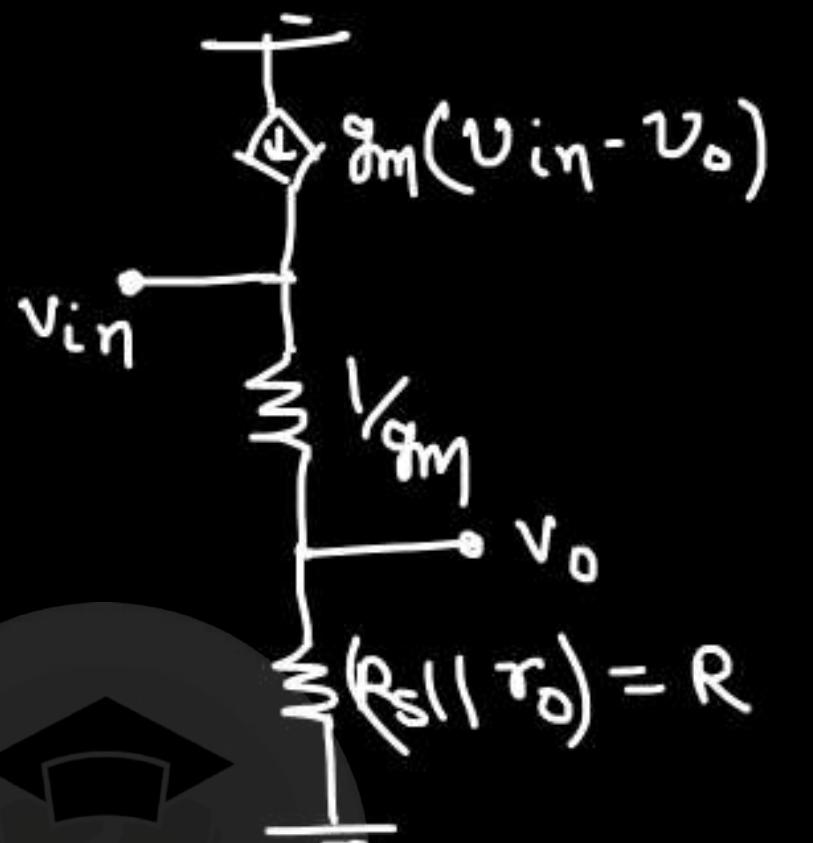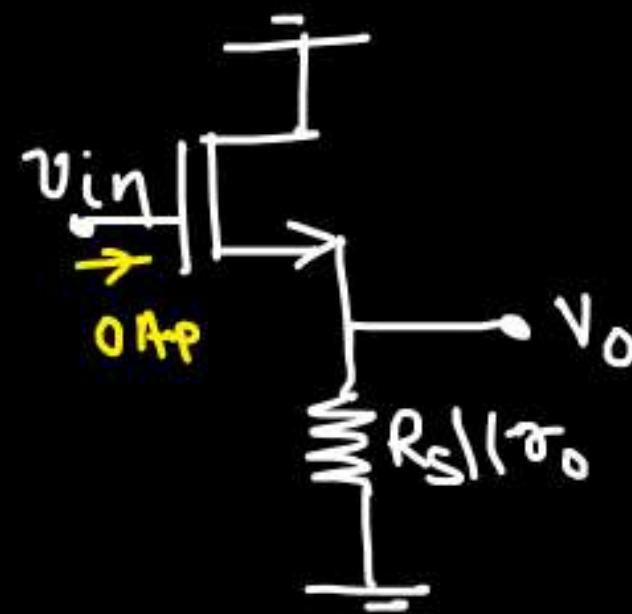

PrepFusion

$$v_o = \frac{R}{R + \frac{1}{g_m}} v_i$$

$$\frac{v_o}{v_i} = \frac{g_m R}{1 + g_m R}$$

$$R = R_S \parallel \tau_0$$


Current gain :-

$$\Delta I = \frac{I_o}{I_{in}} = \frac{I_o}{0} = \infty$$

Input Impedance:-

$$R_i = \frac{V_i}{I_i} = \frac{V_i}{0} = \infty$$

Output Impedance:-

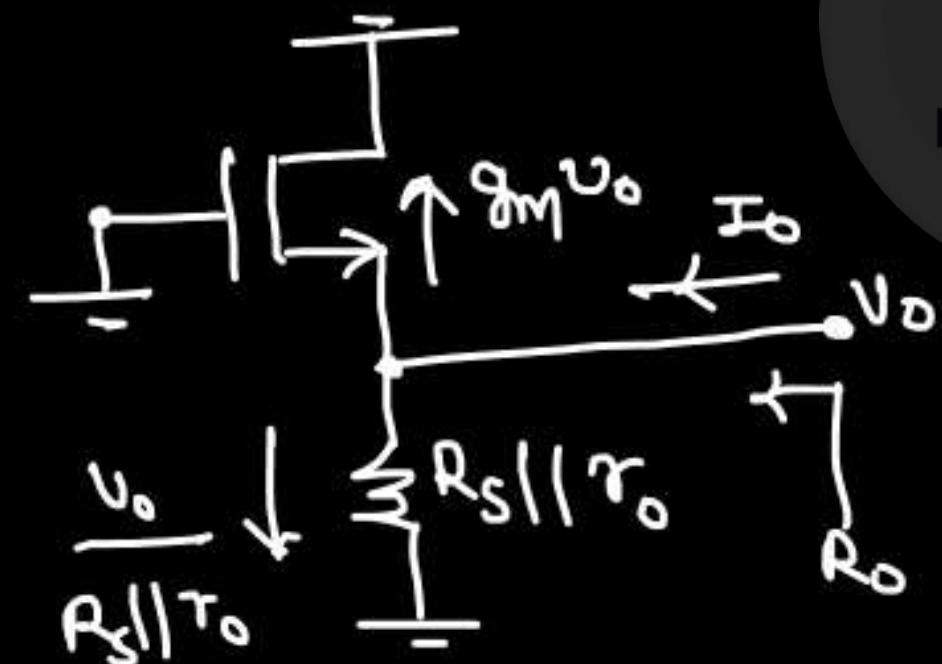


$$R_o = R_s \parallel r_o \parallel \frac{1}{g_m}$$

$$g_m V_o + \frac{V_o}{R_s \parallel r_o} = I_o$$

* Summary:-

① Common Source Amplifier:-

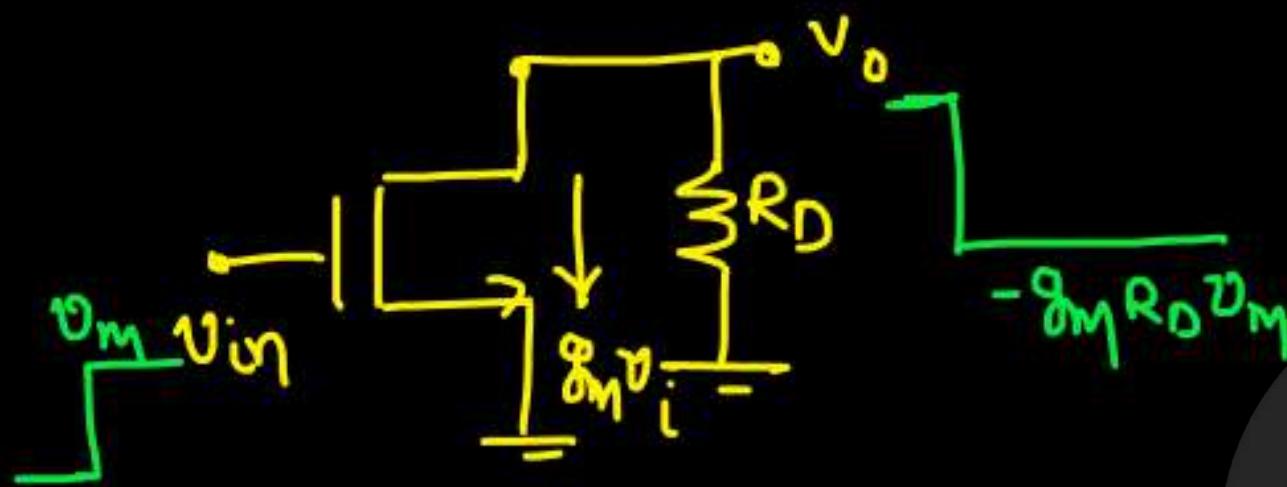


$$A_V = -g_m R_D$$

⇒ There is 180° phase shift
b/w i/p and o/p

$$R_o = R_D // r_o$$

② Common GATE amplifier:-

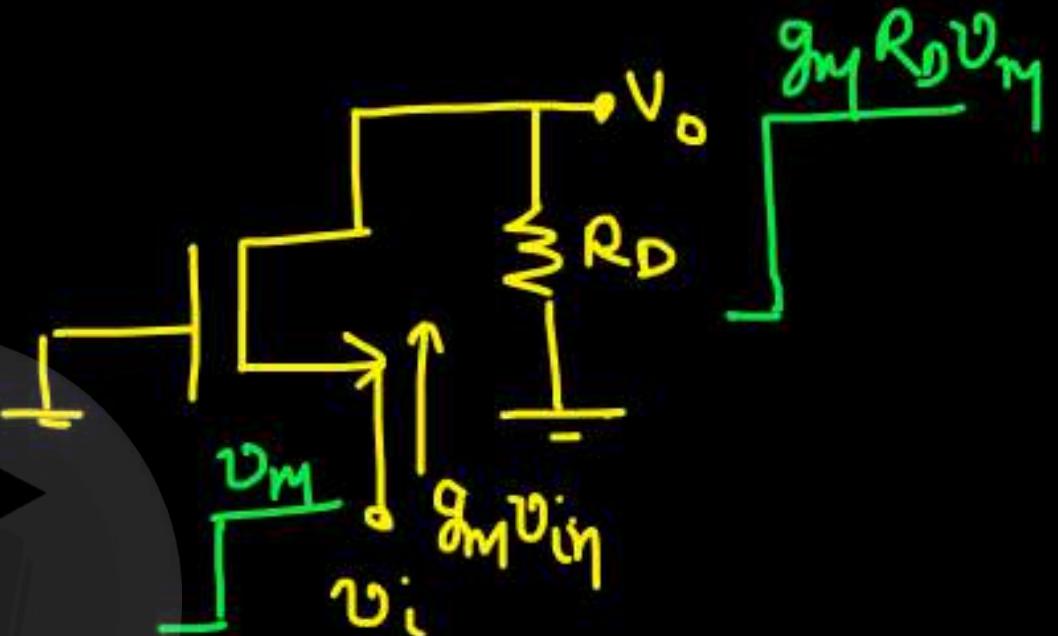

$$A_V = g_m R_D$$


PreFusion

⇒ B/w i/p and o/p there is zero degree phase shift

$$R_o = R_D // r_o$$

$$A_I = 1 \Rightarrow C-Buffer$$

③ Common - Drain Amplifier:-

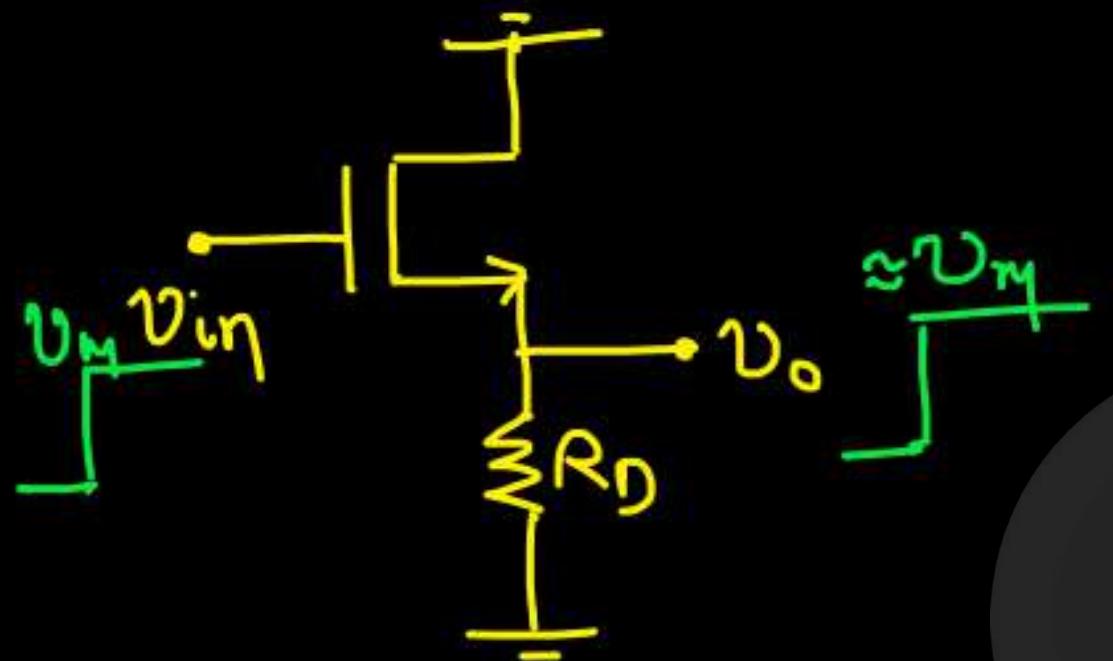


$$\Delta V = \frac{g_m R_D}{1 + g_m R_D} \approx 1$$

⇒ SOURCE - follower

⇒ There is zero degree phase shift b/w ip and op

$$R_o = R_D \parallel r_o \parallel \frac{1}{g_m}$$

Q.

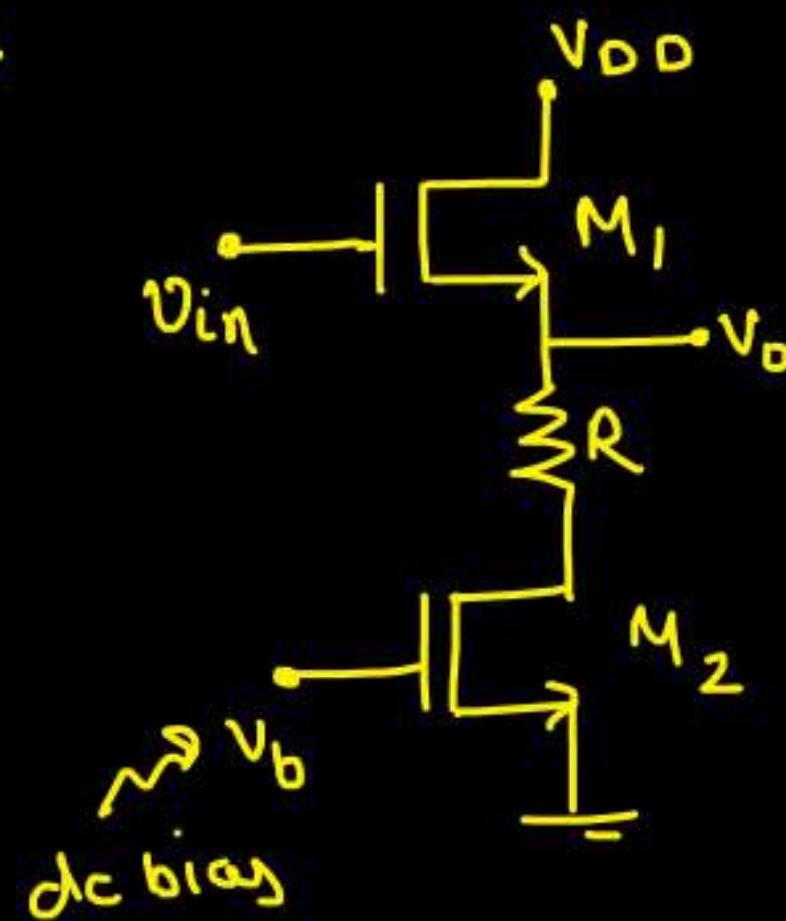

dc bias

$$g_{m_1} = 1.92 \text{ mS}$$

$$g_{m_2} = 1.8 \text{ mS}$$


$$r_{ds1} = 20.63 \text{ k}\Omega = r_{o1}$$



$$r_{ds2} = 23.89 \text{ k}\Omega = r_{o2}$$

$$R = 4.6 \text{ k}\Omega$$

PrepFusion

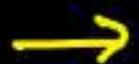Find small signal voltage gain $\frac{V_o}{V_{in}}$.



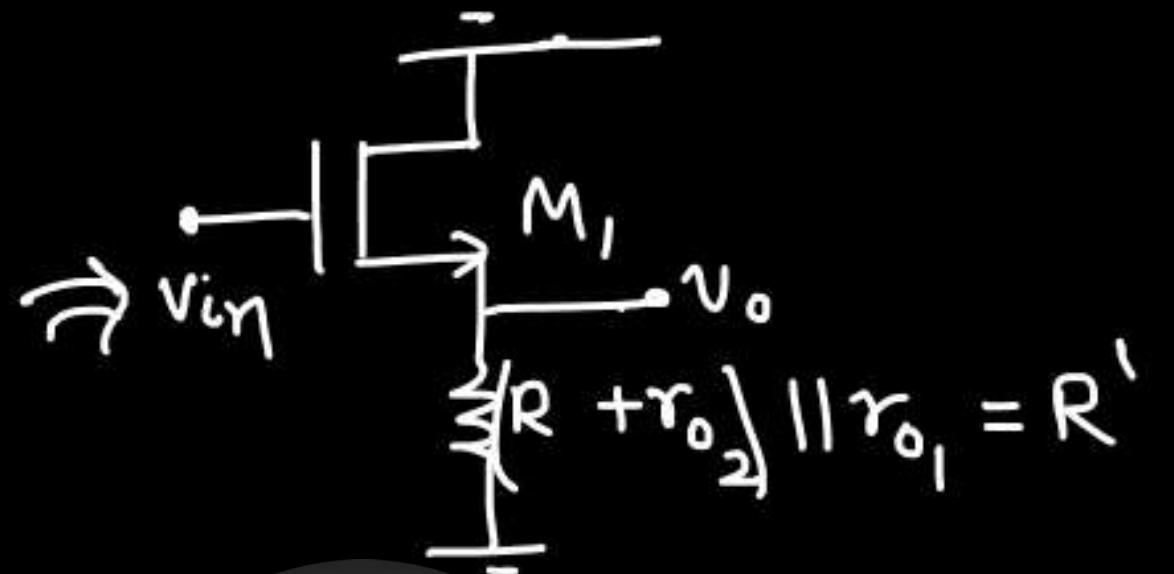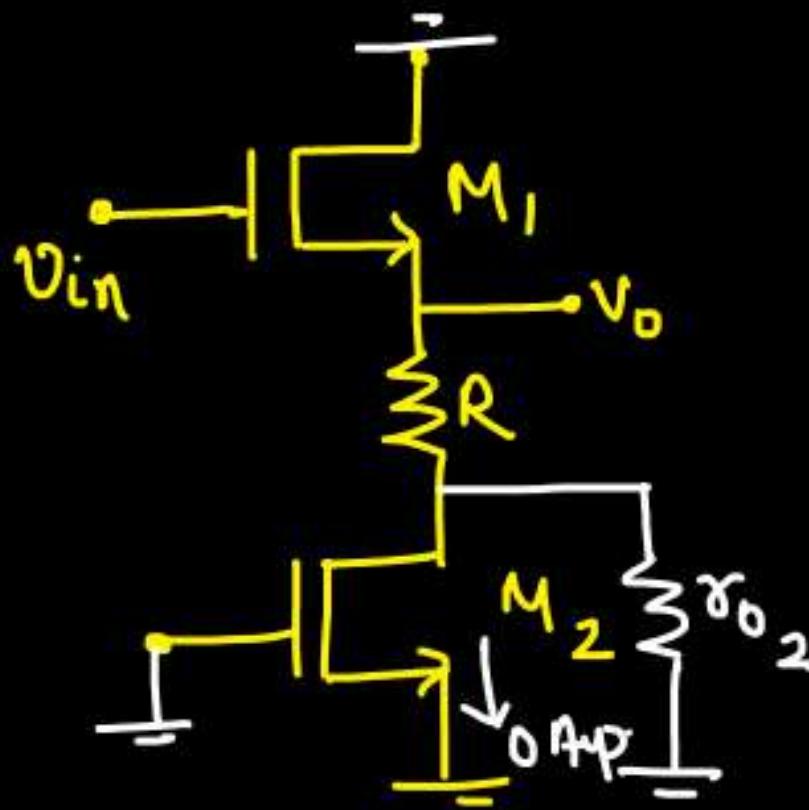

$$\frac{V_0}{V_{in}} = \frac{R'}{R' + \frac{1}{g_m 1}} = \frac{g_m R'}{1 + g_m R'}$$


PrepFusion

$$R' = 28.49 \text{ k}\Omega \parallel 20.63 \text{ k}\Omega = 11.96 \text{ k}\Omega$$

$$g_m R' = 1.92 \text{ m} \times 11.96 \text{ k} = 22.97$$

$$\frac{V_0}{V_{in}} = \frac{22.97}{23.97} \approx 0.96$$

Q.

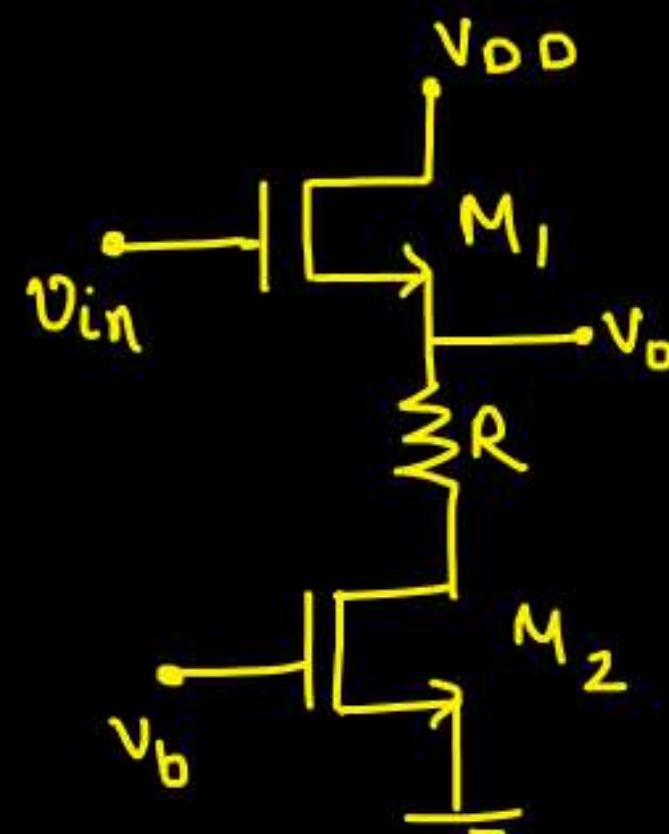

$$g_{m_1} = 1.92 \text{ mS}$$

$$g_{m_2} = 1.8 \text{ mS}$$



$$r_{ds1} = 20.63 \text{ k}\Omega$$

$$r_{ds2} = \infty$$

$$R = 4.6 \text{ k}\Omega$$

PrepFusion

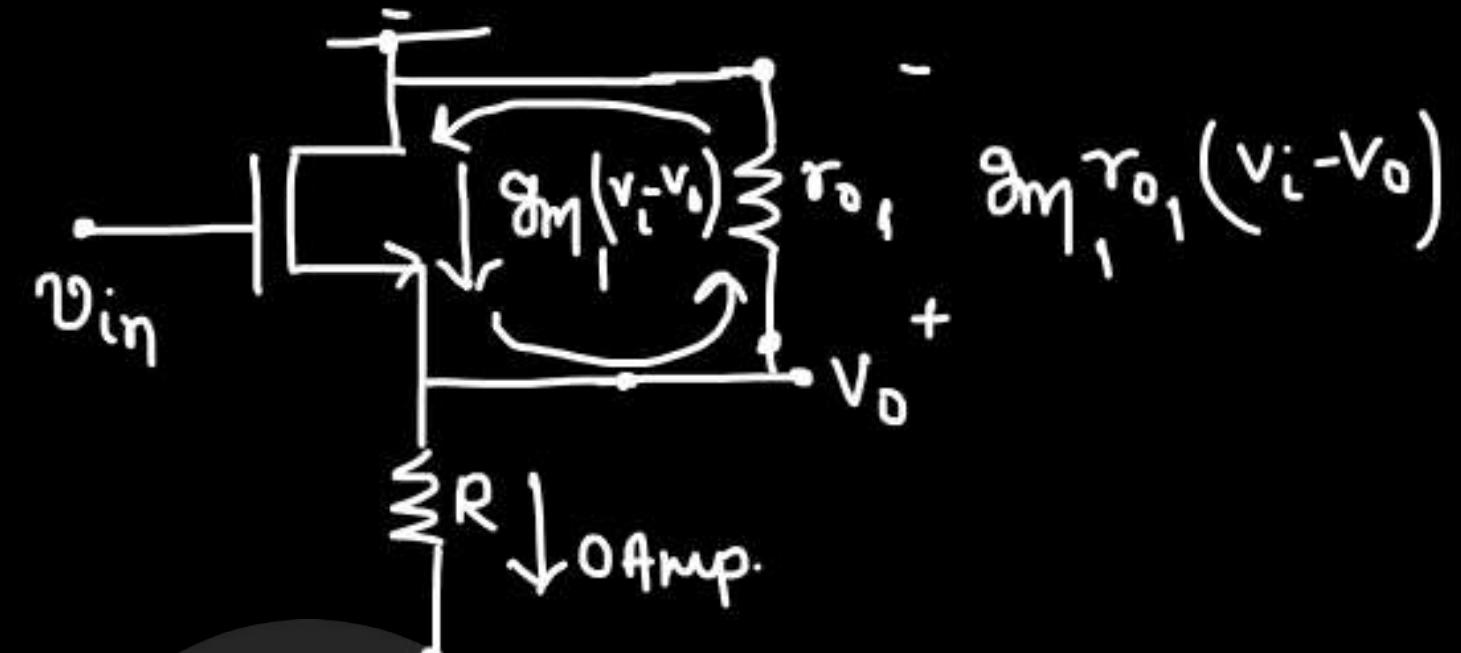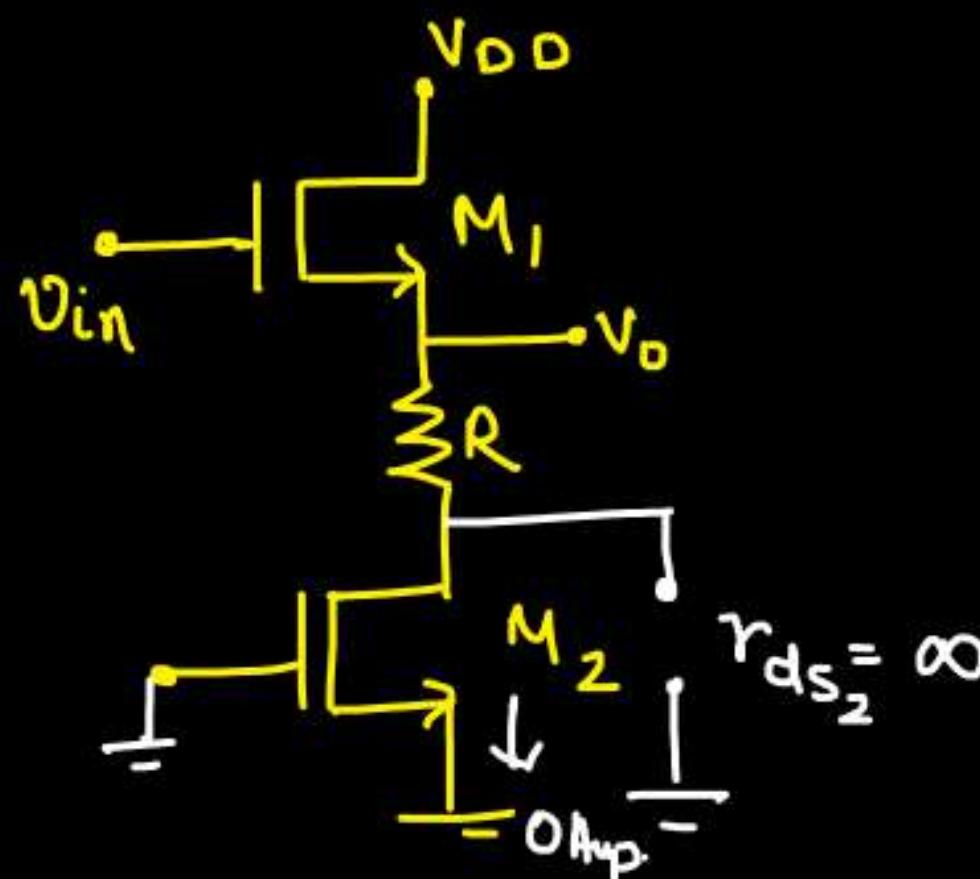small signal voltage gain $\frac{V_o}{V_{in}} = ?$



$$g_{m_1} r_{o_1} (V_i - V_o) = V_o$$


$$g_{m_1} r_{o_1} V_i = (1 + g_{m_1} r_{o_1}) V_o$$

$$\frac{V_o}{V_i} = \frac{39.6096}{40.6096} = 0.975$$

$$\frac{V_o}{V_i} = \frac{g_{m_1} r_{o_1}}{1 + g_{m_1} r_{o_1}}$$



Q.

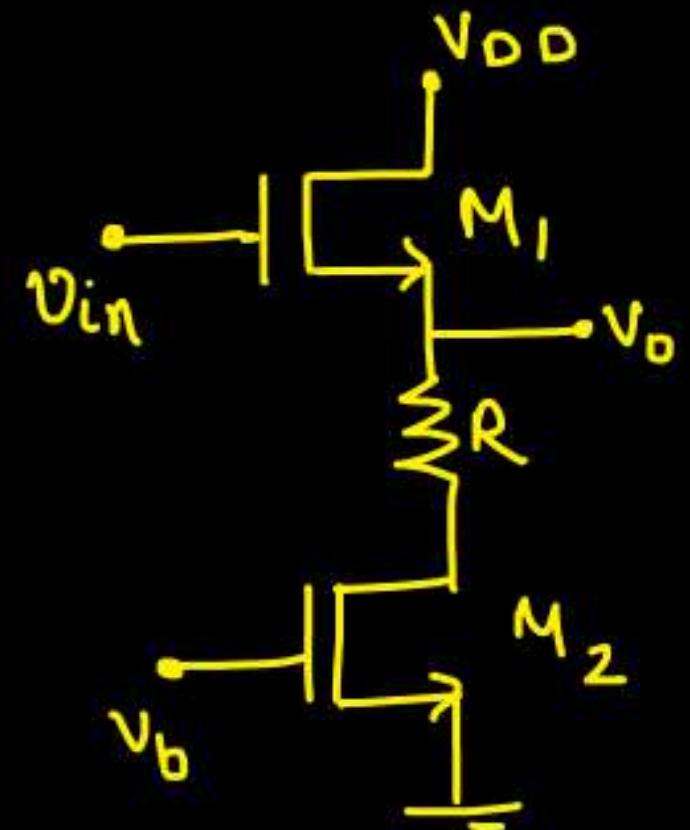

$$g_{m_1} = 1.52 \text{ mS}$$



$$g_{m_2} = 1.8 \text{ mS}$$

$$r_{ds1} = \infty$$

$$r_{ds2} = \infty$$

$$R = 4.6 \text{ k}\Omega$$

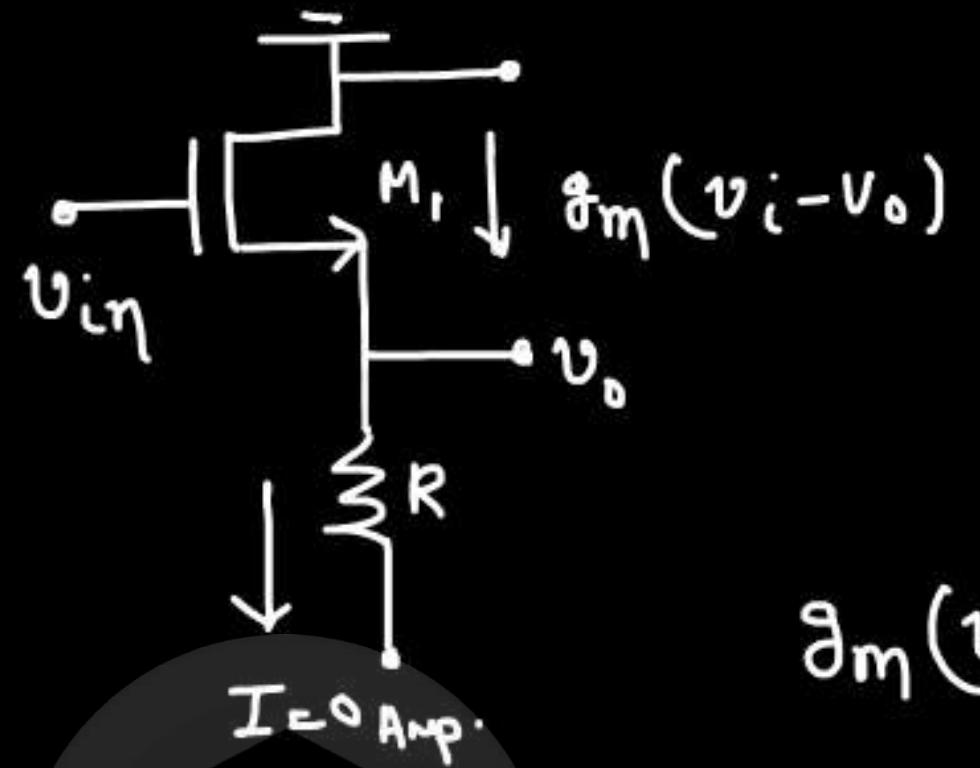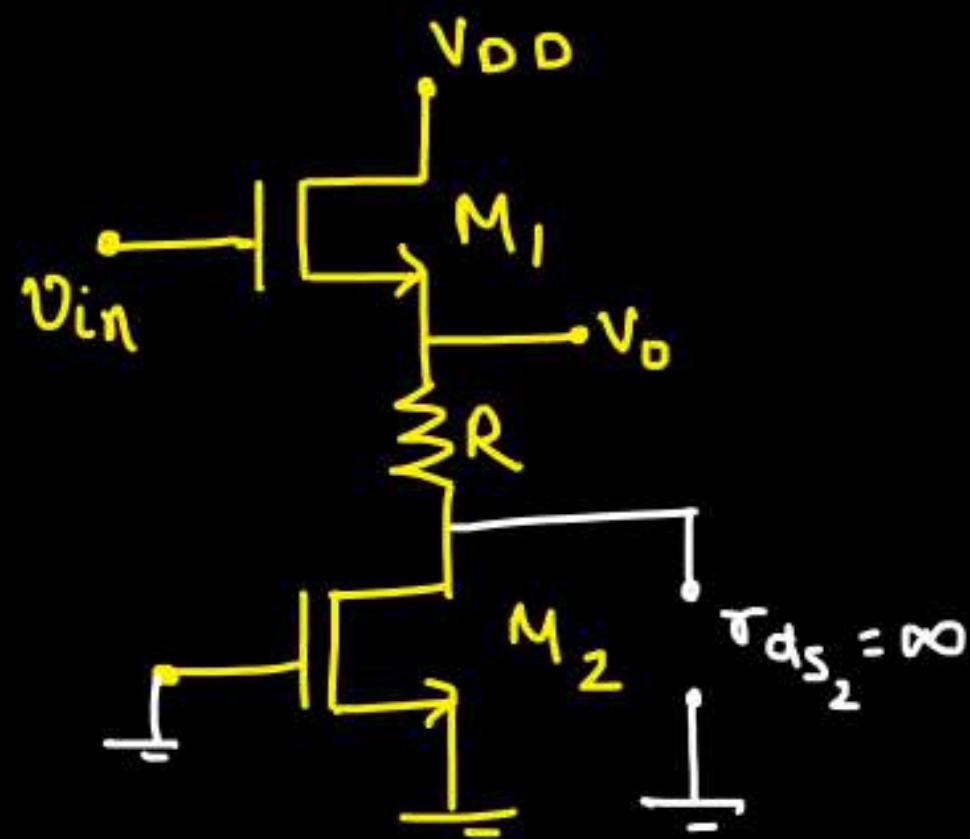small signal voltage gain $\frac{V_o}{V_{in}} = ?$



$$g_m(v_i - v_o) = 0$$

$$v_i = v_o$$

$$\frac{v_o}{v_i} = 1$$

PrepFusion

* Interesting Method of finding voltage gain :. ($G_m R_{out}$ Method)

- * Small signal voltage gain of any configuration




$$G_m \neq g_m$$

$$\Delta V = \frac{V_o}{V_s} = G_m R_{out}$$


① $G_m \rightarrow$

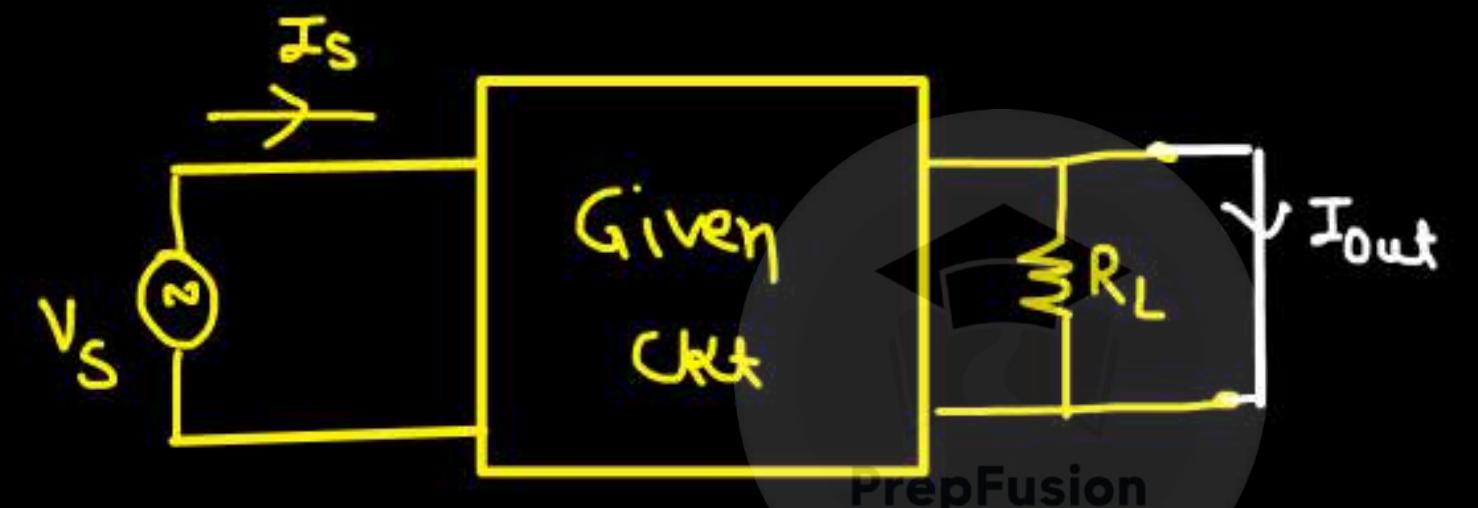Short ckt the o/p and find out the relation
b/w I_{out} and V_s .




$$G_m = \frac{I_{out}}{V_s}$$

② find small signal out resistance:-

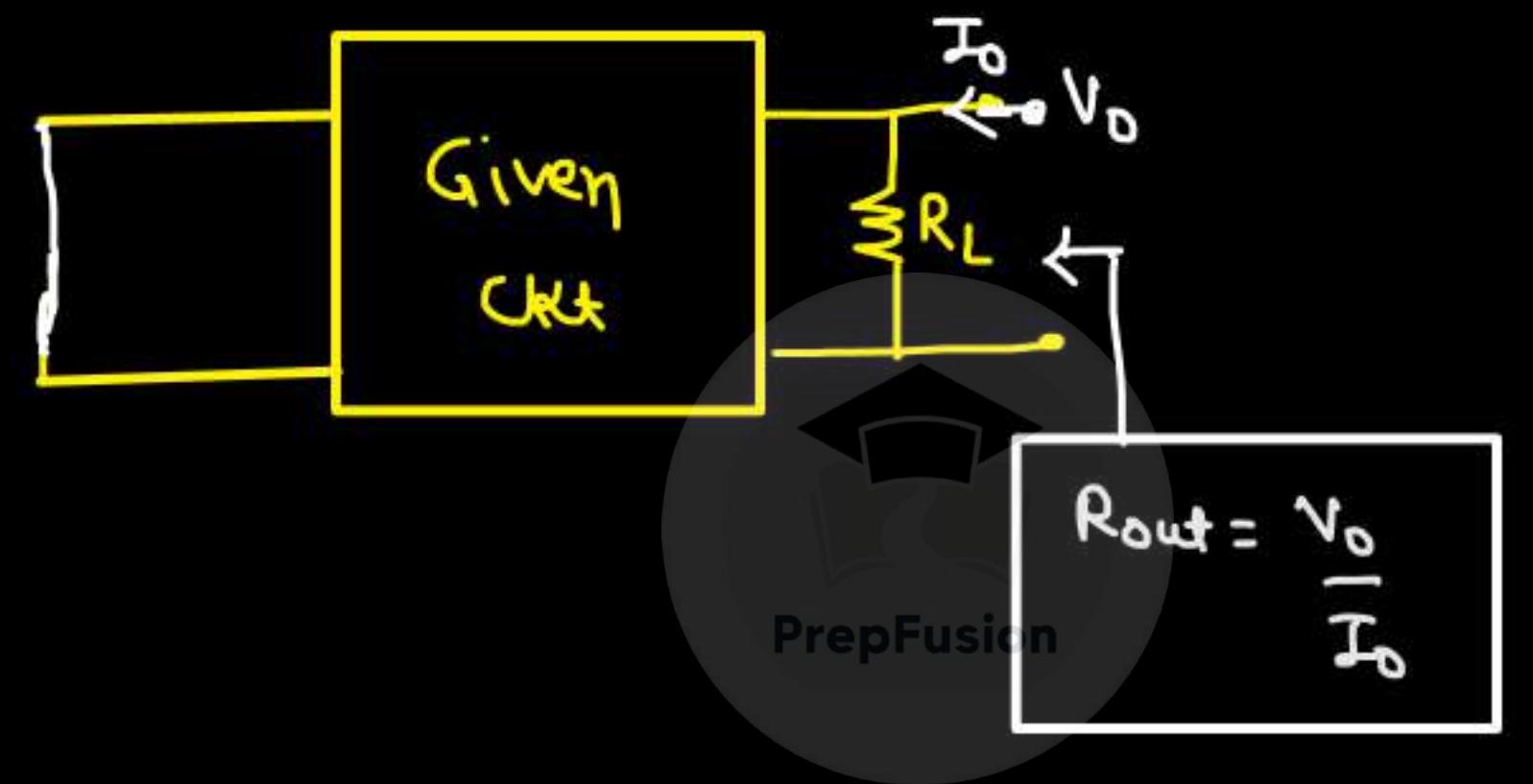


Eg → Find small signal gain.


①

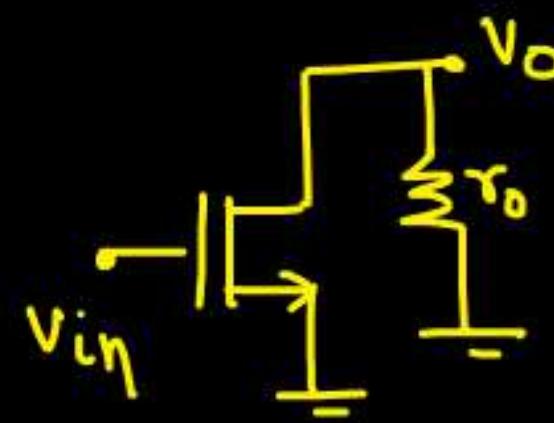

① $G_m \rightarrow$

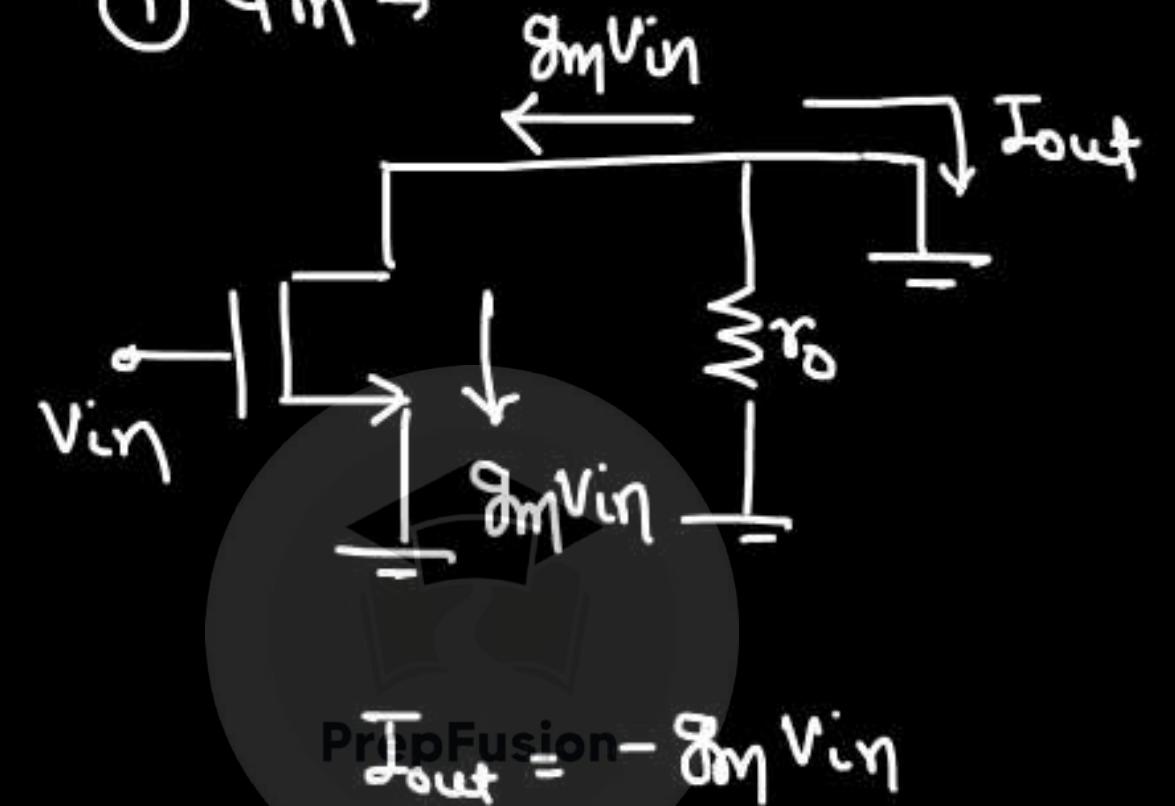


② $R_{out} \rightarrow$

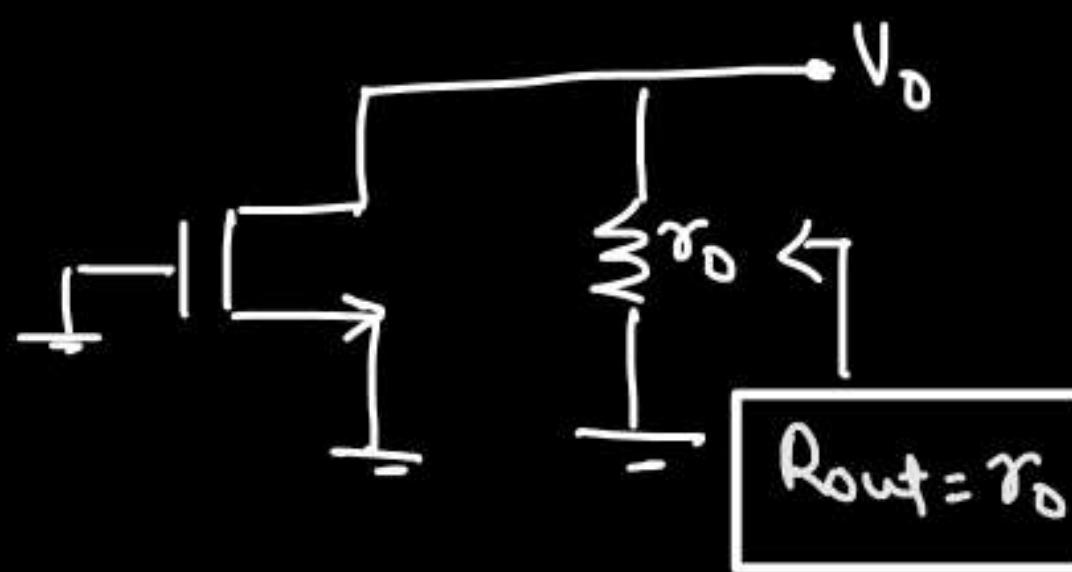


$$G_m = \frac{I_{out}}{V_{in}} = -g_m$$

$$\text{Gain} = -g_m r_o$$

②

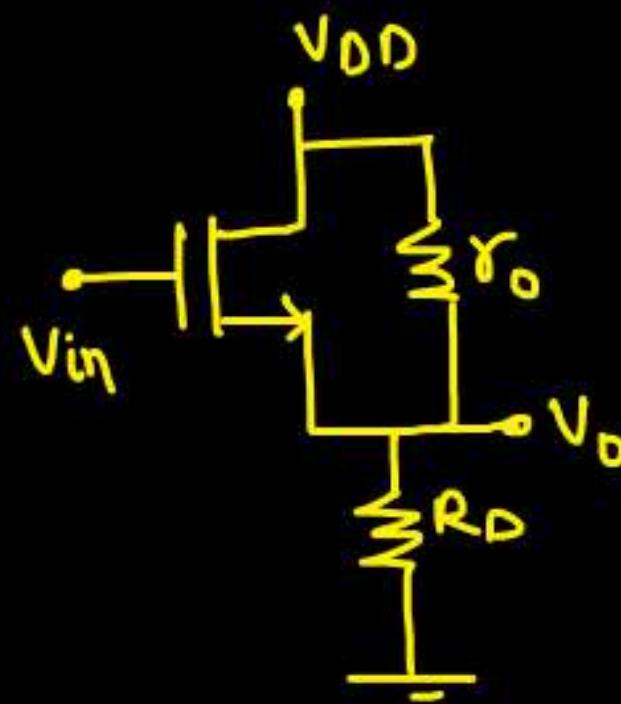

→ ① $g_m \rightarrow$

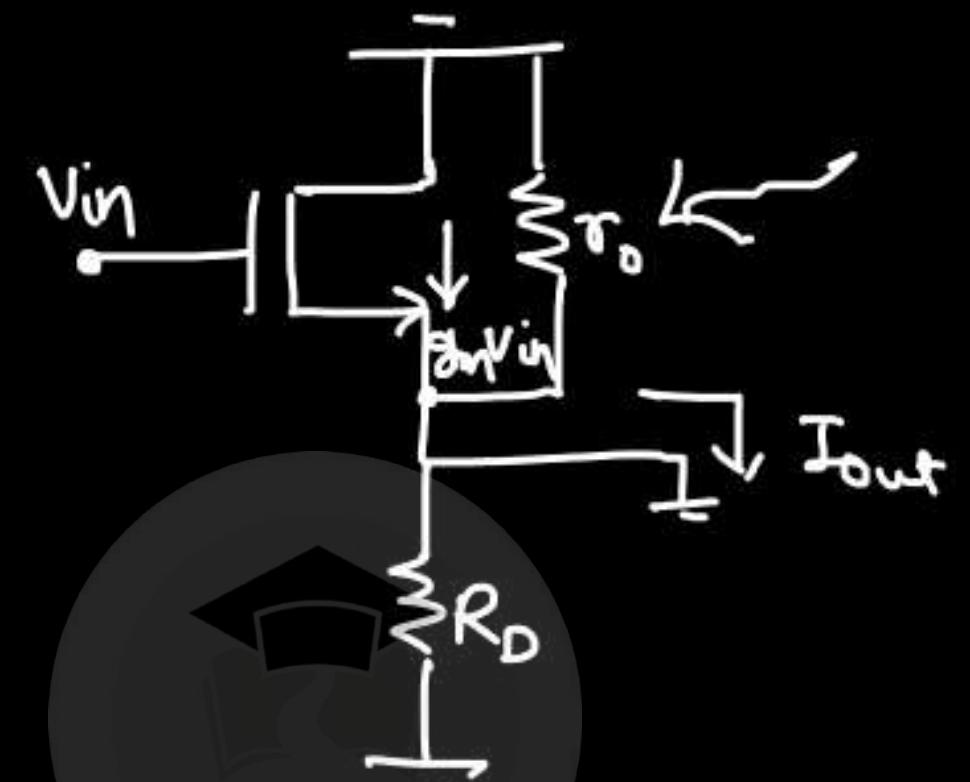


PrepFusion

$$\Rightarrow I_{out} = g_m V_{in}$$

$$g_m = g_m$$


②

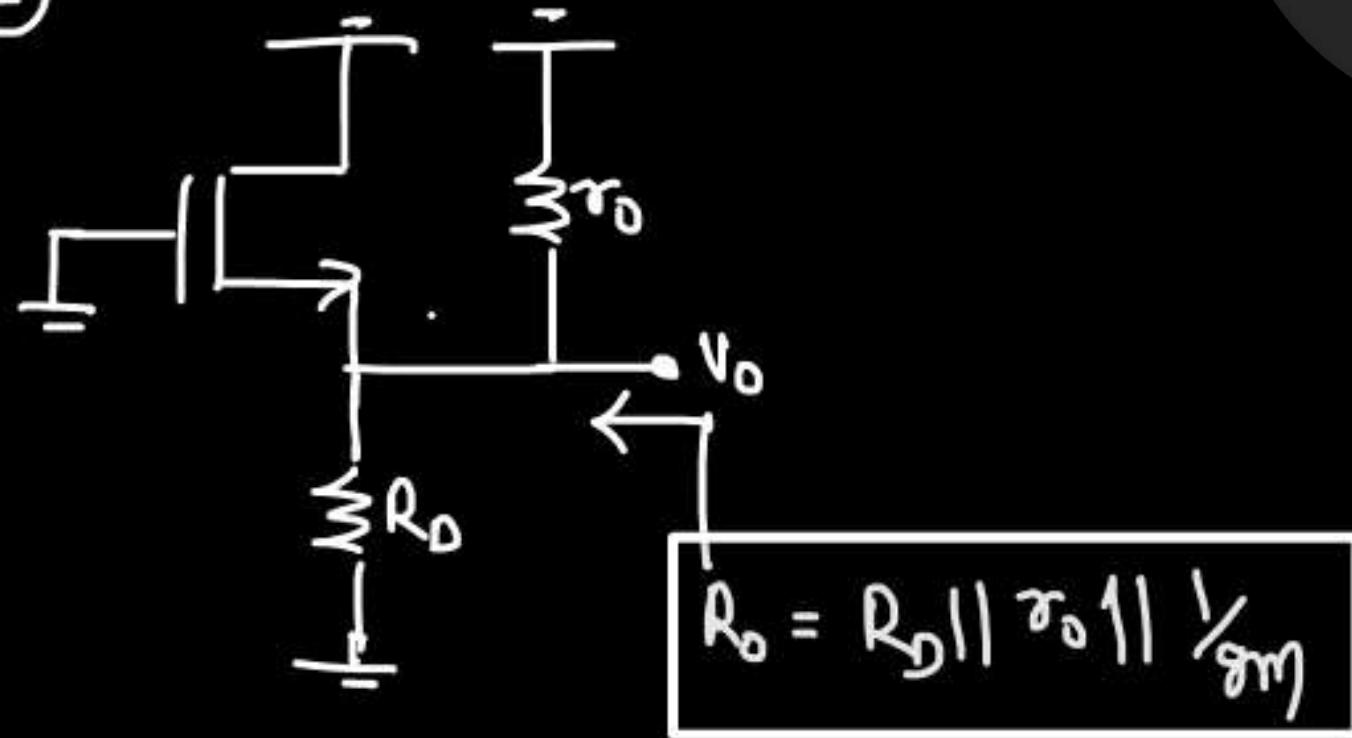


$$R_o = R_D || r_0 || \frac{1}{g_m}$$

$$\Rightarrow A_V = g_m [R_D || r_0 || \frac{1}{g_m}]$$



③

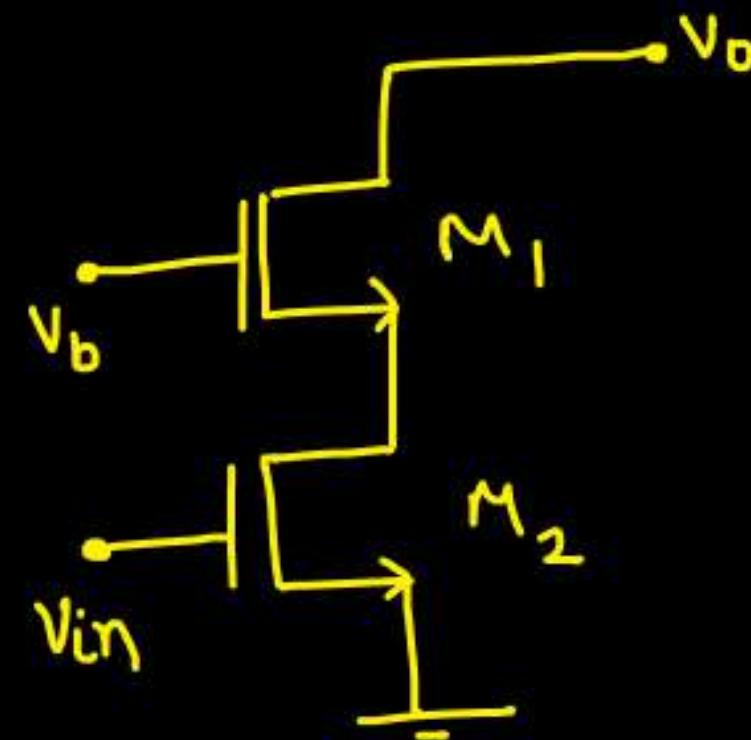

τ_{o1} and τ_{o2} are very high

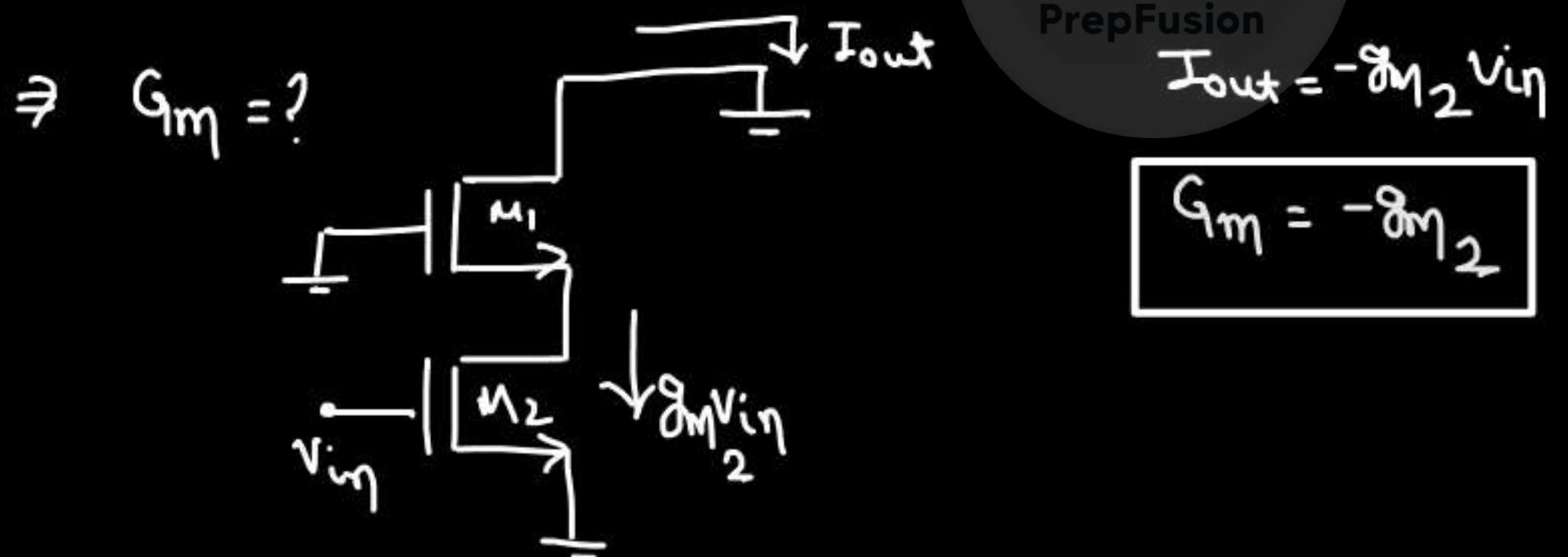

R_{out}

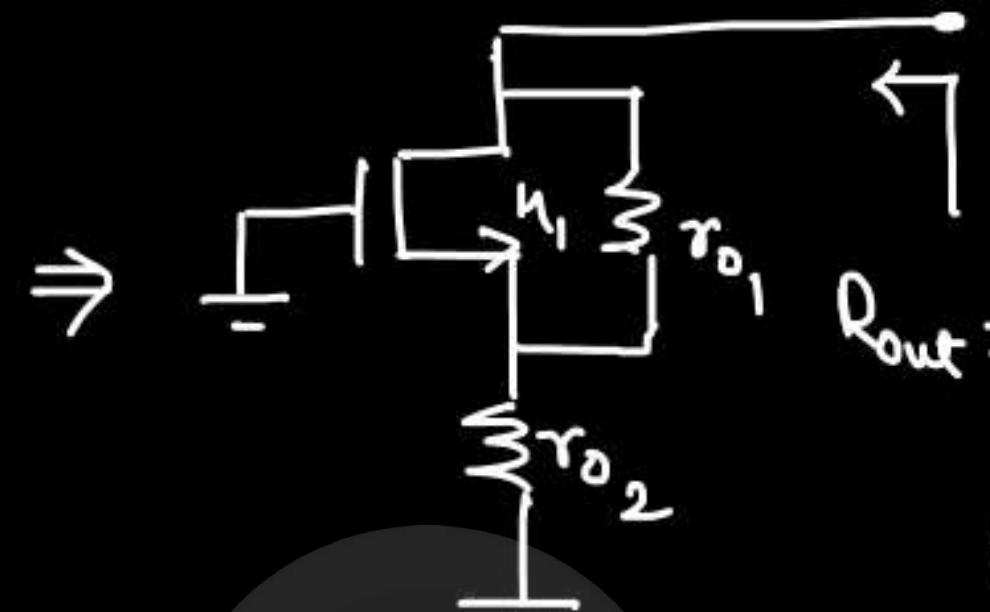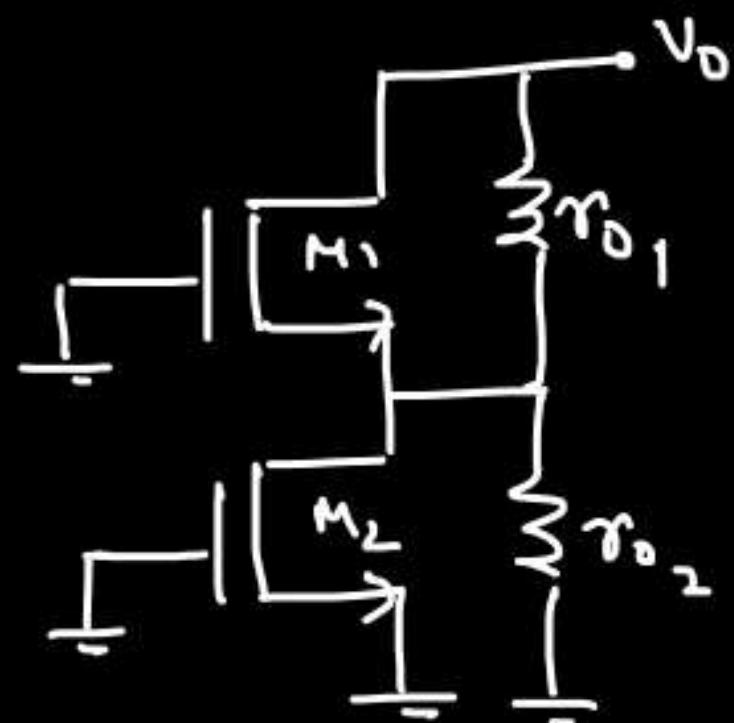

$$R_{out} = r_{o_1} + r_{o_2} + g_m r_{o_1} r_{o_2}$$


$$\approx g_m r_{o_1} r_{o_2}$$

PrepFusion

$$\Rightarrow \text{Gain} \approx -g_{m_2} [r_{o_1} + r_{o_2} + g_m r_{o_1} r_{o_2}]$$

$$\text{Gain} \approx -g_{m_2} g_{m_1} r_{o_1} r_{o_2}$$

Q.

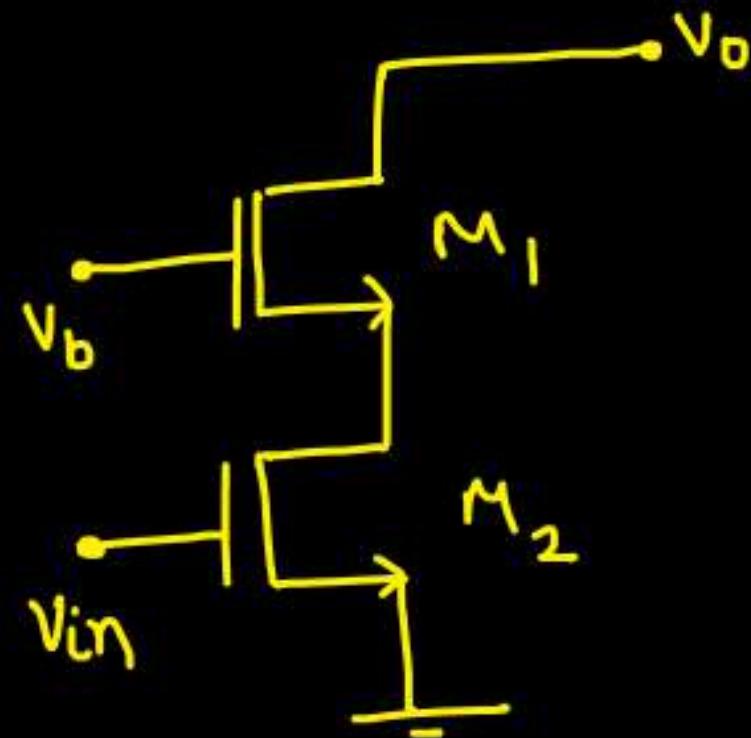

let's assume,

$$\frac{1}{g_m_1} = r_{o_1} = r_{o_2} = 2 \text{ k}\Omega$$


$$g_m_2 = 3 \text{ mS}$$

Find $\frac{V_o}{V_{in}} = ?$

NOTE-

PrepFusion

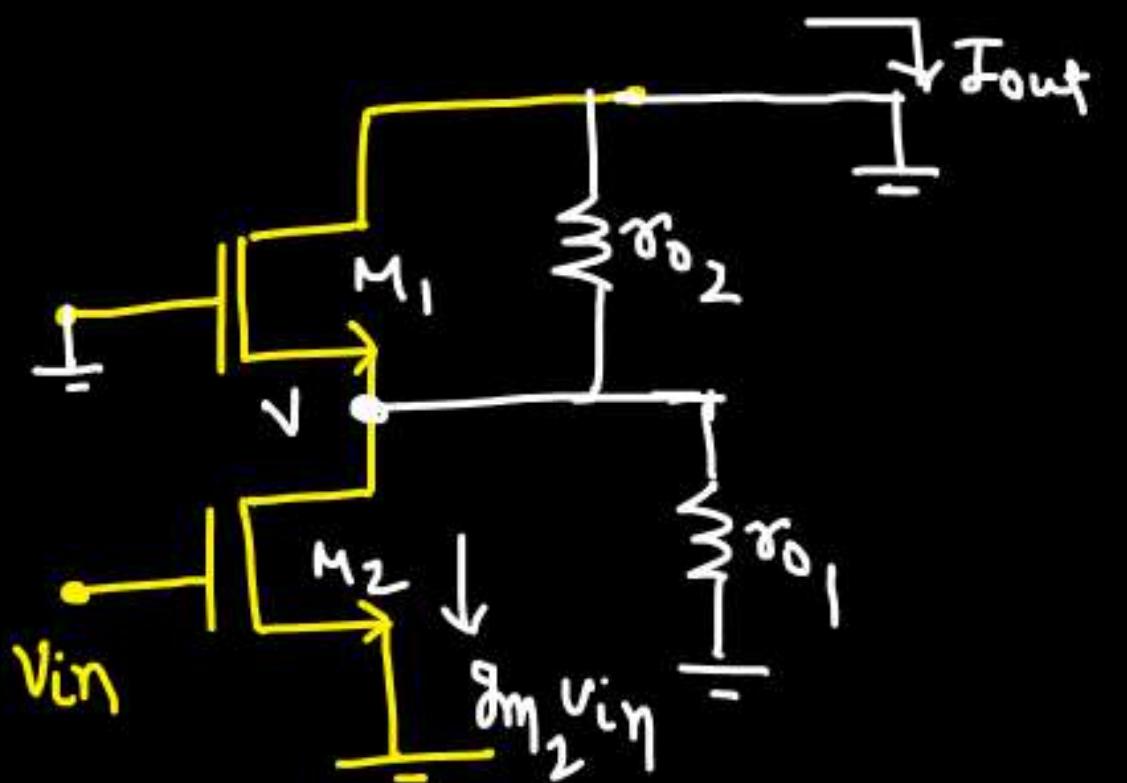Generally g_m values are in mS and r_o values are in $\text{M}\Omega$. We took such values only for understanding purpose.




① $G_m \rightarrow$

$$I_{out} = - \left[\frac{g_m 2 V_{in}}{3} + \frac{g_m 2 V_{in}}{3} \right]$$

$$I_{out} = - \frac{2 g_m 2 V_{in}}{3}$$

$$G_m = - \frac{2 g_m 2}{3}$$

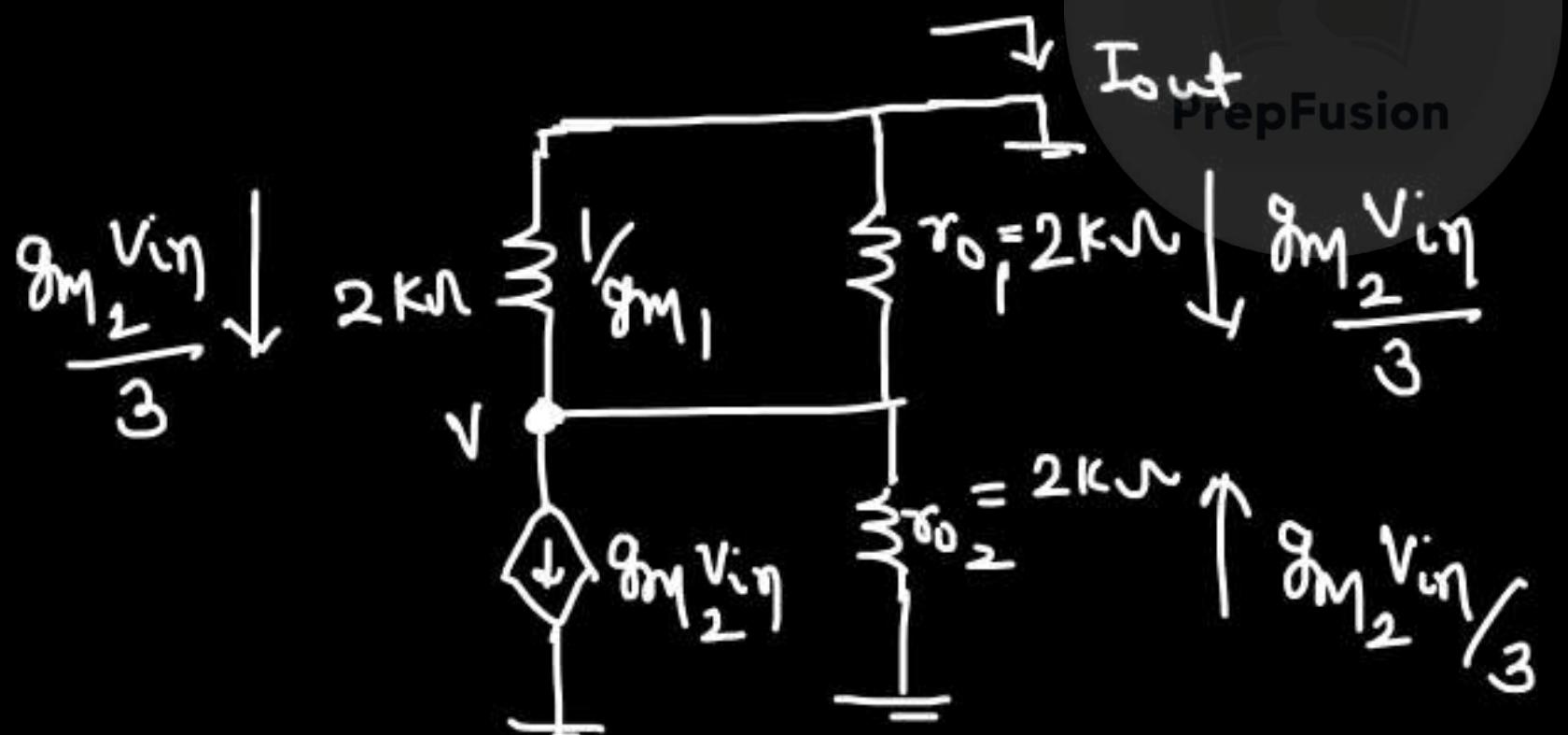

$$R_{out} = r_{o1} + r_{o2} + \delta m_1 r_{o1} r_{o2}$$

$$= 2k + 2k + \frac{1}{2k} \times 2k \times 2k$$

$$R_{out} = 6 \text{ k}\Omega$$



$$\Delta V = -\frac{2}{3} \times 3mS \times 6 \text{ k}\Omega$$

$$\Delta V = -12 \text{ V/V}$$



MOS Amplifiers Using PMOS:-


① Common Source Amplifier:-

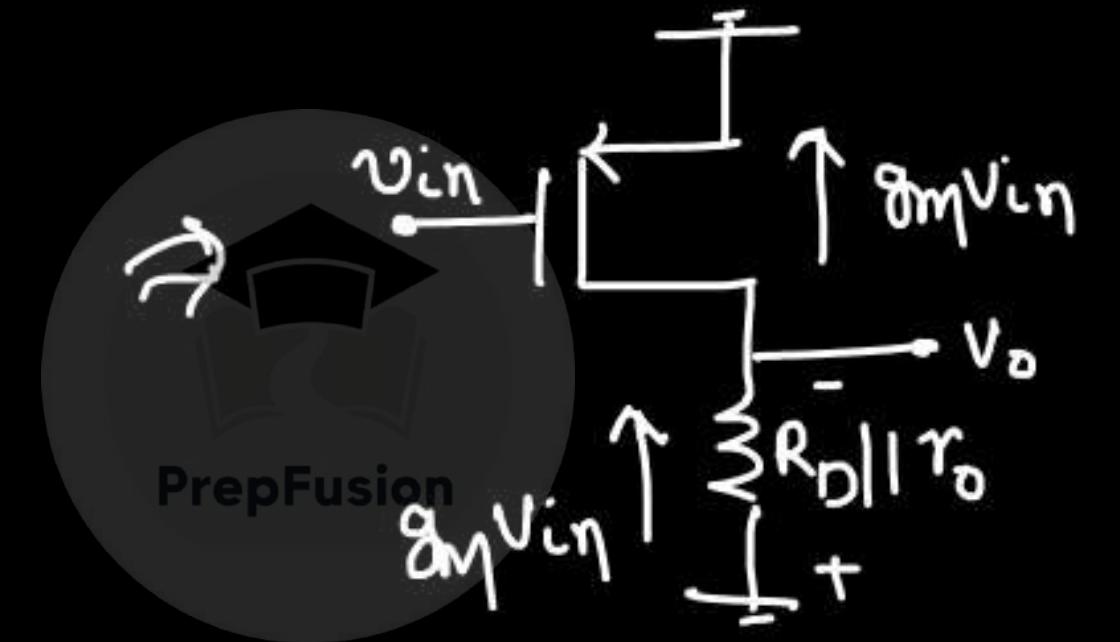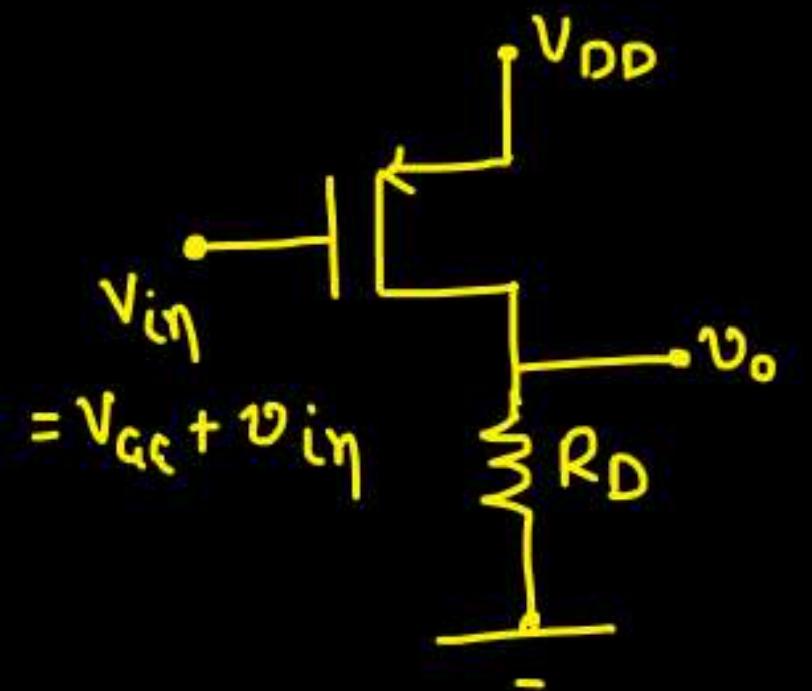


$$\frac{V_o}{V_{in}} = -g_m (R_D || r_o)$$

⇒ Current gain = $\mathcal{I}_P / \mathcal{I}_B$ resistance = ∞ (\mathcal{I}_P current = 0)

⇒ O/P impedance:-

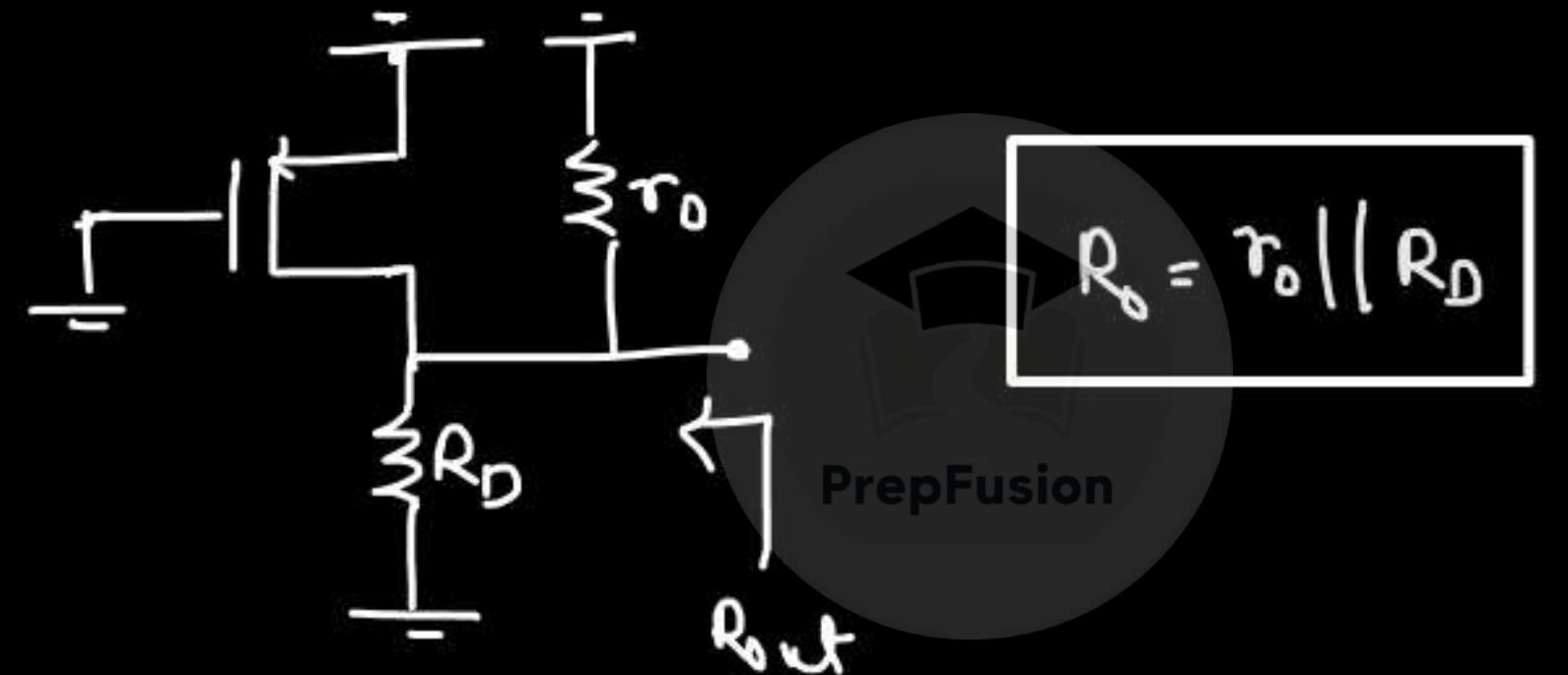

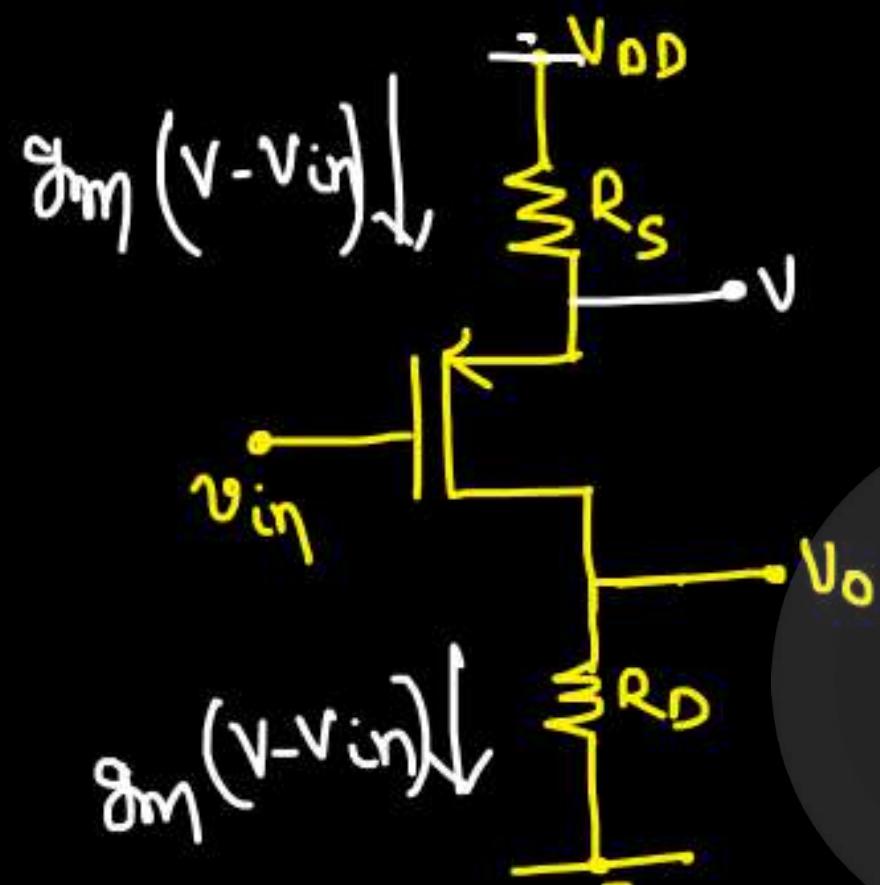Common Source Amplifier with degeneration:-



$\lambda = 0$

$$A_V = -\frac{g_m R_D}{1 + g_m R_s}$$

PrepFusion

$$\Rightarrow \frac{V}{R_s} = -\frac{V_o}{R_D}$$

$$V_o = g_m R_D \left[-\frac{R_s}{R_D} V_o - v_{in} \right]$$

$$V = -\frac{R_s}{R_D} V_o$$

$$V_o [1 + g_m R_s] = -g_m R_D v_{in}$$

$$\Rightarrow \frac{V_o}{v_{in}} = -\frac{g_m R_D}{1 + g_m R_s}$$

$$A_V = -\frac{g_m R_D}{1 + g_m R_S}$$

$$g_m R_S \gg 1$$


$$A_V = -\frac{g_m R_D}{g_m R_S}$$





$$A_V = -\frac{R_D}{R_S}$$

→ constant gain (very stable)

O/P impedance :-

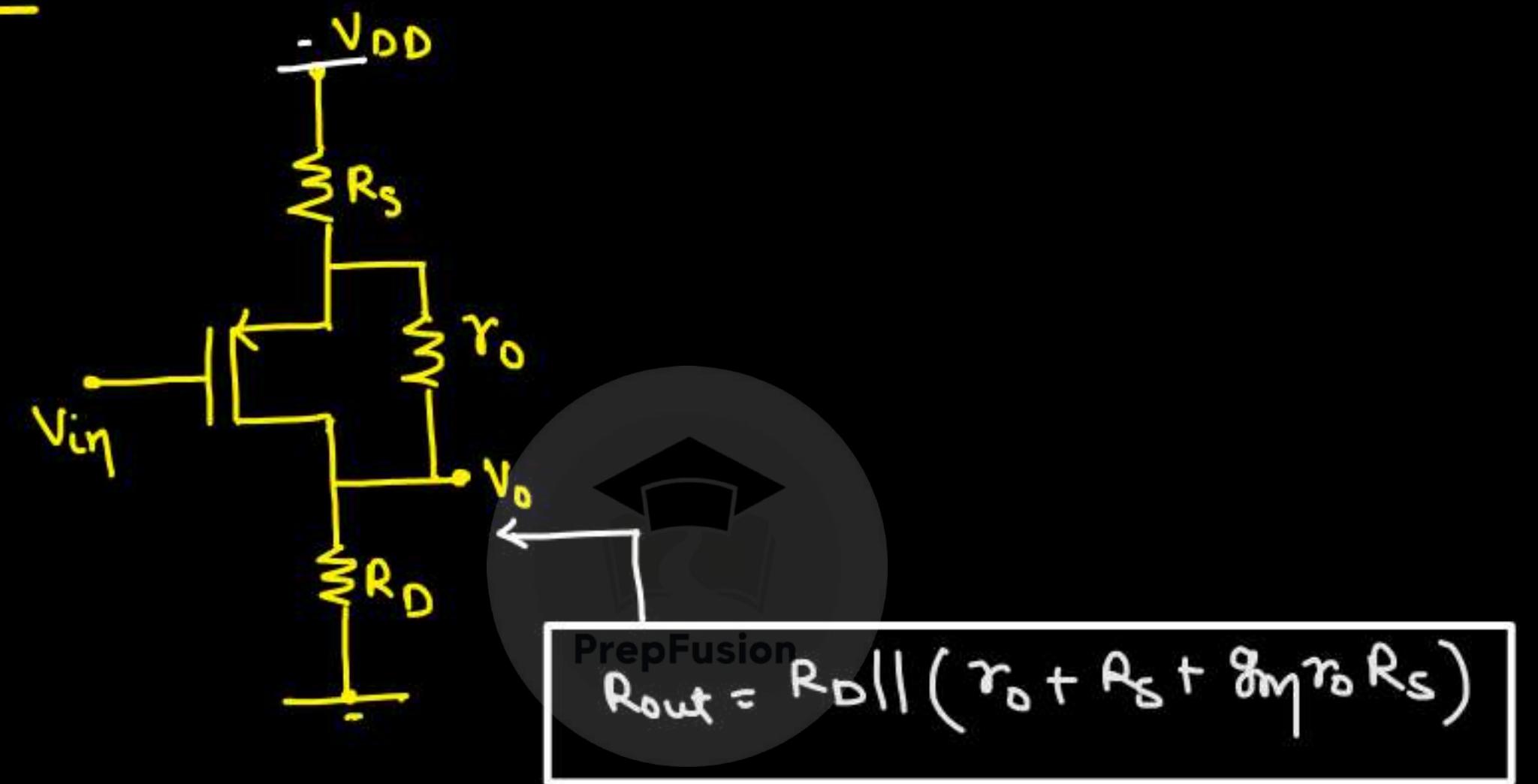


② Common Gate Amplifier:-

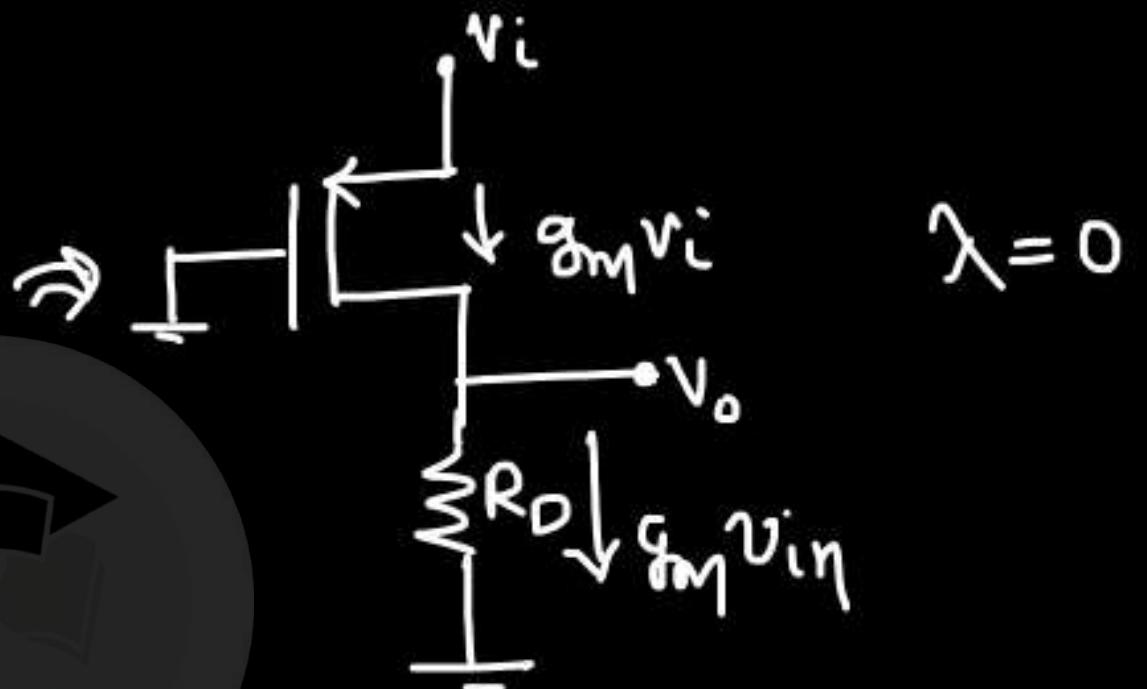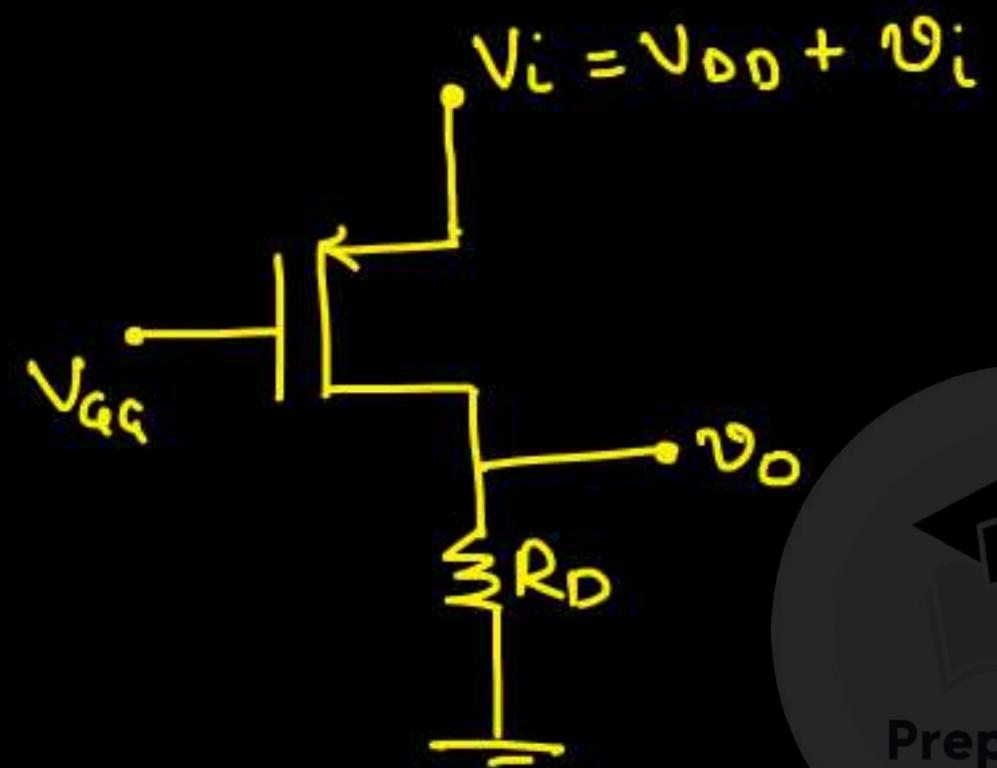

$$\frac{v_o}{v_i} = g_m R_D$$


Input Impedance :-

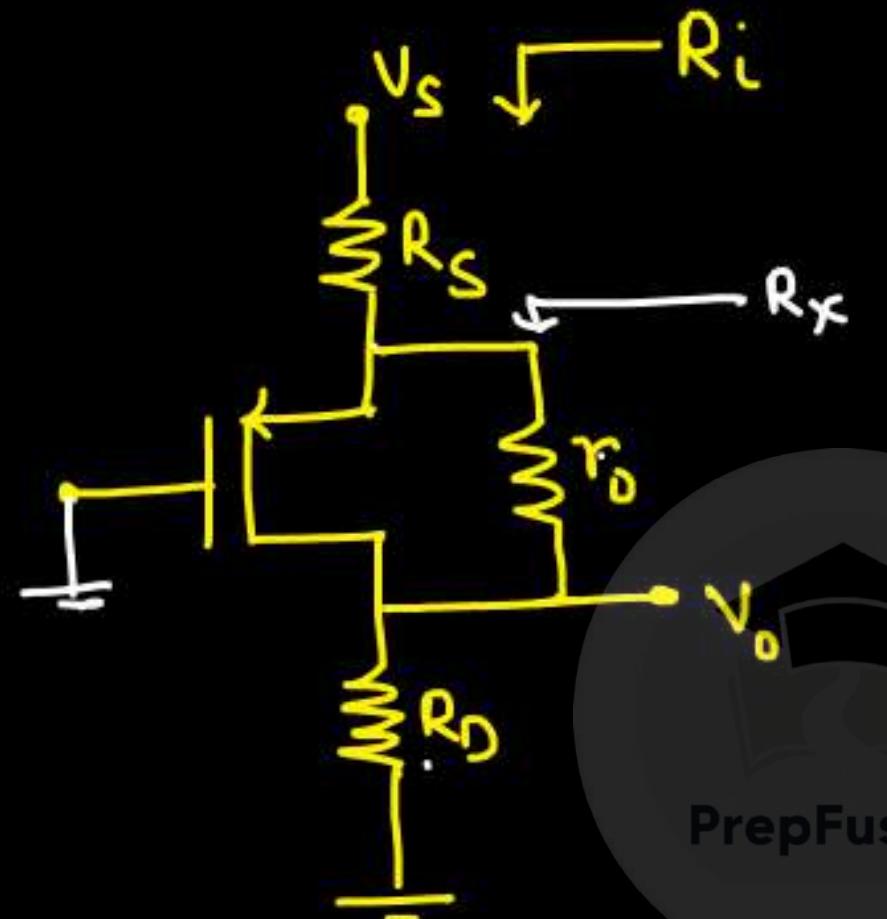

$$R_i = R_s + \frac{R_o + r_o}{1 + g_m R_o}$$

PrepFusion


Output Impedance:-

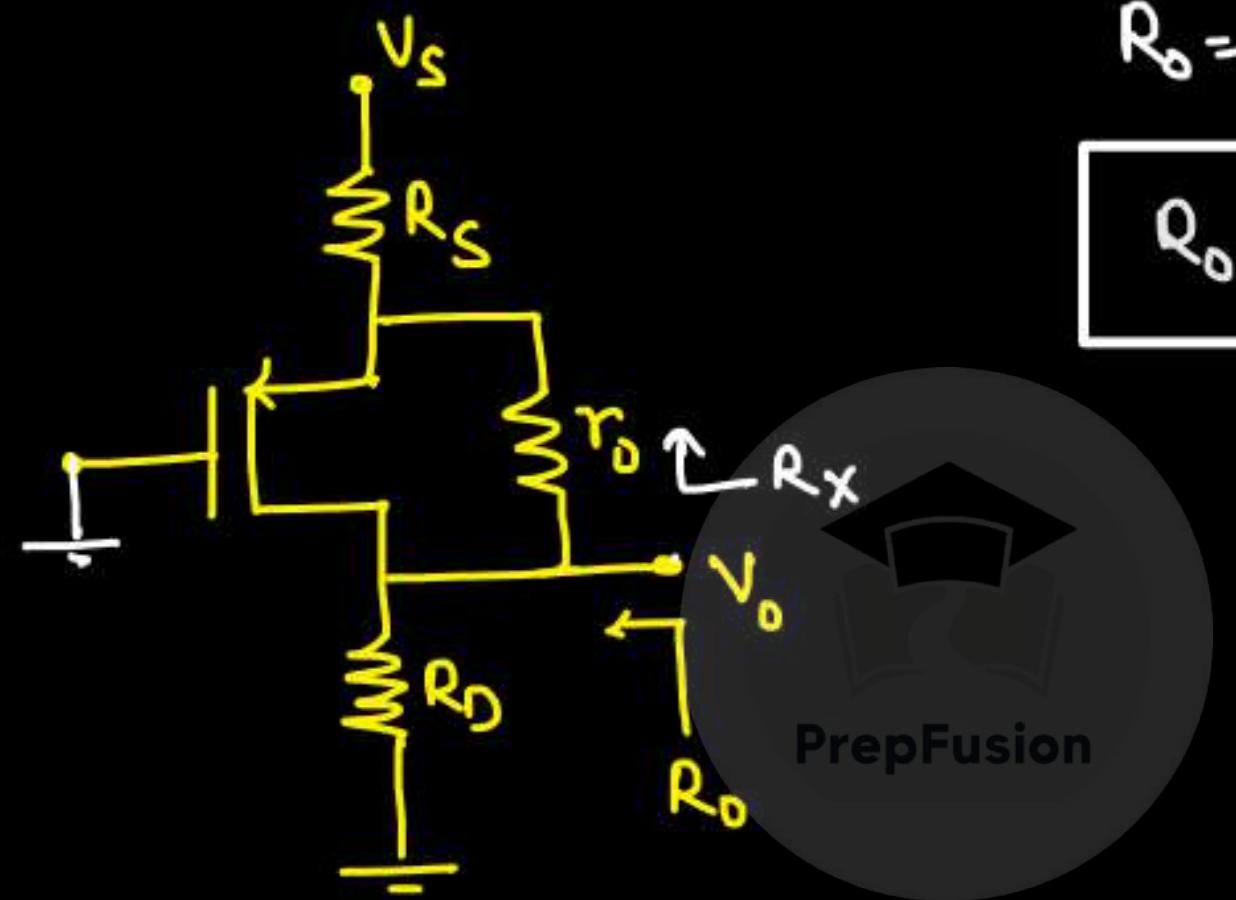


$$R_o = R_D \parallel R_X$$

$$R_o = R_D \parallel r_o + R_s + g_m r_o R_s$$

Current gain :-

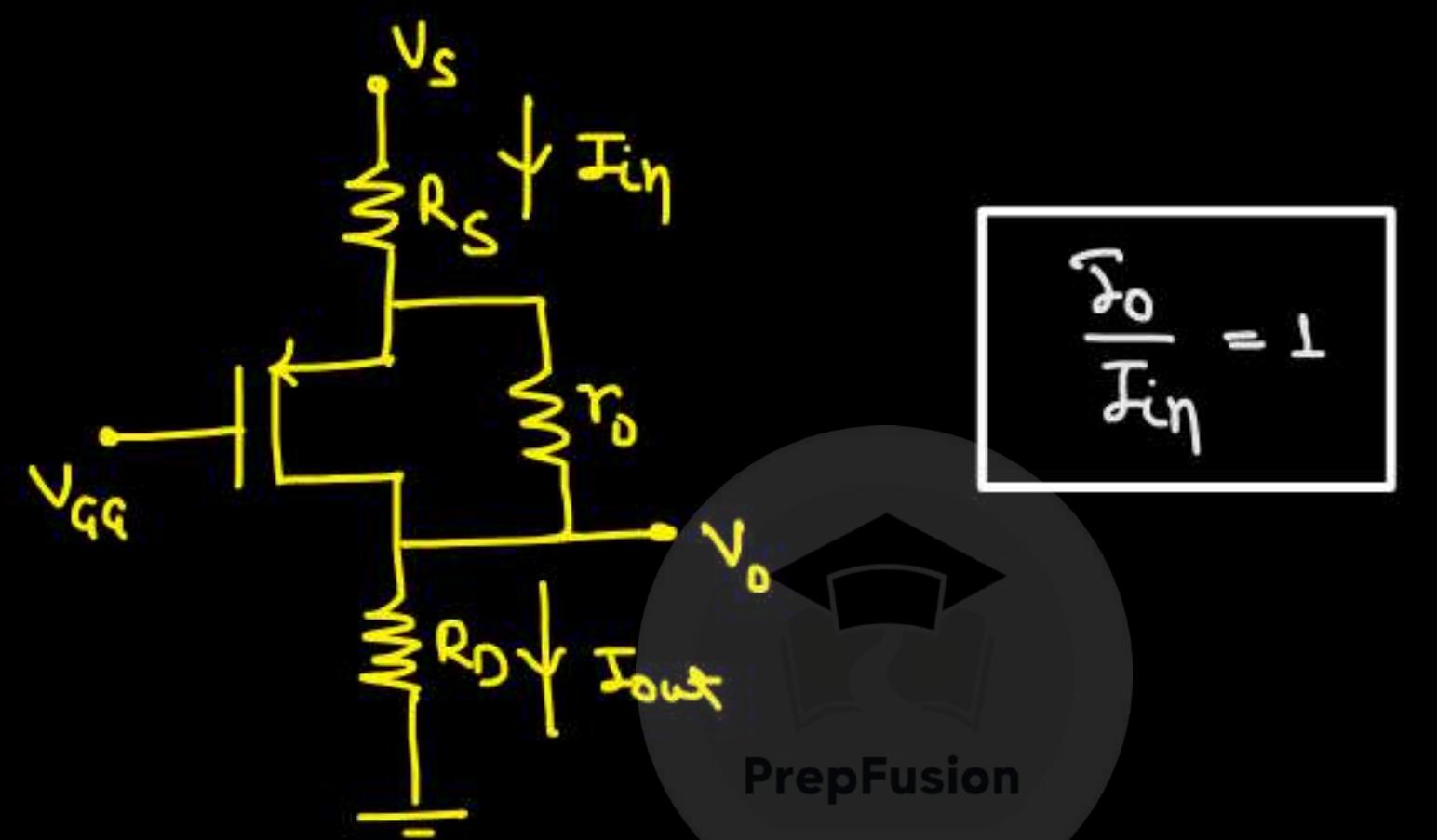

③ Common - Drain Amplifiers:-

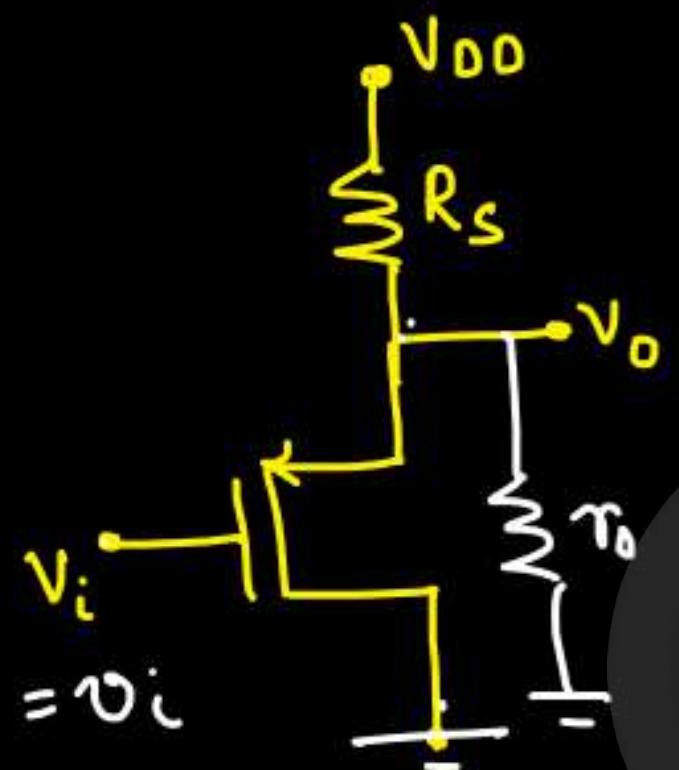

$$\frac{V_o}{V_i} = \frac{R_s}{R_s + \frac{1}{g_m}}$$


$\lambda = 0$

$$\frac{V_o}{V_i} = \frac{g_m R_s}{1 + g_m R_s}$$

$\lambda \neq 0$




$$\frac{V_o}{V_i} = \frac{g_m (R_s || r_o)}{1 + g_m (R_s || r_o)}$$

Output Impedance :-

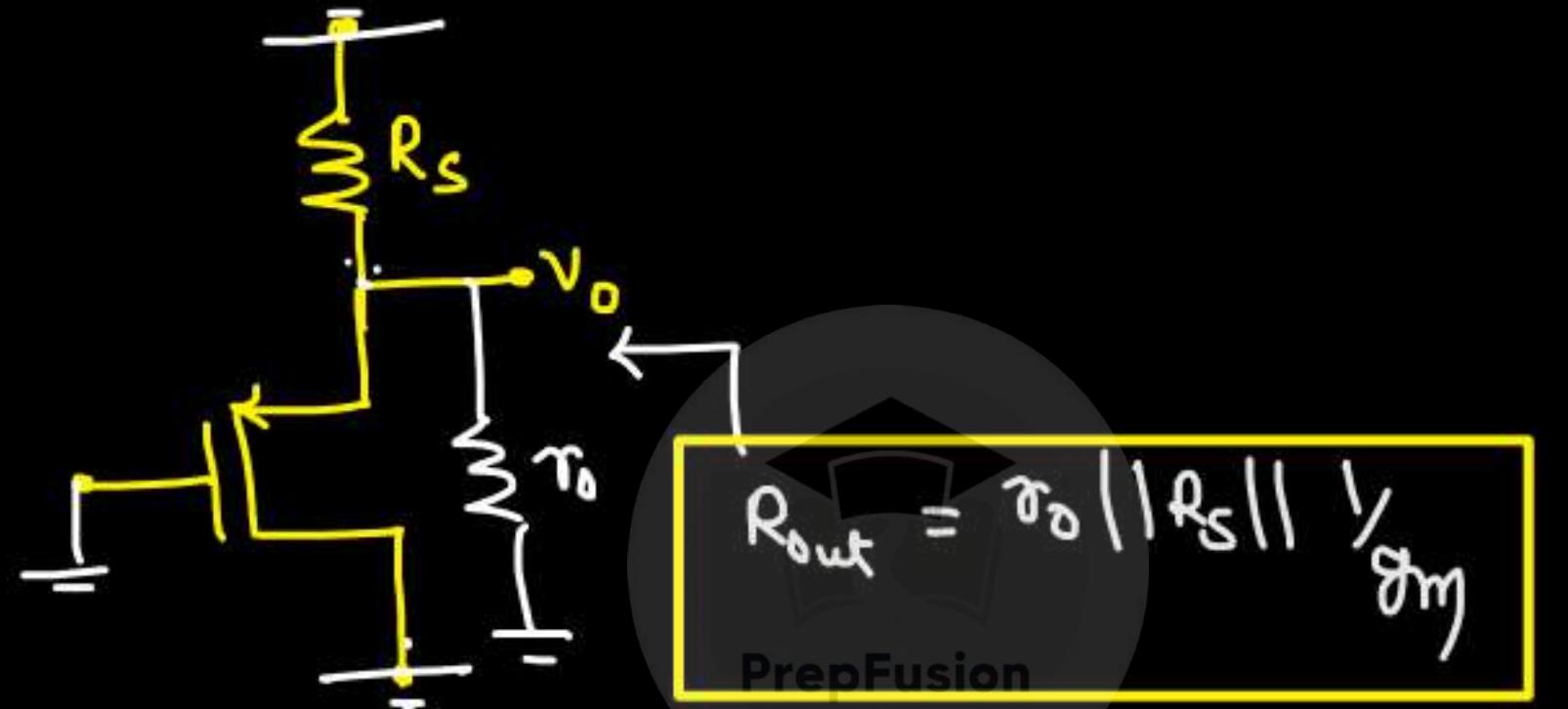


Assignment - 7

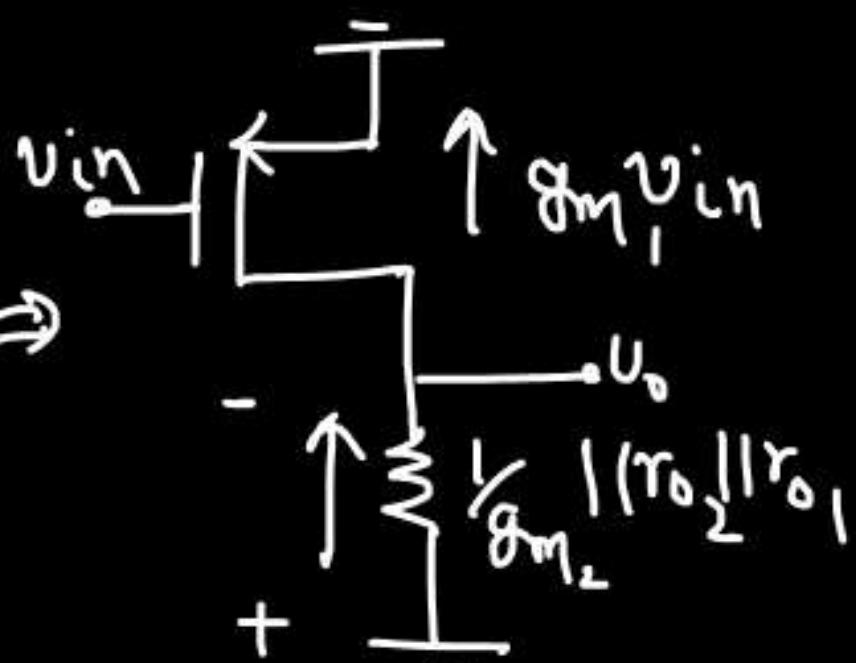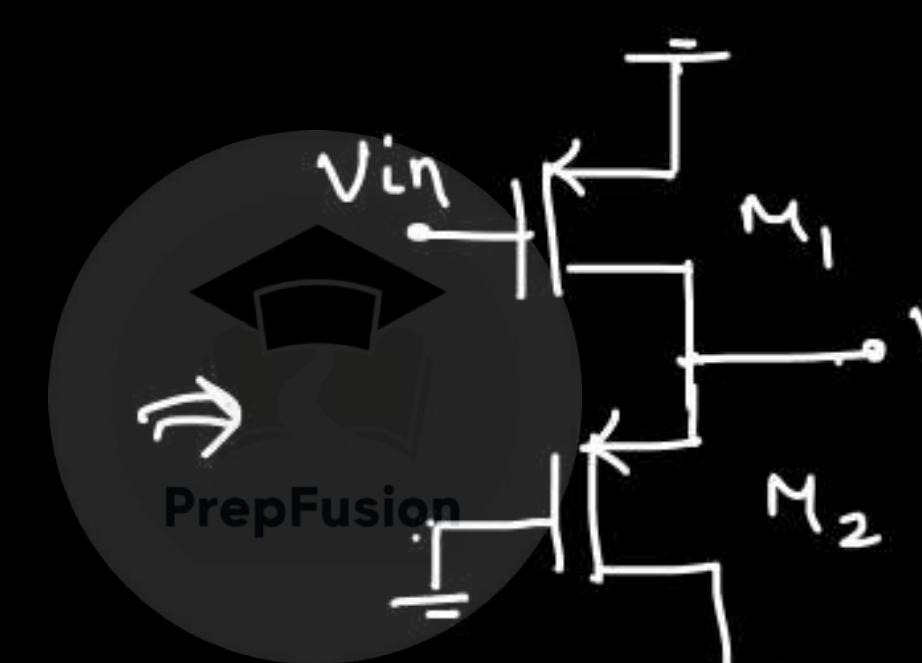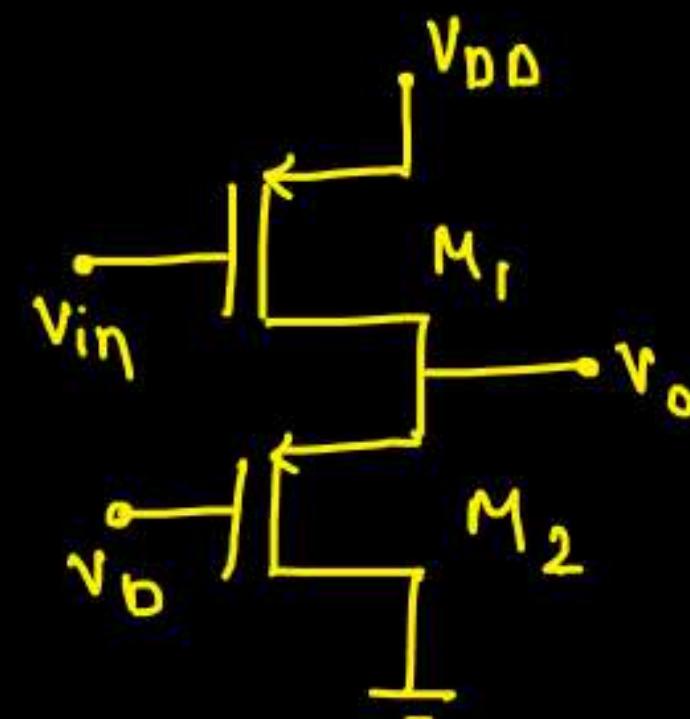Q. Find small signal voltage gain.
 $(\lambda \neq 0)$



$$\frac{v_o}{v_i} = -g_{m1} \left[\frac{1}{g_{m2}} || r_{o2} || r_o \right]$$

Q.

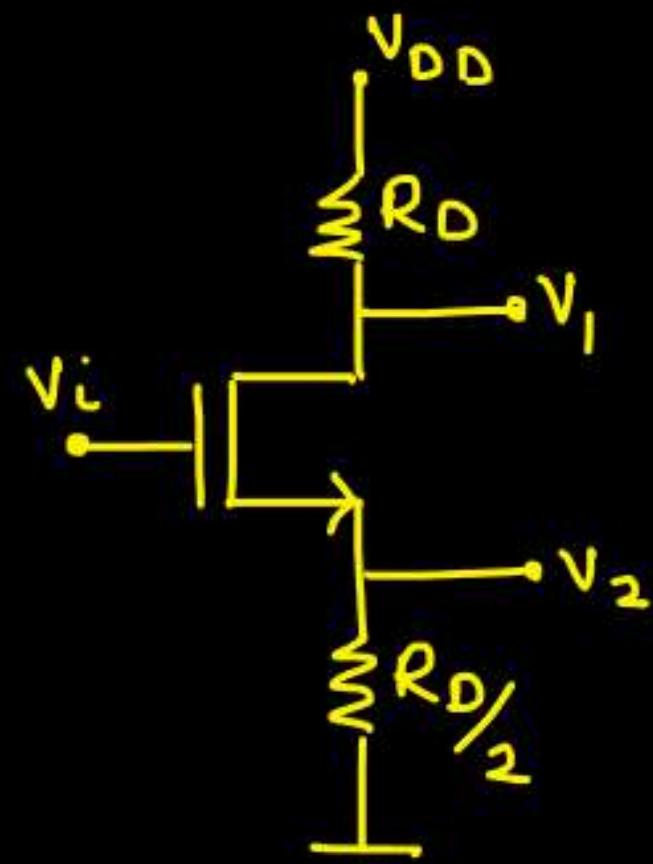


Find $\frac{v_1}{v_2} = ?$ [small signal]
($\lambda \neq 0$)




$$v_1 = -I R_D$$

$$v_2 = -I R_D / 2$$

$$\boxed{\frac{v_1}{v_2} = 2}$$

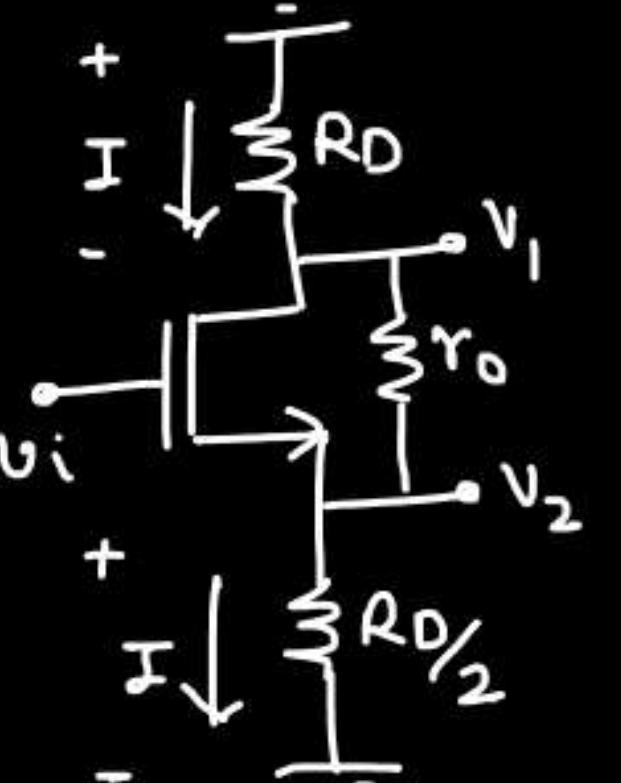

Q.

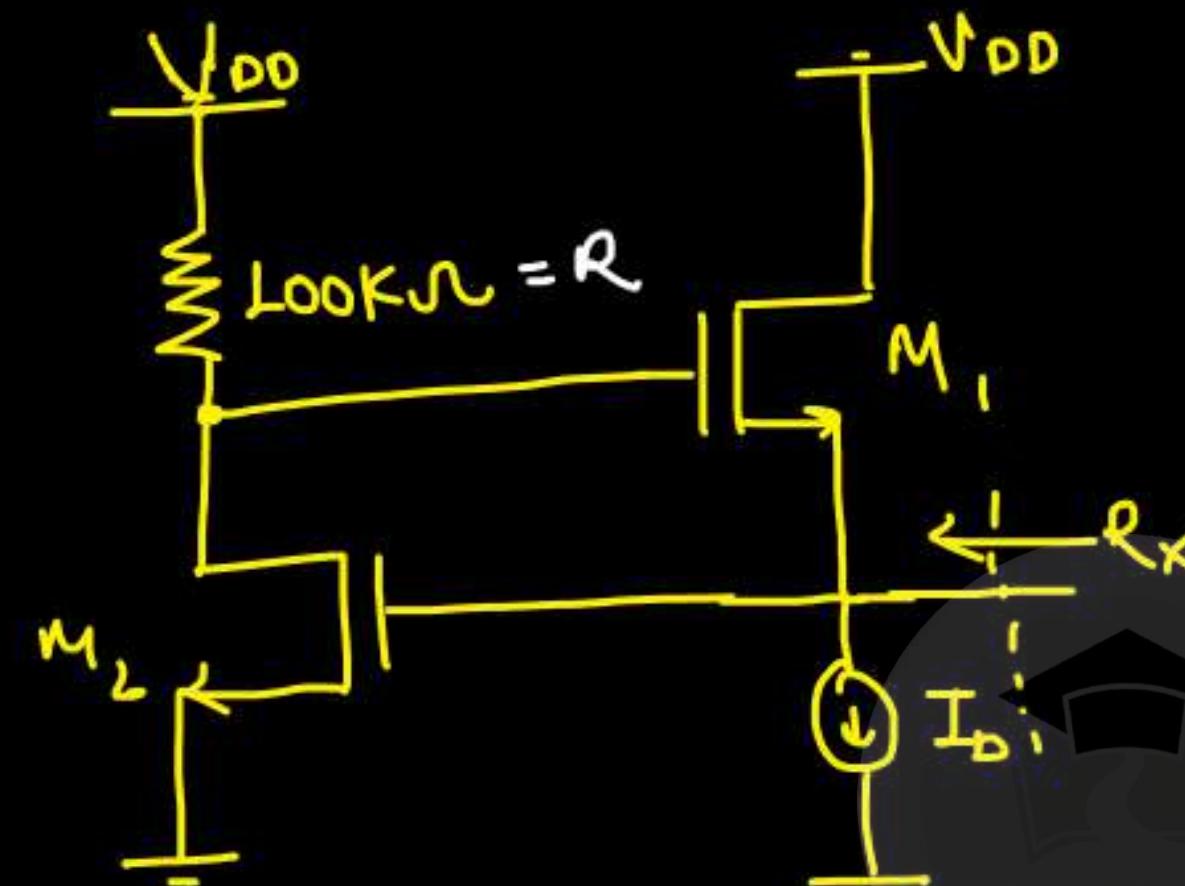

$$g_m = g_{m_1} = g_{m_2} = 100 \mu\text{S}$$


Determine small signal $R_x = ?$

$$R = 100 \text{k}\Omega$$

$$I_x = g_m (V_x - V) \rightarrow ①$$

$$V = -g_m V_x R \rightarrow ②$$

$$I_x = g_m (V_x + g_m V_R R)$$

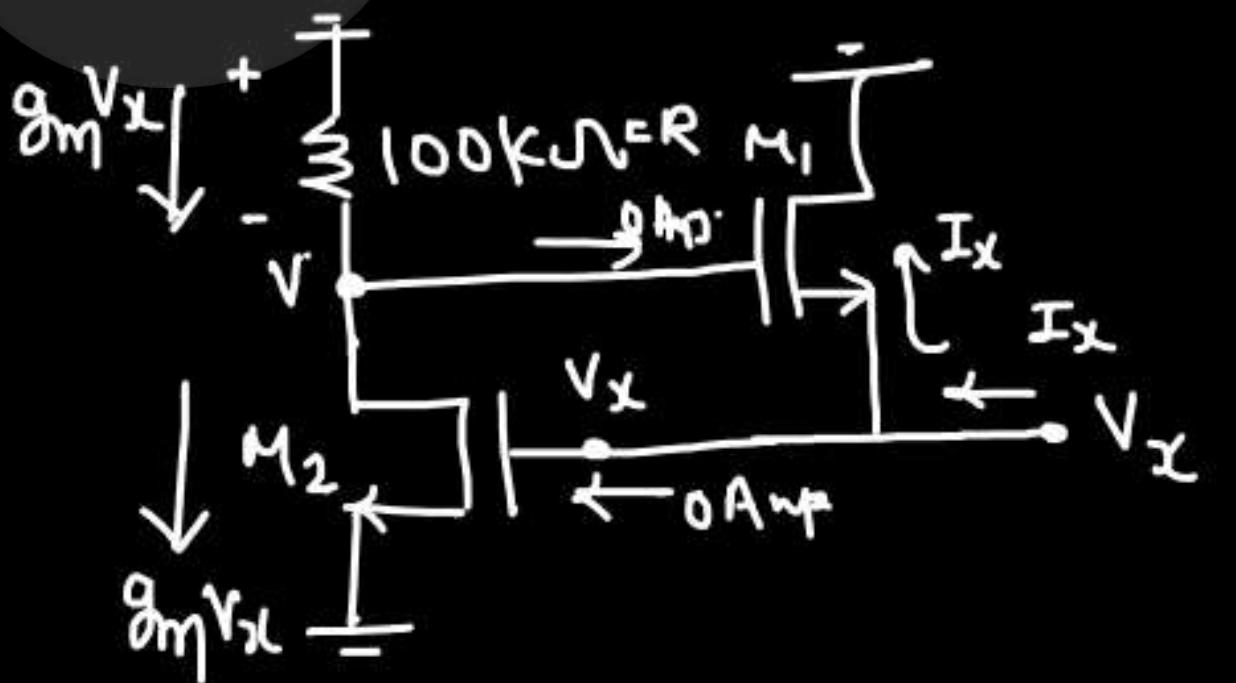

$$R_x = \frac{V_x}{I_x}$$

$$I_L = g_m [1 + g_m R] V_L$$


$$R_x = \frac{V_L}{I_L} = \frac{1}{g_m [1 + g_m R]} \\ = \frac{1}{10^{-4} [1 + 10^{-4} \times 10^5]}$$

$$R_x = \frac{1}{10^{-4}} \times 10^4$$

HrepFusion

* R_x = 909.09 Ω


Q.

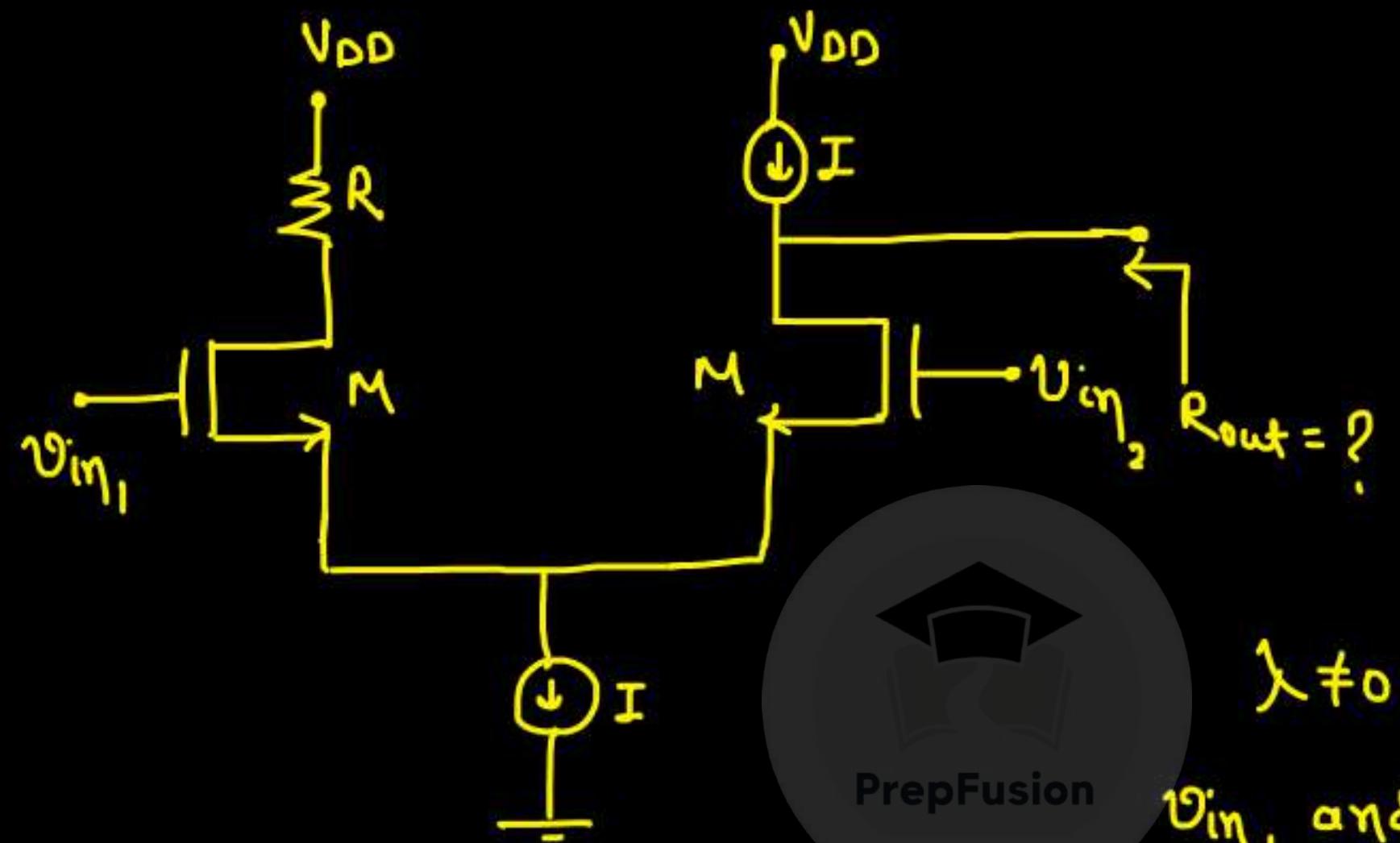


$$\lambda \neq 0$$

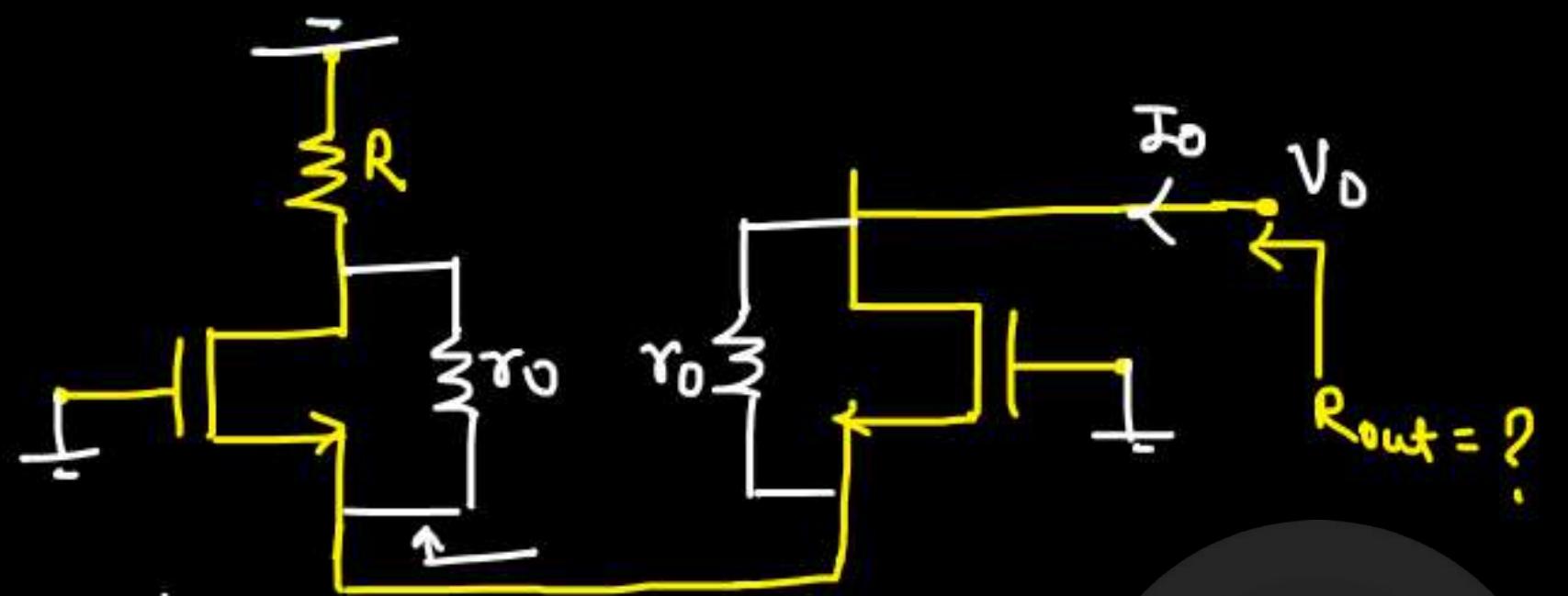v_{in1} and v_{in2} are small signal i/p.
find small signal $R_{out} = ?$





$$R_{out} = \frac{V_D}{I_D}$$

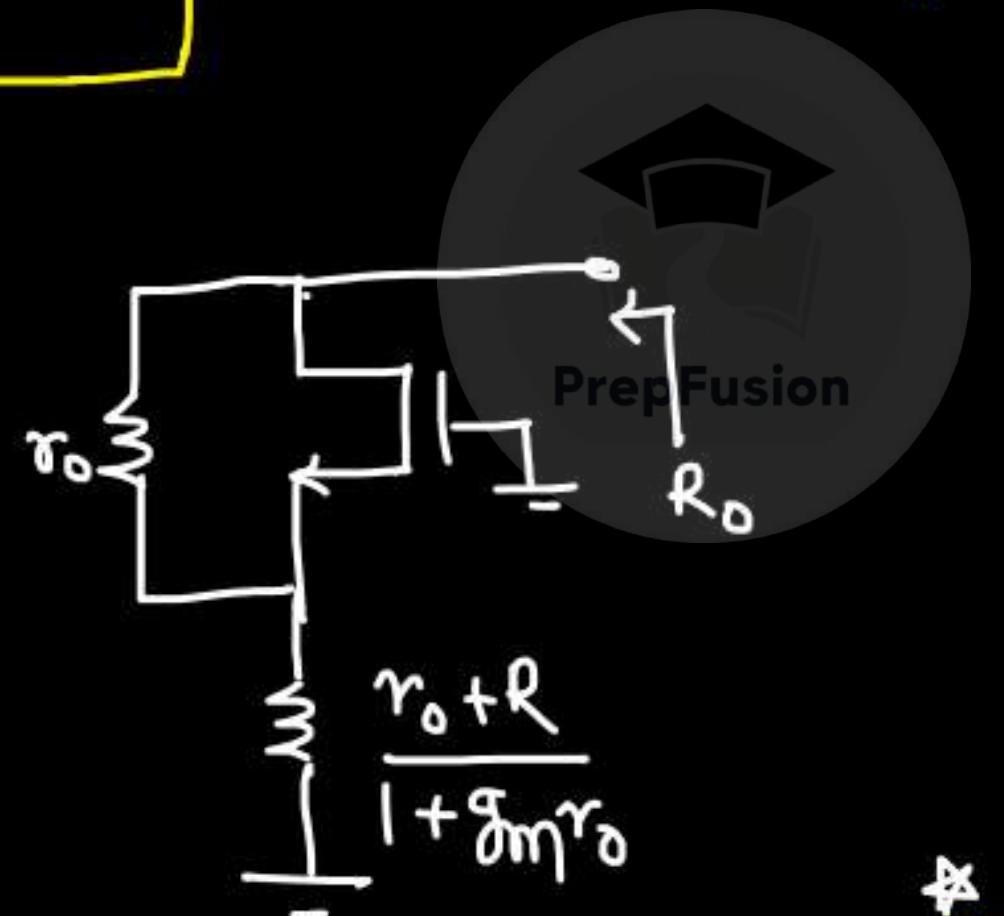





$$R_D = r_o + \frac{r_o + R}{1 + g_m r_o} + g_m r_o \left[\frac{r_o + R}{1 + g_m r_o} \right]$$

$$= r_o + \left(\frac{r_o + R}{1 + g_m r_o} \right) [1 + g_m r_o]$$

* $R_{out} = 2r_o + R$

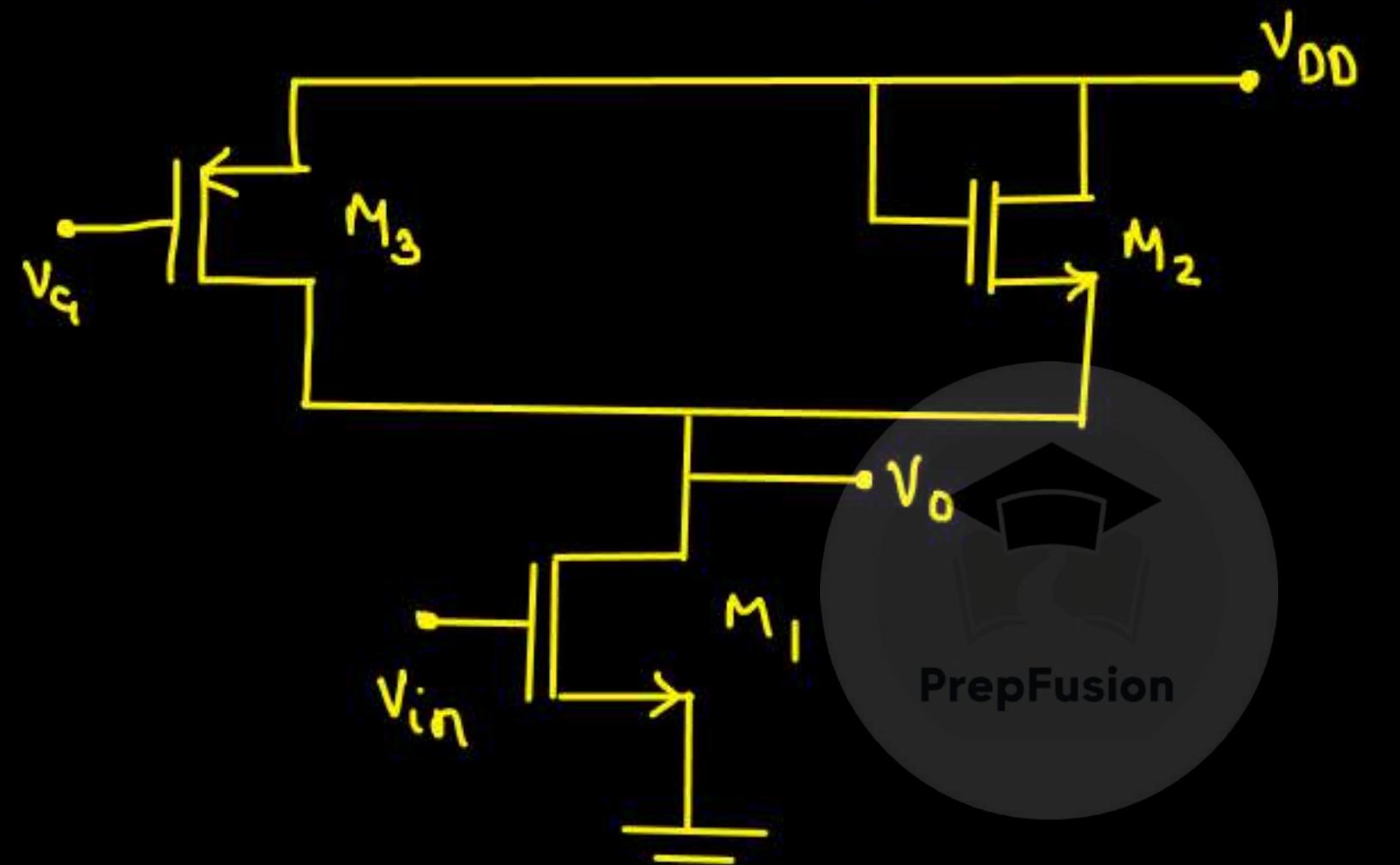Q. find small signal voltage gain. ($\lambda \neq 0$)




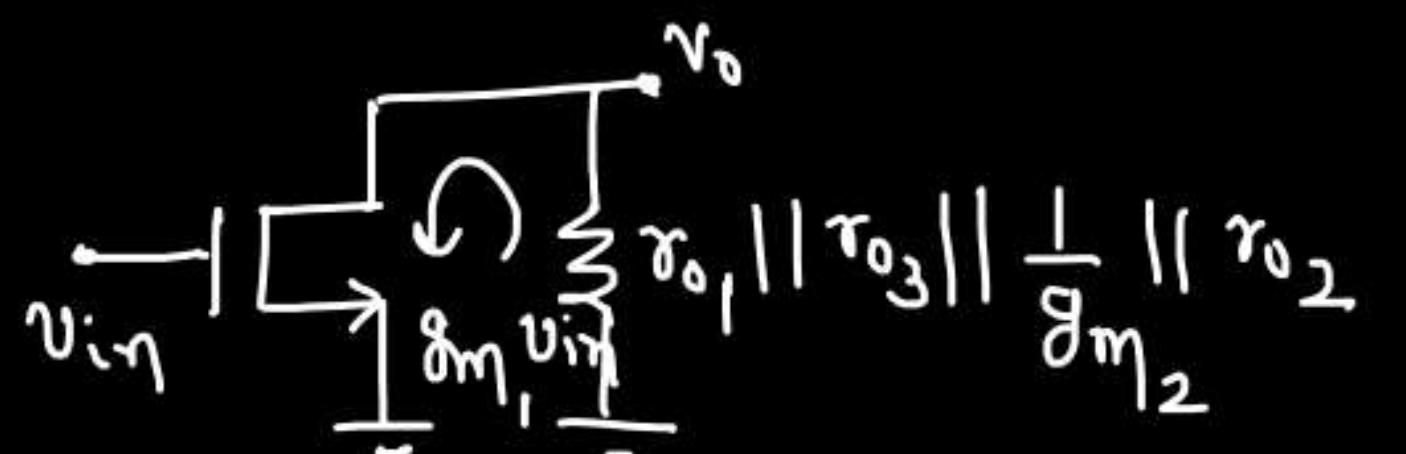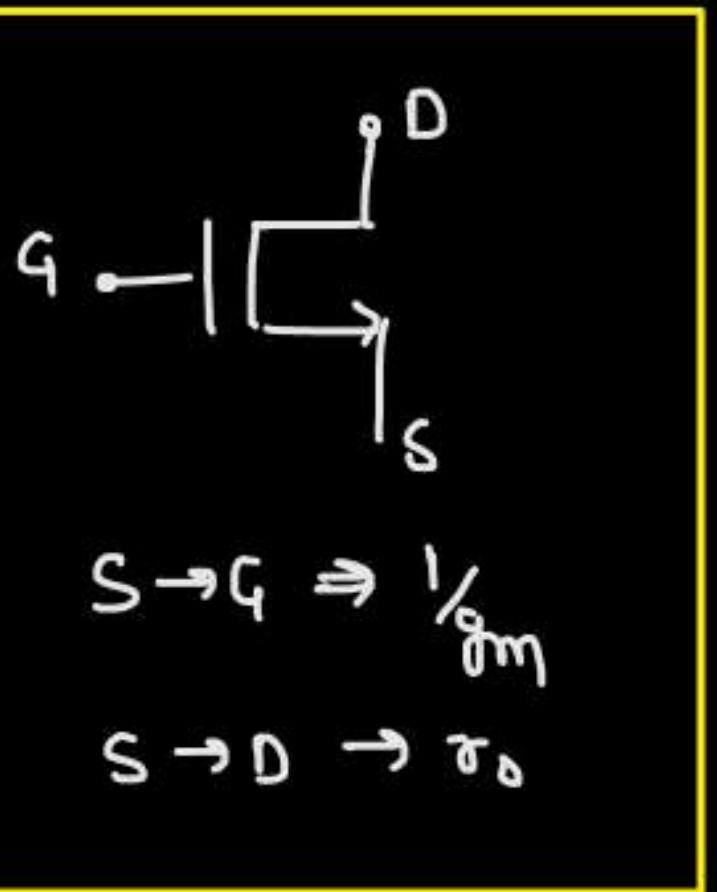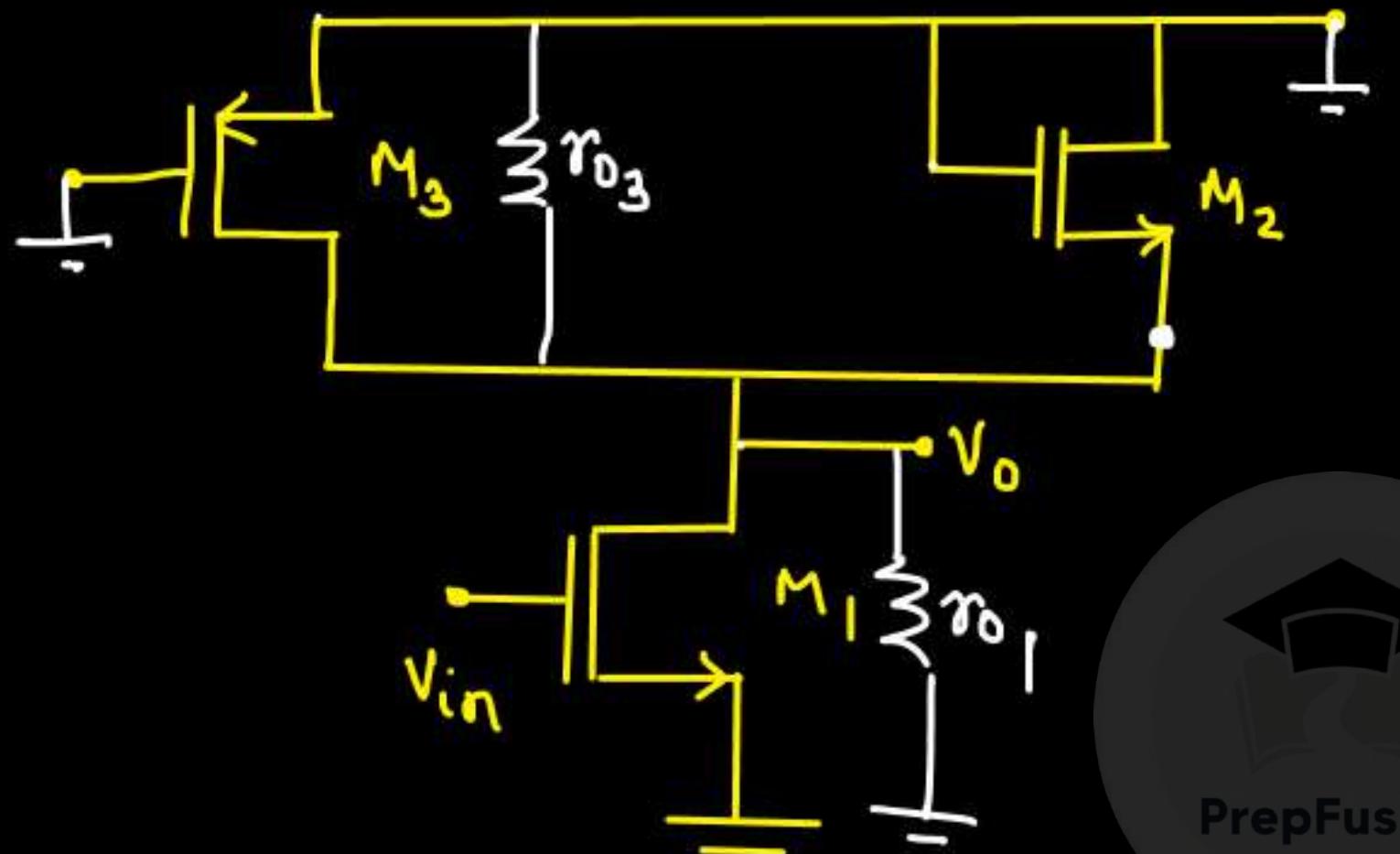

AP

$$\frac{V_o}{V_i} = -g_{m1} \left[\frac{1}{g_{m2}} || r_{o2} || r_{o1} || r_{o3} \right]$$


Q.

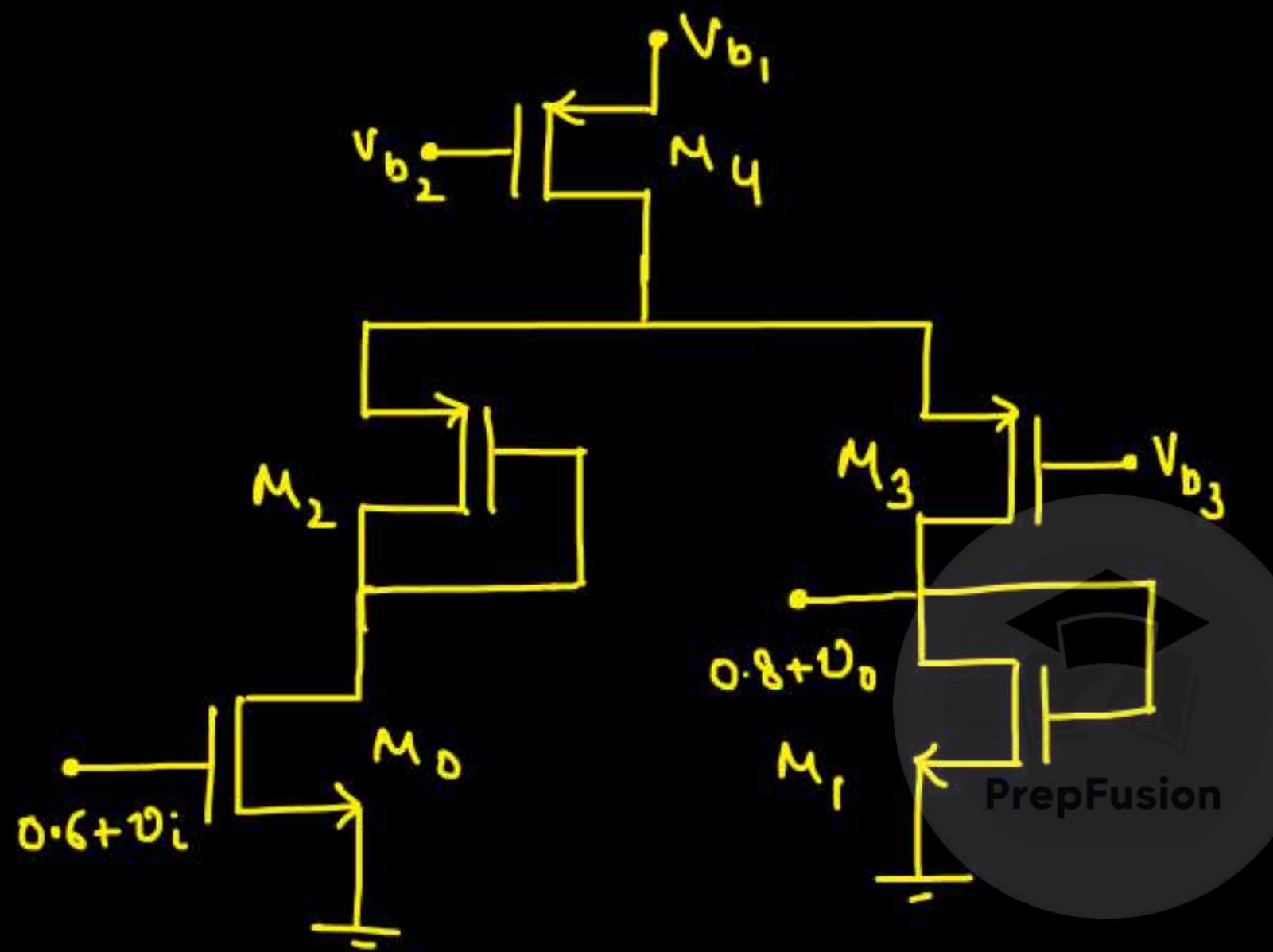

$$\delta m = \frac{2 I_{DC}}{V_{GS} - V_T}$$

Transistors are biased such that all Transistors are working in sat. region.
 $M_0 - M_3$ are biased with $5mA$ current. V_T value for all the transistors is $0.4V$.

find small signal voltage gain v_o/v_i ?

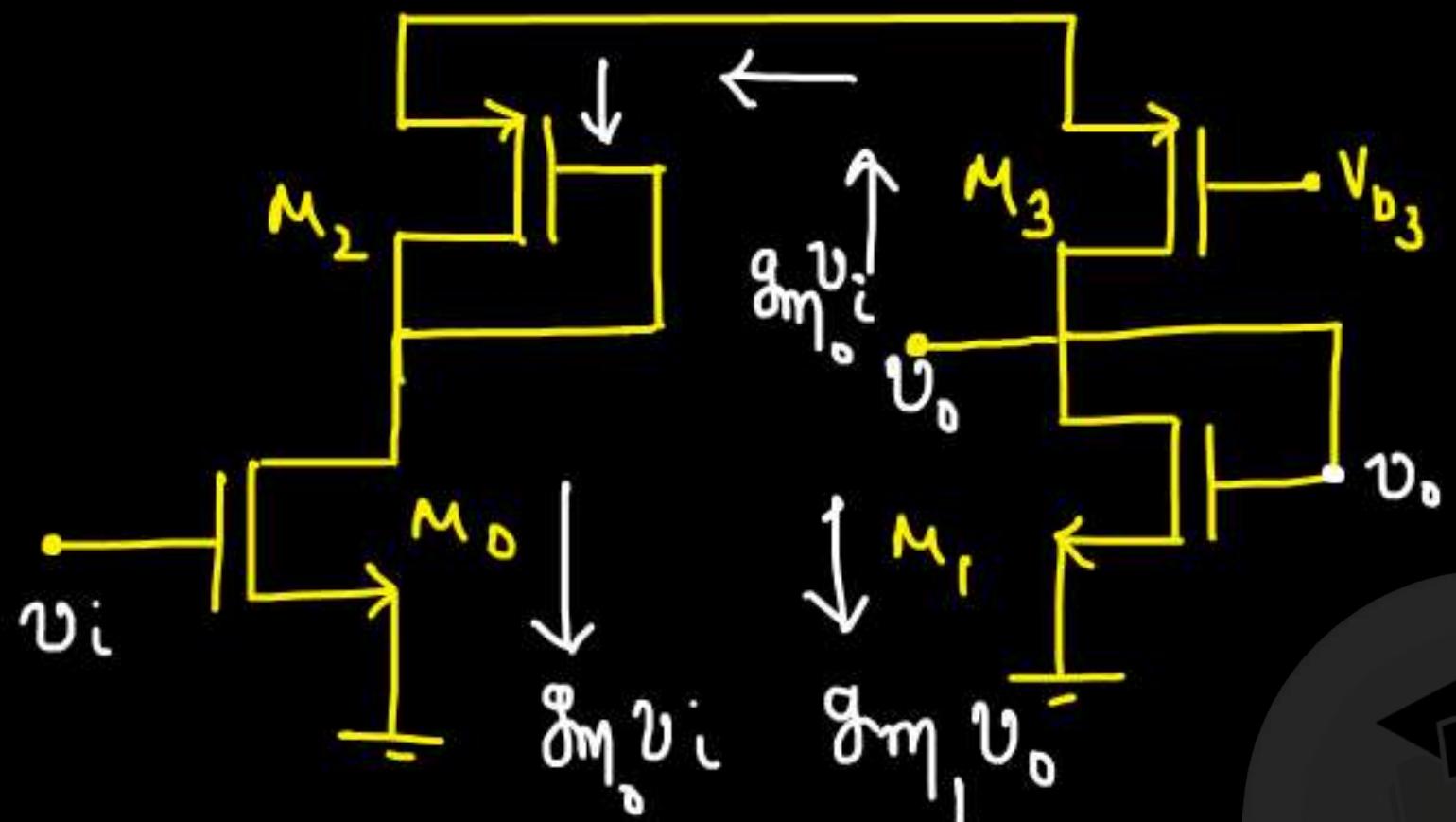

$$\frac{\partial m_0}{\partial m_1} v_L = - \frac{\partial m_1}{\partial m_0} v_0$$

$$\frac{v_0}{v_i} = - \frac{\partial m_0}{\partial m_1}$$




$$\frac{\partial m_0}{(\partial I_{DQ})_{M_0}} = \frac{2 \times 5 \text{ mA}}{0.6 - 0.4} = 50 \text{ mS}$$

$$\frac{\partial m_1}{(\partial I_{DQ})_{M_1}} = \frac{2 \times 5 \text{ mA}}{0.8 - 0.4} = 25 \text{ mS}$$


★ ★

$$\frac{v_0}{v_i} = - \frac{50 \text{ mS}}{25 \text{ mS}} = -2 \text{ V/V}$$

Q. Find small signal voltage gain.

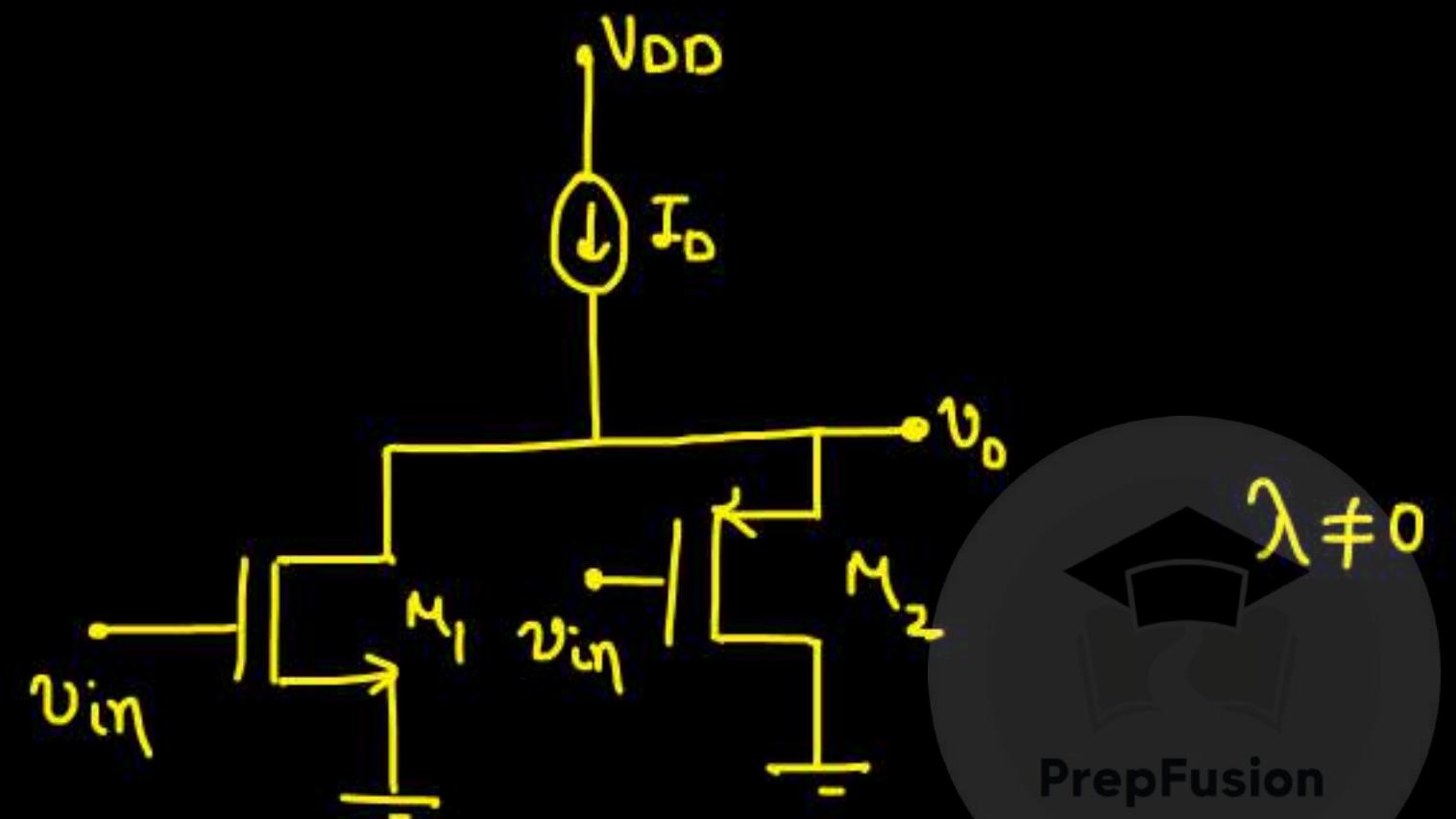

⇒

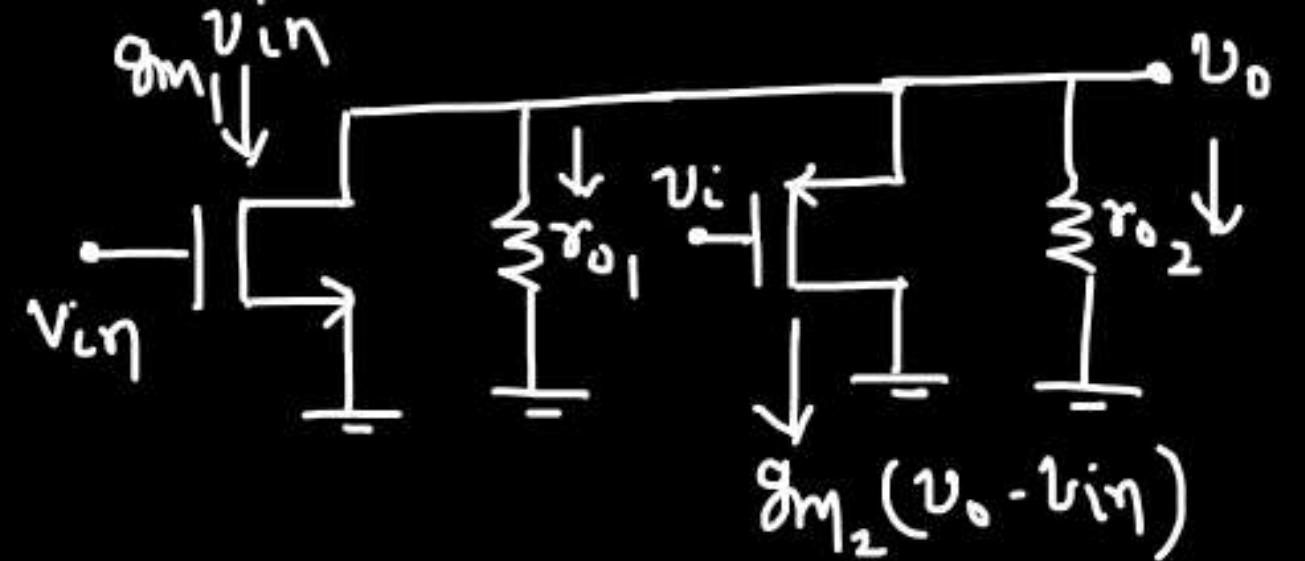

$$g_m_1 v_{in} + \frac{v_o}{r_{o_1}} + g_m_2 (v_o - v_{in}) + \frac{v_o}{r_{o_2}} = 0$$

$$\frac{v_o}{r_{o_1}} + g_m_2 v_o + \frac{v_o}{r_{o_2}} = (g_m_2 - g_m_1) v_{in}$$


$$\frac{V_o}{r_{o_1} \parallel r_{o_2} \parallel \frac{1}{g_m_2}} = (g_m_2 - g_m_1) v_{in}$$

$$\boxed{\frac{V_o}{v_{in}} = (g_m_2 - g_m_1) \left(r_{o_1} \parallel r_{o_2} \parallel \frac{1}{g_m_2} \right)}$$

M-II G_m Rout Mtd:-

PrepFusion


$G_m \rightarrow$

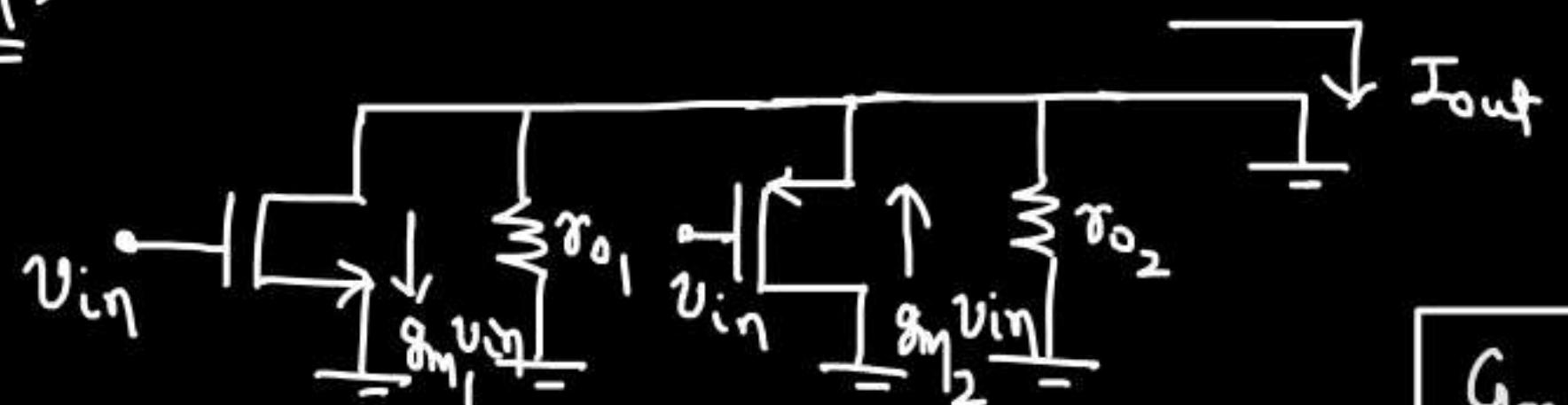

$$g_m v_{in} + I_{out} = g_m v_{in}$$

$$G_m = \frac{I_{out}}{v_{in}} = g_m_2 - g_m_1$$

R_{out} →

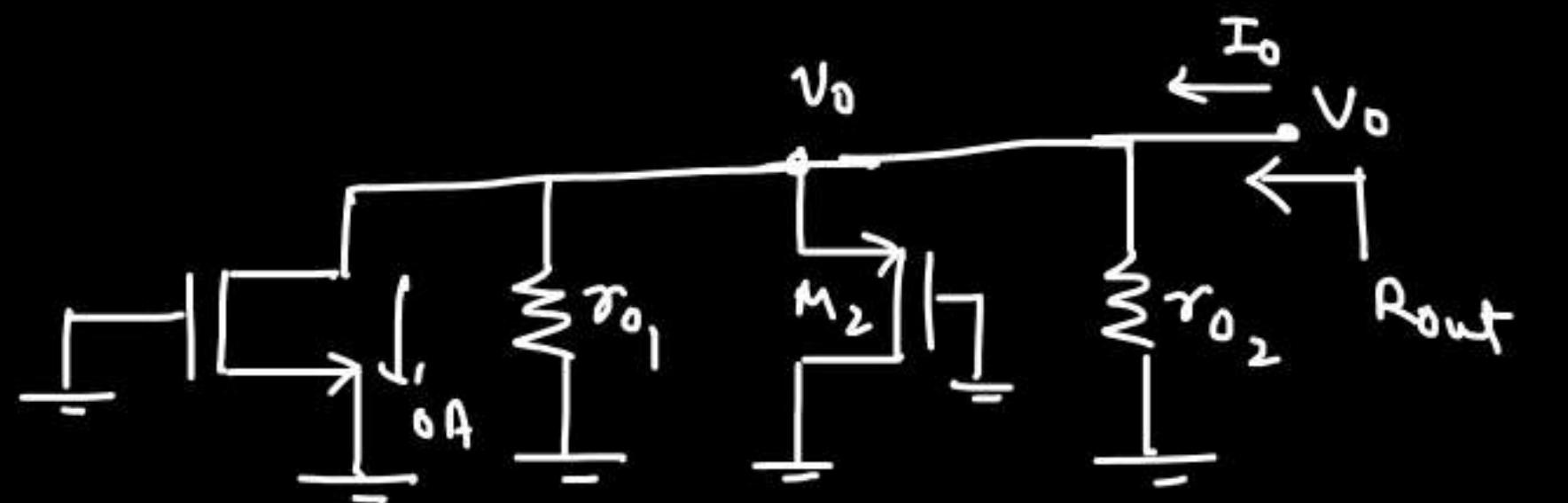



$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m 2}$$

PrepFusion



$$\Delta V = (g_m 2 - g_m 1) \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m 2} \right)$$


Q.

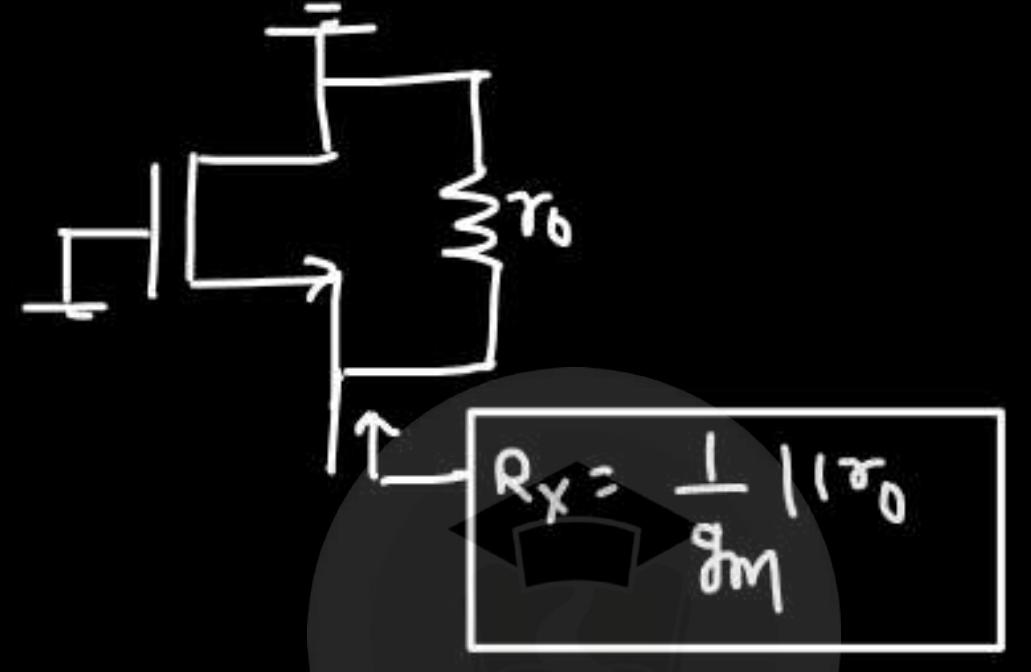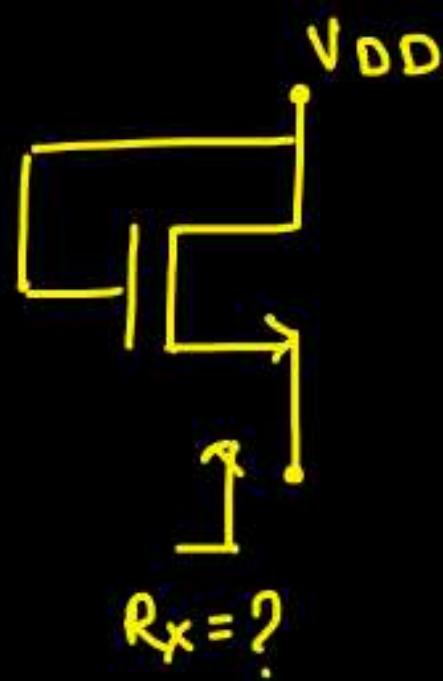



$$R_x = \frac{1}{g_m} || r_o$$

PrepFusion

Q.

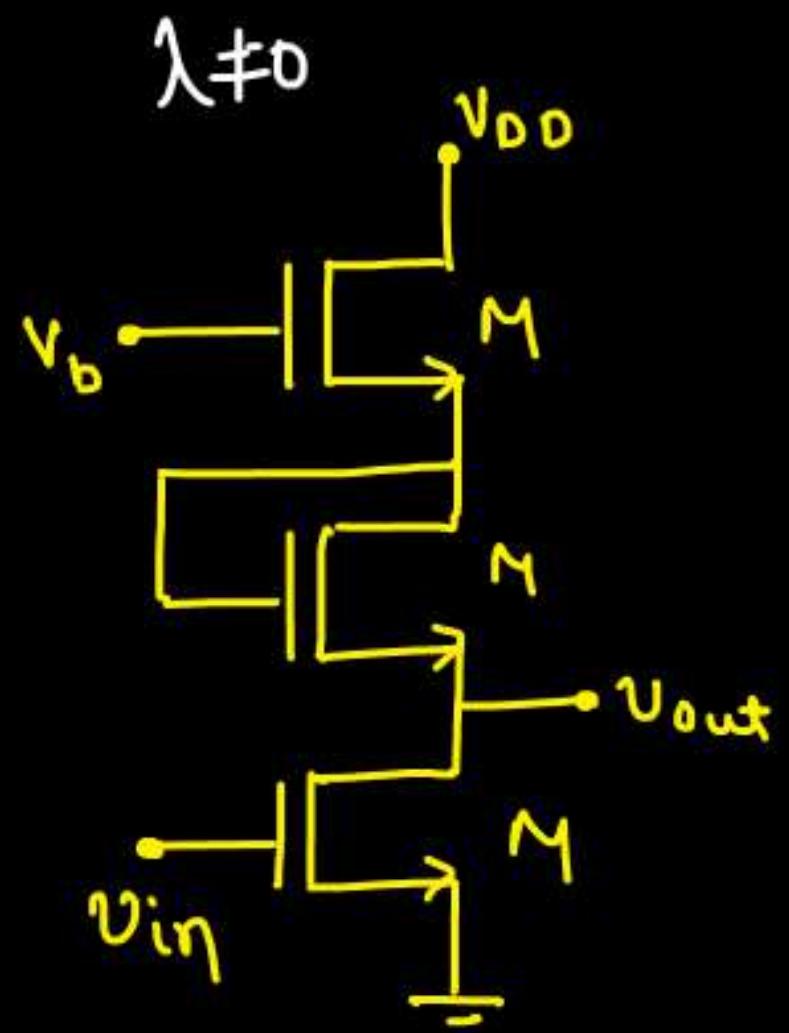

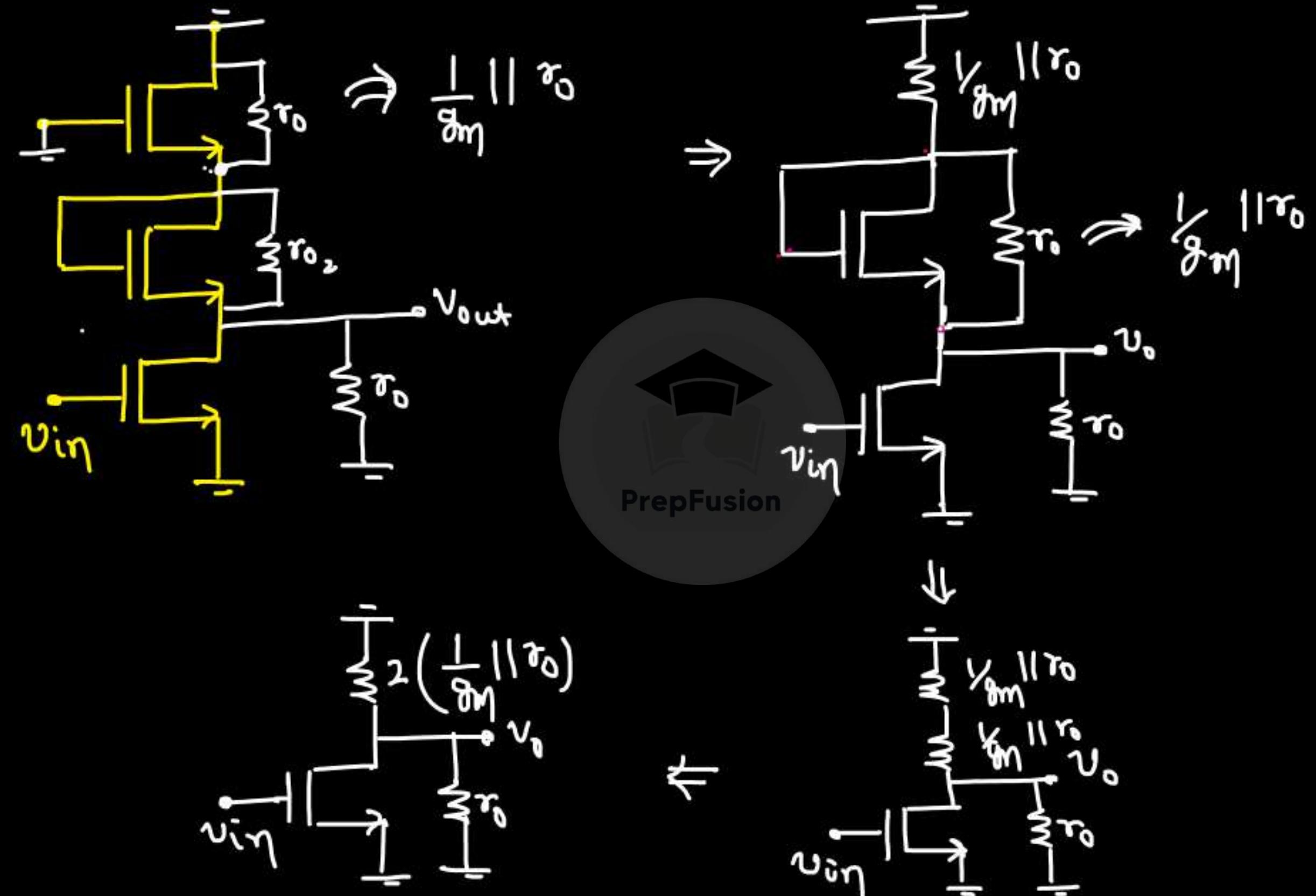


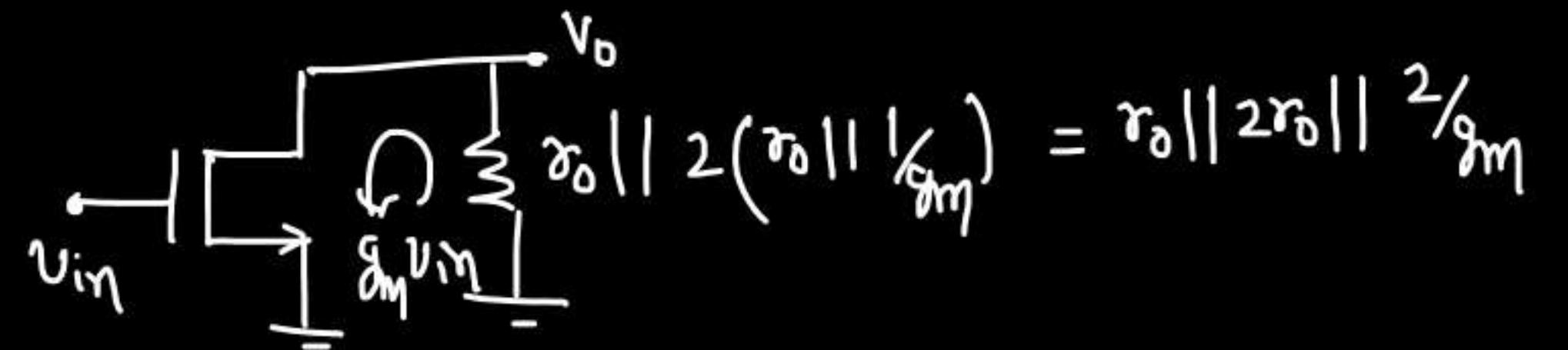

*
$$\frac{V_o}{V_{in}} = -g_m \left[\frac{2}{g_m} \parallel \frac{2r_o}{3} \right]$$

PrepFusion

⇒ Current Source :-

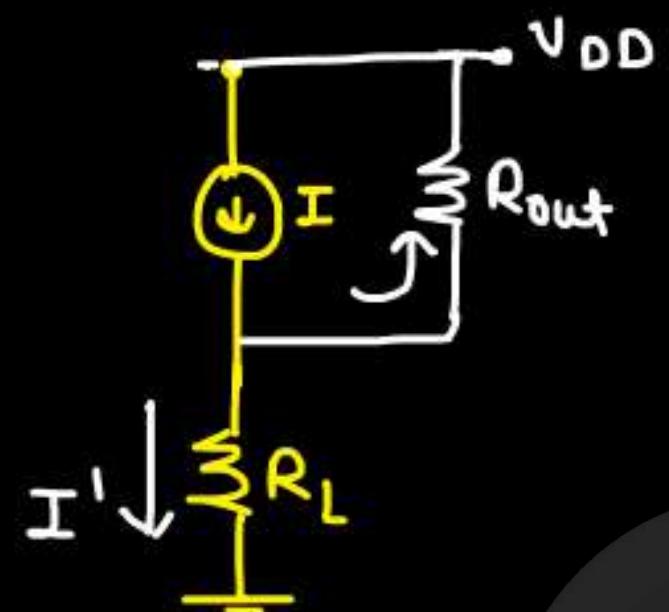

$$I' < I$$


if $R_{out} \rightarrow \infty$

$$I' \rightarrow I$$

PreFusion

more $R_{out} \Rightarrow$ better current source

Making current source from MOS:-

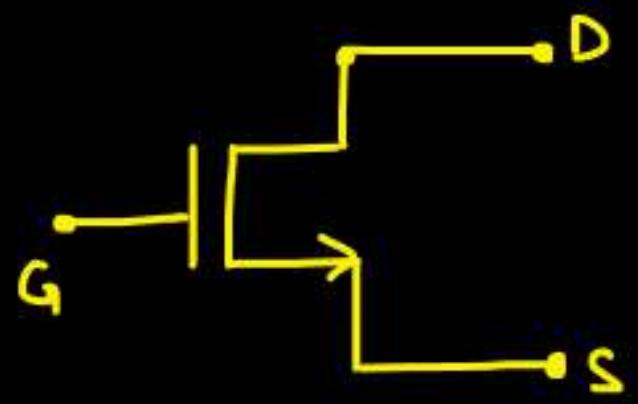


$$\gamma_{01} > \gamma_{02} > \gamma_{03}$$




↓

Bent current source

$M_1 \rightarrow$ Bent current source




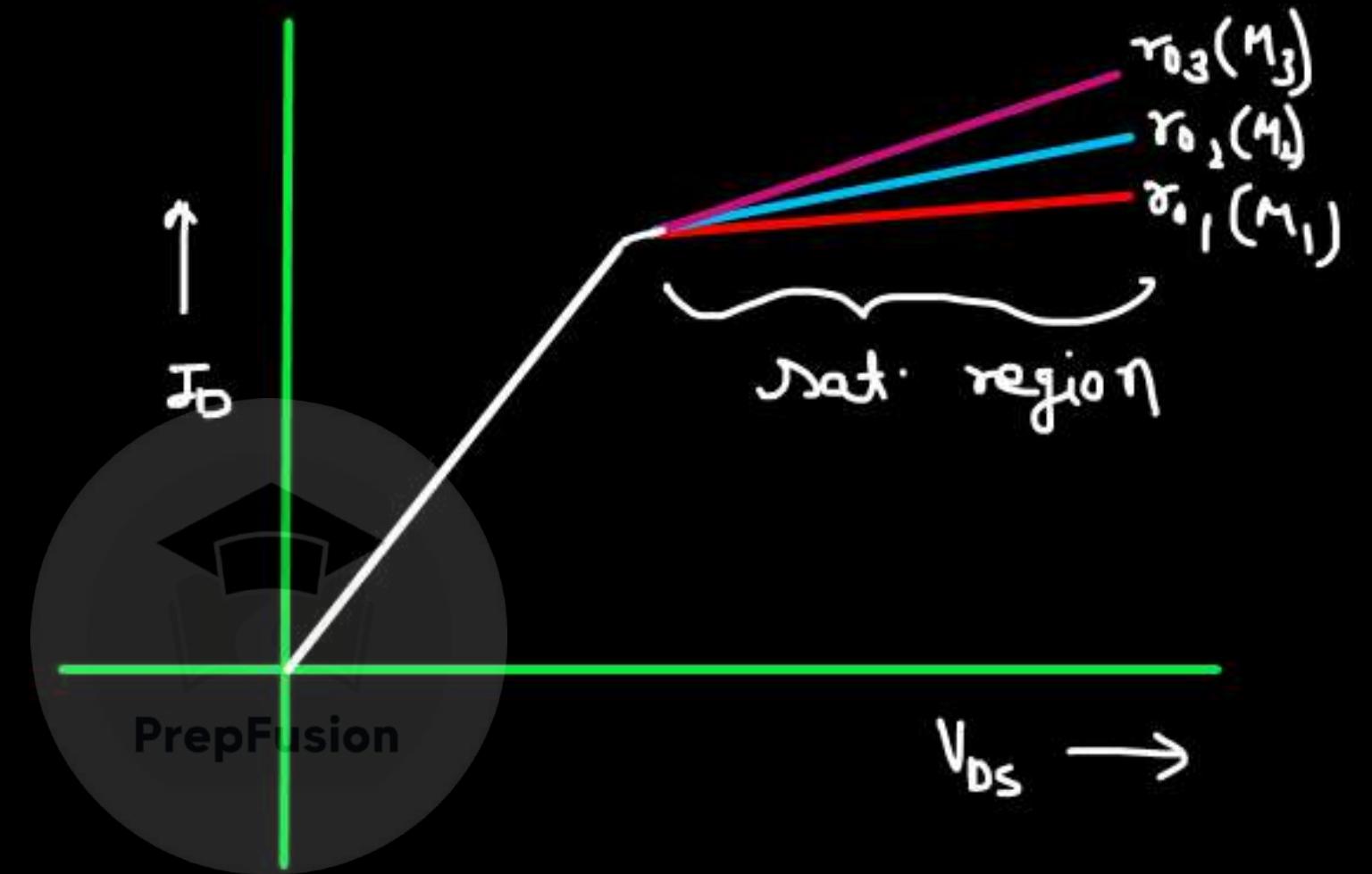


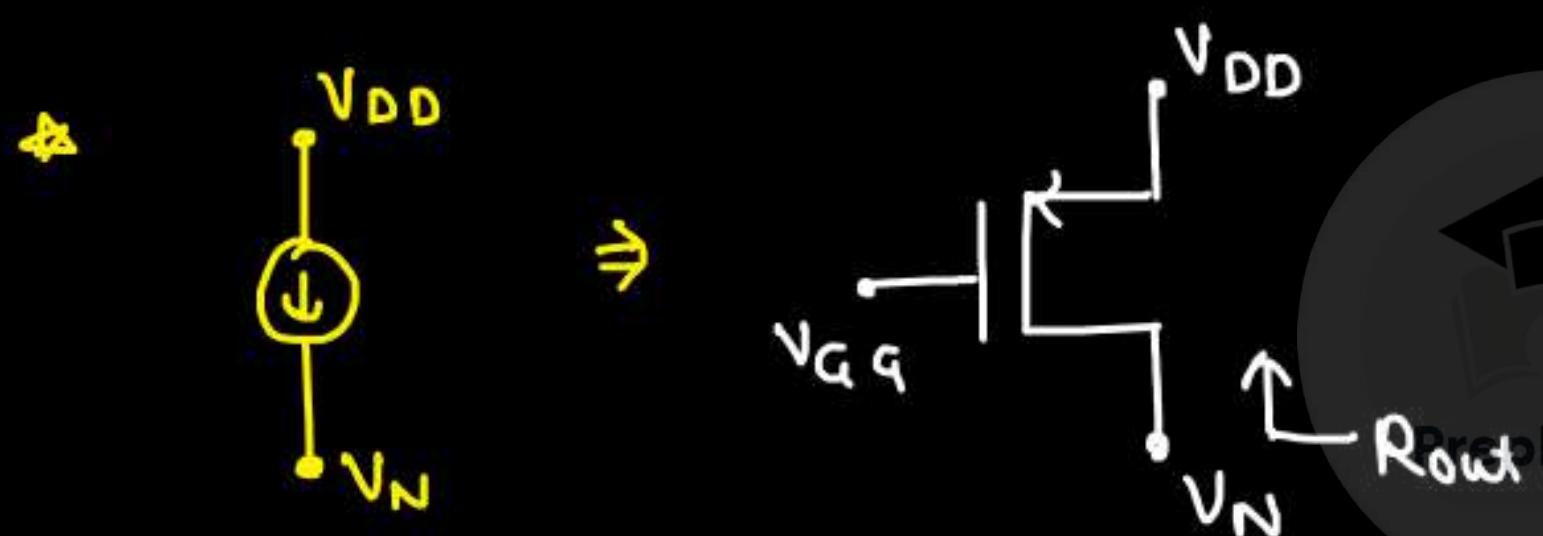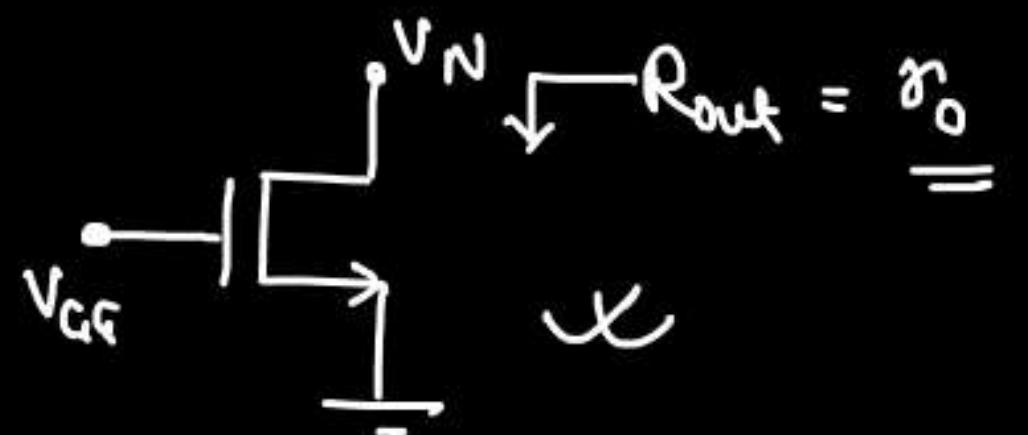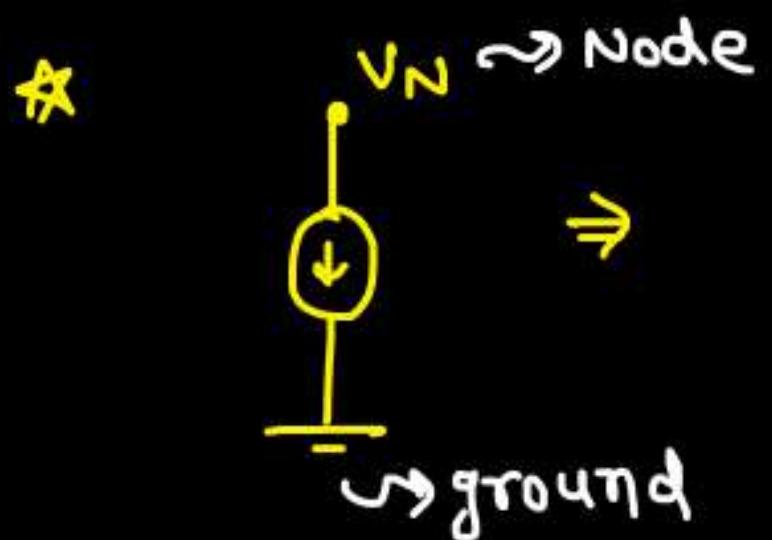For using MOS as a current source,
it should be biased in sat. region.





Node to ground \rightarrow NMOS
Supply to Node \rightarrow PMOS

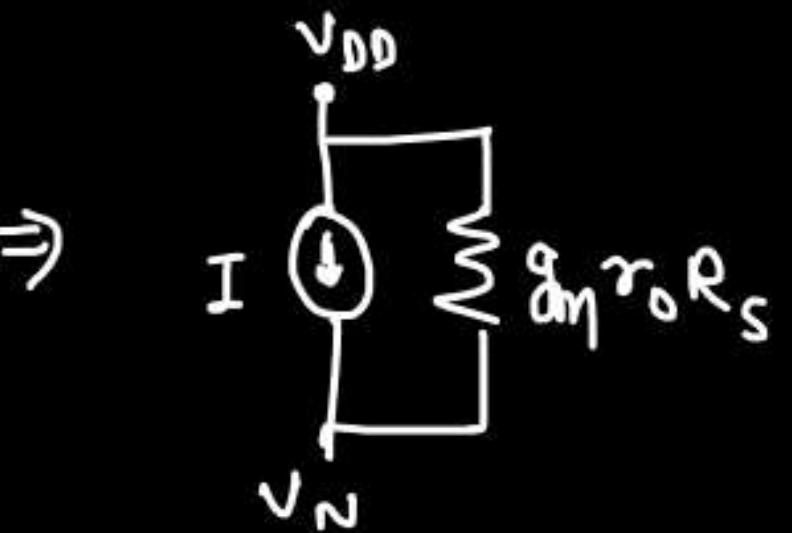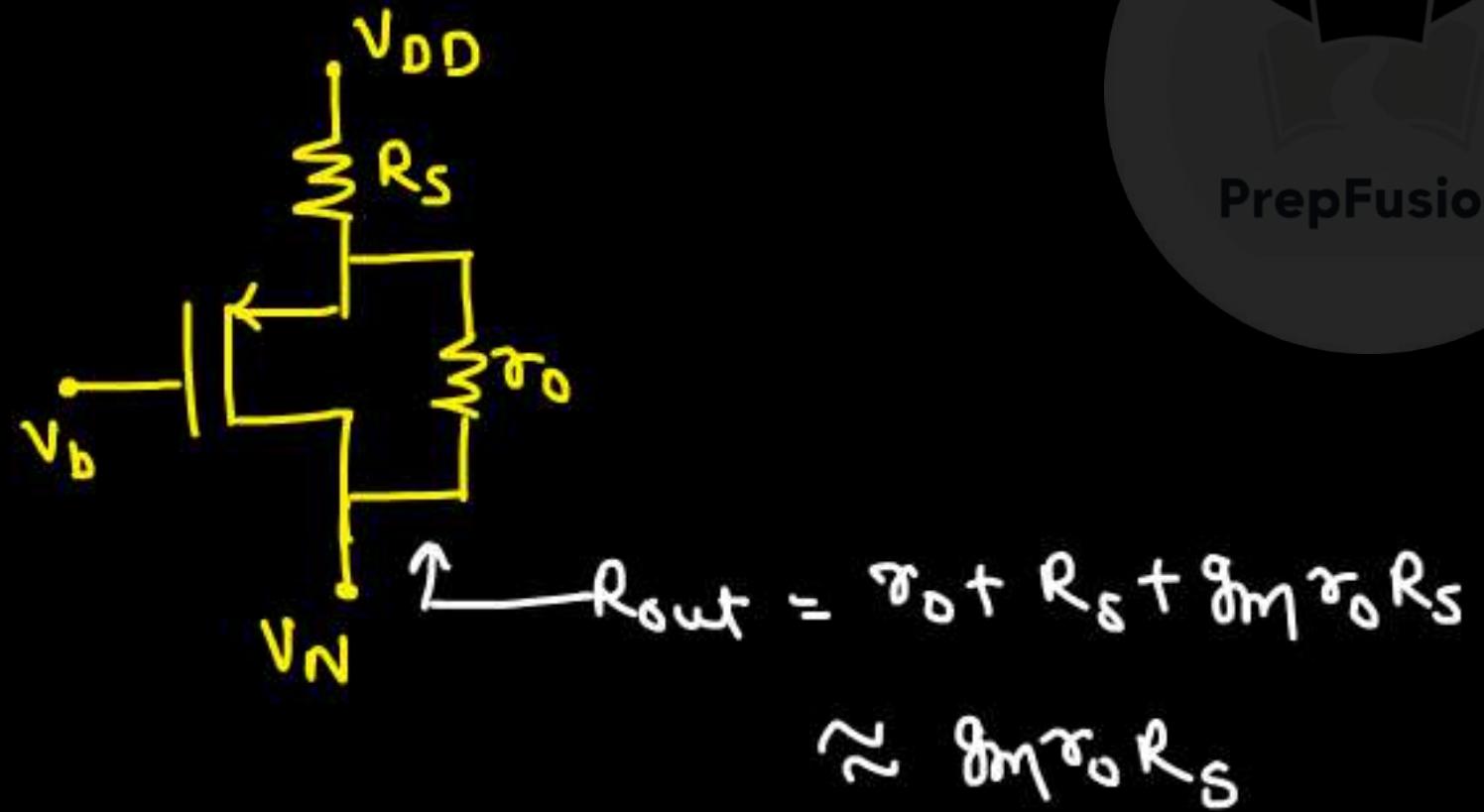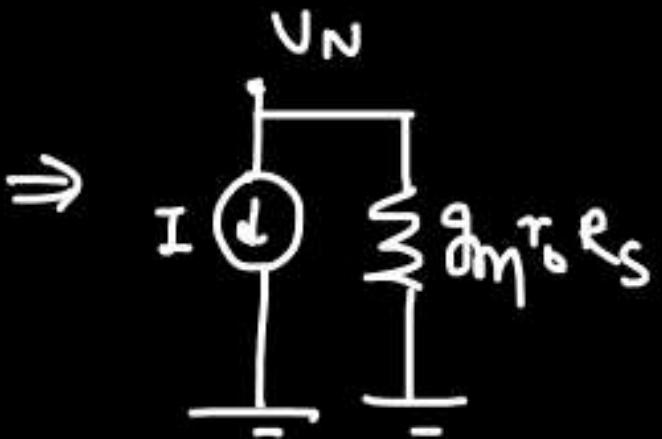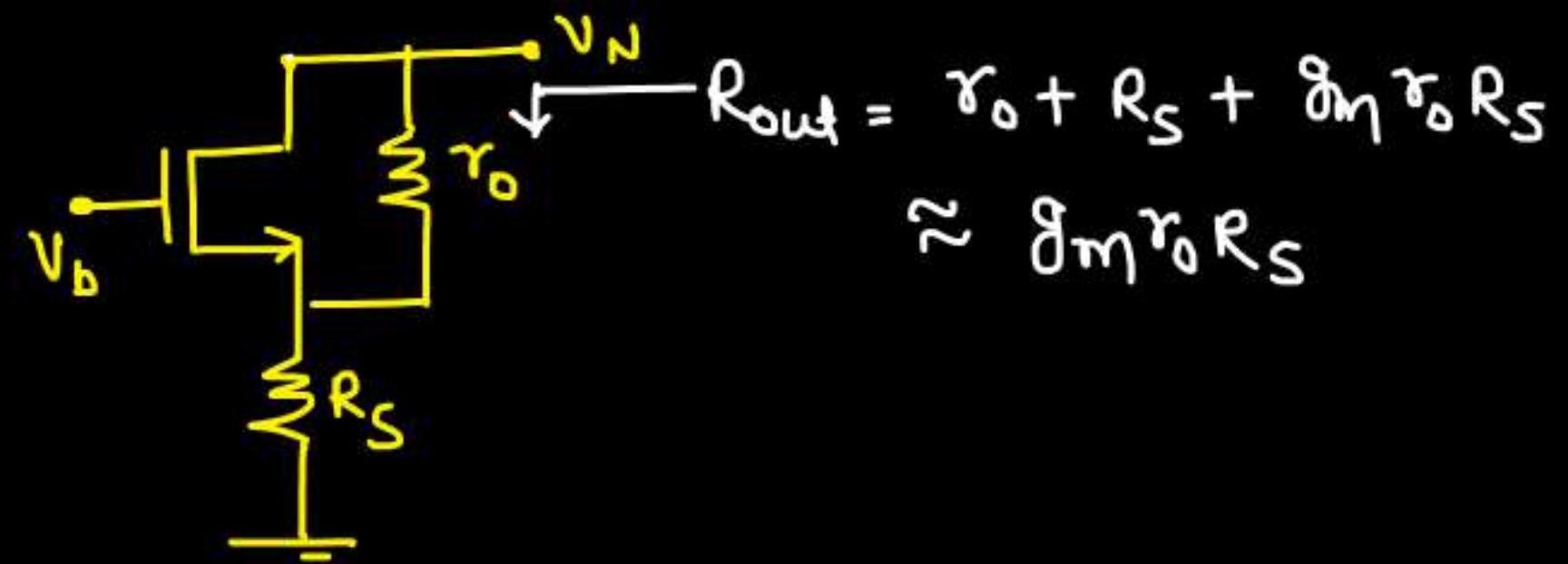\Rightarrow what if I need a Higher o/p impedance?




Cascode Current Source:-

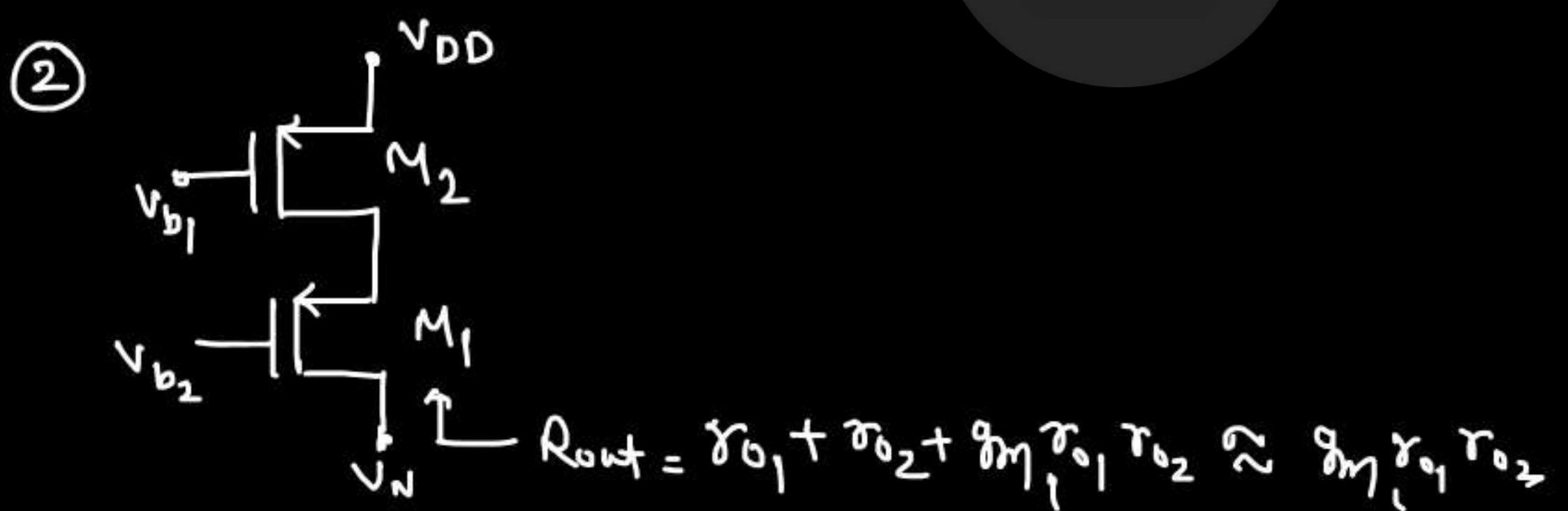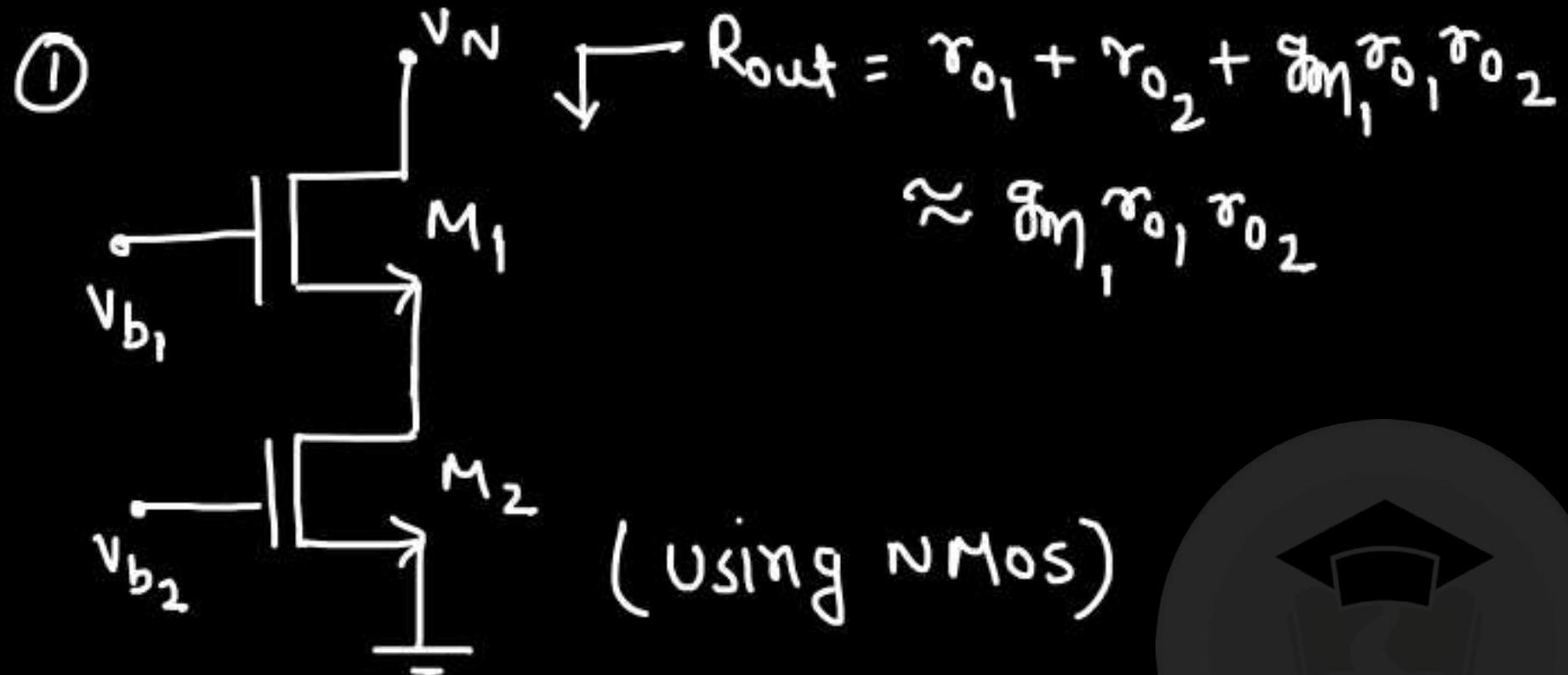


Summary:-

①

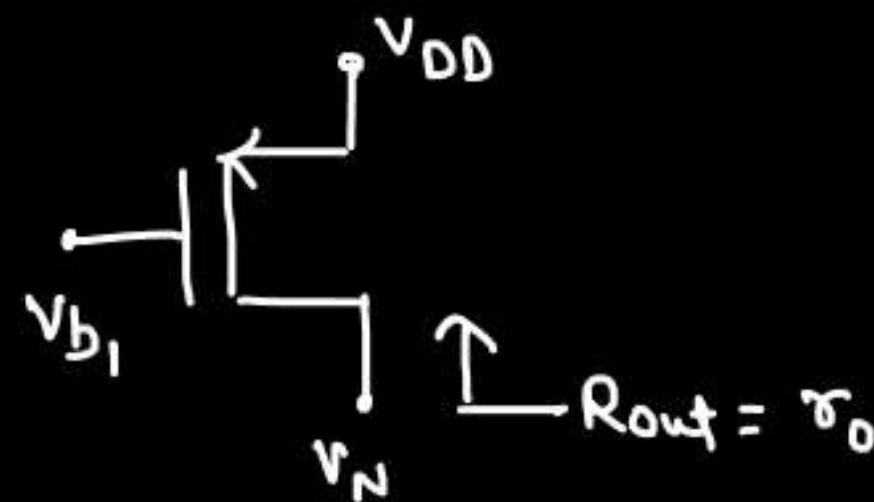


$$R_{out} = \tau_0$$

①

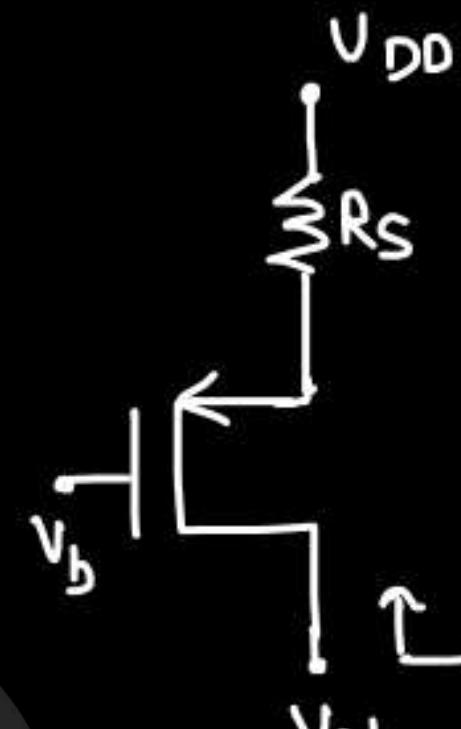

$$R_{out} \approx g_m \tau_0 R_S$$

②

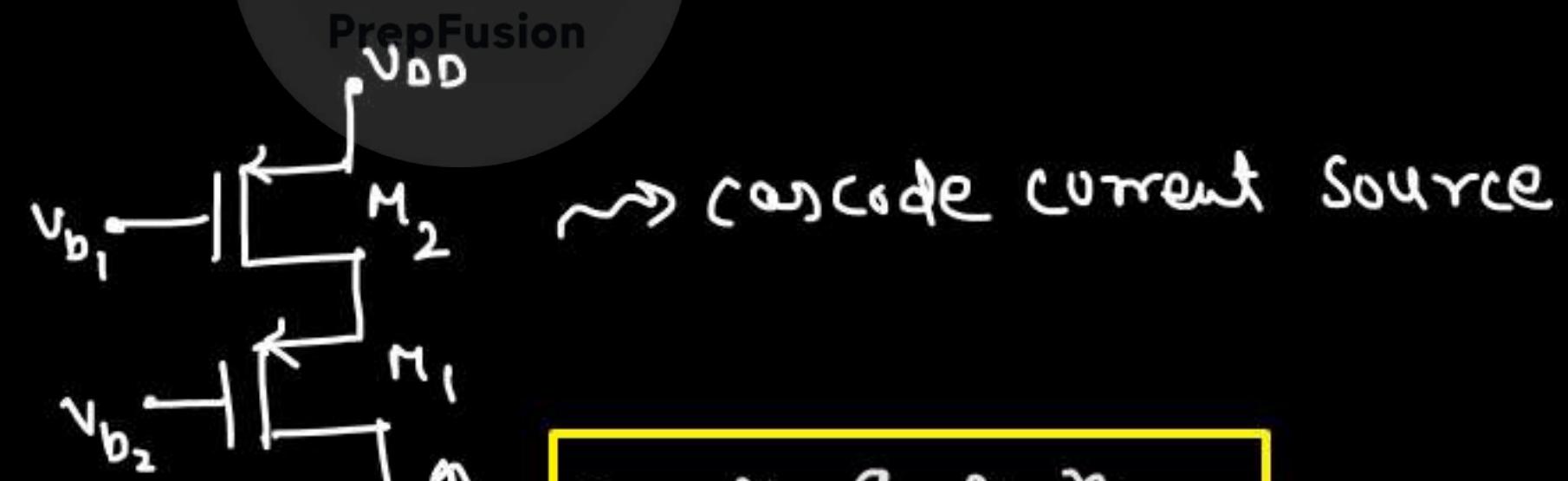

→ cascode current source

$$R_{out} \approx g_{M_1} \tau_{01} \tau_{02}$$


③

PrepFusion


②




⇒

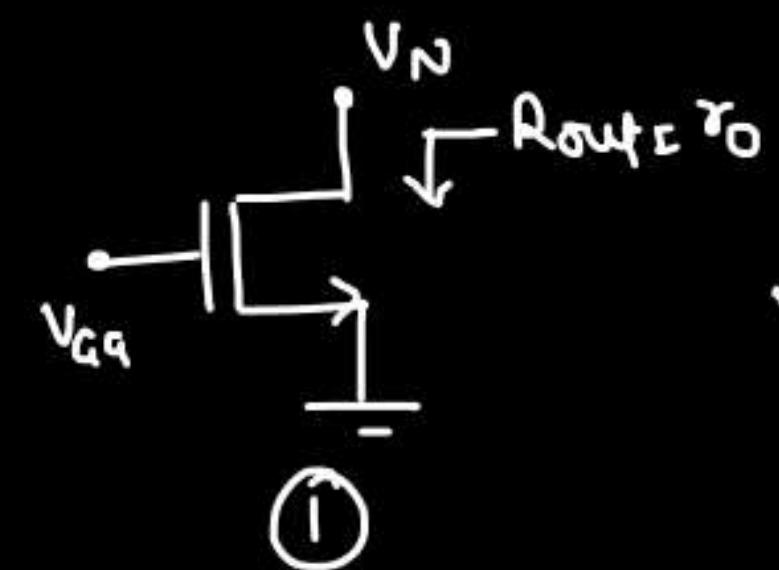

①

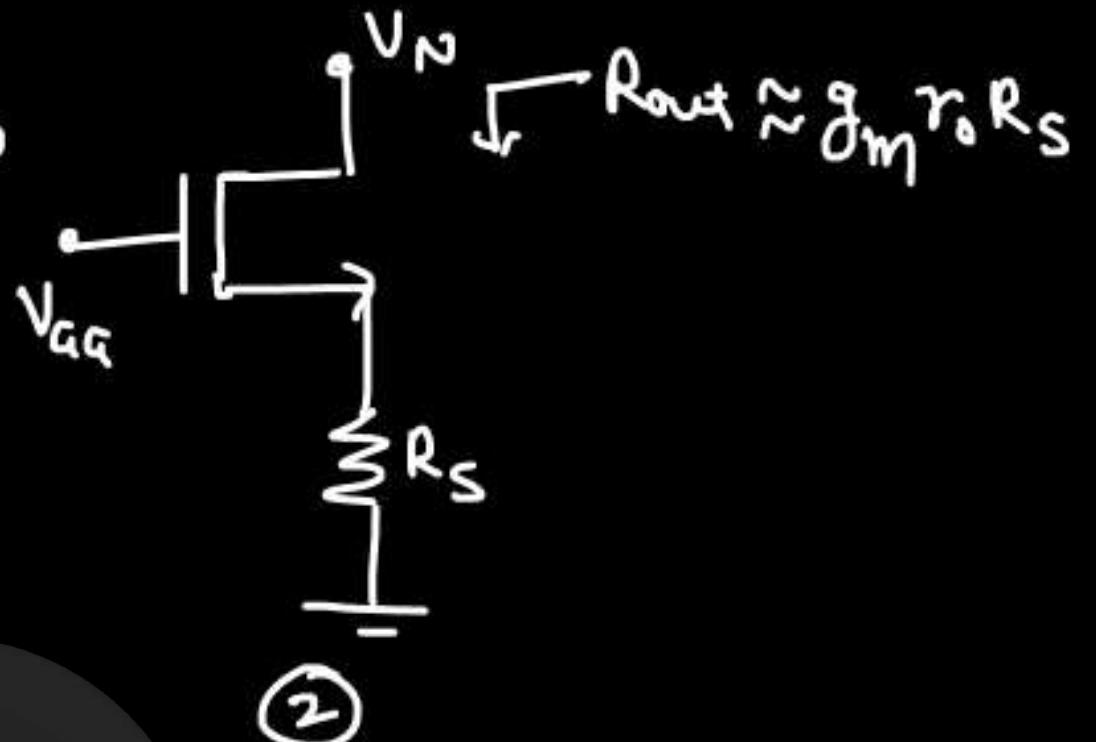

②

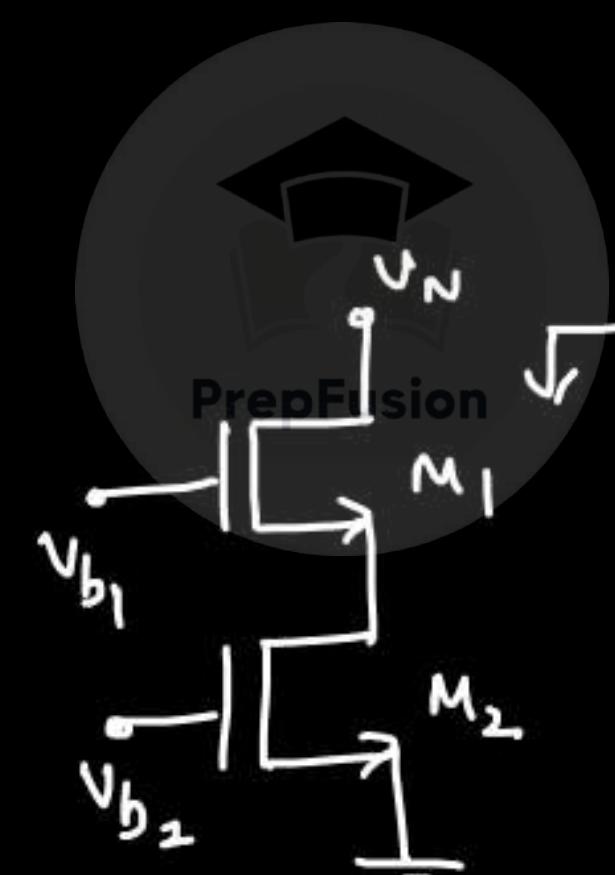


PrepFusion

$$R_{out} \approx g_m r_0 r_{02}$$

Q. Design a common source amplifier with cascode current source in load. Write the small signal gain.
[Using both PMOS & NMOS]

→ CS Amplifier using NMOS, with current source in load:-

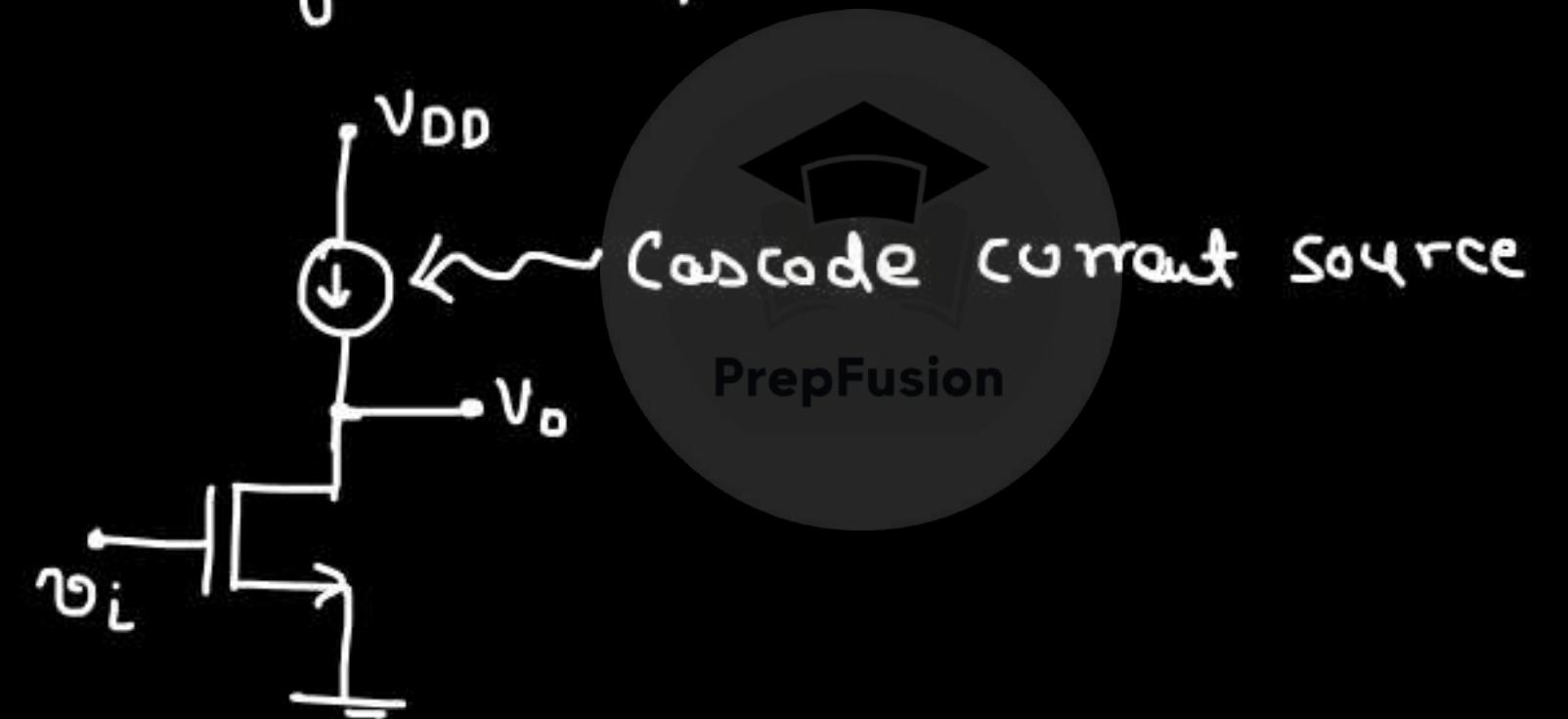


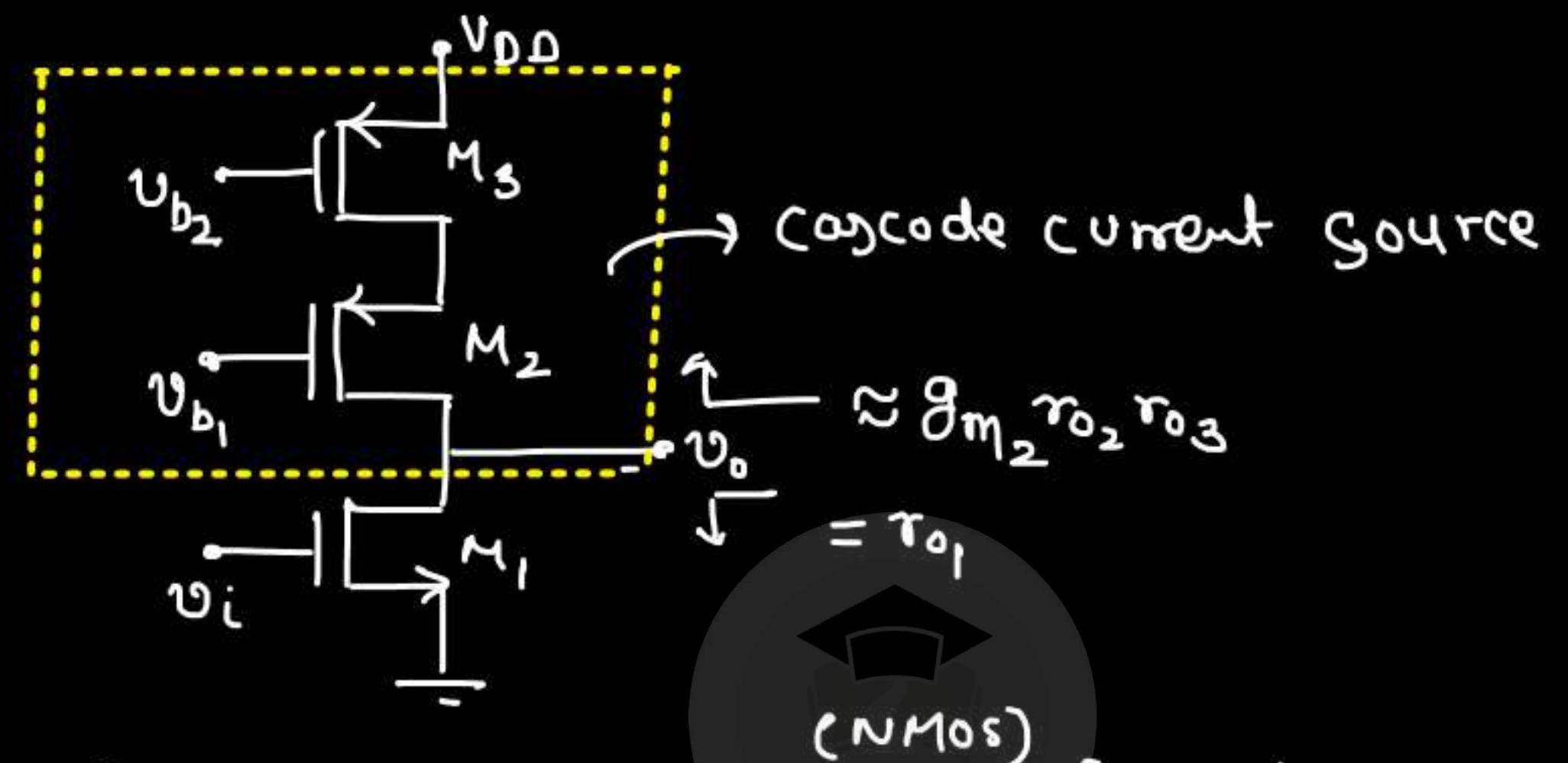


fig → common source amplifier with cascode current source in (cas.) (PMOS)


$$\Delta V \approx -g_m_1 [r_{o_1} || g_m_2 r_{o_2} r_{o_3}]$$

$$\approx -g_m_1 r_{o_1}$$

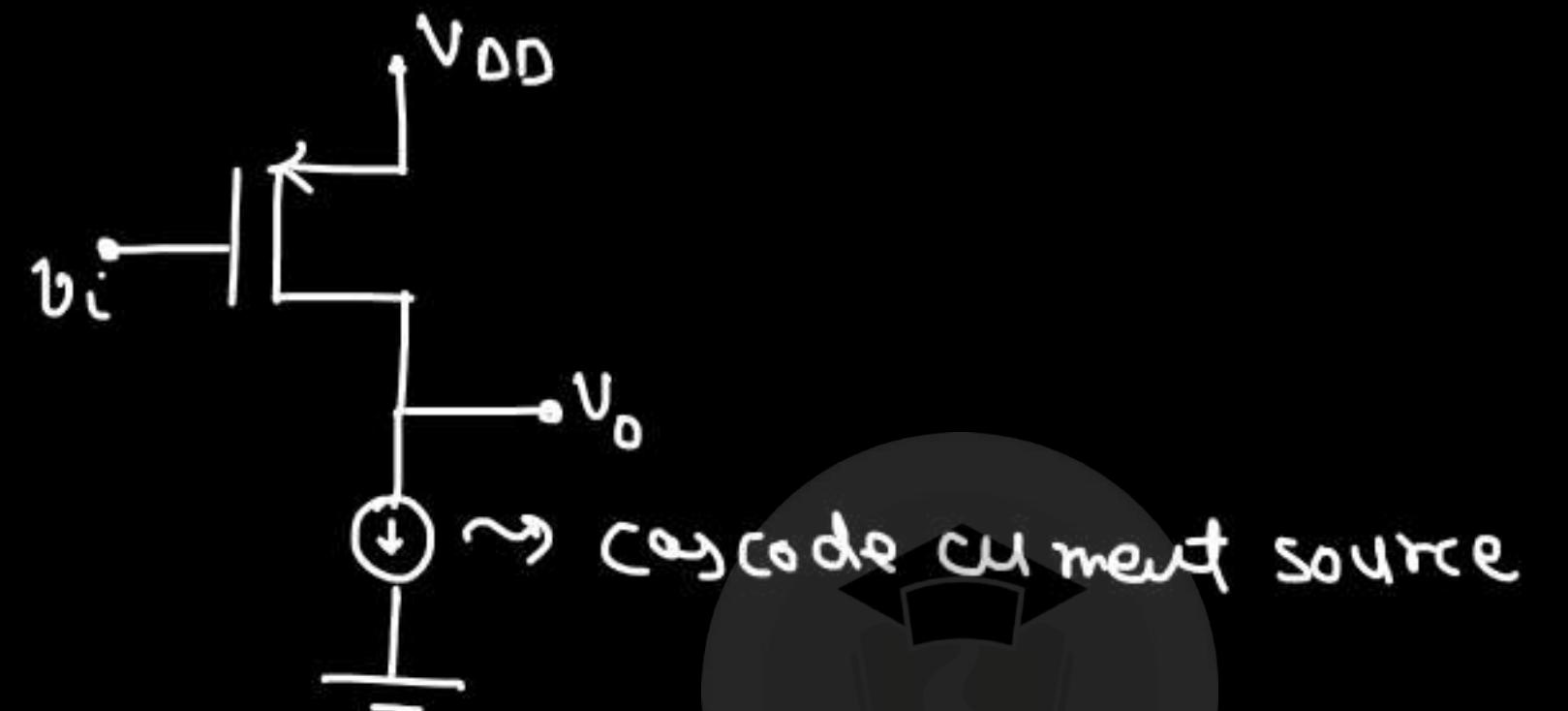⇒ CS amplifier using PMOS with current source in load.



PrepFusion

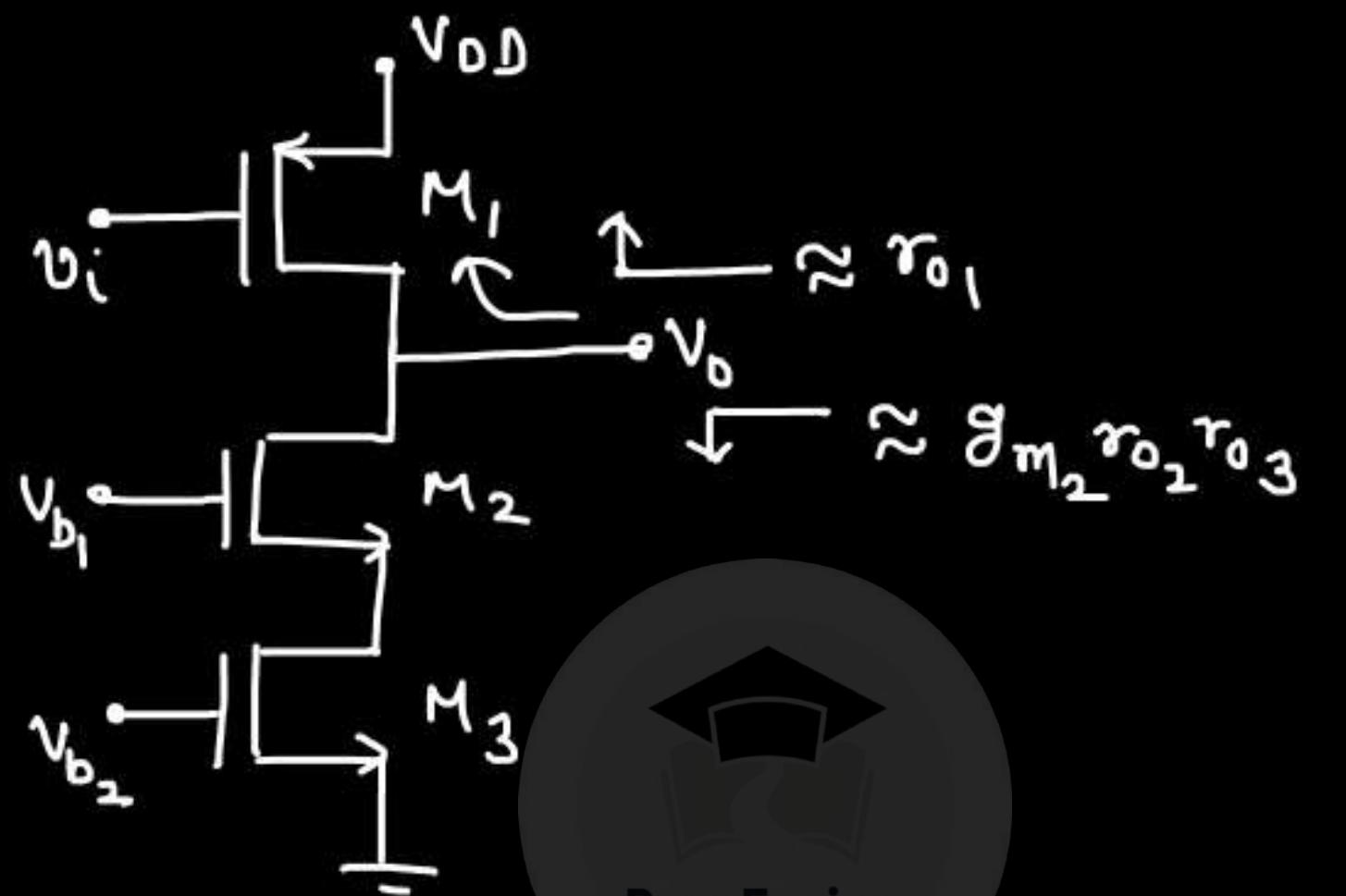

PrepFusion

$$\Delta V = -g_m_1 [r_{o_1} || g_m_2 r_{o_2} r_{o_3}] \approx -g_m_1 r_{o_1}$$

fig → common source amplifier with cascode current source
in load.
(PMOS)

Target :-

Building a High gain Amplifier.

$$A_V = G_m R_{out}$$

keeping G_m constant, increase R_{out}


⇒ The design we made in the previous problem.

$$R_{out} = r_{o1} \parallel g_m r_{o2} r_{o3}$$

Preprusion

↓
increase $R_{out} =$

Cascode Amplifier :-

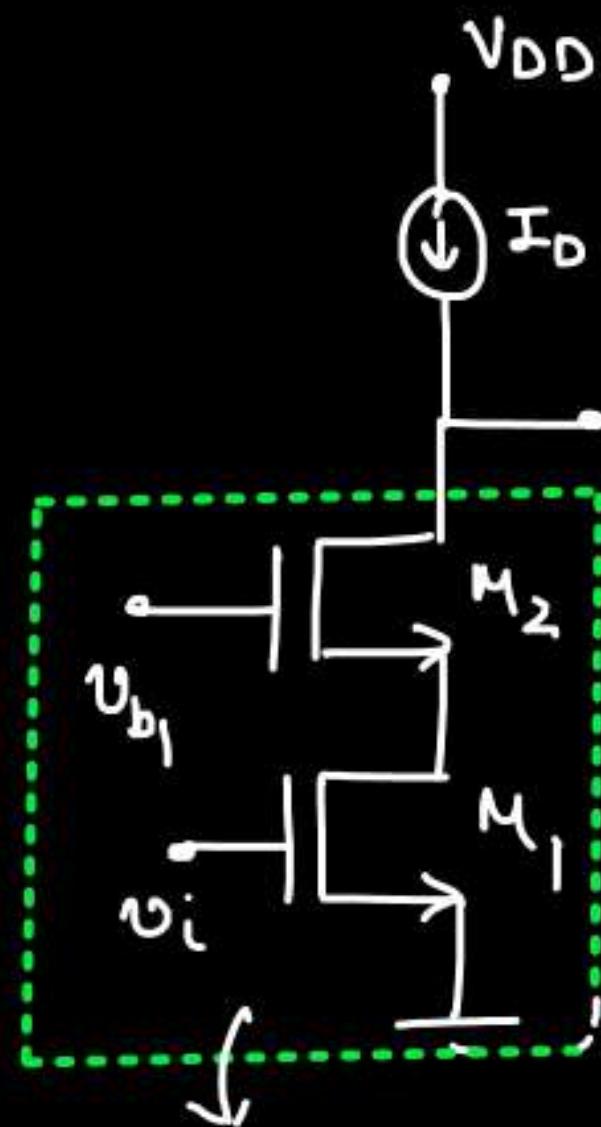


**Cascode
Amplifier
(NMOS)**

$$\boxed{A_V \approx -g_m M_1 g_m M_2 r_{o2} r_{o1}}$$



$$G_m \approx -g_m M_1$$
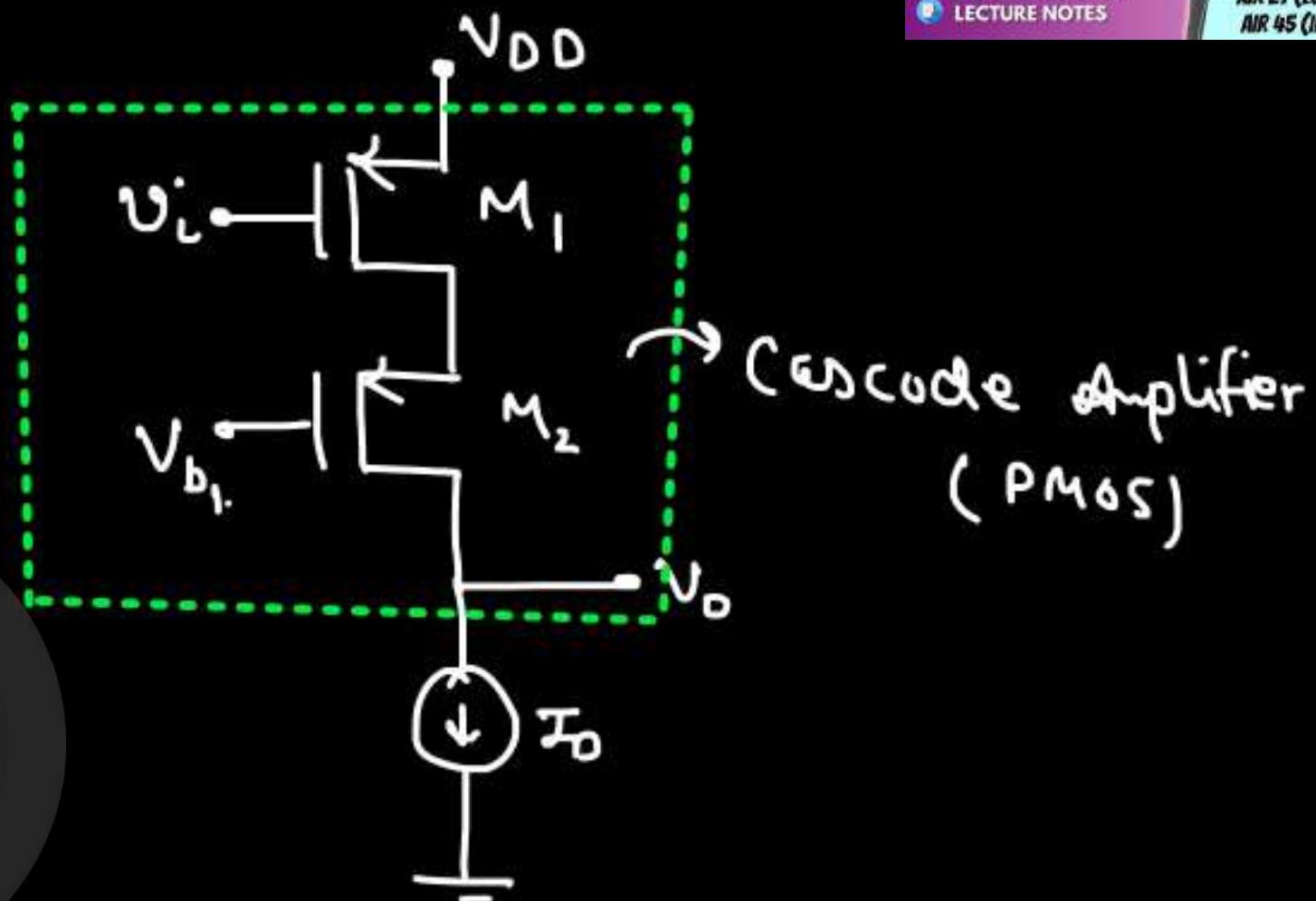
$$R_{out} \approx g_m M_2 r_{o2} r_{o1}$$



$$\boxed{A_V \approx -g_m M_1 g_m M_2 r_{o2} r_{o1}}$$

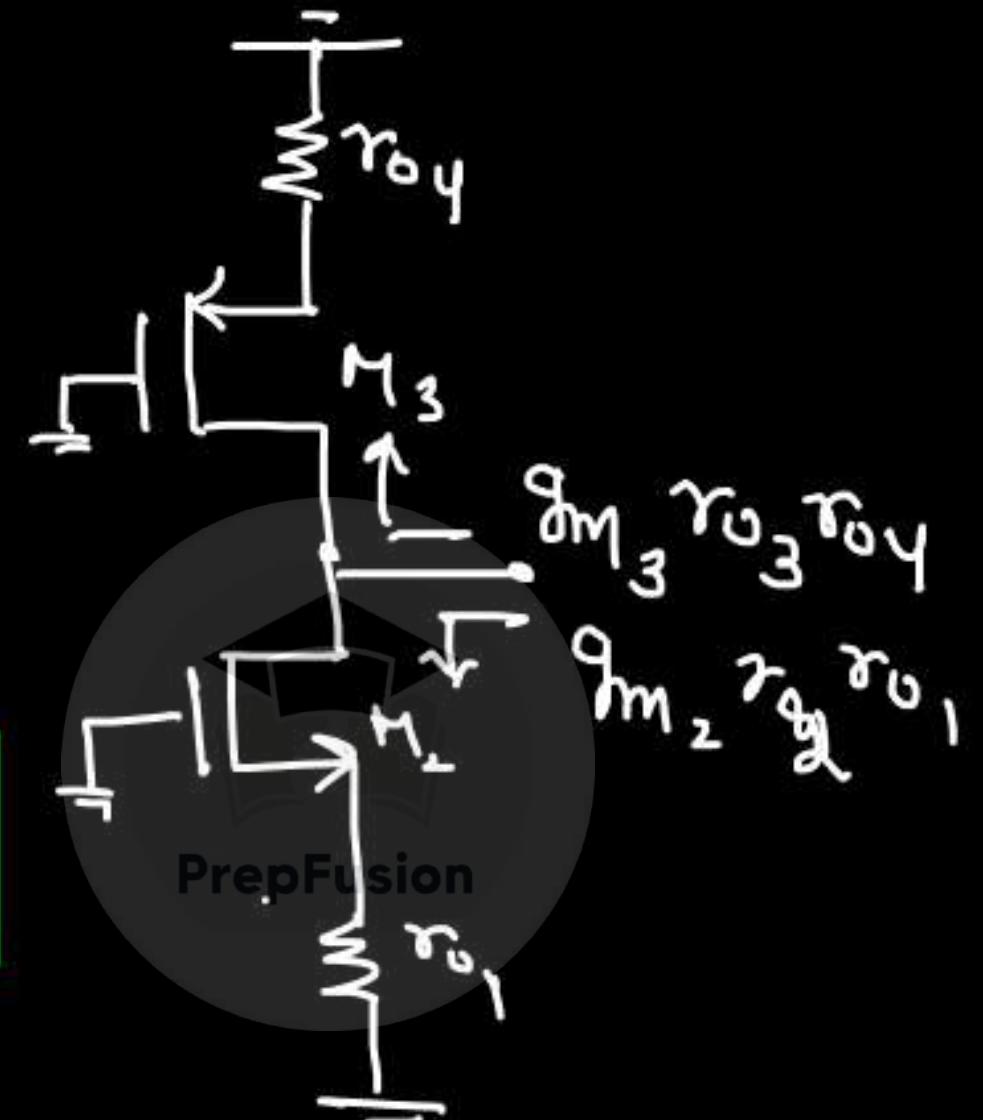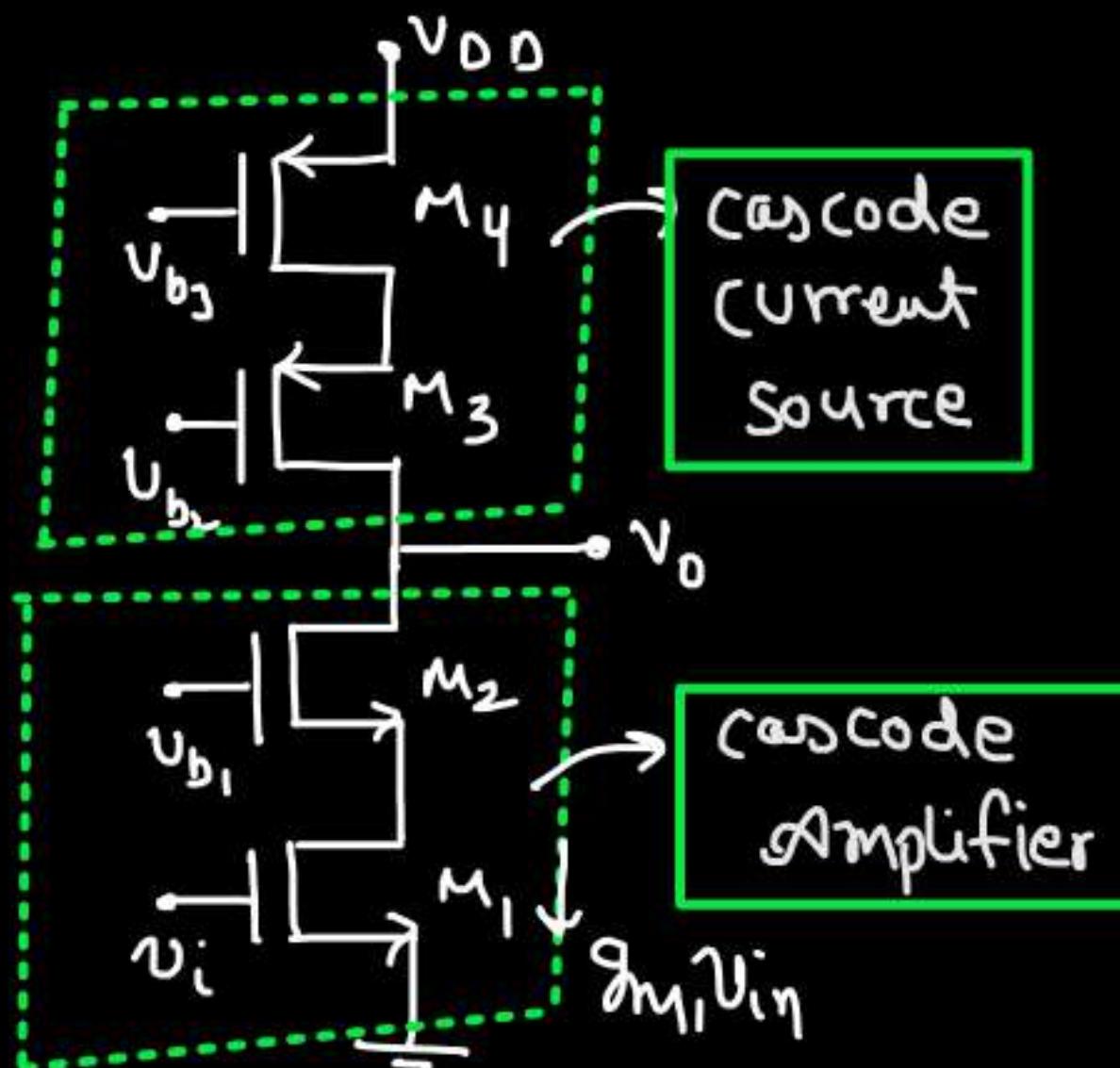
Cascode Amplifier with cascode current source :-



$$g_m \approx -g_{m1}$$

$$R_{out} \approx g_{m3} r_{o3} r_{o4} \parallel g_{m2} r_{o2} r_{o1}$$

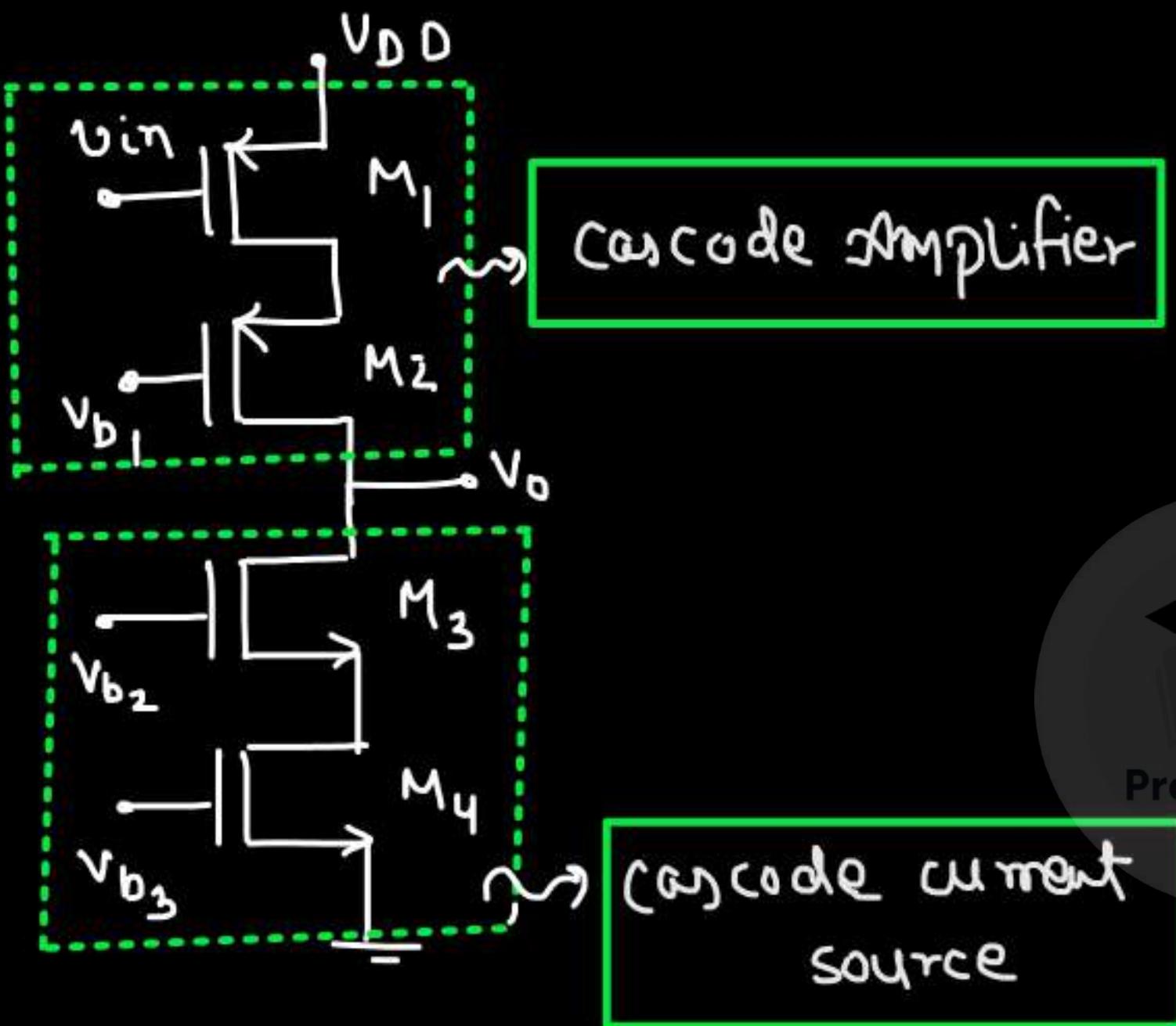
$$\omega_V \approx -g_{m1} [g_{m3} r_{o3} r_{o4} \parallel g_{m2} r_{o2} r_{o1}]$$



$$G_m \approx -g_{m_1}$$


$$R_{out} \approx g_{m_2} r_{o_2} r_{o_1} || g_{m_3} r_{o_3} r_{o_4}$$

$$\Delta V = -g_{m_1} [g_{m_2} r_{o_2} r_{o_1} || g_{m_3} r_{o_3} r_{o_4}]$$

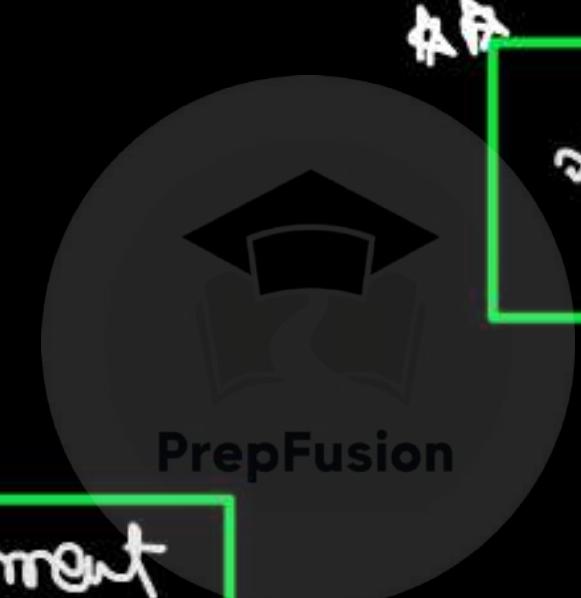





What if :-

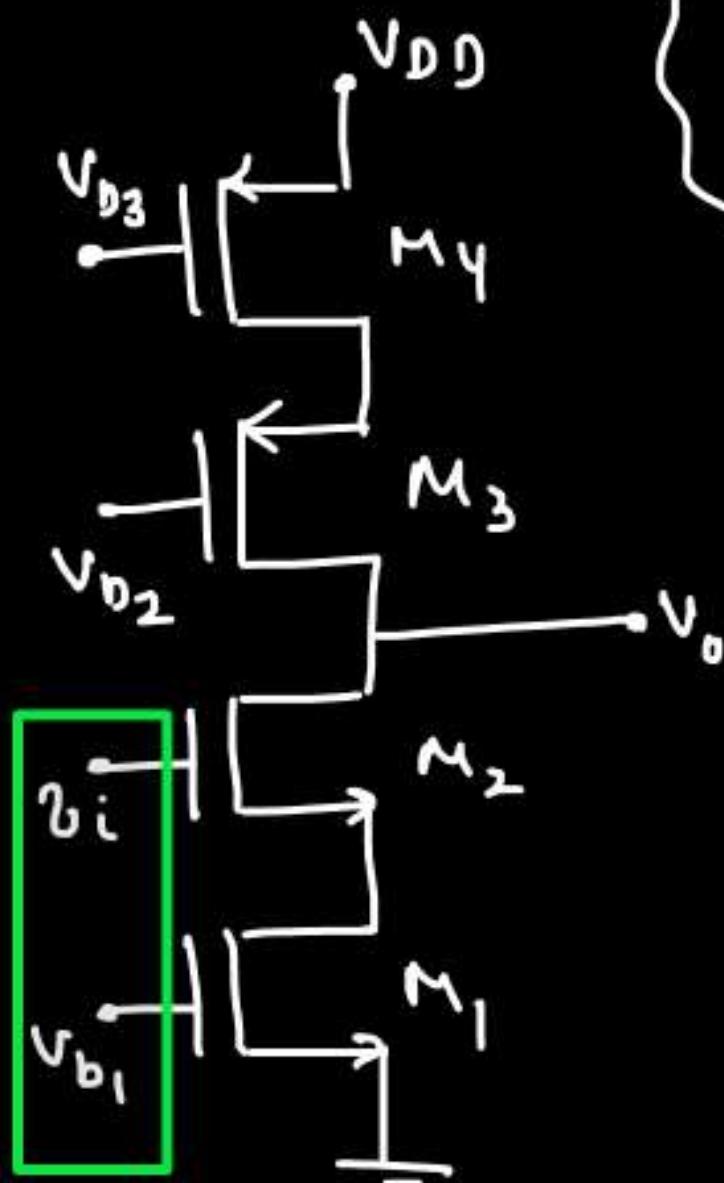


$$R_{out} \approx g_m r_o \parallel g_m r_o$$

Same as before

$G_m = ?$

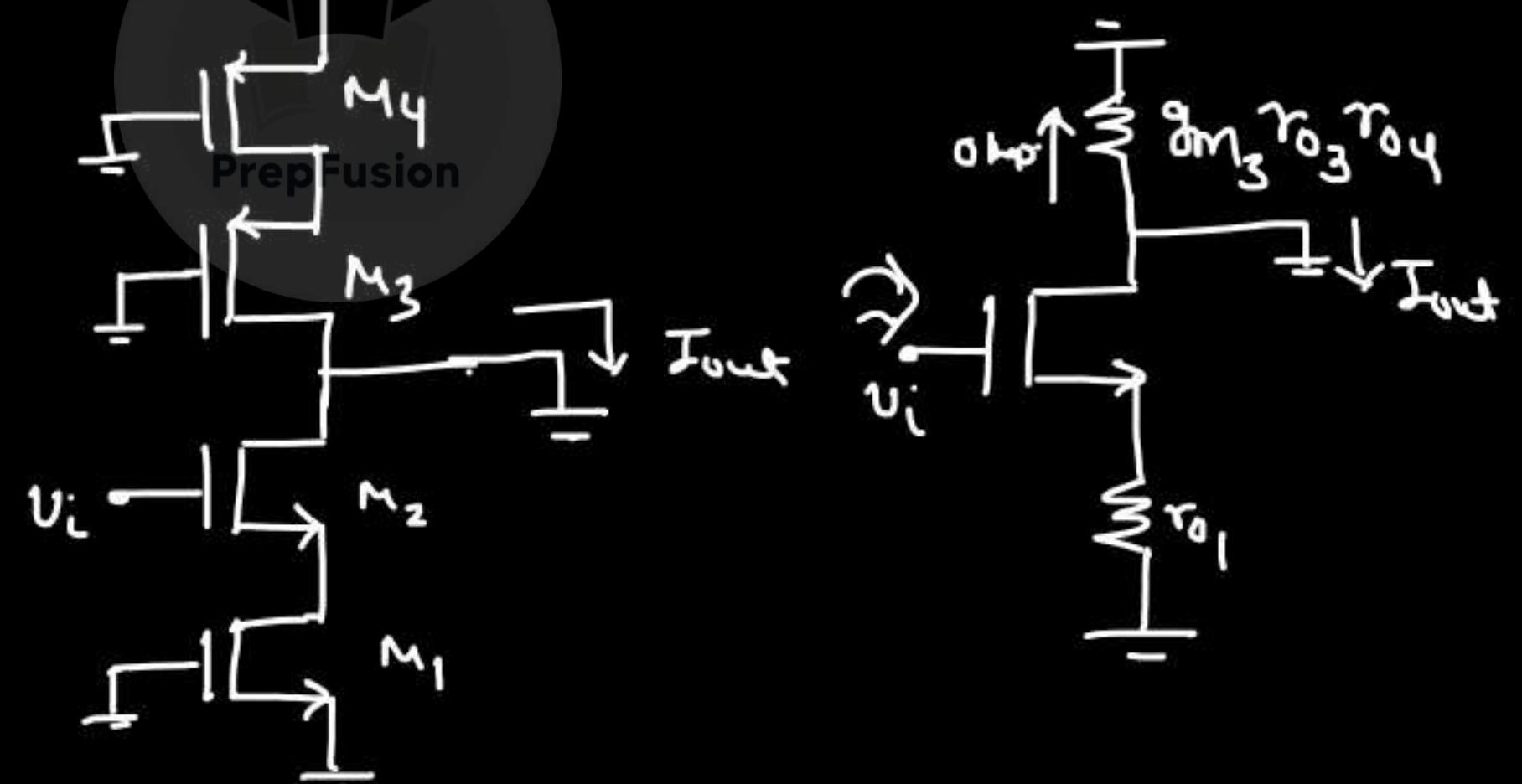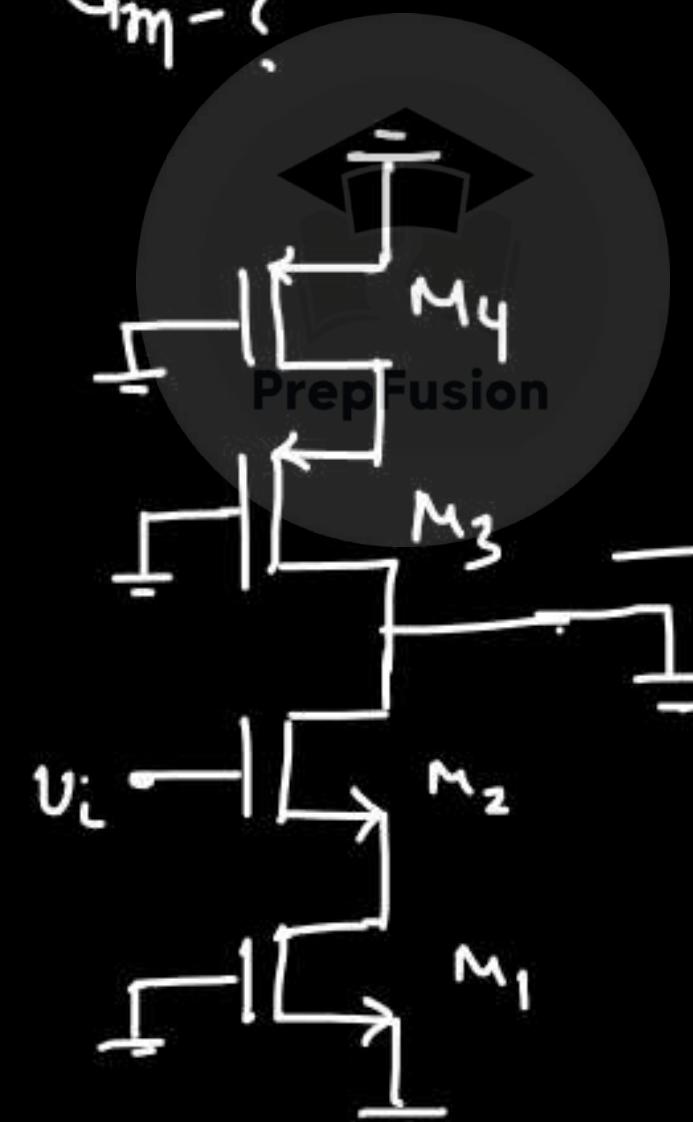

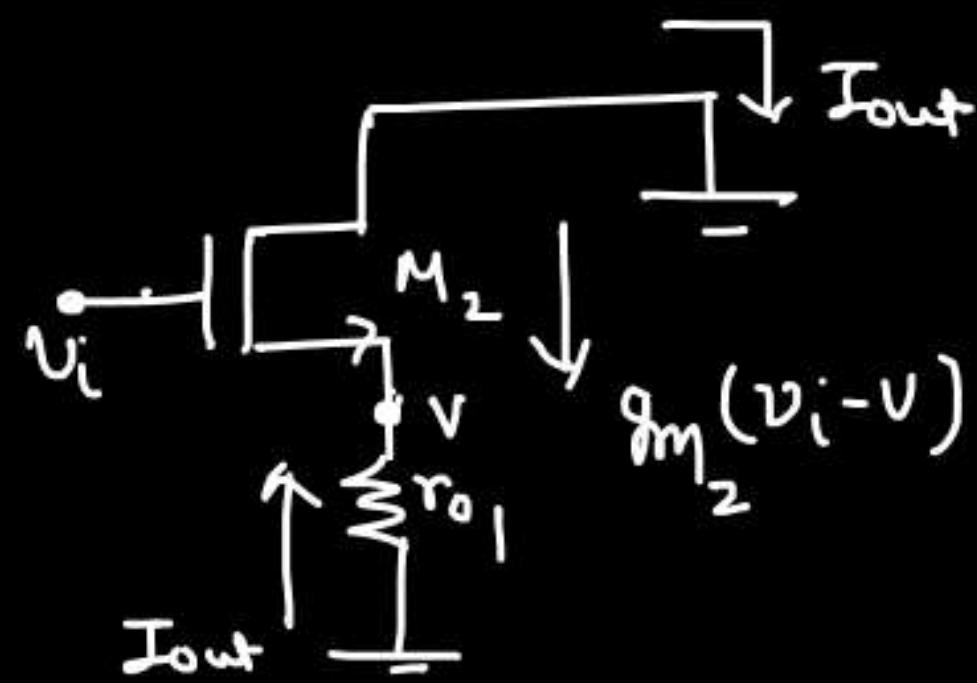

$$I_{out} = -g_m_2(v_i - v)$$

$$\frac{v}{r_{o1}} = -I_{out}$$

$$v = -I_{out} r_{o1}$$

$$I_{out} = -g_m_2(v_i + I_{out} r_{o1})$$

$$I_{out} = -g_m_2 v_i - g_m_2 r_{o1} I_{out}$$


gain $\approx -\frac{g_m_2}{1+g_m_2 r_{o1}} [g_m_3 r_{o3} r_{o4} || g_m_2 r_{o2} r_{o1}]$

$$\frac{I_{out}}{v_i} = G_m = \frac{-g_m_2}{1+g_m_2 r_{o1}} \rightsquigarrow G_m \text{ is reduced}$$

Gain is reduced [then cascode amplifier]


Cascode Amp. v/s Common Source Amp. with degeneration:-

① Cascode Amp. (NMOS)

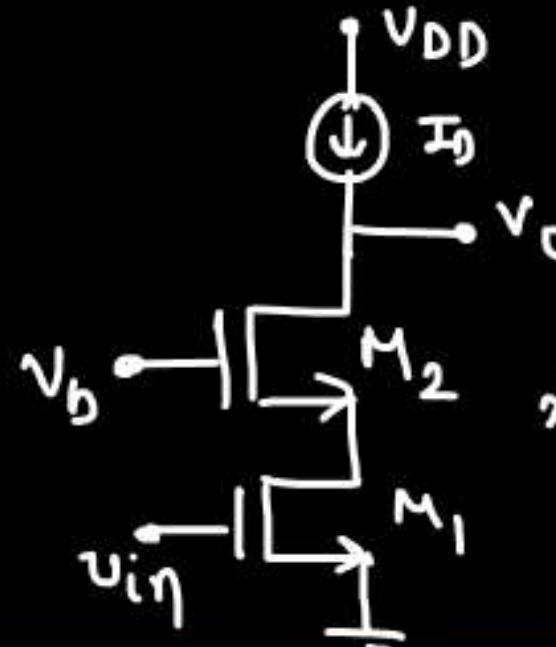


$$A_V = -g_{m_1} [g_{m_2} r_{o_2} r_o]$$

③ Cascode Amp. (PMOS)

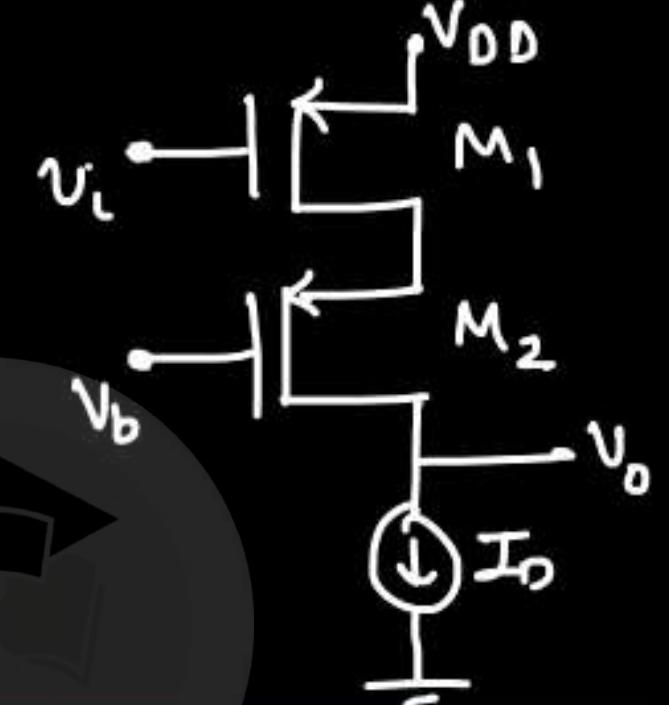


② CS with degen. amp. (NMOS)

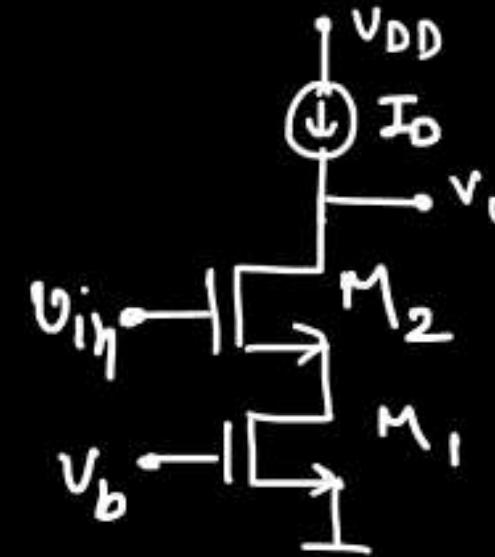

$$A_V = \frac{-g_{m_2} [g_{m_2} r_{o_2} r_o]}{1 + g_{m_2} r_{o_1}}$$

④ CS with degen. amp. (PMOS)

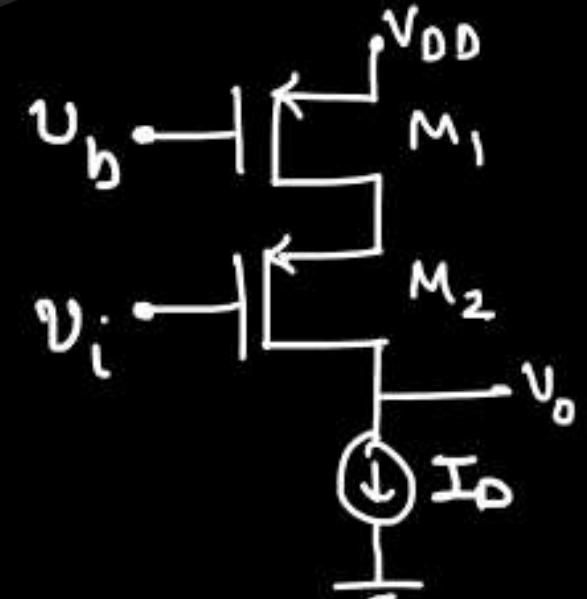


N.B.

**Cascode Amplifier :- Common Source Amp. in series
with common Gate Amp.**





⇒ Using MOS as a current source:-

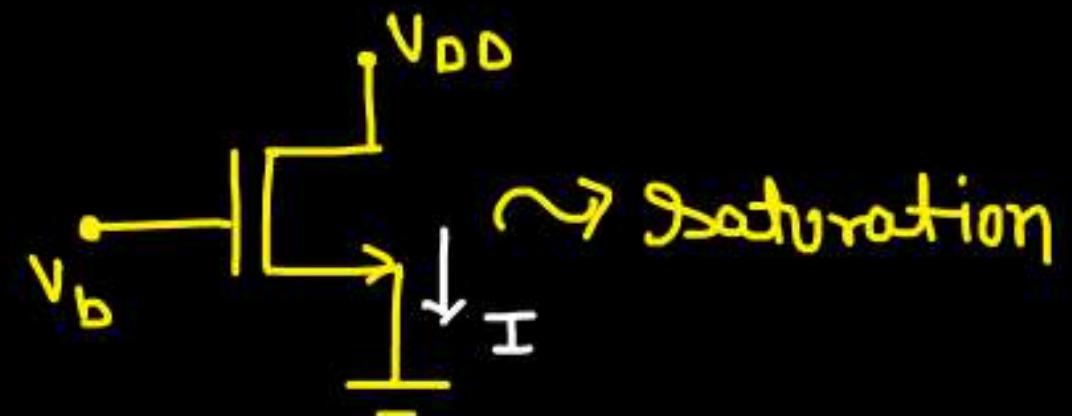

$$I = \frac{\mu_n C_{ox} W}{2L} (V_b - V_T)^2$$

$$I = \left(\frac{\mu_n C_{ox} W}{2L} \left[\frac{R_2}{R_2 + R_1} V_{DD} - V_T \right] \right)^2$$

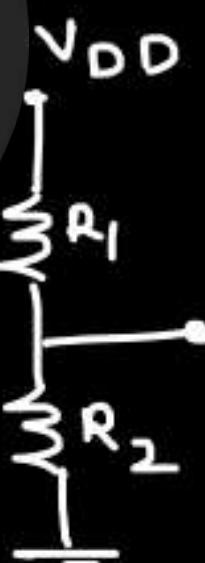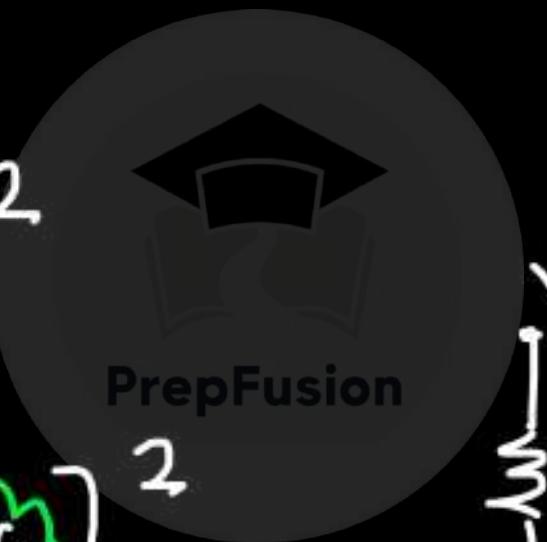Temp. dependent
Supply dependent
Temp. dependent



$$V_b = \frac{R_2}{R_2 + R_1} V_{DD}$$

⇒ **I ≠ constant**

→ for making a current source which is independent of supply and Temp., we need to use "Bandgap variation circuit.

[OUT OF THE
Scope of this
course]


Golden current source \Rightarrow Constant current Source



$$I_{\text{golden}} = I_{\text{ref}}$$


Current Mirror ckt:-

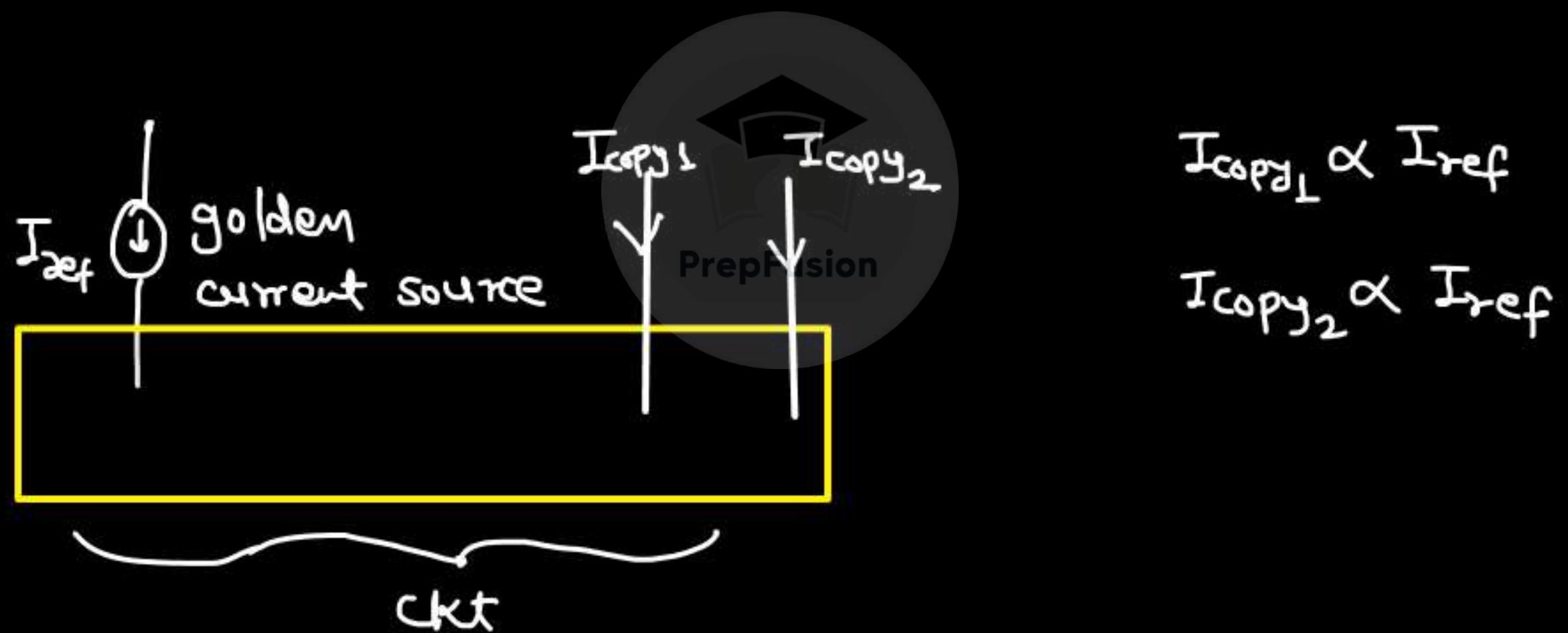With the help of golden current source, we will generate other current sources which are identical to golden current source.



Try-L:-

Using a resistor:-

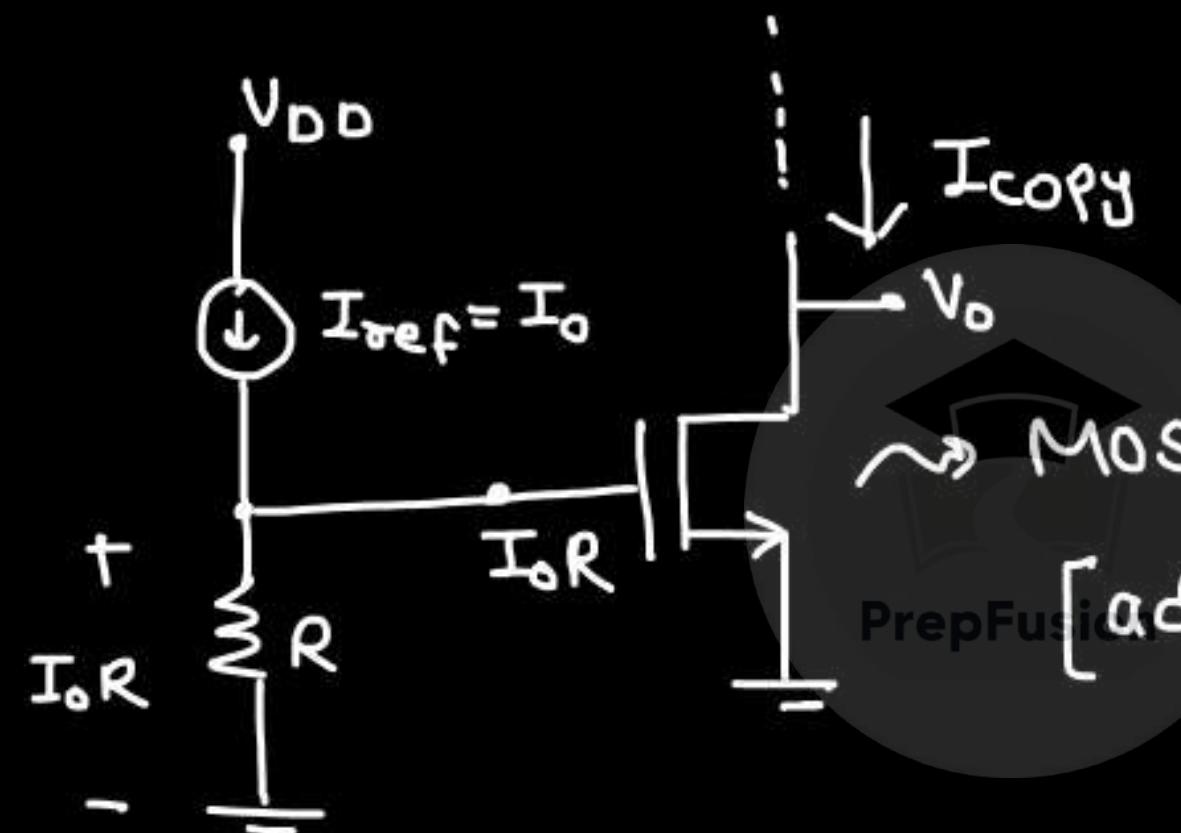


→ MOS is sat region
[adjust V_o such that Mos is working in sat.]

$$I_{\text{copy}} = \frac{k n F_s k_w}{2L} \left[I_0 R - \frac{V_o}{2} \right]^2$$

→ Temp dependent

Try - 2 :-

Using diode connected Transistor :-

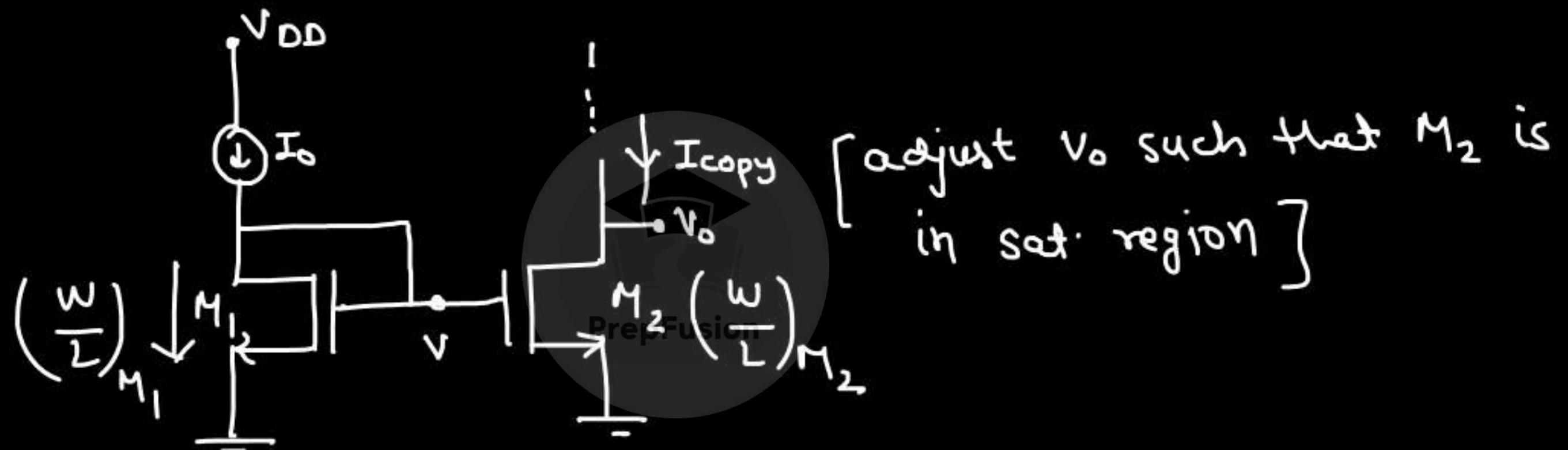

$$I_0 = \frac{\mu_n C_{ox}}{2} \left(\frac{w}{L}\right)_{M_1} (V - V_T)^2$$

$$V = \sqrt{\frac{2I_0}{\mu_n C_{ox} \left(\frac{w}{L}\right)_{M_1}}} + V_T \quad \text{--- (1)}$$

$$I_{\text{copy}} = \frac{\mu_n C_{\text{ox}}}{2} \left(\frac{w}{L}\right)_{M_2} [V - V_T]^2$$

$$= \frac{\mu_n C_{\text{ox}}}{2} \left(\frac{w}{L}\right)_{M_2} \left[\sqrt{\frac{2I_0}{\mu_n C_{\text{ox}} \left(\frac{w}{L}\right)_{M_1}}} + V_T - V_T \right]^2$$


$I_{\text{copy}} = \frac{\left(\frac{w}{L}\right)_{M_2}}{\left(\frac{w}{L}\right)_{M_1}} I_0$

PrePfusion

$I_{\text{copy}} \propto I_0$

independent of supply and Temp variation.

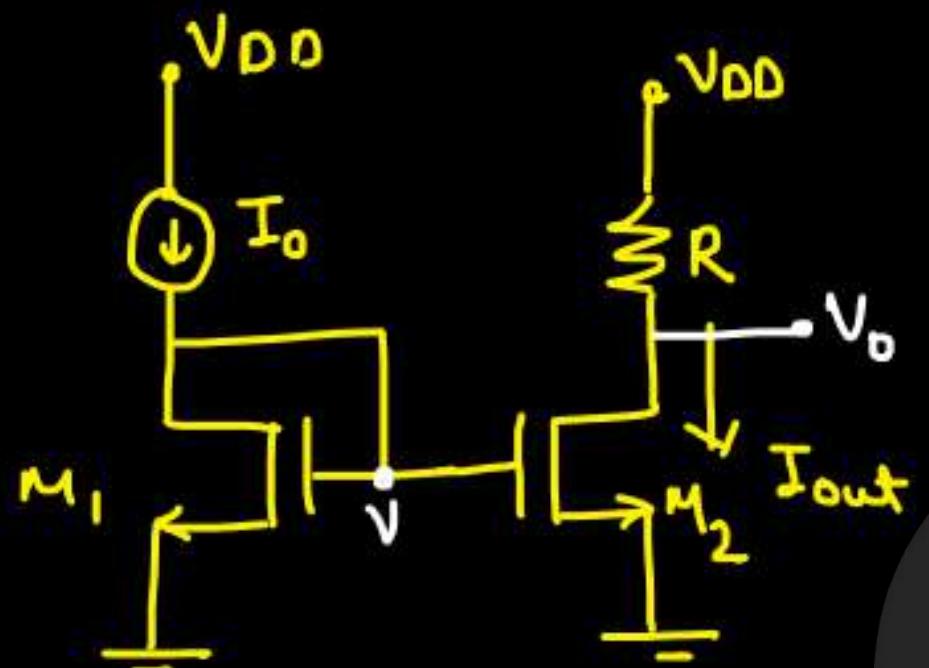Alternative Analysis of current Mirror ckt :-



⇒ Both M_1 and M_2 are in Sat. region.

$$(V_{GS})_{M_1} = (V_{GS})_{M_2} = V$$

PrepFusion


$$I_o = \mu_n C_{ox} \left(\frac{w}{L} \right)_{M_1} (V - V_T)^2 \quad \textcircled{1}$$

$$I_{out} = \mu_n C_{ox} \left(\frac{w}{L} \right)_{M_2} (V - V_T)^2 \quad \textcircled{2}$$

$$\textcircled{2} \div \textcircled{1} \Rightarrow \frac{I_{out}}{I_o} = \frac{\left(\frac{w}{L} \right)_{M_2}}{\left(\frac{w}{L} \right)_{M_1}}$$

$$I_{out} = \frac{\left(\frac{w}{L} \right)_{M_2}}{\left(\frac{w}{L} \right)_{M_1}} I_o$$

Eg.

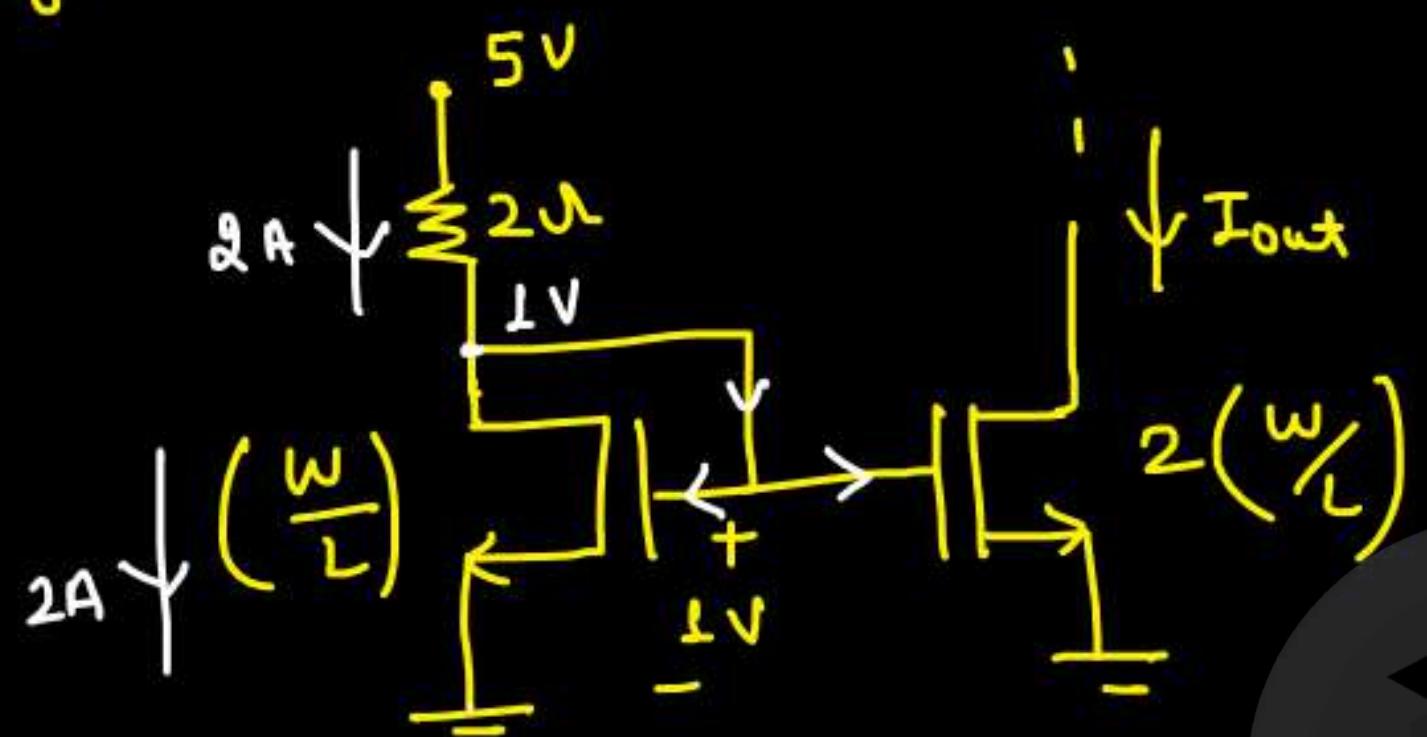


Both Transistors are working in Sat. region.
Find $I_{out} = ?$

$$I_{out} = \frac{2(\omega_L)}{(\omega_L)} \times 2 \text{ Amp.}$$

$I_{out} = 4 \text{ Amp.}$

Current mirror using PMOS :-

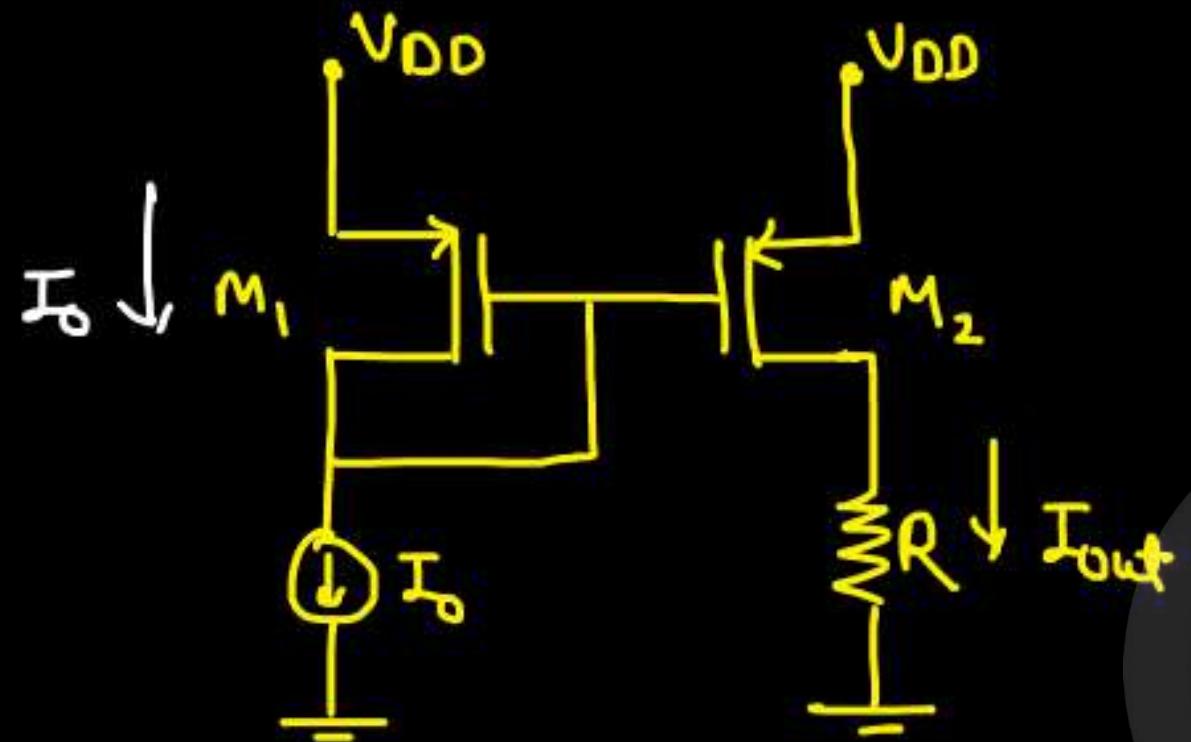

$$I_{out} = \frac{(w_L)M_2}{(w_L)M_1} I_0$$


PrepFusion

Q. Both Transistors are perfectly matched.

$$m_n C_{ox} = 200 \mu A / V^2, W/L = 10, V_T = 0.7V, \lambda = 0$$

Find the value of R to get 100mA o/p current.

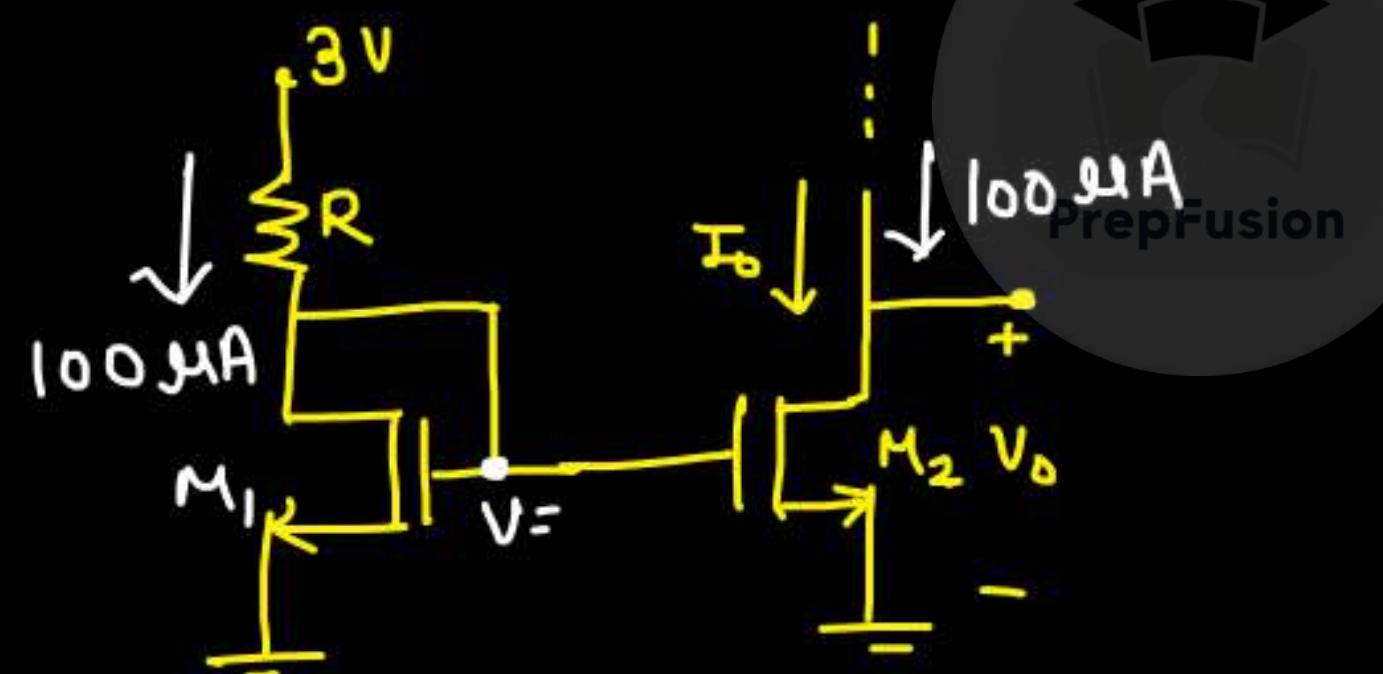
What is the lowest possible value of V_o such that M_2 is working in sat. region.



$$100\mu A = \frac{200\mu A \times 10}{2} [V - 0.7]^2$$

$$V - 0.7 = \sqrt{10}$$

$$V = 1V$$

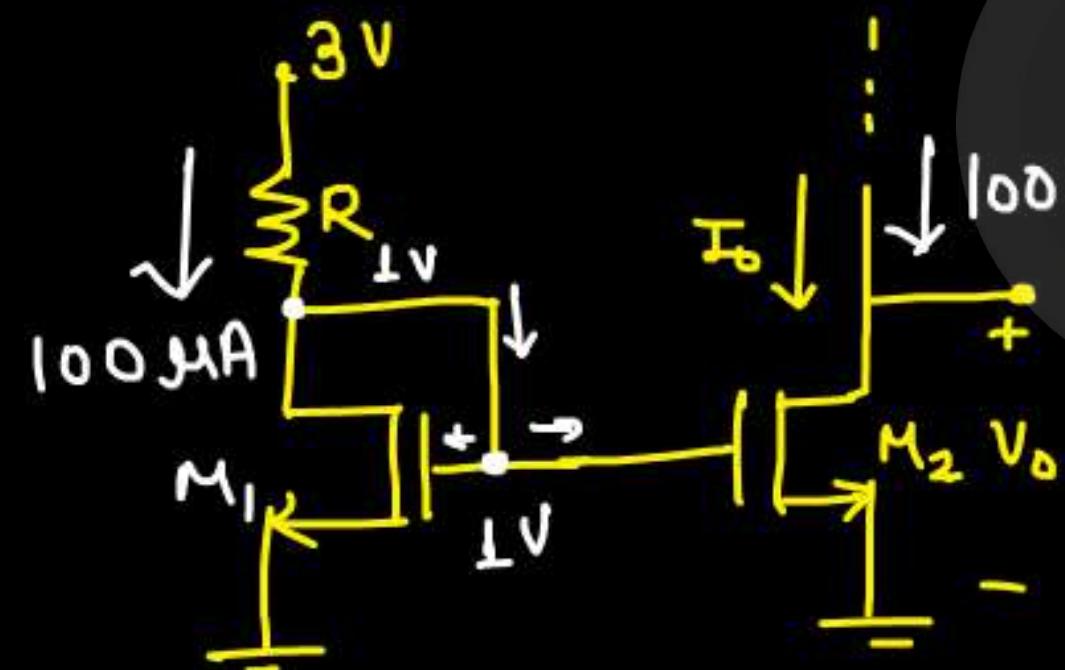

$$\frac{3-1}{R} = 100\mu A$$

$$R = 20k\Omega$$


ANS.

⇒ For sat. region

$$V_{DS} = V_{GS} - V_T$$

$$V_o = 1 - 0.7 = 0.3 \Rightarrow V_o = 0.3V$$


⇒ Building Multiple current sources :-

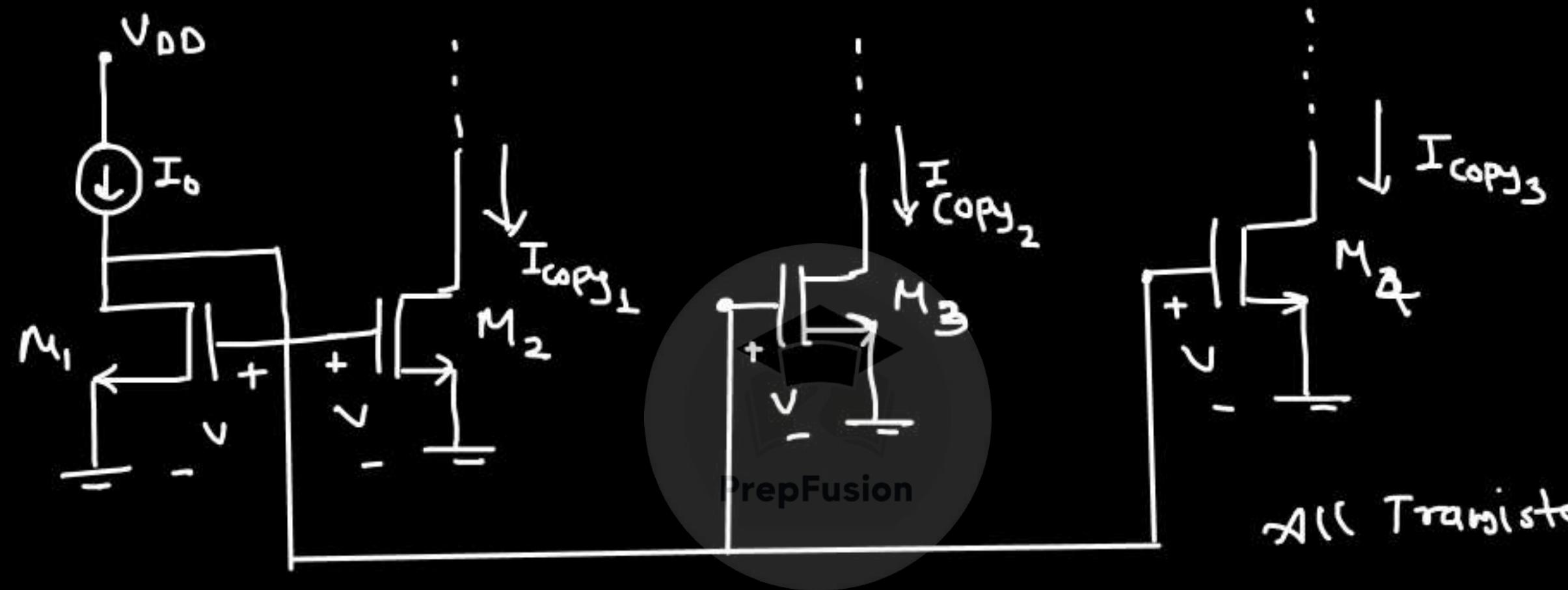

$$I_{\text{copy}_1} = \frac{(w/L)_{M_2}}{(w/L)_{M_1}} I_0$$

$$I_{\text{copy}_2} = \frac{(w/L)_{M_3}}{(w/L)_{M_1}} I_0$$

Other way of showing the same circuit:-

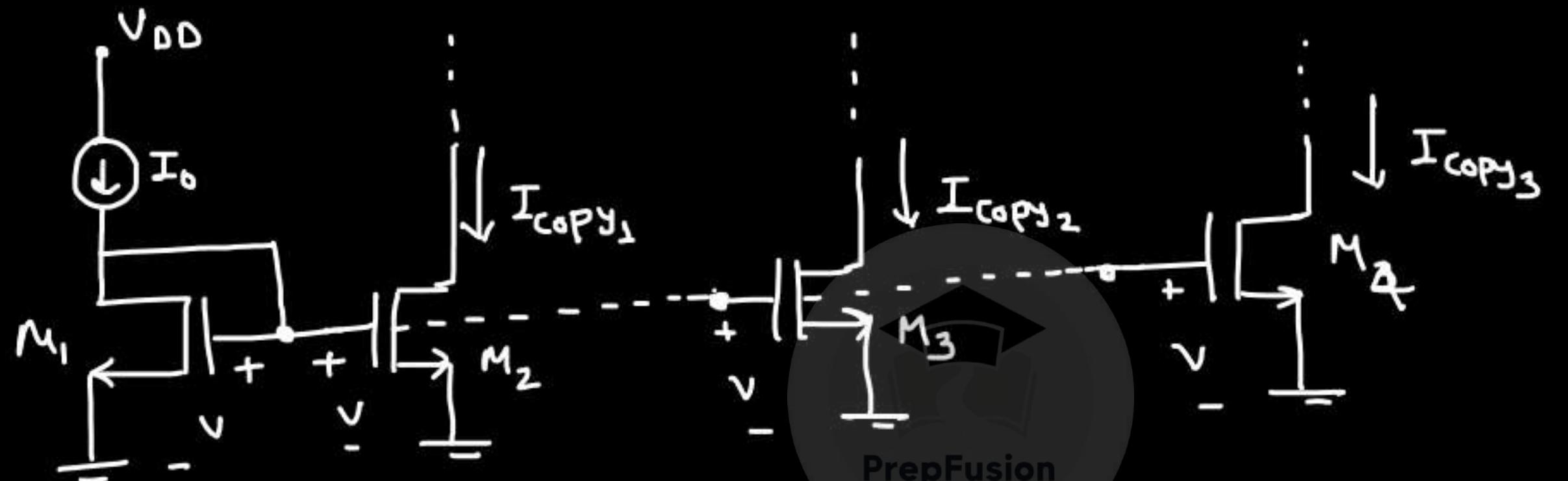

Q. Make a common source Amplifier (using NMOS)


with $100\mu A$ current source in load. You have a reference current source of $200\mu A$.

You only have one supply V_{DD} .

Your small signal i(p) v_s has internal resistance R_S .


After designing the ckt, find the small signal voltage gain.

→

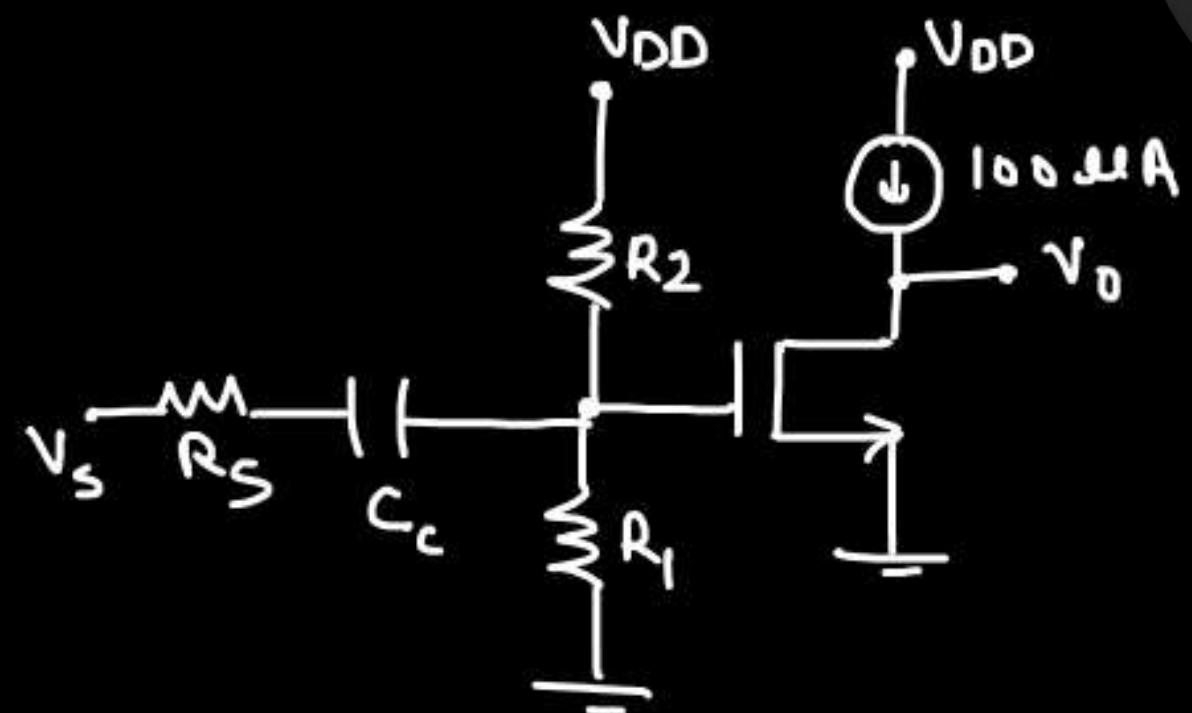


Next task:-

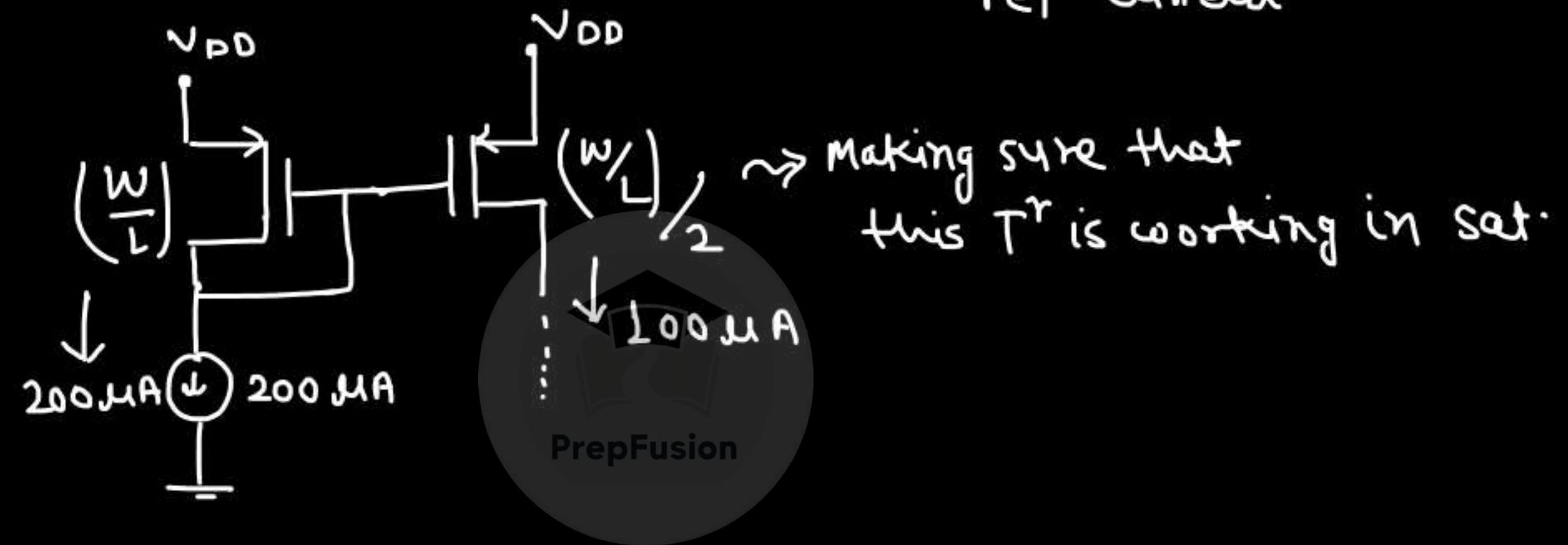designing $100\mu A$ current source from $200\mu A$
ref. current.




Final design :-

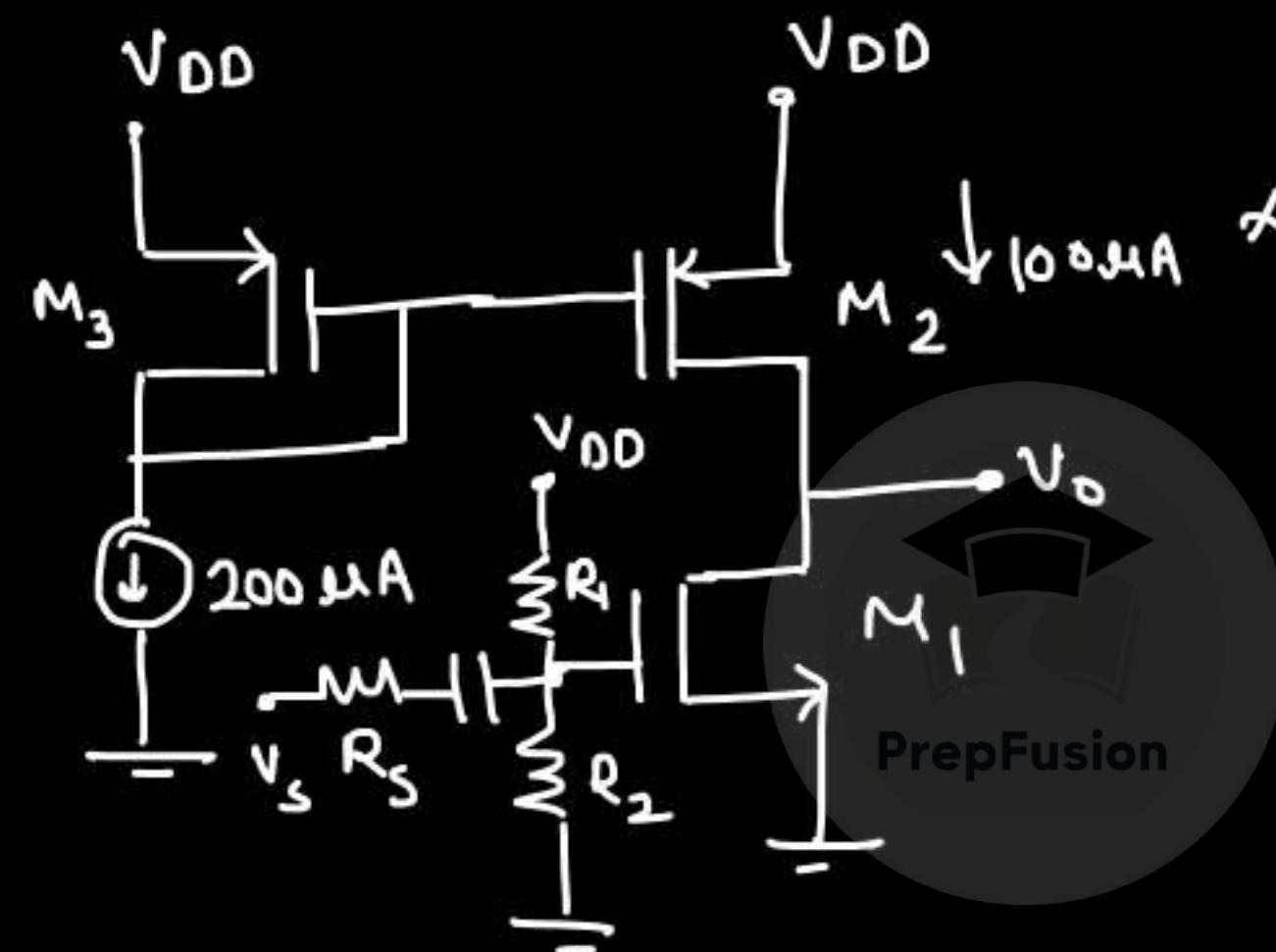

Adjust V_{DD}, R₁, R₂
such that all T's are
working in sat.
 $(\omega_L)_3 = 2 (\omega_L)_2$


Small signal Voltage gain :-

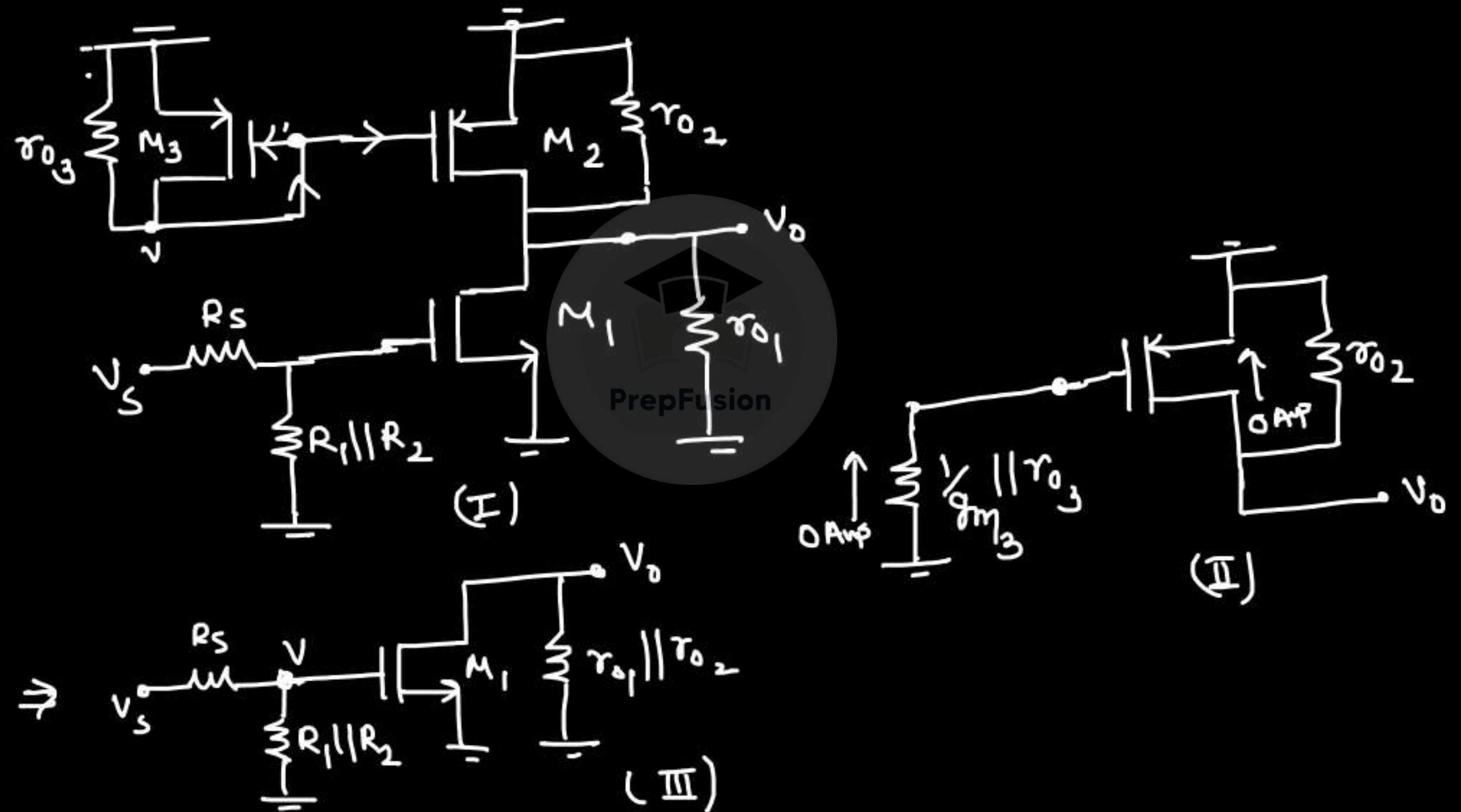



$$\frac{V_o}{V_s} = -g_m [r_{o1} \parallel r_{o2}] \times \frac{(R_1 \parallel R_2)}{R_S + (R_1 \parallel R_2)}$$


M-II

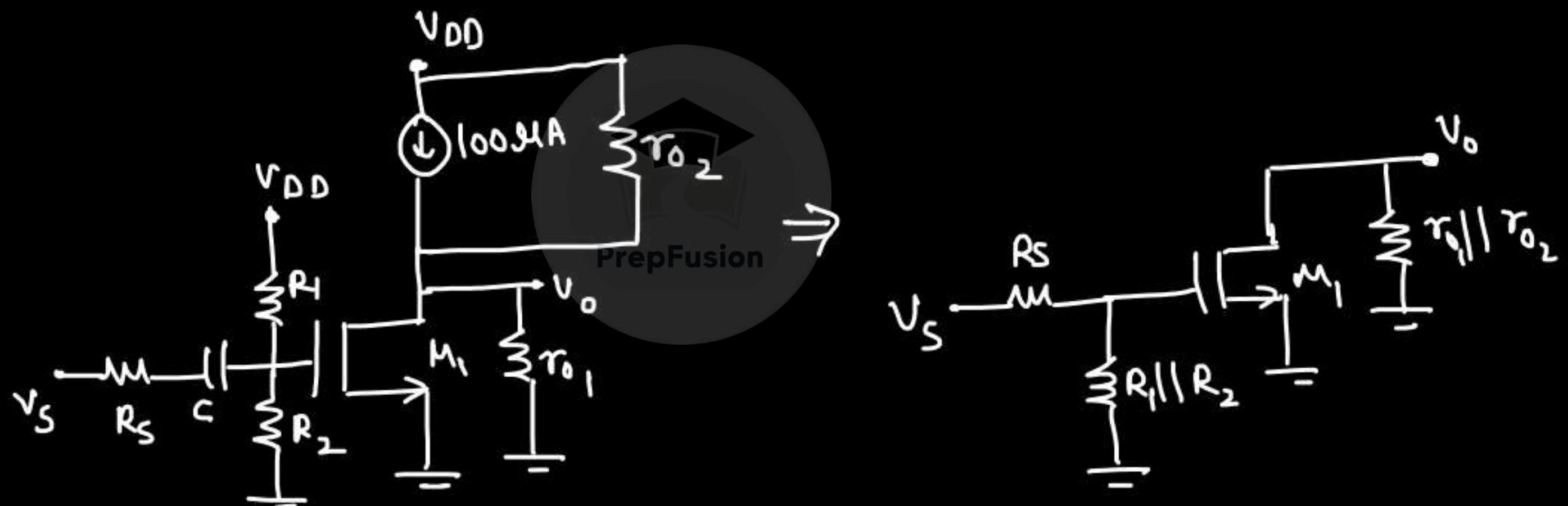

Q. Design a common drain amplifier (using NMOS) with $100\mu A$ current source in load.


You have a reference current source of $200\mu A$.

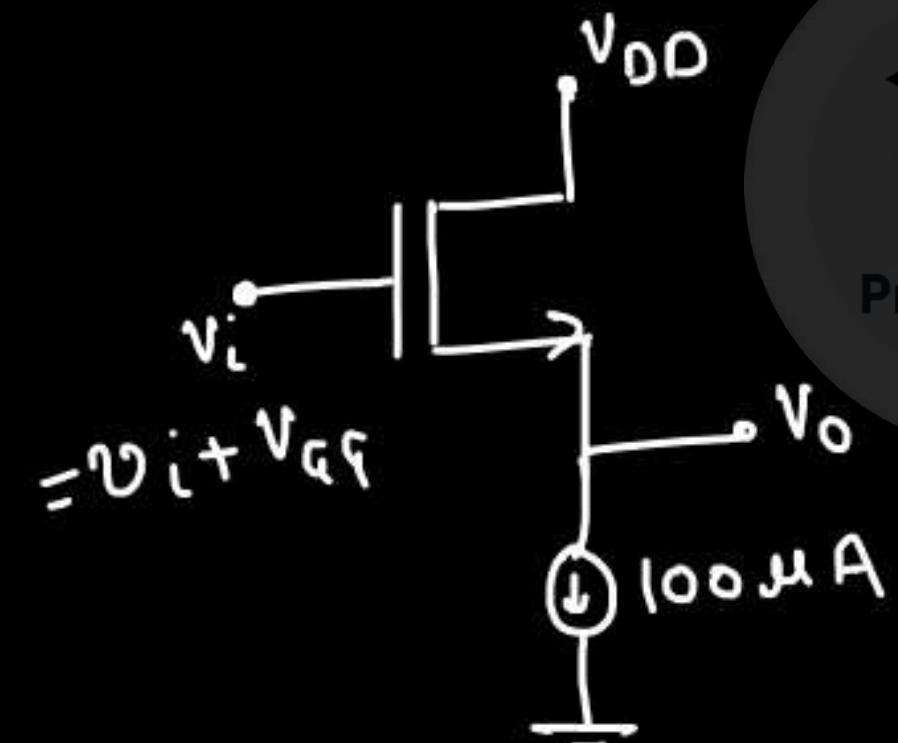[Note: - All the available transistor have same w_L ratios.]




Task:-



designing 100 μA current source:-

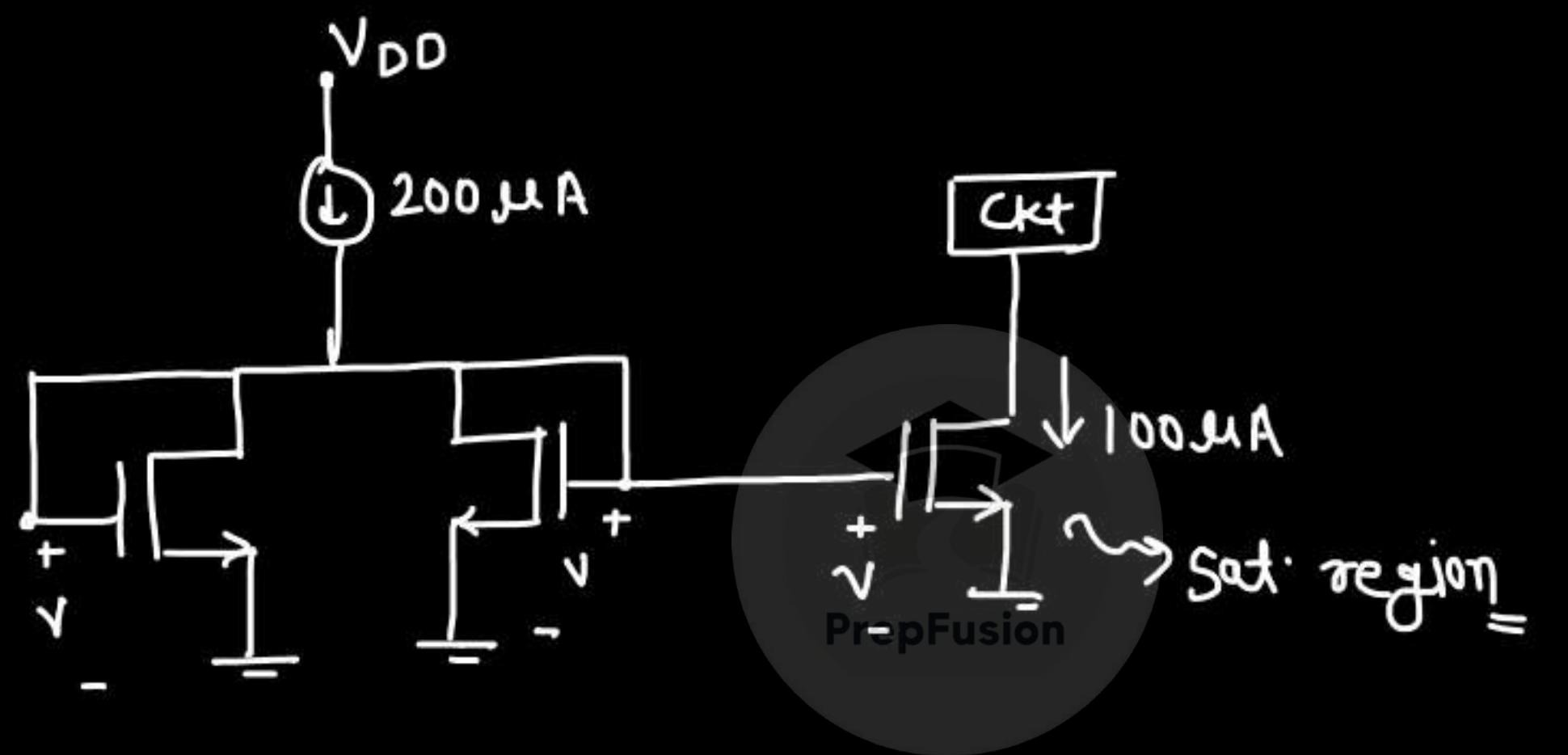

final design:-

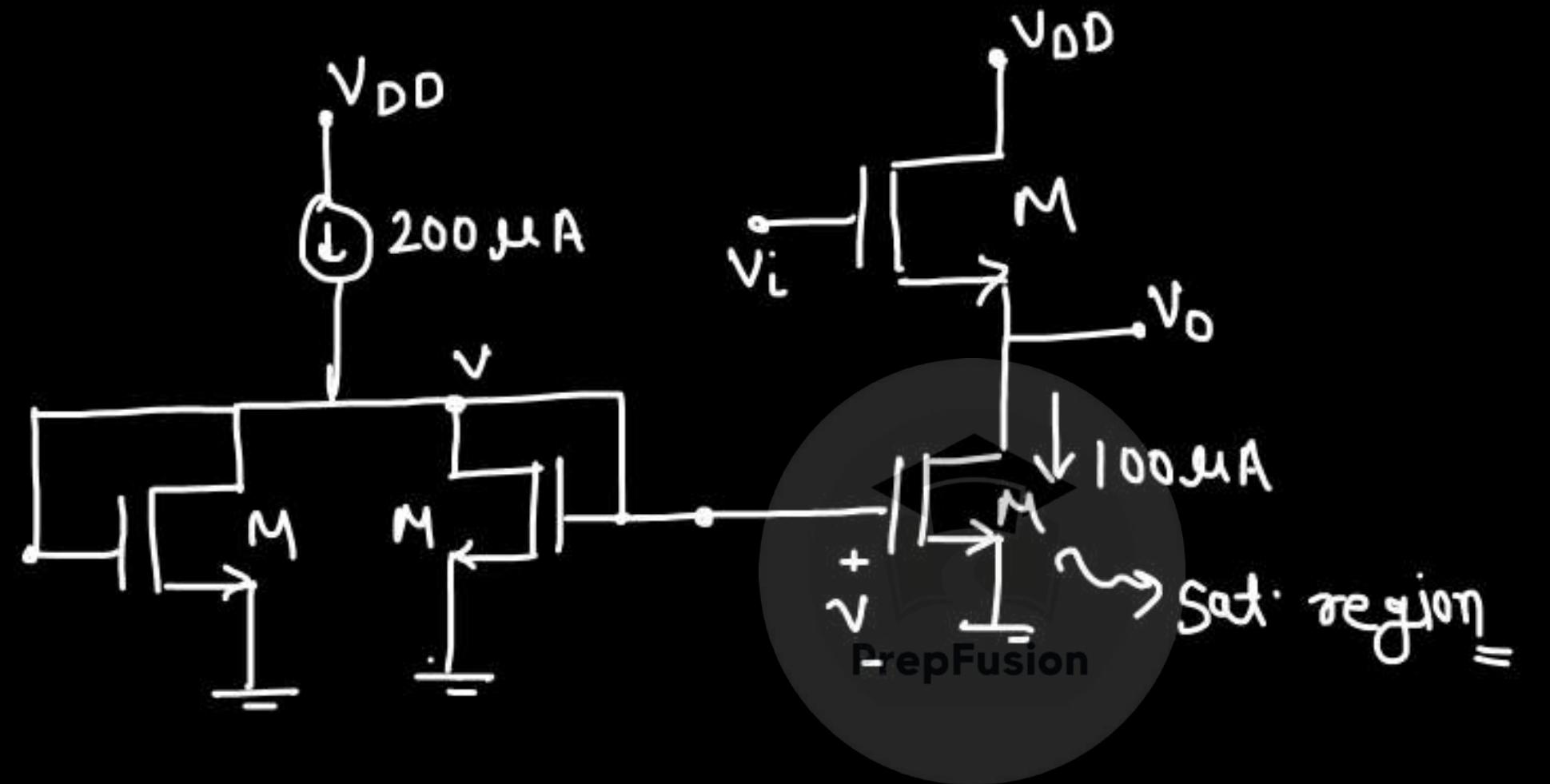

Small signal analysis:-

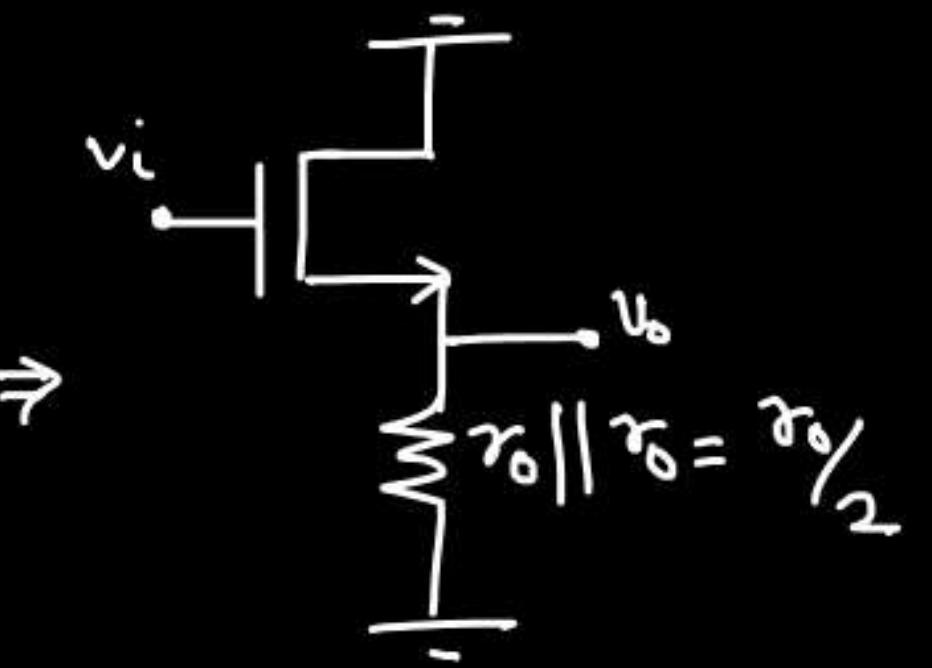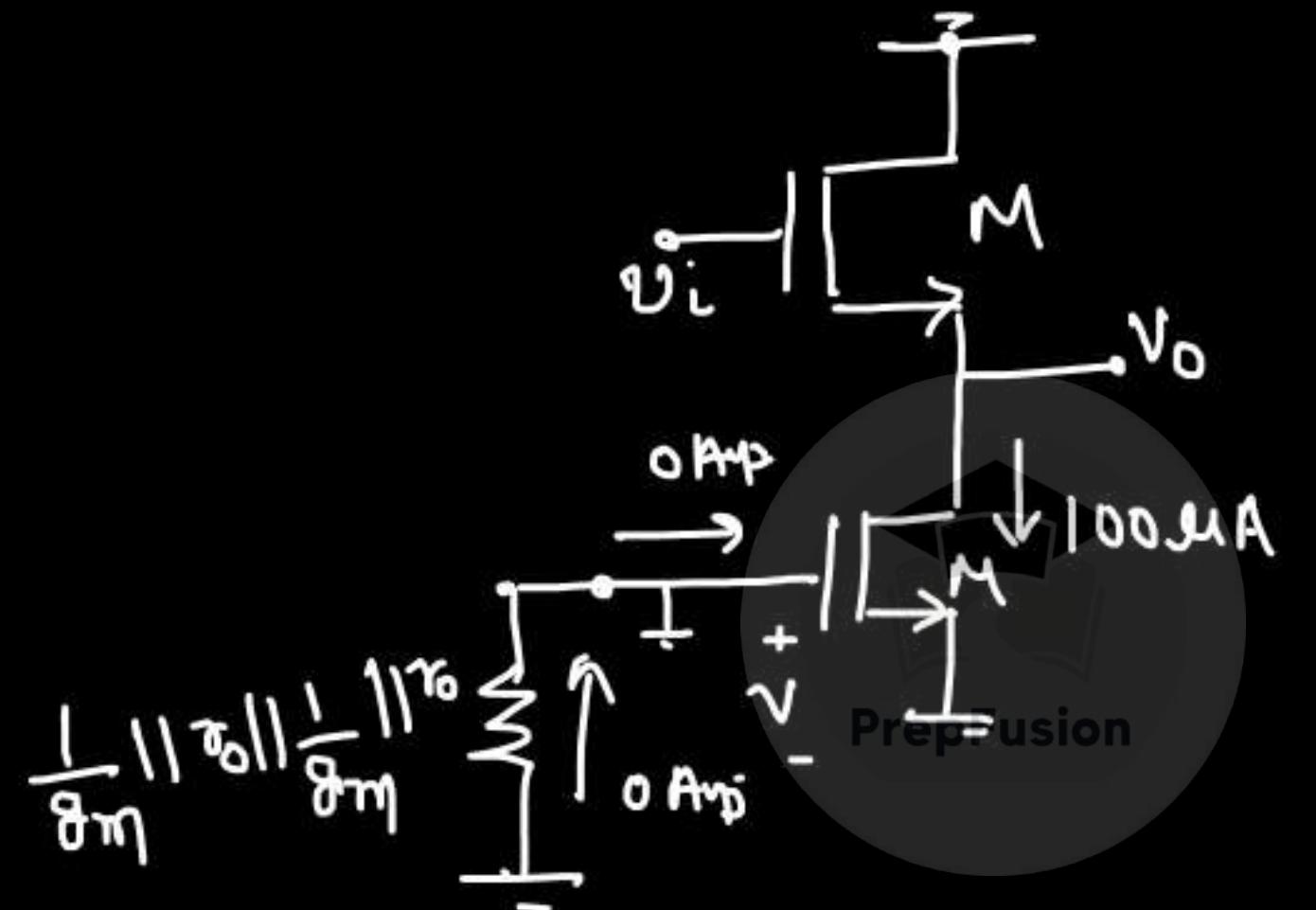


$$\frac{v_o}{v_i} = \frac{r_o/2}{\frac{1}{g_m} + r_o/2}$$




Ans

$$\frac{v_o}{v_i} = \frac{g_m r_o}{1 + g_m r_o}$$

Conclusion :-

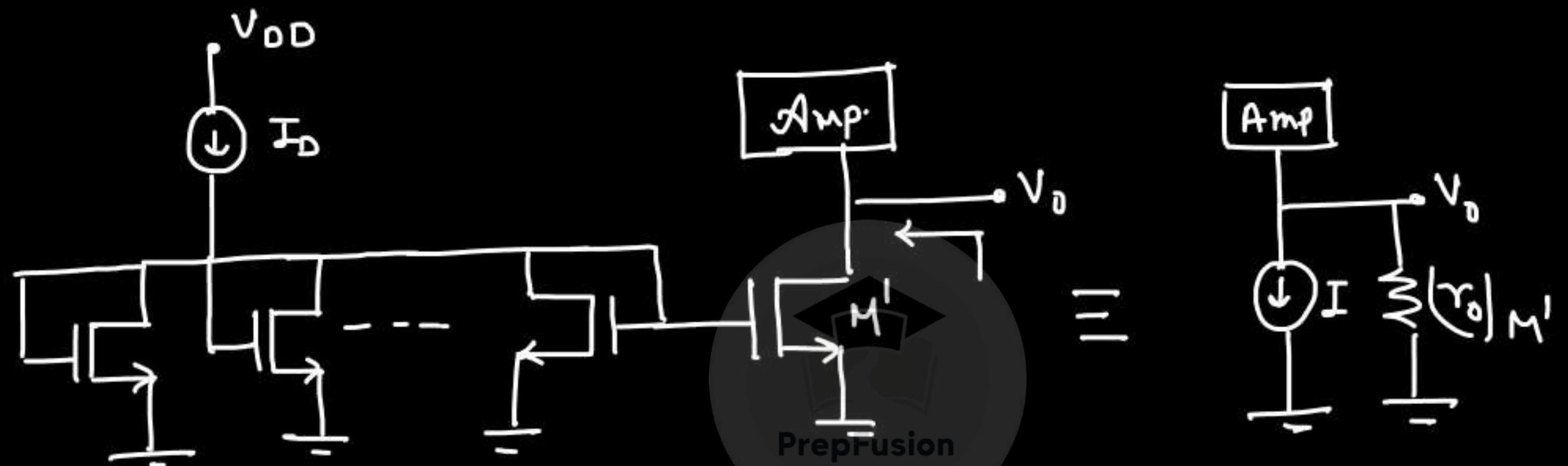

N.B. →

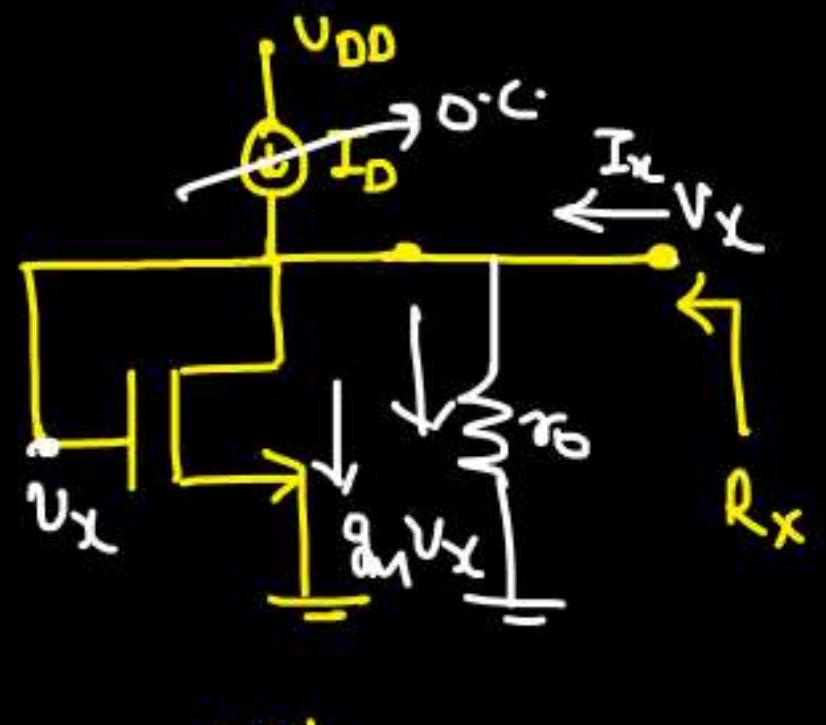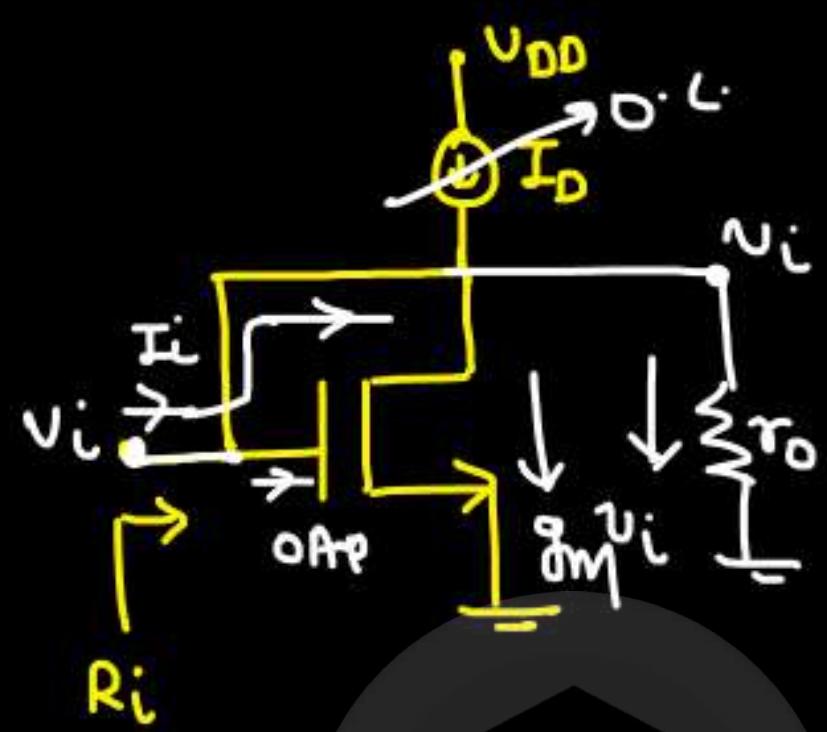
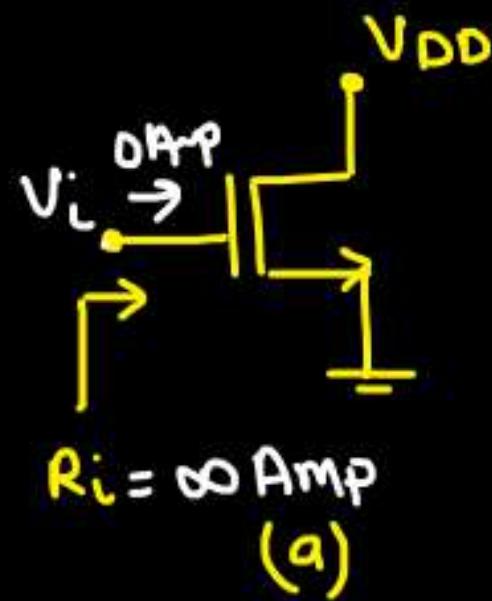


$$I_L = g_m u_i + \frac{u_i}{r_o}$$

$\frac{u_i}{I_L} = R_i = \frac{1}{g_m} || r_o$


$$\frac{u_x}{r_o} + g_m u_x = I_x$$

$\frac{u_x}{I_x} = R_x = \frac{1}{g_m} || r_o$

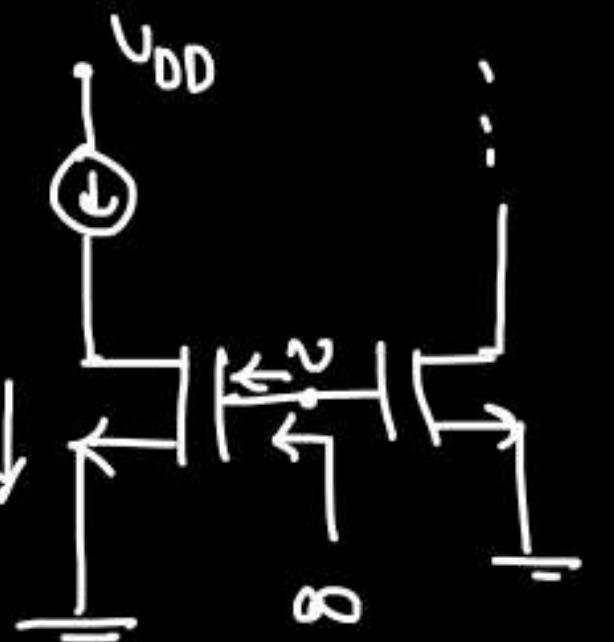
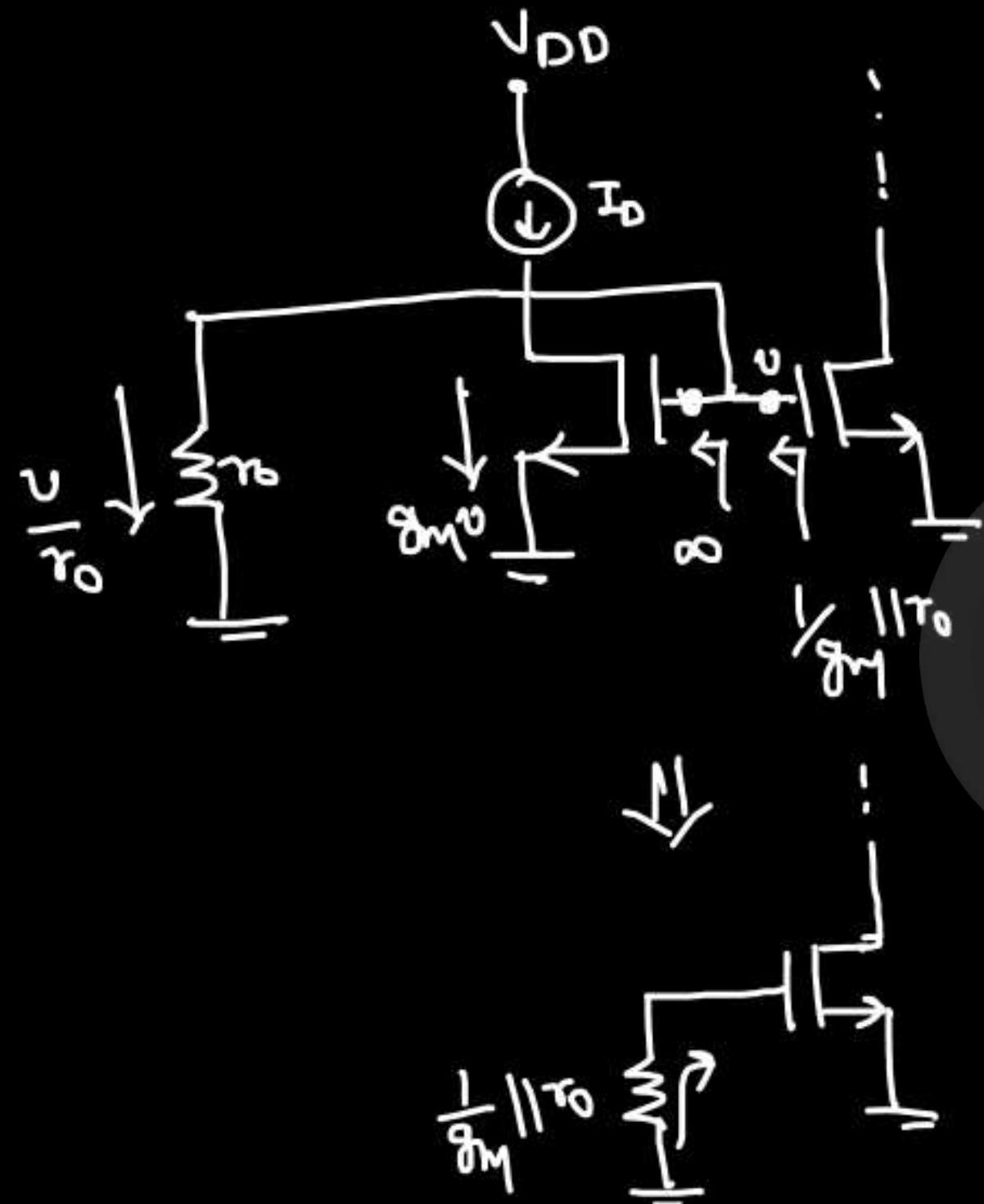



Assignment - 8

Q.

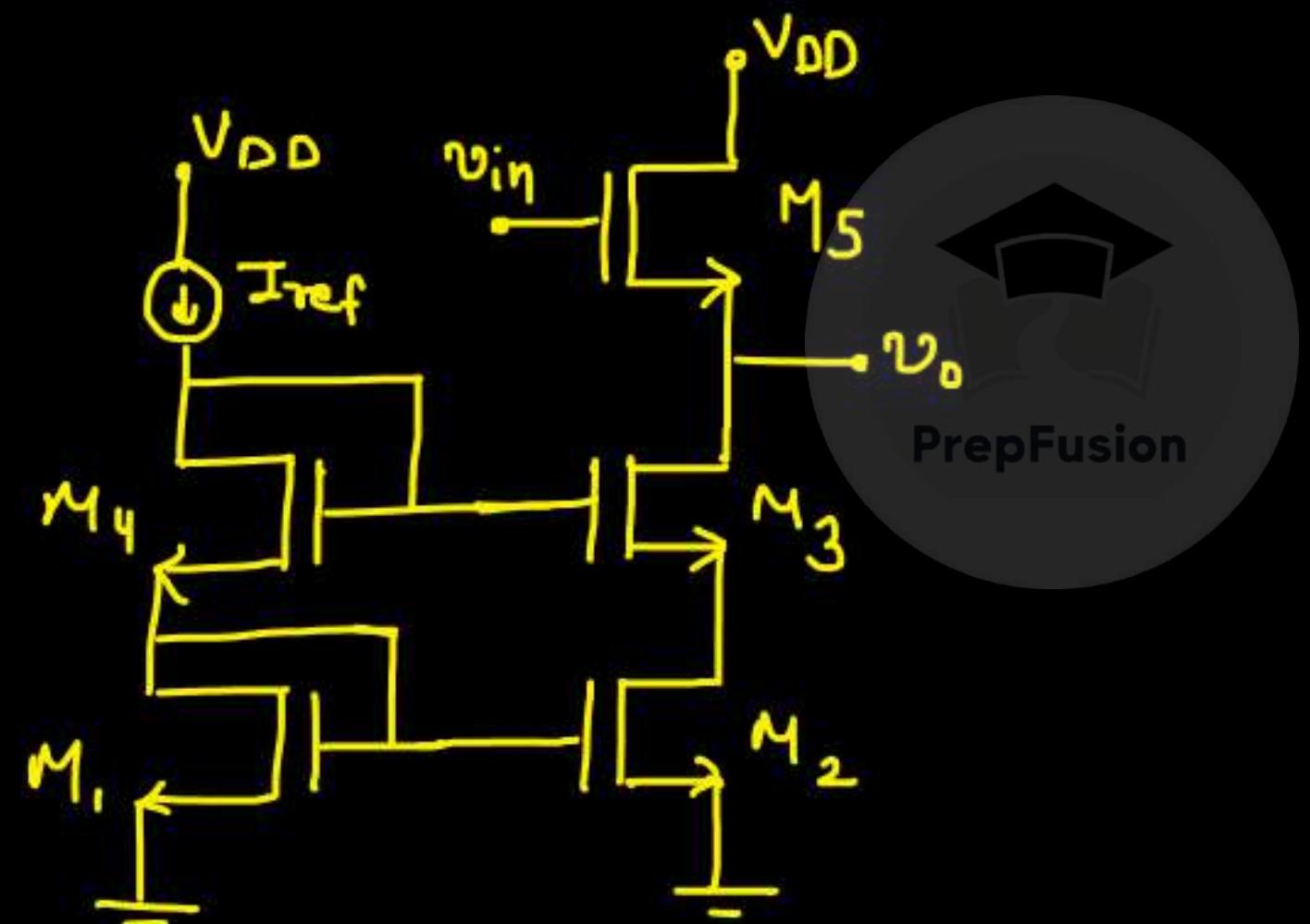

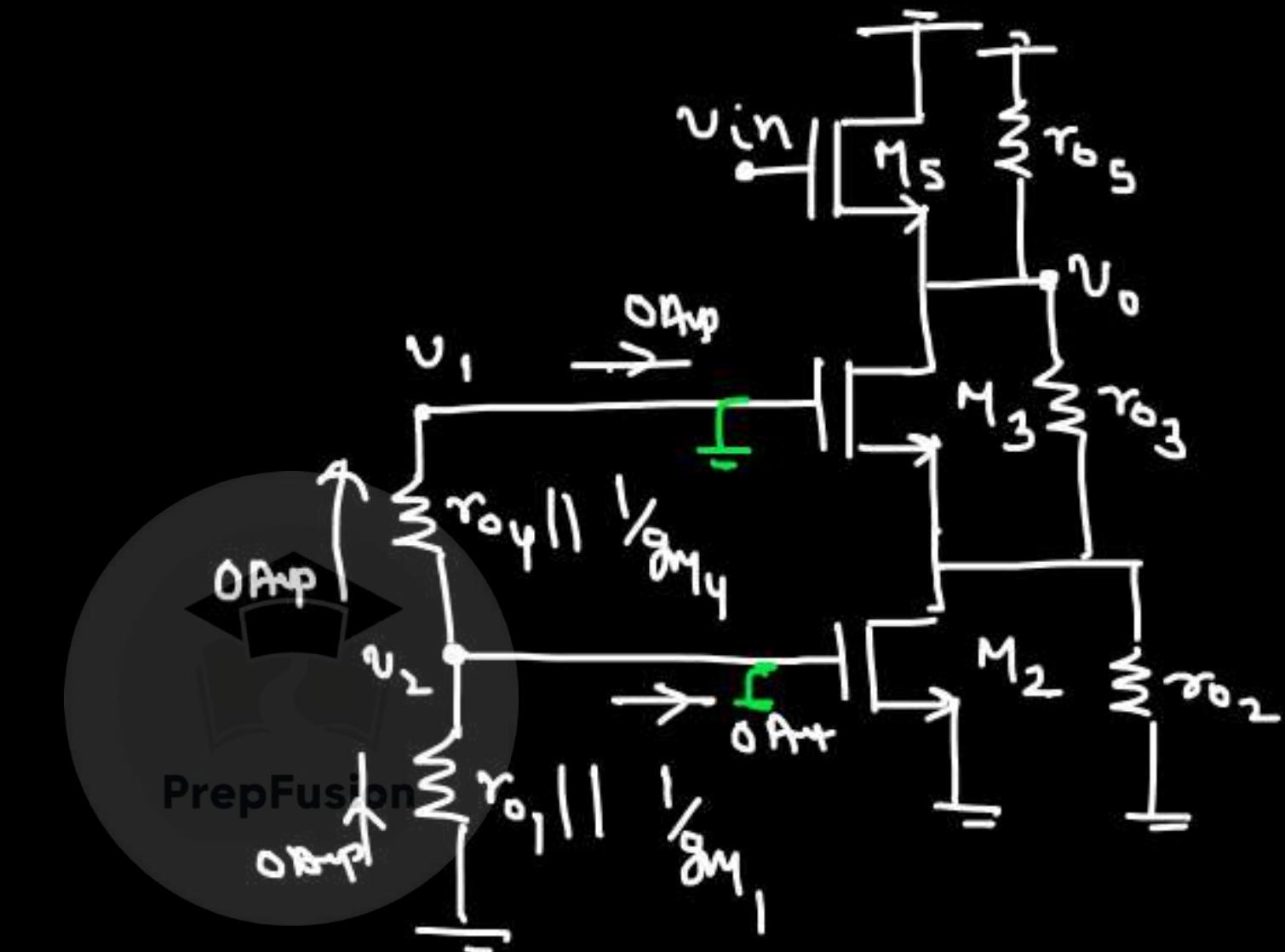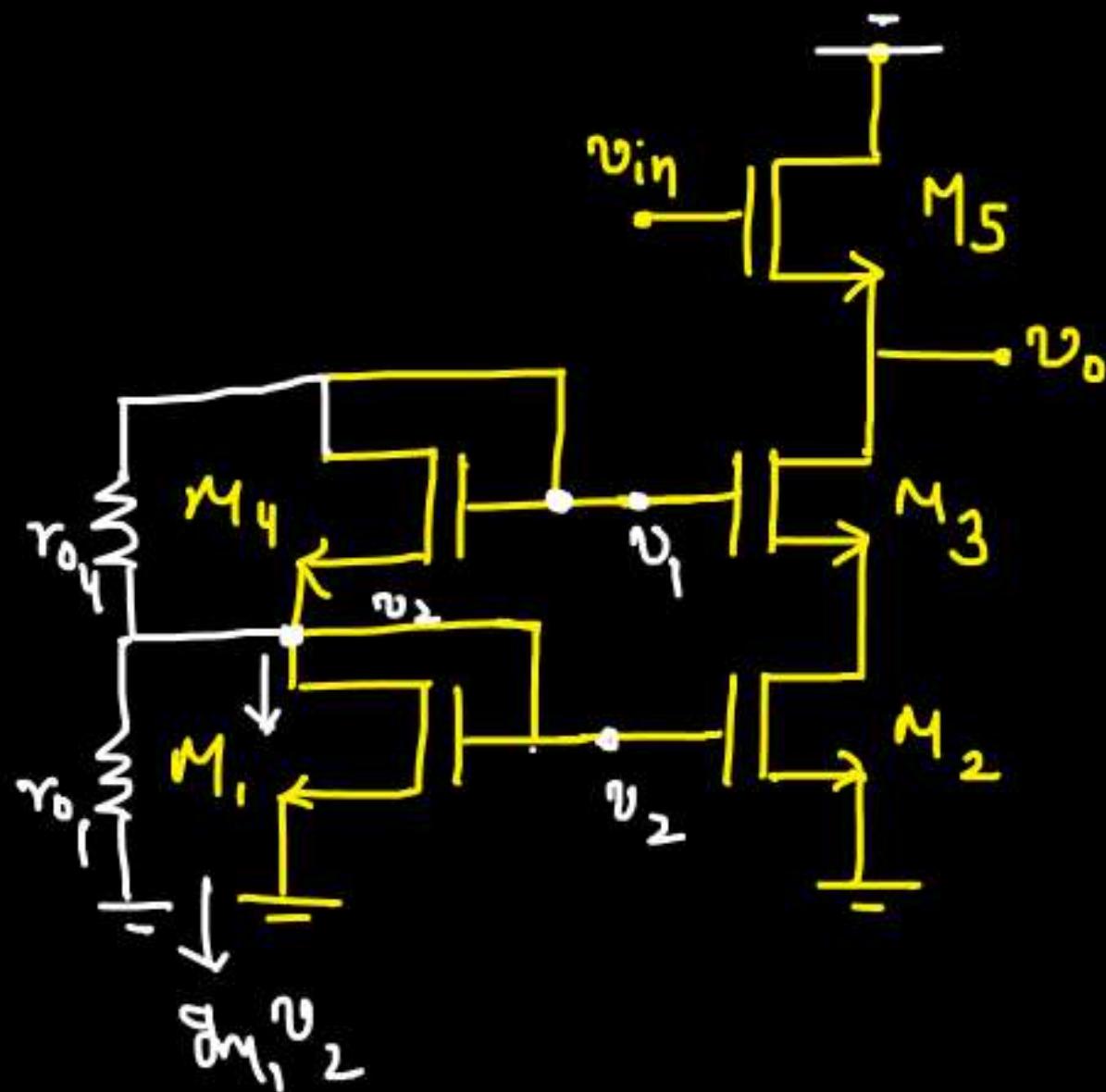Find small signal
Voltage gain $\frac{v_o}{v_i}$?



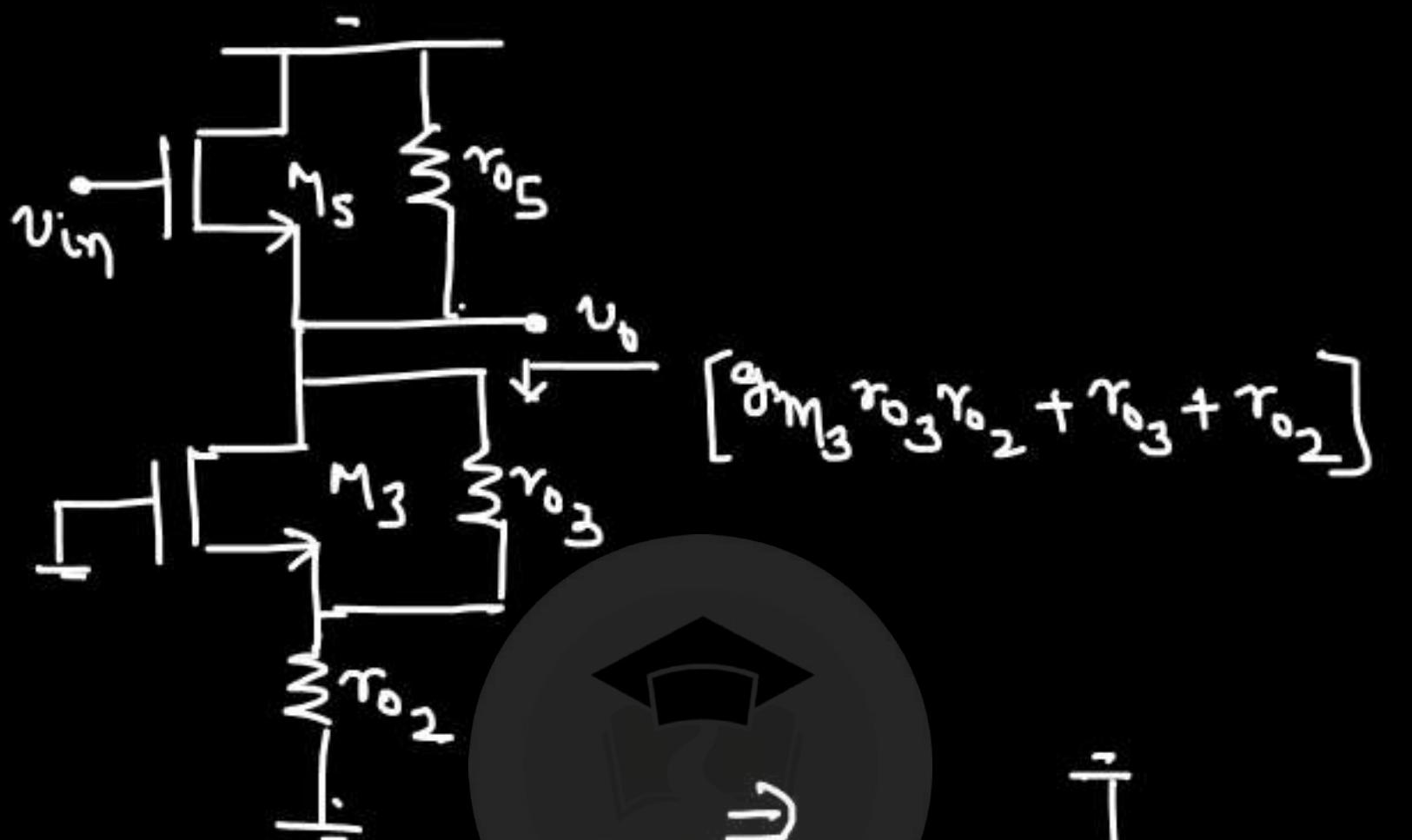


PrepFusion

$$\frac{v_o}{v_i} = \frac{g_m M_5 R}{1 + g_m M_5 R}$$

$$R = r_{o_5} \parallel (g_m M_3 r_{o_3} r_{o_2} + r_{o_3} + r_{o_2})$$

$$[r_{o_5} \parallel (g_m M_3 r_{o_3} r_{o_2} + r_{o_3} + r_{o_2})] = R$$

Q.

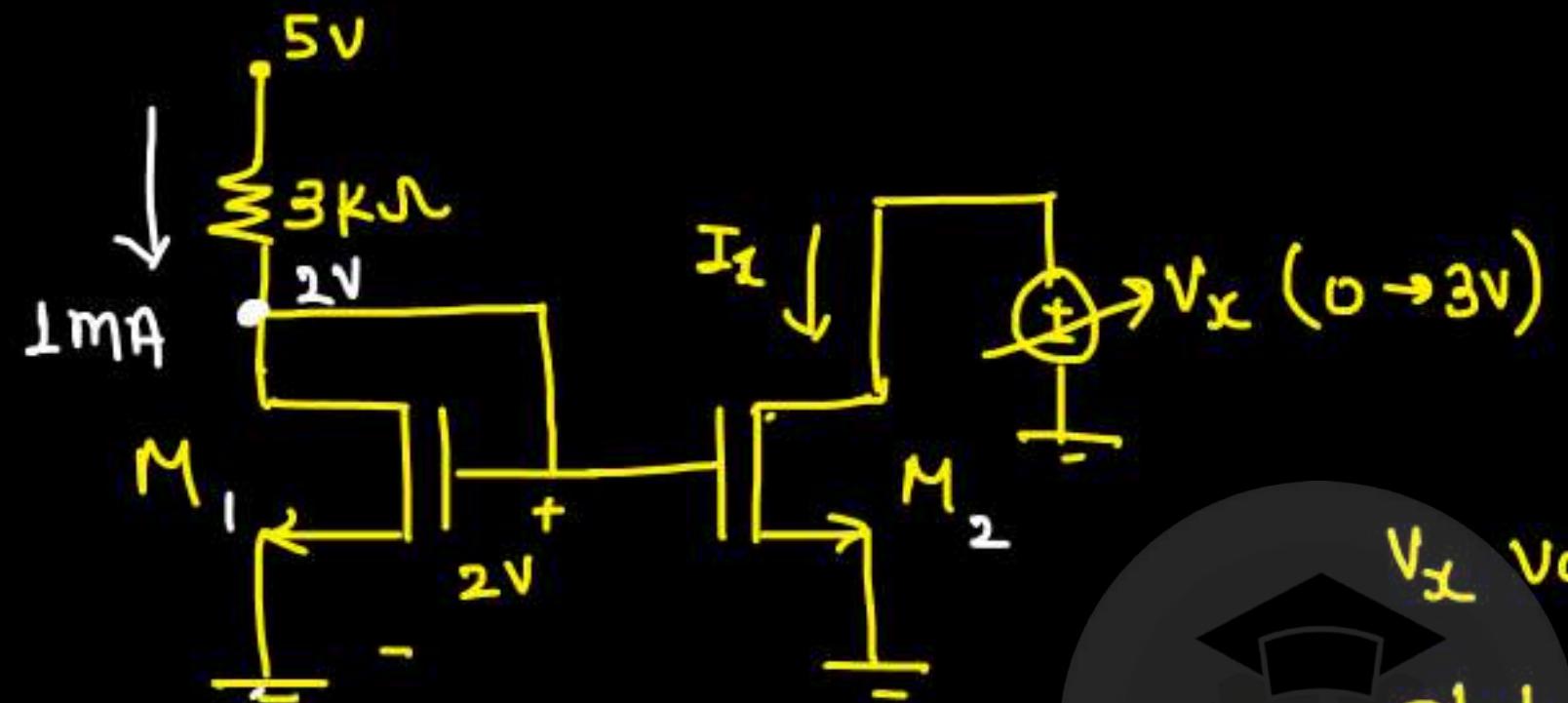

$$V_T = 1V$$

V_x value is swept from $0 \rightarrow 3V$.

plot V_x v/s I_x .

$I_x = I_{MA}$ [when M_2 is in sat]

$V_x > 2 - 1 \Rightarrow V_x > 1V \Rightarrow M_2$ is in sat




$I_x = I_{MA}$ \Leftarrow M_1 & M_2 are
in current mirror

For $V_x > 1V \Rightarrow I_x = 1mA$


For $V_x < 1V \Rightarrow M_2$ is in linear region

current in linear region < current in sat. region

(for fixed V_{GS})

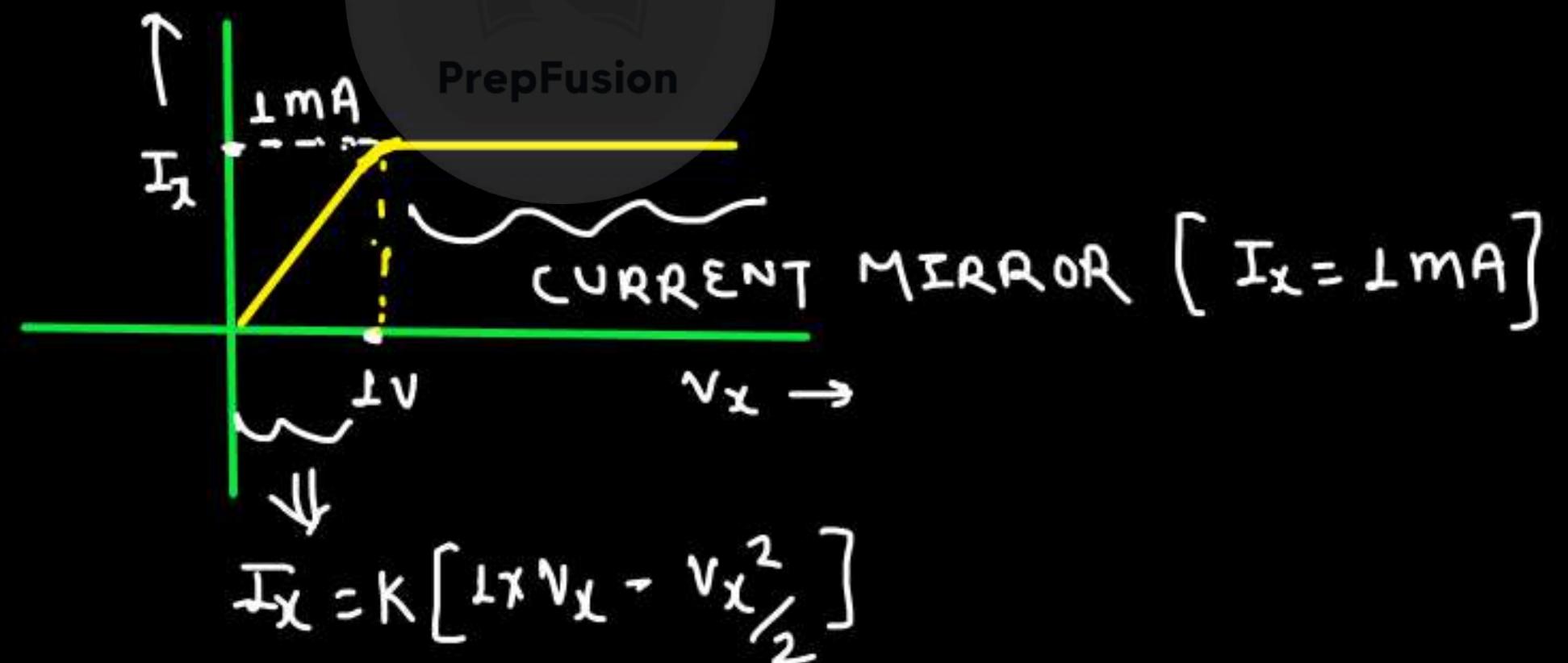


Q.

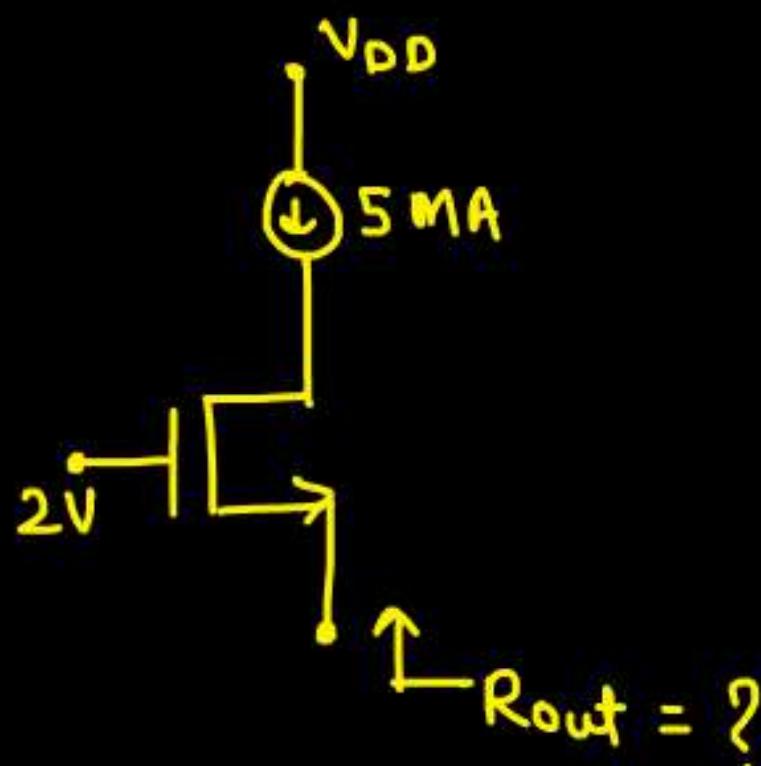


Find R_{out} for $\lambda=0$, $\lambda \neq 0$

$\Rightarrow \lambda=0$

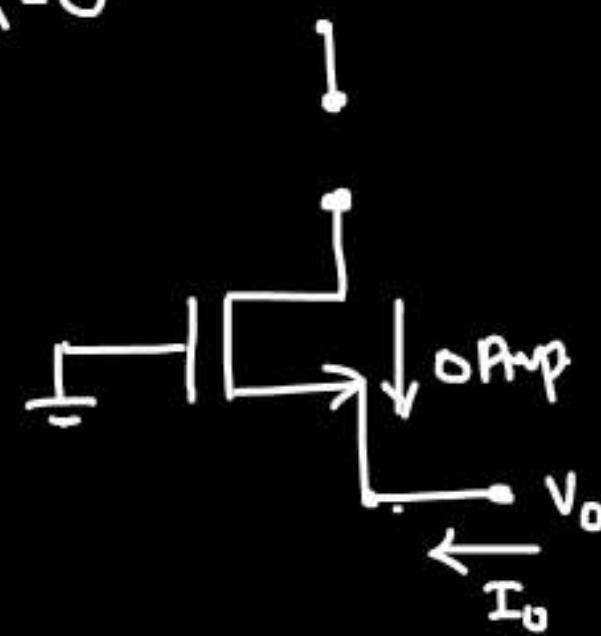

$$R_{out} \approx \frac{V_0}{I_0} = \frac{V_0}{I_0} \approx \infty$$


$\lambda \neq 0$

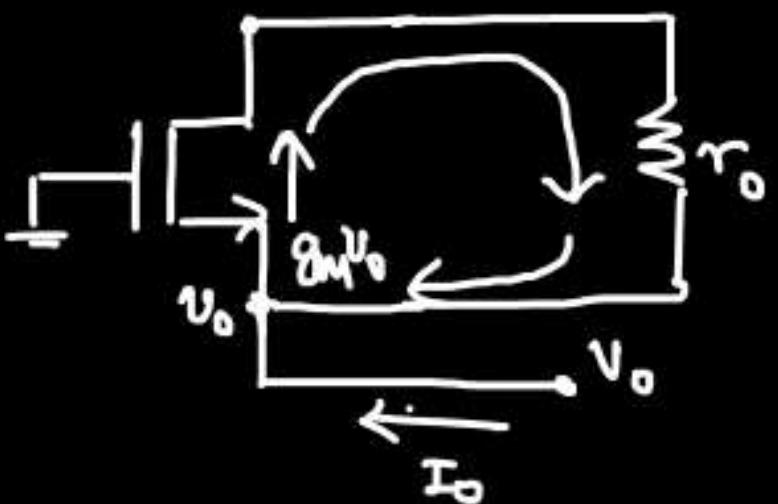

$$I_0 = 0 \text{ Amp.}$$

$$R_0 = \infty$$

Q.

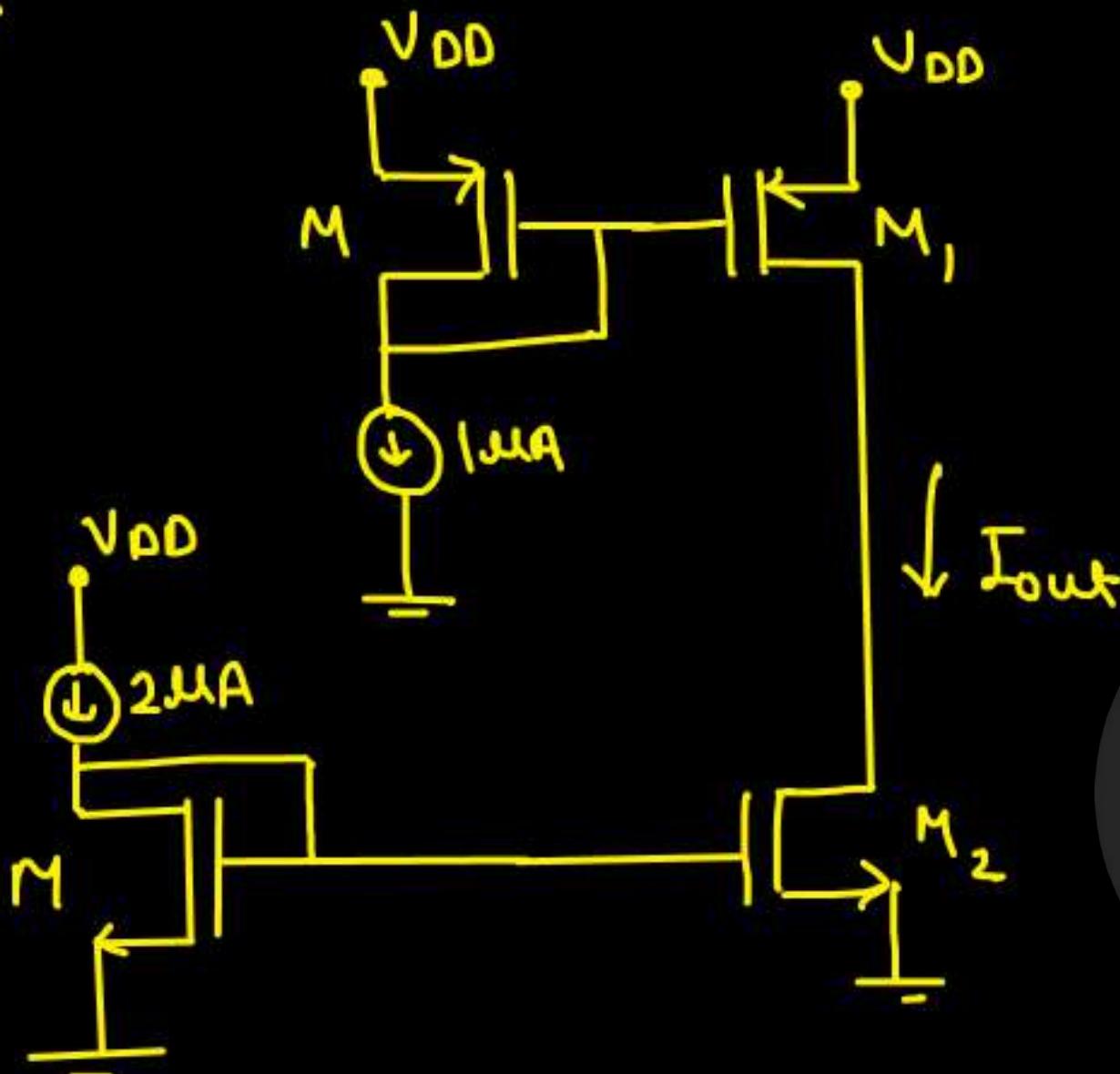

all Tr are identical.

Find I_{out} ?

⇒ if M and M_2 are in c.m. ⇒ $I_{\text{out}} = 2 \mu\text{A}$

if M and M_1 are in c.m. ⇒ $I_{\text{out}} = 1 \mu\text{A}$

PrepFusion

$$I_{\text{out}} = 2 \mu\text{A} = 1 \mu\text{A} \rightarrow \text{NOT POSSIBLE}$$

⇒ There will be only one current mirror working.

⇒ one of M_1 or M_2 will go into triode region and not in sat.

Let M_2 is in sat. and M_1 is in Triode.

$$I_{out} = 2mA$$

↓

Same current is flowing through M_1

[if M_1 was in sat., what is the max current it can take? $\rightarrow 1mA$]

$\Rightarrow M_1$ can take max $1mA$ current, but Here even in Triode region, it's taking $2mA$ current \Rightarrow which is not possible

\Rightarrow Assumption is wrong

Let M_1 is in sat., M_2 is in Triode

$$I_{out} = 1 \mu A$$




Same current is taken by M_2

[M_L can drive maxTM current of $2 \mu A$ in sat. so, it
can certainly take $1 \mu A$ current in Triode region]

⇒ Assumption Preparation is correct

$$I_{out} = 1 \mu A$$

Q.

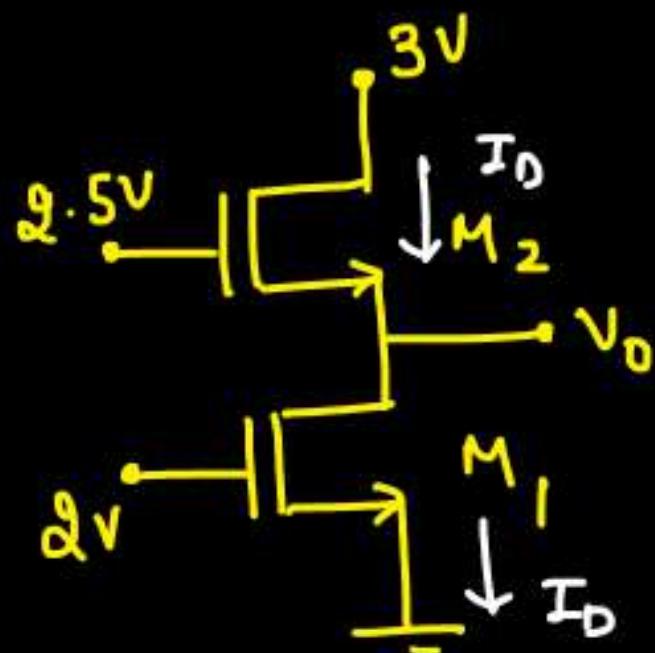

Both Transistors are identical.

$$V_T = 1V$$


Find operating cond'n of M_1 & M_2 .

→ Let both M_1 and M_2 are in sat.

$$(I_D)_{M_2} = (I_D)_{M_1}$$

$$\frac{\mu_n C_o x W}{2L} (2.5 - V_0 - 1)^2 = \frac{\mu_n C_o x W}{2L} (2 - 1)^2$$

V₀ = 0.5V X

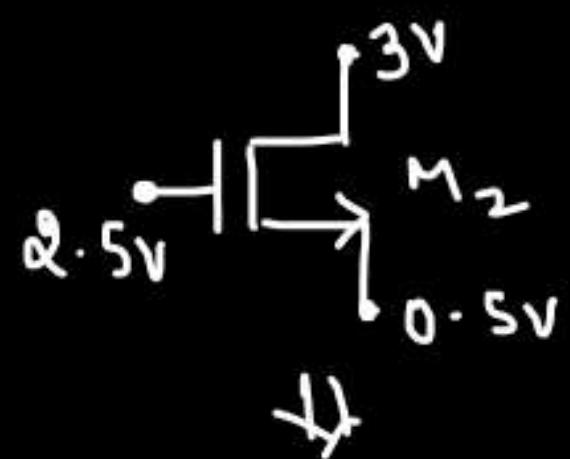


$$V_{DS} = 2.5V$$

$$V_{OV} = 2 - 1 = 1V$$

\$V_{DS} > V_{OV}\$ \Rightarrow sat.

W

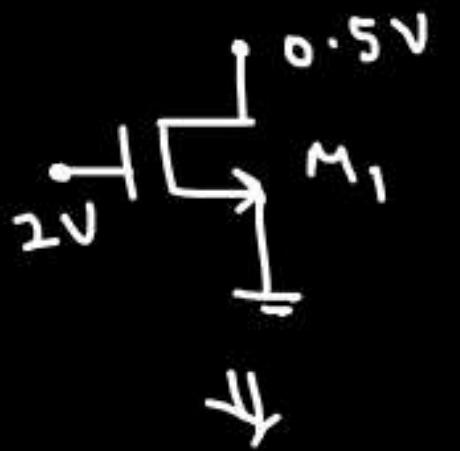

$$V_{DS} = 0.5V$$

$$V_{OV} = 1.5V$$

\$V_{DS} < V_{OV}\$ \Rightarrow linear / Not in sat.

PrepFusion

Let M_1 is in linear, M_2 is in sat.

$$(I_D)_{M_1} = (I_D)_{M_2}$$

$$\frac{\mu_n C_{ox} W}{L} \left[(1)(V_o) - \frac{V_o^2}{2} \right] = \frac{\mu_n C_{ox} W}{2L} [2.5 - V_o - 1]^2$$



$$2V_o - V_o^2 = [1.5 - V_o]^2$$

$$2V_o - V_o^2 = 2.25 + V_o^2 - 3V_o$$

$$2V_o^2 - 5V_o + 2.25 = 0$$

$$V_o = \frac{5 \pm 2.64}{4}$$

$$V_o = 1.9V \text{ OR } 0.6V$$

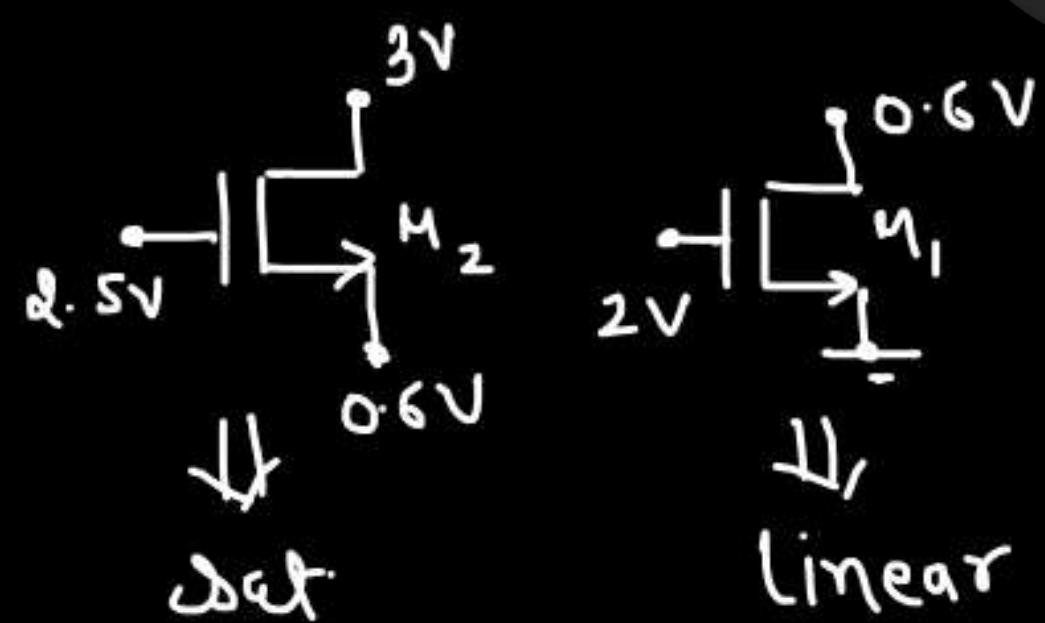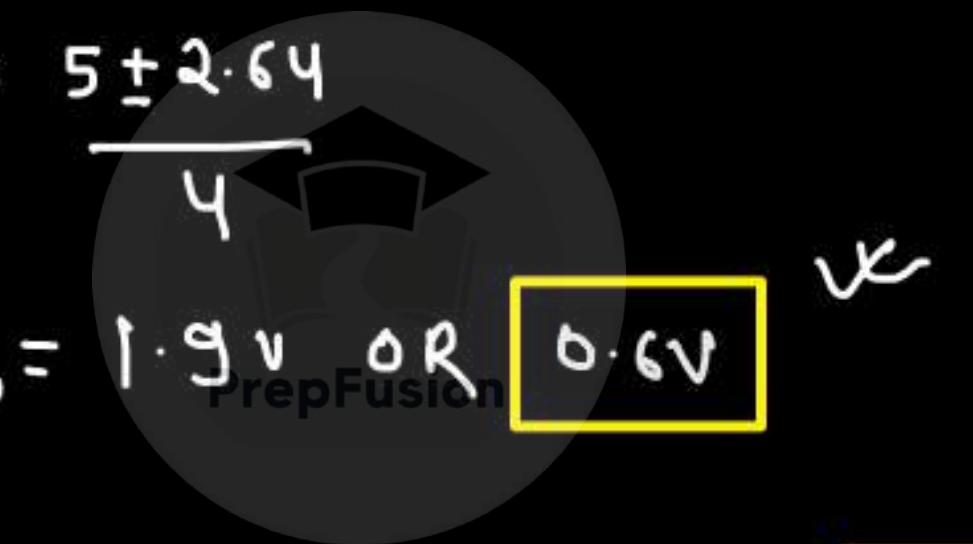

\Rightarrow

M_2 is Sat
 M_1 is in linear
 $V_o = 0.6V$


Q.




In the circuit shown, the threshold voltages of the pMOS ($|V_{tp}|$) and nMOS (V_{tn}) transistors are both equal to 1 V. All the transistors have the same output resistance r_{ds} of 6 MΩ. The other parameters are listed below:


$$\mu_n C_{ox} = 60 \mu A/V^2; \left(\frac{W}{L}\right)_{nMOS} = 5$$

$$\mu_p C_{ox} = 30 \mu A/V^2; \left(\frac{W}{L}\right)_{pMOS} = 10$$

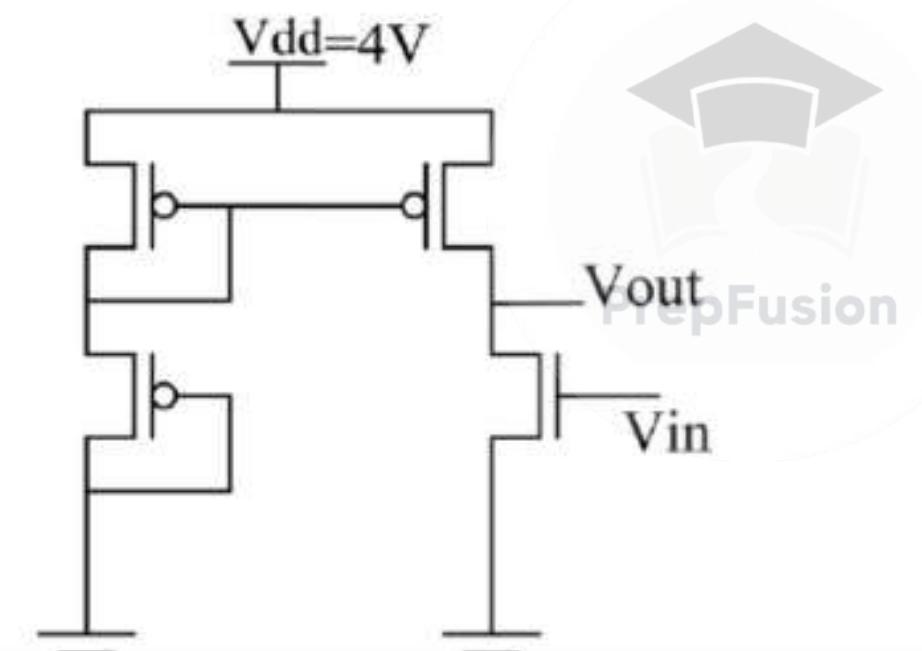μ_n and μ_p are the carrier mobilities, and C_{ox} is the oxide capacitance per unit area. Ignoring the effect of channel length modulation and body bias, the gain of the circuit is _____ (rounded off to 1 decimal place).



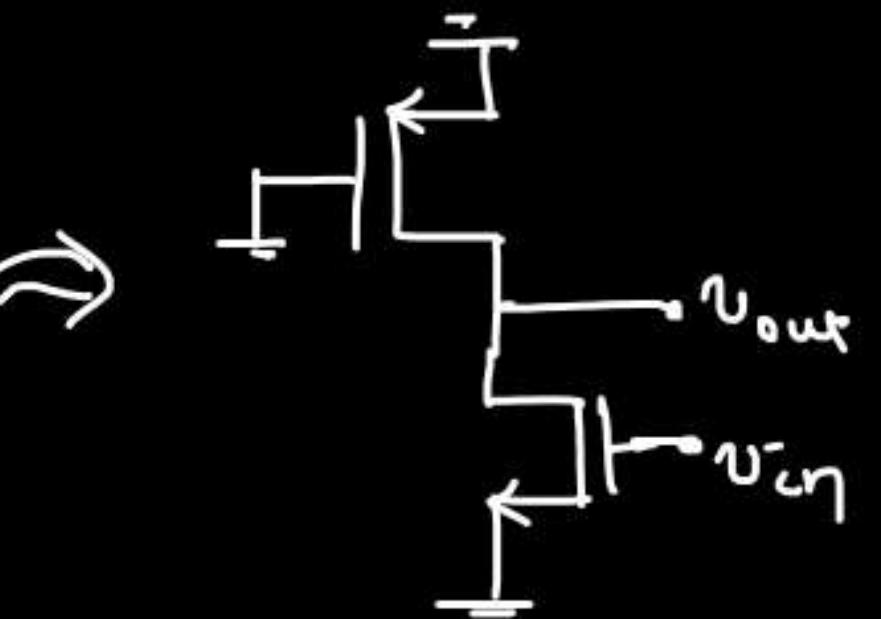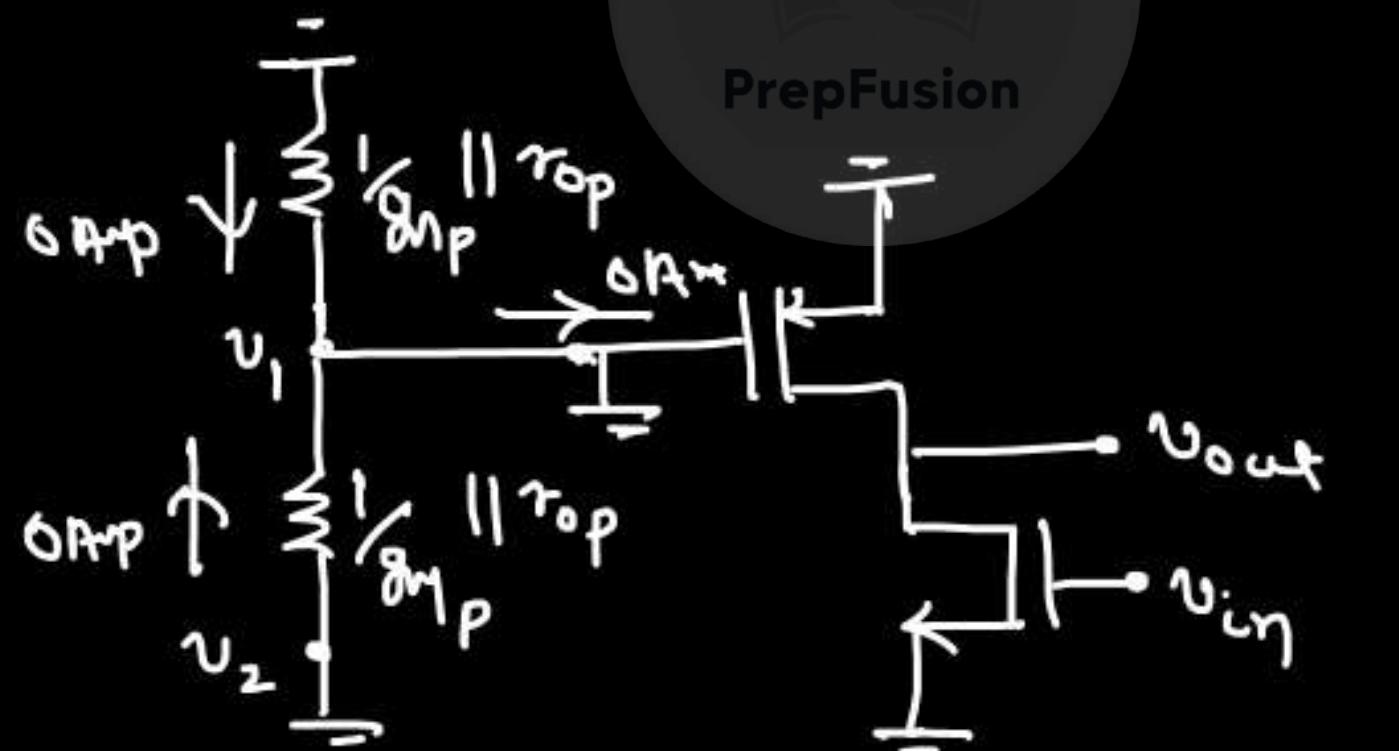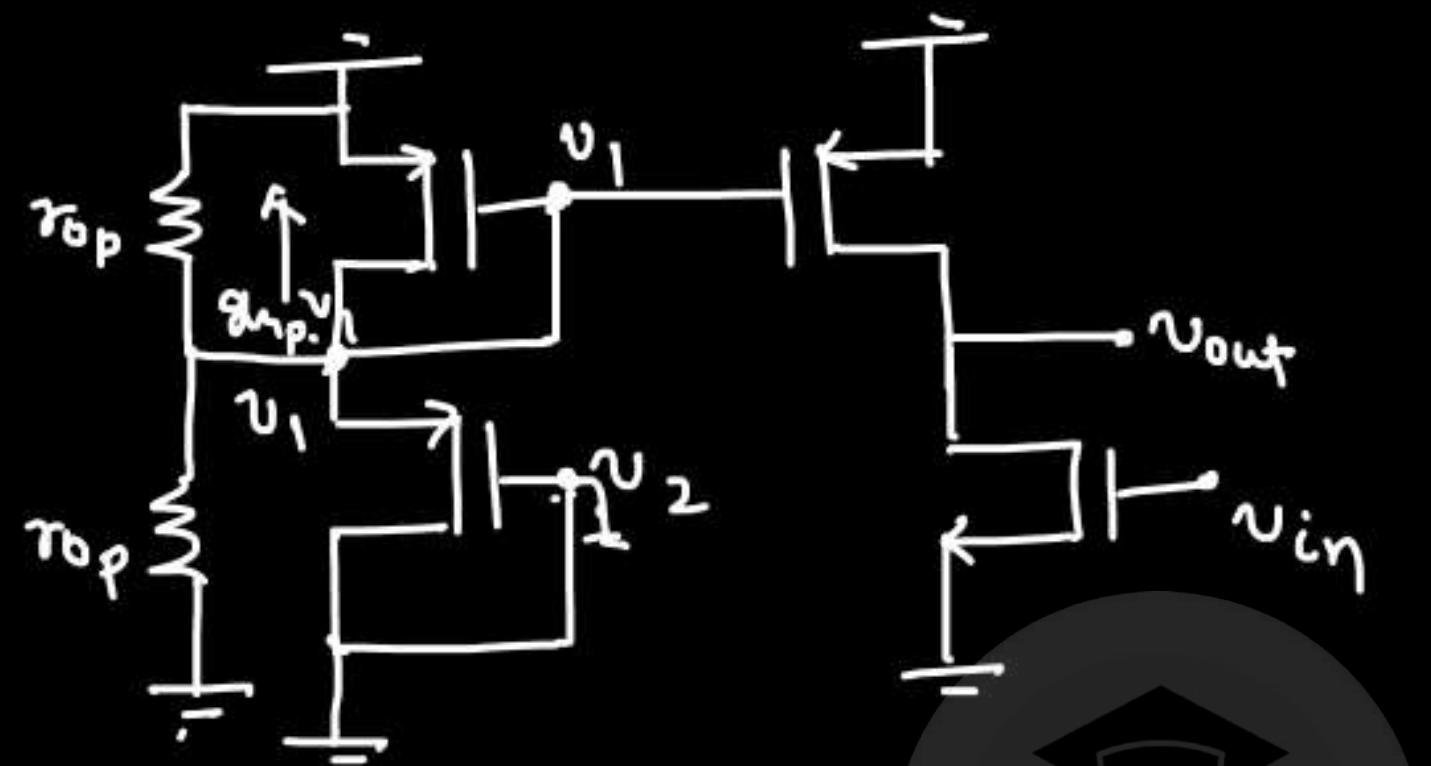

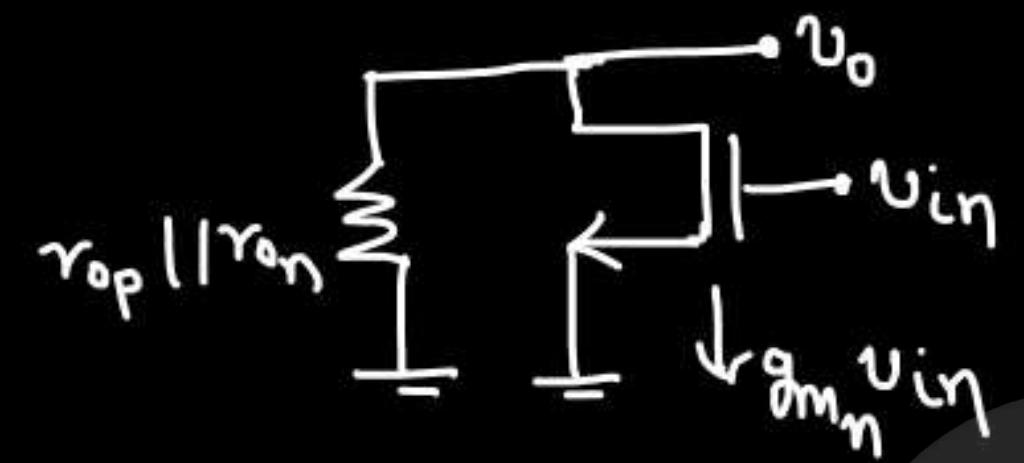


$$\frac{u_o}{u_i} = -g_m \eta [r_{op} || r_{o\eta}]$$

$$r_{op} = r_{o\eta} = 6M\Omega$$

Pre Mission = ?

$$g_m \eta = \sqrt{\frac{2 \mu_n C_{ox} W}{L} I_{D_N}}$$

$$I_{D_N} = ?$$

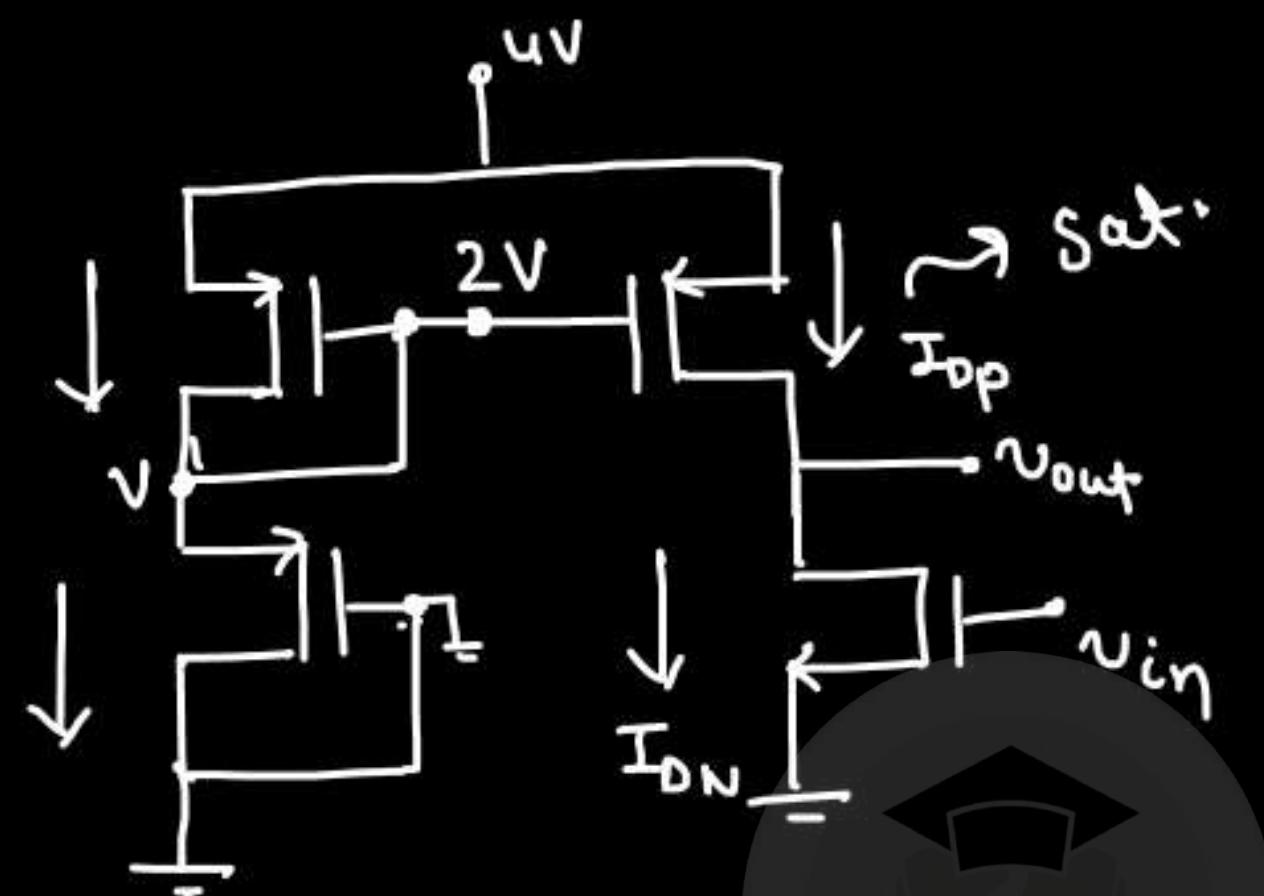

PrepFusion

$$\frac{\mu_p C_{ox} W}{2L} [4 - V_a - 1]^2 = \frac{\mu_p C_{ox} W}{2L} [V_a - 1]^2 \quad \left\{ \lambda \rightarrow \text{very small} \right\}$$

$$3 - V_a = V_a - 1$$

$V_a = 2V$

$$I_{Dp} = \frac{\mu_p C_{ox} W}{2L} (V_{SG} - V_T)^2$$

$$I_{Dp} = \frac{300 \mu}{2} (2 - 1)^2$$

$$I_{Dp} = 150 \mu \text{Amp.} = I_{DN}$$

$$\tau_{m\eta} = \sqrt{2 \times 300 \mu \times 150 \mu} = 300 \mu s$$

PrepFusion

$$\Delta V = -g_m p [r_{op} || r_{o\eta}]$$

$$r_{op} = r_{oN} = 6 M\Omega$$


$$= -300 \mu \times [6M || 6M]$$

$$= -3 \times 10^{-4} \times 3 \times 10^6 = -900$$

$\Delta V = -900 \text{ V/V}$


Ans.

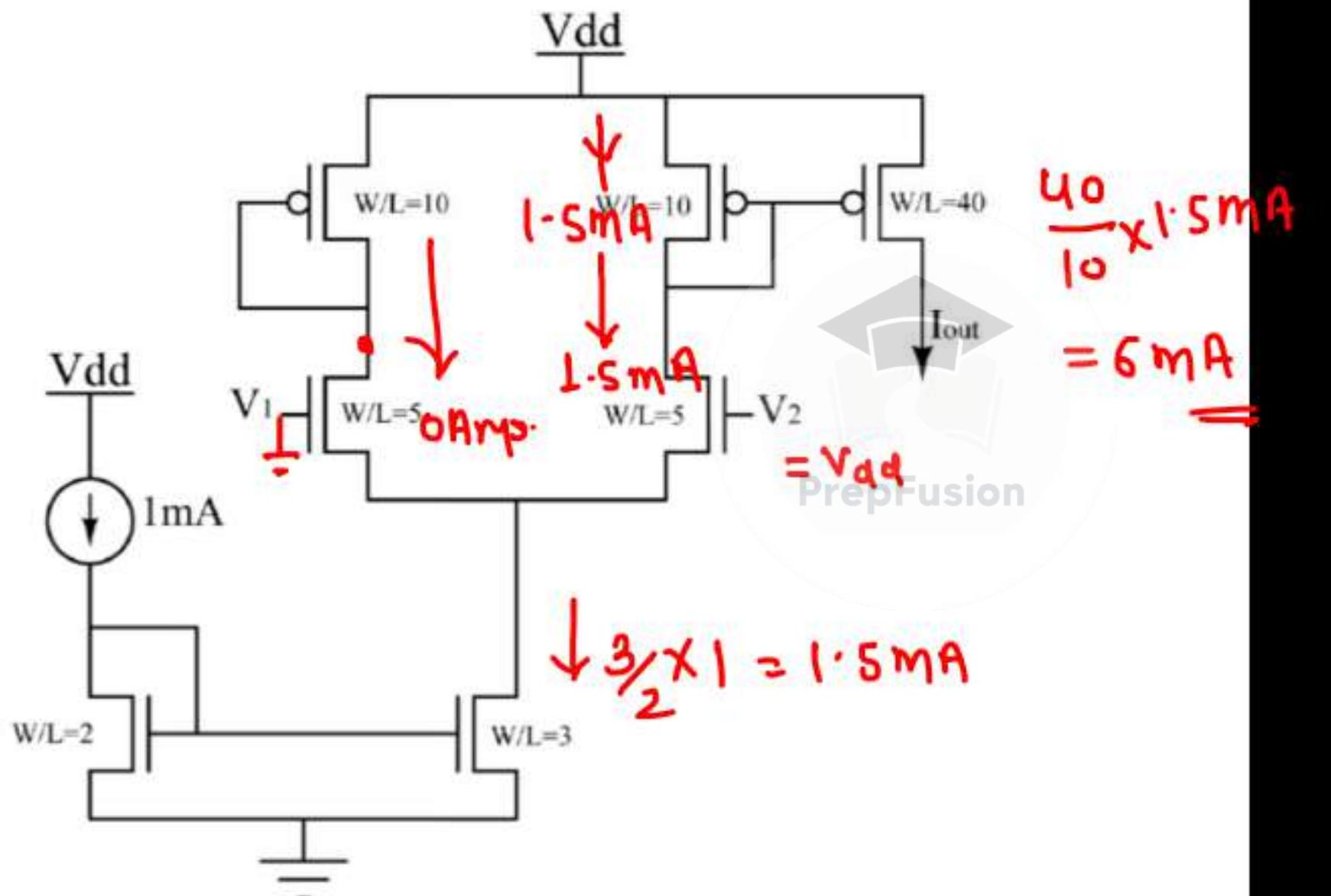In the circuit shown, $V_1 = 0$ and $V_2 = V_{dd}$. The other relevant parameters are mentioned in the figure. Ignoring the effect of channel length modulation and the body effect, the value of I_{out} is _____ mA (rounded off to 1 decimal place).



Assignment-9 [Fusion_Special]

Q.

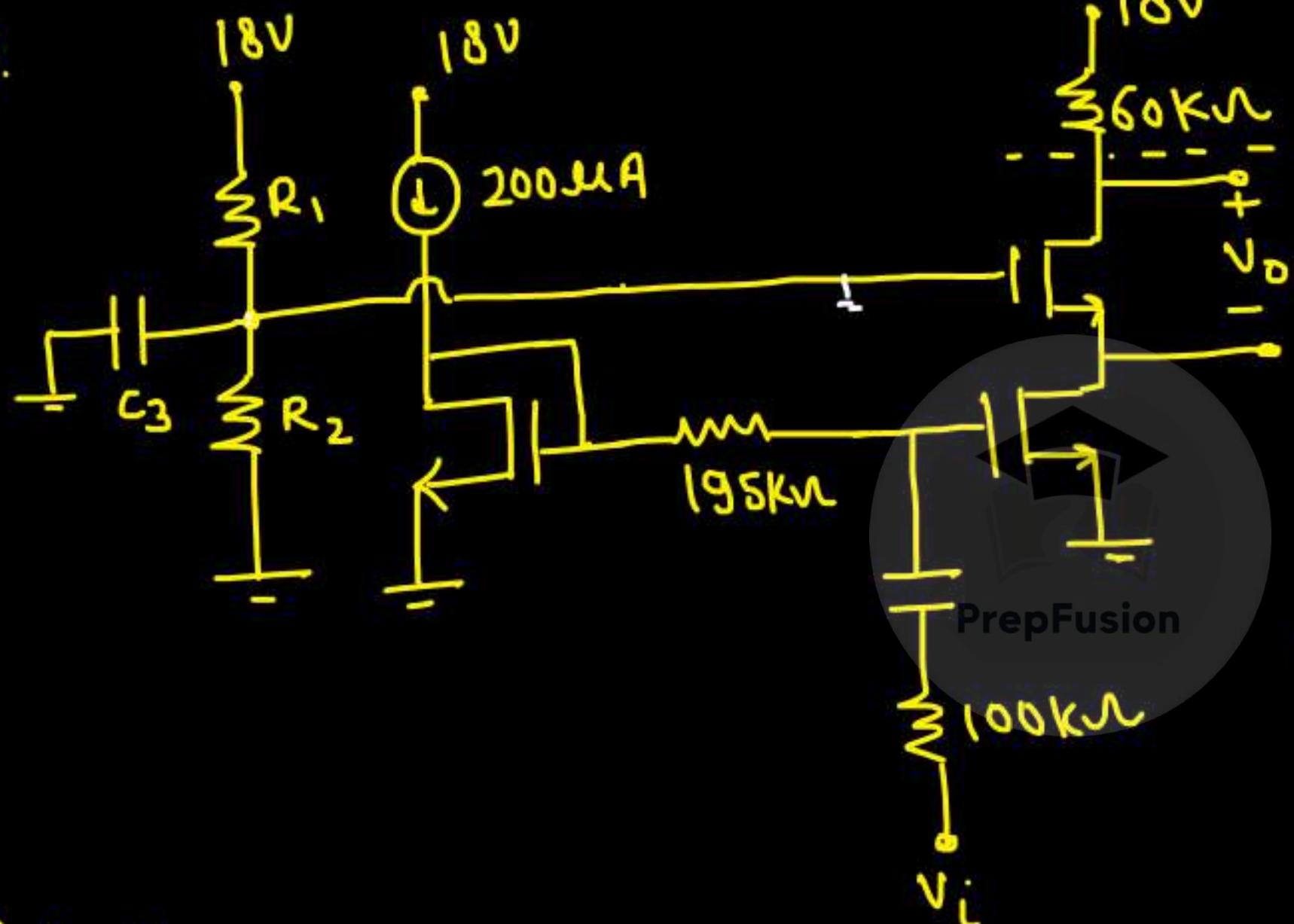

(a) Find small signal
voltage gain $\frac{v_o}{v_i} \cdot (\lambda=0)$


(b) find small signal
 $R_o \cdot (\lambda=0.05 \text{ V}^{-1})$

Given that all Tr are
working in Sat. region.

$$M_{nCo} \times \frac{W}{L} = 100 \mu\text{A}/\text{V}^2$$

$$V_T = LV$$

→ DC Analysis: -

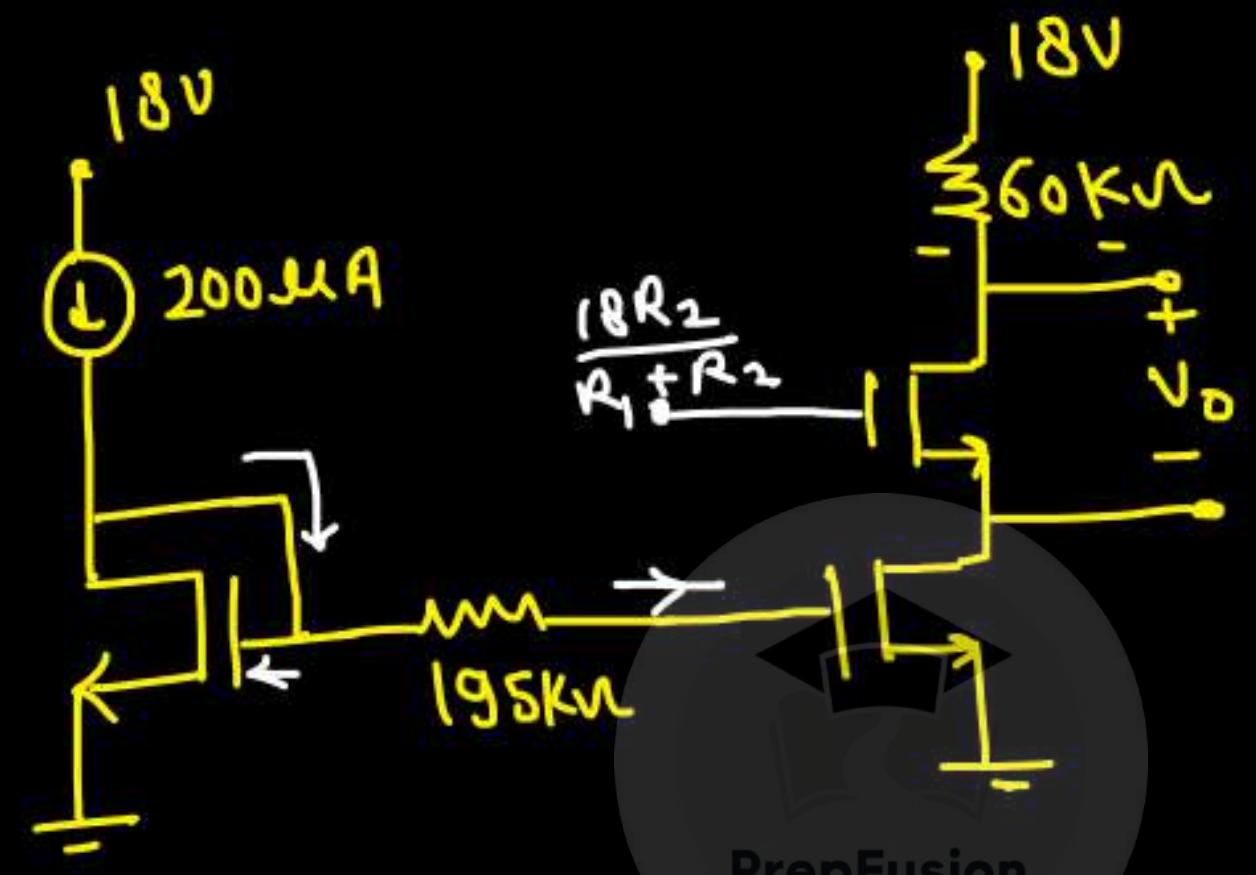

PrepFusion

$$I_D = 200 \mu A$$


$$g_m = \sqrt{2 \mu n C_{ox} W L} I_D = 200 \mu S$$




$$\delta m = 200 \mu S$$

$$1/g_m = 5 k\Omega$$

Ac analysis: -

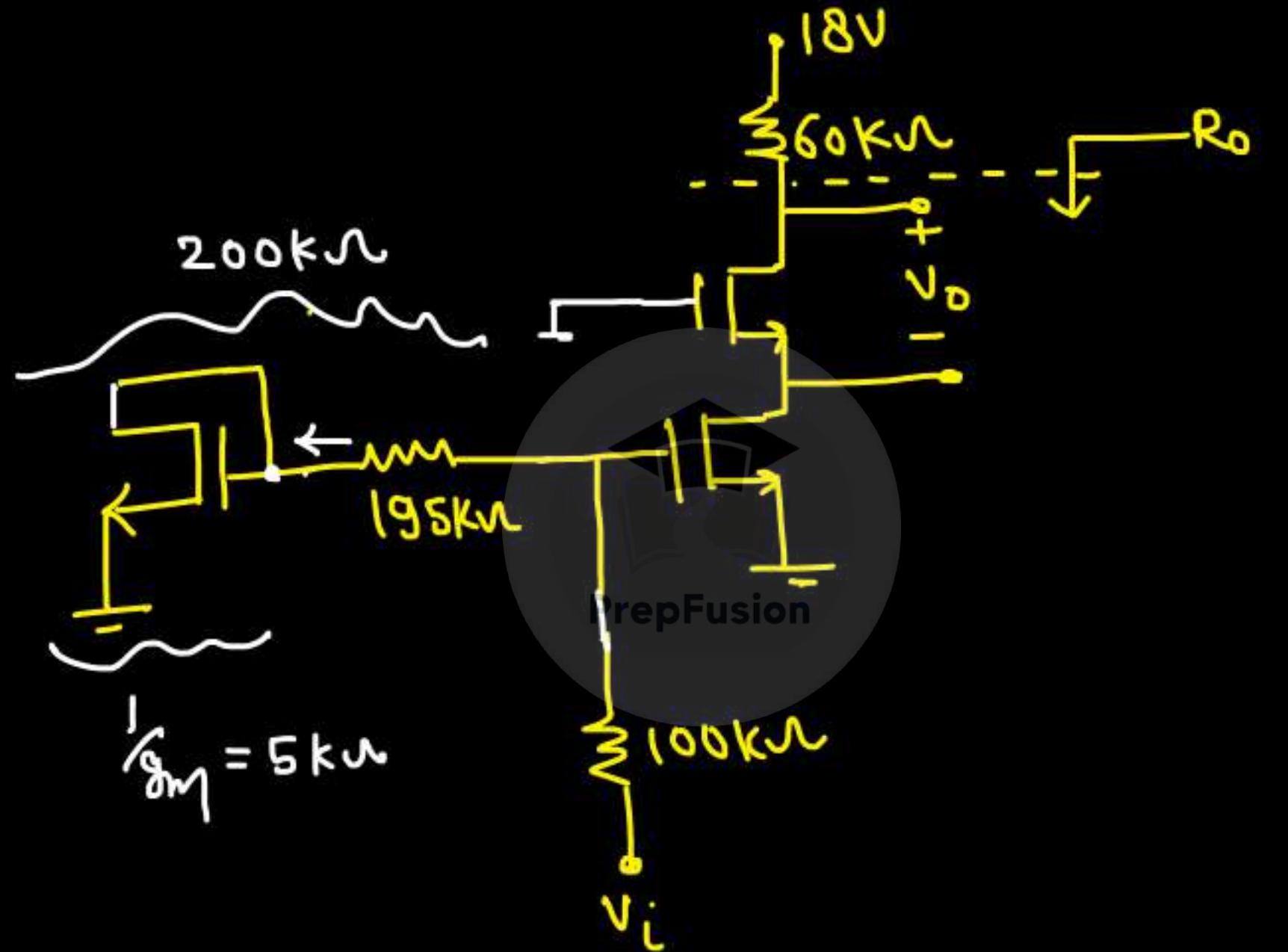

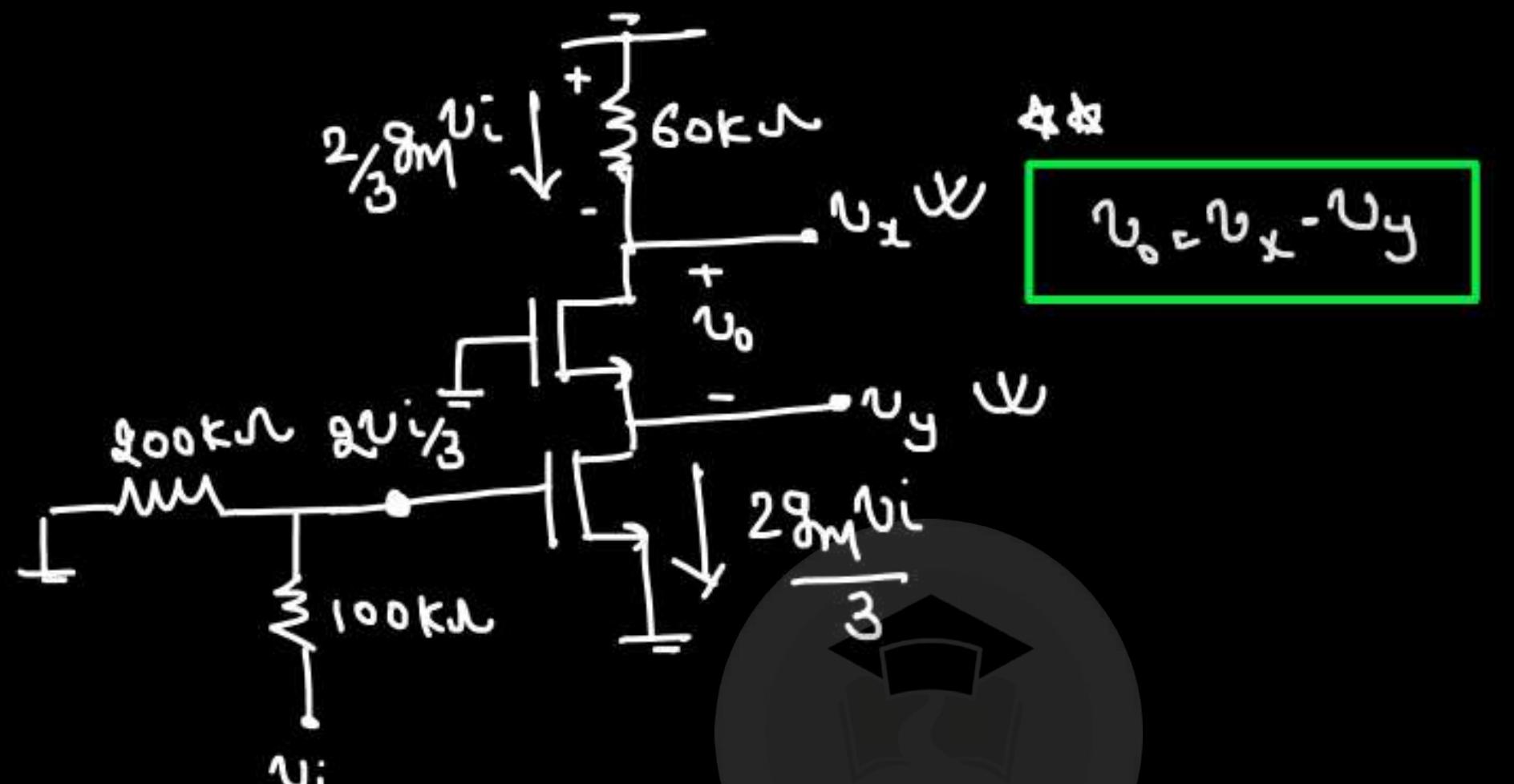


$$v_0 = -\frac{2}{3} g_m v_i \times 60 \text{ km} \quad \times$$

$$v_x = -\frac{2}{3} \cdot 8m \cdot v_i \times 60kN$$

$$= -\frac{2}{3} \times 200 \mu \times 60k \times v_i$$

$$v_x = -8v_i$$

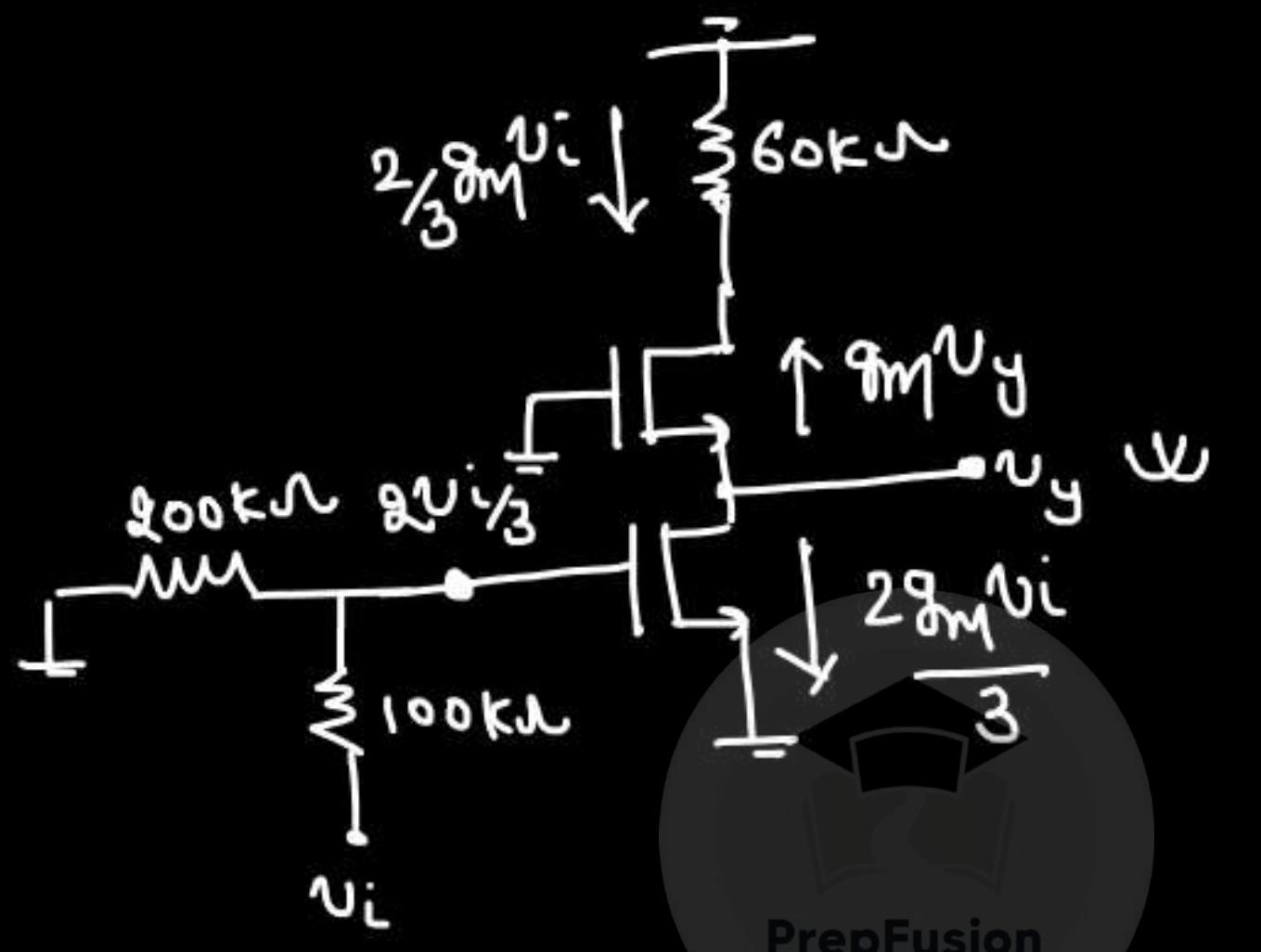

PrepFusion

$$gmU_y = - \frac{2}{3} gmU_i$$


$$U_y = - \frac{2}{3} U_i$$

$$\begin{aligned} U_o &= U_L - U_y \\ &= -8U_i + \frac{2}{3} U_i \end{aligned}$$

$$U_o = -7.33 U_i$$

$$\frac{U_o}{U_i} = -7.33$$

R_o :-

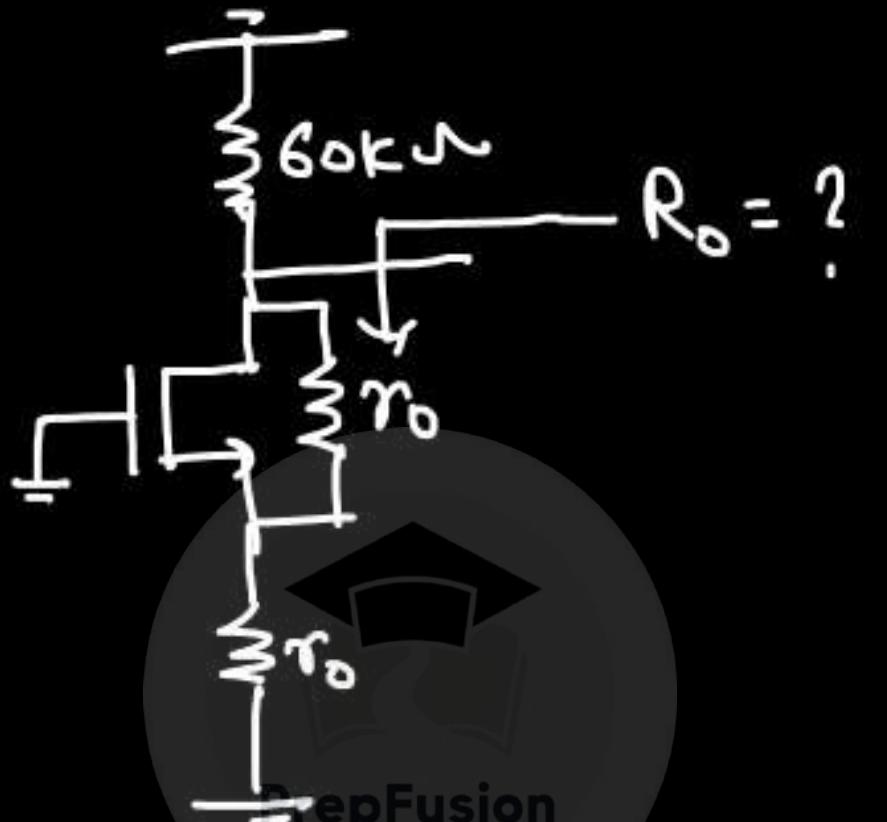


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.05 \times 200 \mu}$$

$r_o = 100k\Omega$

$$\begin{aligned} R_o &= g_m r_o r_o + r_o + r_o \\ &= g_m r_o^2 + 2r_o \\ &= 200 \mu \times 10^{10} + 2 \times 10^5 \\ R_o &= 2.2 M\Omega \end{aligned}$$


Q. M_0 and M_1 are perfectly Matched.

(a) Determine current I_1

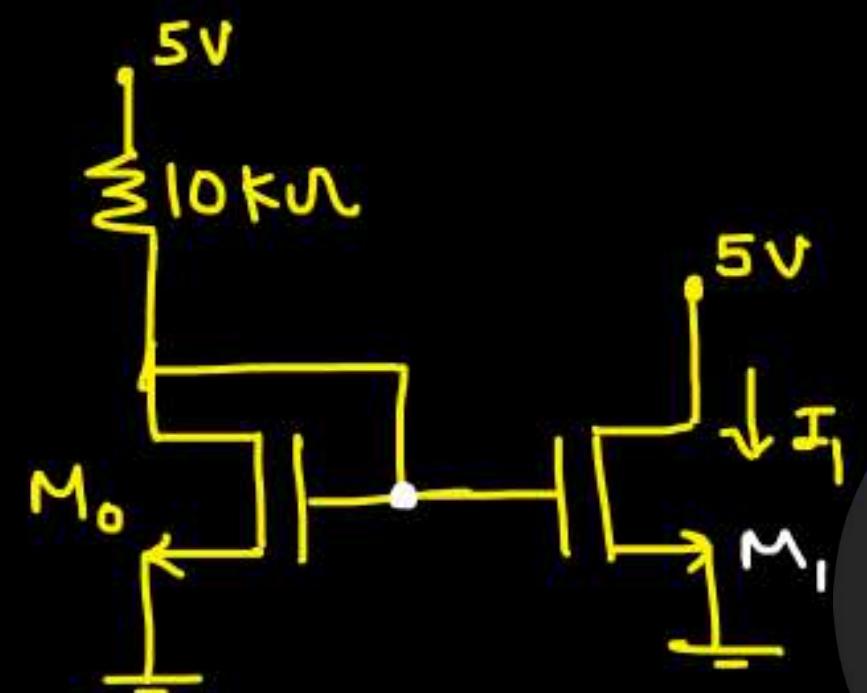

$$\mu n C_{ox} = 100 \mu A/V^2, \quad W/L = 1, \quad V_T = 1V$$

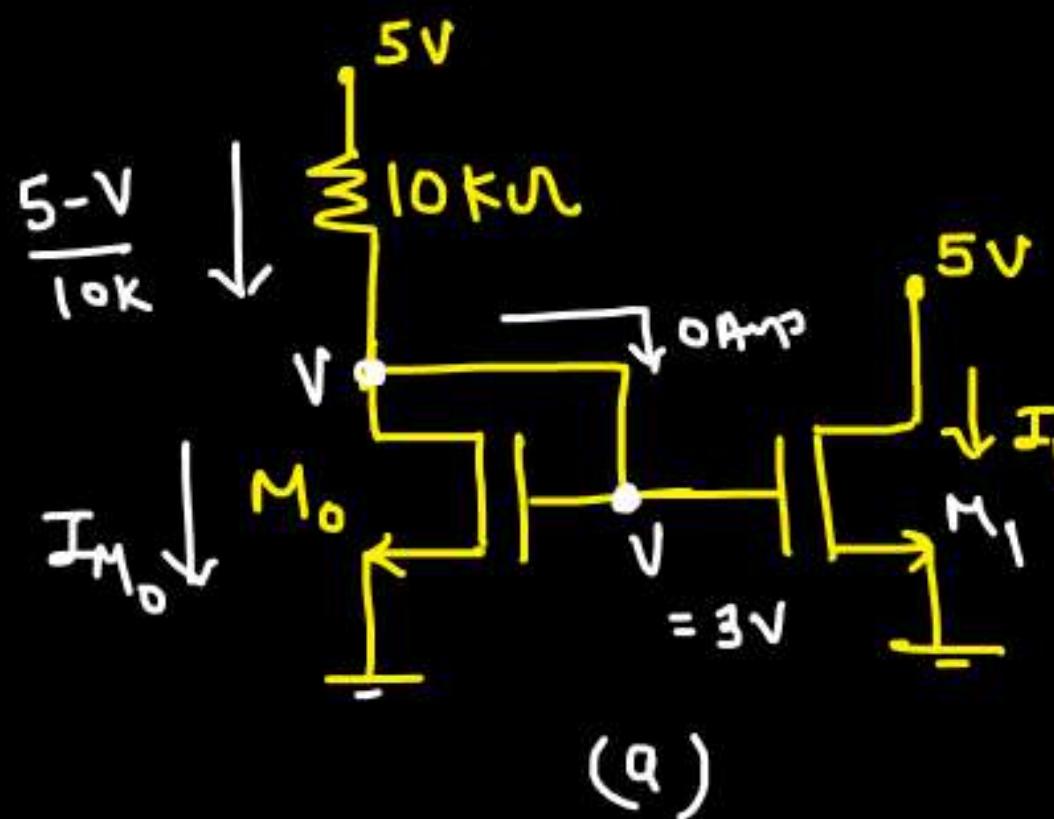(b) V_{DD} increases to 5.5V. Determine the increase in I_1 .



$$I_{M_0} = \frac{4\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$\frac{5-V}{10k} = \frac{100\mu}{2} (V - 1)^2$$

$$5-V = (V-1)^2 / 2$$


PrepFusion
 $10-2V = V^2 + 1 - 2V$

V = 3V_{DS}ukt

I = 200 μA

M₁ →
 $V_{DS} = 5V$
 $V_{GS} = 3V$
 $V_{DS} = 2V$
 Dots →
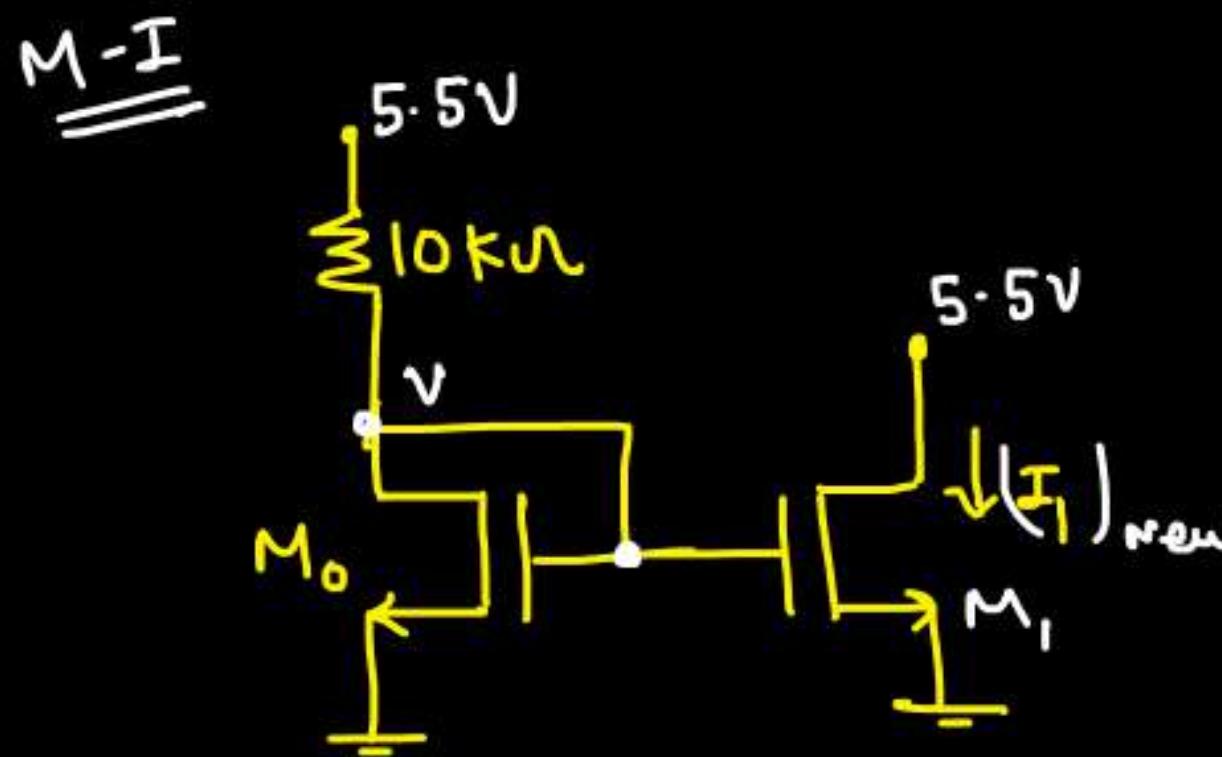
$$I_{M_0} = \frac{5-3}{10k} = \frac{2}{10k} = 200 \mu A = I_1$$



$$\Rightarrow \frac{5.5-V}{10k} = \frac{100\mu}{2} (V-1)^2$$

$$11-2V = V^2 + 1 - 2V$$

$$V^2 = 10$$

$$V = 3.16 \text{ Volt}$$



PrepFusion

$$(I_{M0})_{new} = (I_1)_{new} = \frac{5.5 - 3.16}{10k}$$

(I1)_{new} = 233 \mu A

Ans

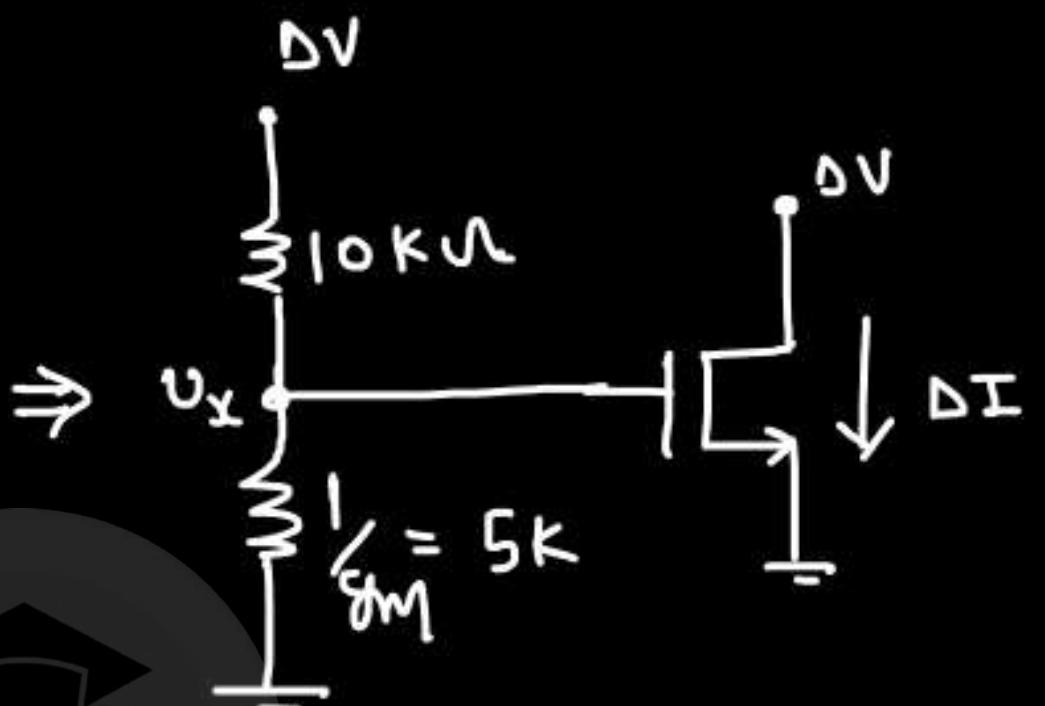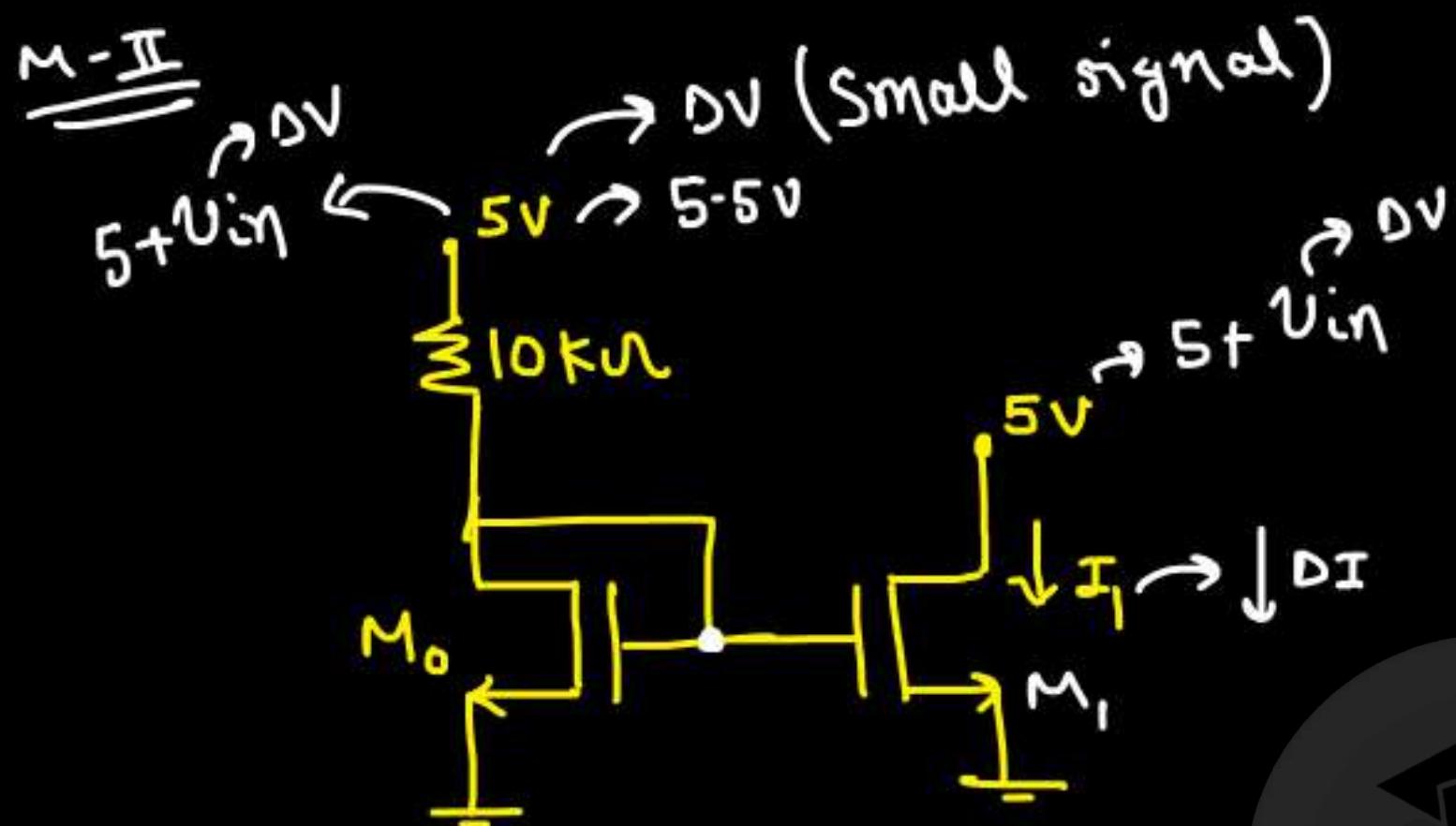$\Delta I = 233 \mu A - 200 \mu A = 33 \mu A \uparrow$



$$g_m = \sqrt{\frac{2\mu n C_{ox} W}{L}} I_D$$

$$= \sqrt{2 \times 100 \mu \times 200 \mu}$$

$$g_m = 200 \mu S$$

$$\frac{1}{g_m} = 5 k\Omega$$

PrepFusion

$$u_x = \frac{5k}{5k + 10k} \times DV = \frac{DV}{3}$$

$$\Delta I = g_m u_x = \frac{g_m DV}{3} = \frac{200 \mu}{3} DV$$

* *

$$\Delta I = \frac{200 \mu}{3} DV$$

Here ; $\Delta V = 5.5 - 5 = 0.5V$

$$\Delta I = \frac{200\mu}{3} \times 0.5$$


$\Delta I = 33.33 \mu\text{Amp}$

For supply,

(i) $5.1V \Rightarrow \Delta I = \frac{200\mu}{3} \times 0.1 = 6.66 \mu\text{Amp}$

(ii) $5.3V \Rightarrow \Delta I = \frac{200\mu}{3} \times 0.3 = 20 \mu\text{Amp}$

Q.

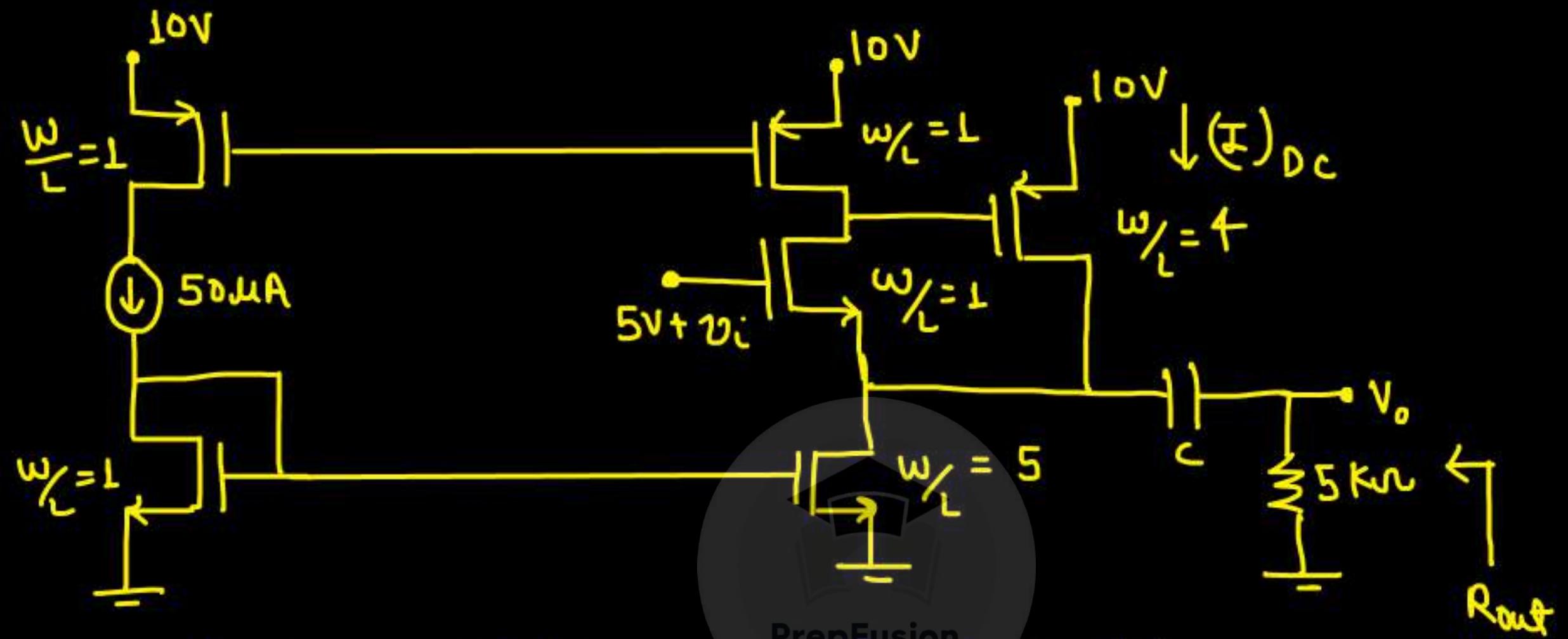


$$\mu_n C_{ox} = 100 \mu A/V^2, \quad \mu_p C_{ox} = 25 \mu A/V^2$$

$$V_{TH} = 1V$$



Given \rightarrow all Trs are biased in sat.


- (a) Determine I_{DC}
- (b) Find small signal voltage gain
- (c) Find small signal R_{out} .

DC Analysis:-

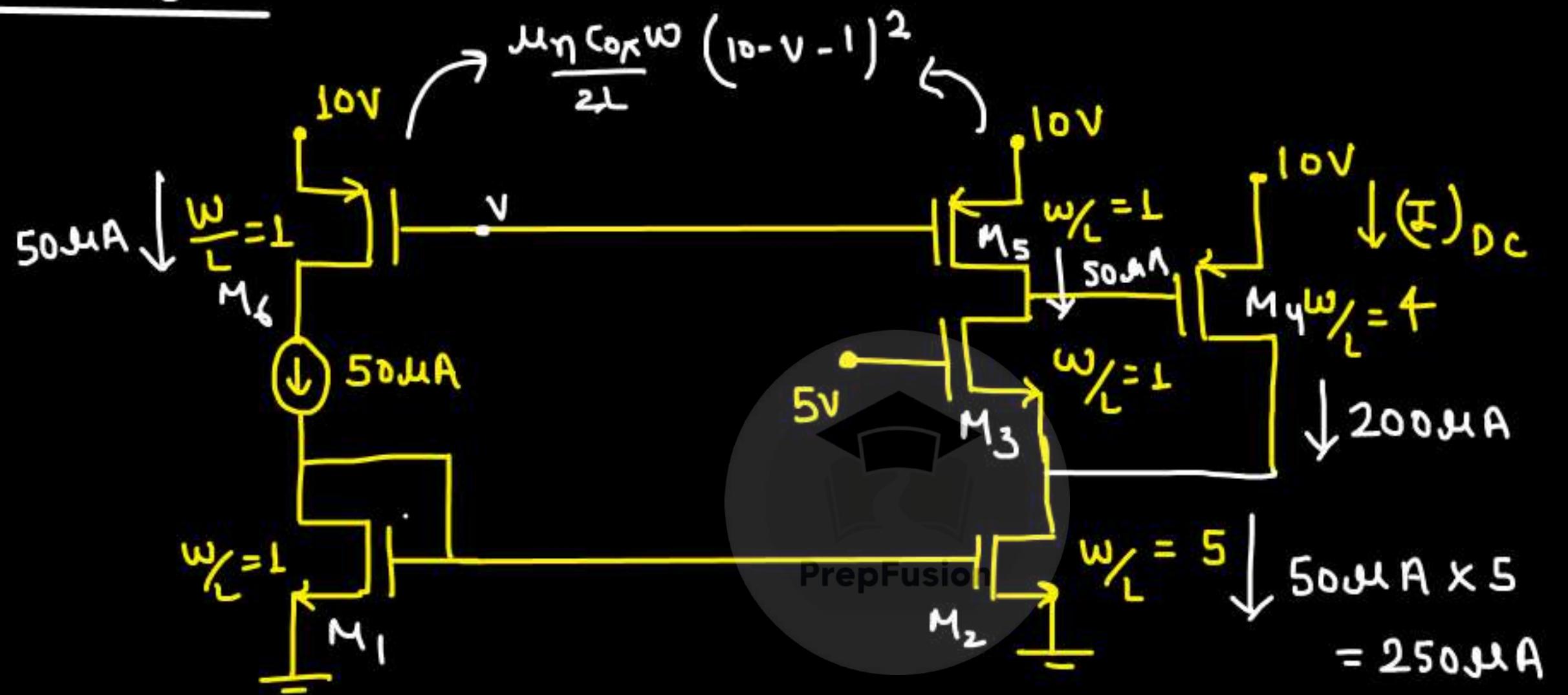

AC Analysis:-

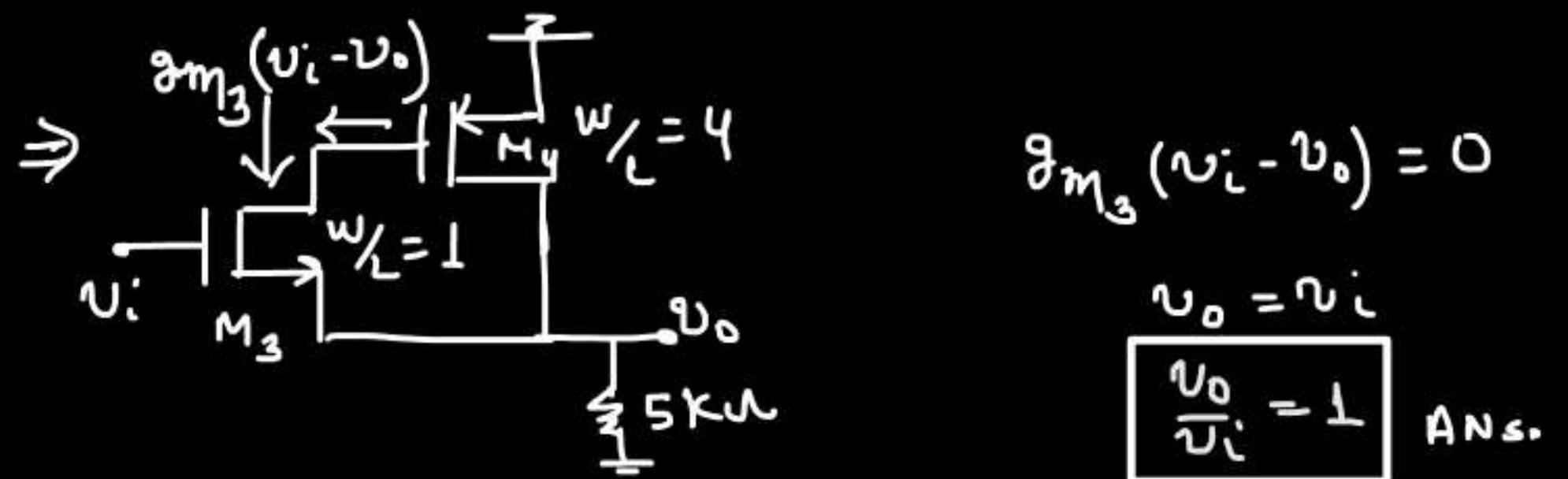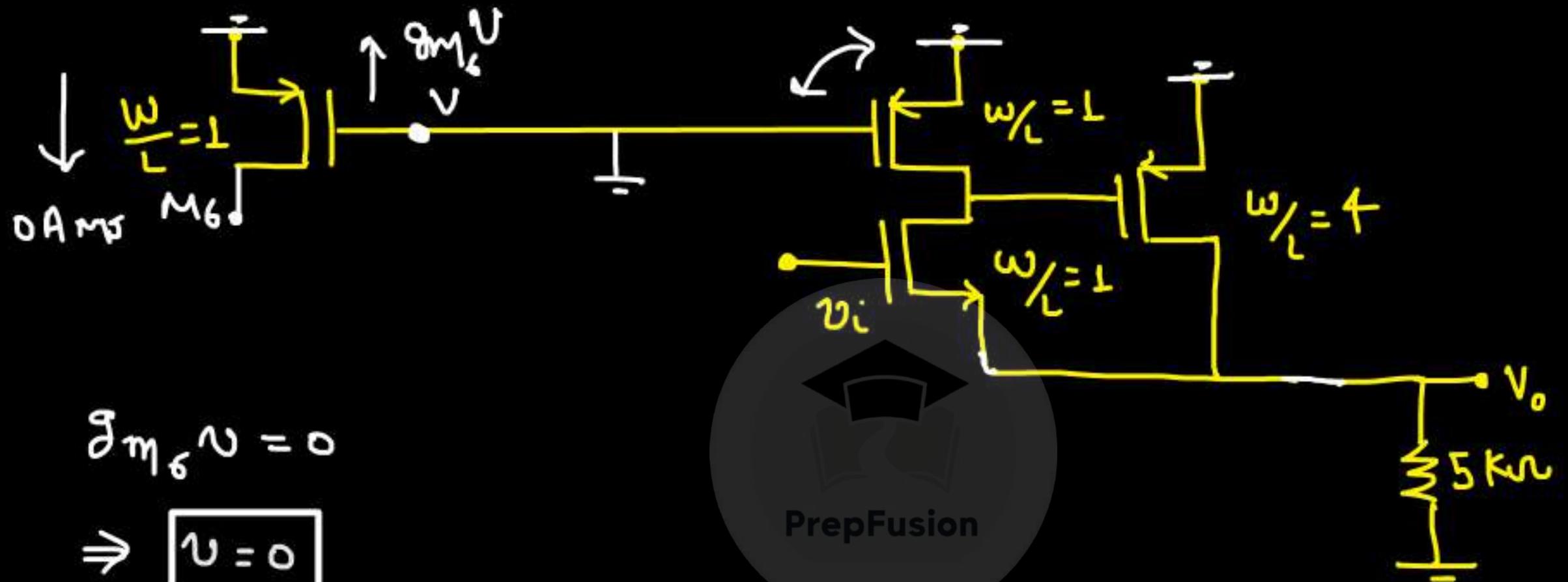

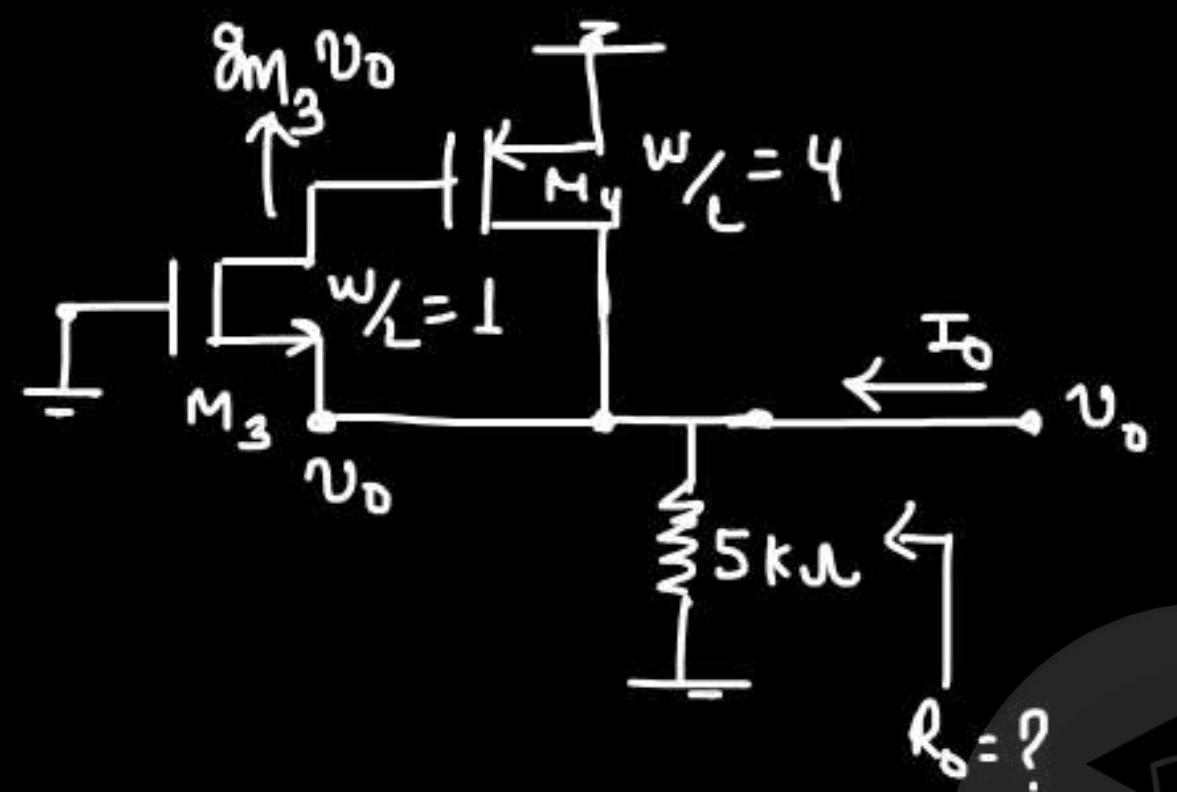

$$\frac{V_o}{I_o} = R_o$$


$$g_m M_3 V_D = 0$$

$$V_o = 0$$

$$R_o = \frac{0}{I_o} = 0 \text{ }\Omega$$



Q.

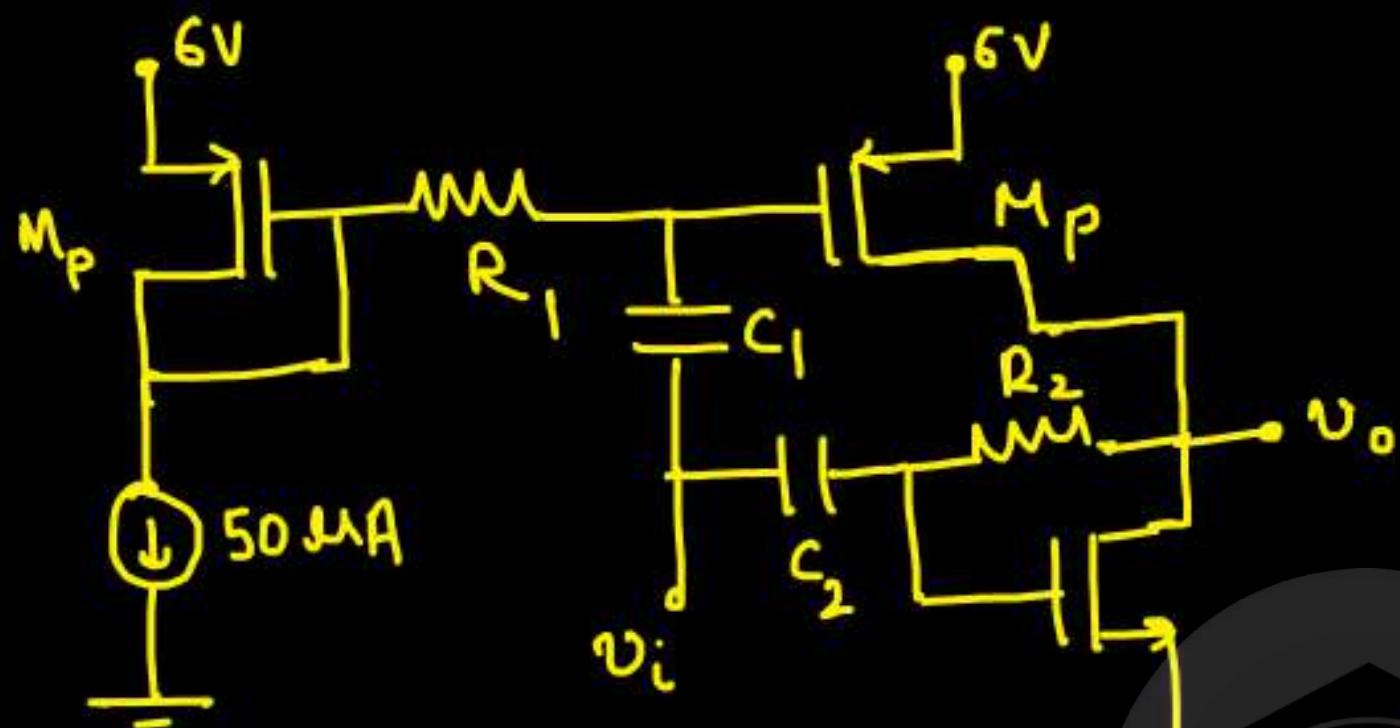

Given $\rightarrow R_1, R_2$ values are very large.


PrepFusion

$$M_P: \mu_P C_{ox} = 100 \text{ mA/V}^2, \frac{w_P}{L_P} = 4, V_{TP} = 0.5 \text{ V}, \lambda_P = 0.05 \text{ V}^{-1}$$

$$M_N: \mu_N C_{ox} = 400 \text{ mA/V}^2, \frac{w_N}{L_N} = 1, V_{TN} = 0.6 \text{ V}, \lambda_N = 0.05 \text{ V}^{-1}$$

Determine small signal voltage gain $\frac{v_o}{v_i}$?

DC Analysis :-

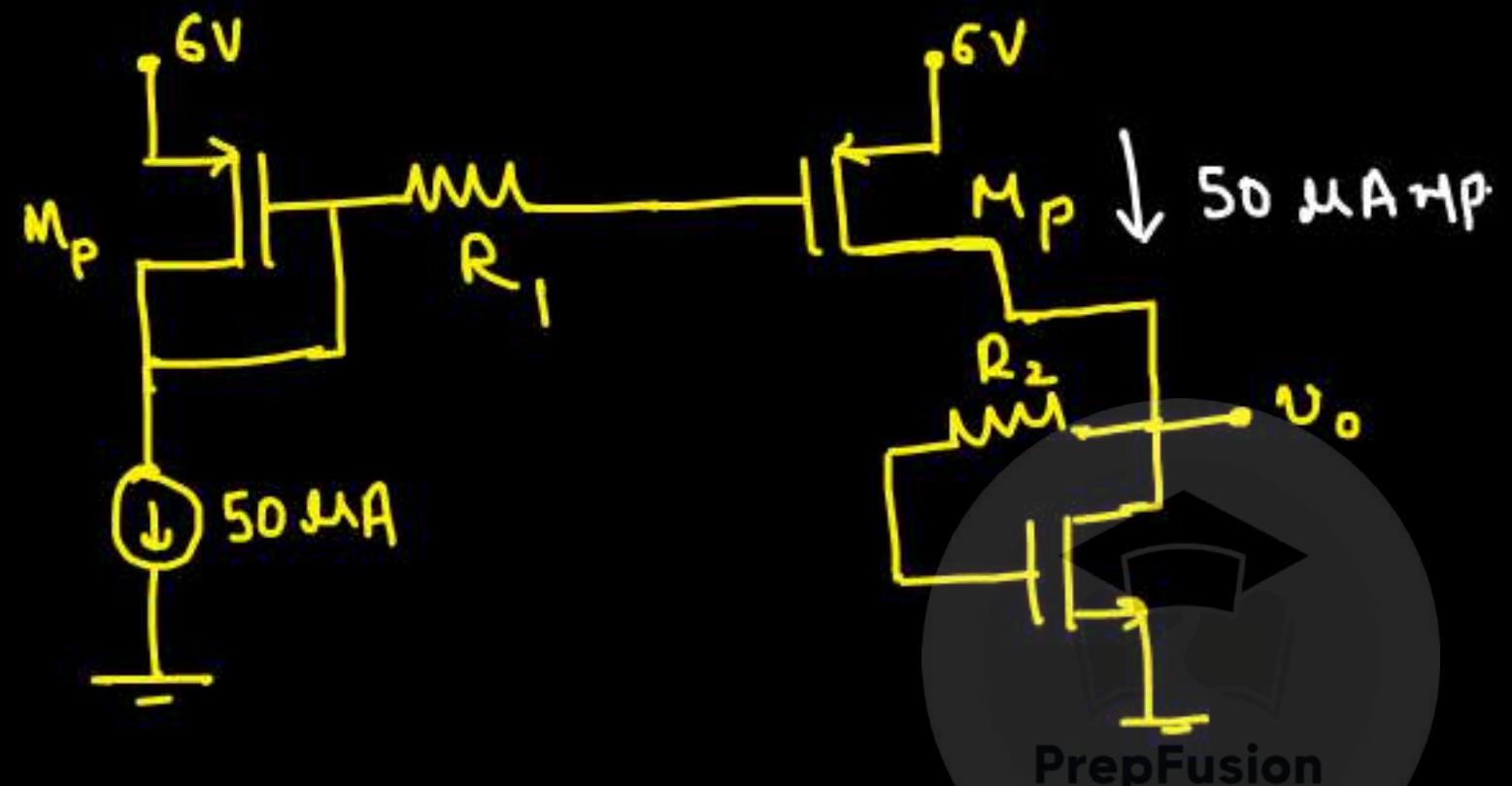

$$g_{m_P} = \sqrt{2 \times \frac{\mu_P C_{ox} W}{L}} I_D = \sqrt{2 \times 400 \mu \text{A} \times 50 \mu \text{A}} = 200 \mu \text{s}$$


$$g_{m_\eta} = \sqrt{2 \times \frac{\mu_\eta C_{ox} W}{L}} I_D = \sqrt{2 \times 400 \mu \text{A} \times 50 \mu \text{A}} = 200 \mu \text{s}$$

$$g_{m_P} = g_{m_\eta} = g_m = 200 \mu \text{s}$$


$$\gamma_{op} = \frac{1}{\lambda_p I_D} = \frac{1}{6.05 \times 50 \mu} = 400 \text{ k}\Omega$$

$$\gamma_{on} = \frac{1}{\lambda_n I_D} = \frac{1}{6.05 \times 50 \mu} = 400 \text{ k}\Omega$$

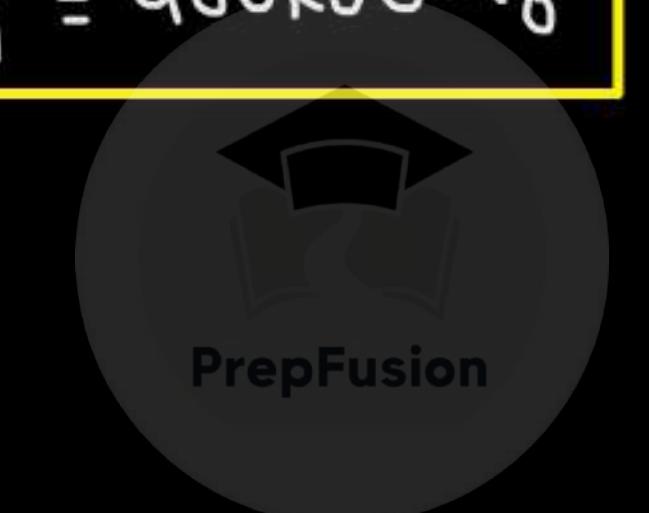$\gamma_{op} = \gamma_{on} = 400 \text{ k}\Omega = \gamma_0$




AC analysis:-

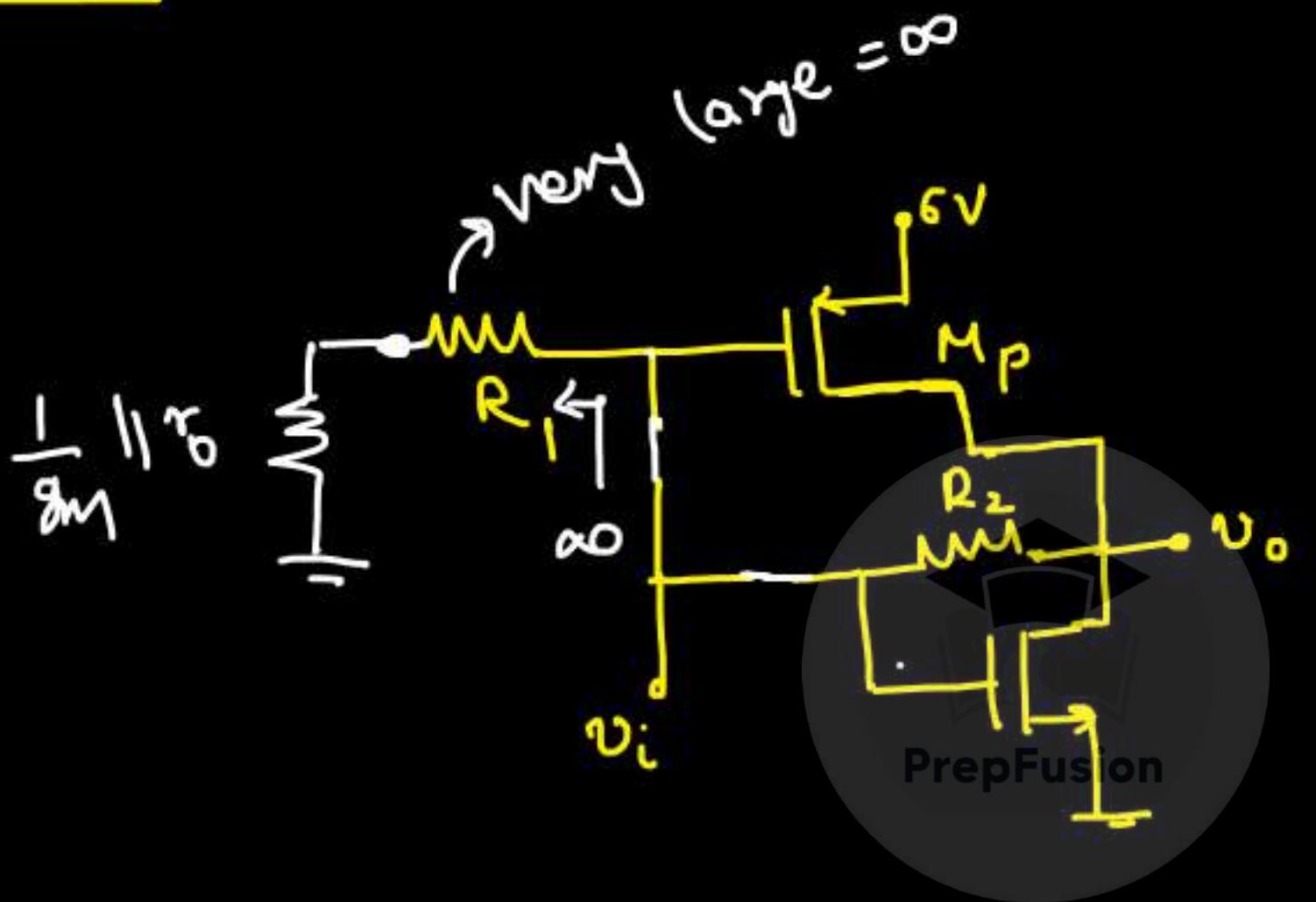

$$\frac{v_o}{r_{oP}} + \frac{v_o}{r_{o\eta}} + g_{mP}v_i + g_{m\eta}v_i = 0$$

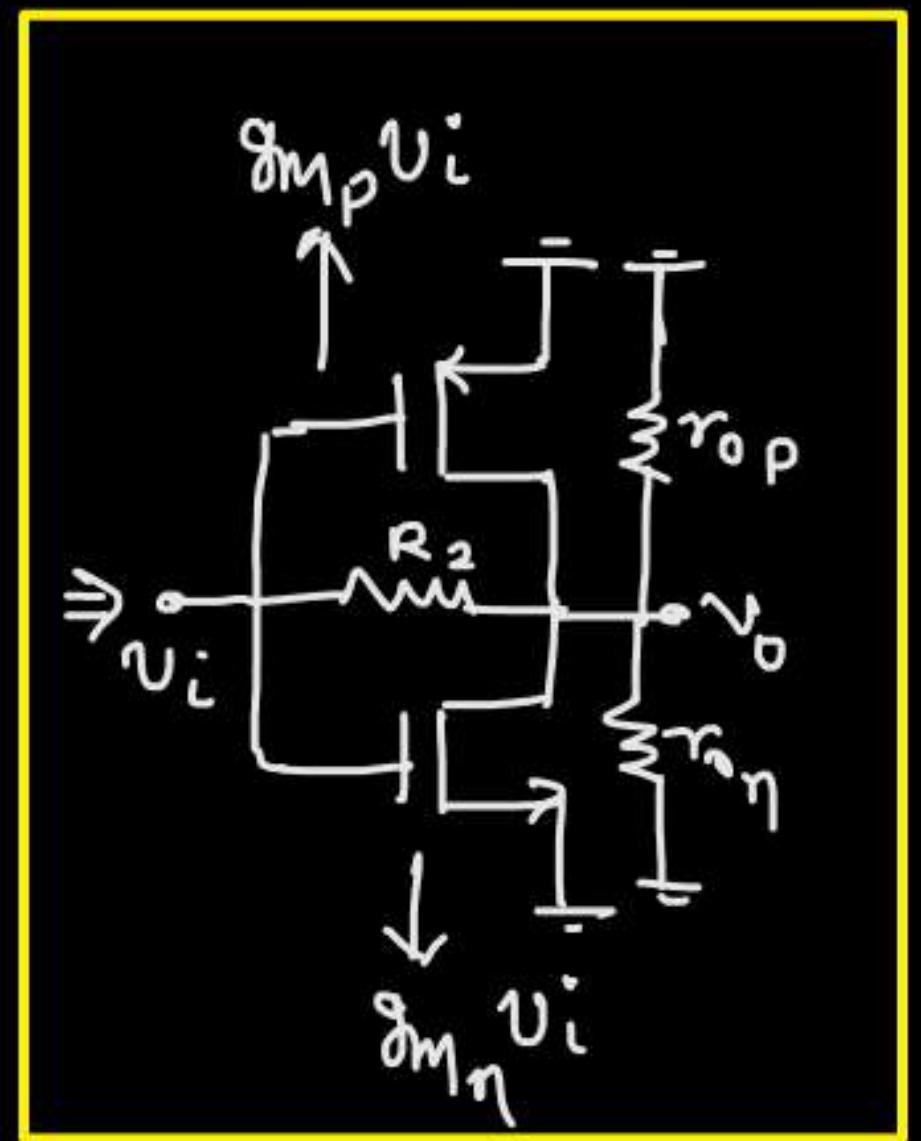
$$\frac{v_o}{r_{oP} \parallel r_{o\eta}} = - (g_{mP} + g_{m\eta}) v_i$$



$$\frac{v_o}{v_i} = - (g_{mP} + g_{m\eta}) (r_{oP} \parallel r_{o\eta})$$

$$\frac{v_o}{v_i} = - 400 \times 10^{-6} \times 200 \times 10^3 = -80$$

Q.

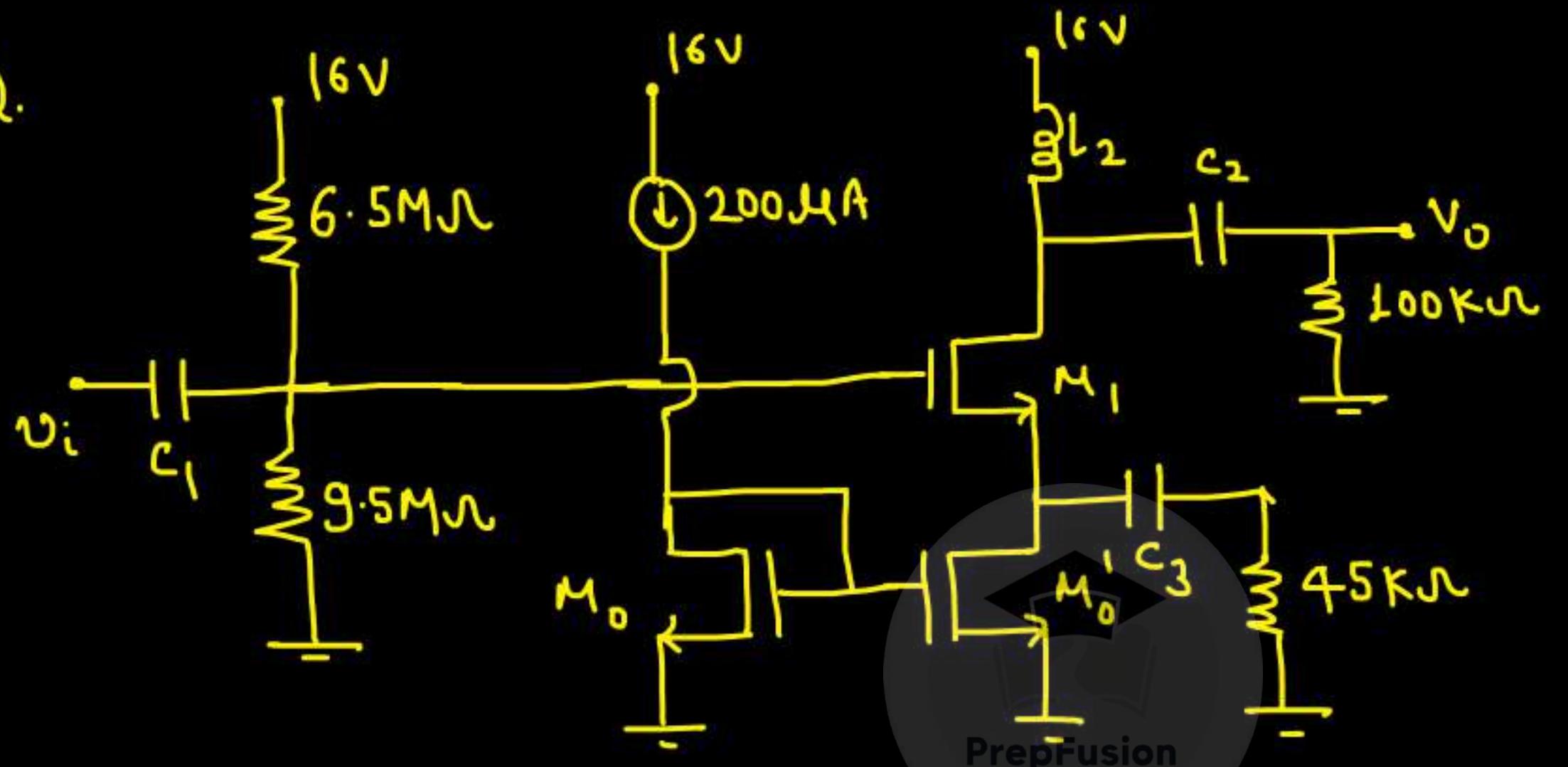


(a) Determine v_i for which M_1 enters into Triode region.

(b) Determine v_i for which M'_0 enters into Triode region.

$$\frac{I_n C_{ox} \omega}{L} = \frac{100 \mu A}{V^2} , V_T = 1V$$

⇒ Considering M_1 and M_0' are working in sat. region based on the given bias.

DC Analysis:-

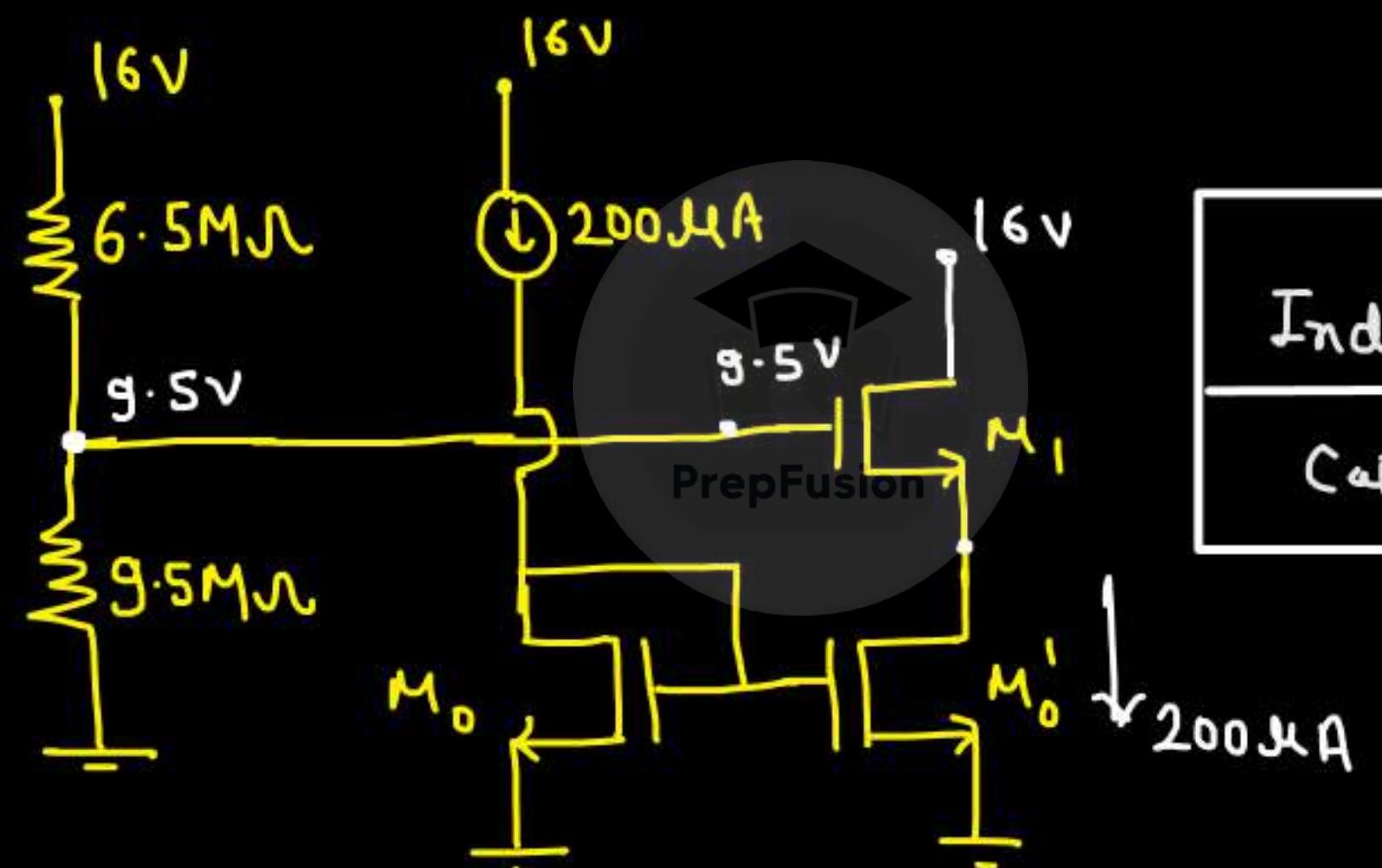



	DC S.C.	AC O.C.
Inductor		
Capacitor	O.C.	S.C.

$$I_{M_0'} = I_{M_1} = 200 \mu$$

$$200 \mu = \frac{100 \mu}{2} (V_{GS} - 1)^2$$


$$V_{GS} = 3V$$

For M_0' and M_1 $V_{GS} = 3V$

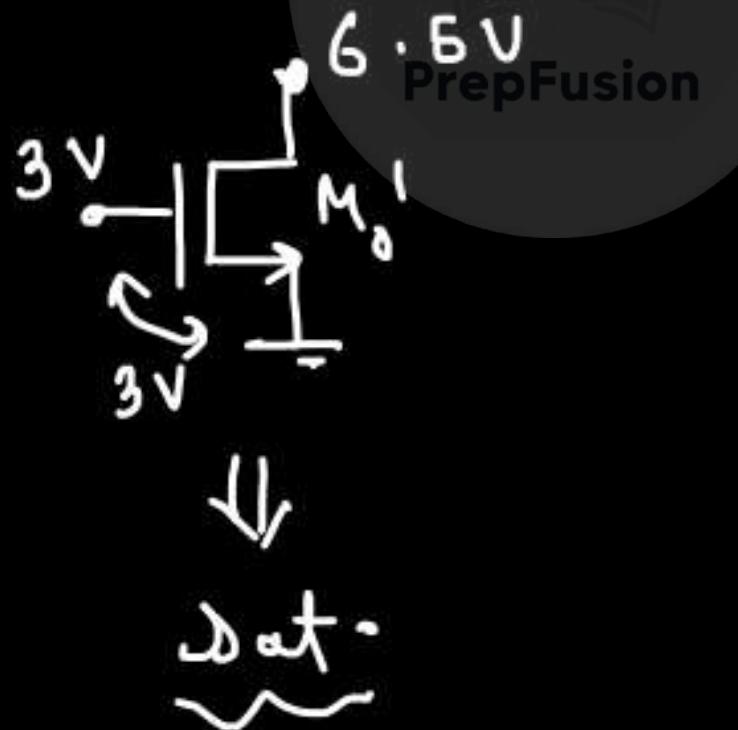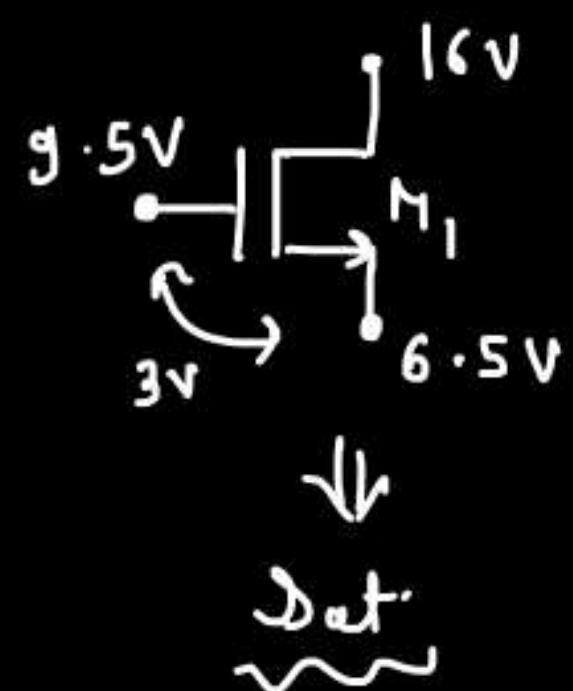



$$g_m = \frac{2 I_D}{V_{GS} - V_T} = \frac{2 \times 200 \mu}{3 - 1} = 200 \mu S$$

AC Analysis:-

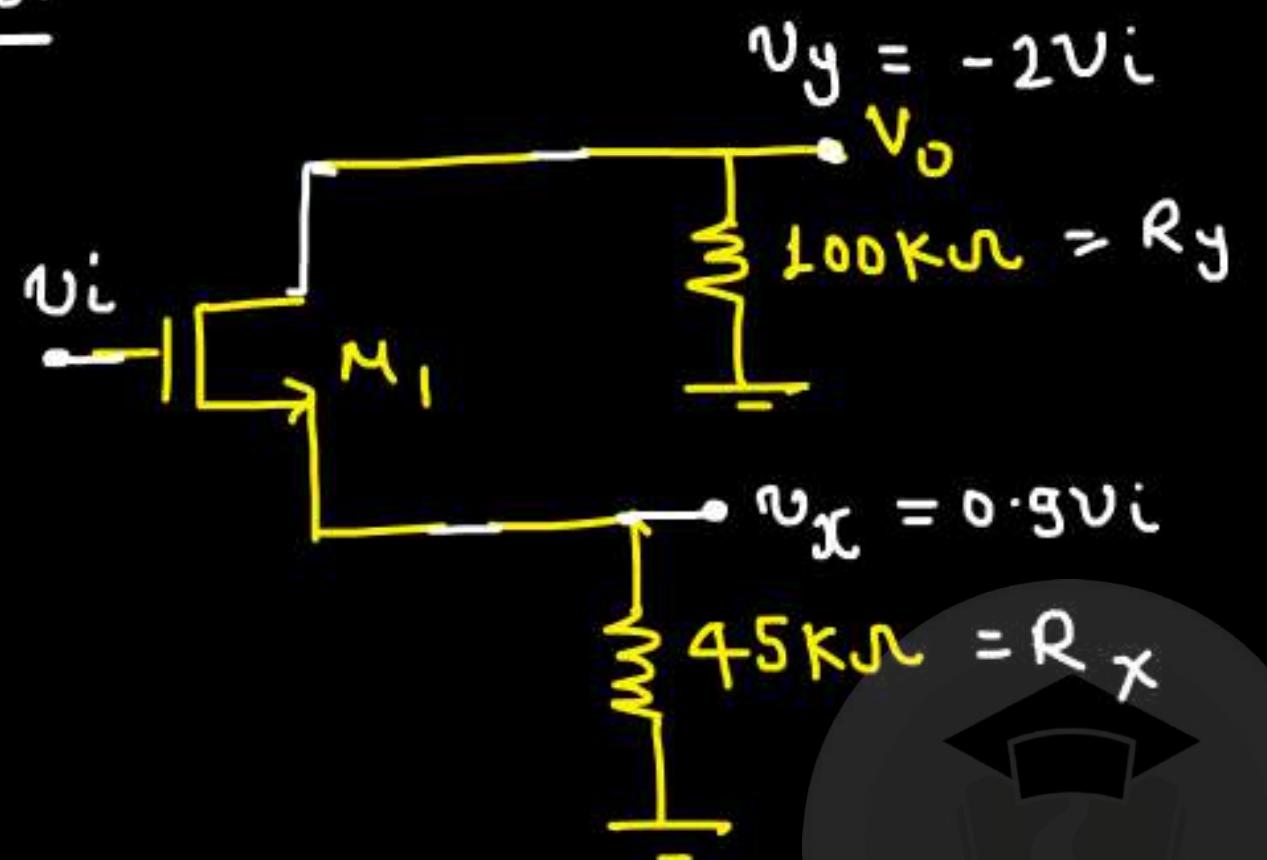

$$v_x = \frac{R_x}{R_y + 1/\text{gm}} v_i = \frac{\text{gm} R_x}{1 + \text{gm} R_x} v_i \stackrel{\text{PrepFusion}}{=} \frac{200\mu\text{x} 45\text{k}}{1 + 200\mu\text{x} 45\text{k}} v_i = 0.9v_i$$
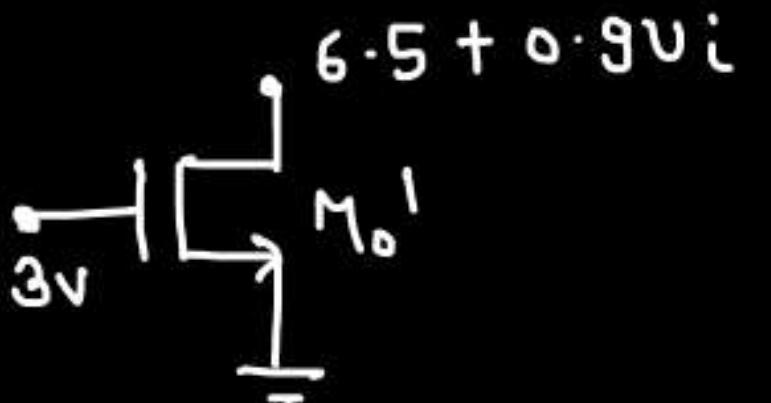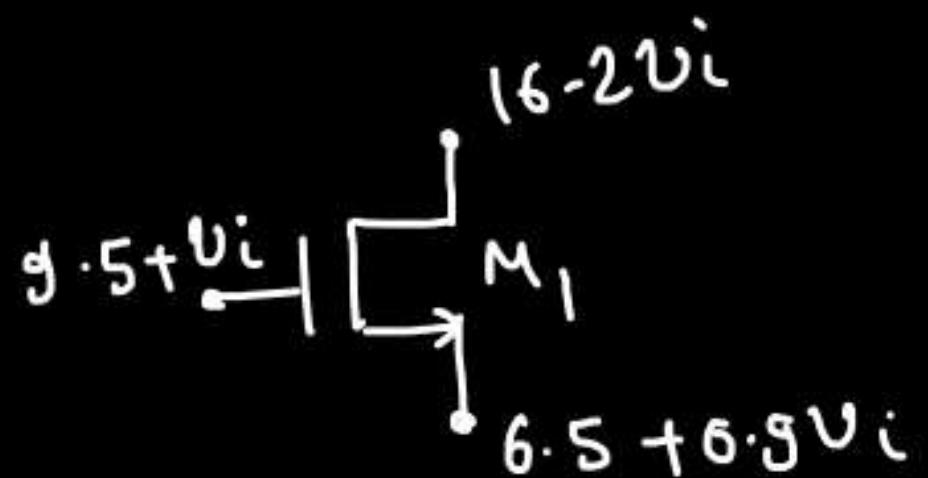
$$v_y = -\frac{\text{gm} R_y}{1 + \text{gm} R_x} v_i = -\frac{200\mu\text{x} 100\text{k}}{1 + 200\mu\text{x} 45\text{k}} v_i = \frac{-20}{10} v_i = -2v_i$$



(a) For M_1 to go into Triode :-

$$V_{DS} \leq V_{GS} - V_T$$

$$V_D - V_S \leq V_G - V_S - V_T$$

$$V_D \leq V_G - V_T$$

$$\Rightarrow 7.5 \leq 3Vi$$


$$16 - 2Vi \leq 9.5 + Vi - 1$$

$$Vi \geq 2.5V$$

$$16 - 2Vi \leq 8.5 + Vi$$

@ $Vi = 2.5V \Rightarrow Tr$ goes into triode.

(c) For M_o^1

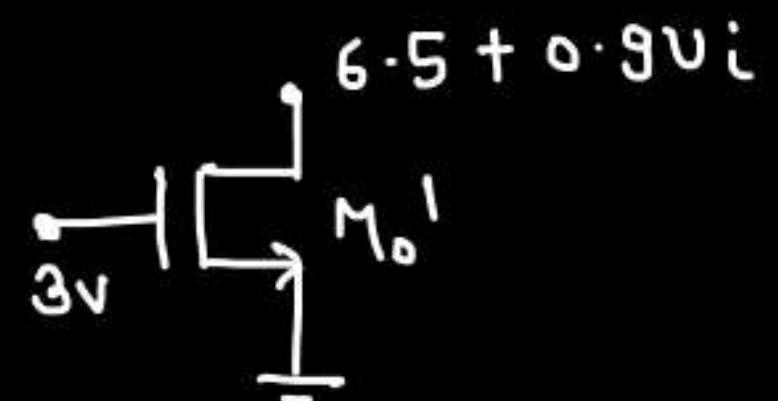

For cut off:-

$$V_{DS} \leq 0$$

$$6.5 + 0.9v_i \leq 0$$

$$0.9v_i \leq -6.5$$

$$v_i \leq -7.28V$$

For Triode ,

$$6.5 + 0.9v_i \leq 3 - 1$$


$$6.5 + 0.9v_i \leq 2$$

$$0.9v_i \leq -4.5$$

$$v_i \leq -5$$

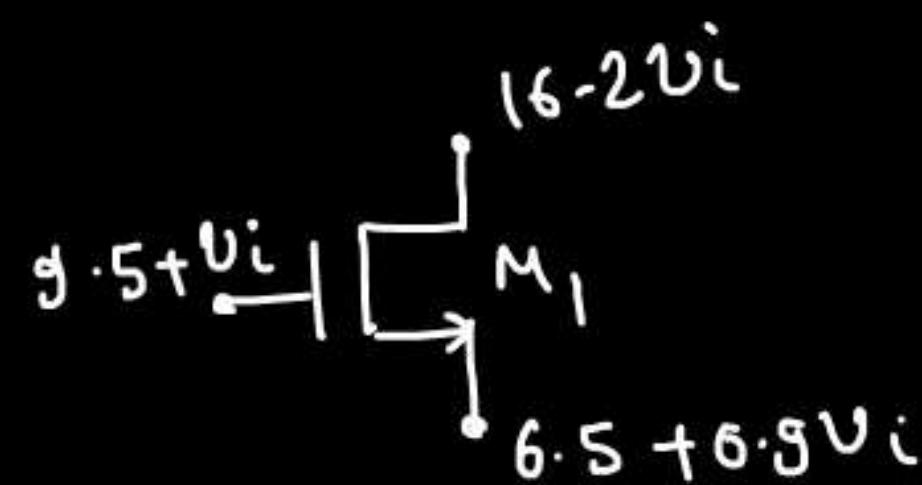@ $v_i = -5V \Rightarrow T_r M_o^1$ goes into Triode region





for cut off M_1

$$\textcircled{1} \quad V_{DS} \leq 0$$

$$16 - 2V_L - 6.5 - 0.5V_L \leq 0$$

$$9.5 - 2.5V_L \leq 0$$

$$2.5V_L \geq 9.5$$

$$V_L \geq 3.27 \text{ V}$$


PrepFusion

$$\textcircled{2} \quad V_{GS} \leq V_T$$


$$9.5 + V_L - 6.5 - 0.5V_L \leq 1$$

$$3 + 6.1V_L \leq 1$$

$$V_L \leq -20 \text{ V}$$

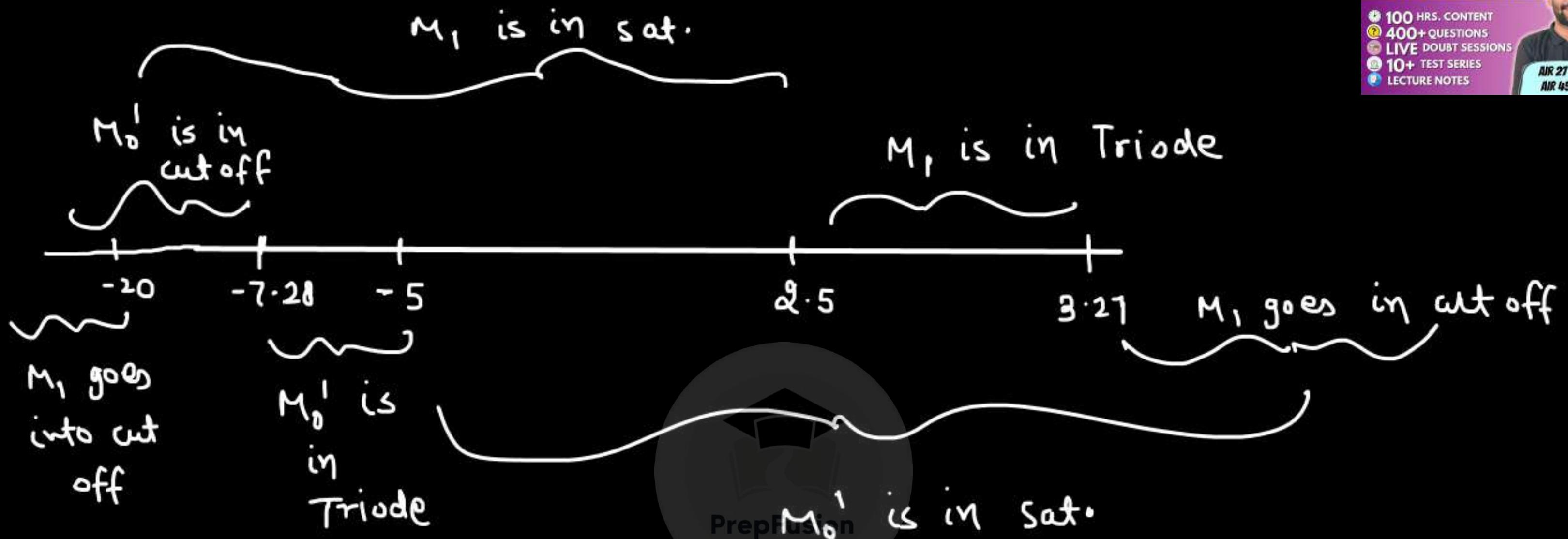

Q.

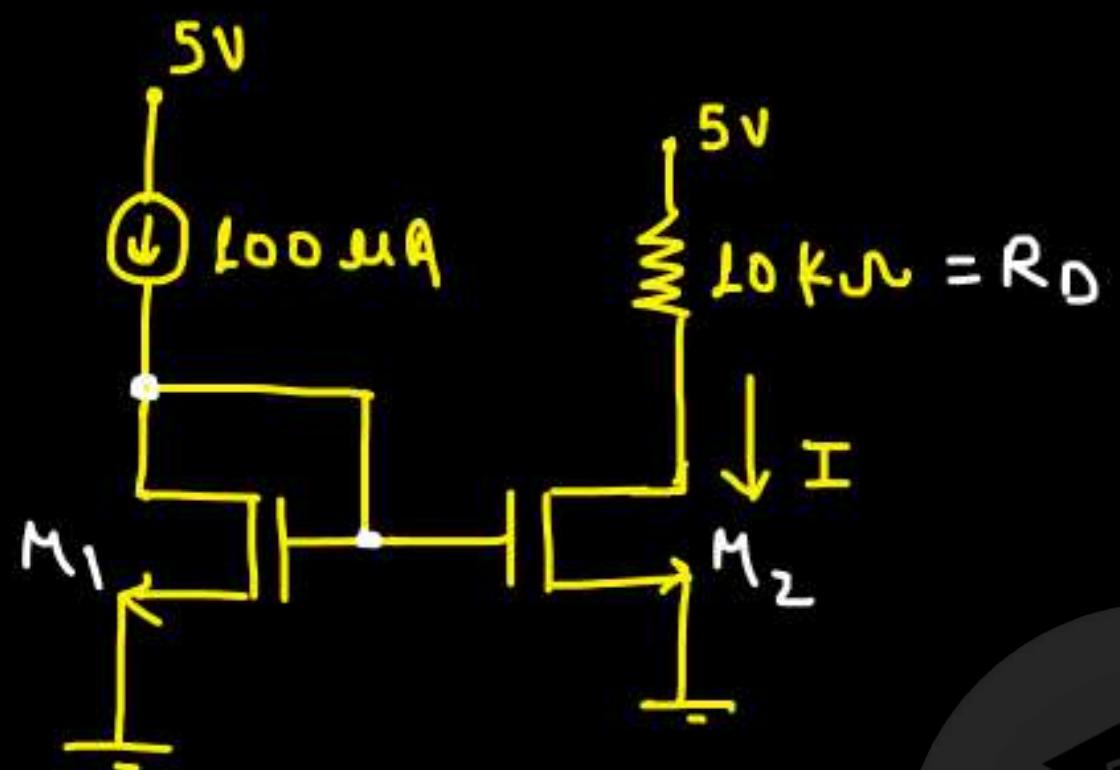

$$\frac{Un Cox \omega}{L} = \frac{50 \mu A}{V^2}$$

$$V_T = LV$$

$$\lambda = 0.01 V^{-1}$$

PreFusion
find current I ?

(a) ~~100 μA~~

(b) ~~100.96 μAmp.~~

(c) ~~99.04 μAmp~~

(d) ~~98.96 μAmp~~

$$I = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$\lambda \neq 0$

$$I_{M_1} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS_1})$$

$$I_{M_2} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS_2})$$

{ let M_2 is in sat }

$$\frac{I_{M_1}}{I_{M_2}} = \frac{(1 + \lambda V_{DS_1})}{(1 + \lambda V_{DS_2})}$$

for M₁

$$100 \mu = \frac{50\mu}{2} (V_{GS} - 1)^2 (1 + \lambda V_{DS})$$

Since λ is very small, let $\lambda V_{DS} \ll L$

$V_{GS} = 3V$

Here $V_{GS} = V_{DS} = 3$

$$\lambda V_{DS} = 0.01 \times 3 = 0.03 \ll L \Rightarrow \text{considerable}$$

$$\frac{I_{M_1}}{I_{M_2}} = \frac{1 + \lambda(3)}{1 + \lambda[V_{DS_2}]}$$



$$V_{DS_2} \approx ?$$

, $I_M = X$

$$V_{DS_2} = 5 - 10^4 X$$

$$\frac{100\mu}{X} = \frac{1 + 3\lambda}{1 + \lambda [5 - 10^4 X]}$$

$$10^{-4} [1 + 5\lambda - \lambda \times 10^4 X] = X + (3\lambda) X$$

PrepFusion

$$10^{-4} + 5 \times 10^4 \lambda - \lambda X = X + (3\lambda) X$$

$$10^{-4} + 0.05 \times 10^{-4} = X + 0.04 X$$

$$1.05 \times 10^{-4} = 1.04 X$$

$$X = \frac{1.05 \times 10^{-4}}{1.04} = 100.96 \mu \text{Amp.}$$

if $R_D = 20 \text{ k}\Omega \Rightarrow I_{M_2} = 100 \mu\text{Amp}$

[Perfectly matched V_{DS}]


if $R_D = 10 \text{ k}\Omega \Rightarrow I_{M_2} > 100 \mu\text{Amp}$

$[V_{DS_2} > V_{DS_1}]$

if $R_D = 25 \text{ k}\Omega \Rightarrow I_{M_2} < 100 \mu\text{Amp}$

Preparation
 $[V_{DS_2} < V_{DS_1}]$

Q.

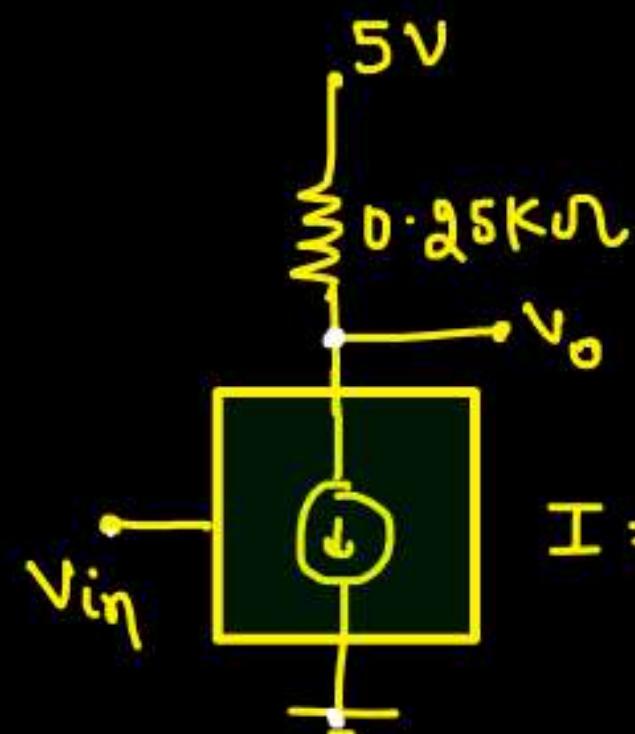

$$I = [V_{in}^2 + 2V_{in} + 1] [1 + 0.05V_o] \text{ mA}$$

Yellow-box is a three terminal element. $V_{in} - Q = 1V$

Find small signal voltage gain $\frac{V_{in}}{V_o} = ?$ (approx)

PrepFusion

(a) -0.95

(b) -19.5

(c) -49.5

(d) -99.5

→ for MOS:-

$$I_D = k_n [V_{GS} - V_T]^2 [1 + \lambda V_{DS}]$$


for given problem,

$$I = [V_{in}^2 + 2V_{in} + 1] [1 + 0.05 V_0] \text{ mA}$$


$$g_m = \frac{\partial I}{\partial V_{in}} = 2V_{in} + 2 \text{ mA} \quad \left\{ \text{Assuming } 1 + 0.05 V_0 \ll 1 \right\}$$

$$\left(g_m \right)_{V_{in}=1V} = 4 \text{ mS}$$
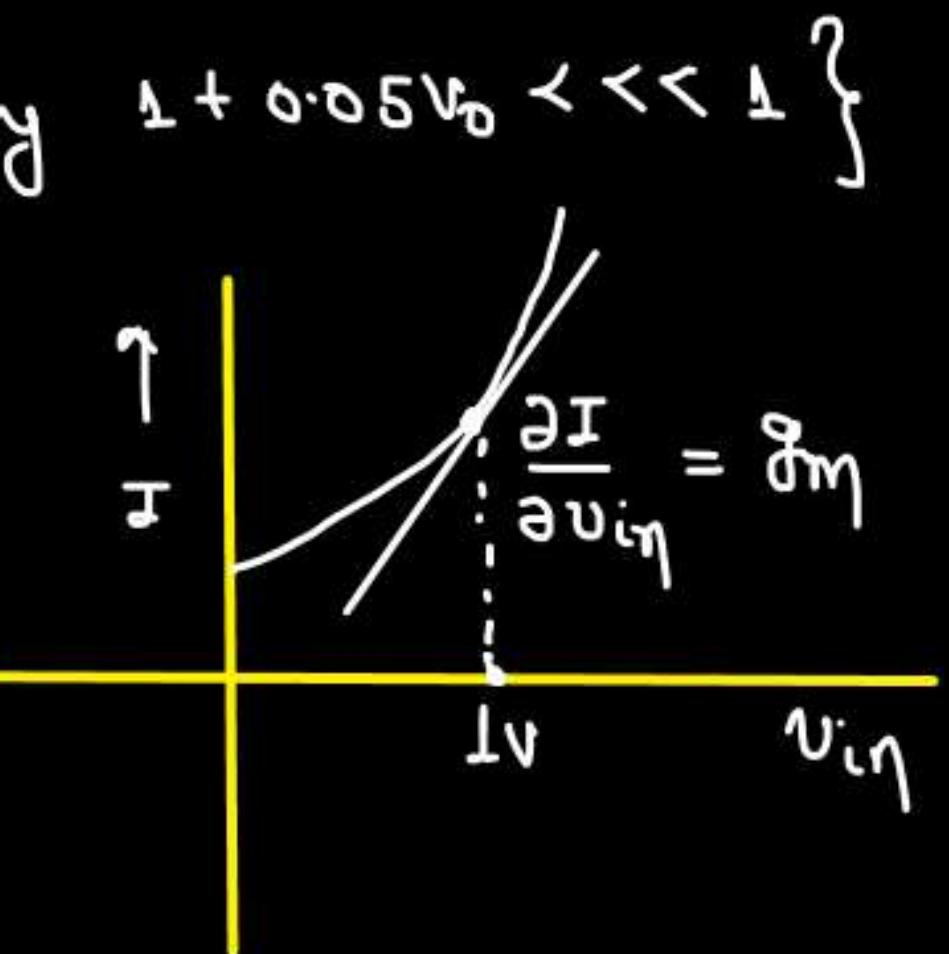
$$\gamma_0 = \frac{1}{\frac{\partial I}{\partial V_0}} = \frac{10^3}{(V_{in}^2 + 2V_{in} + 1)(0.05)}$$



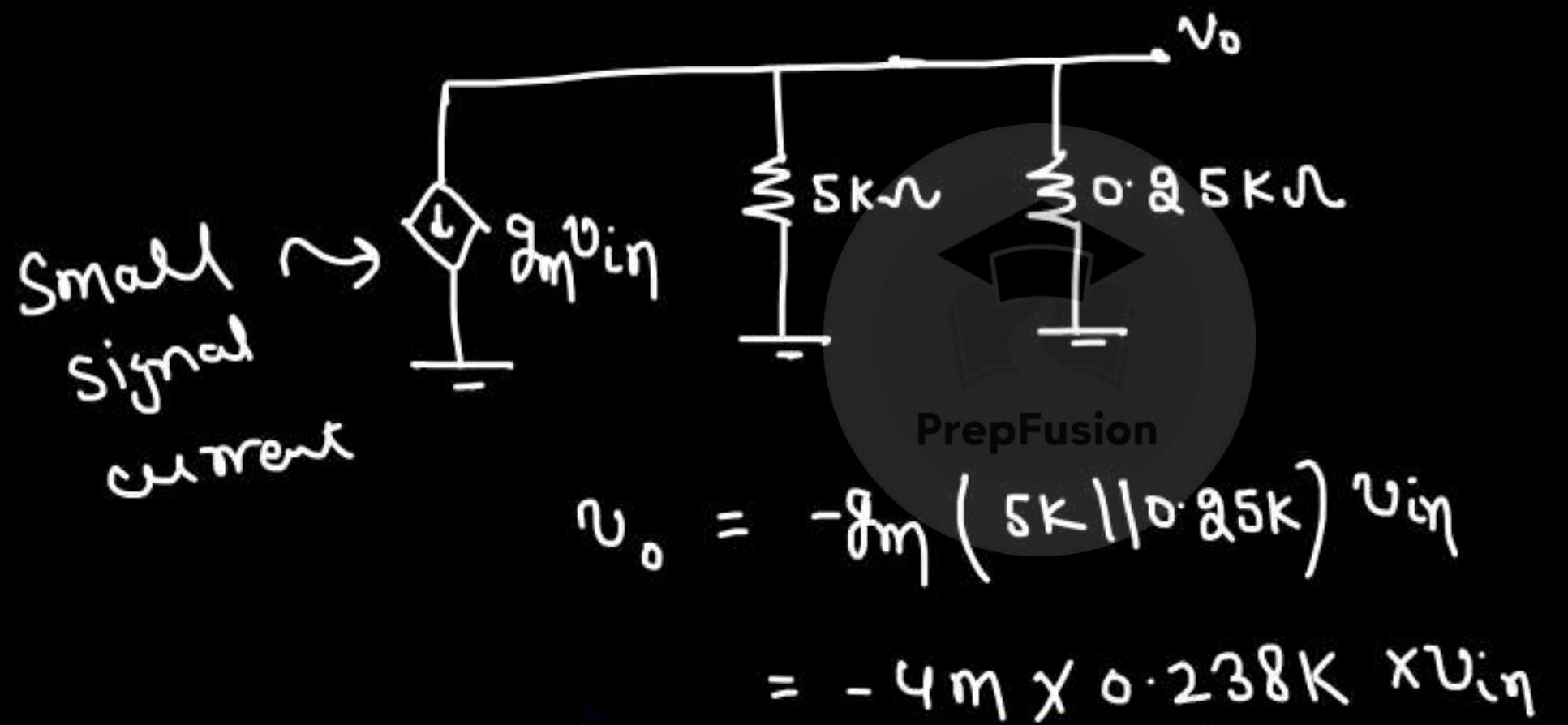
$$(r_d)_{V_{in}-Q=1} = \frac{10^3}{4 \times 10^5} = 5 \text{ k}\Omega$$



$$\frac{V_o}{V_{in}} = -0.95 \text{ V/V}$$

Ans =

Q.

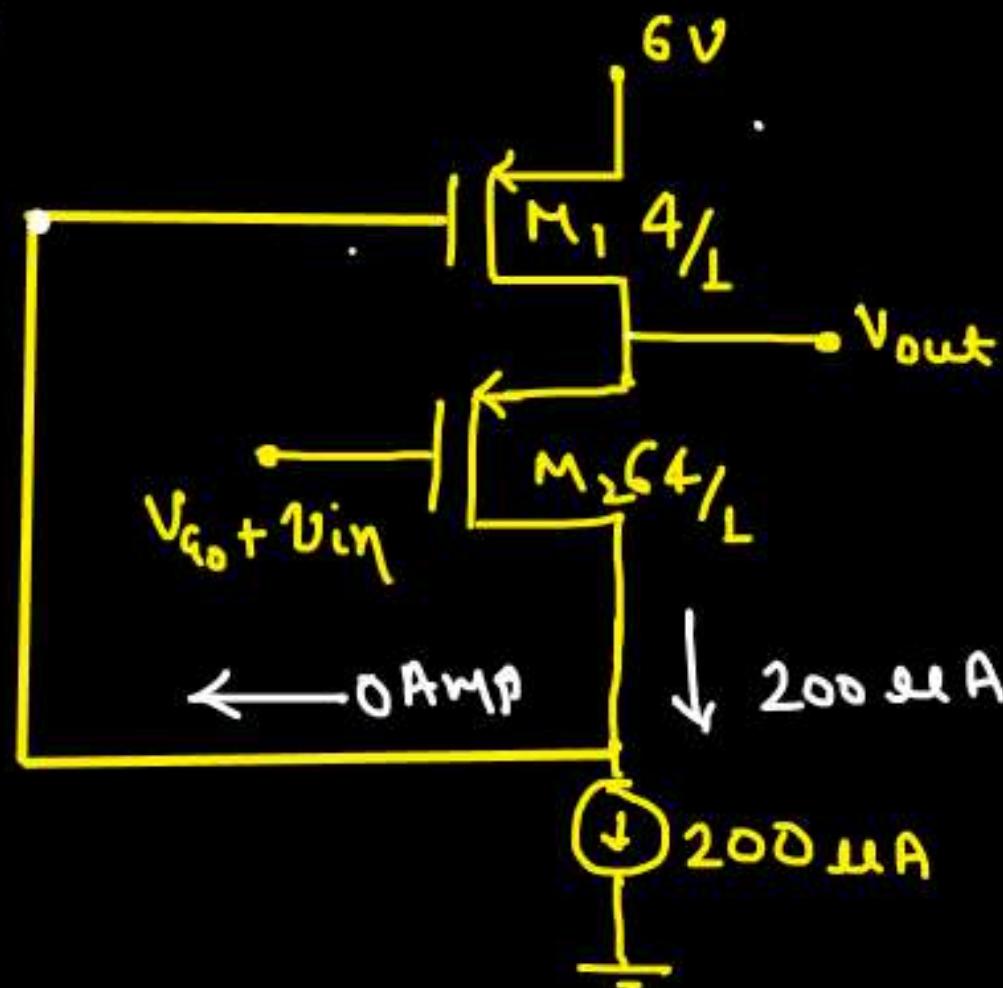

$$\mu_p C_{ox} = 25 \mu A/V^2$$

$$V_T = 1V$$

PrepFusion

$$V_{in} = V_p \cos(\omega t)$$


V_{go} is set such that it maximizes V_p that can be applied while keeping all the Tr. in sat. region.

- (a) Find optimum value of V_{go} (b) Find max value of V_p .

$$I_{M_1} = 200 \mu A$$

$$\Rightarrow 200 \mu A = \frac{25 \mu A \times 4}{2} (V_{SG_{M_1}} - 1)^2$$


$$V_{SG_{M_1}} = 3V$$

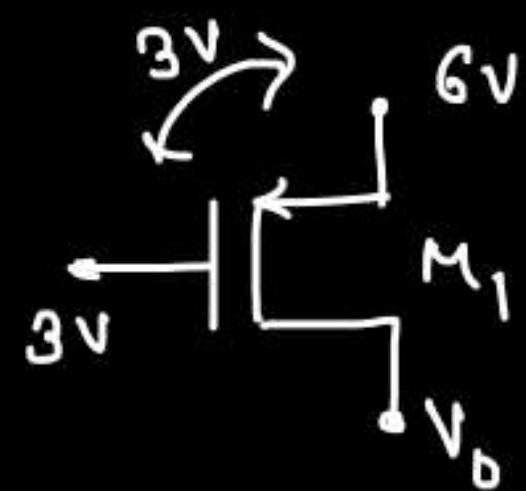

$$I_{M_2} = 200 \mu A$$



$$\Rightarrow 200 \mu A = \frac{25 \mu A \times 64}{2} (V_{SG_{M_2}} - 1)^2$$

$$V_{SG_{M_2}} = 1.5V$$

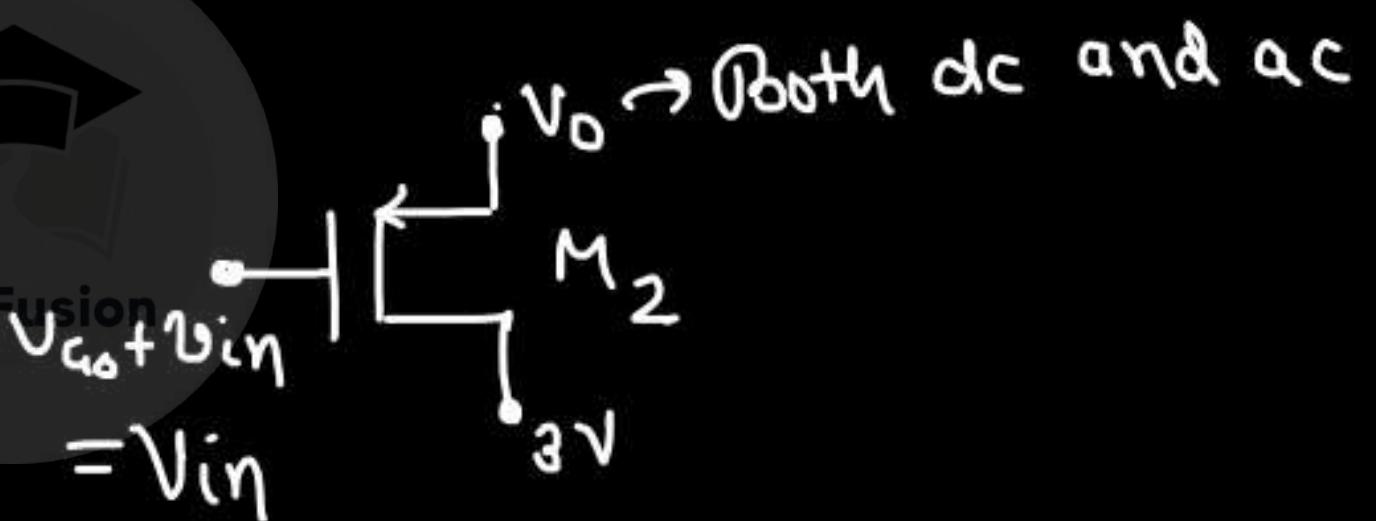

$$V_0 - V_{in} = 1.5$$

$$V_0 = 1.5 + V_{in}$$

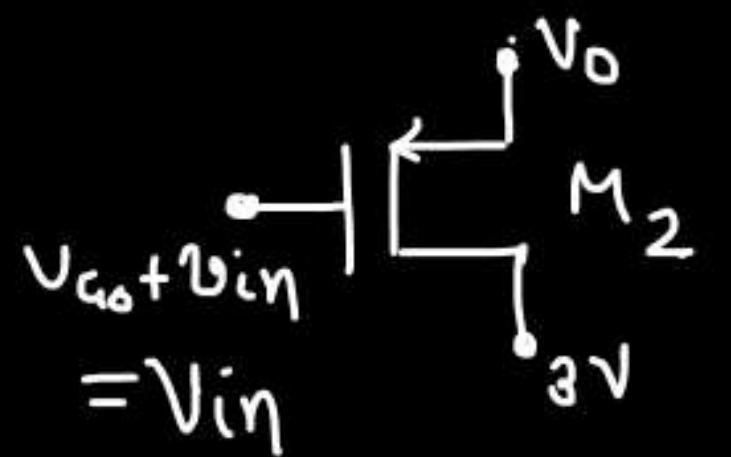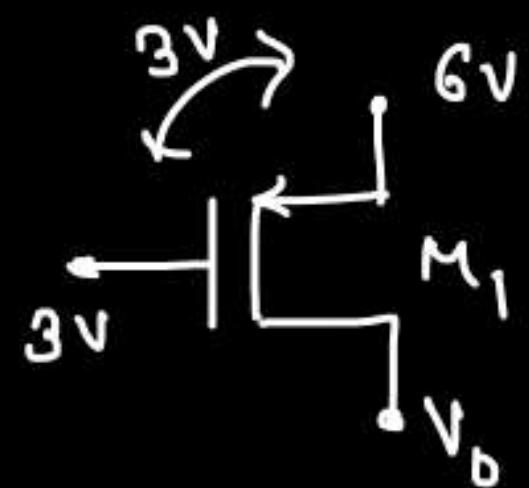

For sat.

$$6 - V_o \geq 6 - 3 - 1$$

$$6 - V_o \geq 2$$

$$V_o \leq 4$$

$$1.5 + V_{in} \leq 4$$

$$V_{in} \leq 2.5V$$

$$V_o - 3 \geq V_o - V_{in} - 1$$

$$-3 \geq -V_{in} - 1$$

~~2.5~~

$$2.5 - 0.2$$

PrepFusion

$$V_{in} \geq 2$$

$$V_{in} = V_{go} + V_{in}$$

$$= V_{go} + V_p \cos \omega t$$

$$(V_{in})_{\max} = V_{go} + V_p, \quad (V_{in})_{\min} = V_{go} - V_p$$

$$V_{Q_0} - V_p = Q$$


$$V_{Q_0} + V_p = Q \cdot 5$$

$$V_{Q_0} = Q \cdot 4.5 V$$

$$V_p = 0.25 V$$

Ans

Ans

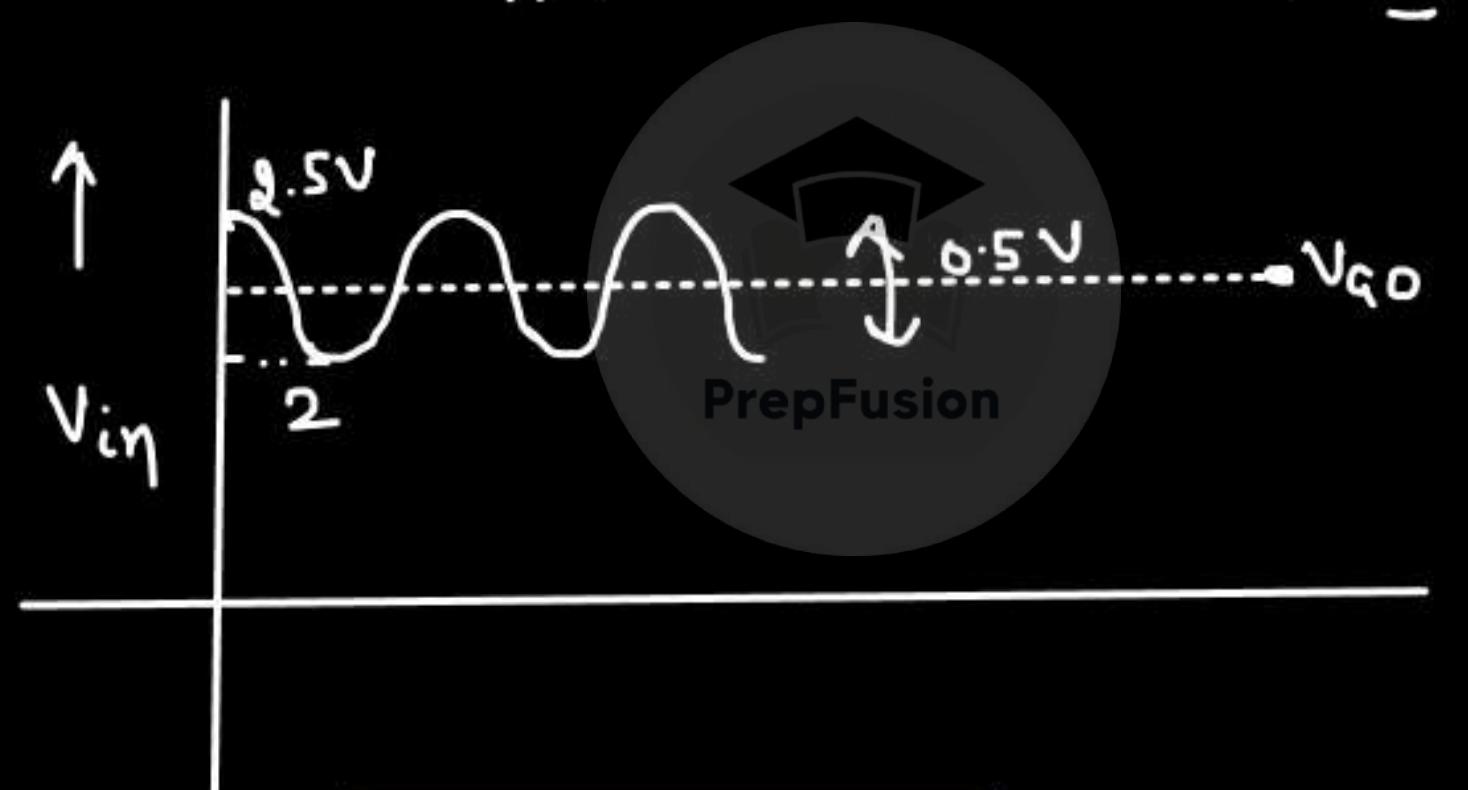


$$\begin{aligned} Q < V_{Q_0} &< Q \cdot 5 \\ 0.5 > V_p &> 0 \end{aligned}$$

⇒ Some Miscellaneous Topics :-


* Multi-stage Amplifiers (Cascade Amplifiers) :-

A series of amplifier

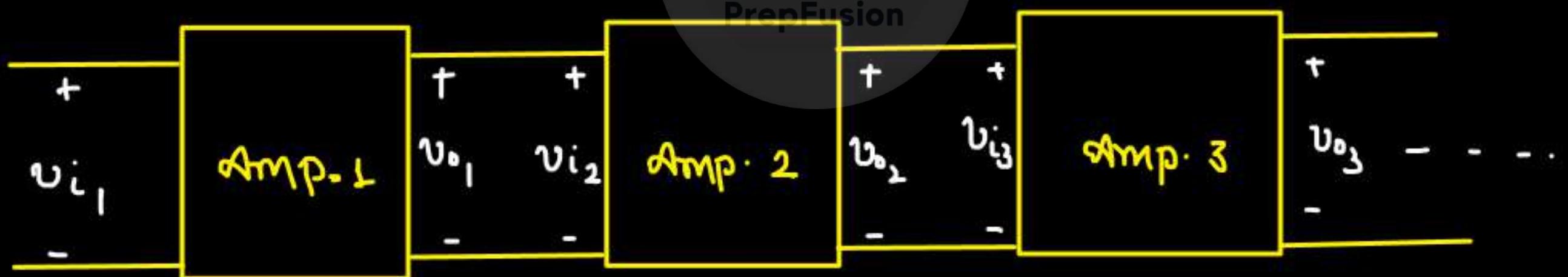in which each amplifier connects its o/p to the i/p of next amplifier in the chain.



Eg. →

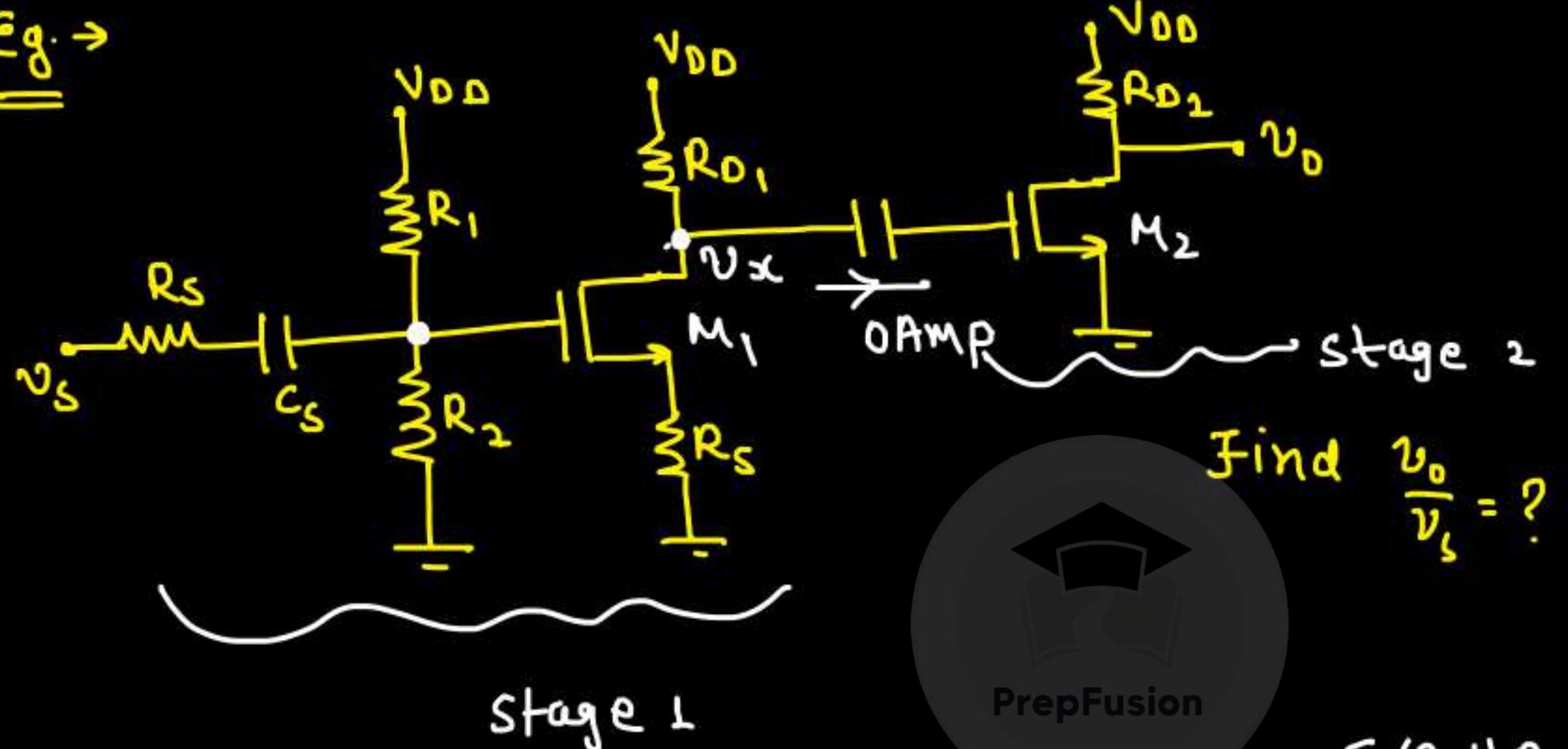

Find $\frac{v_o}{v_s} = ?$

PrepFusion

$$\frac{v_{SL}}{v_s} = -\frac{g_m R_{D1}}{(g_m R_S + g_m R_{D1})} \left[\frac{(R_1 || R_2)}{(R_1 || R_2) + R_S} \right] \quad \textcircled{1}$$


$$\frac{v_o}{v_{SL}} = -g_m R_{D2} \quad \textcircled{2}$$

multiply eqn ① with eqn ②

$$\frac{V_x}{V_s} \times \frac{V_o}{V_x} = \boxed{\frac{V_o}{V_s} = \left[g_m_2 R_D_2 \right] \left[\frac{g_m_1 R_D_1}{1 + g_m_1 R_S} \right] \left[\frac{(R_1 || R_2)}{(R_1 || R_2) + R_S} \right]}$$



②

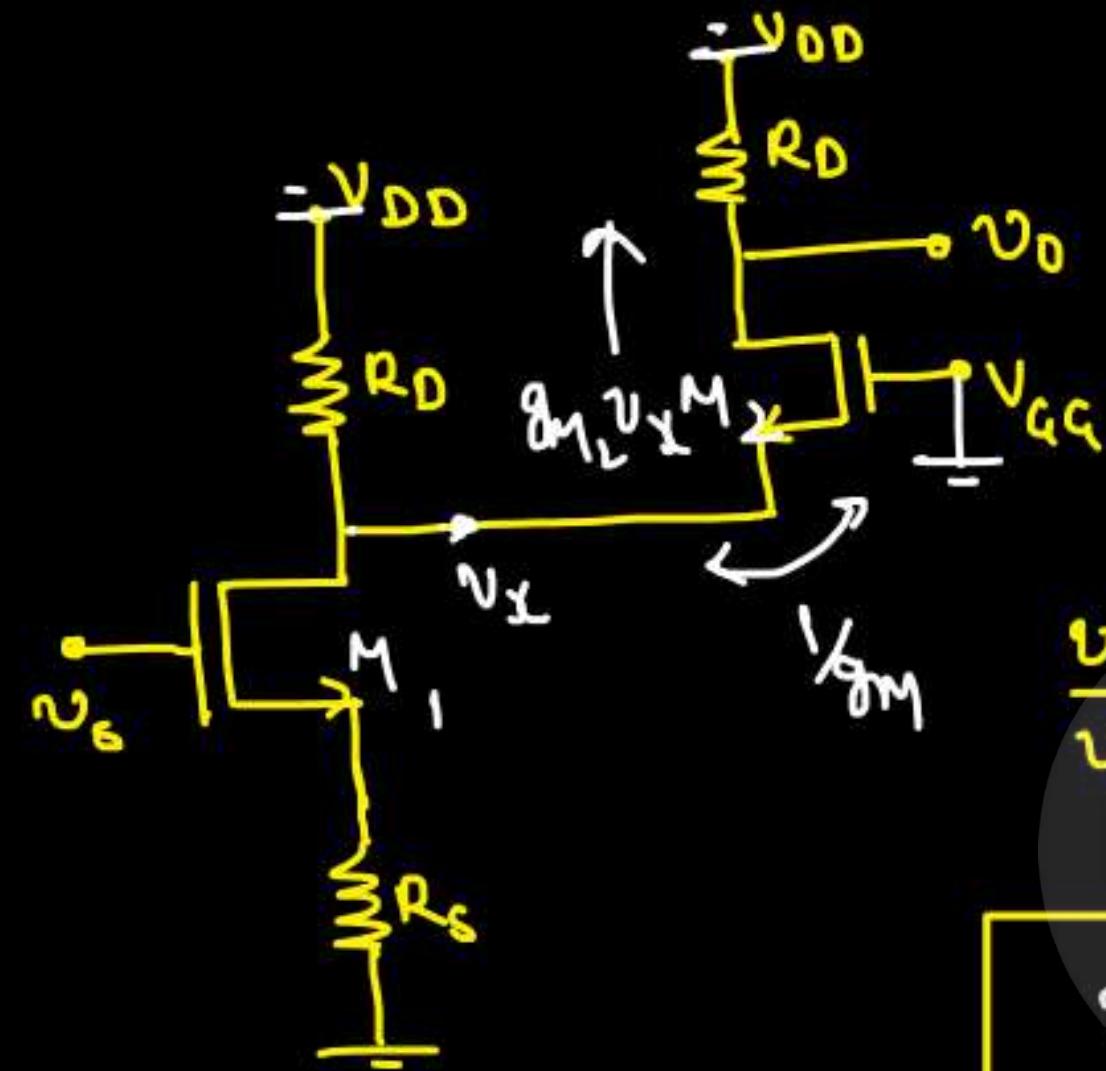

$\frac{v_o}{v_s} = ?$ [Small signal voltage gain]

PrepFusion

$$\frac{v_o}{v_s} = -\frac{g_m R_D}{1 + g_m R_s}$$



$$\frac{v_o}{v_s} = \frac{-g_m [R_D || \frac{1}{g_m_2}]}{1 + g_m_1 R_s} \rightarrow 0$$

$$\frac{V_x}{V_o} = ?$$

$$V_o = g_m V_x R_D$$

$$\frac{V_o}{V_x} = g_m R_D - \textcircled{2}$$

* * *

$$\frac{V_o}{V_s} = -g_m R_D \times$$


$$\frac{g_m \left[R_D \parallel \frac{1}{g_m} \right]}{1 + g_m R_S}$$

PrepFusion

Concept of Pass Transistor Logic:-

Q. Find the steady state value of V_o .

$$(V_T = 1V)$$

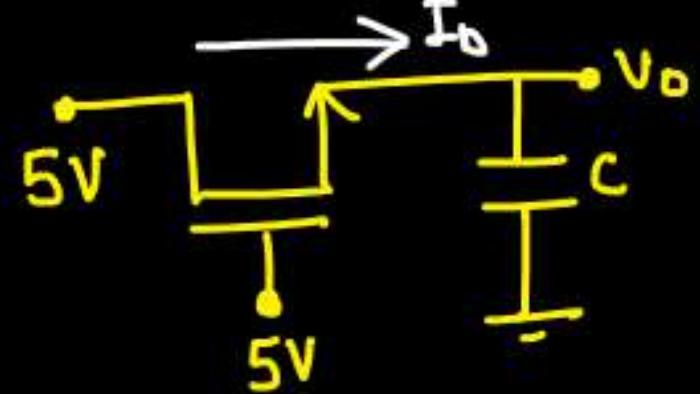

(a)

@ $t=0^+$, $V_o = 0V$

$$V_{DS} = 5V$$

$V_{GS} = 5V \Rightarrow T_r \text{ is ON}$

$$V_T = 1V$$



if T_r is ON $\Rightarrow 5V$ from drain will charge the capacitor

When $I_D = 0 \text{ Amp} \Rightarrow$ No charging on cap.

↓
Steady state

$I_D > 0 \Rightarrow$ cap will be charging



$$\textcircled{1} \quad V_{DS} > V_T$$

$$\Rightarrow 5 - V_D > 1 \Rightarrow V_D \leq 4$$

$$\textcircled{2} \quad V_{DS} > 0$$


$$\Rightarrow 5 - V_D > 0 \Rightarrow V_D \leq 5$$

$$\Rightarrow V_D \leq 4V$$




$$(V_D)_{\text{c.c.}} = 4V$$



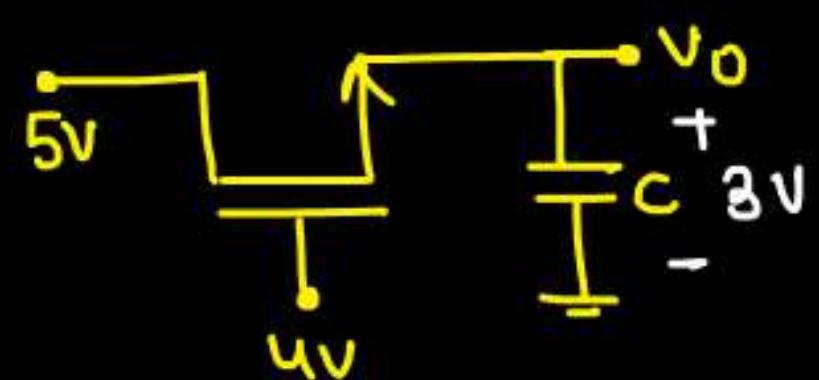


(b)

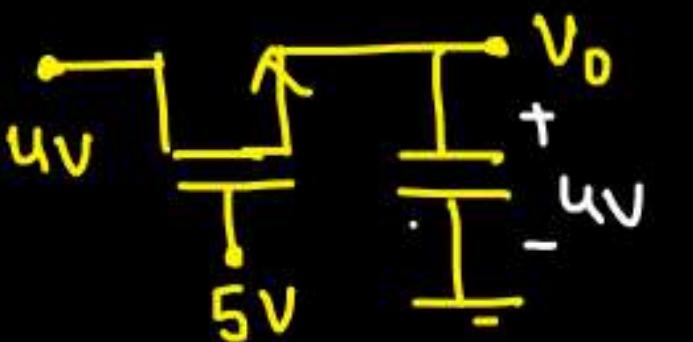


(c)



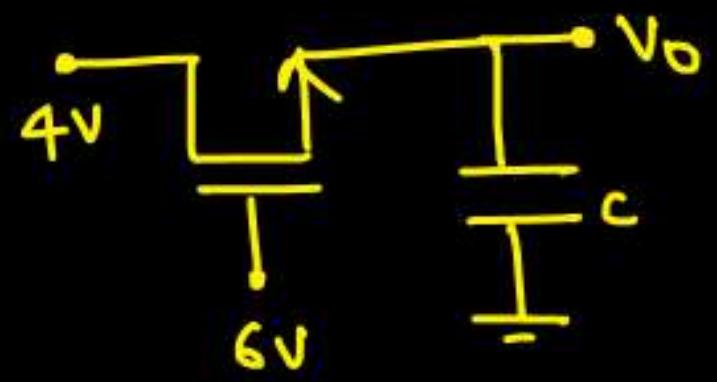

(D)

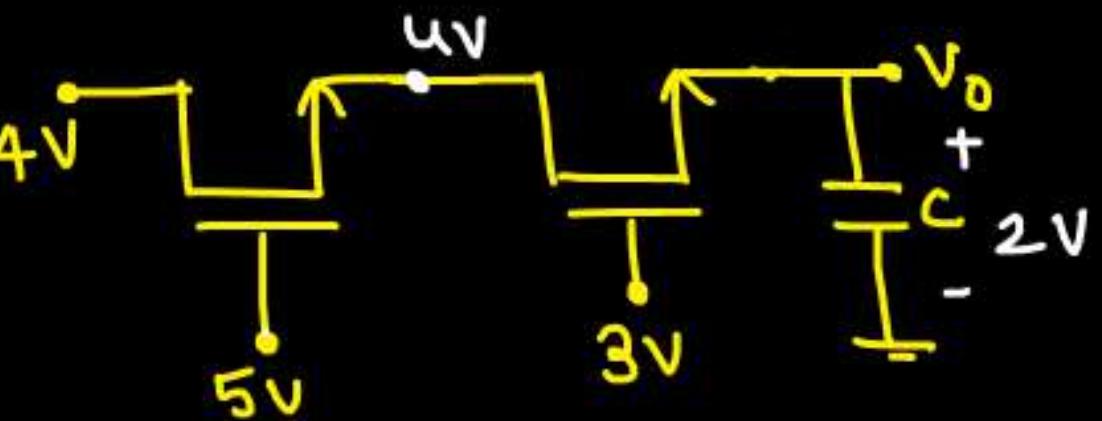

(E)

$$V_{DS} > V_T - \textcircled{1}$$

$$6 - V_O > 1$$



$V_O \leq 5V$


$$V_{DS} > 0 - \textcircled{2} \Rightarrow V_O = 4V$$

$$4 - V_O > 0$$

$V_O \leq 4V$



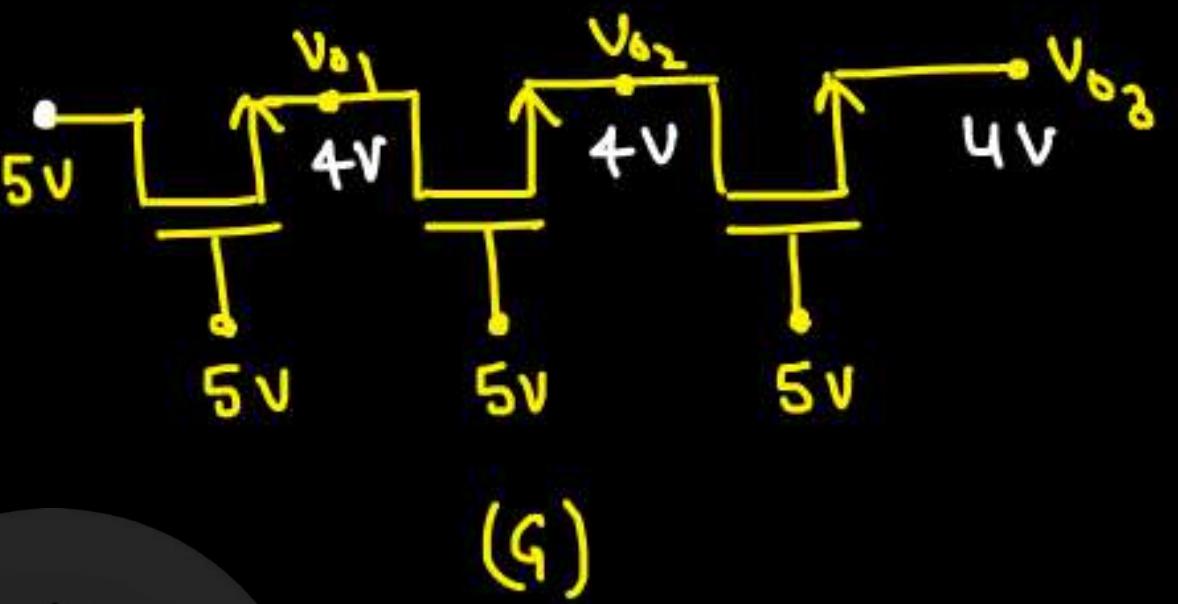
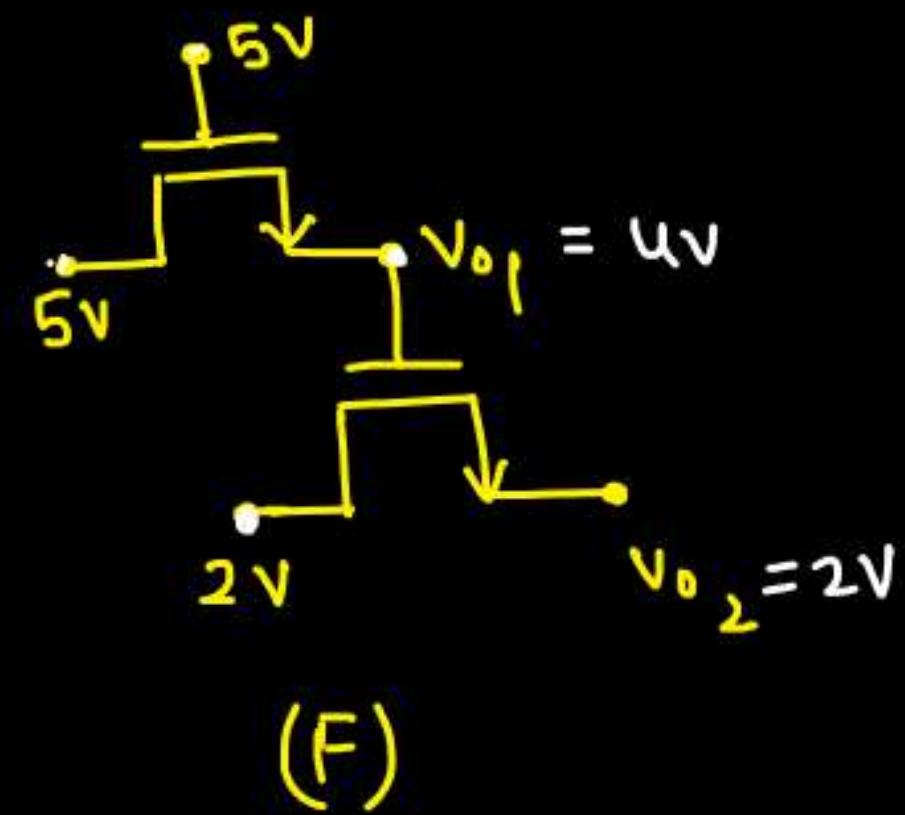


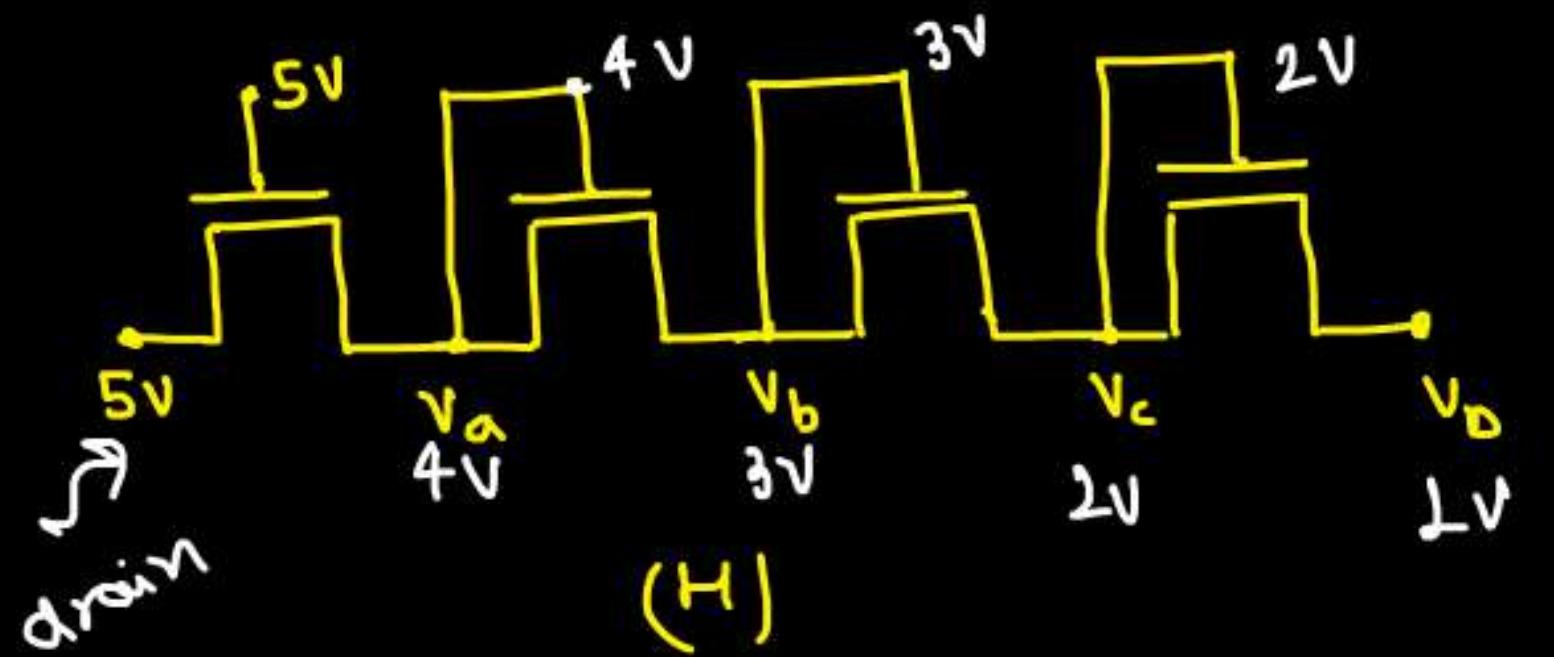

 \Rightarrow NMOS

 \Rightarrow PMOS



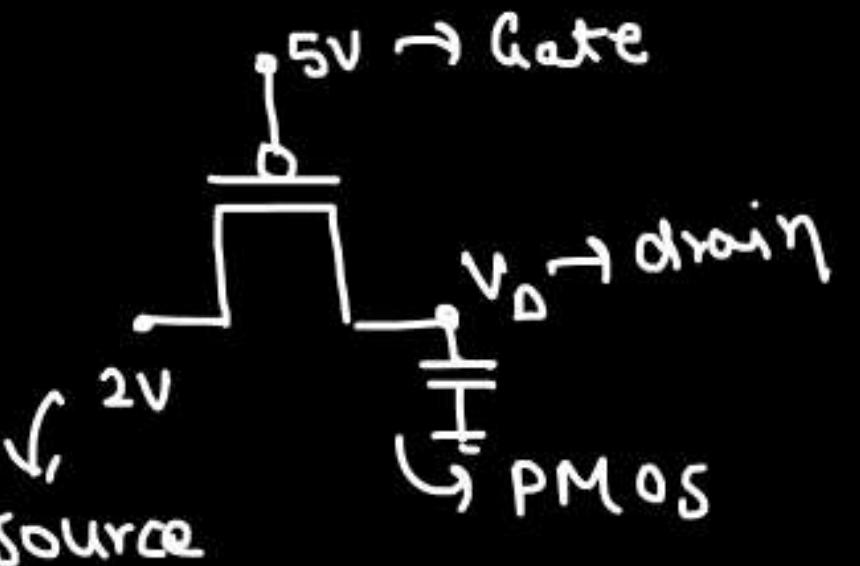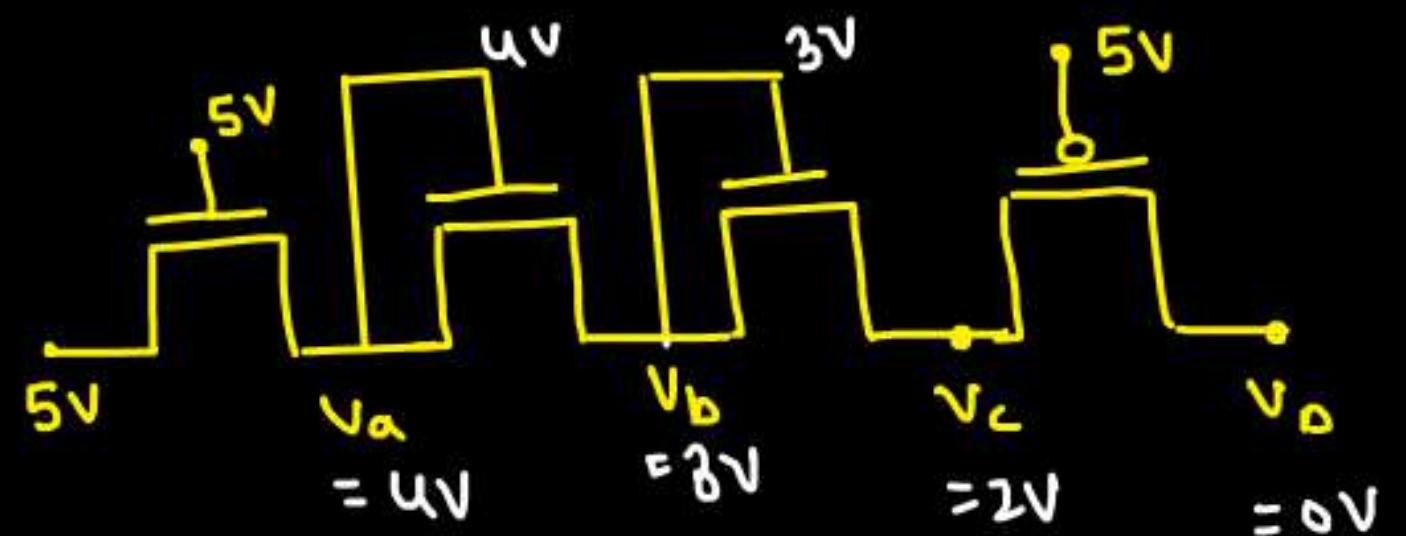


H-p → Source
L-p → Drain

$$V_{SG} = 2 - 5 = -3V$$

↓
MOS is off

↓
No charging for V_D



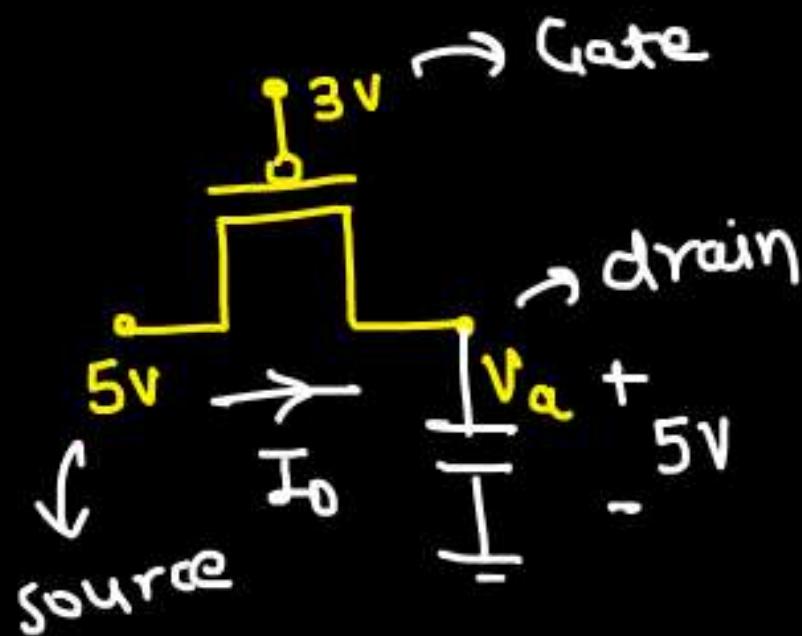

$$V_{SG} = 5 - 3 = 2V > V_T \Rightarrow \text{always}$$

T_r can turn off only when


$$V_{SD} = 0$$

$$5 - V_0 = 0$$

(PrepFusion)

$$(V_0)_{S.S.} = 5V$$

Q

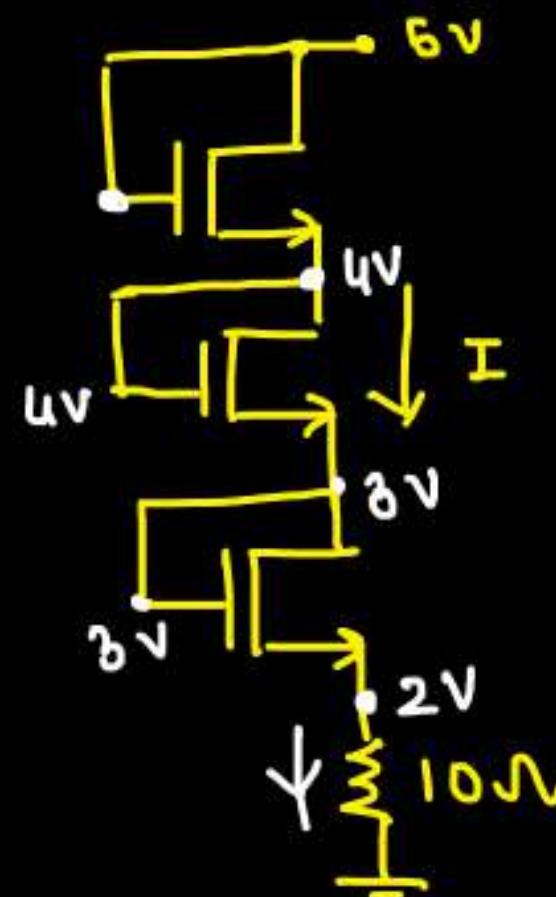

steady state $I = ?$


(PrepFusion)

$$I = \frac{2}{10} = 0.2 \text{ Amp.}$$



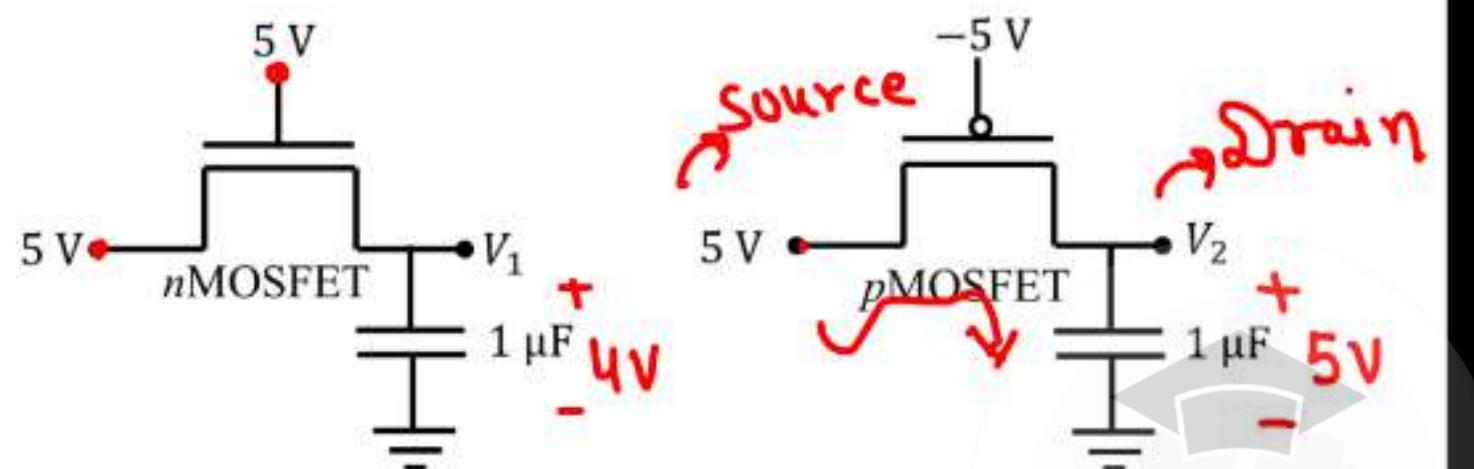Q.20

The ideal long channel *n*MOSFET and *p*MOSFET devices shown in the circuits have threshold voltages of 1 V and -1 V, respectively. The MOSFET substrates are connected to their respective sources. Ignore leakage currents and assume that the capacitors are initially discharged. For the applied voltages as shown, the steady state voltages are _____.



(A) $V_1 = 5 \text{ V}, \quad V_2 = 5 \text{ V}$

$V_{SG} = 5 - (-5) = 10 \text{ V}$

(B) $V_1 = 5 \text{ V}, \quad V_2 = 4 \text{ V}$

↑

(C) $\checkmark V_1 = 4 \text{ V}, \quad V_2 = 5 \text{ V}$

Tr ON

(D) $V_1 = 4 \text{ V}, \quad V_2 = -5 \text{ V}$

Frequency Response of MOS

Pre-requisites..

Transfer fⁿ, pole, zero, Bode plot.

LAUNCHING
ANALOG VLSI MASTERY : COHORT (0-10)

60 HRS OF VIDEO CONTENT ✓
COMPLETE CLASS NOTES ✓
ASSIGNMENTS ✓
DOUBT SOLVING GROUP ✓

▶ PLAY ALL

FREE YOUTUBE COURSE!!

HIMANSHU AGARWAL ANALYST

Analog VLSI Mastery : Cohort (0-10) || Himanshu Agarwal || PrepFusion
Himanshu Agarwal Playlist

Analog VLSI Mastery : Cohort (0-10) || Free YouTube Course || Himanshu Agarwal || @PrepFusion_GA... • 12:03
Day to Day Roadmap to Complete Analog VLSI Mastery : Cohort (0-10) • 10:21

VIEW FULL PLAYLIST

PrepFusion

42

NETWORK ANALYSIS
TRANSIENT ANALYSIS
LECTURE-42
BASICS OF CONTROL SYSTEMS
IN ELECTRICAL CIRCUITS
GATE 2025-26


50:26

Basics of Control Systems in Electrical Circuits || Network Analysis || GATE 2025-26 || PrepFusion

PrepFusion - GATE • 493 views • 2 months ago

: VK


- 19** **ANALOG VLSI MASTERY** Basics of Frequency Response & Bode Plot (Part 1) || Analog VLSI Mastery (Cohort 0-10)
-
- Himanshu Agarwal • 708 views • 2 months ago
- 20** **ANALOG VLSI MASTERY** Basics of Frequency Response & Bode Plot (Part 2) || Analog VLSI Mastery (Cohort 0-10)
-
- Himanshu Agarwal • 323 views • 2 months ago
- 21** **ANALOG VLSI MASTERY** Basics of Analog Filters || Analog VLSI Mastery (Cohort 0-10) || Himanshu Agarwal
-
- Himanshu Agarwal • 688 views • 2 months ago
- 22** **ANALOG VLSI MASTERY** Finding Poles and Zeros of Electrical Circuits Intuitively || Analog VLSI Mastery (Cohort 0-10)
-
- Himanshu Agarwal • 418 views • 2 months ago
- 23** **ANALOG VLSI MASTERY** Intuitively Drawing Bode Plots of Electrical Circuits || Analog VLSI Mastery (Cohort 0-10)
-
- Himanshu Agarwal • 364 views • 2 months ago

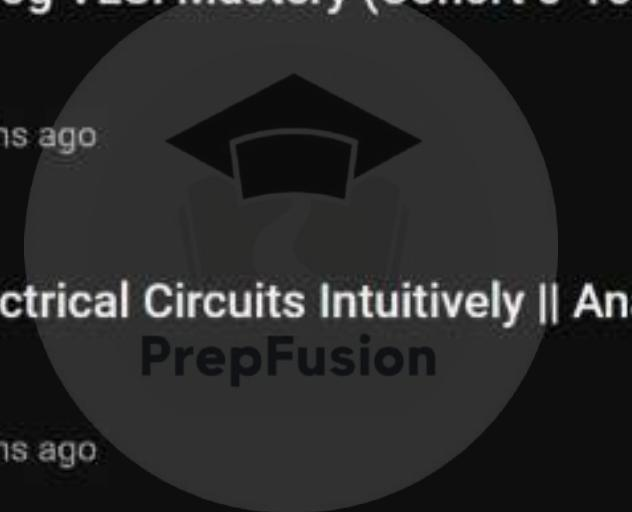

Concepts of frequency response of Bode Plot.

Q. $f(\omega) = \begin{cases} \omega, & 0 \leq \omega \leq 100 \\ 0, & \omega > 100 \end{cases}$


Draw $f(\omega)$ v/s ω .

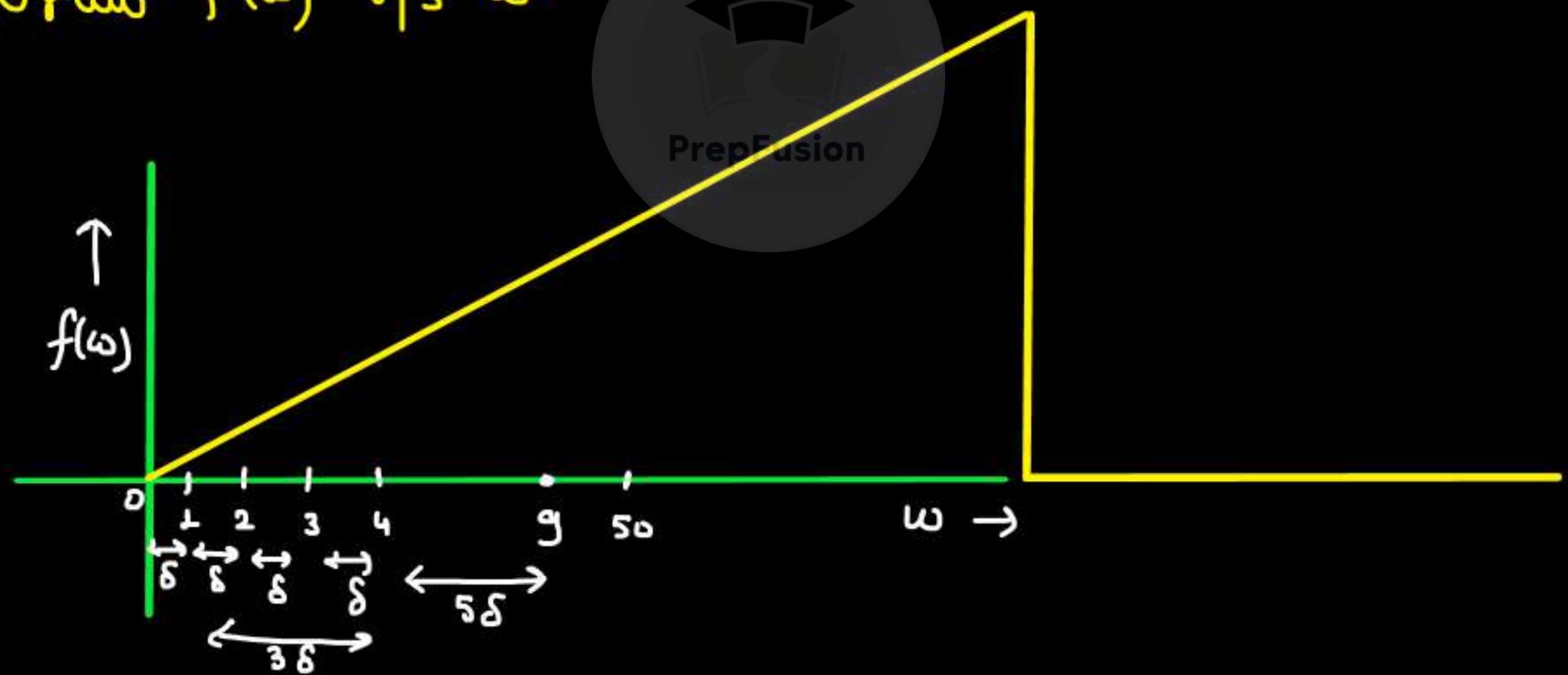

Q.

$$f(\omega) = \begin{cases} \omega, & 0 \leq \omega \leq 100 \\ 0, & \omega > 100 \end{cases}$$

Draw $f(\omega) v/s \sqrt{\omega}$.

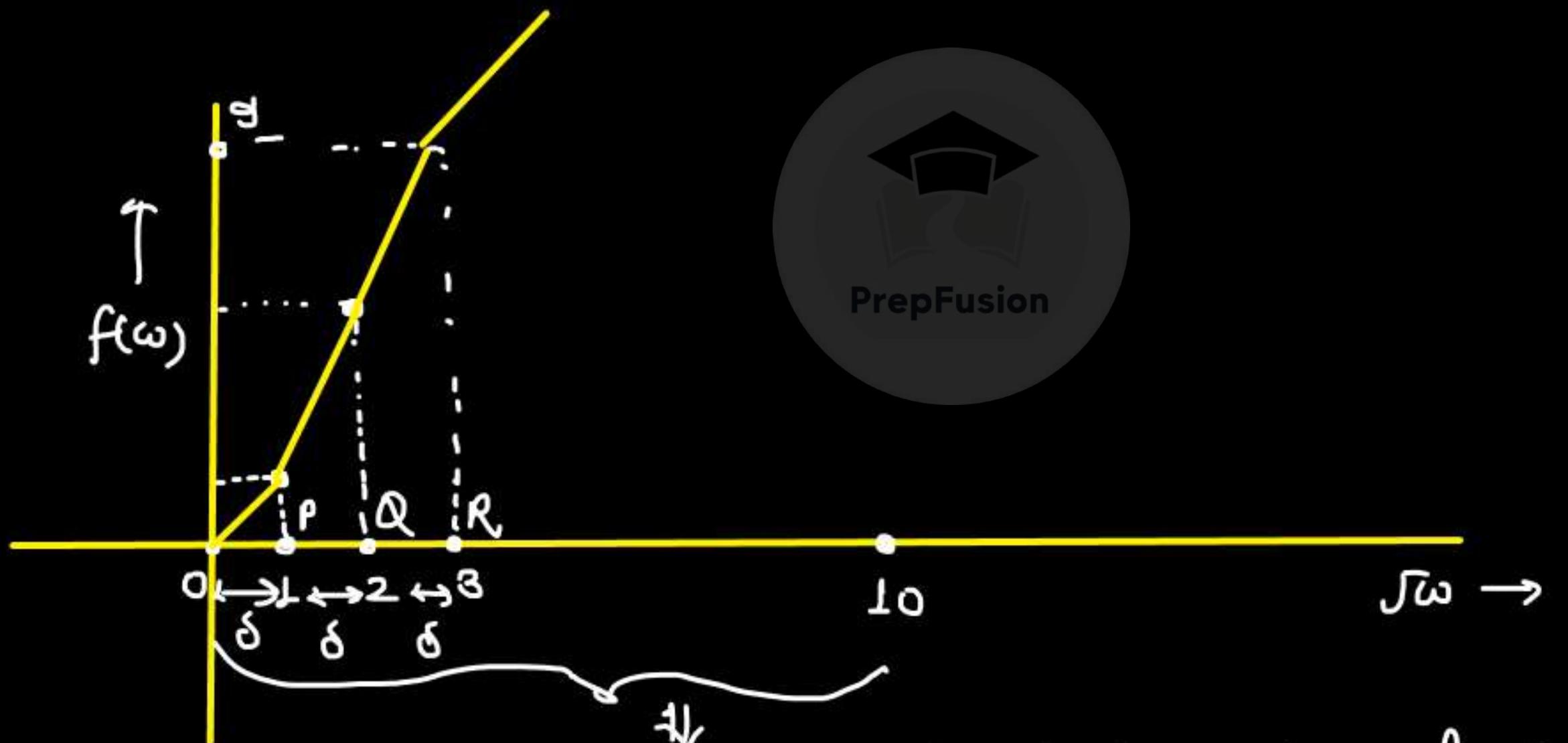

Have covered all the values of ω


Q.

$$f(\omega) = \begin{cases} \underline{\omega}, & 0 \leq \omega \leq 100 \\ 0, & \omega > 100 \end{cases}$$

Draw $f(\omega)$ v/s ω .

But x-axis is in Square root scale.

→

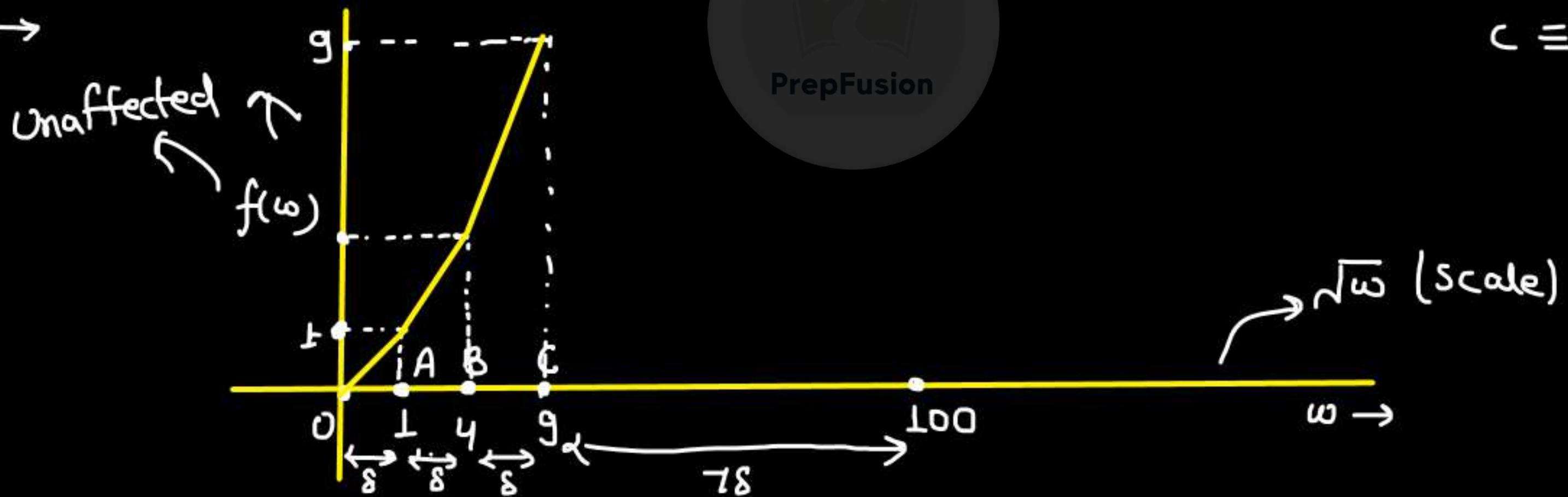


$$\begin{aligned} A &\equiv P \\ B &\equiv Q \\ C &\equiv R \end{aligned}$$

Q.

$$f(\omega) = \begin{cases} \omega, & 0 \leq \omega \leq 100 \\ 0, & \text{otherwise} \end{cases}$$

Draw $f(\omega)$ v/s $\log_{10}\omega$.

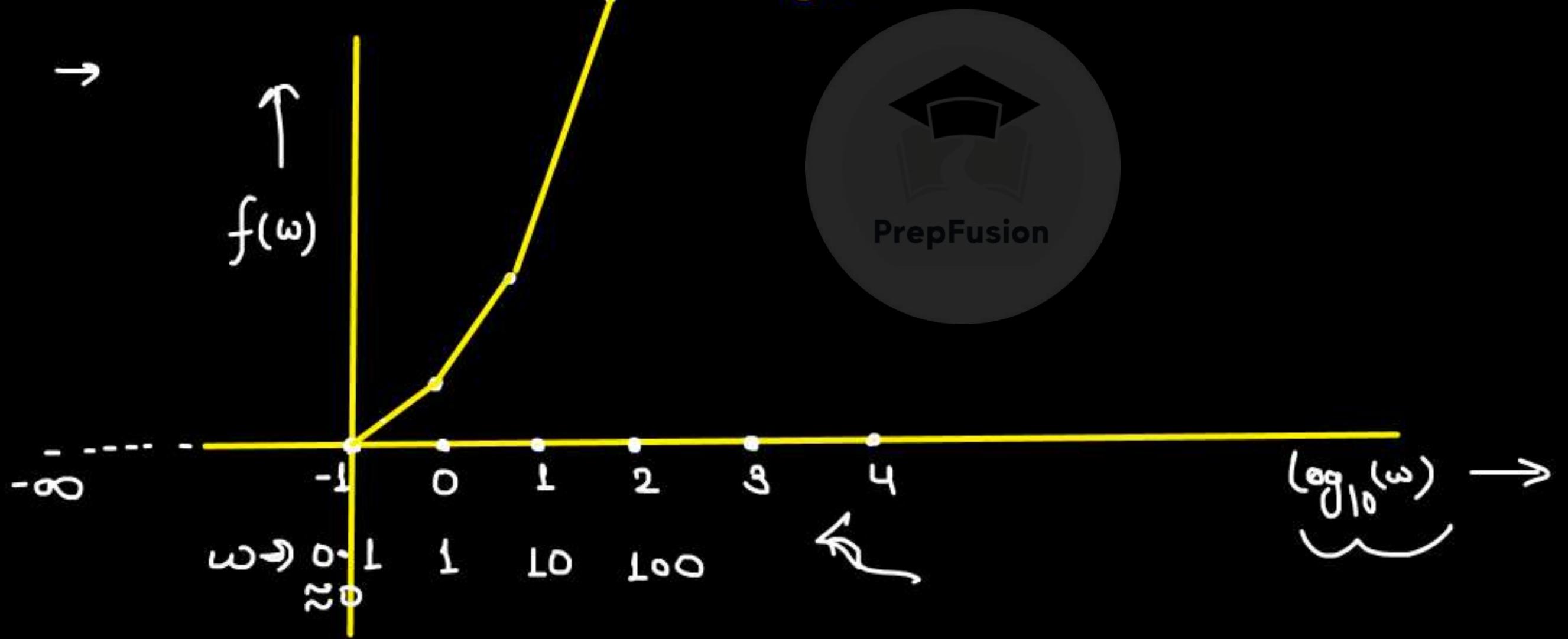


Q.
★ ★

$$f(\omega) = \begin{cases} \omega, & 0 \leq \omega \leq 100 \\ 0, & \text{o/w} \end{cases}$$

Draw $f(\omega)$ v/s ω .

↳ But the x-axis is in log scale.

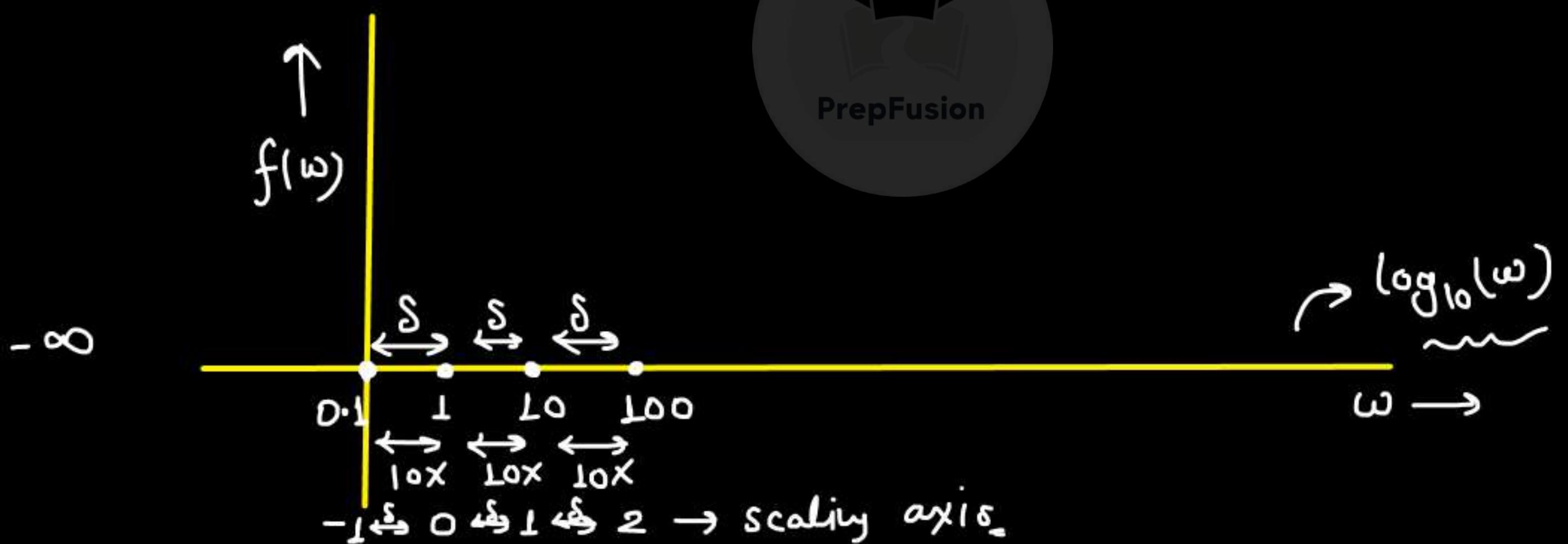


Q.

$$f(\omega) = \begin{cases} \omega, & 0 \leq \omega \leq 100 \\ 0, & 0/\omega \end{cases}$$

Draw $|f(\omega)|_{dB}$ vs ω .

Considering x-axis in log-scale.

→

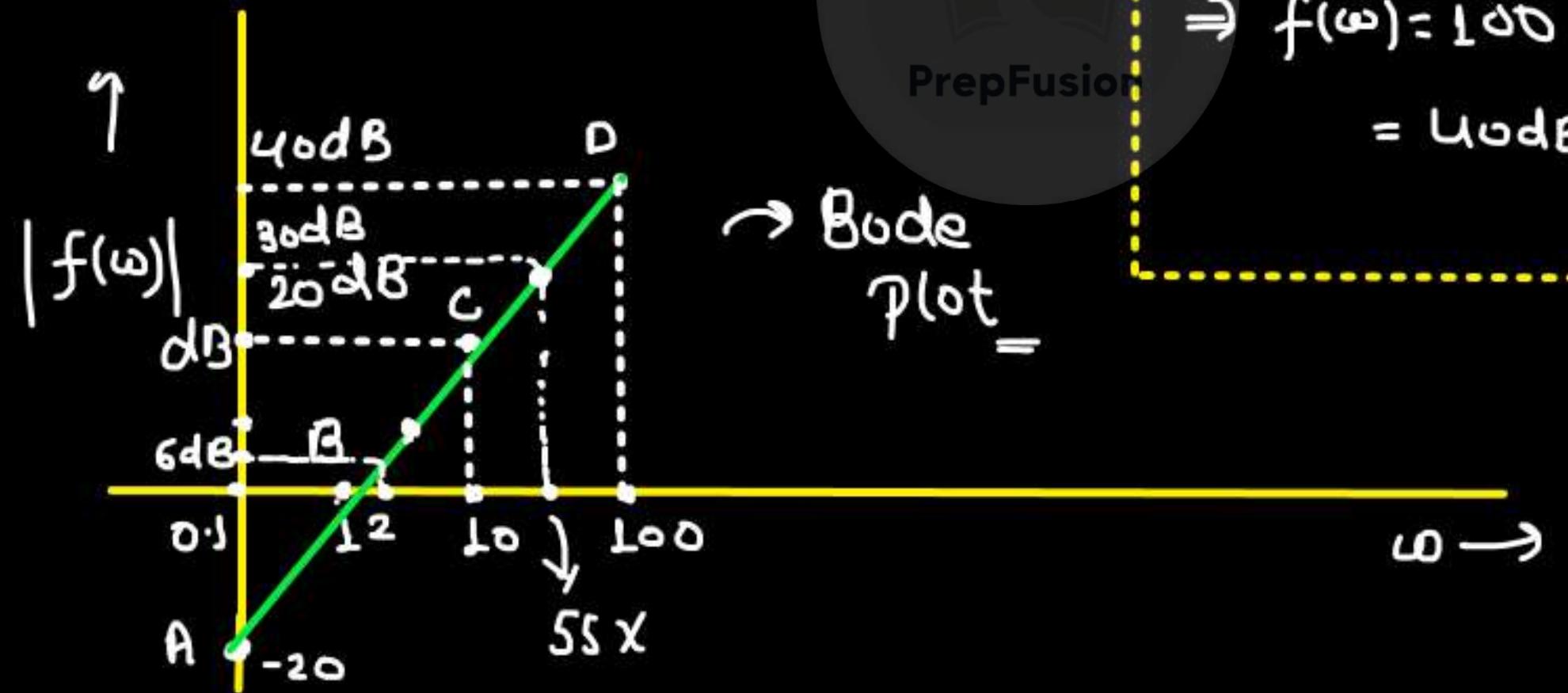

* Decimal to dB conversion

$$x = 20 \log_{10} \frac{x}{\text{decimal}}$$

Q. Convert 10 in dB
 $\rightarrow 20 \log_{10} 10 = 20$ dB

$$\omega = 10^0 \Rightarrow f(\omega) = 100 = 40 \text{ dB}$$

$$\omega = 0.1 \Rightarrow f(\omega) = 0.1 = -20 \text{ dB}$$

$$\omega = 1 \Rightarrow f(\omega) = 1 = 0 \text{ dB}$$

$$\omega = 2 \Rightarrow f(\omega) = 2 = 6 \text{ dB}$$

$$\omega = 10 \Rightarrow f(\omega) = 10 = 20 \text{ dB}$$

Slope of AB = Slope of BC = Slope of CD
= Slope of AD

* Slope of AD = $\frac{40 - (-20)}{\log_{10} 100 - \log_{10} 0.1}$

$$= \frac{60}{\log_{10}\left(\frac{100}{0.1}\right)}$$

Slope of AD = 20 dB/dec.

* Frequency Response :-

↳ ***
↳ Magnitude + Phase =

Q. Draw the frequency response of the following Transfer function.

$$T(s) = \frac{L}{2s+L}$$



$$s = j\omega$$

$$T(j\omega) = \frac{L}{2j\omega + L}$$

$$|T(j\omega)| = \frac{L}{\sqrt{L^2 + 4\omega^2}}$$



$$\angle T(j\omega) = -\tan^{-1}(2\omega)$$



$$|T(j\omega)| = \frac{1}{\sqrt{1+4\omega^2}}$$

$$\angle T(j\omega) = -\tan^{-1}(2\omega)$$

ω	$ T(j\omega) $	$\angle T(j\omega)$
0	1	0°
$\frac{1}{2}$	$\frac{1}{\sqrt{2}}$	-45°
∞	0	-90°

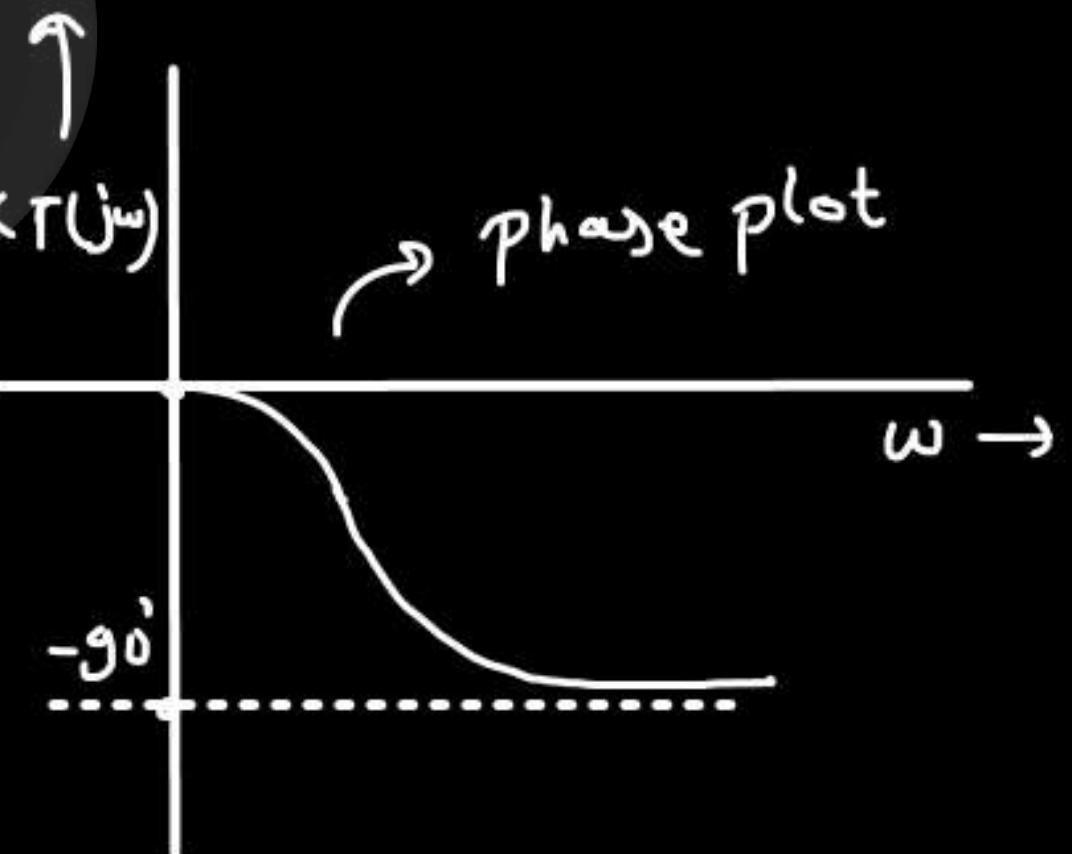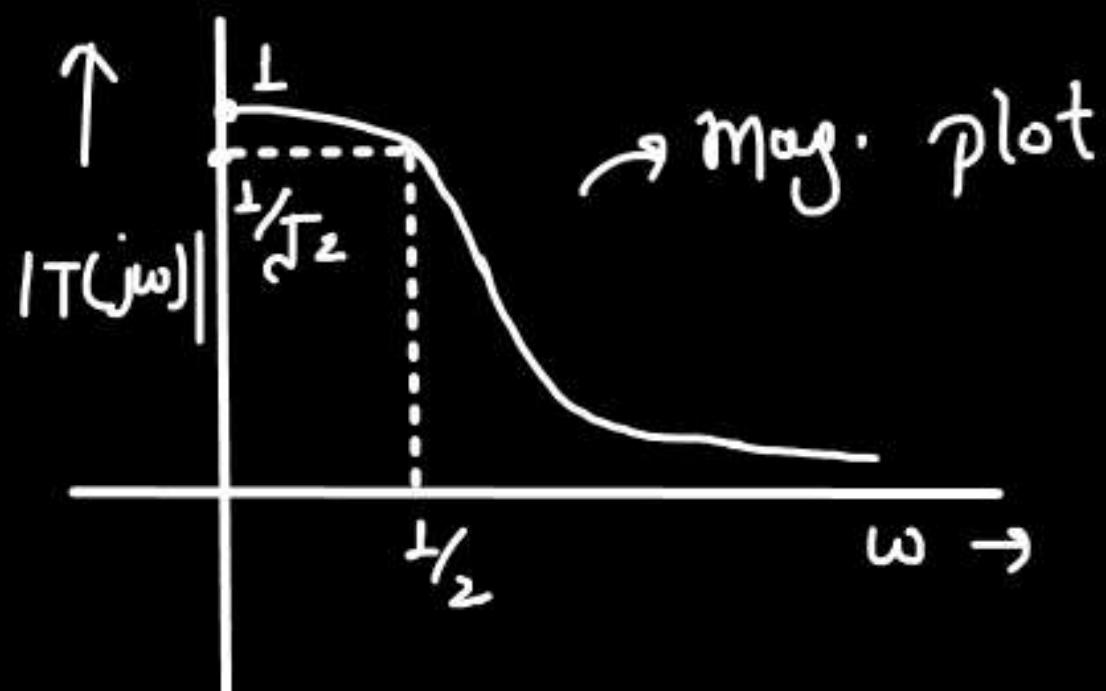

Q. Draw the frequency response of the following Transfer function.

$$T(s) = \frac{1}{2s}$$


take gain in dB.

→ $T(j\omega) = \frac{1}{2j\omega}$

$$|T(j\omega)| = \frac{1}{2\omega}$$

ω	$ T(j\omega) $	$ T(j\omega) \text{ dB}$
0	∞	∞
$\frac{1}{2}$	$\frac{1}{2}$	-6
∞	0	- ∞

PrepFusion

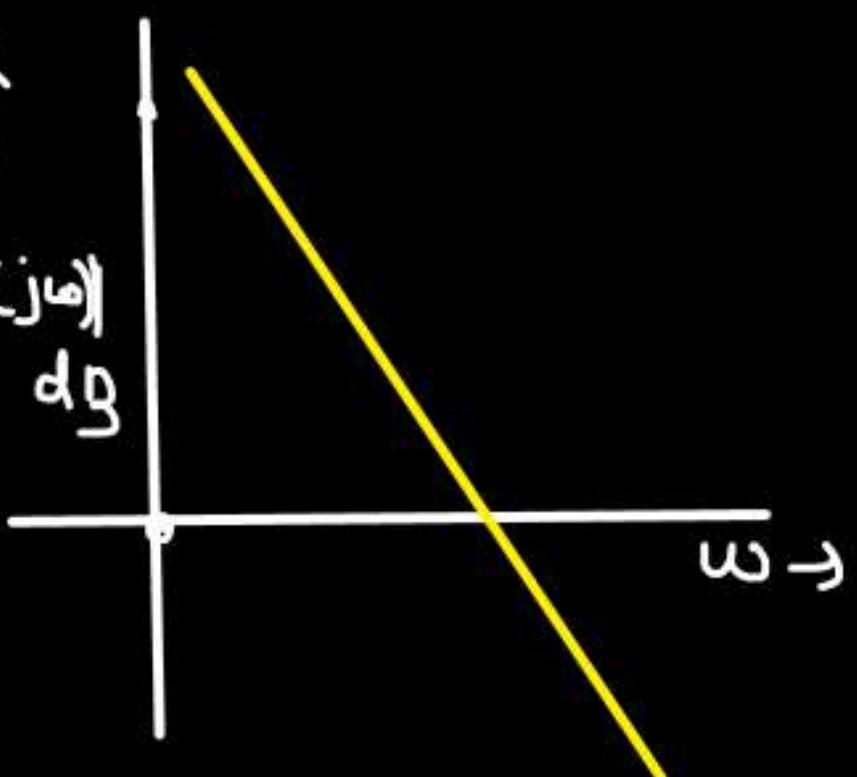

Q. Draw the frequency response of the following Transfer function.

$$T(s) = \frac{1}{2s}$$

take gain in dB. Take ω -axis in log-scale.


→ If you have a pole @ $\omega=0$

$$T(j\omega) = \frac{1}{2j\omega}$$

$$|T(j\omega)| = \frac{1}{2\omega}$$

ω	$ T(j\omega) $	$ T(j\omega) $ dB
0	∞	∞
0.1	5	13.97
1	$\frac{1}{2}$	-6
∞	0	$-\infty$

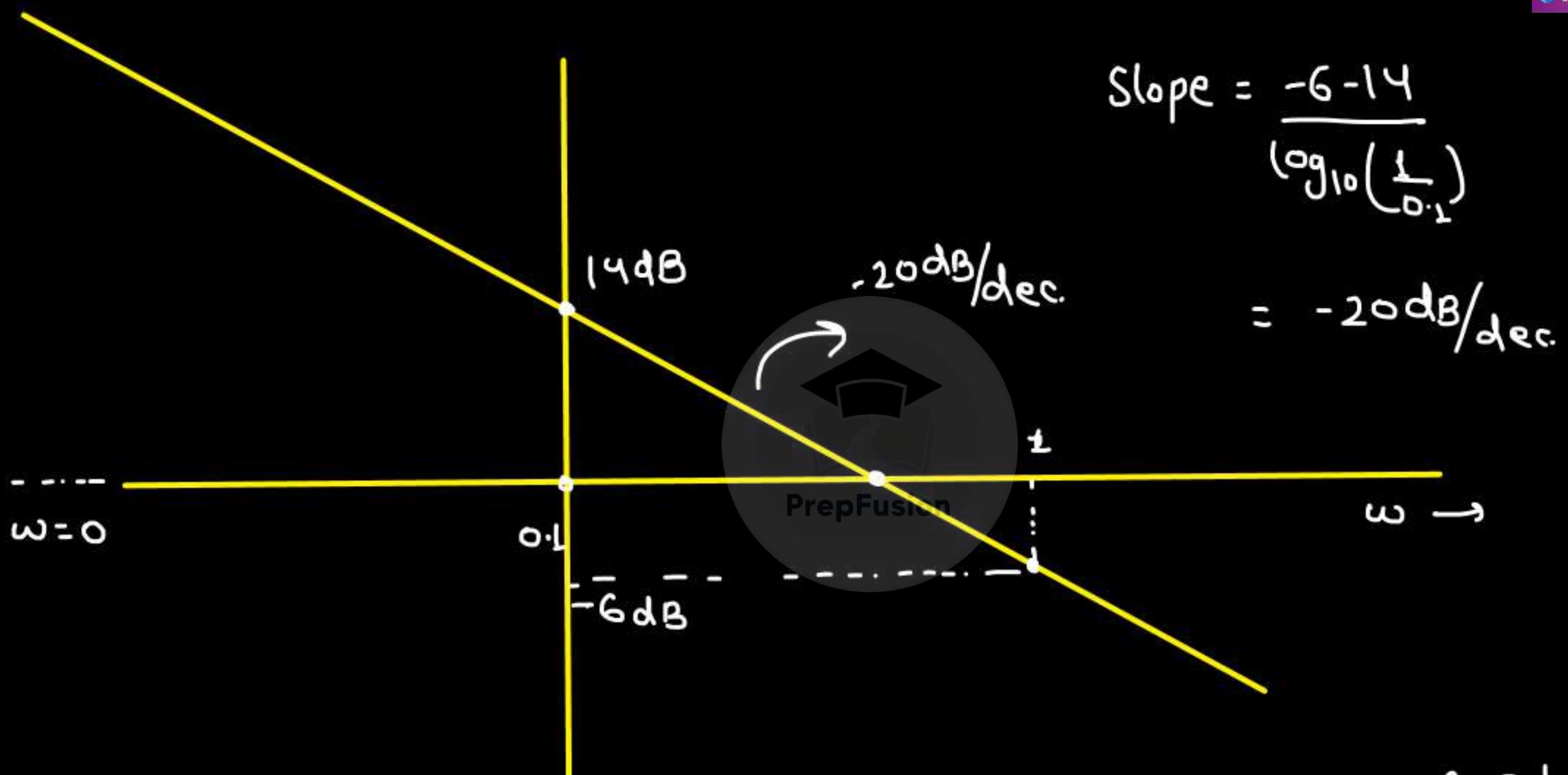when $\omega \rightarrow 0 \Rightarrow$ log scale will take $\log_{10}(0) = \underline{\underline{-\infty}}$



$$\begin{aligned} \text{Slope} &= \frac{-6 - 14}{\log_{10}\left(\frac{\omega}{\omega_1}\right)} \\ &= -20 \text{ dB/dec.} \end{aligned}$$

Prep.

N.B. → A pole gives you a slope of -20 dB/dec.

n poles give
 $-20n \text{ dB/dec.}$ slope

Q. Draw the frequency response of the following Transfer function.



$$T(s) = 2s$$

take gain in dB.



$$T(j\omega) = 2j\omega$$

$$|T(j\omega)| = 2\omega$$

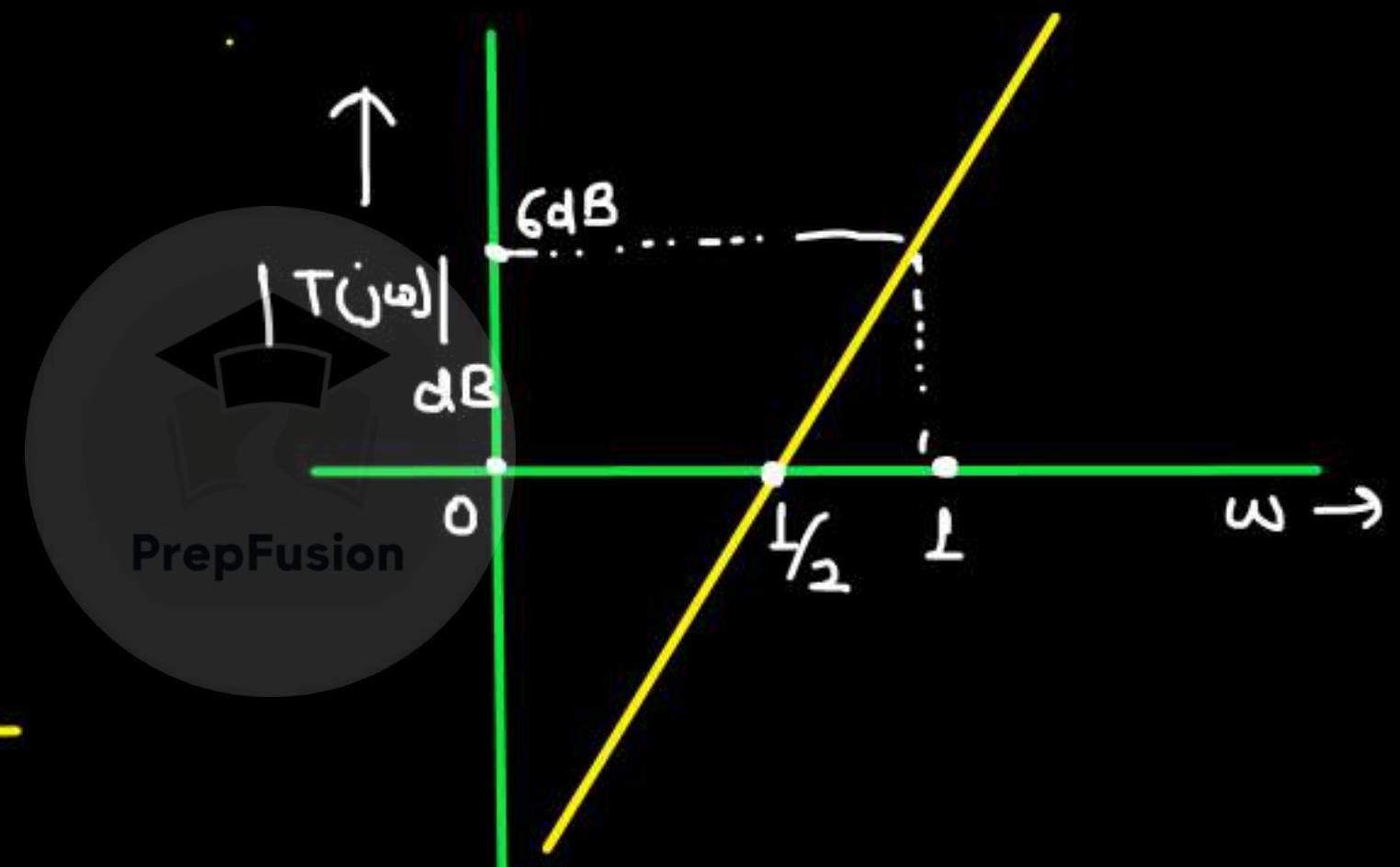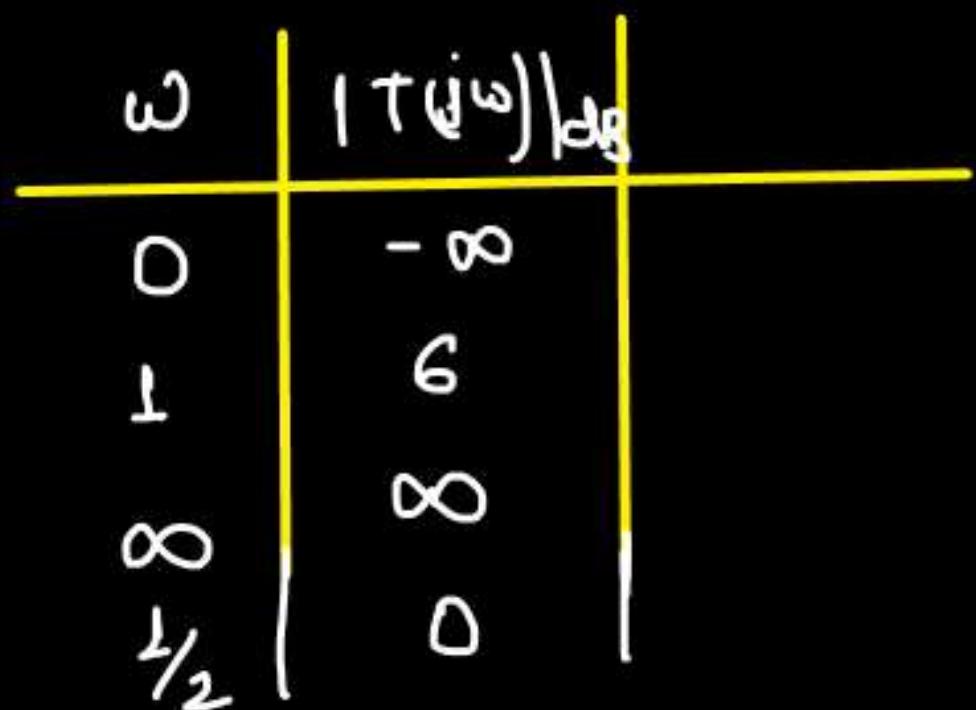


Q. Draw the frequency response of the following Transfer function.

$$T(s) = 2s$$


take gain in dB. Take x-axis in log scale.

→ $T(j\omega) = 2j\omega$

$$|T(j\omega)| = 2\omega$$

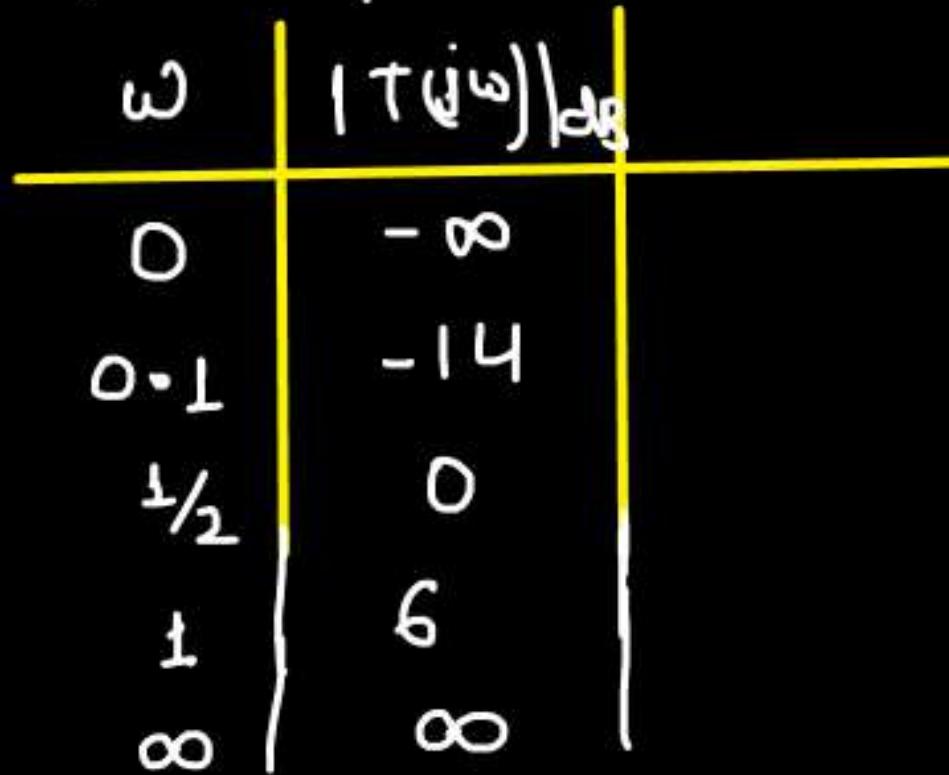

O ---

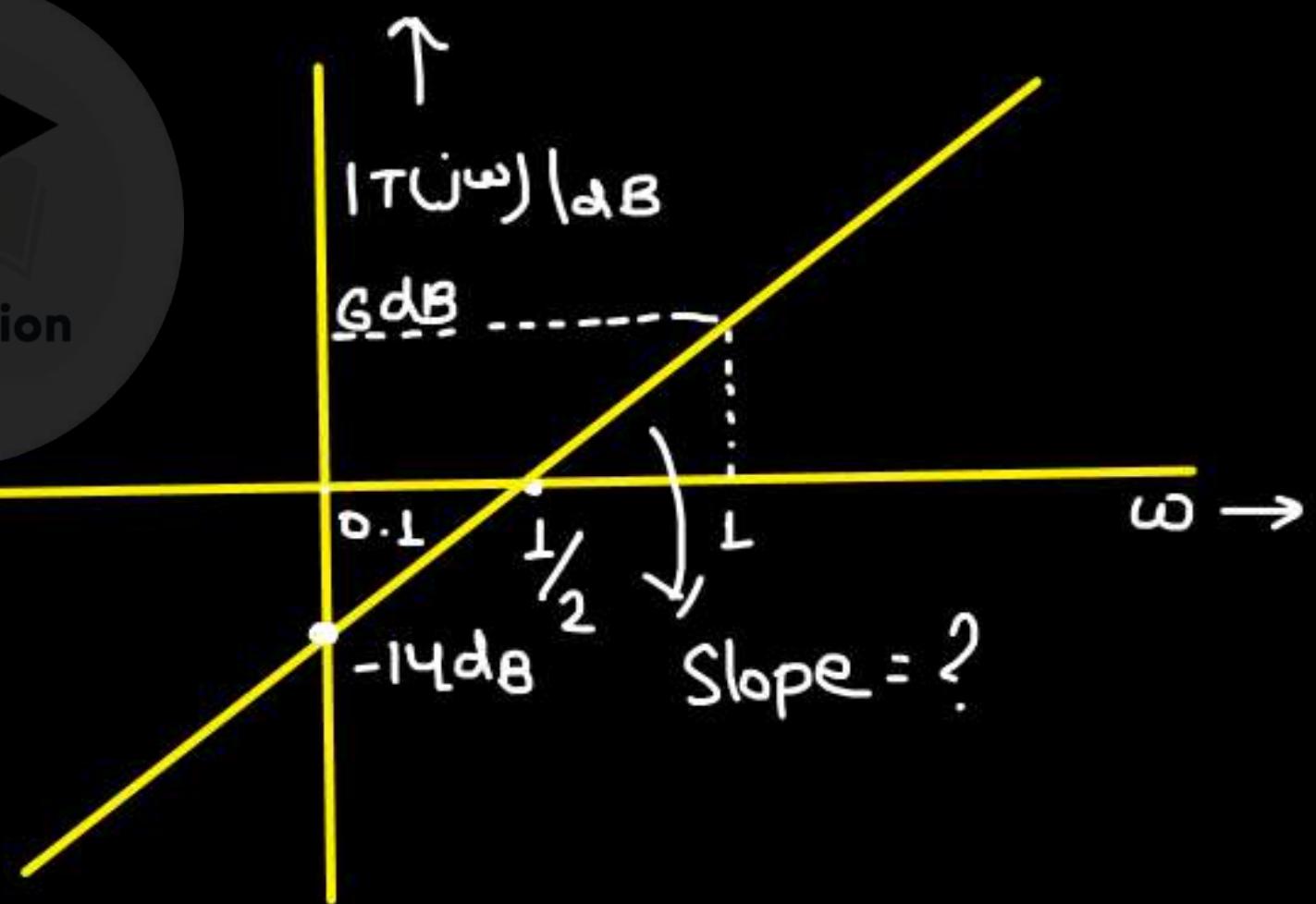

$$\text{Slope} = \frac{6 - (-14)}{\log_{10}(\frac{1}{0.1})}$$

Slope = 20 dB/dec.

Here, you had a zero @ $\omega = 0$

Ex., A zero will give you a ^{Pre} 20 dB/dec slope.

n zero will give you 20ndB/dec. slope.

* Bode plot:-

Important points :-

- ① A pole gives a slope of -20 dB/dec.
- ② A zero gives a slope of 20 dB/dec.
- ③ Assumption mode in bode plot-

$$\text{let } T(s) = s\tau + L$$

→ For $s\tau < L$

$$T(s) \approx L$$

For $s\tau > L$

$$T(s) \approx s\tau$$



* for bode plot
 ↳ gain will be in dB
 ↳ x-axis will be in log-scale
 Semi-log graph paper

Q. Draw the bode plot for the TF:

$$T(s) = \frac{3}{2s + 1}$$

→ ① Find the dc gain in dB

$$(w=0)$$

$$T(j\omega) = \frac{3}{2j\omega + 1}$$

$$T(j0) = 3$$


$$|T(j0)| = 20 \log_{10} 3 = 9.54 \text{ dB} \rightarrow \underline{\text{dc gain}}$$

② Find location of poles and zeros

$$\omega_p = -\frac{1}{2}, \text{ no zeros}$$

③ @ pole, -20 dB/dec slope.


@ zero, 20 dB/dec slope.

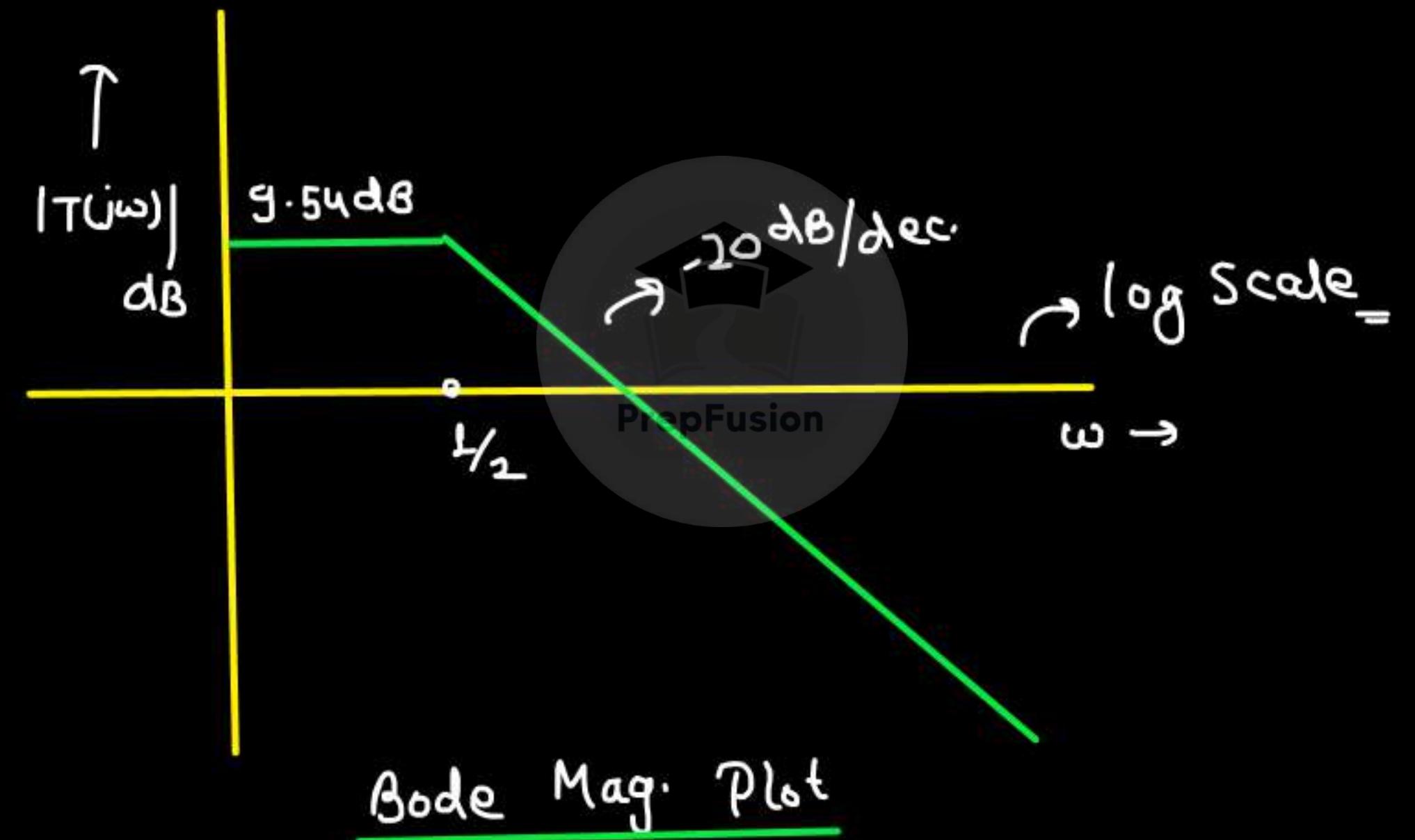

Q. find the value of A and ω' .

Freq. $2x \Rightarrow \pm 6\eta \text{ dB}$

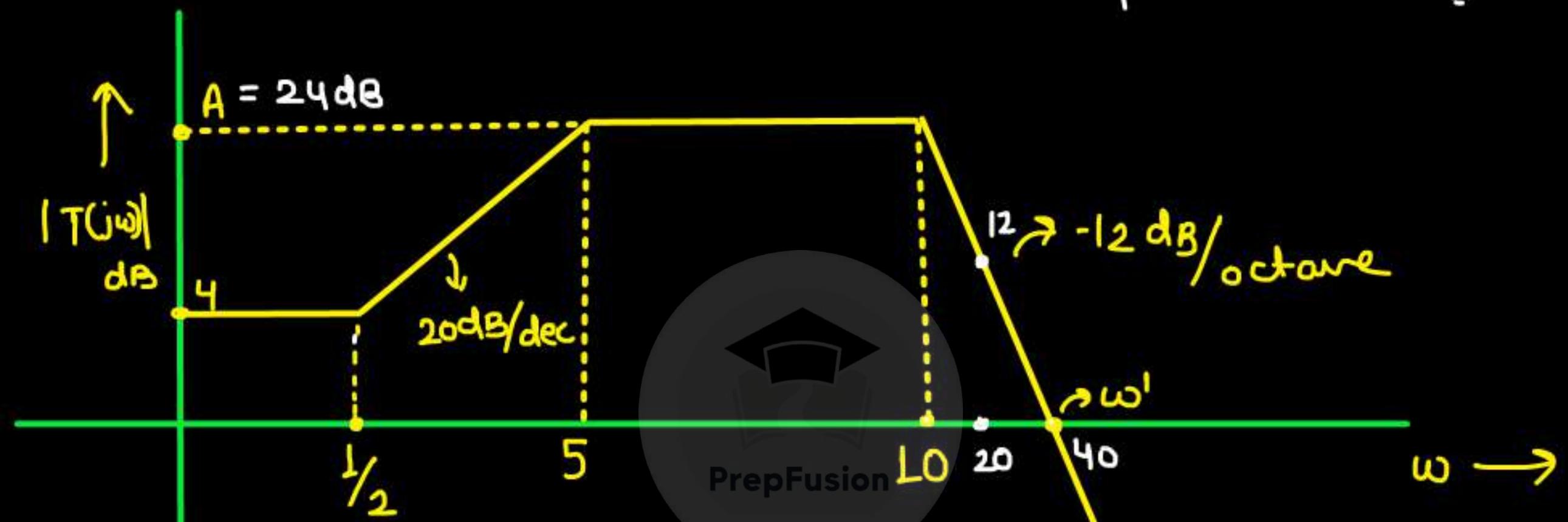Freq. $Lox \Rightarrow \pm 20\eta \text{ dB}$



$$\rightarrow 20 = \frac{A - 4}{\log_{10}\left(\frac{\omega'}{\omega_L}\right)}$$

$A = 24 \text{ dB}$

$$-12 = \frac{0 - 24}{\log_2\left(\frac{\omega'}{\omega_L}\right)}$$

$\omega' = 40 \text{ rad/sec.}$


dB/dec.

$$\text{Slope} = \frac{[y_2 - y_1] \text{ dB}}{\log_{10}\left(\frac{x_2}{x_1}\right)}$$

dB/octave

$$\text{Slope} = \frac{[y_2 - y_1] \text{ dB}}{\log_2\left(\frac{x_2}{x_1}\right)}$$


$$20 \text{ dB/dec} = 6 \text{ dB/oct}$$

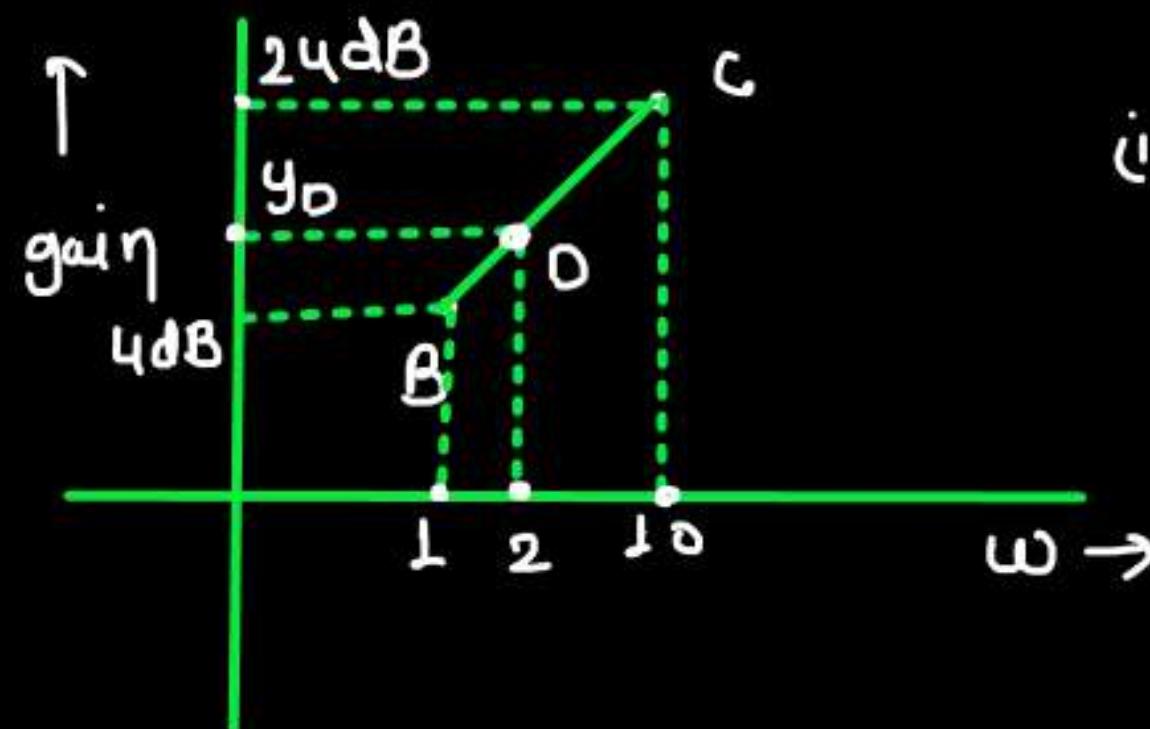

(i) Slope of BC = $\frac{20}{\log_{10}(10)} = 20 \text{ dB/dec.}$

(ii) $20 = \frac{y_D - 4}{\log_{10}(2)} \Rightarrow y_D = 4 + 20 \log_{10}(2)$

$y_D = 10 \text{ dB}$

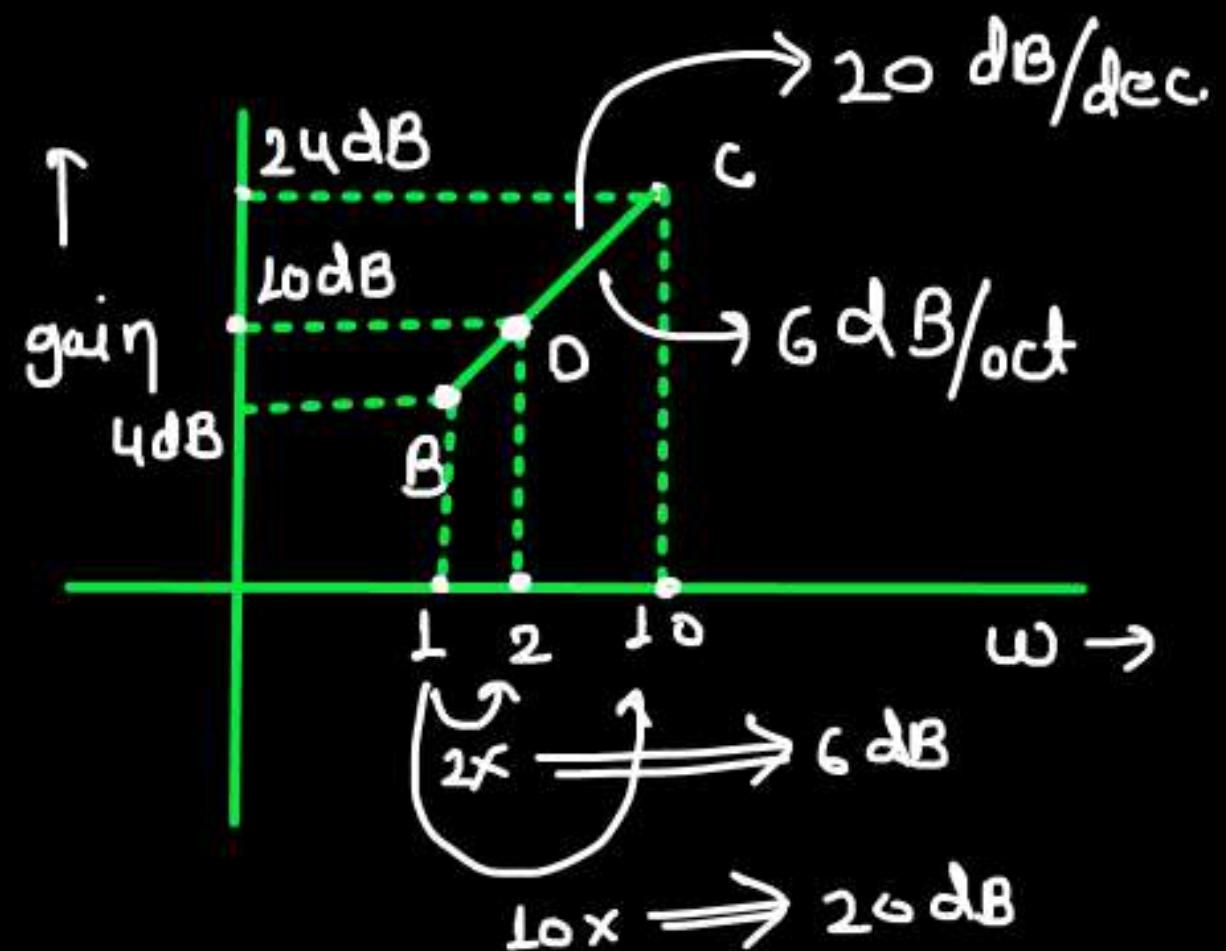

dB/dec

$$\text{Slope} = \frac{24 - 4}{\log_2(10)}$$

Slope = 6 dB/oct

* $20 \text{ dB/dec} = 6 \text{ dB/oct}$
PrepFusion

$$40 \text{ dB/dec} = 12 \text{ dB/oct}$$



$\pm 20n \text{ dB/dec} = \pm 6n \text{ dB/oct}$


Q. Draw bode plot for

$$T(s) = 2s + 1$$

→ DC gain ($\omega=0$)

$$|T(j\omega)| = 1 = 0 \text{ dB}$$

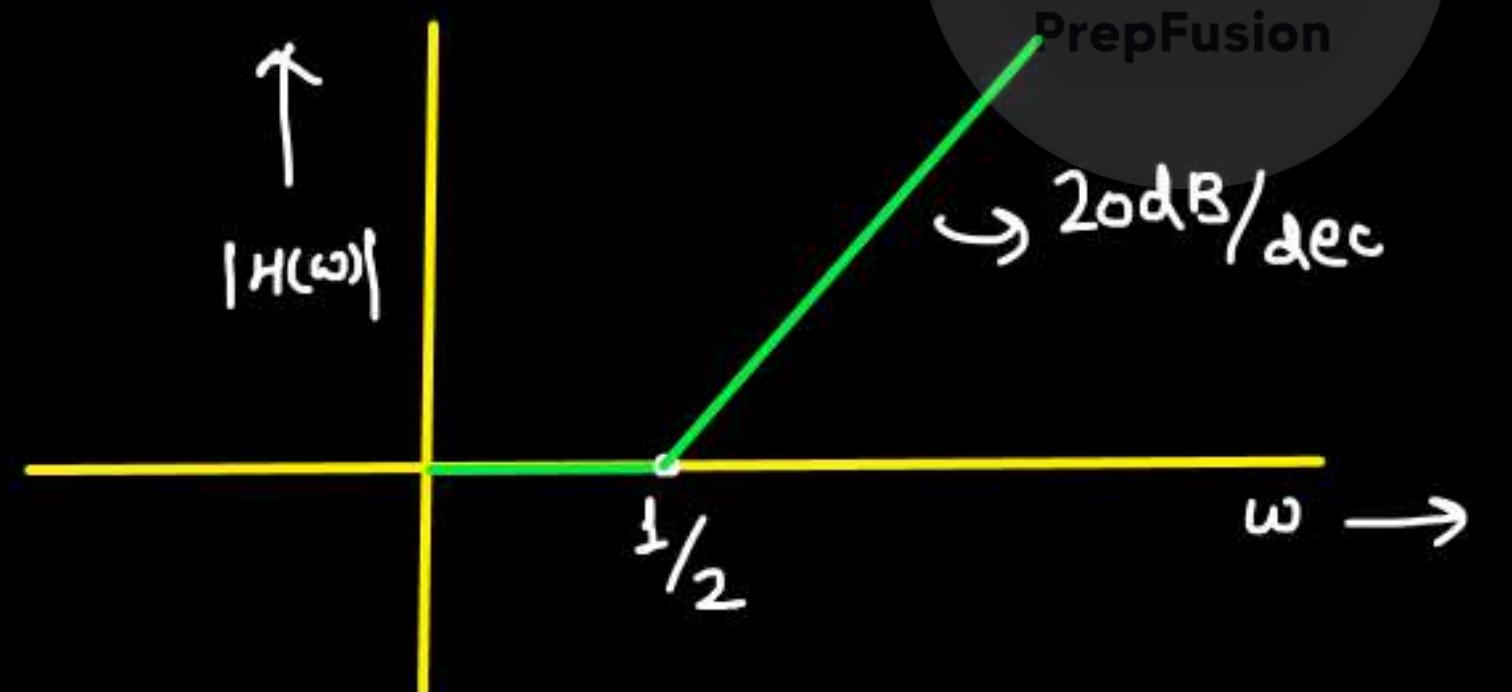$\omega_z = -1/2 \rightarrow \text{zero will give } +20 \text{ dB/dec. slope.}$



Q. Draw bode plot for

$$T(s) = \frac{10(s+4)}{(s+2)(s+10)}$$


→ DC gain = $\frac{10 \times 4}{10 \times 2} = 2 \Rightarrow 20 \log 2 = 6 \text{ dB}$

$\geq 1 \Rightarrow +\text{ve dB}$

$< 1 \Rightarrow -\text{ve dB}$

$$\omega_p = -2, -10$$

$$\omega_\infty = -4$$

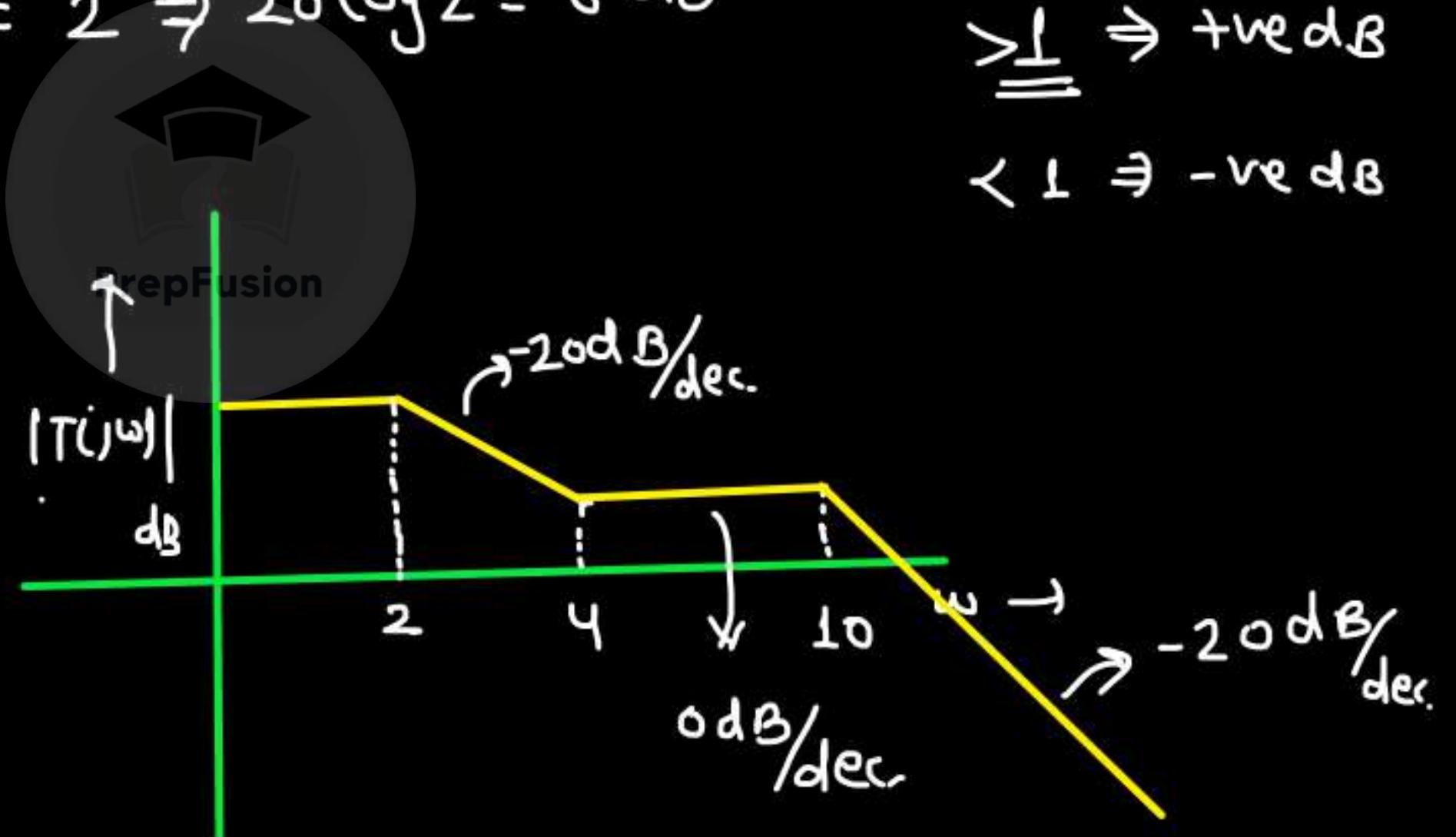


Q. Draw bode magnitude plot for

$$T(s) = \frac{10(s+2)(s+4)}{(s+1)(s+3)}$$

→ dc gain = $\frac{80}{3} = 28.5 \text{ dB}$

$$\omega_p = -1, -3$$

$$\omega_z = -2, -4$$

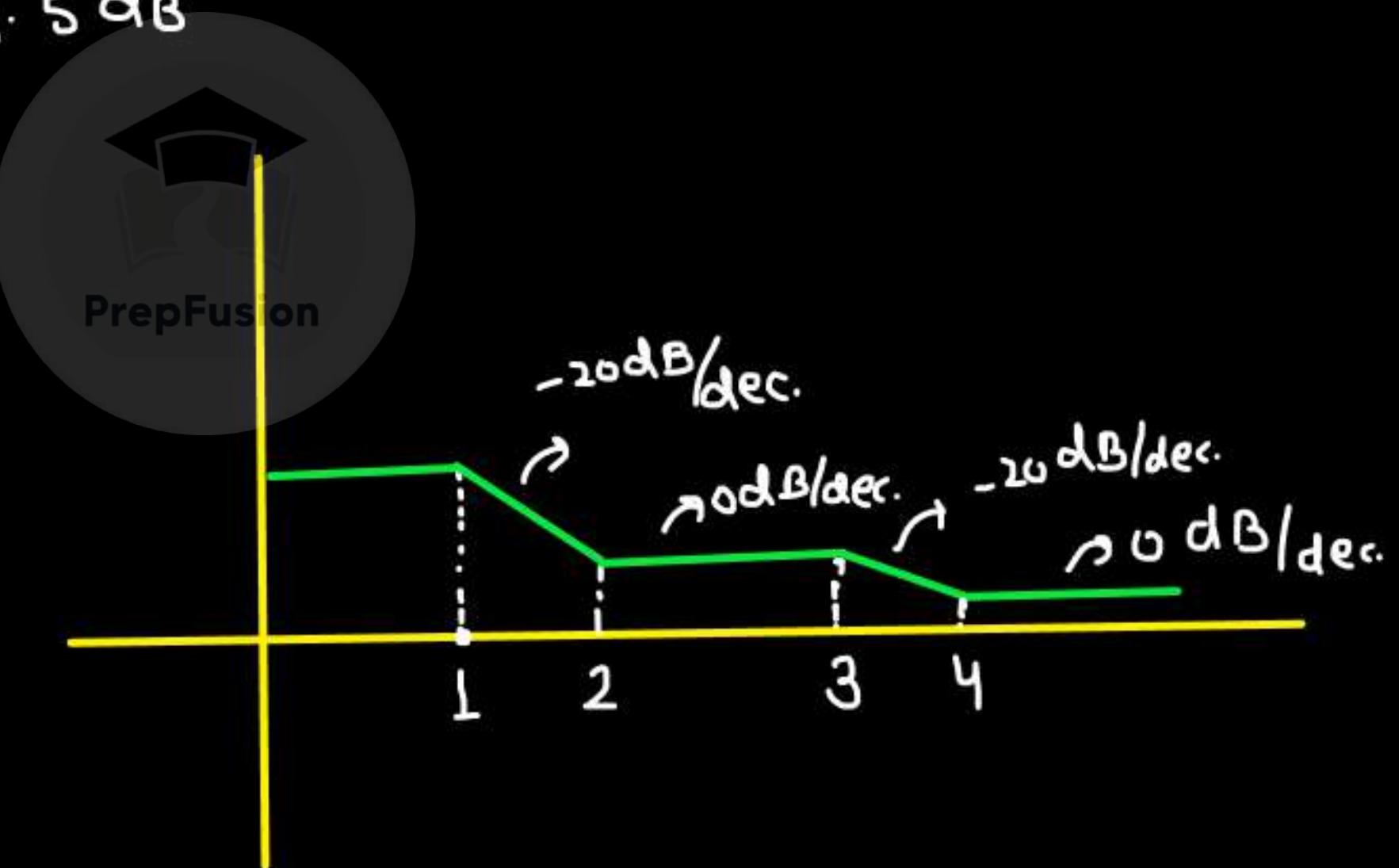


Q. Draw bode - plot for

$$T(s) = \frac{10(s+2)}{(s+3)^2(s+5)}$$

→ dc gain = -7

$\omega_p = -3, -3, -5$

$\omega_z = -2$

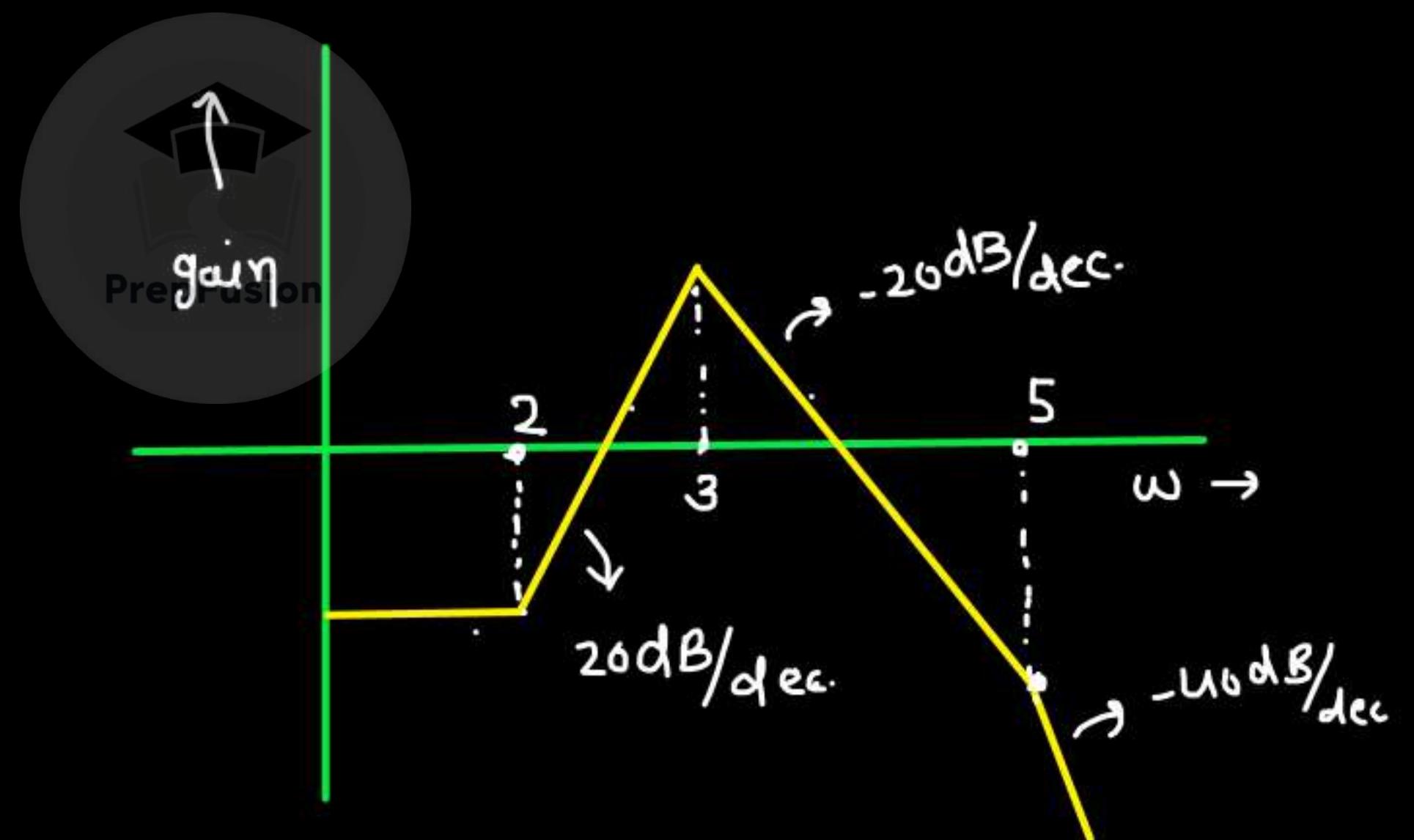


Q. Draw bode plot for:-

$$T(s) = \frac{2}{s(s+2)}$$




dc gain = ∞ = ∞ dB , Poles= 0, -2

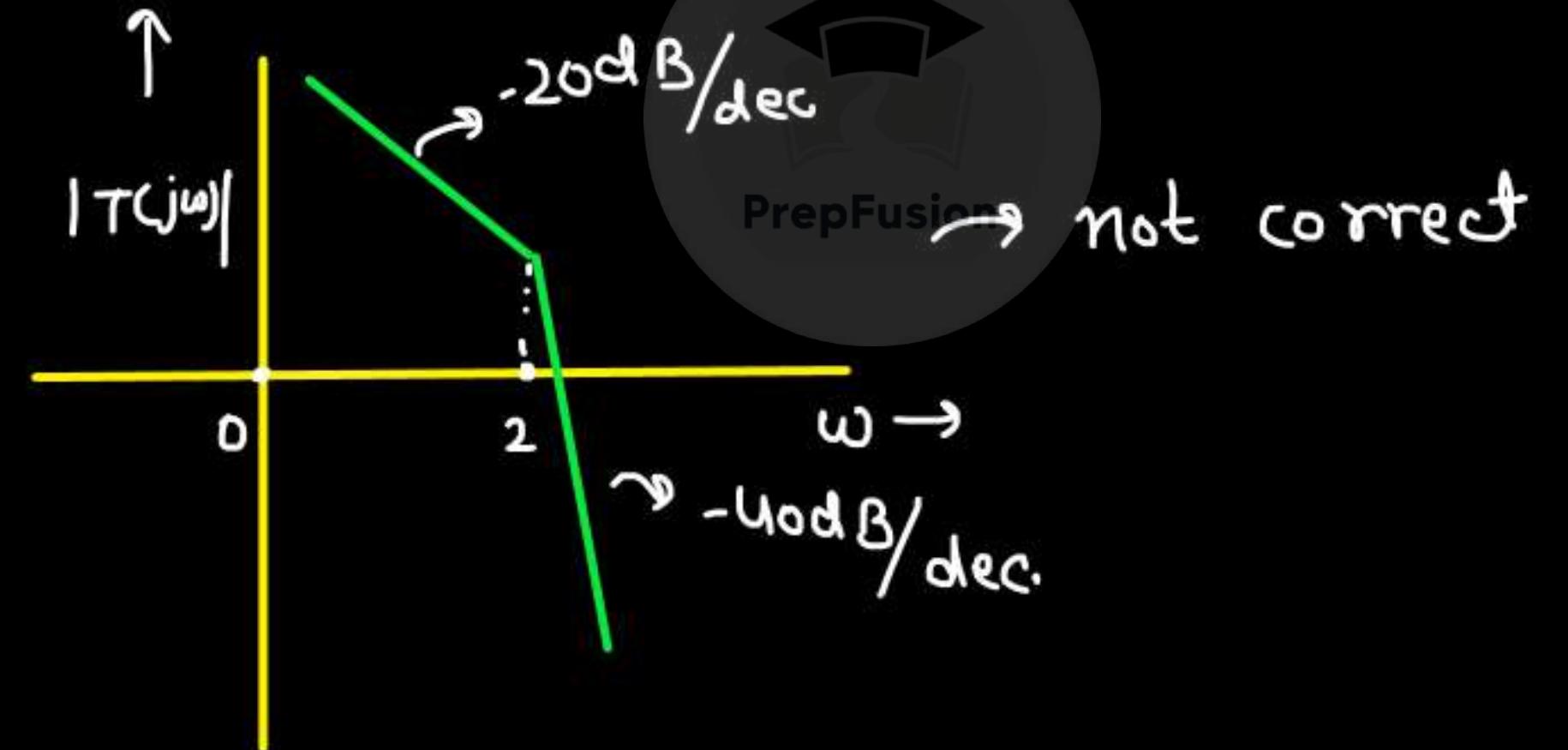


gain $\omega = 0 \cdot 1$

Here, we have pole @ $\omega = 0$ [Type -1 s/s]
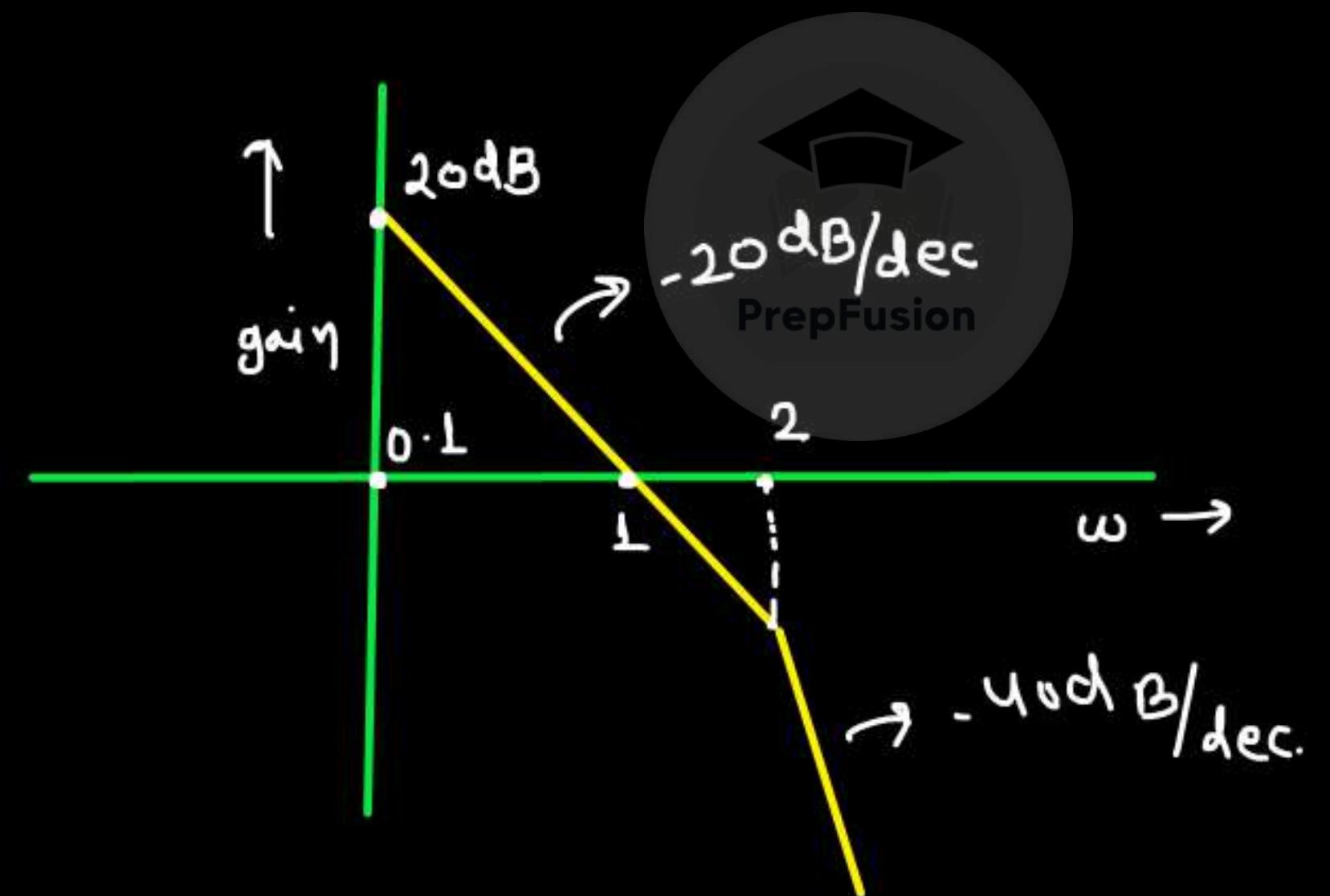
$$T(j0 \cdot 1) = \frac{2}{(0 \cdot 1)(2)} = 10 \Rightarrow 20 \text{ dB}$$



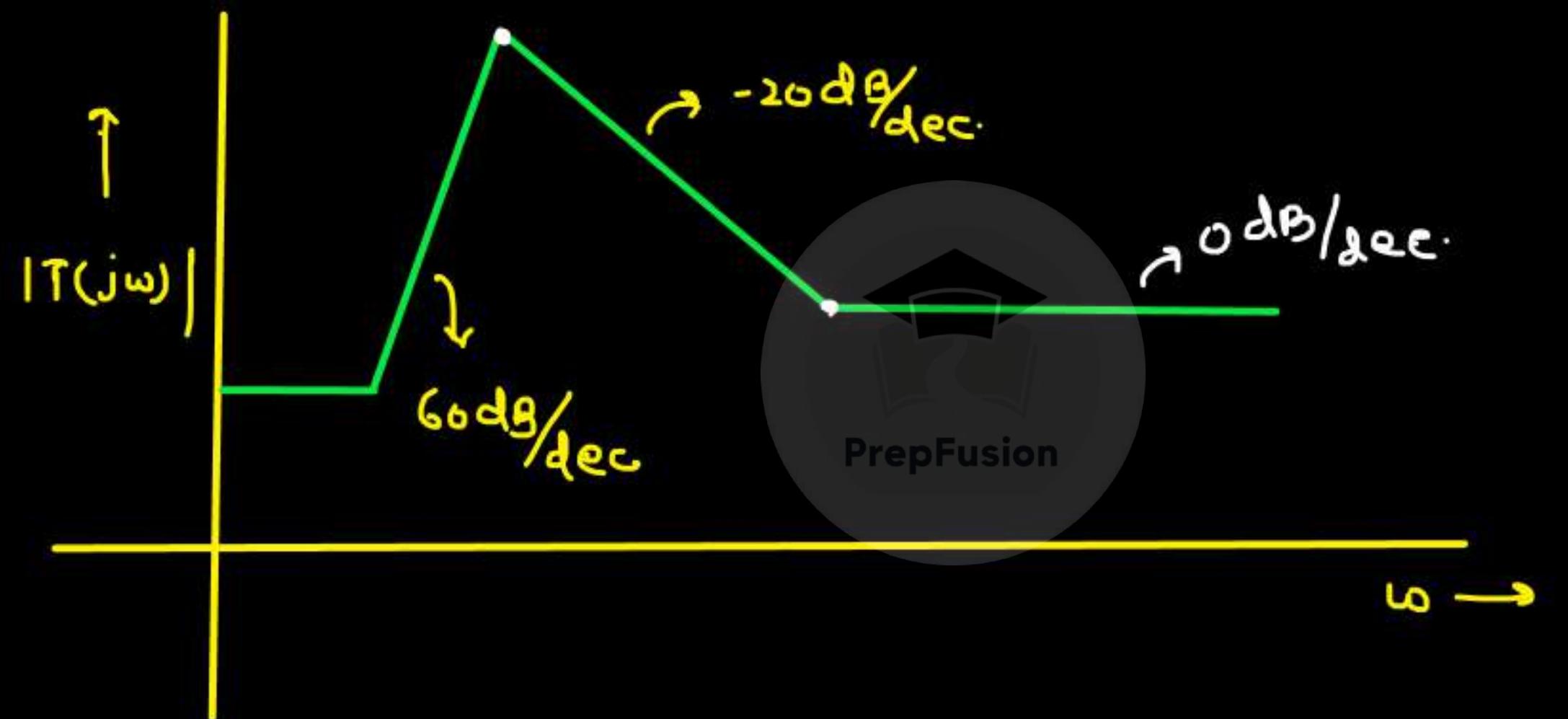
Q. find the number of poles and zero of the Transfer fⁿ.



→ $3 \text{ zeros} + 4 \text{ poles} + 1 \text{ zero} \Rightarrow 4z + 4p$


Q. Find the number of poles and zero of the Transfer f^n .

→

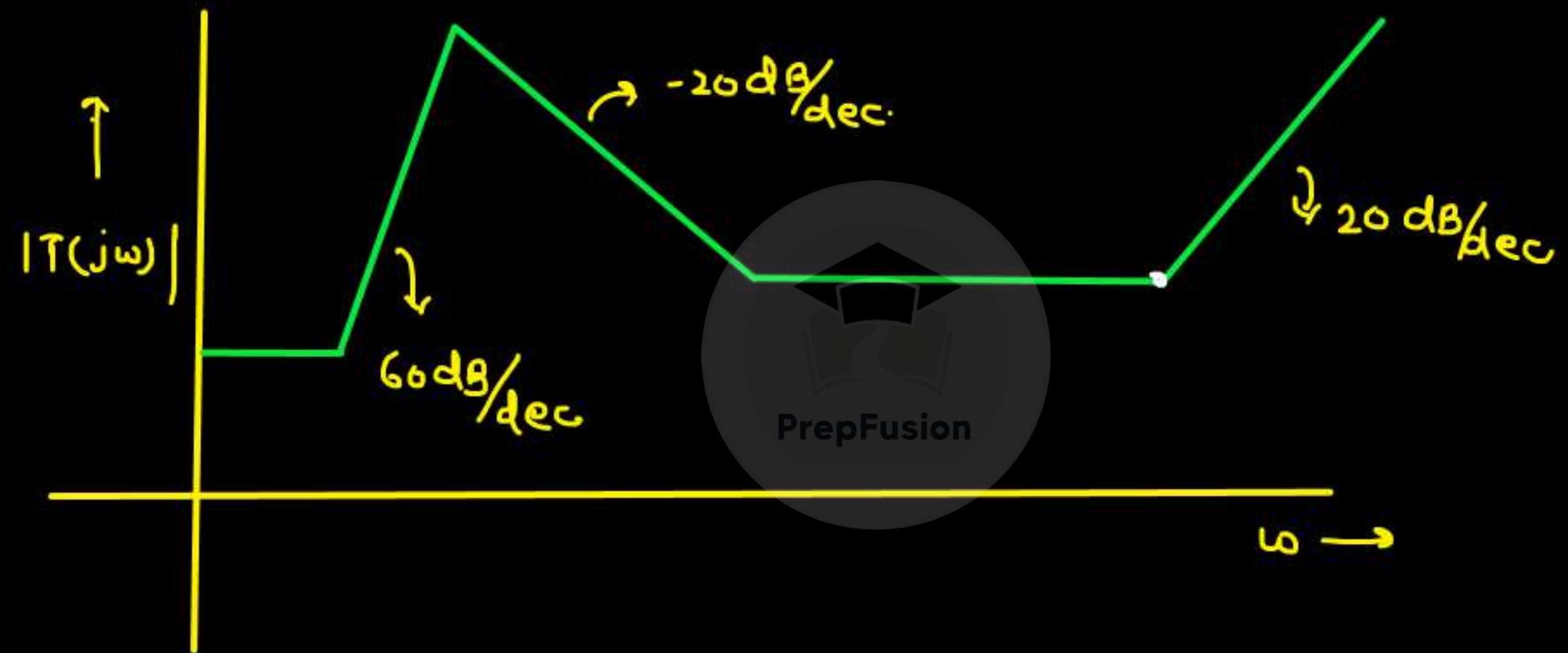

$$\rightarrow 4Z + 4P + 1Z \Rightarrow 5Z + 4P$$

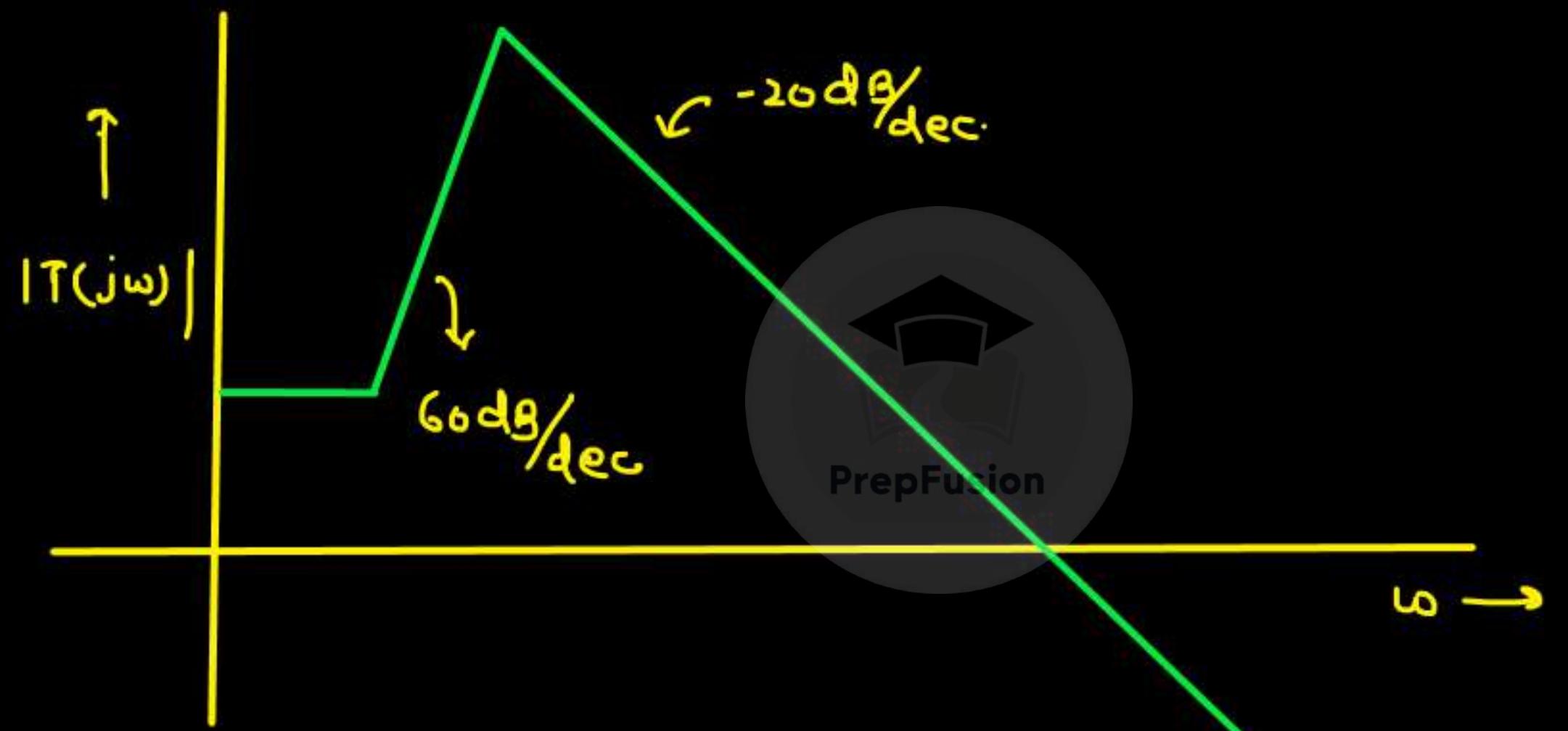Q. Find the number of poles and zero of the Transfer f^1 .



$$3Z + 4P$$

N.B. --

① For $\omega = \infty \Rightarrow$ if the slope is 0 dB/dec



No. of poles = No. of zeros

② For $\omega = \infty \Rightarrow$ if the slope is negative



No. of poles > No. of zeros

③ For $\omega = \infty \Rightarrow$ if the slope is positive



No. of poles < No. of zeros

* Bode phase plot :-

Q. Draw phase plot for

$$T(s) = s\tau + 1$$





$$T(j\omega) = j\omega\tau + 1$$

$$\angle T(j\omega) \approx \tan^{-1}(\omega\tau)$$

$$\omega = 0 \Rightarrow \angle T(j0) = 0^\circ$$
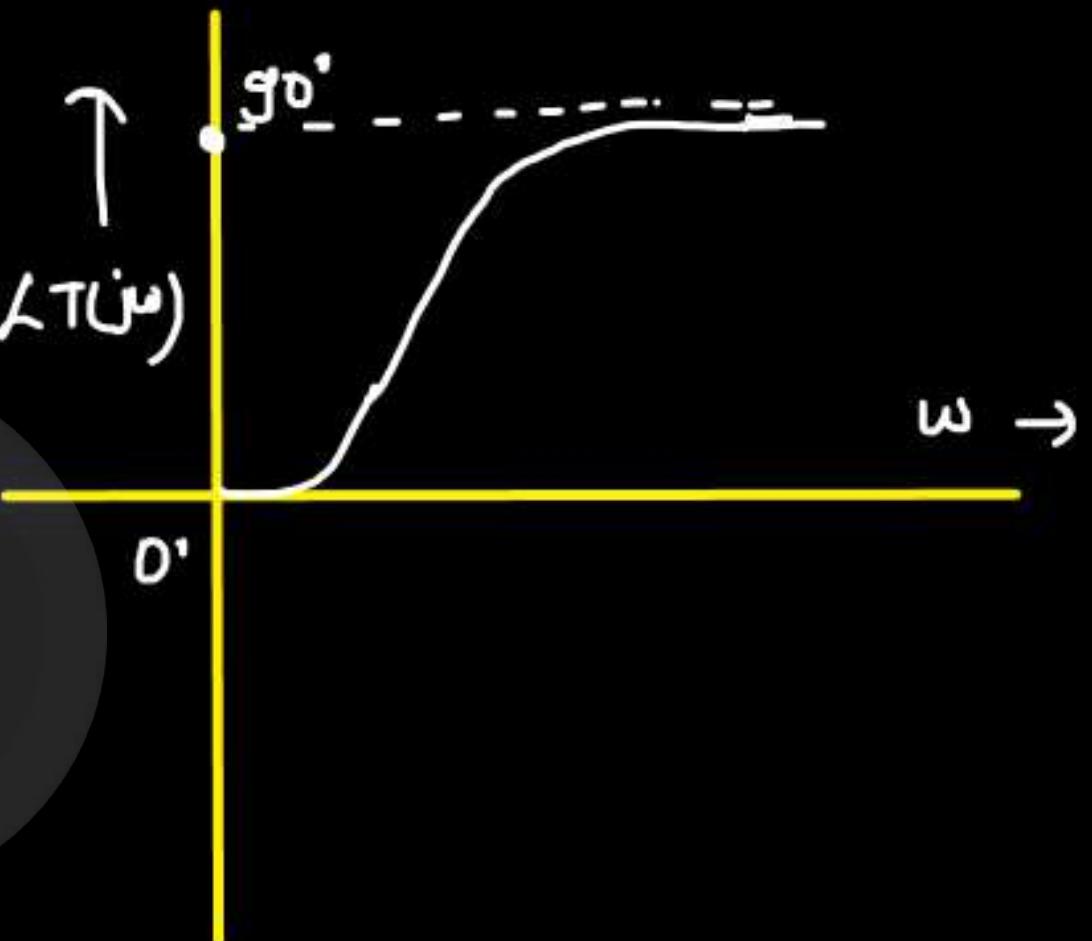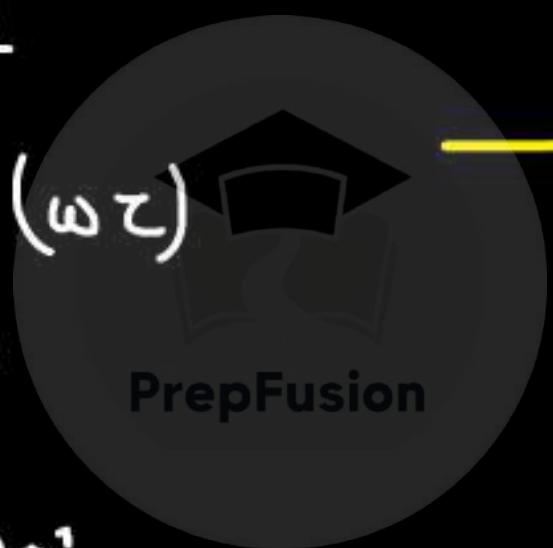
$$\omega = \infty \Rightarrow \angle T(j\infty) = 90^\circ$$




Q. Draw Bode phase plot for


$$T(s) = 2s + 1$$

→ zero $\rightarrow \omega_z = -\frac{1}{2}$

$$\angle T(j\omega) = \tan^{-1}(2\omega)$$
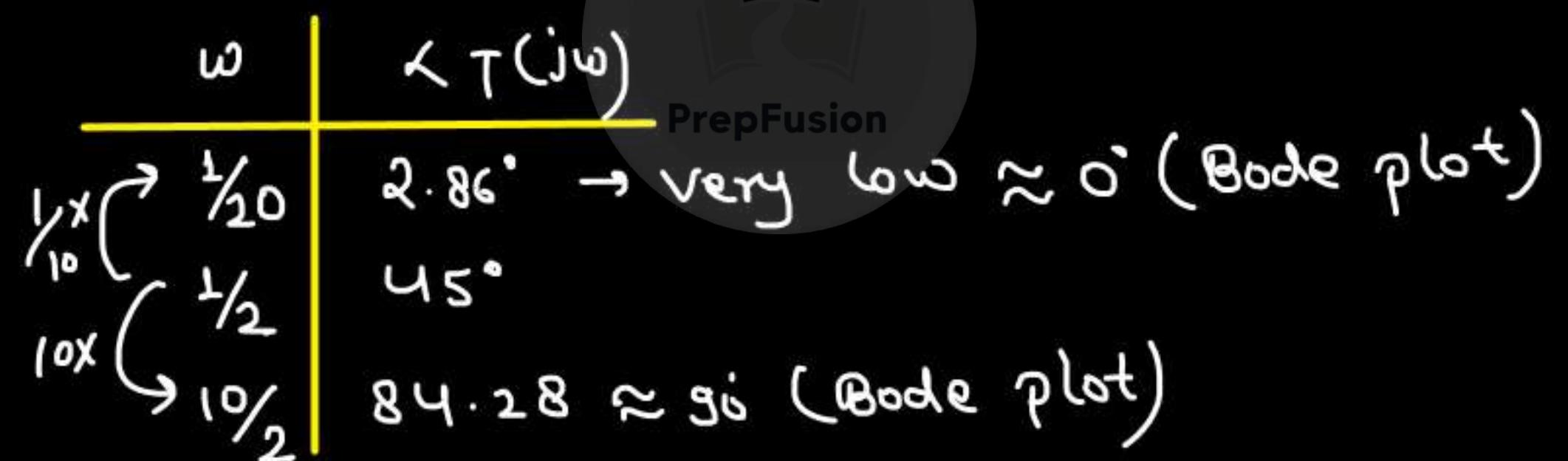
$$\tan^{-1}\left(\frac{2\omega}{\omega_z}\right)$$



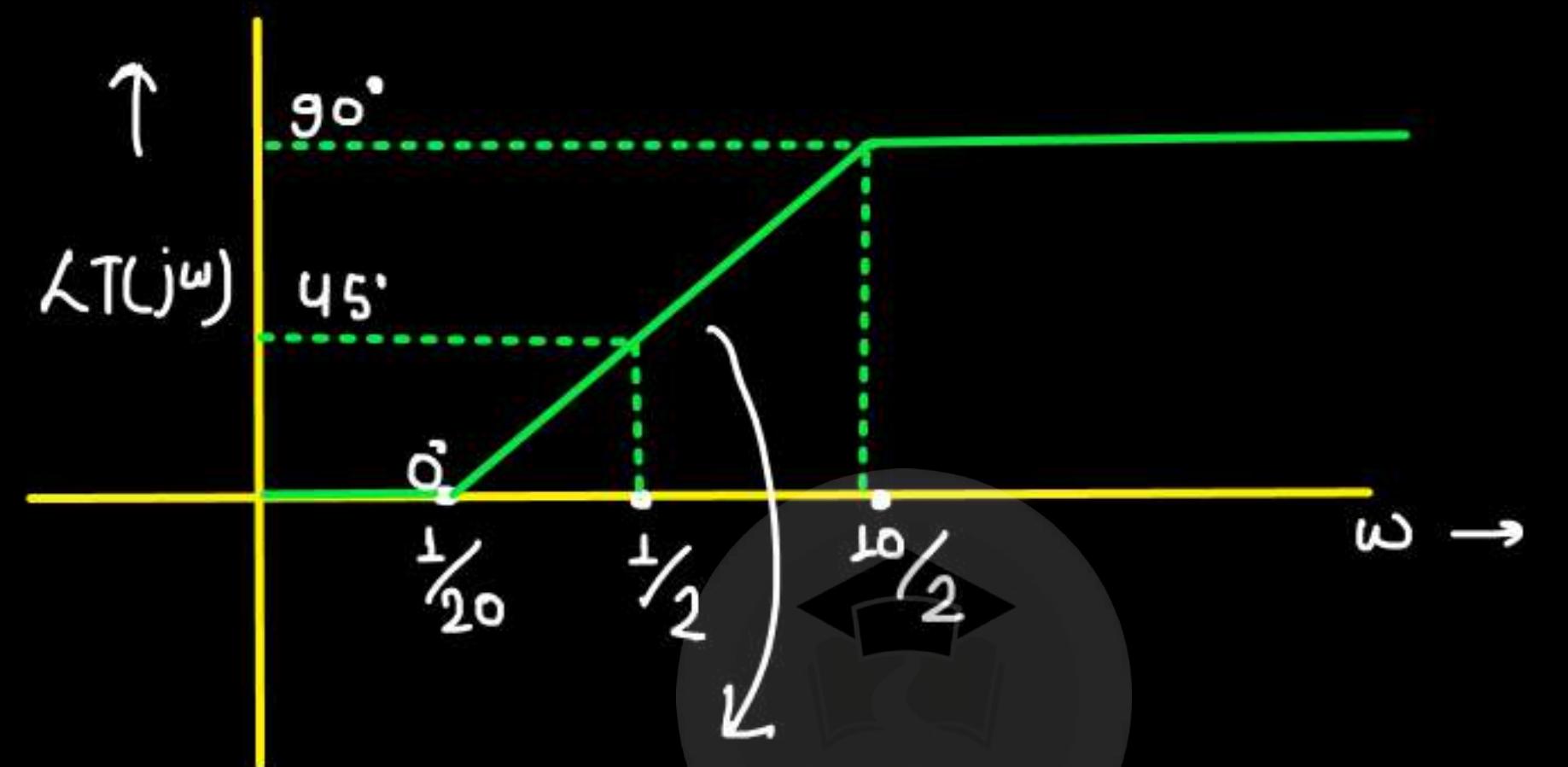

PrepFusion
 $45^\circ/\text{dec}$

η zeros will give $45^\circ\eta/\text{dec}$. slope


Q. Draw bode phase plot for


$$T(s) = \frac{L}{2s + L}$$

→

$$s_p = -\frac{1}{2}$$
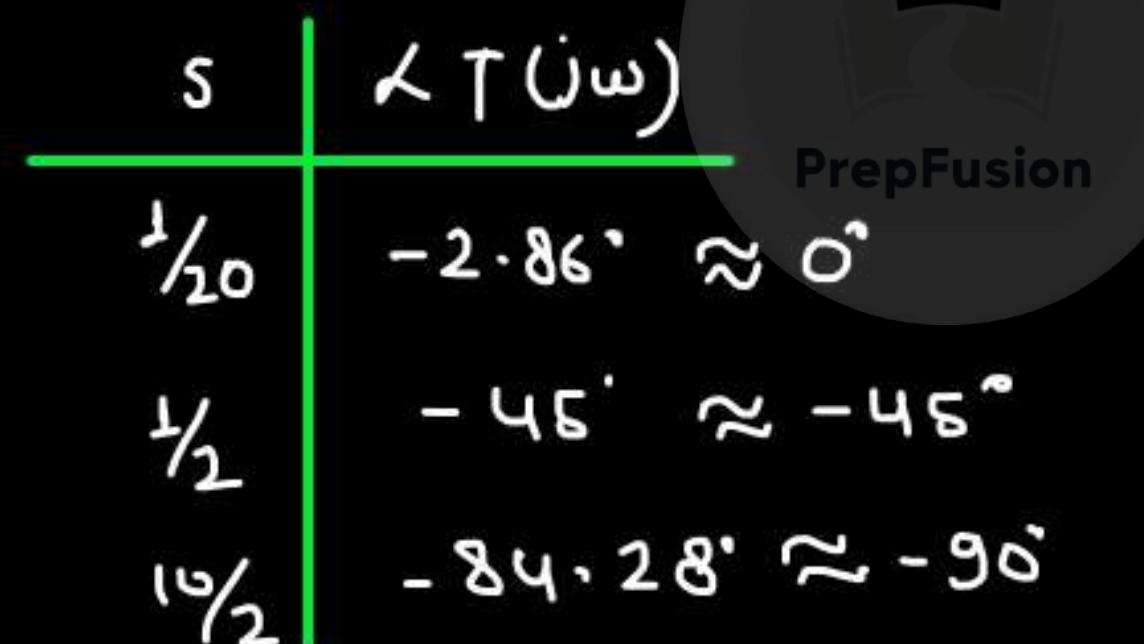
$$\angle T(j\omega) = -\tan^{-1}(2\omega)$$



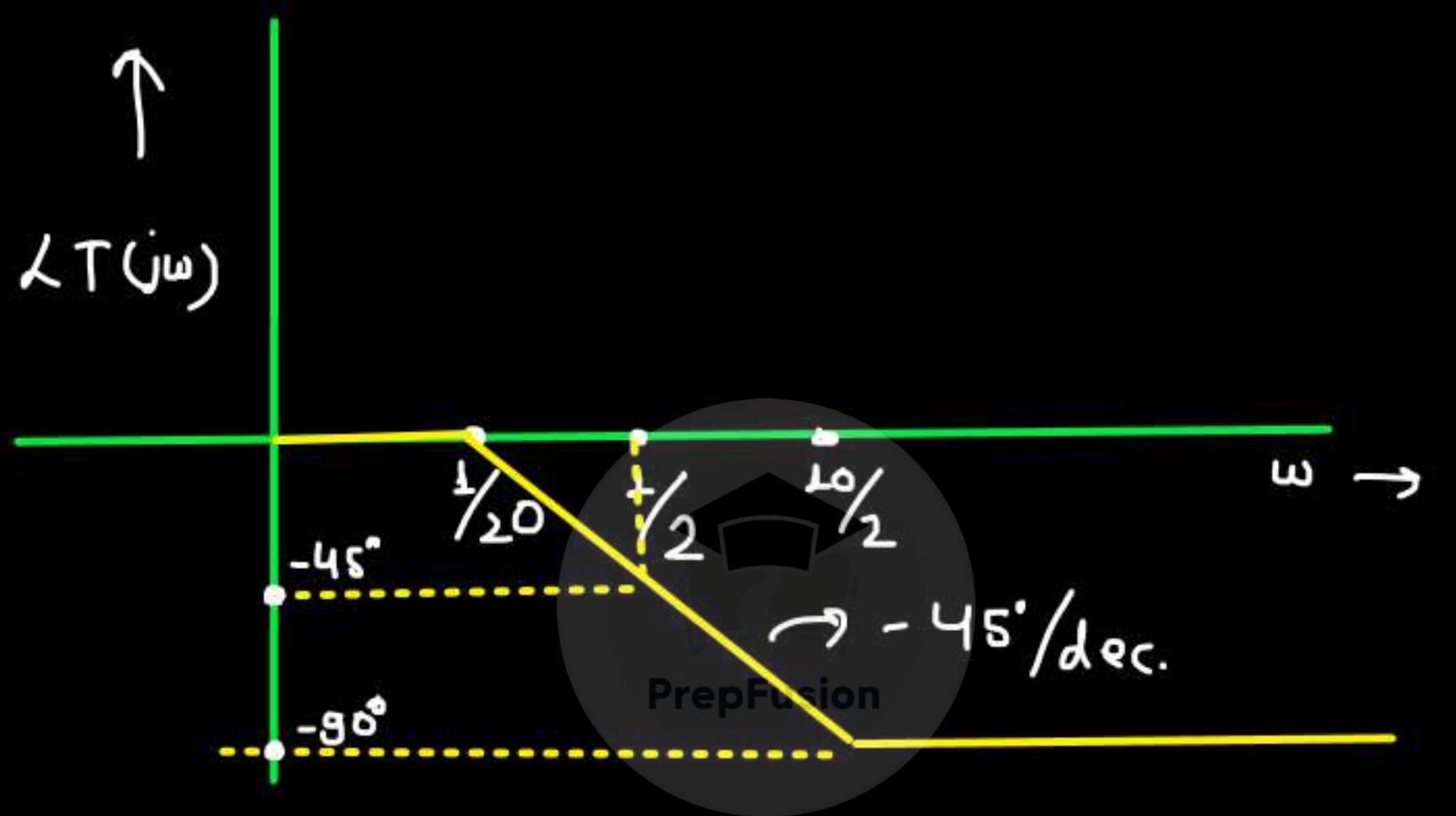


n poles will give you $-45n^\circ/\text{dec}$ slope.

Q. Draw the bode phase plot for

$$T(s) = \frac{(s + 500)}{(s + 5)}$$




→ $T(s) = T_1(s) \times T_2(s)$

$$T_1(s) = s + 500$$

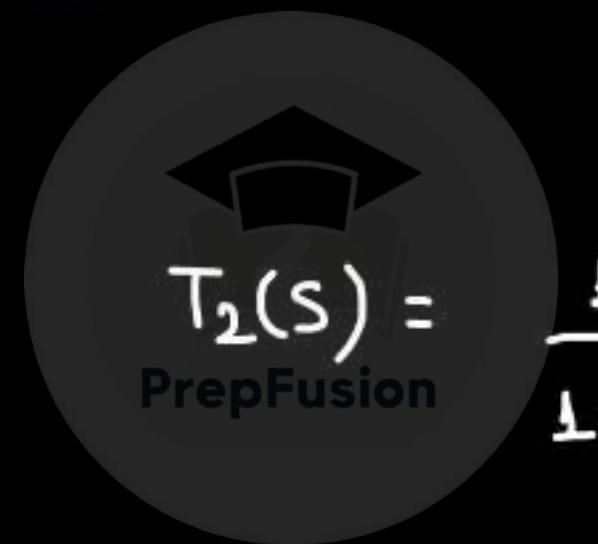

$$\frac{1}{s + 5}$$
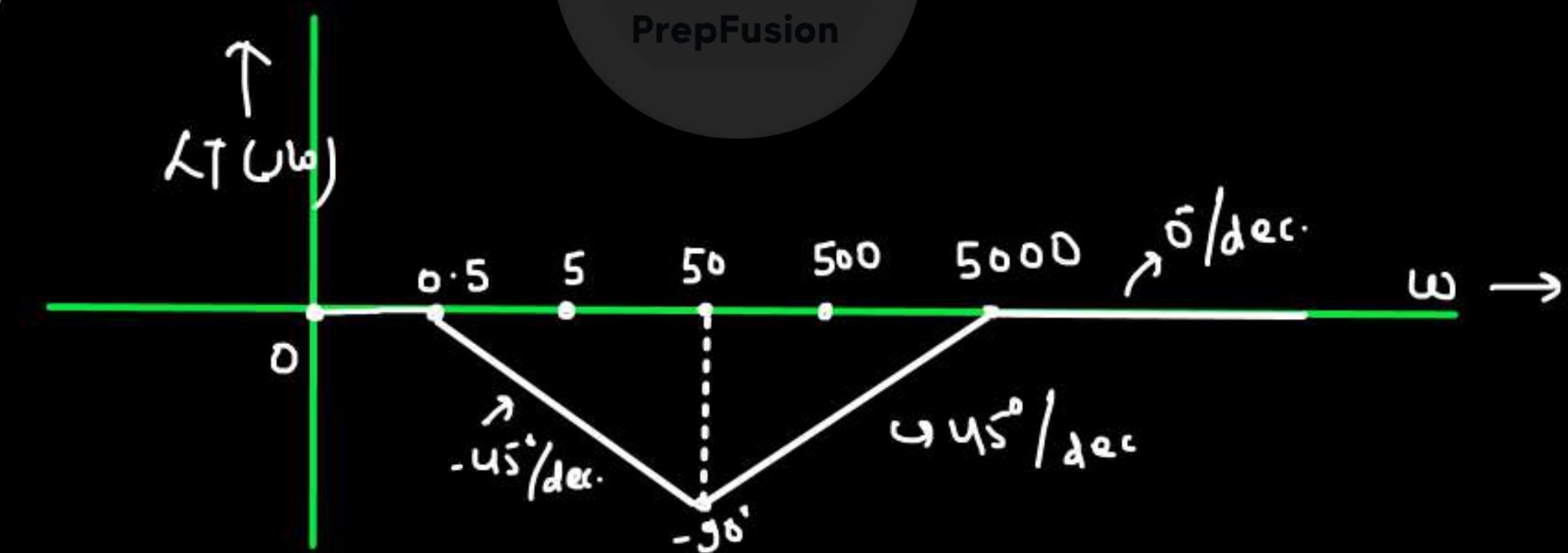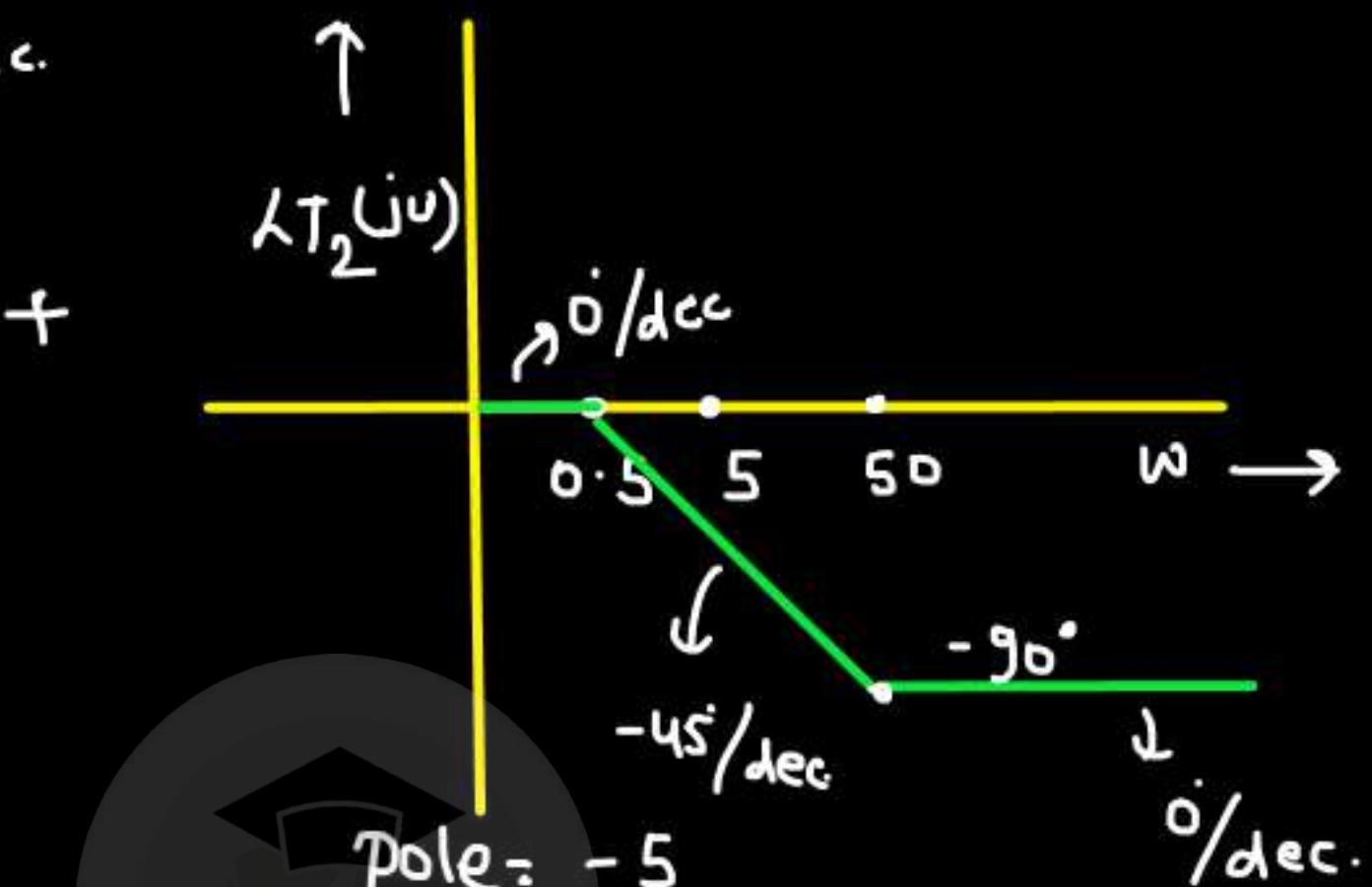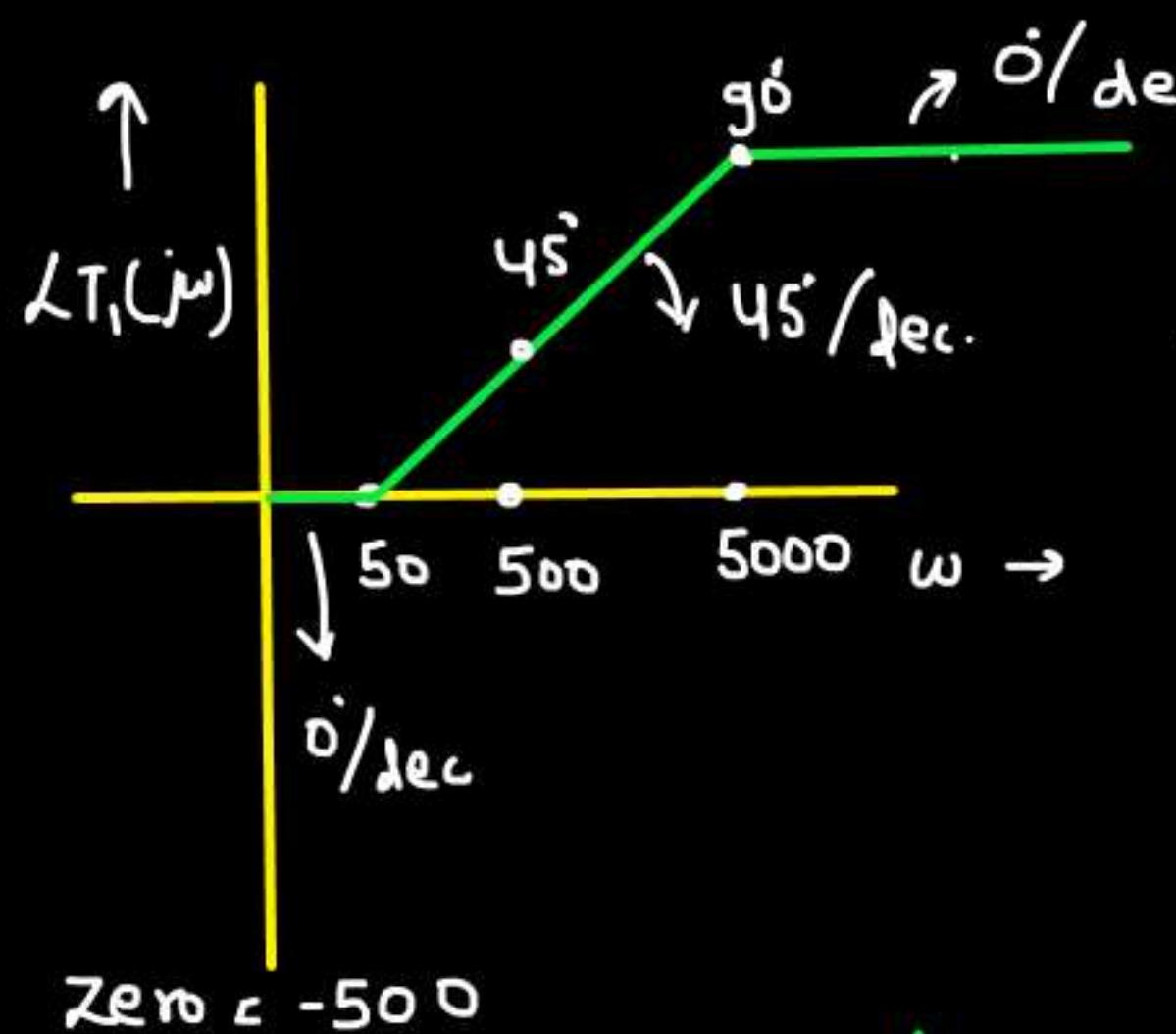
$$\angle T(j\omega) = \angle T_1(j\omega) + \angle T_2(j\omega)$$




Q. Draw bode phase plot for


$$T(s) = \frac{A}{(s+1)^2(s+5)}$$

→ $T(j\omega) = -2\tan^{-1}(\omega) - \tan^{-1}(5)$

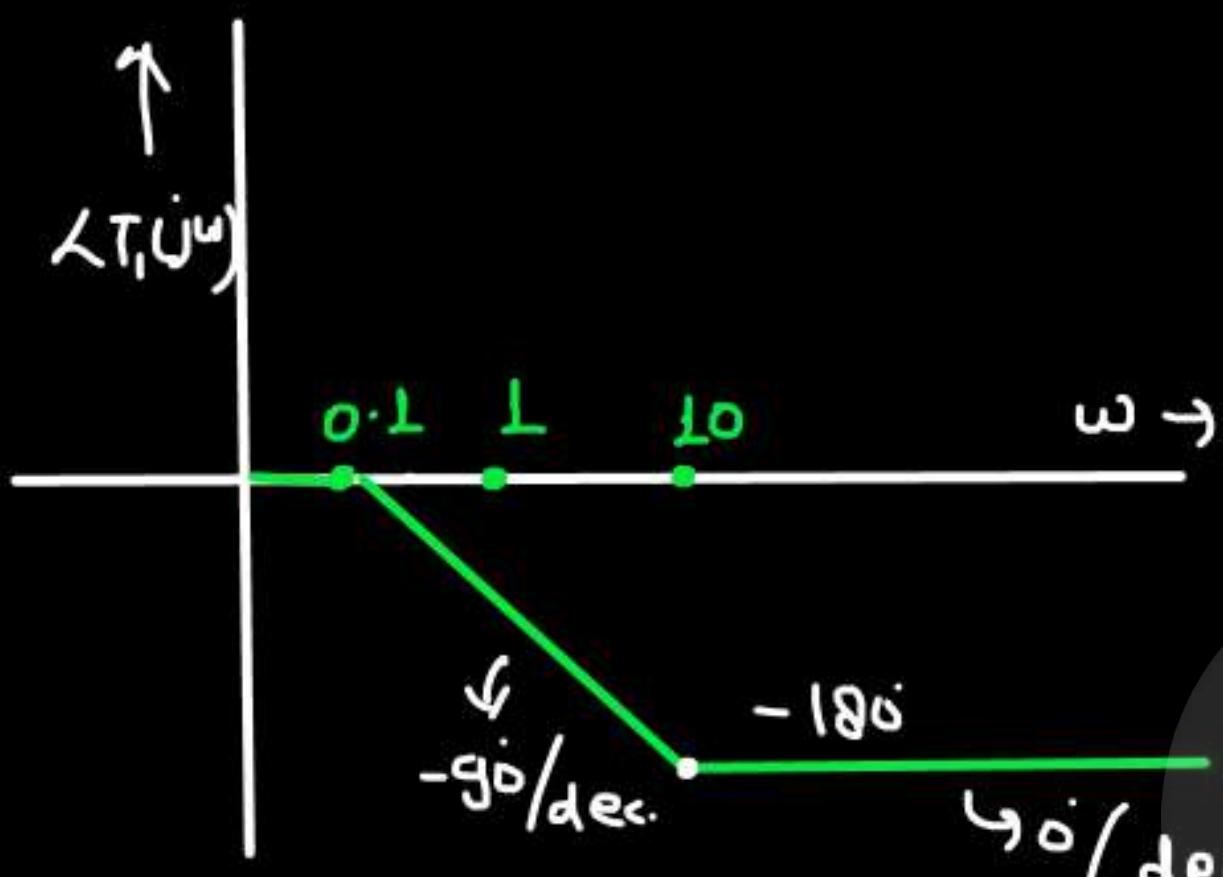
$$\begin{aligned} T(s) &= \frac{A_1}{s+1} \times \frac{A_2}{s+5} \\ &= \angle T_1(j\omega) + \angle T_2(j\omega) \end{aligned}$$




⇒ Two poles @ $\omega = 1$

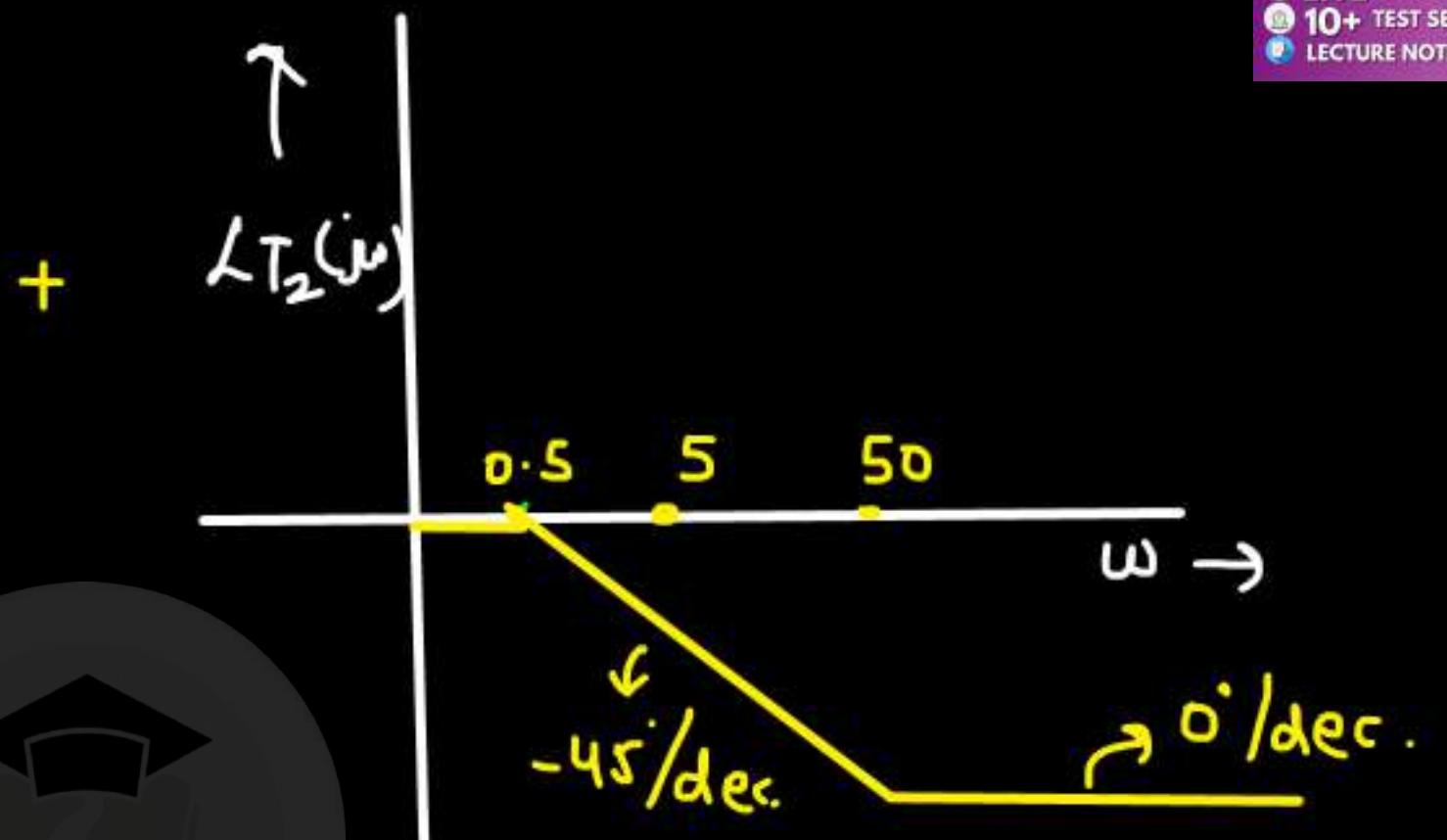


⇒ one pole @ $\omega = 5$

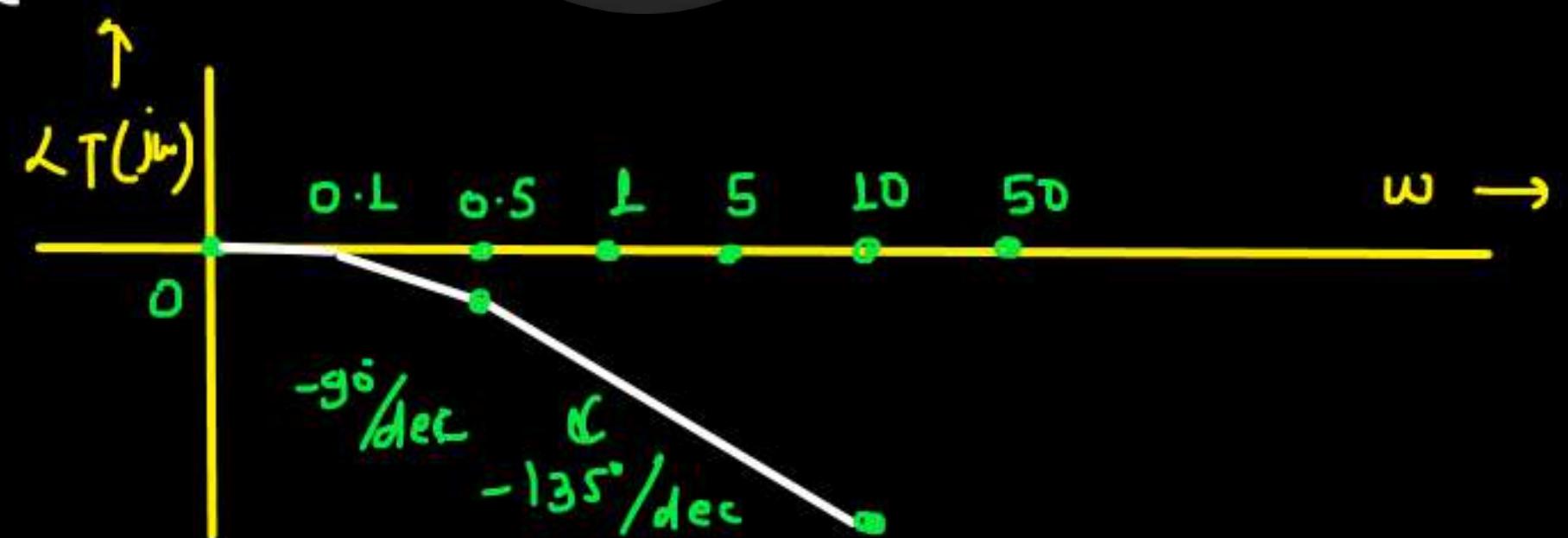

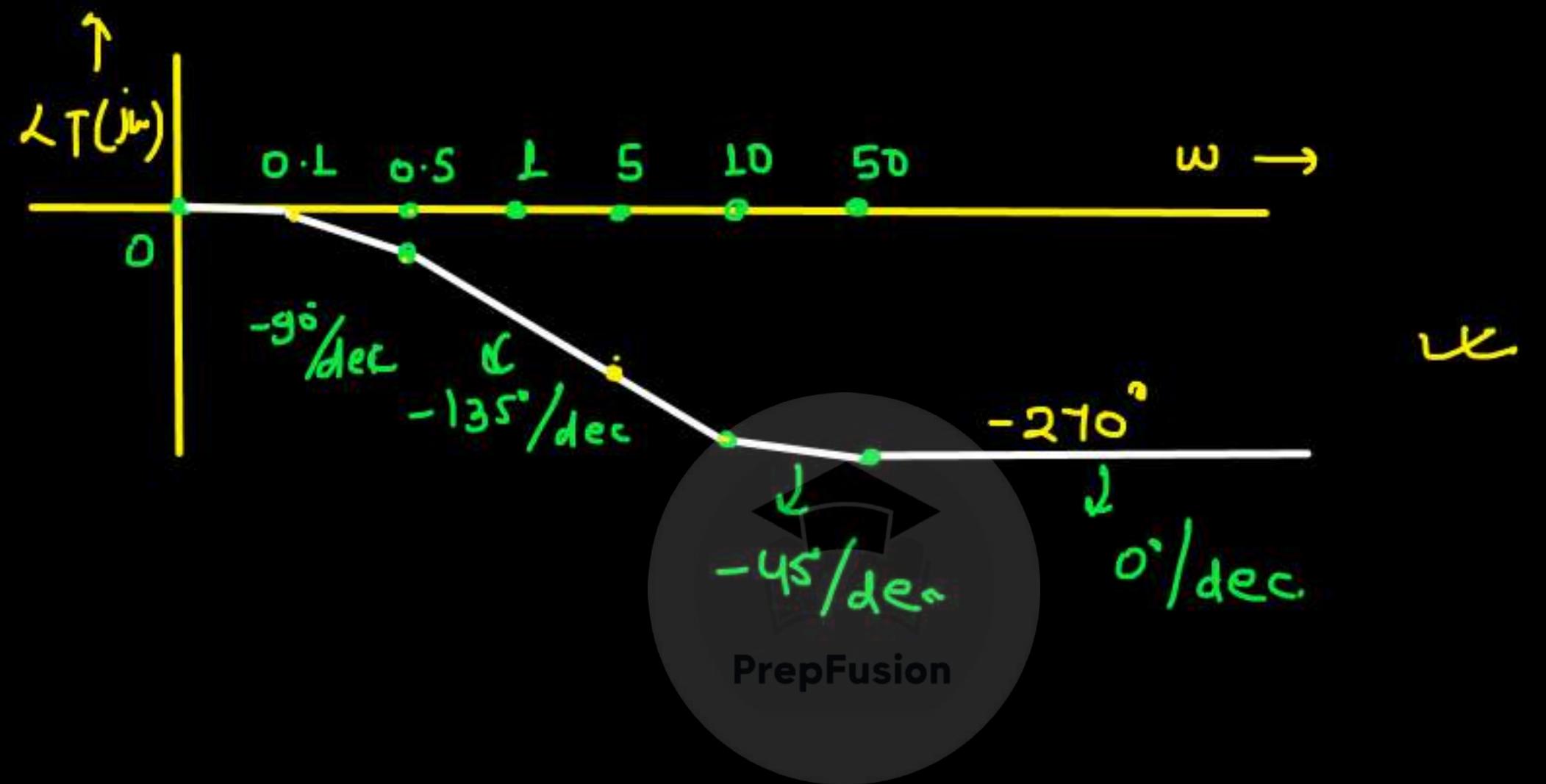

* Analog filters:-

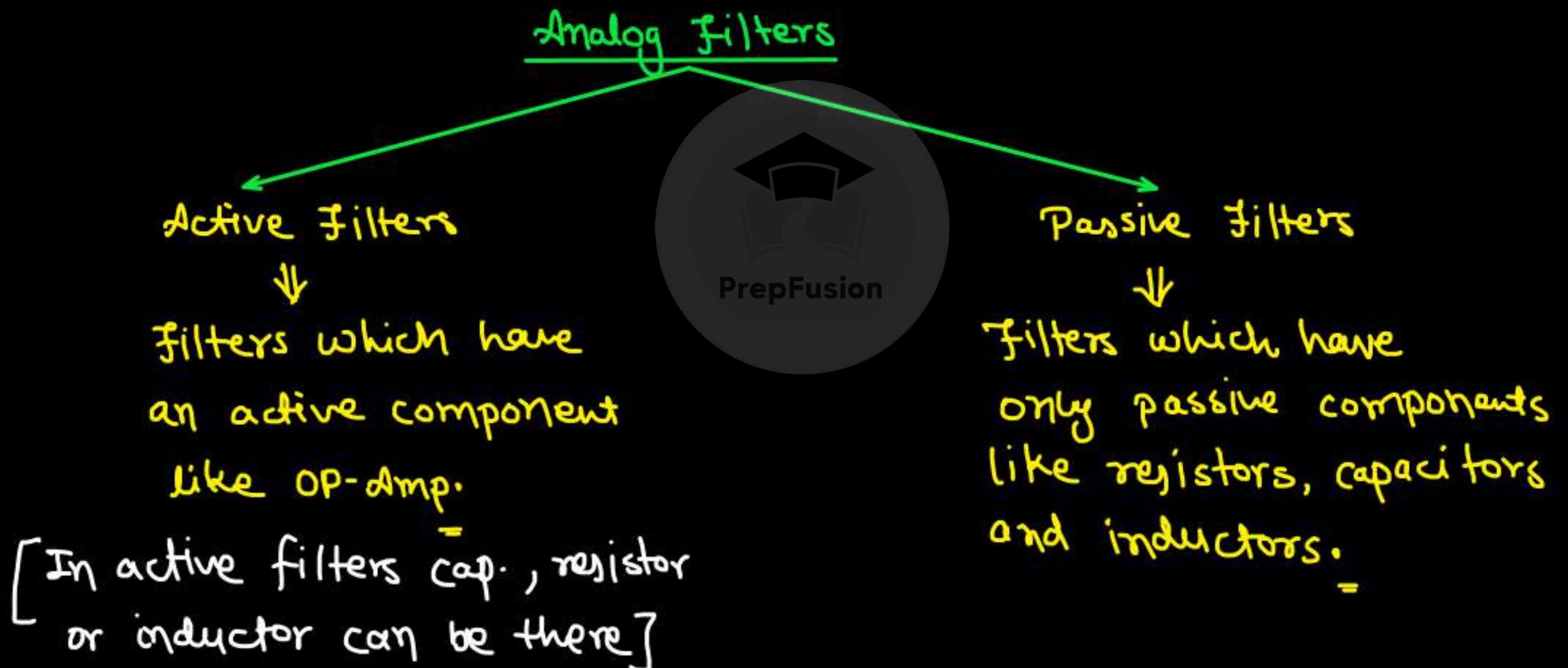The ckt which passes some particular frequency components and rejects all other components.



Analog filters


- low Pass filter (LPF)
- High pass filter (HPF)
- Band pass filter (BPF)
- Band Reject filter / Band stop filter / Notch filter (BSF)
- all pass filter (APF)



To how Pass filter (LPF) :-

Low Frequency component → Passes


High Frequency component → attenuates

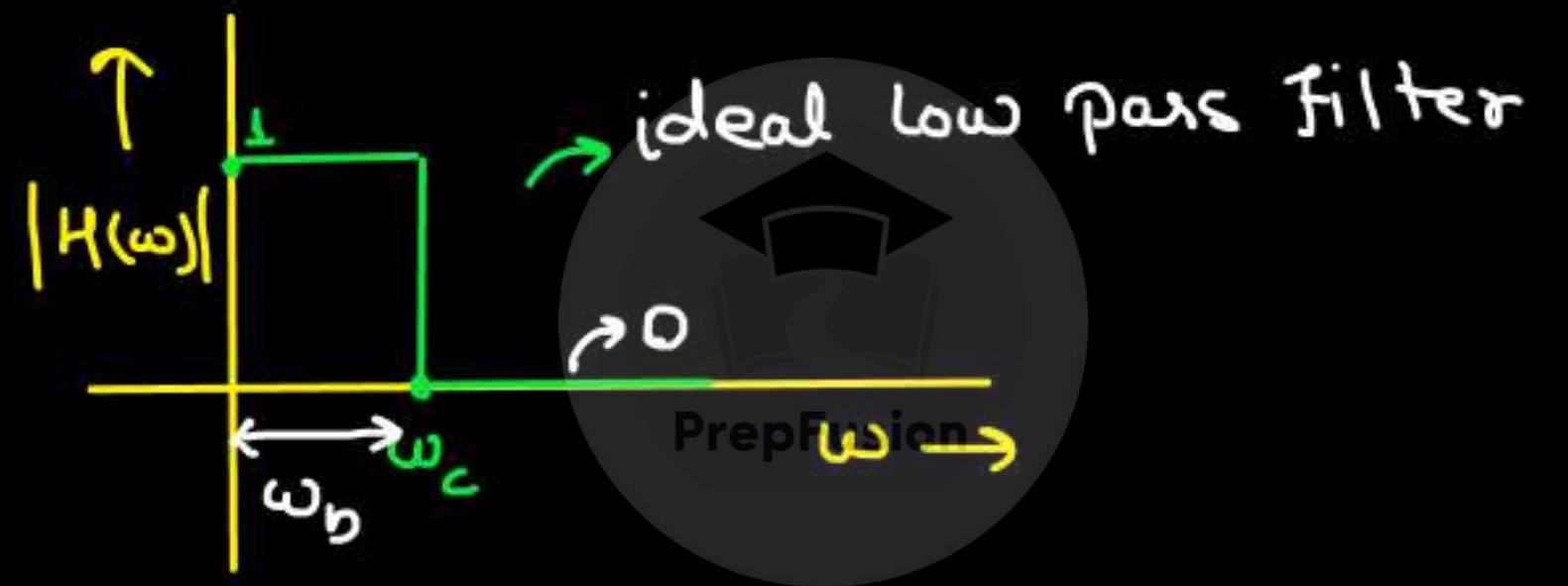




$\omega_c \rightarrow$ cut-off freq.

$$(\omega_b)_{LPF} = \omega_c = \underline{3-\text{dB}} \text{ Bandwidth}$$

Practical LPF :-

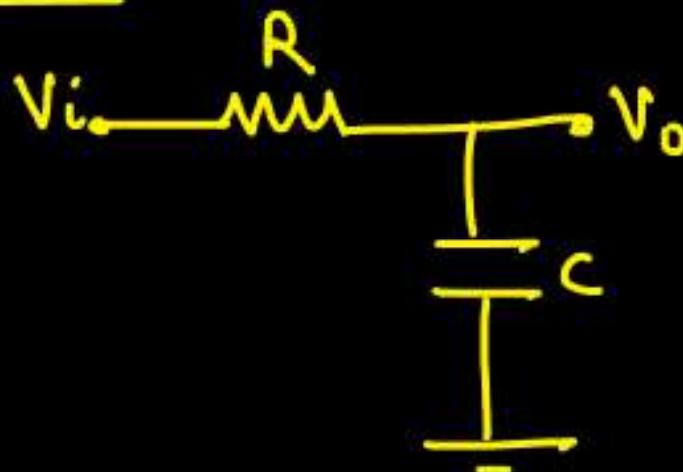
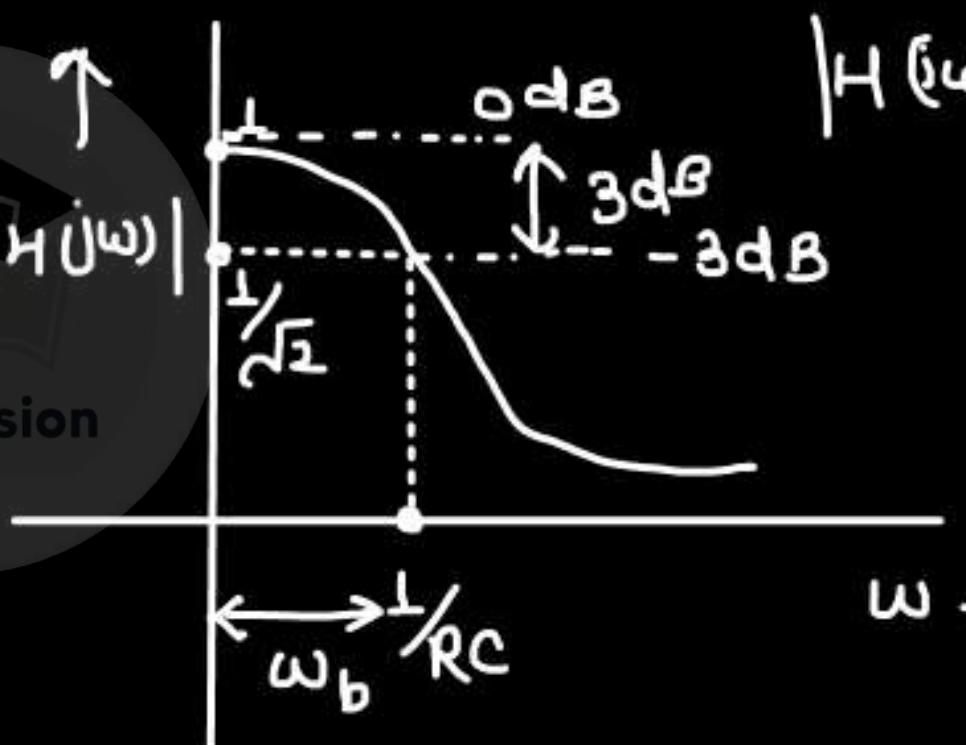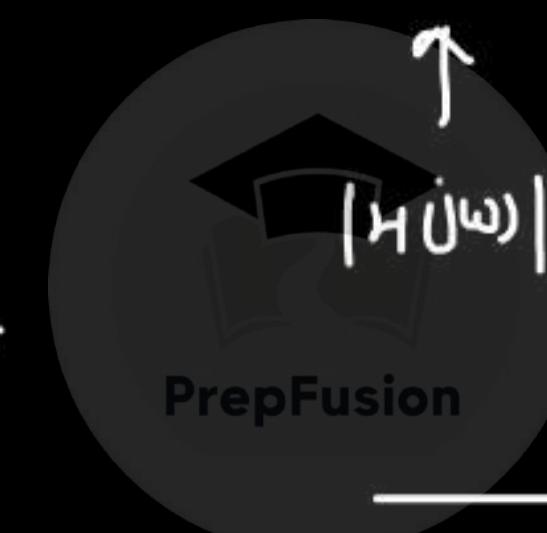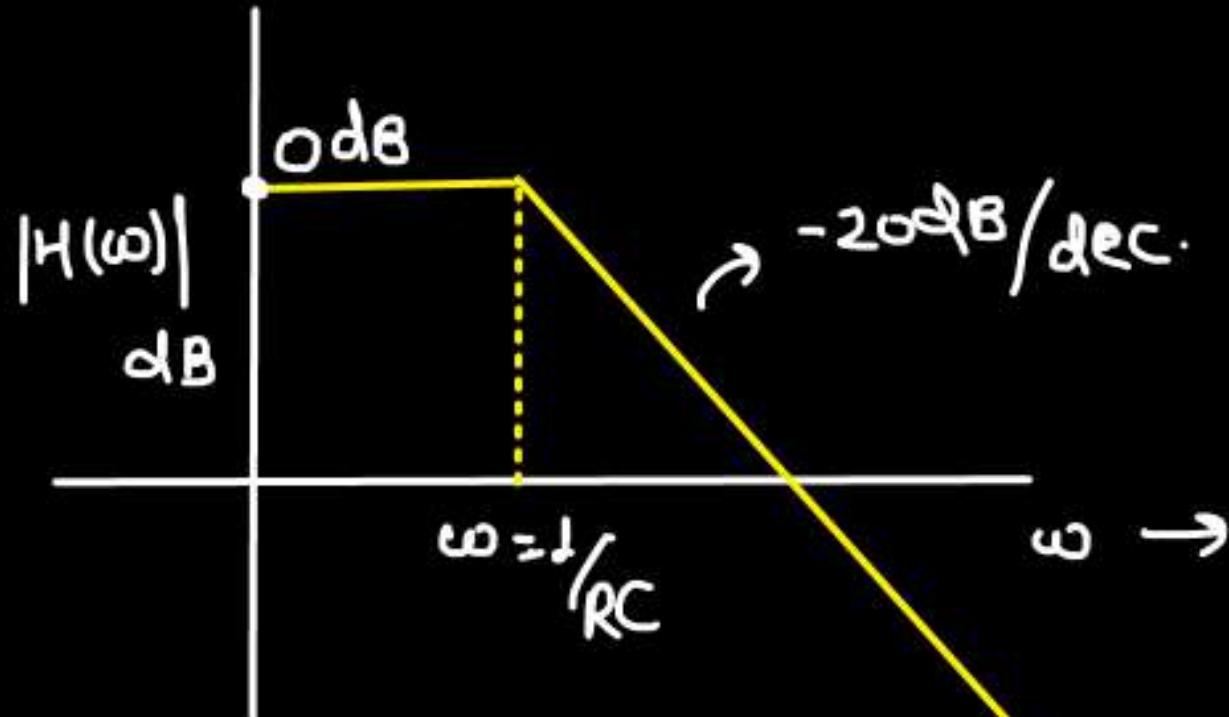
$$\frac{V_o(s)}{V_i(s)} = \frac{1}{sRC + 1}$$




$$|H(j\omega)| = \frac{1}{\sqrt{1+\omega^2 R^2 C^2}}$$

gain @ $\omega = \frac{1}{RC}$

$$= \frac{1}{\sqrt{2}}$$

$$\left. \begin{array}{l} \omega = 0 \Rightarrow \text{gain} = 1 \\ \omega = 0.0001 \Rightarrow \text{gain} < 1 \\ \omega > \frac{1}{RC} \Rightarrow \text{gain} \neq 0 \end{array} \right\} \rightarrow \text{Practical LPF}$$

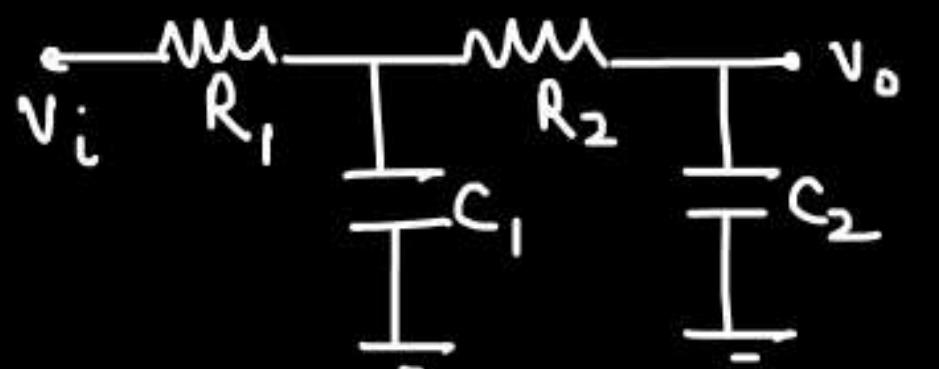How to check the type of filter in complex circuits?



@ $\omega=0 \Rightarrow V_o=V_i \Rightarrow$ some o/p is observed \Rightarrow low freq. passed


@ $\omega=\infty \Rightarrow V_o=0 \Rightarrow$ no o/p \Rightarrow High freq. doesn't pass



② High Pass Filter (HPF) :-

High freq. component \rightarrow passes
low freq. component \rightarrow attenuates


ideal HPF:-

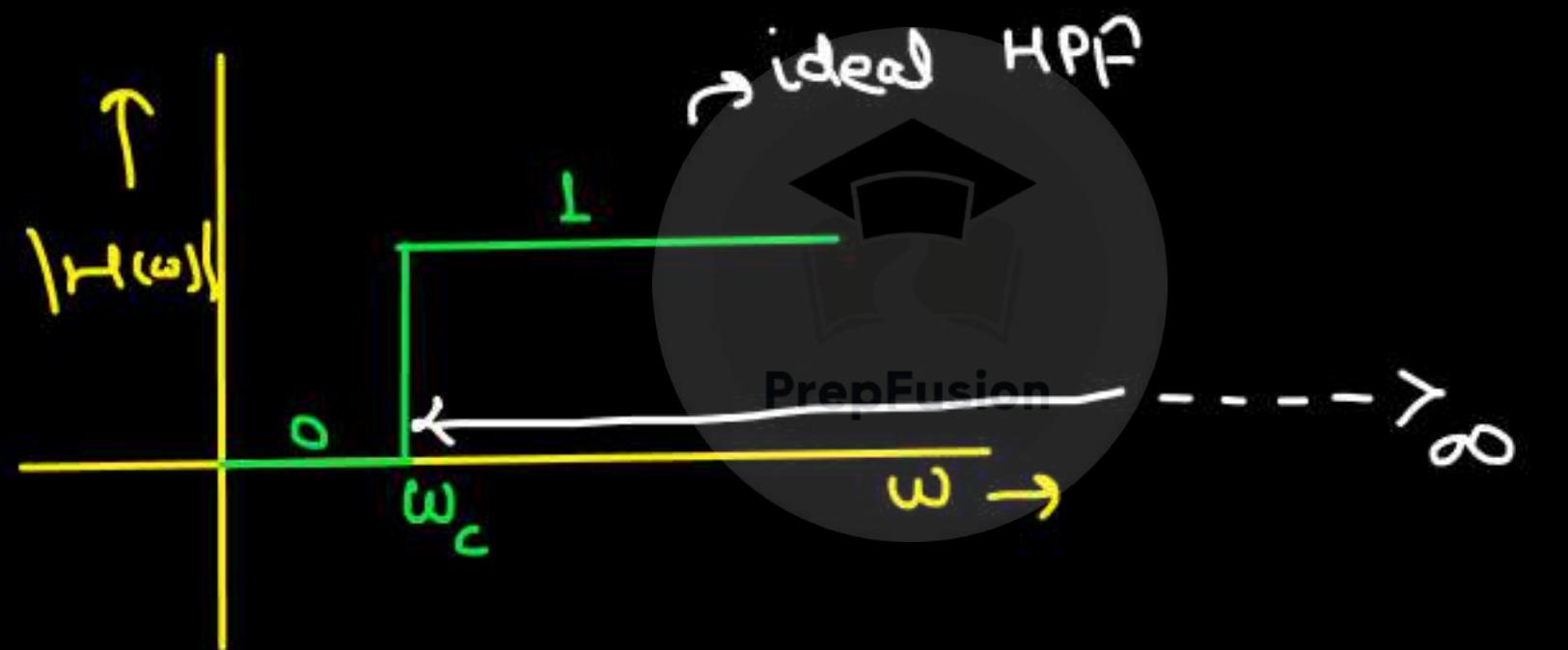

$\omega_c \rightarrow$ cut-off High pass filter




3-dB Bandwidth $\rightarrow \infty$

* Practical HPF :-

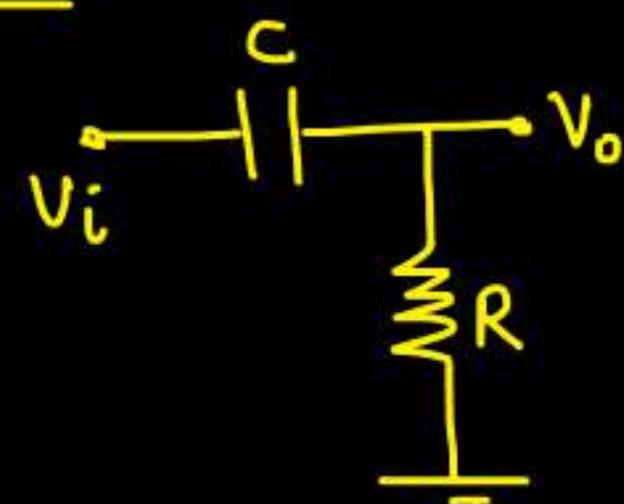


$$\frac{V_o(s)}{V_i(s)} = \frac{RC}{RC + L}$$

$$|H(j\omega)| = \frac{\omega RC}{\sqrt{\omega^2 R^2 C^2 + L}}$$

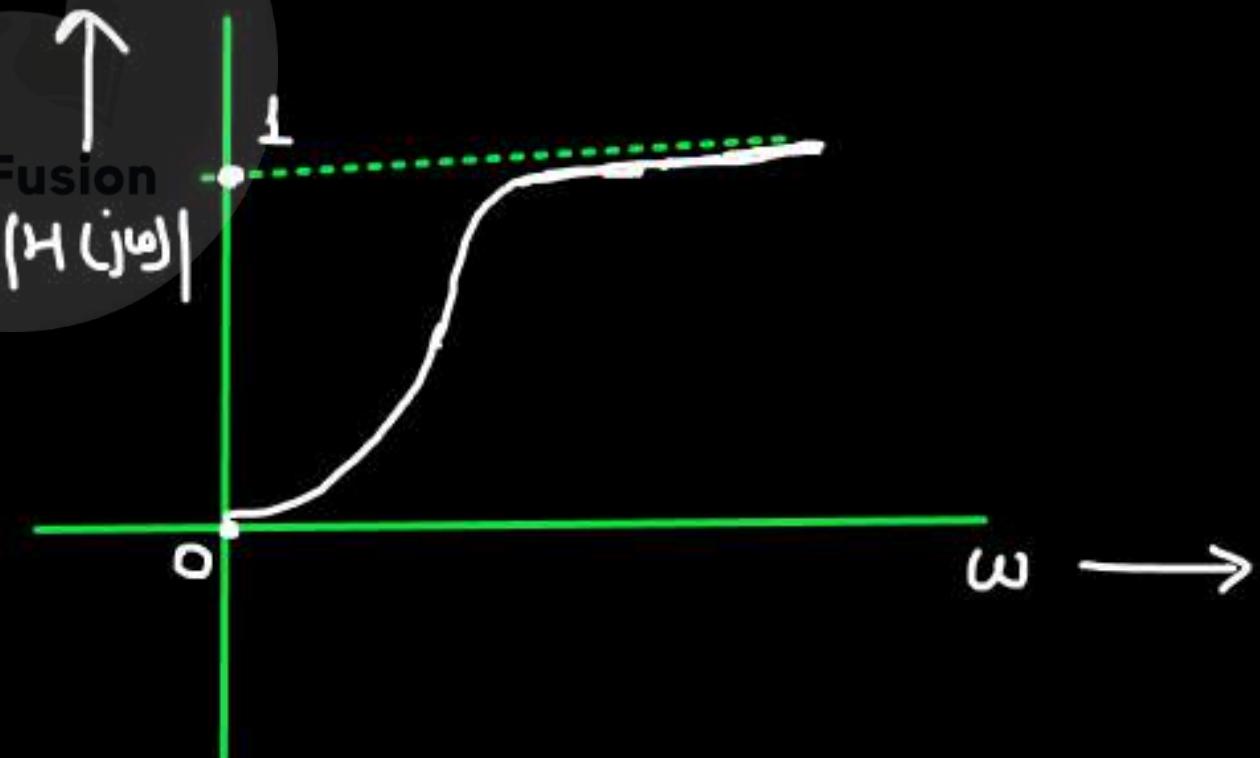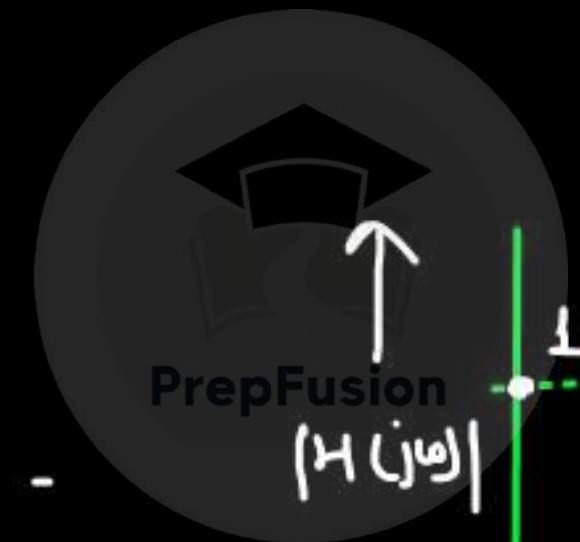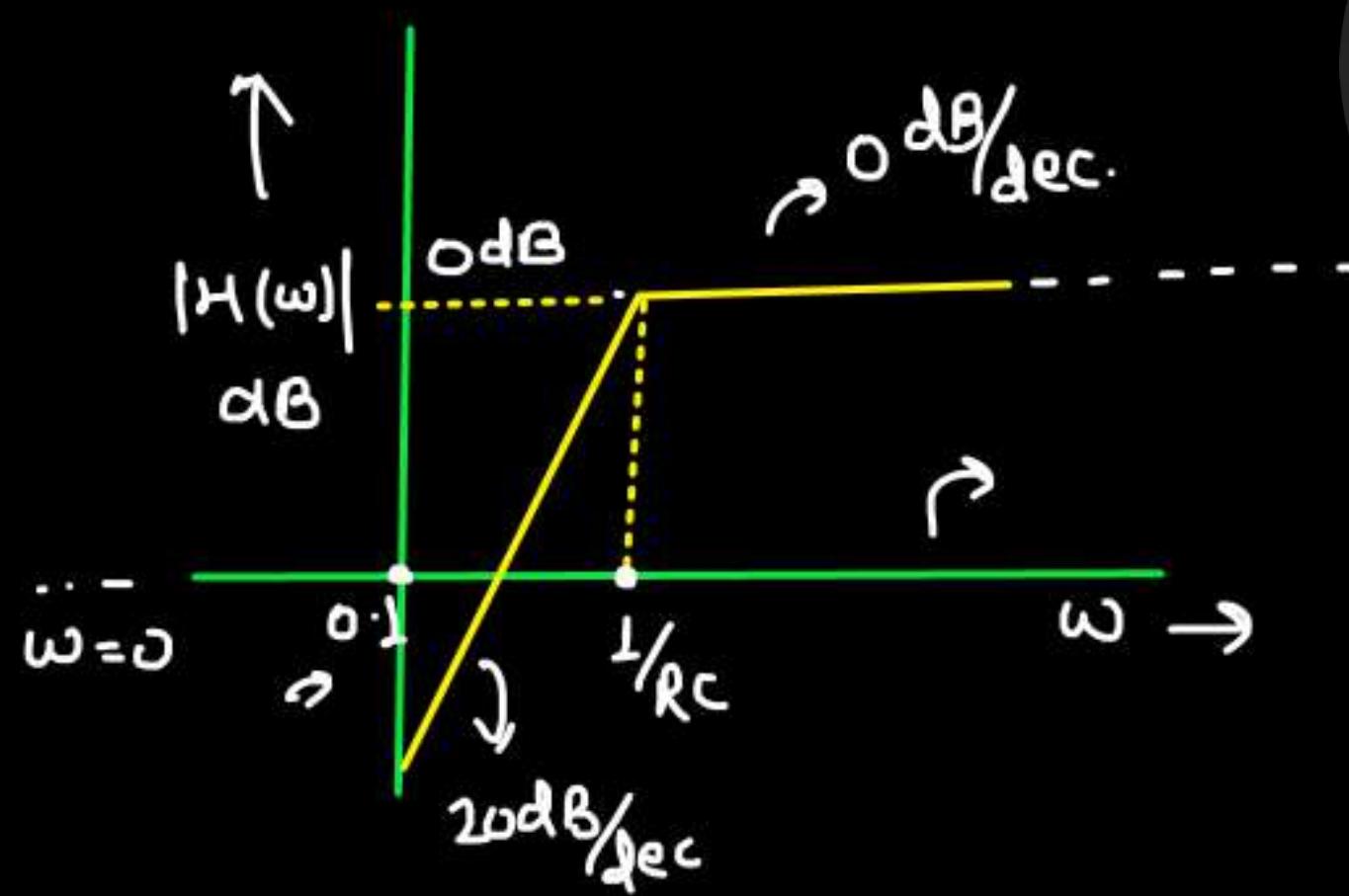

③ Band Pass filter :-

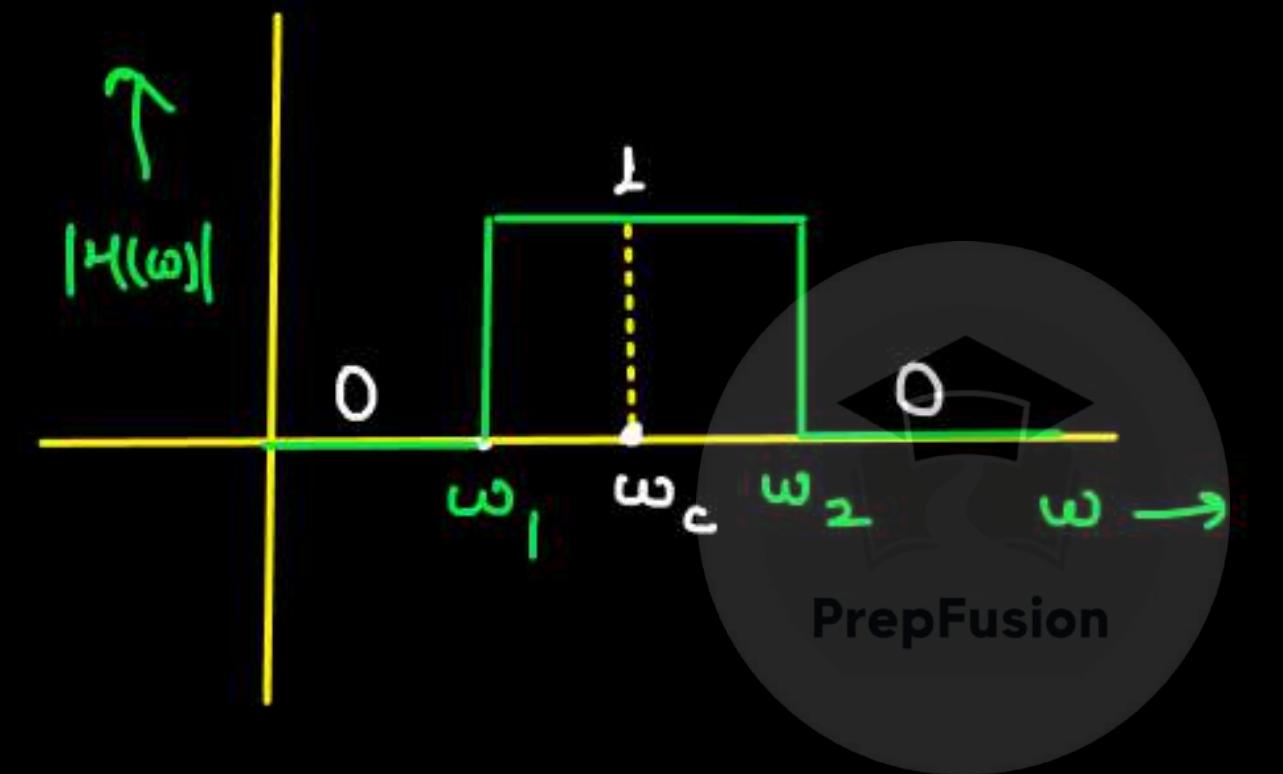Passes a particular range of frequencies.







$$3-\text{dB Bandwidth} = \omega_2 - \omega_1$$

$$\omega_c = \text{centre freq.} = \sqrt{\omega_1 \omega_2}$$


How to make a band pass filter :-

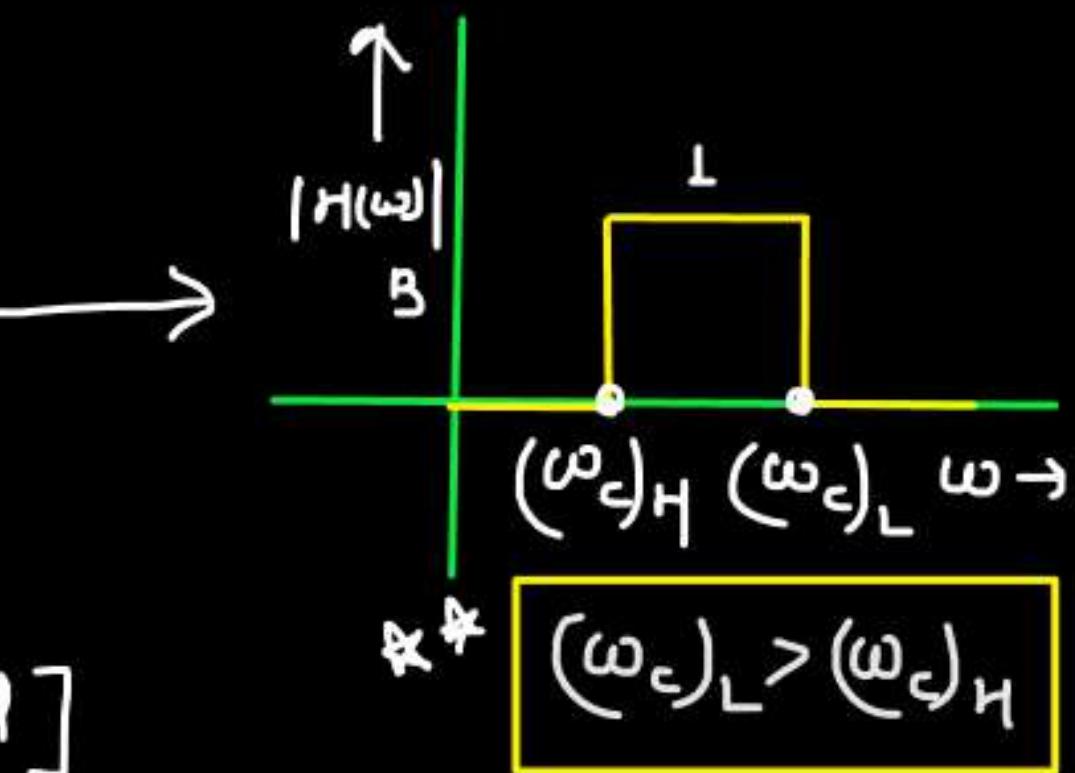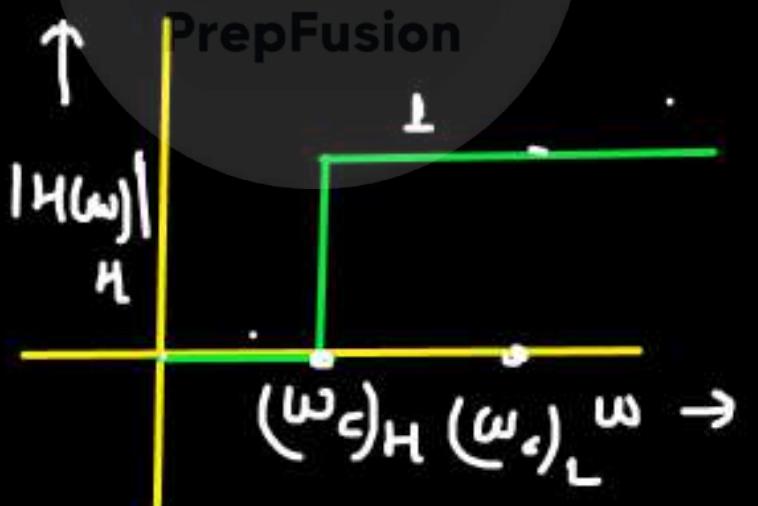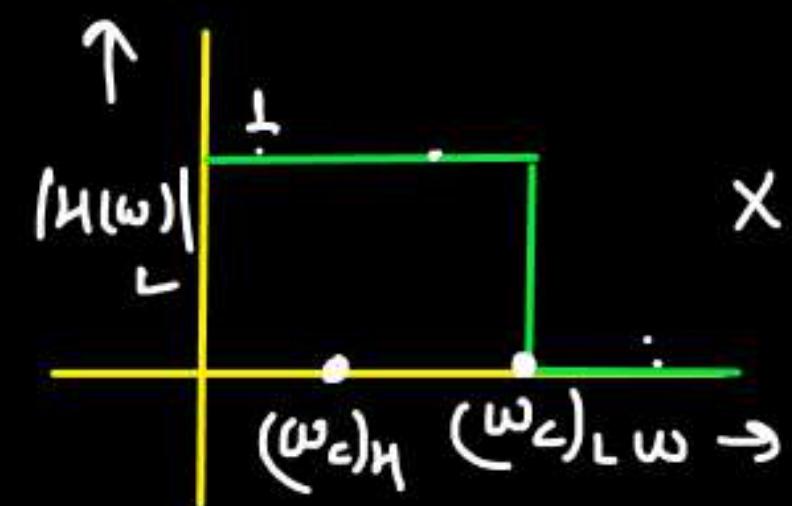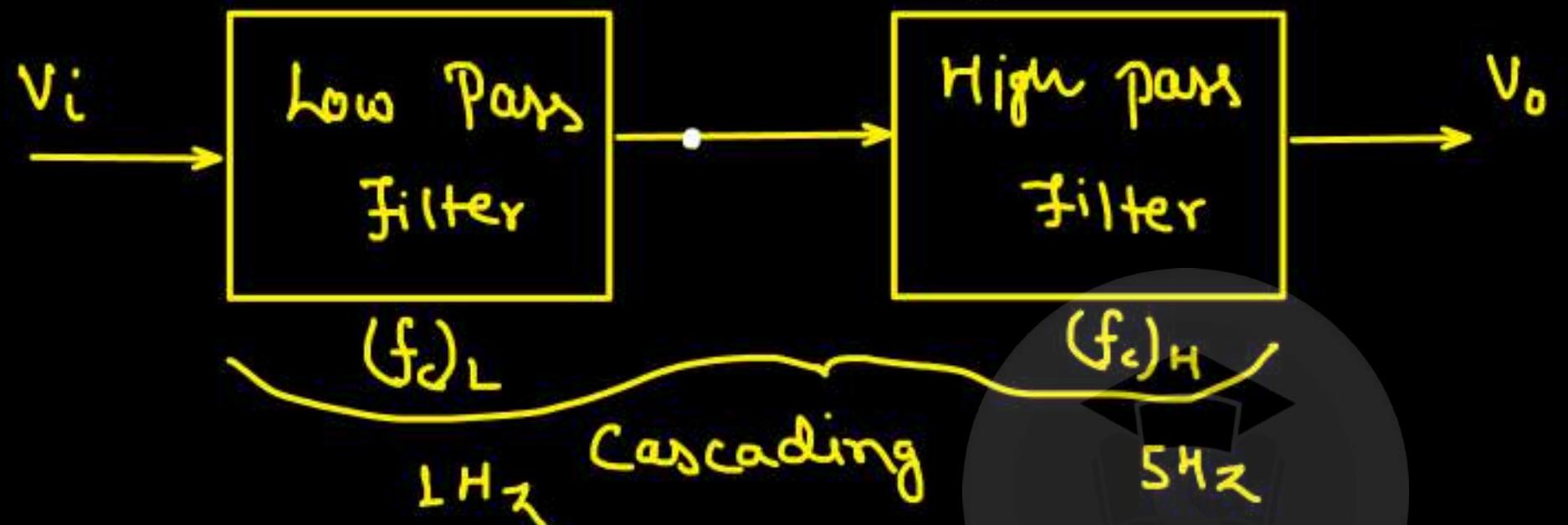Cascading:- O/P of first in connected to the i/p of 2nd stage.





[N.B. → in cascade, freq. response are multiplied]

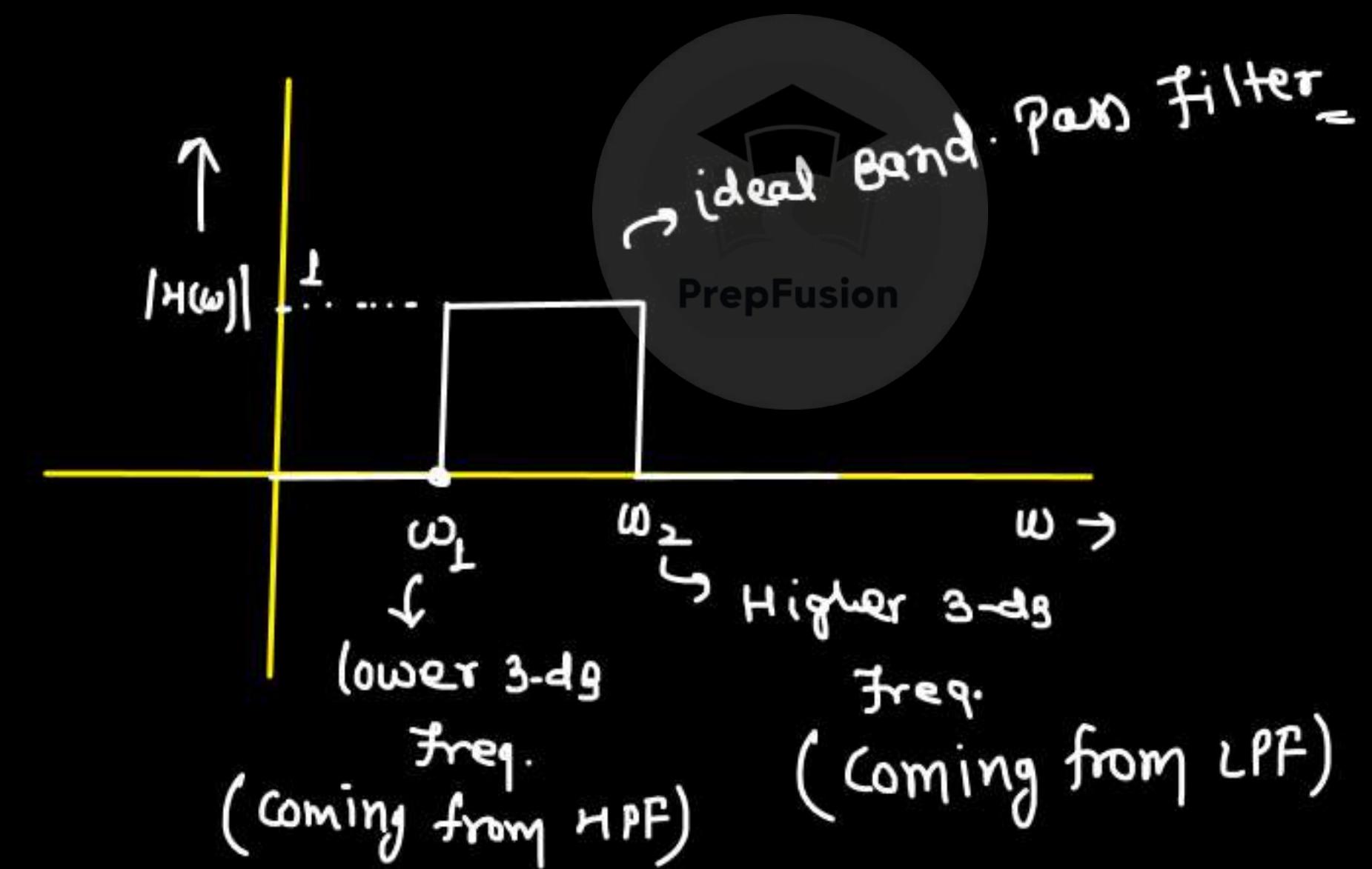⇒ To make a BPF from LPF and HPF, you should connect both LPF and HPF in cascaded with the condition that the cut-off freq. of low pass filter is higher than the cut-off freq. of High pass filter.






Practical BPF :-

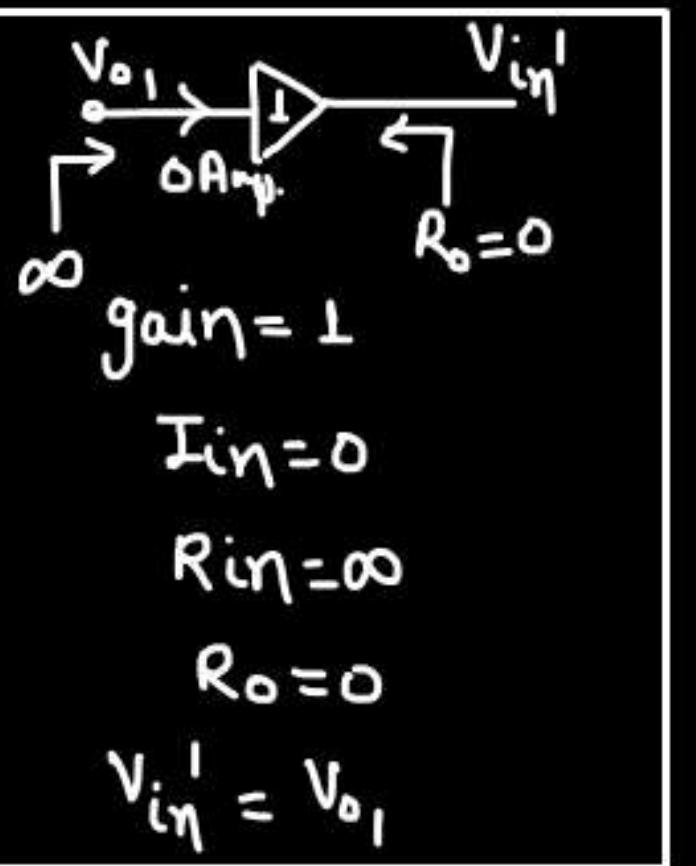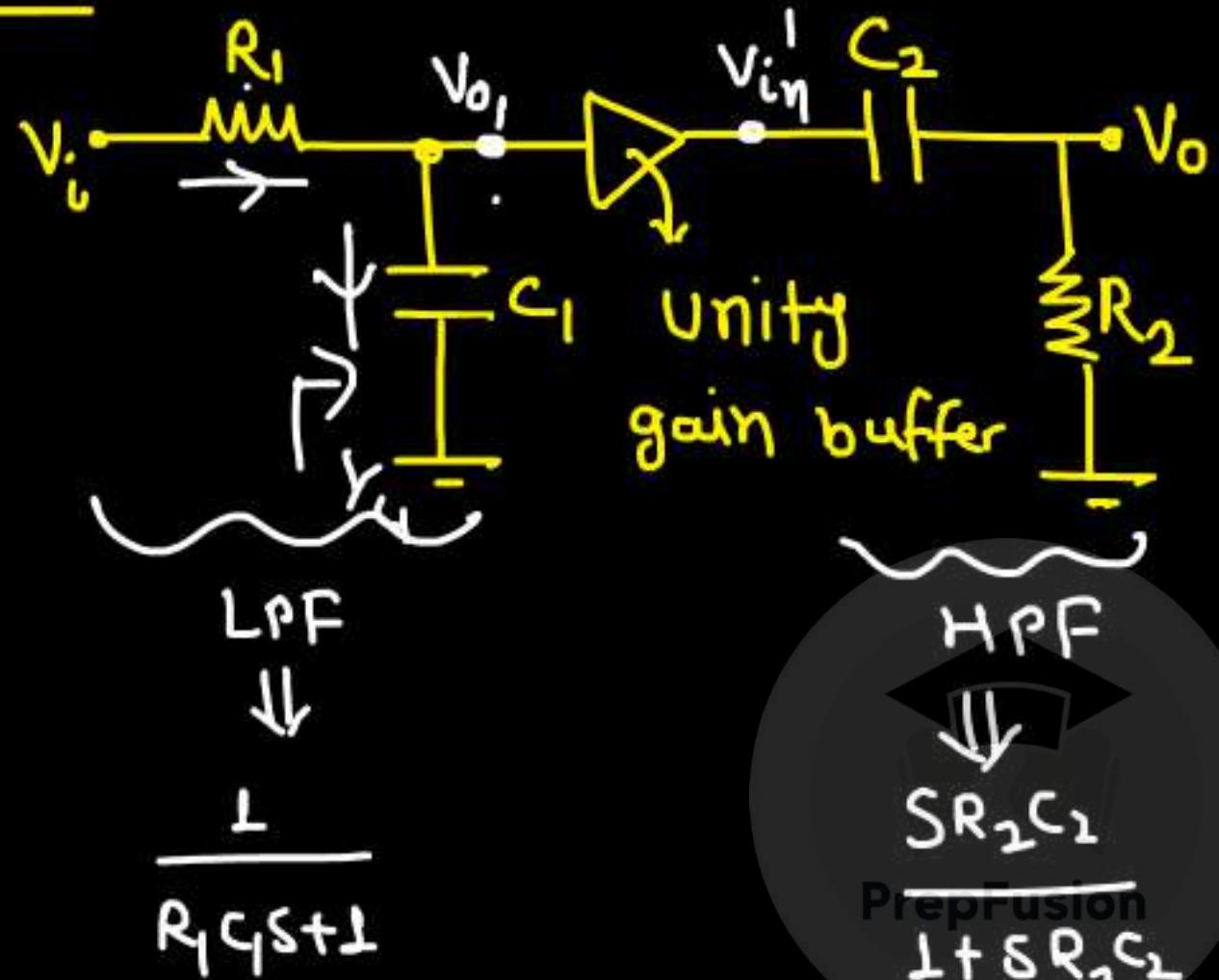

$$\frac{V_o(s)}{V_i(s)} = \frac{SR_2C_2}{(R_1C_1 + L)(L + SR_2C_2)} \Rightarrow (\omega_c)_L > (\omega_c)_H$$

$$\frac{1}{R_1C_1} > \frac{1}{R_2C_2}$$

$R_2C_2 > R_1C_1$

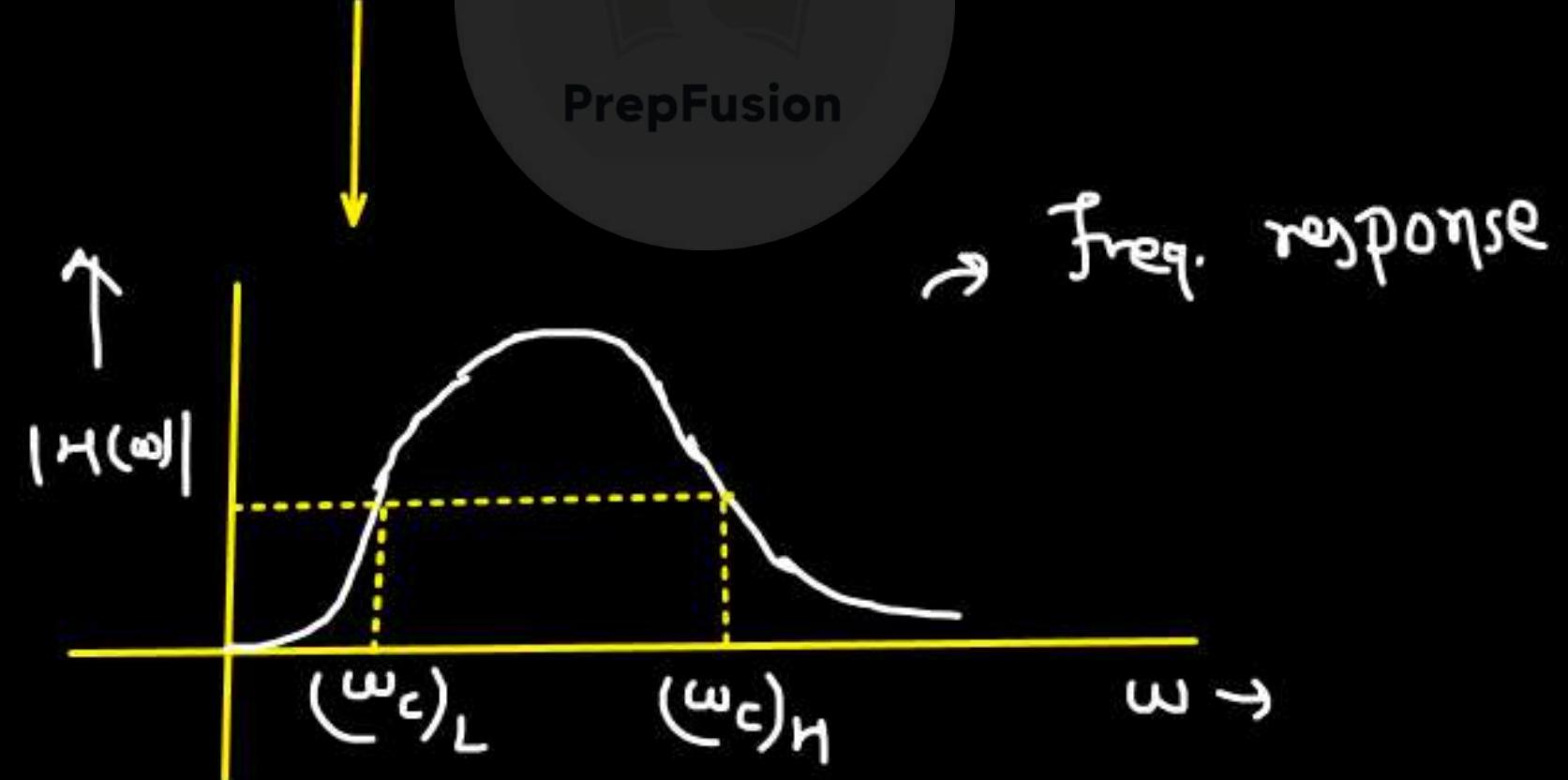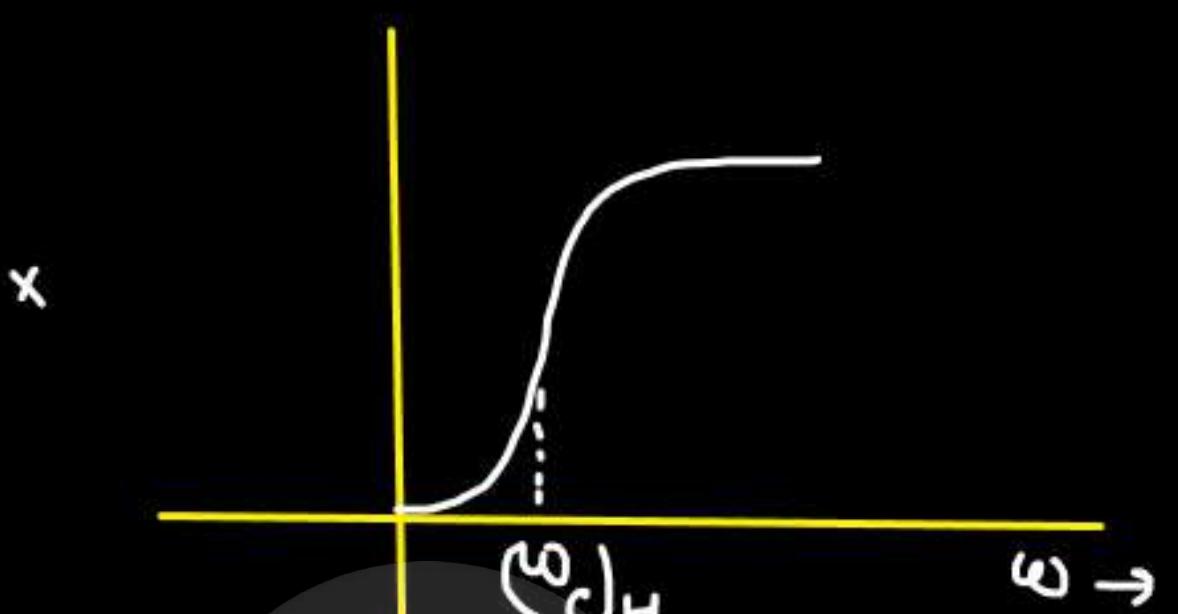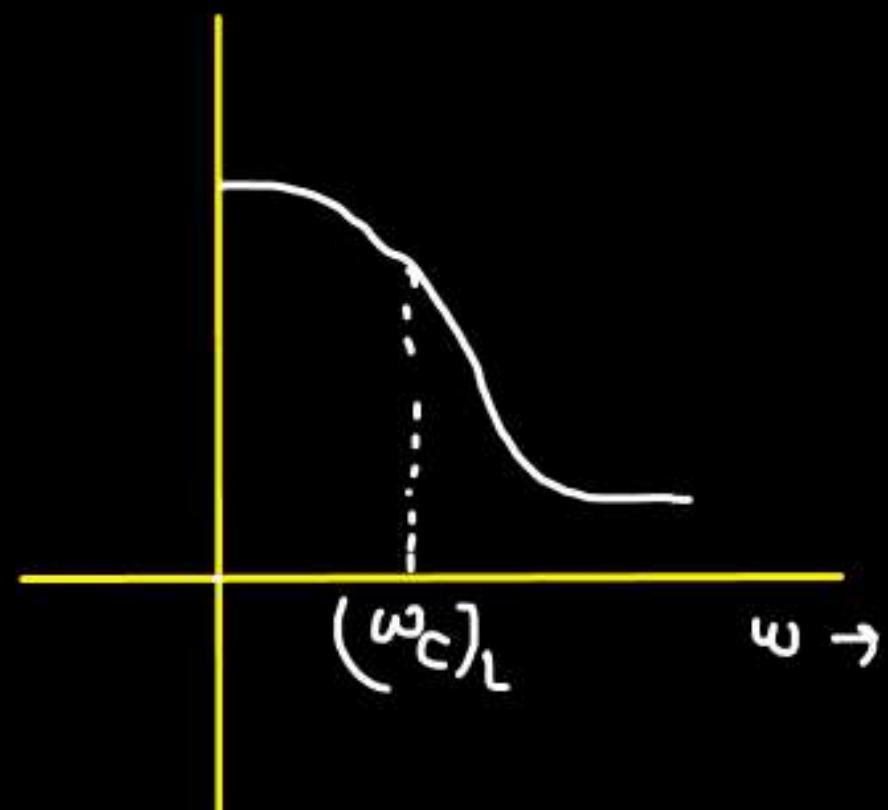


$$H(s) = \frac{SR_2C_2}{(SR_1C_1 + L)(SR_2C_2 + L)}$$

Zero $\rightarrow \omega_Z = 0$


Poles $\rightarrow \omega_p = \frac{1}{R_1C_1}, \frac{1}{R_2C_2}$

$$\frac{1}{R_2C_2} < \frac{1}{R_1C_1}$$

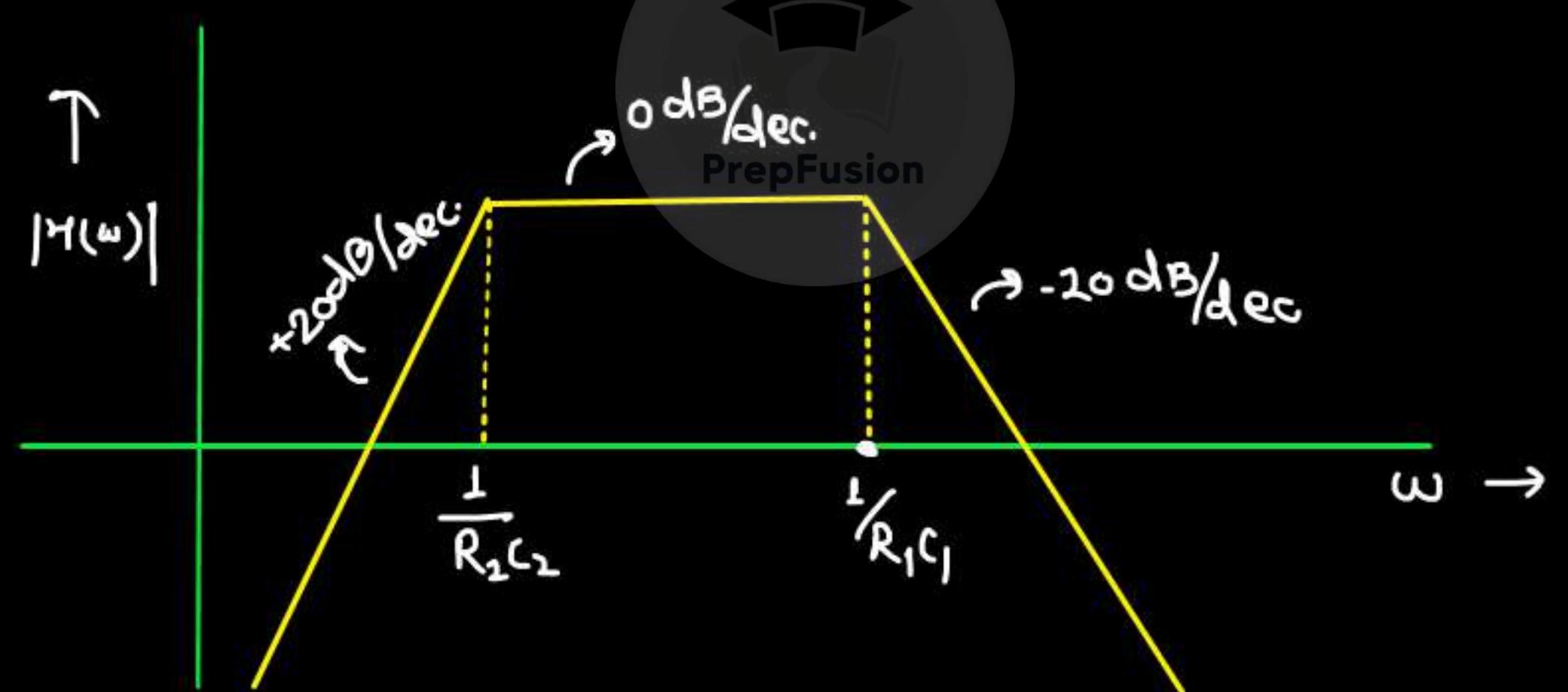

④ Band reject filter | Band stop filter | Notch filter:-


Rejects a particular range of freq.

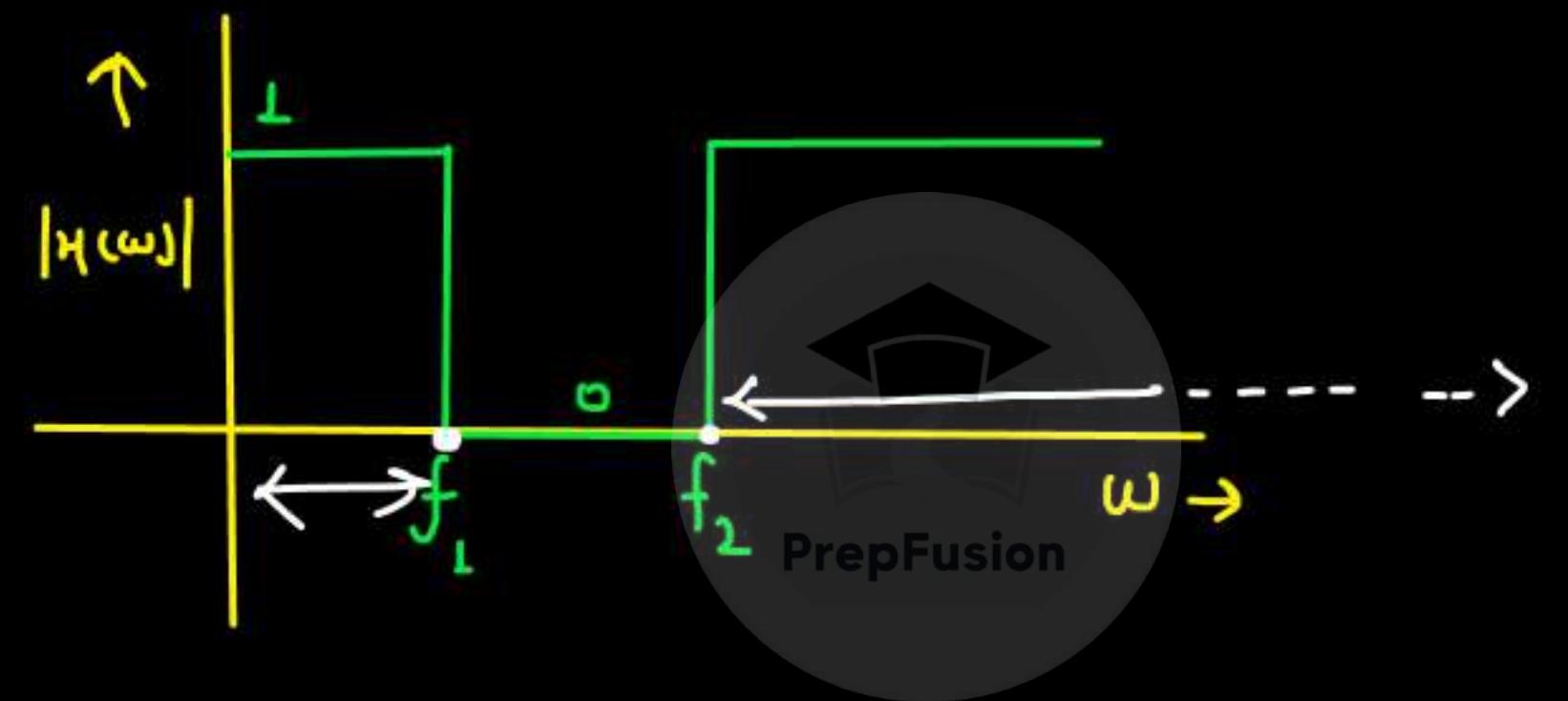


Bandwidth of BSF = ∞

How to make band reject filter:-

Cascade?

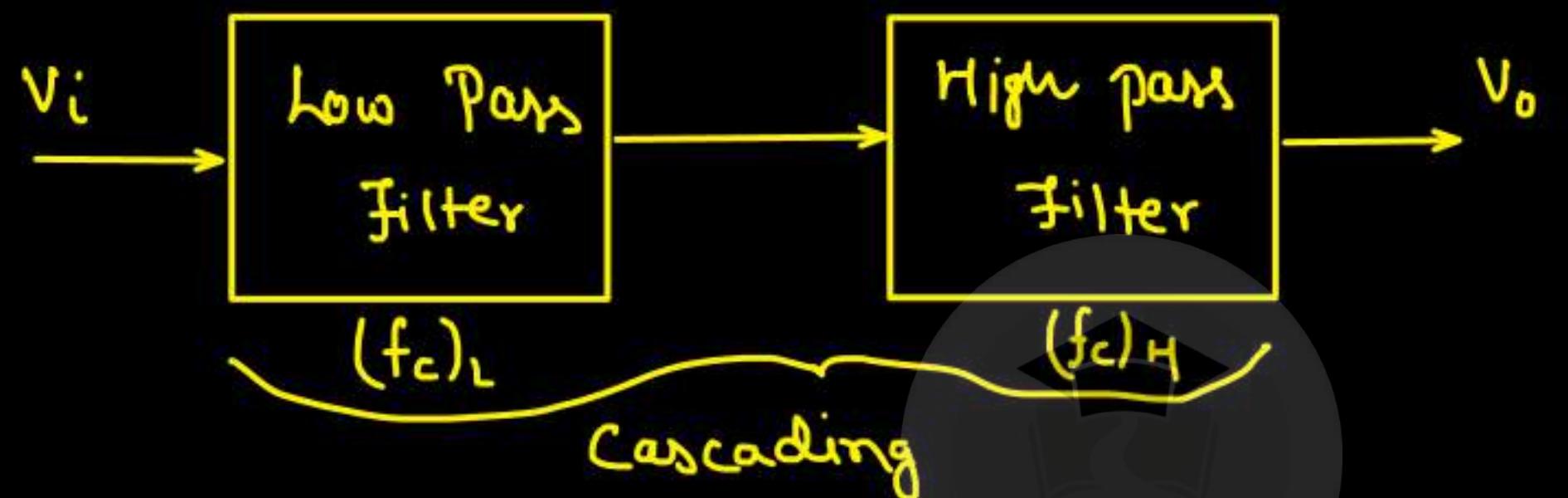


consider $(\omega_c)_L < (\omega_c)_H$

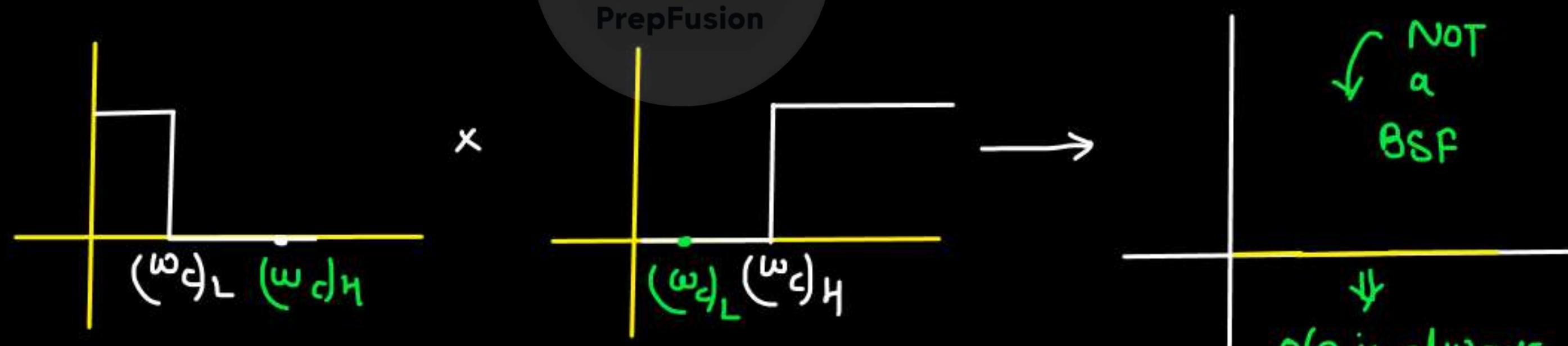


⇒ cascading doesn't give you Band Reject filter.

NOT
a
BSF
 \Downarrow
o/p is always
zero.


Connect in parallel :-

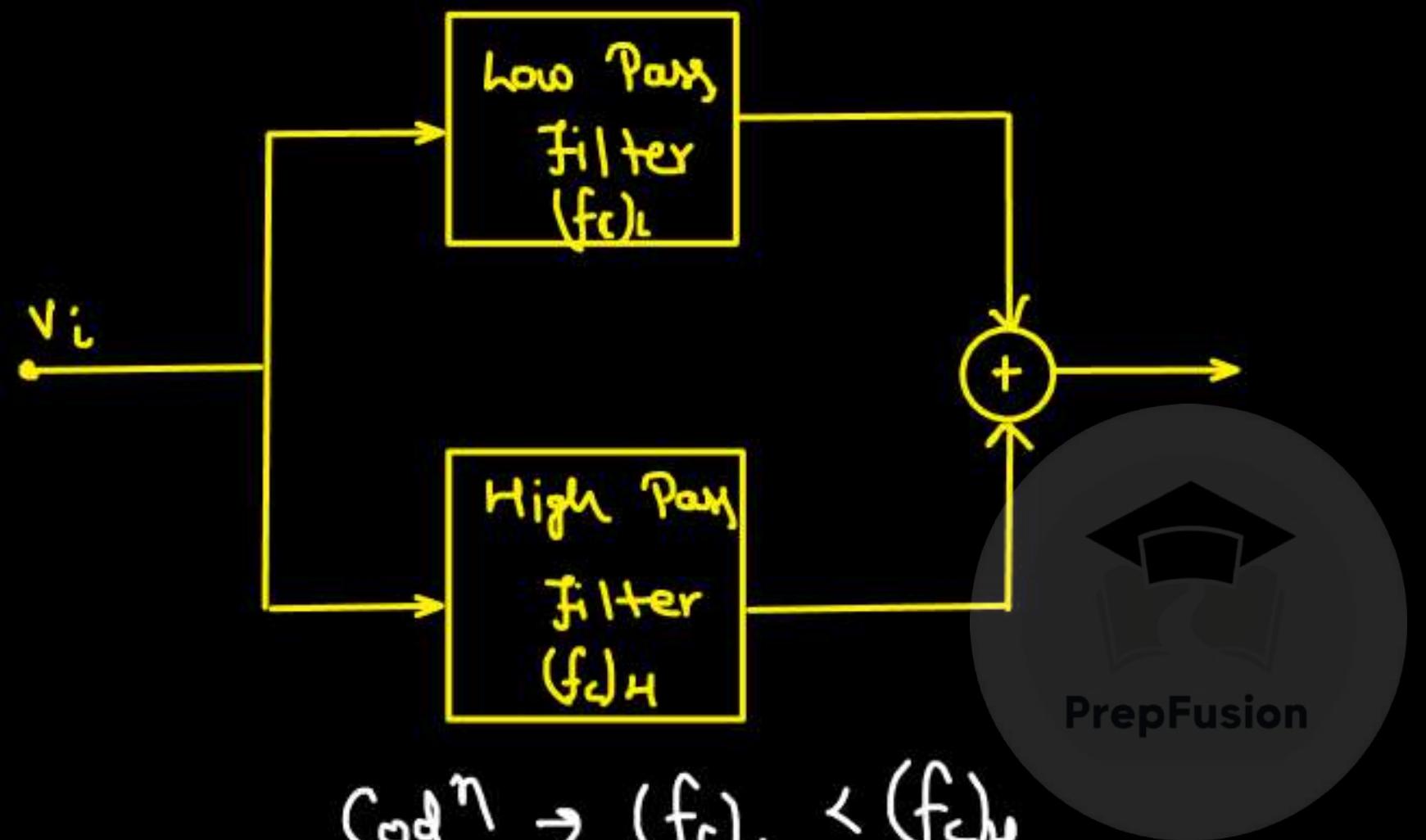
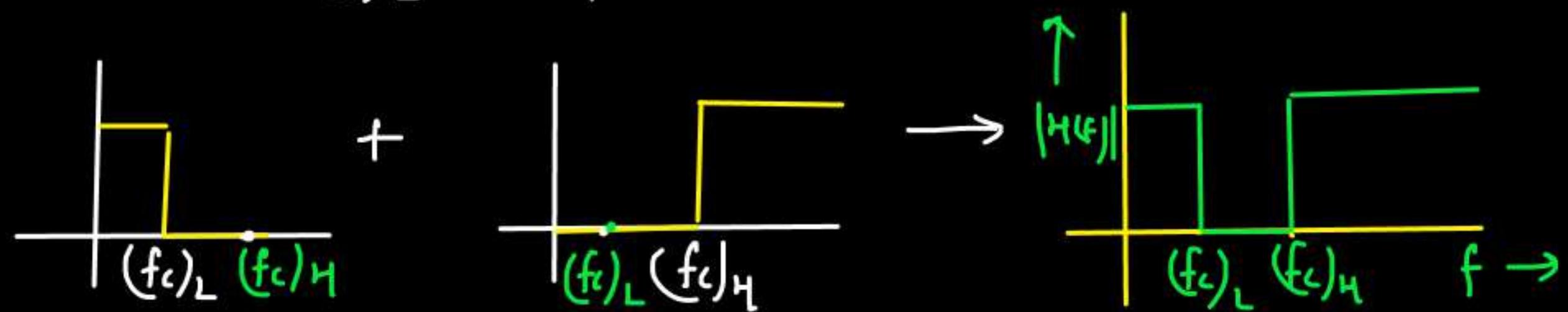
$$\text{Code} \rightarrow (f_c)_L \leftarrow (f_c)_H$$



Practical Band reject filter:-

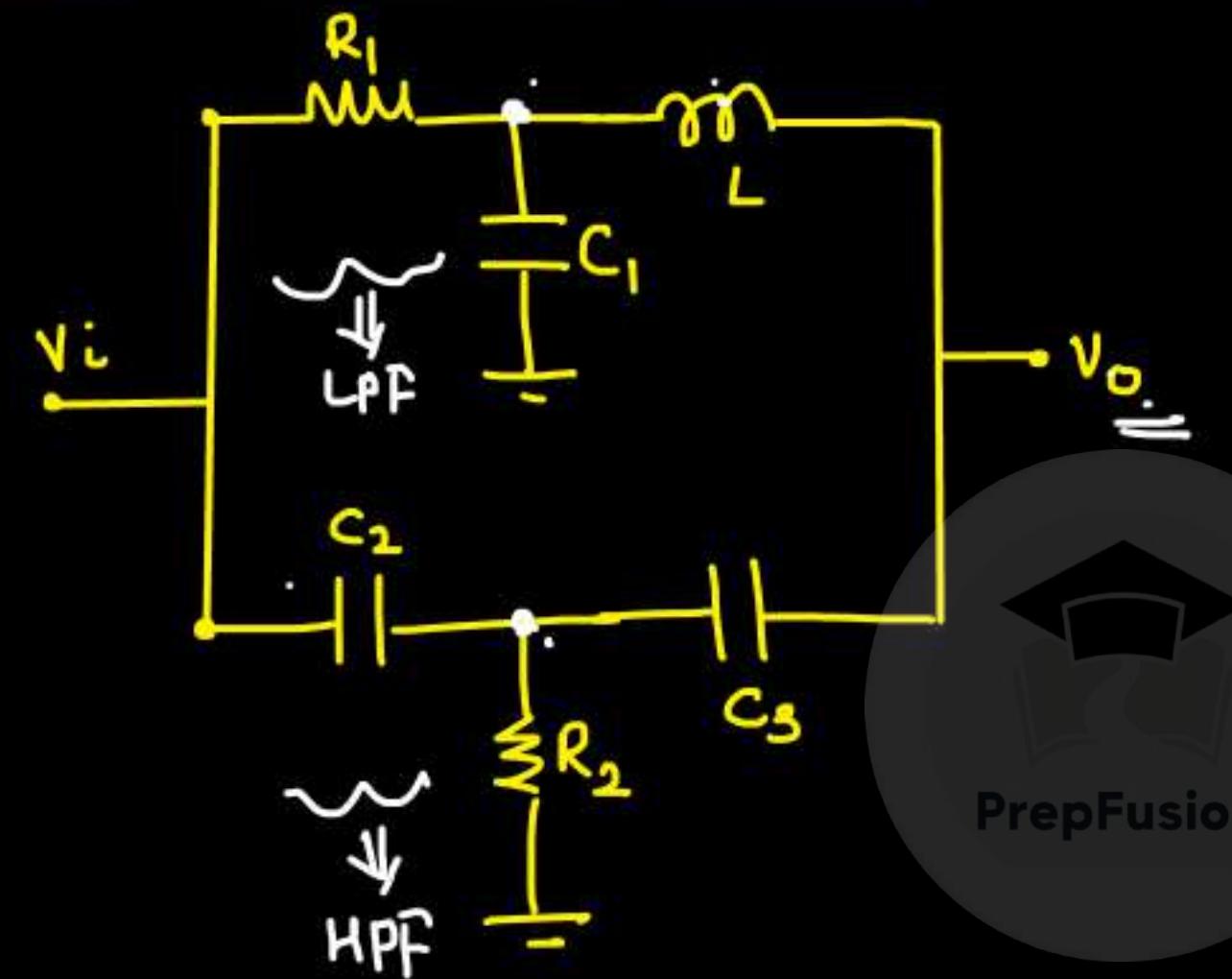


$$\omega = 0 \Rightarrow V_0 = V_L$$

$$\omega = \infty \Rightarrow V_0 = V_i$$

=


⑤ All Pass filter:-

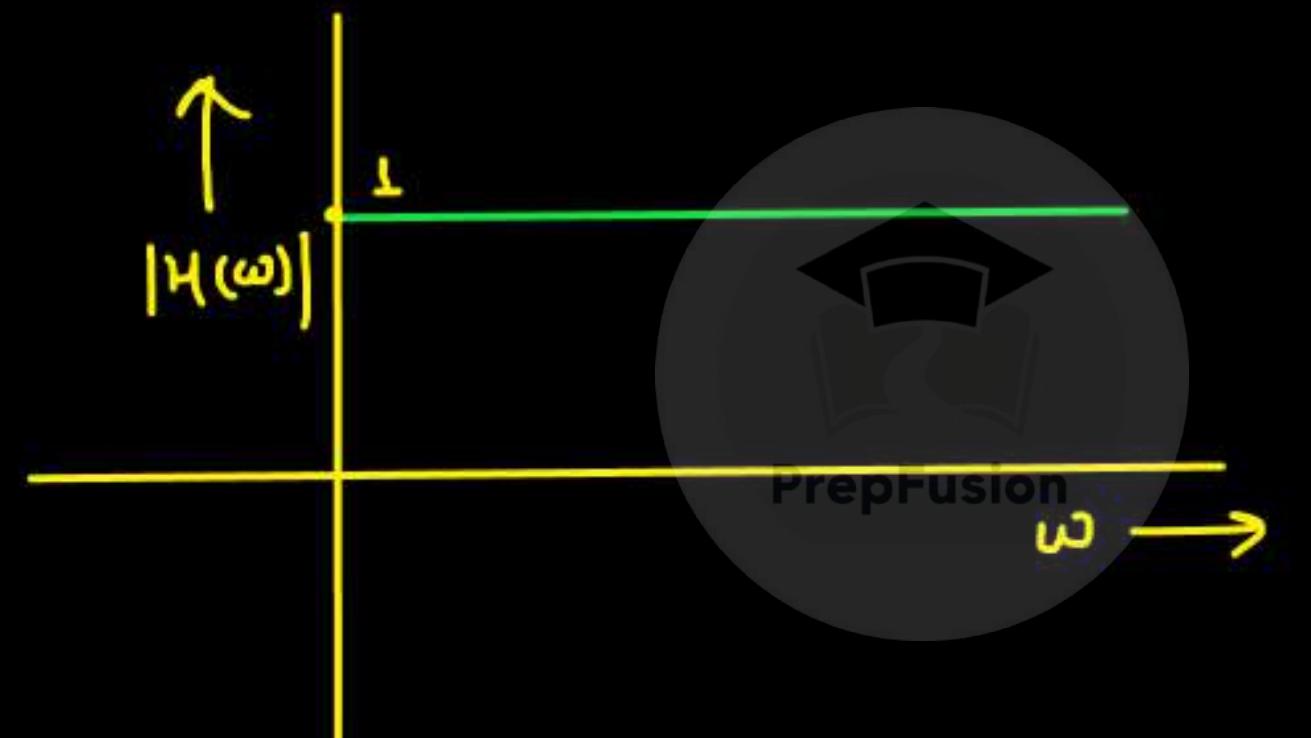Passes all the freq. Component but
ideal APF:- Provides some phase shift




N.B. -

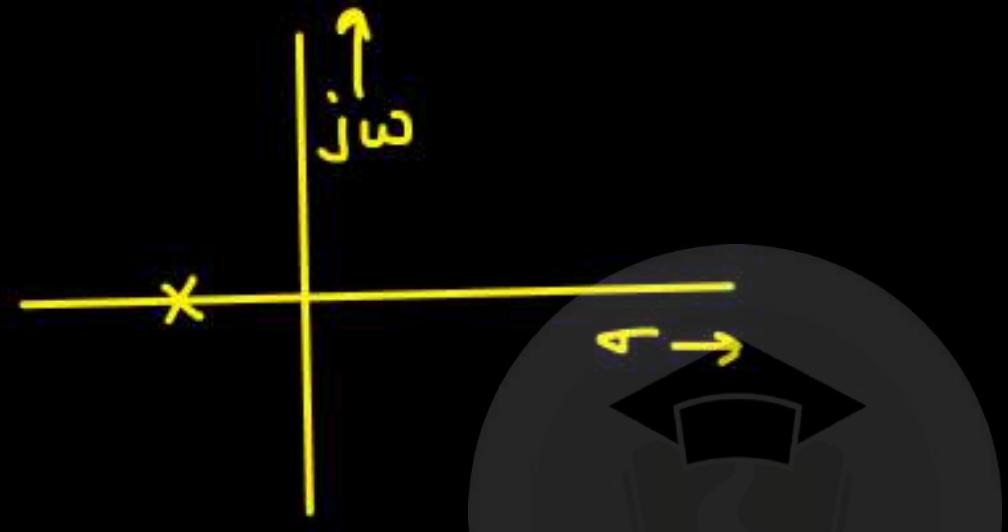- ⇒ (i) For a stable S/S the poles should always be on the left half of s-plane.



- (ii) For APF, poles and zero are symmetric about jω axis.

Practical QPF :-

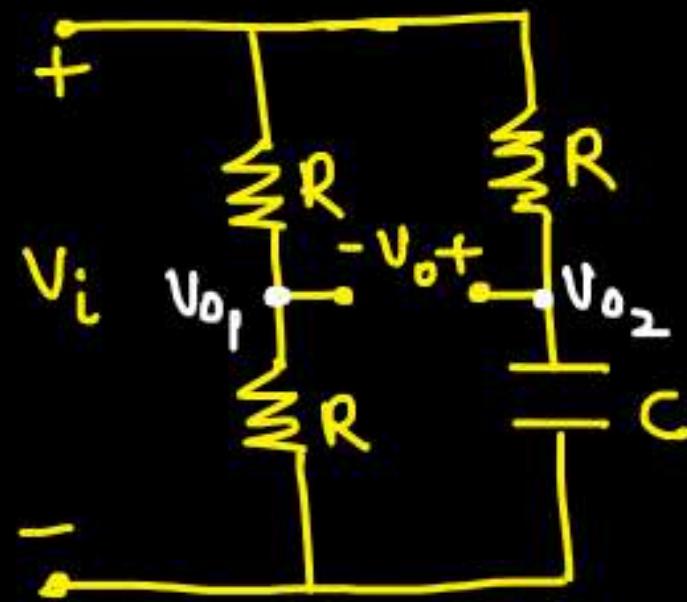

$$\omega=0 \Rightarrow V_o = V_i/2$$


$$\omega \rightarrow \infty \Rightarrow V_o = V_i/2$$

$$V_o = V_{o_2} - V_{o_1}$$

$$V_o(s) = \frac{1}{1+RCs} V_L(s) - \frac{V_i(s)}{2}$$

$$\frac{V_o(s)}{V_L(s)} = \frac{1}{2} \left[\frac{1 - sRC}{1 + sRC} \right]$$

PrepFusion



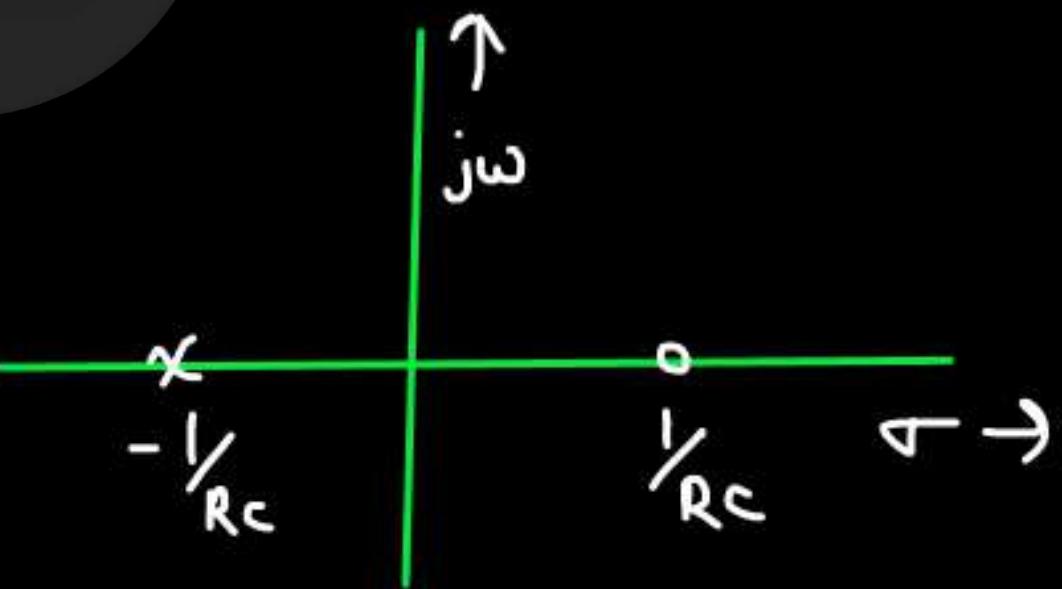





Both BSF and APF will give some o/p @ $\omega=0$ and
@ $\omega=\infty$

but in case of APF, poles and zero will be of
symmetric nature.



Q. Find the types of filter.

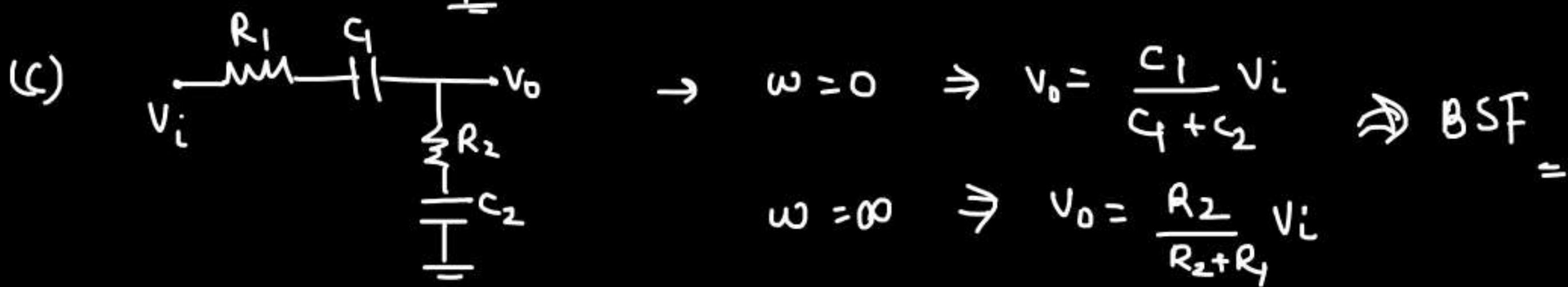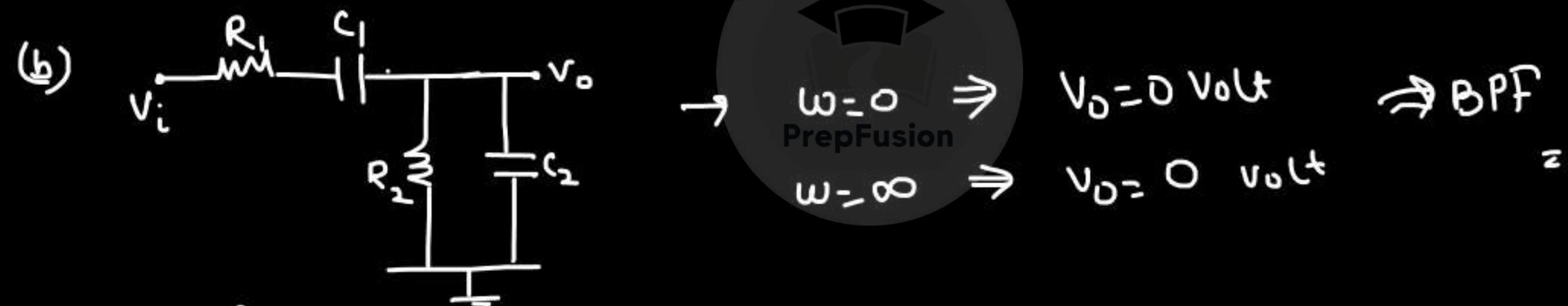
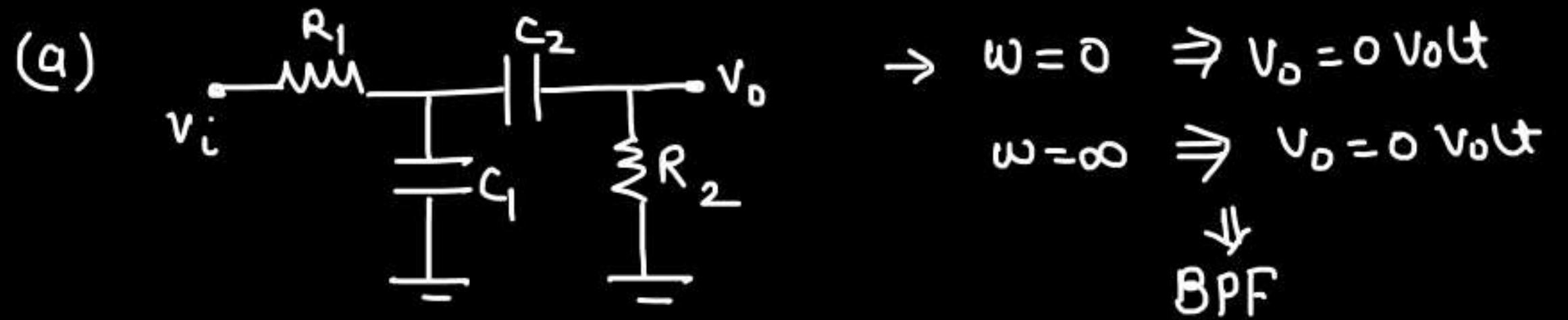


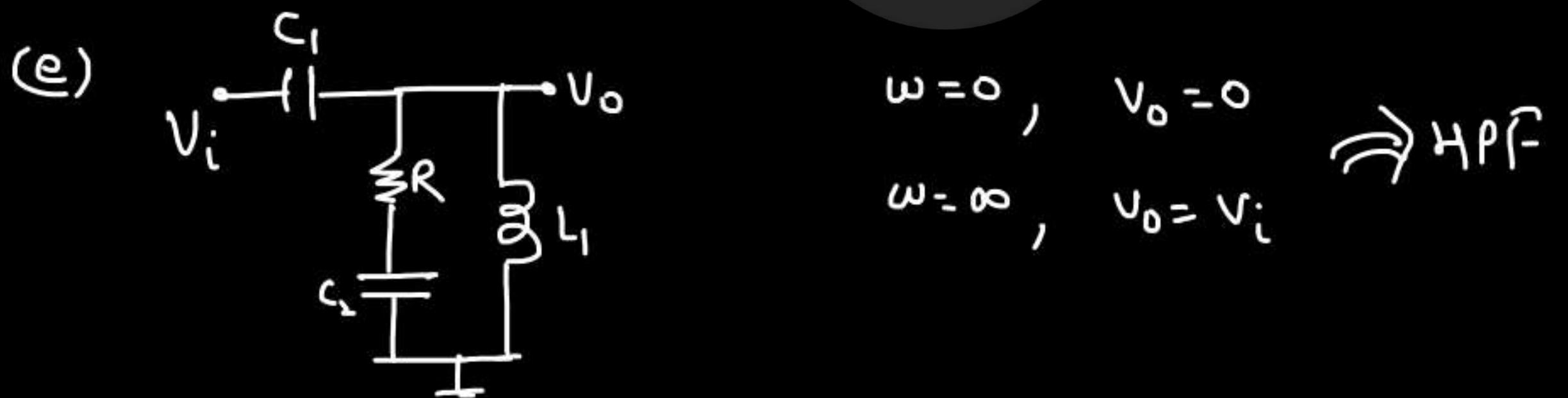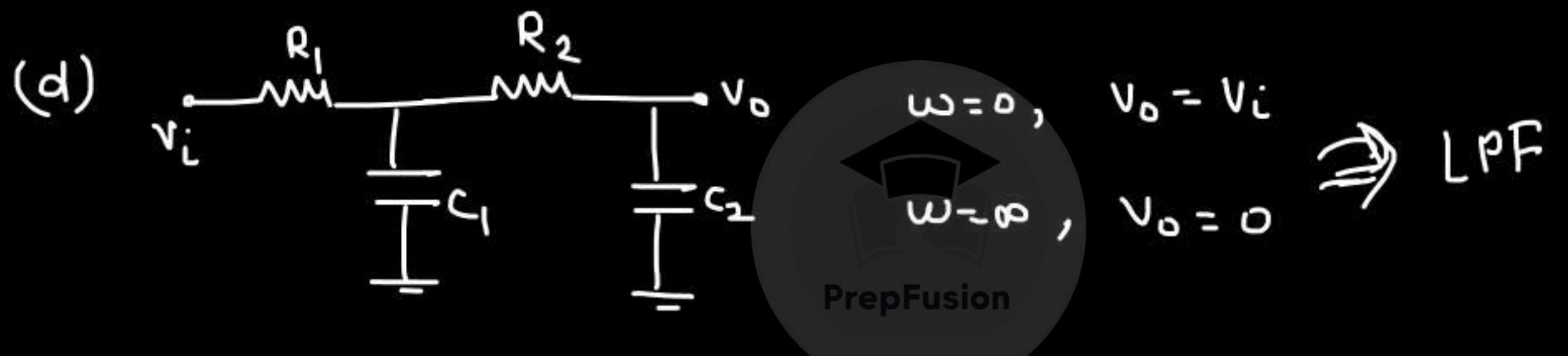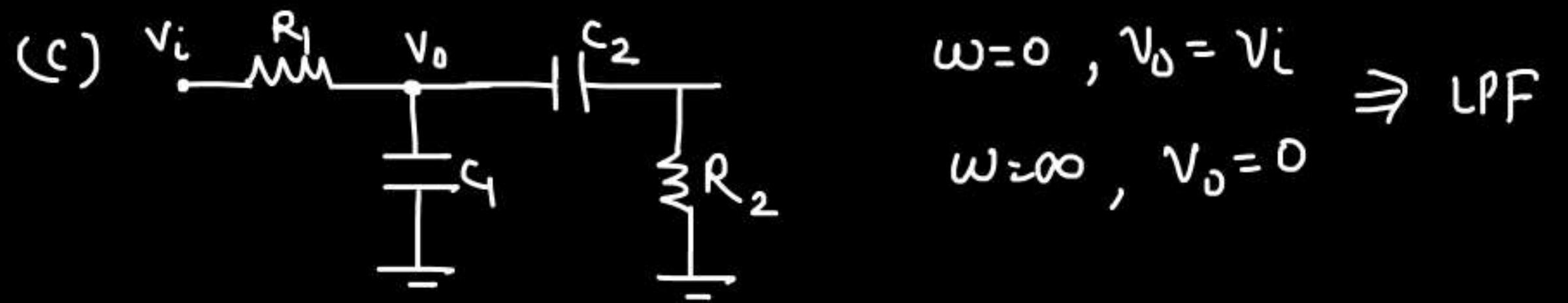

Finding Poles and zeros intuitively :-

$$\frac{V_o(s)}{V_i(s)} = H(s)$$

$$H(s) \Big|_{s=s_z} \rightarrow 0 \quad , \quad H(s) \Big|_{s=s_p} \rightarrow \infty$$

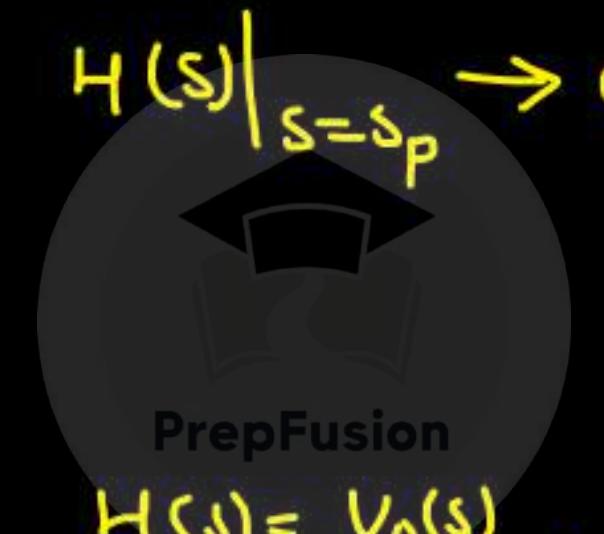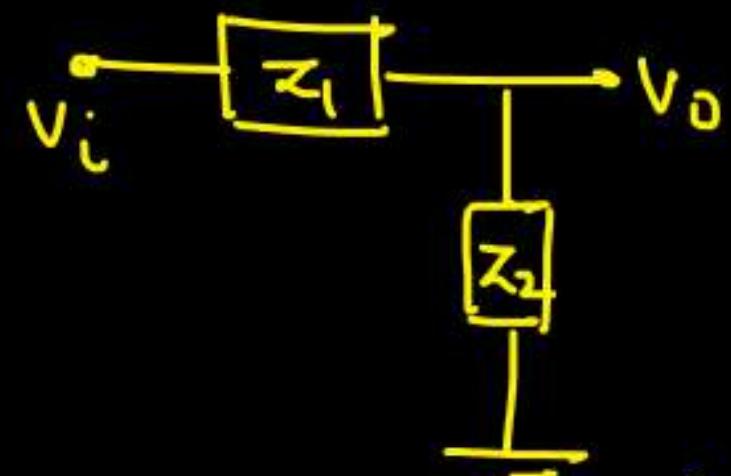

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_2}{Z_2 + Z_1}$$

For poles:-

$$Z_2 = -Z_1 \quad (Z_1 = Z_2 \neq 0)$$

for zeros :-

(i) Break the link b/w $0/p$ & i/p

$$z_1 \rightarrow \infty \quad (z_2 \neq \infty)$$

(ii) $z_2 \rightarrow 0 \quad (z_1 \neq 0)$

→ Some more imp. Points:-

(i) For any T.F., no of poles and no of zeros are equal.

$$H(s) = \frac{s+a}{(s+b)(s+c)}$$

Poles $\Rightarrow -b, -c$

Zeros $\Rightarrow -a, \infty \rightarrow$ not finite


(ii)



$$Z_{eq} = R_1 + R_2 \rightarrow$$


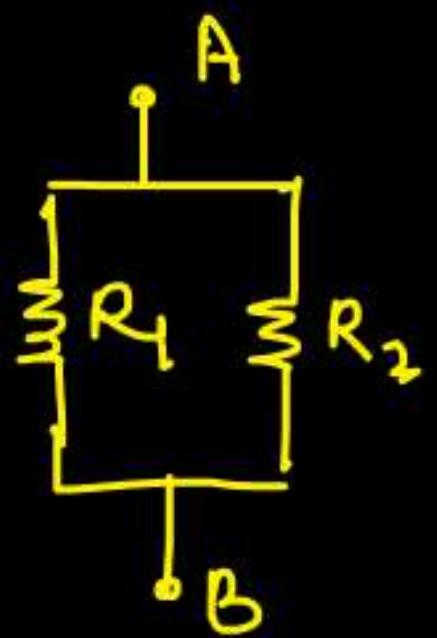
$$R_2 = -R_1 \quad \underline{\underline{=}}$$



$$Z_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$




$$R_1 = -R_2$$



PrepFusion

Eg. - 1

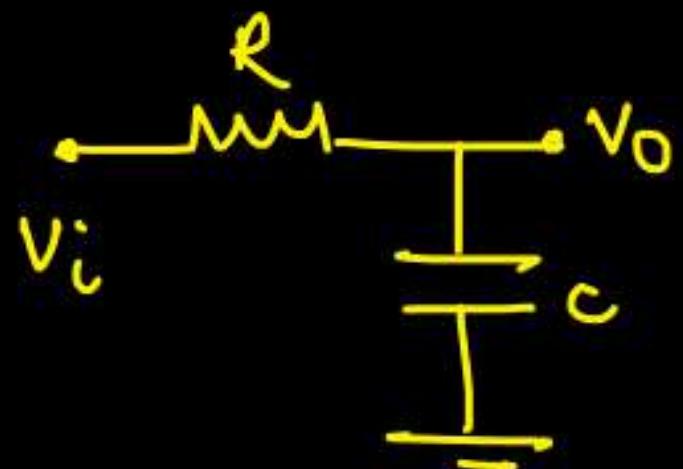

for zero's

(i) $Z_1 = R \rightarrow \text{fixed}$

$\Rightarrow Z_2$ can never go to ∞ .

(ii) $S = \infty \Rightarrow \frac{1}{sC} = 0 \Rightarrow V_o = 0$

\Downarrow
we have a zero at $s_C = \infty$

for poles:-


$$Z_2 = -Z_1$$

$$\frac{1}{sC} = -R$$

$$s_p = -\frac{1}{RC} \approx$$

Alternative method for finding pole :-

Put $V_i \rightarrow 0$

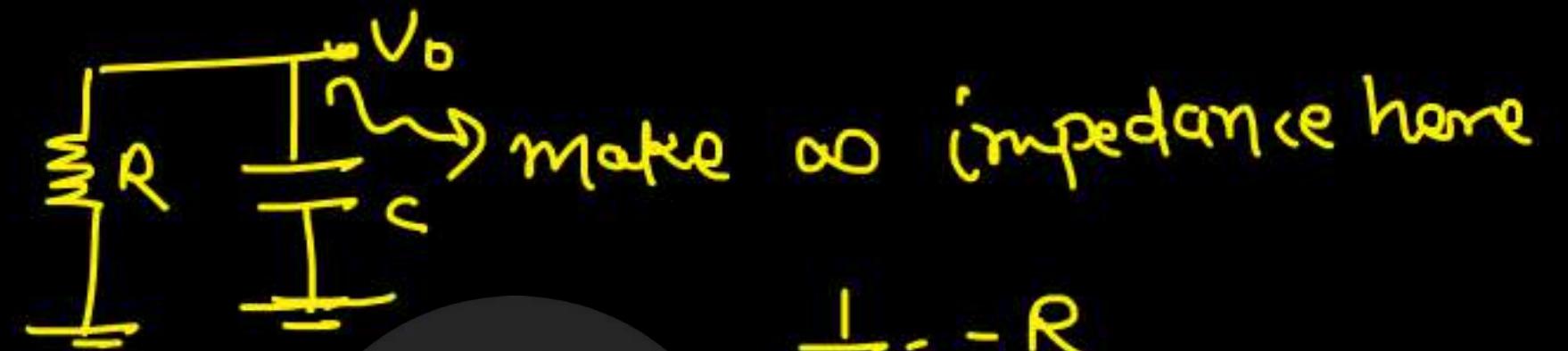

$$\frac{1}{sC} = -R$$


$$s_p = -\frac{1}{RC}$$

$$H(s) = \frac{A}{sRC + 1}$$


$$H(0) = A \Rightarrow V_o = V_i \Rightarrow H(0) = 1$$

$$A = 1 \Rightarrow H(s) = \frac{1}{sRC + 1}$$

②

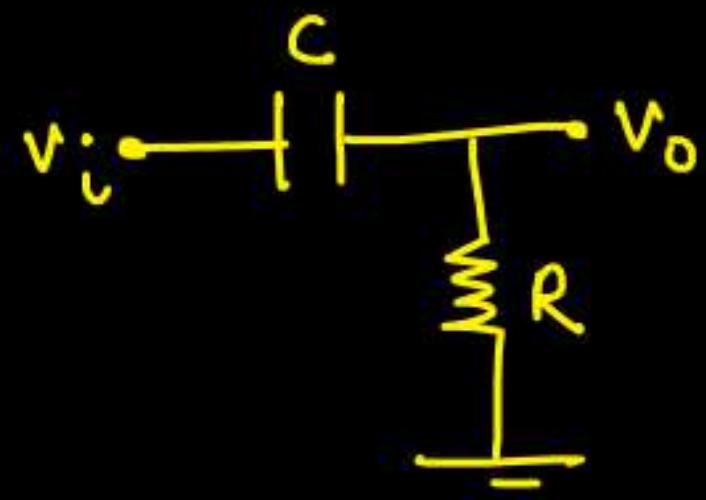

for pole:-

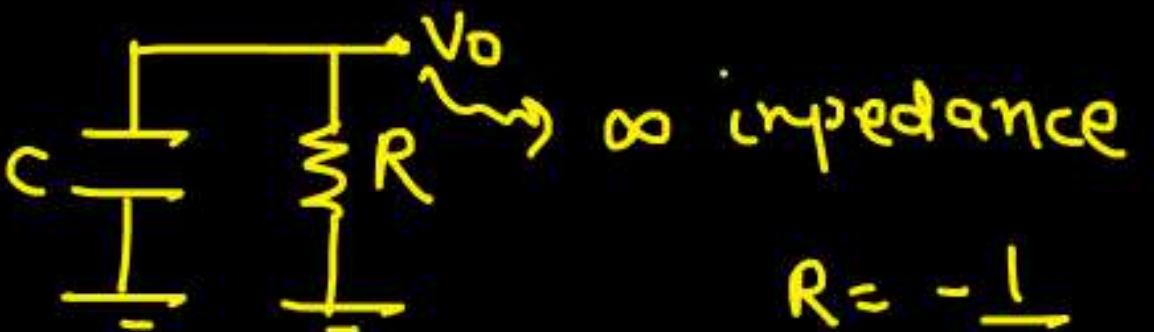

$$R = -\frac{1}{SC}$$

$$s_p = -\frac{1}{RC} =$$

for zero:-

$$(i) z_1 \rightarrow \infty \Rightarrow \frac{1}{SC} = \infty \Rightarrow s_z = 0 =$$

$$(ii) z_2 \rightarrow 0 \Rightarrow \text{Not possible}$$


PrepFusion

$$H(s) = A \left(\frac{s}{sRC + 1} \right)$$

$$H(\infty) = \frac{A}{RC} = 1 \Rightarrow A = RC$$

$$\Rightarrow H(s) = \frac{sRC}{sRC + 1} =$$

③

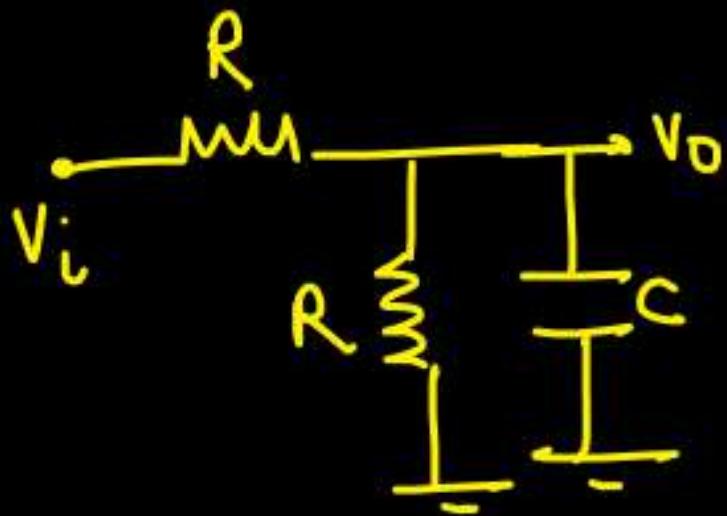

for zero


if $Z_1 \rightarrow \infty \Rightarrow$ not possible

(ii) $s=0 \Rightarrow Z_2=0$

$$\Rightarrow s_{Z_2} = \infty$$

$$H(s) = \frac{A}{\frac{SRC}{2} + 1}$$

for pole

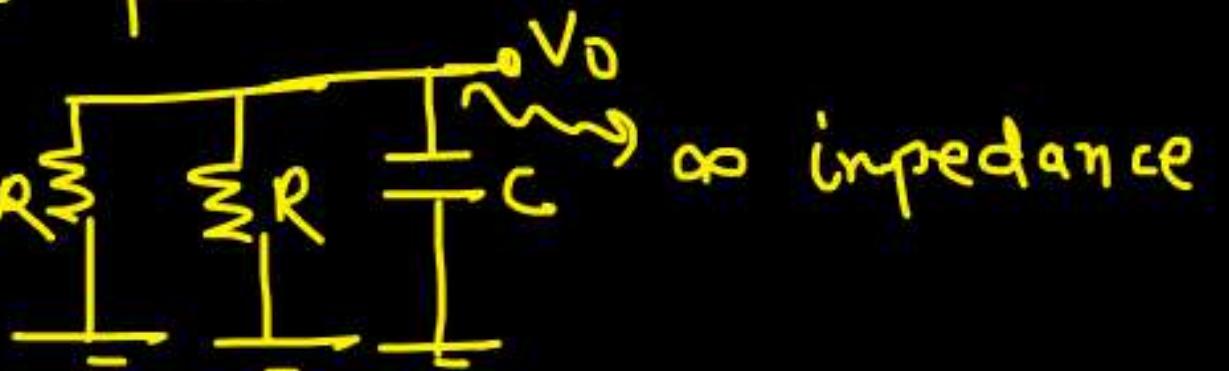


$$\frac{1}{\frac{R}{2} + \frac{1}{C}} \Rightarrow s_p = \frac{-2}{RC} =$$

$$H(0) = A = \frac{1}{2}$$

$$H(s) = \frac{\frac{1}{2}}{\frac{SRC}{2} + 1}$$

$$H(s) = \frac{1}{SRC + 1}$$

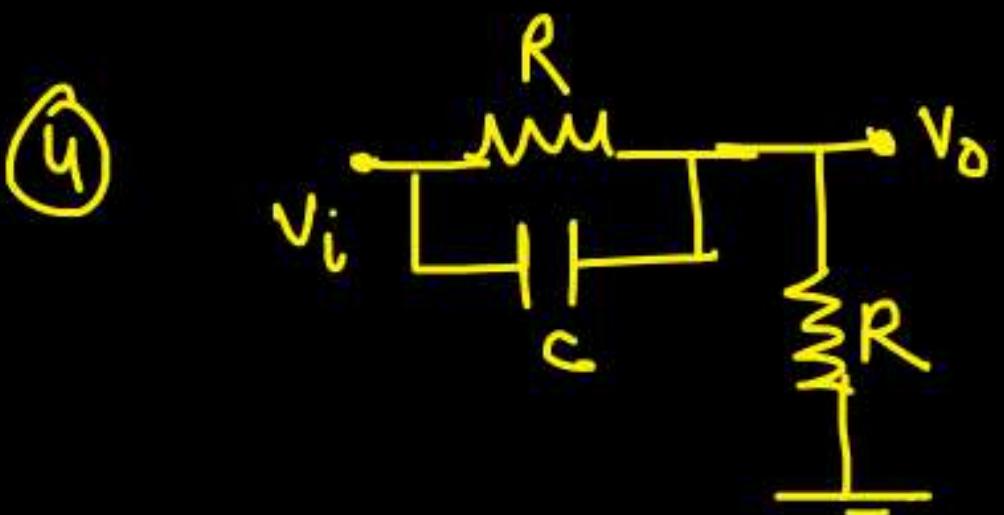

for pole :-

$$s_p = -\frac{1}{RC}$$

for zero :-

(i) $z_1 \rightarrow \infty$

$$\frac{1}{sC} = -R$$

$$s_z = -\frac{1}{RC}$$

(ii) $z_2 \rightarrow 0 \Rightarrow$ Not possible




$$H(s) = A \left[\frac{SRC + 1}{\frac{SRC}{2} + 1} \right]$$

$$H(0) = A = \frac{1}{2}$$

↓

$$H(\omega) = \frac{SRC + 1}{SRC + 2}$$

⑥

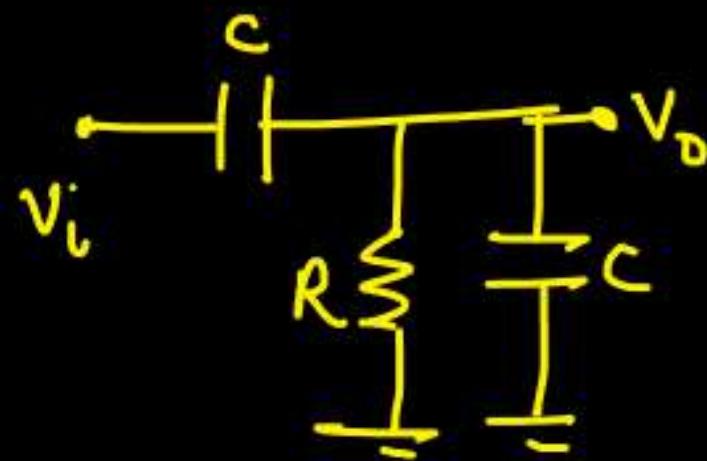

for pole:-

$$s_p = -\frac{1}{2RC}$$

for zero:-

(i) $s=0 \Rightarrow z_1=\infty \Rightarrow s_z=0$ ✅

$\hookrightarrow z_2=R$

(ii) $s=\infty \Rightarrow z_1=0$ ✅

\hookrightarrow zero at $s=\infty$ ✅

because

$s=\infty \Rightarrow z_1=0$

both $z_1 \ll z_2=0$


not acceptable

$$H(\infty) = \frac{A}{2RC} = \frac{1}{2}$$

$$A = RC$$

$$H(s) = \frac{sRC}{2sRC + 1}$$

⑥

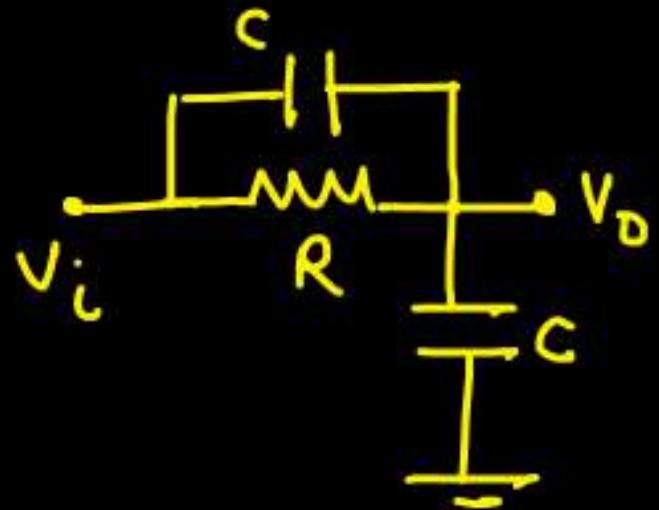

for pole :-

$$s_p = -\frac{1}{2RC}$$

for zero -

$$(i) \quad s_z = -\frac{1}{RC} =$$

$$(ii) \quad s = \infty \Rightarrow \frac{1}{CS} = 0 \Rightarrow z_2 = 0$$




also, $z_1 = 0$
not acceptable

$$H(s) = A \left[\frac{sRC + 1}{2sRC + 1} \right]$$


$$H(0) = A = 1$$

$$H(s) = \frac{sRC + 1}{2sRC + 1} \quad \underline{\text{Ans}}$$

Q7

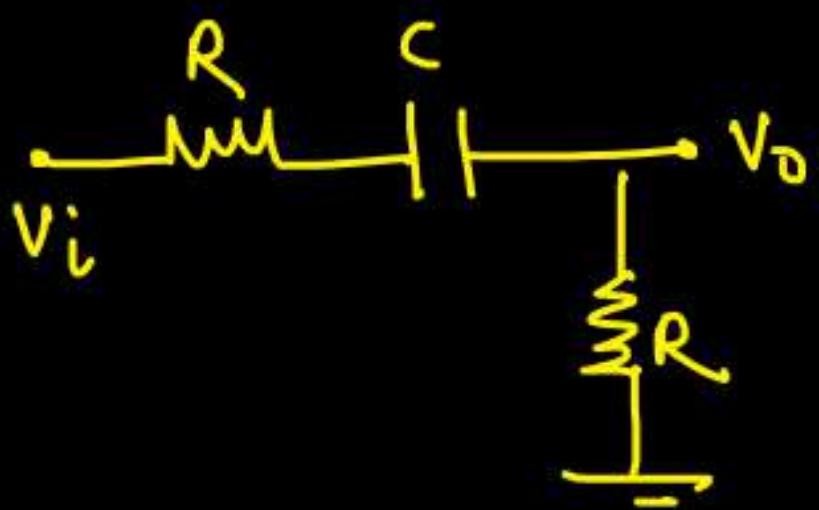

for pole:-

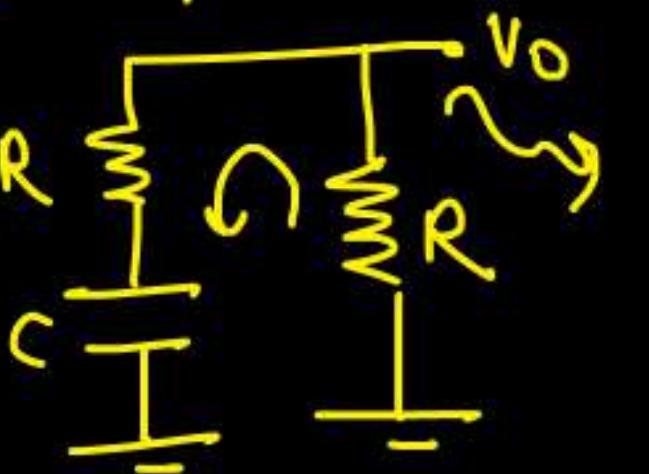

$$-R = R + \frac{1}{\omega} \quad S_p = -\frac{1}{2RC}$$

for zero:-

(i) $S=0 \Rightarrow \frac{1}{\omega} \rightarrow \infty \Rightarrow Z_1 = \infty \Rightarrow S_1 = 0$


(ii) $Z_2 \rightarrow 0 \Rightarrow$ Not possible

$$H(s) = \frac{AS}{2SRC + 1}$$

$$H(\infty) = \frac{A}{2RC} = \frac{1}{2}, \quad A = RC$$

$$H(s) = \frac{SRC}{2SRC + 1}$$

8

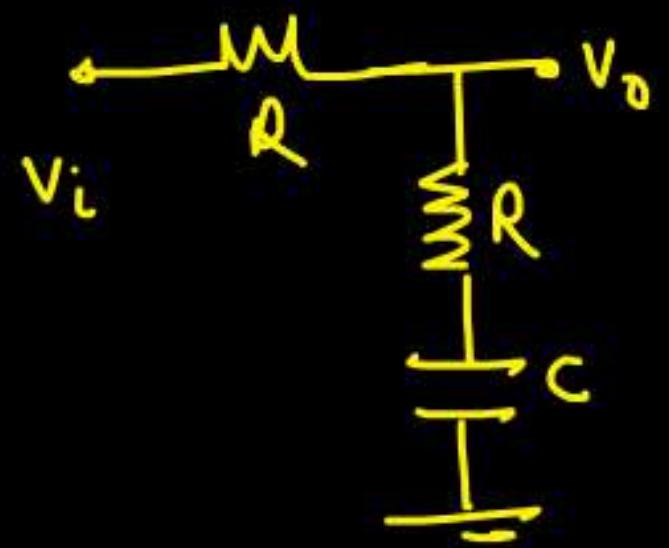

For poles :-


$$s_p = -\frac{1}{2RC}$$

For zero's :-

$$Z_2 \rightarrow 0 \Rightarrow R + \frac{1}{sC} \rightarrow s_z = -\frac{1}{RC}$$

$$H(s) = \frac{sRC + 1}{2sRC + 1} \quad \text{PreFusion}$$

⑨

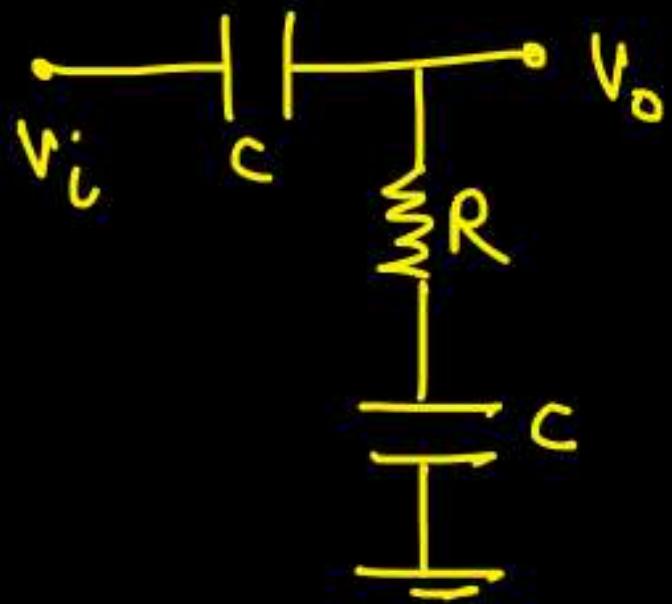

for poles :-

$$Sp = -\frac{2}{RC}$$

for zeros :-

(i) $Z_1 \rightarrow \infty \Rightarrow S_z = 0 \rightarrow \text{zero } X$


Because, $S=0 \rightarrow Z_2=0$

$\therefore S=0 \Rightarrow Z_1 = Z_2 = \infty \rightarrow \text{NOT acceptable}$

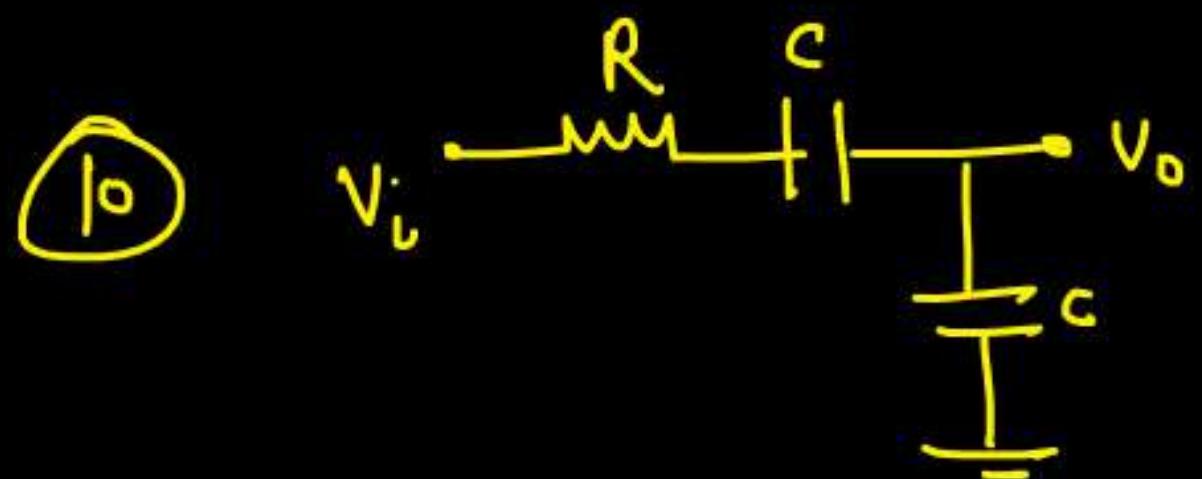(ii) $Z_2 = 0$

$$S_z = -\frac{1}{RC}$$

$$H(s) = \frac{sRC + 1}{sRC + 2} \Rightarrow$$




for poles

$$s_p = -\frac{2}{RC}$$

for zeros:-

$H(s) = \frac{1}{sRC + 2} =$

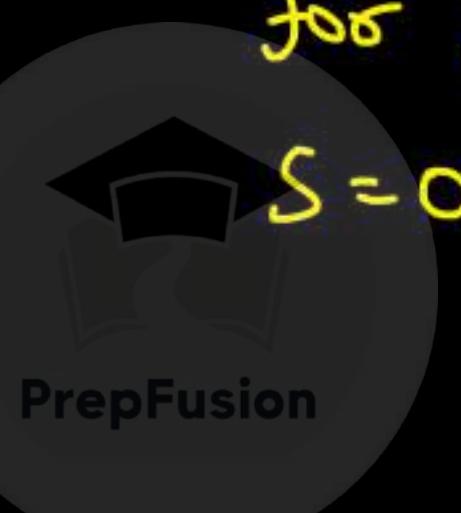


$$s=0 \Rightarrow z_1 \rightarrow \infty \quad z_2 \rightarrow \infty \Rightarrow \text{Not acceptable}$$

$$s=\infty \Rightarrow z_2=0$$

$\therefore z_1=R$

2nd order ckt:-

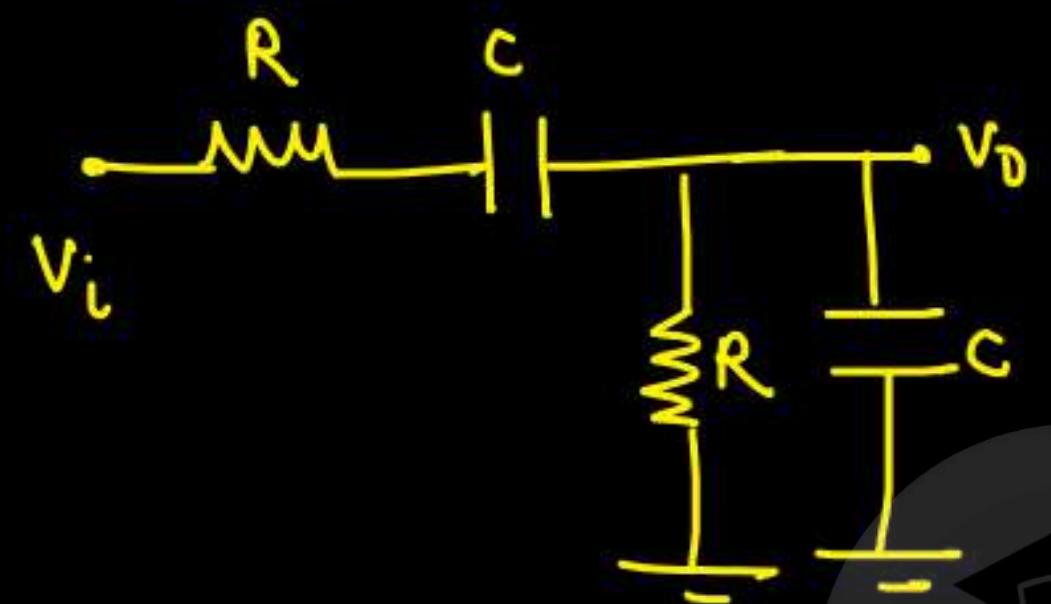

Two storing element =
 \Downarrow


Two poles =

for zeros:-

$$s=0 \Rightarrow z_1=\infty, z_2=R \rightarrow \text{Acceptable } (s_2=0)$$

$$s=\infty \Rightarrow z_2=0, z_1=R \rightarrow \text{Acceptable}$$
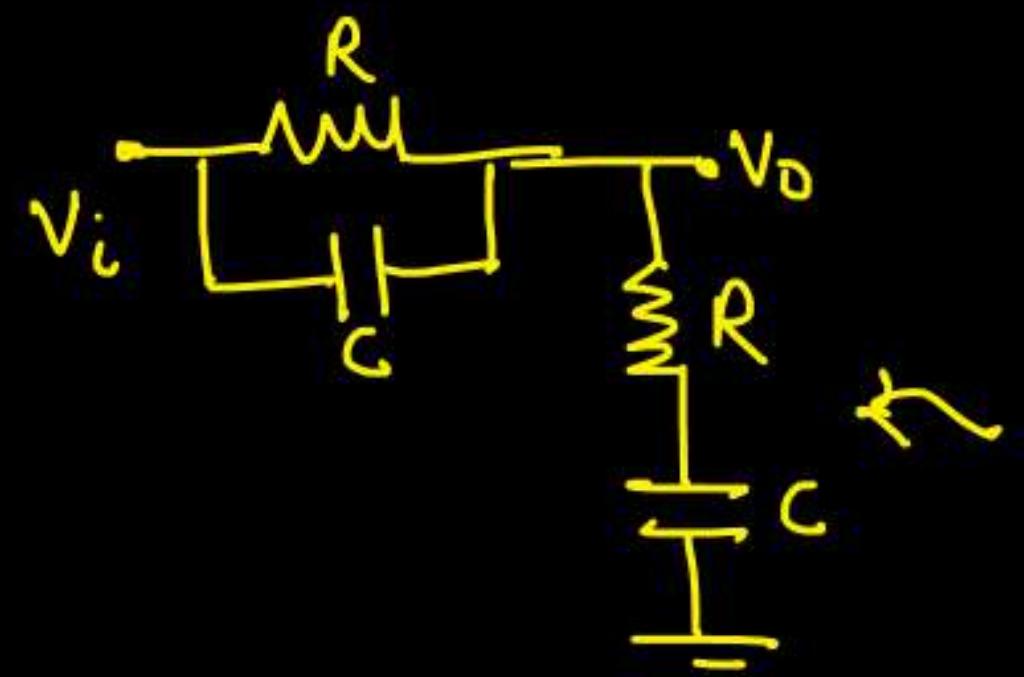
$$H(s) = \frac{AS}{s^2 + bs + c} \quad \Downarrow \quad \Downarrow$$



① Two poles :-

② For zeros

$$(i) R + \frac{1}{sC} = 0 \Rightarrow s_2 = -\frac{1}{RC} \leftarrow$$

↙ acceptable

$$Z_1 = \infty, Z_2 = 0$$

$$(ii) R + \frac{1}{sC} = 0$$

$$\Rightarrow s_1 = -\frac{1}{RC} \leftarrow$$


$$\left[s \rightarrow \infty, Z_1 = 0, Z_2 = R \right]$$

Not a zero at $s = \infty$

$$H(s) = \frac{A(sRC + 1)^2}{s^2 + bs + c}$$

\approx

PrepFusion

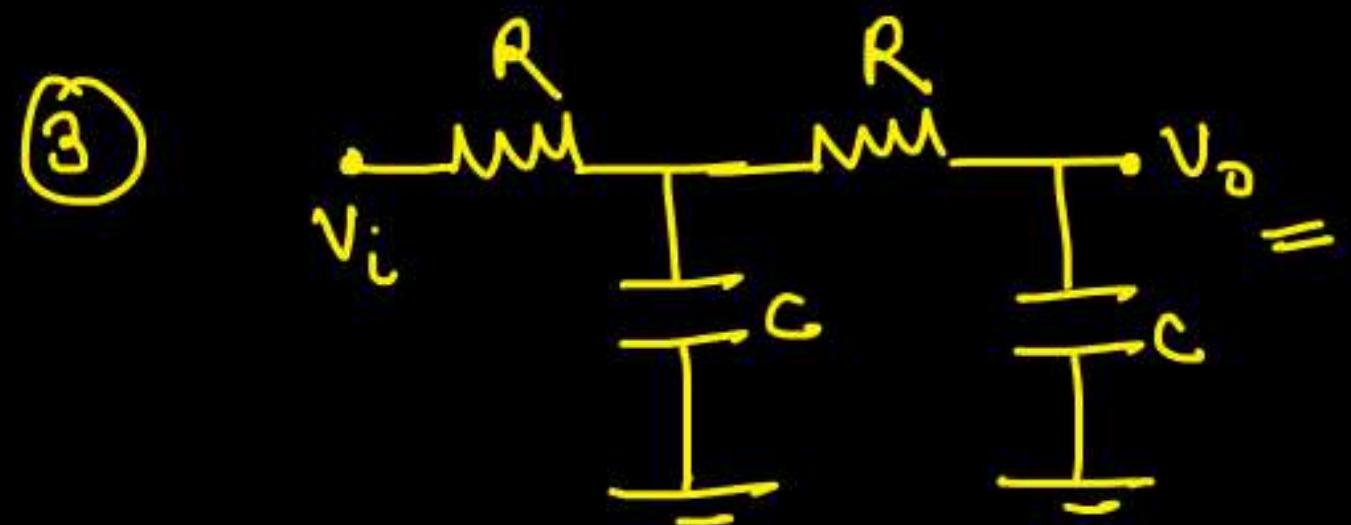

① Two poles:-

② For zeros:-


$$s = \infty \Rightarrow V_o = 0 \Rightarrow \text{zero at } s = \infty$$

$$s_L = \infty =$$

Two zero's at $s = \infty$

PrepFusion

$$H(s) = \frac{A}{s^2 + bs + c} =$$

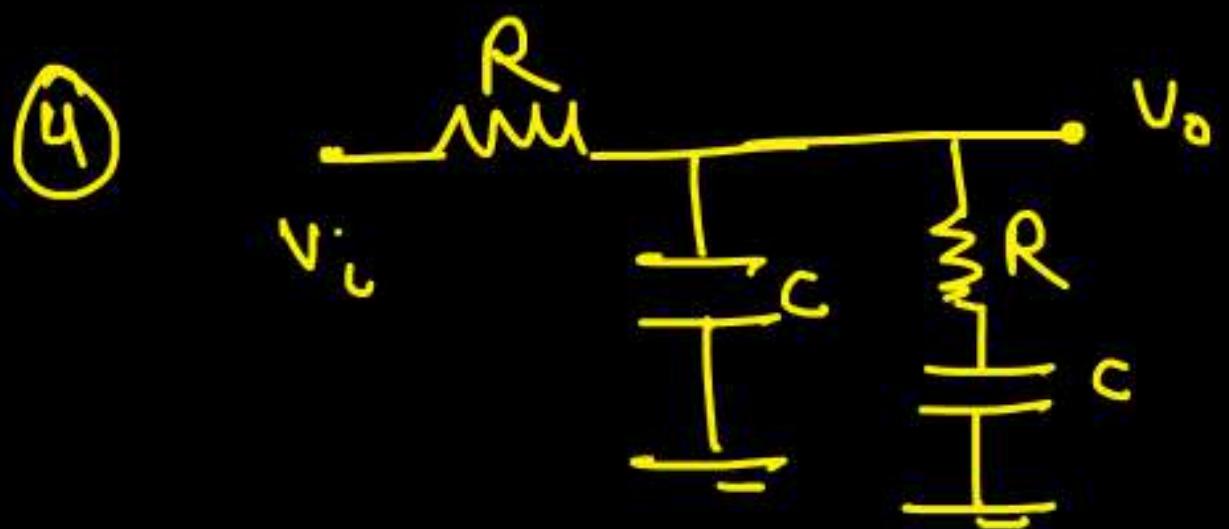

Two poles

(1) Zeros

$$R + \frac{1}{\omega} = 0 \Rightarrow \zeta \omega^2 = -\frac{1}{RC}$$

$$\zeta = \infty \Rightarrow \frac{1}{\omega} = 0 \quad \Leftarrow \\ \hookrightarrow V_0 = 0 \Rightarrow \zeta = \infty$$

$$H(s) = A \frac{(sRC + 1)}{(s^2 + \omega s + b)}$$

Drawing bode plots of first order RC circuits :-


$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{s+a}{s+b} ; \quad a > b$$

\approx pole


$$H(0) = \frac{a}{b}$$

$$H(\infty) = \frac{1}{\infty} = 0 \text{ dB}$$

pole $\rightarrow -20 \text{ dB/dec.}$

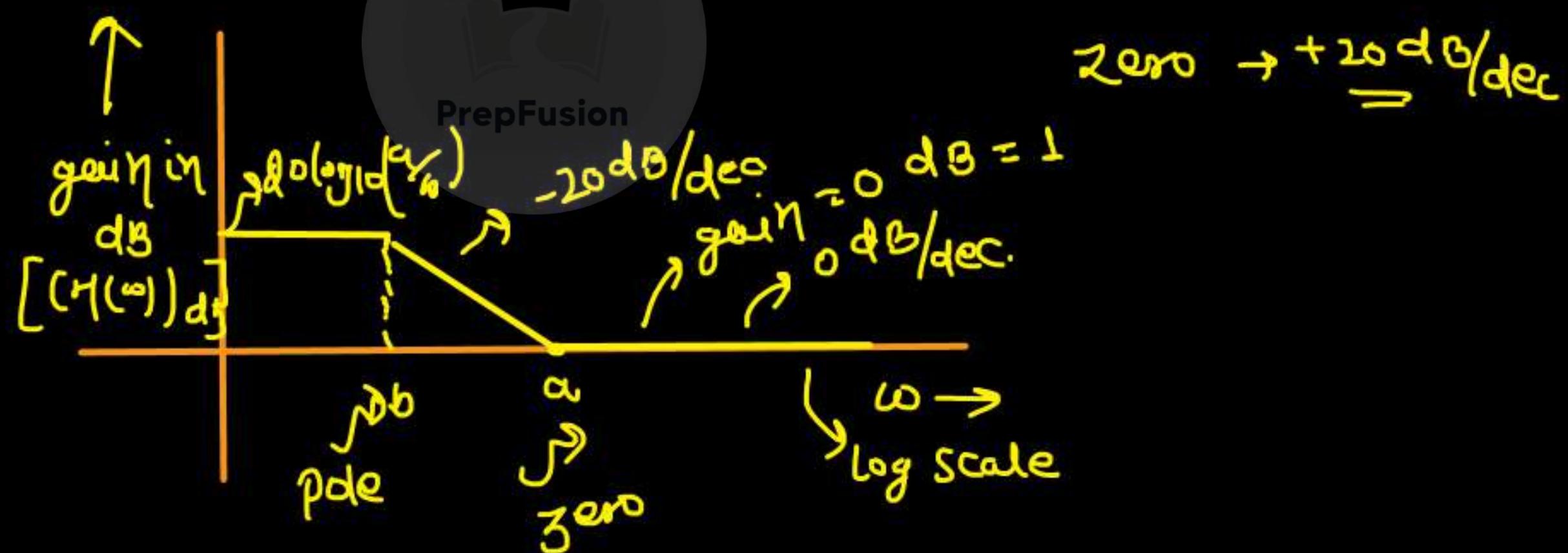


Eg. - 1

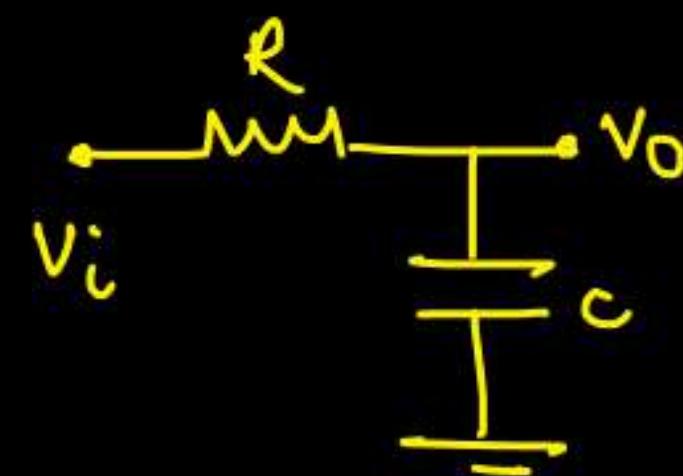

$$s_p = -\frac{1}{RC}$$

$$H(s) = \frac{1}{sRC + 1} \rightarrow \text{pole} = -\frac{1}{RC}$$
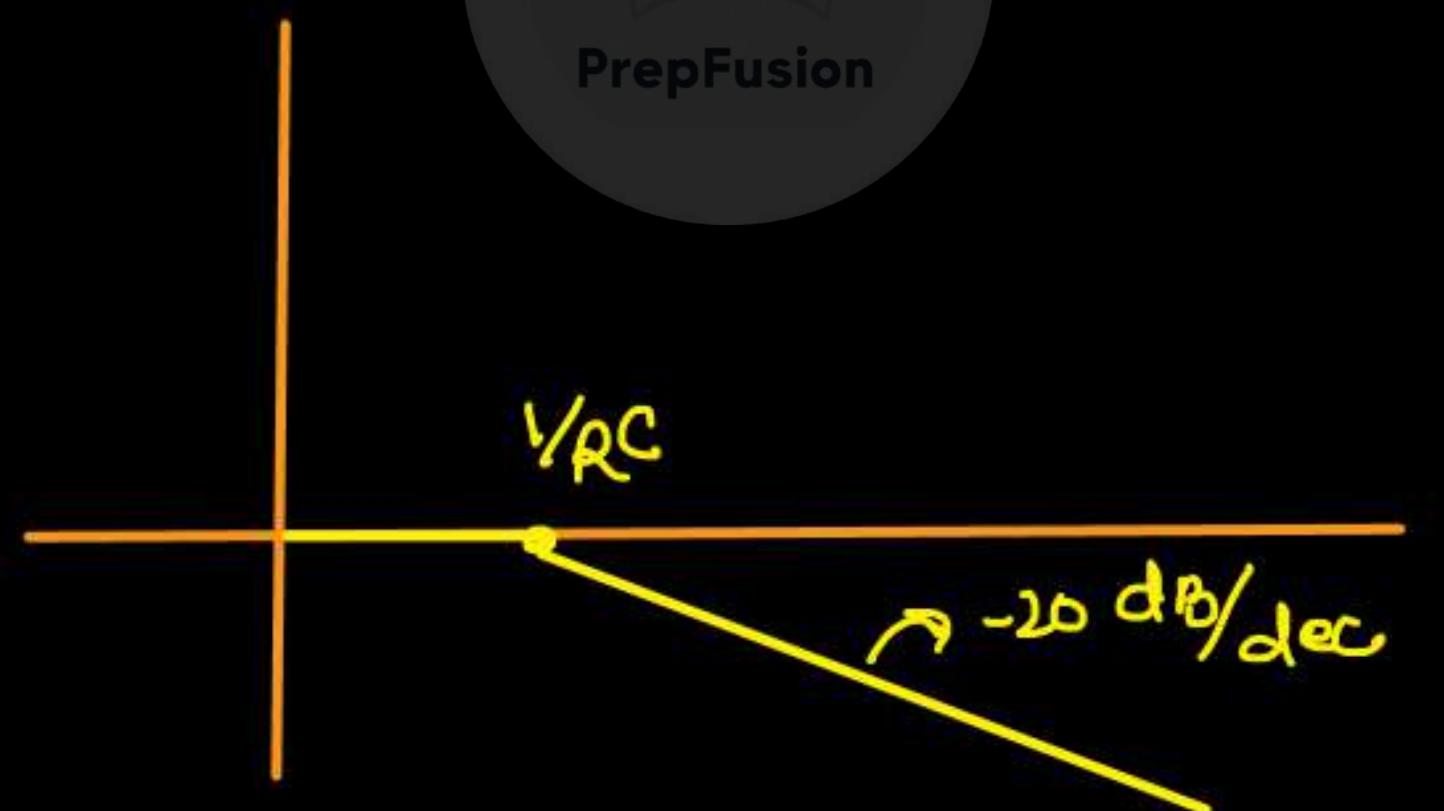
$$\left. \begin{aligned} H(0) &= 0 \text{ dB} \\ H(\infty) &= 0 = -\infty \text{ dB} \end{aligned} \right\} =$$



PrepFusion