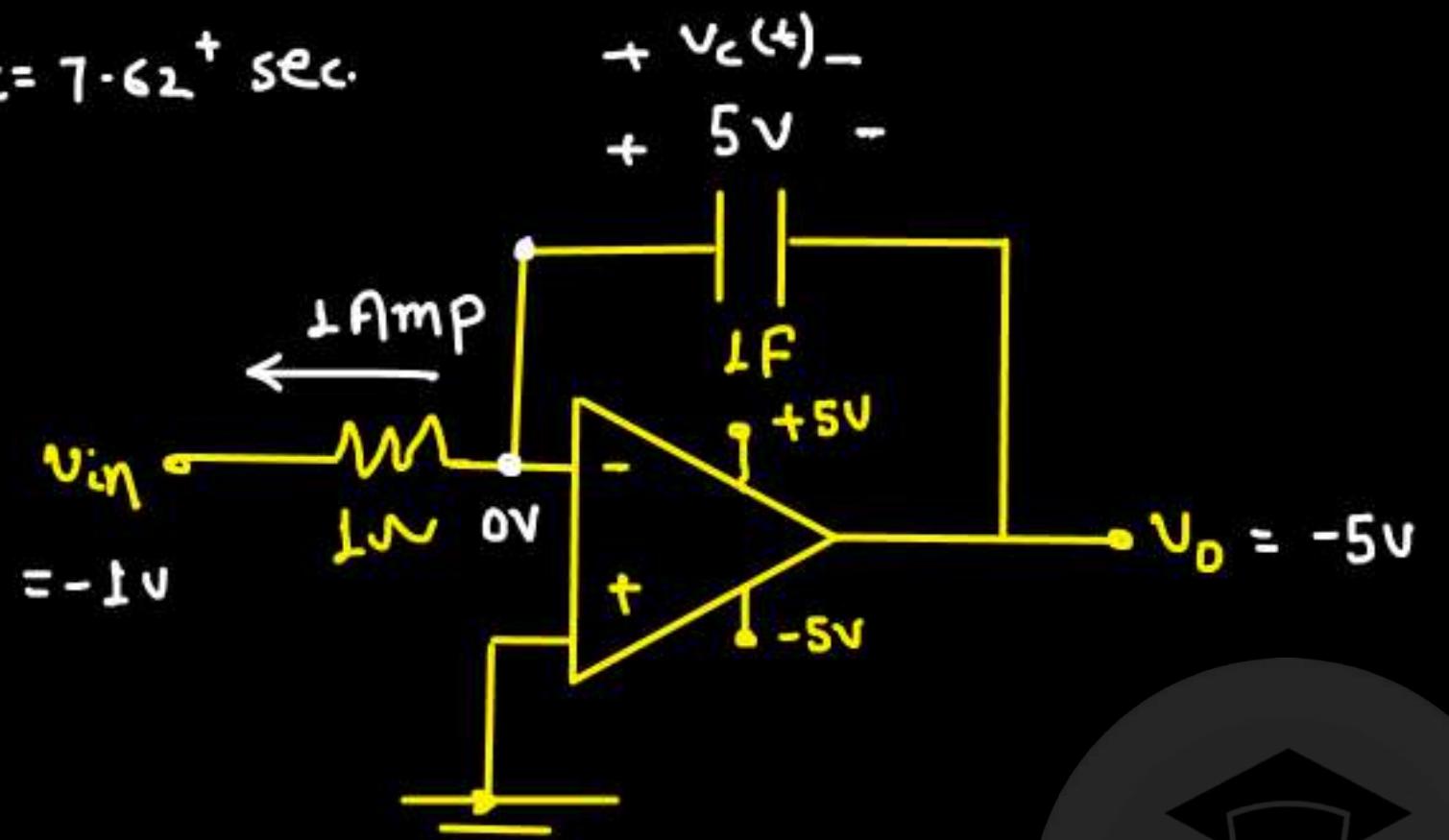


at  $t = 7.62^+$  sec.



$$V_c(t) = 5 - \frac{1}{C} (1)(t - 7.67)$$




$$V_c(t) = 5 - (t - 7.62)$$

PrepFusion

$$V_o(t) = (t - 7.62) - 5$$


$$V_o(t) = 1.38V$$
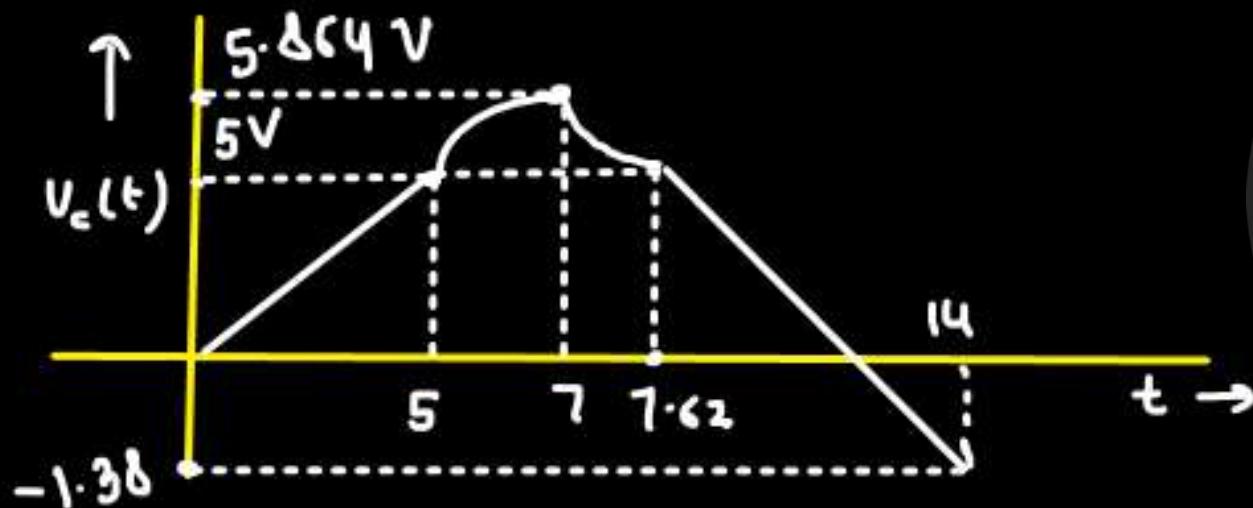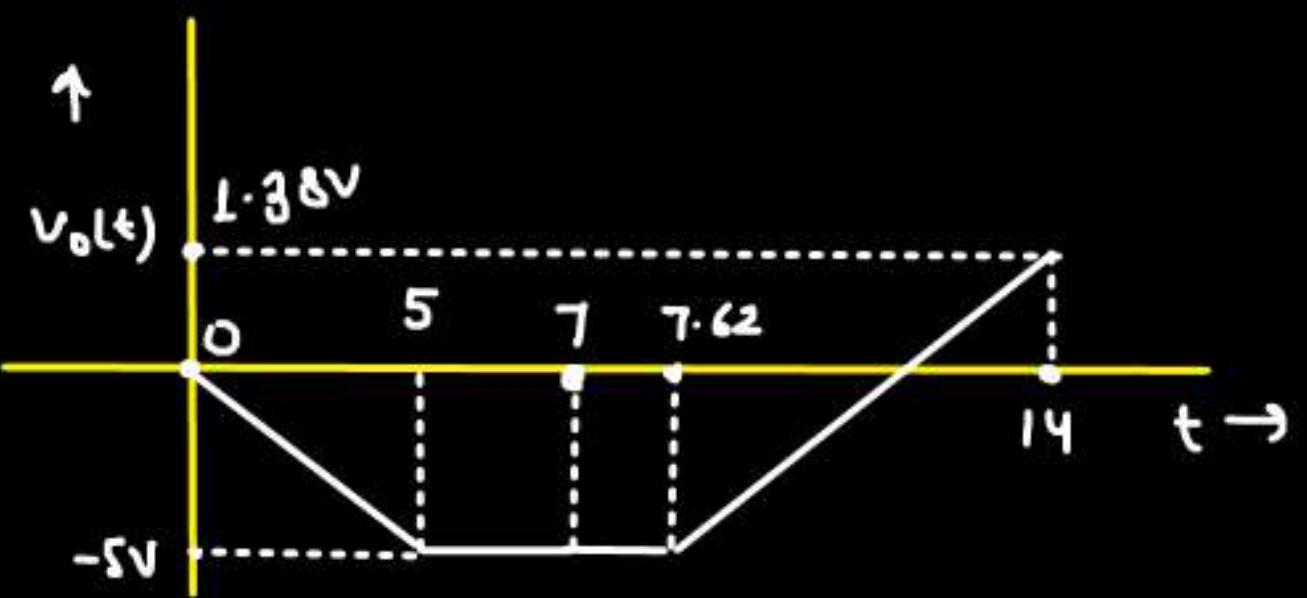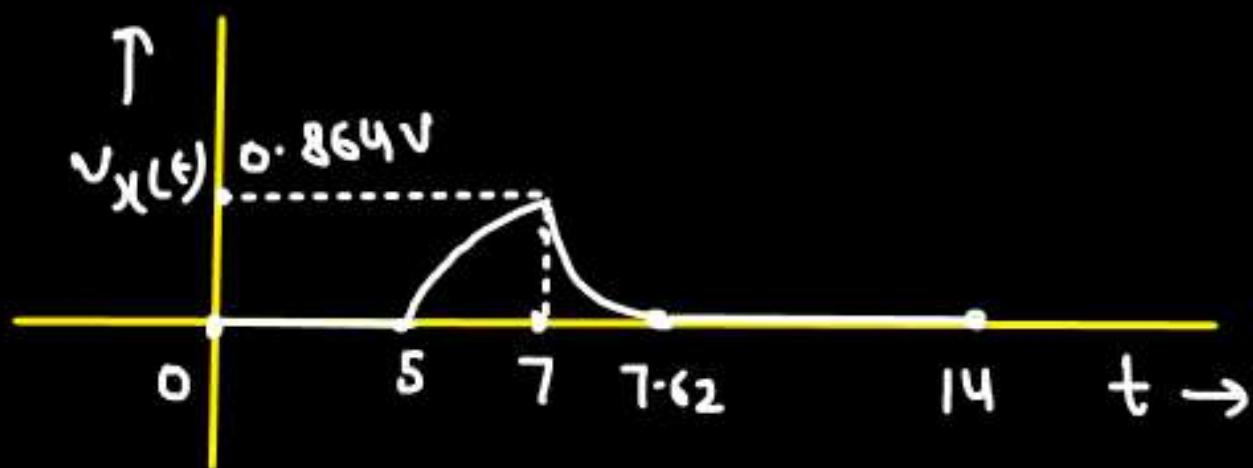
$$V_c(14 \text{ sec.}) = 5 - (14 - 7.62) = -1.38V$$



$$\begin{aligned}
 v_o(10\text{sec}) &= (10 - 7.62) - 5 \\
 &= -2.62\text{V} \quad \text{Ans.}
 \end{aligned}$$

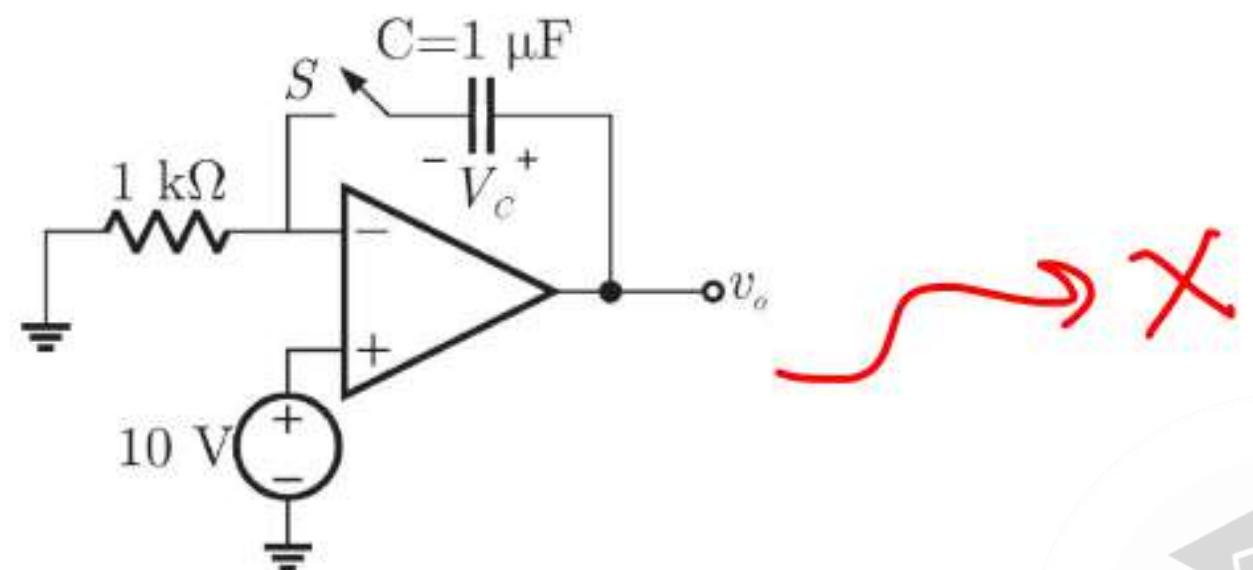For the circuit shown in the following figure, the capacitor C is initially uncharged. At  $t = 0$ , the switch S is closed. The voltage  $V_C$  across the capacitor at  $t = 1 \text{ millisecond}$  is:




(GATE-2006)

In the figure shown above, the OP-AMP is supplied with  $\pm 15V$


PrepFusion

- (A) 0 Volt
  - (B) 6.3 Volts
  - ~~(C) 9.45 Volts~~
  - (D) 10 Volts
- ~~(E) 8.93V~~


for  $t < 0$

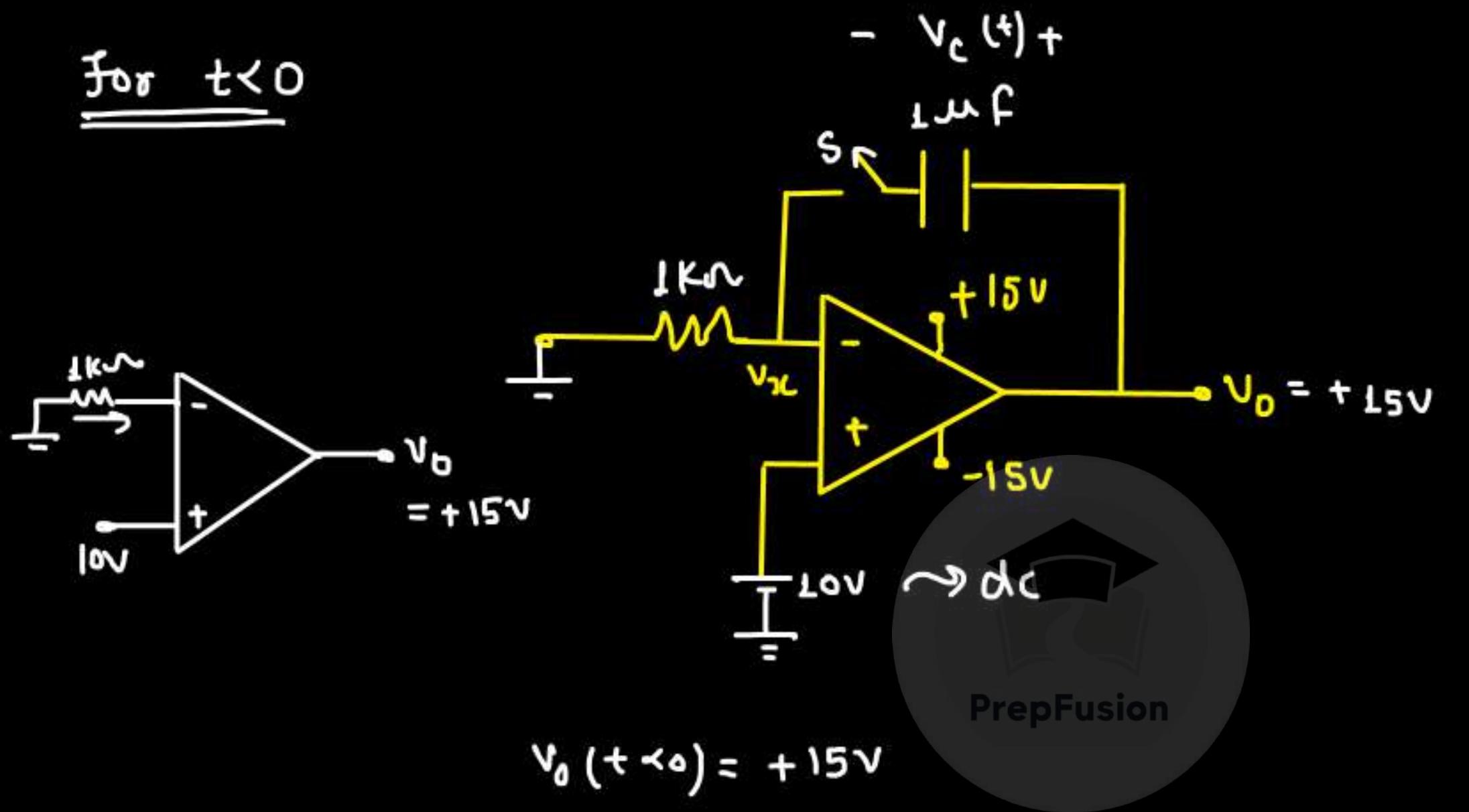

For  $t > 0$  :-

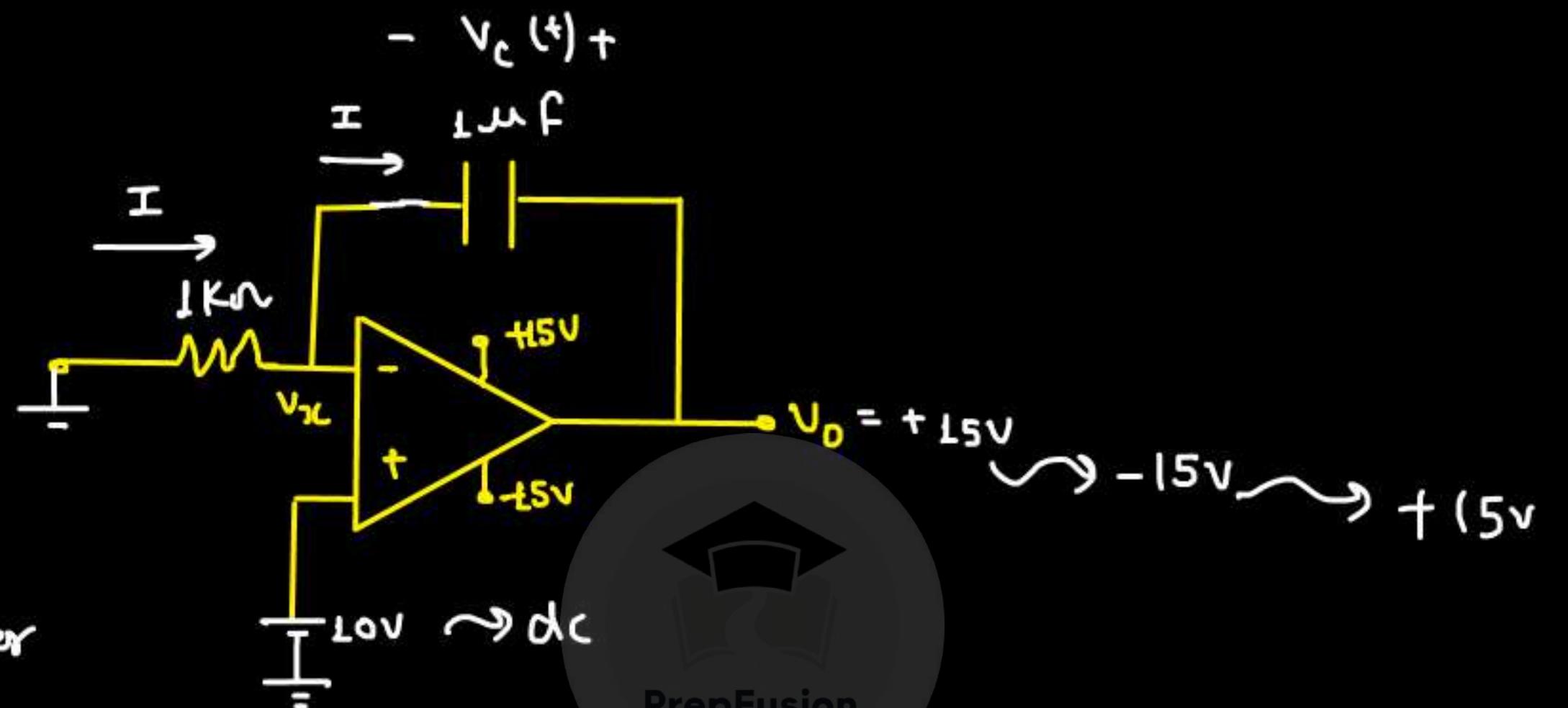

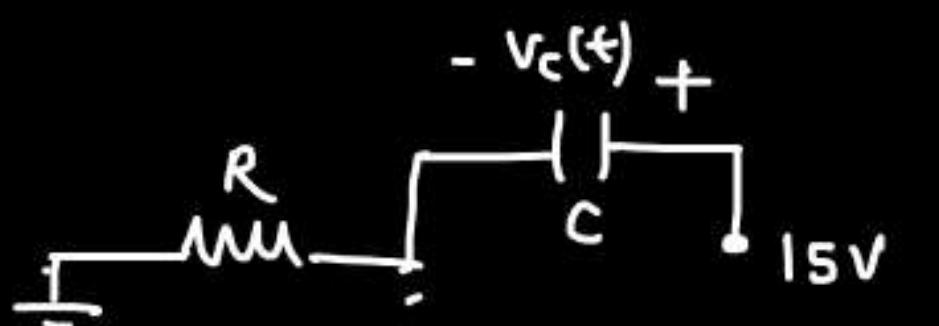O/P saturated  $\Rightarrow$  virtual short not valid  $\Rightarrow$



$$V_C(1ms) = 15 \left(1 - e^{-1m/1m}\right)$$

$$\boxed{V_C(1ms) = 9.48V} \quad \times$$

$$v_x(0^+) = 15V$$

$$v_x(\infty) = 0V$$

$$\boxed{v_x(t) = 15e^{-t/1m}}$$

at  $t=0^+$

$$V_- = 15V, V_+ = 10V \Rightarrow v_o(0^+) = -15V$$


Now

$$v_x(0^+) = -15V$$

$$\Rightarrow V_- = -15V, V_+ = 10V \Rightarrow v_o(0^+) = +15V$$

\*

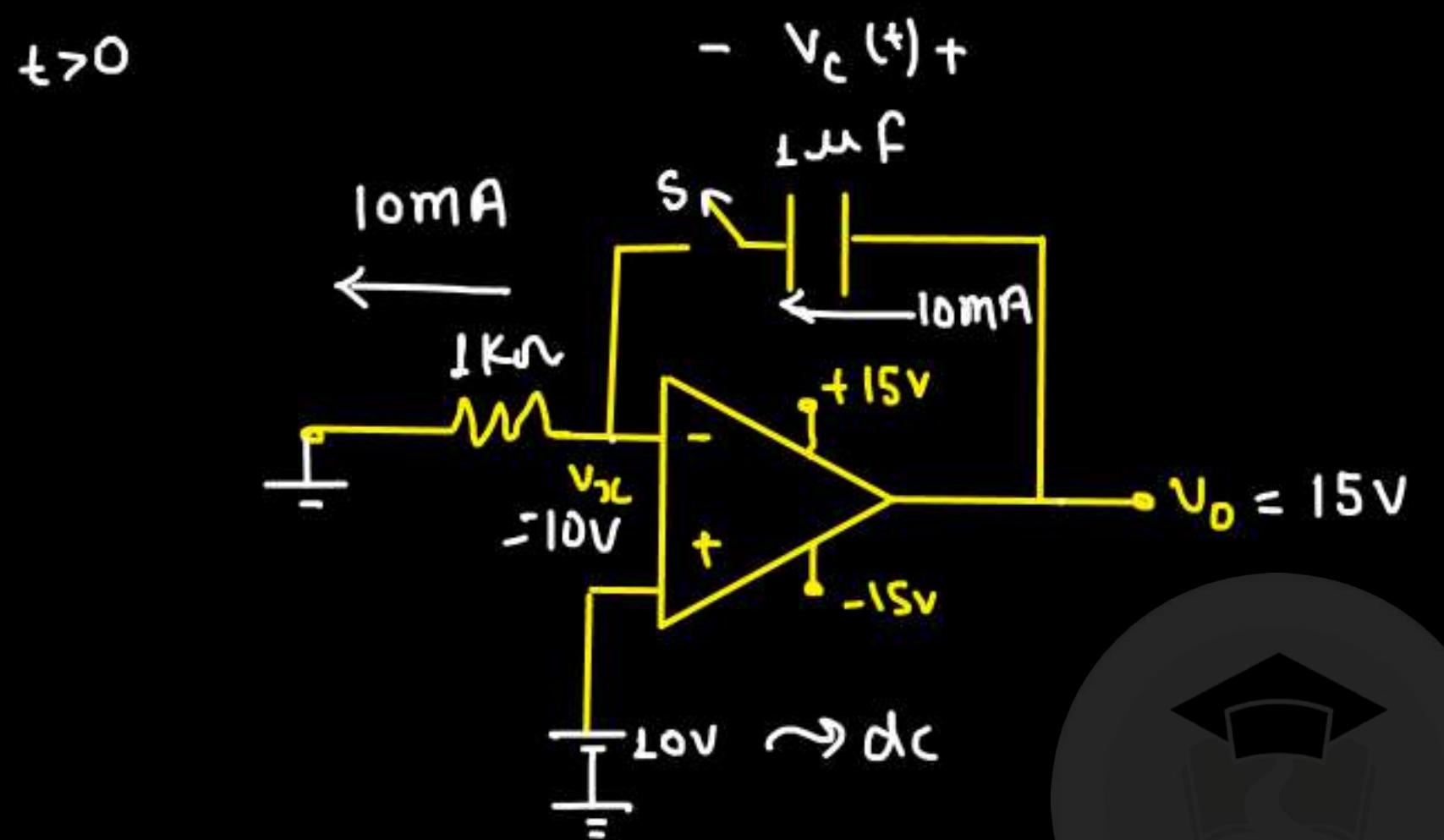$\Rightarrow v_o$  is toggling b/w  $+15V$  and  $-15V$ , only @  $t=0^+$   $\Rightarrow$  The ckt will not work



$$V_C(0^-) = 0V$$

$$V_C(0^+) = 5V$$



## Correct Question :-


$$- V_C(t) +$$

$1\mu F$

Q. The switch is closed


@  $t=0$  . Find  $V_C$  at

$t=1ms$

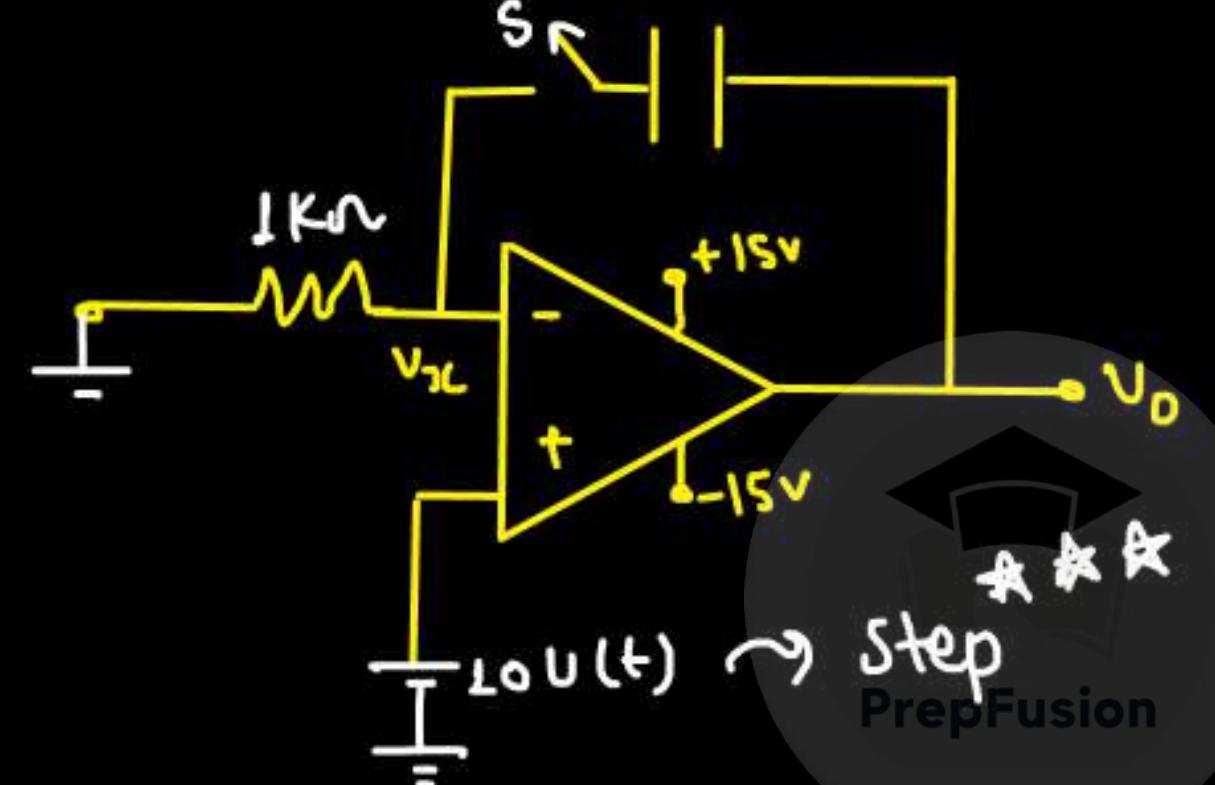

→ @  $t=0^+$

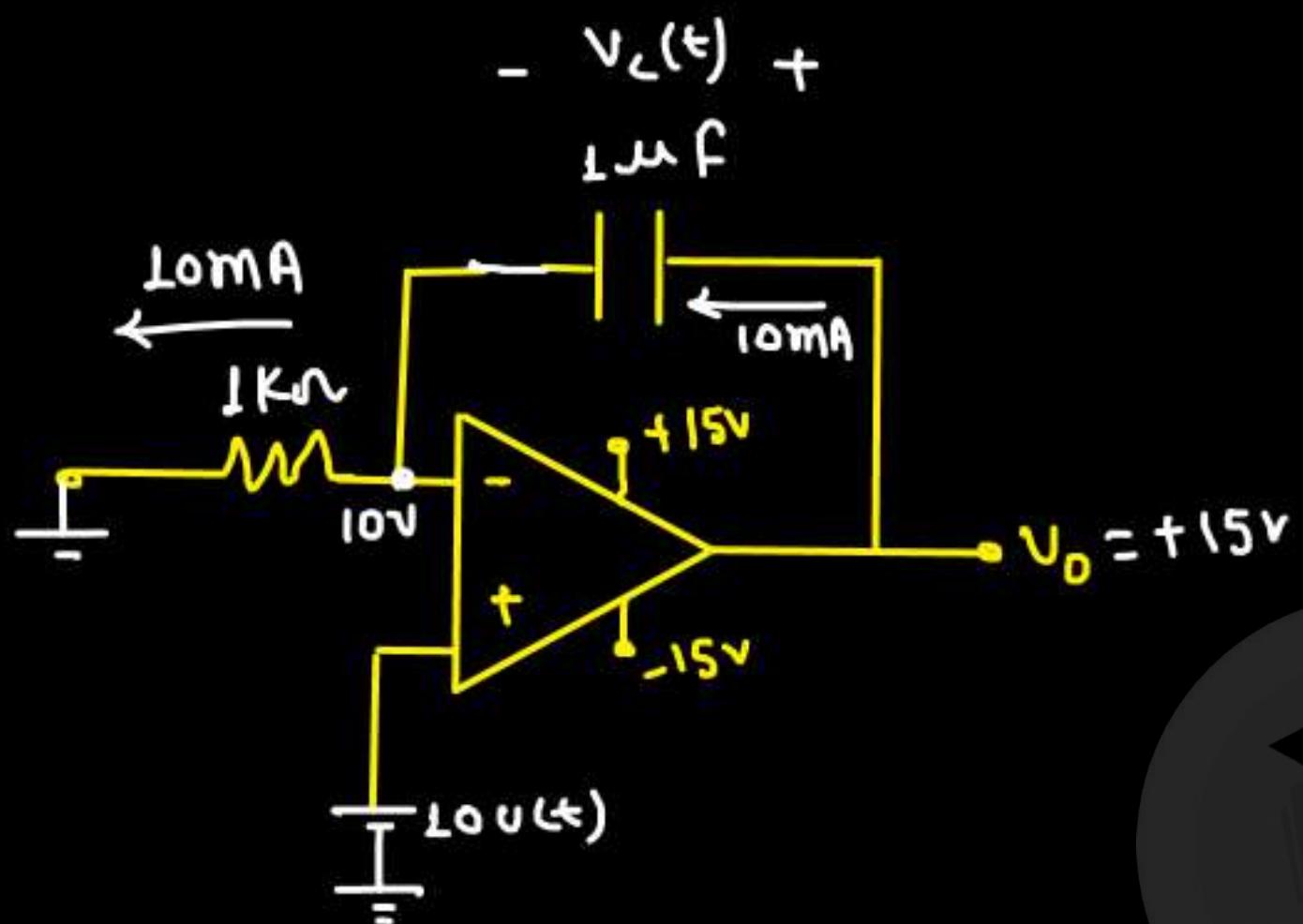o/p is not saturated + negative fb is +ve  $\Rightarrow$  virtual short valid



$$V_c(t) = \frac{1}{1\mu F} \int 10mA dt$$


$$V_c(t) = 10t \times 10^3$$

$$V_o(t) = 10 + V_c(t)$$

$$V_o(t) = 10 + 10^4 t \text{ volt}$$

$$V_o(0.5m) = 15 \text{ volt}$$


PrepFusion

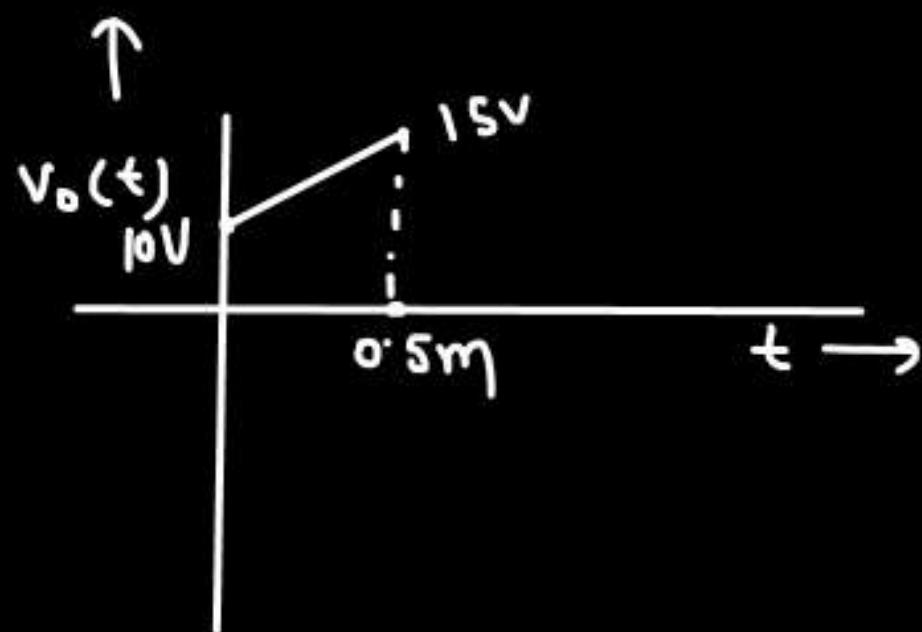

@  $t = 0.5m \text{ sec.} \Rightarrow \text{o/p is saturated.}$

$$- V_c(t) + \downarrow$$

- 5V + virtual short NOT valid

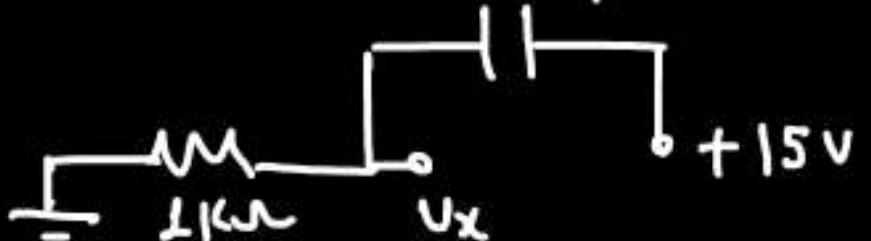

$$v_c(0.5m^+) = 5V, \quad v_c(\infty) = 15V$$




$$v_c(t) = 15 - 10 e^{-(t-0.5m)/1m}$$

$$v_L(0.5m^+) = 10V, \quad v_L(\infty) = 0V$$

$$v_L(t) = 10 e^{-(t-0.5m)/1m}$$


$$v_c(1ms) = 15 - 10 e^{-(0.5m)/1m}$$

$$v_c(1ms) = 8.93V$$

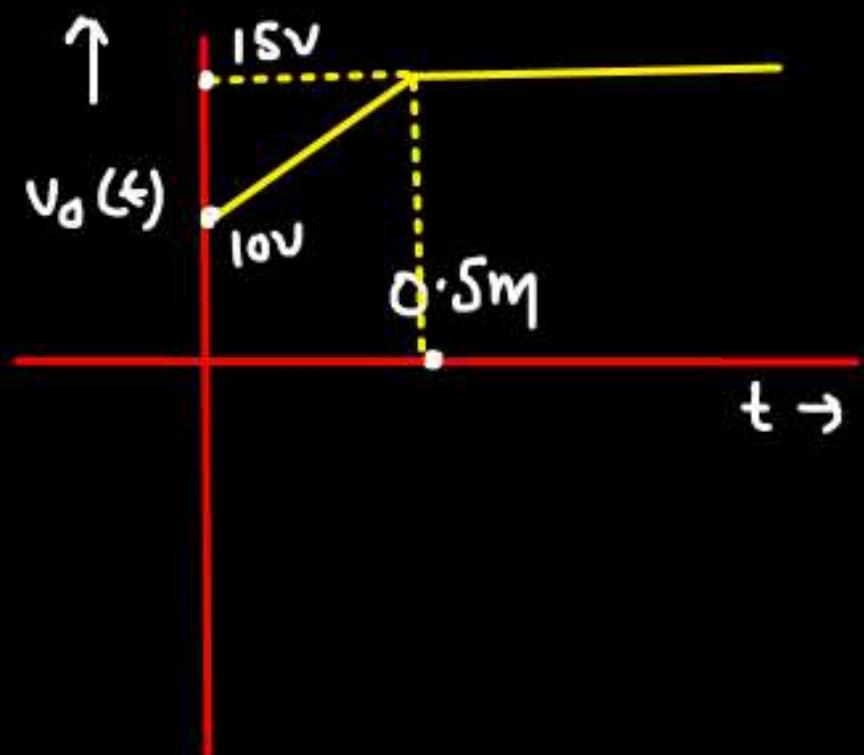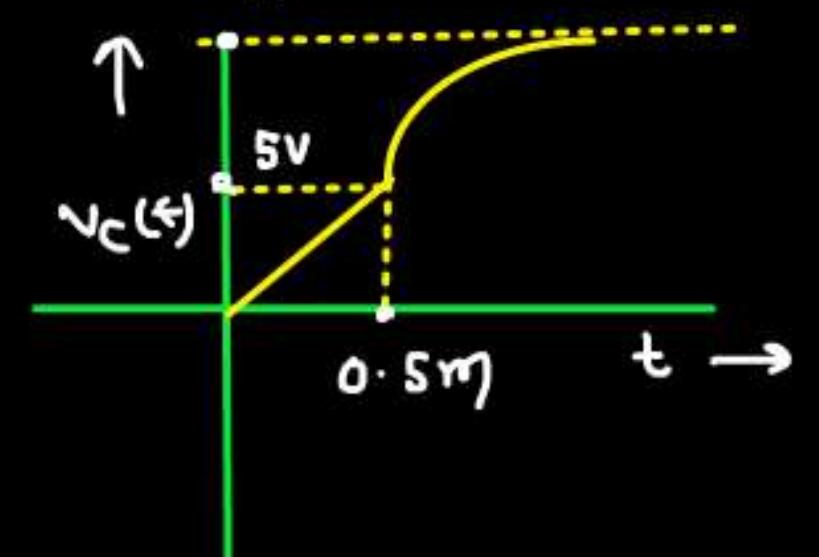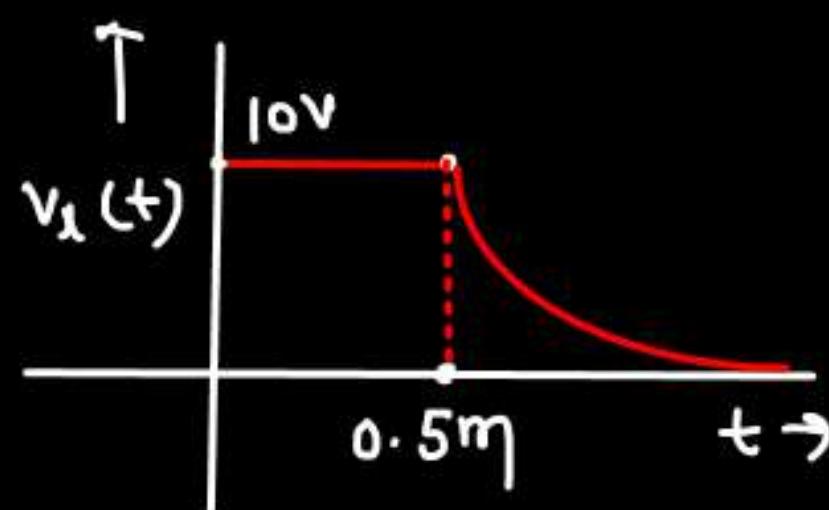

## Differentiator:-

Frequency response:-

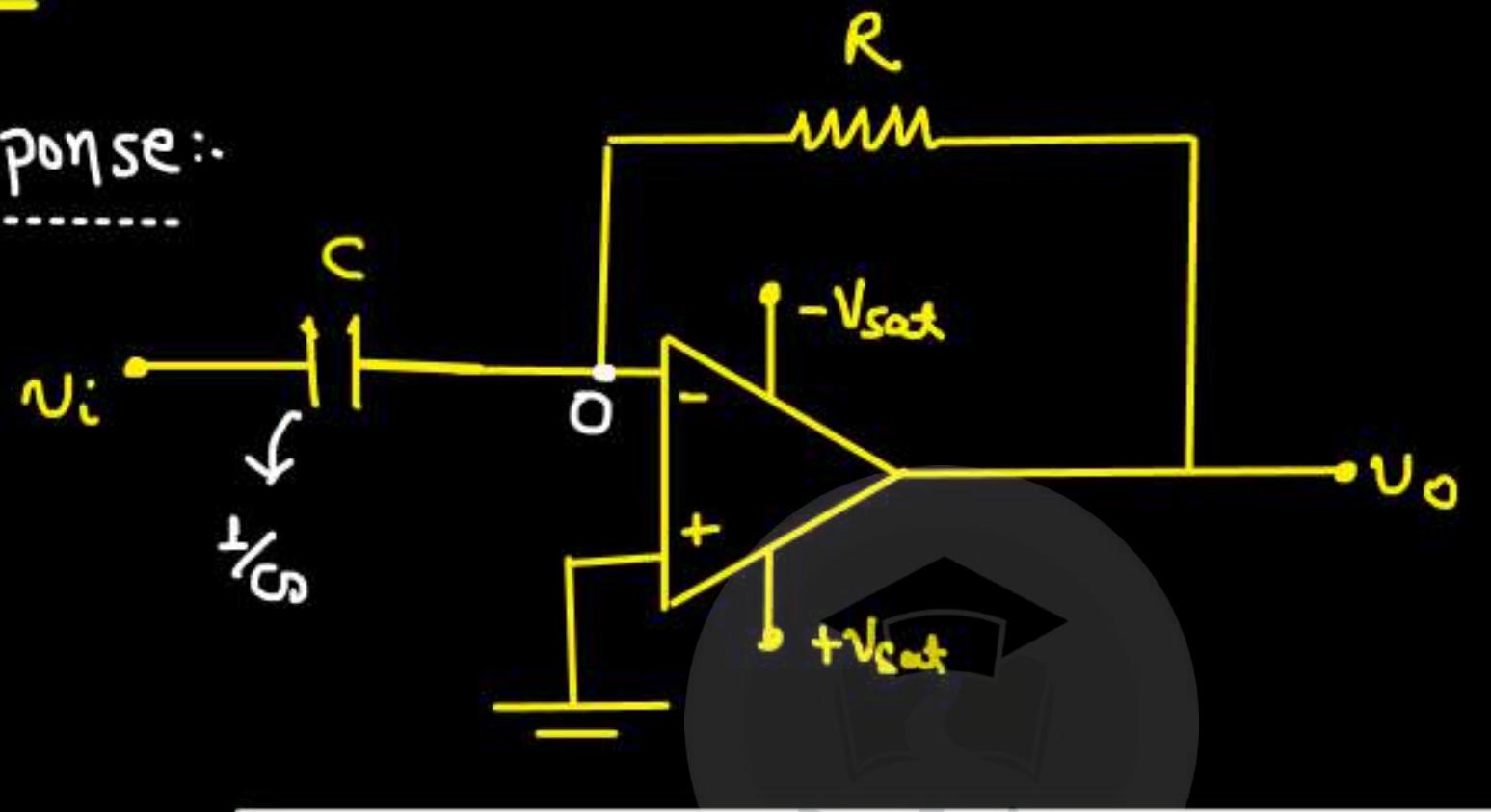

$$\frac{V_o(s)}{V_i(s)} = -SRC$$

Prefusion

$$\frac{V_o(s)}{V_i(s)} = -\frac{R}{1/C} = -RC = T(s)$$

$$\omega_L = 0$$


$$\omega_P = \infty$$

$$V_o(s) = -SRC \times V_i(s)$$

$$|T(j\omega)| = \omega RC$$

$$V_o(t) = -RC \frac{d}{dt} V_i(t)$$

→ acting as differentiator

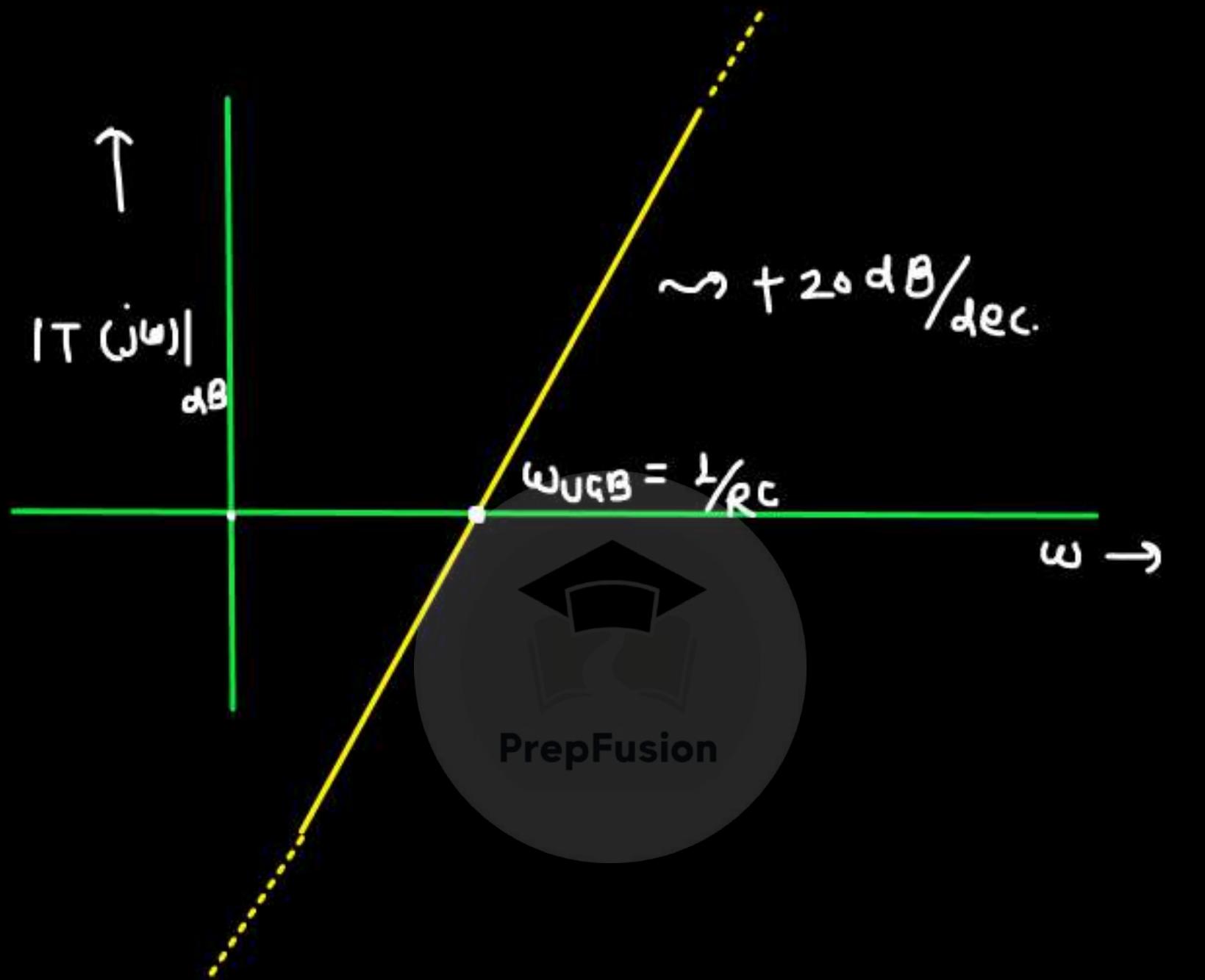


PrepFusion

## Draw back :-

- ↳ Very High gain at High freq.  
(High freq. Noise will be amplified)

## Practical Differentiator:-

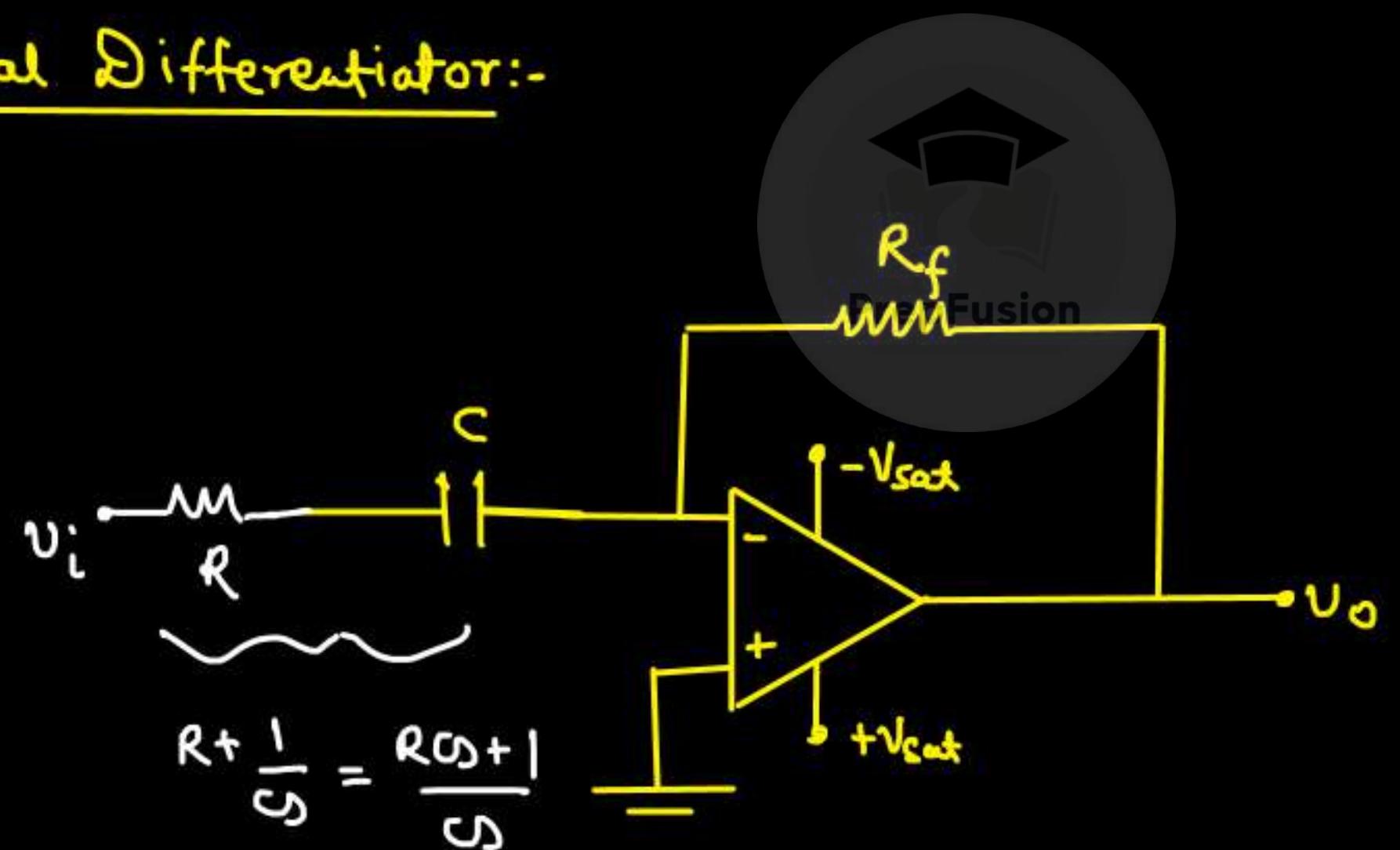


$$\frac{V_o(s)}{V_i(s)} = \frac{-R_f C s}{R C s + 1} = T(s)$$

$$\omega_z = 0$$


$$\omega_p = \frac{1}{RC}$$

$$|T(j\omega)| = \frac{\omega R_f C}{\sqrt{\omega^2 R^2 C^2 + 1}}$$


$$|T(j\infty)| = \frac{R_f}{R}$$

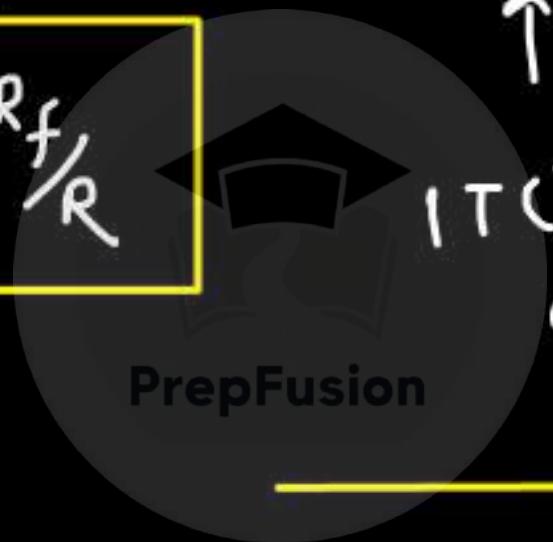

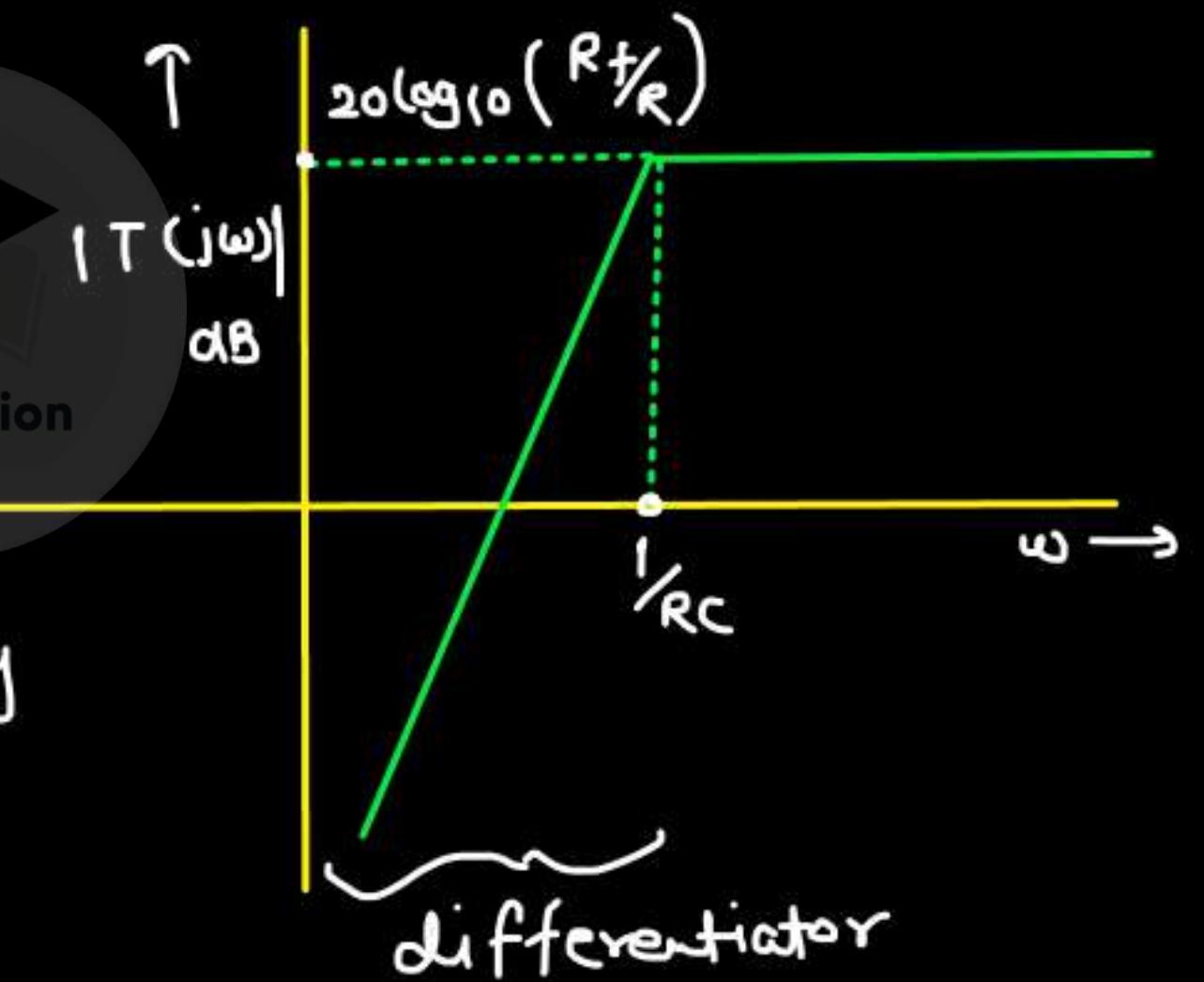→ we will try to reduce High frequency noise more.



## Modified Practical Differentiator :-

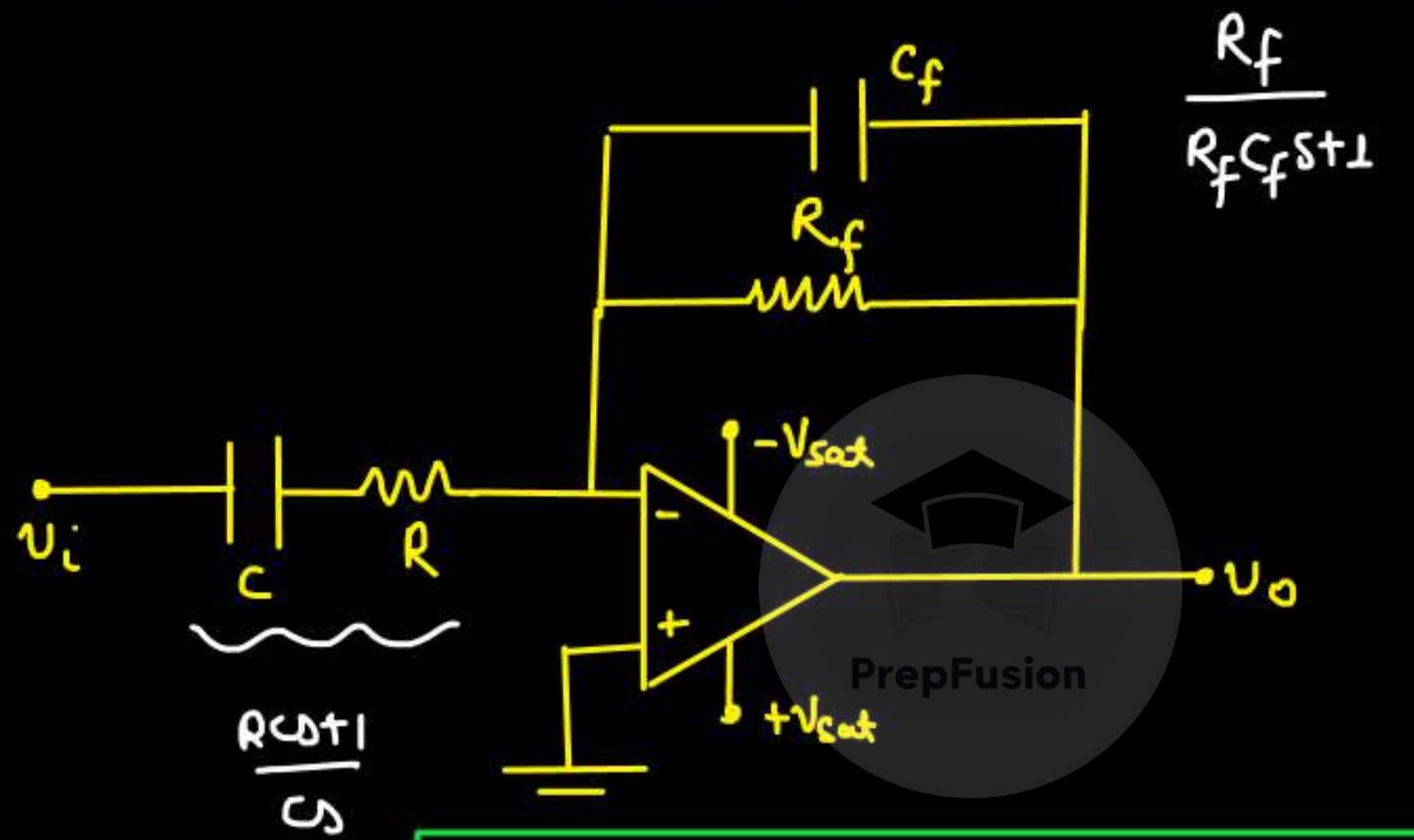

$$\frac{R_f}{R_f C_f s + 1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{-R_f}{R_f C_f s + 1}}{\frac{RCs+1}{s}} = \frac{-R_f s}{(R_f C_f s + 1)(R C s + 1)}$$

$$T(s) = \frac{-R_f Cs}{(R_f C_f s + 1)(R C s + 1)}$$


$$\omega_z = 0$$

$$\omega_{P_1} = \frac{1}{RC}$$


$$\omega_{P_2} = \frac{1}{R_f C_f}$$

$$|T(j\infty)| = 0$$


[Generally  $R_f C_f < R C$ ]

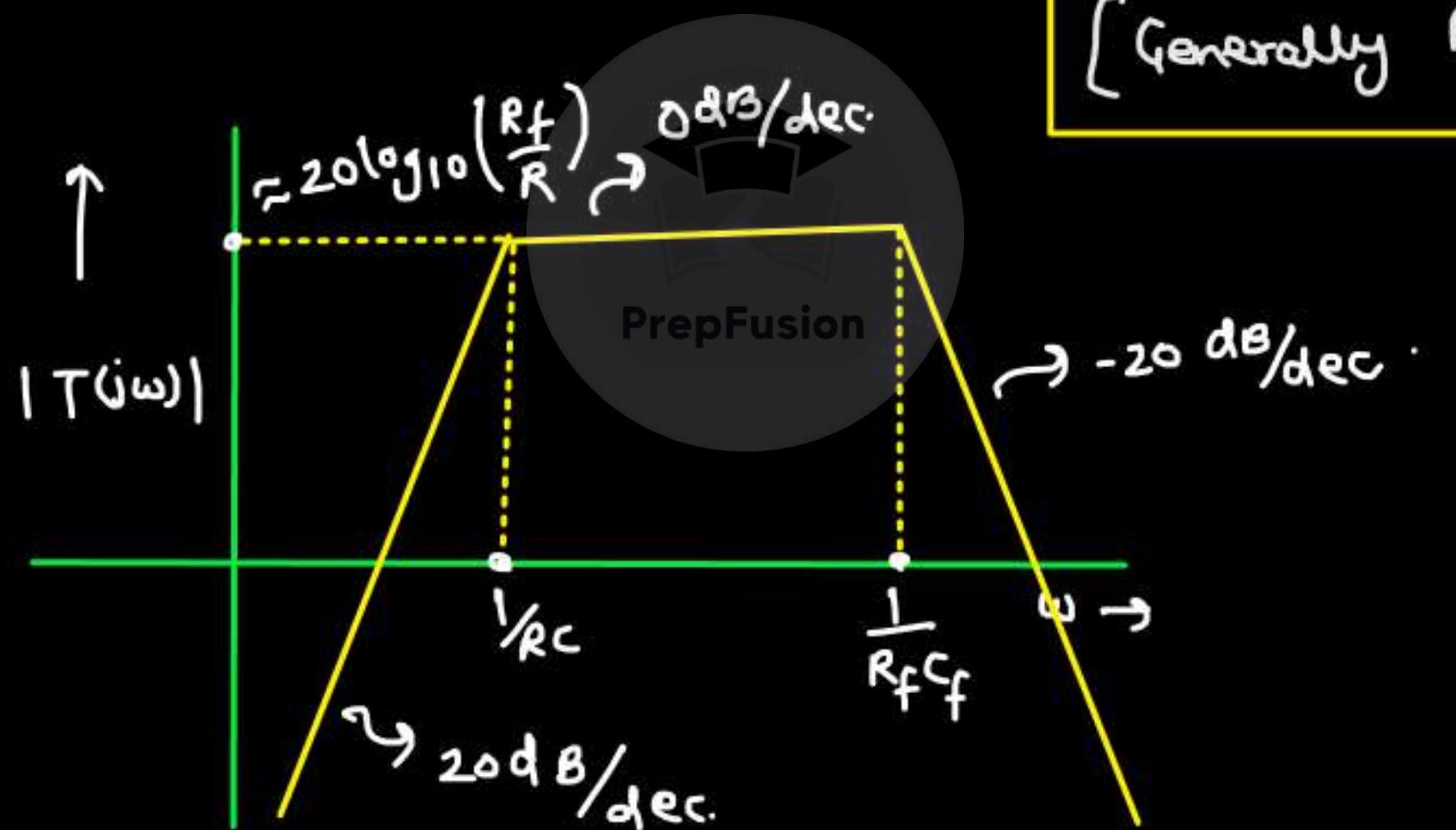

## Time domain analysis:-

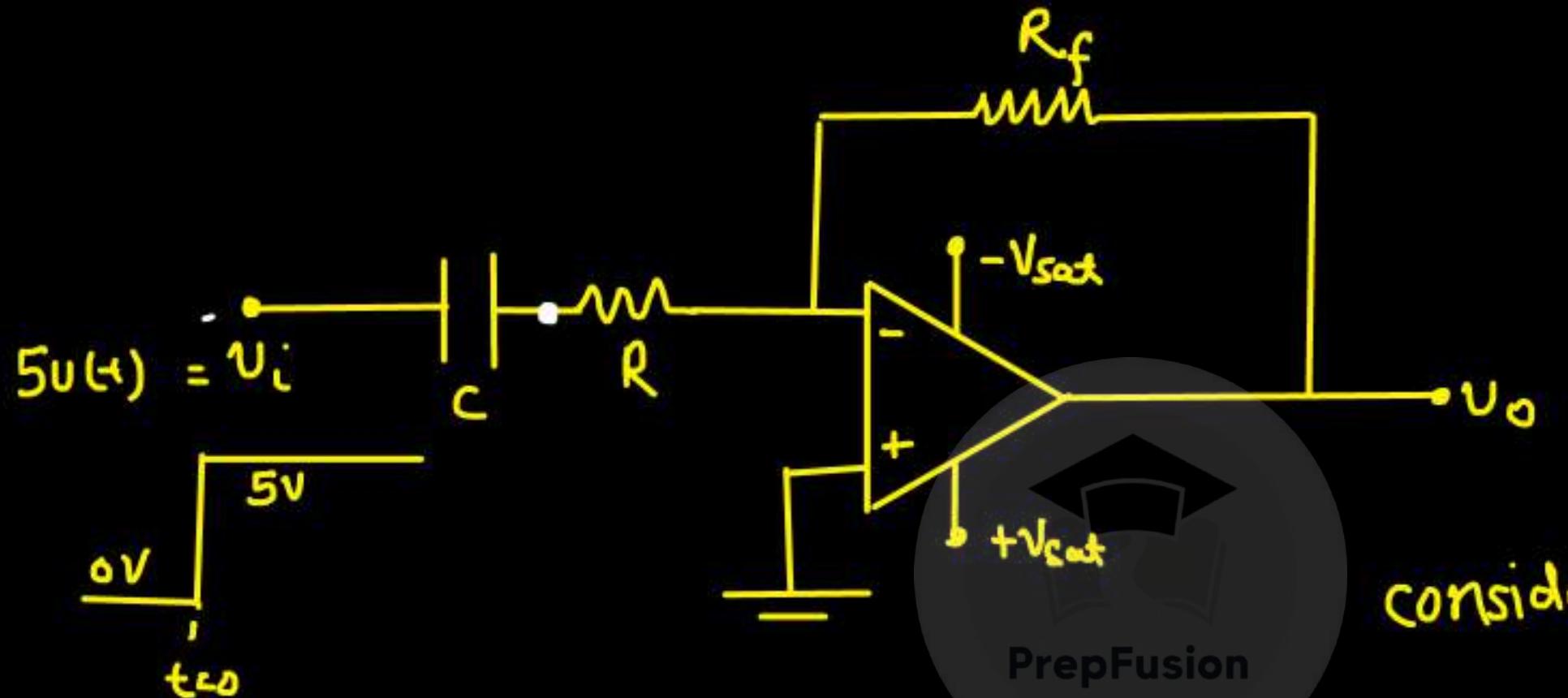


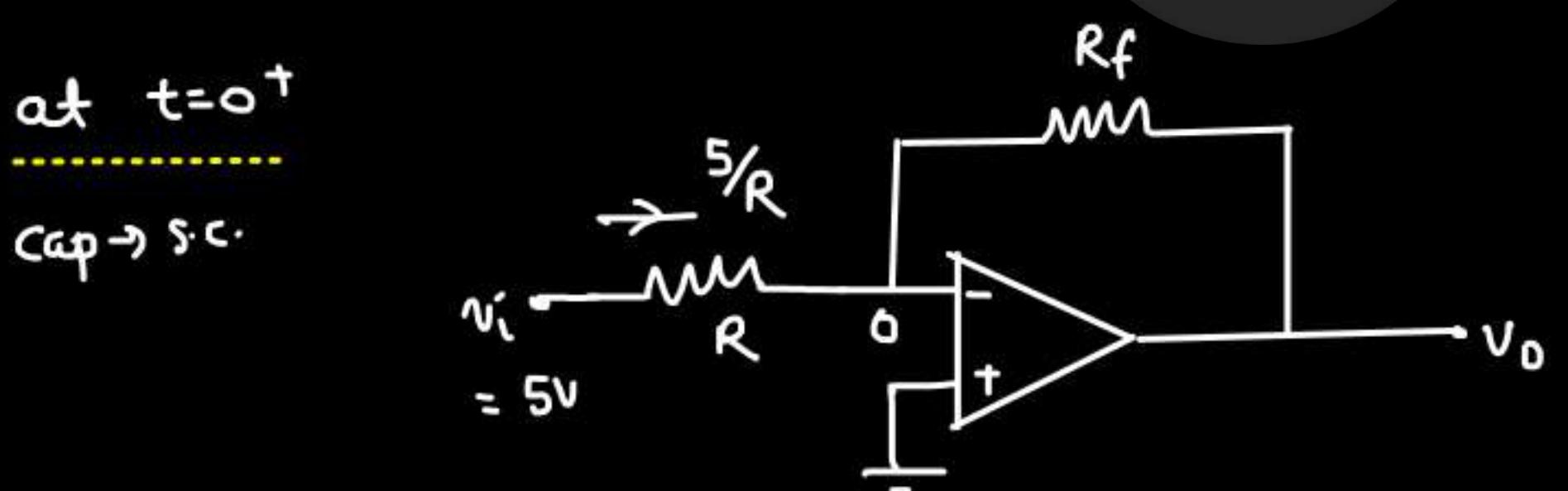consider  $\pm V_{sat}$  to be very High.




$$V_o(0^+) = -\frac{R_f}{R} \times 5$$

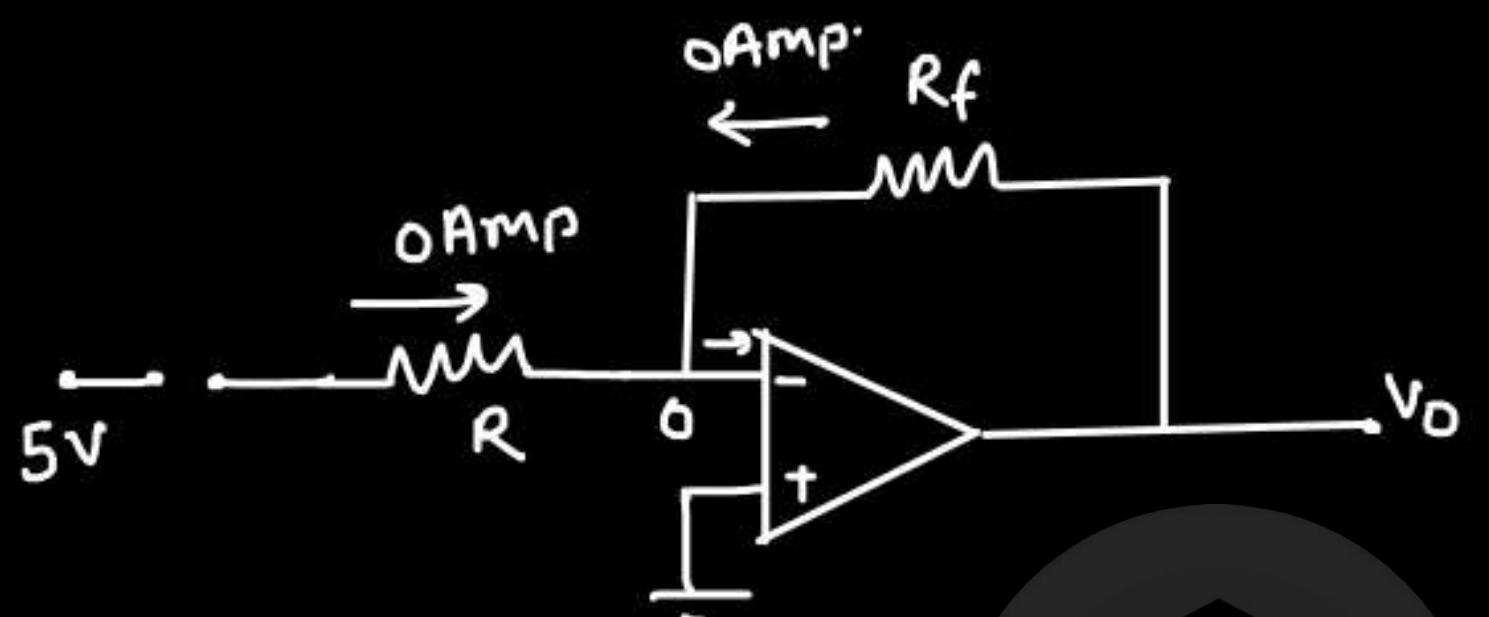
at  $t = \infty \rightarrow C_{ap} \Rightarrow 0 \cdot \infty$



$$V_o(\infty) = 0 \text{ V}$$

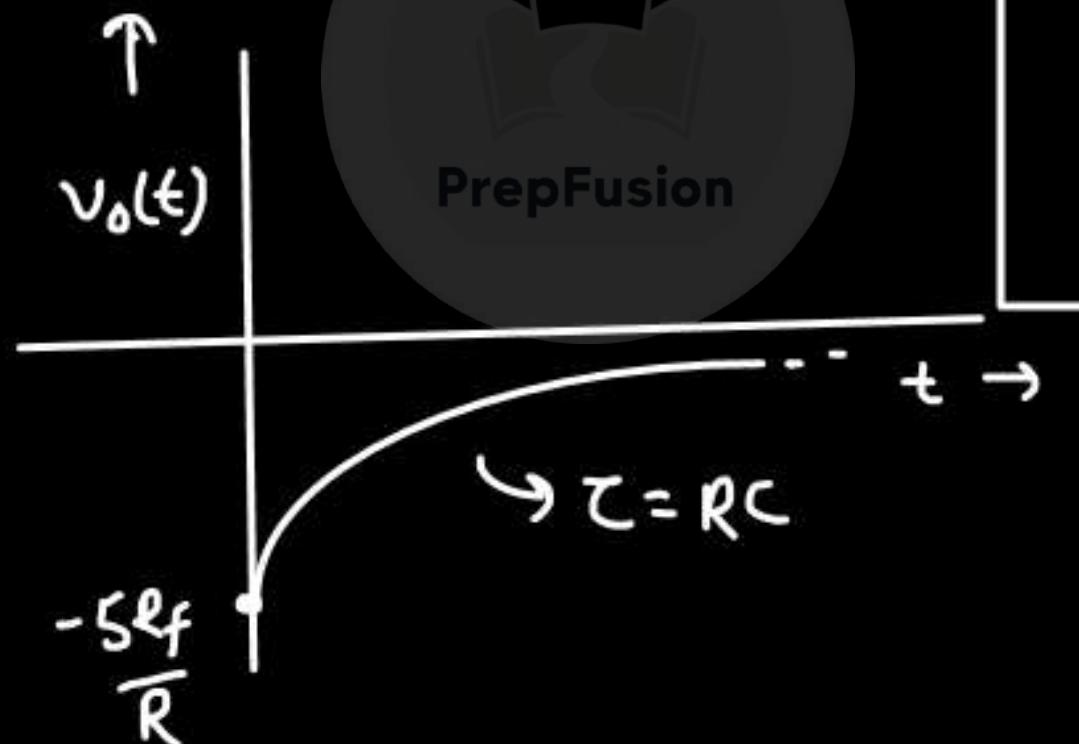
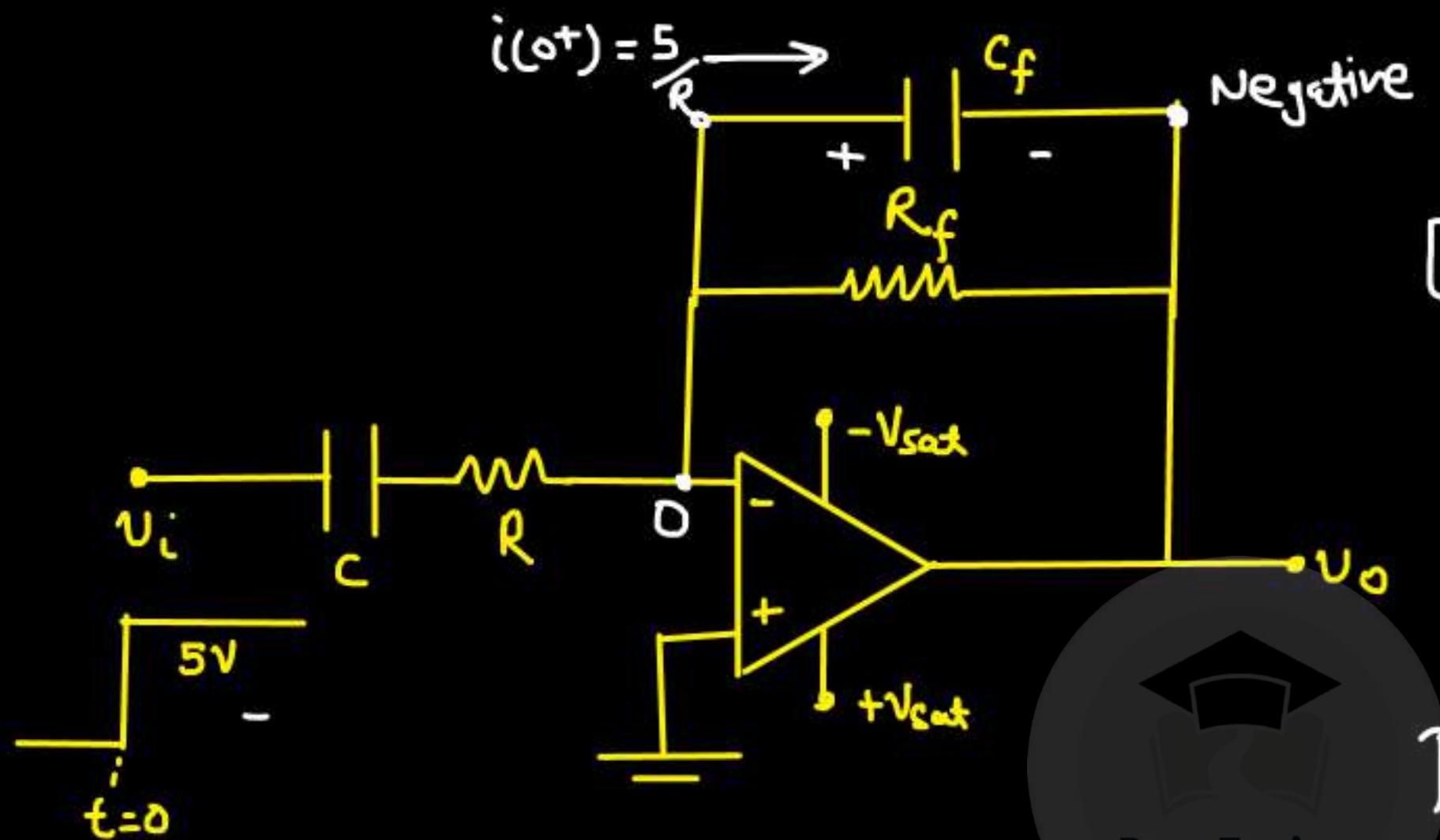
$$V_o(t) = -\frac{5R_f}{R} e^{-\frac{t}{RC}} U(t)$$




→ order = 2<sup>nd</sup> order


$$u_o(0^+) = 0V$$

$$u_o(\infty) = 0V$$

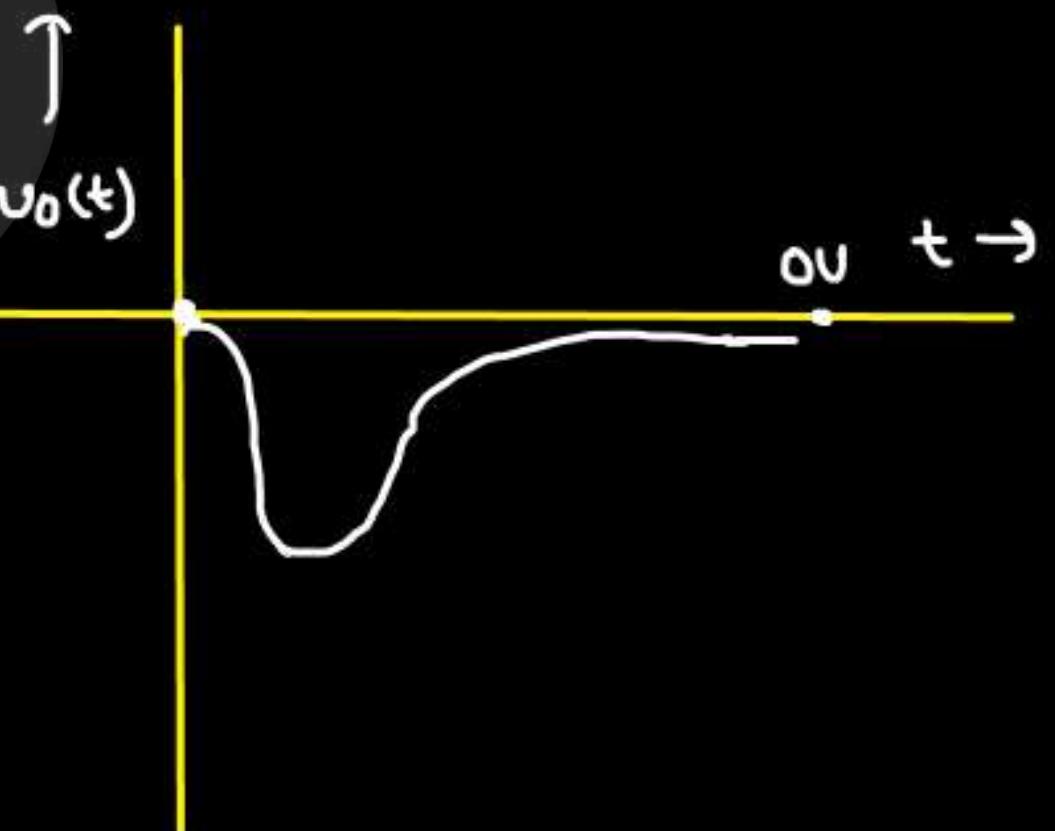Draw  $u_o$  waveform.  
[Considering  $\pm V_{sat}$  to  
be very High]


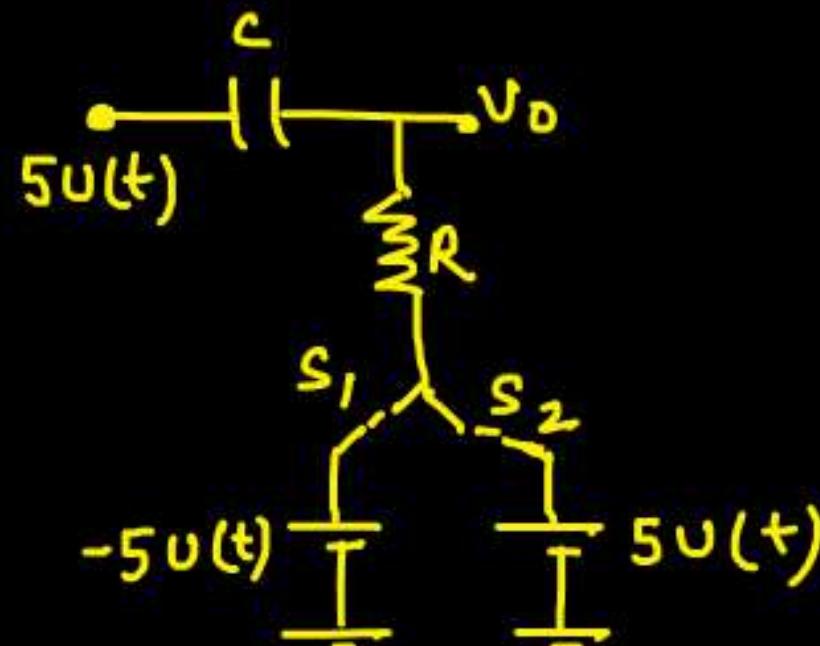
## ⇒ Interesting concept of Differentiator:-




initially switch  $S_1$  is closed and switch  $S_2$  is open.

at time  $t = RC \ln(2)$ , switch  $S_1$  is opened and  $S_2$  is closed.

Draw  $v_o$  waveform.

PrepFusion

$$\rightarrow 0 < t < RC \ln(2)$$

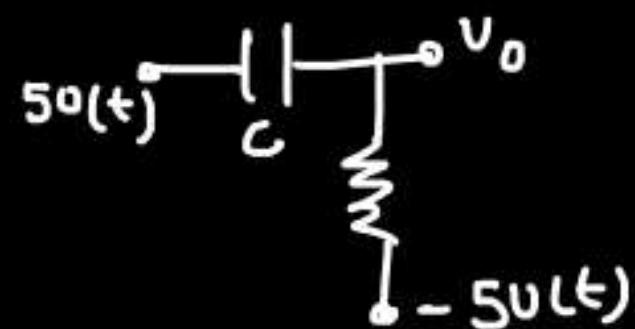


$$v_o(0^+) = 5V$$


$$v_o(\infty) = -5V$$

$$v_o(t) = -5 + 10 e^{-t/RC}$$

$$v_o(RC \ln 2) = 0$$

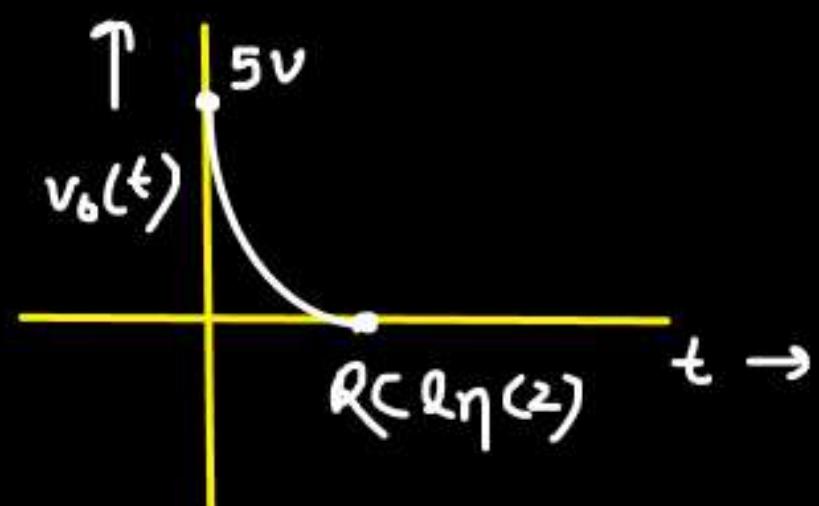


$$t > RC \ln(2)$$

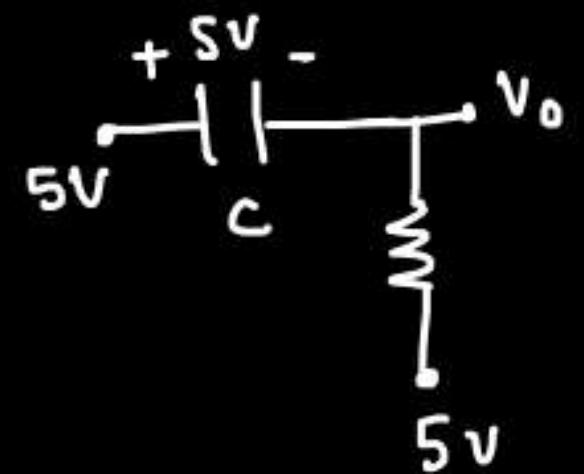

$$v_o(RC \ln 2) = 0$$

$$v_o(\infty) = 5V$$

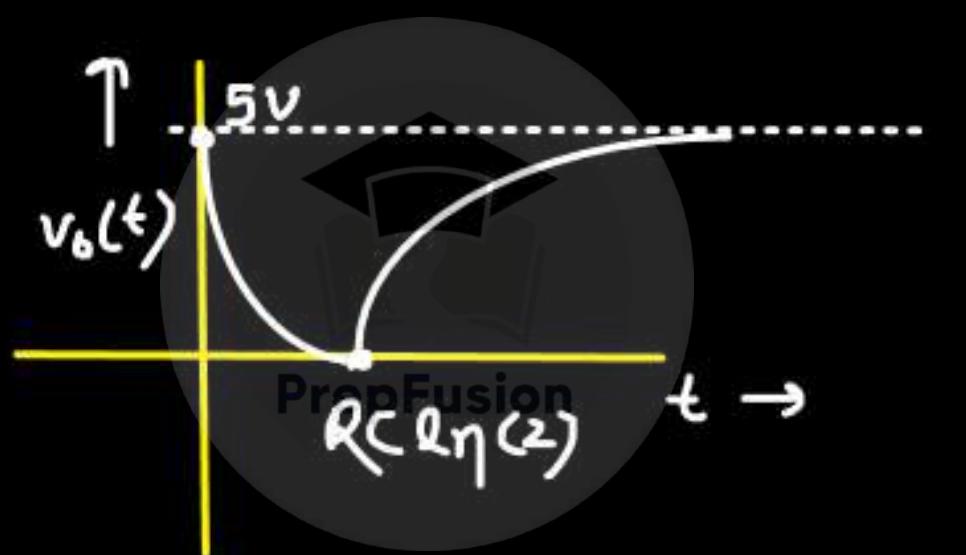





- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

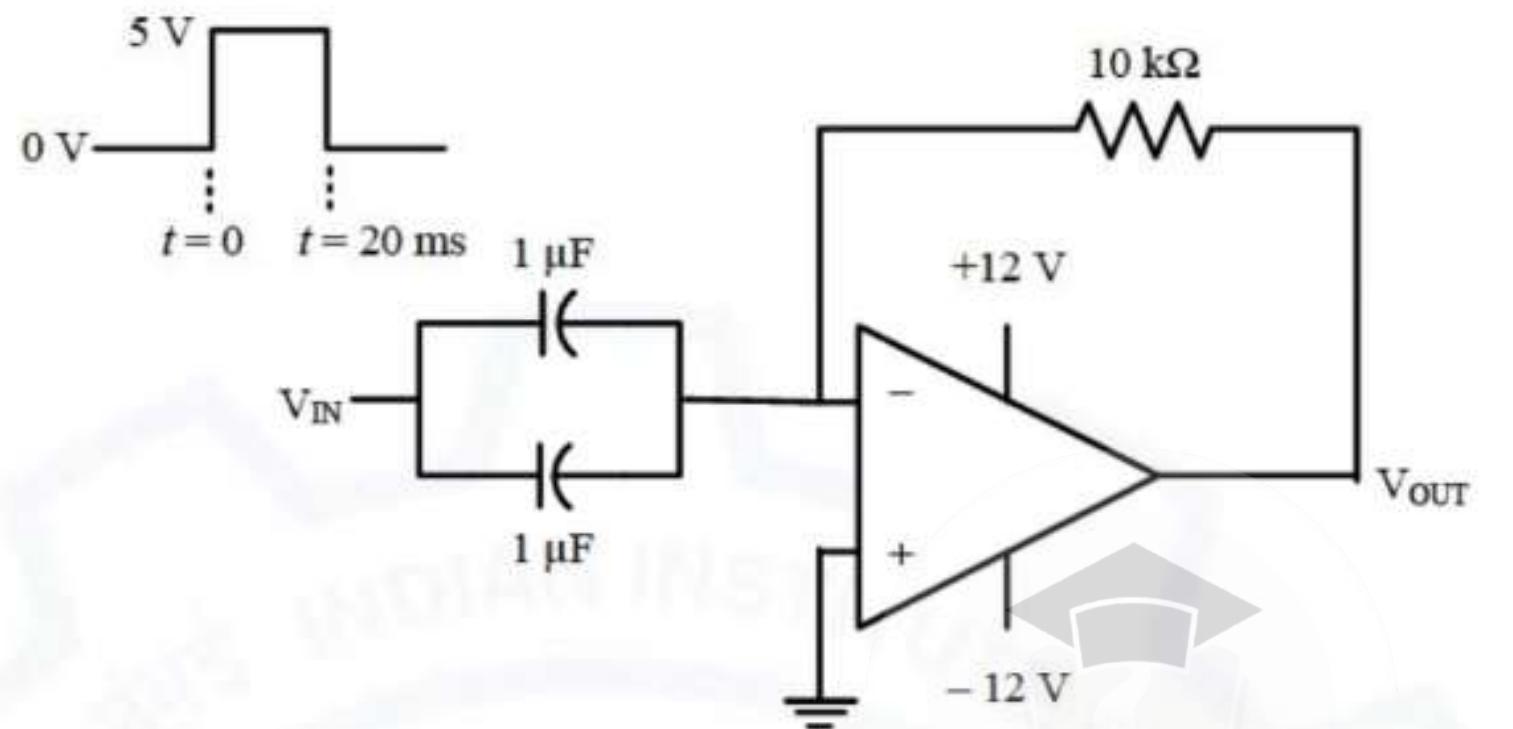Q.45

A circuit with an ideal OPAMP is shown in the figure. A pulse  $V_{IN}$  of 20 ms duration is applied to the input. The capacitors are initially uncharged.



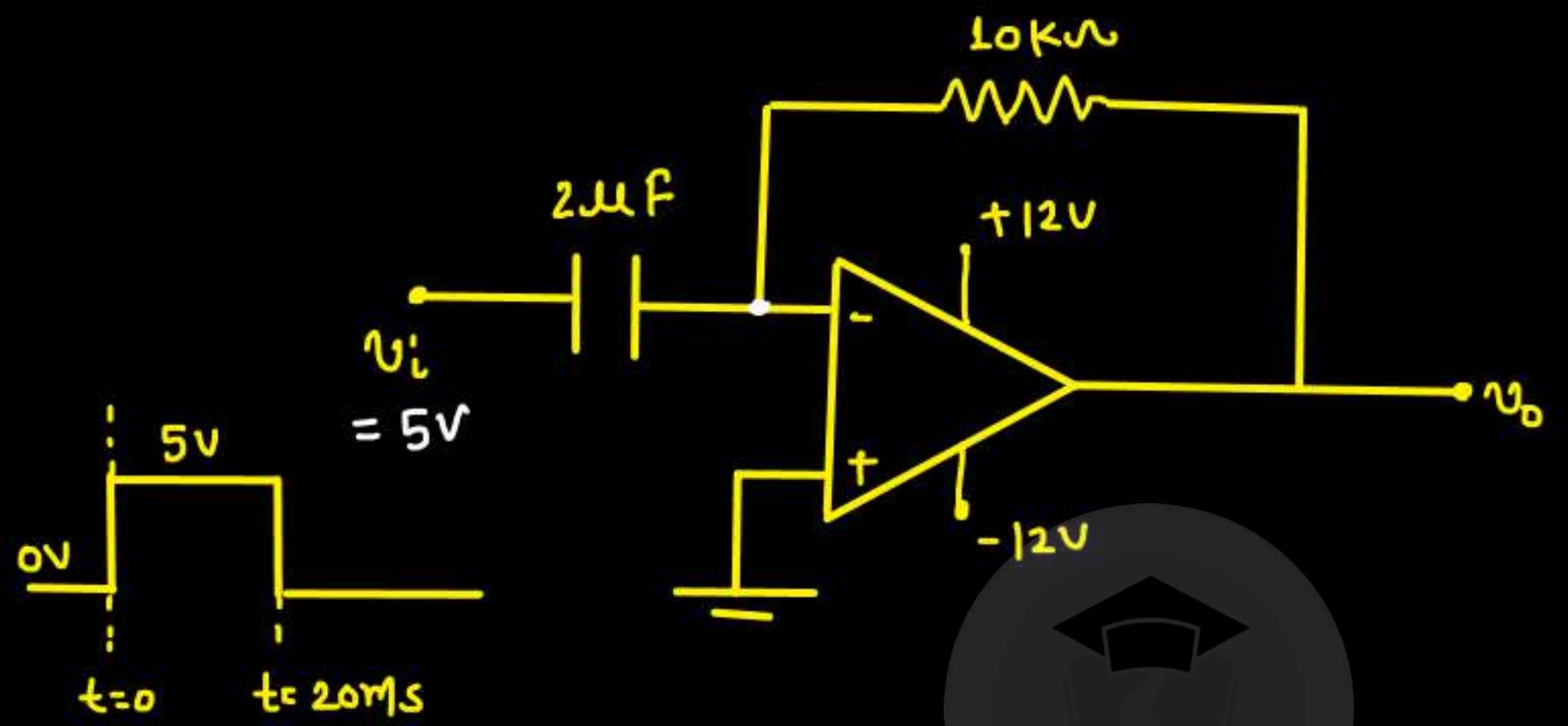
The output voltage  $V_{OUT}$  of this circuit at  $t = 0^+$  (in integer) is \_\_\_\_\_ V.




$$v_x(t=0^+) = 5\text{V}^{\text{PrePfusion}}$$

$$v_o(t=0^+) = -12\text{V}$$

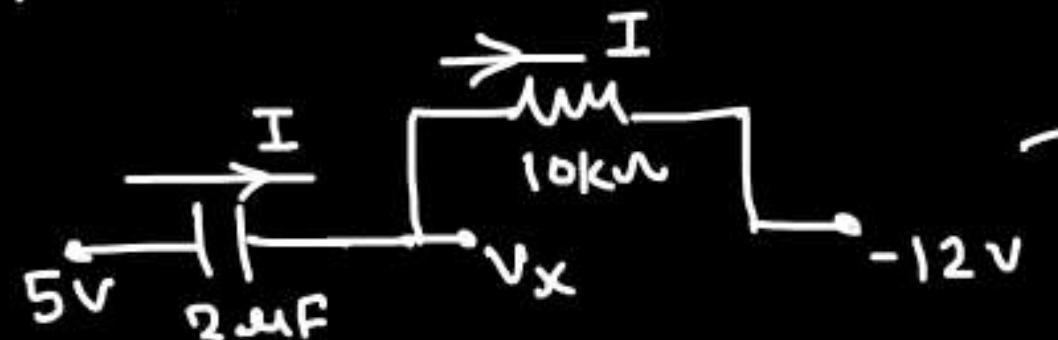O/P saturated  $\Rightarrow$  virtual short not valid



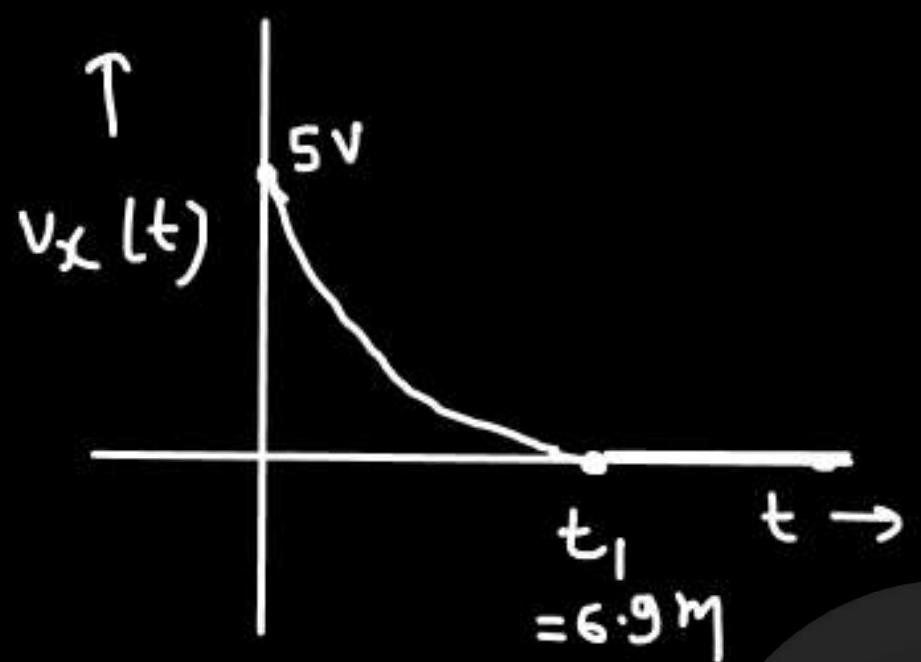first order series RC ckt  
 $v_x(0^+) = 5\text{V}$     $v_x(\infty) = -12\text{V}$





$$v_x(t) = -12 + 17 e^{-t/20m}$$

$$v_x(t_1) = 0$$

$$t_1 = 20m \ln(17/12)$$

$$t_1 = 6.9m$$

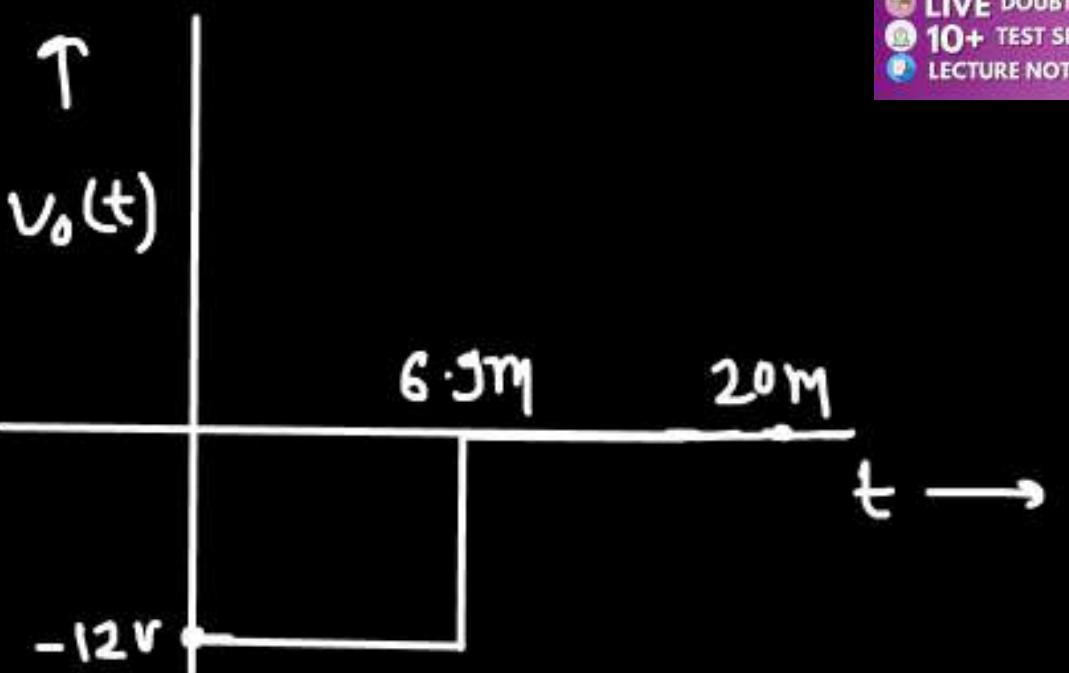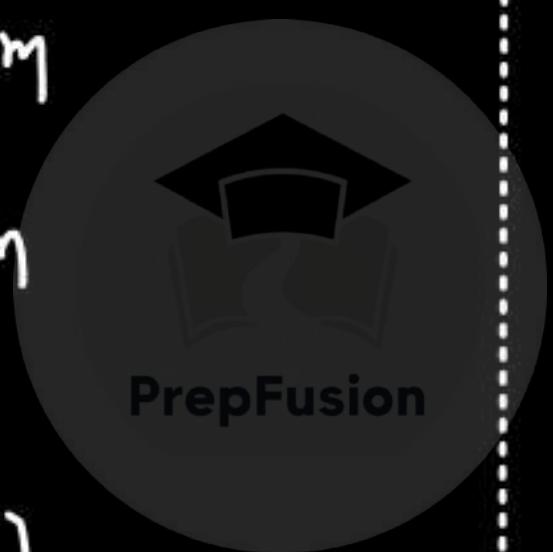$v_x$  stays  $\leftarrow$  forces  $\leftarrow$  o/p goes  $\leftarrow$   $v_x$  goes  $\leftarrow$  It will force  $v_x$   
at 0V  $\leftarrow$   $v_x$  to  $-12V$   $\leftarrow$   $-12V$   $\leftarrow$  to go to  $+12V$   
forever



For  $t > t_1 \Rightarrow v_x$  goes negative




o/p goes  $+12V$



It will force  $v_x$   
to go to  $+12V$

for  $t > 20\text{ms}$

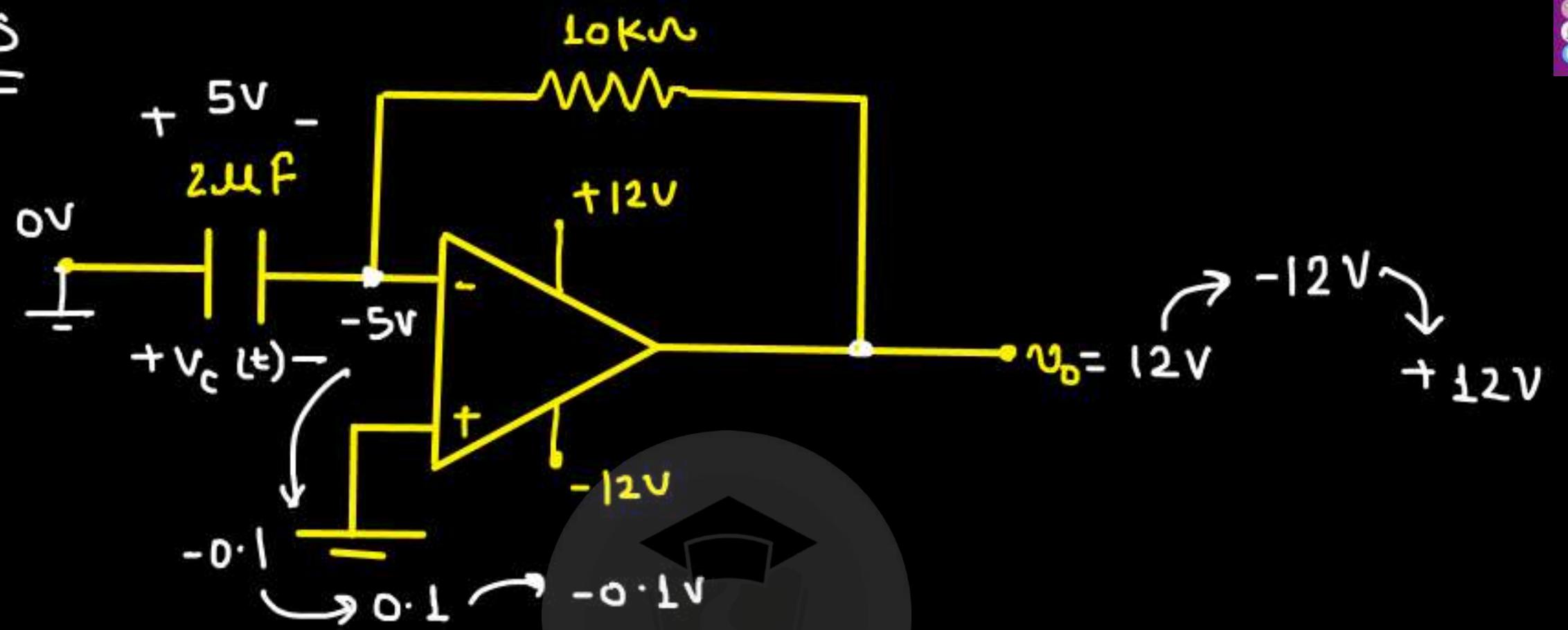


$$V_c(20\text{ms}^-) = 5\text{V}$$

$$V_c(20\text{ms}^+) = 5\text{V}$$




$$V_o(20\text{ms}^+) = +12\text{V}$$

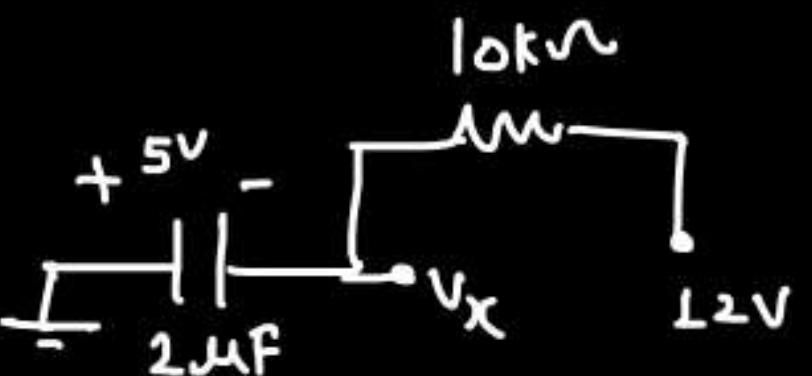O/P saturated  $\Rightarrow$  virtual short not valid



$$V_x(20\text{ms}^+) = -5\text{V}$$


$$V_x(\infty) = 12\text{V}$$

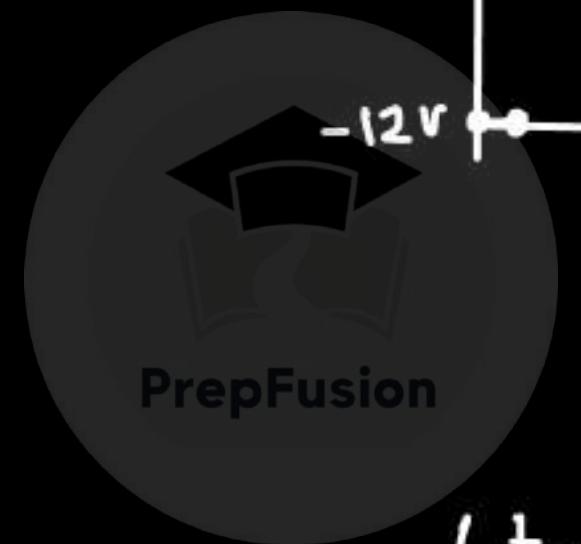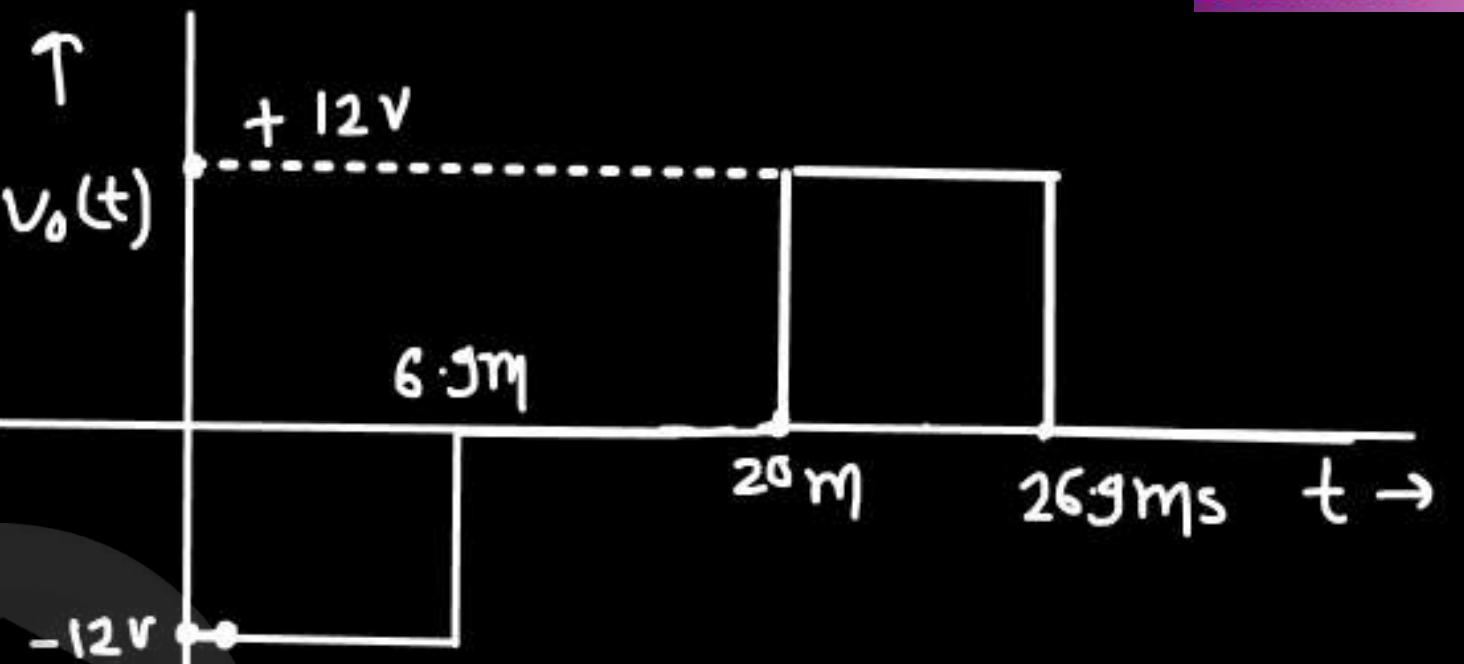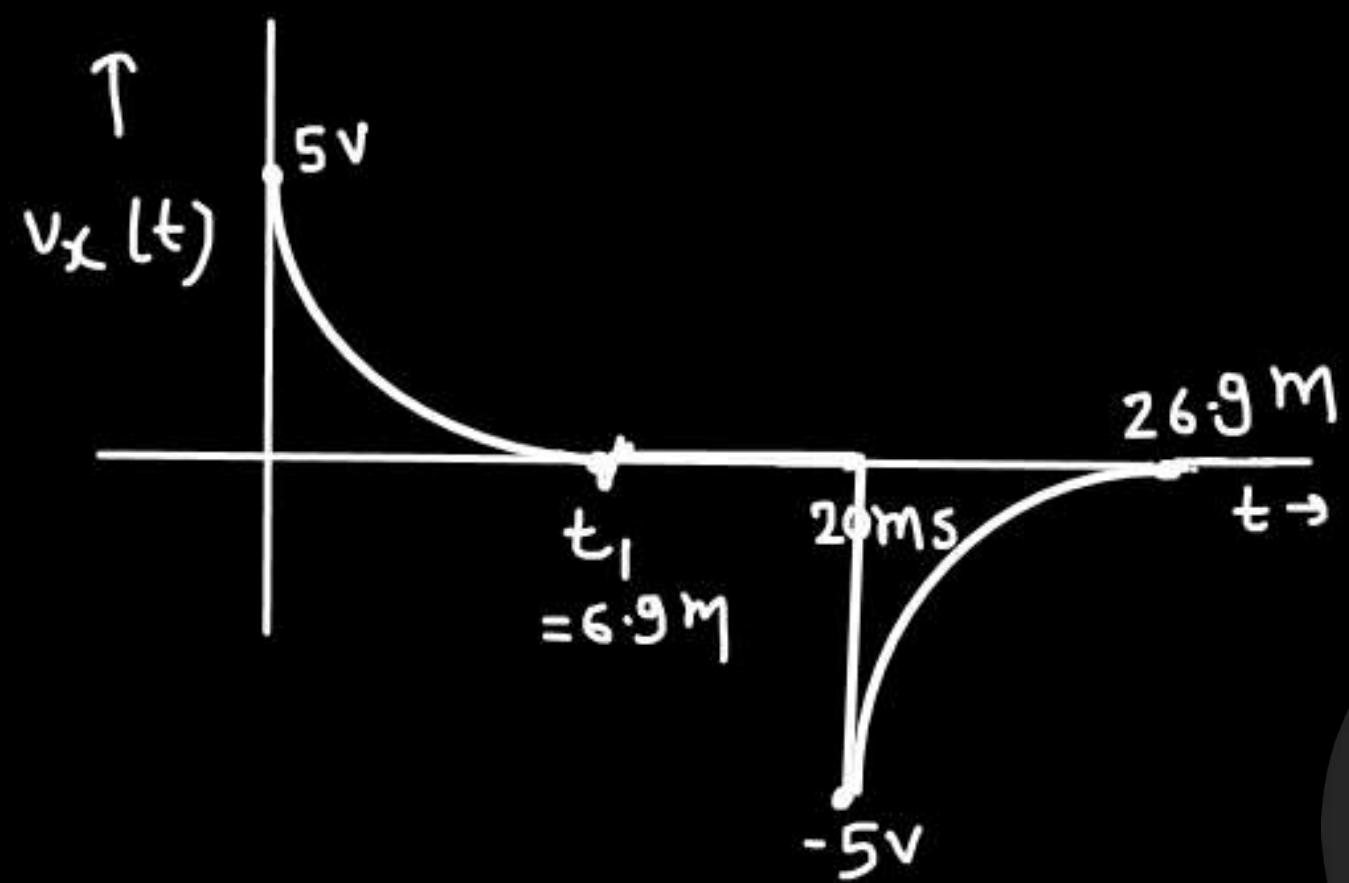


$$v_C(t) = 12 - 17 e^{-(t-20\text{ms})/20\text{ms}}$$

$$\text{at } v_C(t_2) = 0$$

$$t_2 = 26.9 \text{ ms sec}$$

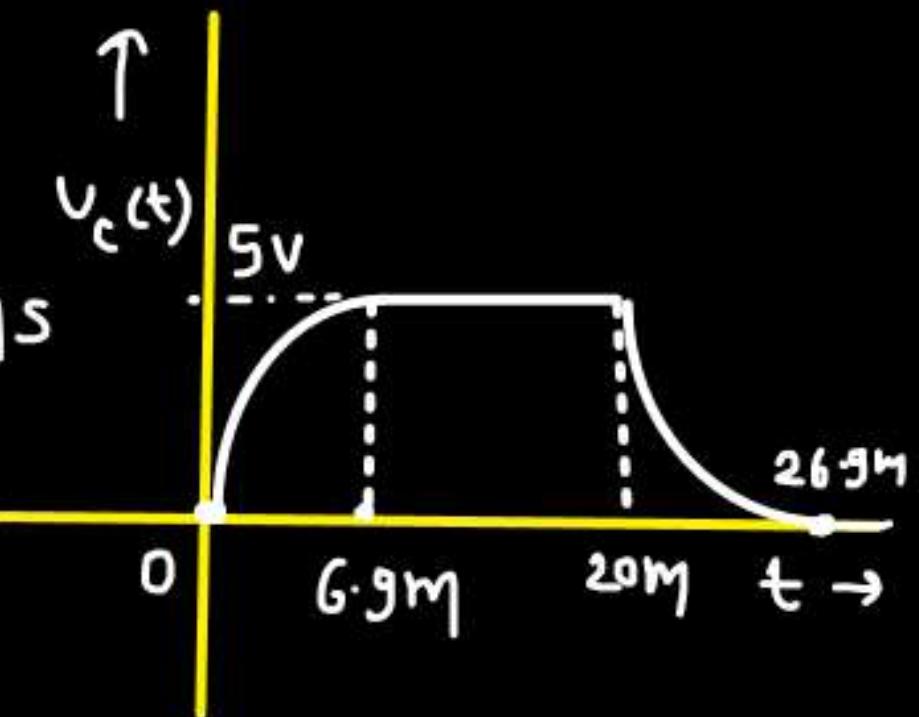


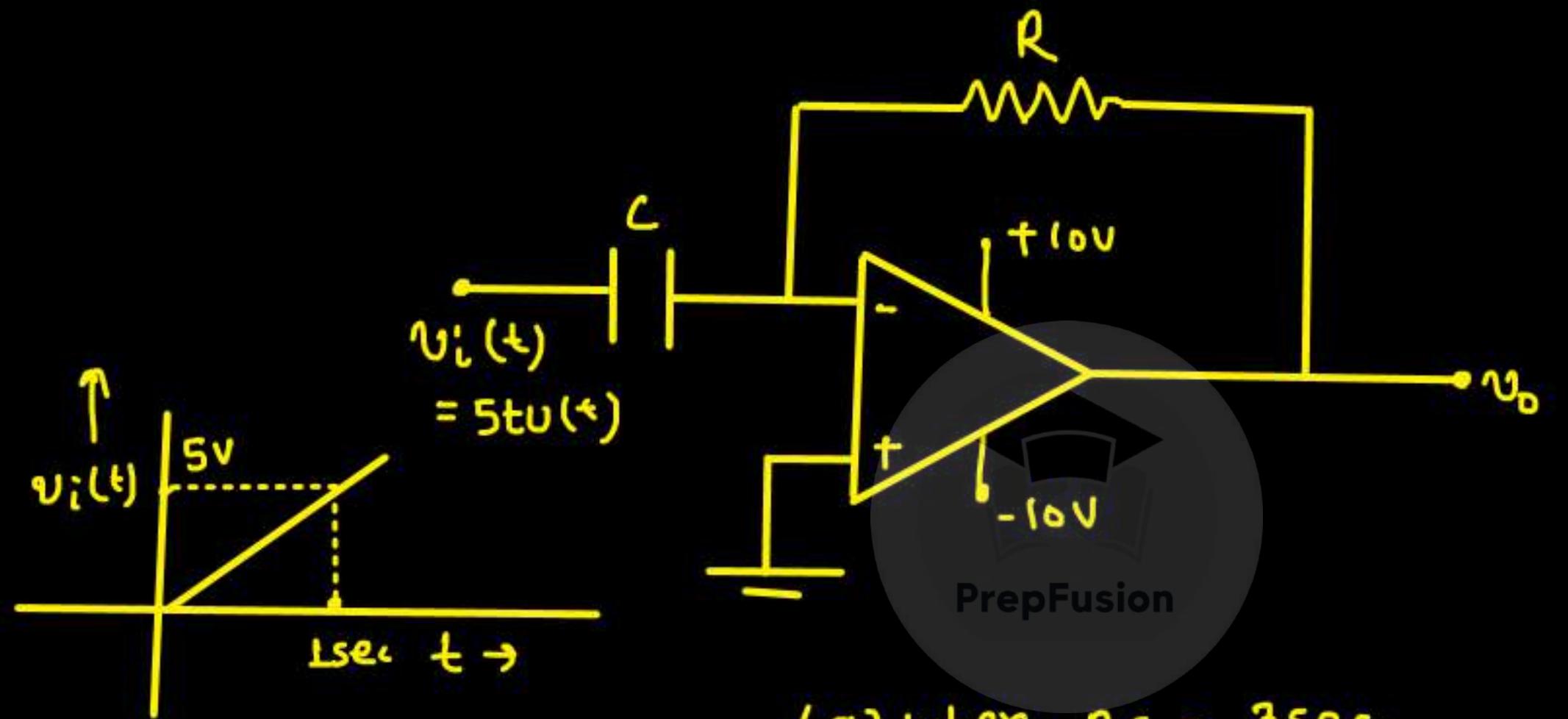Q. For the given ckt, find steady state o/p voltage.



(a) when  $RC = 3\text{ sec}$ .

(b) when  $RC = 1\text{ sec}$ .

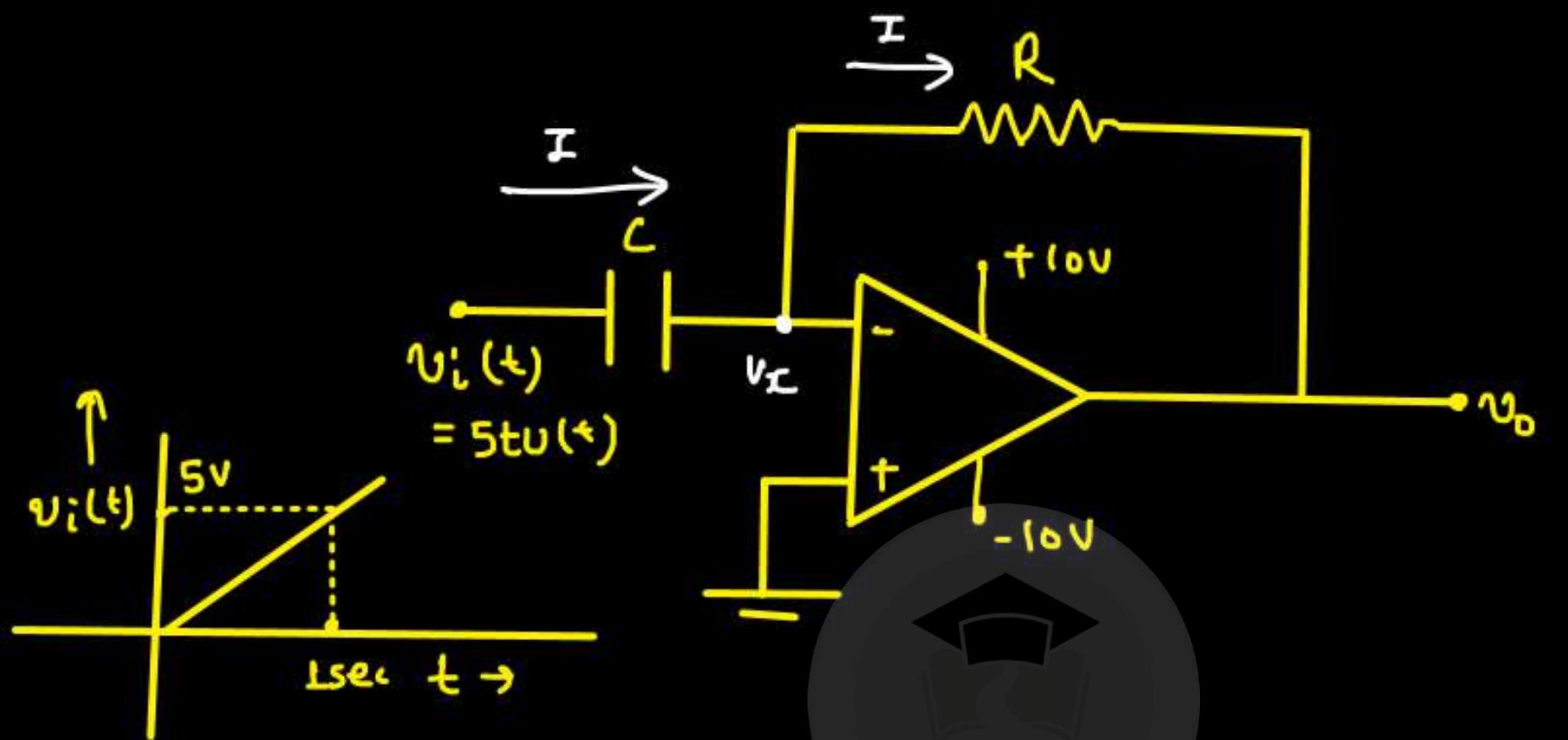


at  $t = 0^+$


$$v_x(0^+) = 0^+ = v_- \quad \Rightarrow \quad v_o(0^+) = -v_{sat} = -10V$$

$$v_t = 0$$

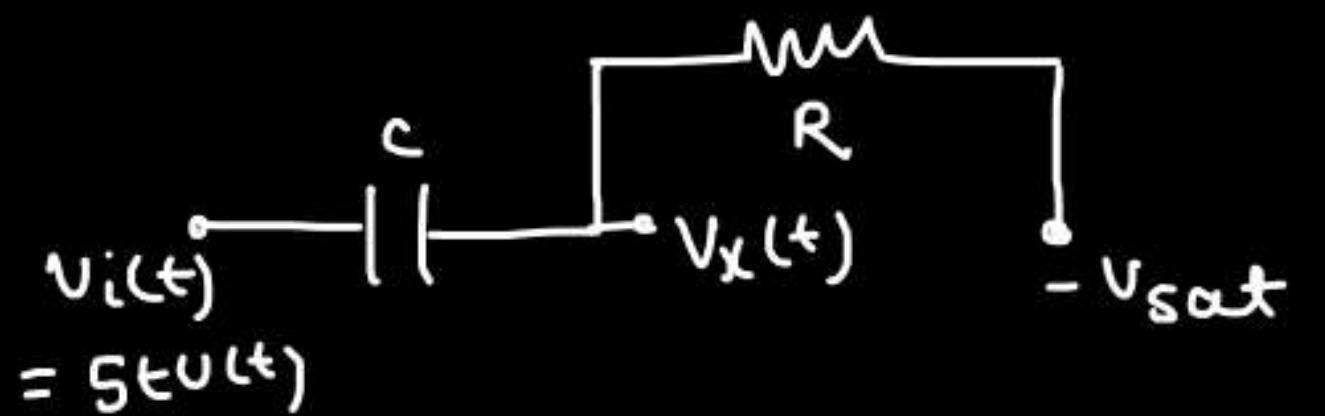$\Rightarrow$  o/p saturated  $\Rightarrow$  virtual short Not Valid



III

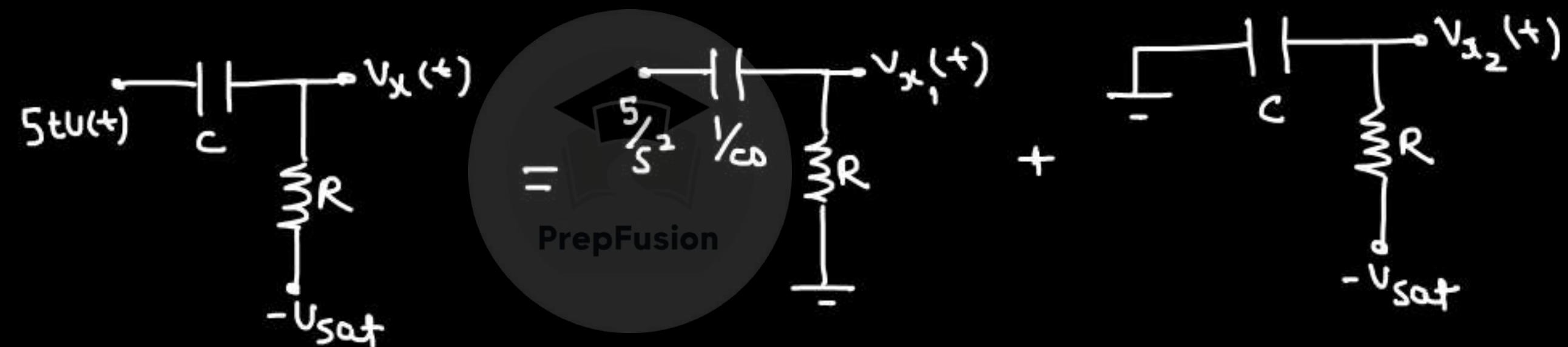

$$v_{x_1}(s) = \frac{RC}{RC + 1} \times \frac{5}{s^2}$$

$$= \frac{5RC}{s(RC + 1)}$$

$$v_{x_2}(0^+) = 0V$$

$$v_{x_2}(\infty) = -V_{SAT}$$

$$V_{X_1}(s) = \frac{5RC}{s(sRC + L)} = \left[ \frac{1}{s} - \frac{RC}{sRC + L} \right] \times 5RC$$

$$V_{X_1}(s) = 5RC \left[ \frac{1}{s} - \frac{1}{s + \frac{1}{RC}} \right]$$

$$v_{x_1}(t) = 5RC \left[ 1 - e^{-\frac{t}{RC}} \right] u(t)$$

$$v_{x_2}(t) = -v_{sat} \left[ 1 - e^{-\frac{t}{RC}} \right] u(t)$$



PrepFusion

$$v_x(t) = [5RC - v_{sat}] \left[ 1 - e^{-\frac{t}{RC}} \right] u(t)$$

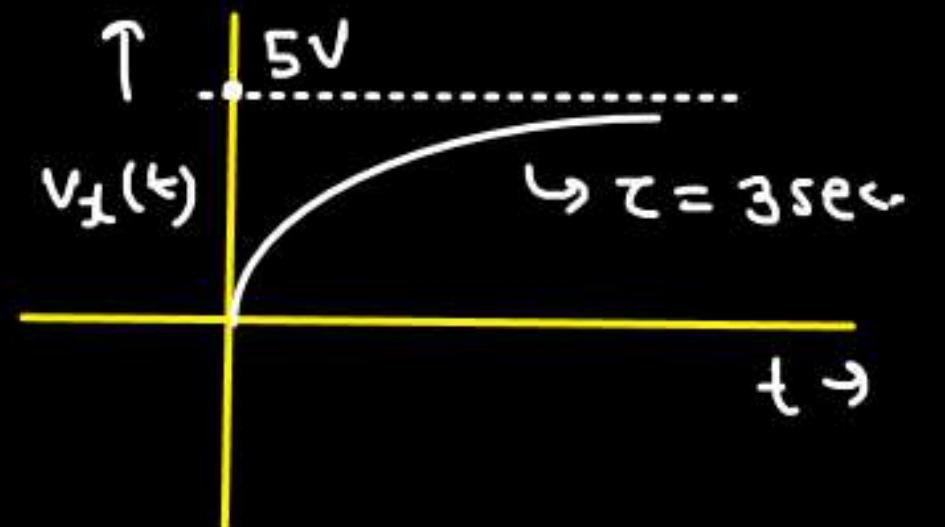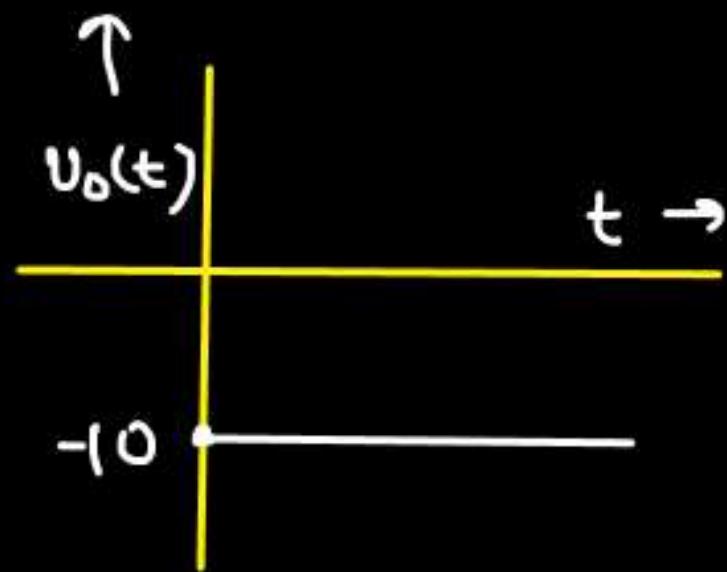(a)  $RC = 3\text{sec}$ .

$$v_x(t) = [15 - 10] \left[ 1 - e^{-\frac{t}{3}} \right] u(t)$$

$$v_x(t) = 5 \left( 1 - e^{-\frac{t}{3}} \right) u(t) \Rightarrow 0 \rightarrow 5$$





(b)  $RC = 1 \text{ sec.}$

$$v_x(t) = [5 - 10] [1 - e^{-t/1}] u(t)$$

$$v_x(t) = -5 (1 - e^{-t}) u(t) \Rightarrow 0 \rightarrow -5V$$

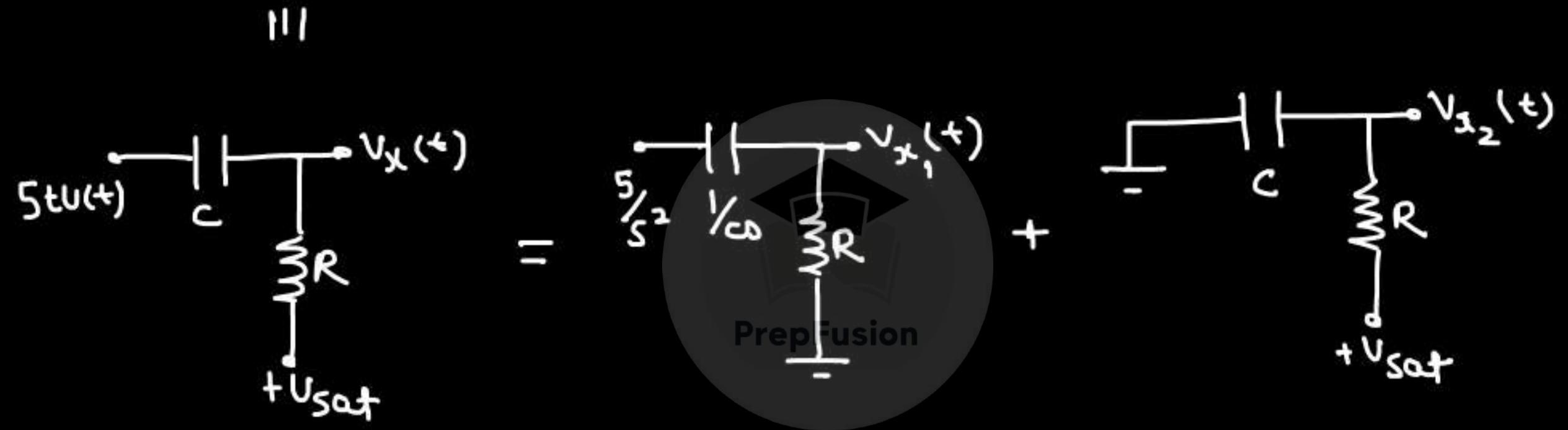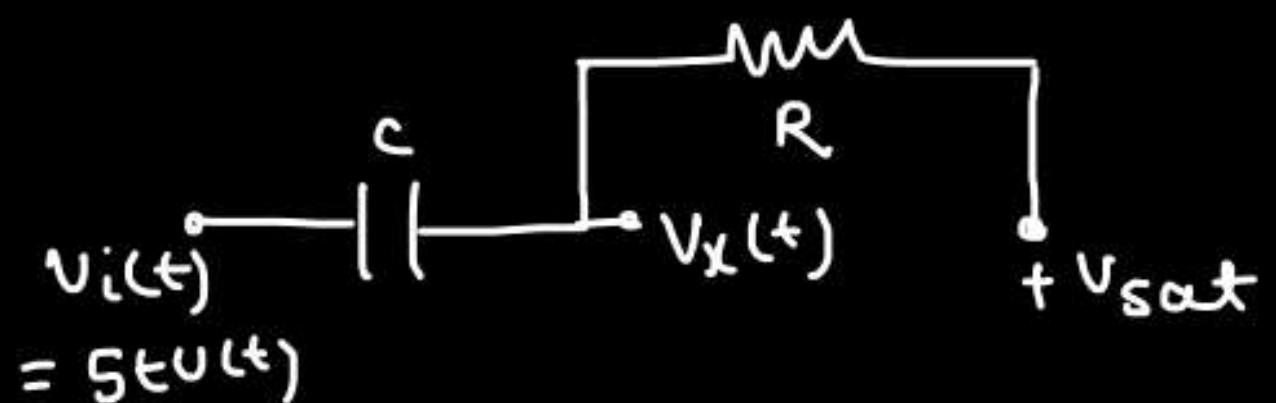$\Rightarrow @ t=0^+$  only o/p will move to  $+v_{sat}$ .



$$V_{x_1}(s) = \frac{RC}{RCs+1} \times \frac{5}{s^2}$$

$$\begin{aligned} V_{x_2}(0^+) &= 0V \\ V_{x_2}(\infty) &= +V_{sat} \end{aligned}$$

$$V_x(t) = [5RC + V_{sat}] [1 - e^{-t/RC}] u(t)$$


$$= \frac{5RC}{s(5RC+1)}$$

$$v_x(t) = 15 (1 - e^{-t}) v(t) \Rightarrow 0 \rightarrow 15V$$

O/P will immediately move to  $-V_{sat}$

$$v_x = \begin{cases} 0.1V & \text{upward arrow} \\ 0 & \text{square symbol} \\ -0.1V & \text{downward arrow} \end{cases}$$

$v_x$  node will be fixed @  $v_x = 0V$

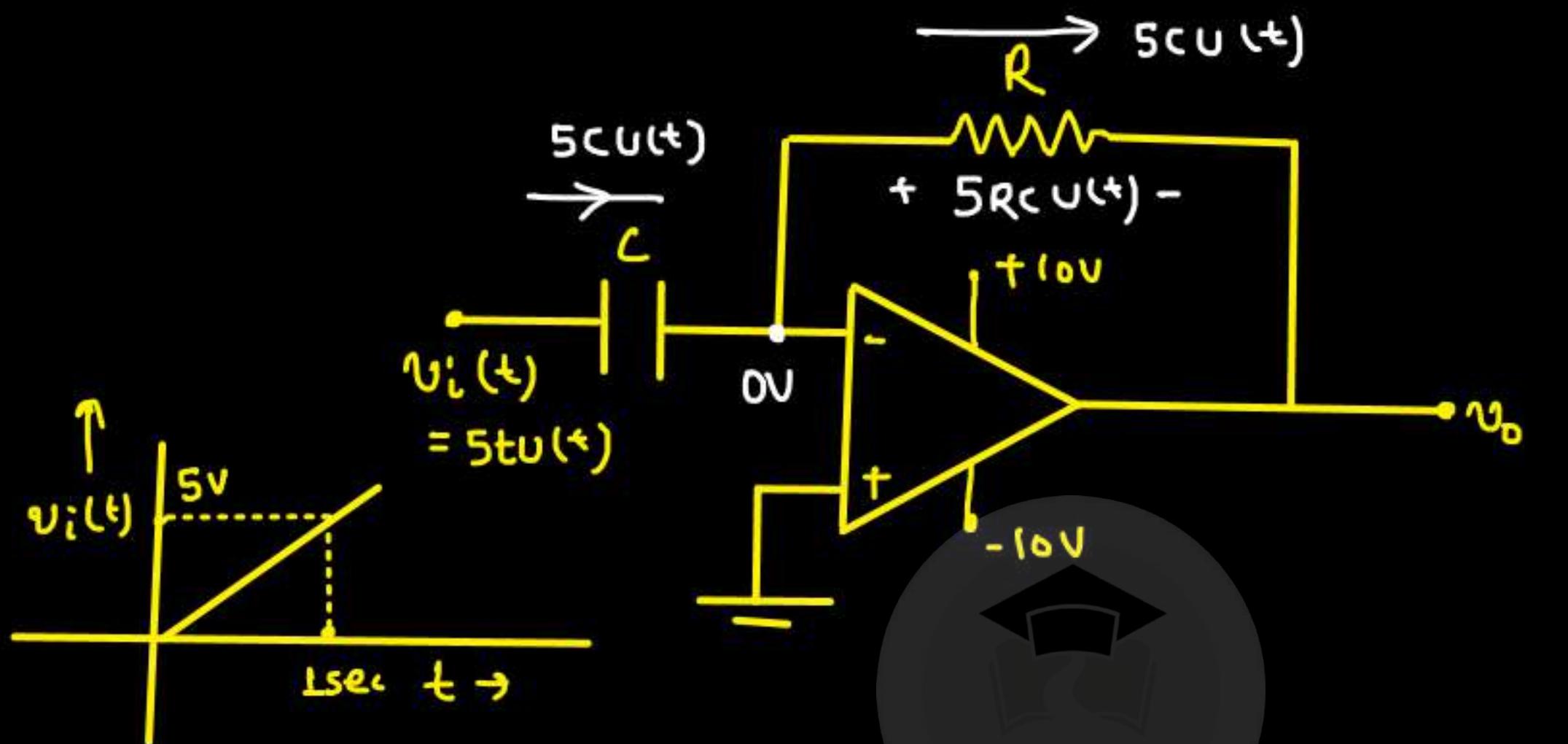

$$I_c(t) \rightarrow$$

$5tU(t)$





$$I_c(t) = C \frac{dV_c(t)}{dt} = C \frac{d}{dt} 5tU(t) = 5C \left[ t \delta(t) + U(t) \right] \\ = 5Cu(t)$$

$$v_o = -5RC v(t)$$

$$v_o = -5v(t)$$


{  $RC = 1 \text{ sec.}$  }

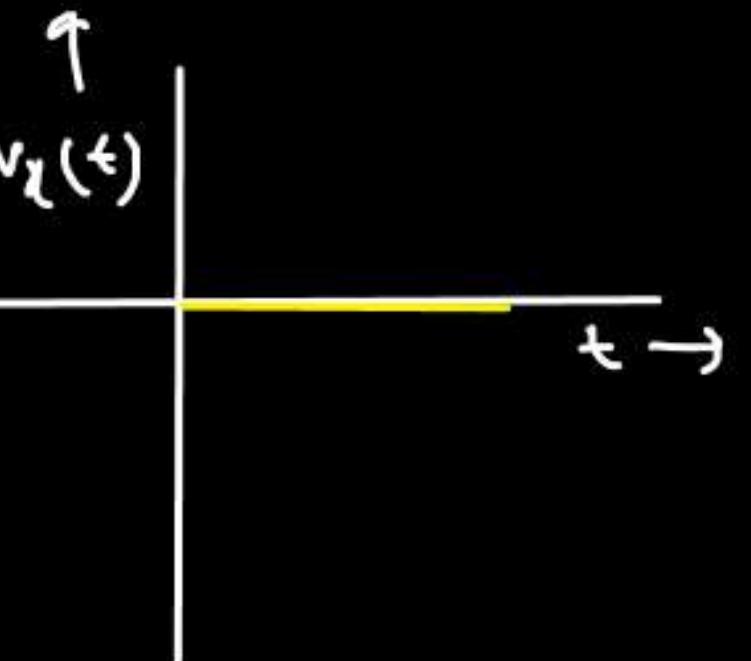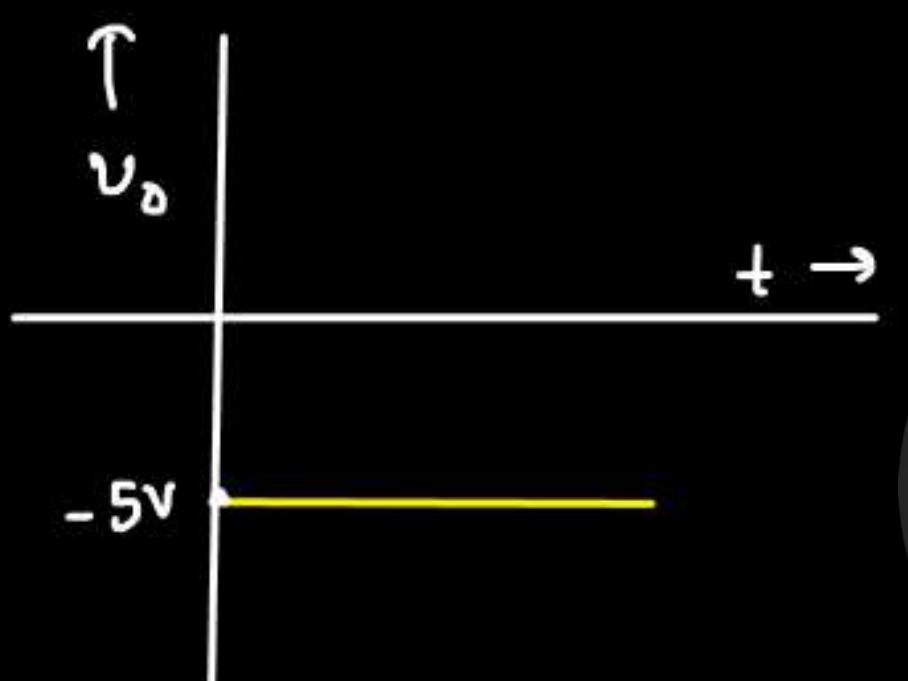

- (a)  $RC = 3 \text{ sec.} \quad v_o(t) = -15V$
- (b)  $RC = 3 \text{ sec.} \quad v_o(t) = -5V$

ANS =

M-II

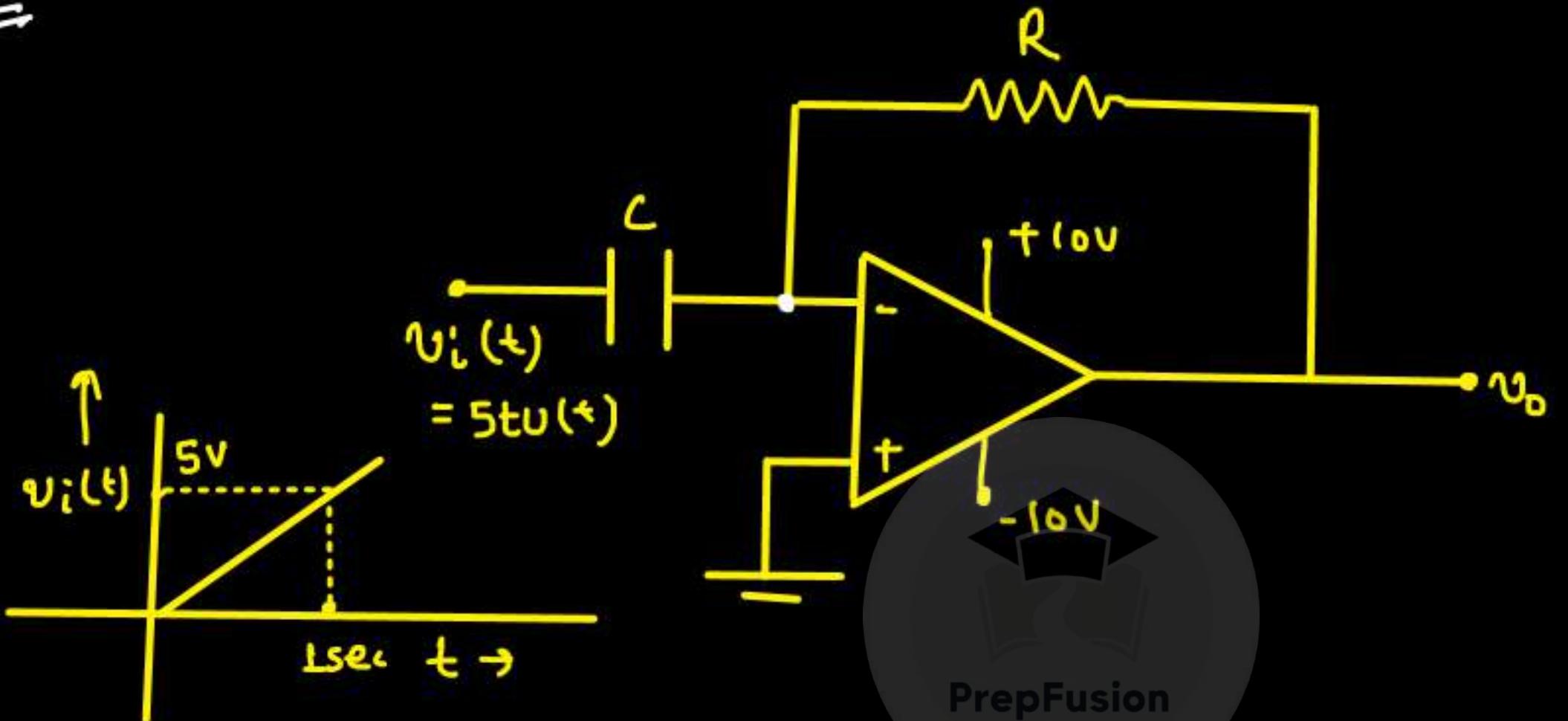

$$\frac{v_o(s)}{v_i(s)} = -5RC$$

$$v_o(t) = -RC \frac{d}{dt} v_{in}(t)$$

$$v_o(t) = -RC \times 5 v(t)$$

$$v_o(t) = -5RC v(t)$$

(a)  $RC = 3 \text{ sec.}$

$$\begin{aligned}
 v_o(t) &= -5RC v(t) \\
 &= -5(3)v(t) \\
 &= -15v(t) \times \left\{ -v_{sat} = -10 \right\}
 \end{aligned}$$

$v_o(t) = -10v(t)$

(b)  $RC = 1 \text{ sec.}$


$$v_o(t) = -5RC v(t)$$

$v_o(t) = -5v(t)$



## Assignment - 15 (Fusion - Special)

Q.

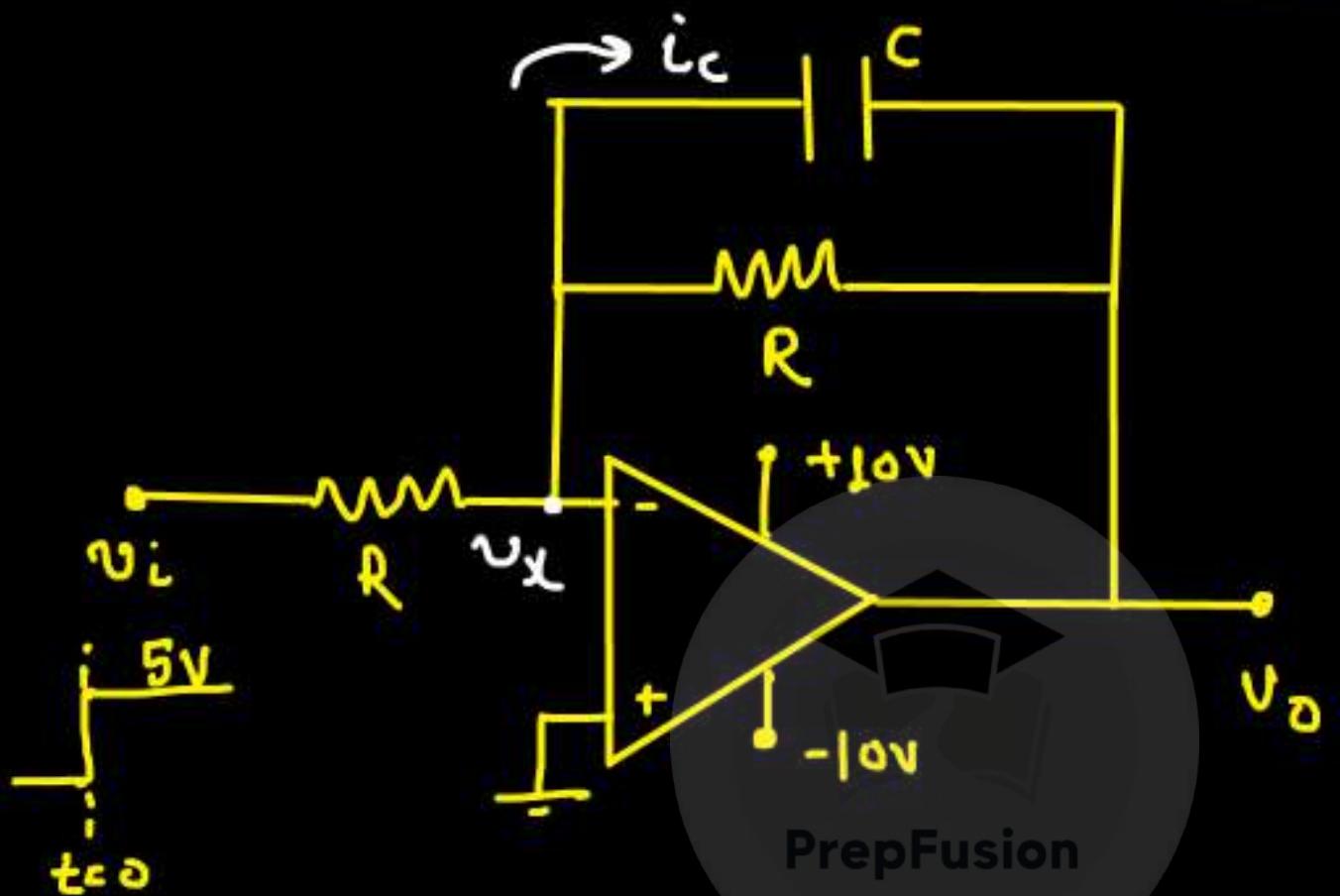


Draw  $V_o$  waveform.


$$\rightarrow V_o(t=0^+) = 0 \quad ; \quad i_C(0^+) = \frac{5}{R}, \quad i_C(\infty) = 0 \text{ Amp}$$

$$V_o(t=\infty) = -5V \quad [\text{NOT saturated}]$$
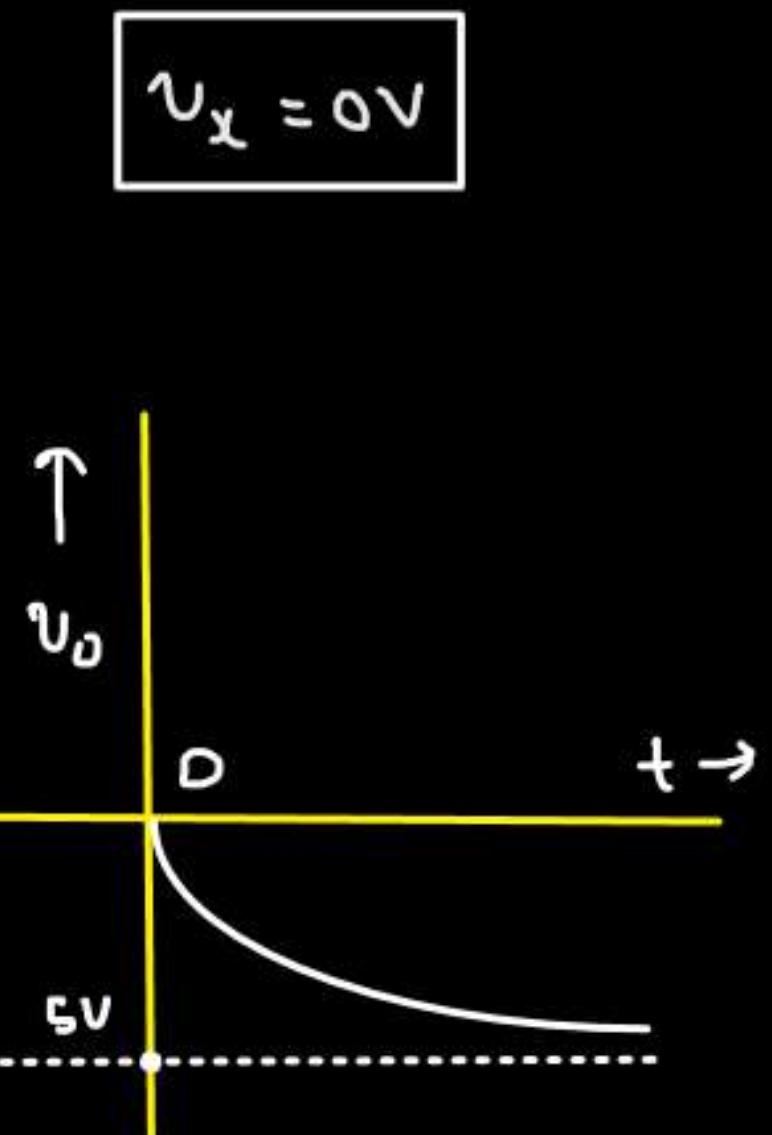
$$V_o(t) = -5 [1 - e^{-t/RC}] V(t); \quad i_C(t) = \frac{5}{R} e^{-t/RC} V(t)$$



Q. 2

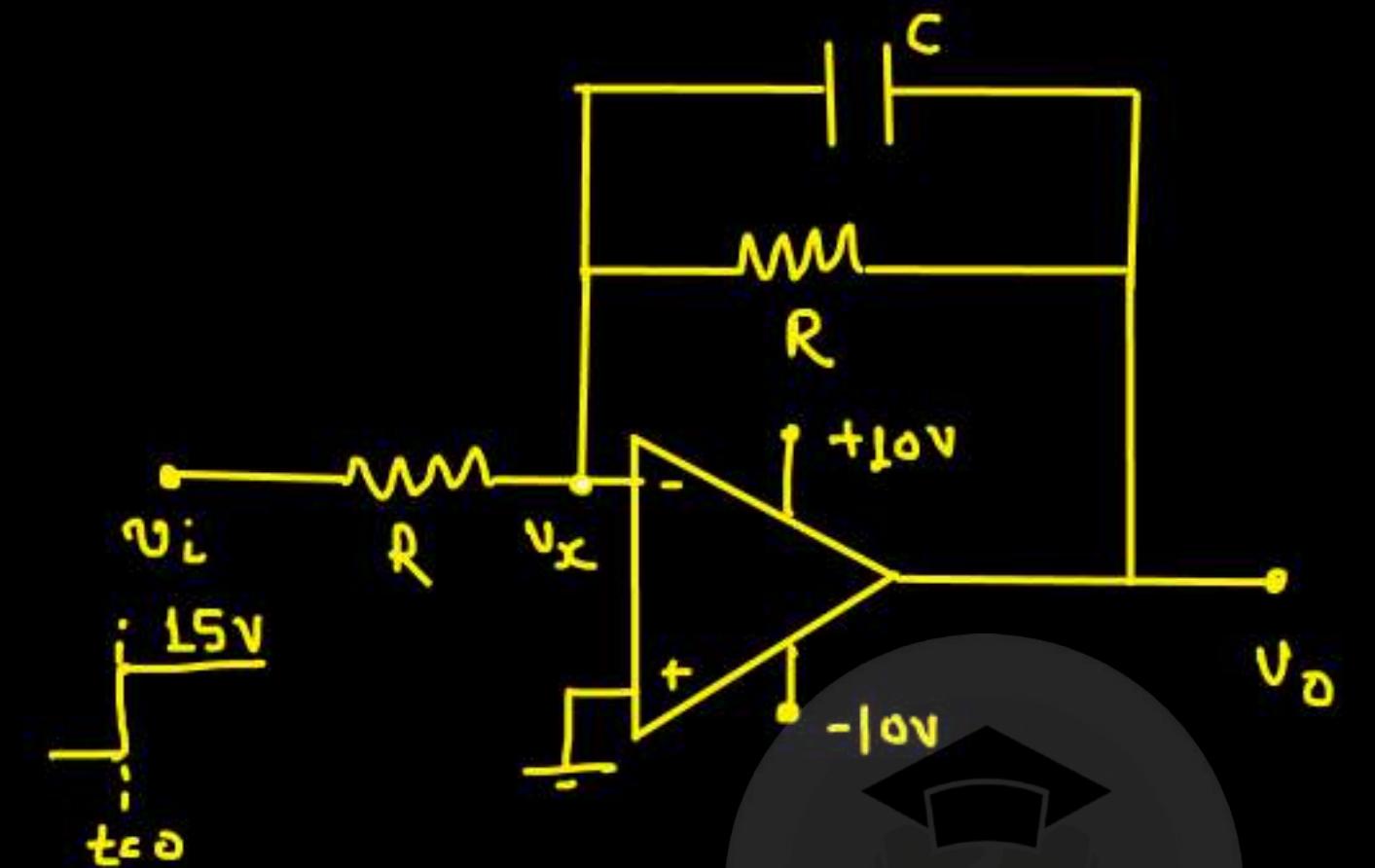



PrePfusion  
Take  $RC = 1 \text{ sec.}$

The value of  $v_x$  @  $t = 2 \text{ sec.}$

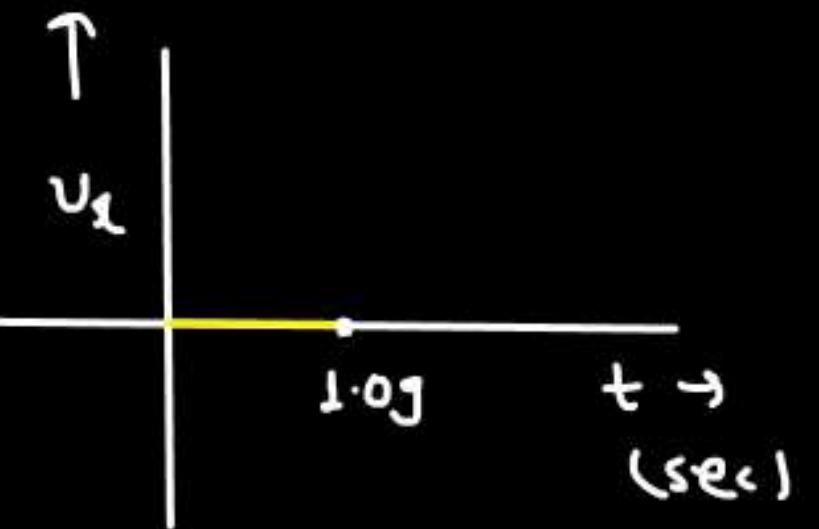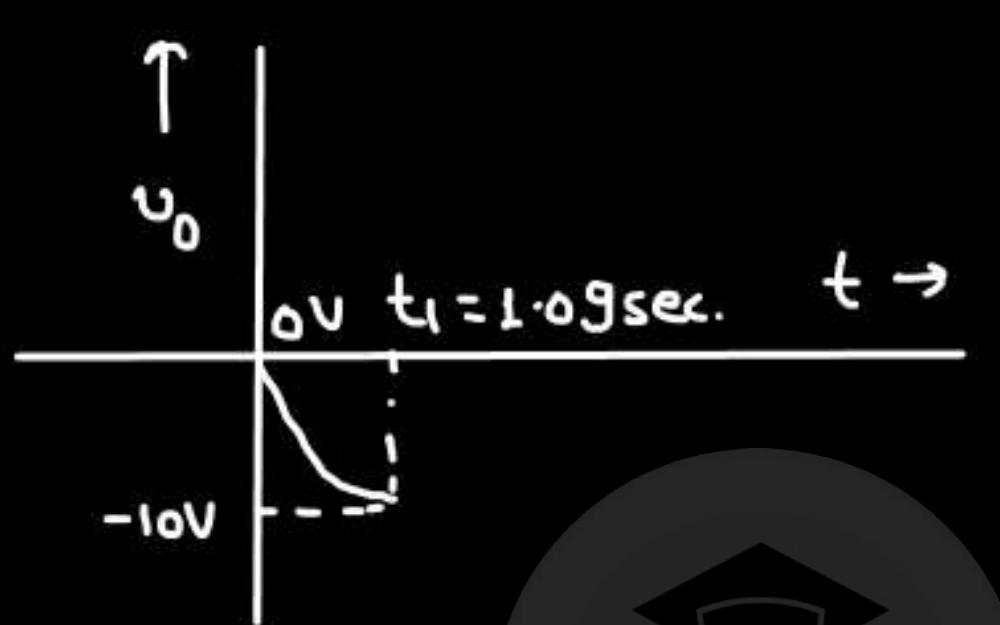- (a) 0 V      (b) 1 V      (c) -10 V      (d) 1.5 V

$$\rightarrow v_o(0^+) = 0 \text{ V}, \quad v_o(\infty) = -15 \text{ V}$$

$$v_o(t) = -15 \left( 1 - e^{-t/RC} \right) v(t)$$



@  $t = t_1$ ;  $v_o(t_1) = -10 \Rightarrow 0|P$  saturated

PrepFusion





After  $t > t_1 \Rightarrow$  virtual short NOT

Valid

$$-10 = -15 \left( 1 - e^{-t_1/1} \right)$$

$t_1 = 1.09 \text{ sec.}$

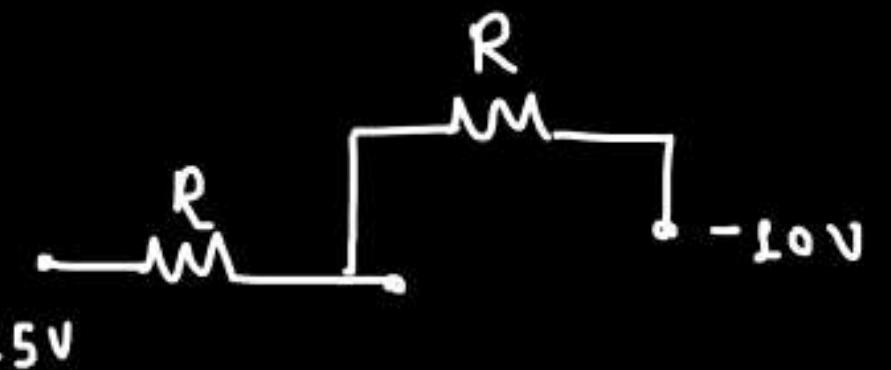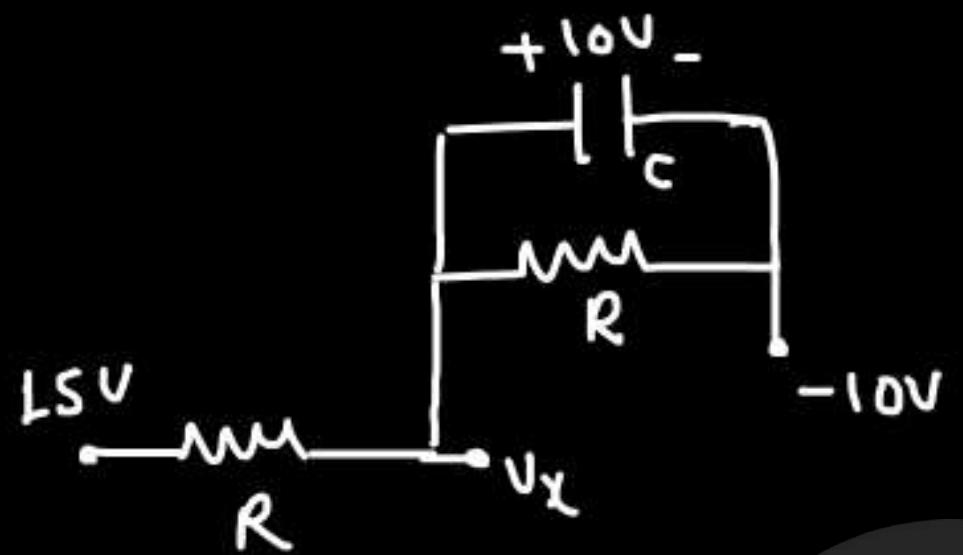for  $t > 1.09 \text{ sec} \Rightarrow$  virtual short NOT valid





$$v_x(t = 1.09^+) = 0$$

$$v_x(\infty) = 2.5 \text{ V}$$

$$v_x(t) = 2.5 \left( 1 - e^{-(t - 1.09)/1\text{sec}} \right)$$


$$v_x(2\text{sec}) = 2.5 \left( 1 - e^{-(2 - 1.09)/1\text{sec}} \right)$$

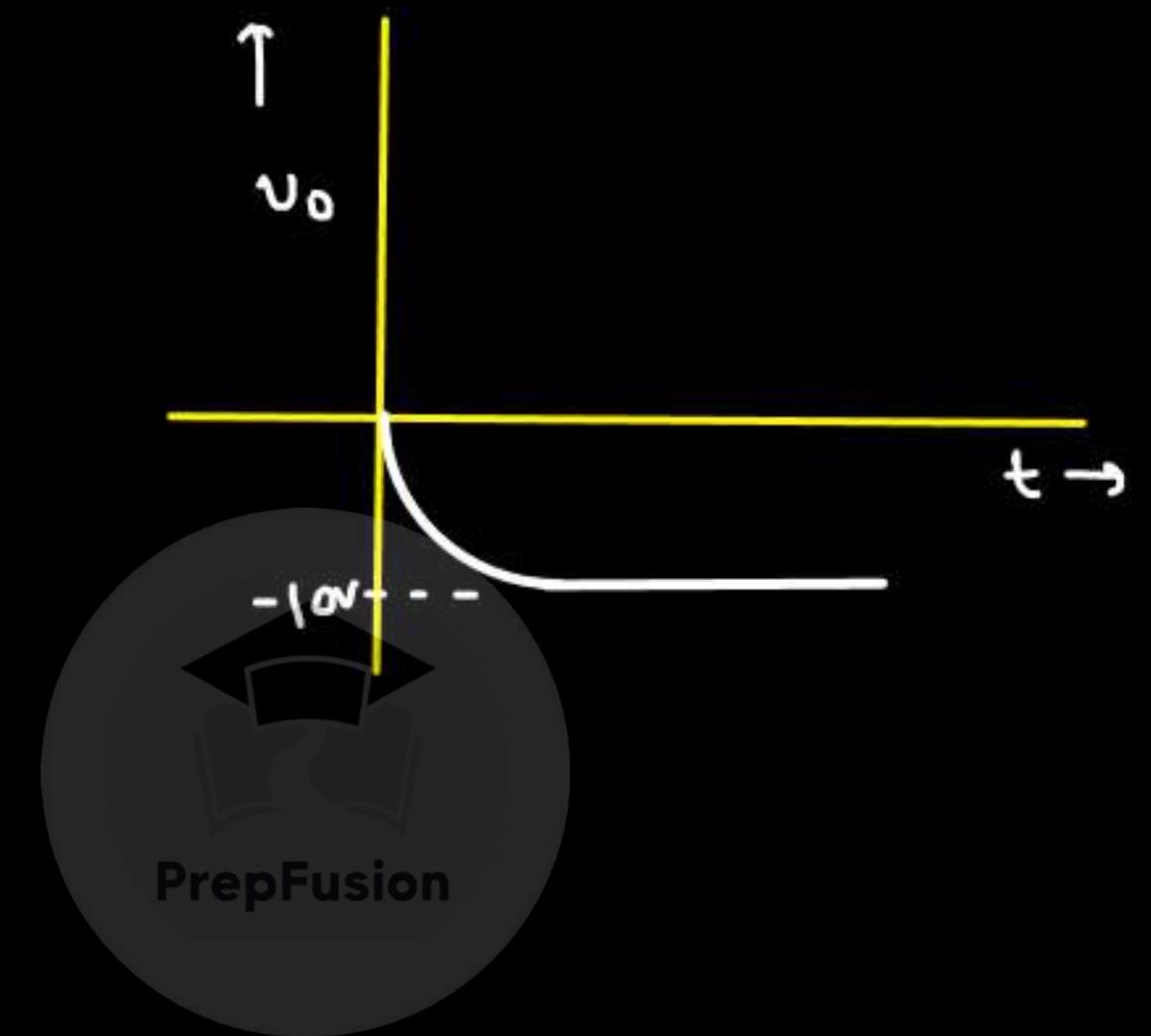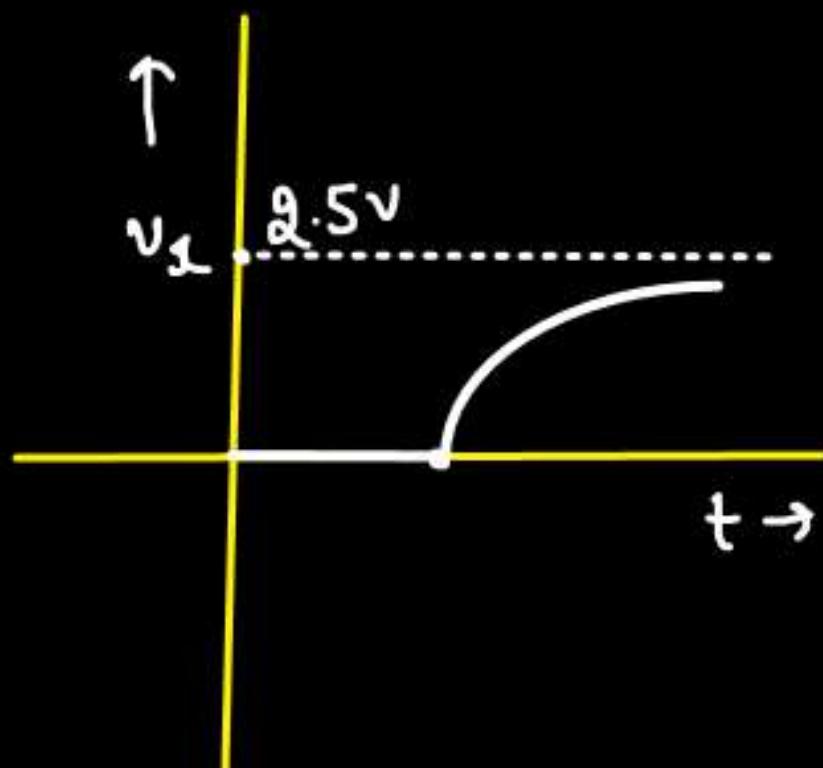$v_x(2\text{sec}) \approx 1.48 \text{ V}$



PrepFusion

Q. 3



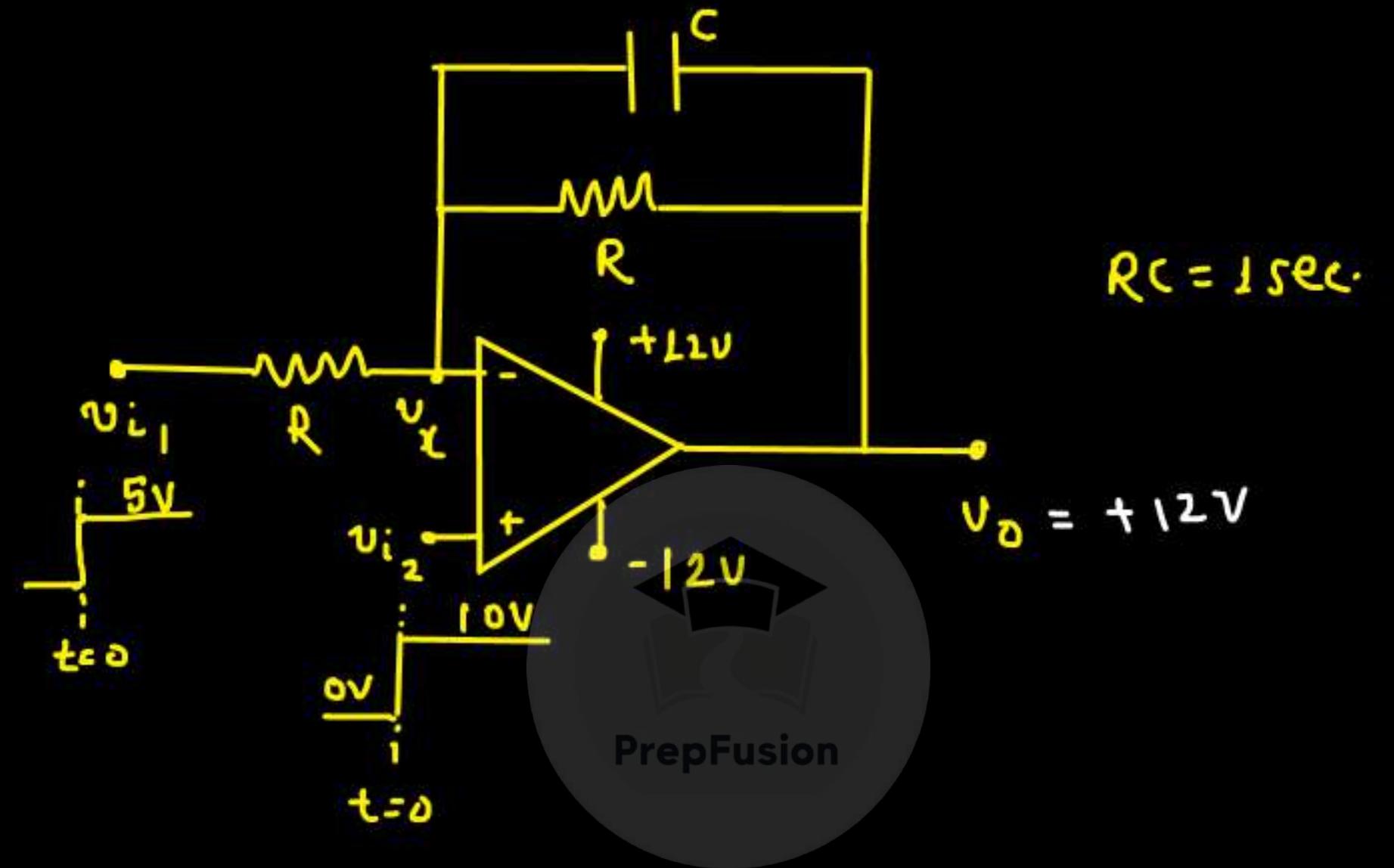


Draw  $v_x$  and  $v_o$  waveforms.

$$\rightarrow v_o(0^+) = 10V$$

$$v_o(\infty) = 15V$$

$$v_o(t) = [15 - 5e^{-t/RC}] v_o(t)$$

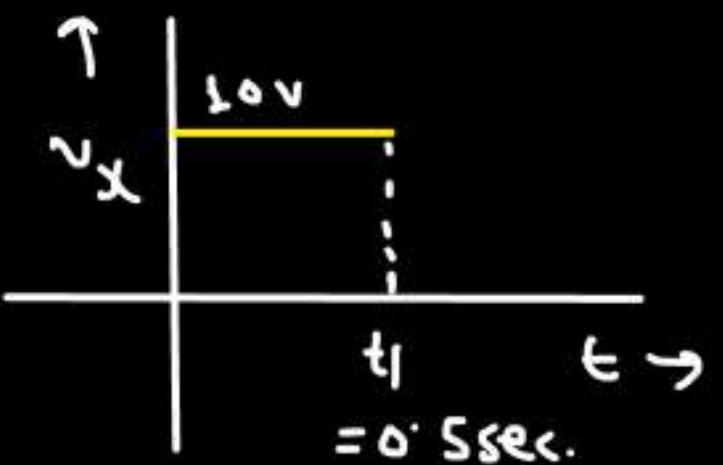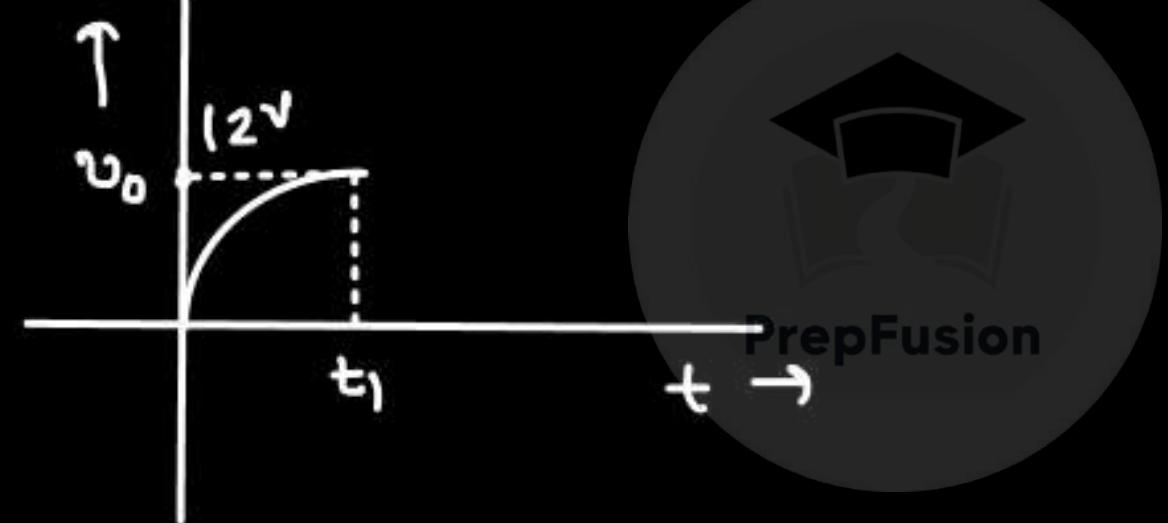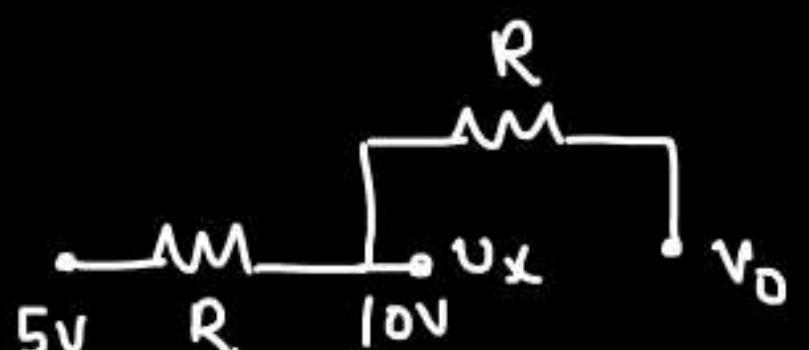


@  $t = t_1 \Rightarrow o/p$  saturates @ 12V

$$12 = 15 - 5e^{-t_1/1}$$

$t_1 = 0.5\text{ sec.}$

$t > 0.5 \text{ sec.}$


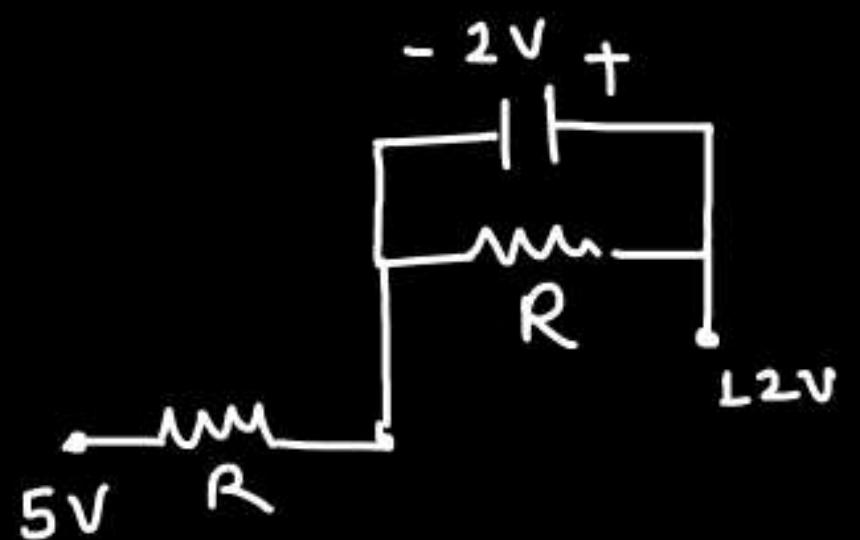


$$v_x(t=0.5^+) = 10V$$


$$v_x(0) = \frac{12R + 5R}{2R} = 8.5V$$

$$v_x(t) = [8.5 + 1.5 e^{-\frac{(t-0.5)}{1}}] v(t-0.5)$$

$$v_o(t) = 12 v(t-0.5)$$

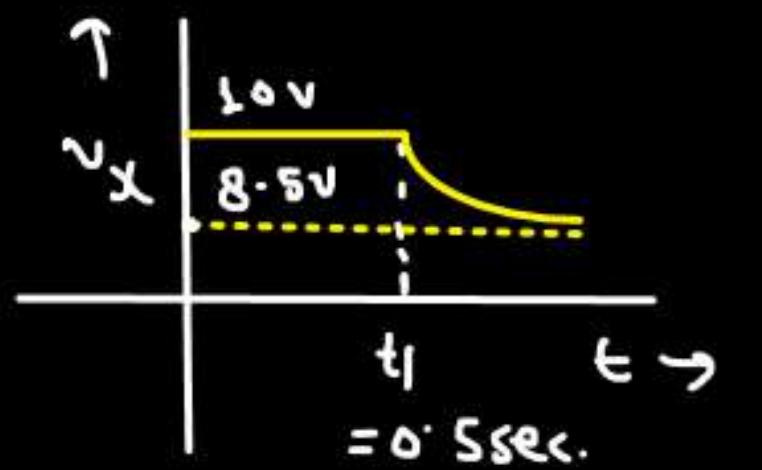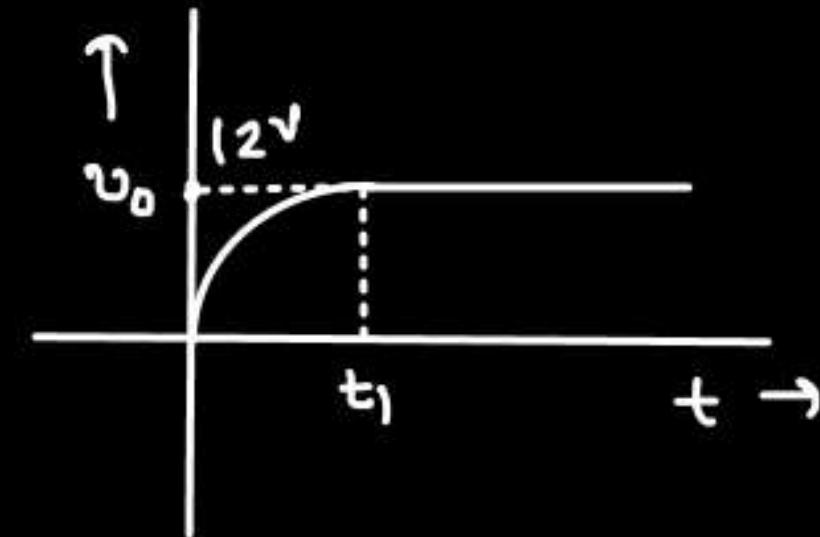


Q.

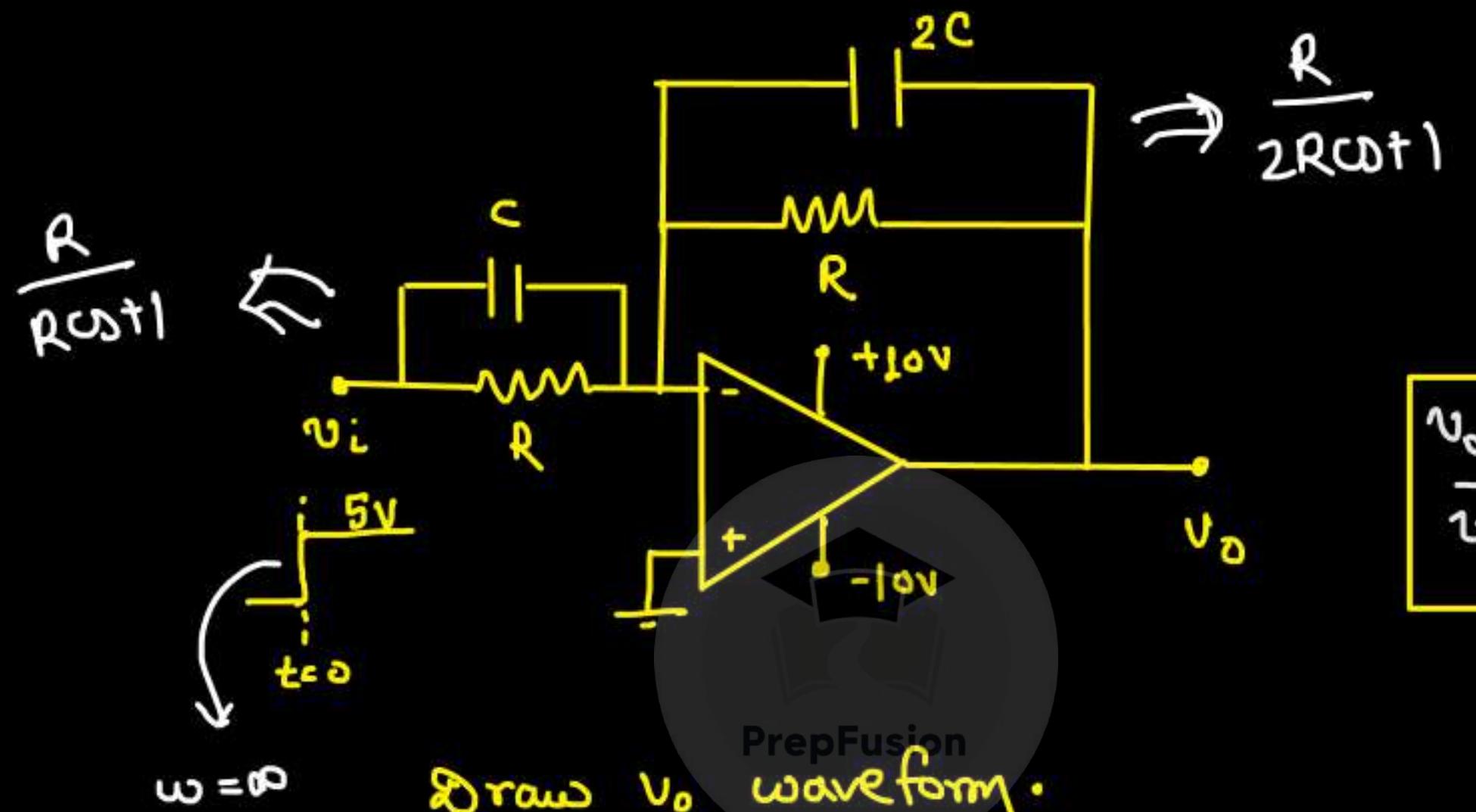


$$\frac{V_o(s)}{V_i(s)} = - \frac{(R\omega + 1)}{2R\omega t + 1}$$

First order  
 $\tau = 2RC$

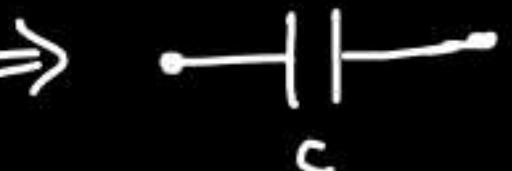→ @  $t=0^+$  ⇒  $\omega=\infty$  ⇒  $\text{R} \rightsquigarrow \text{finite impedance}$   
 $\text{C} \rightsquigarrow \text{low impedance}$




at  $t=0^+$ :

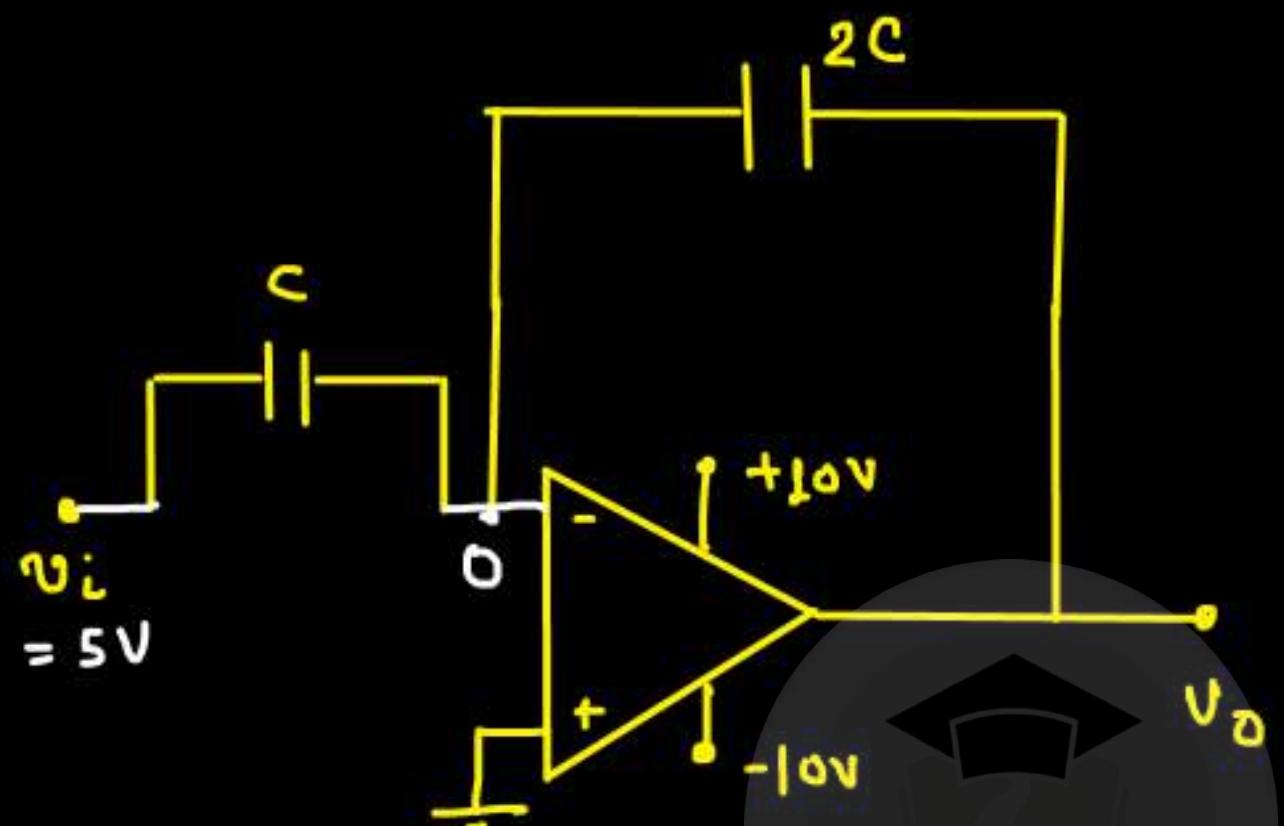

$$[(0 - v_i)]C + [(0 - v_o)]2C = 0 \quad \text{@ } t=0^+$$

$$\frac{v_o}{v_i} = -\frac{1}{2}$$

$$v_o(t=0^+) = -2.5V$$

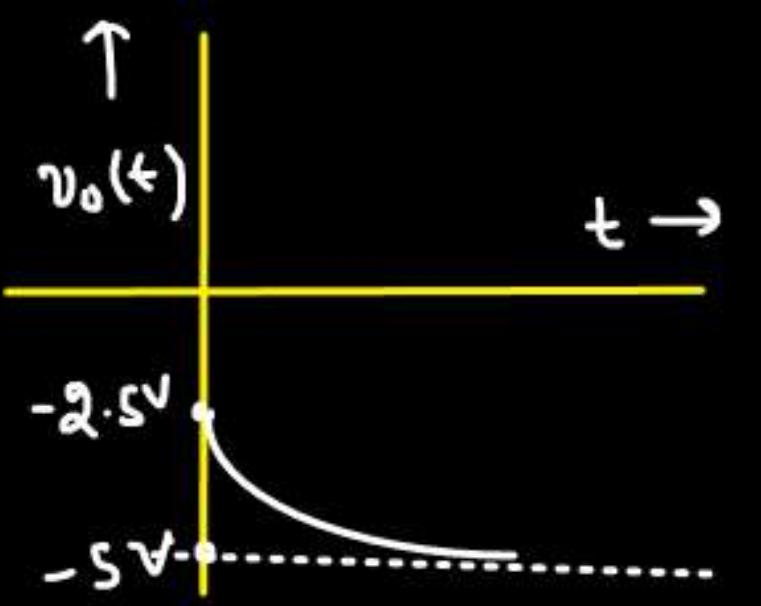


at  $t=\infty$


$$v_o(\infty) = -5V$$

$$v_o(t) = -5 + 2.5e^{-t/2RC}$$

Q.

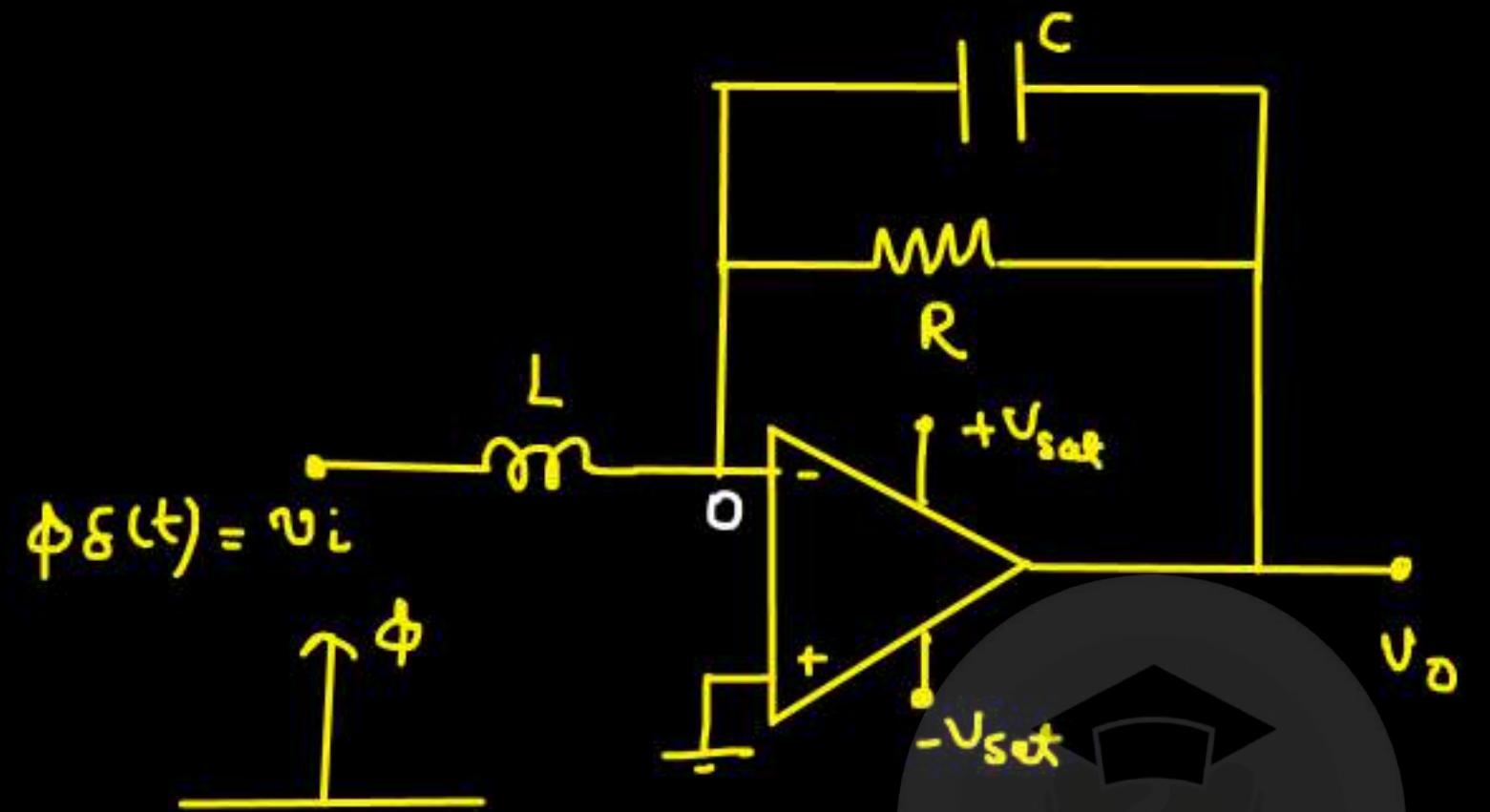

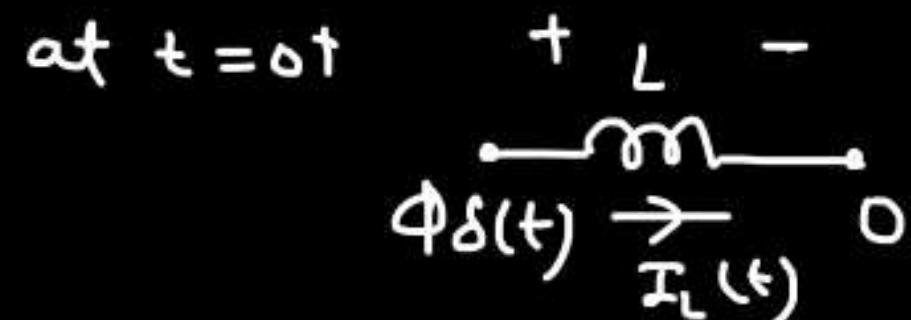→ at  $t=0^+$  ⇒ negative f/b + nt ⇒ virtual short is valid




$$I_L(0^-) = 0 \text{ Amp}$$

$$I_L(0^+) = 0 \text{ Amp} \quad X = \frac{\phi}{L}$$

$$I_L(t) = \frac{1}{L} \int_{0^-}^t v(t) dt = \frac{1}{L} \int_{0^-}^t \phi \delta(t) dt$$
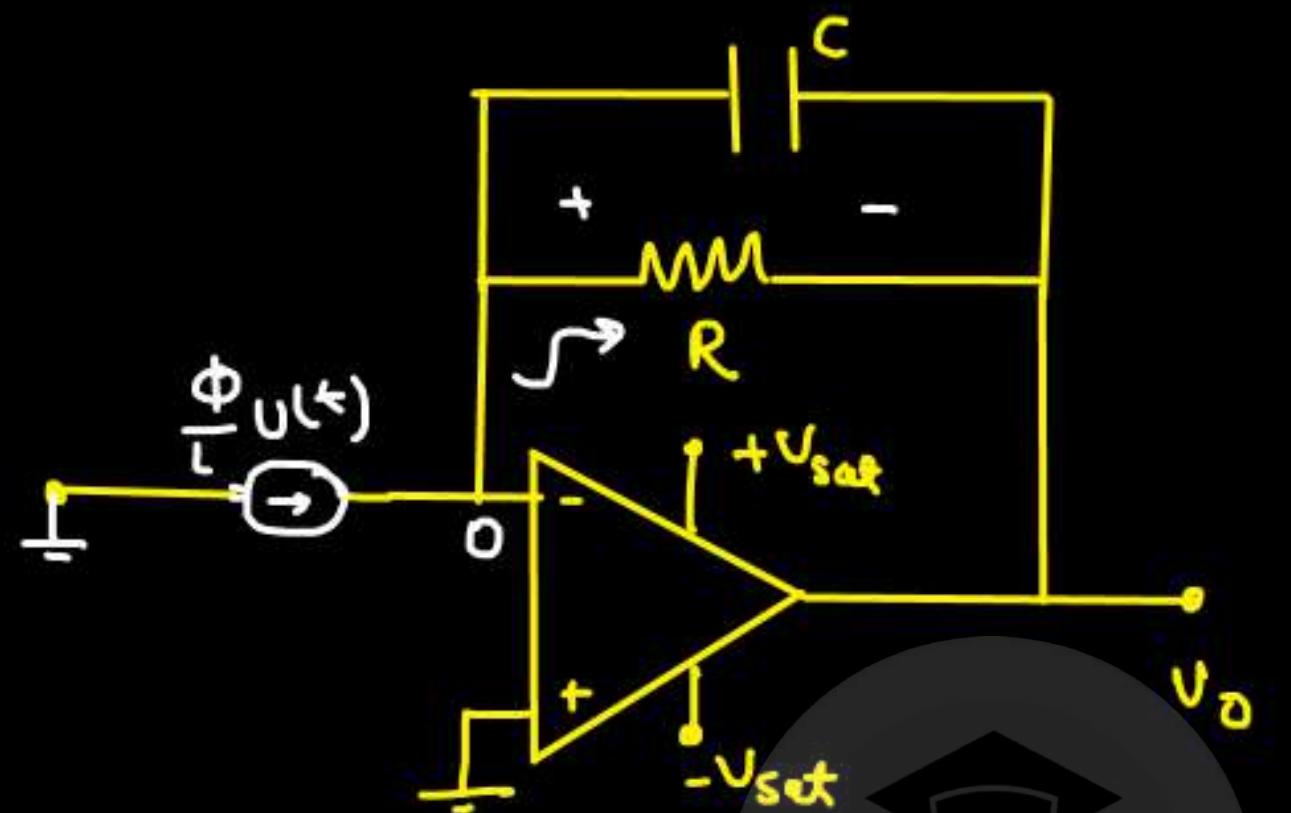
$$I_L(t) = \frac{\phi}{L} v(t) \quad \checkmark$$




$$v_o(0^+) = 0 \text{ V}$$


$$v_o(\infty) = -\frac{\Phi}{L} R$$

PrepFusion

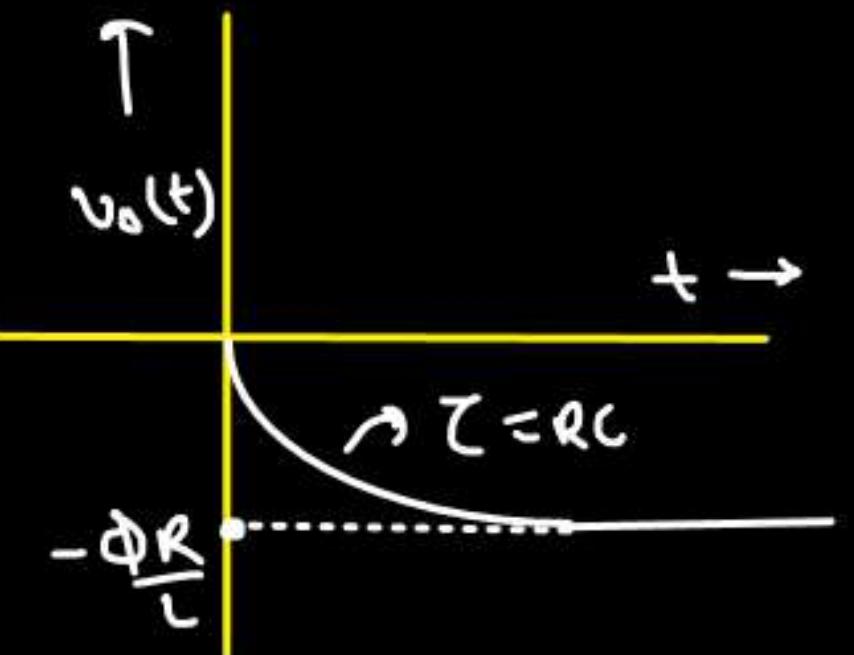
$$v_o(t) = -\frac{\Phi R}{L} \left( 1 - e^{-t/Rc} \right) v_U(t)$$



## Active Clipper Circuit:-

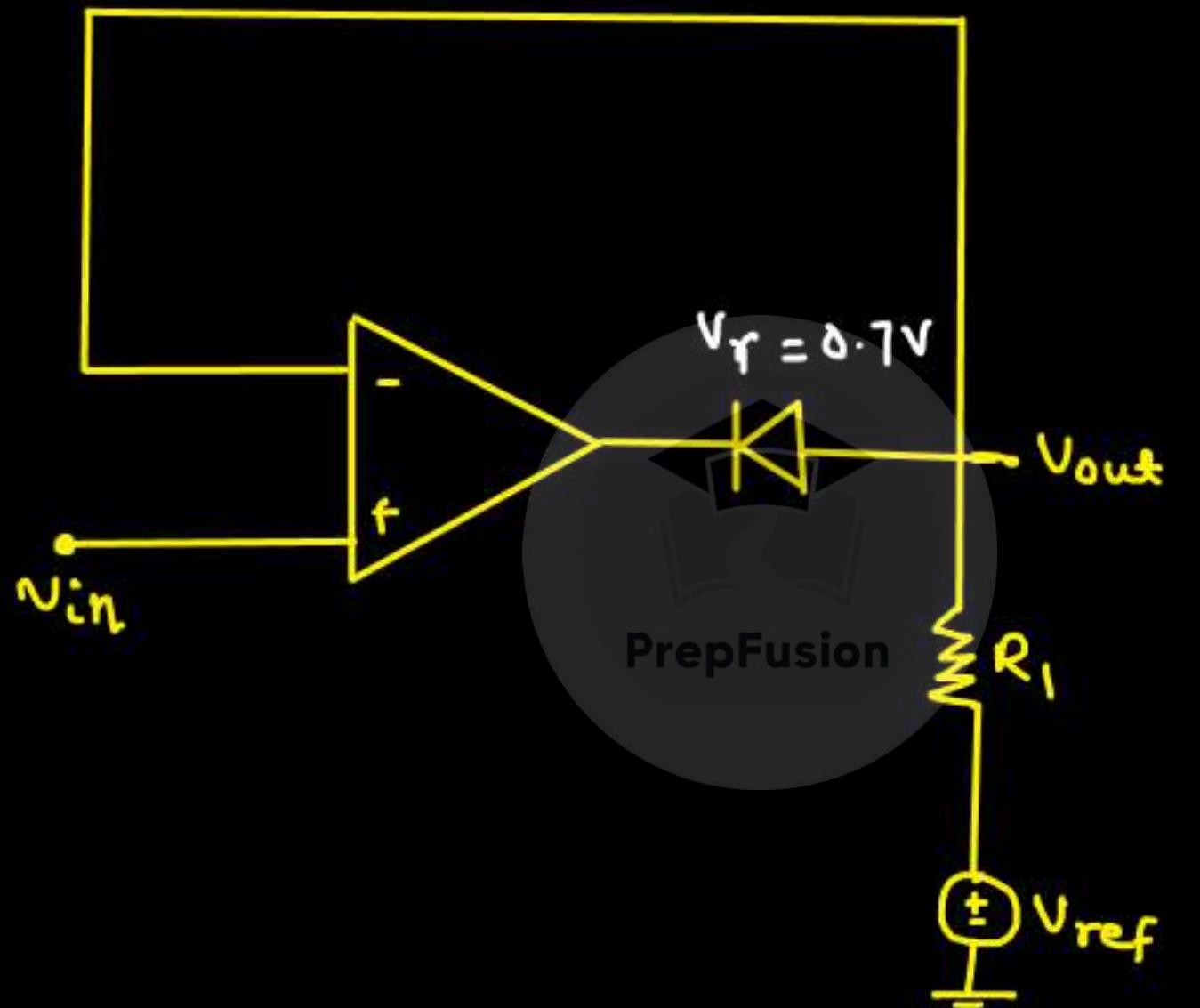

Take  $V_{ref}$  to be +ve.

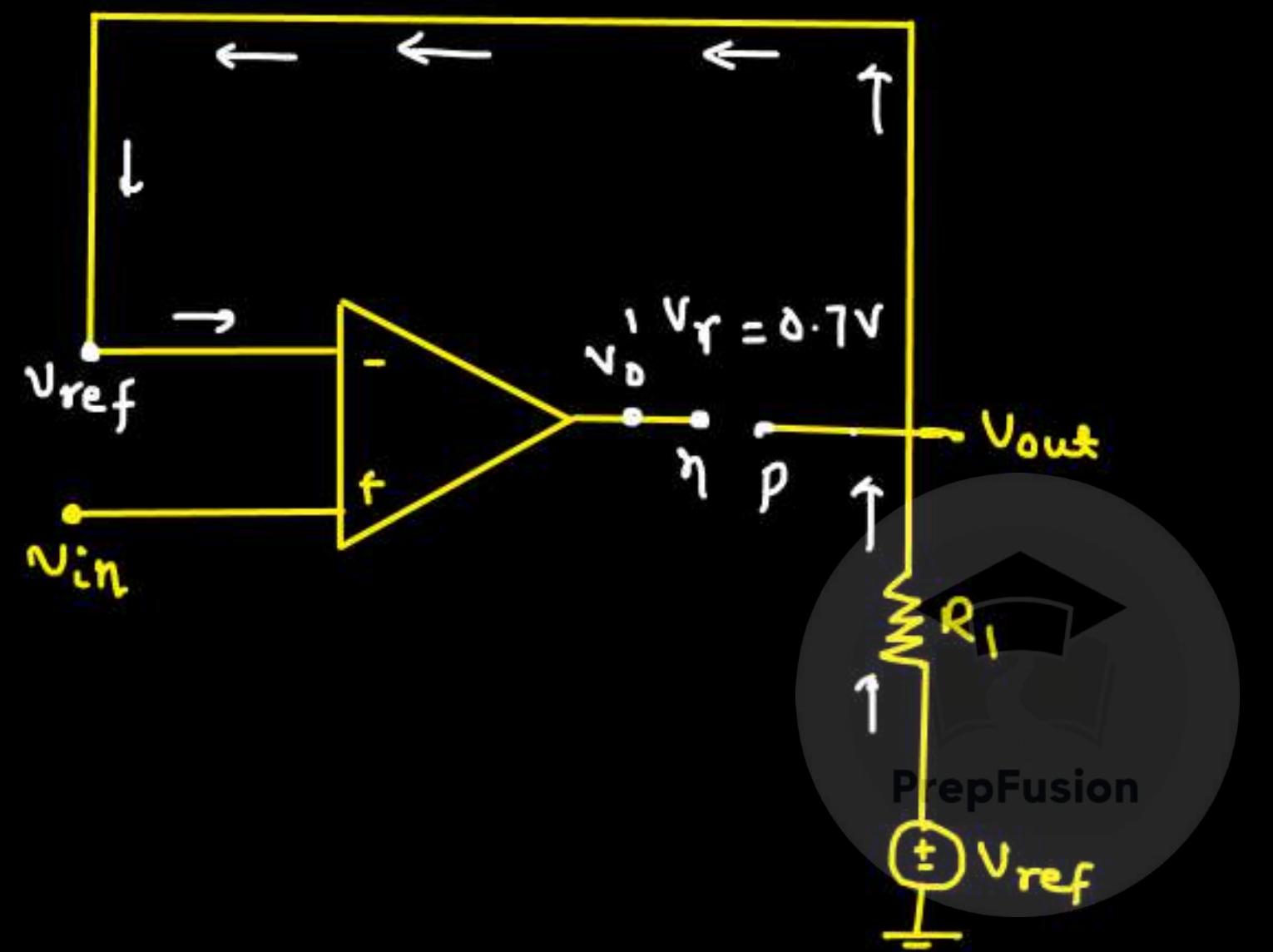


$$V_{in} > V_{ref}$$

$$V_0 = V_{ref}$$


$$\Rightarrow V_0' = +V_{sat}$$

$+V_{sat}$   $V_{ref}$   $\Rightarrow$  diode off

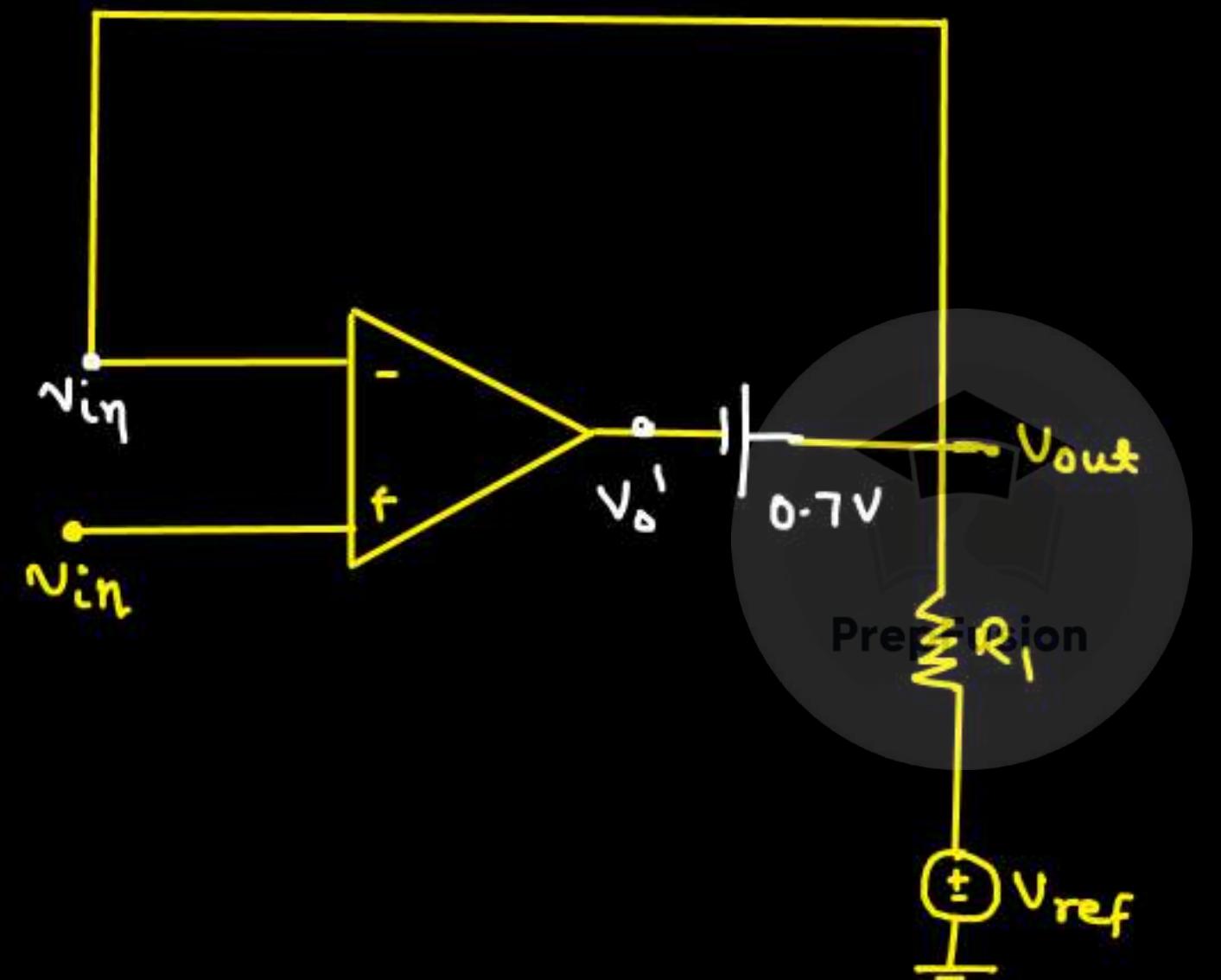$v_{in} < v_{ref}$   $\Rightarrow v_o' = -v_{sat} \Rightarrow$  diode ON  $\Rightarrow$  Negative f/b




$$v_o = v_{in}$$

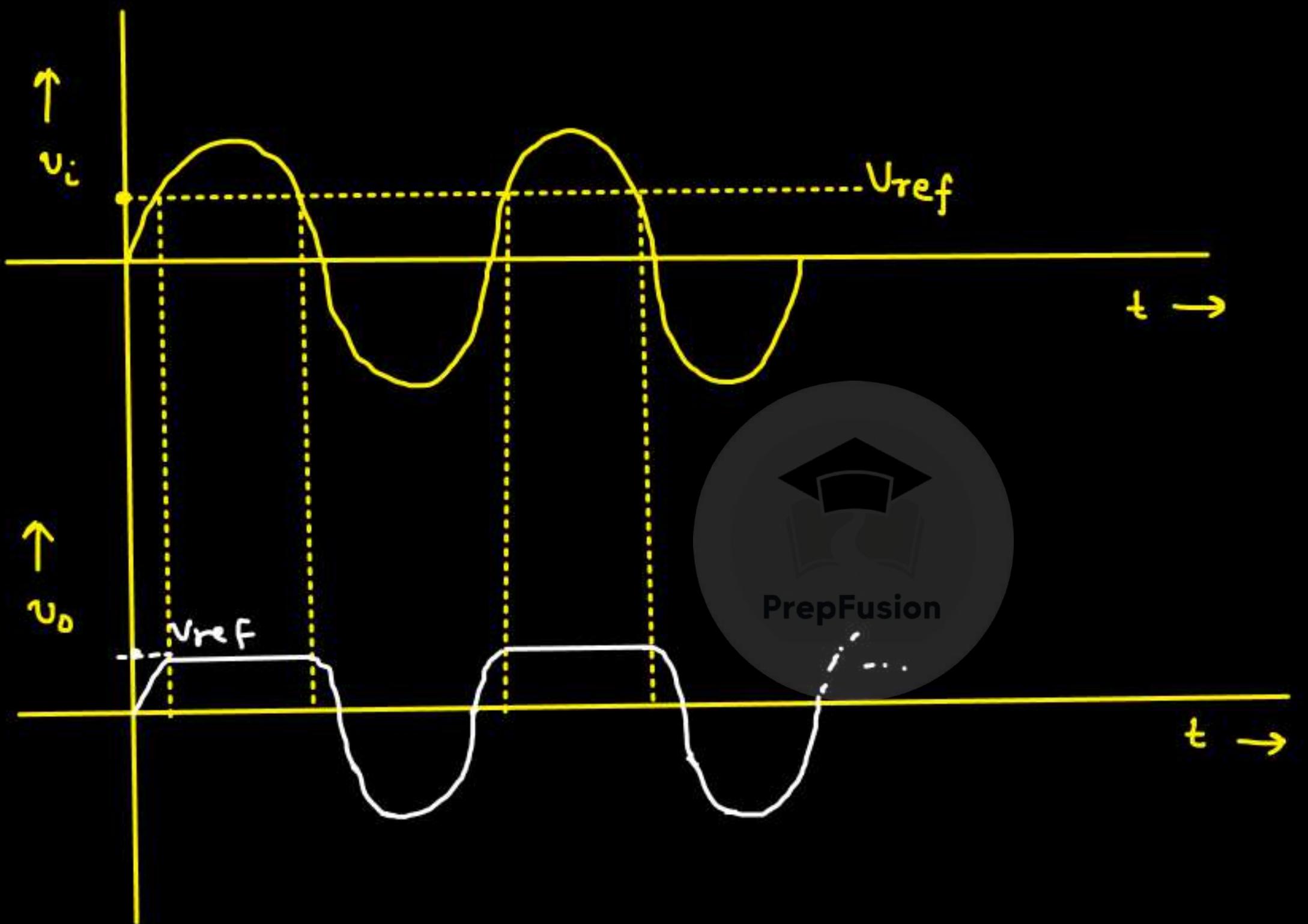

Q. Draw Transfer Characteristics.

O.C. Test

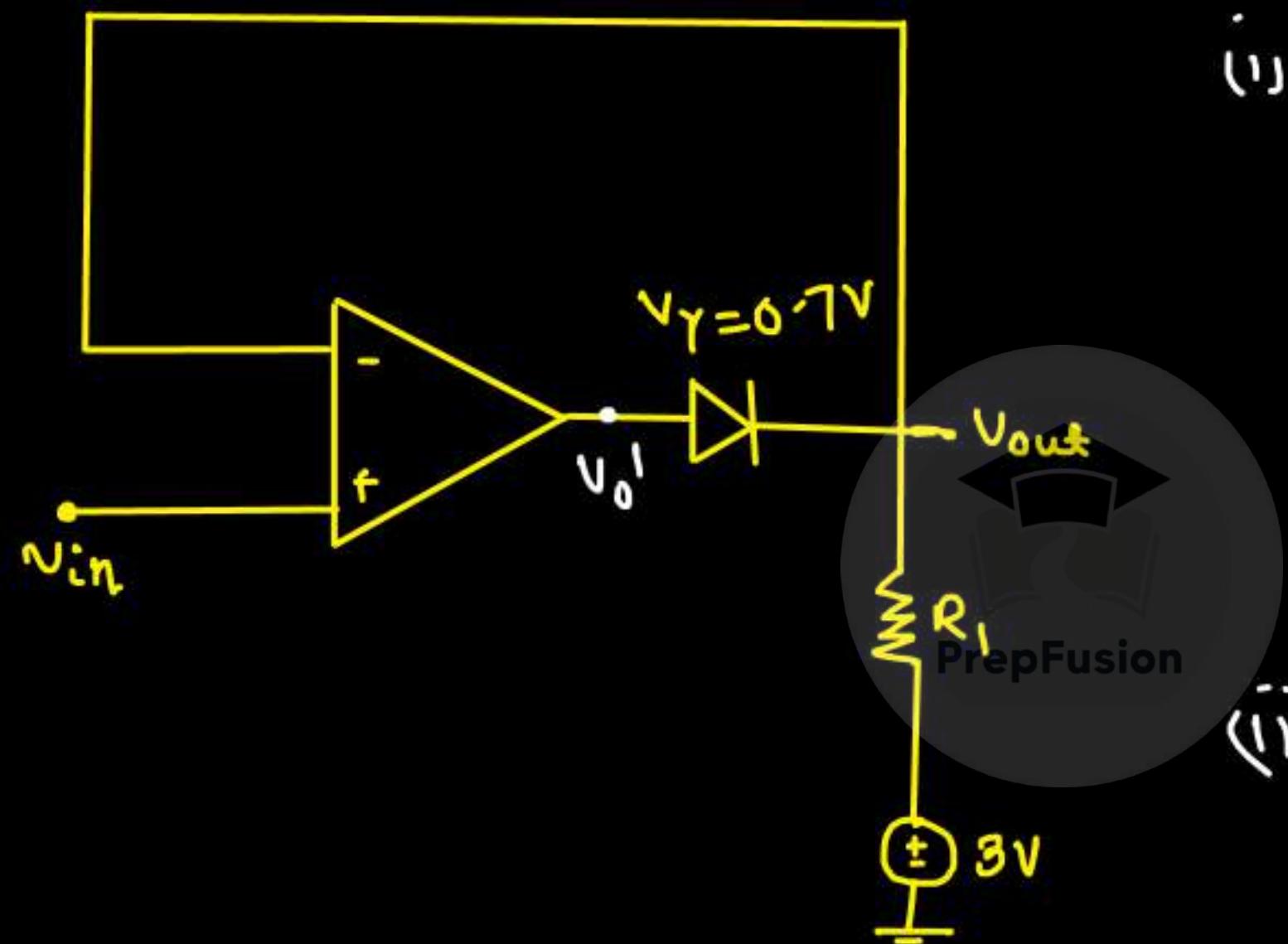

(i)  $V_{in} > 3V$

$$V_o' = +V_{sat}$$

⇒ diode ON

⇒ Negative feedback present


$$V_o = V_i$$

(ii)  $V_{in} < 3V$


$$V_o' = -V_{sat}$$


⇒ diode off

$$V_{out} = 3V$$

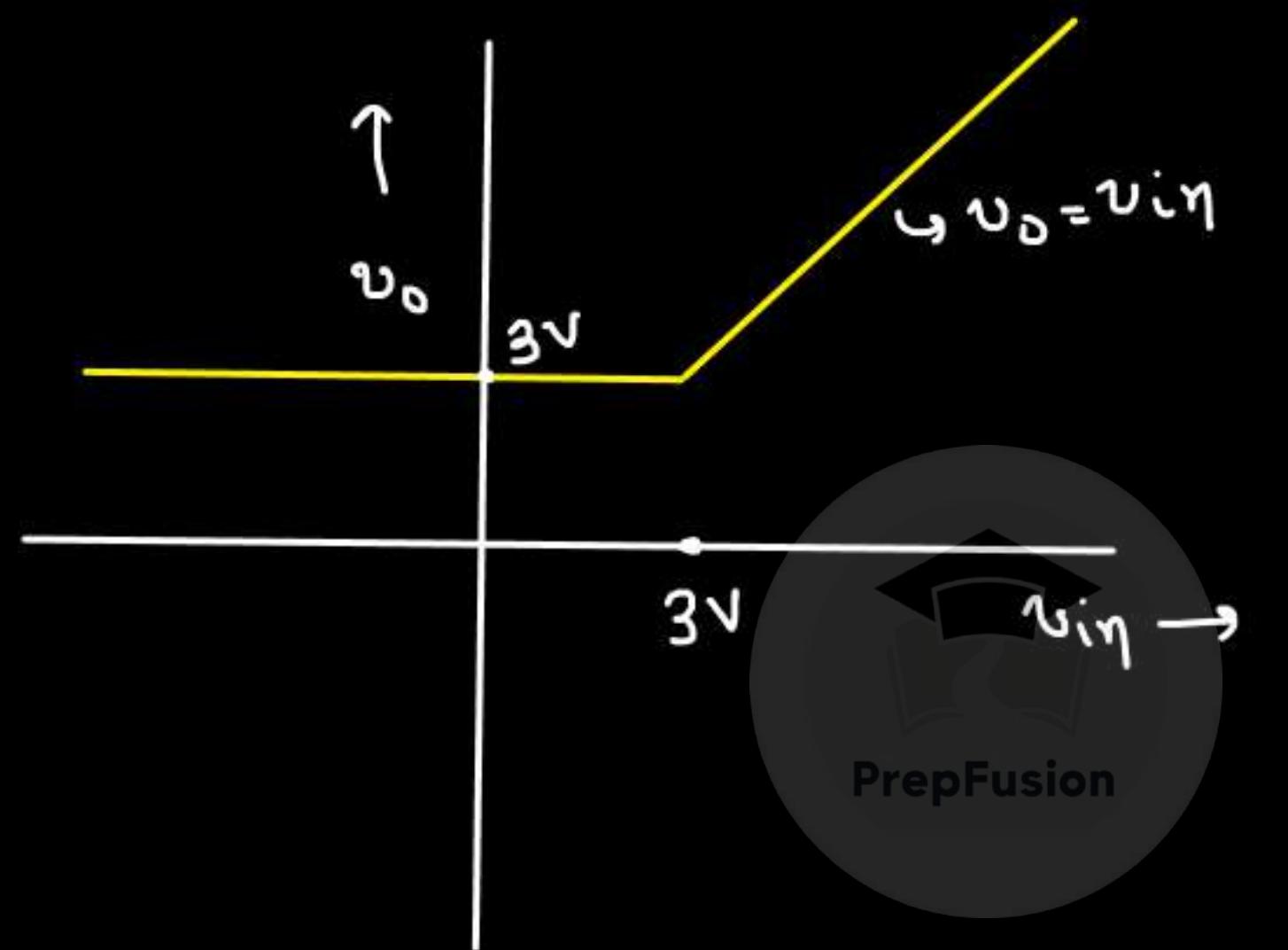

## \* Active Peak detector :-

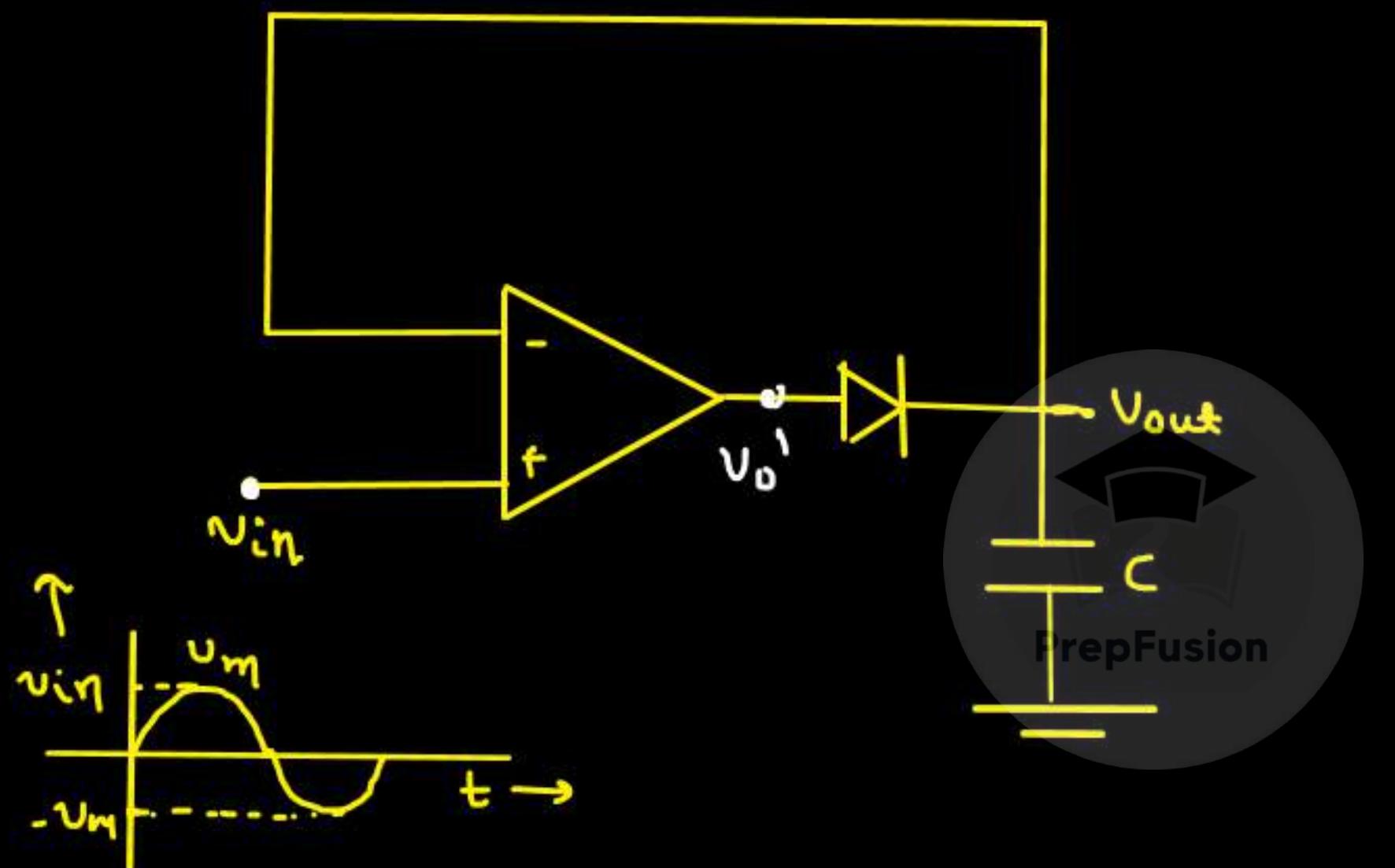

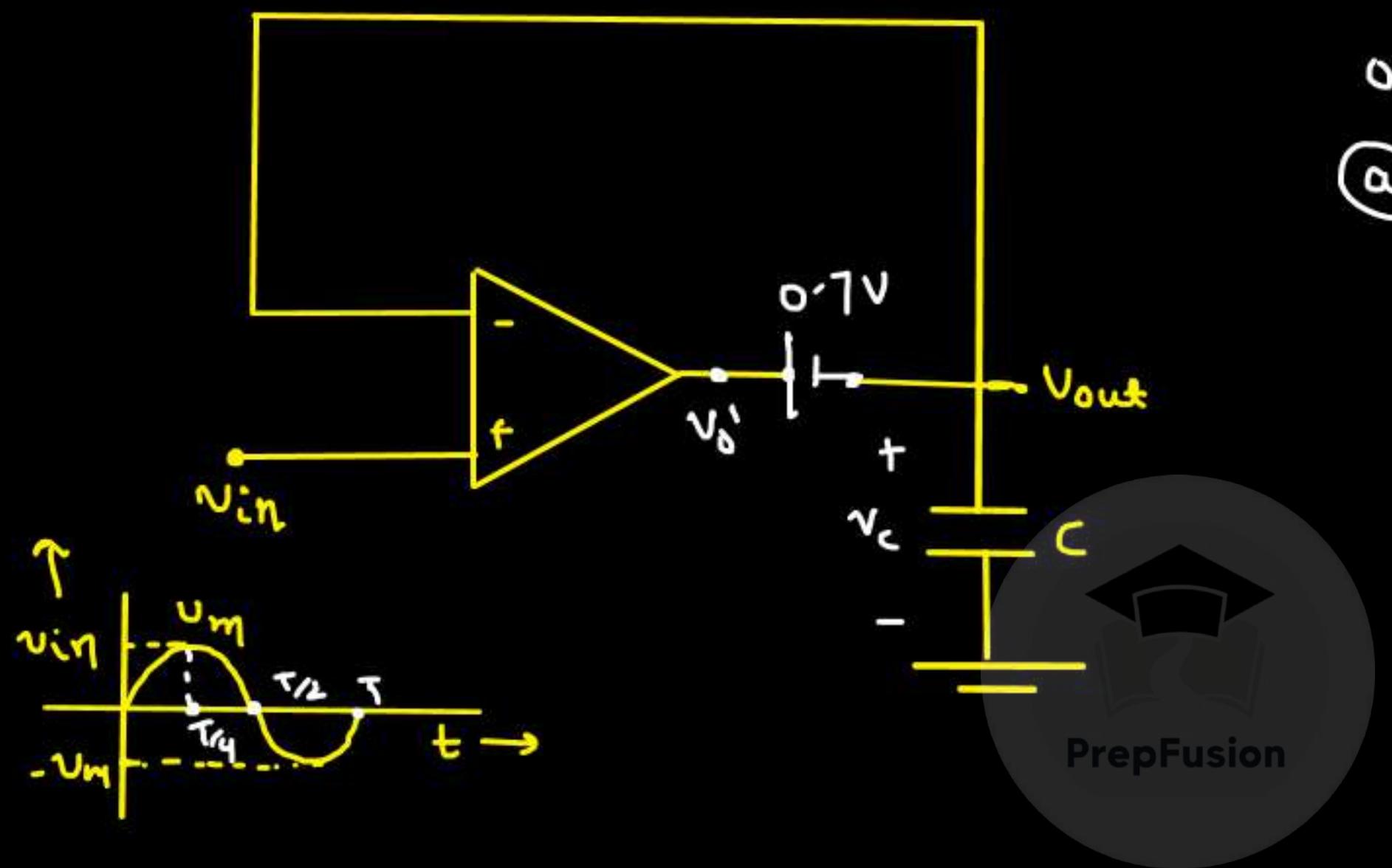

O.C. Test.

@  $t=0^+$

$$v_{in} > 0 \Rightarrow v_+ > 0$$


$$v_c = 0 \Rightarrow v_- = 0$$

$$\Rightarrow v'_o = +v_{sat} \Rightarrow \text{diode ON}$$

↓  
Neg. f/b tnt

$$v_o = v_{in} \left\{ 0 < t < \frac{\tau}{4} \right\}$$

at  $t = T/4^+$

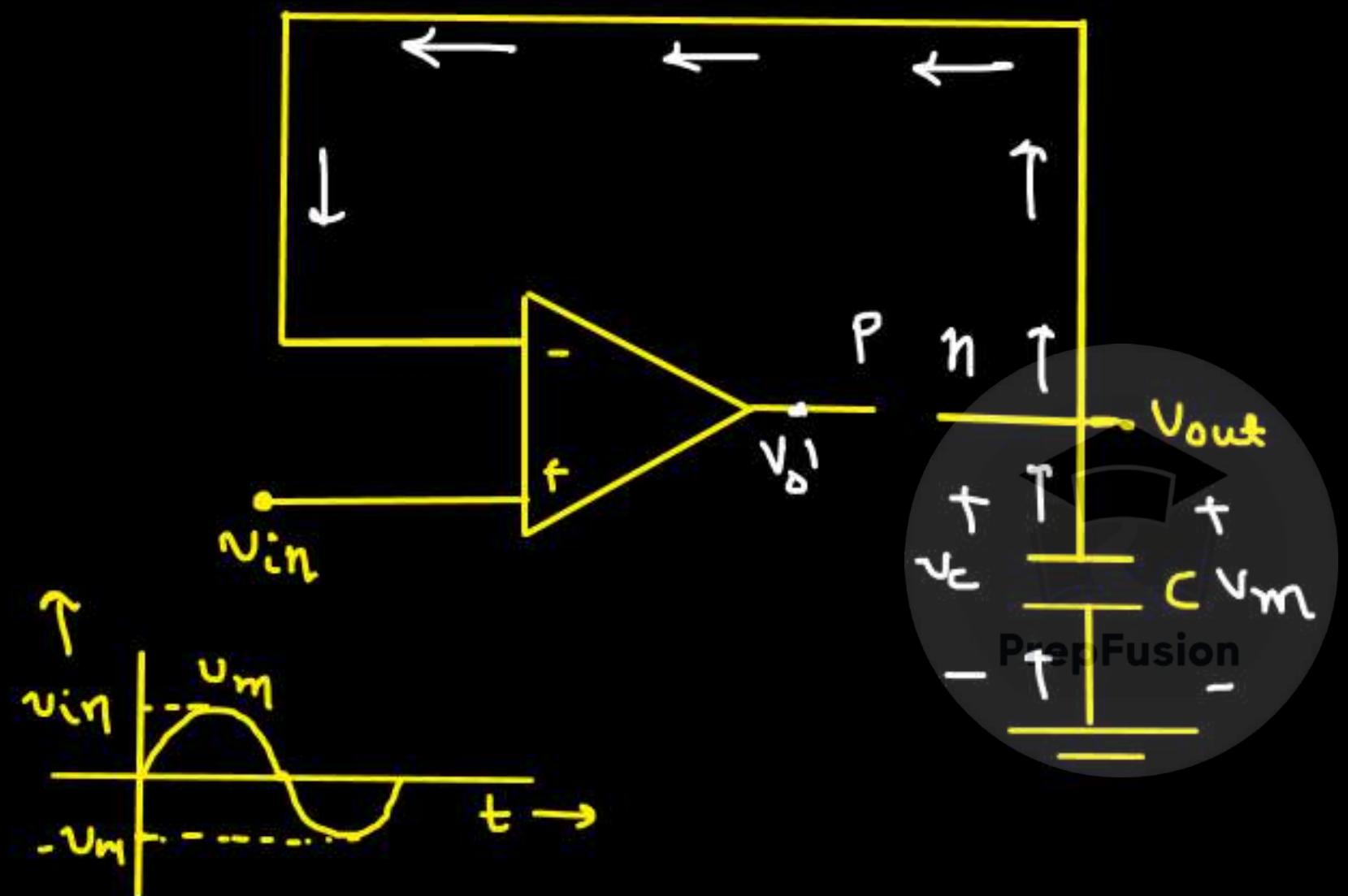

$$v_+ = v_{in} < v_m$$

$$v_- = v_m$$

Here  $v_- > v_+$

$$\Rightarrow v_o' = -v_{sat}$$




diode off

$$v_o = v_m$$


To turn on the diode,

$$v_o' = +v_{sat} \leftarrow \text{required}$$
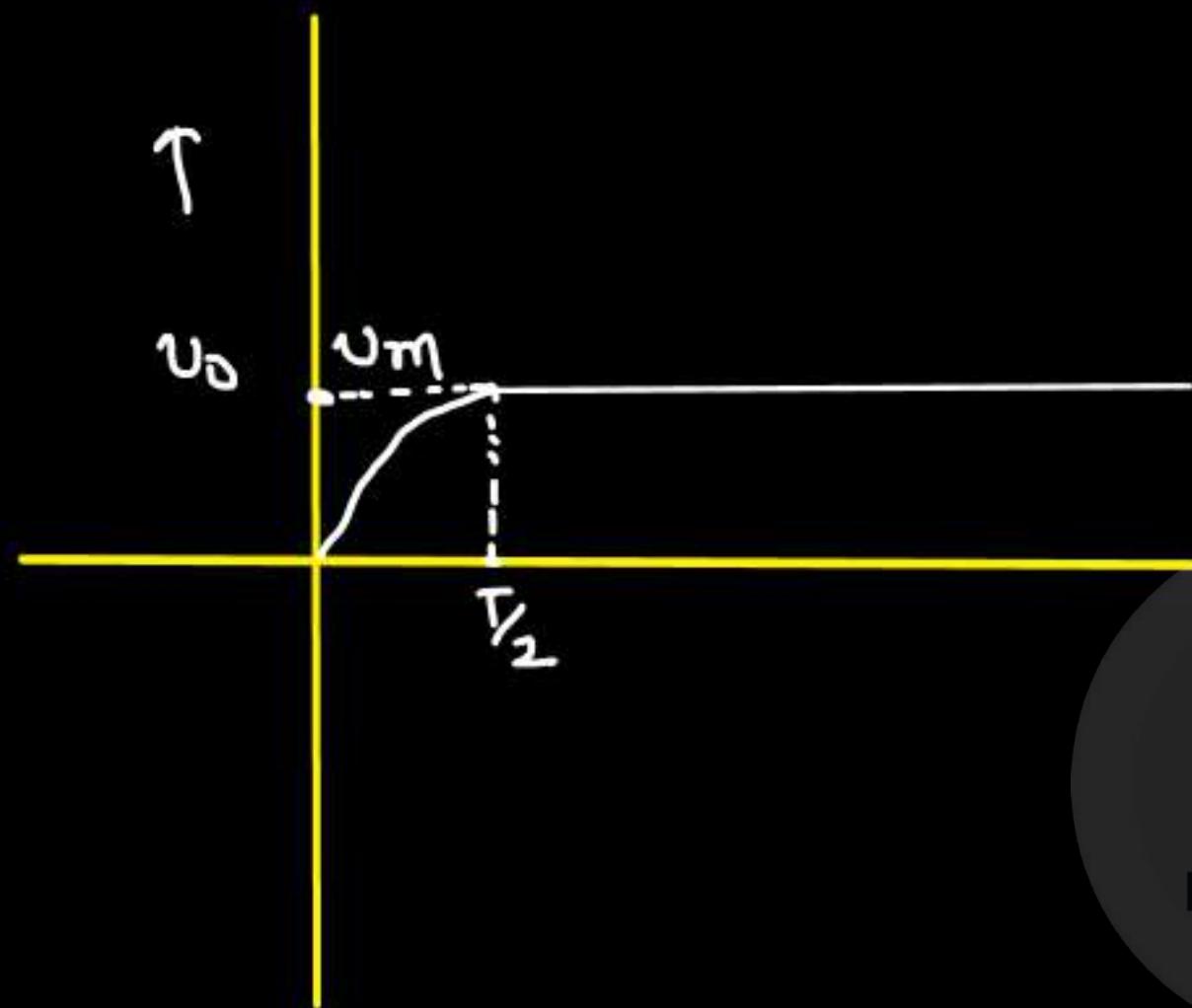
$$v_{in} > v_m \rightarrow \text{NOT POSSIBLE}$$




Q.


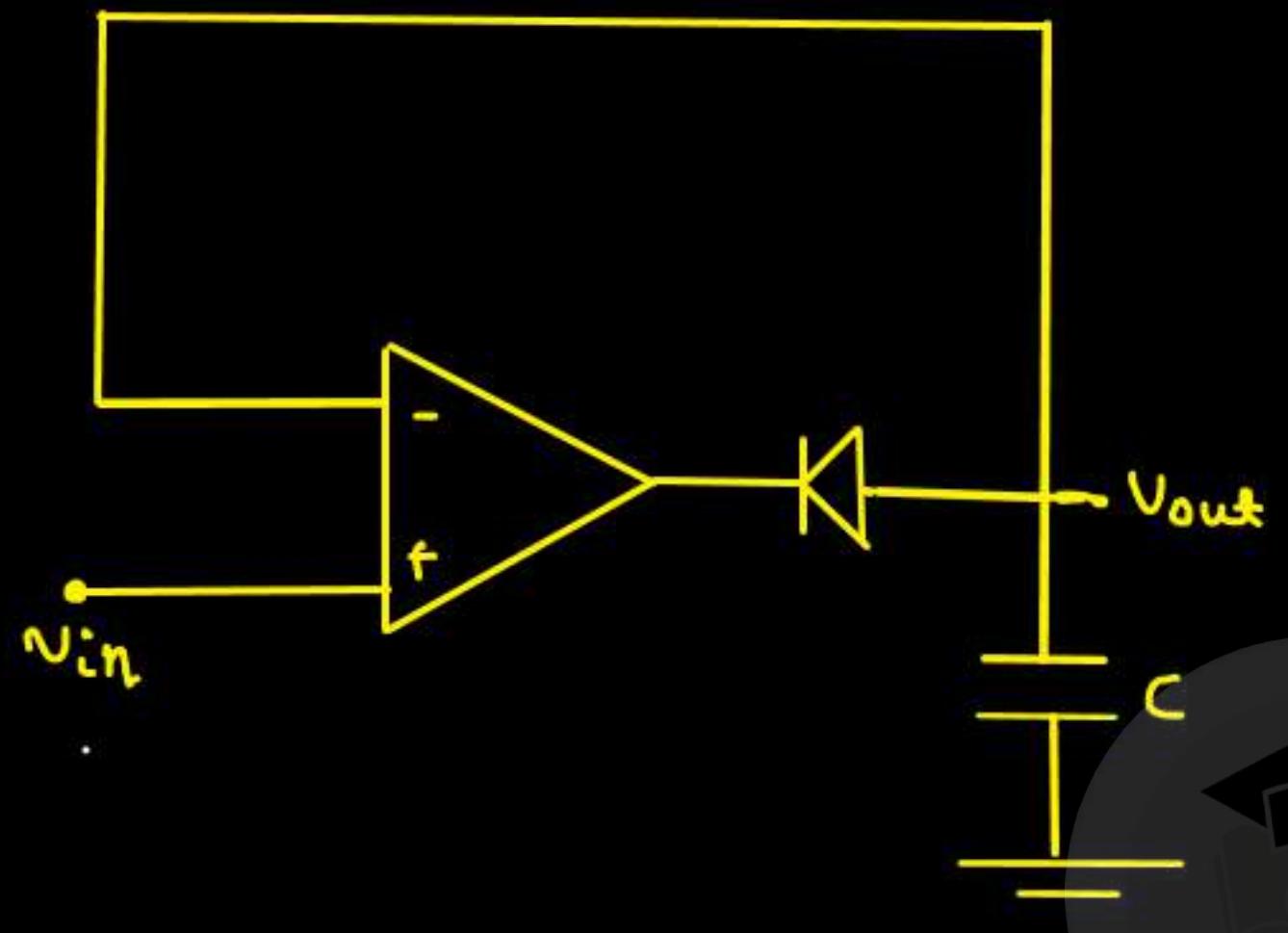


Draw  $V_o$  waveform.


↓  
negative peak detector

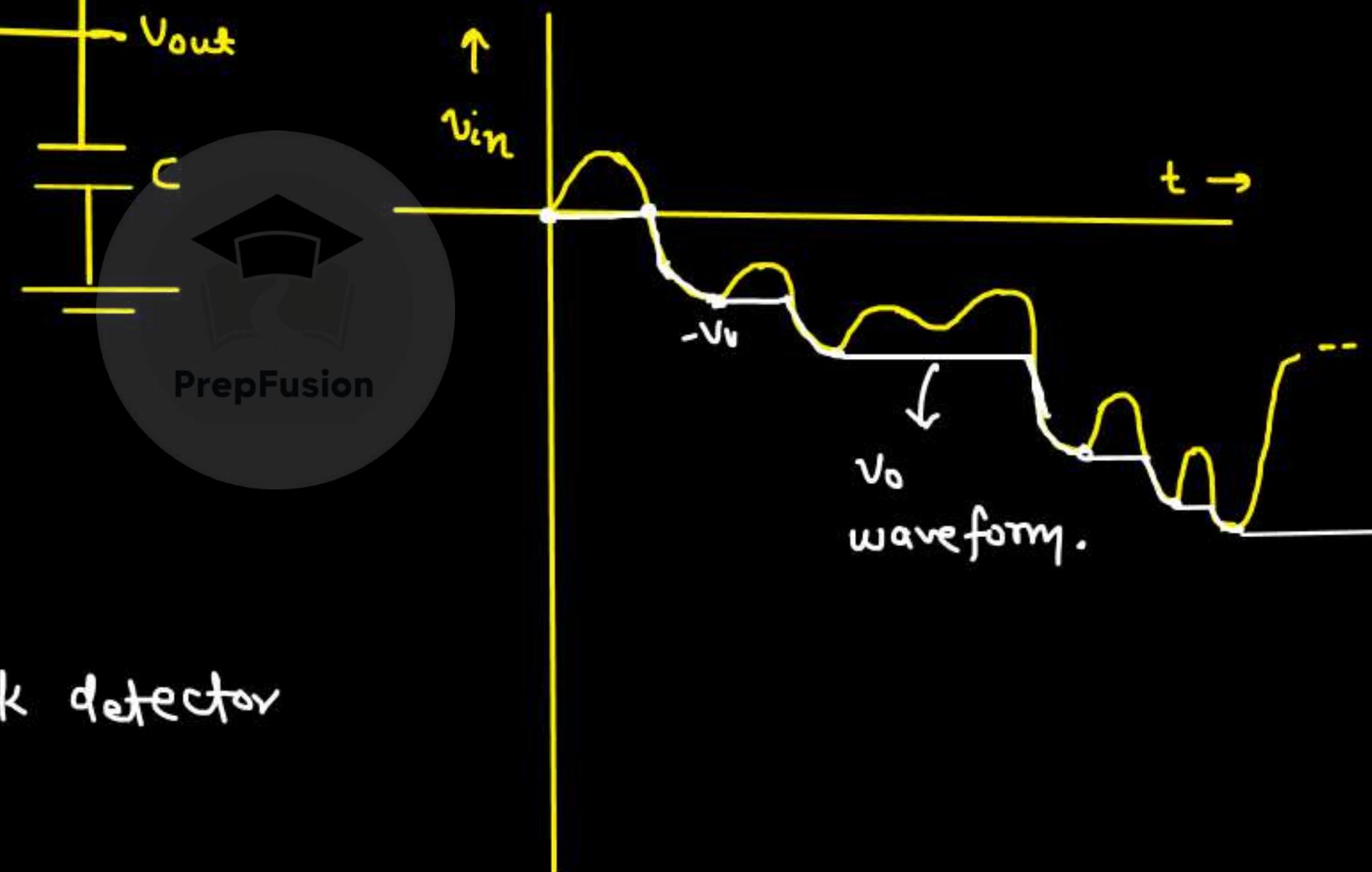

## \* Active clamper circuit:-

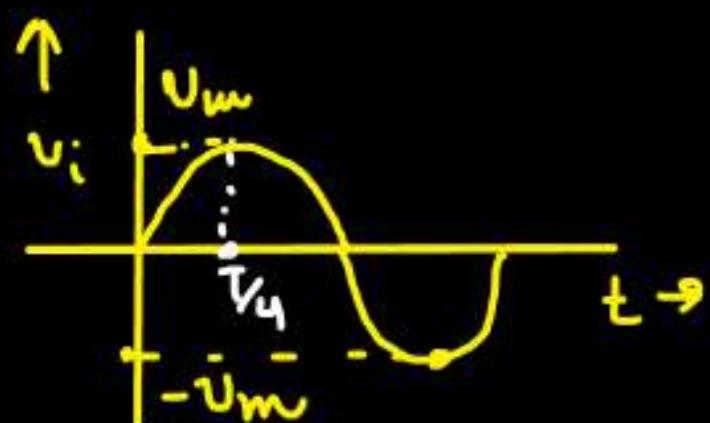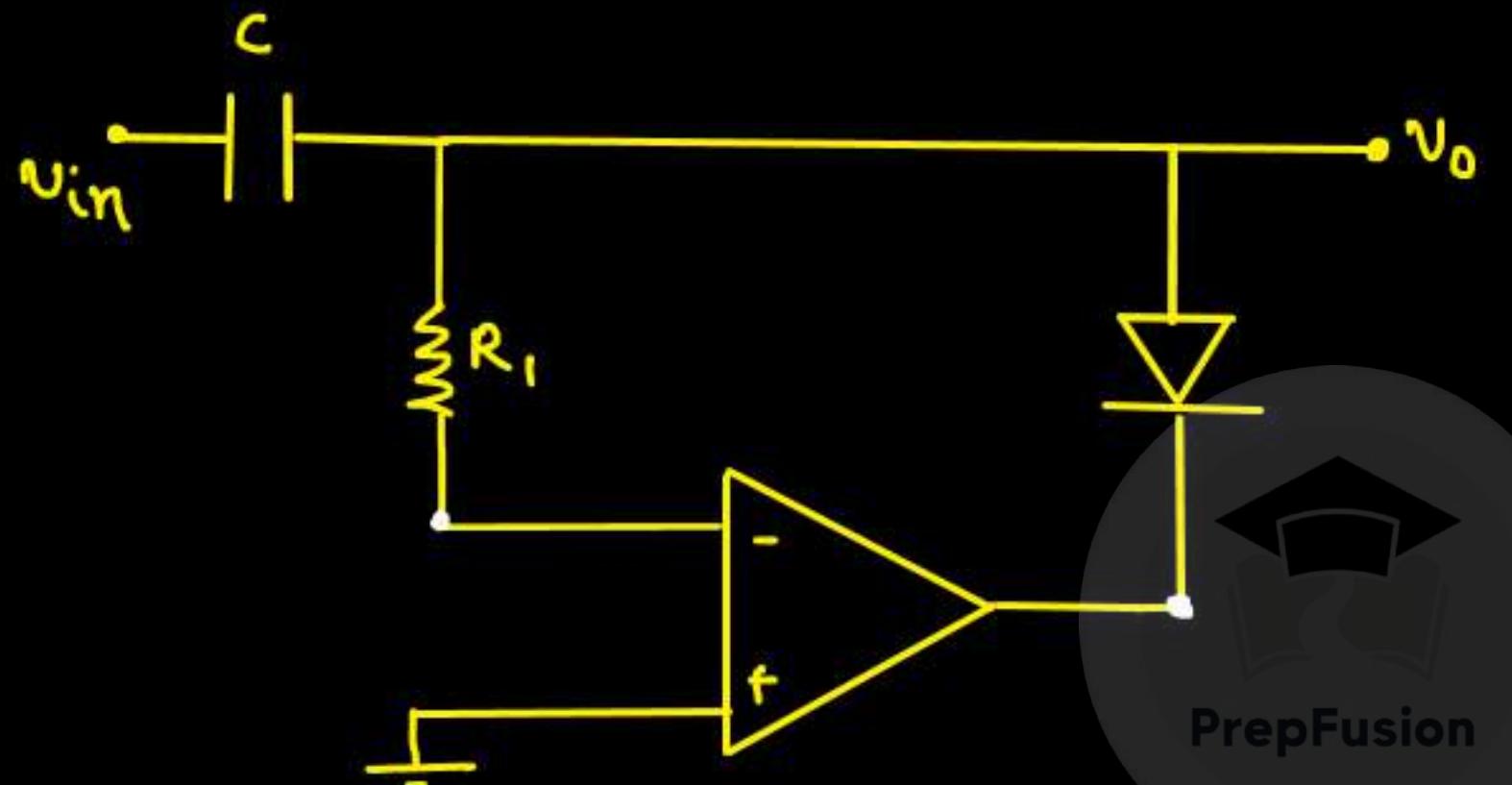

O.C. Test :-

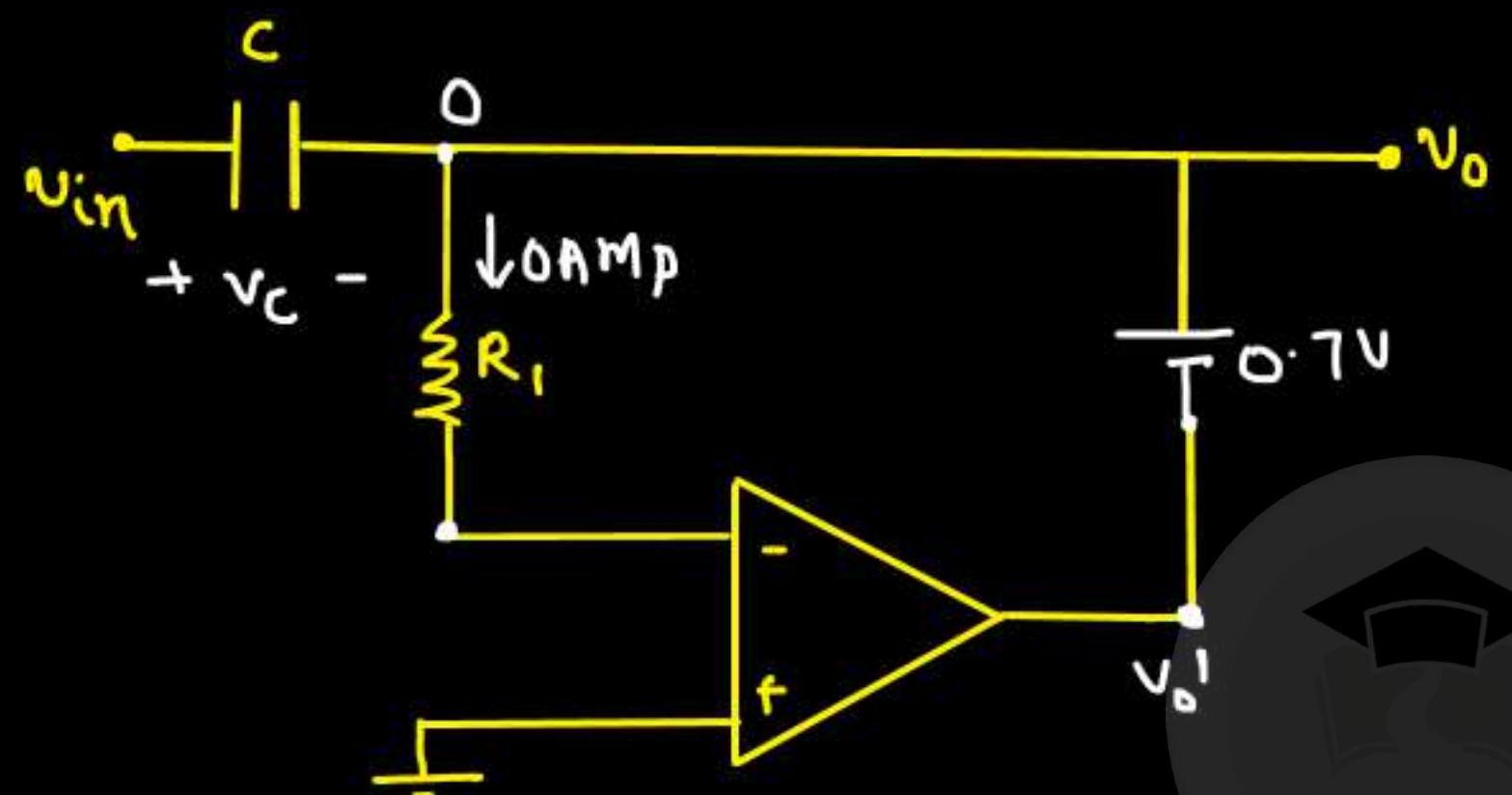

@  $t=0^+$

$$v_{in} > 0 \Rightarrow v_+ > 0$$

$$v_- = 0$$


$$\Rightarrow v_o' = -v_{sat}$$

↓  
diode ON

↓  
negative feedback

$$0 < t < T_d$$

$$v_o = 0V$$

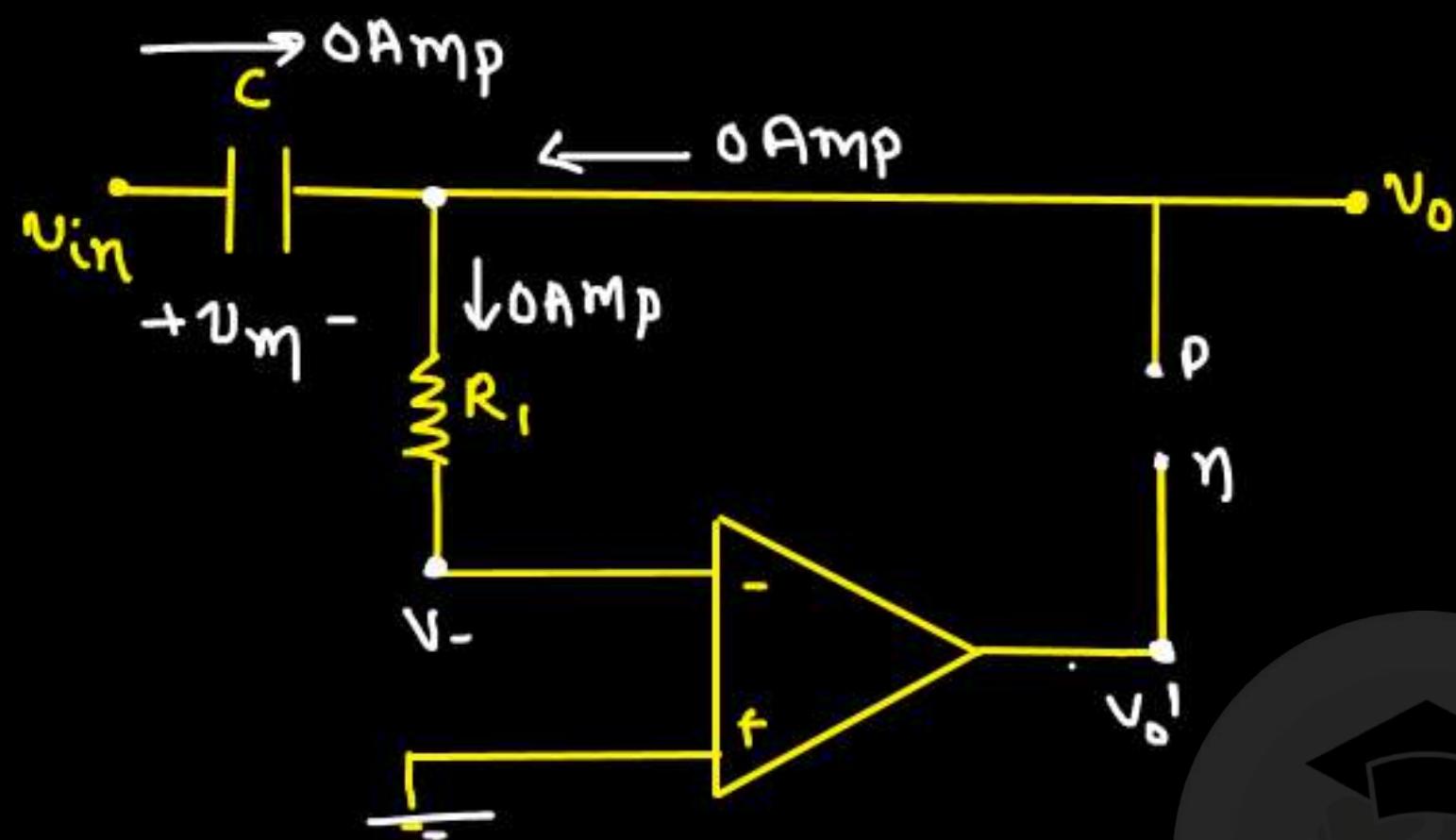

@  $t = T_4^+$

$$v_{in} < v_m$$

$$v_- < 0$$

$$\Rightarrow v_o' = +v_{sat}$$

↓  
diode is off

↓  
cap. holds its voltage


To turn on the diode


$$v_- > 0$$

$$v_{in} - v_m > 0$$

$v_{in} > v_m \rightarrow \text{NOT possible}$
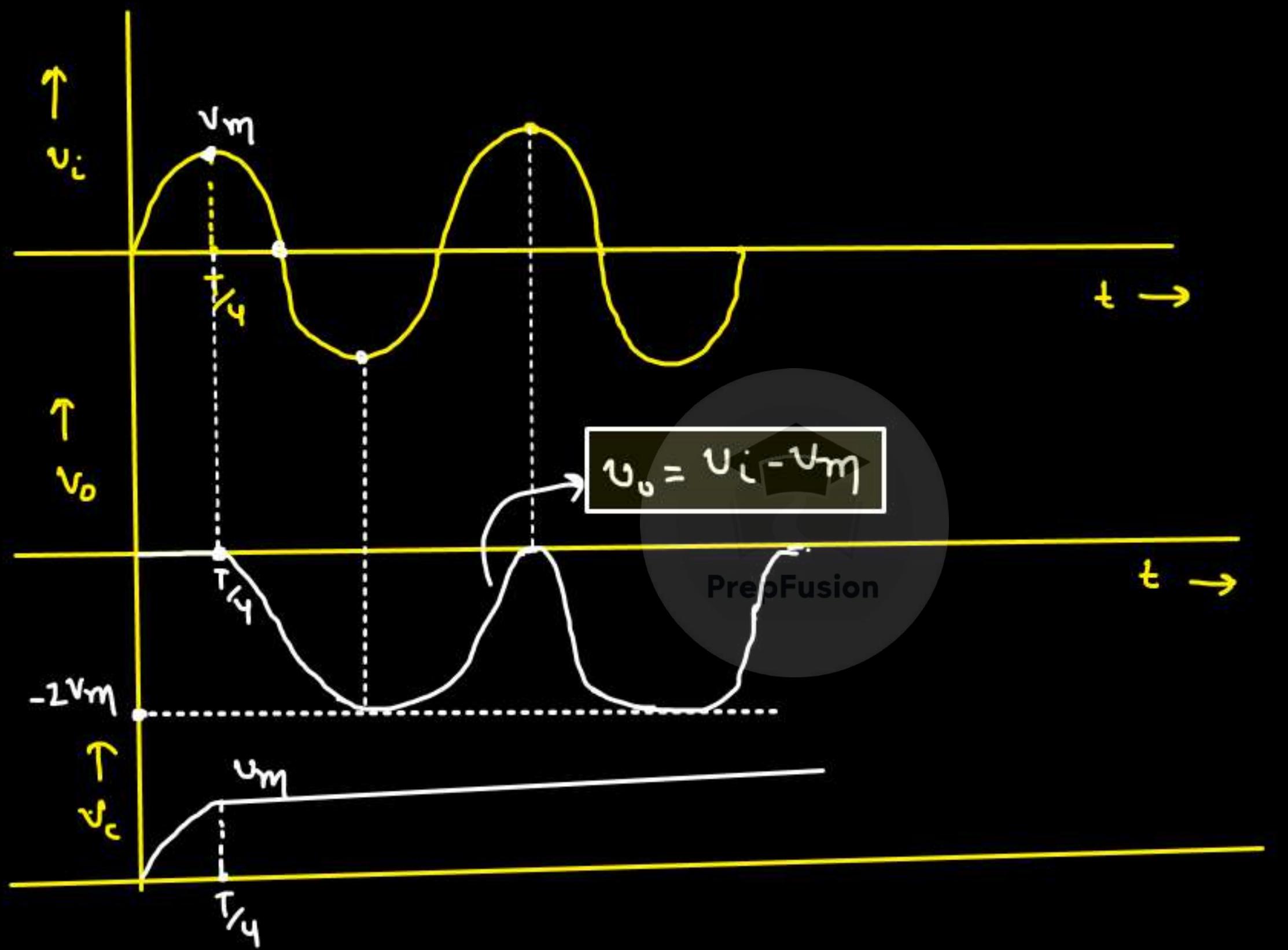
$$v_o = v_i - v_m \rightarrow \text{steady state}$$



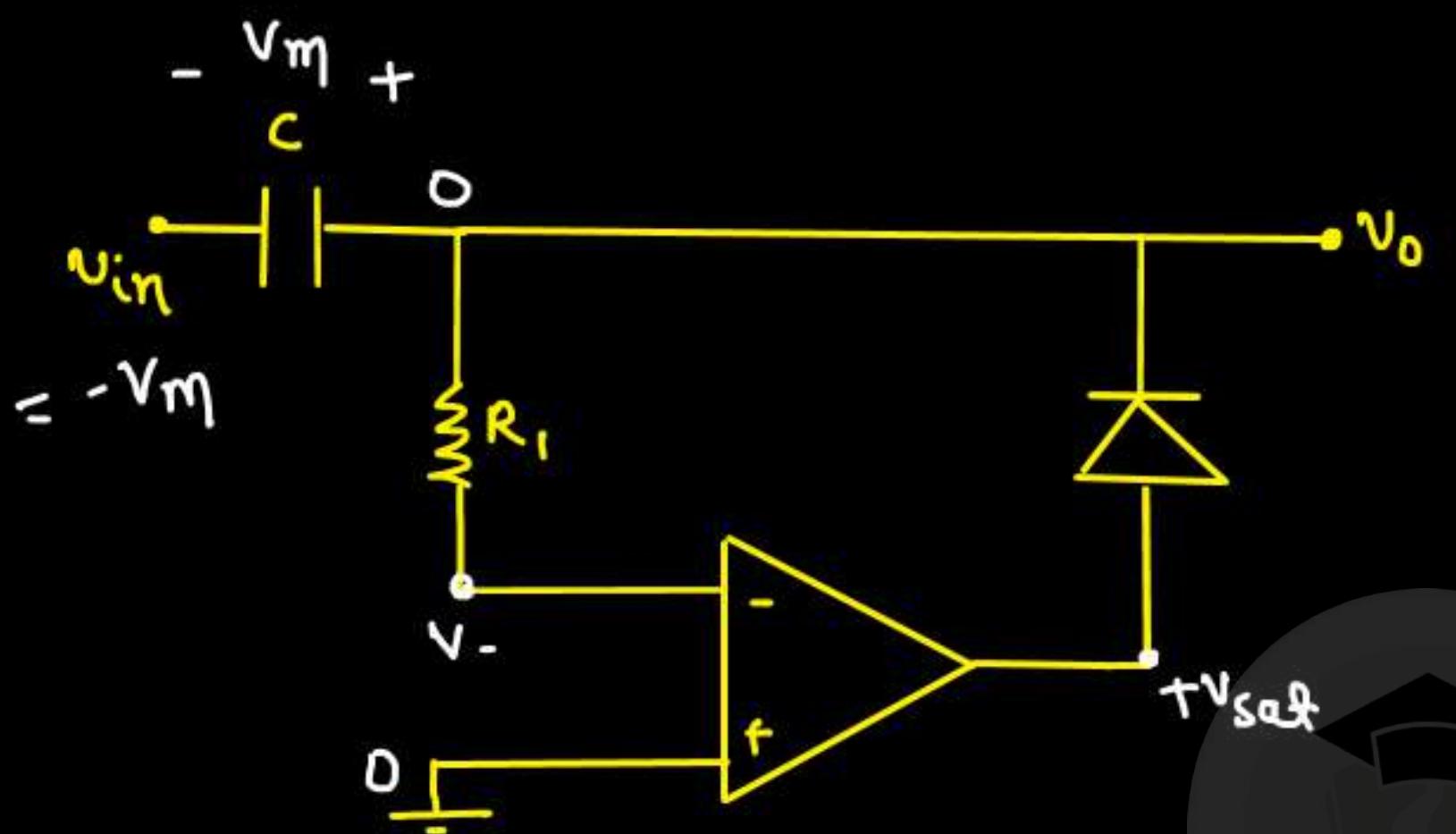



Q. steady state  $v_o$ ?

$$(v_o)_{SS} = v_{in} + v_m$$



## ⇒ OP-Amp in positive feedback :-

Q.

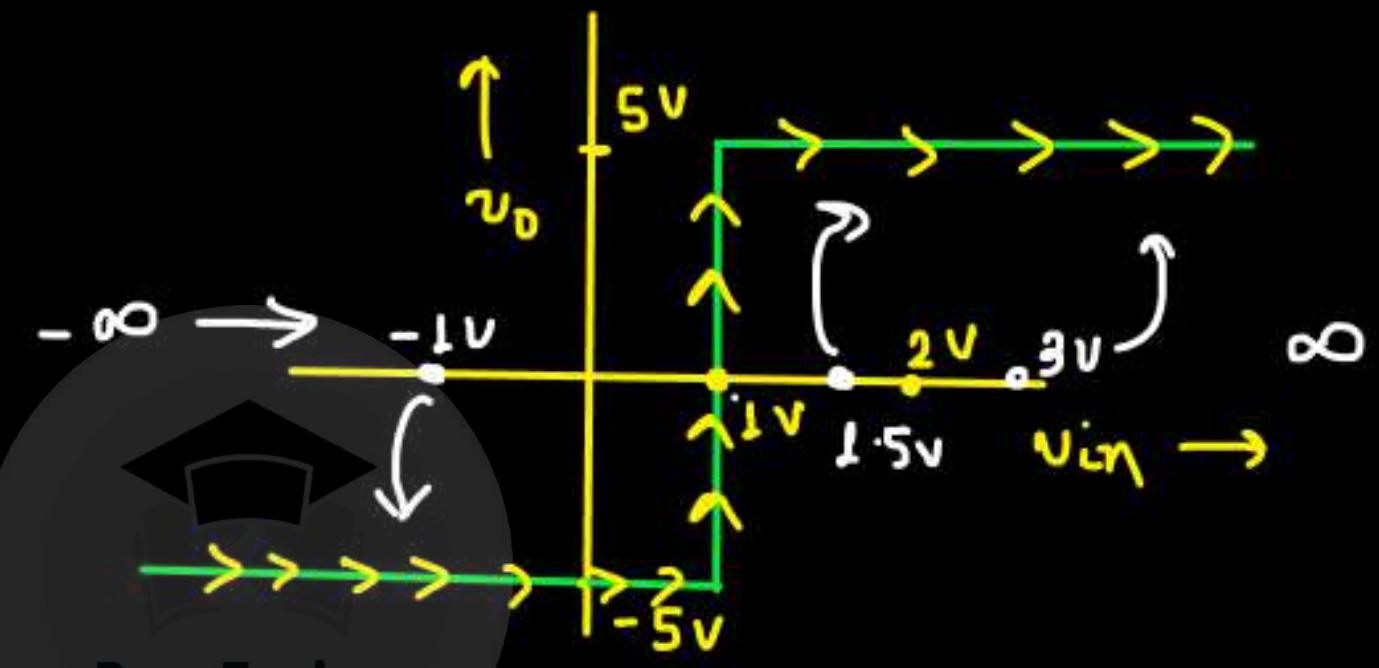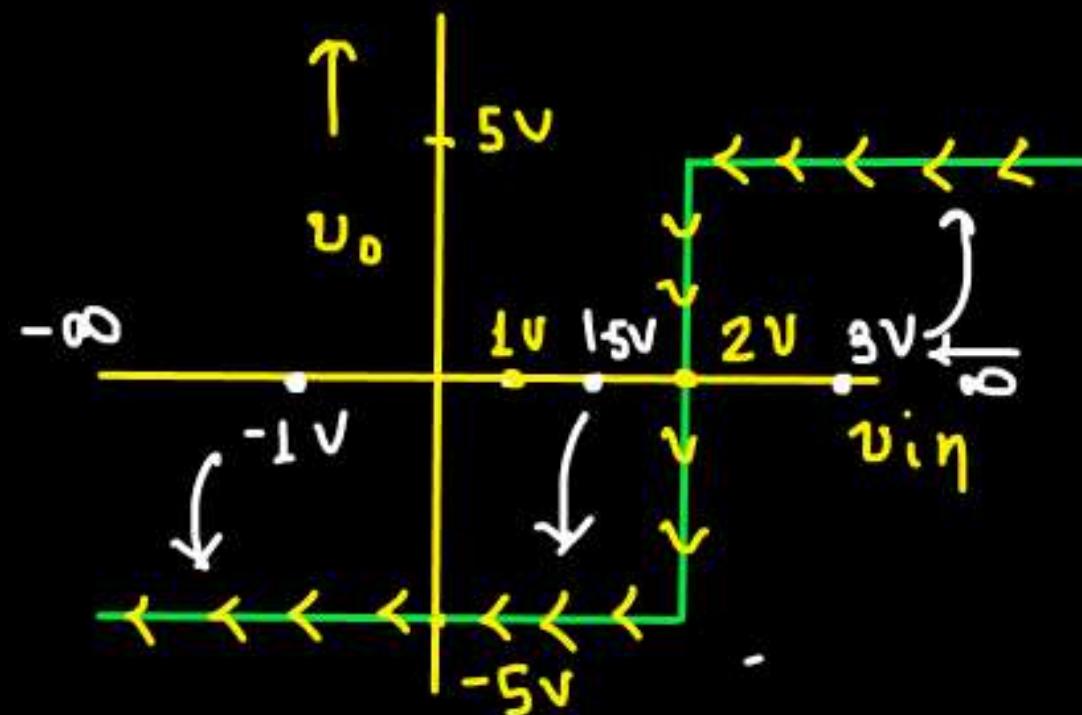

Based on the transfer characteristic given, find  $v_o$  value for -

$$(a) v_{in} = -1V$$



$$v_o = -5V$$

$$(b) v_{in} = 3V$$



$$v_o = +5V$$

$$(c) v_{in} = 1.5V$$



can't determine (Insufficient Info)

(d)  $V_{in} = 1.5 \{ V_{in} \text{ is changing from } -\infty \text{ to } \infty \}$

$\Downarrow$

+5V

(e)  $V_{in} = 1.5 \{ V_{in} \text{ is changing from } \infty \text{ to } -\infty \}$

$\Downarrow$

-5V




\*  $V_{in} > 2V \Rightarrow V_o = +5V$  [always]

$V_{in} < 1V \Rightarrow V_o = -5V$  [always]

Threshold voltage = 2V, 1V


Upper threshold voltage = 2V ( $V_{UTh}$ )

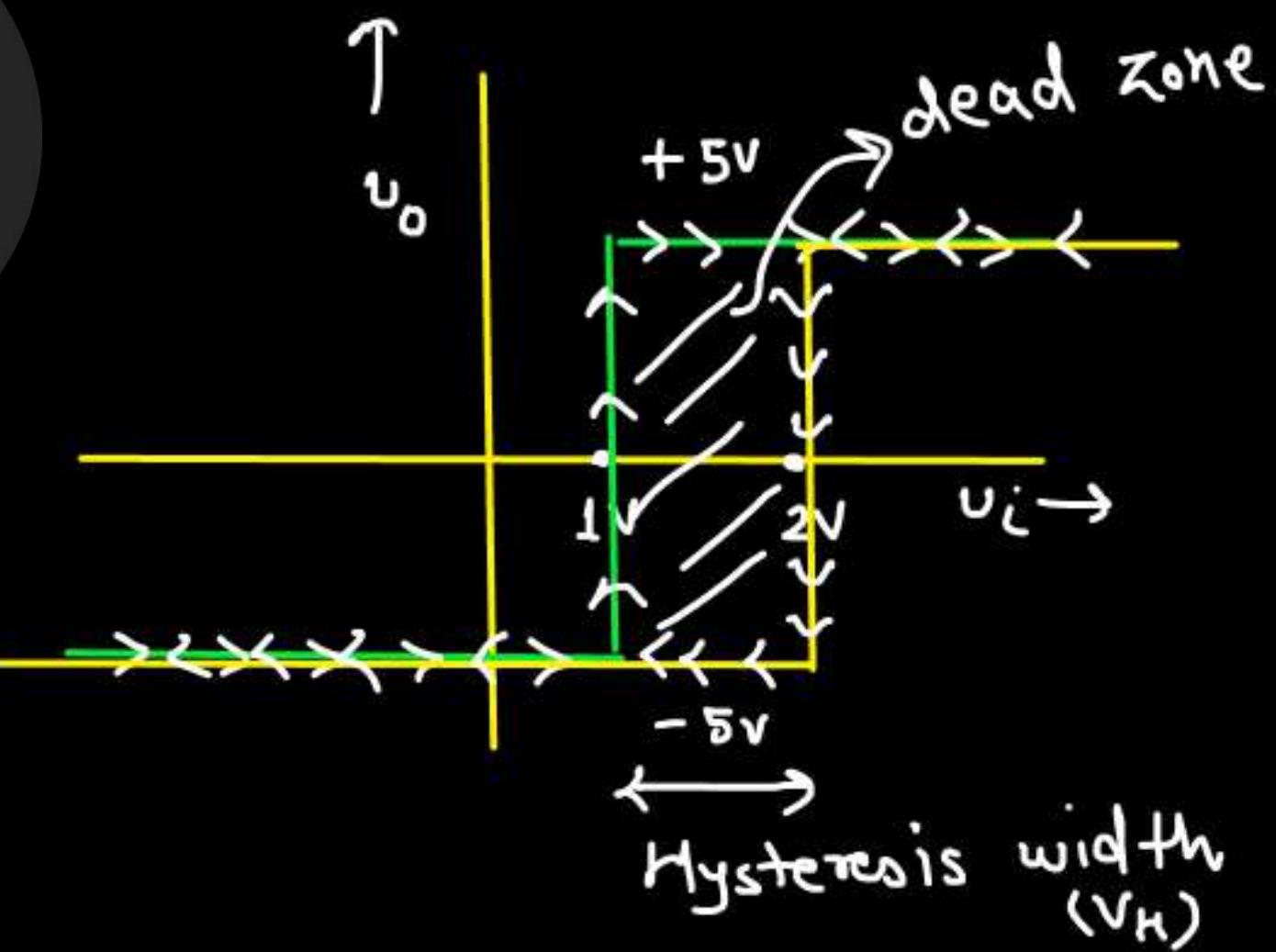Lower threshold voltage = 1V ( $V_{LTh}$ )



## ⇒ Concept of Schmitt trigger :-

### (i) Non-inverting Schmitt trigger :-

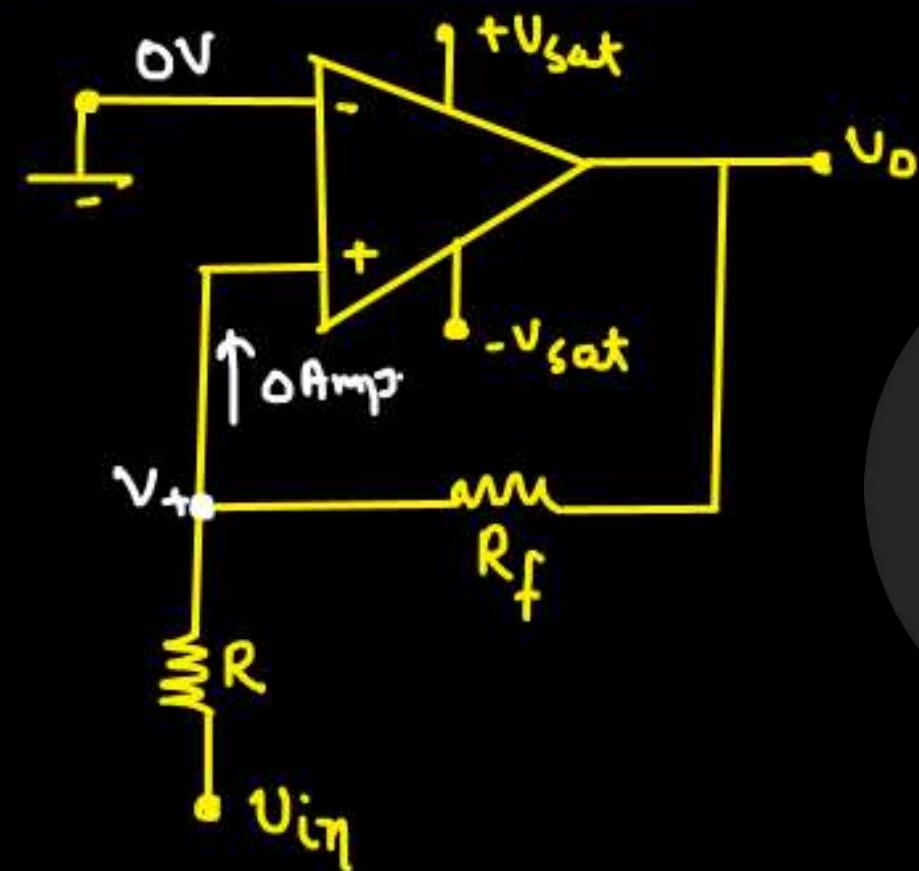

$$V_o = -\frac{R_f}{R} V_{in}$$

concept of virtual short is  
not valid in positive f/b

$V_o$  can be either  $+V_{sat}$  or  $-V_{sat}$

$$V_- = 0V$$

$$V_+ = \frac{V_{in} R_f + V_o R}{R_f + R}$$

(i) Assuming  $v_o = +v_{sat}$

$$v_+ = \frac{v_{sat} R + v_{in} R_f}{R + R_f}, \quad v_- = 0V$$

$$v_+ > v_- \Rightarrow v_o = +v_{sat}$$



$$\frac{v_{sat} R + v_{in} R_f}{R + R_f} > 0$$

$$v_{in} > -\frac{v_{sat} R}{R_f}$$

$$v_{in} > -\beta v_{sat}$$

where  $\beta = \frac{R}{R_f} \Rightarrow v_o = +v_{sat}$
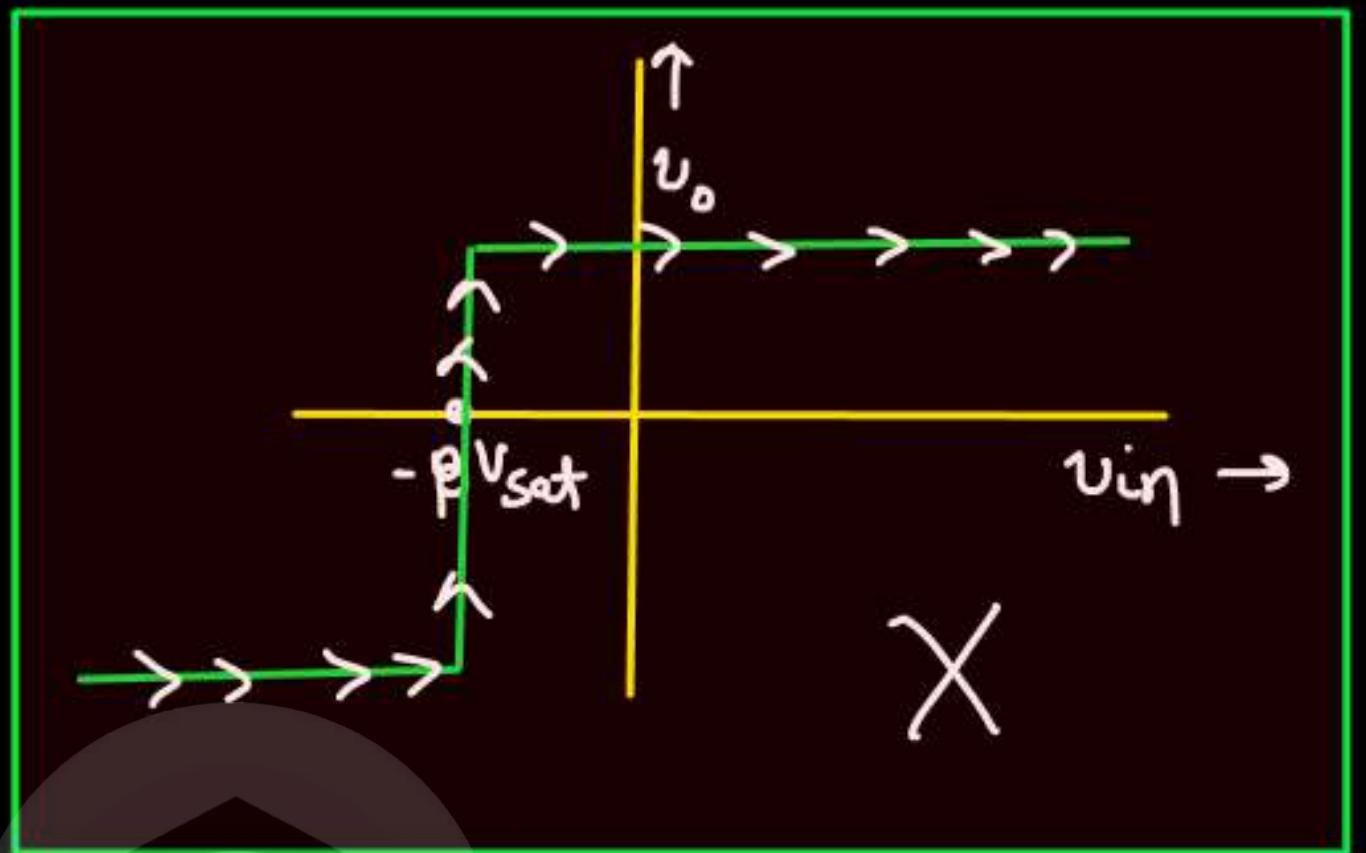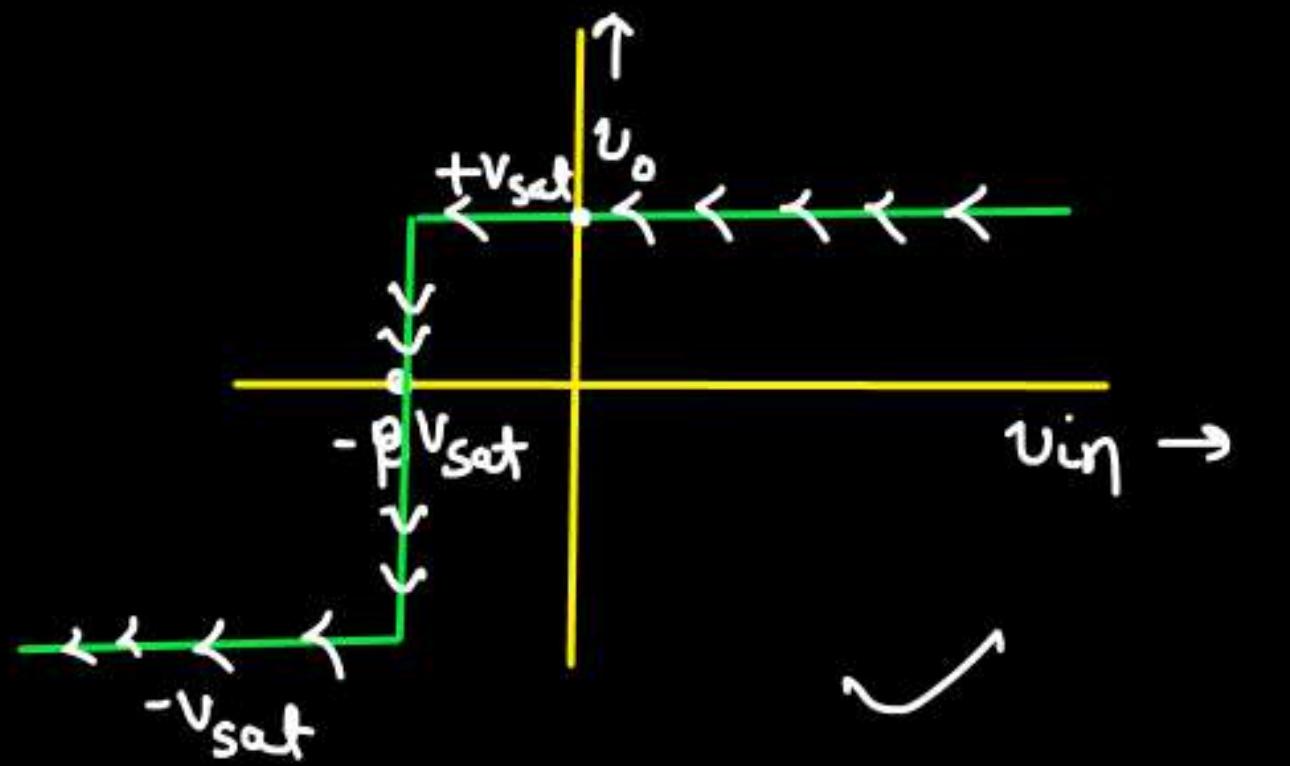
$$v_{in} < -\beta v_{sat} \Rightarrow v_o = -v_{sat}$$



(ii)

Assuming  $V_o = -V_{sat}$

$$V_t = \frac{-V_{sat} R + V_{in} R_f}{R_f + R}, \quad V_- = 0V$$


$$V_t < V_- \Rightarrow V_o = -V_{sat}$$

$$\frac{-V_{sat} R + U_{in} R_f}{R_f + R} < 0$$


$$U_{in} < \frac{R}{R_f} V_{sat}$$


$$\Rightarrow \begin{cases} U_{in} < \beta V_{sat} & \Rightarrow U_o = -V_{sat} \\ U_{in} > \beta V_{sat} & \Rightarrow U_o = +V_{sat} \end{cases}$$

PrepFusion


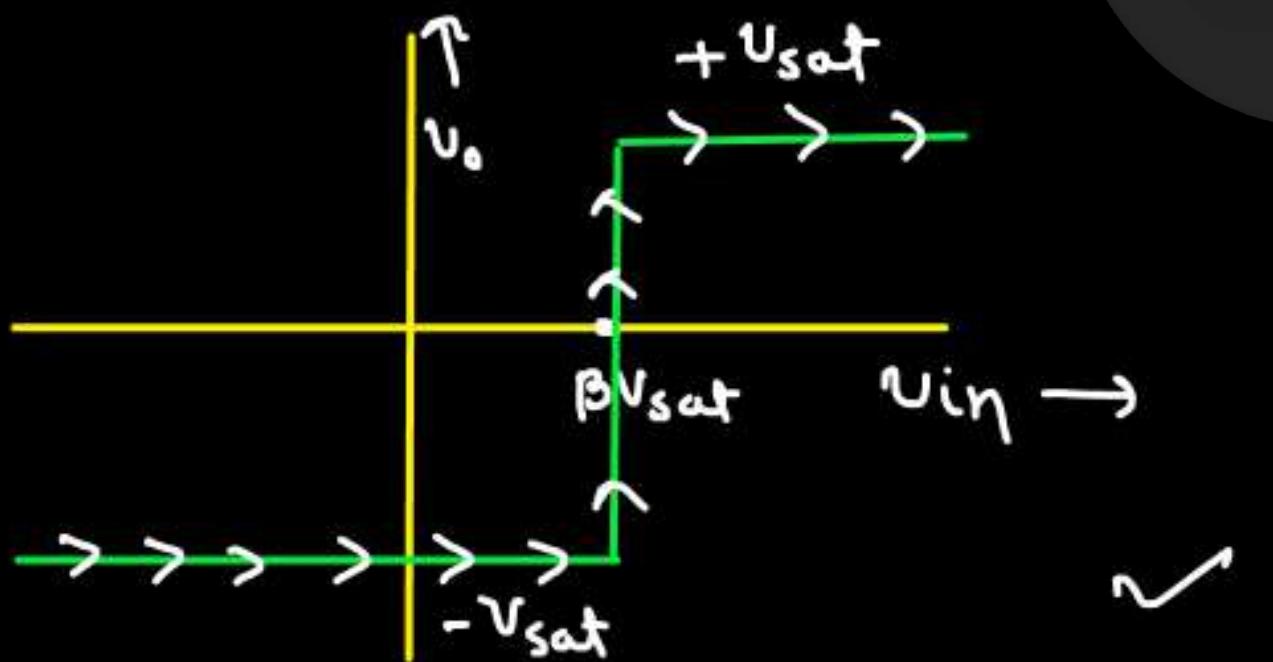


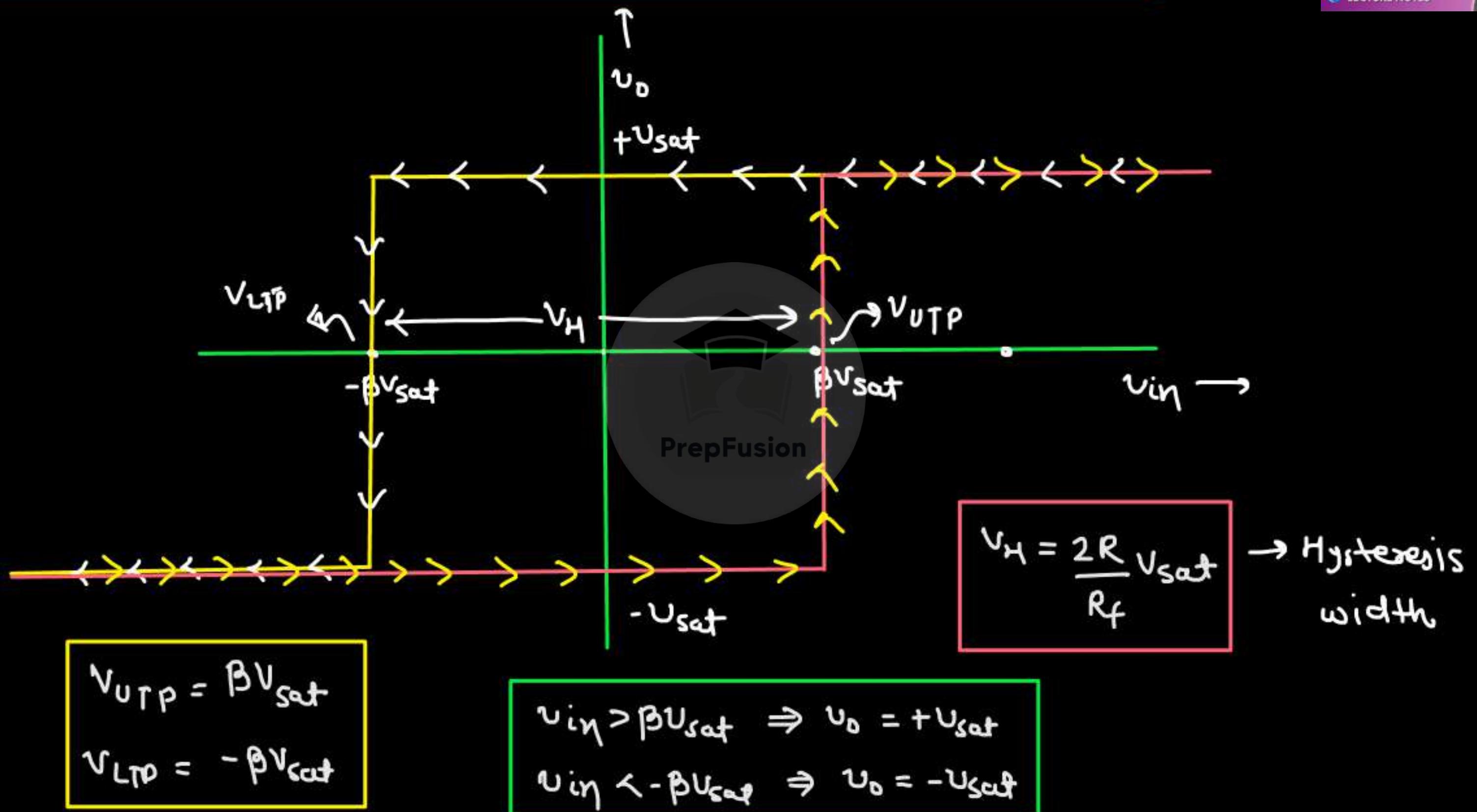\* For Non-inverting Schmitt trigger, Hysteresis is acw.



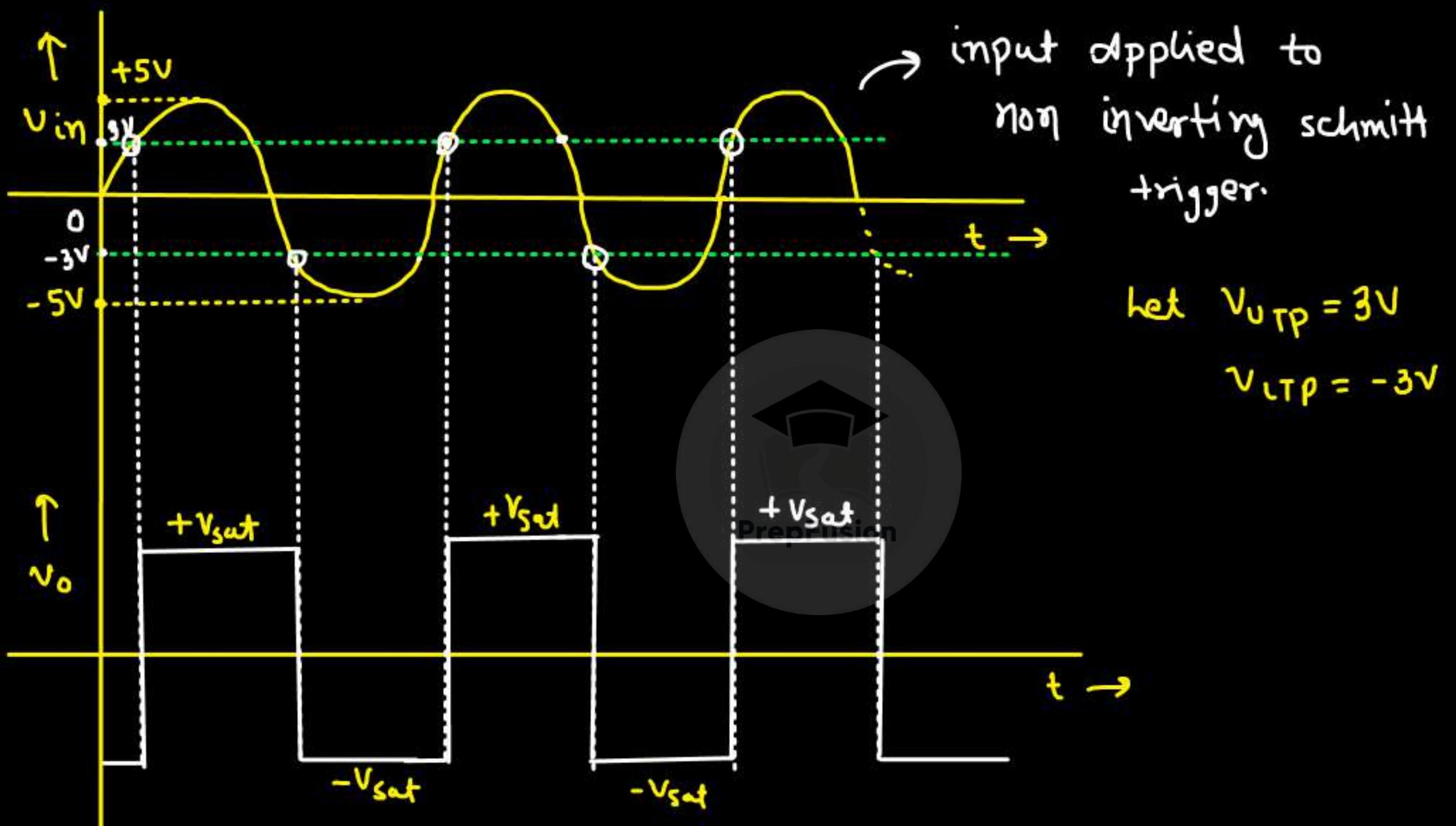


## Non-inverting Schmitt Trigger :-

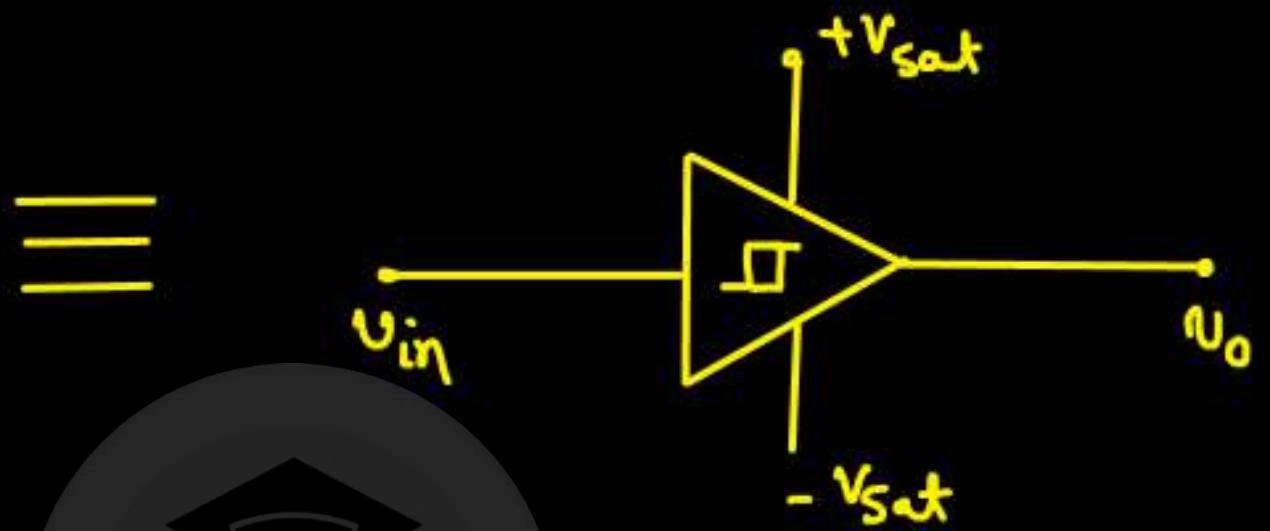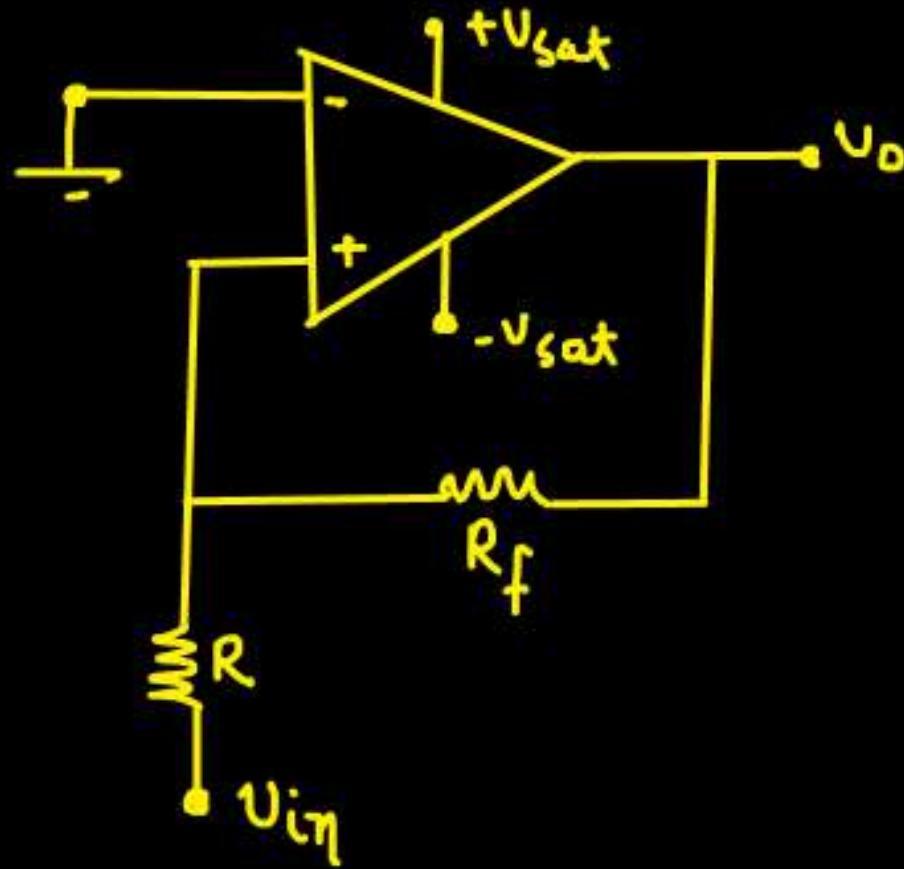

PrepFusion

$\uparrow \uparrow \uparrow \Rightarrow V_o = +V_{sat}$  or High  
 $\downarrow \downarrow \downarrow \Rightarrow V_o = -V_{sat}$  or Low  
 dead zone / Hysteresis

## (ii) Inverting Schmitt trigger:-

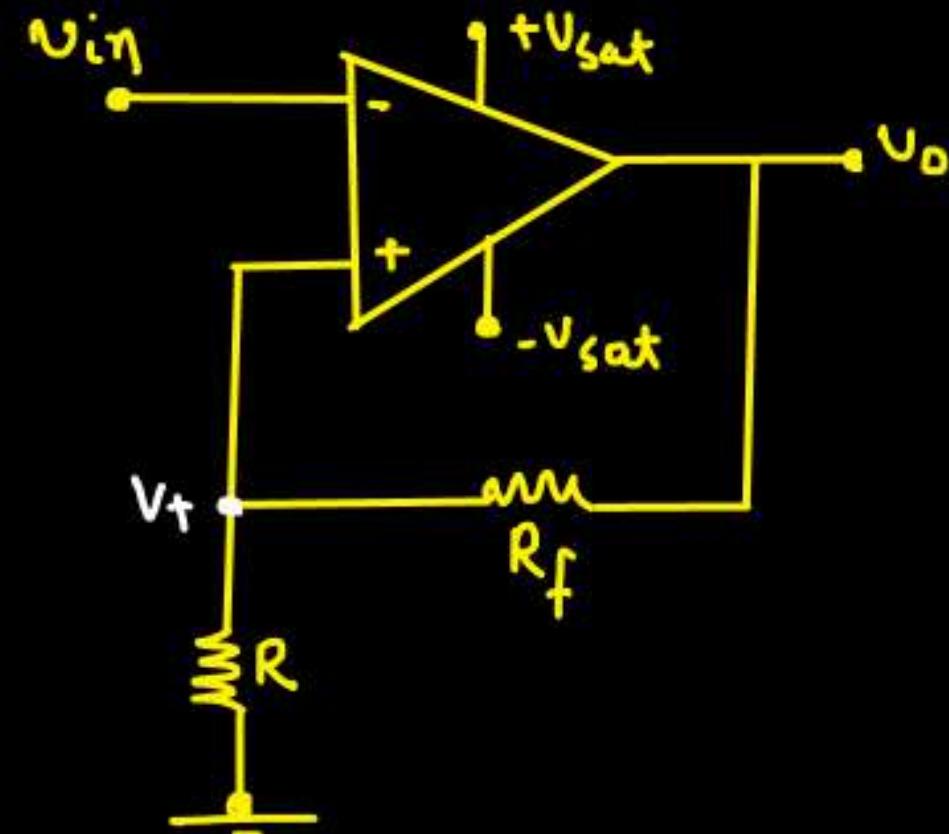

$$V_+ = \frac{V_o R}{R + R_f}, \quad V_- = V_{in}$$

Trick:-


$$V_t = \frac{V_o R}{R + R_f}, \quad V_- = V_{in}$$

$$V_{in} = \frac{V_o R}{R + R_f}$$

$$V_{U_{TP}} = \frac{V_{sat} R}{R + R_f}$$

$$, \quad V_{L_{TP}} = -\frac{V_{sat} R}{R + R_f}$$

PrepFusion

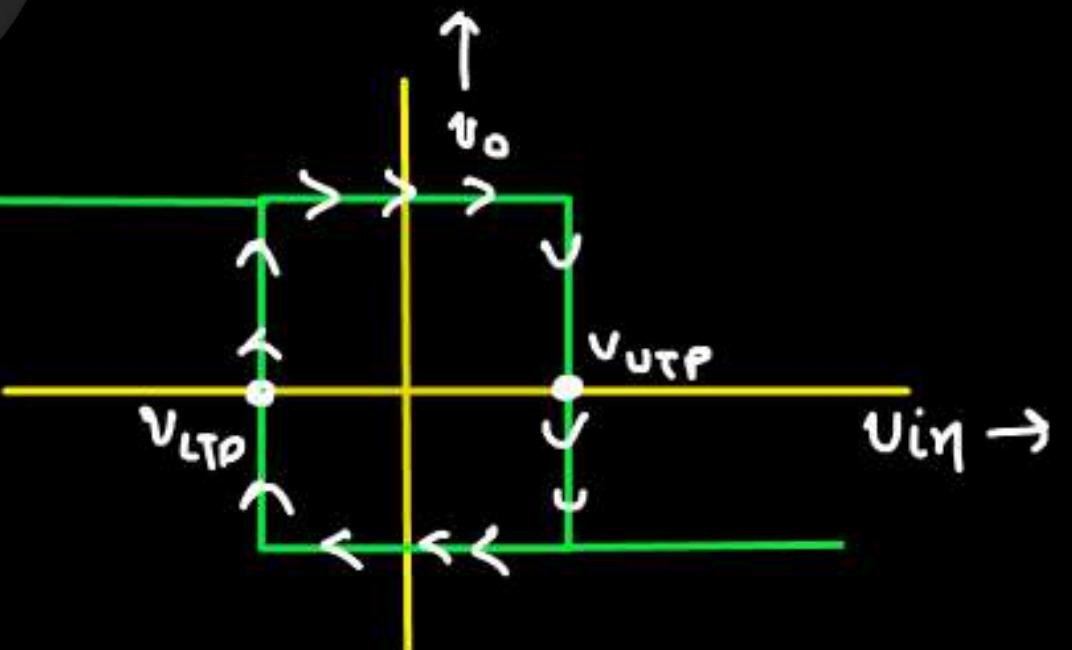

(i)

Assuming  $V_o = -V_{sat}$

$$V_+ = \frac{-V_{sat} R}{R + R_f}, \quad V_- = V_{in}$$

$$V_+ < V_- \Rightarrow V_o = -V_{sat}$$

$$V_{in} > \frac{-V_{sat} \times R}{R + R_f} \Rightarrow V_o = -V_{sat}$$

PrepFusion

$$V_{in} > -\beta V_{sat} \Rightarrow V_o = -V_{sat}$$

$$V_{in} < -\beta V_{sat} \Rightarrow V_o = +V_{sat}$$

$$\beta = \frac{R}{R + R_f}$$

(ii) Assuming  $v_o = +v_{sat}$

$$v_+ = \frac{v_{sat} R}{R + R_f}, \quad v_- = v_{in}$$


$$v_+ > v_- \Rightarrow v_o = +v_{sat}$$

$$v_{in} < \frac{v_{sat} R}{R + R_f} \Rightarrow v_o = +v_{sat}$$

$$v_{in} < \beta v_{sat} \Rightarrow v_o = +v_{sat}$$

$$v_{in} > \beta v_{sat} \Rightarrow v_o = -v_{sat}$$

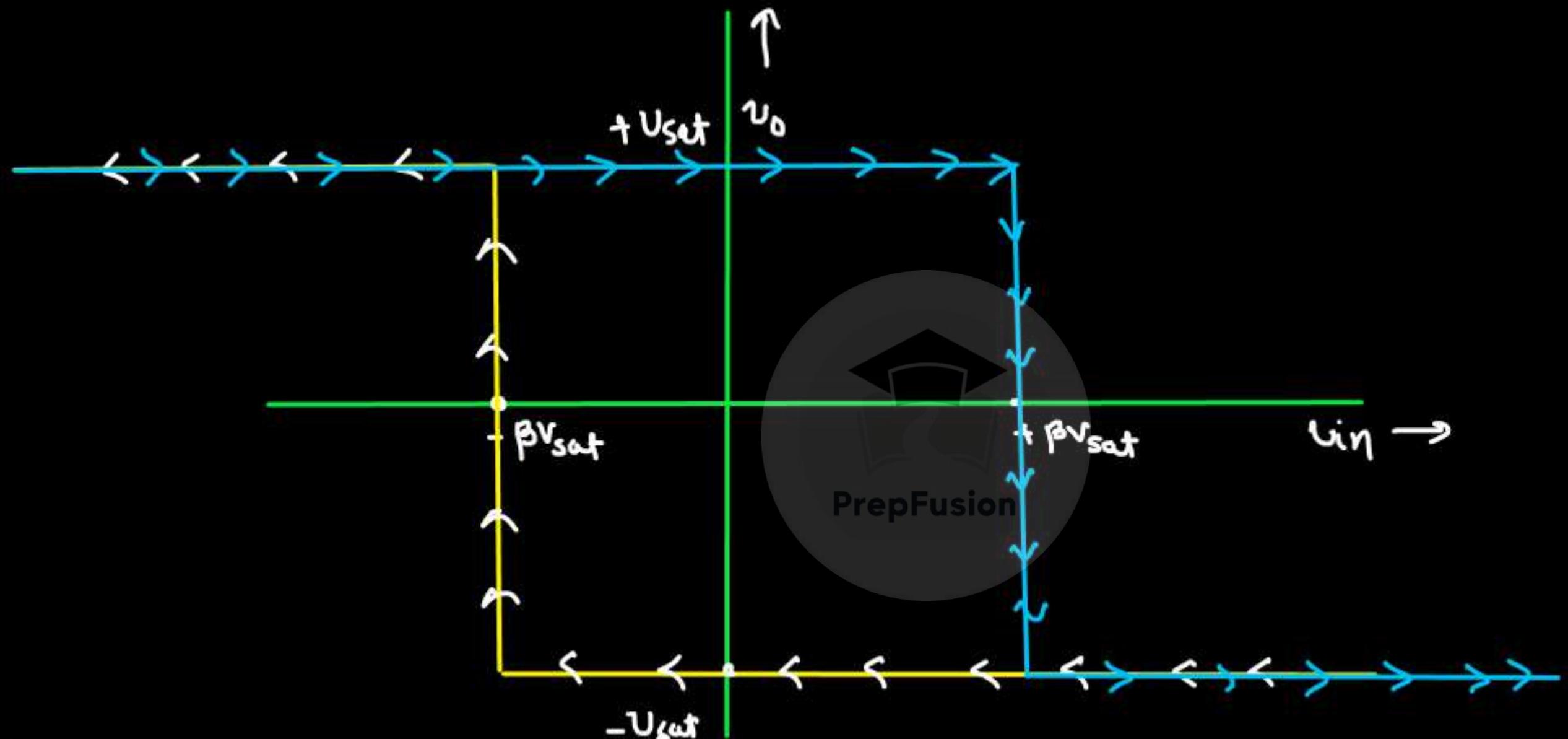
For Inverting schmitt trigger, the dirn of Hysteresis is CW





$$V_{U_{TP}} = +\beta V_{sat}$$

$$V_{L_{TP}} = -\beta V_{sat}$$
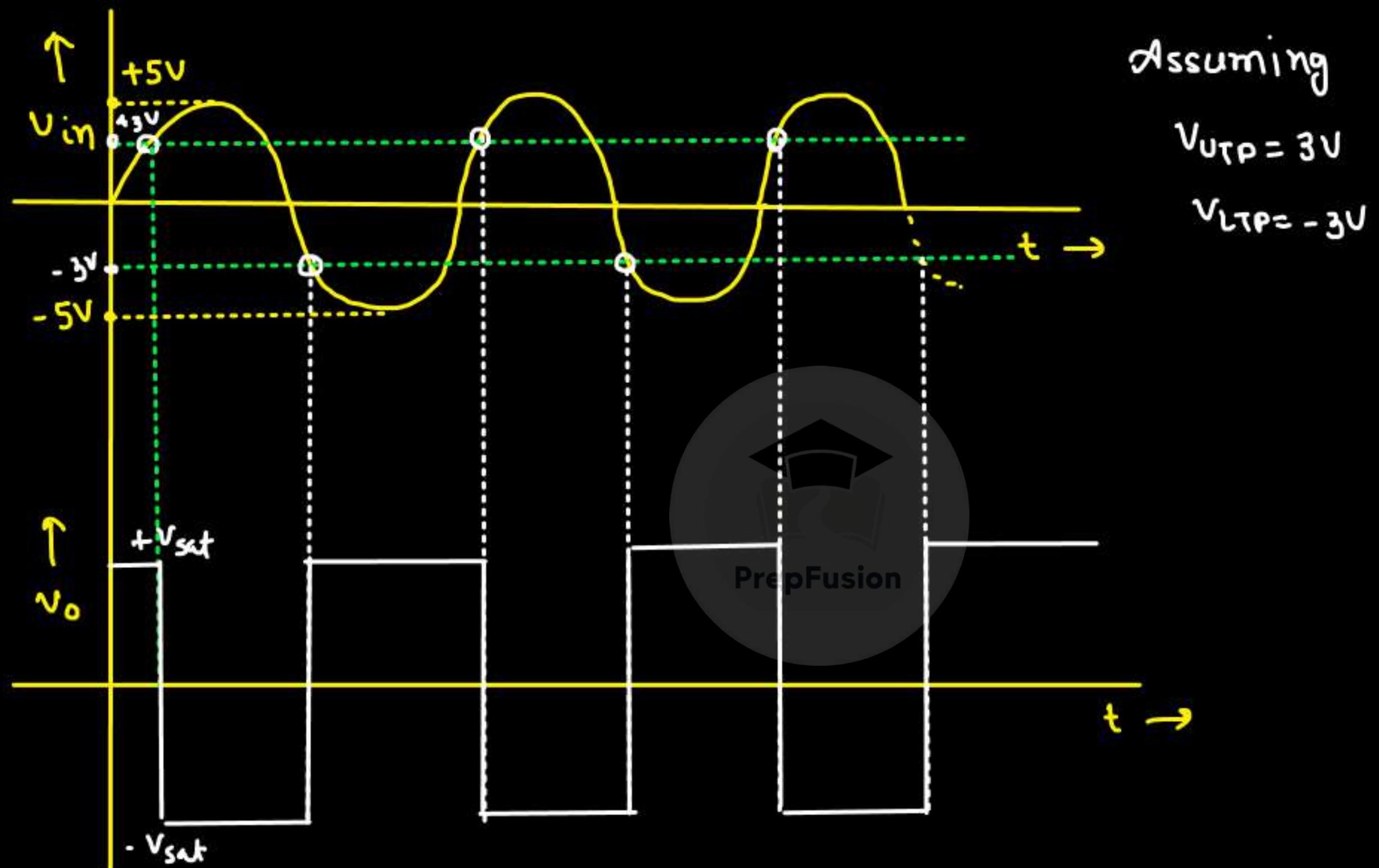
$$V_H = 2\beta V_{sat} = \frac{2R}{R + R_f} V_{sat}$$



## Inverting Schmitt Trigger :-

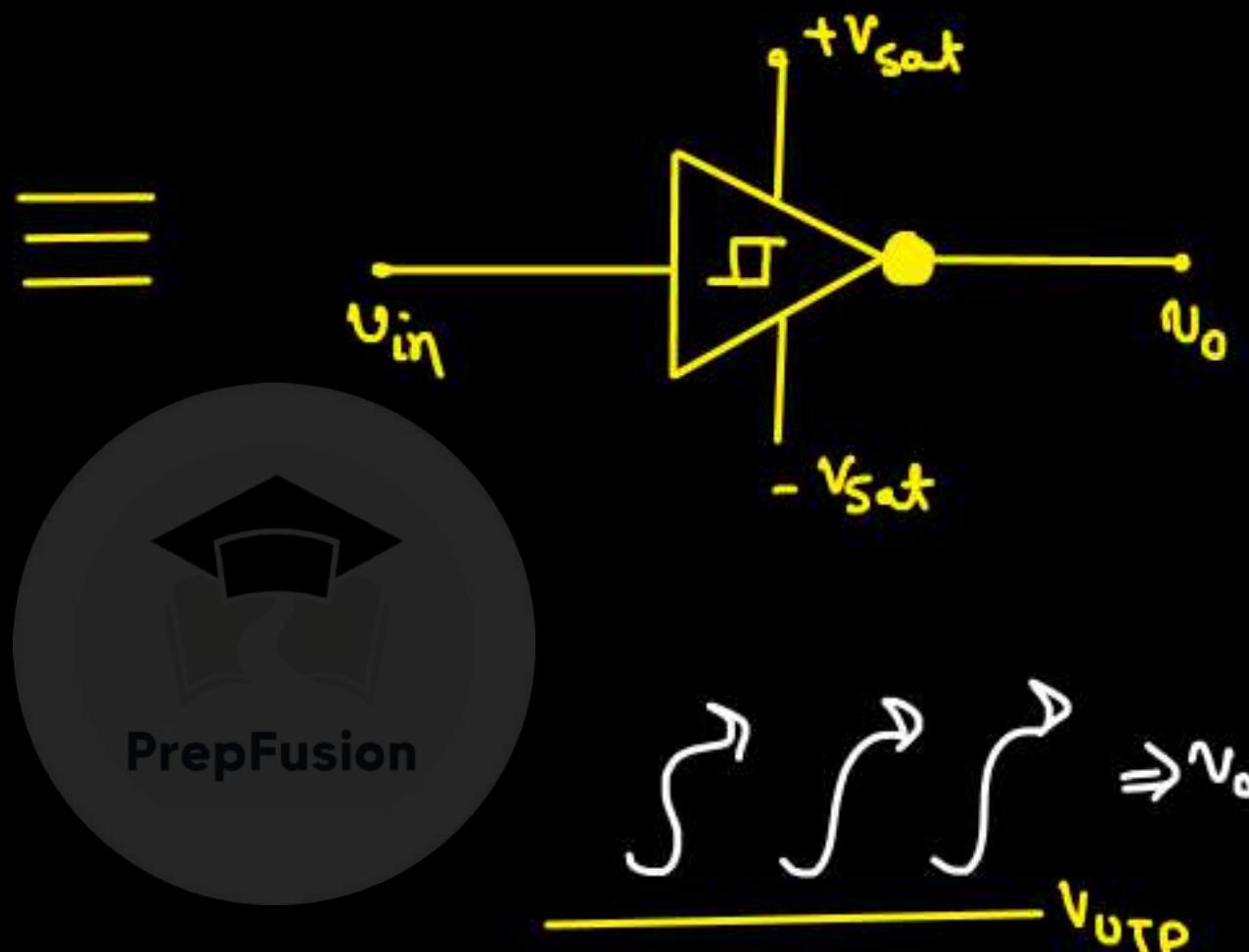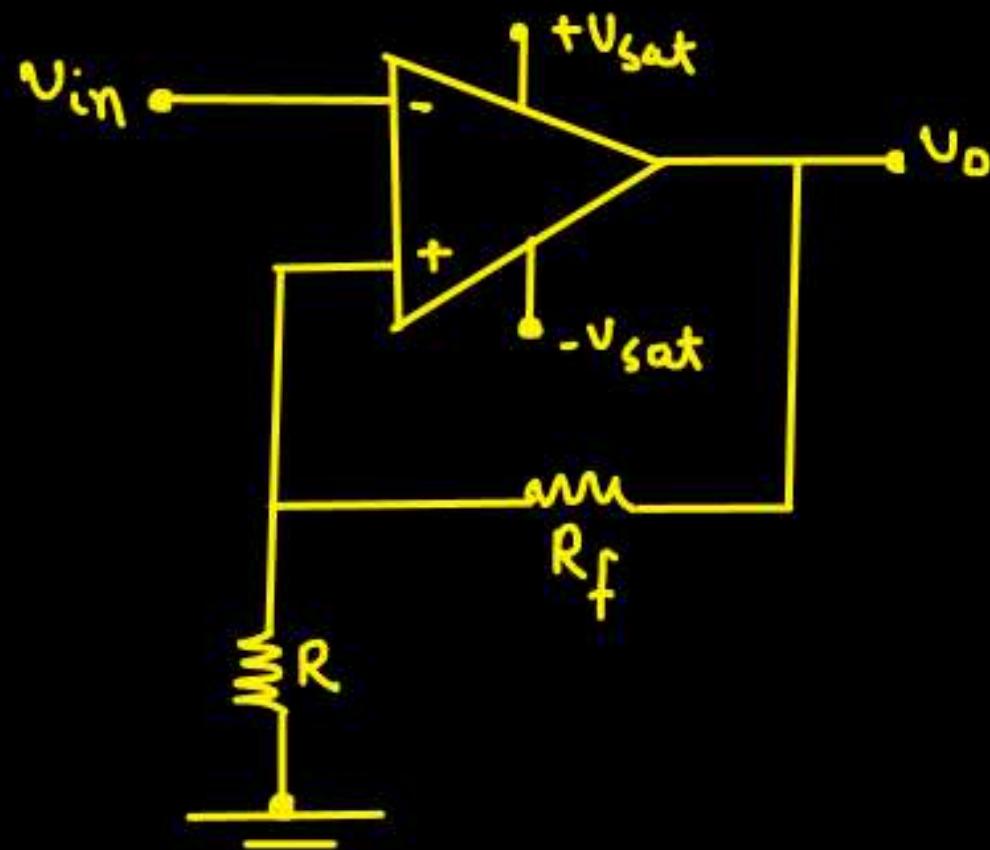


PrepFusion

$$\Rightarrow V_o = -V_{sat} \Rightarrow \text{Low}$$

$$\Rightarrow V_o = +V_{sat} \Rightarrow \text{High}$$

Q.

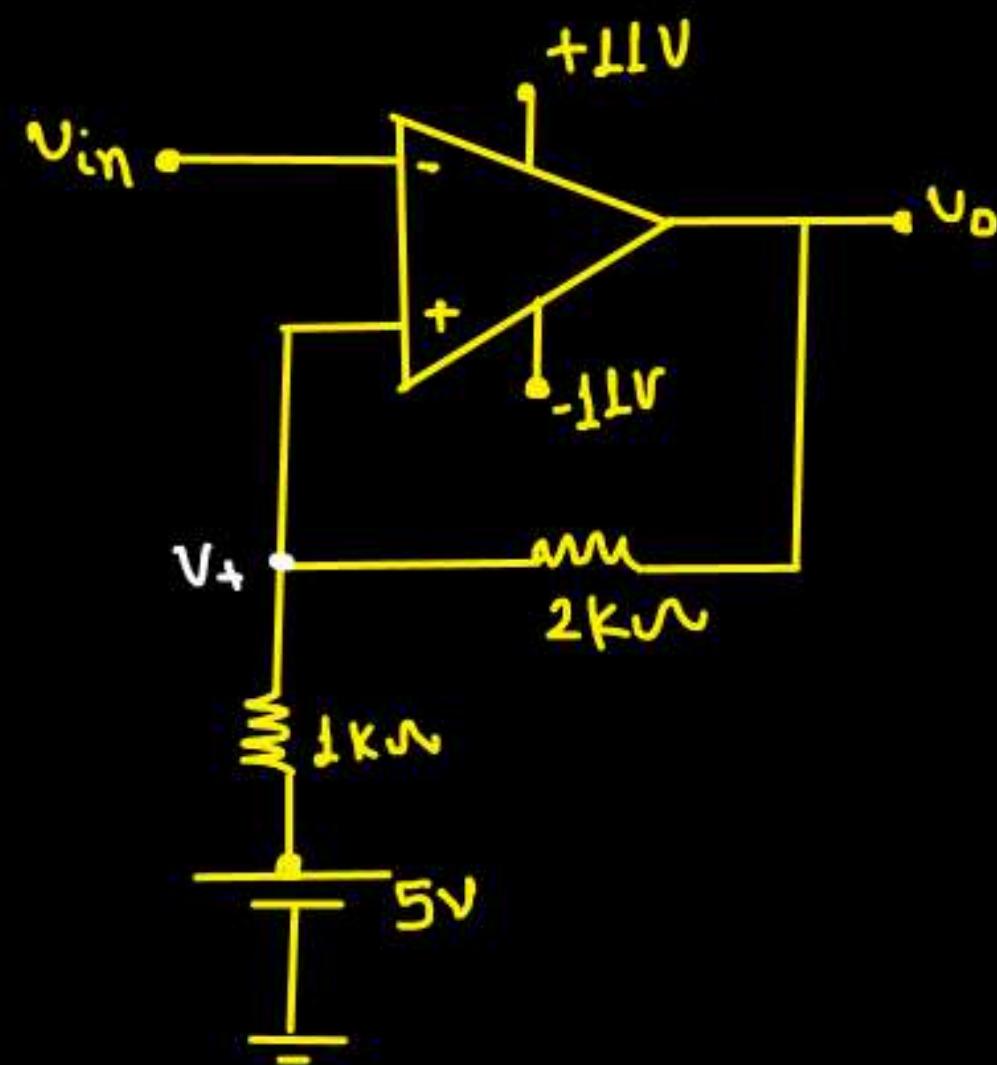

Draw Transfer characteristic.  
Find  $V_{UTP}$ ,  $V_{LTP}$ ,  $V_H$



→ Inverting schmitt trigger


$$V_+ = \frac{10 + U_o}{3}, \quad V_- = V_{in}$$

$$V_{in} = \frac{10 + V_0}{3}$$

$$V_{UTP} = \frac{10 + 11}{3} = 7V$$


$$V_{LTP} = \frac{10 - 11}{3} = -\frac{1}{3}V$$
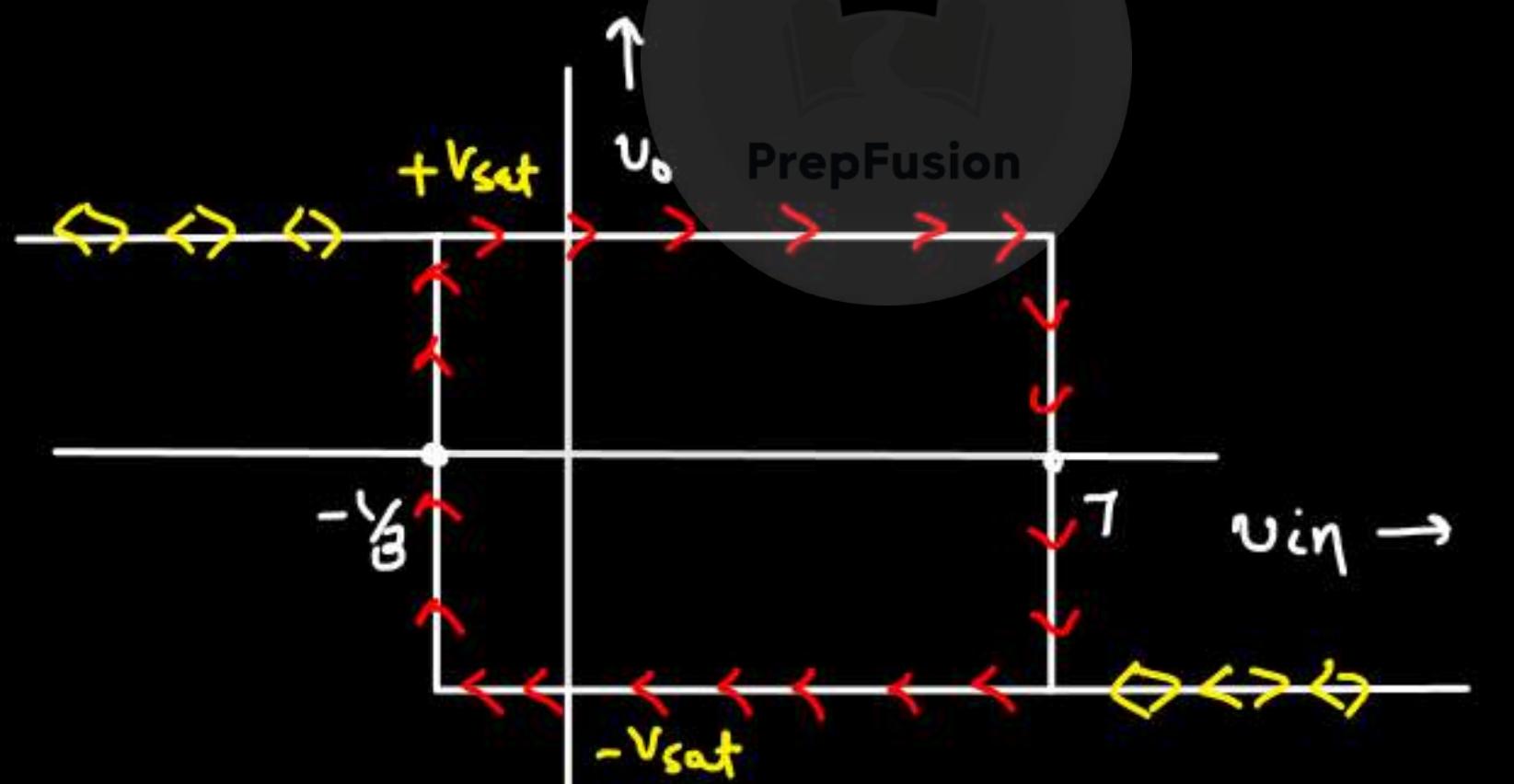
$$\begin{aligned} V_H &= V_{UTP} - V_{LTP} \\ &= 7 + \frac{1}{3} = 7.33V \end{aligned}$$



## Assignment - 16

Q.

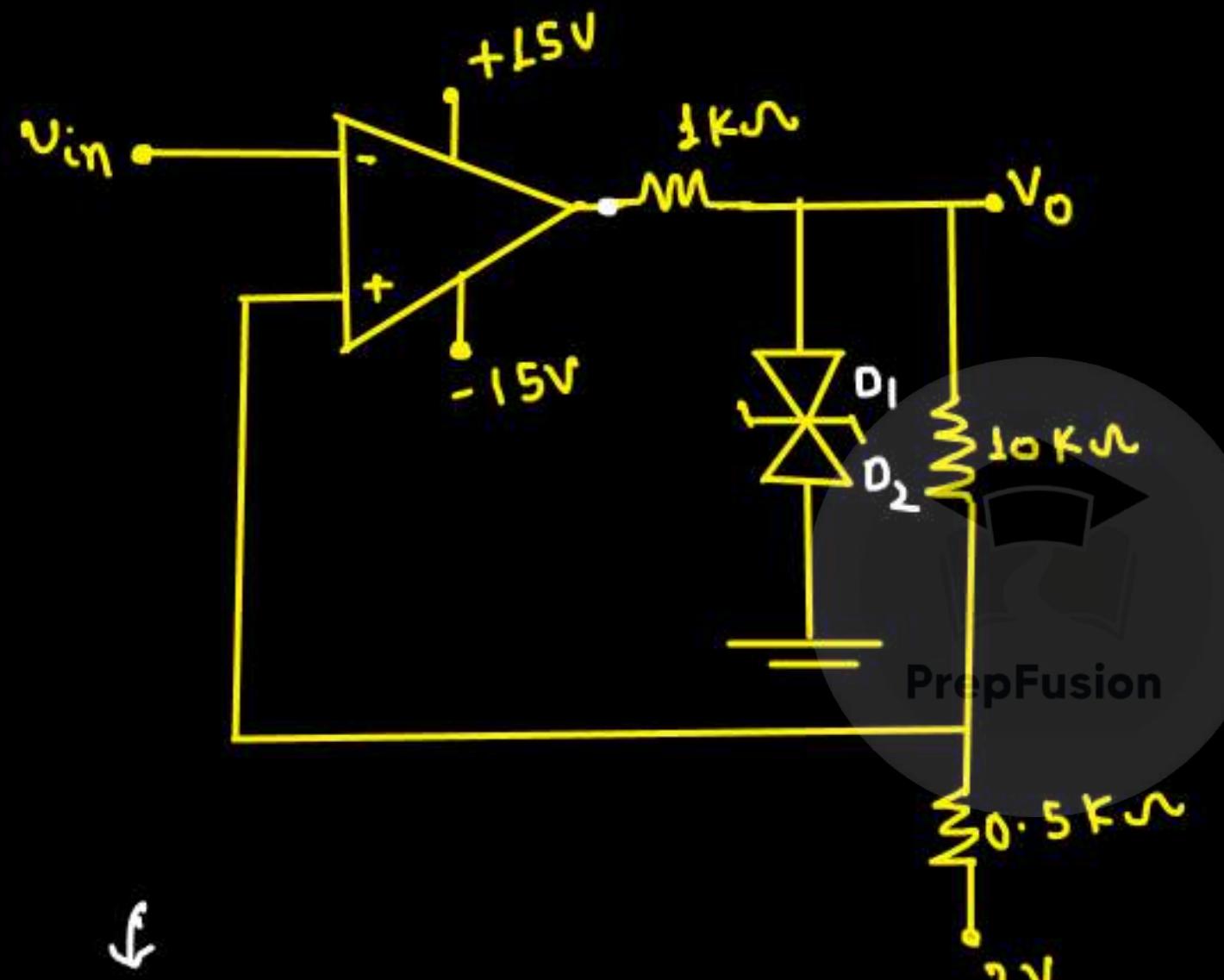


Inverting Schmitt trigger

$$V_Z = 6.3 \text{ V}$$

$$V_T = 0.7 \text{ V}$$

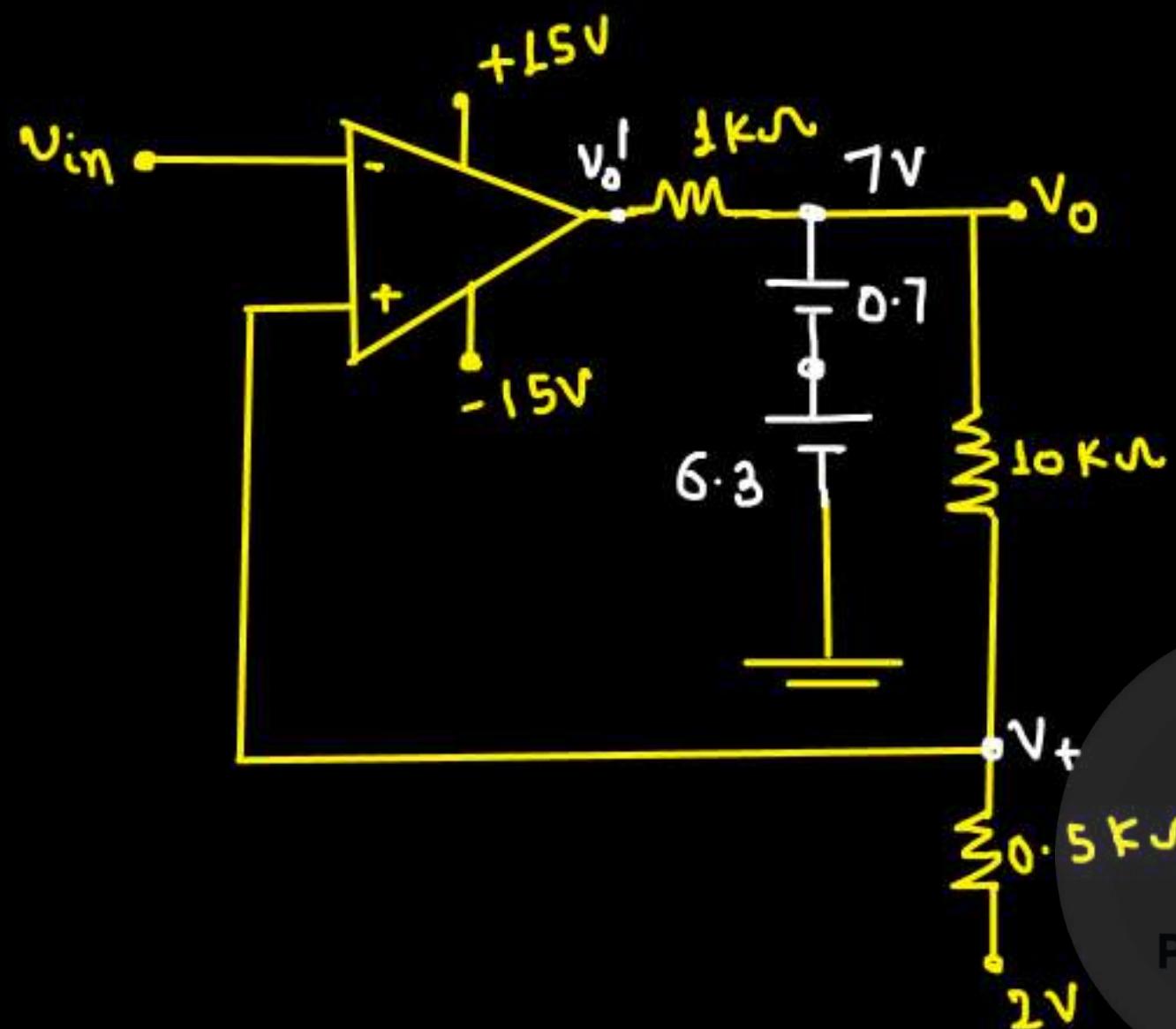Draw Transfer characteristic  
and find Hysteresis width.



if  $V_o' = +15V$



$$V_x = \frac{15 \times 10.5 + 2 \times 1}{11.5} \\ = 13.52V$$

$\Rightarrow$  Zener  $D_1$  goes into f.B.  
 $D_2$  goes into B.D.

$$\Rightarrow V_o = +7V$$

if  $V_o' = -15V$
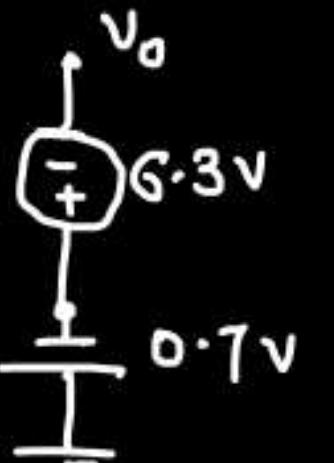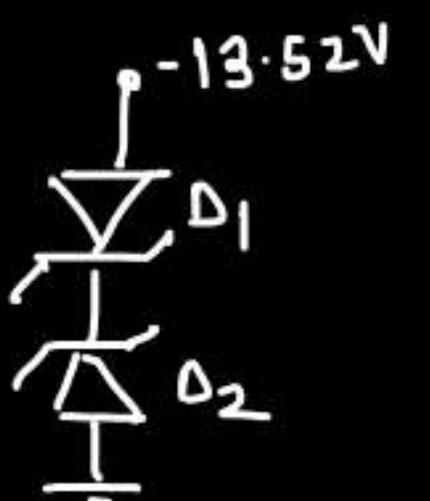
$$V_x = \frac{-15 \times 10.5 + 2 \times 1}{11.5} \\ = -13.52V$$



$$V_o = -7V$$

$$V_+ = \frac{V_o(0.5) + 2 \times 10}{10.5}$$


$$V_- = V_{in}$$

$$V_{in} = \frac{V_o/2 + 20}{10.5}$$


when  $V_o = +7V \Rightarrow V_{OTP} = \frac{3.5 + 20}{10.5} = 2.24V$

$$V_o = -7V \Rightarrow V_{OTP} = \frac{-3.5 + 20}{10.5} = 1.57V$$

$V_H = 0.69V$

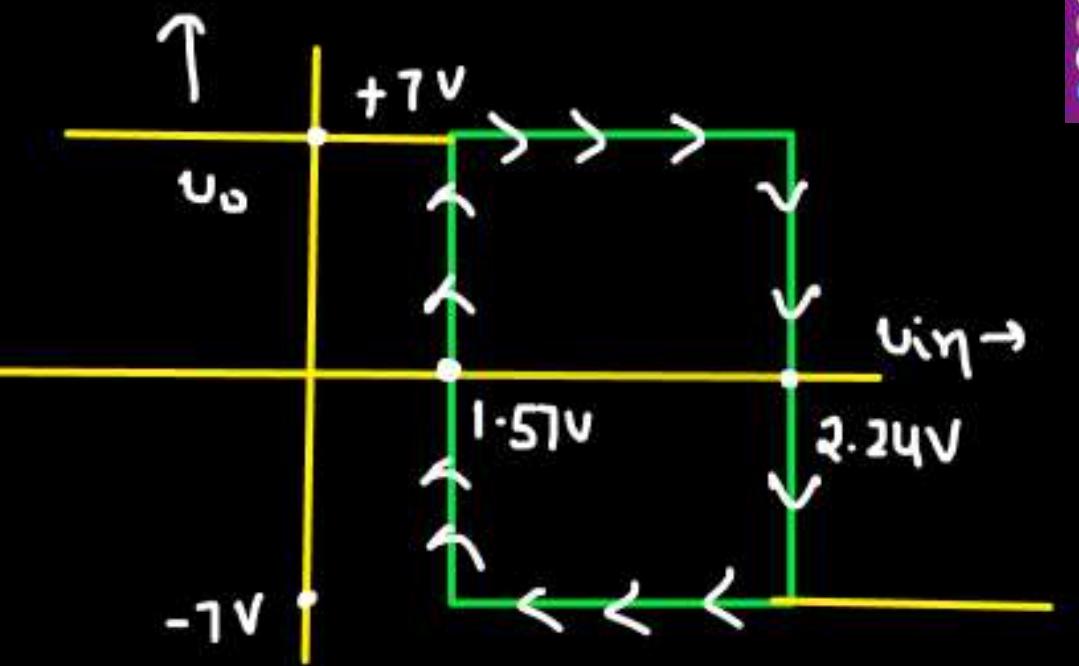

Q.

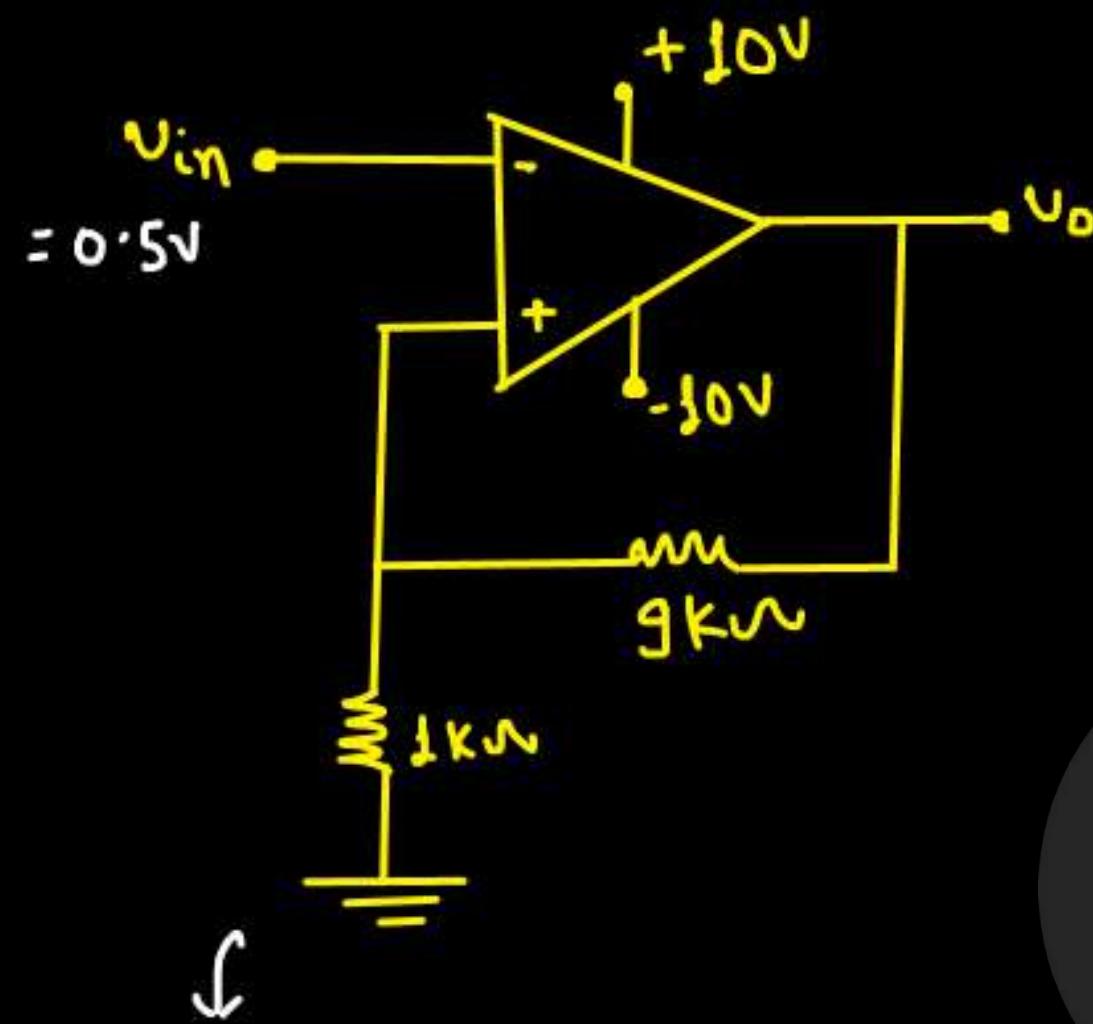

→

Inverting Schmitt trigger

$$V_+ = \frac{V_o}{10}, \quad V_- = V_{in}$$

$$V_{U_{TP}} = 1V$$

$$V_{L_{TP}} = -1V$$

$V_{in}$  is gradually increasing from 0 to 10V.



$V_o$  will change from

(a) -10V to +10V, when  $V_i = -1V$


(b) -10V to +10V, when  $V_i = 1V$

(c) +10V to -10V, when  $V_i = \pm 1V$

(d) +10V to -10V, when  $V_i = -1V$

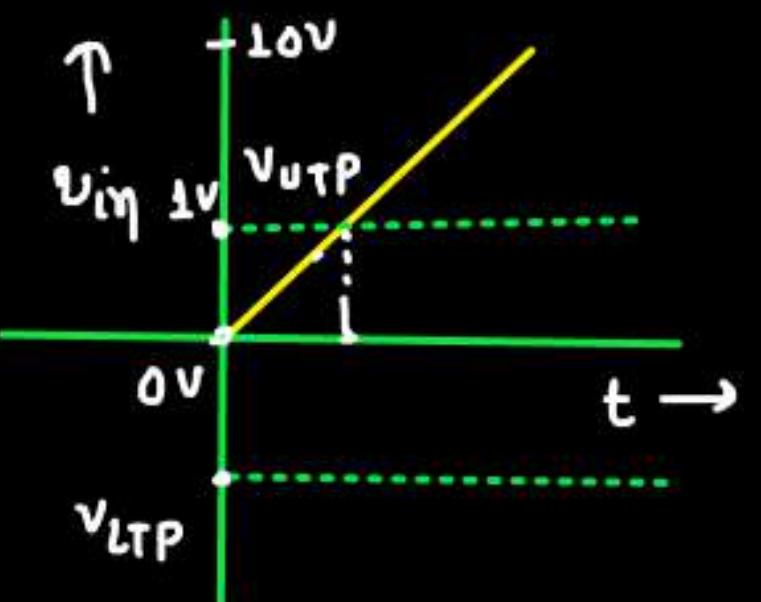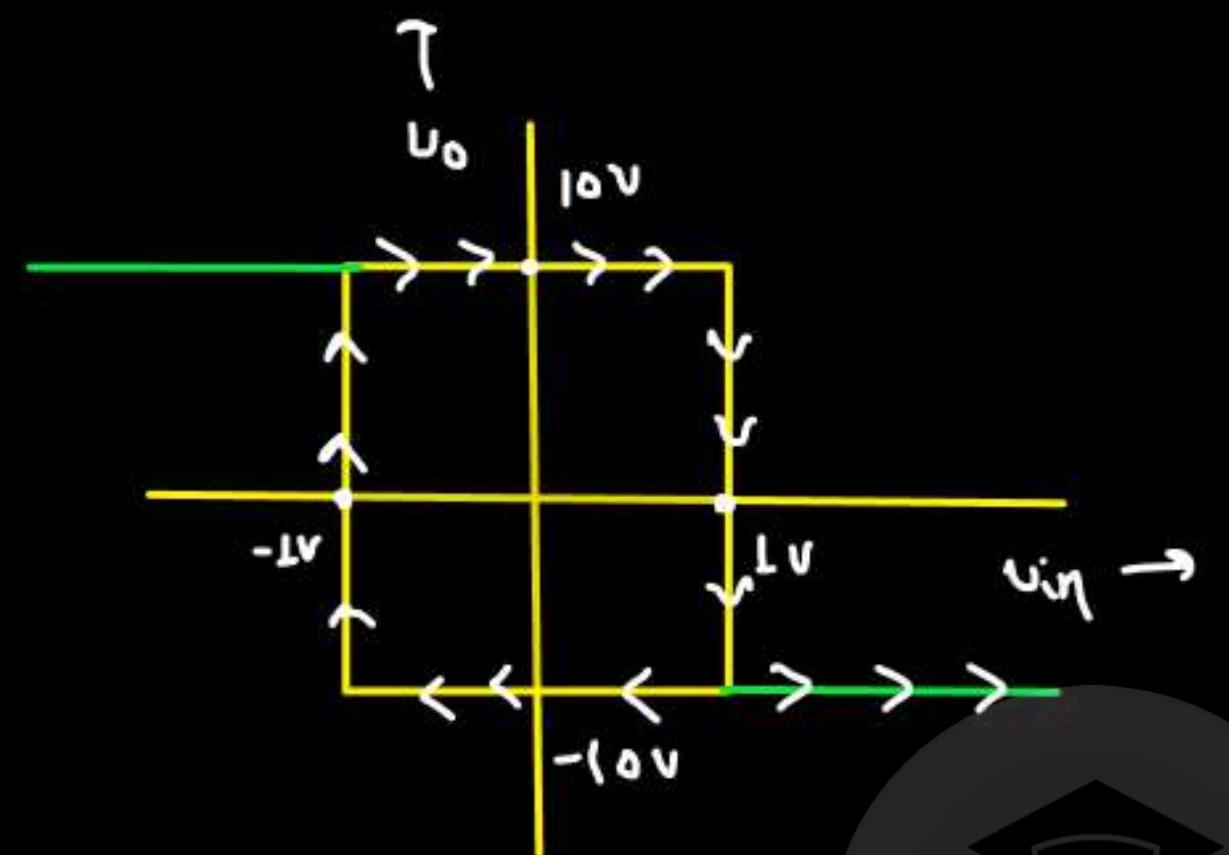

Q.

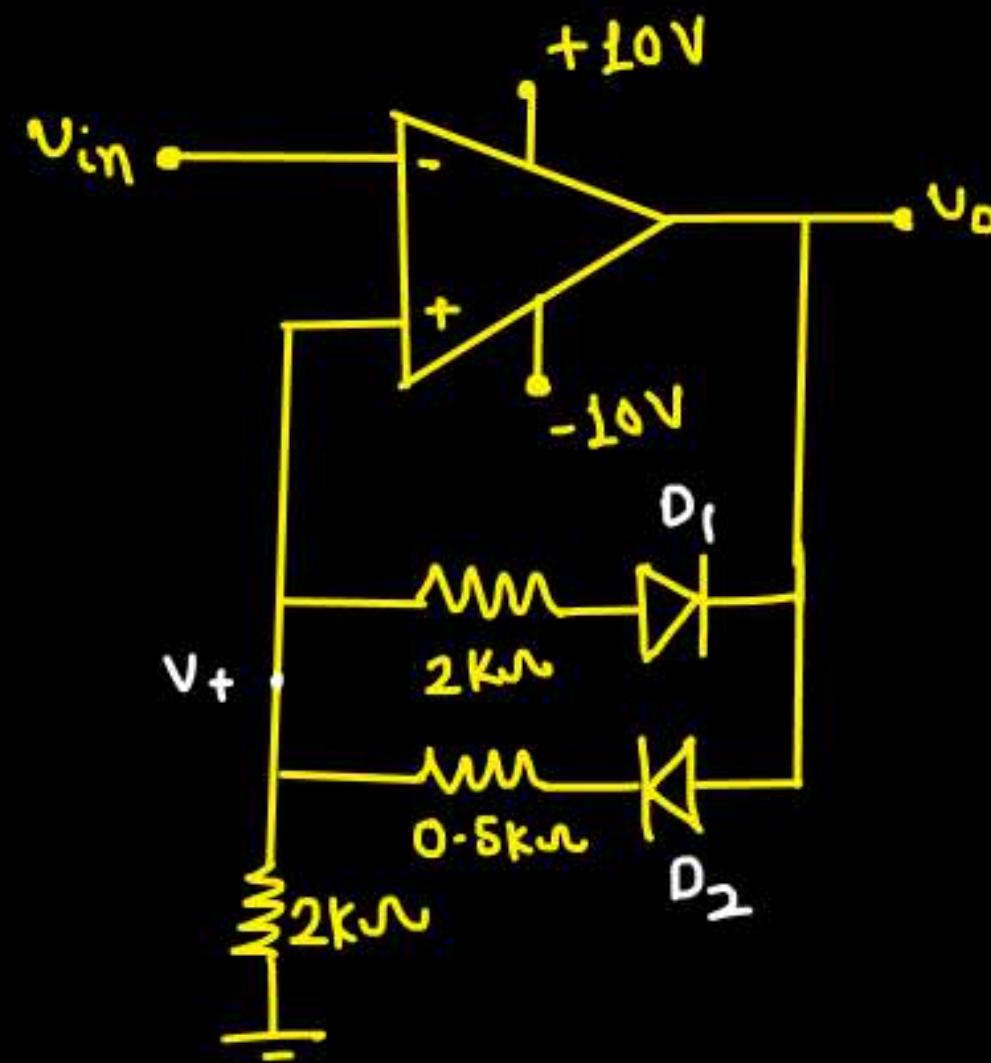

Considering diodes are ideal.

Find Hysteresis width.

⇒ if  $V_o = +10V \Rightarrow D_2 \text{ ON}, D_1 \text{ off}$

PrepFusion

$$V_+ = \frac{2}{2.5} \times 10 = 8V \rightarrow V_{UTP}$$

if  $V_o = -10V \Rightarrow D_1 \text{ ON}, D_2 \text{ off}$

$$V_{UTP} = 8V$$


$$V_{LTP} = -5V$$

$v_H = 13V$

Ans.

$$V_+ = \frac{2}{4} \times (-10) = -5V \rightarrow V_{LTP}$$

Q.

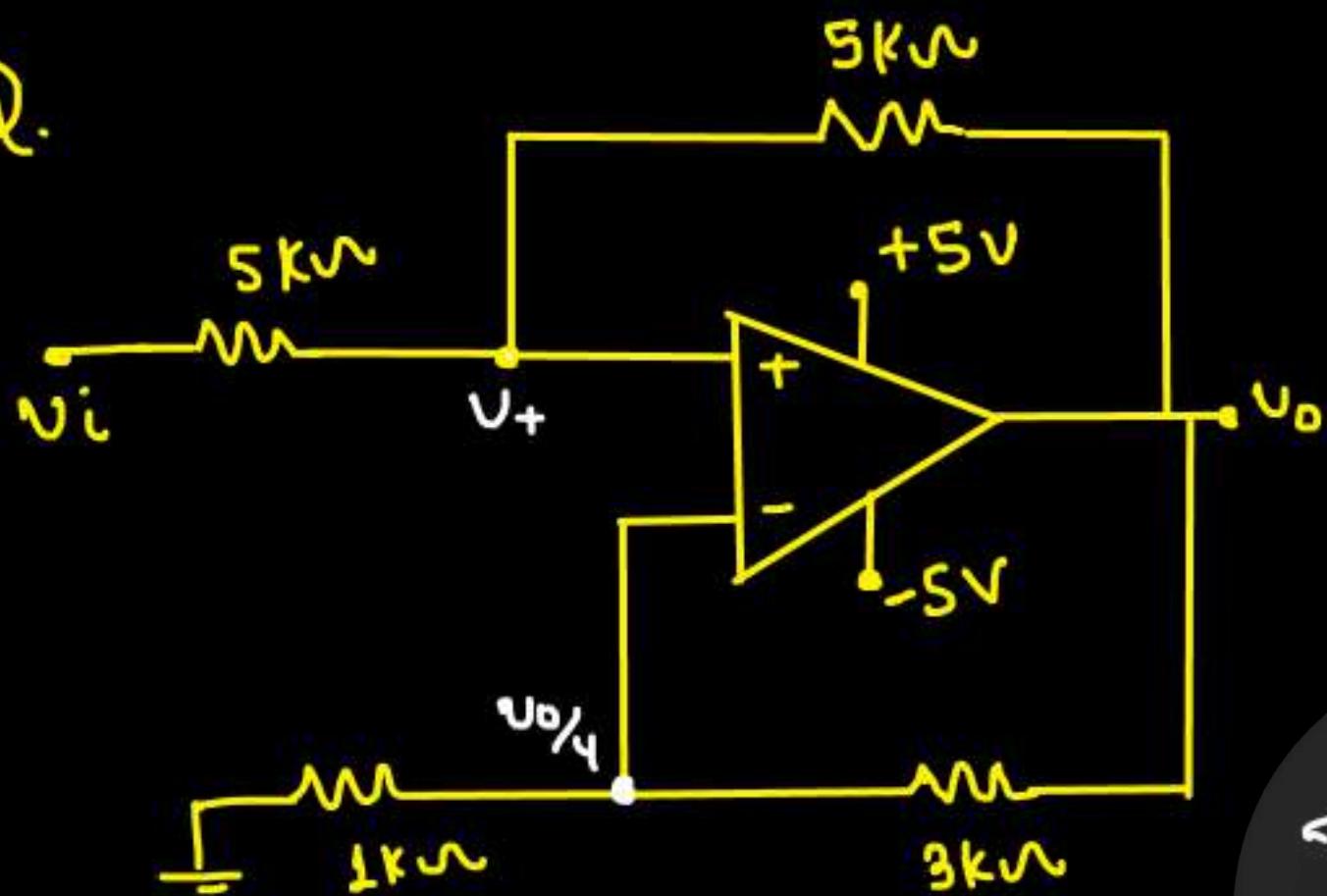

Draw Transfer characteristic.

Non-inverting Schmitt trigger

PrepFusion

$$\rightarrow v_+ = \frac{v_o}{2} \quad v_- = \frac{v_o}{4}$$

⇒ positive f/b

$$v_+ = \frac{v_i(5) + v_o(5)}{10} = \frac{v_i + v_o}{2}$$



$$V_+ = V_-$$

$$\frac{V_i + V_o}{2} = \frac{V_0}{4}$$


$$V_i = -\frac{V_0}{2}$$

$$V_0 = +5V \quad , \quad V_{LTP} = -\frac{5}{2} = -2.5V$$
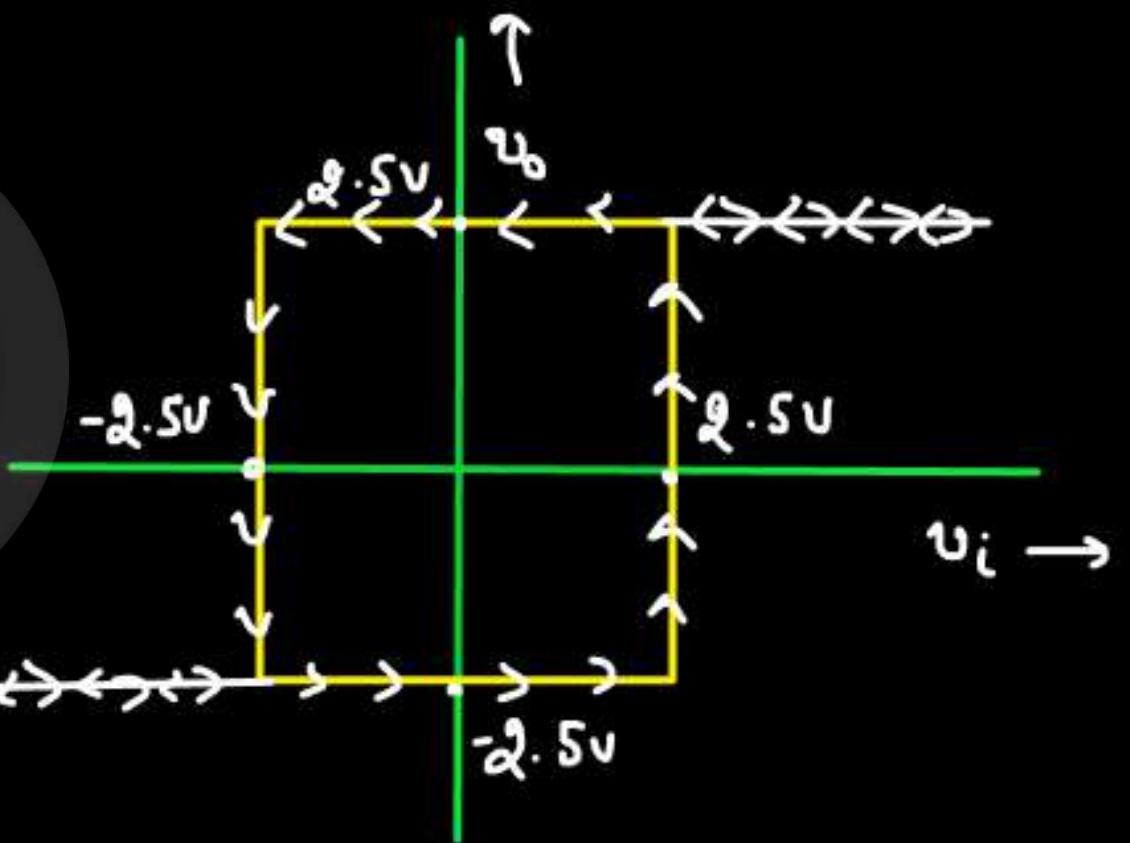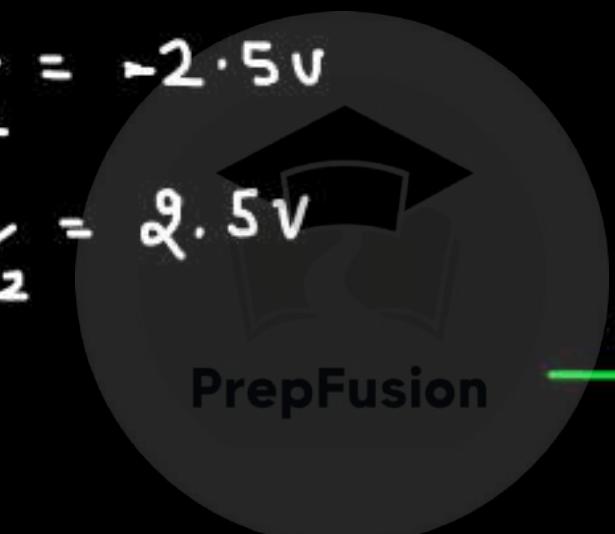
$$V_o = -5V \quad , \quad V_{UTP} = \frac{5}{2} = 2.5V$$



Q.

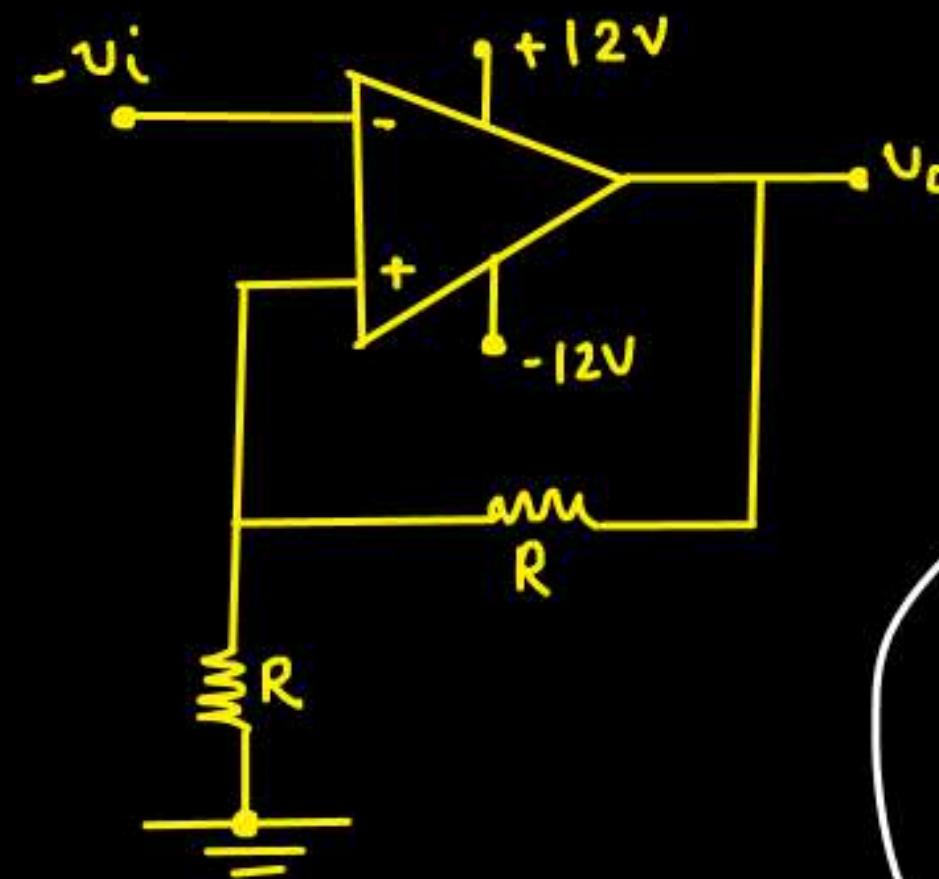

$-U_{in} = \text{High} \Rightarrow U_o = \text{Low}$

$U_{in} = \text{Low} \Rightarrow U_o = \text{Low}$

$U_{in} = \text{High} \Rightarrow U_o = \text{High}$

Draw Transfer characteristic  $U_o$  vs  $U_i$ .

PrepFusion

$w.r.t -U_{in} \Rightarrow \text{Inverting Schmitt trigger}$

$w.r.t U_{in} \Rightarrow \text{Non-inverting " " }$


$$V_+ = U_o/2, V_- = -U_i$$

$$-U_i = U_o/2 \Rightarrow U_i = -U_o/2$$

$$V_{UTP} = 6V$$


$$V_{LTP} = -6V$$



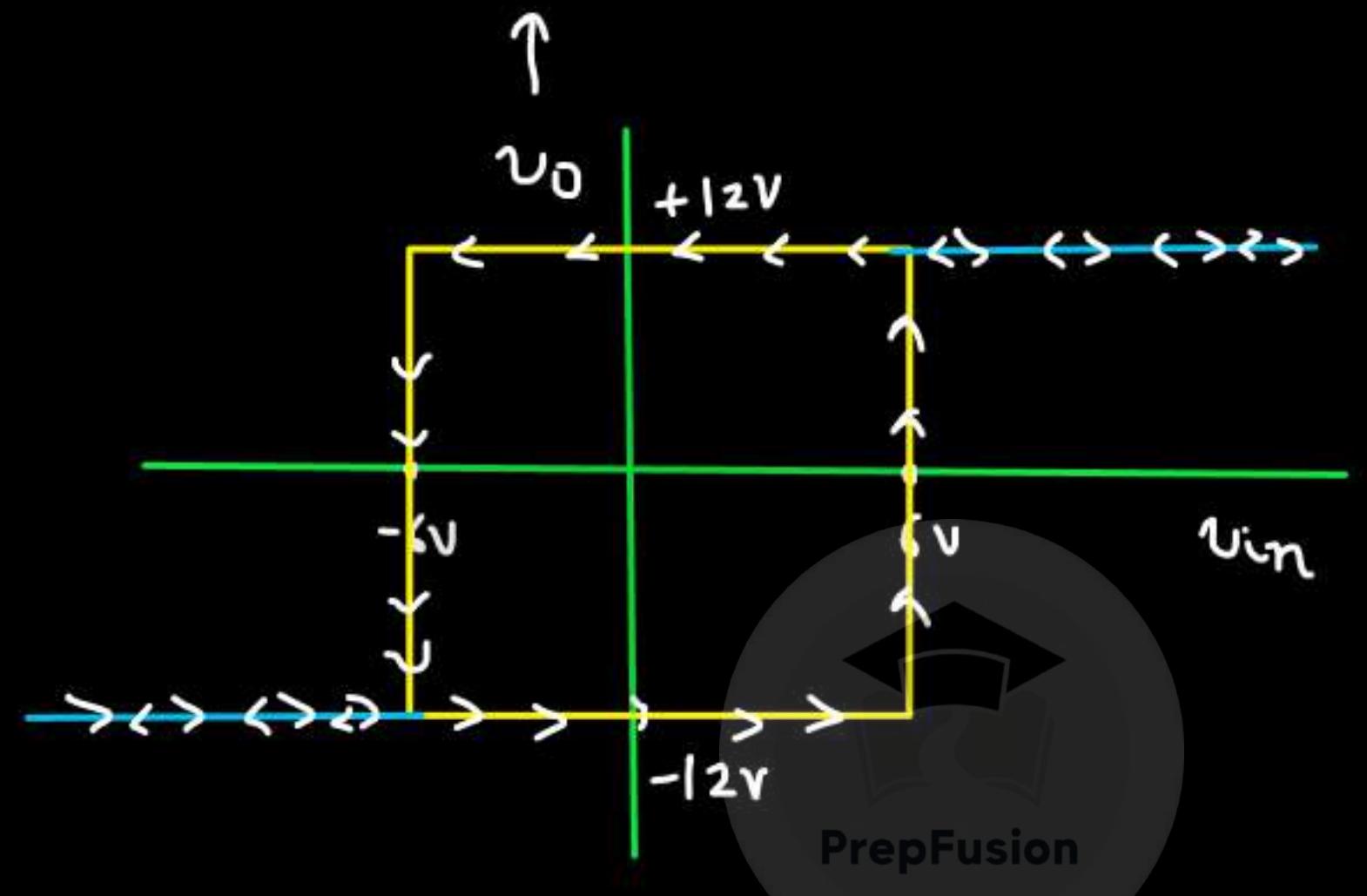

Q.

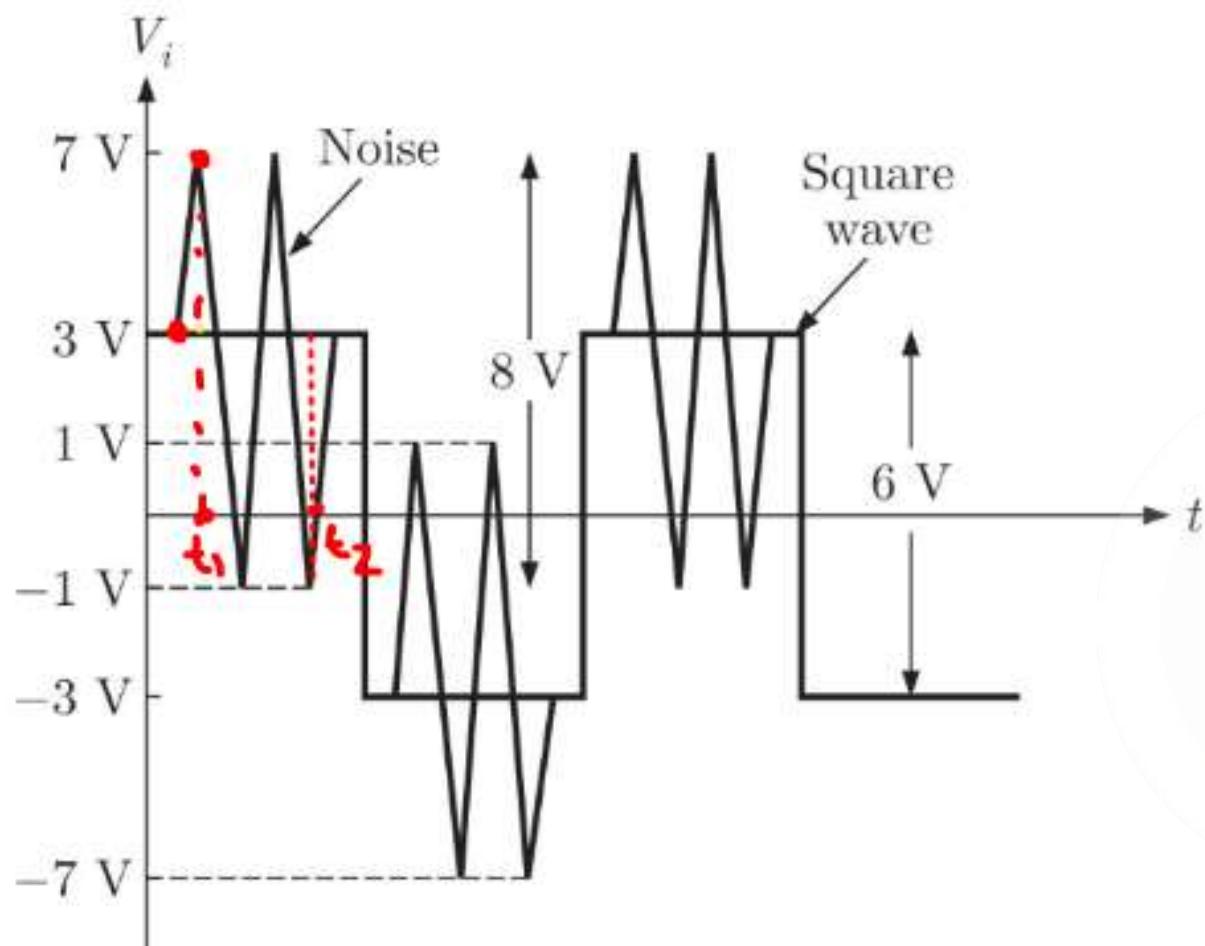The input signal shown in the figure below is fed to a Schmitt trigger. The signal has a square wave amplitude of 6 V p-p. It is corrupted by an additive high frequency noise of amplitude 8V p-p.



$$+ve \text{ cycle} \Rightarrow v_{in}: [2, 10]$$

PrepFusion


$$-ve \text{ cycle} \Rightarrow v_{in}: [-2, -10]$$

$$v_{in}(t = t_1) = 7 + 3 \\ = 10 \text{ V}$$

$$v_{in}(t = t_2) = 3 - 1 \\ = 2 \text{ V}$$


Which one of the following is an appropriate choice for the upper and lower trip points of the Schmitt trigger to recover a square wave of the same frequency from the corrupted input signal  $V_i$  ?

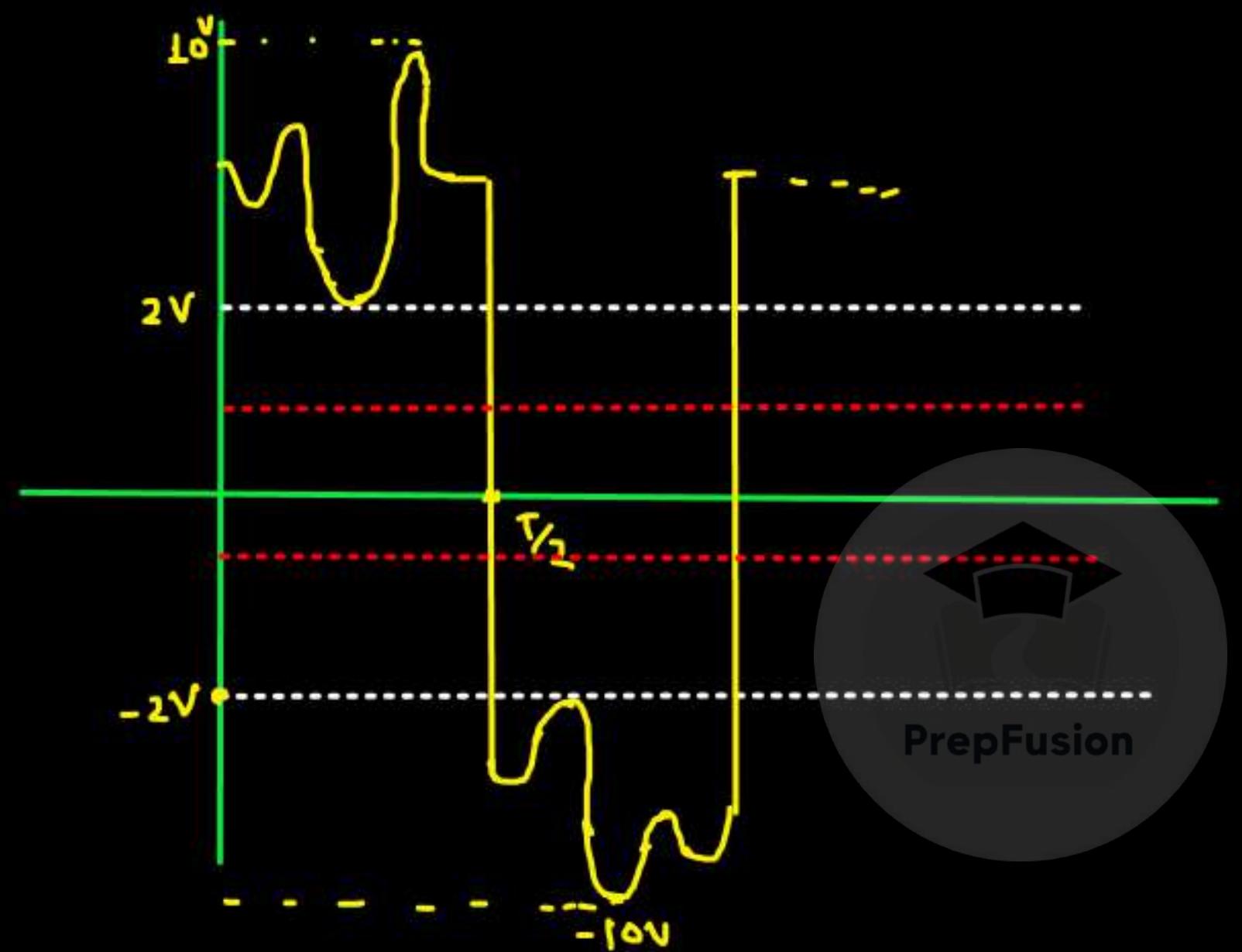- (A)  ~~$\pm 8.0 \text{ V}$~~
- (C)  ~~$\pm 0.5 \text{ V}$~~
- (B)  $\checkmark \pm 2.0 \text{ V}$
- (D) ~~?~~  $0 \text{ V}$



$$V_{U_{TP}} = +2V$$


$$V_{L_{TP}} = -2V$$

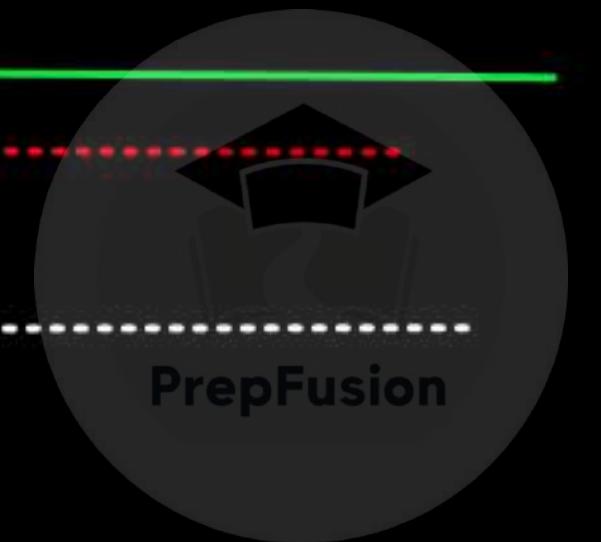
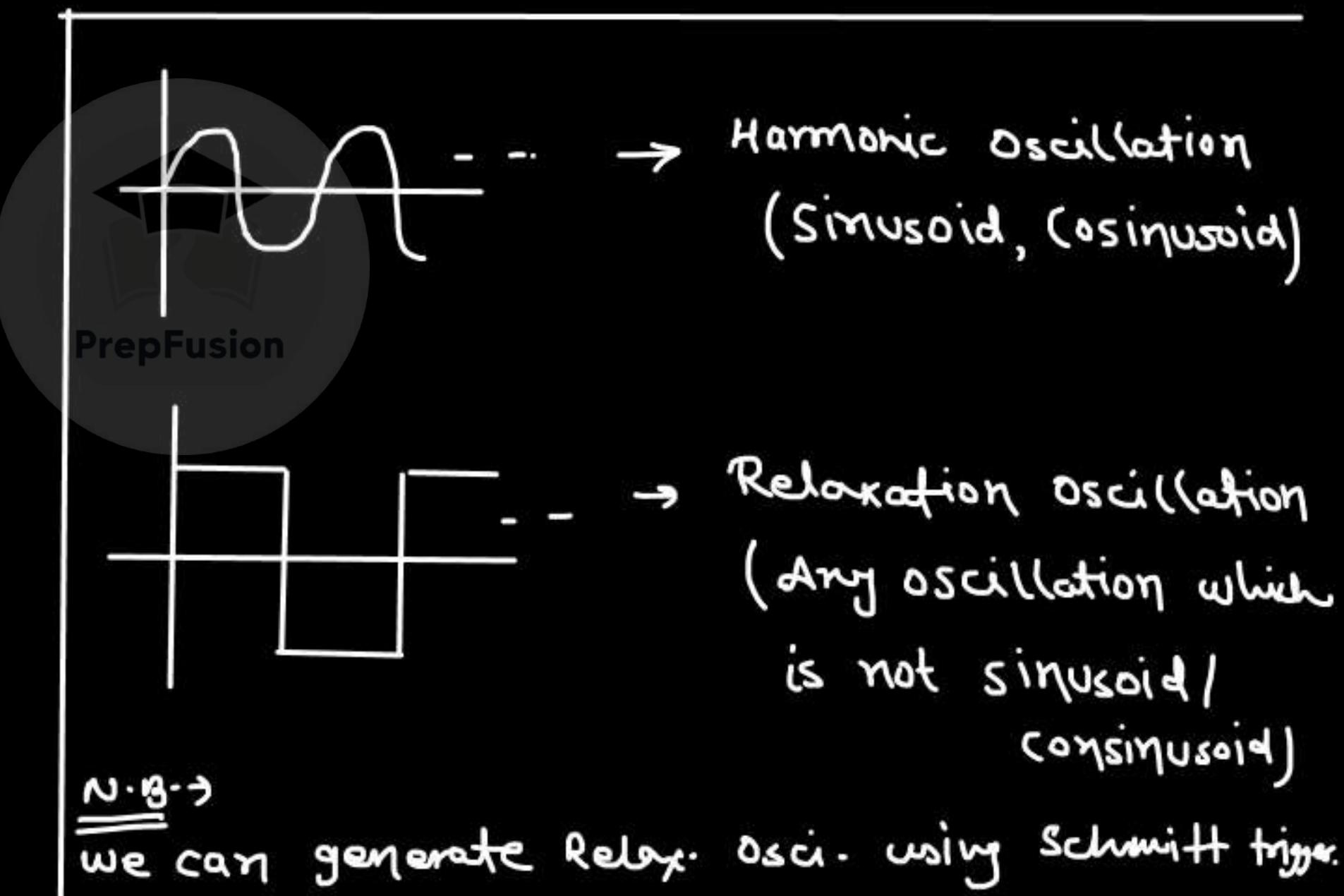
## ⇒ Concept of Multivibrators :-


Electronic circuits which are used to implement two state devices like oscillator, Timer and flip-flops.

- Astable Multivibrators
- Monostable
- Bistable


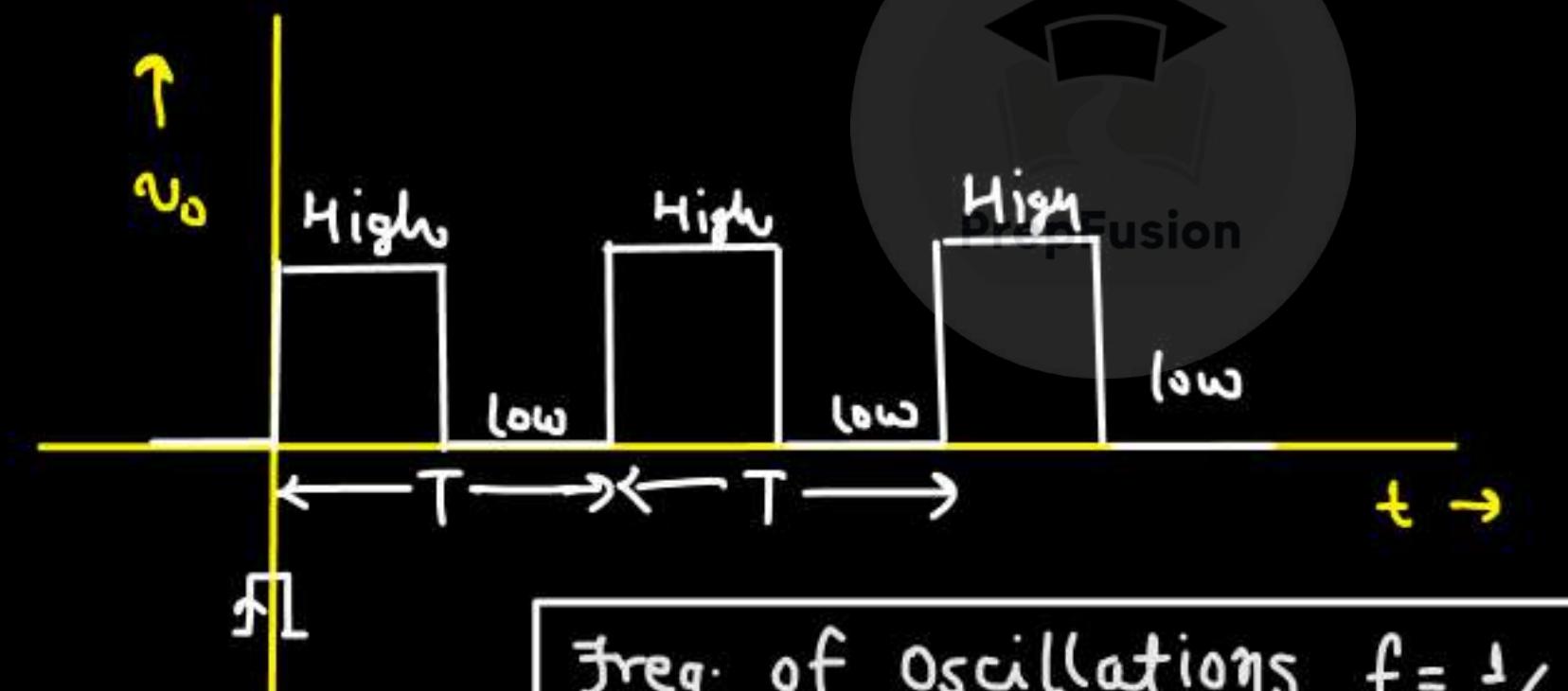
## \* Astable Multivibrator:-


These are free running oscillators which oscillates b/w two states continuously producing two square-wave output waveforms.



$$\text{Freq. of oscillations } f = \frac{1}{T}$$

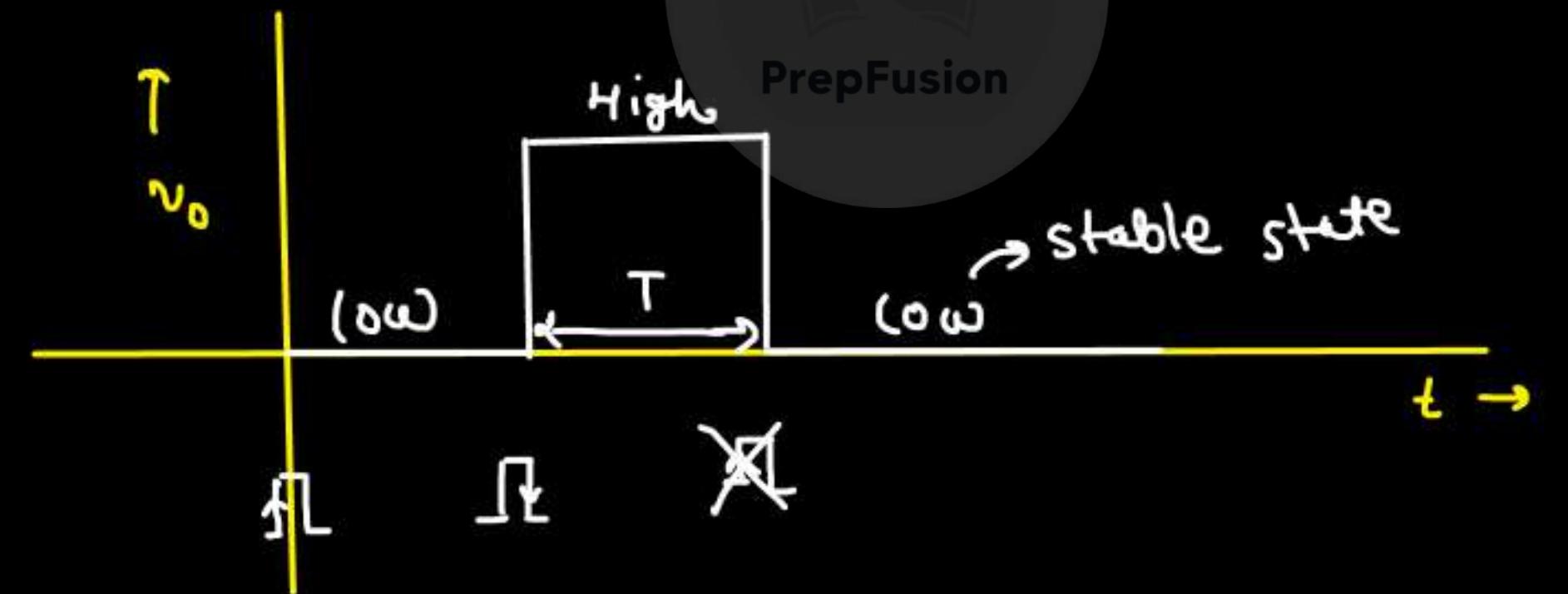
## Monostable Multivibrators :-

They have one stable state and one monostable state, where a trigger (external signal) is required to enter the monostable state and return back to the stable state.






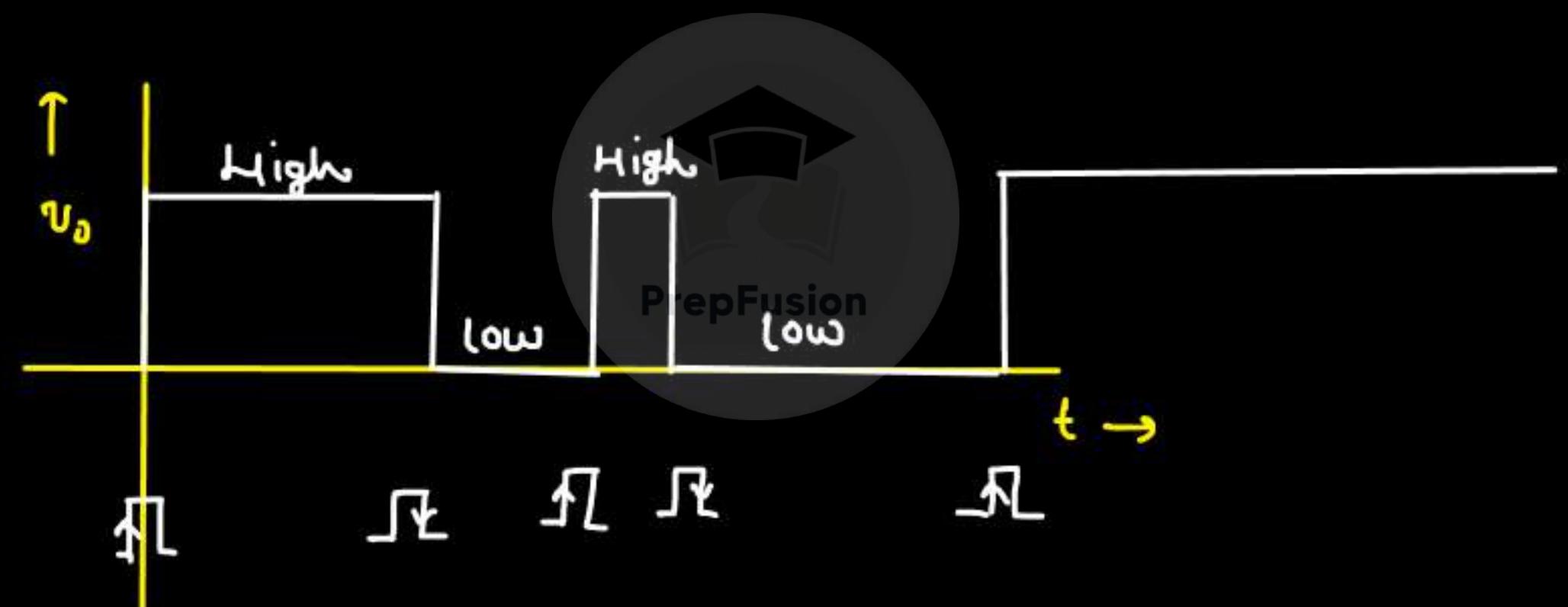
## ★ Bistable Multivibrator :-

It's a two stable state device  
where an external signal needs to be applied to change  
a particular state.


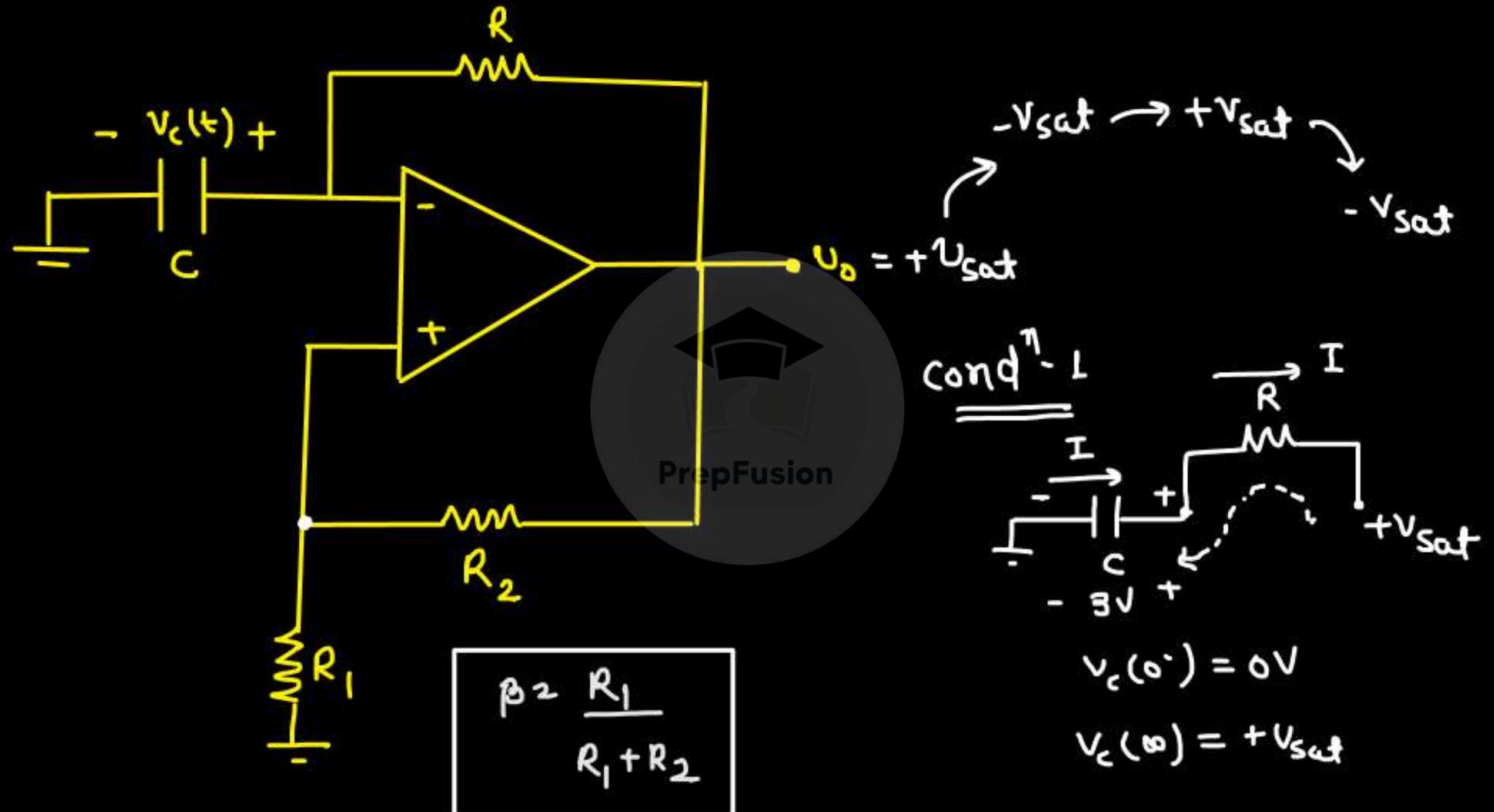
## \* Astable Multivibrator Using Schmitt trigger..



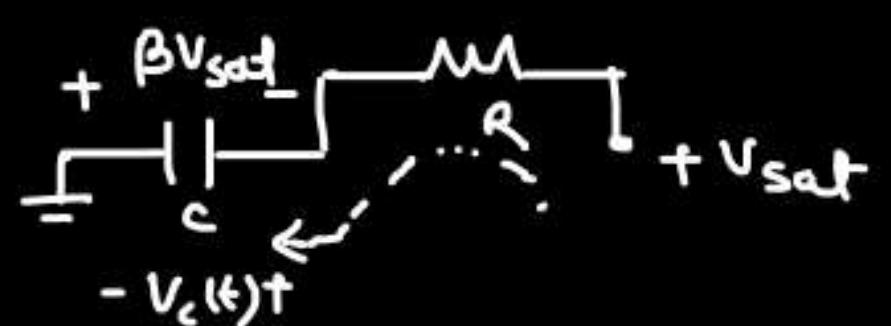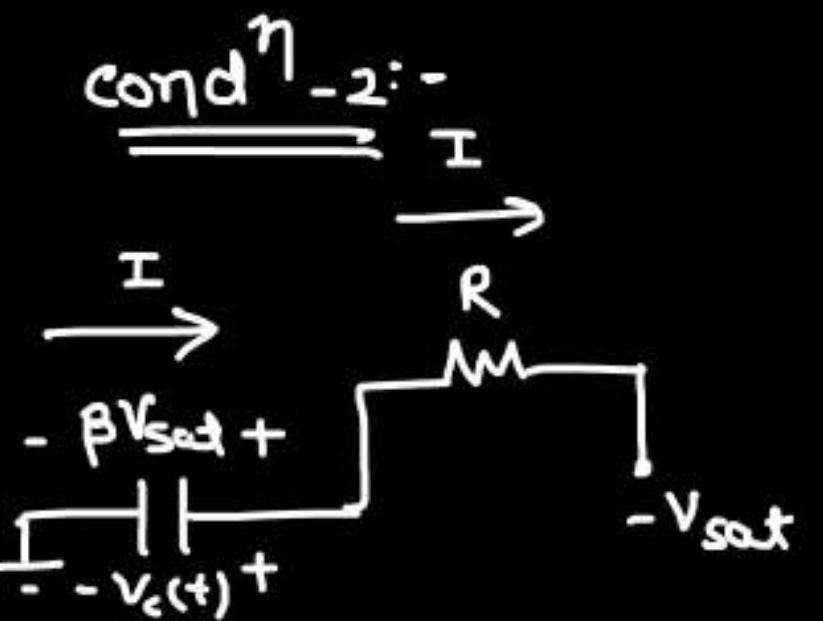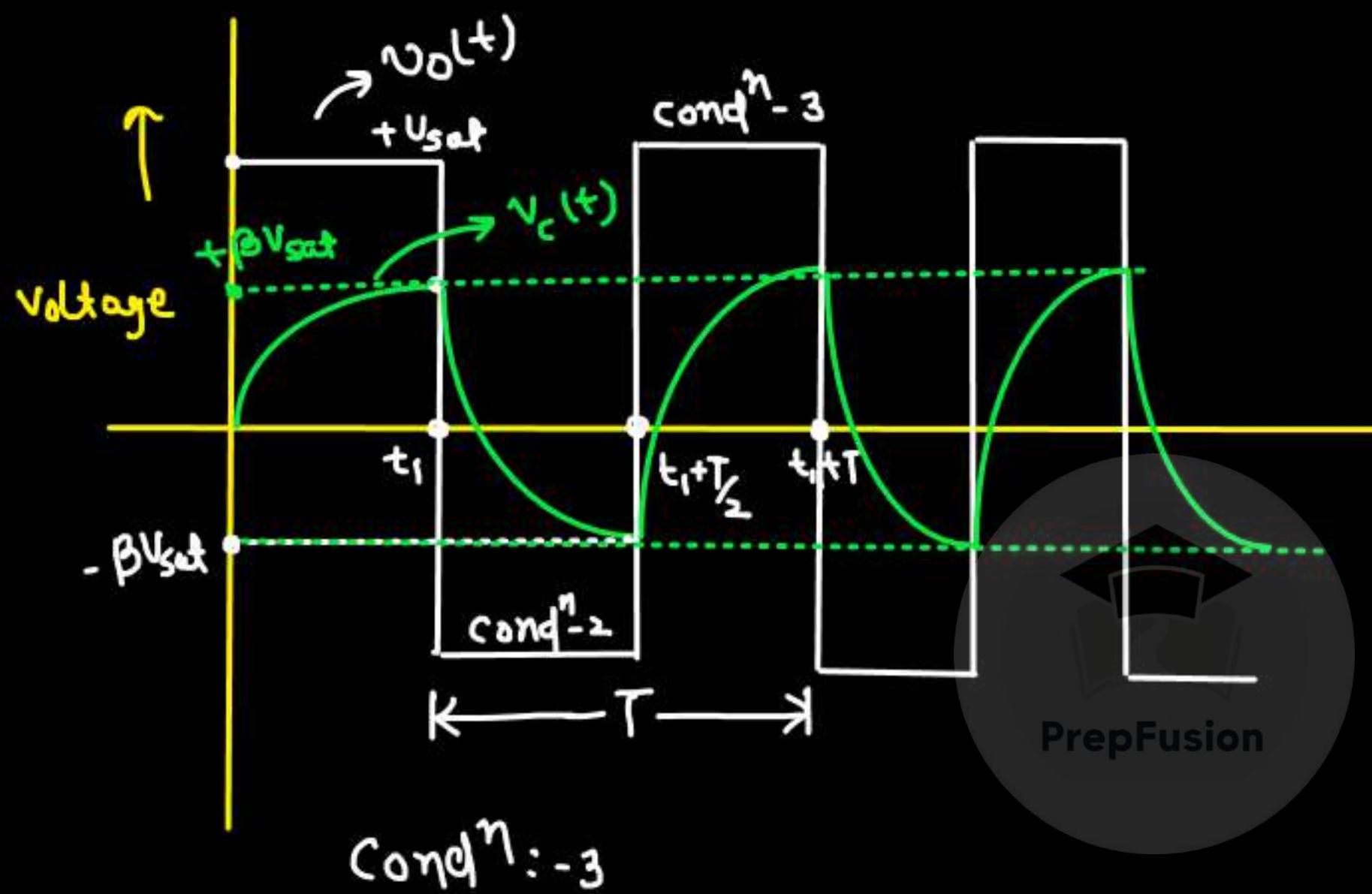

$$v_c(t_1 + T_1/2) = -\beta v_{sat}; v_c(\infty) = +v_{sat}$$


$$v_c(t_1) = \beta v_{sat}$$

$$v_c(\infty) = -v_{sat}$$

How to find  $T \rightarrow ?$

$$v_c(t) = [v_c(\infty) + [v_c(0^+) - v_c(\infty)] e^{-t/RC}] u(t)$$

cond 2 :-

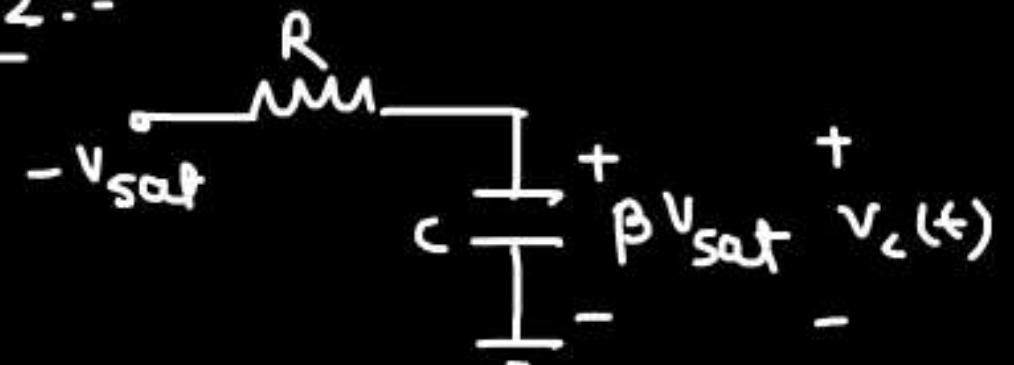

$$v_c(t_1) = \beta V_{sat}$$

$$v_c(\infty) = -V_{sat}$$

$$v_c(t) = -V_{sat} + (\beta V_{sat} + V_{sat}) e^{-|t-t_1|/RC}$$

But

$$@ t = t_1 + T_{1/2} \Rightarrow v_c(t_1 + T_{1/2}) = -\beta V_{sat}$$

$$-\beta V_{sat} = -V_{sat} + (\beta V_{sat} + V_{sat}) e^{-(t_1 + T_{1/2} - t_1)/RC}$$

$$V_{sat} (1 - \beta) = V_{sat} (1 + \beta) e^{-T_{1/2} RC}$$

$$e^{-\frac{T}{2RC}} = \frac{1-\beta}{1+\beta}$$

$$\frac{T}{2} = RC \ln \left( \frac{1+\beta}{1-\beta} \right)$$




$$T = 2RC \ln \left( \frac{1+\beta}{1-\beta} \right)$$


$$\beta = \frac{R_1}{R_1 + R_2}$$

Freq. of oscillation

$$f_{osc} = \frac{1}{T}$$

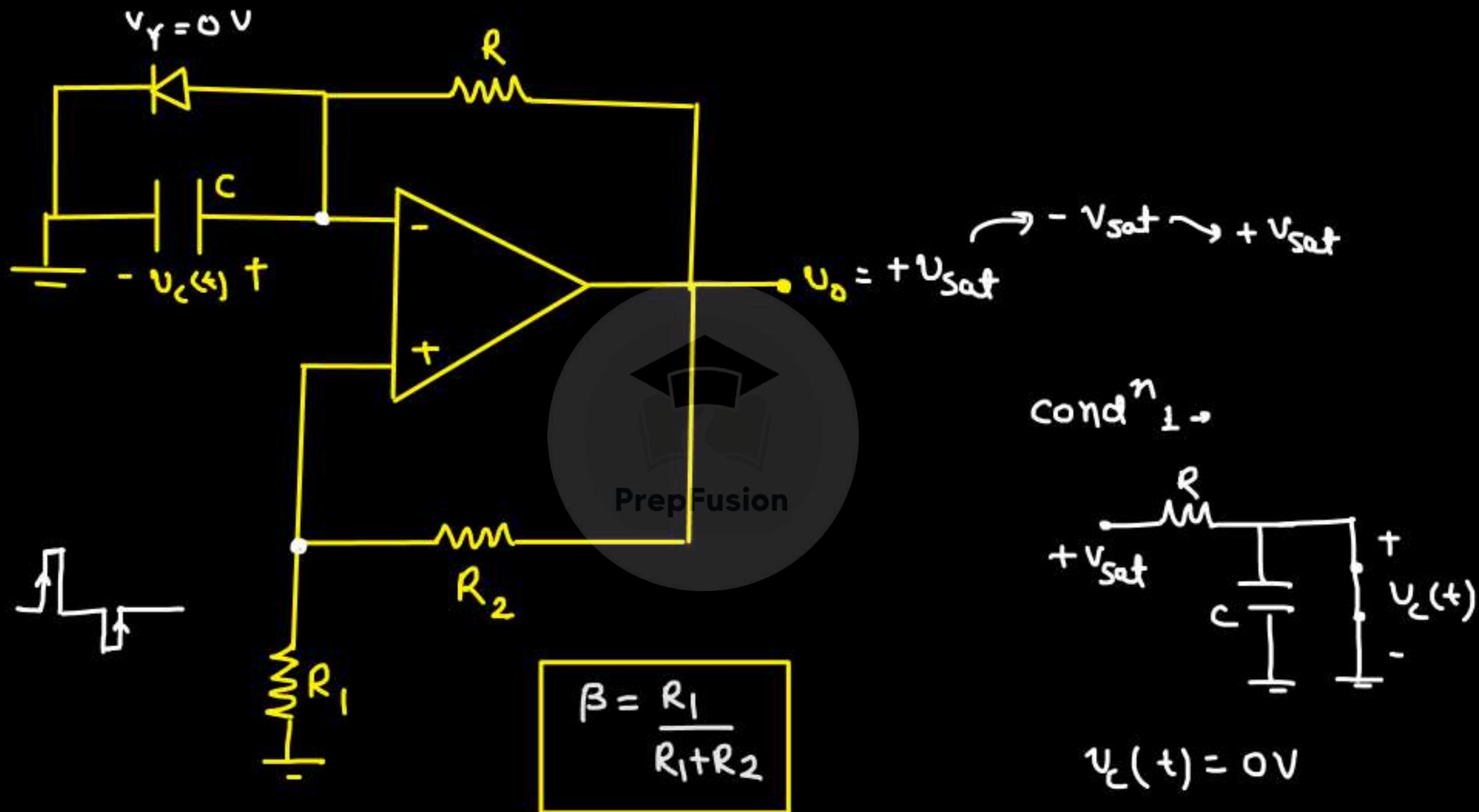
## Monostable Multivibrator Using Schmitt trigger..



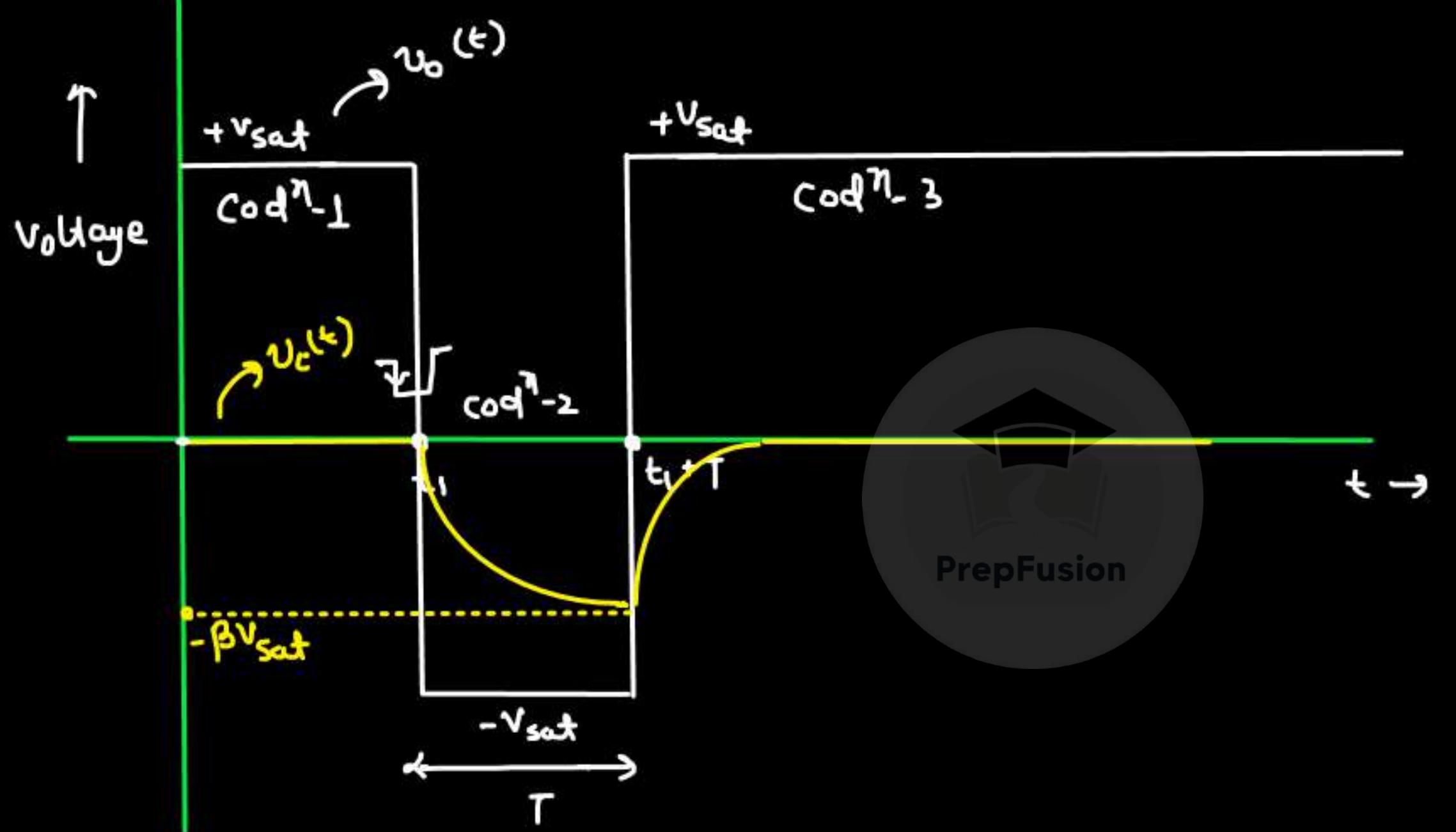

cond<sup>n</sup> 2 :-

$$V_+ = -\beta V_{sat}$$

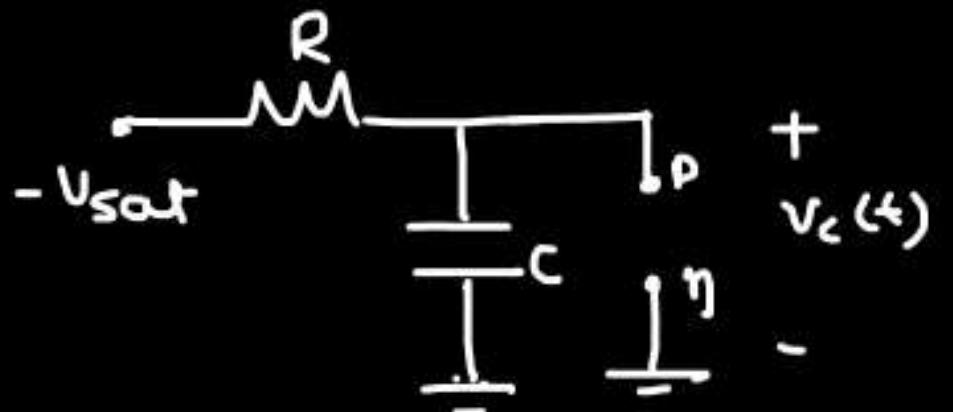


diode turned off

$$V_c(t_1) = 0 \text{ V}$$

$$V_c(\infty) = -V_{sat}$$

cond<sup>n</sup> 3

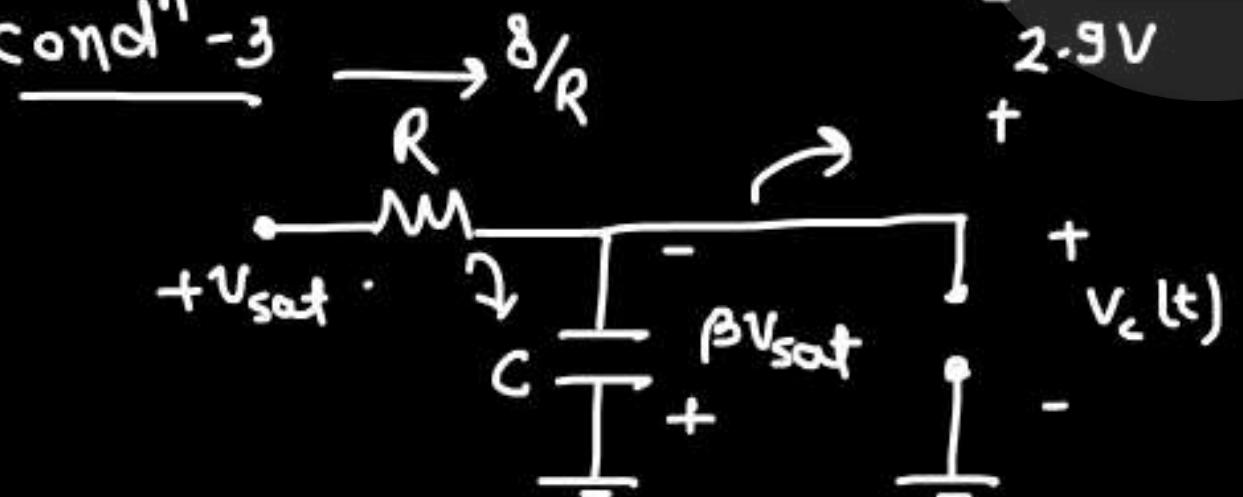

PrepFusion


$$V_c(t_1 + T) = -\beta V_{sat}$$

$$V_c(\infty) = +V_{sat} \times$$

when  $V_c = 0 \text{ V} \Rightarrow$  diode will turn on

$V_c$  potential remains at  
0V only until some external  
Trigger makes  $\alpha_D$  to go to  $-V_{sat}$
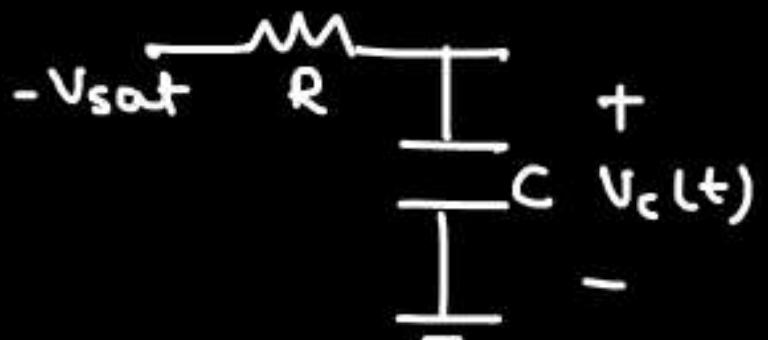
## Pulse width ( $T$ ) of Astable Multivibrator:-



$$V_c(t_1) = 0 \text{ V}$$

$$V_c(\infty) = -V_{sat}$$

$$V_c(t) = -V_{sat} \left[ 1 - e^{-\frac{(t-t_1)}{RC}} \right]$$

②  $t = t_1 + T$  ,  $V_c(t_1 + T) = -\beta V_{sat}$

$$-\beta V_{sat} = -V_{sat} \left[ 1 - e^{-\frac{(t_1 + T - t_1)}{RC}} \right]$$




$$T = -RC \ln(1 - \beta)$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

Q.

## Assignment - 17

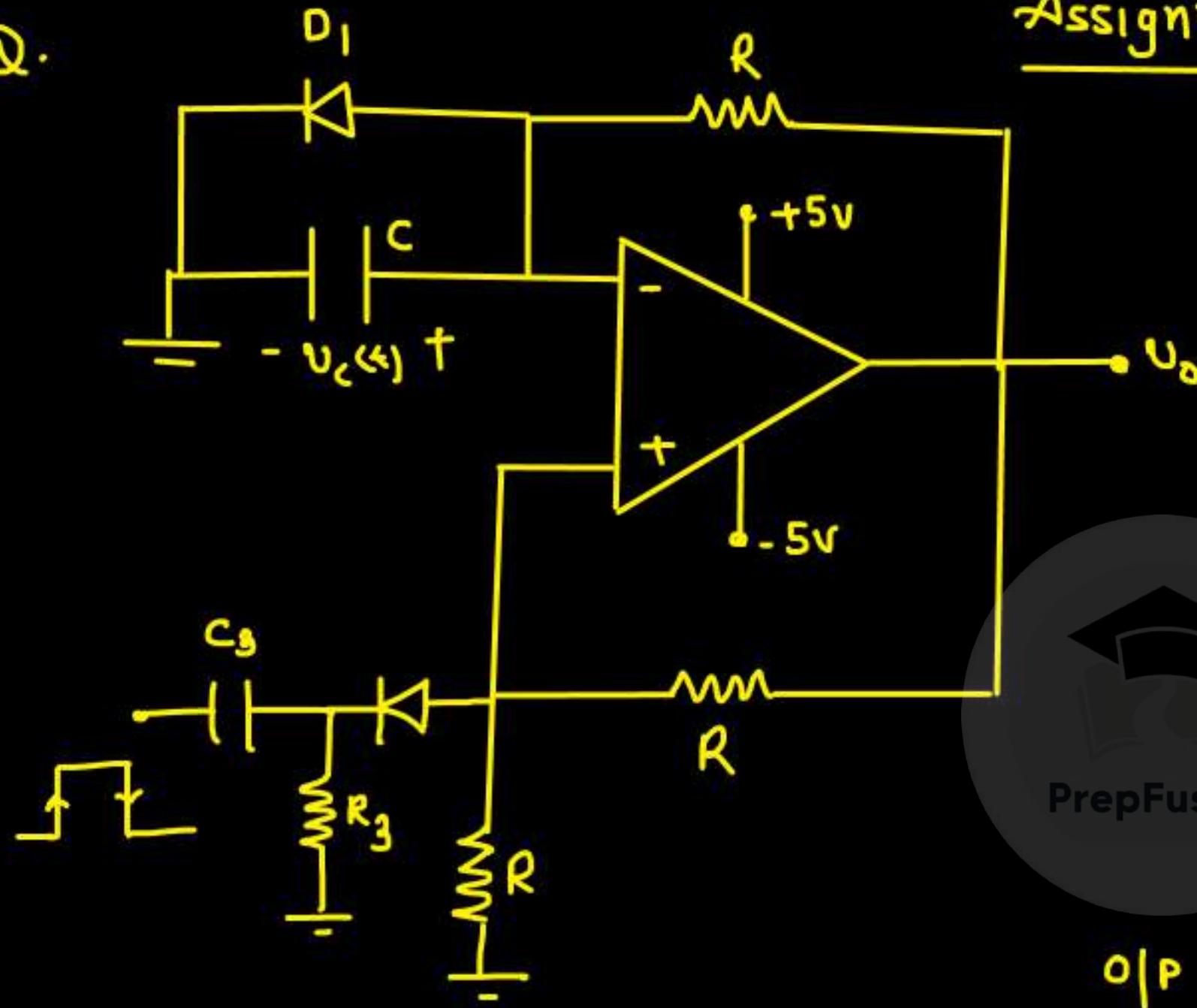

Given that

$R_3 C_3$  value is very small.


$$R = 1\text{ k}\Omega, C = 1\mu\text{F}$$

diode  $D_1$  has  $V_F = 0.7\text{ V}$


O/P will be there in unstable state for —

- (a)  $0.693\text{ ms}$
- (b)  $0.724\text{ ms}$
- (c)  $0.824\text{ ms}$

- (d)  $0.937\text{ ms}$


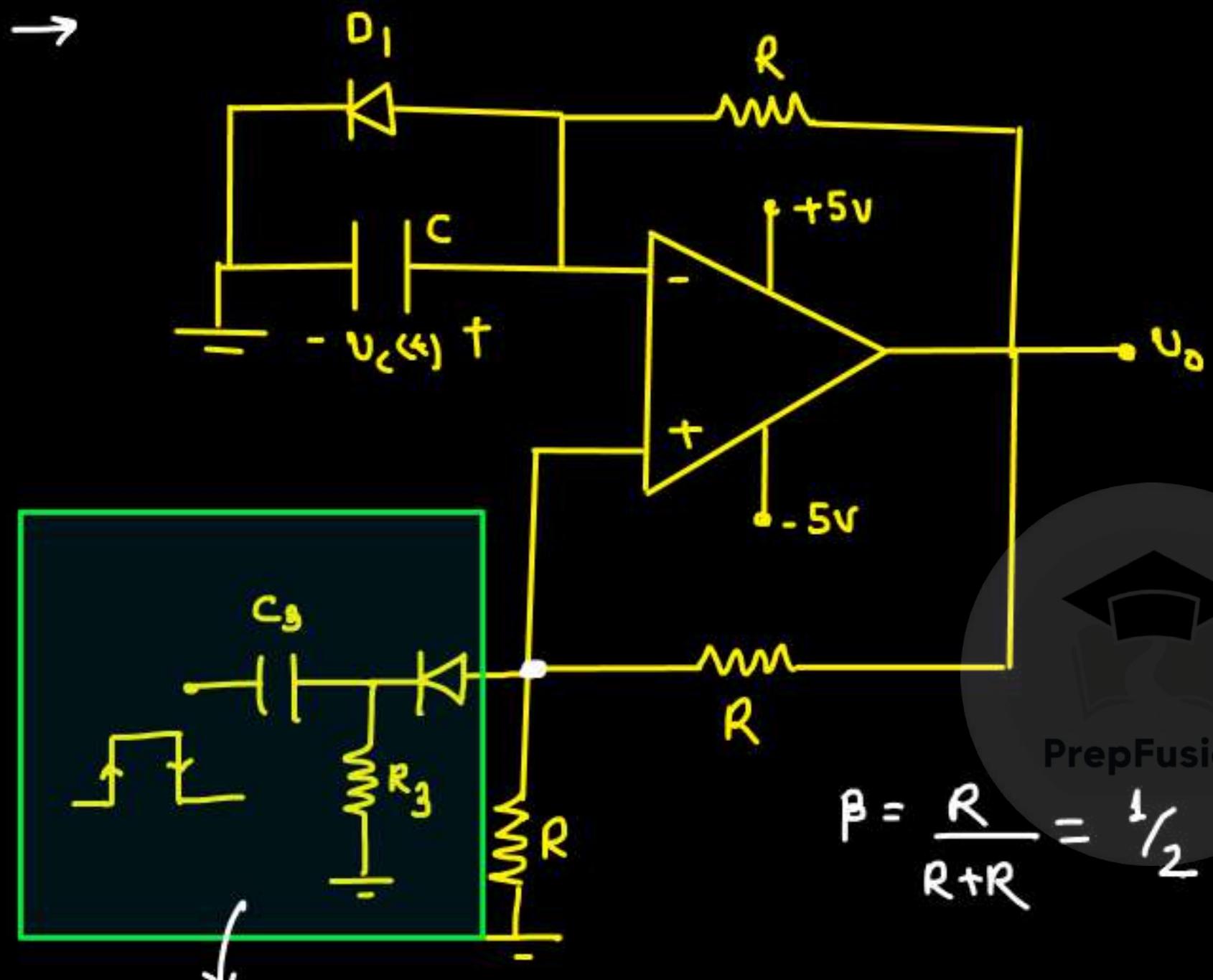


For producing the trigger


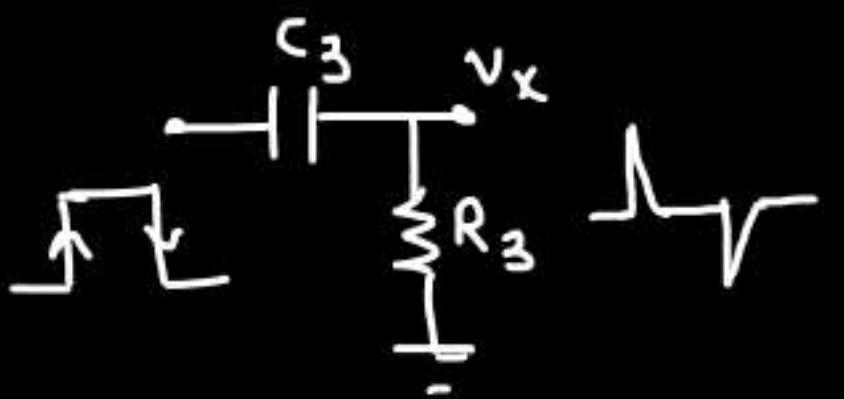

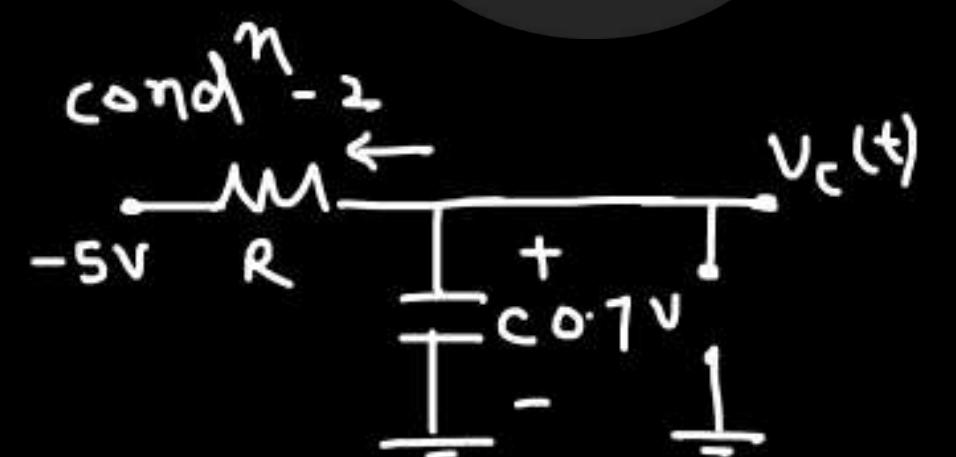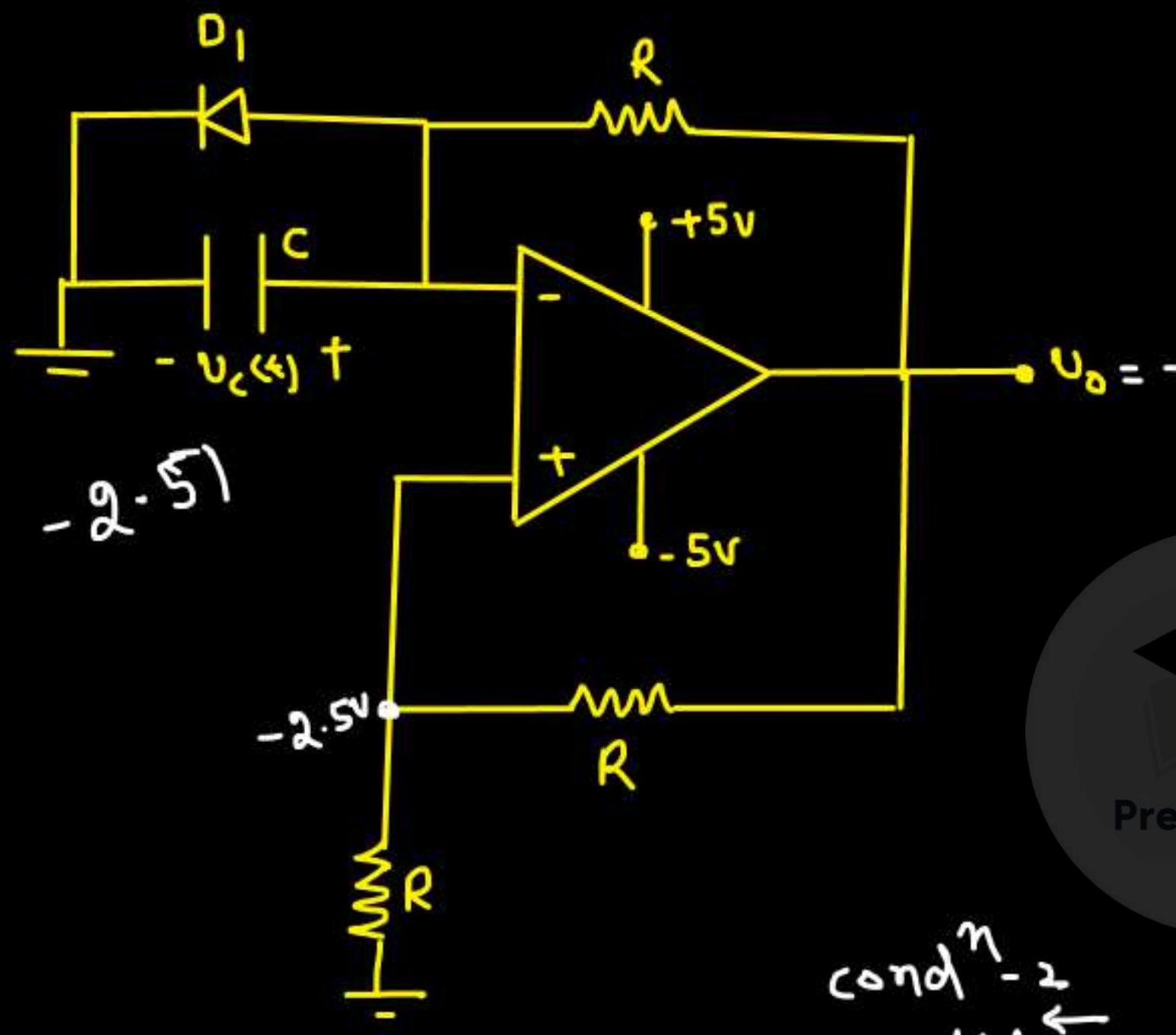
$$\begin{aligned}
 T &= -RC \ln(1-\beta) \\
 &= -Lm \ln(1-\frac{1}{2}) \\
 &= Lm \ln(2) \\
 T &= 0.693ms
 \end{aligned}$$




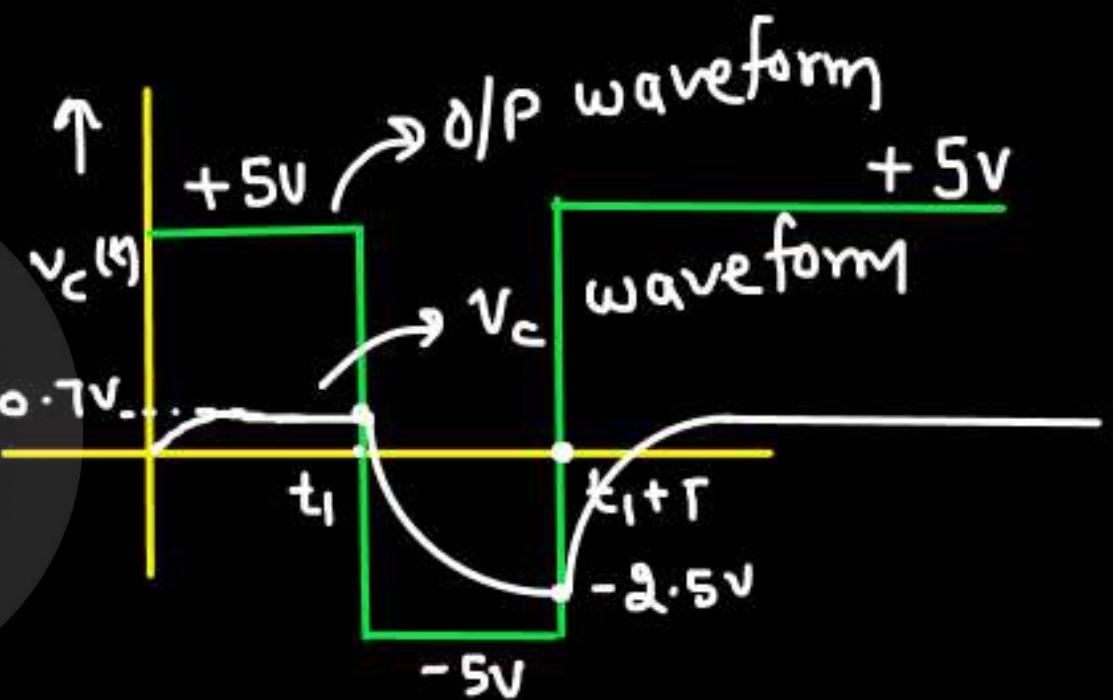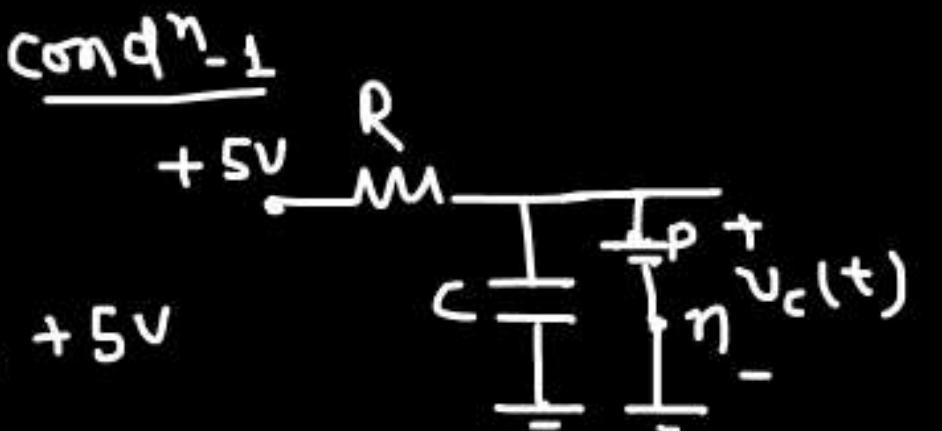
$$V_c(t_1) = 0.7V, \quad V_c(\infty) = -5V$$



$$V_c(t) = -5 + 5 \cdot 7 e^{-\frac{(t-t_1)}{RC}}$$


$$\text{at } t = t_1 + T \quad ; \quad V_C(t_1 + T) = -2.5V$$

$$-2.5V = -5 + 5.7 e^{-T/RC}$$

$$T = RC \ln \left( \frac{5.7}{2.5} \right)$$



$$= 1m \ln(2.28)$$

$T = 0.824 \text{ msec.}$

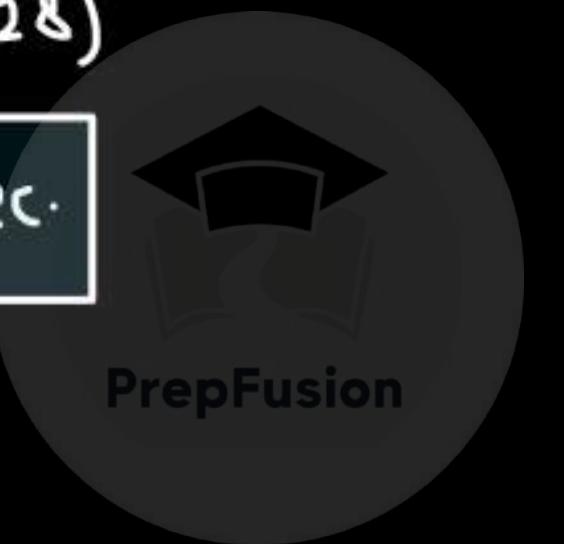

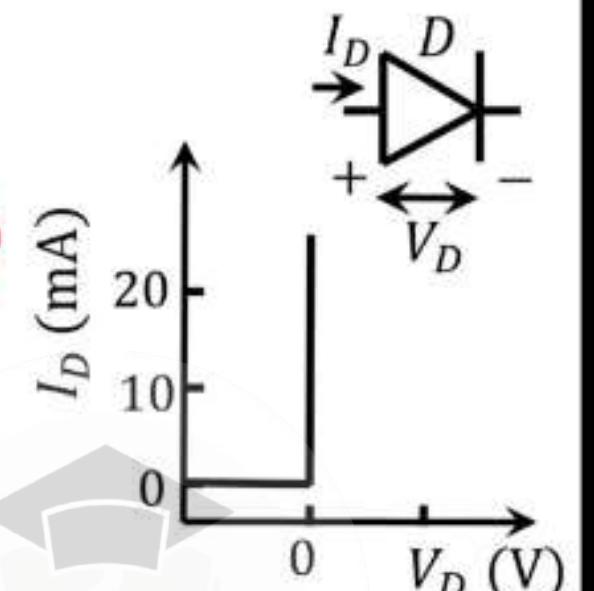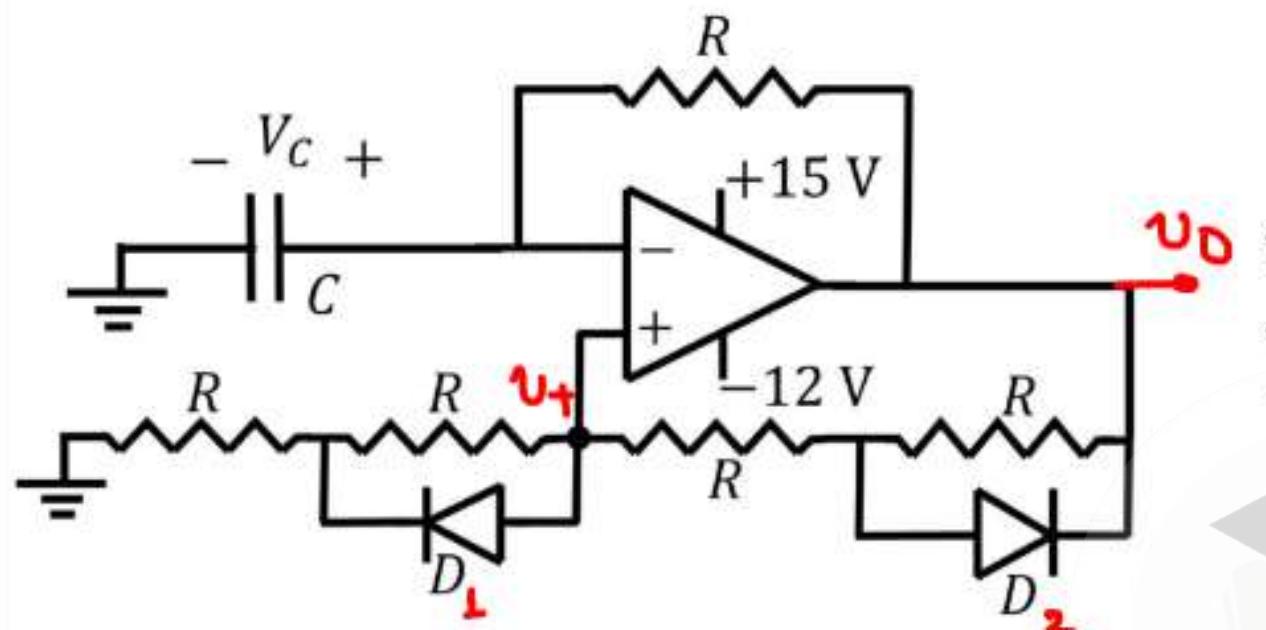Q.41

For the following circuit with an ideal OPAMP, the difference between the maximum and the minimum values of the capacitor voltage ( $V_c$ ) is \_\_\_\_\_.



- (A) 15 V  
 (B) 27 V  
 (C) 13 V  
 (D) 14 V

PrepFusion


if  $u_o = +15V$ ,  $D_1 \rightarrow ON$

$$u_t = \frac{15}{3} = +5V$$



if  $u_o = -12V$ ,  $D_2 \rightarrow ON$

$$u_t = \frac{2}{3} \times (-12) = -8V$$

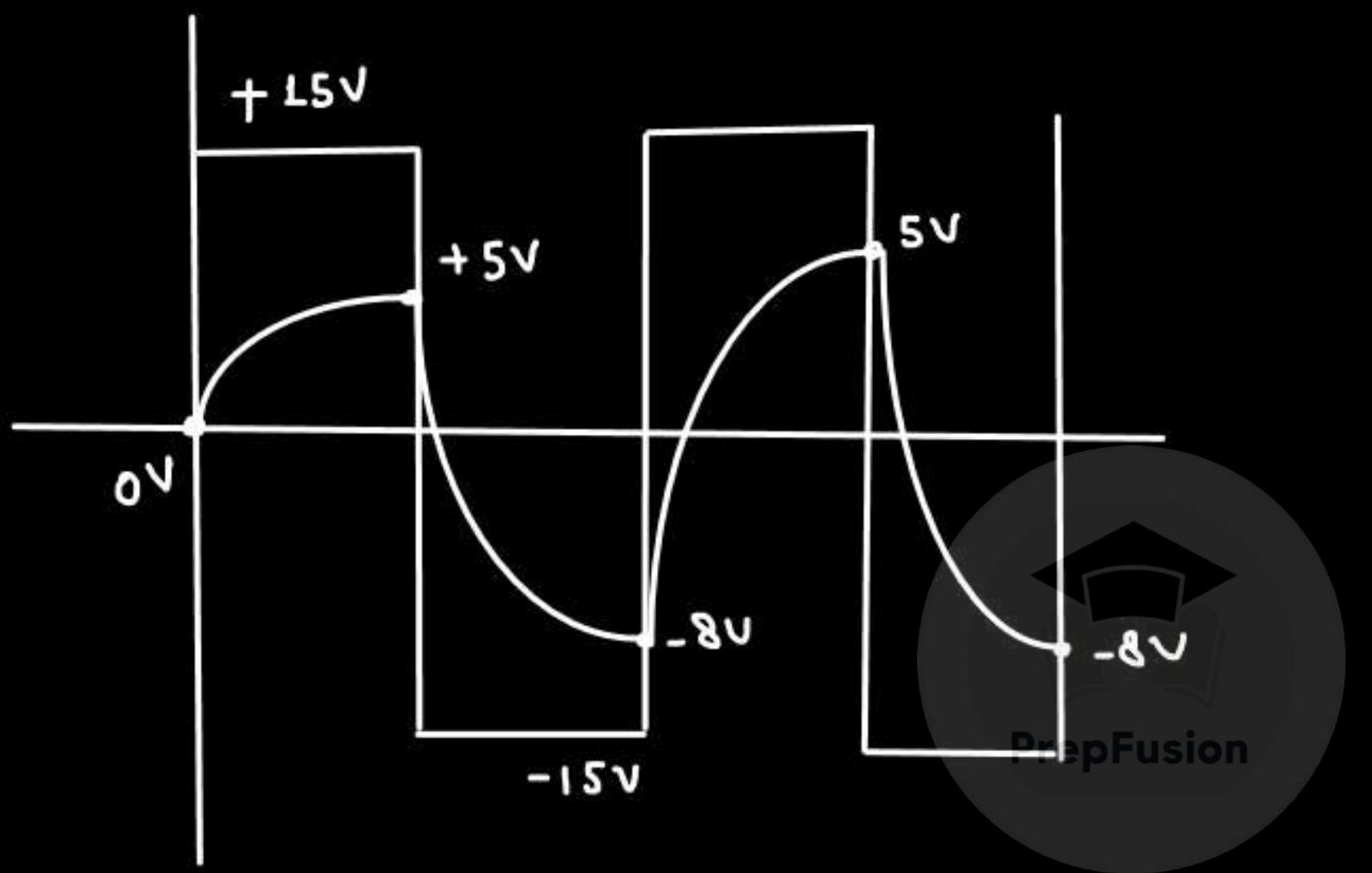


$$(V_C)_{\max} = +5V$$

$$(V_C)_{\min} = -8V$$


$$(V_C)_d = 5 + 8 = 13V$$

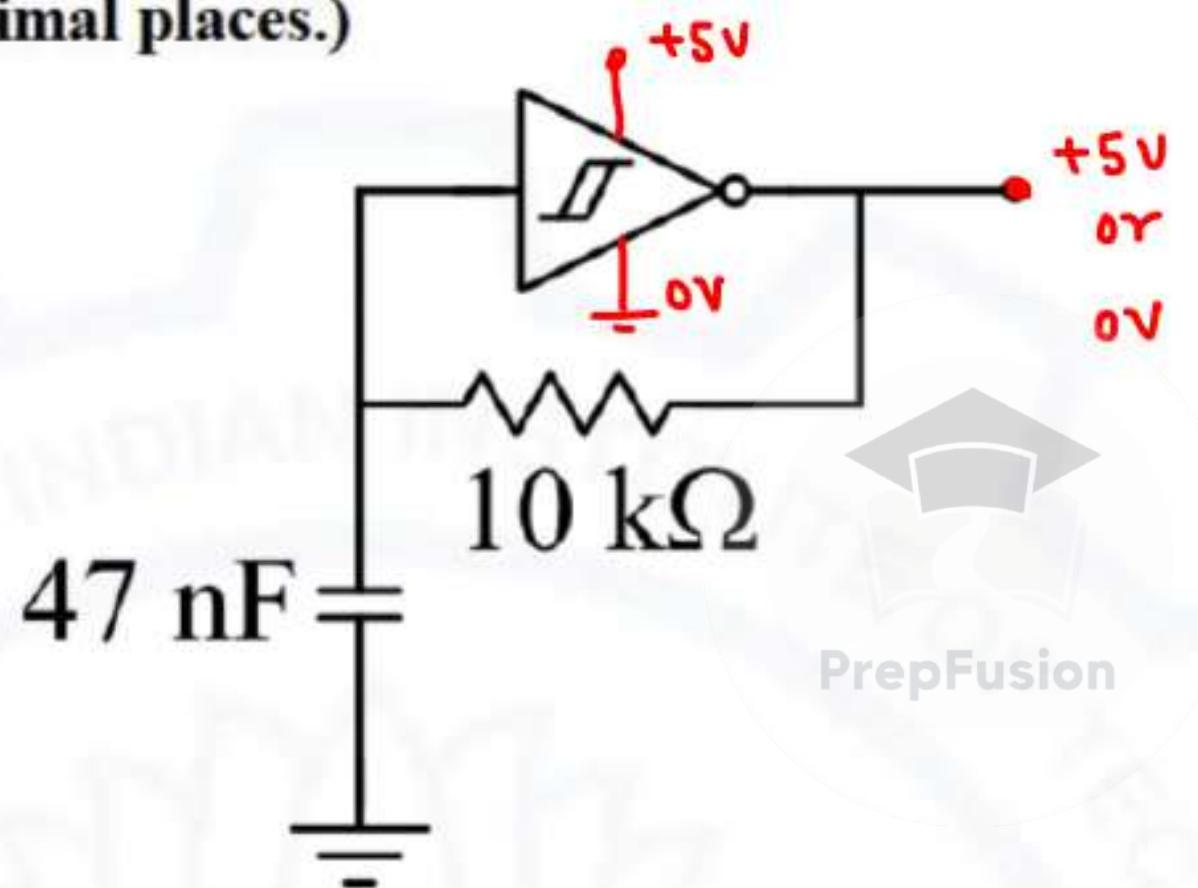A CMOS Schmitt-trigger inverter has a low output level of 0 V and a high output level of 5 V. It has input thresholds of 1.6 V and 2.4 V. The input capacitance and output resistance of the Schmitt-trigger are negligible. The frequency of the oscillator shown is \_\_\_\_\_ Hz.  
(Round off to 2 decimal places.)



$$\frac{1}{2\pi f C} \Rightarrow 0/P \text{ Low} \Rightarrow V_o = 0V$$
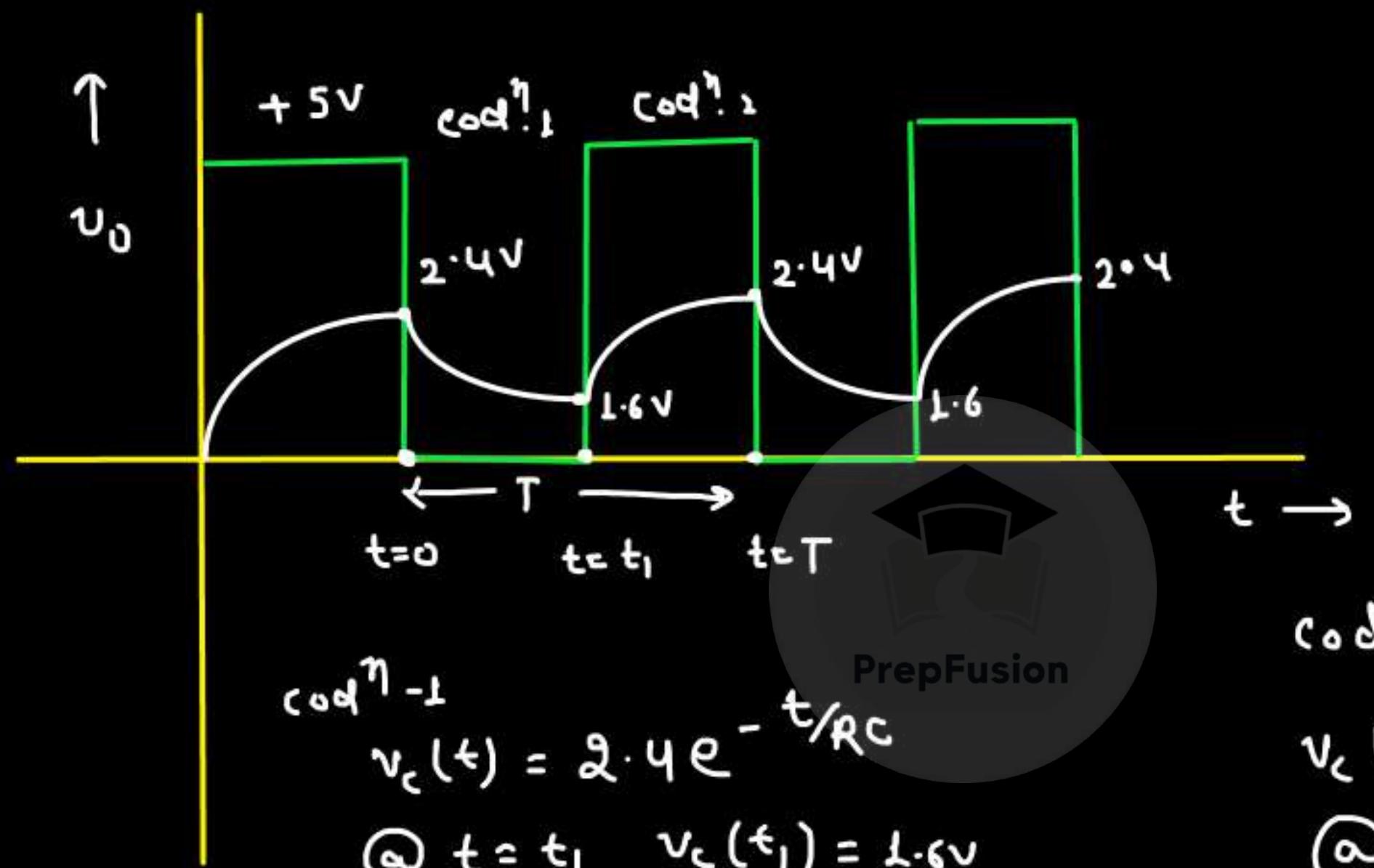
$$\frac{1}{2\pi f C} = 1.6V \Rightarrow 0/P \text{ High} \Rightarrow V_o = +5V$$



$$1.6 = 2.4 e^{-t_1/RC}$$

$$t_1 = RC \ln \left( \frac{3}{2} \right)$$

$t \rightarrow$

$\text{cod } 2$

$$v_c(t) = 5 - 3.4 e^{-(t-t_1)/RC}$$

$$@ t = T \Rightarrow v_c(T) = 2.4$$

$$2.4 = 5 - 3.4 e^{-(T-t_1)/RC}$$

$$T - t_1 = RC \ln \left( \frac{17}{15} \right)$$

$$T - t_1 + t_1 = RC \ln \left( \frac{17}{13} \right) + RC \ln \left( \frac{3}{2} \right)$$

$$= RC \ln \left( \frac{17}{13} \times \frac{3}{2} \right)$$

$$T = 47\pi \times 10 \text{ K} \ln \left( \frac{51}{26} \right)$$



$$f = \frac{1}{T}$$

PrepFusion

$$f = 3158.03 \text{ Hz}$$



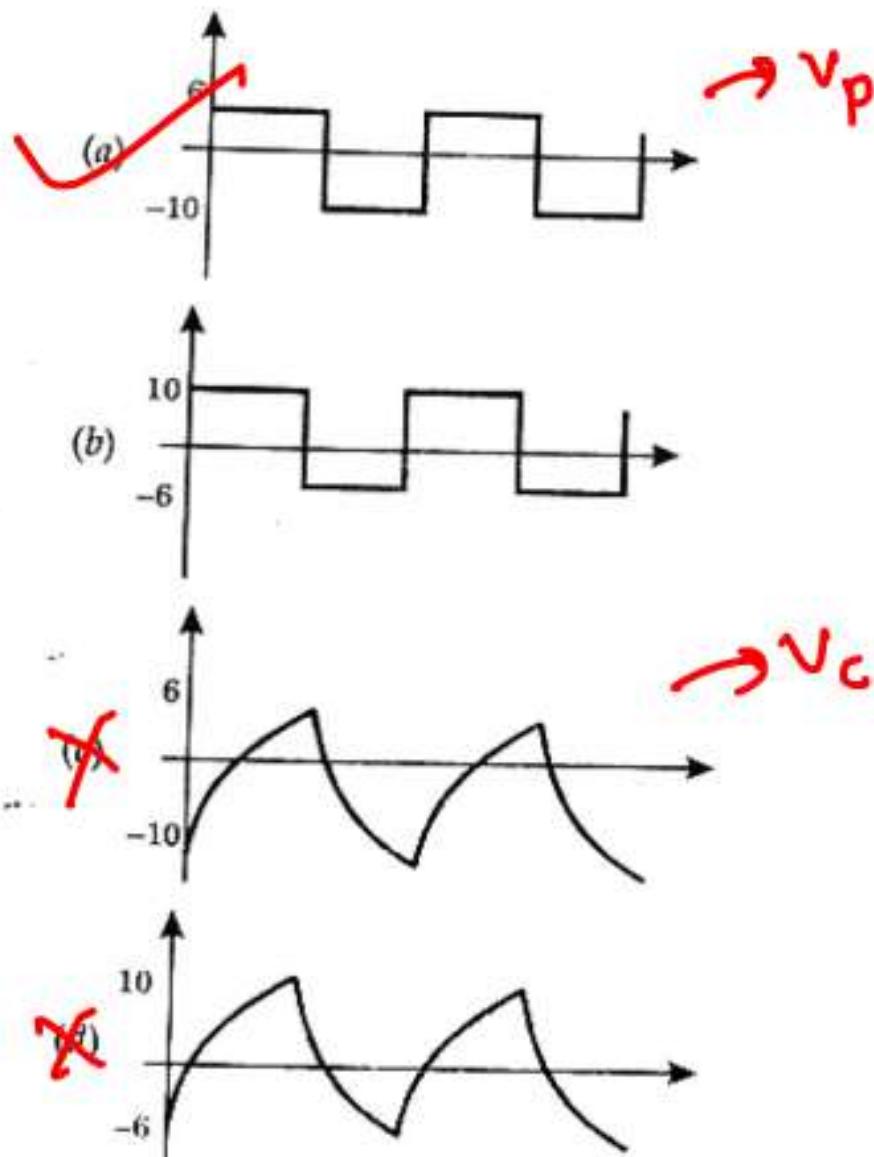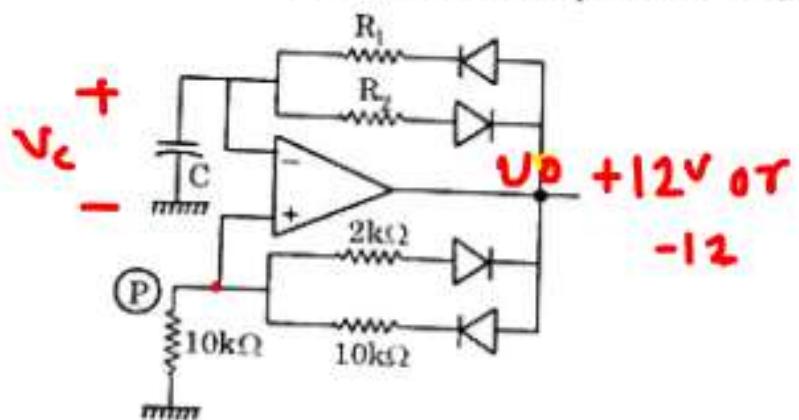59. A relaxation oscillator is made using OPAMP as shown in figure. The supply voltages of the OPAMP are  $\pm 12V$ . The voltage waveform at point P will be




→ if  $U_o = +12V$

$$v_p = +\frac{12}{2} = +6V$$

if  $U_o = -12V$
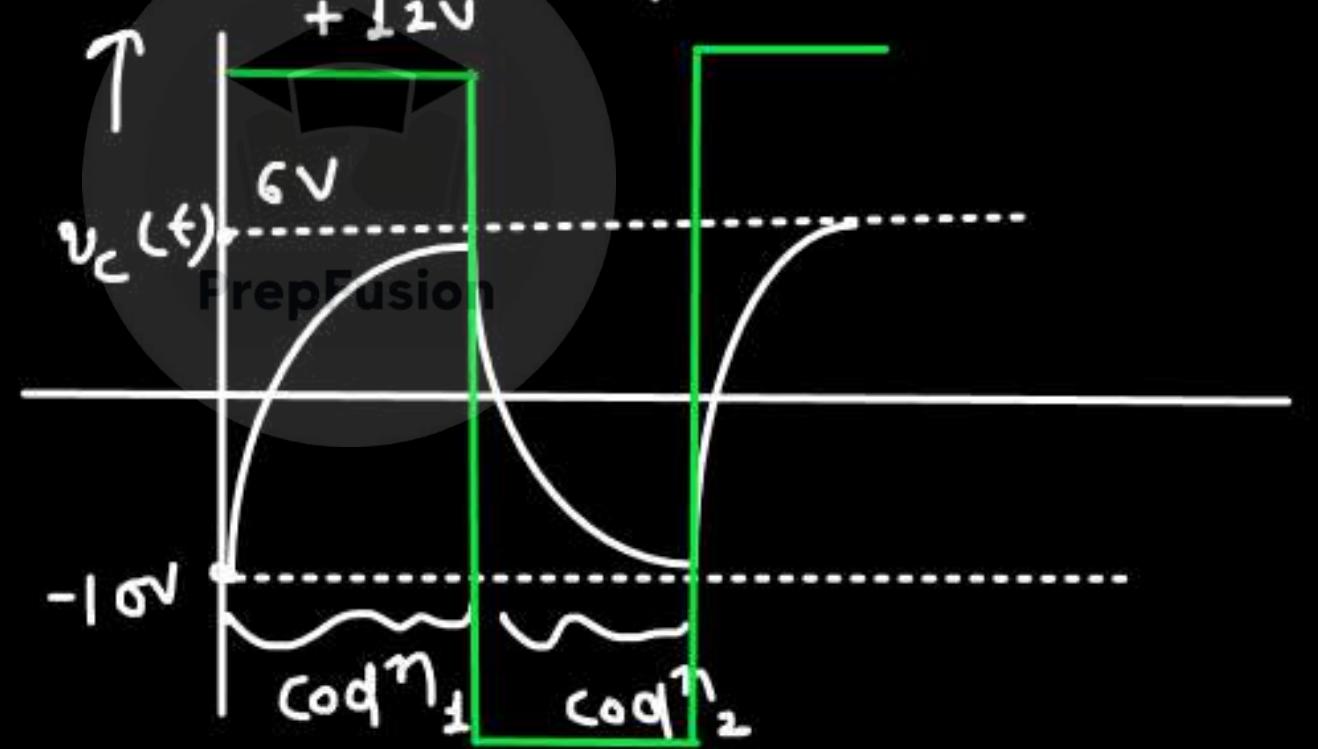
$$v_p = -12 \times \frac{10}{12} = -10V$$



$$v_c(t) = 12 - 22 e^{-t/R_F C}$$

$$6 = 12 - 22 e^{-t_1/R_1 C}$$

$$t_1 = R_1 C \ln(22/6)$$

$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty)) e^{-t/R_1 C}$$


Ques 1-2

$$v_c(t) = -12 + 18 e^{-t/R_2 C}$$


$$-10 = -12 + 18 e^{-t_2/R_2 C}$$

$$t_2 = R_2 C \ln(9)$$
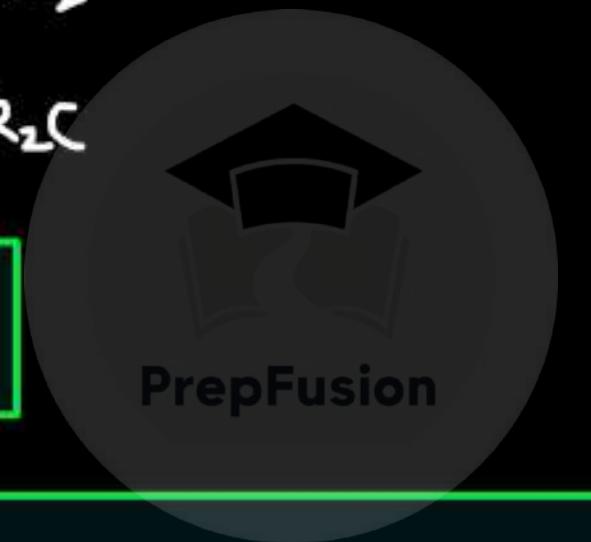
$$\text{Time period } T = t_1 + t_2 = R_1 C \ln\left(\frac{22}{6}\right) + R_2 C \ln(9)$$



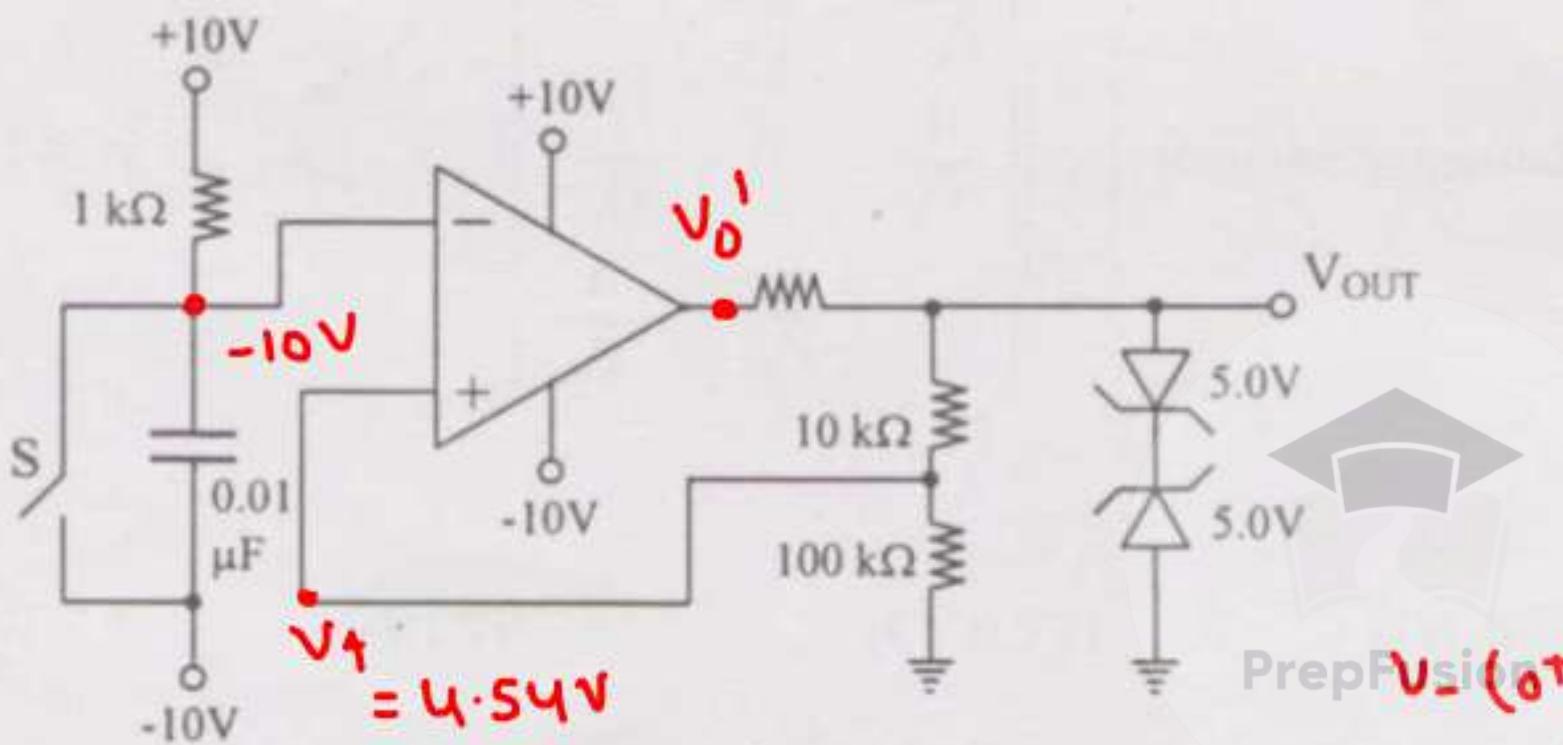The switch S in the circuit of the figure is initially closed. It is opened at time  $t = 0$ . You may neglect the Zener diode forward voltage drops. What is the behaviour of  $V_{\text{OUT}}$  for  $t > 0$ ?



$$\text{Prep} V_{\text{out}}(0^+) = -10 \text{V}$$

$$V_{\text{out}}(\infty) = +10 \text{V}$$

- (A) It makes a transition from  $-5 \text{ V}$  to  $+5 \text{ V}$  at  $t = 12.98 \mu\text{s}$
- (B) It makes a transition from  $-5 \text{ V}$  to  $+5 \text{ V}$  at  $t = 2.57 \mu\text{s}$
- (C) It makes a transition from  $+5 \text{ V}$  to  $-5 \text{ V}$  at  $t = 12.98 \mu\text{s}$
- (D) It makes a transition from  $+5 \text{ V}$  to  $-5 \text{ V}$  at  $t = 2.57 \mu\text{s}$

@  $t = 0^+$

$$V_- = 10 \text{V}$$

Assuming  $V_o' = +10 \text{V}$


$$V_o = +5 \text{V}$$

$$v_t = 5 \times \frac{100}{110} = 4.54 \text{V}$$

Assumption correct

$$V_o(0^+) = 5 \text{V}$$

$$v_t(0^+) = 4.54 \text{V}$$

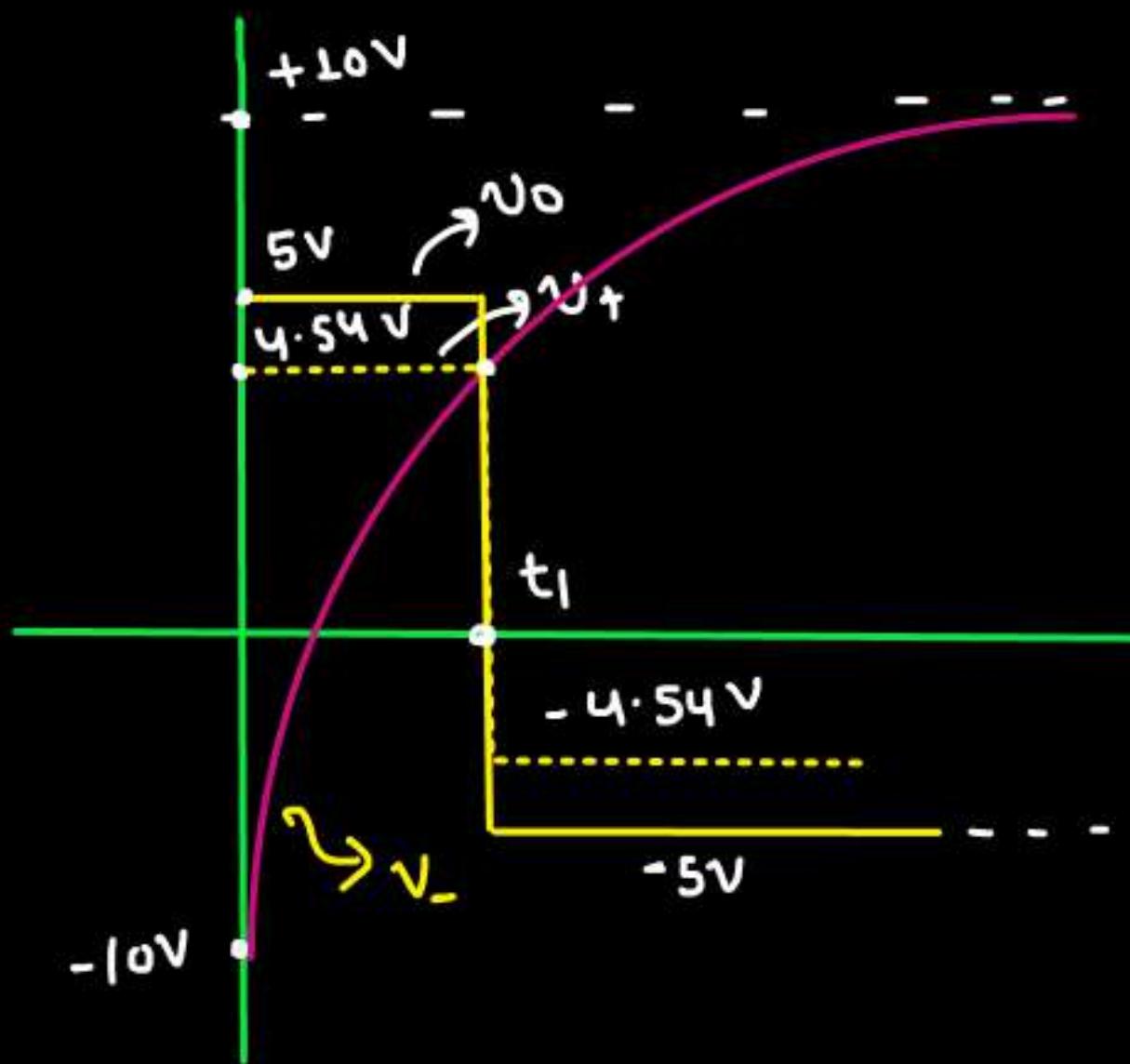

$$v_-(t_1^+) > 4.54V$$

$$v_+(t_1^+) < v_-(t_1^+)$$

↓

$$v_o(t_1^+) = -5V$$

$$v_+(t_1^+) = -4.54V$$



always  $v_- > v_+$  ( $t > t_1$ )

$$v_o = -5V$$

$$v_-(0^+) = -10$$

$$v_-(\infty) = +10$$

$$v_-(t) = 10 - 20 e^{-t/RC}$$

at  $t = t_1 \Rightarrow$  Transition in o/p


$$v_-(t_1) = 4.54V$$

$$4.54 = 10 - 20 e^{-t_1/RC}$$

$$t_1 = 12.98 \mu s$$

⇒

Q.

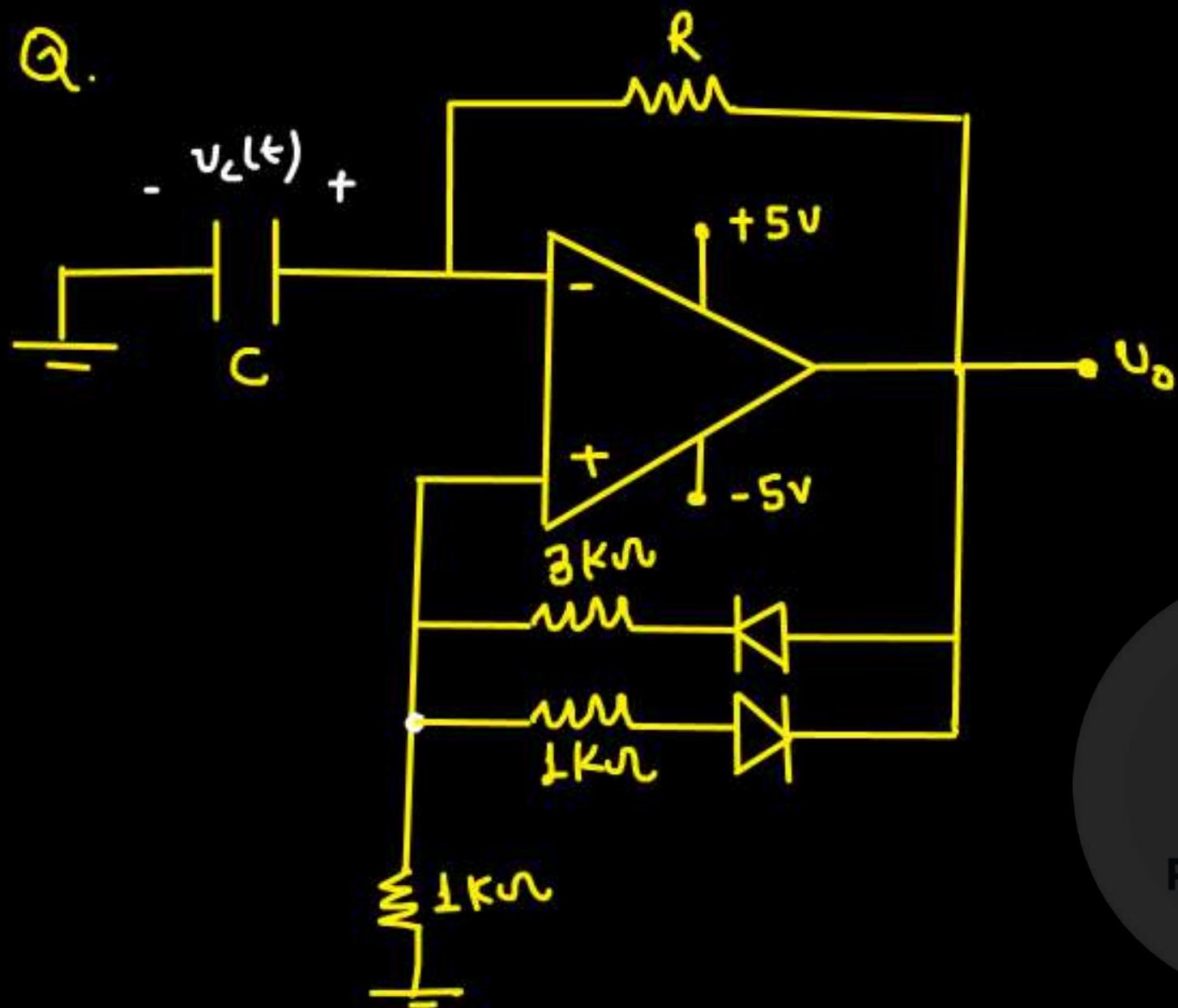


the time duration for +ve part of cycle is  $\Delta t_1$ , and for -ve part of cycle is  $\Delta t_2$ .

Find the value of  $\exp\left(\frac{\Delta t_1 - \Delta t_2}{R_C}\right)$ .  
PrepFusion

→ if  $U_o = +5V$ ,  $U_+ = 1.25V$

if  $U_o = -5V$ ,  $U_+ = -2.5V$

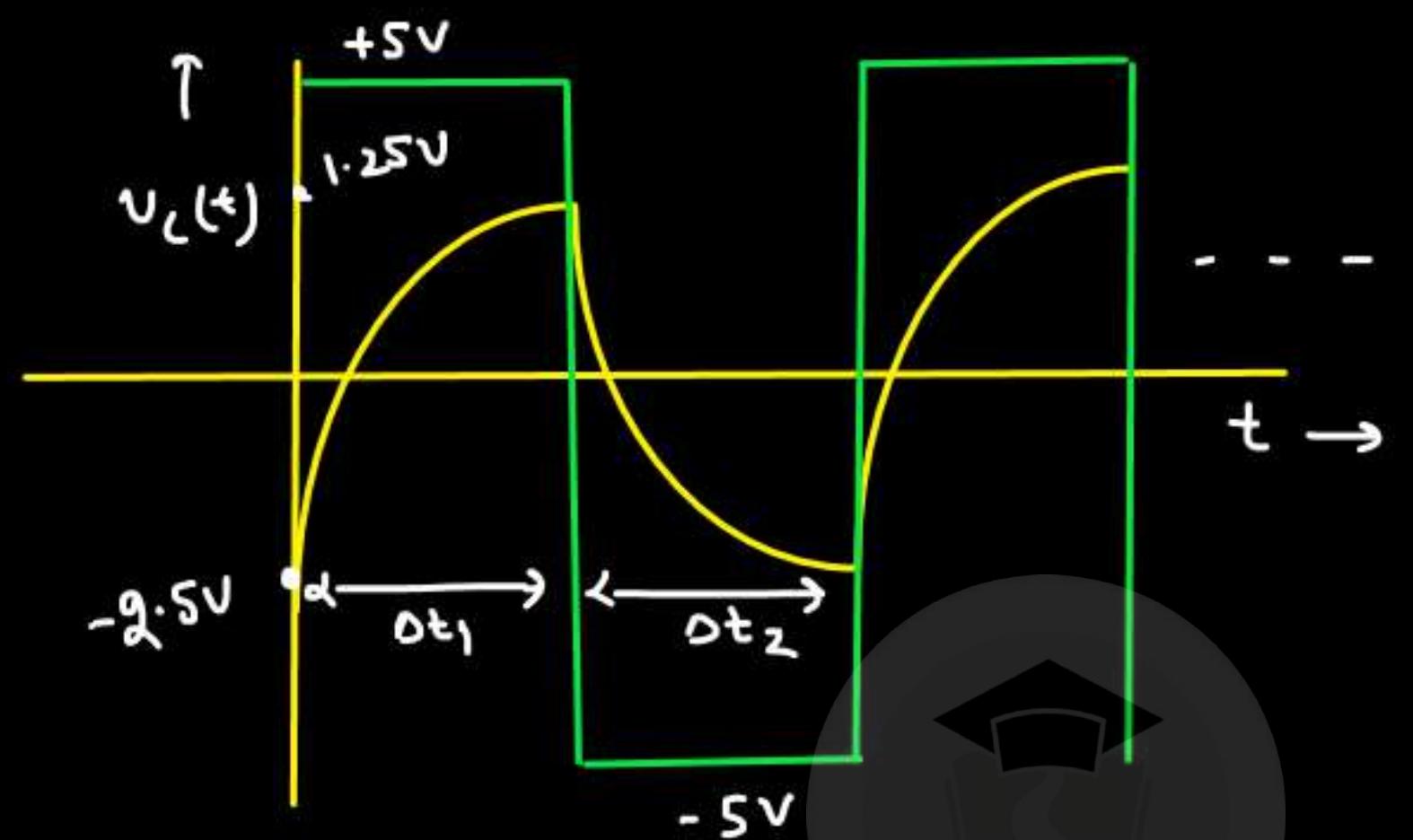

PrepFusion

$$1.25 = 5 - 7.5 e^{-\Delta t_1 / RC}$$

$$e^{-\Delta t_1 / RC} = 0.5 \quad \text{--- } \textcircled{1}$$


$$\text{eq } \textcircled{2} \div \text{eq } \textcircled{1} \Rightarrow e^{\Delta t_1 - \Delta t_2 / RC} = \frac{0.4}{0.5} = 0.8$$

ANS.

$$-2.5 = -5 + 6.25 e^{-\Delta t_2 / RC}$$

$$e^{-\Delta t_2 / RC} = 0.4 \quad \text{--- } \textcircled{2}$$

Q.

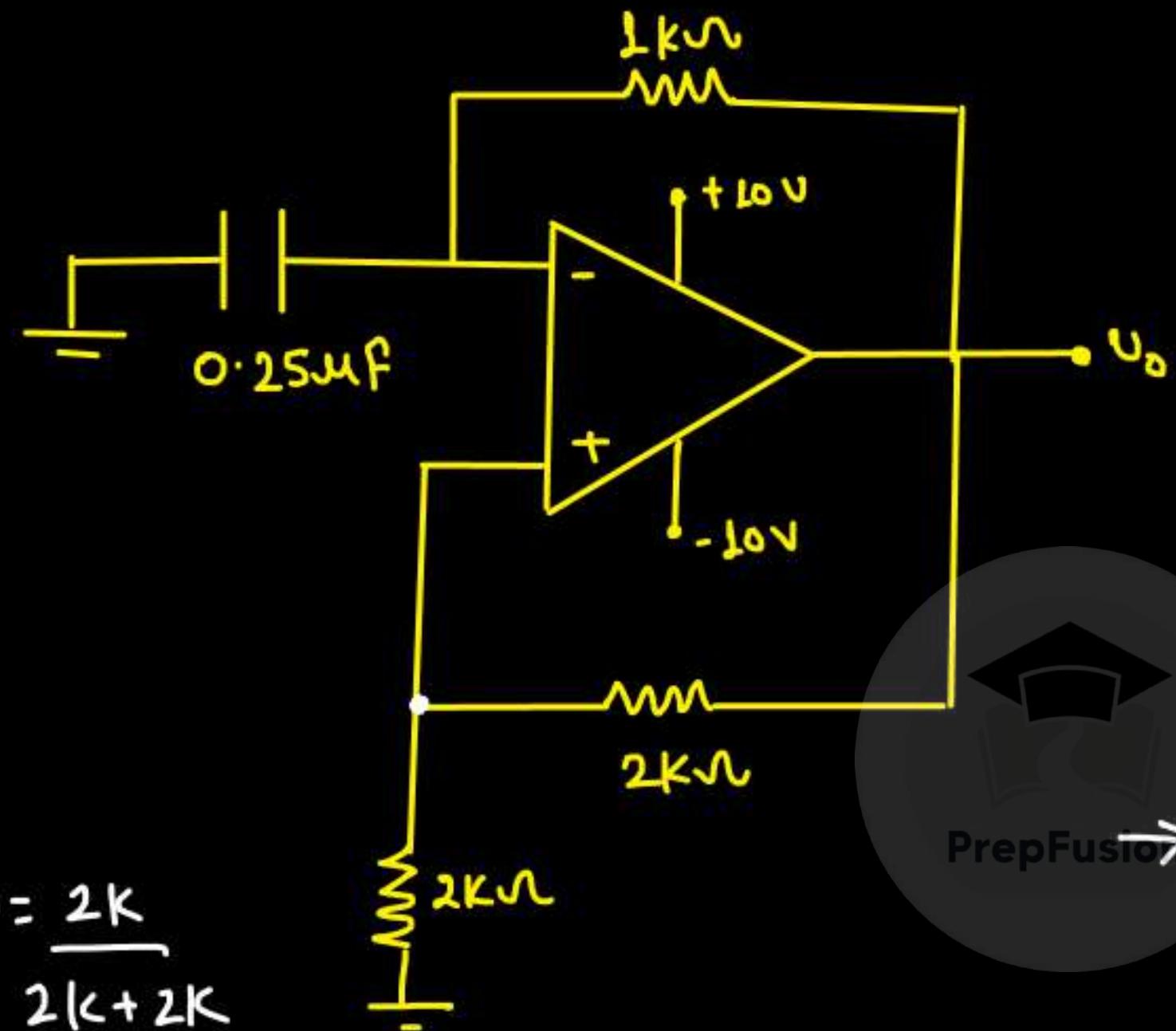

$$\beta = \frac{2K}{2(K+2K)} = \frac{1}{2}$$


Time period of o/p waveform?

PrepFusion →

$$T = RC \ln \left( \frac{1+\beta}{1-\beta} \right) = 0.25\text{m} \ln \left( \frac{3/2}{1/2} \right)$$


T = 0.214 ms

## ⇒ Concept of oscillators :-

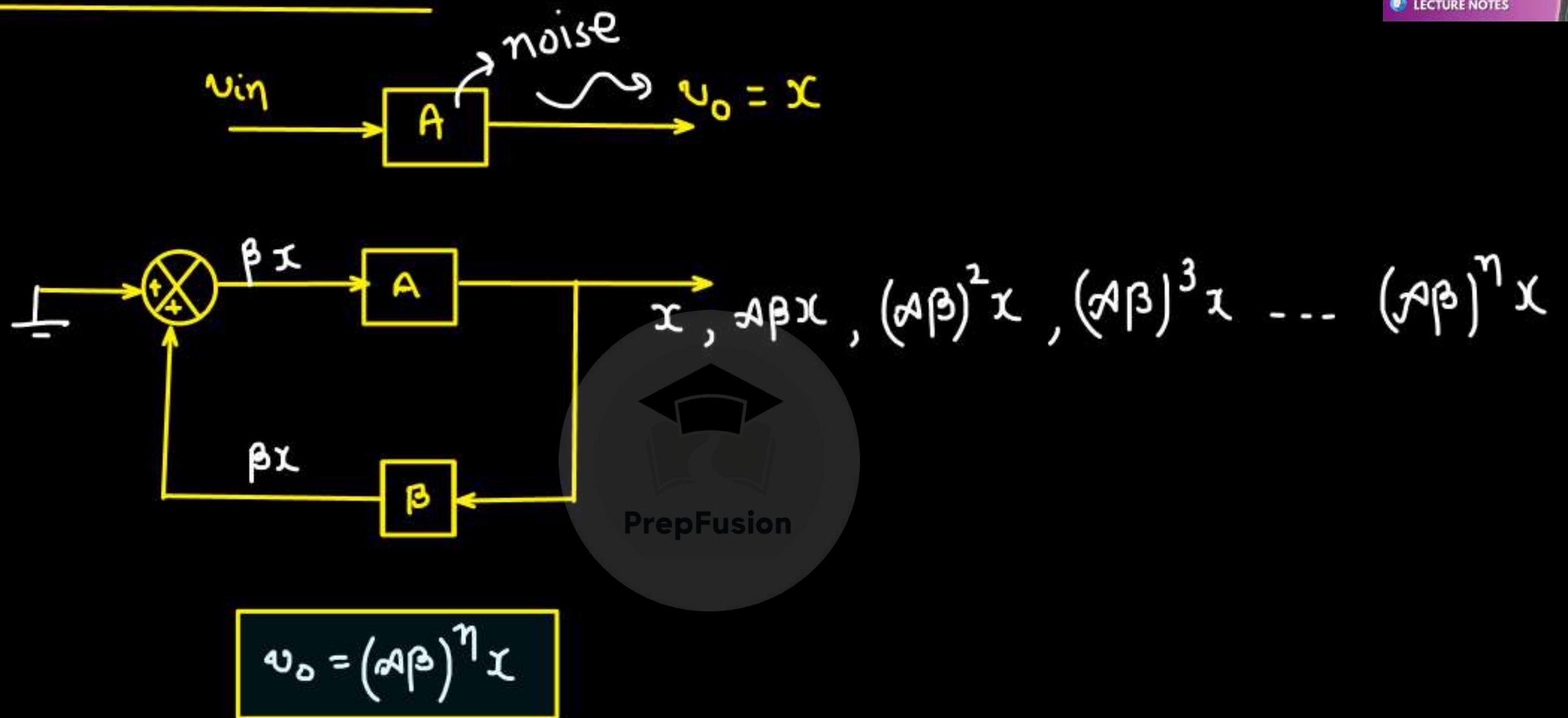

Case 1:-  $\alpha\beta < 1$  {let  $\alpha\beta = 0.5$ }

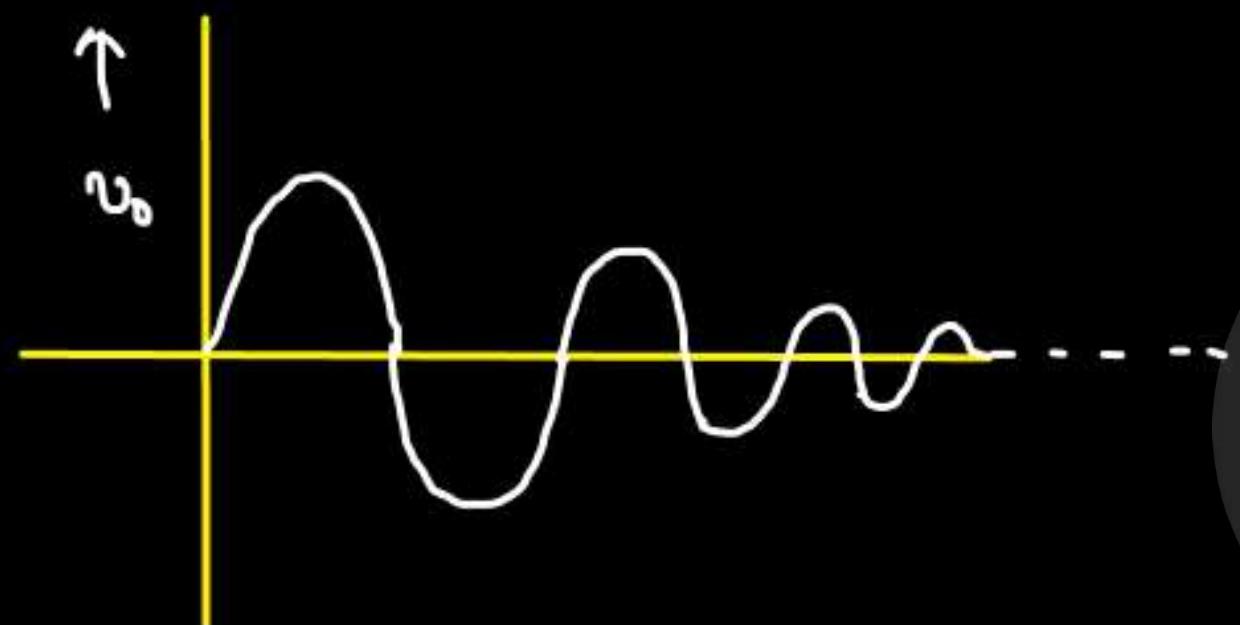
$$v_o = (0.5)^n x \Rightarrow \{0.5x, (0.5)^2 x, (0.5)^3 x \dots\}$$



Case -2:-  $\alpha\beta > 1$

{ let  $\alpha\beta = 2$  }

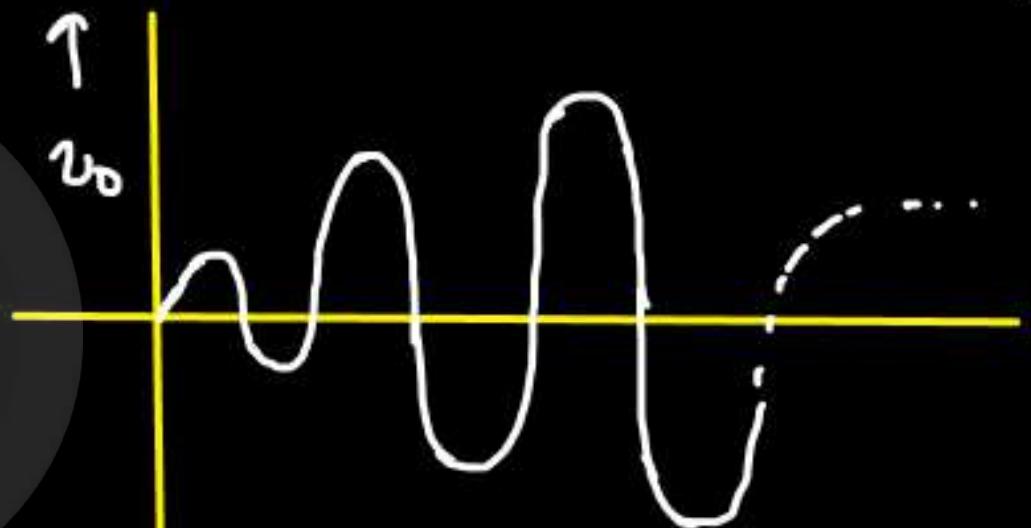
$$v_o = (2)^n x \Rightarrow \{2x, 4x, 8x \dots\}$$



PrepFusion

Case-3 :-  $\alpha\beta = 1$


$$v_o = x$$

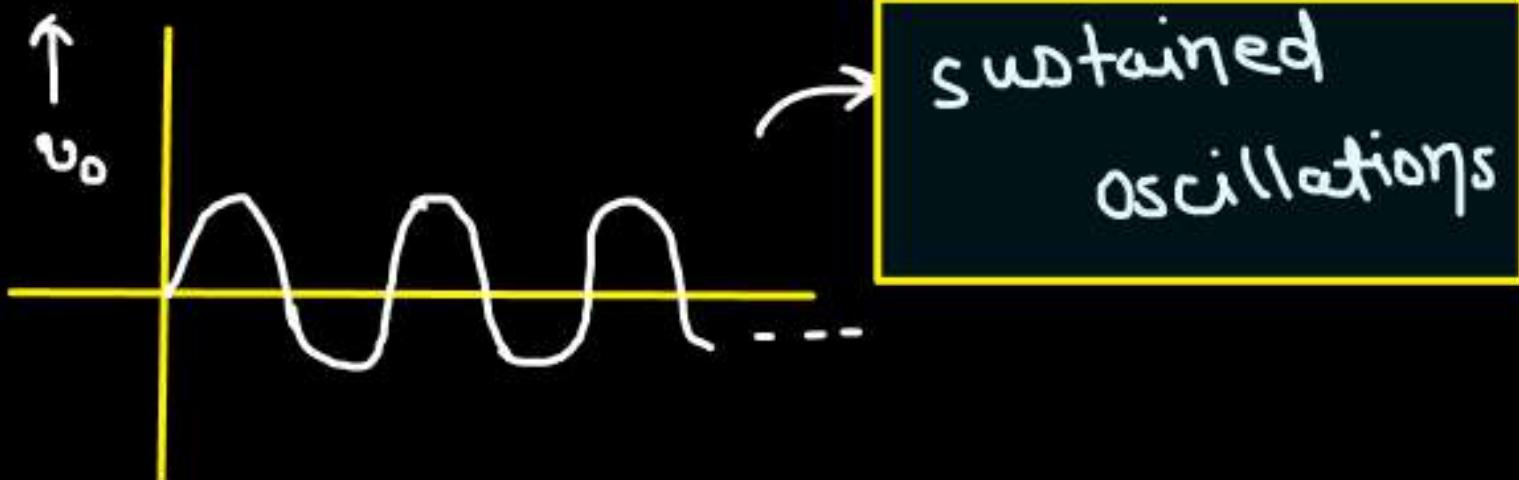




\* For sustained oscillation:-

- (i)  $|A\beta|=1 \Rightarrow$  loop gain should be 1. [Magnitude]
- (ii)  $\angle A\beta = 0^\circ, 360^\circ, 720^\circ \dots 2n\pi$  {where,  $n=0, 1, 2 \dots$ }


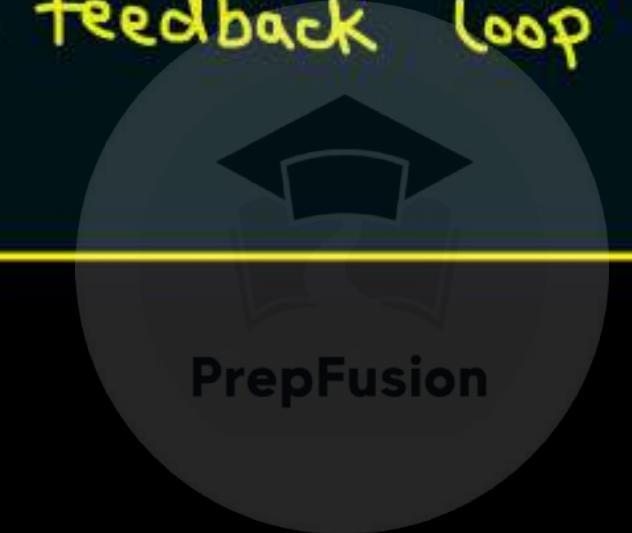
Phase shift around the feedback loop must be zero/multiple of  $2\pi$ .



## ⇒ Amplifiers v/s Oscillators :-

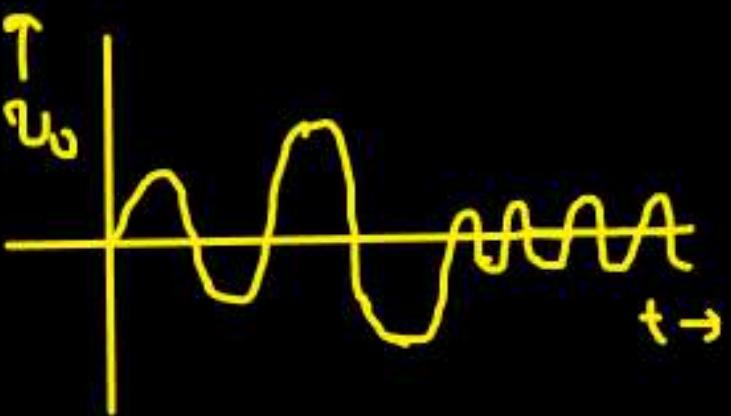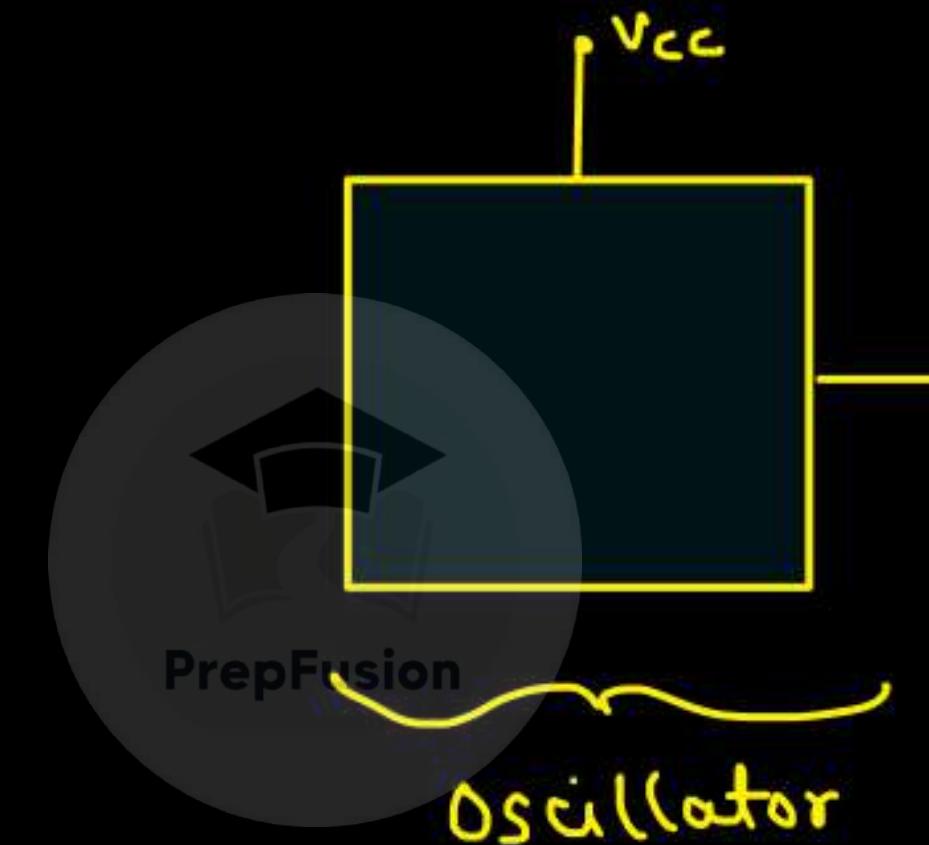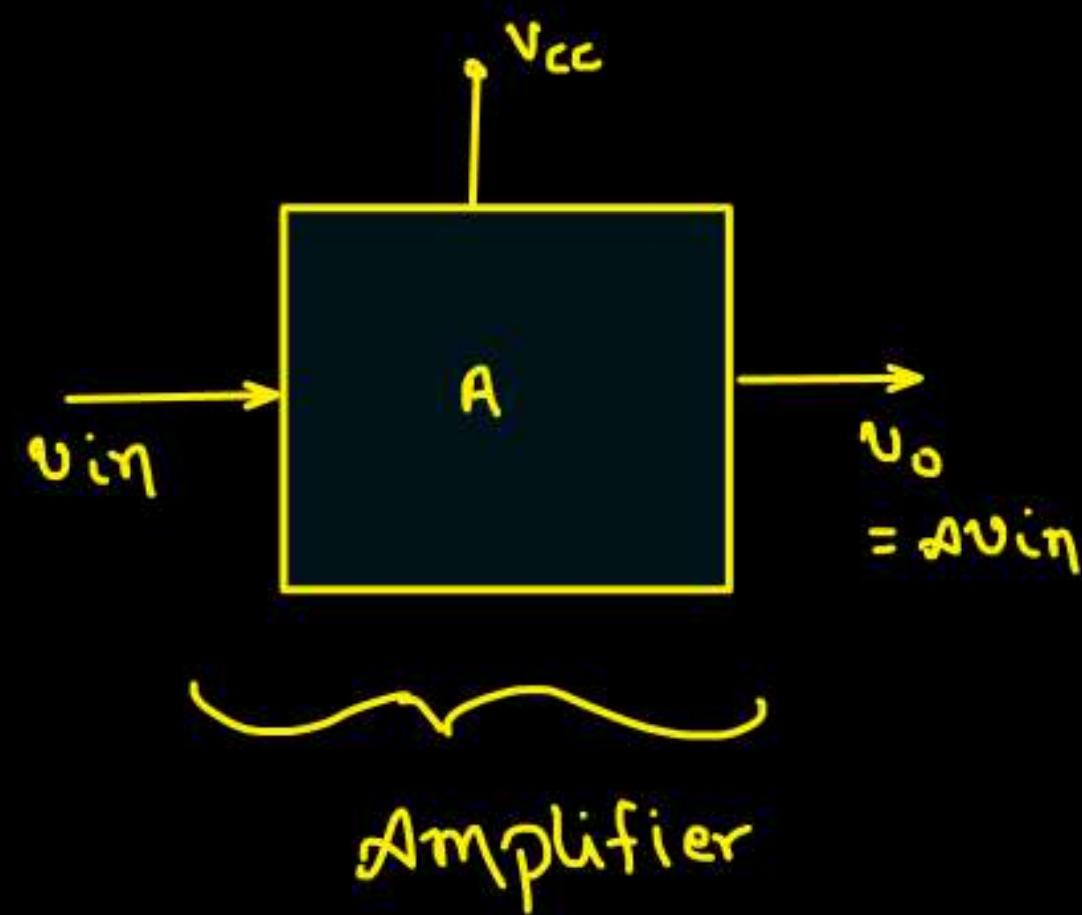

Q.

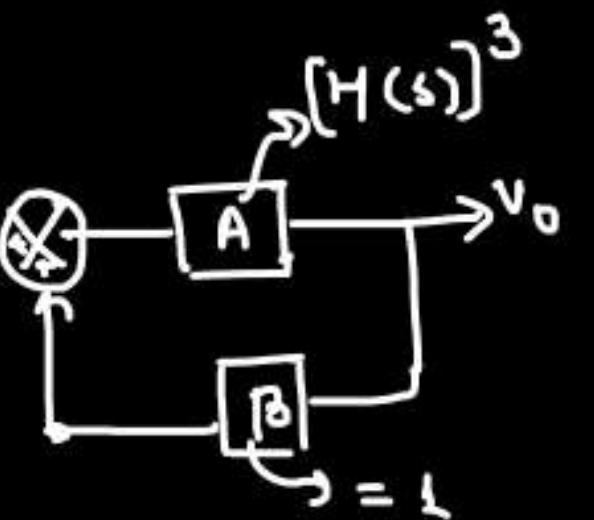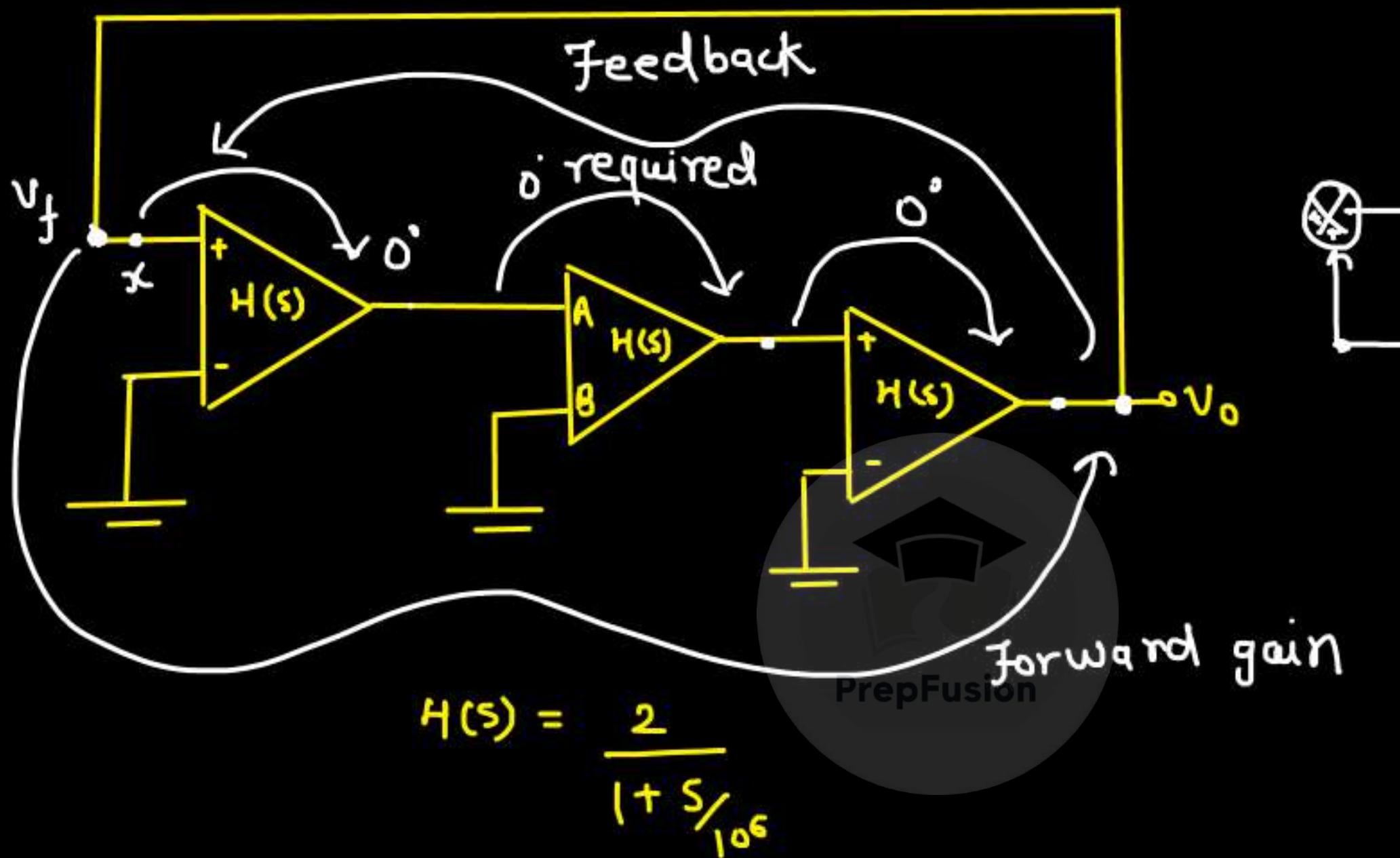

- For sustained Oscillations, what should be sign of A and B ?
- What will be the frequency of oscillations ?

(a) Here

$$V_f = V_o$$

$$\beta = 1$$

$\Rightarrow$  phase shift in f/b path = 0

$$\angle \beta = 0^\circ$$

required :-  $\angle A = 0^\circ \Rightarrow$  forward path phase shift = 0

$$A = +ve, \quad B = -ve$$

$$A = -ve, \quad B = +ve$$



(b)

$$\beta = 1$$

$$A = -[H(s)]^3 = -\frac{(2)^3}{\left(1 + \frac{s}{10^4}\right)^3}$$

$$A\beta = \frac{-8}{\left(1 + \frac{s}{10^6}\right)^3}$$

$$\begin{aligned} A\beta &= \frac{-8}{1 + \frac{s^3}{(10^6)^3} + \frac{3s^2}{(10^6)^2} + \frac{3s}{10^6}} \\ &= \frac{-8}{1 - j\omega^3 - \frac{3\omega^2}{(10^6)^2} + \frac{3j\omega}{10^6}} \\ &= \frac{-8}{1 - \frac{3\omega^2}{(10^6)^2} + j\left[\frac{3\omega}{10^6} - \frac{\omega^3}{(10^6)^3}\right]} \end{aligned}$$

$\angle A\beta = 0^\circ$  PrepFusion → required

$$\text{Imag. } [A\beta] = 0$$


$$\frac{3\omega}{10^6} = \frac{\omega^3}{(10^6)^3}$$

$$\omega = \sqrt[3]{3} \times 10^6 \text{ rad/sec.} \rightarrow \text{freq. of oscillation}$$

$$\alpha\beta \left[ \text{at } \omega = \sqrt{3} \times 10^6 \right] = \frac{-8}{1 - 3 \times 3 \times (10)^6} = 1$$

Here  $\angle \alpha\beta = 0^\circ$




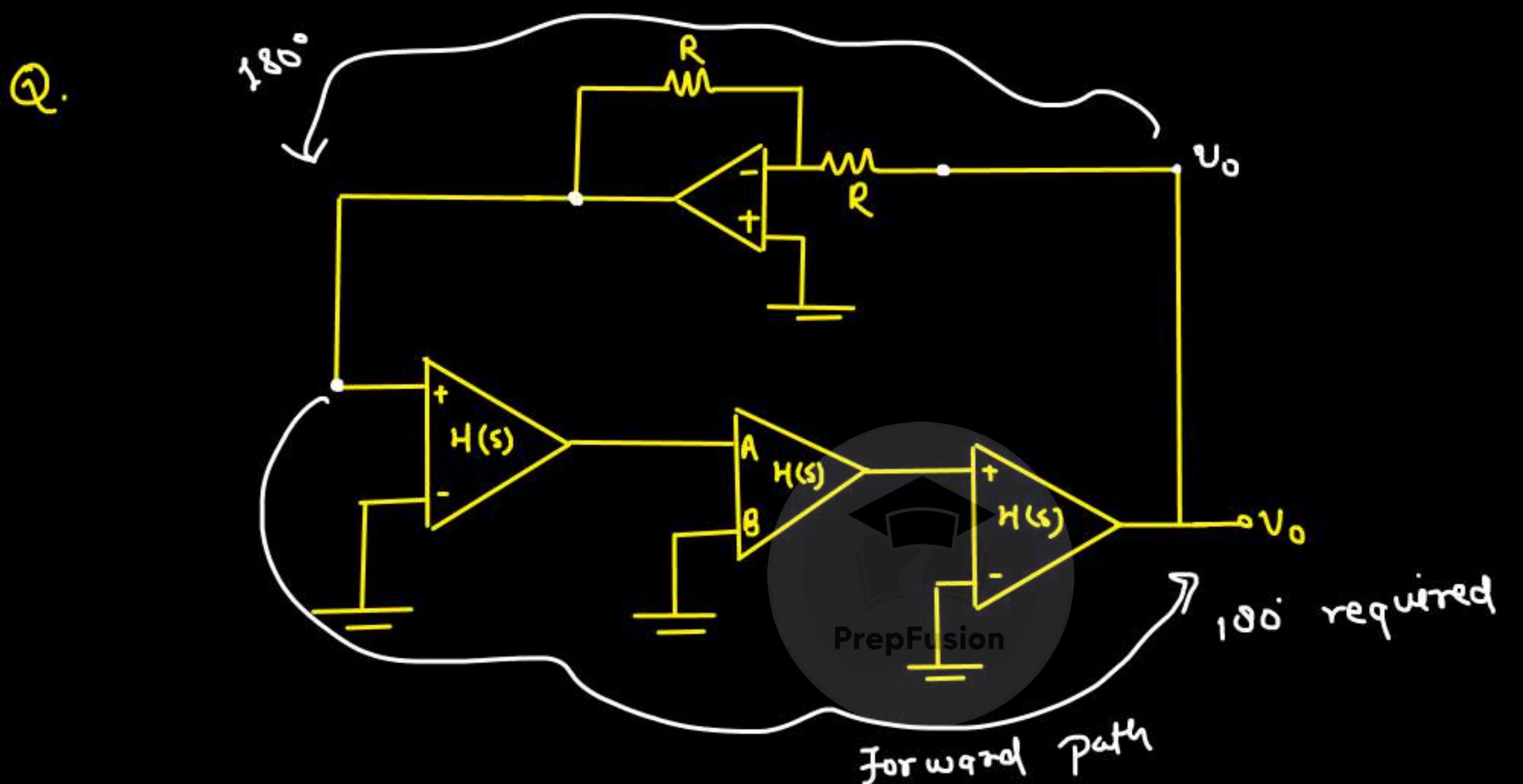

(a) For sustained oscillations, what should be sign of A and B ?

$$\rightarrow A = +\text{ve}, \quad B = -\text{ve}$$


Q.

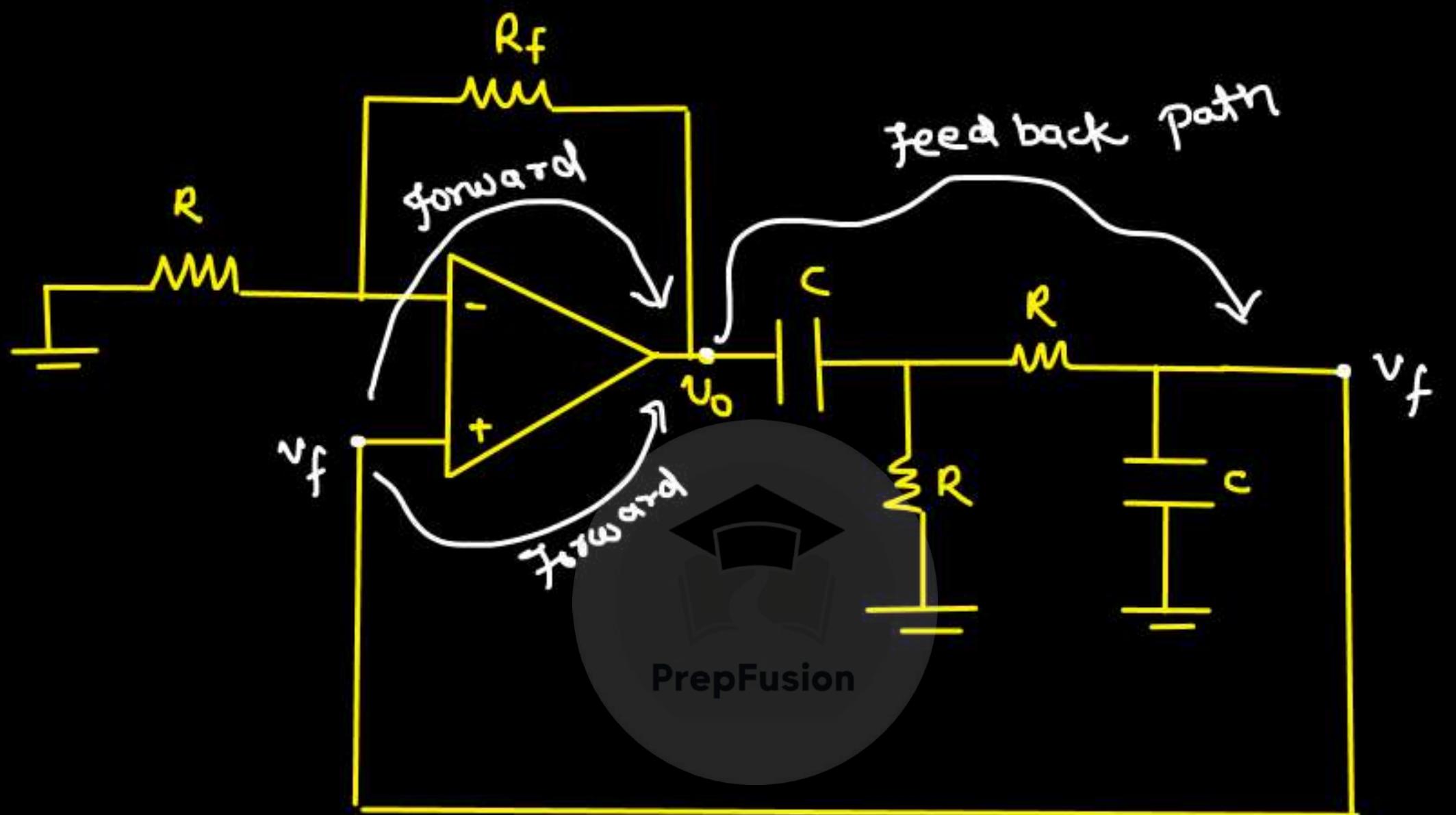

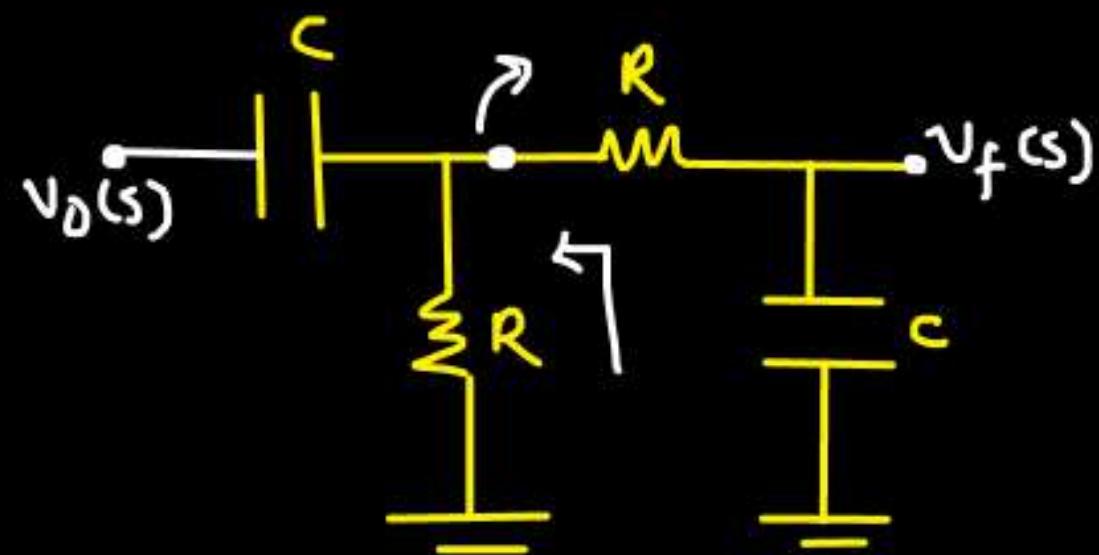- (a) Find the freq. of sustained oscillations.  
 (b) Find the ratio  $\frac{R_f}{R}$  for sustained oscillations.

→ forward path is non-inverting amp.  $\Rightarrow$


$$A = 1 + \frac{R_f}{R}, \quad \angle A = 0^\circ$$



$$v_f(s) = \beta v_o(s)$$

$$\boxed{\beta = \frac{v_f(s)}{v_o(s)}}$$

PrepFusion

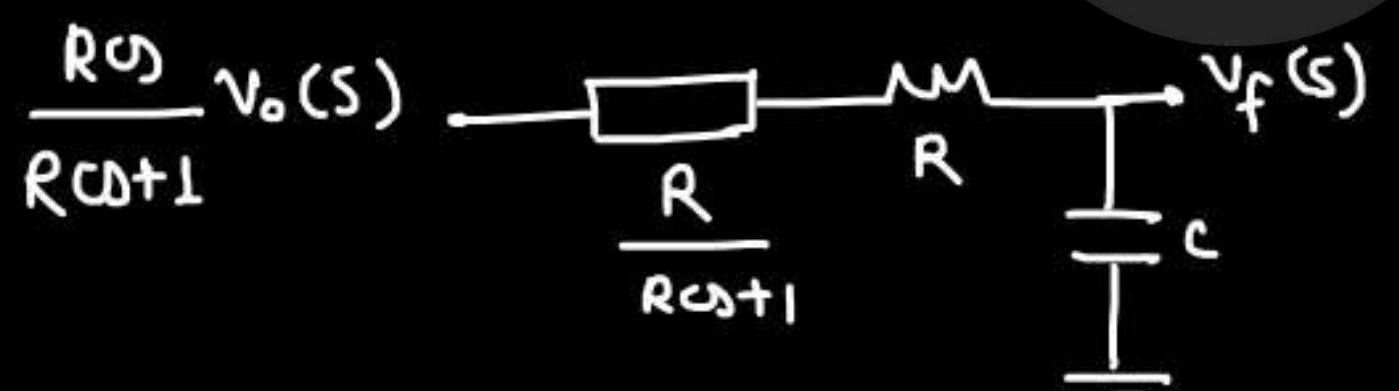

$$v_f(s) = \frac{\frac{1}{C_s}}{\frac{RCs+1}{C_s} + \frac{R}{RCs+1}} \times \frac{RCs}{RCs+1} v_o(s)$$

$$\boxed{\frac{v_f(s)}{v_o(s)} = \frac{RCs}{1 + 3RCs + (RCs)^2}}$$

$$\beta = \frac{j\omega RC}{1 + 3j\omega RC - \omega^2 R^2 C^2} = \frac{j\omega RC}{[1 - \omega^2 R^2 C^2] + 3j\omega RC}$$

$\angle \beta = 0^\circ \rightarrow$  required



$\beta$  has to be real

if  $1 - \omega^2 R^2 C^2 = 0 \Rightarrow \beta$  will be real

\*  $\omega = \frac{1}{RC}$  PrepFusion  $\Rightarrow$  Frequency of Oscillation

$\beta (@ \omega = 1/RC) = 1/3 \Rightarrow \angle \beta = 0^\circ, \angle A = 0^\circ$

$|\alpha \beta| = 1 \Rightarrow \alpha = 3 \Rightarrow 1 + \frac{R_f}{R} = 3 \Rightarrow R_f = 2R$

## \* Wein bridge oscillator:-


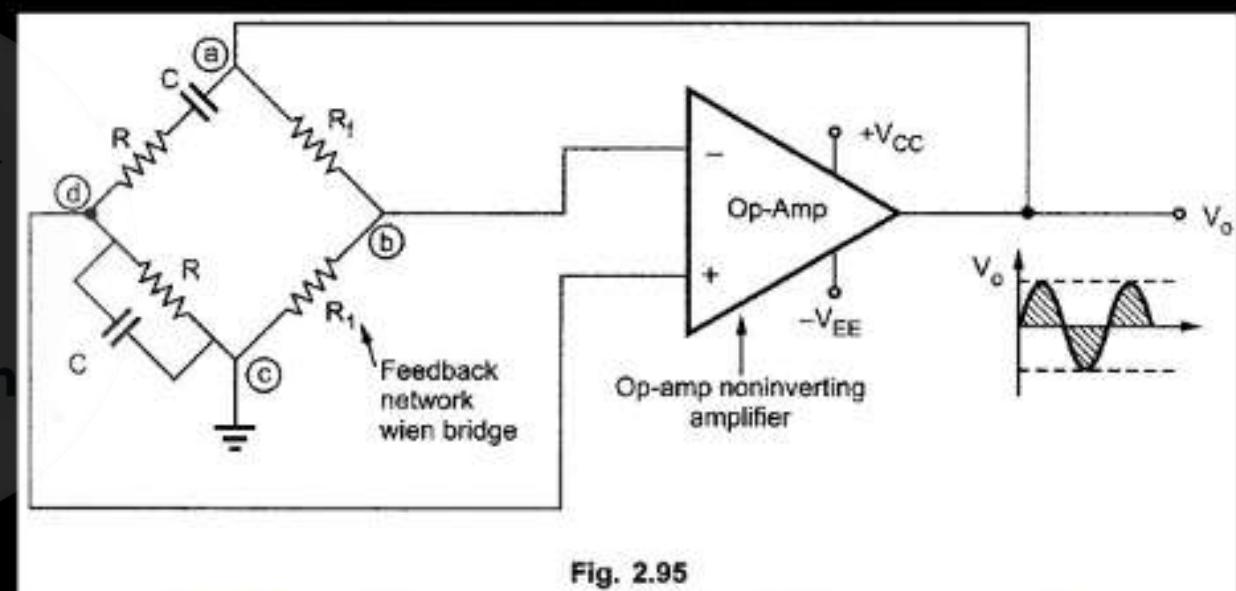
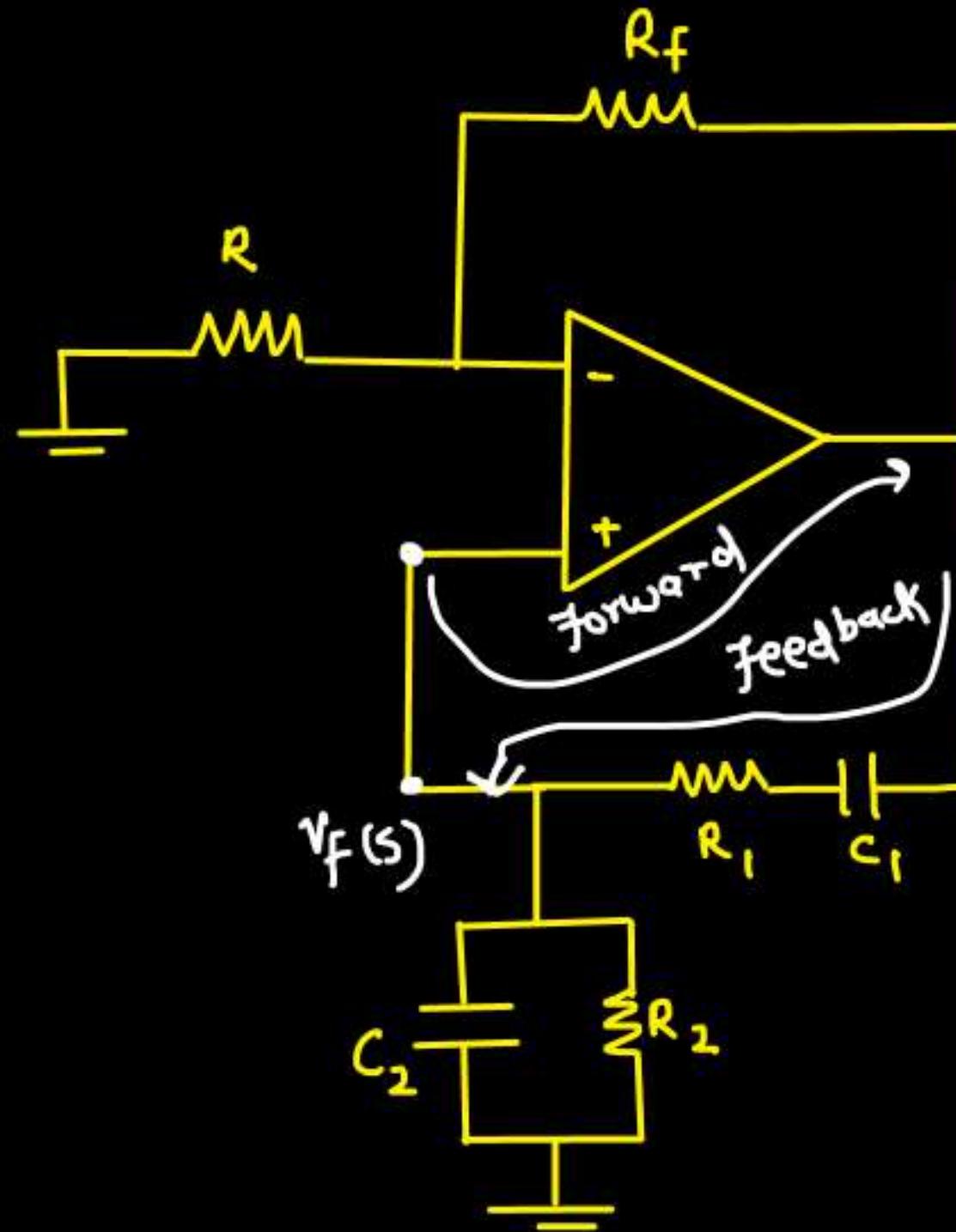


Fig. 2.95

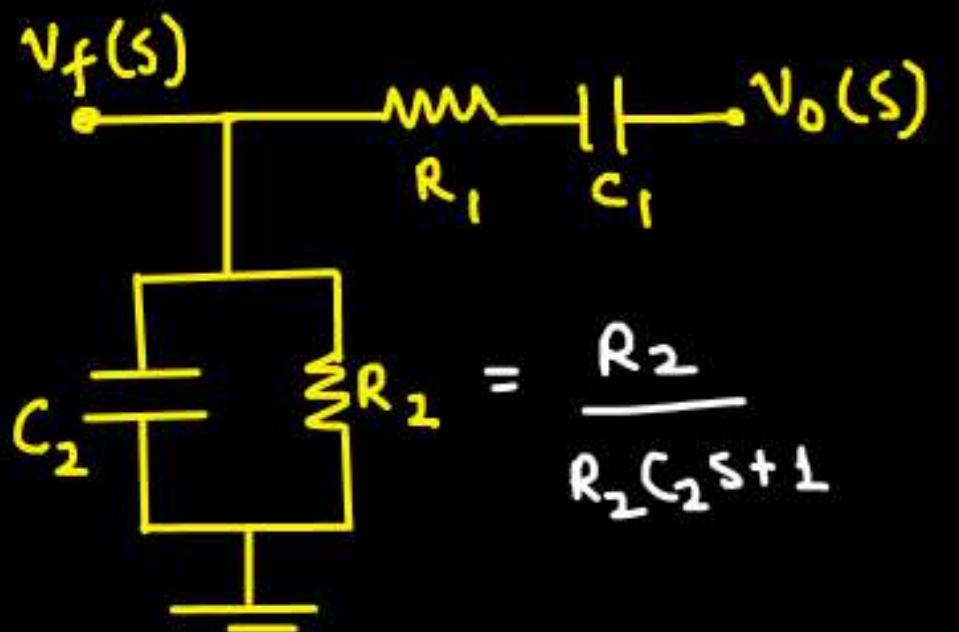[Pic from [eeeguide.com](http://eeeguide.com)]



$$Z_{R_2} = \frac{R_2}{R_2 C_2 s + 1}$$

$$A = 1 + \frac{R_f}{R}$$

$$\angle A = 0^\circ$$

$$V_f(s) = \frac{\frac{R_2}{R_2 C_2 s + 1}}{\frac{R_2}{R_2 C_2 s + 1} + \frac{R_1 C_1 s + 1}{C_1 s}} = \frac{R_2 C_1 s}{R_2 C_1 s + R_1 R_2 C_1 C_2 s^2 + R_2 C_2 s + R_1 C_1 s + 1} V_o(s)$$

$$\beta = \frac{j\omega R_2 C_1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega [R_2 C_1 + R_2 C_2 + R_1 q]}$$

$$\angle \beta = 0^\circ \rightarrow \text{required}$$



$\beta$  has to be real

$$1 - \omega^2 R_1 R_2 C_1 C_2 = 0$$

$$\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

→ Freq. of oscillations

$$\beta \left[ @ \omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \right] = \frac{R_2 C_1}{R_2 C_1 + R_2 C_2 + R_1 C_1}$$


\* 

$$\beta = \frac{1}{1 + \frac{C_2}{C_1} + \frac{R_1}{R_2}}$$

↳  $\angle \beta = 0^\circ$

PreFusion

$$|\alpha \beta| = 1 \quad \Rightarrow \quad \alpha = \frac{1}{\beta} \quad \Rightarrow \quad 1 + \frac{R_f}{R} = 1 + \frac{C_2}{C_1} + \frac{R_1}{R_2}$$

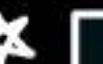\* 

$$\frac{R_f}{R} = \frac{C_2}{C_1} + \frac{R_1}{R_2}$$

if  $R_1 = R_2 = R$


$C_1 = C_2 = C$


$$\omega = \frac{L}{\sqrt{R^2C^2}} = \frac{1}{RC}$$

$$\frac{R_f}{R} = 2$$



## \* RC Phase Shift Oscillators:-

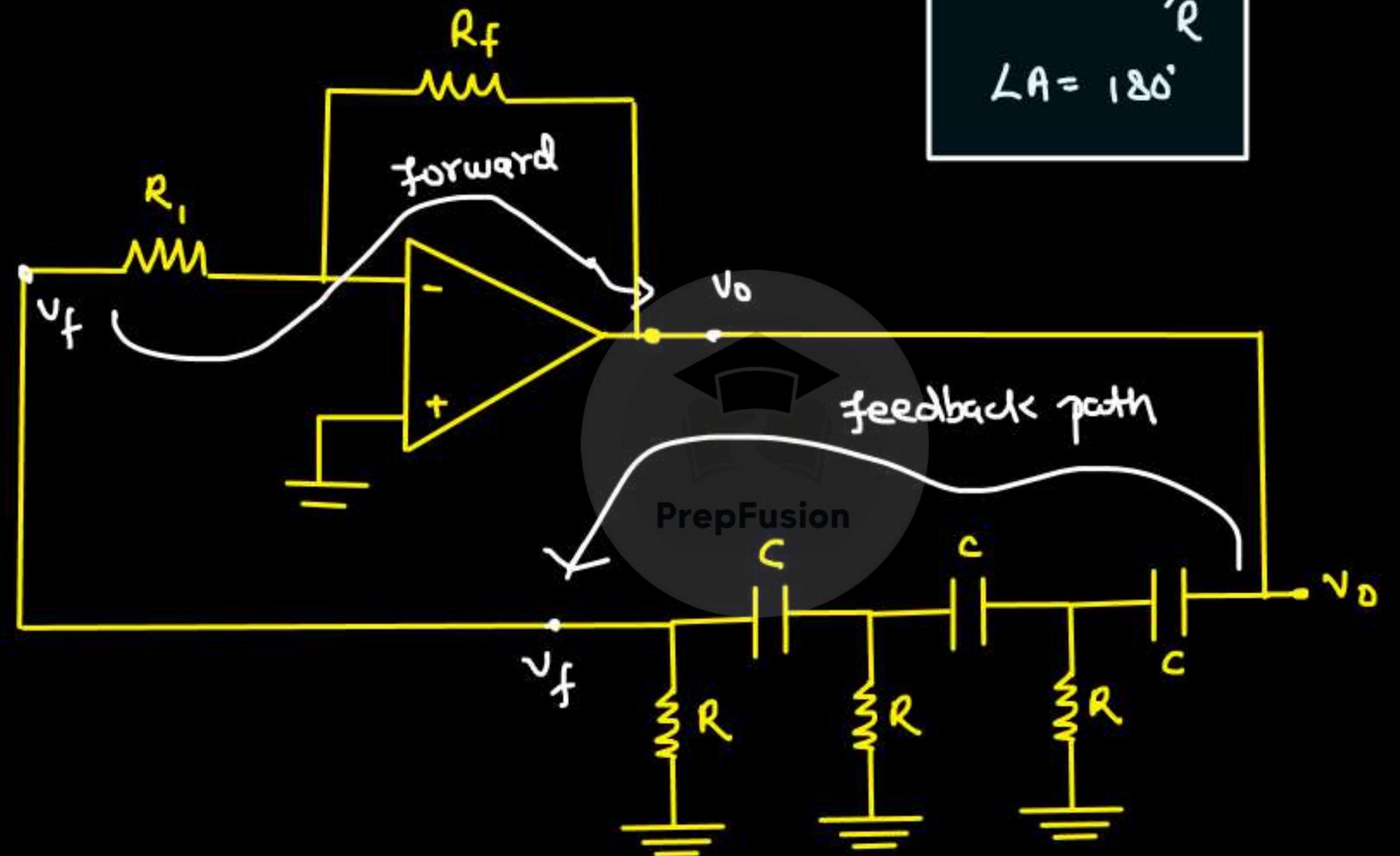

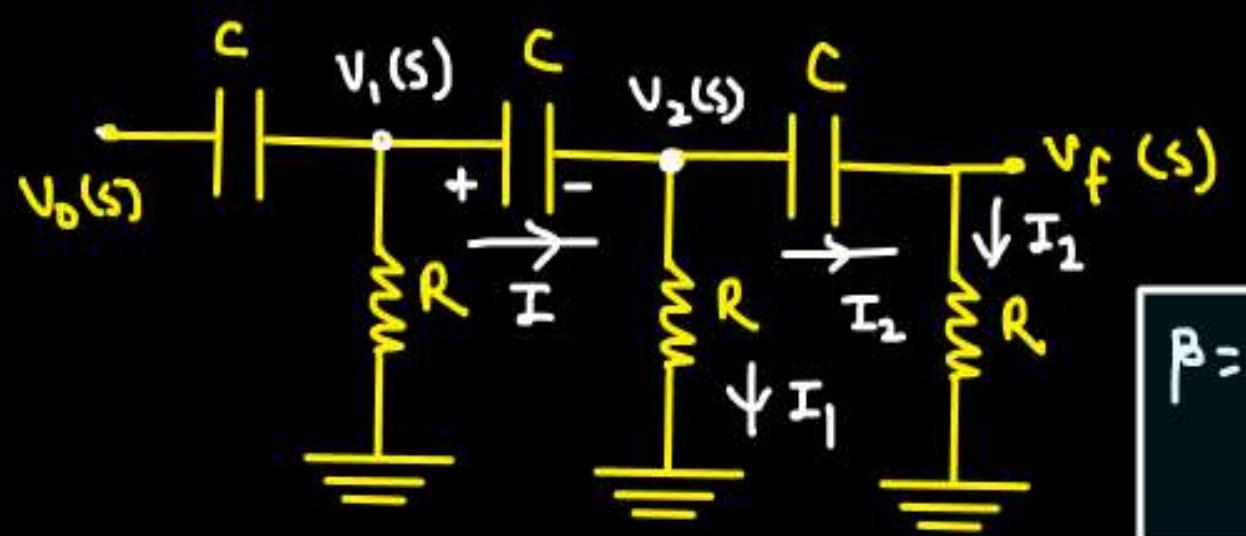

$$\beta = \frac{v_f(s)}{v_o(s)}$$

$$v_f(s) = \frac{R\omega s}{R\omega s + 1} v_2(s)$$

$$v_2(s) = \frac{R\omega s + 1}{R\omega s} v_f(s) \quad \text{--- (1)}$$

\*\*  $I = I_1 + I_2$

$$I = \frac{v_2(s)}{R} + \frac{v_f(s)}{R}$$

By eqn ①

$$I = \frac{v_f(s)}{R} \left[ \frac{1 + R\omega s}{R\omega s} \right] + \frac{v_f(s)}{R}$$

$$I = \frac{v_f(s)}{R} \left[ \frac{1 + 2R\omega s}{R\omega s} \right] \quad \text{--- (2)}$$

$$v_1(s) = I \times \frac{1}{s} + v_2(s)$$

$$= \frac{v_f(s)}{R\omega s} \left[ \frac{1 + 2R\omega s}{R\omega s} \right] + \frac{v_f(s)}{R\omega s} [R\omega s + 1]$$

{ By eqn ① & ② }

$$V_1(s) = \frac{V_f(s)}{R\omega} \left[ \frac{1 + 2R\omega + (R\omega)^2 + R\omega}{R\omega} \right] - ③$$

$$[V_o(s) - V_1(s)] CS = \frac{V_1(s)}{R} + I$$

$$V_o(s) = V_1(s) \left[ \frac{R\omega + 1}{R\omega} \right] + \frac{I}{CS}$$

By eqn ② and ③

$$V_o(s) = \frac{V_f(s)}{(R\omega)^3} [1 + 3R\omega + (R\omega)^2] [R\omega + 1] + \frac{V_f(s)}{(R\omega)^2} [1 + 2R\omega]$$

\*  $V_o(s) = \frac{V_f(s)}{(R\omega)^3} [(R\omega)^3 + 6(R\omega)^2 + 5R\omega + 1]$

$$\beta = \frac{V_f(s)}{V_o(s)} = \frac{(RC)^3}{(RC)^3 + 6(RC)^2 + 5RC + 1}$$

$$\beta = \frac{-j\omega^3 R^3 C^3}{-j\omega^3 R^3 C^3 - 6\omega^2 R^2 C^2 + 5j\omega RC + 1}$$

$\angle \beta = 180^\circ \rightarrow$  required

For  $\beta$  real

$$1 - 6\omega^2 R^2 C^2 = 0$$



PrepFusion

$\Downarrow$   
 $\beta = \text{real}$

$$\omega = \frac{1}{RC\sqrt{6}}$$

~ Frequency of oscillation

$$\beta \left[ @ \omega = \frac{1}{RC\sqrt{6}} \right] = \frac{-\frac{1}{\sqrt{6}} \times \frac{1}{R^3 C^3} \times R^3 C^3}{-\frac{1}{\sqrt{6}} \times \frac{1}{R^3 C^3} \times R^3 C^3 + 5 \frac{1}{\sqrt{6} RC} \times RC} = \frac{-\frac{1}{\sqrt{6}}}{-\frac{1}{\sqrt{6}} + \frac{5}{\sqrt{6}}} = \frac{-1}{-1 + 5} = -\frac{1}{4}$$

$$\beta = -\frac{1}{2g} \rightarrow \angle \beta = 180^\circ$$

$$\angle A = 180^\circ$$

$$\Rightarrow \angle A\beta = 0^\circ$$

$$(\alpha\beta) = 1$$

$$\Rightarrow |A| = \frac{1}{|\beta|} = 2g$$




$$|A| = \frac{R_f}{R} = 2g$$

$$R_f = 2gR$$

$$\omega = \frac{1}{\sqrt{\epsilon} \times RC} \Rightarrow \text{Freq. of oscillation}$$

$$= \frac{1}{\sqrt{2N} \times RC} \quad N \Rightarrow \text{no. of CR ckt}$$


## \* LC Oscillators :-

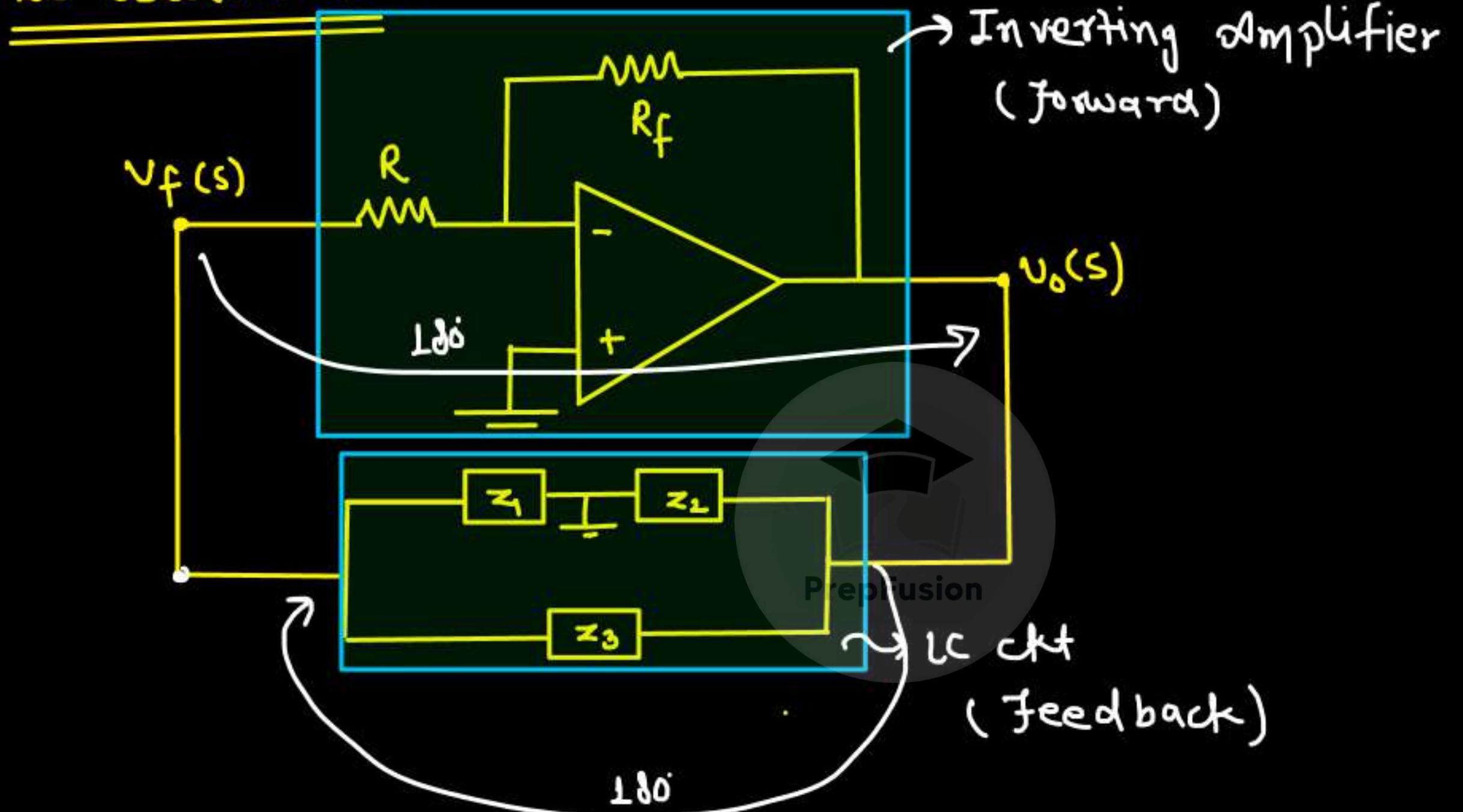

(a) Forward gain ( $A$ ) :-


$$A = -\frac{R_f}{R}$$

$$|A| = \frac{R_f}{R}$$

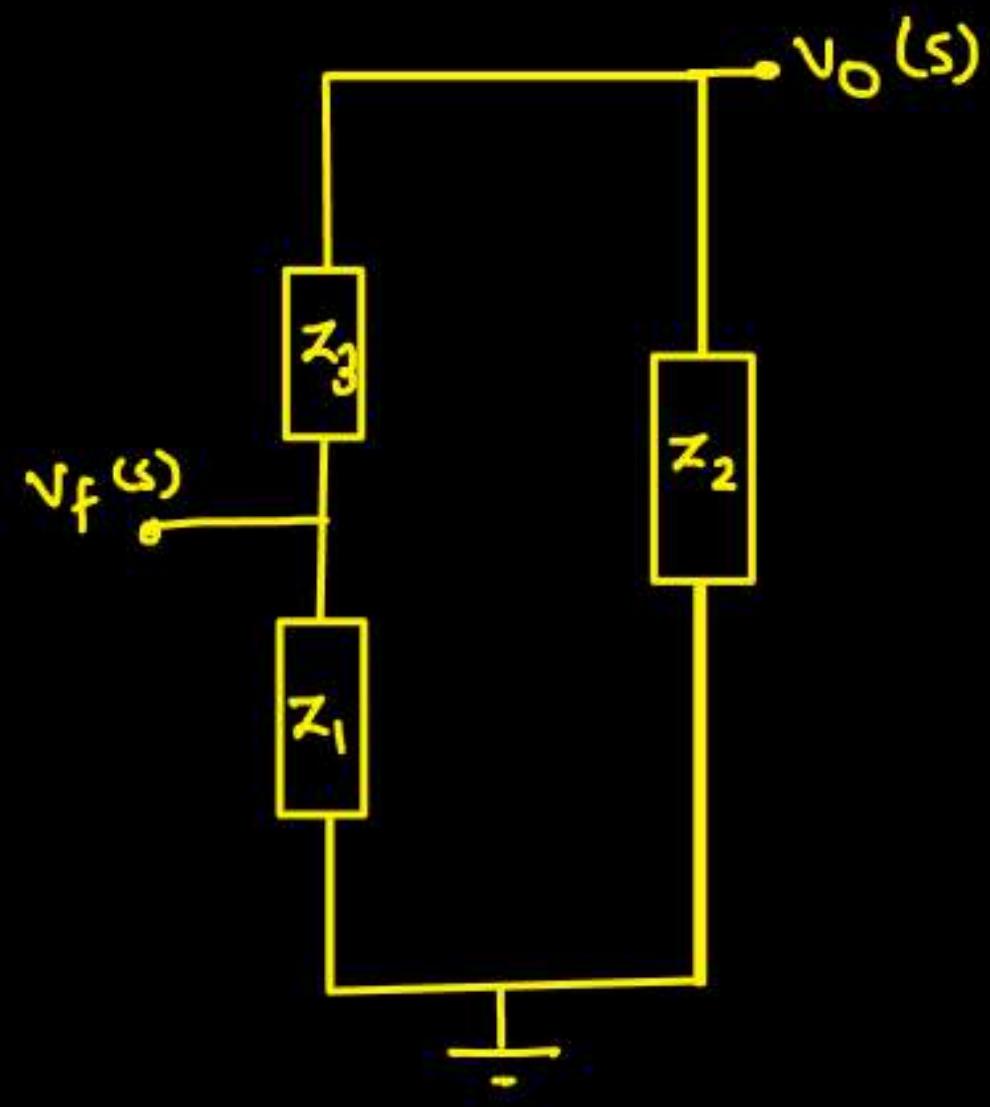

$$v_f(s) \approx \frac{z_1}{z_1 + z_3} v_o(s)$$
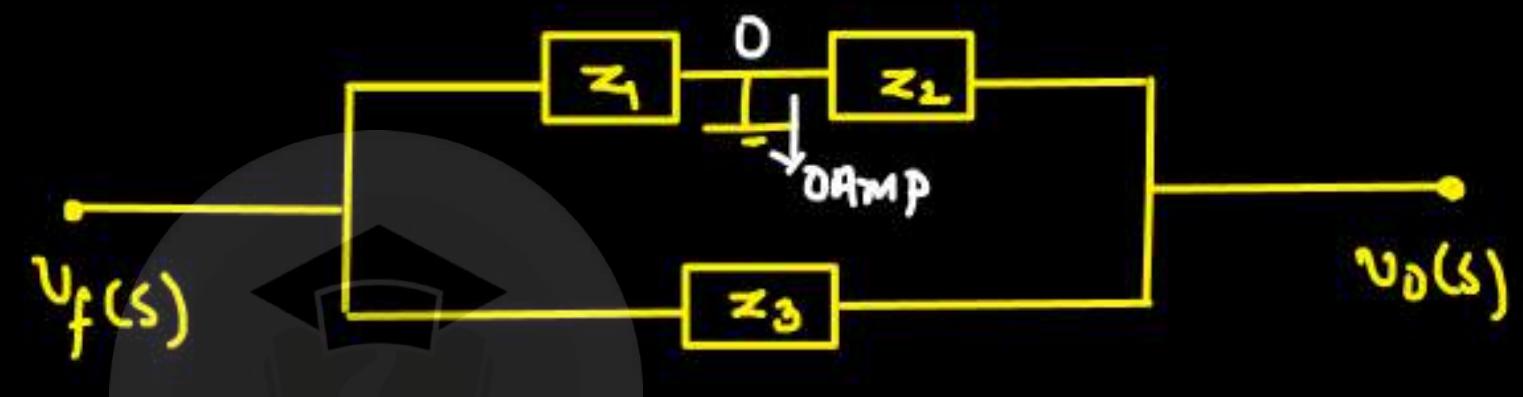
$$\beta(s) \approx \frac{z_1}{z_1 + z_3}$$



PrepFusion


$$-\frac{v_f(s)}{z_1(s)} - \frac{v_o(s)}{z_2(s)} = 0$$

$$\frac{v_f(s)}{v_o(s)} = -\frac{z_1(s)}{z_2(s)}$$

Remember This one

$$|\beta| = \frac{z_1(s)}{z_2(s)}$$

For finding Freq. of oscillations:-

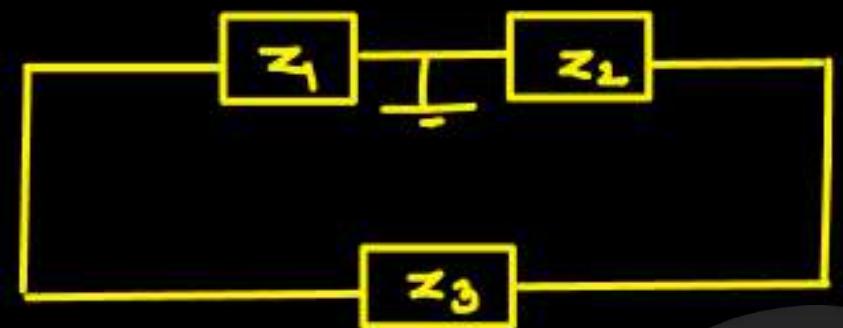

$$z_1 + z_2 + z_3 = 0$$




1.  $z_1, z_2 \rightarrow$  cap.,  $z_3 \rightarrow$  inductor  $\Rightarrow$  Colpitt's oscillator
2.  $z_1, z_2 \rightarrow$  Ind.,  $z_3 \rightarrow$  cap.  $\Rightarrow$  Hartley oscillator

## Colpitt's Oscillator :-

$Z_1, Z_2 \rightarrow$  Capacitor

$Z_3 \rightarrow$  Inductor

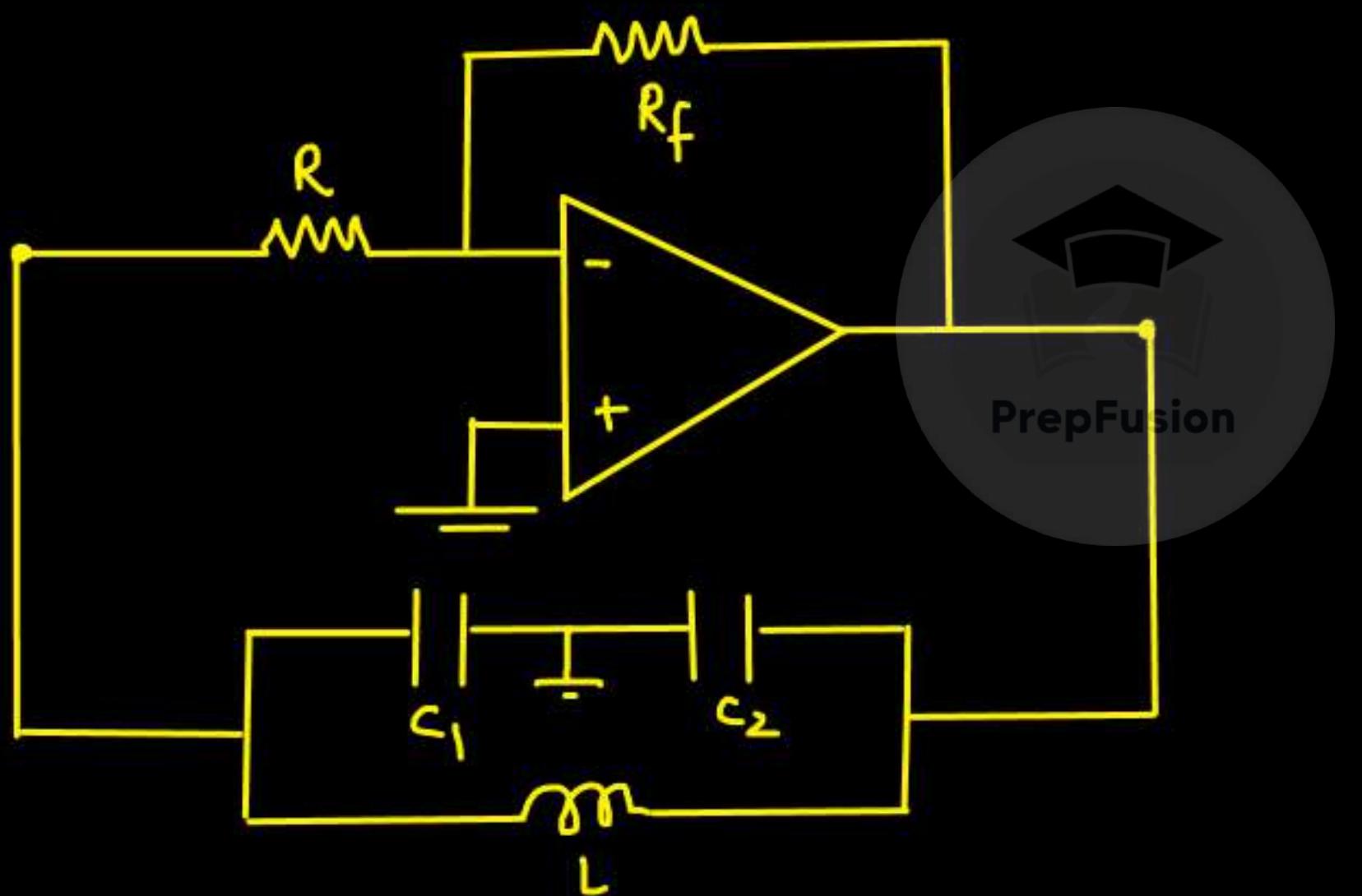

LC Circuits

(a) Forward gain (A) :-

$$A = -\frac{R_f}{R}, \quad |A| = \frac{R_f}{R}, \quad \angle A = 180^\circ$$

(b) Frequency of Oscillations :-

$$\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L = 0$$

PrepFusion


$$j \left[ \frac{-1}{\omega C_1} - \frac{1}{\omega C_2} + \omega L \right] = 0$$

$$\omega_L = \frac{1}{\omega} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$\omega_z = \frac{1}{\sqrt{L(\frac{1}{C_1} + \frac{1}{C_2})}}$$

$$\omega = \frac{1}{\sqrt{L C_1 C_2}} \frac{1}{C_1 + C_2}$$

## (c) Feedback factor ( $\beta$ ):-

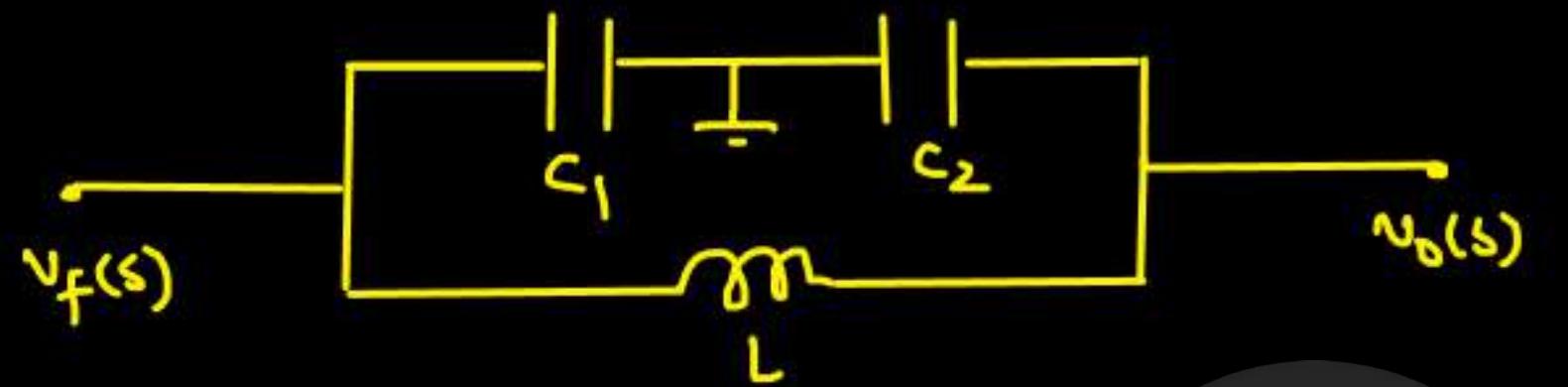

$$-v_f(s) \times C_1 s - v_o(s) C_2 s = 0$$

$$\frac{v_f(s)}{v_o(s)} = - \frac{C_2}{C_1}$$

PrepFusion


$$|\beta| = \frac{C_2}{C_1}$$

For sustained oscillations;  $|a\beta| > 1$

★ ★

$$\frac{R_f}{R} \times \frac{C_2}{C_1} > 1$$

## Hartley Oscillator :-

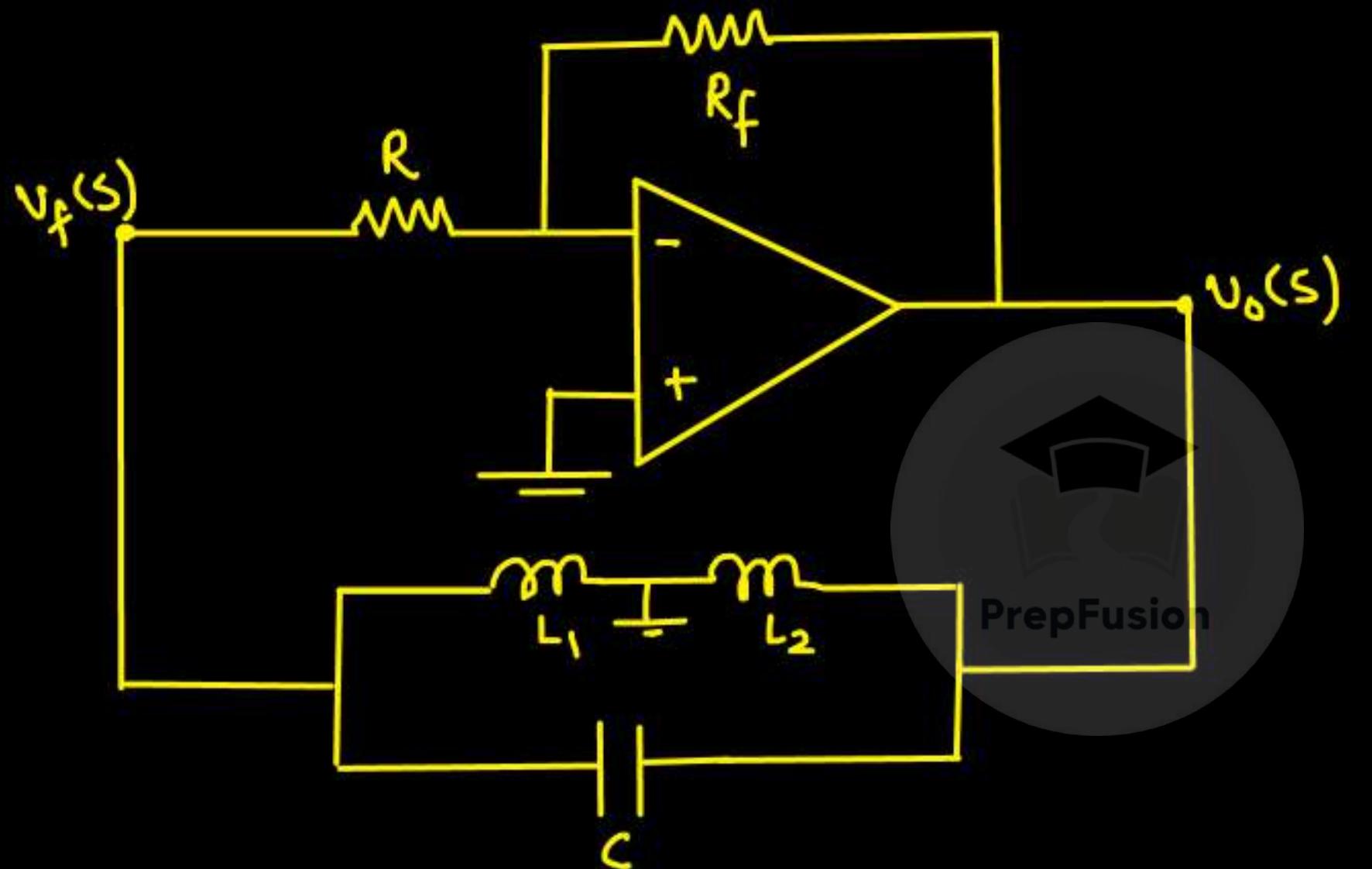

PrepFusion

(a) Forward gain ( $A$ ):-

$$A = -\frac{R_f}{R}, \quad |A| = \frac{R_f}{R}, \quad \angle A = 180^\circ$$

(b) Frequency of Oscillation ( $\omega$ ):-


$$j\omega L_1 + j\omega L_2 + \frac{1}{j\omega C} = 0$$

$$\omega L_1 + \omega L_2 - \frac{1}{\omega C} = 0$$

$$\omega (L_1 + L_2) = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{(L_1 + L_2)C}}$$

Feedback Factor:-

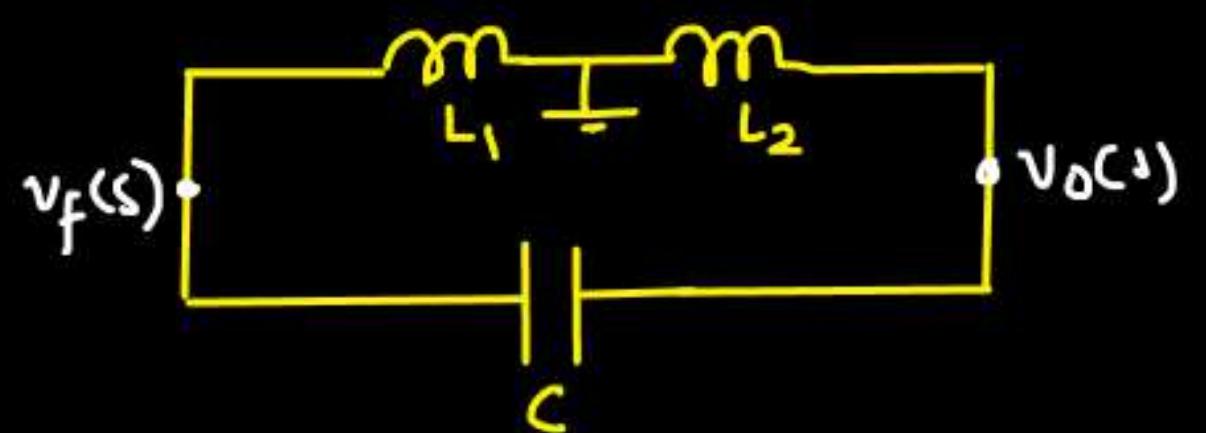

$$-\frac{V_f(s)}{L_1 s} - \frac{V_o(s)}{L_2 s} = 0$$

$$\frac{V_f(s)}{V_o(s)} = \beta(s) \approx -\frac{L_1}{L_2}$$


$$|\beta| = \frac{L_1}{L_2}$$

For sustained oscillations:-


$$|\alpha\beta| = 1$$

$$\frac{R_f}{R} \times \frac{L_1}{L_2} = 1$$

Q.

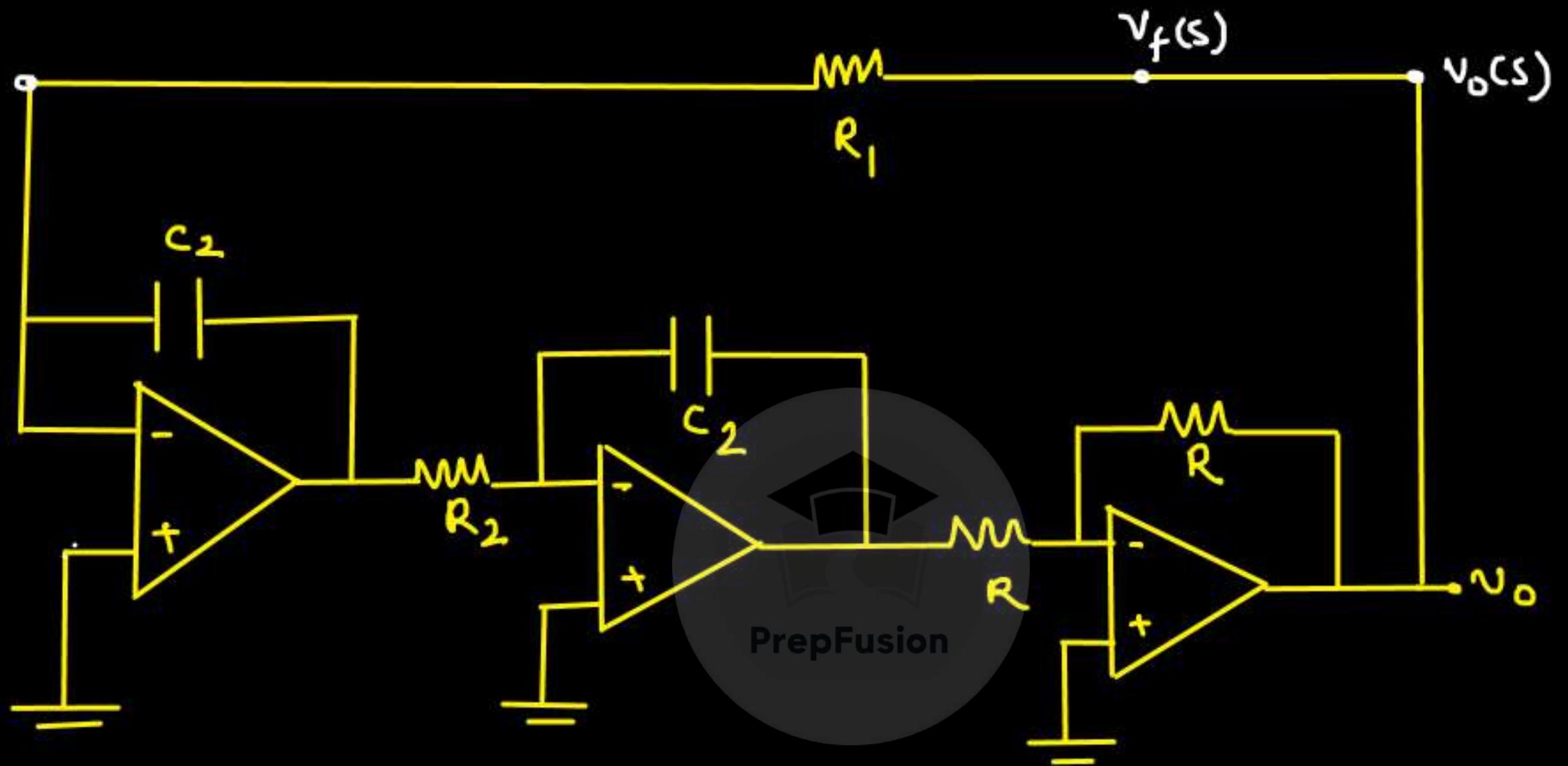

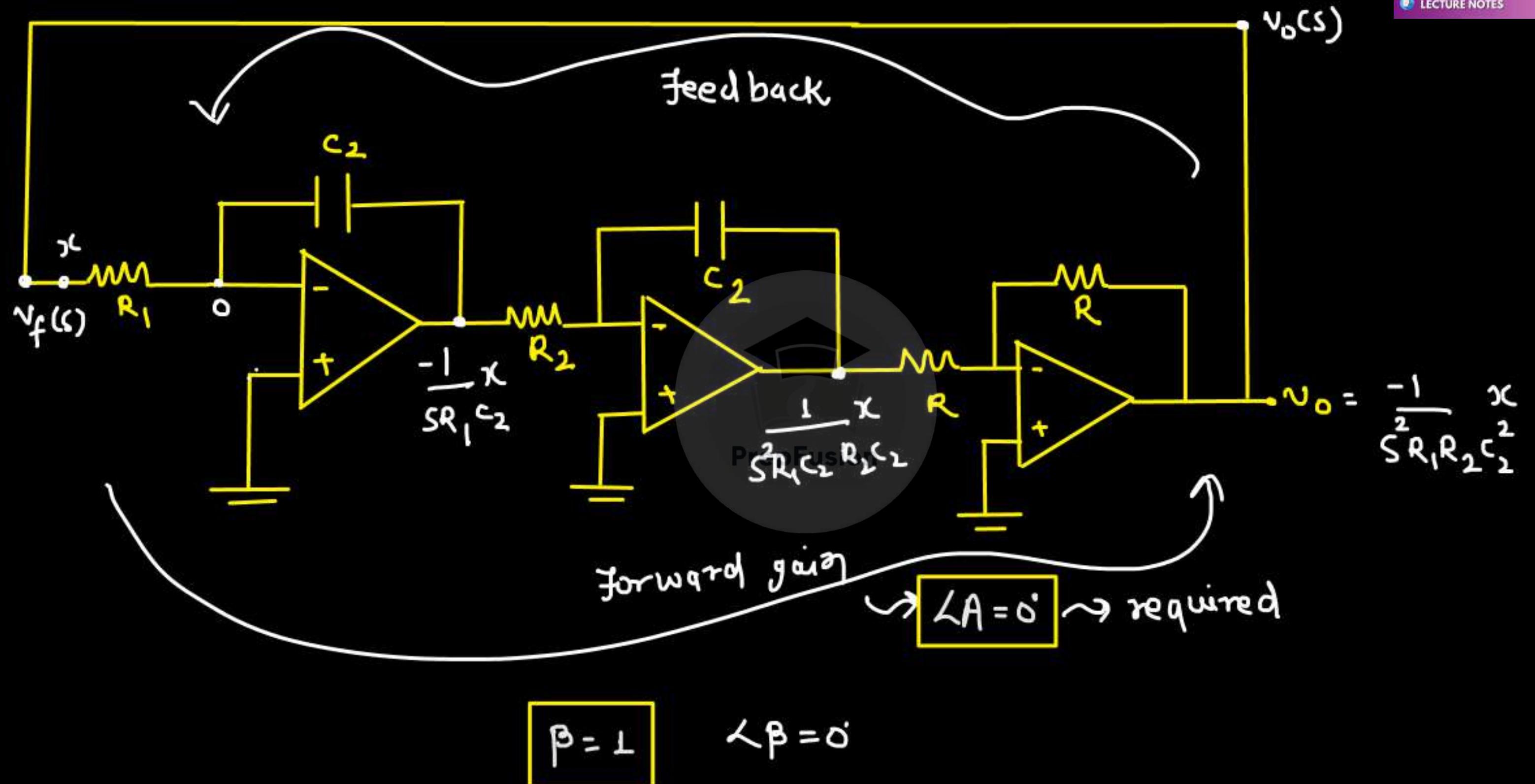Find the frequency of Sustained oscillations.



Forward gain  $A = \frac{-1}{s^2 R_1 R_2 C_2^2} = \frac{-L}{-\omega^2 R_1 R_2 C_2^2}$

$$= \frac{L}{\omega^2 R_1 R_2 C_2^2} \quad \angle A = 0^\circ$$

For sustained oscillation :-


$$|A\beta| = 1$$

$$\frac{1}{\omega^2 R_1 R_2 C_2^2} = 1$$

$$\omega = \frac{1}{C_2 \sqrt{R_1 R_2}} \rightarrow \text{frequency of oscillations}$$




Q.

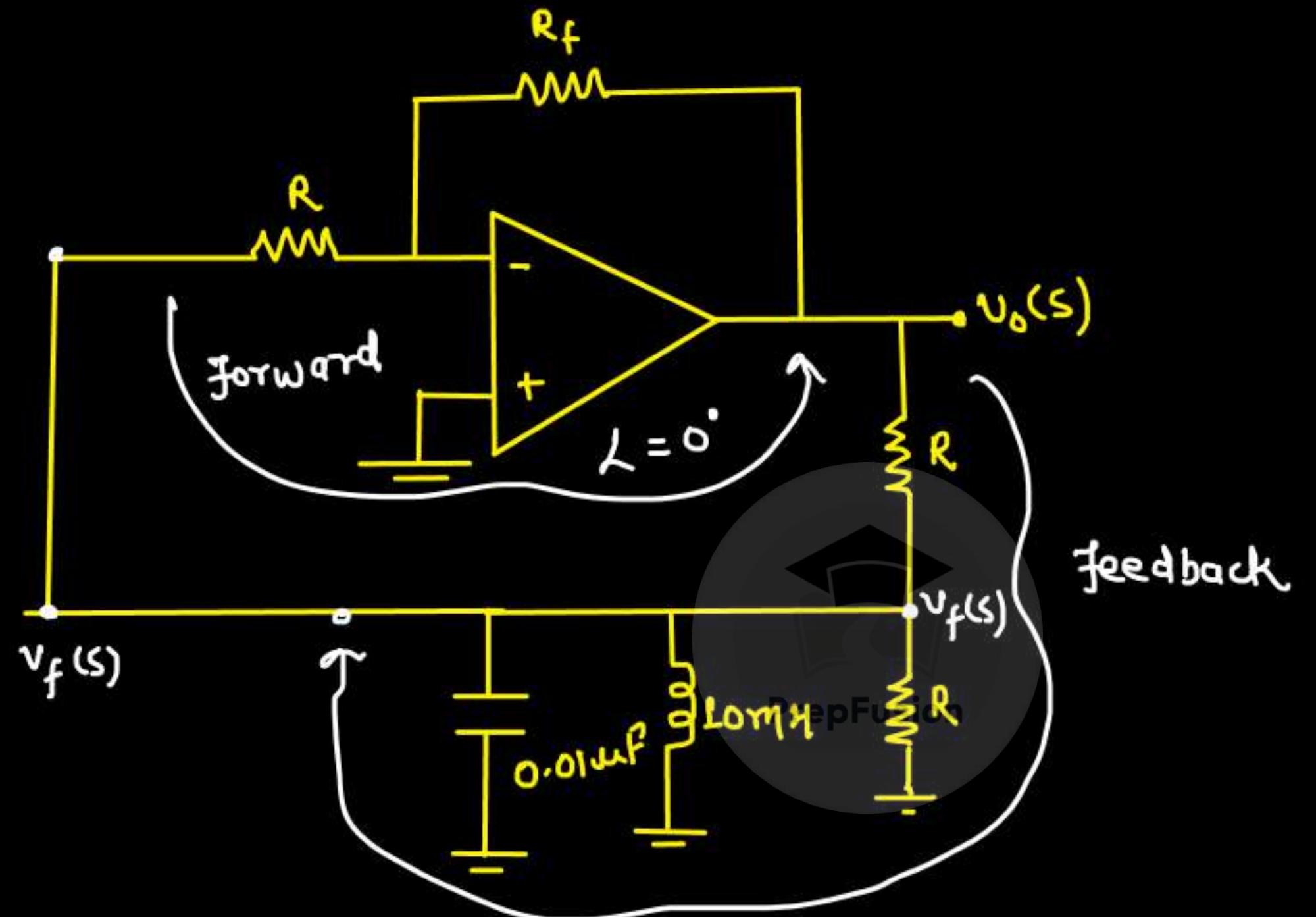

- (a) Find the frequency of sustained oscillations?
- (b) The ratio of  $R_f/R$  for sustained oscillations?



required  $\angle \beta = 0^\circ$

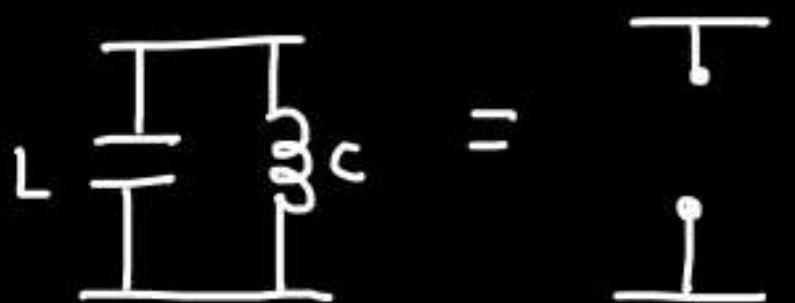


$$Ls \parallel \frac{1}{Cs} = \infty$$

$$\Rightarrow Ls + \frac{1}{Cs} = 0$$

$$j\omega L - \frac{j}{\omega C} = 0$$


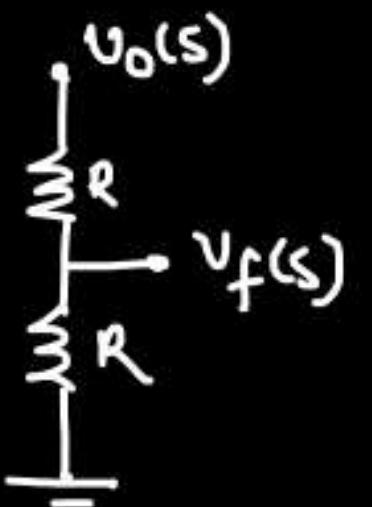
$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4} \times 10^{-2}}} = 10^5 \text{ rad/sec.}$$



$$V_f(s) = \frac{1}{2} V_o(s)$$

$$\beta = \frac{1}{2}$$

$$\angle \beta = 0^\circ$$

$$\hookrightarrow |A\beta| = 1$$


$$\left(1 + \frac{R_f}{R}\right) \left(\frac{1}{2}\right) = 1$$

$$\frac{R_f}{R} = 1$$



Q. The forward gain A can be written as


$$A = |A| \angle 90^\circ$$

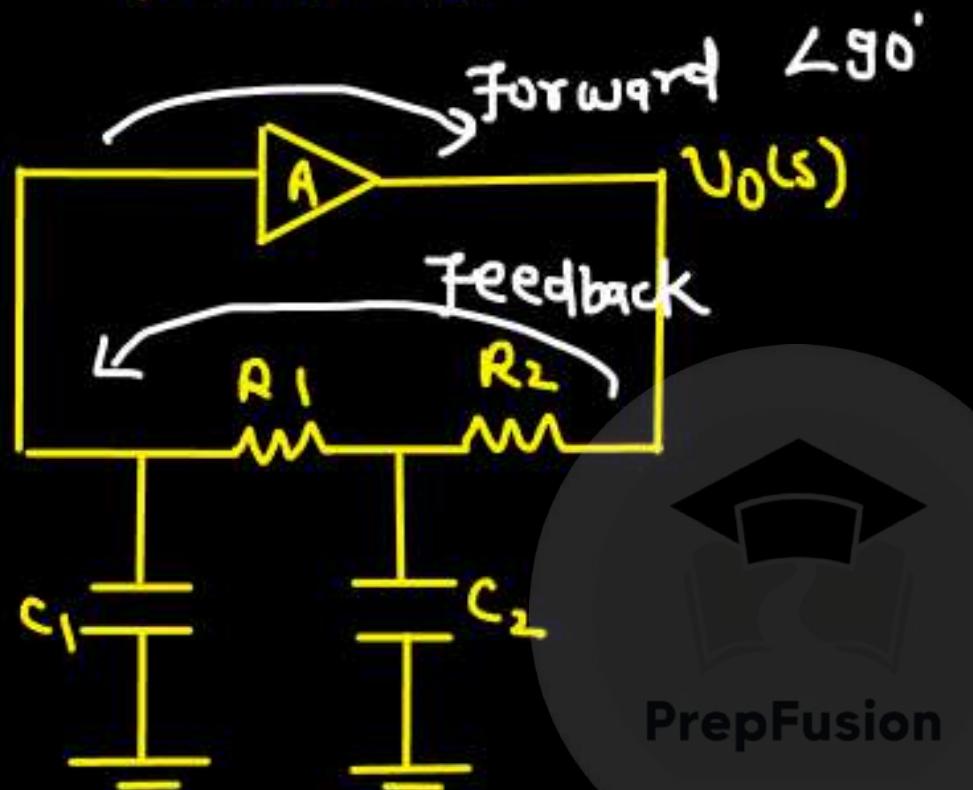

For sustained oscillations, find the magnitude of  $A$  and the freq. at which the circuit oscillates.


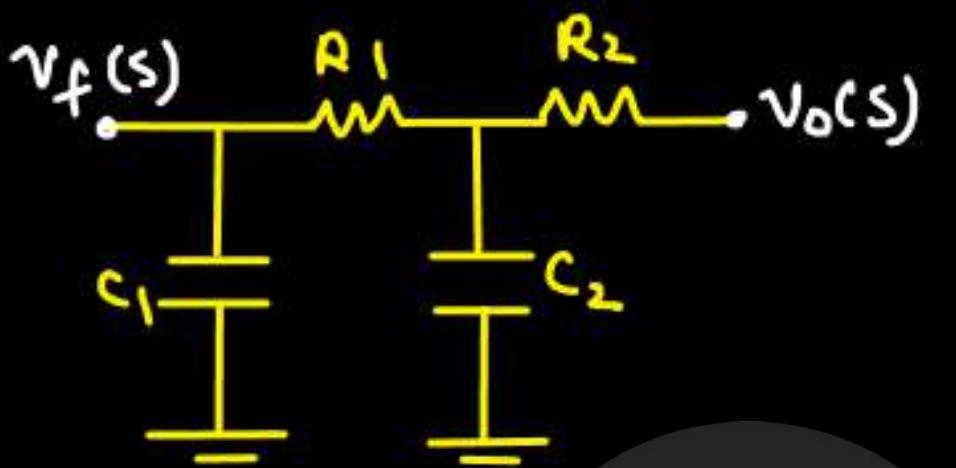
$$\angle \beta = -90^\circ \rightarrow \text{required}$$



$$\frac{v_f(s)}{v_o(s)} = \frac{L}{s^2 C^2 R^2 + 3 R C s + L}$$



$$\beta = \frac{L}{-\omega^2 R^2 C^2 + 3j\omega R C + L}$$

$$\text{For } \angle \beta = -90^\circ, \quad 1 - \omega^2 R^2 C^2 = 0$$

$$\omega = \frac{1}{RC} \rightarrow \text{Freq. of oscillations}$$

$$\beta \left( \text{at } \omega_c \frac{1}{RC} \right) = \frac{L}{3j \times \frac{1}{RC} \times RC} = -\frac{j}{3}$$

$$\angle \beta = -90^\circ$$

$$|\beta| = \frac{1}{\sqrt{3}}$$

$$\hookrightarrow |\omega \beta| < 1$$

$$|A| = 3$$

Ans.




## ↓ Bipolar Junction Transistors

Two charge carrier (BJTs)  
[ $e^-$ , holes]


BJT [NPN, PNP]


NPN

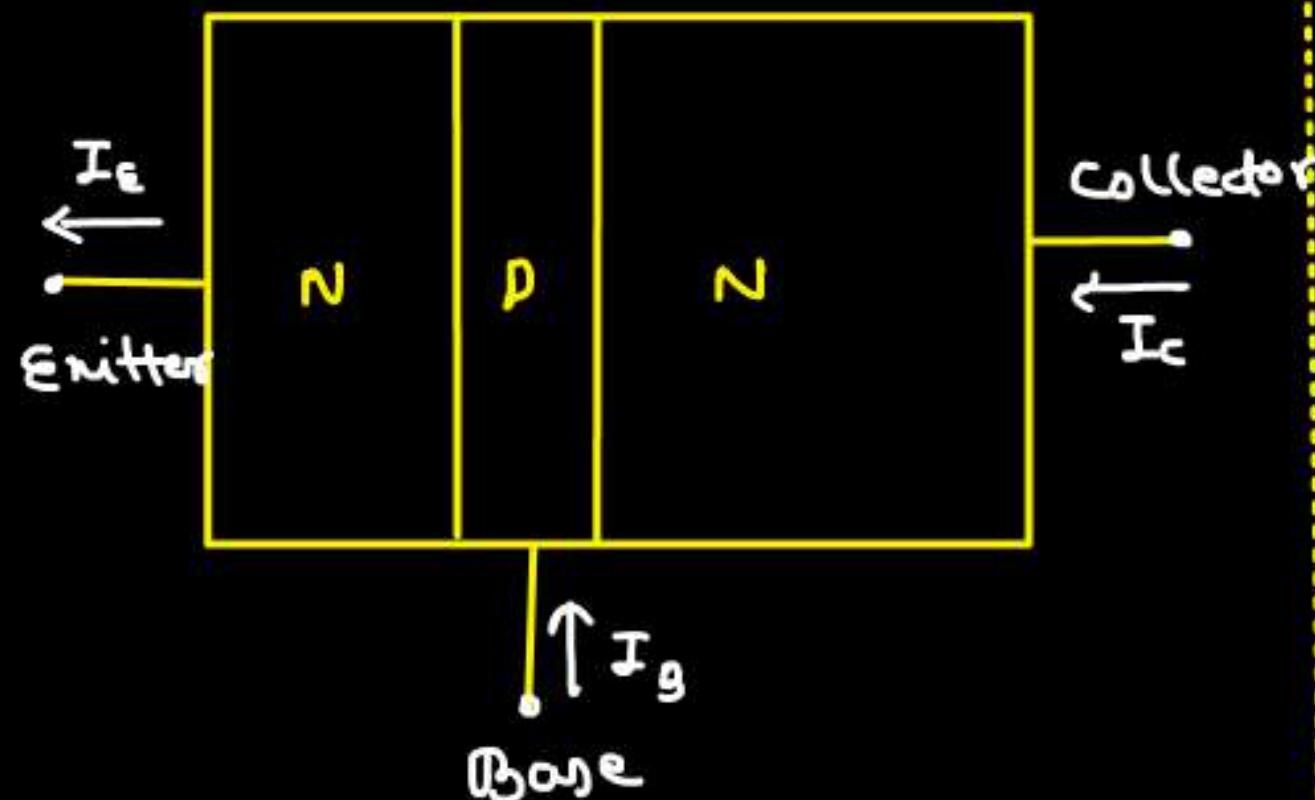

$$A_C > A_E > A_B$$

MOS [NMOS, PMOS]

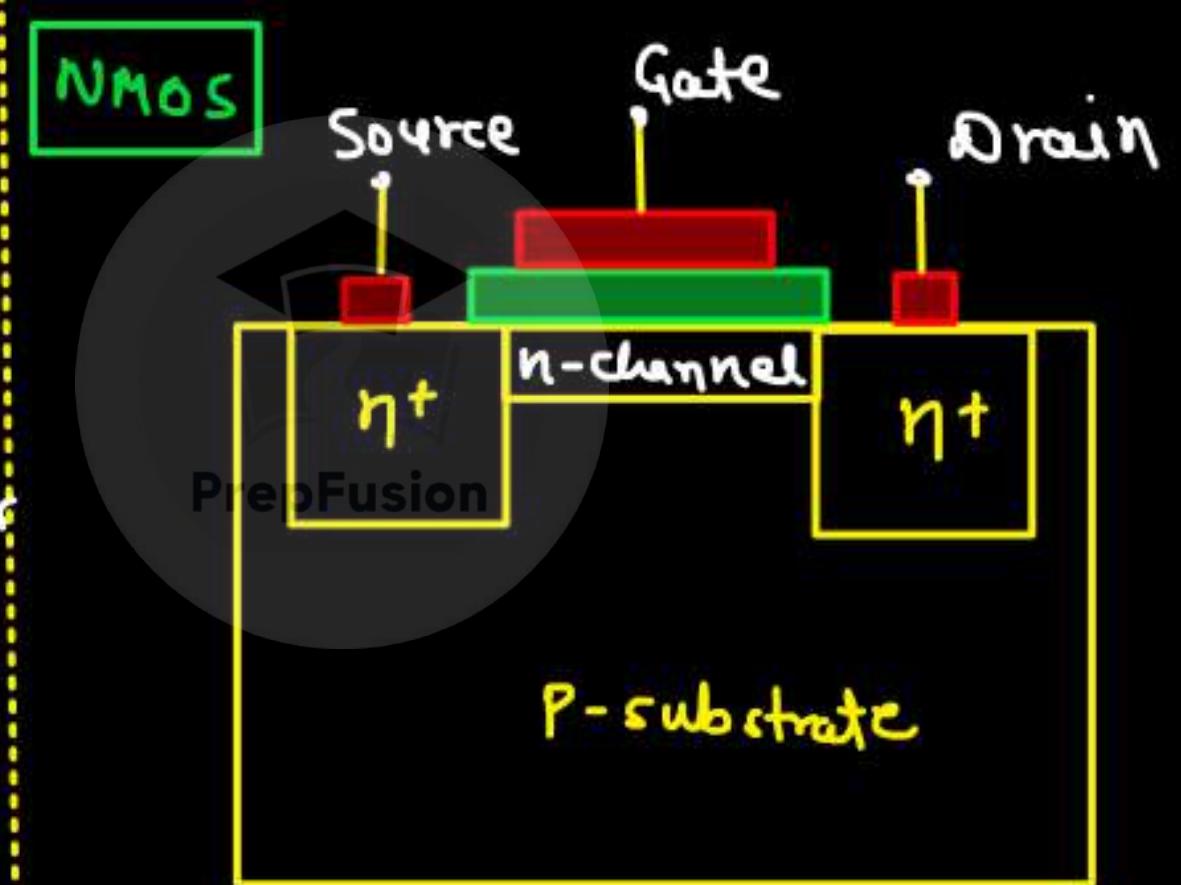

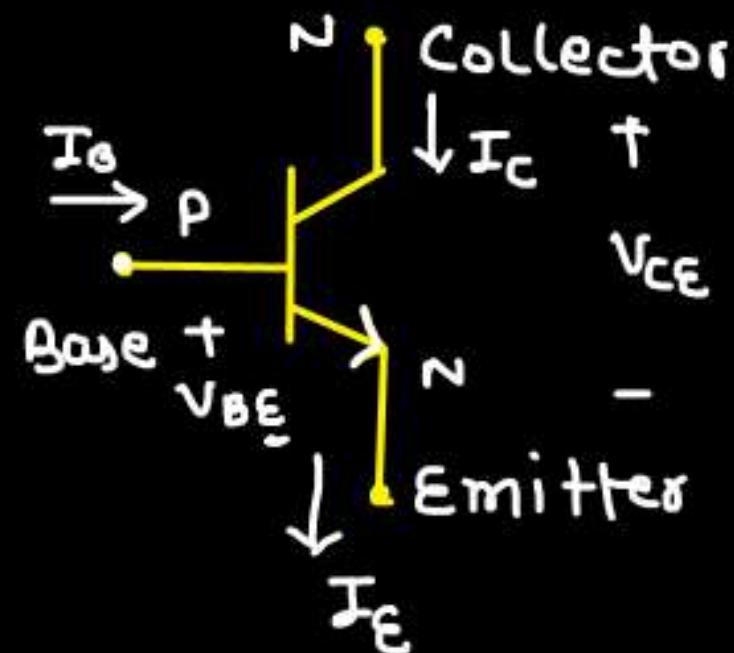

$$I_C \approx I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \quad (V_{CE} > V_{CE})_{sat}$$

$I_S = \text{Reverse sat-current}$


$$I_E = I_C + I_B$$

$V_T \rightarrow \text{Thermal voltage}$

$$V_T \propto T$$

$V_A \rightarrow \text{Early voltage}$        $V_T = 25 \text{ mV} @ 300 \text{ K}$
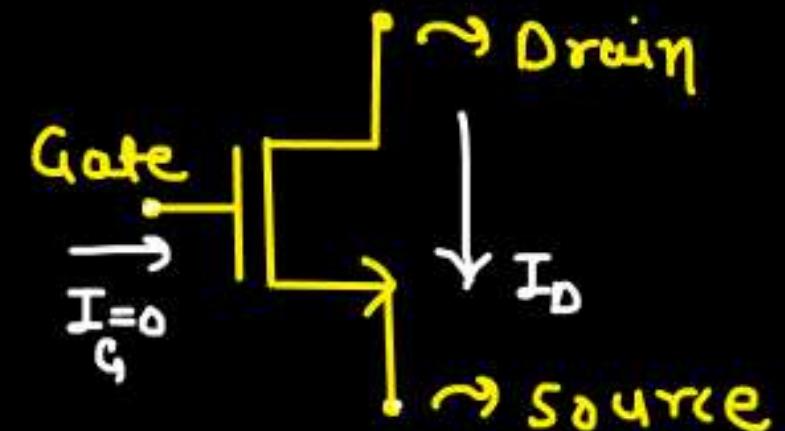
$$I_C = I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$



$$I_D = \frac{\mu n C_{ox} W}{2L} \left[ (V_{GS} - V_T)^2 \right]$$

PrepFusion

$$V_{DS} > V_{GS} - V_T$$

$$I_D = \frac{\mu n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



$$I_E = I_C + I_B \quad - \textcircled{1}$$

\*  $I_C = \beta I_B \quad - \textcircled{2}$   $\beta \rightarrow$  Common Emitter current gain

$$I_B = \frac{I_C}{\beta}$$

\* if  $\beta = \infty$

$$I_B = 0 \text{ Amp}$$

By eqn ① and ②

$$I_E = \beta I_B + I_B$$

\*  $I_E = (\beta + 1) I_B \quad - \textcircled{3}$




$$I_C = \alpha I_E \quad \text{--- (4)}$$

$\alpha$  = common base current gain

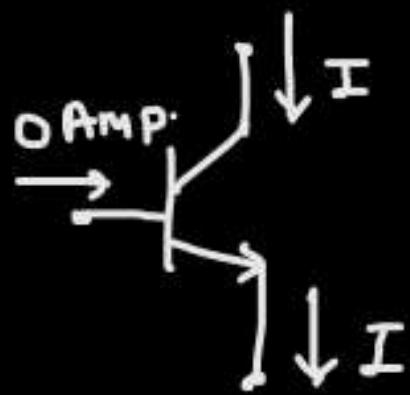(3)  $\div$  (2)

$$\frac{I_E}{I_C} = \frac{(\beta + 1) I_B}{\beta I_B}$$

$$I_E = \left( \frac{\beta + 1}{\beta} \right) I_C$$



for  $\beta = \infty$

$$I_C = I_E = I$$

From (4) and (5)

$$\alpha = \frac{\beta}{\beta + 1}$$


$$\left\{ \begin{array}{l} \alpha \approx 1 \text{ or } \alpha < 1 \\ \text{if } \beta = \infty \\ \alpha = 1 \end{array} \right.$$

$$I_E = I_C + I_B$$

$$I_C = \beta I_B$$

$$I_E \approx (\beta + 1) I_B$$


$$\alpha = \frac{\beta}{\beta + 1}$$

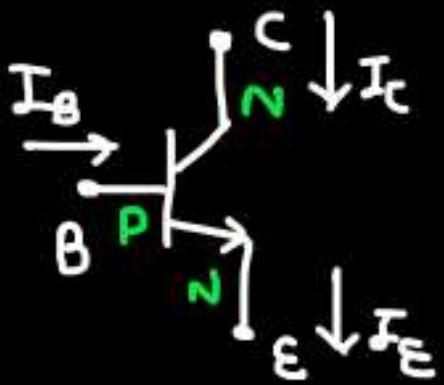

$$I_B \rightarrow B \quad I_C \downarrow C$$


$$I_E \downarrow E$$

$I_C \propto v/s \propto V_{BE}$

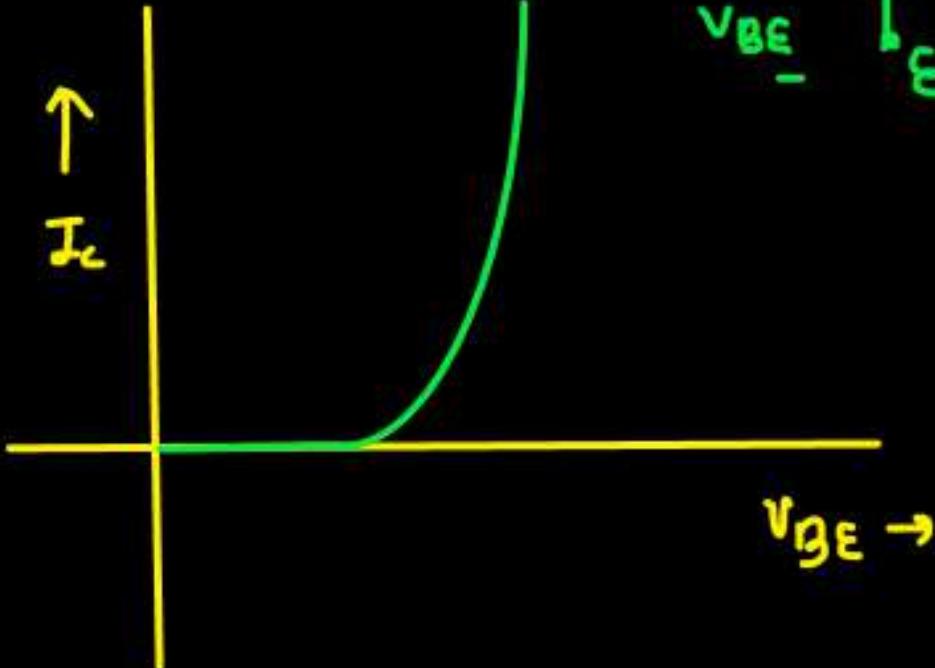

$$I_C = I_S \exp\left(\frac{V_{BE}}{nV_T}\right)$$

$I_D \propto v/s \propto V_{GS}$

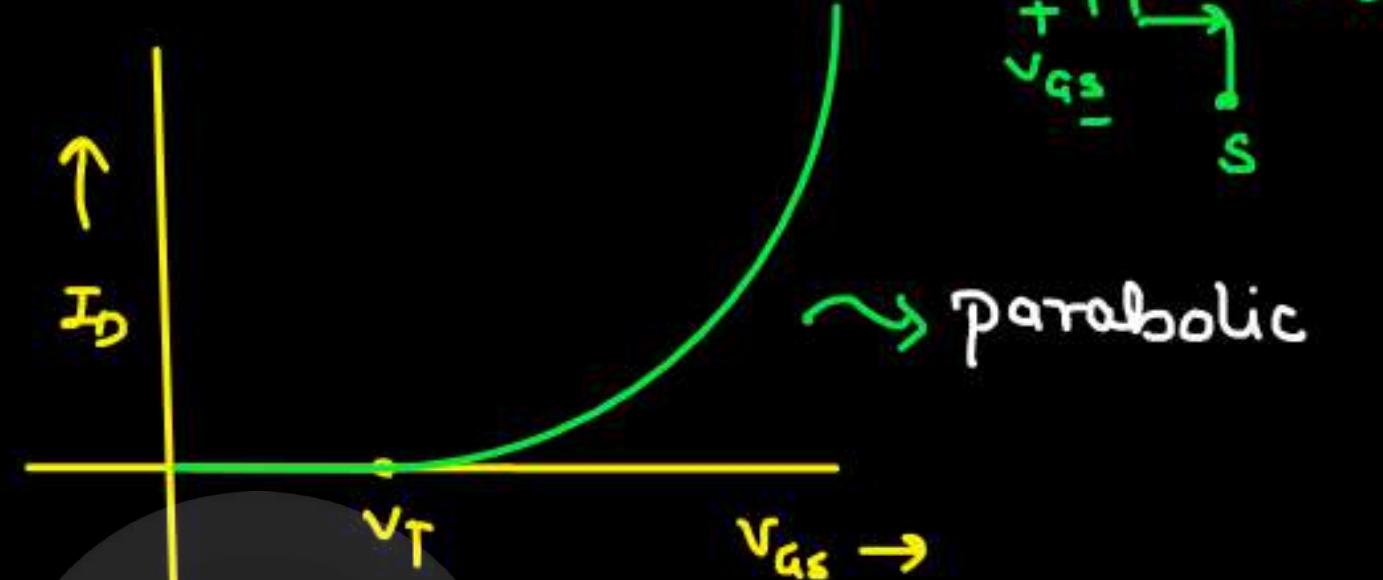

Q. For 10x increase in  $I_C$ , find change in  $V_{BE}$ . ( $V_T = 25\text{mV}$ ),  $n=1$

→

$$I_C = I_S \exp\left(\frac{V_{BE_1}}{V_T}\right) - \textcircled{1}$$

$$10I_C = I_S \exp\left(\frac{V_{BE_2}}{V_T}\right) - \textcircled{2}$$

② ÷ ①

$$I_D = \frac{\exp\left(\frac{V_{BE_2}}{V_T}\right)}{\exp\left(\frac{V_{BE_1}}{V_T}\right)}$$


$$I_D = \exp\left(\frac{V_{BE_2} - V_{BE_1}}{V_T}\right)$$

$$V_{BE_2} - V_{BE_1} = V_T \ln(I_D)$$

**ΔV<sub>BE</sub> = 57 mV**


↳ in the question, Typically **V<sub>BE</sub> = 0.7V**

$I_C$  v/s  $V_{CE}$  curve:

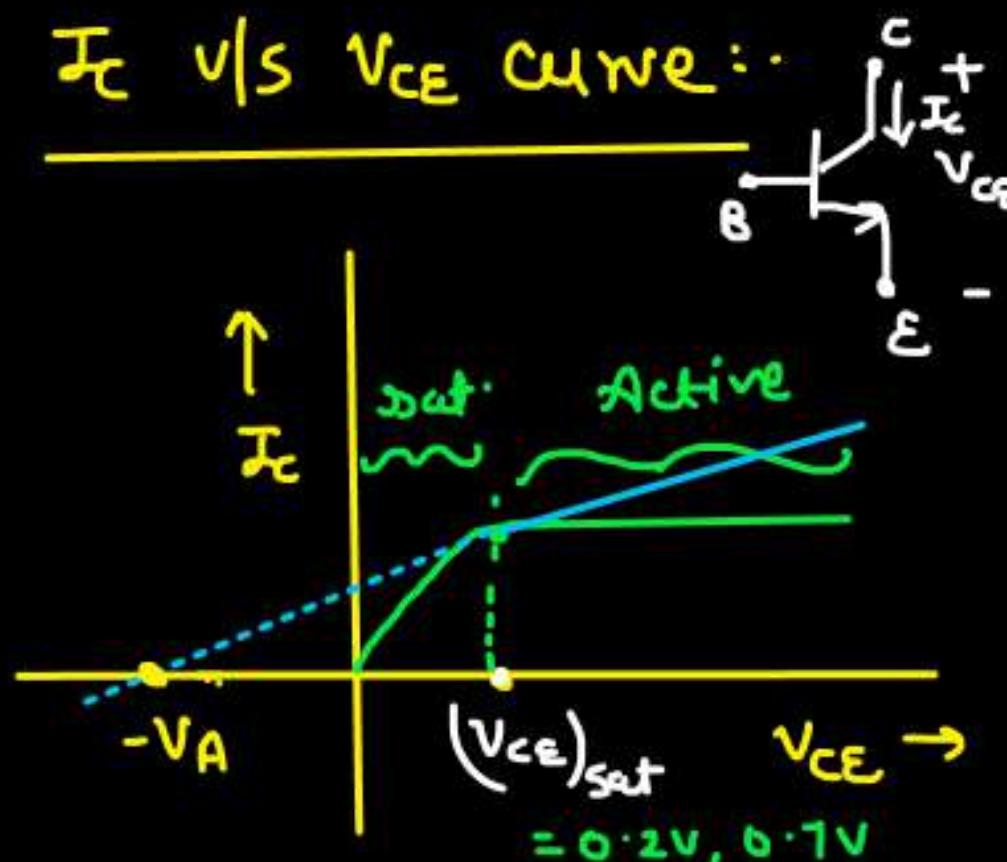


$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$


$V_{CE} > (V_{CE})_{sat}$

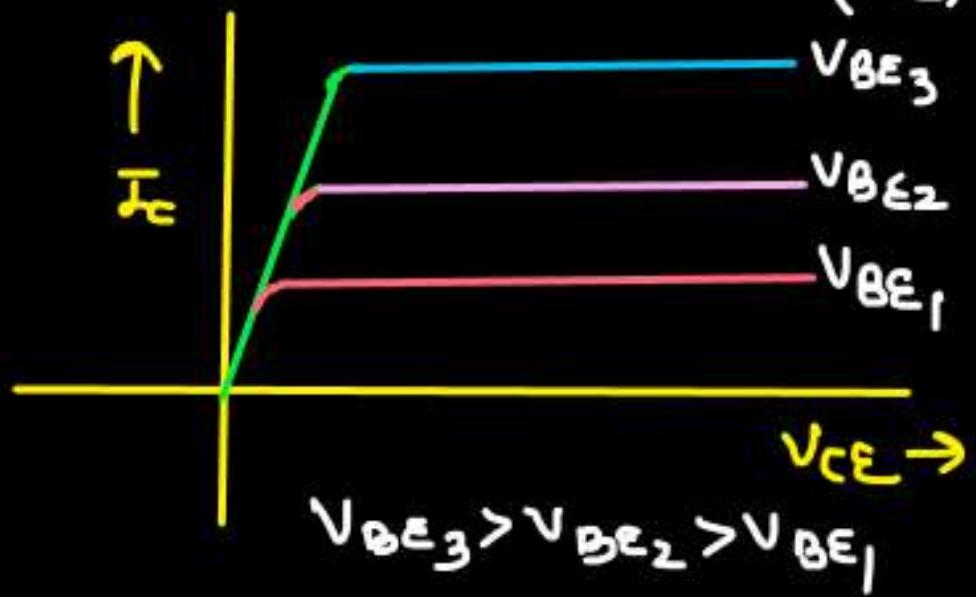

$I_D$  v/s  $V_{DS}$  curve


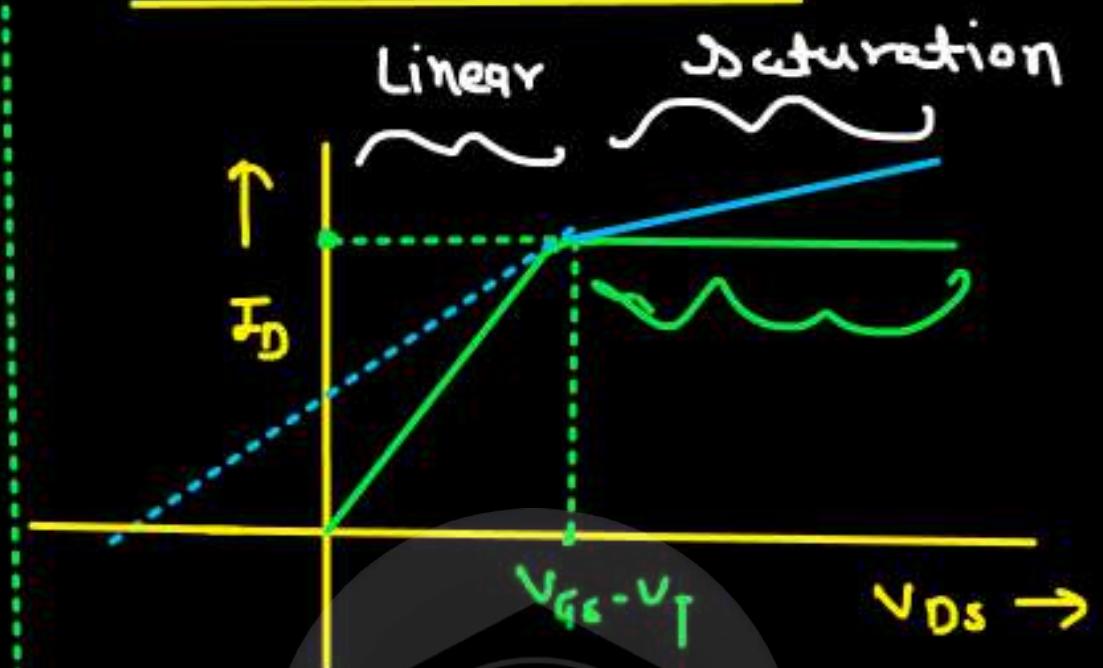

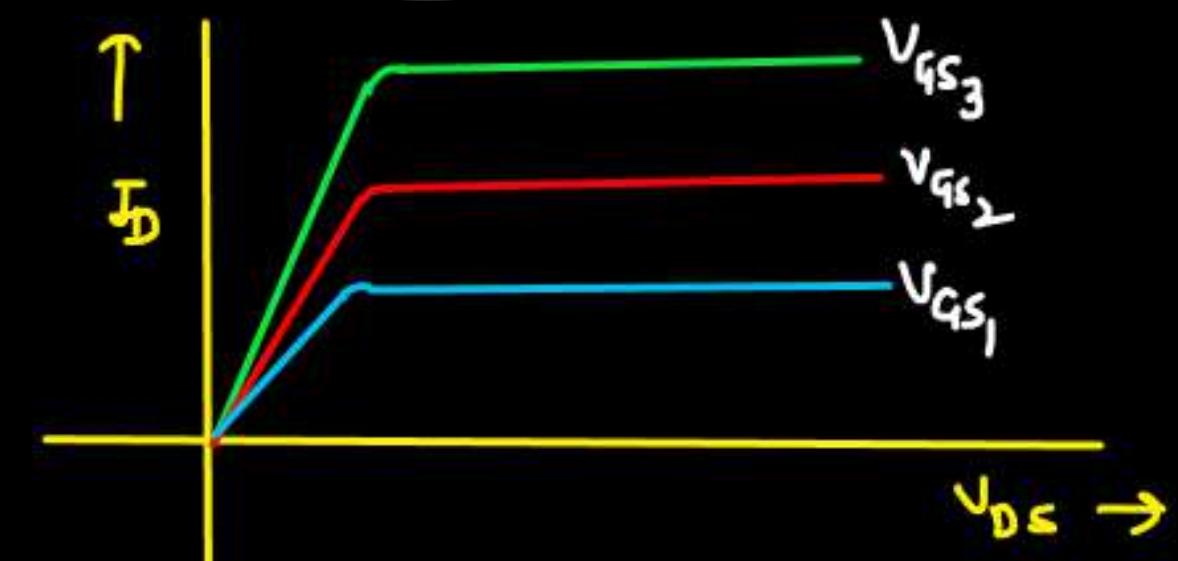
$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \quad \{ V_{DS} > V_{GS} - V_T \}$$



$$V_{GS_3} > V_{GS_2} > V_{GS_1}$$

## Region of Operations in BJTs:-

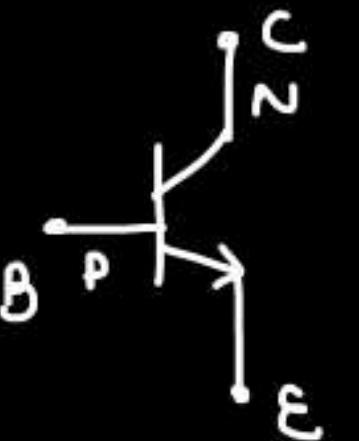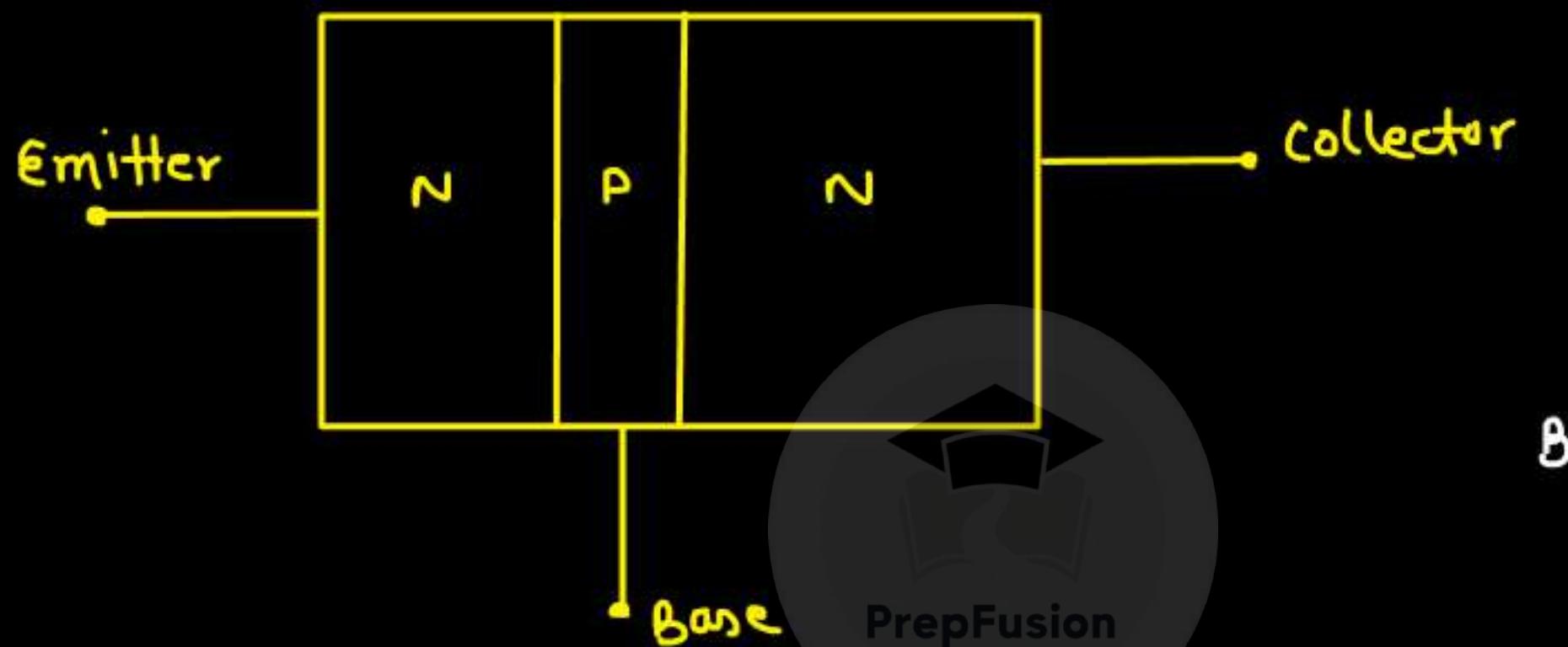

Emitter - Base → Emitter Junction ( $J_E$ )

Collector - Base → Collector Junction ( $J_C$ )

**Region of Operation**

	$J_E$	$J_C$
① Cut-off	RB	RB
② Saturation	FB	FB
③ Forward Active	FB	RB
④ Reverse Active	RB	FB

[ Active ]

PrepFusion

## Active region of operation:-

$$J_E \rightarrow FB$$

$$J_E = J_C + J_B \quad \checkmark$$

$$J_C \rightarrow RB$$

$$J_C = \beta J_B \quad \checkmark$$

$$J_C = \alpha J_E \quad \checkmark$$

$$V_{BE} = 0.7V \text{ [or given]} \quad \checkmark$$

$$V_{CE} > (V_{CE})_{sat}$$

$$I_C \rightarrow \max^n$$

## Saturation Region:-

$$J_E \rightarrow FB$$

$$J_C \rightarrow FB$$

$$J_E = J_C + J_B \quad \checkmark$$

$$J_C = \beta J_B$$

$$J_C = \alpha J_E$$


$$V_{BE} = 0.7V \text{ [or given]} \quad \checkmark$$

$$V_{CE} = (V_{CE})_{sat} = 0.2V \text{ [or given]} \quad \checkmark$$

$$I_C \rightarrow \min^n$$

PrepFusion

Q.

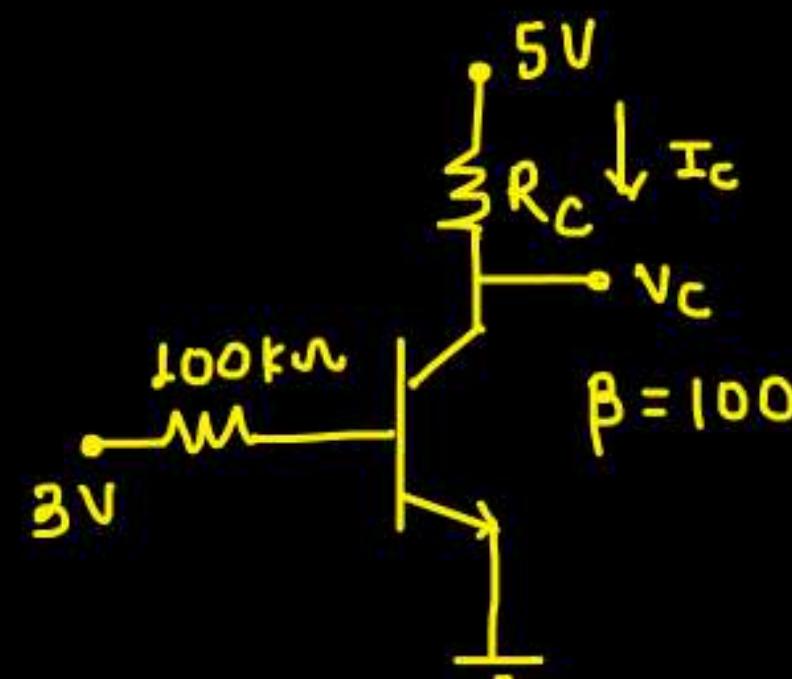

$$V_{BE} = 0.7\text{V}$$


$$(V_{CE})_{sat} = 0.2\text{V}$$

Find the value of  $V_{CE}$  and  $I_C$  for

(a)  $R_C = 1\text{k}\Omega$


(b)  $R_C = 10\text{k}\Omega$

PrepFusion

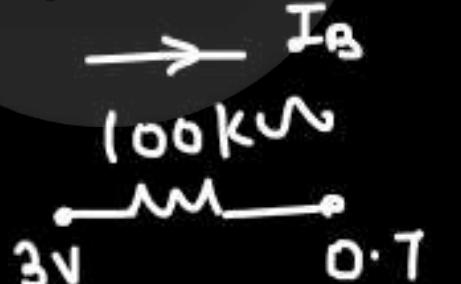


$$I_B = \frac{2.3}{100\text{k}}$$

**$I_B = 23\mu\text{A}$**

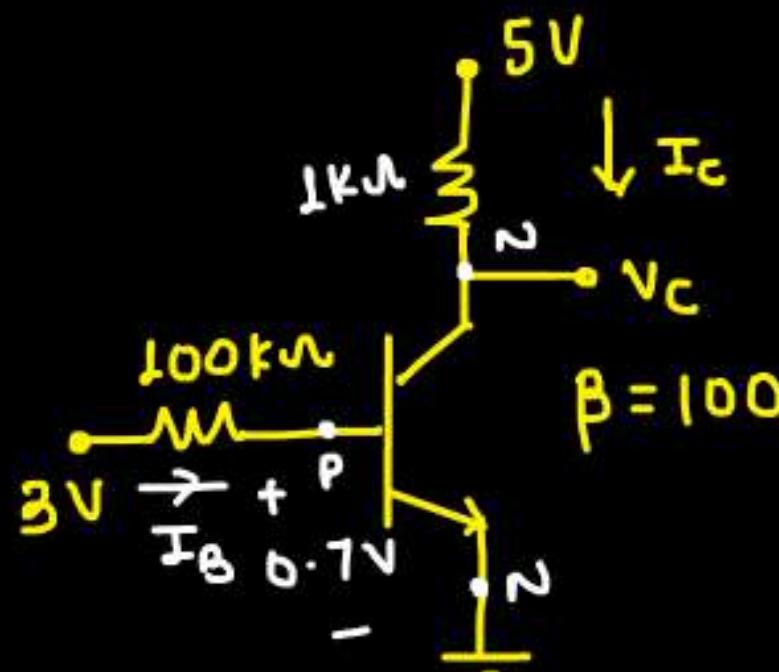

## Assuming BJT in active region

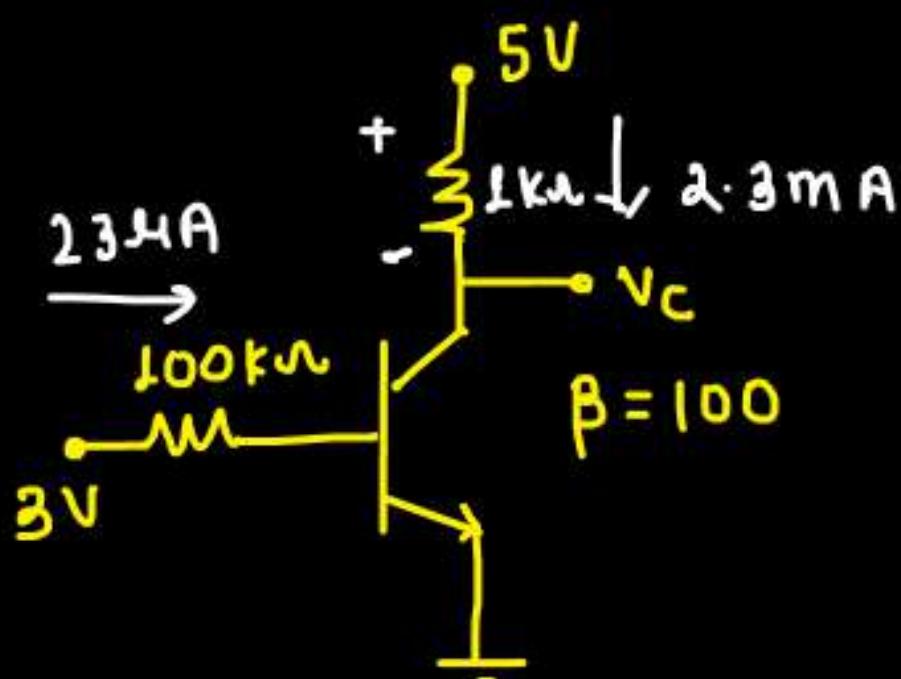

$$I_C = \beta I_B$$


$$I_C = 100 \times 23 \times 10^{-6} \text{ Amp}$$

$$I_C = 2.3 \text{ mA} \quad \approx$$

$$V_C = 5 - (1k)(2.3 \text{ mA})$$

$$V_C = 2.7 \text{ V} \quad \approx$$

PrepFusion

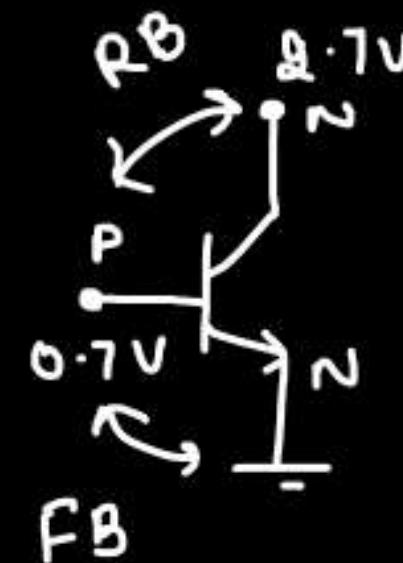


$\Rightarrow$  BJT is in active region

Assumption correct

$$I_E = (\beta + 1) I_B = 101 \times 23 \mu = 2.323 \text{ mA}$$

(b)

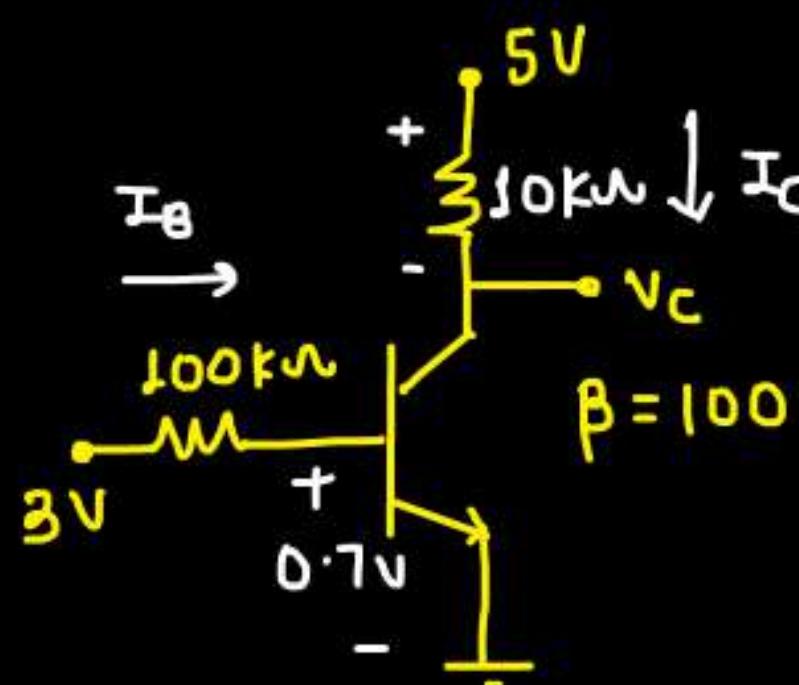


$$I_B = \frac{2 \cdot 3}{100k} = 2.3 \mu A$$

Assuming, BJT in active


$$\begin{aligned} I_C &= \beta I_B \\ &= 100 \times 2.3 \mu \\ &= 2.3 \text{ mA} \quad \times \end{aligned}$$

PrepFusion
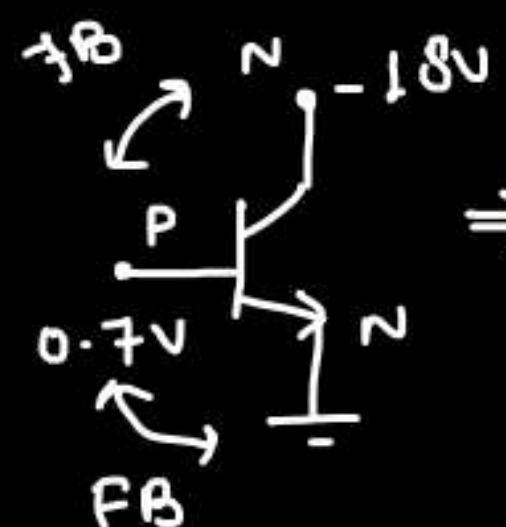
$$\begin{aligned} V_C &= 5 - 10k \times I_C \\ &= 5 - 10k \times 2.3 \\ &= 5 - 23 \\ &= -18V \quad \times \end{aligned}$$



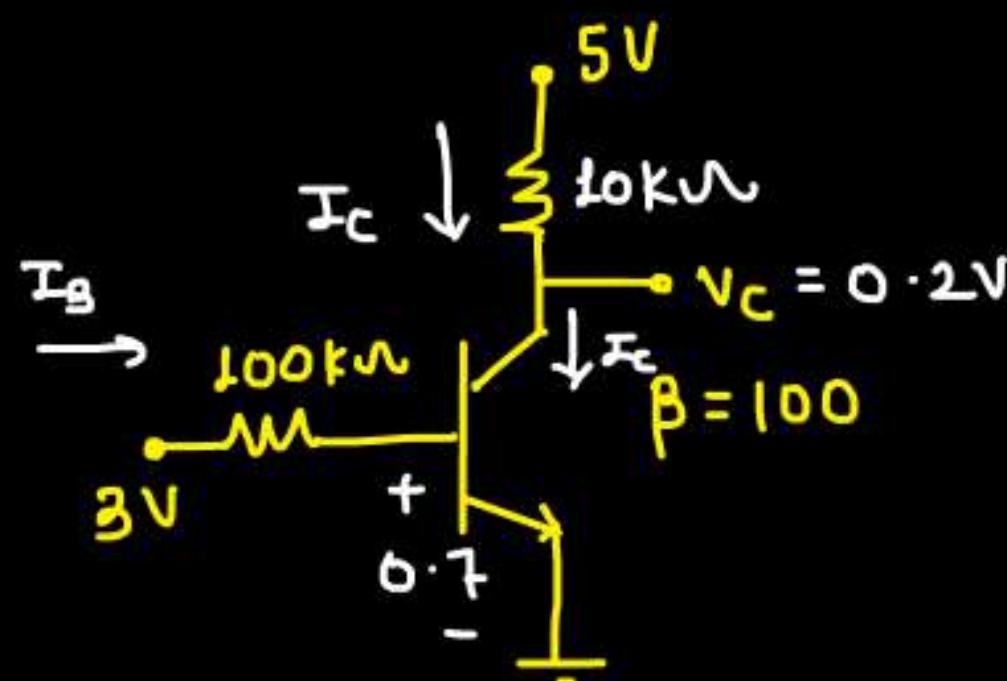$\Rightarrow$  Sat. region  
∴ Assumption wrong



$$I_B = \frac{2 \cdot 3}{100k}$$

$$I_B = 23 \mu\text{Amp}$$

$$I_E = I_C + I_B$$

$$= 480 + 23$$

$$I_E = 503 \mu\text{A}$$

Given, if BJT is in sat.

$$\Rightarrow V_{CE} = (V_{CE})_{Sat} = 0.2V$$


$$I_C = \frac{5 - 0.2}{10k} = 0.48 \text{ mA}$$

$$V_C = 0.2V$$

PrepFusion  $I_B = ?$

$$I_B = I_C / \beta = ?$$

## PNP Transistor:-

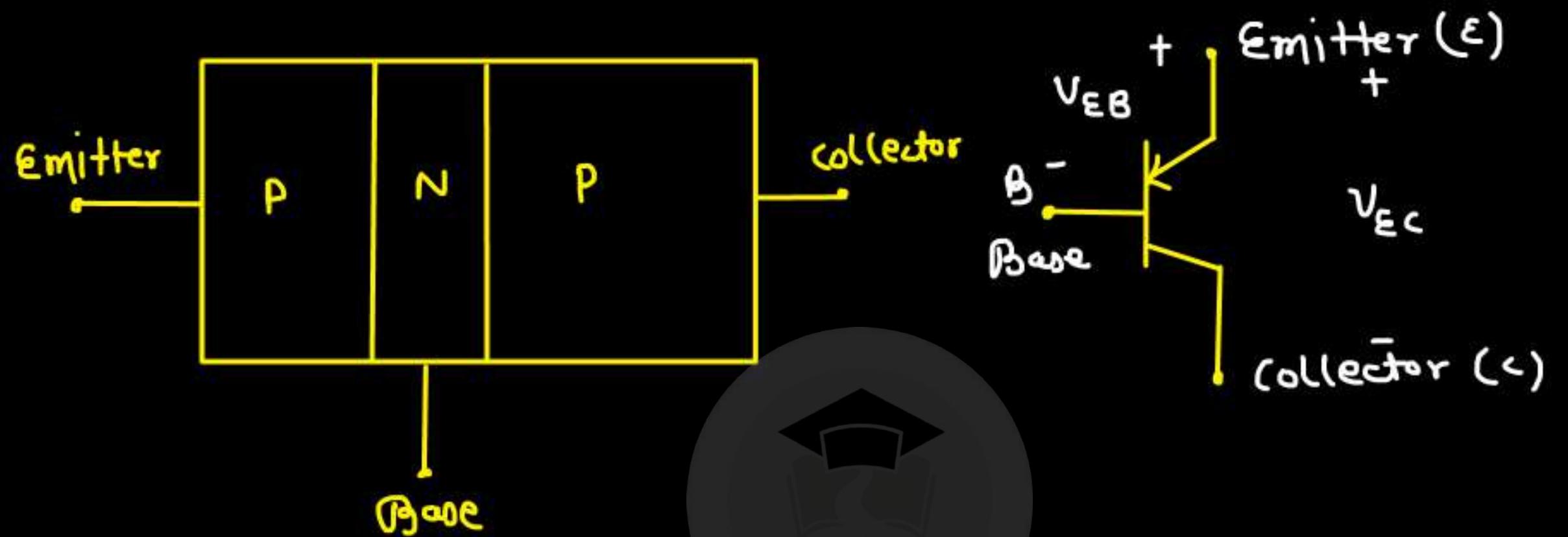

PrepFusion

$$I_C = I_S \exp\left(\frac{V_{EB}}{nV_T}\right) \left(1 + \frac{V_{EC}}{V_A}\right)$$




$$V_{EC} > (V_{EC})_{sat}$$

$$I_E = I_C + I_B$$

$$I_C = \beta I_B$$

$$I_E = (\beta + 1) I_B$$

Active  
region

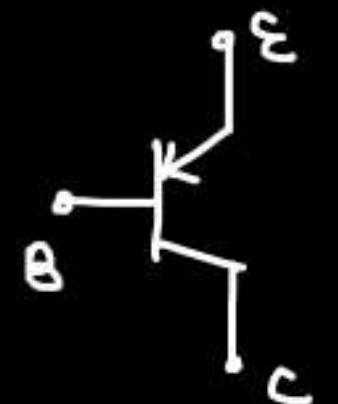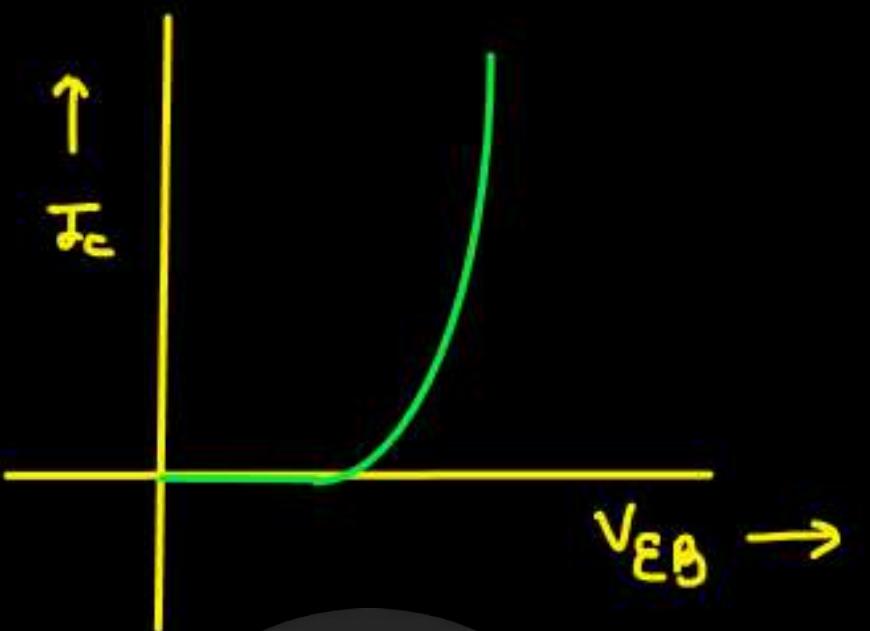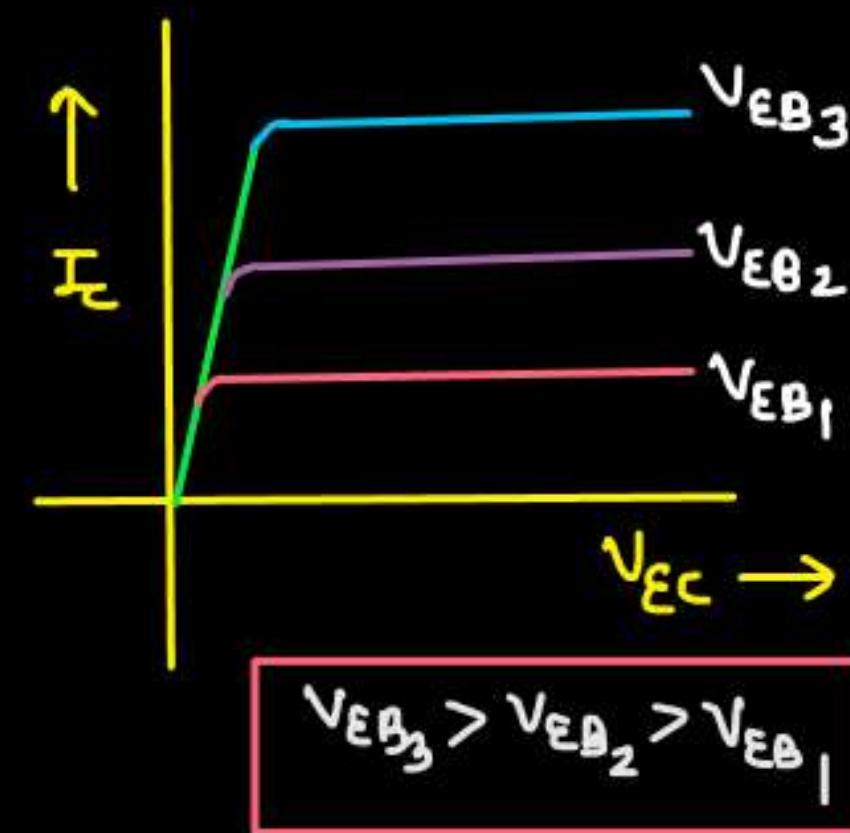

Region of operation:-

Active  $\equiv J_E \rightarrow FB, J_C \rightarrow RB \quad \{$


Sat.  $\equiv J_E \rightarrow FB, J_C \rightarrow FB \quad \}$

Cut off  $\equiv J_E \rightarrow RB, J_C \rightarrow RB$

Reverse Active  $\equiv J_E \rightarrow RB, J_C \rightarrow FB$

## Assignment - 18

Q.

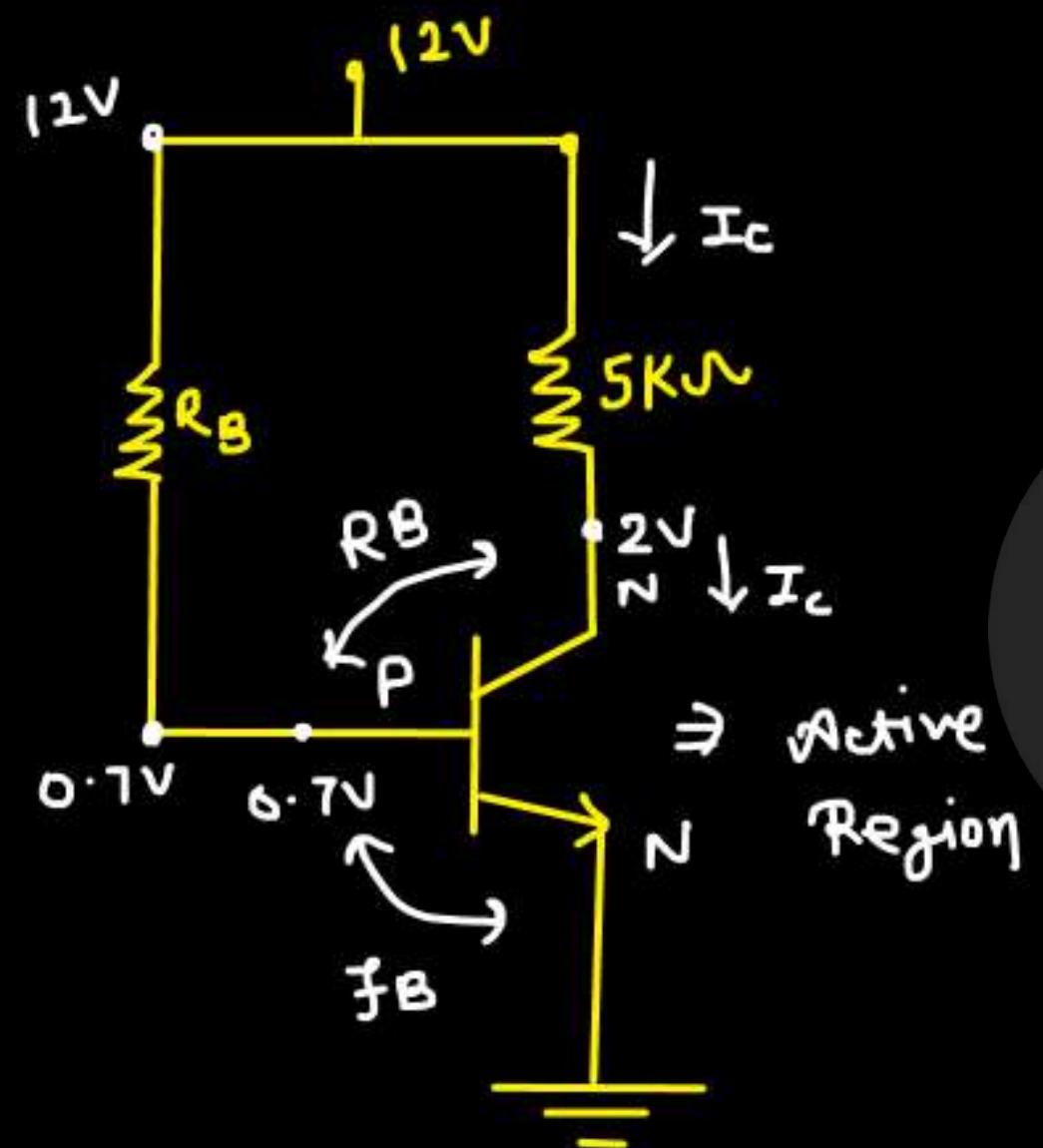

$$V_{CE} = 2V$$

$$V_{BE} = 0.7 \text{ V}$$

$$\beta = 50$$

Find Reg.  
PrepFusion

$$I_c = \frac{10}{5k} = 2 \text{ mA}$$


$$I_B = \frac{11.3}{R_B}$$

$$I_c = \beta I_B$$

$$2mA = \frac{50 \times 11.3}{R_B}$$

$$R_B = 282.5 \Omega$$

Q.

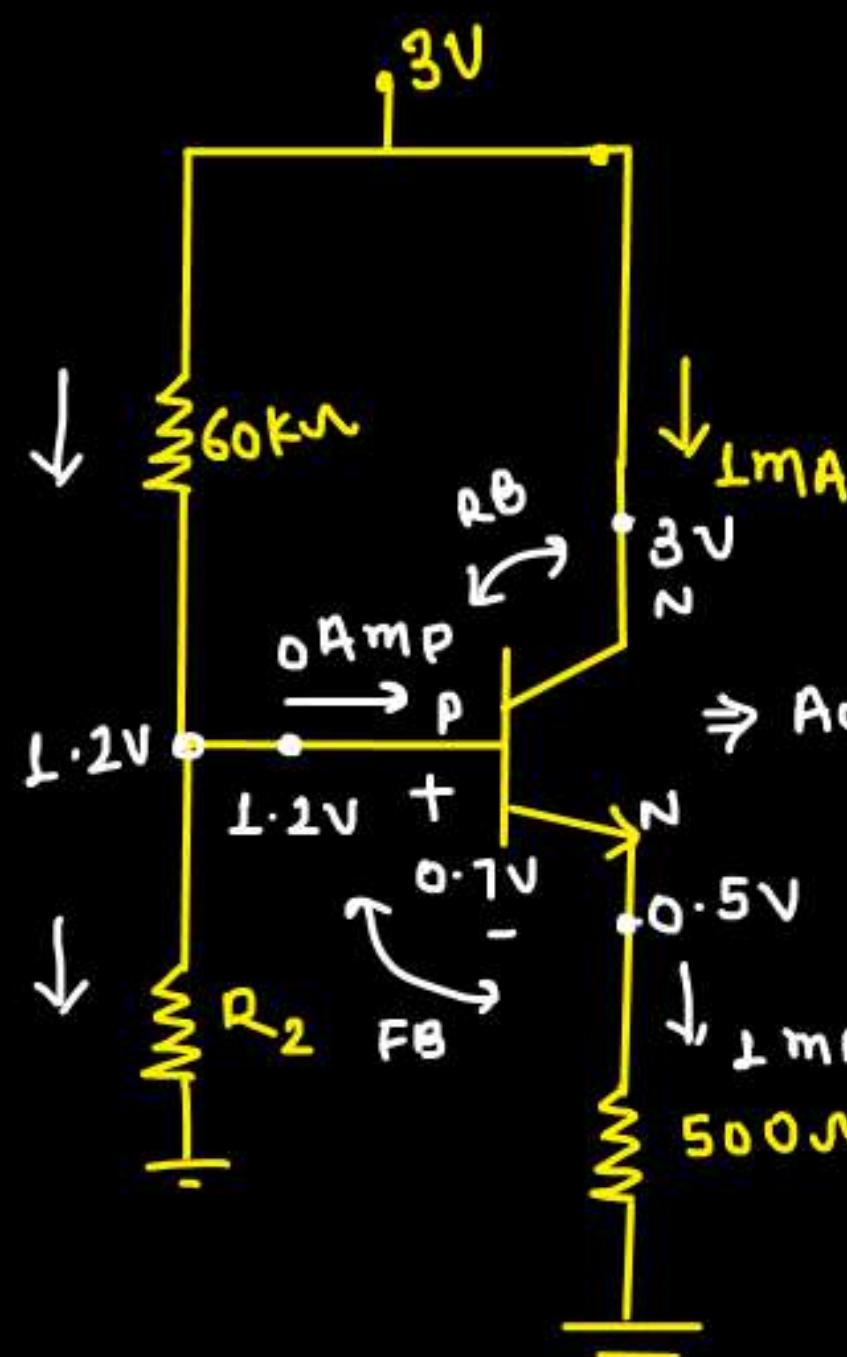

$$I_C = 1 \text{ mA}$$

$$\beta = \infty$$

Find  $R_2$

$$V_{BE} = 0.7$$

$$\beta = 0 \Rightarrow I_C = I_E = 1 \text{ mA}, I_B = 0$$


PrepFusion

$$\frac{3 - 1.2}{60} = \frac{1.2}{R_2} \quad \{ R_2 \text{ in k}\Omega \}$$

$$R_2 = 40 \{ \text{in k}\Omega \}$$

$$\Rightarrow R_2 = 40 \text{ k}\Omega$$

Q.

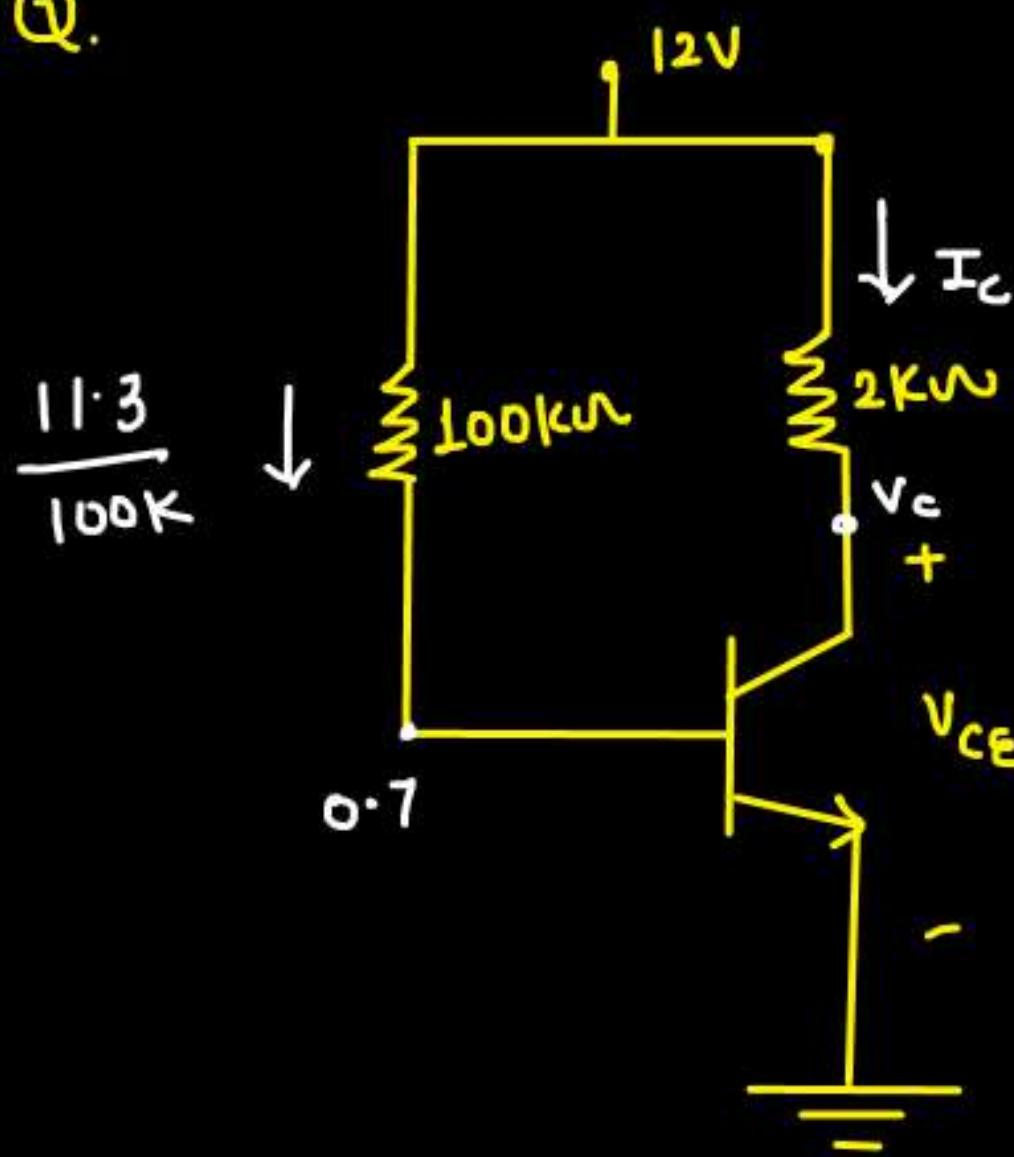

$$I_B = 11.3 \mu\text{Amp}$$

if  $\beta = 80$ ,  $V_{BE} = 0.7V$

Find  $V_{CE}$ ?

(a) -6.08V


(b) 0.2V

(c) 1.2V

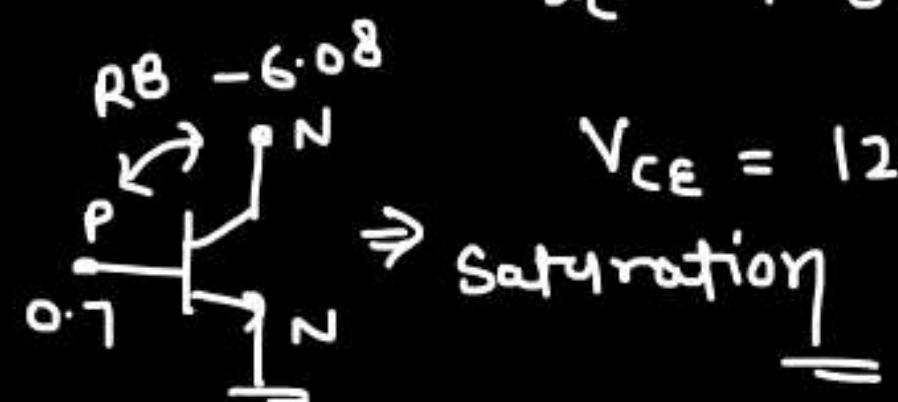(d) 6.08V

Active  $\rightarrow$  Assume

$$I_C = \beta I_B = 80 \times 11.3 \mu\text{A} = 9.04 \text{ mA}$$




$$V_{CE} = 12 - 2k(9.04\text{mA}) = -6.08V$$

$$(V_{CE})_{sat} = 0.2V = V_{CE}$$

Q.

$$I_E = (\beta + 1) I_B$$

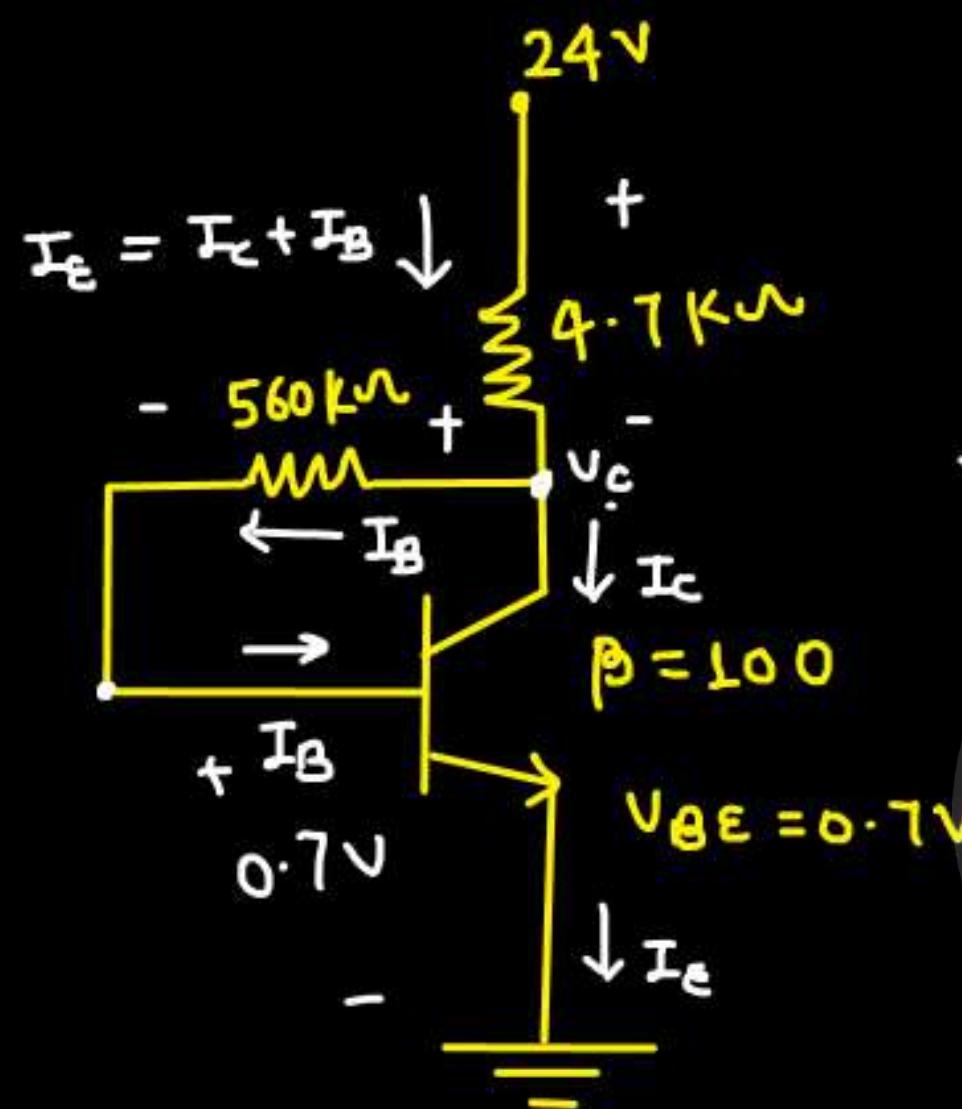

Find collector current.

$$\rightarrow 24 = (4.7k \times I_E) + (560k \times I_B) + 0.7$$

Assuming → Active

$$24 = 4.7 (101) I_B + 560 I_B + 0.7$$

$$I_B = 0.0225 \{ \text{in mA} \}$$


$$I_B = 0.0225 \text{ mA} = 22.5 \mu\text{A}$$

$I_C = \beta I_B = 2.25 \text{ mA}$  Ans.


$$I_E = 2.27 \text{ mA}$$

$$\rightarrow V_C = 24 - 4.7k \times 2.27 \text{ mA}$$

$V_C = 13.3V$

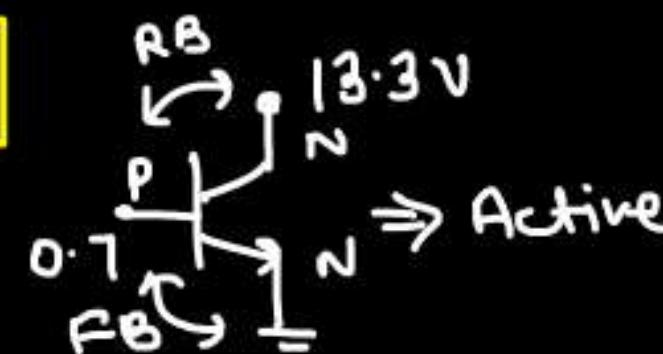

Q.

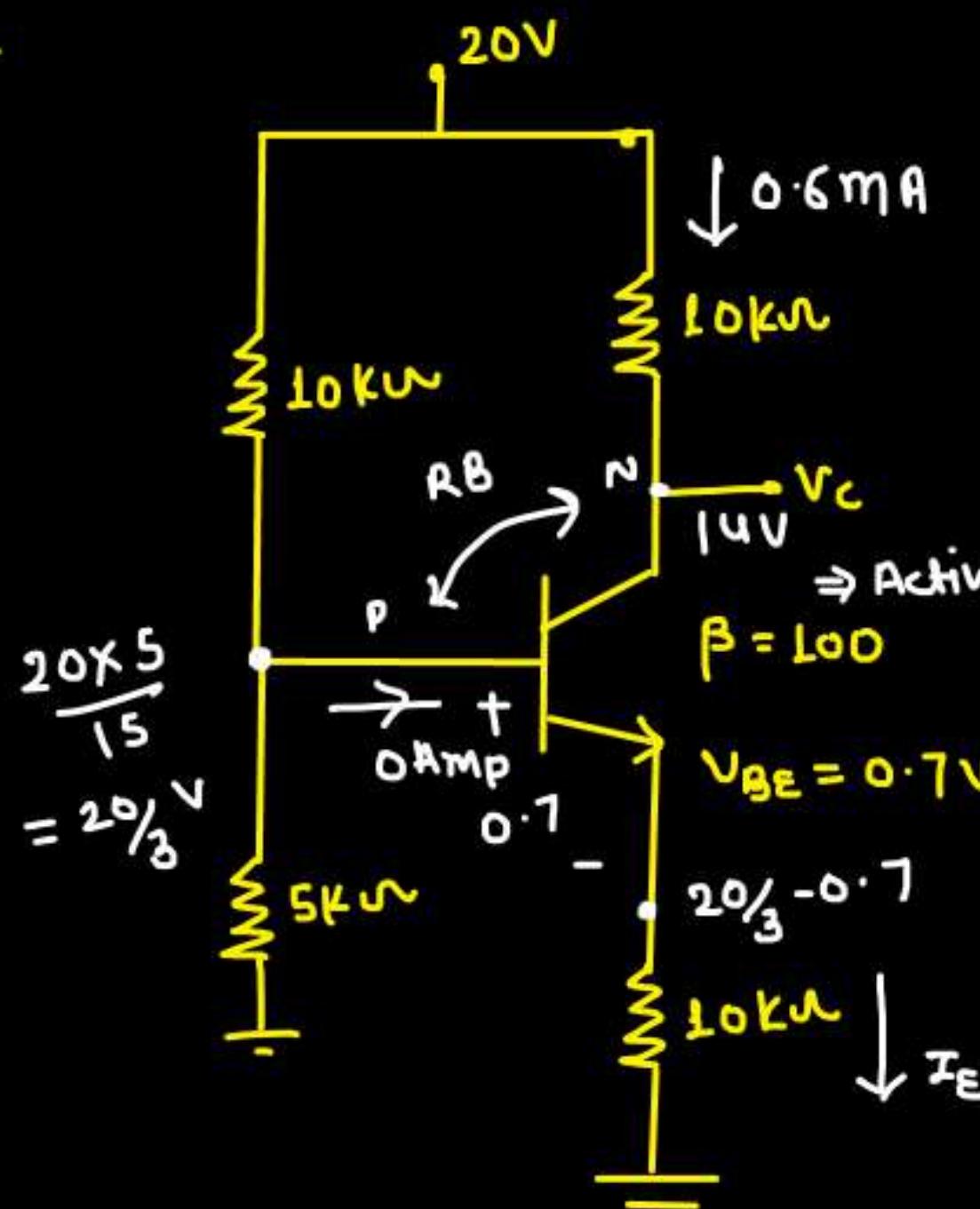


- (a)  $\frac{20}{3}V = 6.66V$
- (b) 10V
- (c) 14V
- (d) 20V

→ since, options are far from each other  
PrepFusion we are taking  $\beta \rightarrow \infty$  for ease of calculation

$$I_E = \frac{6.66 - 0.7}{10k} = 0.6 \text{ mA} \approx I_C$$

$$V_C = 20 - 10 \times (0.6) = 14V$$

Q.

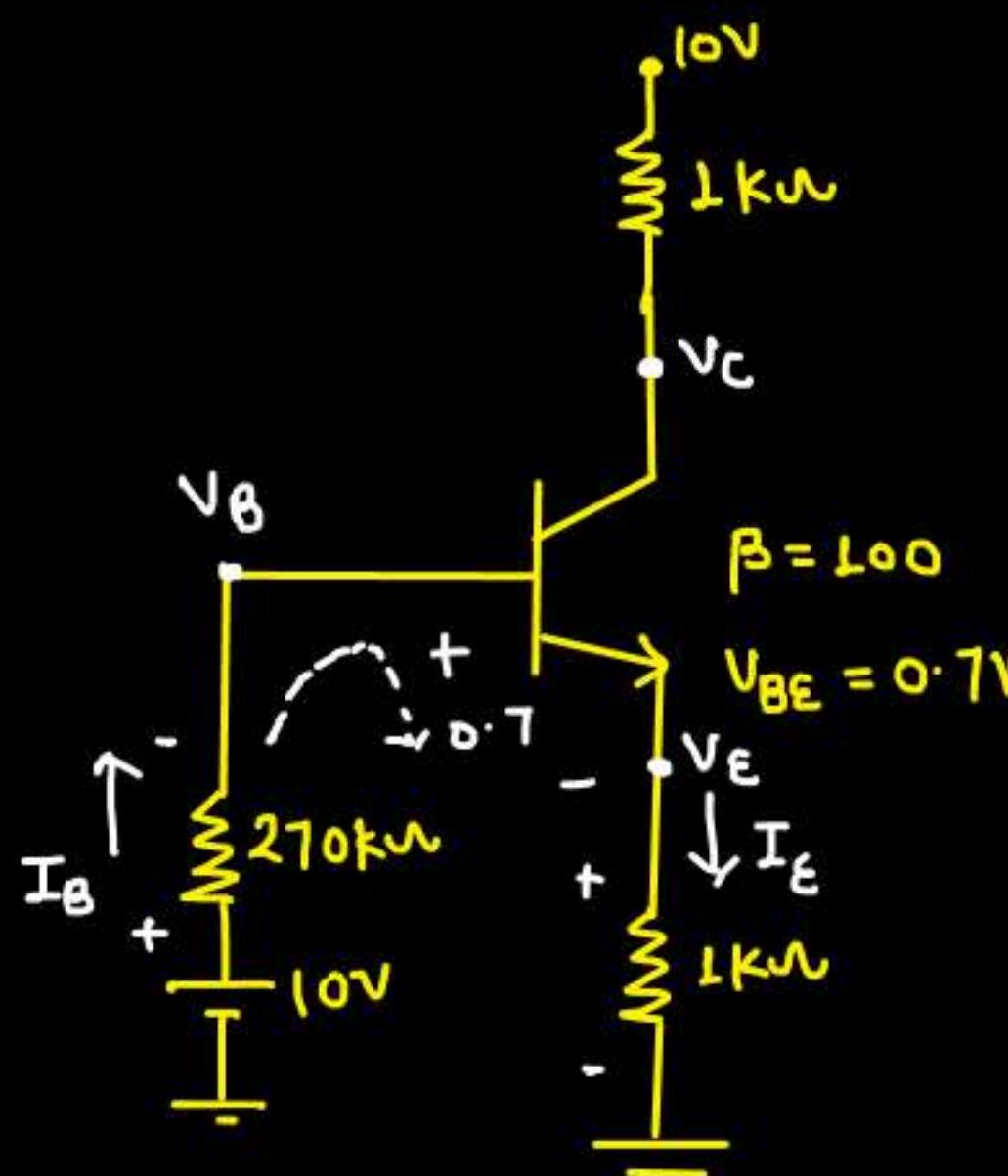

Find the region of operation.



$$I_O = 270 I_B + 0.1 + I_E$$

Assuming  $\rightarrow$  Active


$$I_O = 270 I_B + 0.1 + 101 I_B$$

PrepFusion

$$I_B = 0.025 \text{ mA}$$

$$I_E = 2.53 \text{ mA}$$


$$I_C = 2.5 \text{ mA}$$

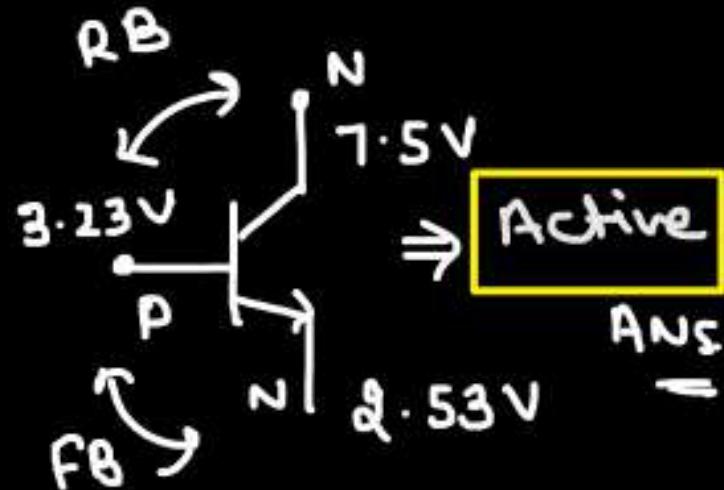

$$V_B = 3.23 + 0.7 = 3.93 \text{ V}$$

$$V_B = 2.53 + 0.7 = 3.23 \text{ V}$$

Q.

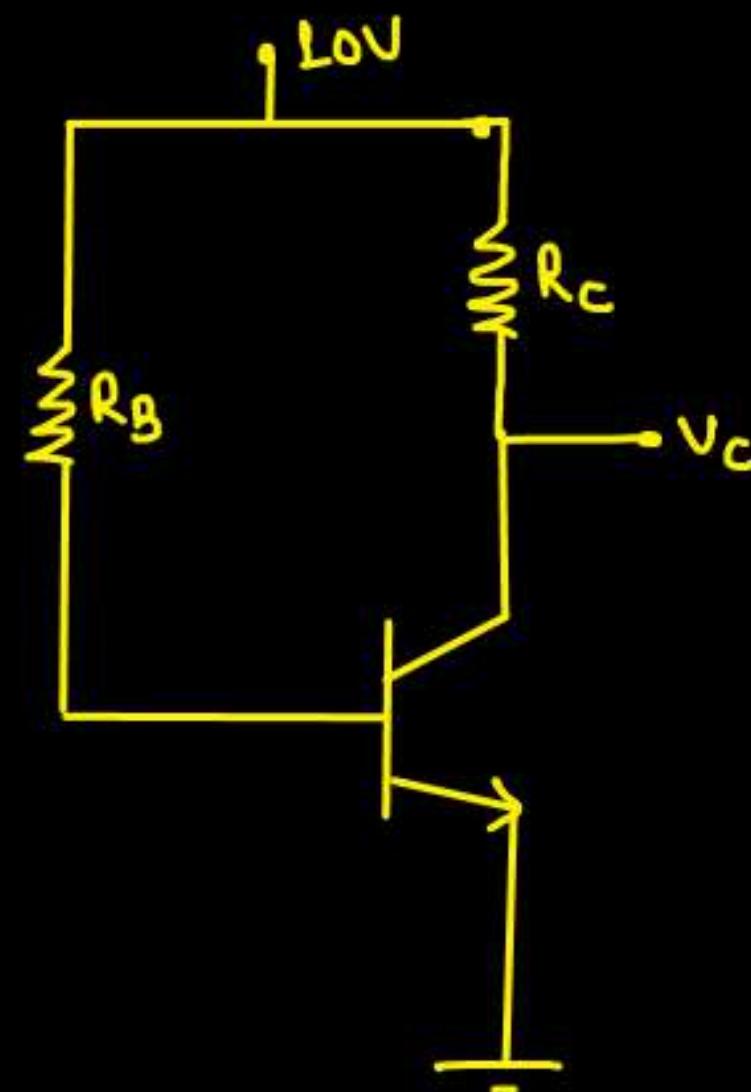

Transistor is working in active mode.

When  $V_C = 2V$ ,  $R_C = R_{C_1}$

when  $V_C = 4V$ ,  $R_C = R_{C_2}$

Find the ratio  $\frac{R_{C_2}}{R_{C_1}} = ?$


Even if  $V_{CE}$  is changing,  $I_C$  will be same.

$$\frac{10 - 2}{R_{C_1}} = \frac{10 - 4}{R_{C_2}} \Rightarrow \frac{R_{C_2}}{R_{C_1}} = 0.15$$



$$I_C \neq f(V_{CE})$$

Q.

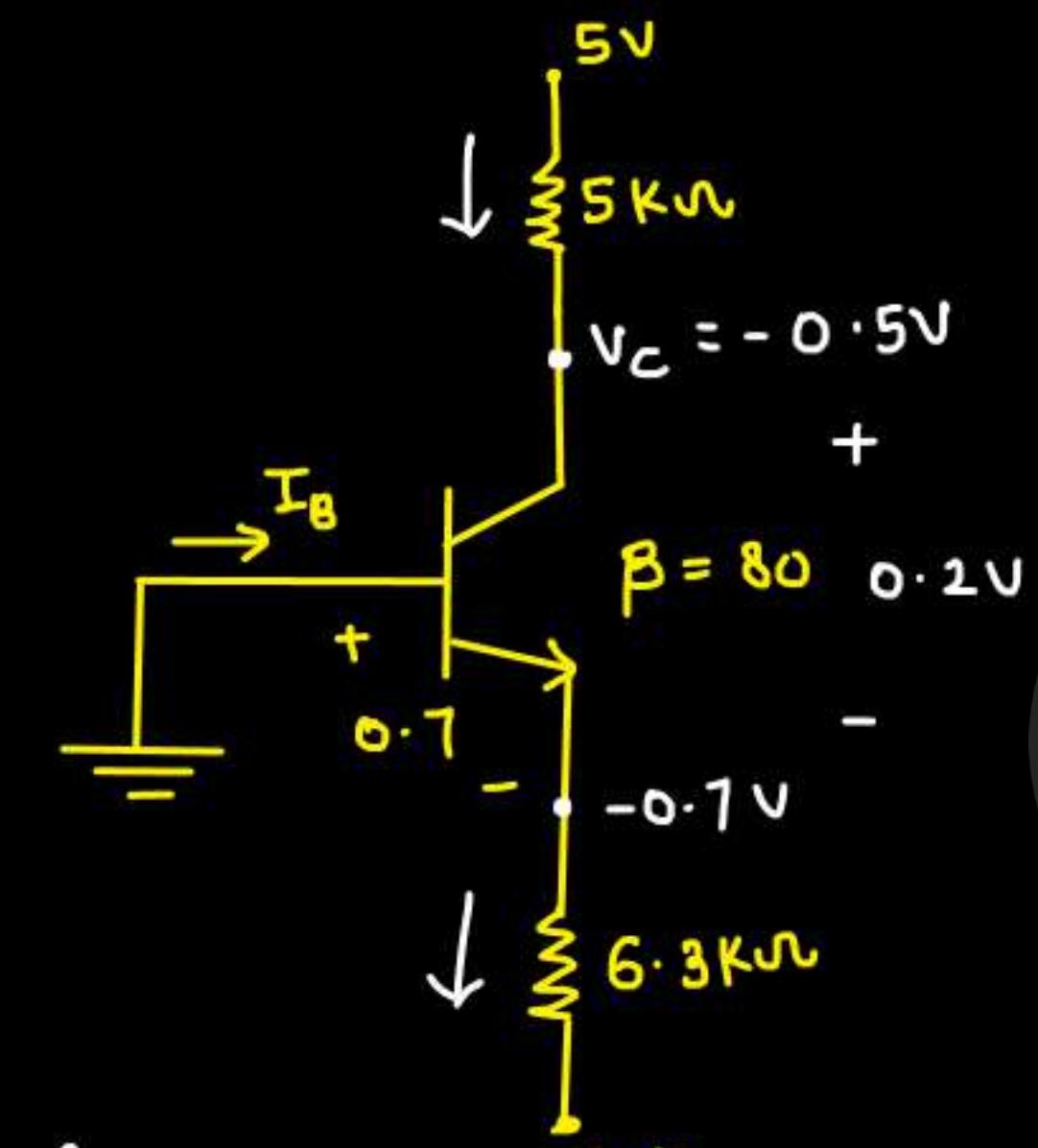

Find  $I_B$ ,  $(V_{CE})_{sat} = 0.2\text{V}$

$$I_E = \frac{-0.7 + 1.0}{6.3\text{k}} = 1.48\text{mA}$$

X Prep Fusion

$$I_B = \frac{1.48}{80} = 18.2\text{ }\mu\text{Amp}$$

{ Assumptions }  
→ Active

$$I_C \approx 1.48\text{mA}$$

$\beta B \rightarrow N -2.38\text{V} -10\text{V}$   
0V → P → N -0.7V  
 $f_B$

$\Rightarrow$  Det. { Assumption }  
wrong


$$V_C = 5 - (1.48 \times 5) = -2.38\text{V}$$

$$I_C = \frac{5.5}{5\text{k}} = 1.1\text{mA}$$

Ans.

$$I_B = 1.48 - 1.1 \\ = 0.38\text{mA}$$

Q.

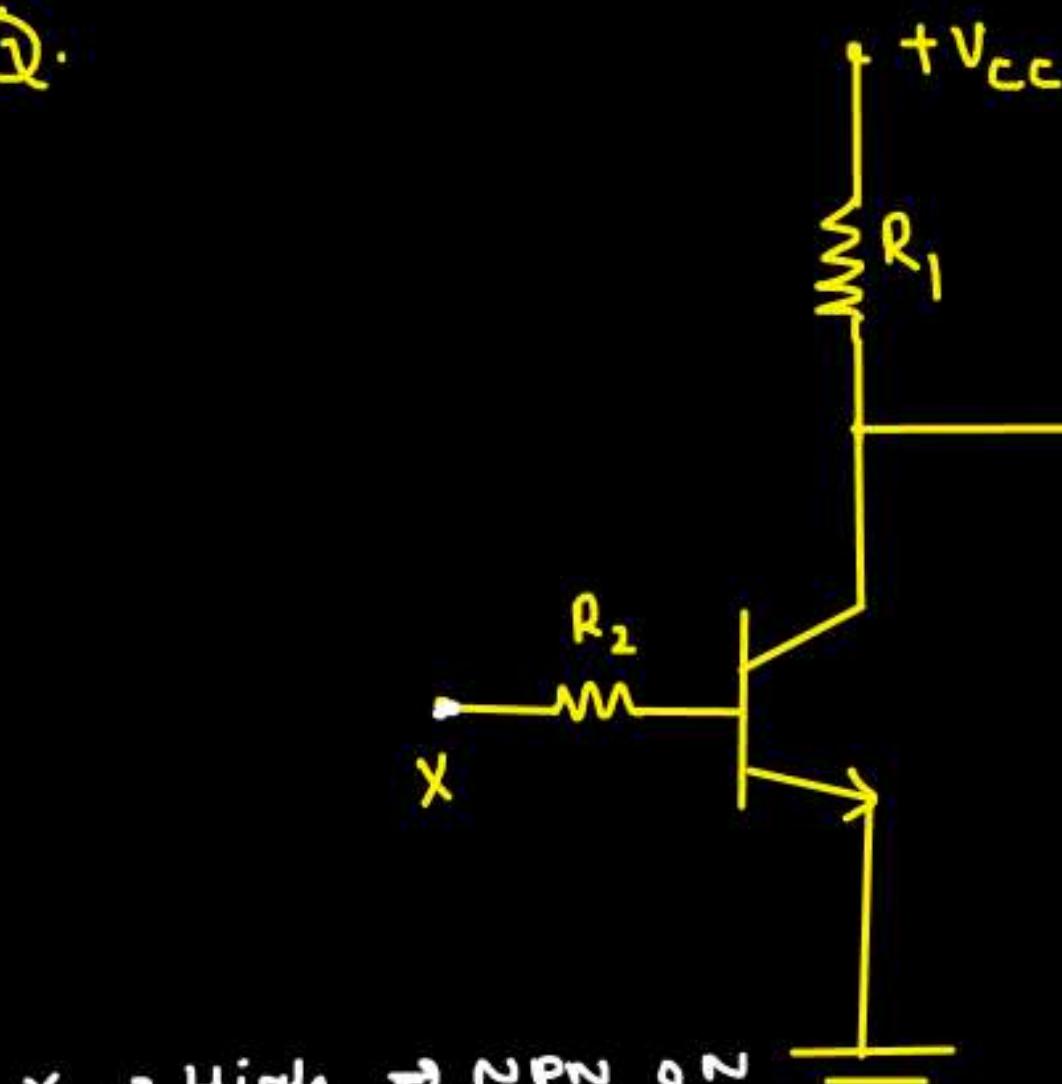

$X \rightarrow \text{High} \Rightarrow \text{NPN ON}$

$X \rightarrow \text{Low} \Rightarrow \text{NPN OFF}$

$L \rightarrow V_{CC}$

$0 \rightarrow \text{Ground}$


Boolean Expression for  $Z$ ?



$X$	$Y$	$Z$
0	0	0
0	1	1
1	0	0
1	1	0

$$Z = \bar{X}Y$$

Q.  $V_{EB} = 0.6V$

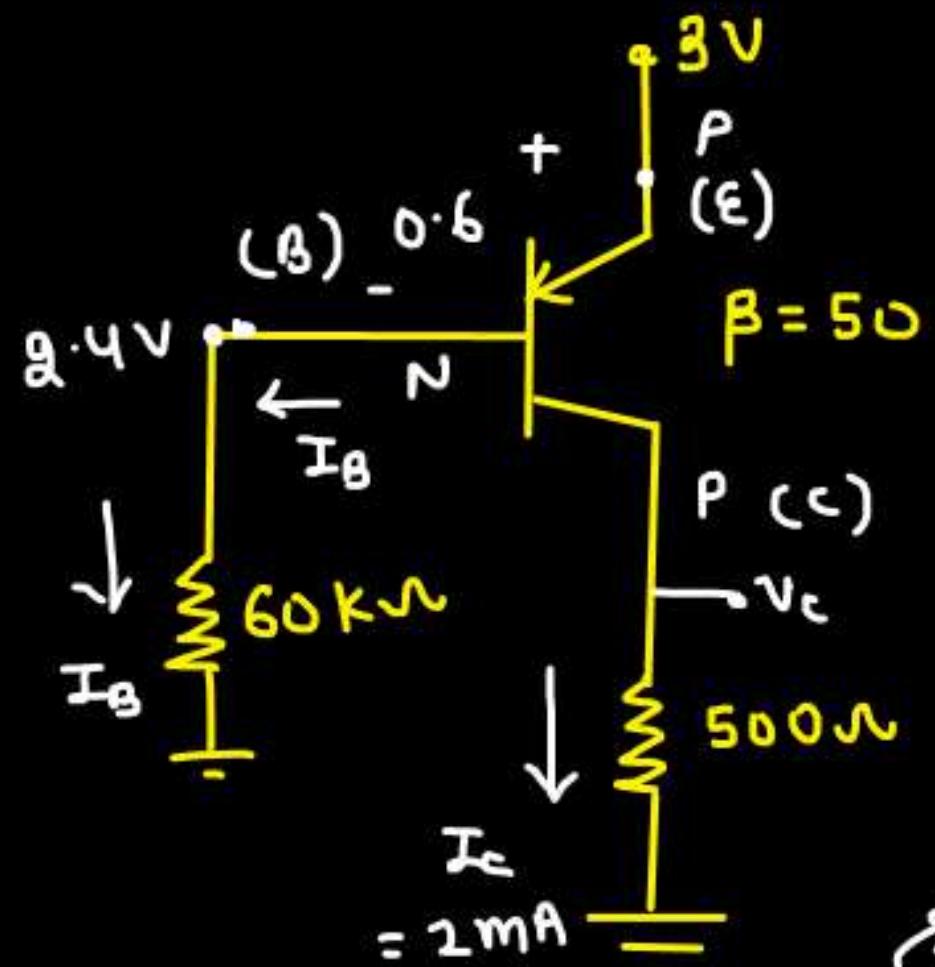


Find  $V_{EC}$ ?

$$I_B = \frac{2.4}{60k} = 0.04mA$$

Assuming  $\rightarrow$  Active


PrepFusion  $I_C = 0.04 \times 50 = 2mA$

$V_C = 500 \times 2mA = 1V$

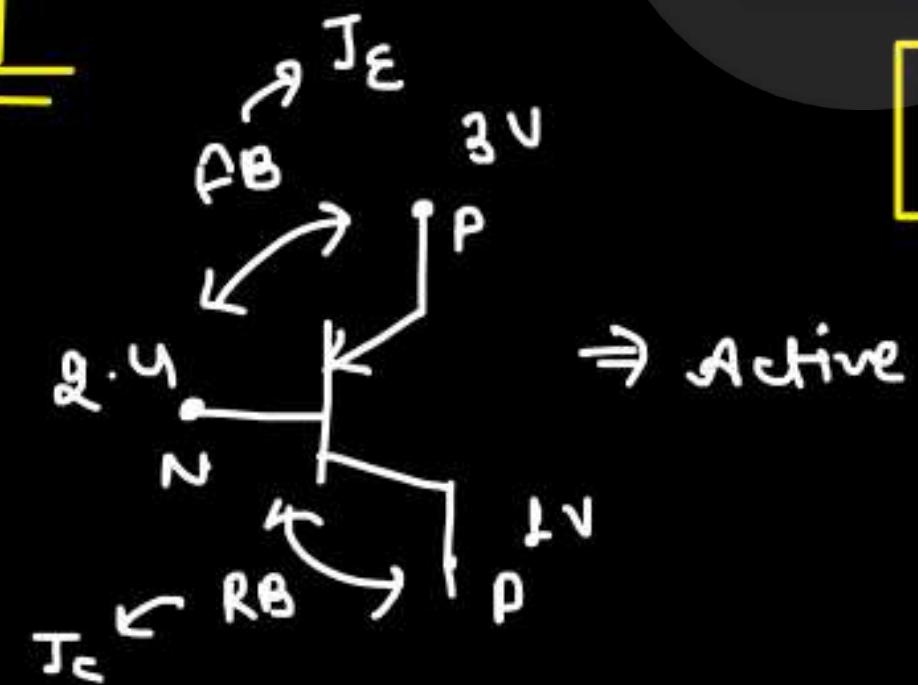

$V_{EC} = 3 - 1 = 2V$

Q.

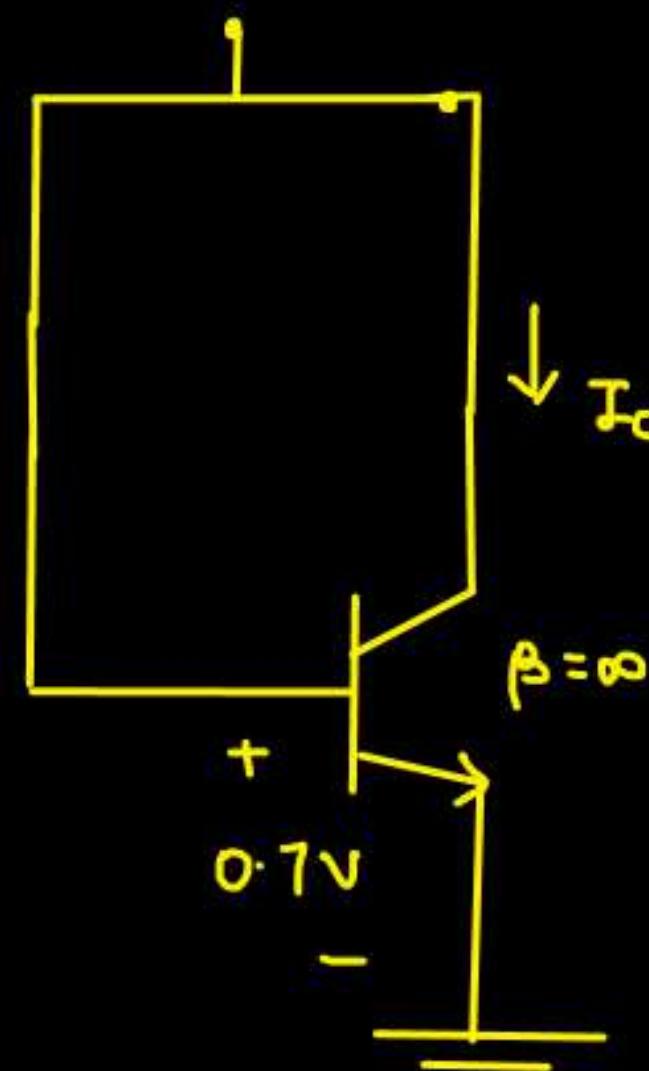

$$V_{BE} = 0.7V$$

Reverse saturation current =  $10^{-13}$  Amp

$$V_T = 26mV$$

Emitter current = ?

→  $I_C = I_E = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \rightarrow \text{Active region}$

PrepFusion


$$= 10^{-13} \exp\left(\frac{0.7}{0.025}\right)$$

$I_C = 49.2 \text{ mA}$



→ diode connected

Q.

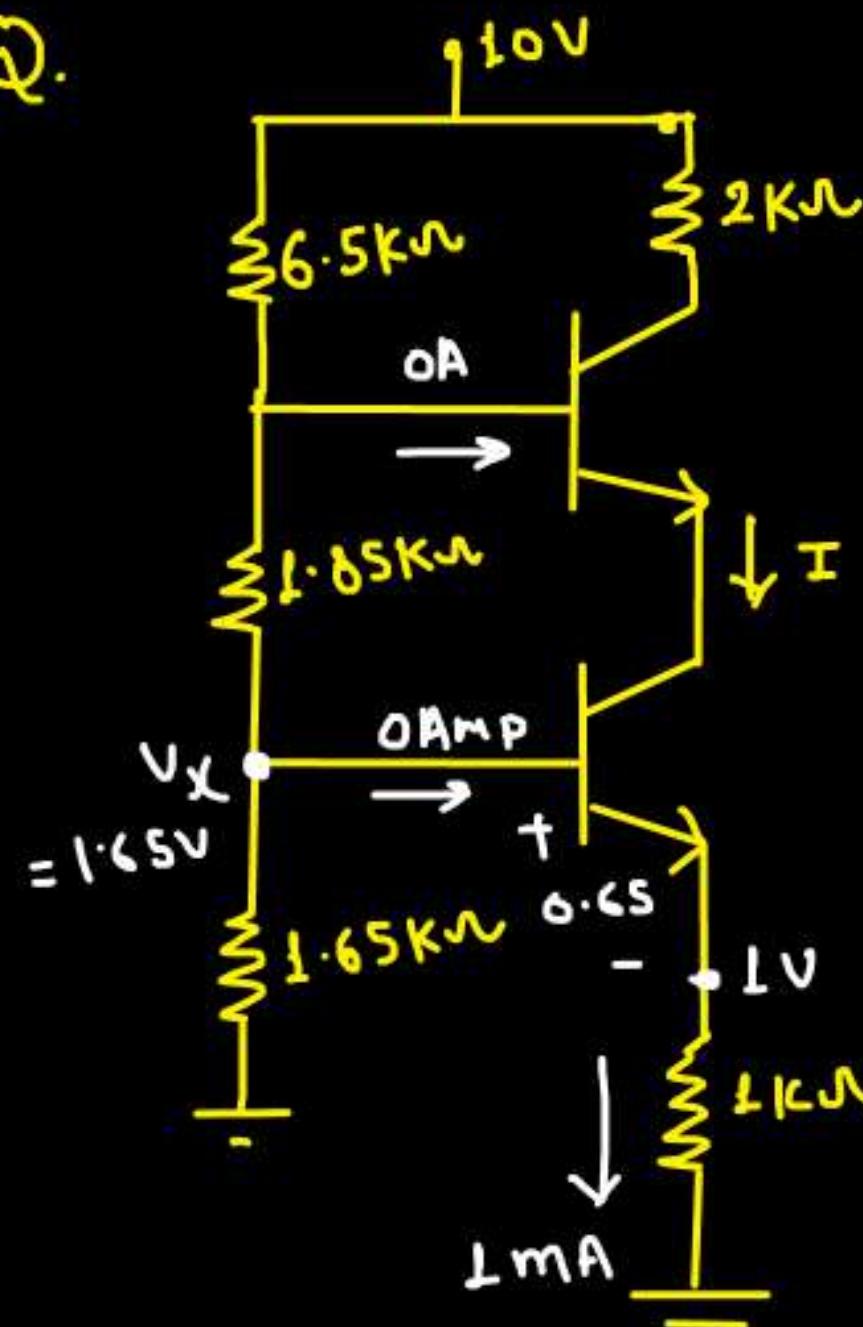

$$V_{BE} = 0.65$$

$\beta = \infty \rightarrow$  Active region


Find  $I$ ?

$$V_x = \frac{1.65}{1.65 + 1.85 + 6.5} \times 10 = 1.65V$$

PrepFusion

$$I = 1mA$$

Q.

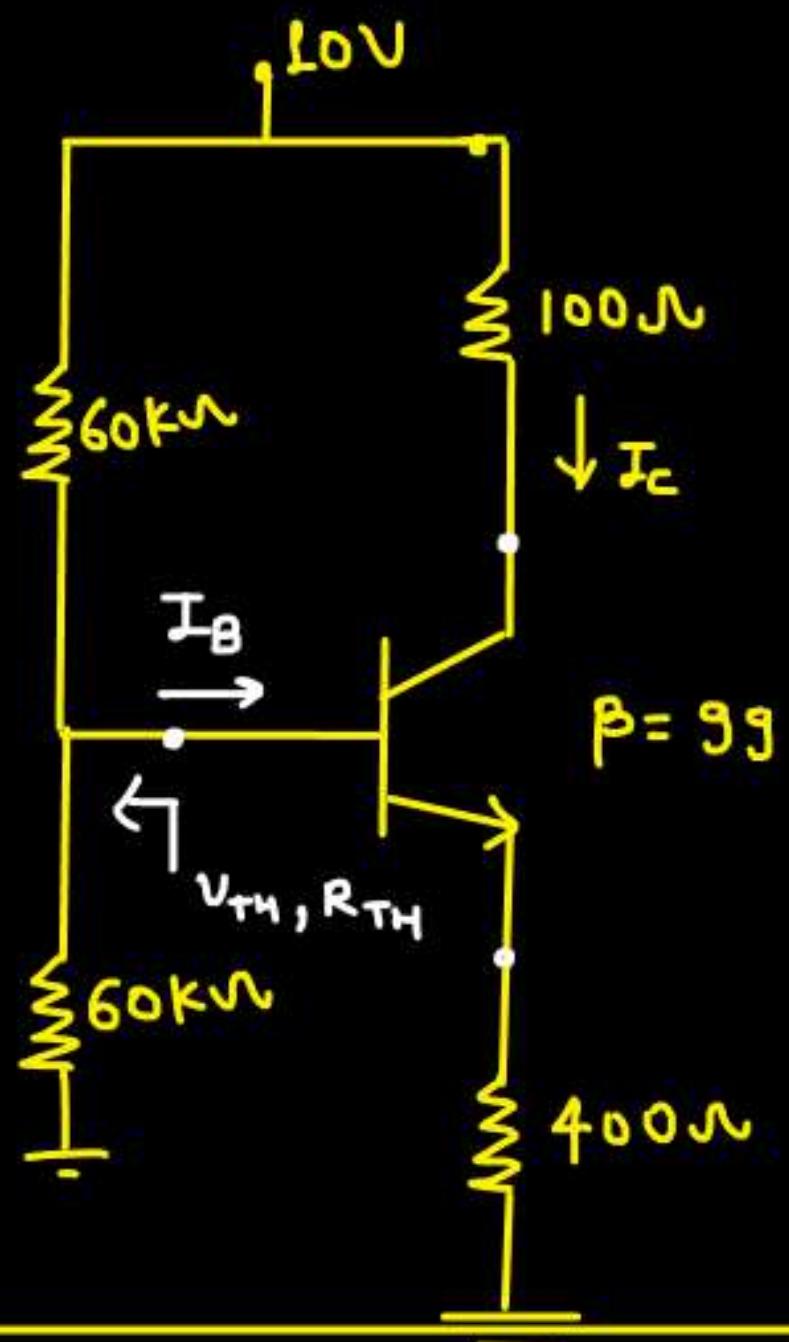

$$V_E = 0.4 \times 5.7 = 2.28V$$

$$V_C = 10 - (0.1 \times 5.65) = 9.43V$$

$$V_B = 3.28V$$

⇒ Active


$$V_{BE} = 1V$$

Find  $I_C$  ?

$$\rightarrow V_{TH} = \frac{10 \times 60}{120} = 5V$$

$$R_{TH} = 30k\Omega$$

PrepFusion

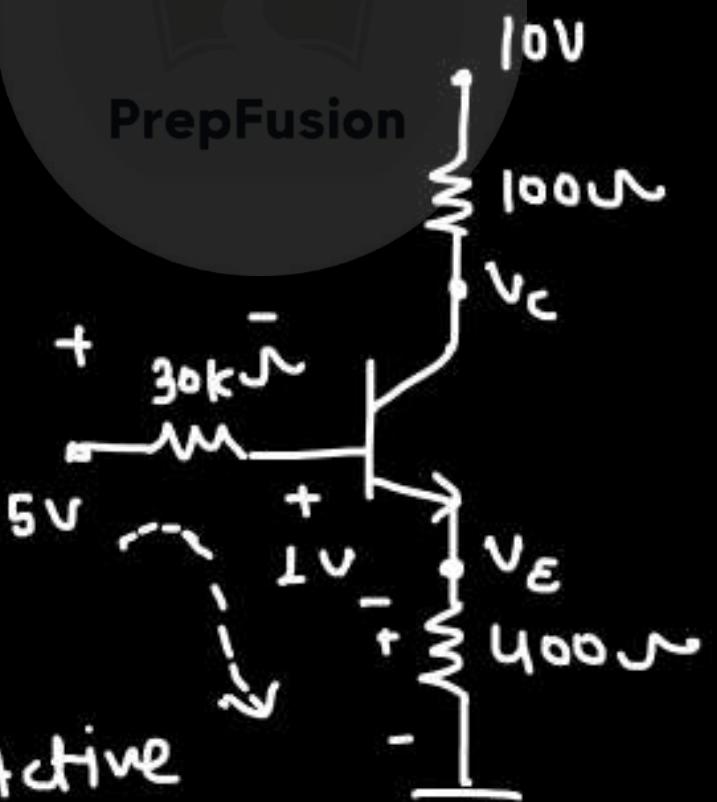

Assuming → Active

$$5 = 30 I_B + L + 0.4 (100) I_B$$


$$4 = 70 I_B$$

$$I_B = 0.057mA$$

$$I_C = 5.65mA \rightarrow \text{ANS} =$$

$$I_E = 5.7mA$$

Q.

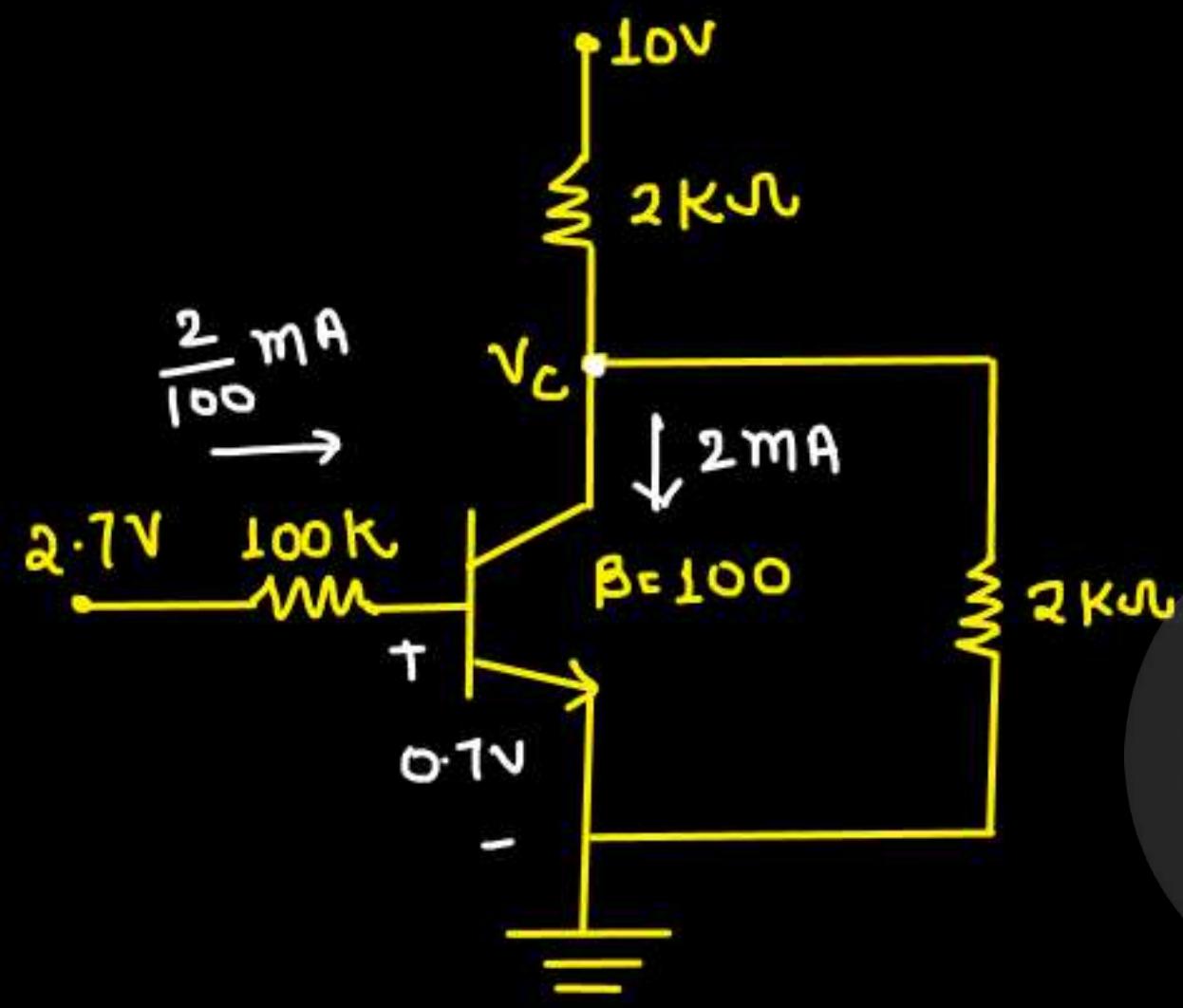



$$V_{BE} = 0.7V$$

Find  $V_C$ .


$$\frac{V_C - 10}{2k} + \frac{V_C}{2k} + 2mA = 0$$

$$2V_C - 10 + 4 = 0$$

$$V_C = 3 \text{ volt}$$

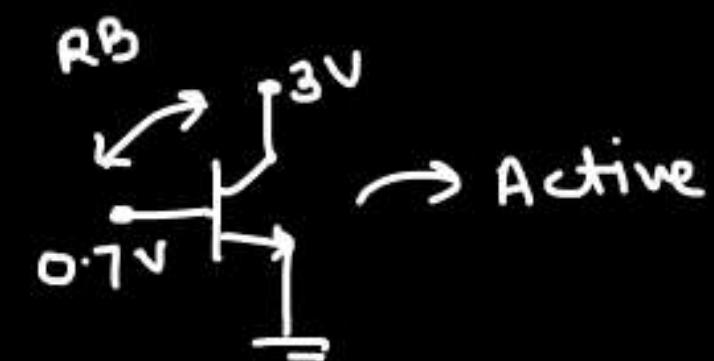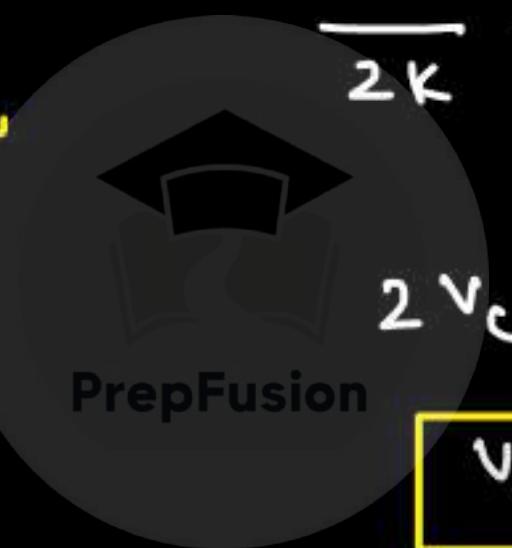

Q.

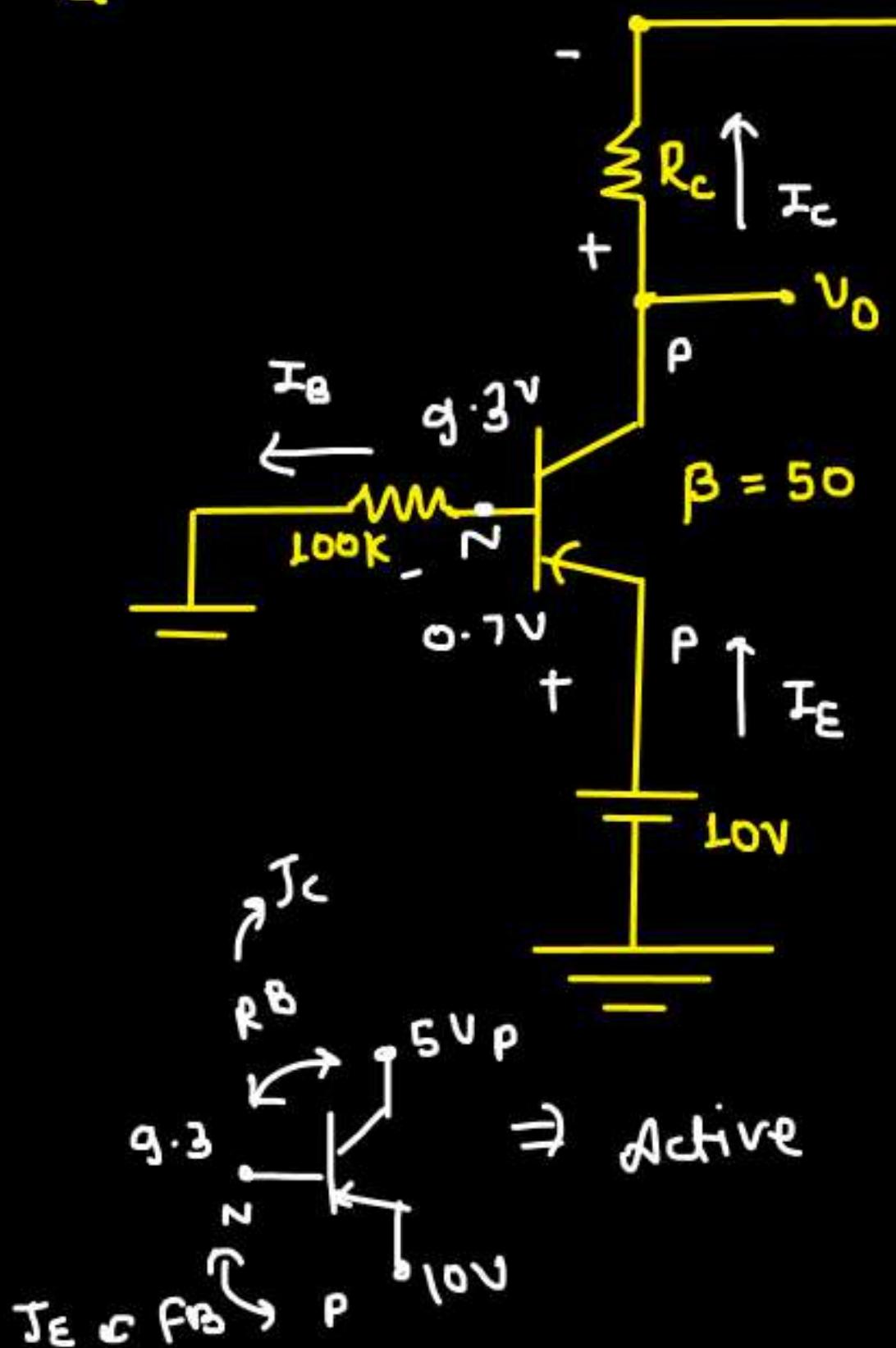

$$|V_{BE}| = 0.7V$$

For  $V_o$  to be 5V, the value of  $R_C$  (in k $\Omega$ ) is \_\_\_\_.

PrepFusion

$$I_B = \frac{3 \cdot 3}{100k} = 93 \mu A, \quad I_C = 4.65mA$$


$$V_o = I_C \times R_C$$

$$5 = 4.65mA \times R_C$$

$R_C = 1.07 k\Omega$

## Assignment - 19

Q.

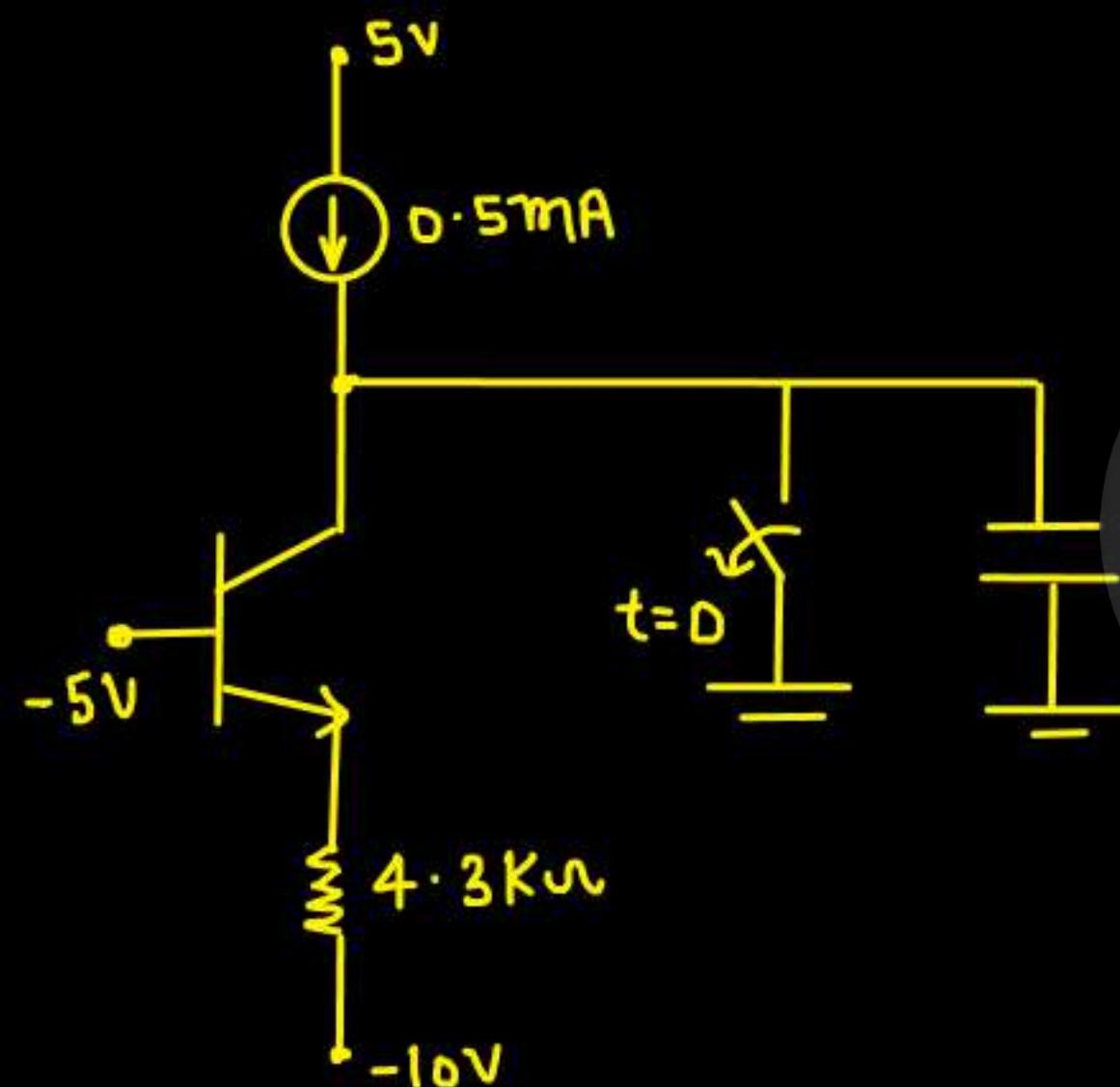


$$\beta = \infty$$

$$(V_{GE})_{ON} = 0.7V$$

$$(V_{CE})_{SAT} = 0.7V$$


The switch  $S$  is initially closed.  
At time  $t=0$ , switch is opened.

The time  $t$  at which Transistor leaves the active region.

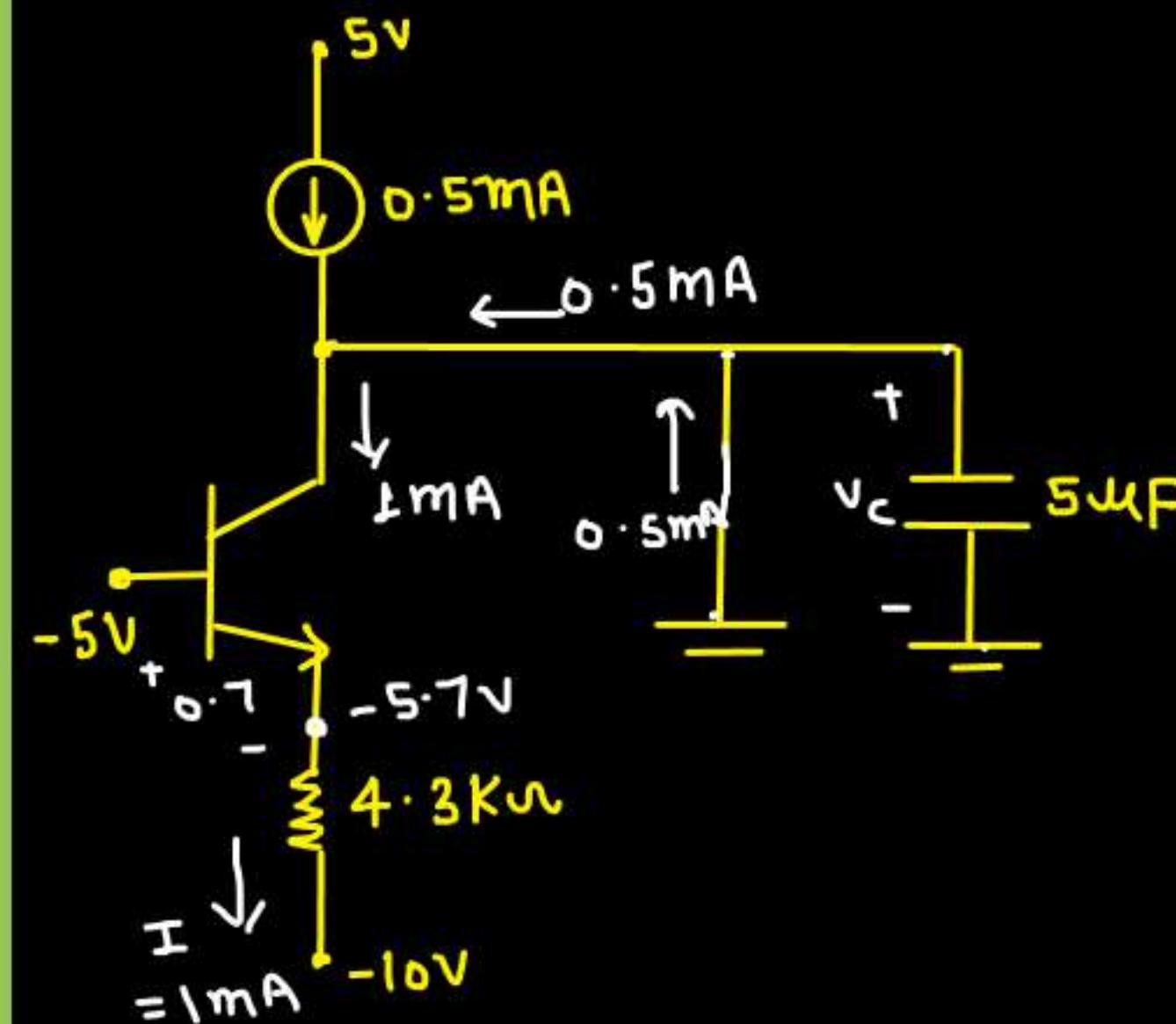For  $t < 0$  :-


$$I = \frac{-5.1 + 10}{4.3k} = 1\text{mA}$$

$$V_c(0^-) = 0\text{V}$$

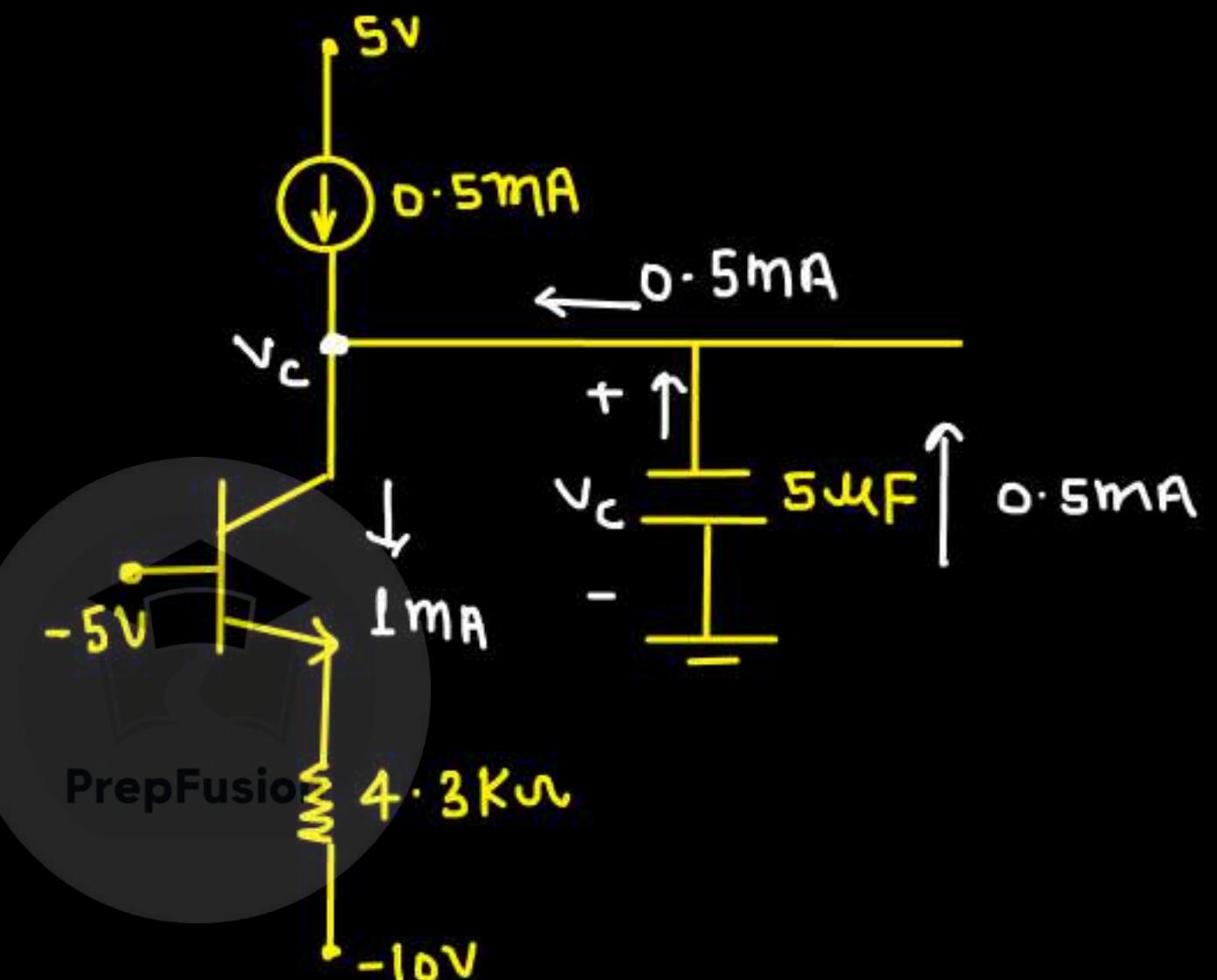For  $t > 0$  :-

$$V_c(t) = \frac{1}{5\mu} \int_0^t 0.5m \cdot dt$$

$$V_c(t) = -100t$$

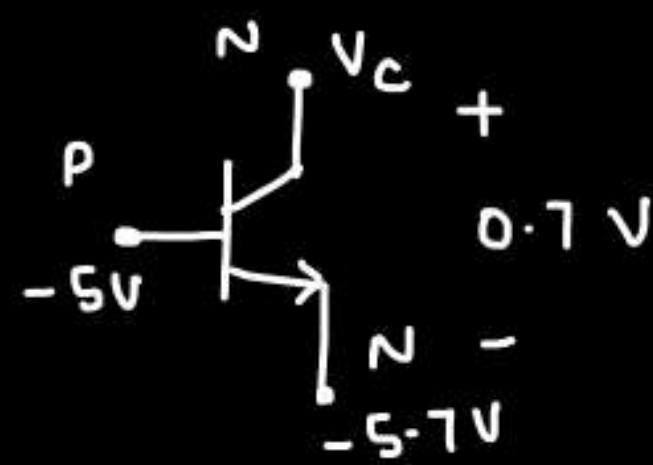

$$V_C(0^+) = 6V$$

↳ Active region of Tr

$V_C$  is going down.



Tr moving Towards saturation

Given,  $(V_{CE})_{sat} = 0.7V$

PrepFusion

$$\Rightarrow V_C - (-5.7) = 0.7$$


$V_C = -5V \rightarrow$  sat. cond'n

$$-100t = -5$$

$t = 50\text{msec}$



Q.

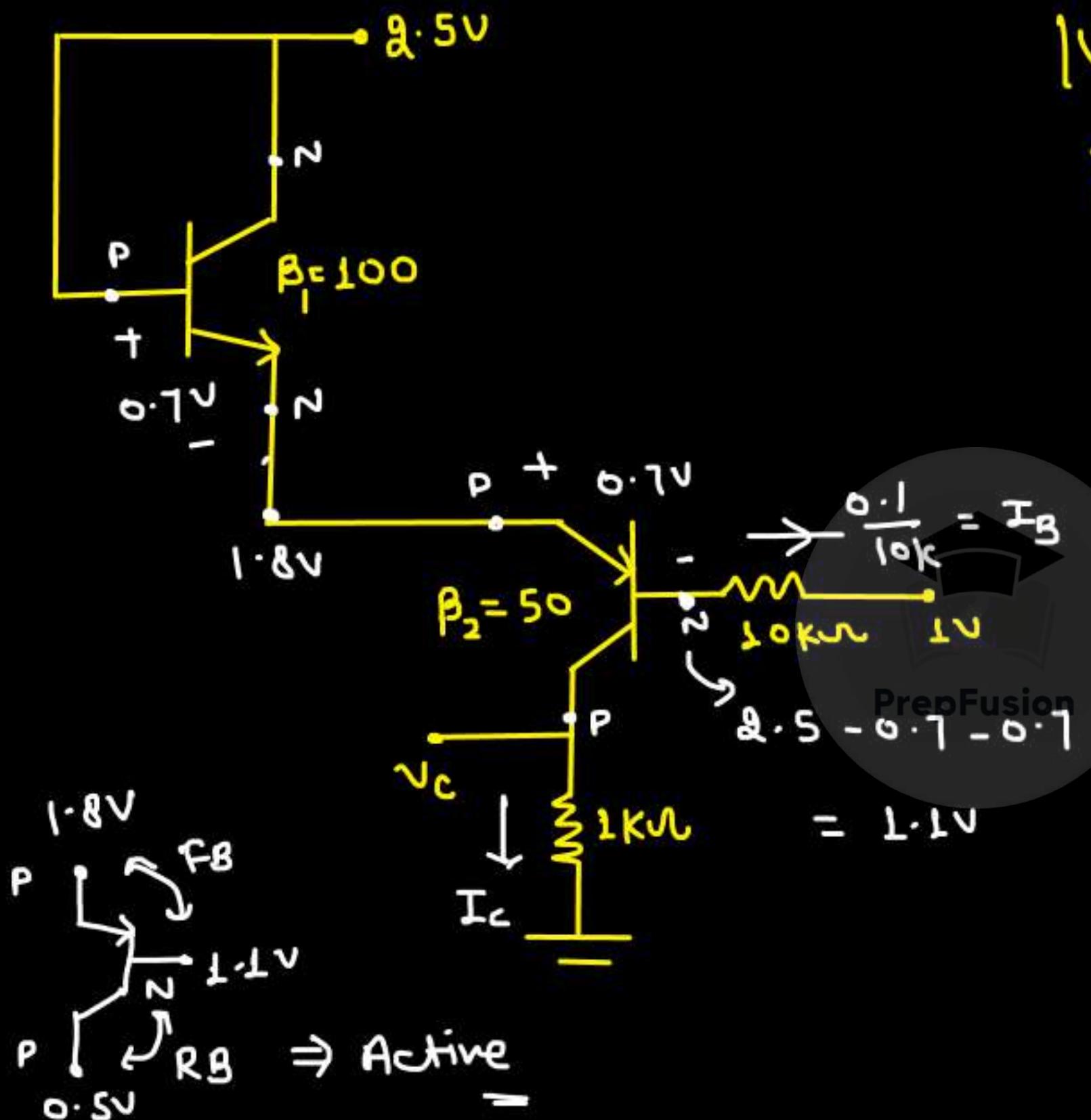

$$|V_{B\epsilon}| = 0.7V$$

Find  $v_c$ .

$$I_B = \frac{0.1}{10K}$$


$$I_B = 6.01 \text{ mA}$$

↳ Assuming active

$$V_c = I_c \times L_{k\mu} \\ = 50 \times 0.01m \times 1K$$

$$V_C = 0.5V \quad | \quad \text{Ans}$$

Q.

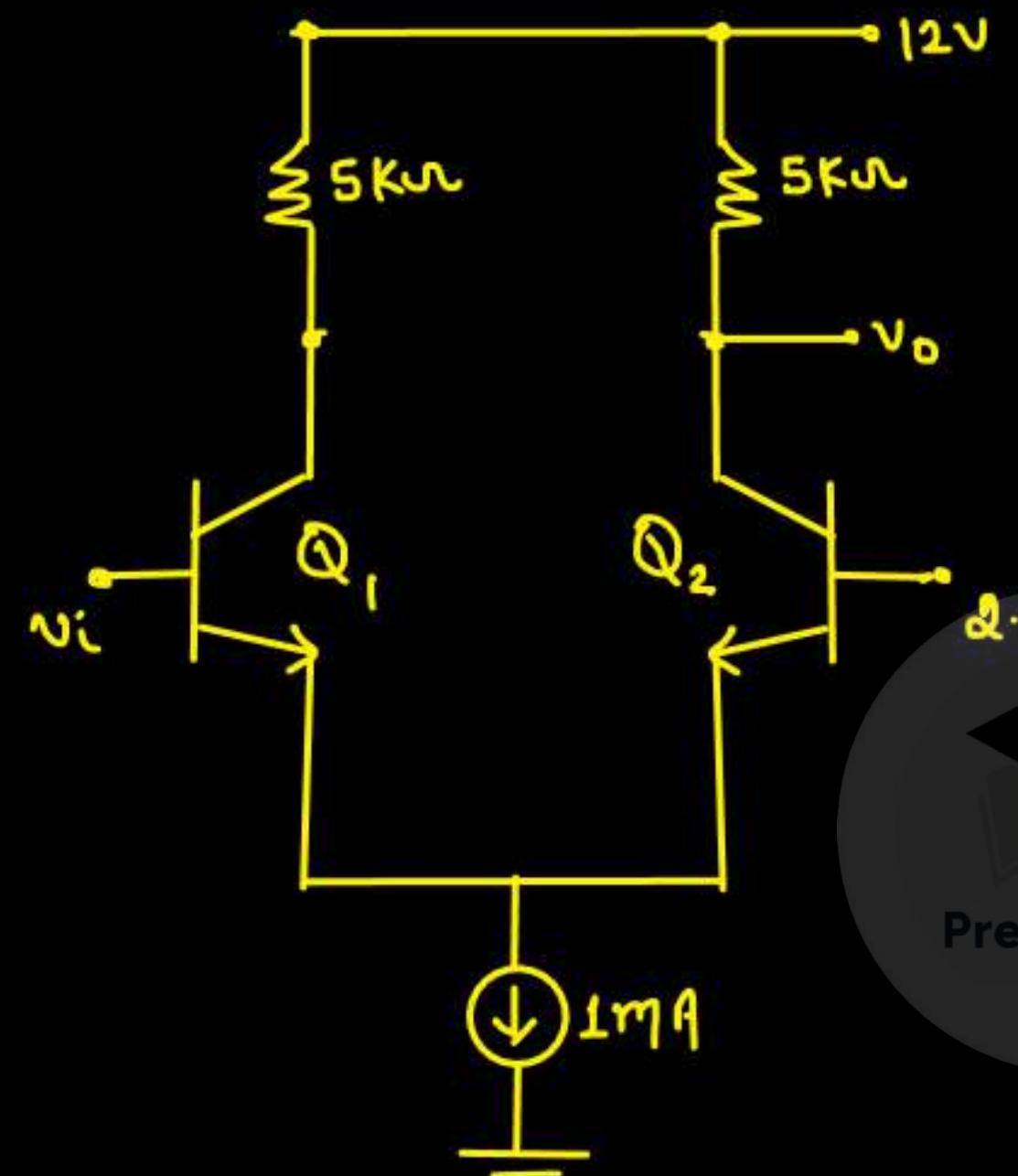

Reverse sat current  
is same. ↪


Both Transistors are matched.

$$(V_{BE})_{ON} = 0.7V, \quad \beta = 100$$

find  $V_0$  when

- (a)  $V_i = 5V$   
(b)  $V_i = 0V$

(a)  $U_i = 5V$

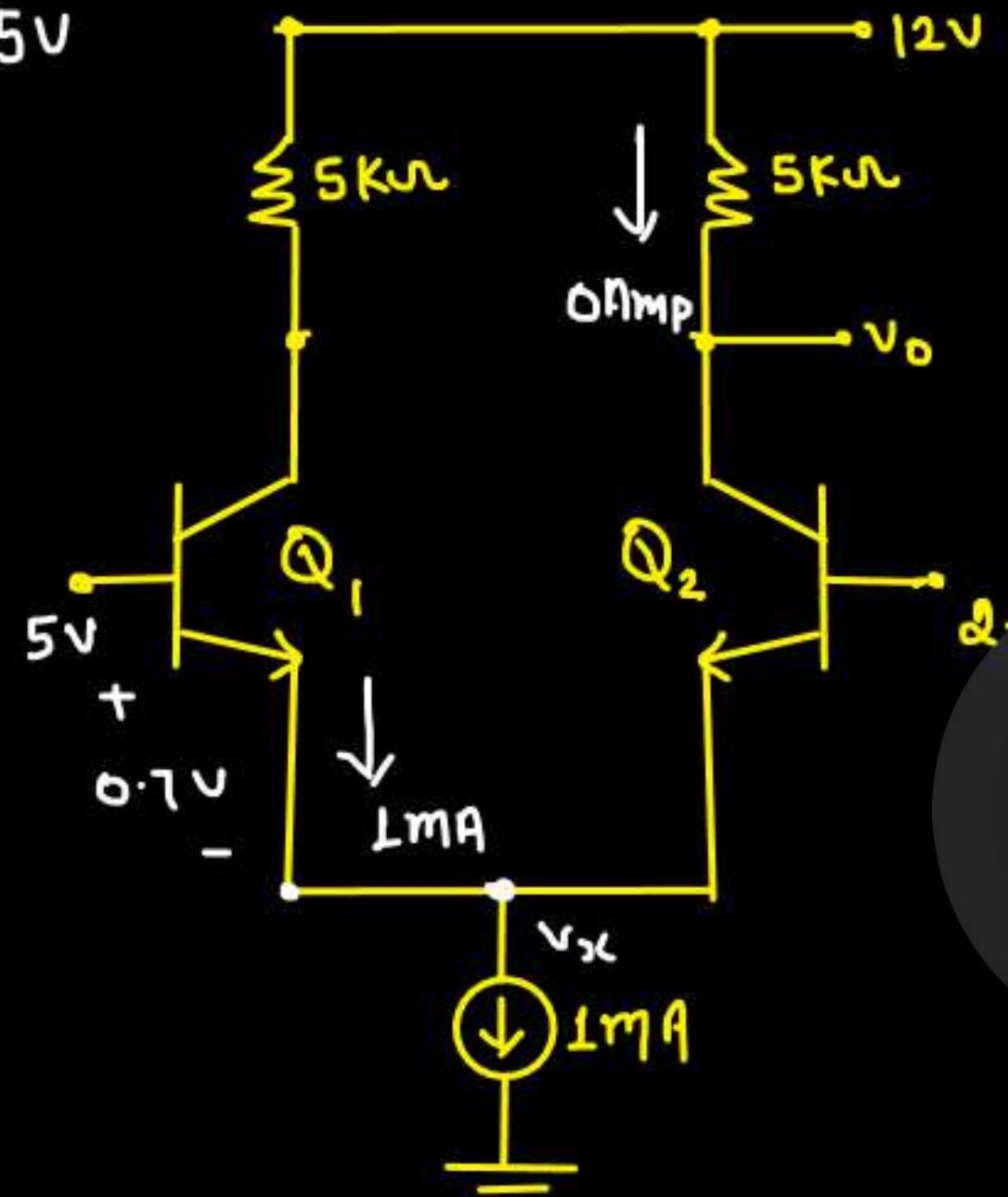

①  $Q_1, Q_2$  both ON  $\rightarrow X$


②  $Q_2$  ON      }  $\rightarrow X$   
 $Q_1$  OFF

③  $Q_1$  ON      }  $X$   
 $Q_2$  OFF

$Q_1$  ON,  $Q_2$  OFF

$$v_o = 12V$$

(b)

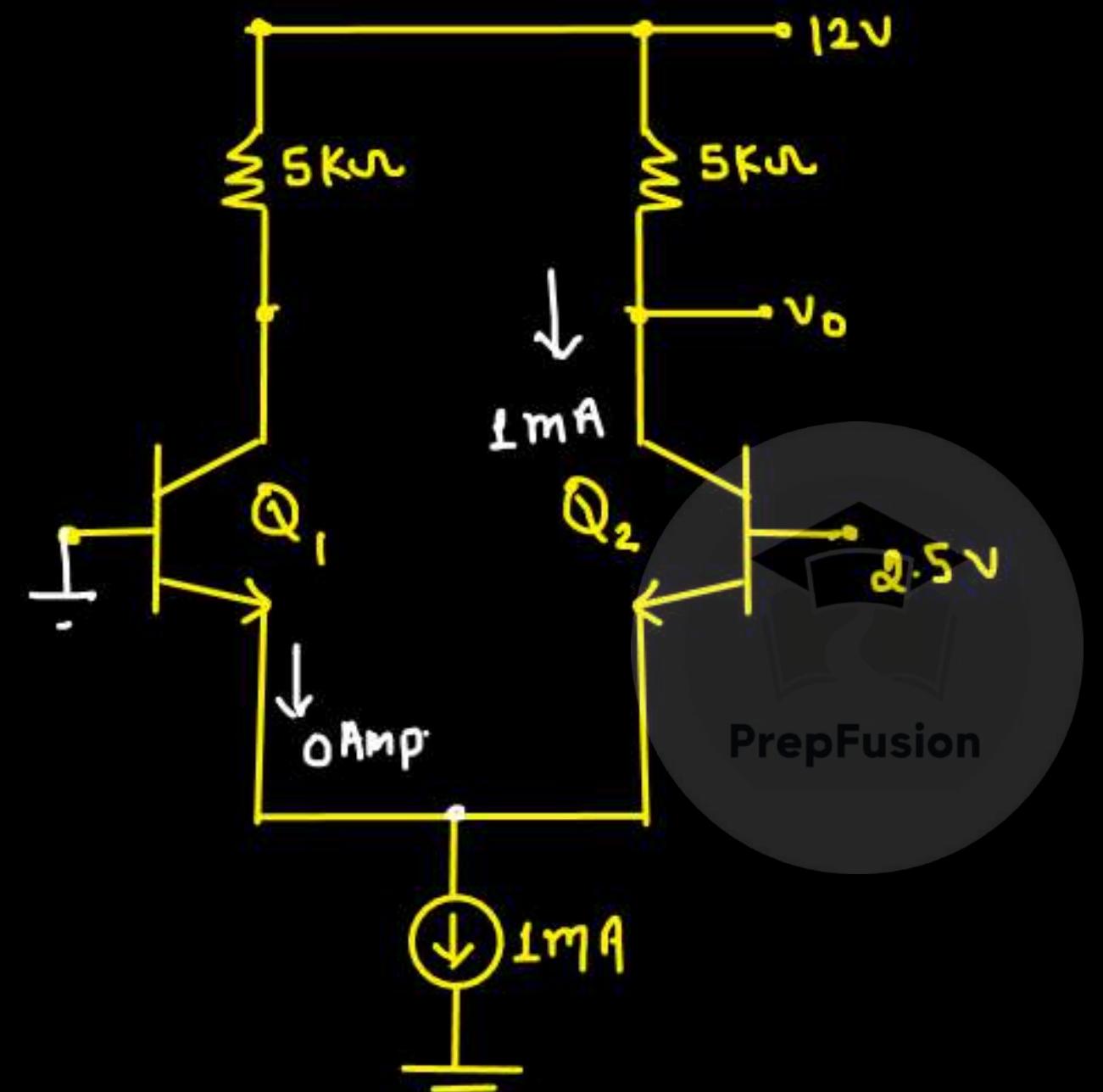

$Q_2$  ON

$Q_1$  OFF


$$V_o = 12 - 5 \times 1$$

$$V_o = 7 \text{ V}$$




Q.

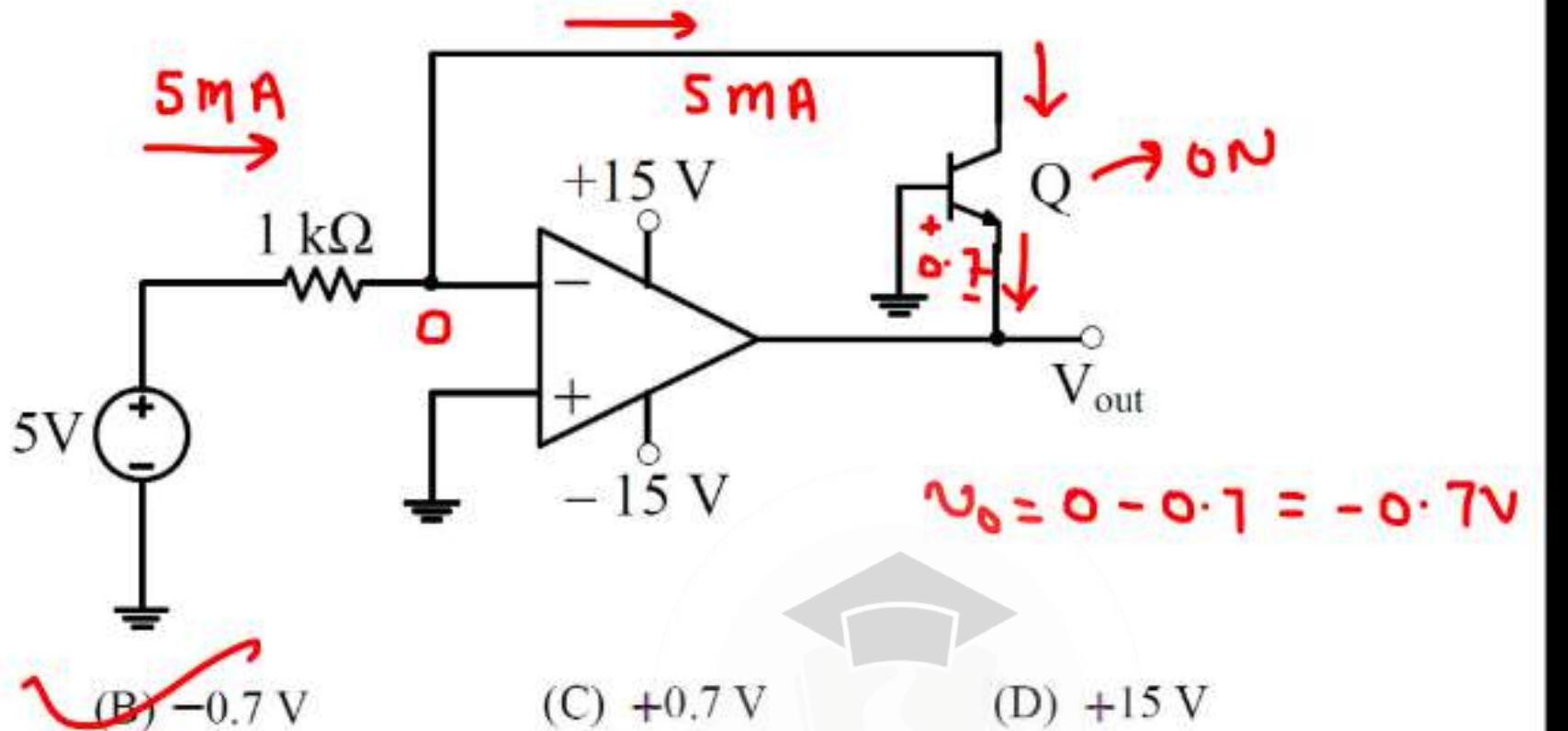
In the circuit shown below what is the output voltage ( $V_{out}$ ) if a silicon transistor Q and an ideal op-amp are used?



Q.

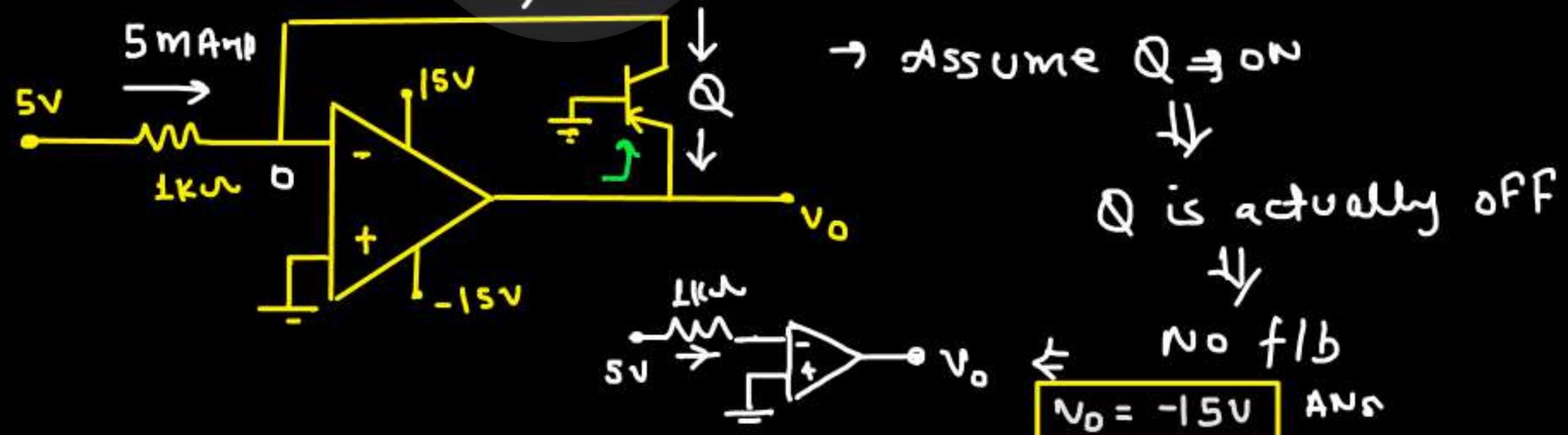

Q.  
x

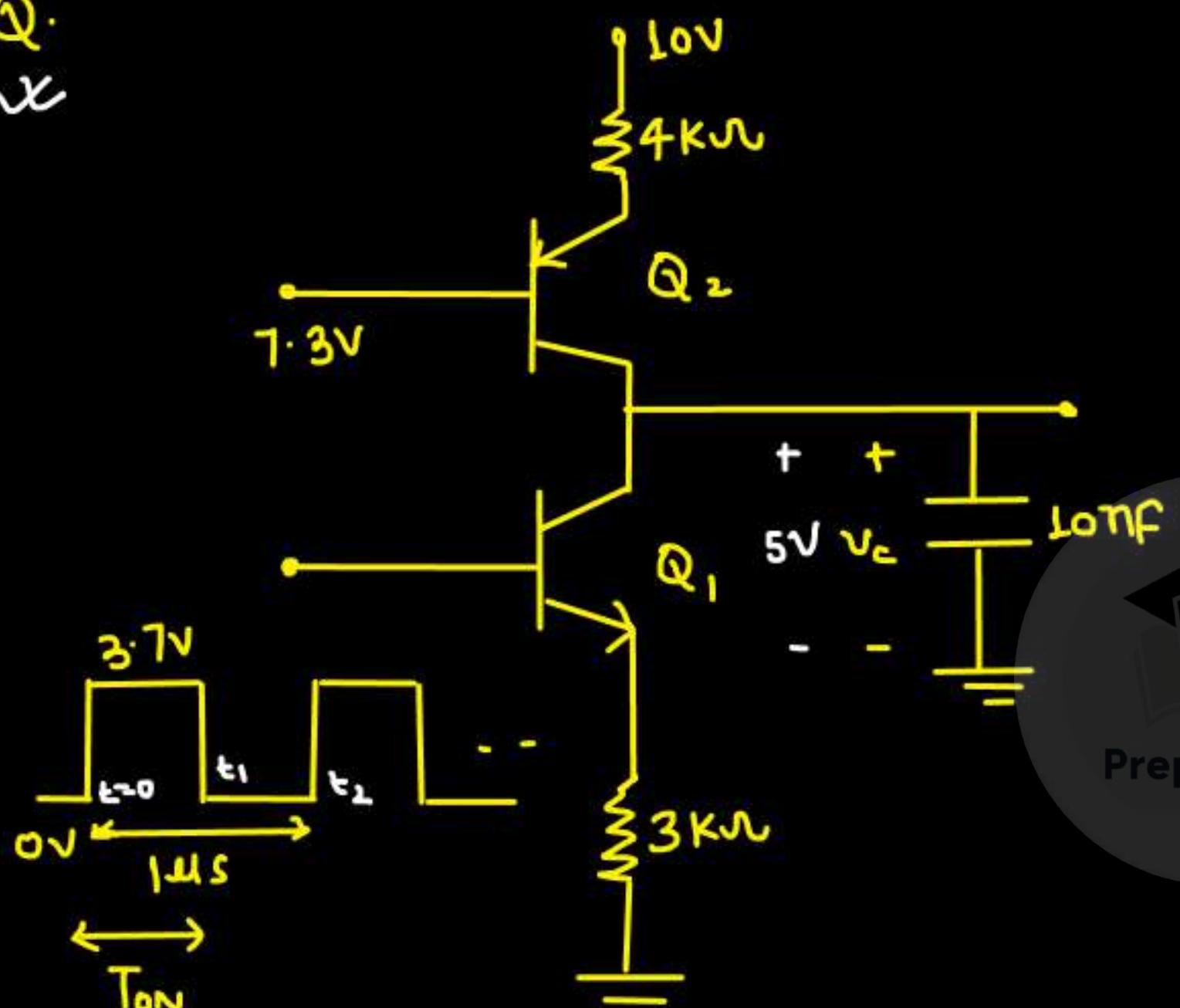

$$|V_{EB}| = 0.7V$$



capacitor is initially charged  
to 5V.

The input to Q<sub>1</sub> Transistor is  
shown.


Determine T<sub>on</sub> such that Tr.

never enter into saturation even  
after arbitrarily long time.


@  $t=0^+$

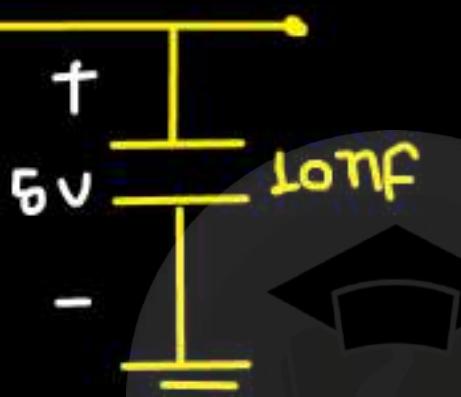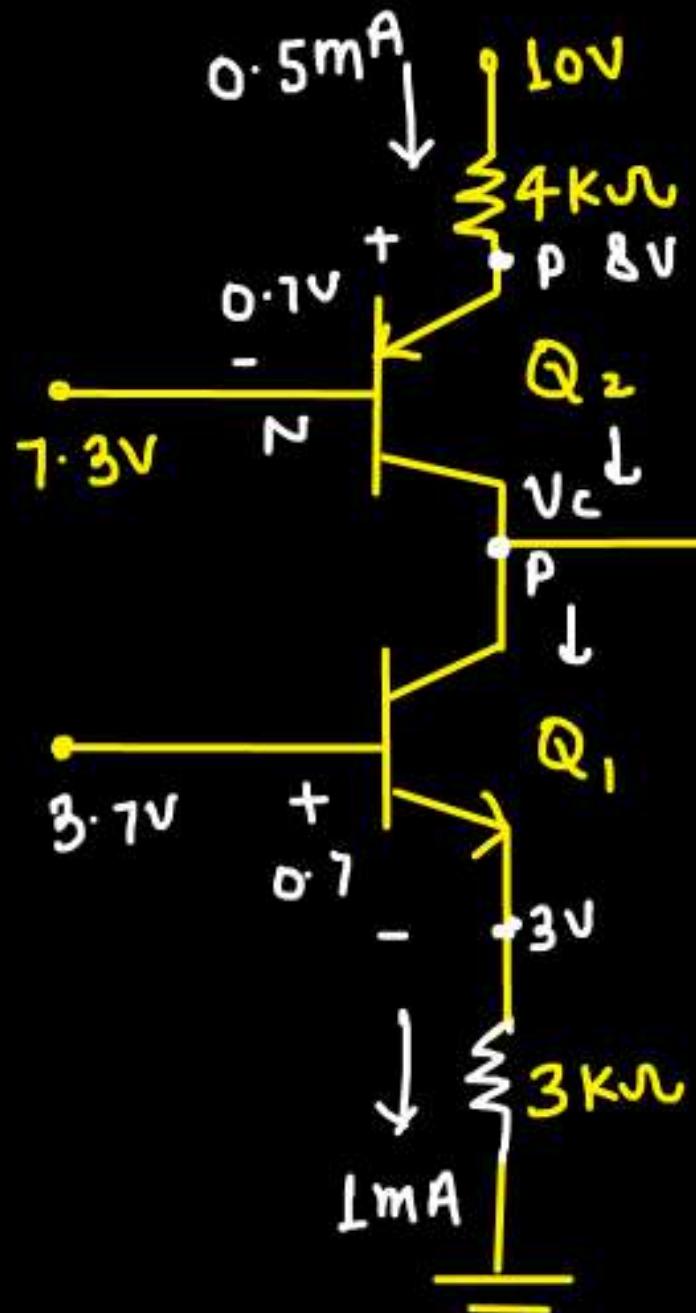


PrepFusion

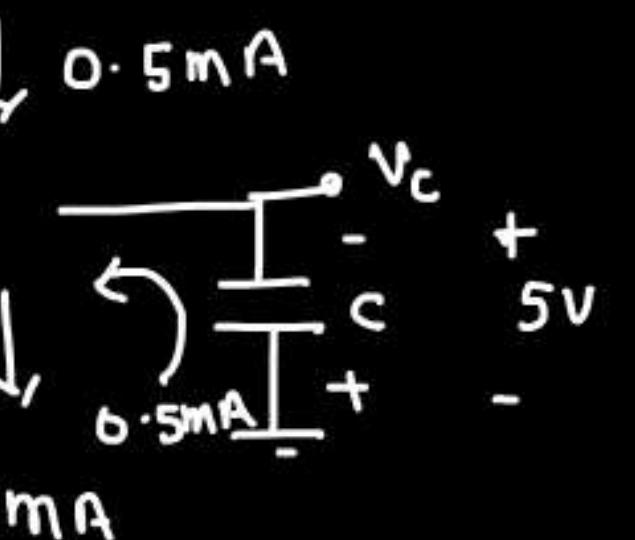


$$V_C(t) = 5 - \frac{0.5m[t]}{10n}$$

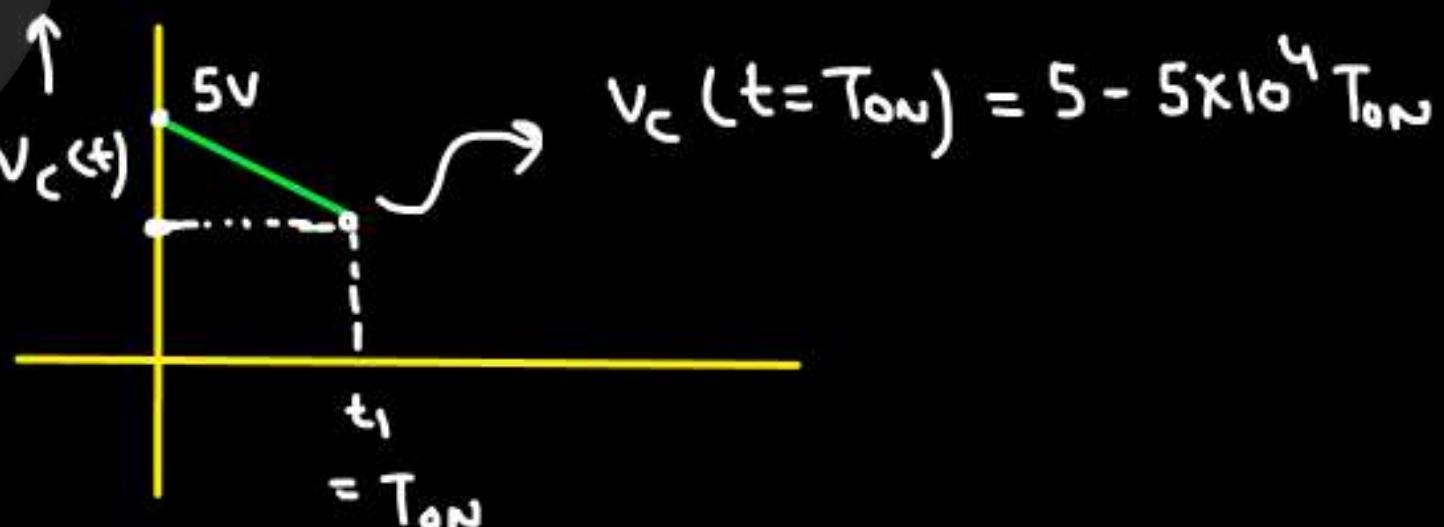
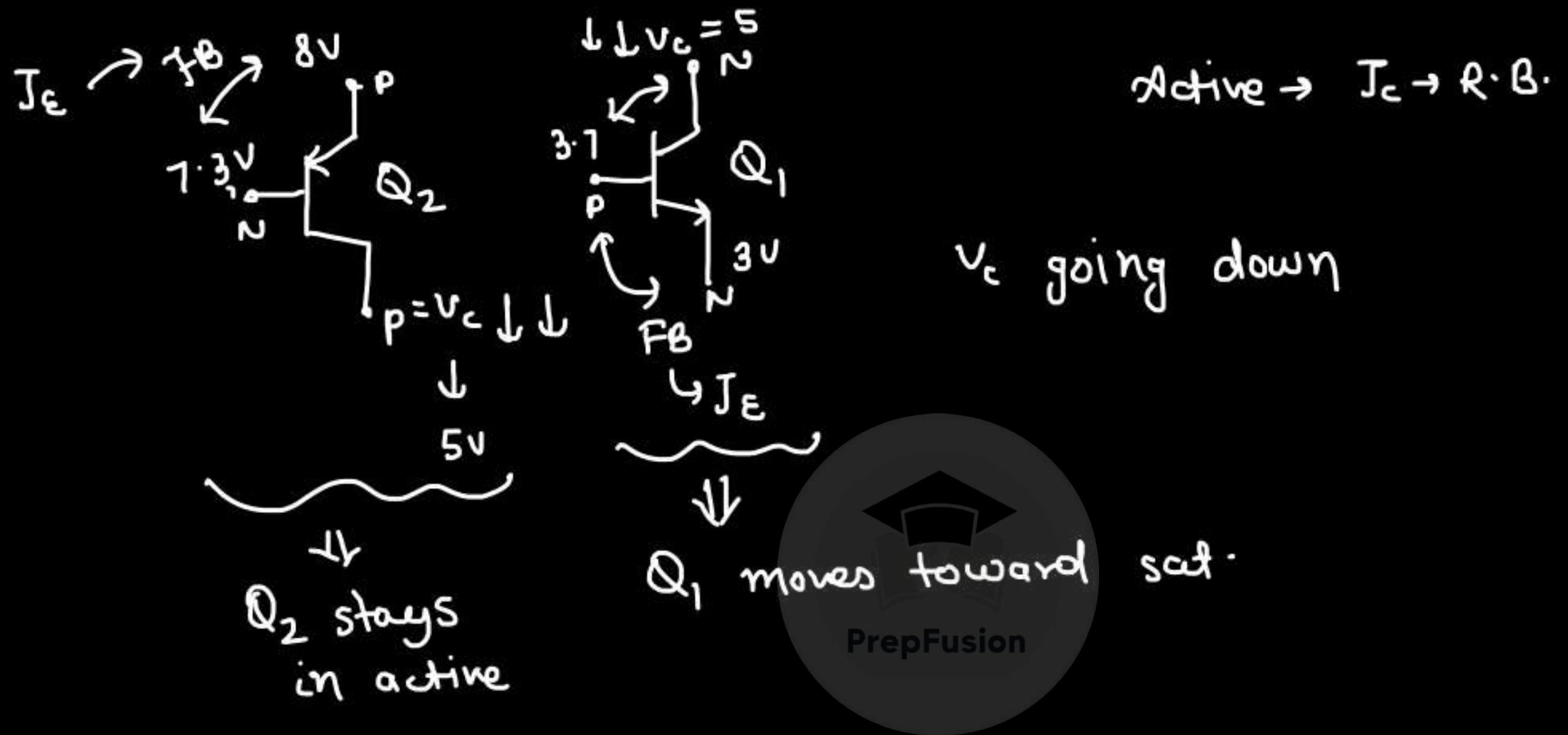
$$V_C(t=T_{ON}) = 5 - 5 \times 10^{-4} T_{ON}$$




@  $t = t_1^+$

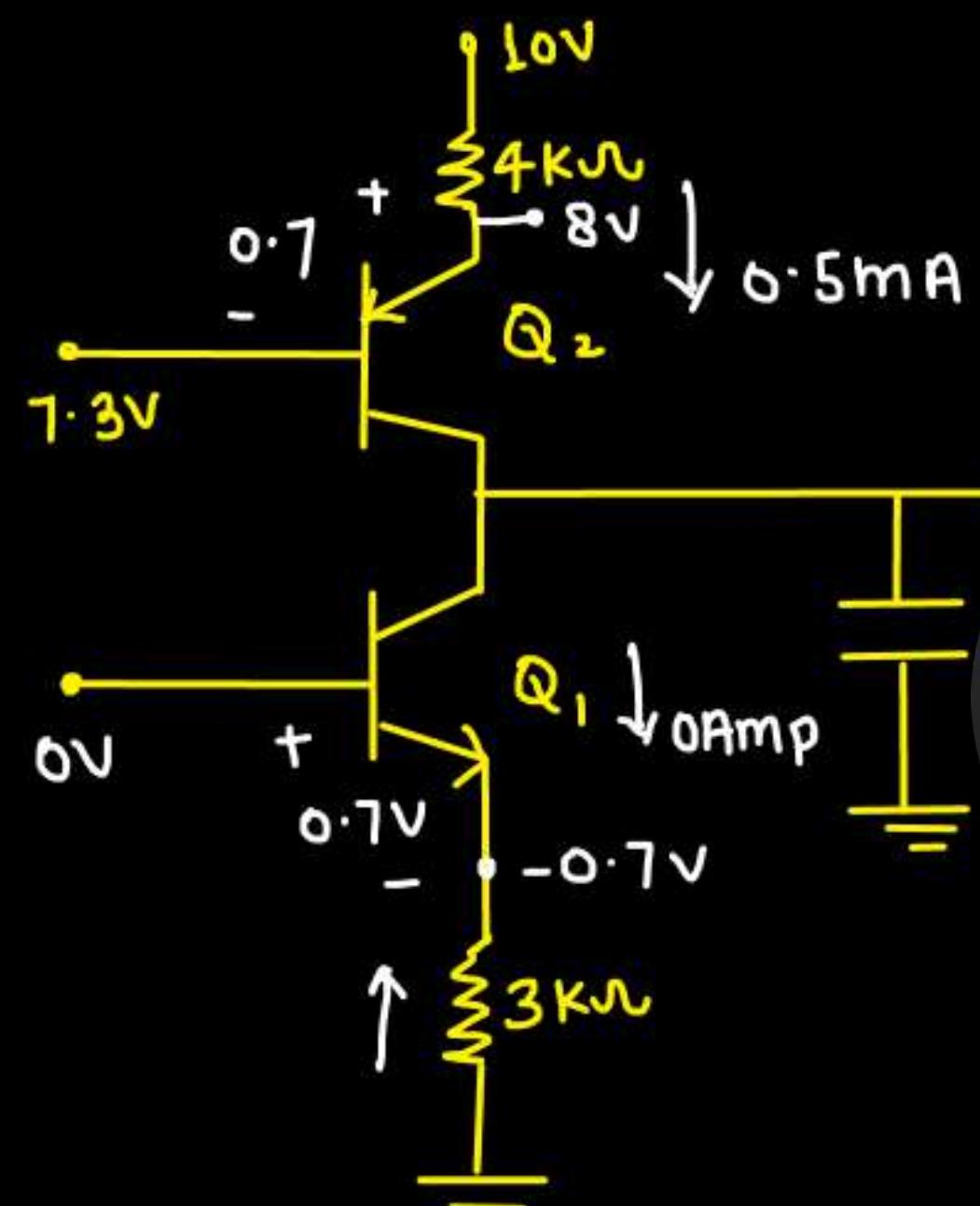


Q<sub>1</sub> is off.


↓ 0.5mA

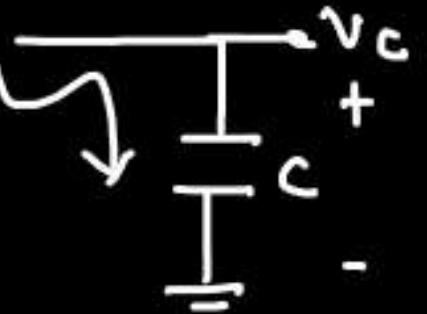


10nF 5 - 5 × 10<sup>4</sup> T<sub>ON</sub>  
PrepFusion
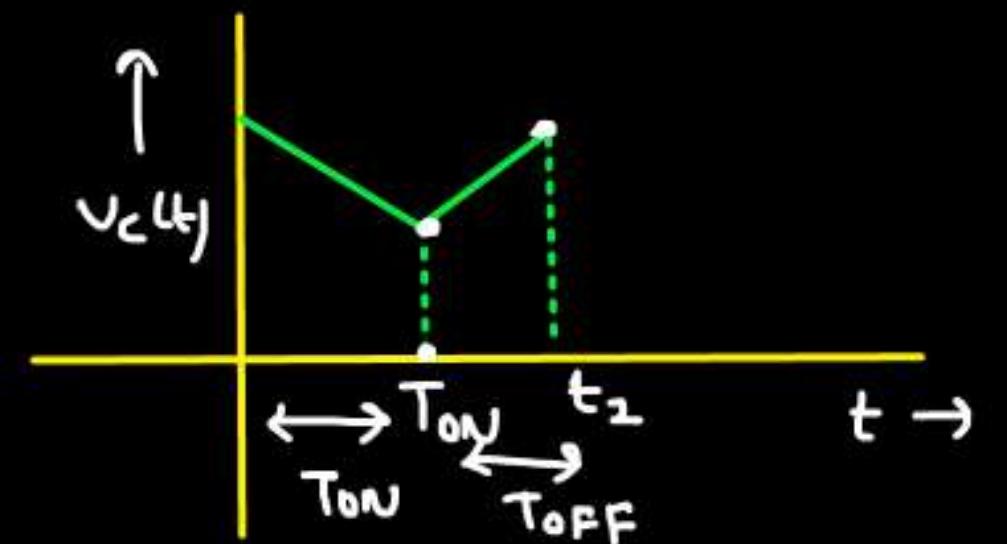
$$v_c(t) = 5 - 5 \times 10^4 T_{ON} + \frac{0.5m}{10n} (t - t_1)$$



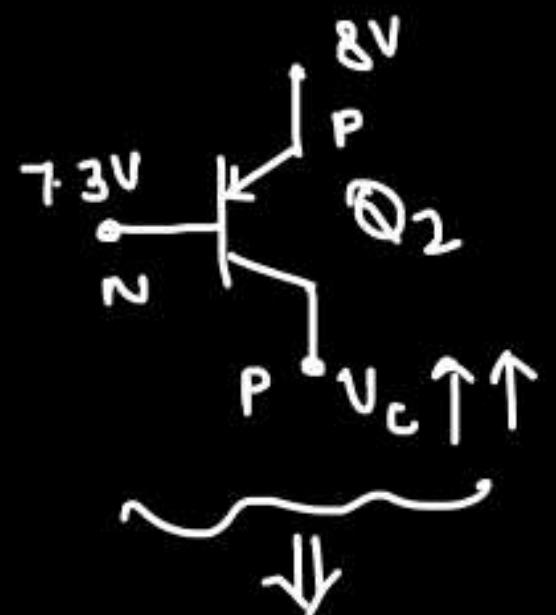


$Q_2$  moves towards set.

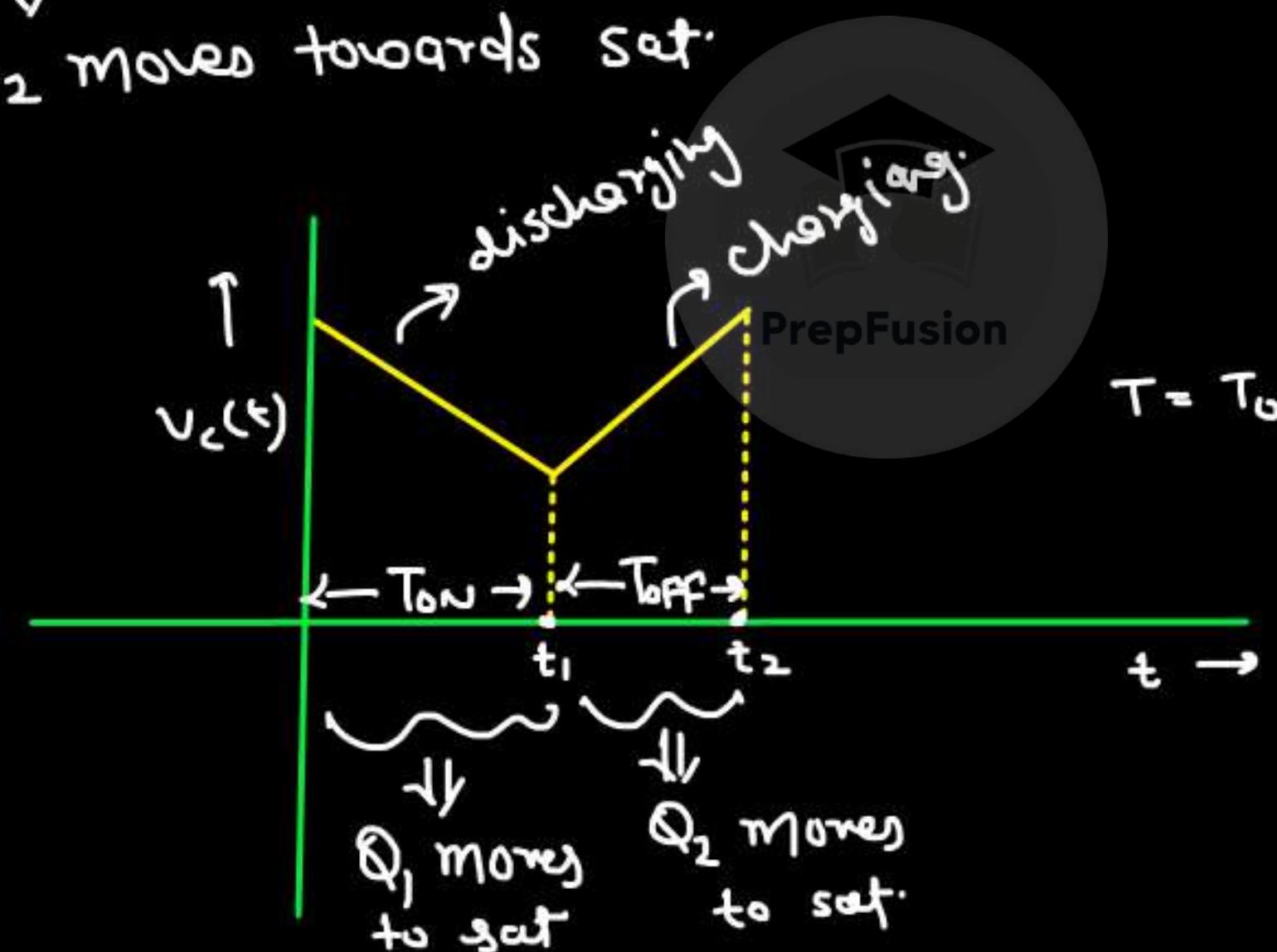


$$T = T_{ON} + T_{OFF}$$


(ii) discharging > charging

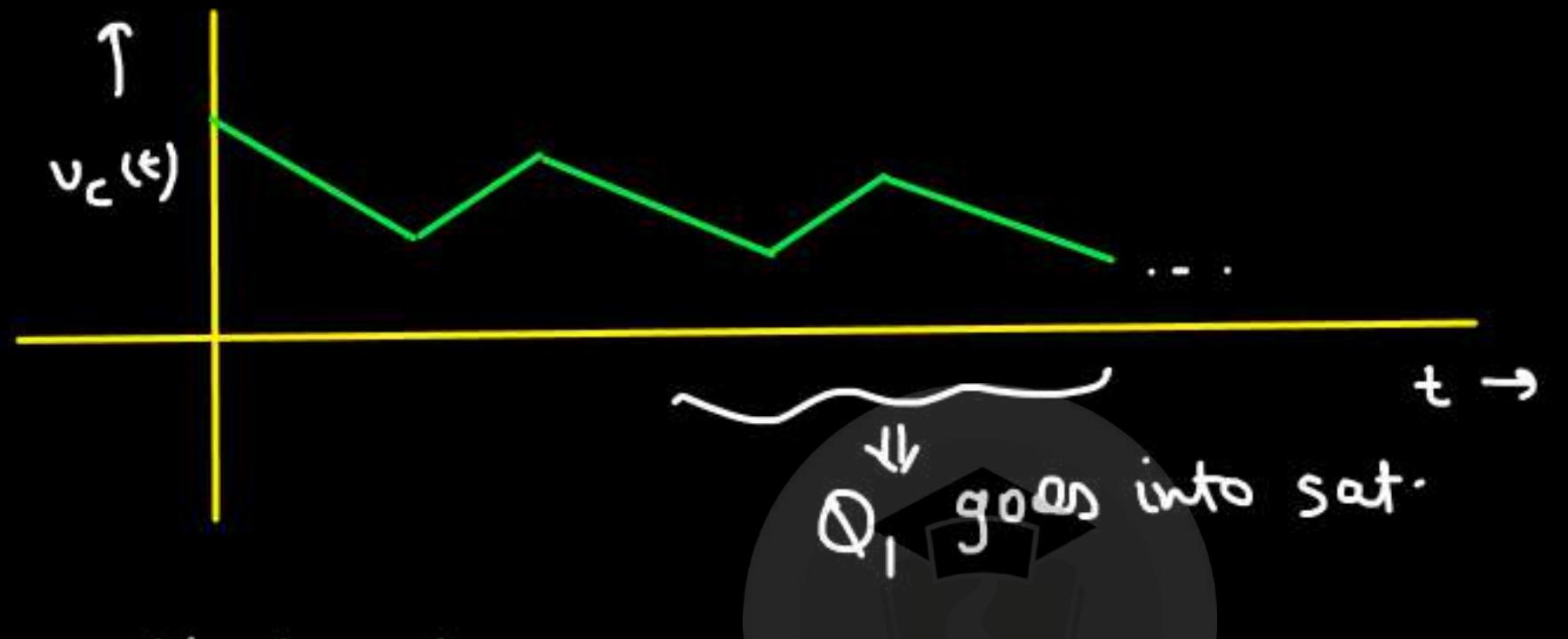

(ii) charging > discharging

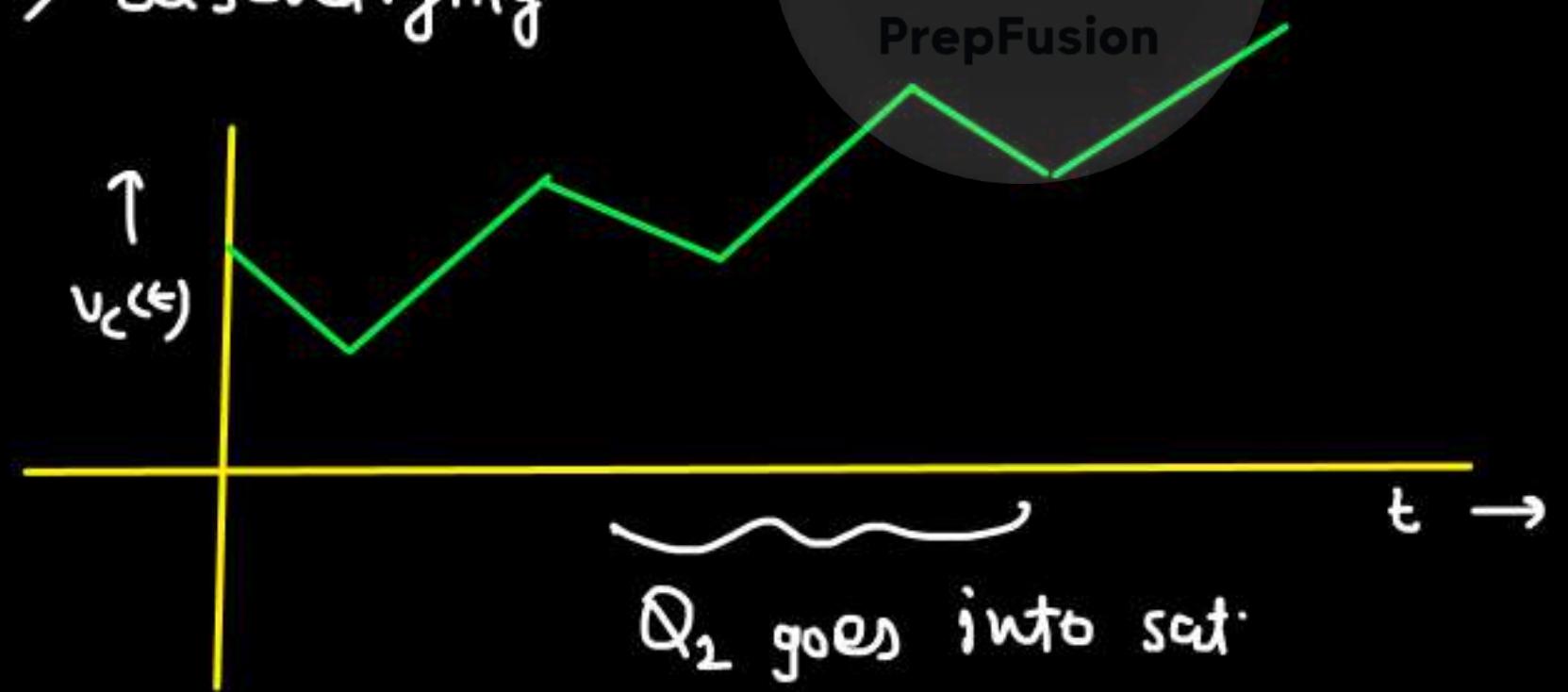

(iii) charging = discharging

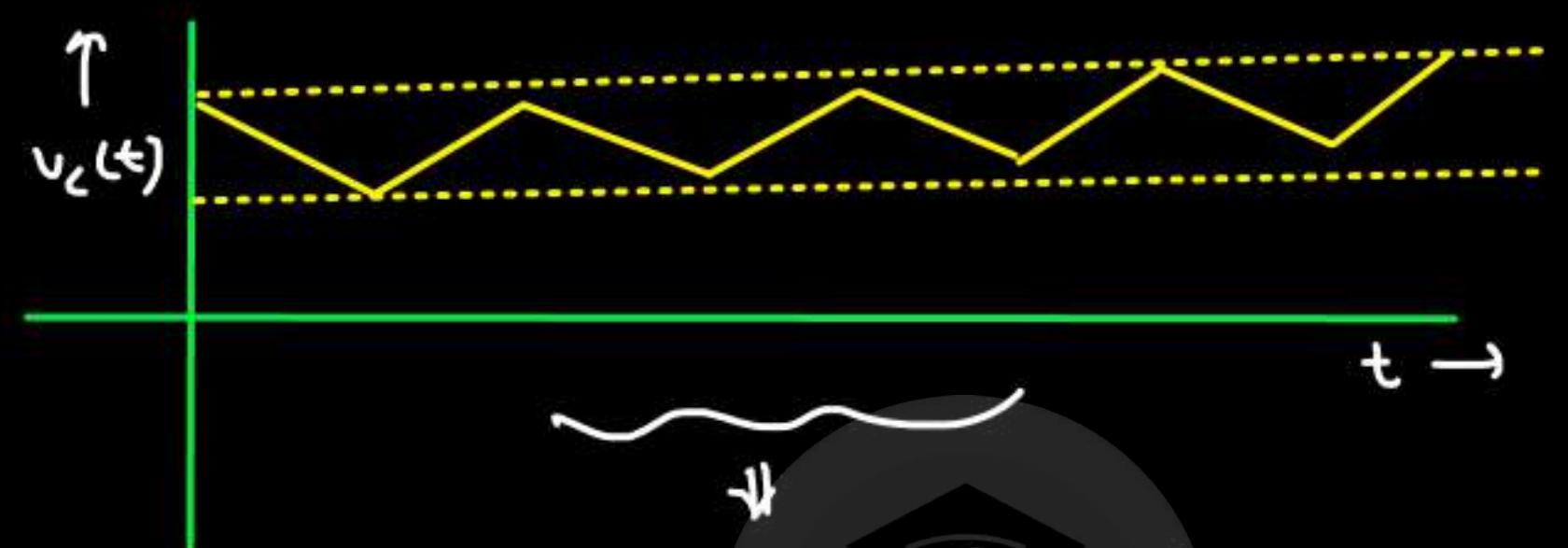


$Q_1$  and  $Q_2$  both never enter into sat.

PrepFusion

$$\frac{0.5m \times T_{OFF}}{C} = \frac{0.5m \times T_{ON}}{C} \Rightarrow T_{ON} = T_{OFF}$$

$$T = 1\text{ms}$$

$$T_{ON} = \frac{1}{2}\text{ms}$$

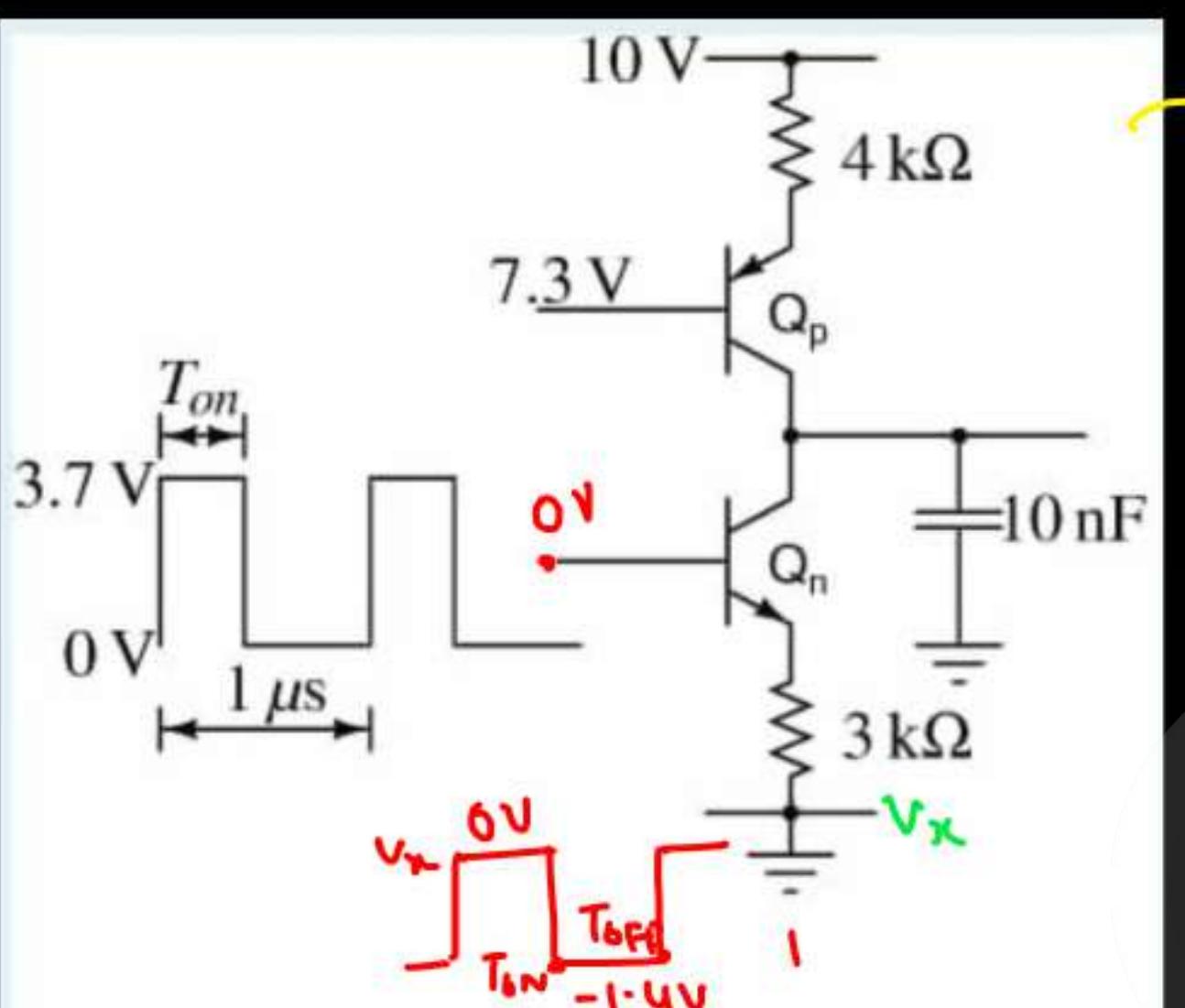

In this circuit, the  $10\text{ nF}$  capacitor is initially charged to  $5\text{ V}$ . The NPN transistor is driven with a  $1\text{ }\mu\text{s}$  period rectangular wave going from  $0$  to  $3.7\text{ V}$  and an ON duration of  $T_{on}$ . Determine  $T_{on}$  so that the transistors never leave the active region even after an arbitrarily long time. NPN and PNP transistors are active with  $V_{BE} = 0.7\text{ V}$  and  $V_{EB} = 0.7\text{ V}$ , respectively.

(The answer must be in **micro-seconds** [ $\mu\text{s}$ ]. Round off fractional answers to two decimal places.)

→ Asked in written Test

$$\rightarrow v_i = 3.7\text{ V}$$

$$0.5\text{ mA} \quad \frac{1}{T}$$

$v_i = 0\text{ V}$   
PrepFusion

$$\begin{aligned} & -6.1\text{ V} \\ & \downarrow 3\text{ k}\Omega \\ & 0.7 \quad -1.4\text{ V} \\ & \quad 3\text{ mA} \end{aligned}$$

$$\begin{aligned} & \downarrow 0.5\text{ mA} \\ & \downarrow \left(0.5 - \frac{0.7}{3}\right)\text{ mA} \\ & \downarrow \frac{0.1}{3}\text{ mA} \end{aligned}$$

$$\frac{0.5 \text{ mA} \times T_{ON}}{C} = \frac{0.8 \text{ mA}}{3} \times \frac{T_{OFF}}{C}$$

$$\frac{1.5}{0.8} T_{ON} = T_{OFF}$$

$$T = 1 \mu$$

$$T_{ON} + \frac{1.5}{8} T_{ON} = 1 \mu$$

$$T_{ON} = \frac{8}{23} \mu$$


$T_{ON} = 0.347 \mu\text{sec.}$

## Current Mirror Circuits

[Copying Current]

$$I_{S_1} = I_{S_2} = I_S$$

$$\beta_1 = \beta_2 = \beta$$

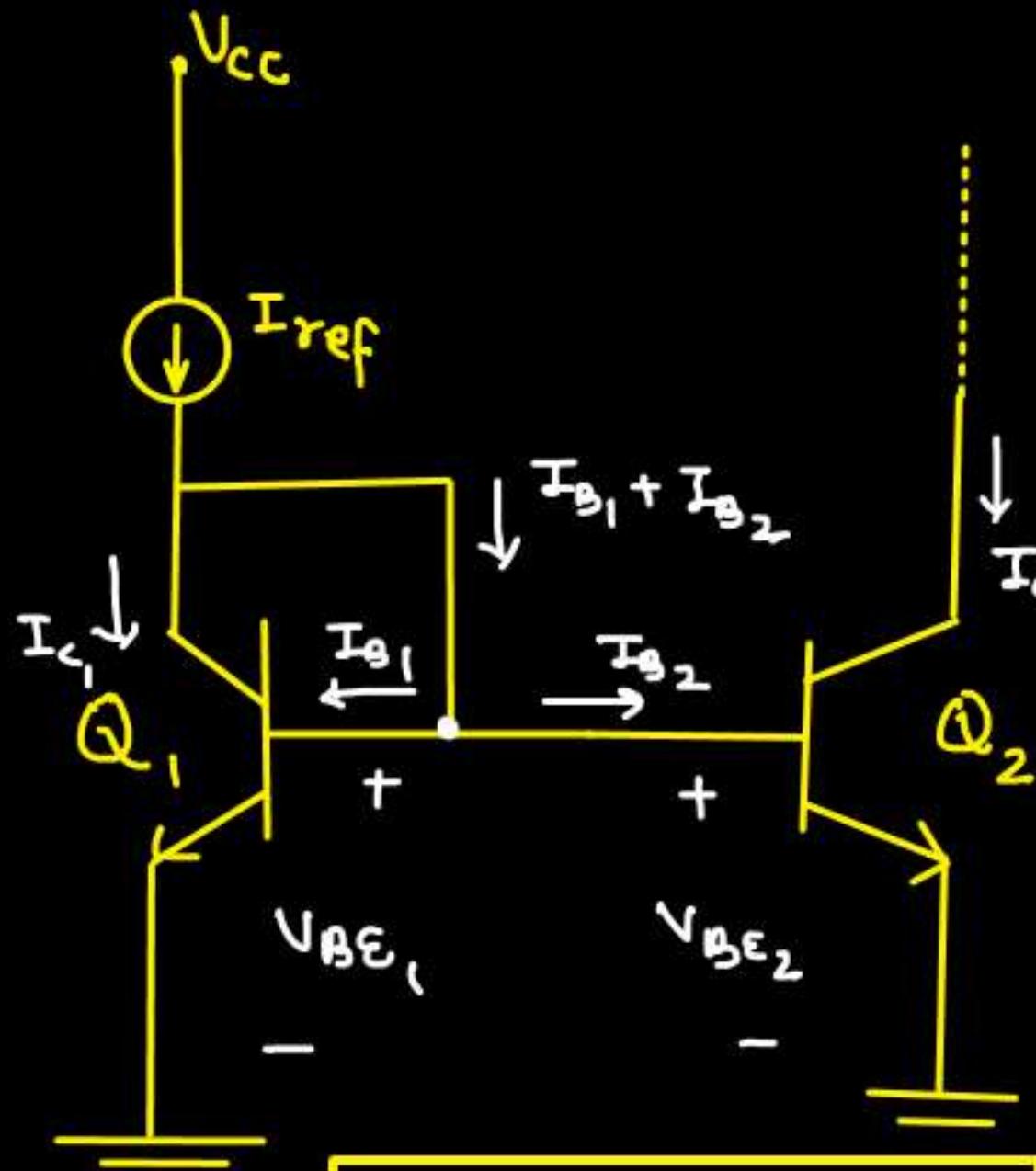

Both  $Q_1$  and  $Q_2$  are matched.

Both  $Q_1$  and  $Q_2$  are in active region

$$\{ V_A = \infty \}$$

$$I_{C_1} = I_{S_1} \exp\left(\frac{V_{B_1} \epsilon_1}{n k T}\right)$$

$$I_{C_2} = I_{out} = I_{S_2} \exp\left(\frac{V_{B_2} \epsilon_2}{n k T}\right)$$

Here  $I_{S_1} = I_{S_2}$ ,  $V_{B_1} \epsilon_1 = V_{B_2} \epsilon_2$

$$I_{C_1} = I_{C_2} = I_{out}$$

$$V_{B_1} \epsilon_1 = V_{B_2} \epsilon_2 = V_{BE}$$

$$I_{out} = I_C - \odot$$

$$I_{ref} = I_C + I_{B_1} + I_{B_2} - \odot$$

$$I_{B_1} = \frac{I_C}{\beta_1}$$

$$I_{B_2} = \frac{I_C}{\beta_2}$$

PrepFusion

↳ Here, we know  $I_C = I_2$ ,  $\beta_1 = \beta_2 = \beta$

$$\Rightarrow I_{B_1} = I_{B_2} = I_B$$

$$I_{ref} = I_C + 2 I_B$$

$$I_{ref} = I_C + 2 \frac{I_C}{\beta}$$


$$I_{ref} = \left(1 + \frac{2}{\beta}\right) I_{out}$$

$$\frac{I_{out}}{I_{ref}} = \frac{\beta}{\beta+2}$$



$$I_{out} = \left(\frac{\beta}{\beta+2}\right) I_{ref}$$

PrepFusion

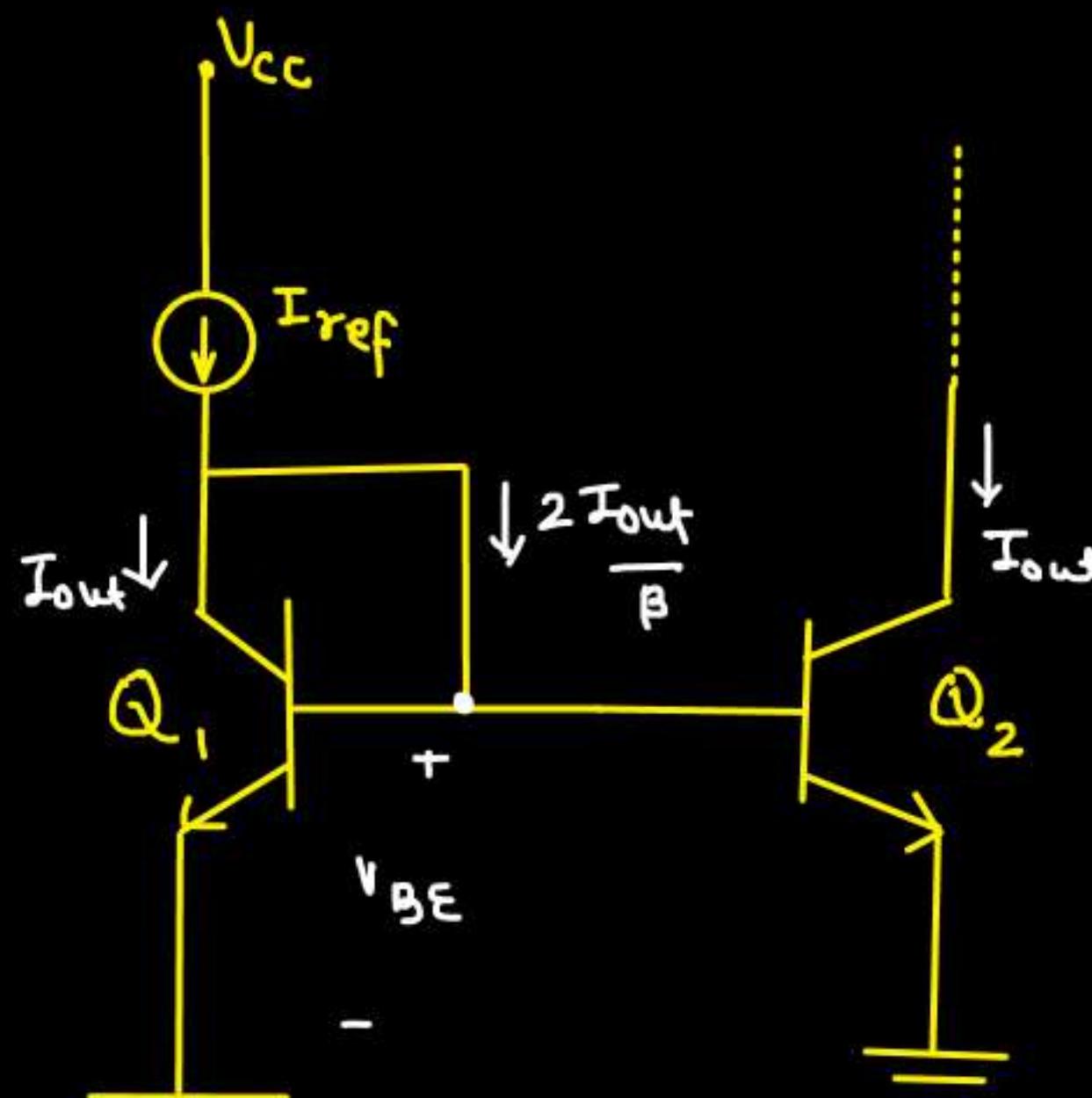

$\beta$  - Same

$I_s$  = same

both active,  $V_A = \infty$

$\beta, I_s, V_{BE}$  same }  $\Rightarrow I_c, I_B$  same

$$I_{ref} = I_{out} + \frac{2 I_{out}}{\beta}$$


$$I_{out} = \frac{\beta}{\beta + 2} I_{ref}$$

Ans



$V_{BE}$

$$I_S \propto A_Q$$

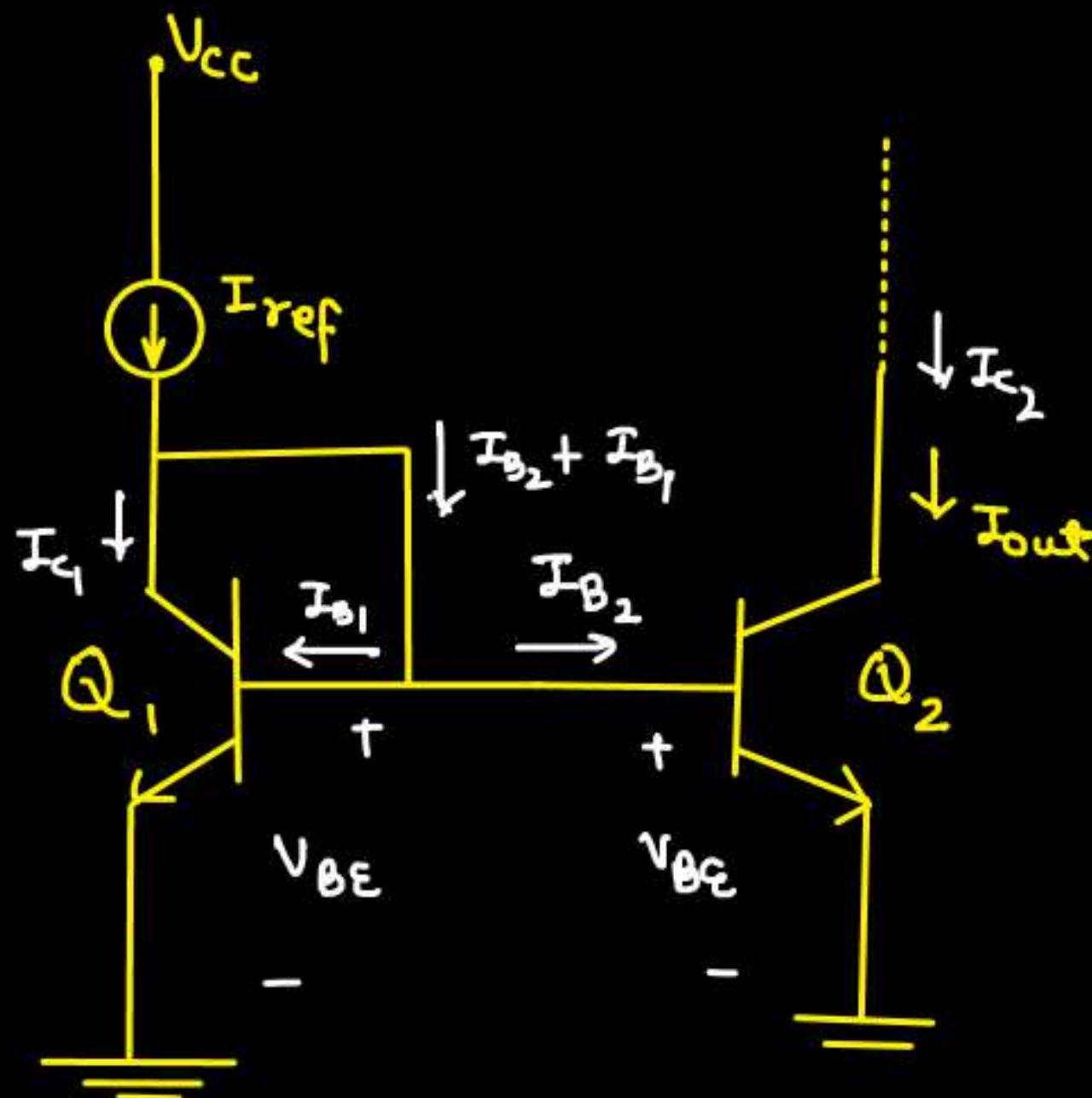

Q. Both Tr.  $Q_1$  and  $Q_2$  have  $\beta$  values of 10 and 20 respectively.

Tr.  $Q_1$  and  $Q_2$  have cross-section area of  $A_{Q_1}$  and  $A_{Q_2}$ .

PrepFusion

Given

$$\frac{A_{Q_2}}{A_{Q_1}} = 2, \beta_1 = 10, \beta_2 = 20$$

Find  $\frac{I_{out}}{I_{ref}} = ?$

$$\frac{I_{S2}}{I_{S1}} = 2 , \quad \beta_1 = 10 , \quad \beta_2 = 20$$

$$I_C1 = I_{S1} \exp\left(\frac{V_{BE}}{nV_T}\right) \quad \textcircled{1}$$

$$I_C2 = I_{S2} \exp\left(\frac{V_{BE}}{nV_T}\right) \quad \textcircled{2}$$

② ÷ ①

$$\frac{I_{C2}}{I_{C1}} = 2 \Rightarrow \boxed{I_{C2} = 2 I_{C1}}$$

$$I_{out} = 2 I_{C1}$$

$$\Rightarrow I_{ref} = I_{C1} + I_{B2} + I_{B1}$$

$$I_{ref} = I_{C1} + \frac{I_{C2}}{\beta_2} + \frac{I_{C1}}{\beta_1}$$


$$I_{ref} = \frac{I_{out}}{2} + \frac{I_{out}}{\beta_2} + \frac{I_{out}}{2\beta_1}$$


$$I_{ref} = \frac{I_{out}}{2} + \frac{I_{out}}{20} + \frac{I_{out}}{20}$$

$$I_{ref} = \frac{6}{10} I_{out}$$

$$\frac{I_{out}}{I_{ref}} = \frac{10}{6} = \text{Proportion}$$

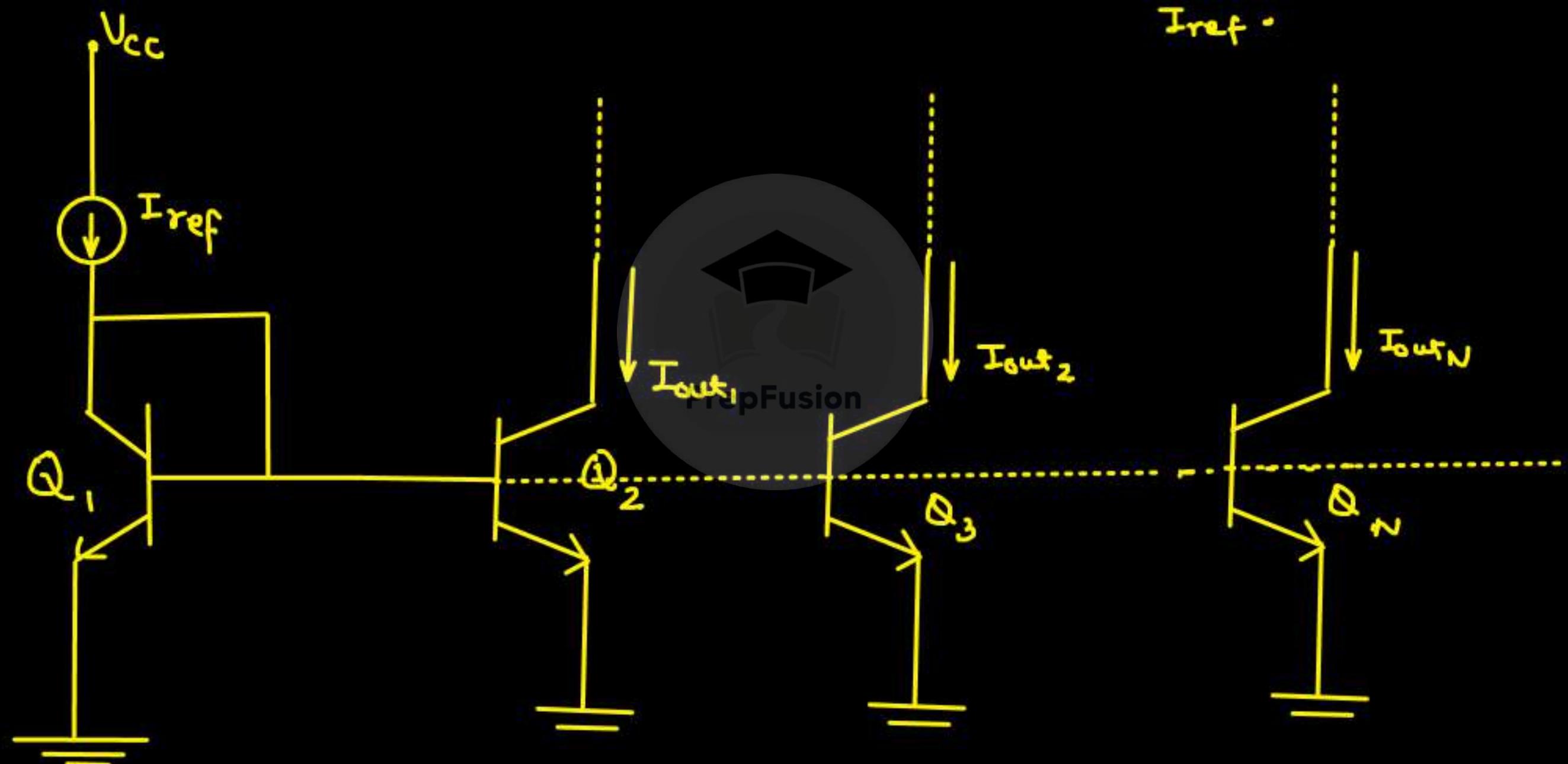Q. All the N Transistors are matched and have same  $\beta$  value. Find  $I_{out_1}$ ,  $I_{out_2}$  ---  $I_{out_N}$  in terms of  $I_{ref}$ .



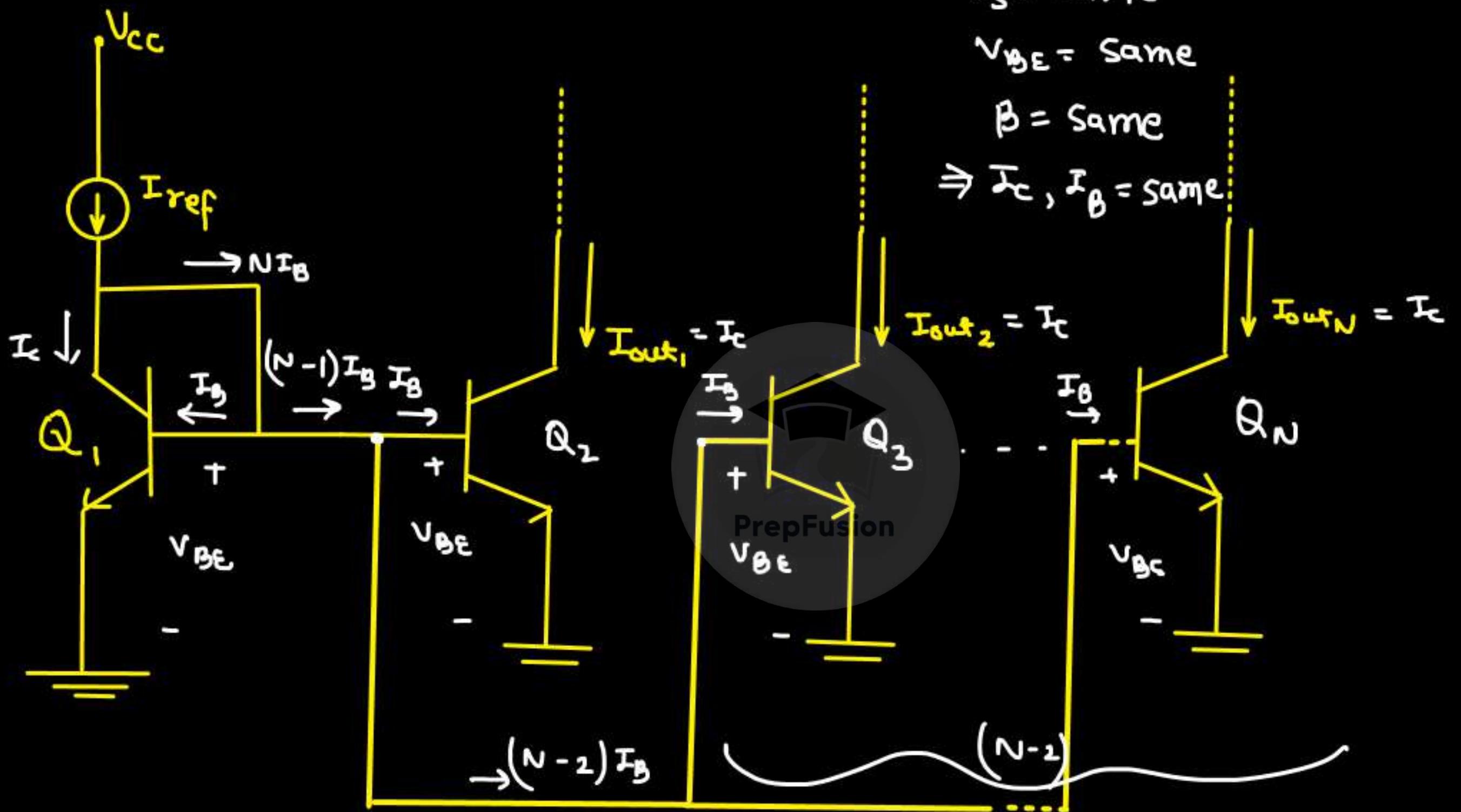

$$I_{c_1} = I_{out_1} = I_{out_2} = I_{out_3} = \dots = I_{out_N} = I_c = I_{out}$$

$$I_{ref} = I_C + N I_B$$

$$I_{ref} = I_C + \frac{N I_C}{\beta}$$


$$I_{ref} = I_{out} + \frac{N I_{out}}{\beta}$$

$$I_{out} = I_{ref} \left( \frac{\beta}{\beta + N} \right)$$

\*  $= I_{out_1} = I_{out_2} = \dots = I_{out_N}$

PrepFusion  
if  $\beta = \infty$
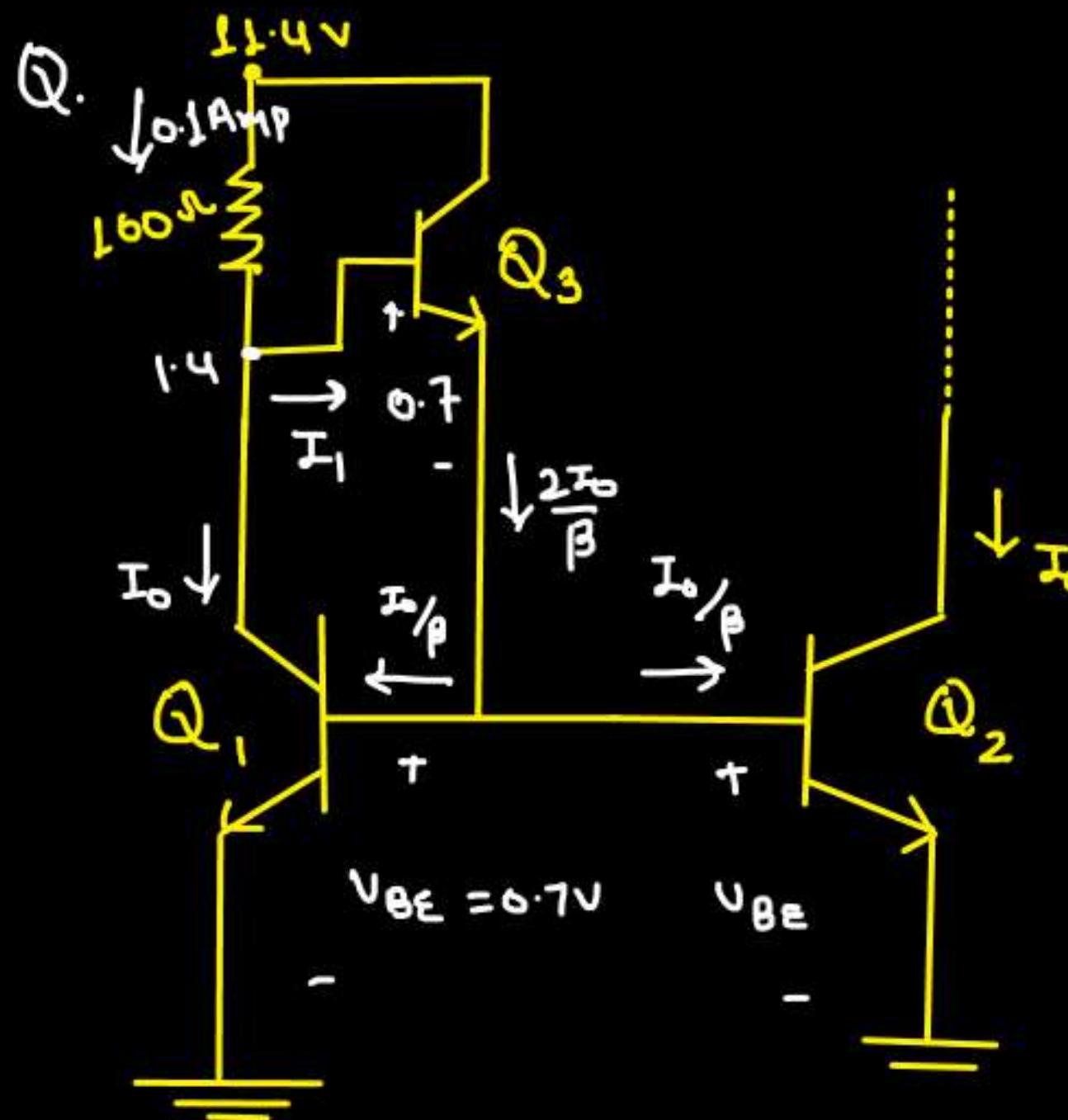
$$I_{out} = I_{ref} = I_{out_1} = I_{out_2} = \dots = I_{out_N}$$



Tr. Q<sub>1</sub> and Q<sub>2</sub> are matched.

All Tr. are working in active mode.

$$\beta_1 = \beta_2 = 100 ; \beta_3 = 99$$

$$(V_{BE})_{ON} = 0.7$$

Find  $I_0 = ?$

PrepFusion

↳ For Q<sub>1</sub> and Q<sub>2</sub>

$V_{BE}$  same,  $I_S$  same,  $\beta$  same

$\Rightarrow I_c, I_B$  same

$$I_{c1} = I_{c2} = I_c$$

$$I_{B1} = I_{B2} = I_B$$

$$I_1 = I_{B3} = \frac{I_{E3}}{\beta_3 + 1} = \frac{2I_0}{\beta(\beta_3 + 1)}$$

$$0.1 \text{ Amp} = I_0 + I_1$$


$$0.1 = I_0 + \frac{2I_0}{\beta(\beta_3 + L)}$$

$$0.1 = I_0 \left[ 1 + \frac{2}{100 \times 100} \right]$$

$I_0 = 99.98 \text{ mAmp}$

PrepFusion

Q.

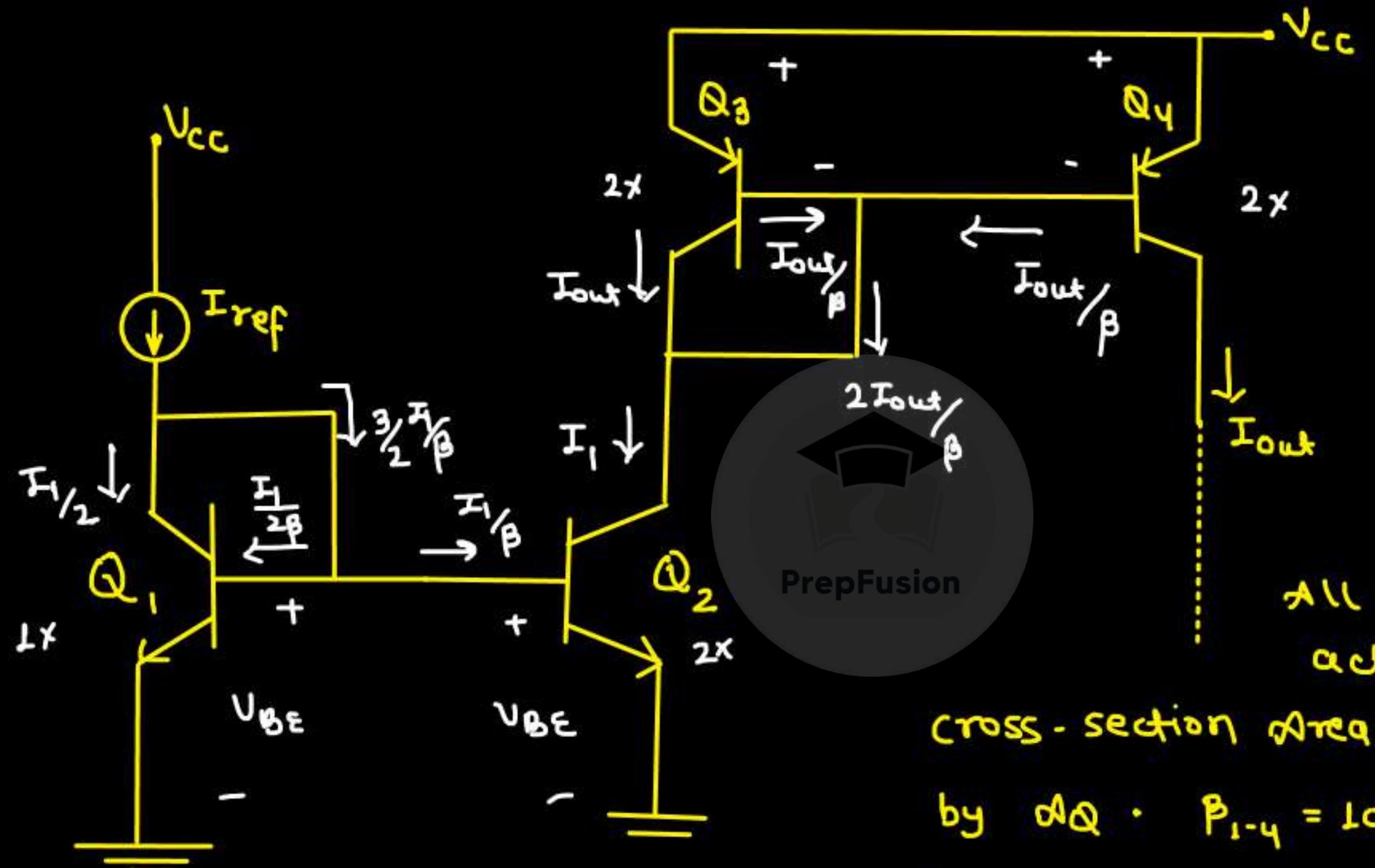

All Tr. are working in active mode of operation.  
cross-section area of Tr is shown

$$\text{by } A_Q \cdot \beta_{1-4} = 100$$

$$A_{Q_2} = 2A_{Q_1}, \quad A_{Q_3} = A_{Q_2} - A_{Q_4}$$

Find  $\frac{I_{out}}{I_{ref}}$ .

For  $Q_3$  and  $Q_4$

$$\Delta Q_3 = \Delta Q_4 \Rightarrow I_{S3} = I_{S4}$$

$$V_{EB3} = V_{EB4}$$

$$\beta_3 = \beta_4$$

$$\Rightarrow I_{C3} = I_{C4} = I_{out} \quad \left. \begin{array}{l} \\ I_{B3} = I_{B4} = I_{out}/\beta \end{array} \right\} - \textcircled{1}$$

$$\Rightarrow I_1 = I_{out} + 2 \frac{I_{out}}{\beta} - \textcircled{2}$$

↳  $I_1 = I_2 = I_{S2} \exp(V_{BE2}/V_T)$

$$I_1 = I_{S1} \exp(V_{BE1}/V_T)$$

$$\frac{\Delta Q_2}{\Delta Q_1} = 2 = \frac{I_{S2}}{I_{S1}}$$

$$\frac{I_{C_2}}{I_{C_1}} = 2$$

$$I_1 = 2I_{C_1}$$

$$I_4 = I_1 / 2$$

$$I_{ref} = \frac{I_1}{2} + \frac{3}{2} \frac{I_1}{\beta}$$

$$I_{ref} = \left( \frac{1}{2} + \frac{3}{2\beta} \right) \left( I_{out} + 2 \frac{\bar{I}_{out}}{\beta} \right) \quad \{ \text{By eqn ②} \}$$

$$I_{ref} = \left[ \frac{\beta + 3}{2\beta} \right] \left( \frac{\beta + 2}{\beta} \right) I_{out}$$


$$I_{ref} = \frac{103}{200} \times \frac{102}{100} \bar{I}_{out}$$

$$\frac{I_{out}}{I_{ref}} = 1.90$$
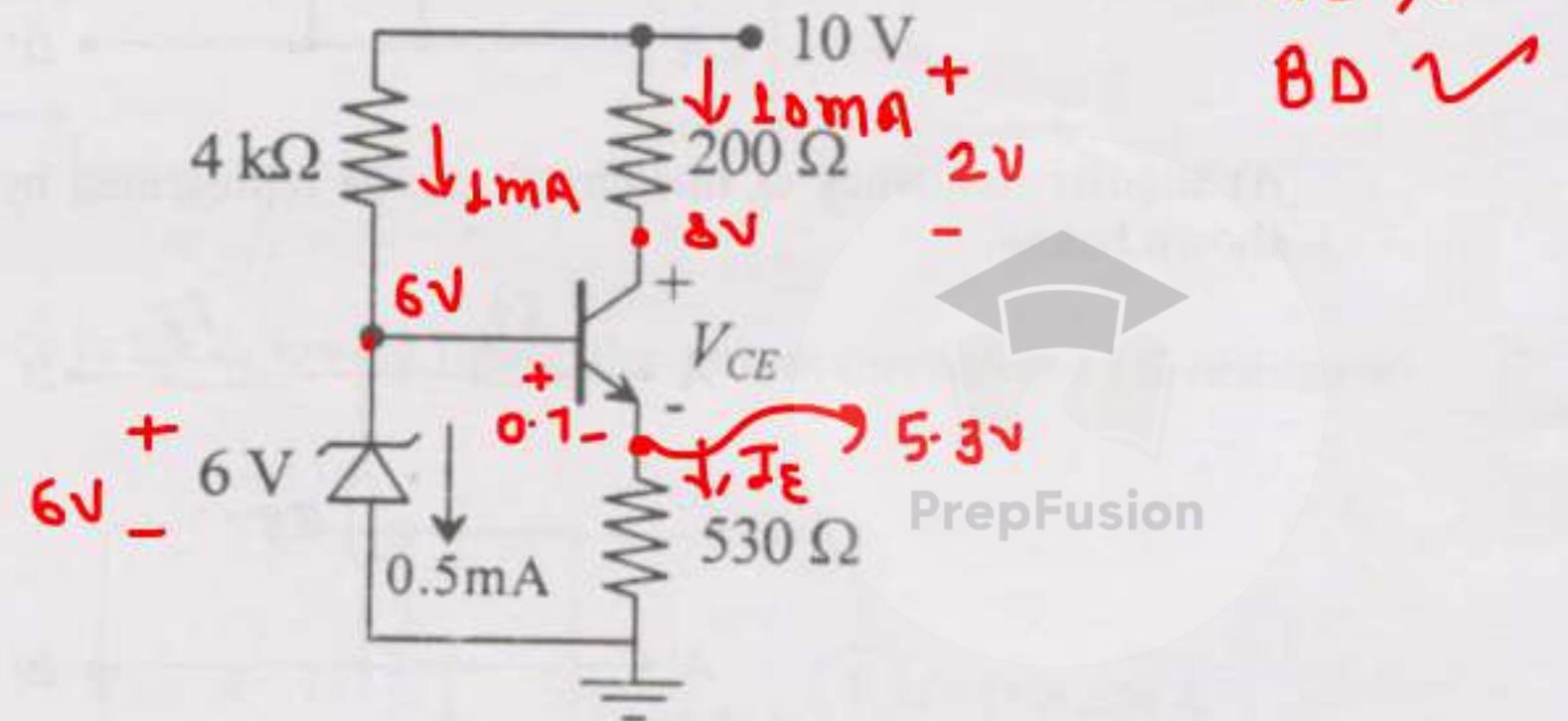
## Assignment - Ig

Q.

In the circuit shown below,  $V_{BE} = 0.7$  V.



PrepFusion

The  $\beta$  of the transistor and  $V_{CE}$  are, respectively

- (A) 19 and 2.8 V      (B) 19 and 4.7 V      (C) 38 and 2.8 V      (D) 38 and 4.7 V

J<sub>B</sub> X  
RB X  
BD ✓

$$I_E = \frac{5.3}{530} = 10 \text{ mA}$$

$$I_B = 0.5 \text{ mA}$$


$$\beta = (\beta + 1) \approx 5$$

**$\beta = 19$**

$$V_{CE} = 8 - 5.3 \\ = 2.7 \text{ V}$$

Q.

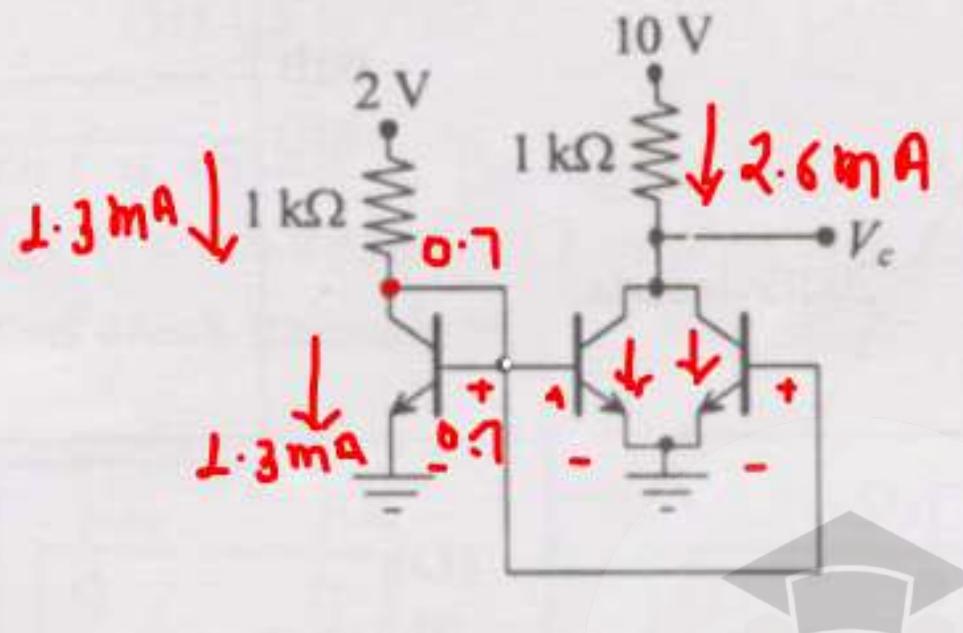The three transistors in the circuit shown below are identical, with  $V_{BE} = 0.7$  V and  $\beta = 100$ .



option → 398


Take  $\beta = \infty$

The voltage  $V_c$  is


- (A) 0.2 V      (B) 2 V      (C) 7.4 V      (D) 10 V

$$V_c = 10 - 2.6 \text{ mV} (1k)$$


$$V_c = 7.4 \text{ V}$$

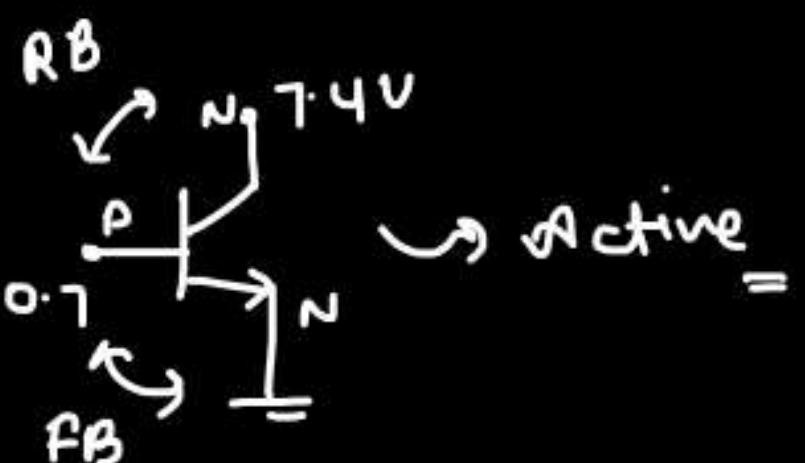

Q.

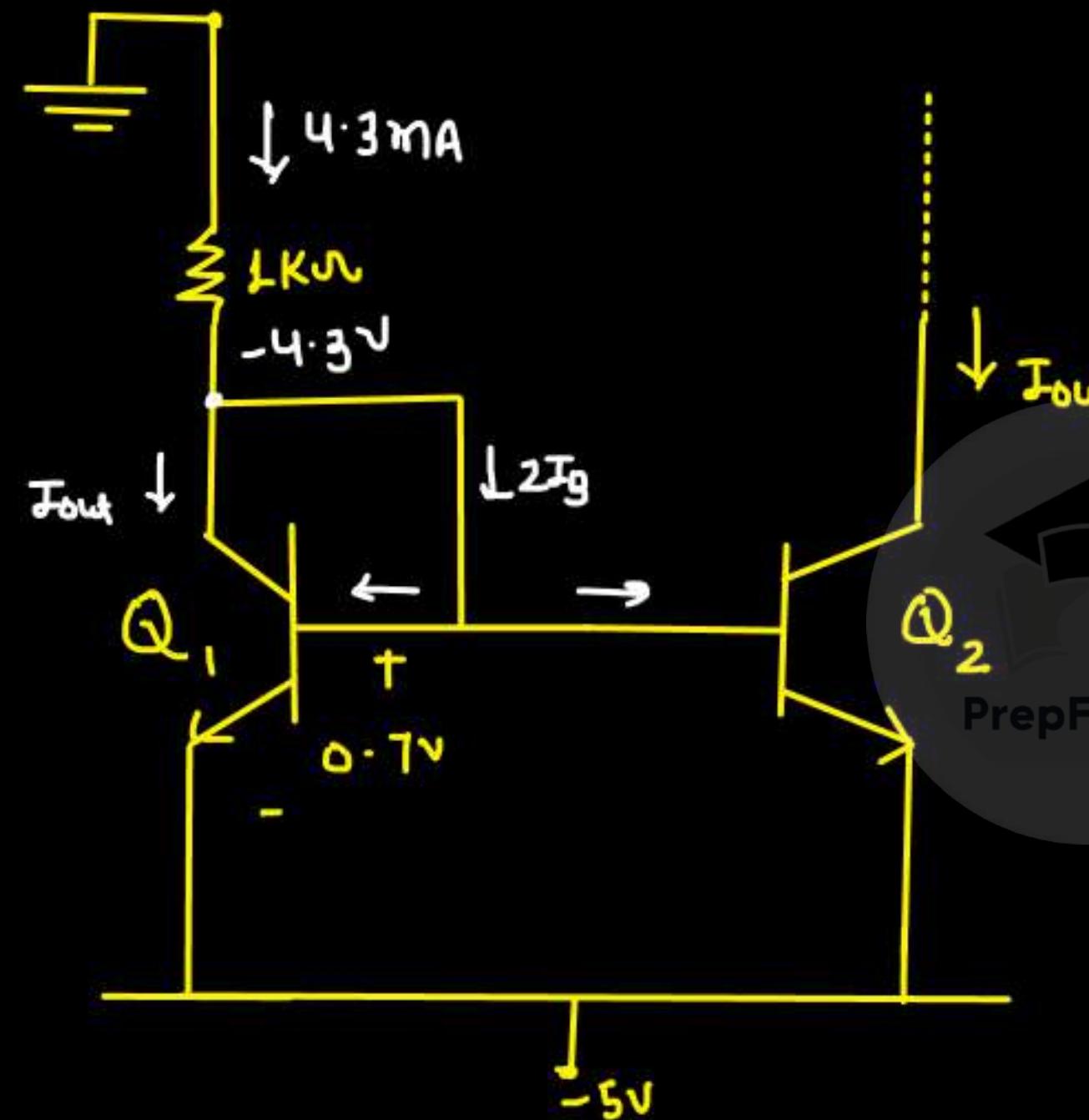

Q.

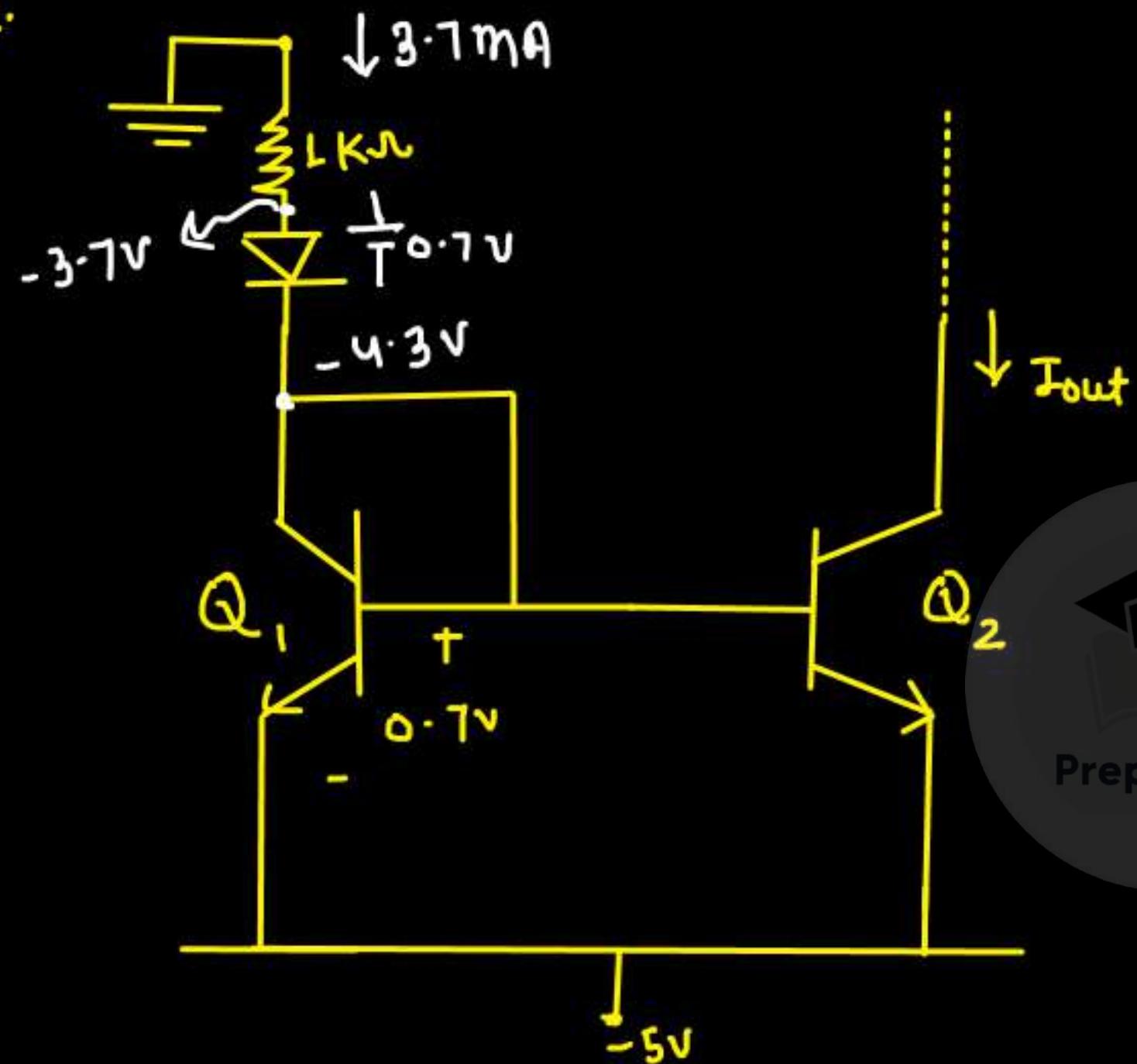

$$\beta = \infty$$


$$V_T \text{ for diode} = 0.7\text{V}$$

find  $I_{out}$ ?

$$I_{out} = 3.7\text{mA}$$



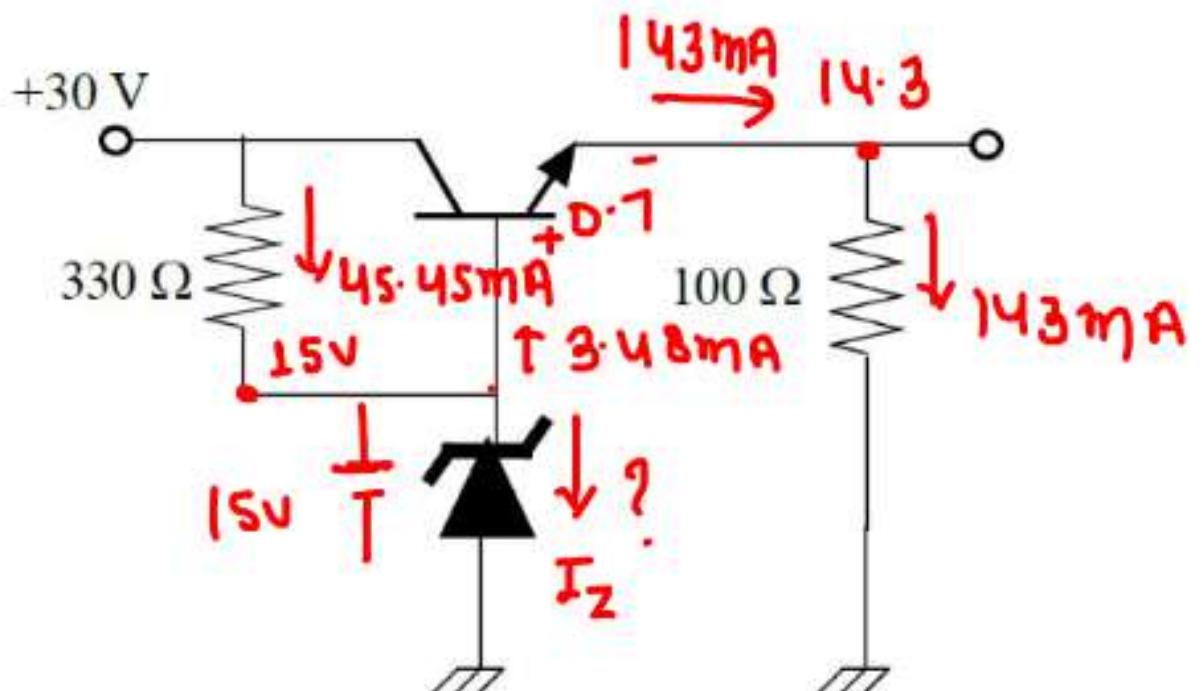For the circuit shown in the figure, the transistor has  $\beta = 40$ ,  $V_{BE} = 0.7$  V, and the voltage across the Zener diode is 15 V. The current (in mA) through the Zener diode is \_\_\_\_\_.



FB  
RB  
BD


↳ Zener probably will go into B-D → assuming

$$I_E = 143 \text{ mA}$$

$$I_B = \frac{143}{41} = 3.48 \text{ mA}$$

$$I_Z = 45.45 - 3.48 = 41.96 \text{ mA}$$

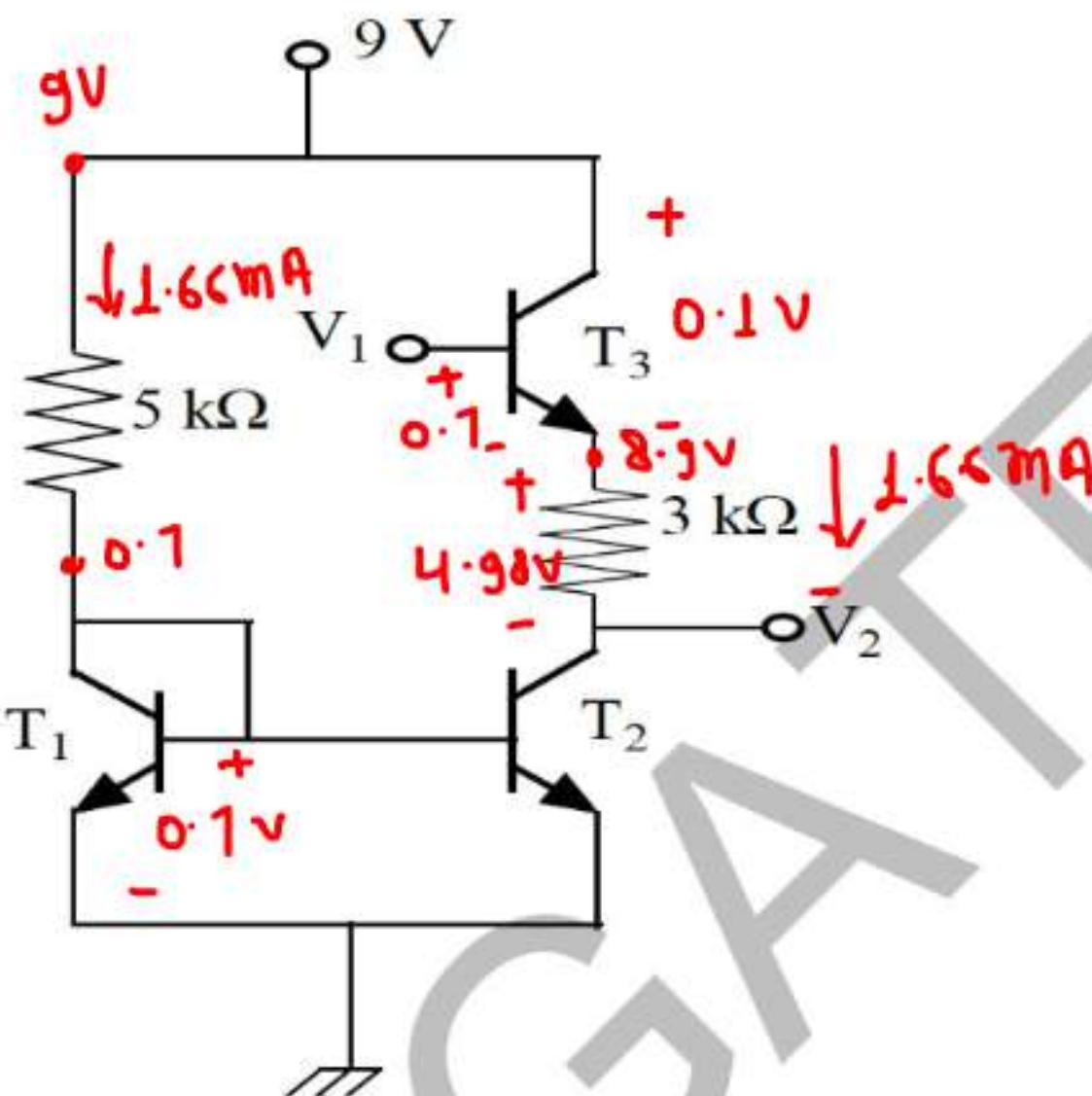In the figure, transistors  $T_1$  and  $T_2$  have identical characteristics.  $V_{CE(sat)}$  of transistor  $T_3$  is 0.1 V. The voltage  $V_1$  is high enough to put  $T_3$  in saturation. Voltage  $V_{BE}$  of transistors  $T_1$ ,  $T_2$  and  $T_3$  is 0.7 V. The value of  $(V_1 - V_2)$  in V is \_\_\_\_\_.



$$V_1 = 8.9 + 0.1 = 9.0 \text{ V}$$

Assuming →

$T_2$  in active ✓


$$V_2 = 3.92 \text{ V}$$



$$V_1 - V_2 = 9.0 - 3.92 = 5.08 \text{ V}$$

Ans.

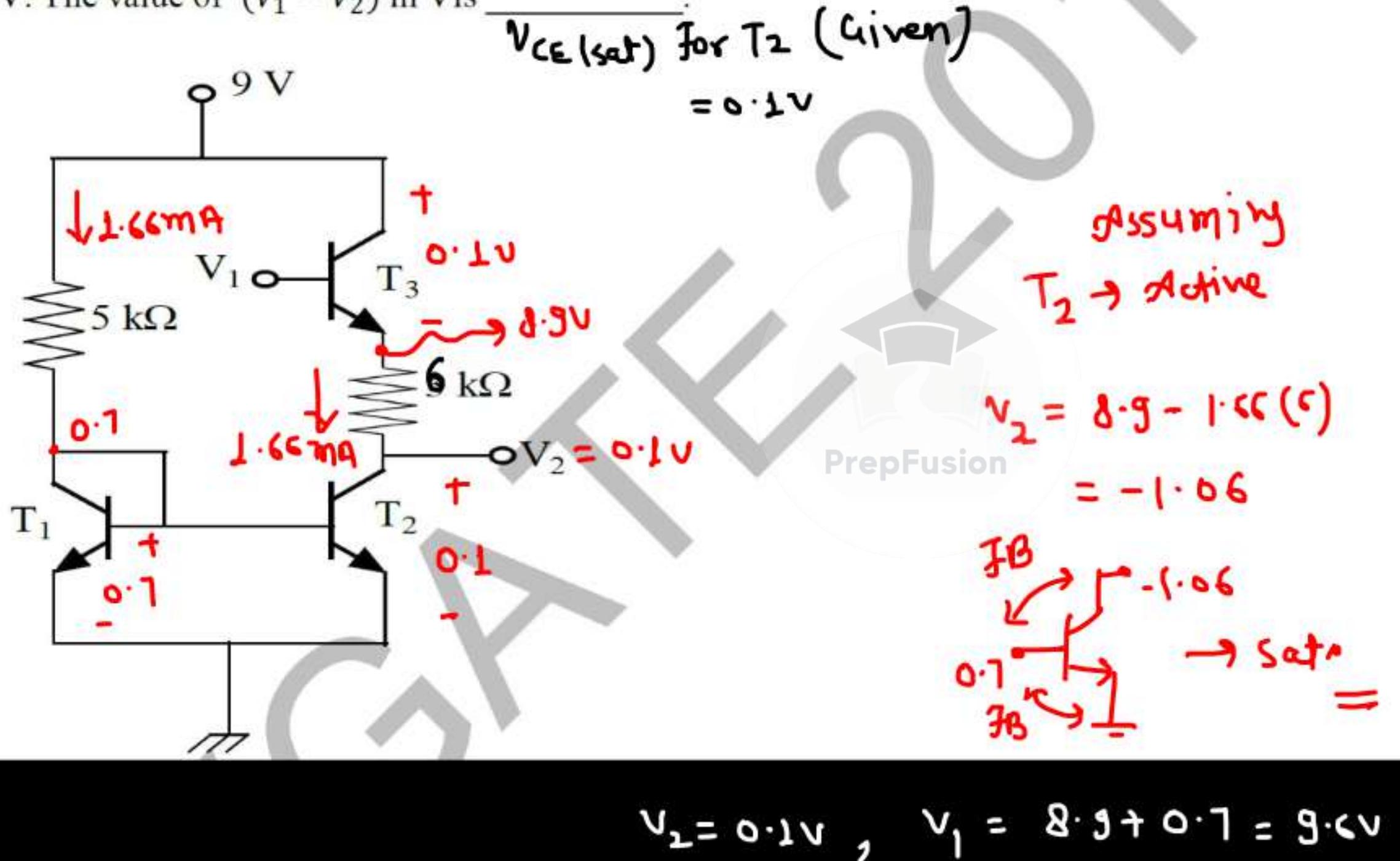
In the figure, transistors  $T_1$  and  $T_2$  have identical characteristics.  $V_{CE(sat)}$  of transistor  $T_3$  is 0.1 V. The voltage  $V_1$  is high enough to put  $T_3$  in saturation. Voltage  $V_{BE}$  of transistors  $T_1$ ,  $T_2$  and  $T_3$  is 0.7 V. The value of  $(V_1 - V_2)$  is



$$V_1 - V_2 = 0.9 - 0.1 \\ = 0.8 \text{ V}$$

Ans =

Q.

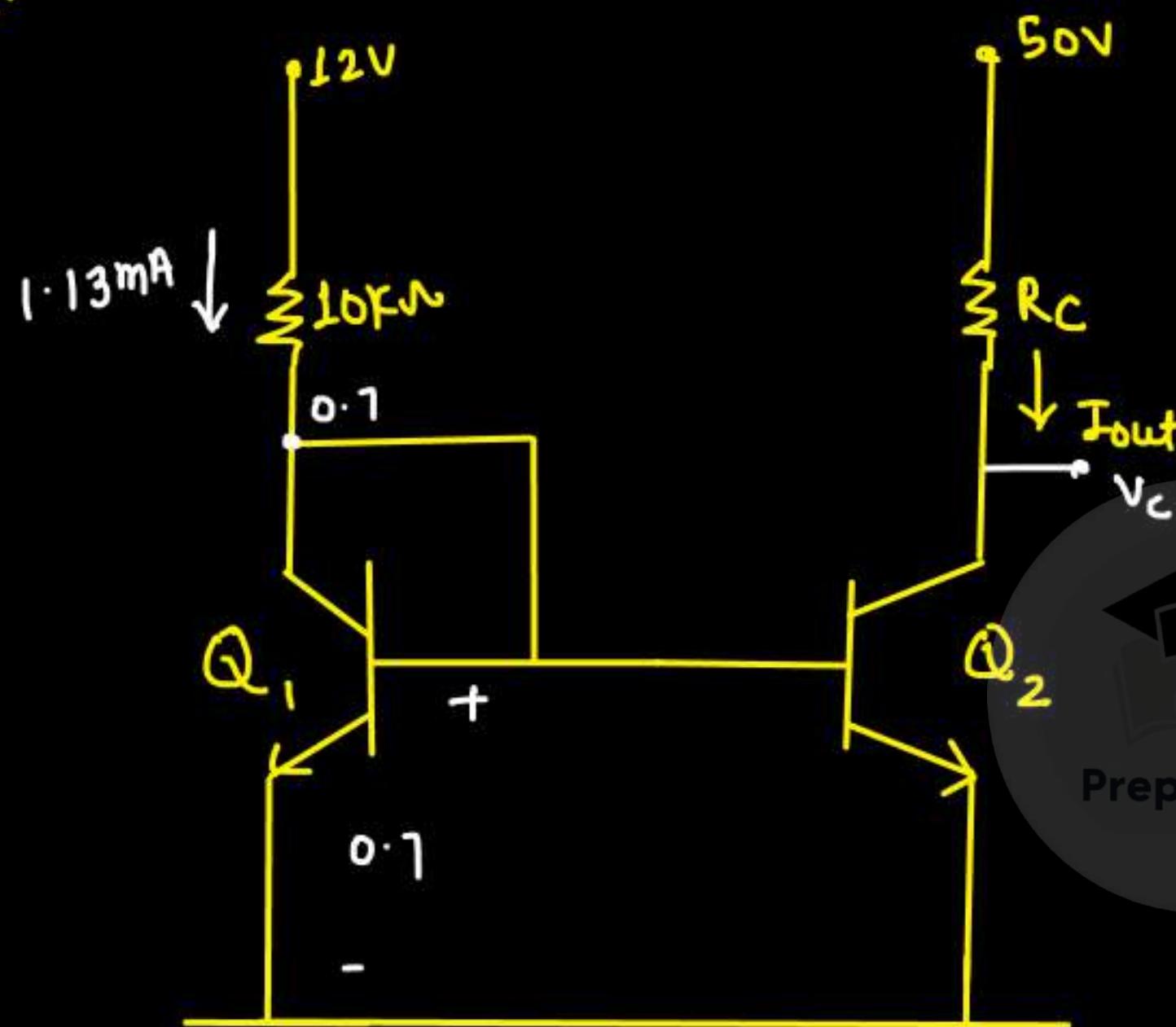

(a)  $R_C = 20 \text{ k}\Omega$

$Q_2 \rightarrow \text{Active} \text{ (Assuming)}$

$$I_{out} = \frac{100}{202} \times 1.13 = 1.1 \text{ mA}$$

ANS.

$$V_C = 50 - 1.1 \text{ mA} \times 20 \text{ k} = 39 \text{ V}$$



(b)  $R_C = 50 \text{ k}\Omega$


$Q_2 \rightarrow \text{active} \text{ (Assuming)}$

$$I_{out} = 1.1 \text{ mA}$$

X
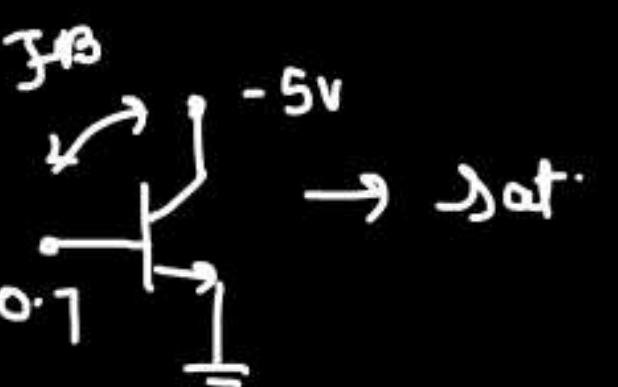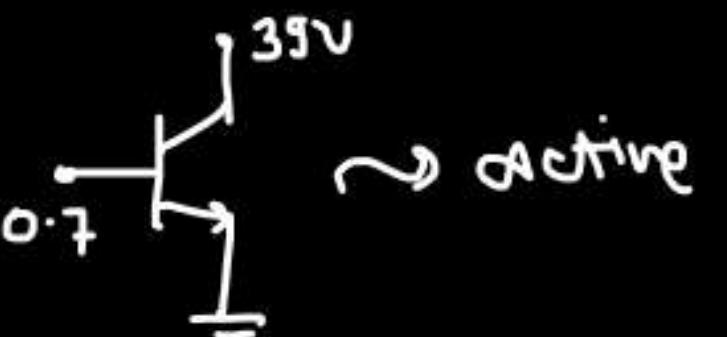
$$V_C = 50 - 1.1 \times 50 = -5 \text{ V}$$



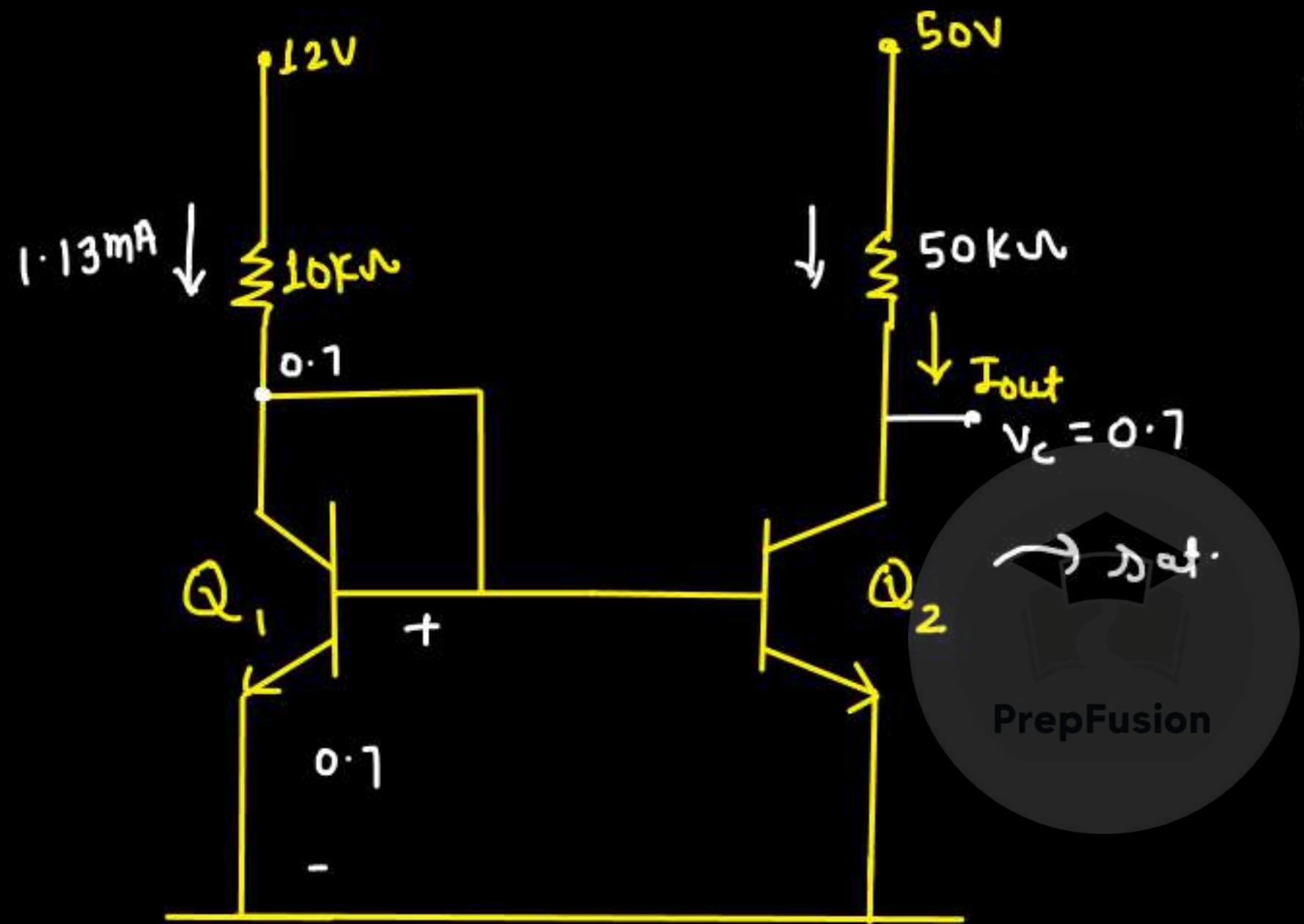


$$I_{out} = \frac{49.3}{50k}$$

$I_{out} = 0.98mA$

ANS =

~~Standard~~

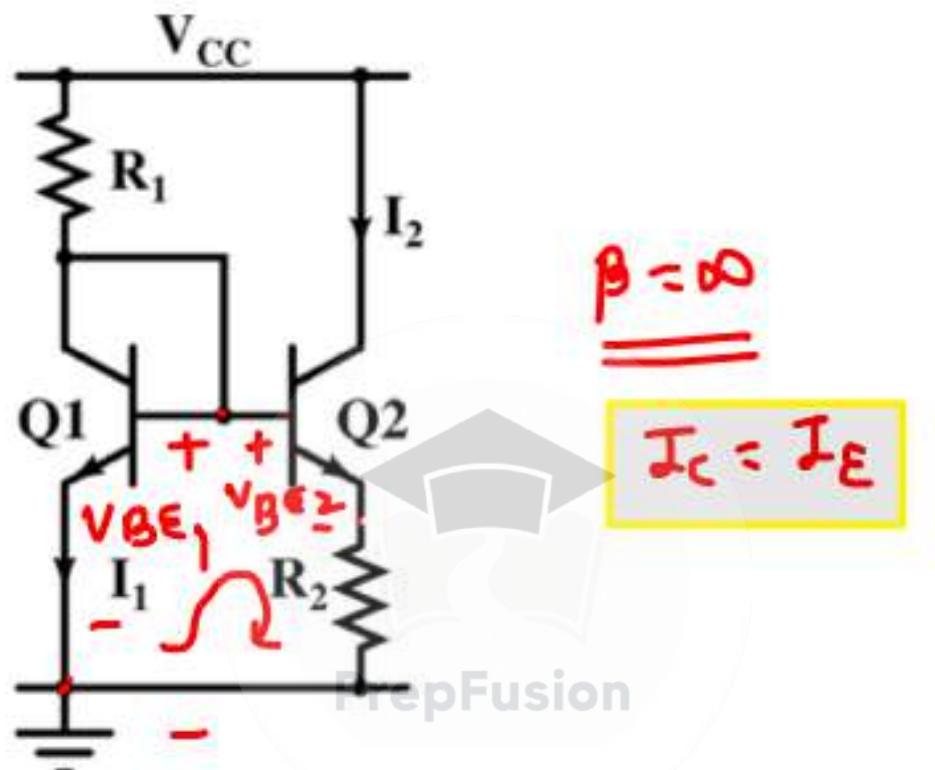Resistor  $R_1$  in the circuit below has been adjusted so that  $I_1 = 1 \text{ mA}$ . The bipolar transistors Q1 and Q2 are perfectly matched and have very high current gain, so their base currents are negligible. The supply voltage  $V_{cc}$  is 6 V. The thermal voltage  $kT/q$  is 26 mV.



The value of  $R_2$  (in  $\Omega$ ) for which  $I_2=100 \mu\text{A}$  is \_\_\_\_\_

$$I_1 = I_s \exp\left(\frac{V_{BE1}}{V_T}\right) \quad \text{--- (1)}$$

$$I_2 = I_s \exp\left(\frac{V_{BE2}}{V_T}\right) \quad \text{--- (2)}$$

$$\frac{0 + V_{BE1} - V_{BE2}}{R_2} = I_2$$

$$\frac{V_{BE_1} - V_{BE_2}}{I_2} = R_2 \quad \text{--- (3)}$$

(1) ÷ (2)

$$\frac{I_1}{I_2} = \frac{e^{(V_{BE_1}/V_T)}}{e^{(V_{BE_2}/V_T)}}$$

$$I_o = \exp \left( \frac{V_{BE_1} + V_{BE_2}}{V_T} \right)$$

From eqn (3)

$$R_2 = \frac{59.86 \text{ mV}}{0.1 \text{ mA}}$$


$$V_{BE_1} - V_{BE_2} = 26 \text{ mV} \times \ln(20)$$

$$R_2 = 598.67 \Omega$$

$$V_{BE_1} - V_{BE_2} = 59.8 \text{ mV}$$

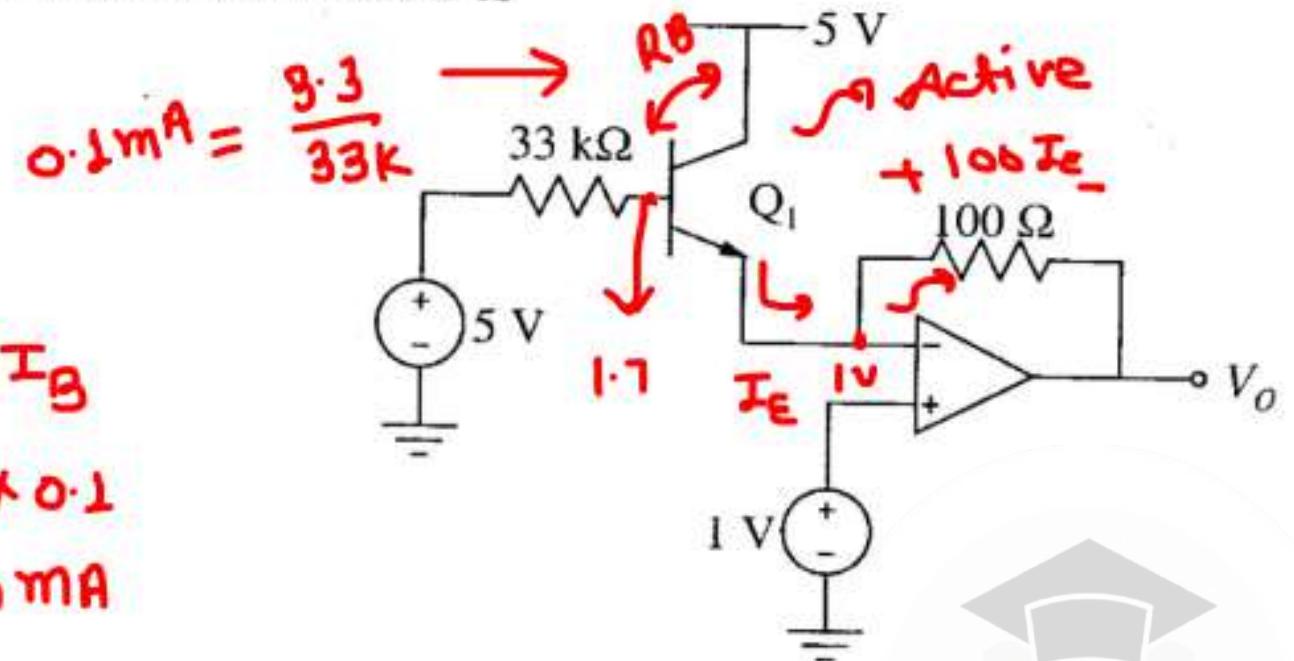Q.36 Assuming base-emitter voltage of 0.7 V and  $\beta = 99$  of transistor  $Q_1$ , the output voltage  $V_O$  in the ideal opamp circuit shown below is

$$\begin{aligned} I_E &= (\beta + 1) I_B \\ &= 100 \times 0.1 \\ &= 10 \text{ mA} \end{aligned}$$



$$\begin{aligned} V_O &= 1 - 100 I_E \\ &= 1 - 100 \times 10 \text{ mA} \\ &= 0 \text{ V} \end{aligned}$$

- (A) -1 V      (B) -1/3.3 V      (C) 0 V      (D) 2 V

(a) The value of  $V_o$  of the series regulator shown below is


(b) Find power dissipated in BJT.  
( $\beta = \infty$ )

(A) 24 V

(B) 28 V

PreFusion  
(C) 30 V

(D) 32 V

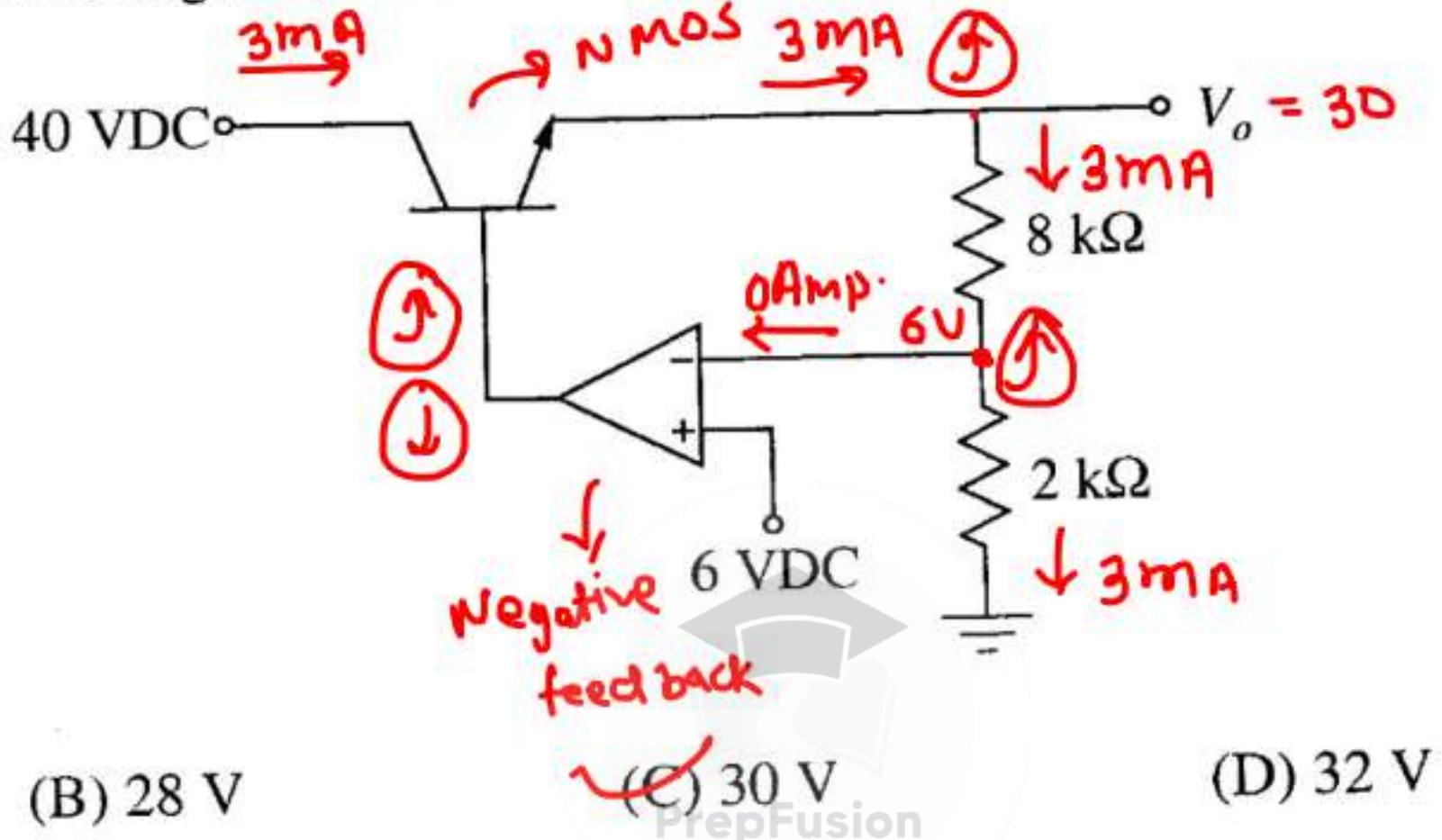

$$6V = \frac{2V_o}{10}$$

**$V_o = 30 V$**

**Ans.**


(b) Power dissipated in BJT =  **$V_{CE} \times I_C$**

$$V_{CE} = 40 - 30 = 10V$$

$$I_C = 3mA$$

**$P_d = 10 \times 3m = 30mW$**  Ans..

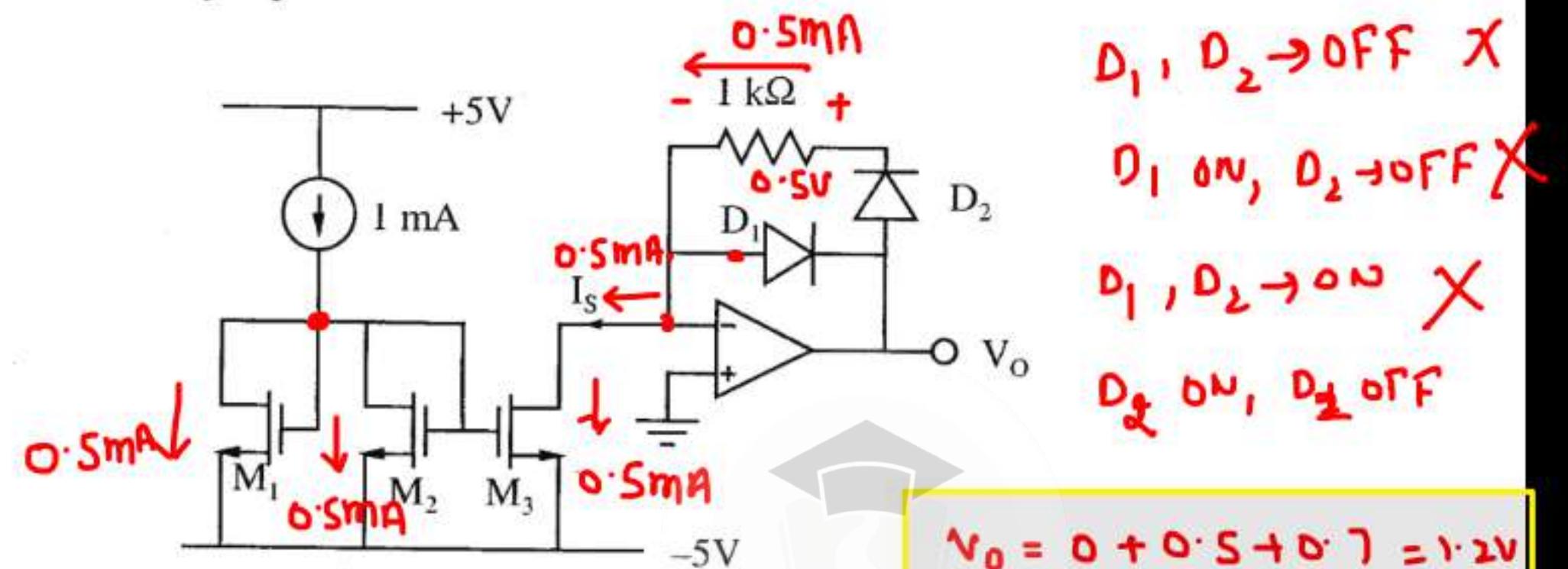M1, M2 and M3 in the circuit shown below are matched N-channel enhancement mode MOSFETs operating in saturation mode, forward voltage drop of each diode is 0.7 V, reverse leakage current of each diode is negligible and the opamp is ideal.




Q.54 The current I<sub>S</sub> in the circuit is

- (A) -1 mA      (B) 0.5 mA      (C) 1 mA      (D) 2 mA

Q.55 For the computed value of current I<sub>S</sub>, the output voltage V<sub>O</sub> is

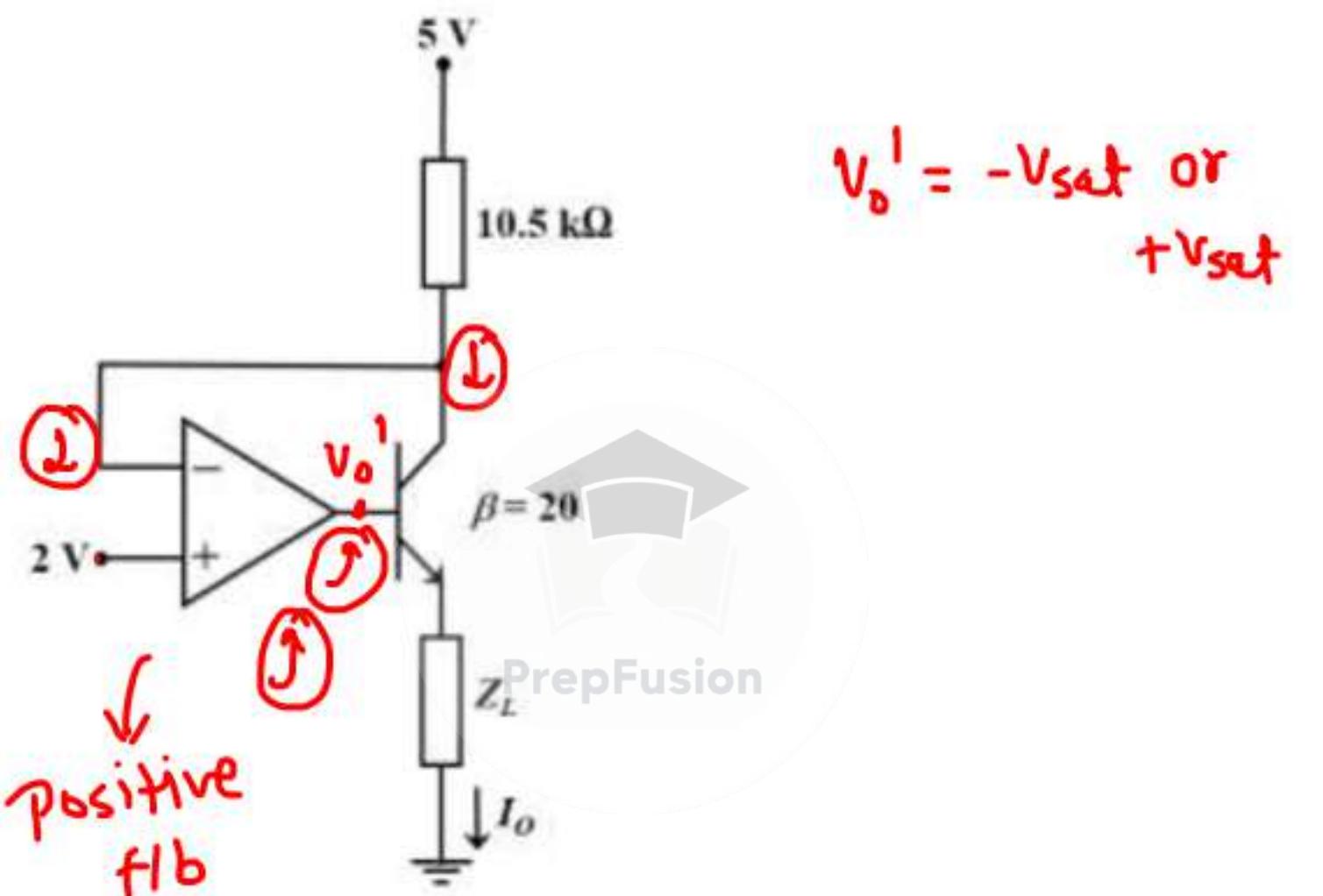- (A) 1.2 V      (B) 0.7 V      (C) 0.2 V      (D) -0.7 V


In the given circuit, assume that the opamp is ideal and the transistor has a  $\beta$  of 20. The current  $I_o$  (in  $\mu\text{A}$ ) flowing through the load  $Z_L$  is \_\_\_\_.



if  $V_o' = +V_{sat} \Rightarrow \text{BJT ON} \Rightarrow V_- = ? \Rightarrow \text{can't determine} \Rightarrow \text{No conclusion}$

↙ if  $V_o' = -V_{sat} \Rightarrow \text{BJT OFF} \Rightarrow V_- = 5V \Rightarrow V_o' = -V_{sat} \Rightarrow I_o = 0 \text{ Amp.}$

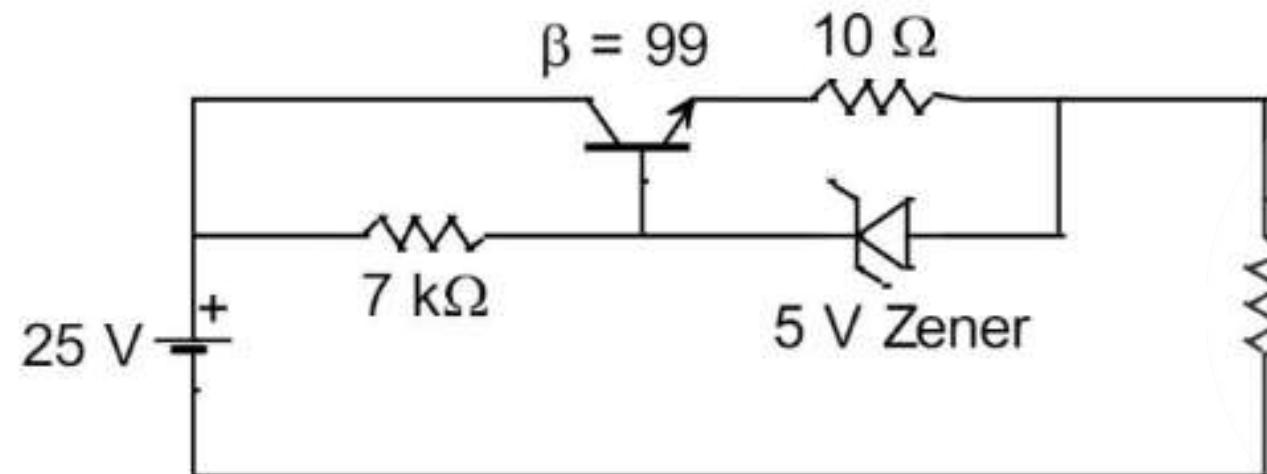The Zener diode in circuit has a breakdown voltage of 5 V. The current gain  $\beta$  of the transistor in the active region is 99. Ignore base-emitter voltage drop  $V_{BE}$ . The current through the  $20 \Omega$  resistance in milliamperes is \_\_\_\_\_ (Round off to 2 decimal places).




$$V_{BE} = 0 \text{ V}$$



Let Zener goes into B.D.

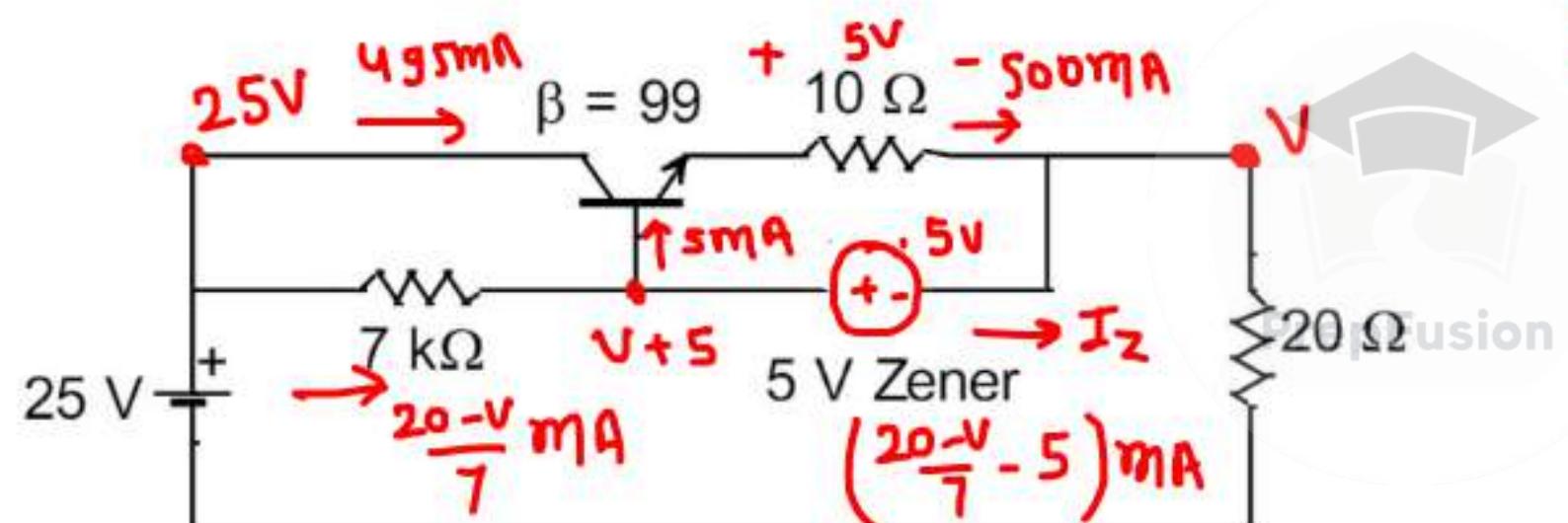The Zener diode in circuit has a breakdown voltage of 5 V. The current gain  $\beta$  of the transistor in the active region is 99. Ignore base-emitter voltage drop  $V_{BE}$ . The current through the  $20 \Omega$  resistance in milliamperes is \_\_\_\_\_ (Round off to 2 decimal places).



$$I_C = 0.5 \text{ Amp}$$

$$I_B = \frac{0.5}{100} = 5 \text{ mA}$$

$$\frac{20}{7} - 5 - \frac{V}{10} + 500 = \frac{V}{20} \times 1000$$

$$497.6 = 50.14 V$$


$$\Rightarrow V = 9.92 \text{ V}$$

$$I_K = -3.56 \text{ mA}$$



Zener NOT in BD.

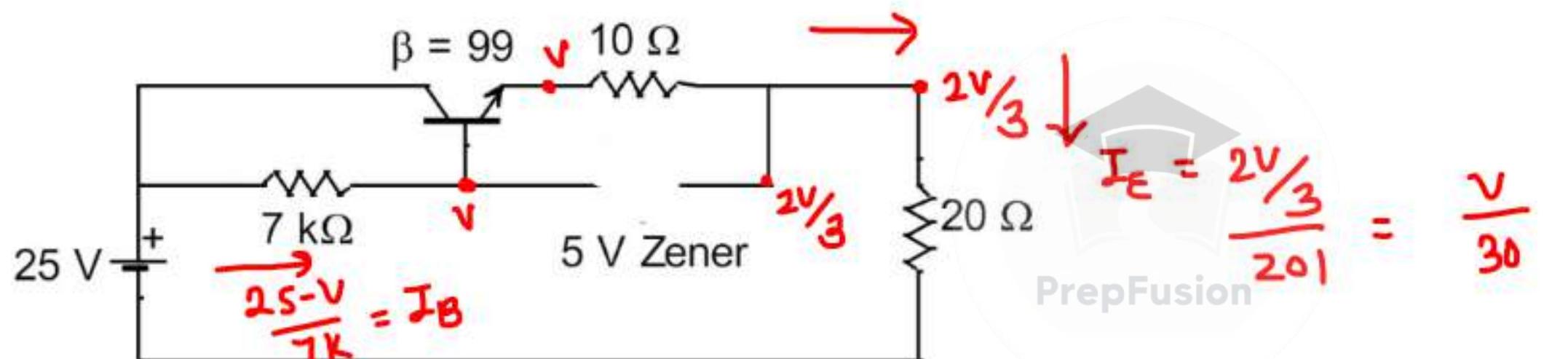
The Zener diode in circuit has a breakdown voltage of 5 V. The current gain  $\beta$  of the transistor in the active region is 99. Ignore base-emitter voltage drop  $V_{BE}$ . The current through the  $20 \Omega$  resistance in milliamperes is \_\_\_\_\_ (Round off to 2 decimal places).



$$I = \frac{2V/3}{20} = \frac{15}{60}$$

$$\frac{25-V}{7000} \times 100 = \frac{V}{30}$$

$$15 - 3V = 7V \Rightarrow V = 7.5V$$

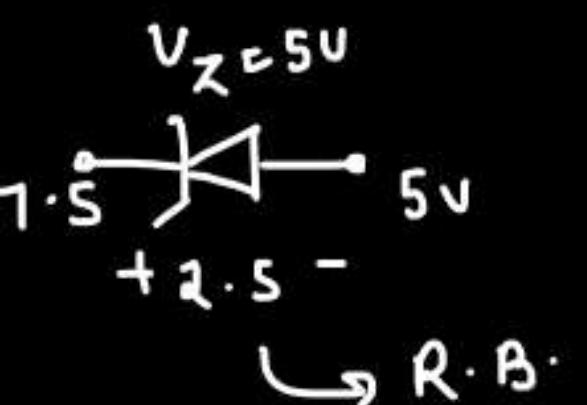


$$I = 250mA$$

Q.

In the voltage reference circuit shown in the figure, the op-amp is ideal and the transistors  $Q_1, Q_2, \dots, Q_{32}$  are identical in all respects and have infinitely large values of common-emitter current gain ( $\beta$ ). The collector current ( $I_c$ ) of the transistors is related to their base-emitter voltage ( $V_{BE}$ ) by the relation  $I_C = I_S \exp(V_{BE}/V_T)$ , where  $I_S$  is the saturation current. Assume that the voltage  $V_p$  shown in the figure is 0.7 V and the thermal voltage  $V_T = 26$  mV.

$$I = I_s \exp\left(\frac{V_x}{V_T}\right)$$

$$I'' = \frac{v_x + 20I - v_x}{20} = I$$

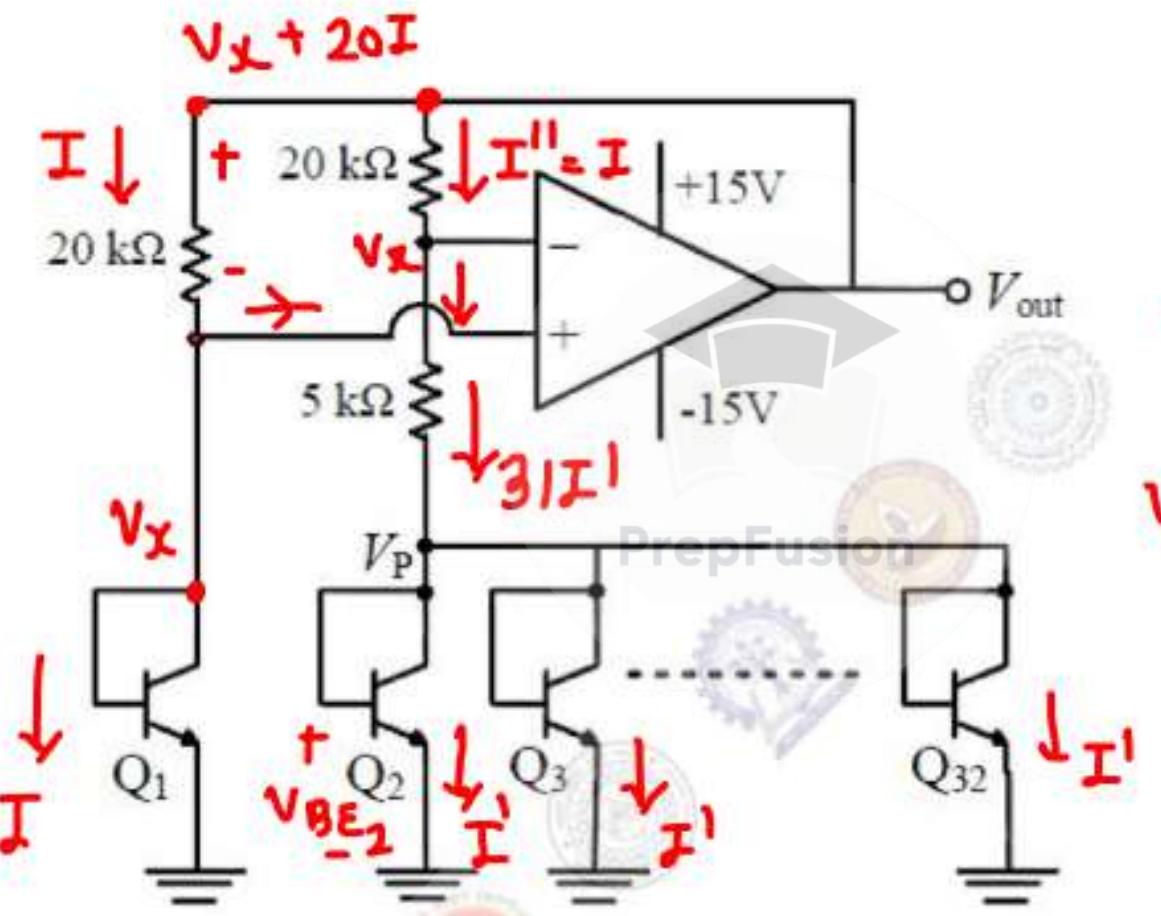

matched

$$V_{BE_1} = V_x$$

$$V_{BE_2} = V_{BE_3} = -V_{BE_{32}} = V_p = 0.7$$

The output voltage  $V_{\text{out}}$  (in volts) is \_\_\_\_\_

$$I = 31 I^1$$

$$I_S \exp\left(\frac{V_x}{V_T}\right) = 31 I_S \exp\left(\frac{0.7}{V_T}\right)$$

$$\exp\left(\frac{V_x - 0.7}{V_T}\right) = 31$$



**V<sub>x</sub> = 0.789V**



PrepFusion

$$V_o = 0.789 + 20k \times I$$

$$= 0.789 + 20 \left( \frac{0.789 - 0.7}{5} \right)$$


**V<sub>D</sub> = 1.15V**
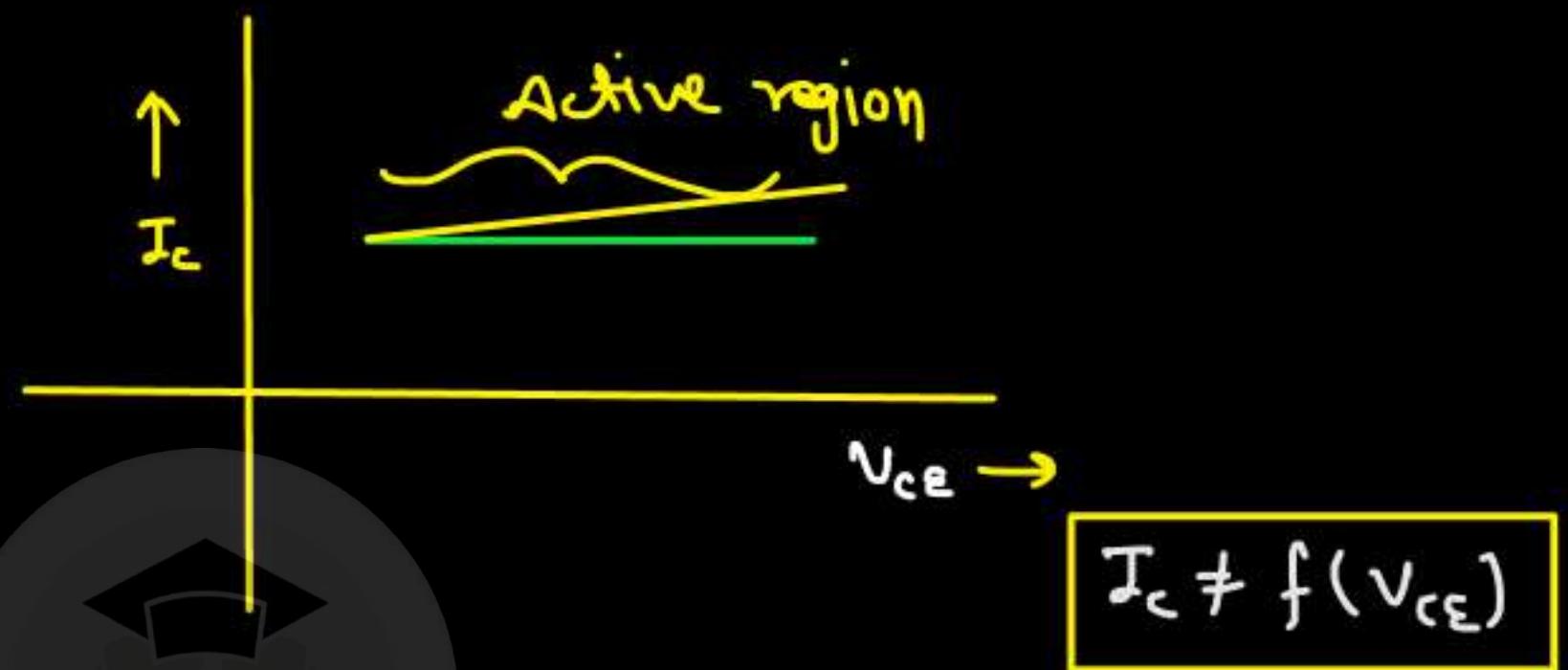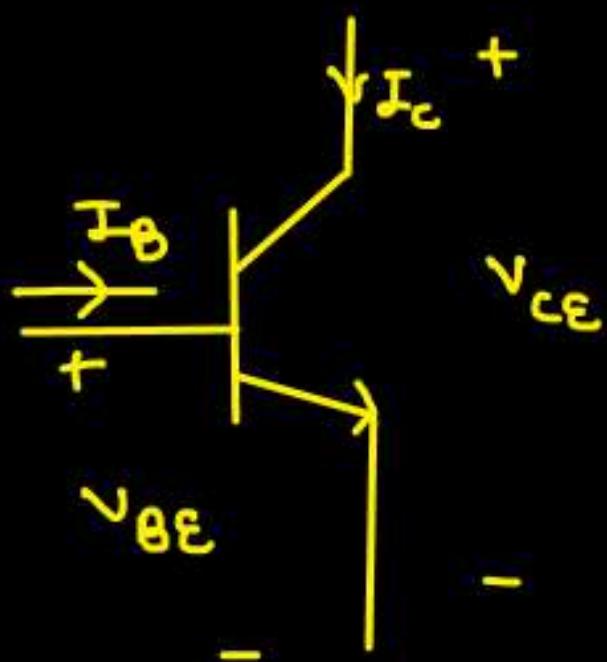
## ⇒ Small Signal Model of BJT Amplifier:-



$$I_C = I_s \exp\left(\frac{V_{BE}}{nV_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right) - 0 \quad \text{PrepFusion}$$

$$I_B = \frac{I_C}{\beta} \quad - ②$$

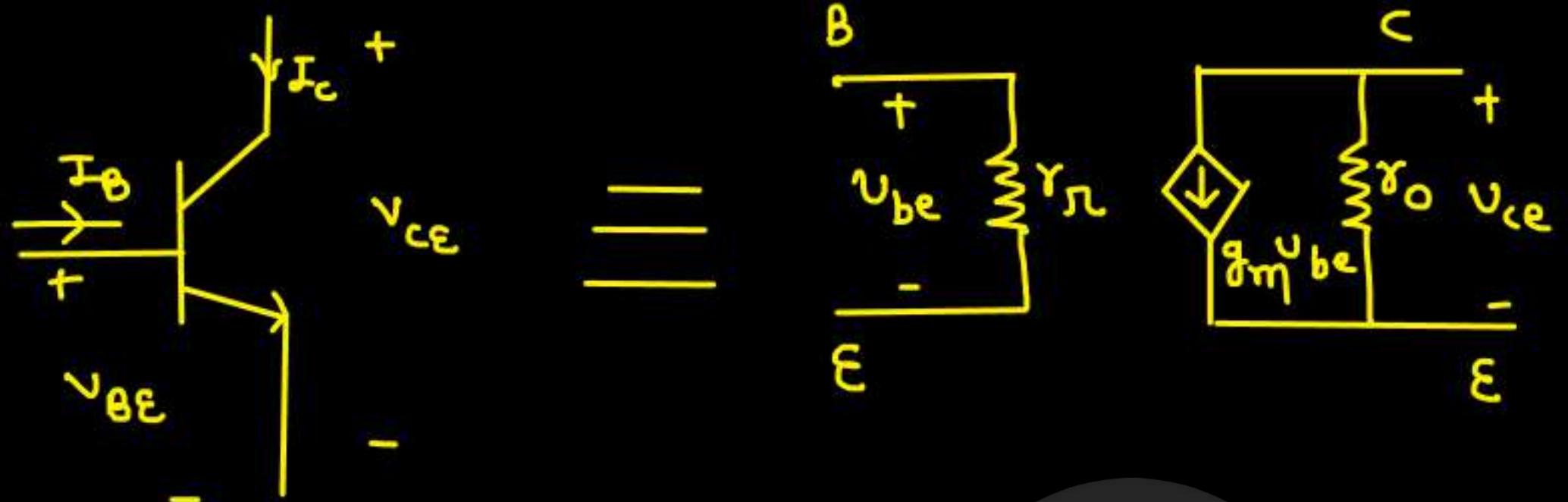

$$g_m = \frac{\partial I_C}{\partial V_{BE}}$$



$$g_m = \frac{I_C}{nV_T}$$

$$I_C = I_s \exp\left(\frac{V_{BE}}{nV_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$\frac{\partial I_C}{\partial V_{BE}} = I_s \frac{\exp\left(\frac{V_{BE}}{nV_T}\right)}{nV_T} \left(1 + \frac{V_{CE}}{V_A}\right)$$

if  $n=1$

\* \*

$$g_m = \frac{I_C}{V_T}$$

$$\hookrightarrow \gamma_0 = \frac{\partial V_{CE}}{\partial I_C} = \frac{1}{\left( \frac{\partial I_C}{\partial V_{CE}} \right)}$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$\frac{\partial I_C}{\partial V_{CE}} = I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \times \frac{1}{V_A}$$

$$\frac{1}{\gamma_0} = \frac{I_C (\text{ideal})}{V_A}$$

\*\*

$$\gamma_0 = \frac{V_A}{\frac{\partial I_C}{\partial V_{CE}}}$$

if  $V_A \rightarrow \infty$ ,  $\gamma_0 \rightarrow \infty$

$$\gamma_{\pi} = \frac{\partial V_{BE}}{\partial I_B} = \frac{1}{\frac{\partial I_B}{\partial V_{BE}}}$$

$$I_B = \frac{I_C}{\beta}$$



$$\frac{\partial I_B}{\partial V_{BE}} = \frac{1}{\beta} \frac{\partial I_C}{\partial V_{BE}}$$

$$\frac{1}{\gamma_{\pi}} = \frac{\partial I_C}{\partial V_{BE}}$$

$$\gamma_{\pi} = \frac{\beta}{\partial I_C / \partial V_{BE}}$$

if  $\beta \rightarrow \infty$ ,  $\gamma_{\pi} \rightarrow \infty$

N.B. -

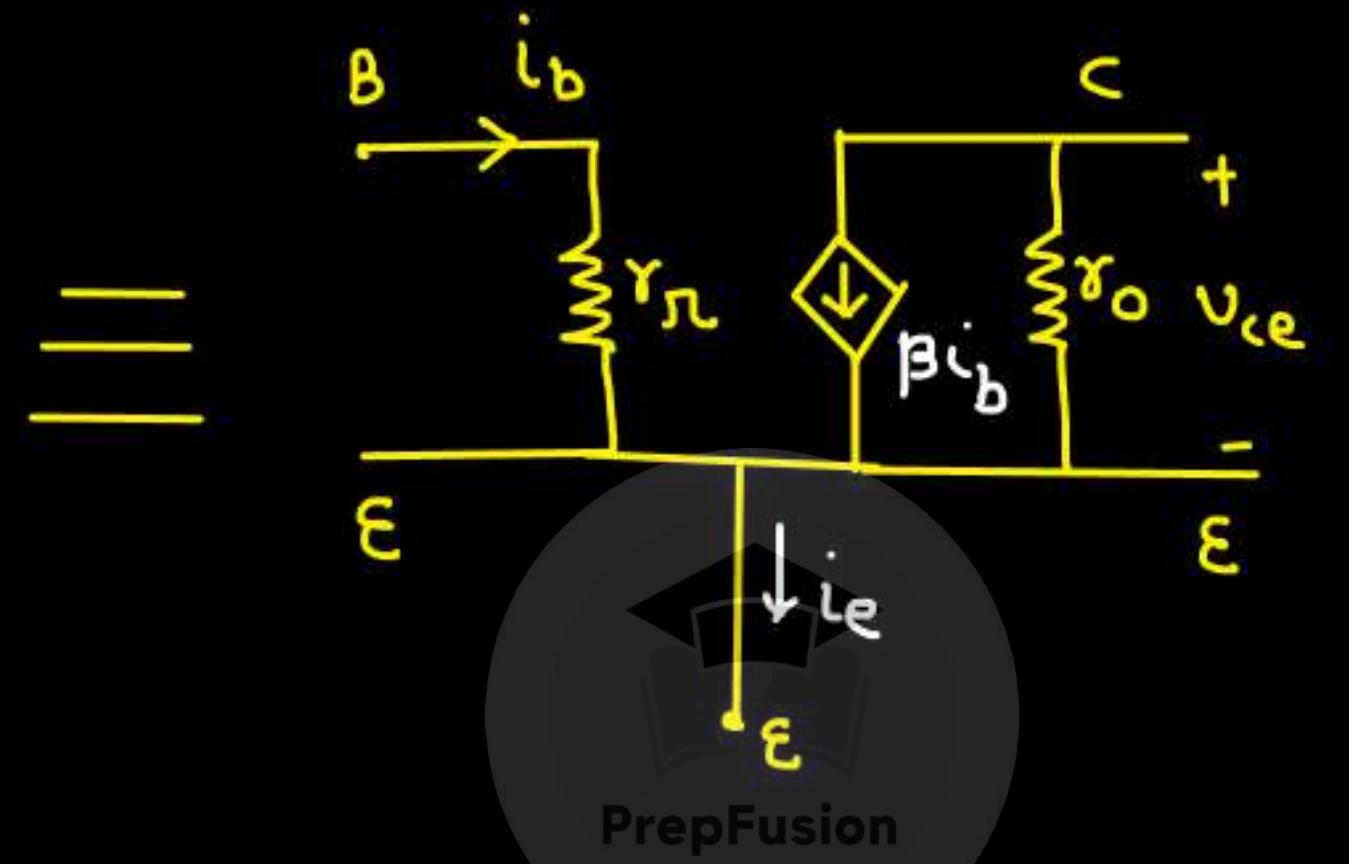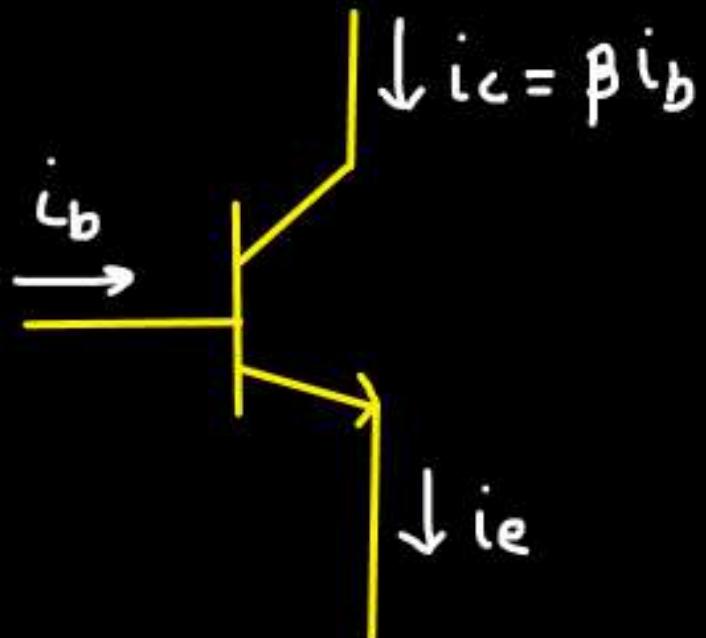


$$\gamma_R = \frac{\beta}{\delta m}$$

$$\gamma_0 = \frac{V_A}{I_C}$$

$$\delta m = \frac{I_C}{n V_T}$$

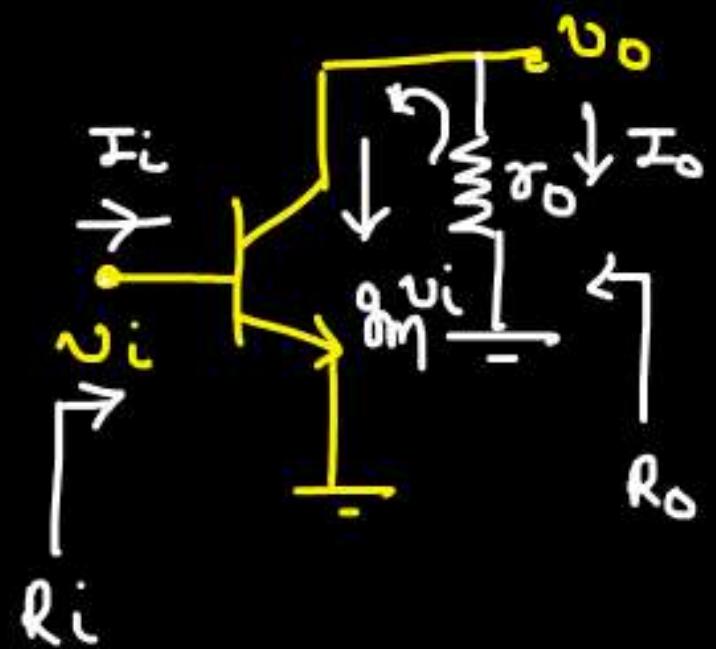Q. Find voltage gain. ( $V_A \neq \infty$ )



$$V_o = -g_m \tau_0 V_i$$

$$\frac{V_o}{V_i} = -g_m \tau_0$$

$$R_i = \tau_\pi$$

PrepFusion


$$R_o = \tau_0$$

$$V_i \xrightarrow{I_i} \tau_\pi \quad \Rightarrow \quad I_i = \frac{V_i}{\tau_\pi}$$

$$I_o = \frac{V_o}{\tau_0}$$

$$\frac{I_o}{I_i} = \frac{V_o}{\tau_0} \times \frac{\tau_\pi}{V_i} = -g_m \tau_0 \times \frac{\tau_\pi}{\tau_0} = -g_m \tau_\pi = -\beta$$

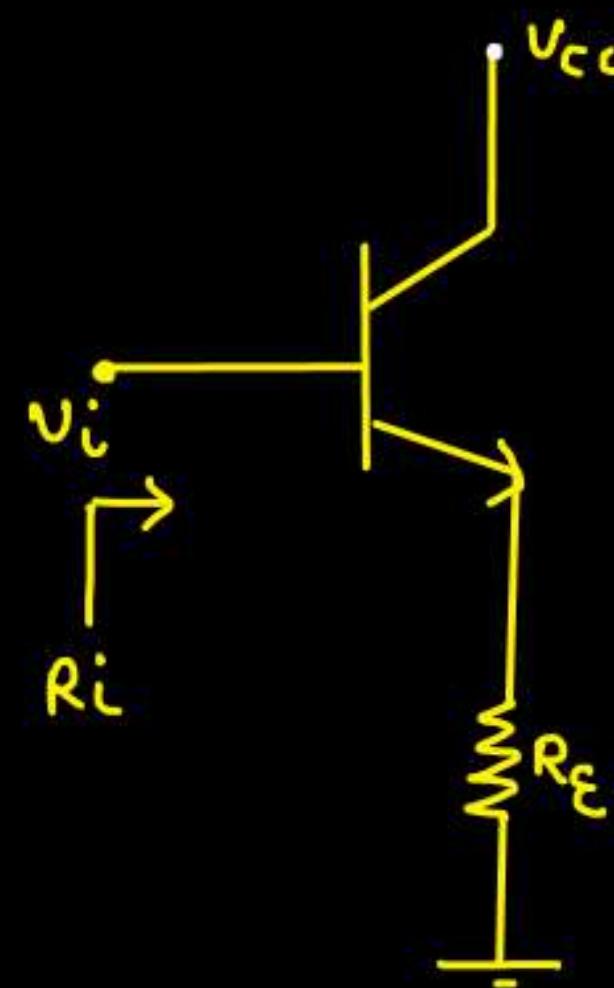Q. Find Small Signal  $R_i$  ( $V_A = \infty$ )



$$R_i = \frac{v_i}{i_b}$$




PrepFusion

$$v_i = i_b r_{\pi} + (\beta + 1) i_b R_E$$

$$\frac{v_i}{i_b} = R_i = r_{\pi} + (\beta + 1) R_E$$

ANS.

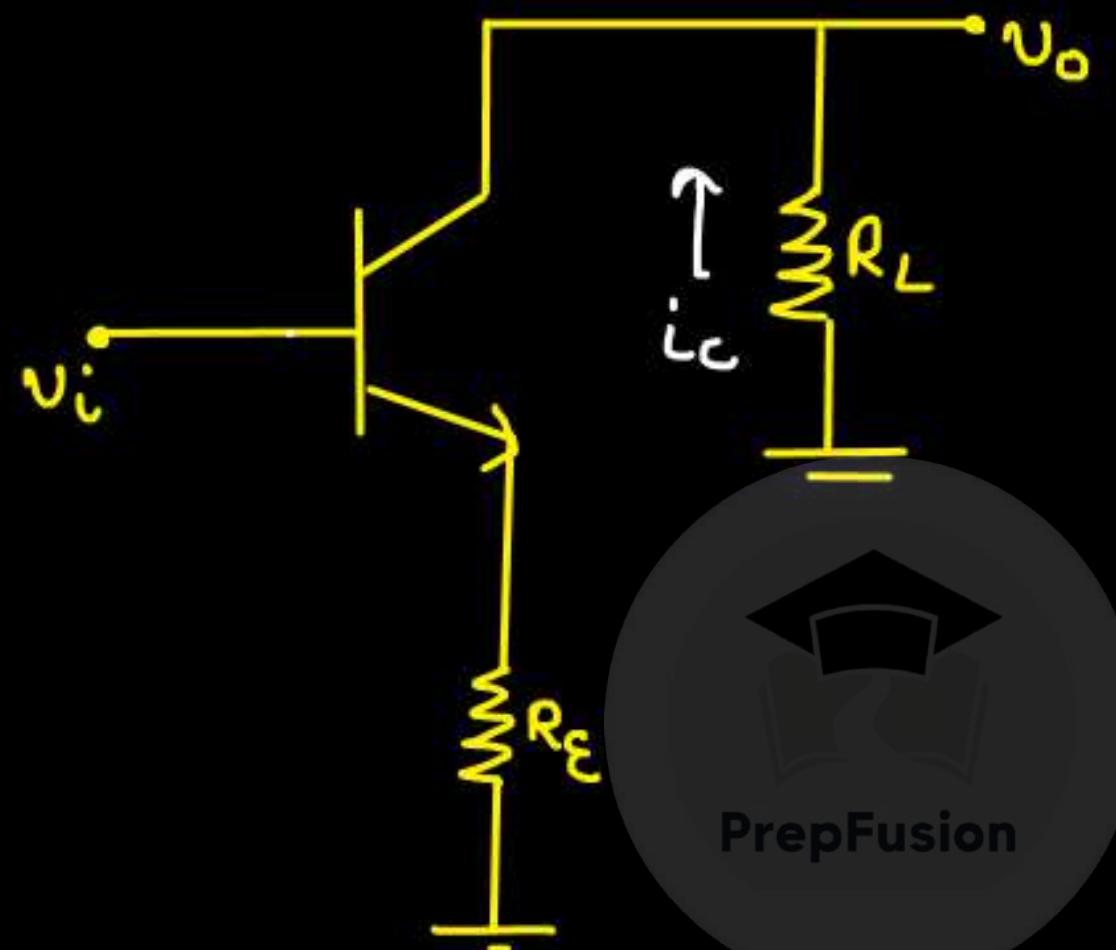Q. Find small signal voltage gain. ( $V_A = \infty$ )



$$i_c = \beta i_b$$

$$i_c = \frac{\beta v_i}{r_\pi + (\beta + 1) R_E}$$

$$v_o = -\frac{\beta R_L}{r_\pi + (\beta + 1) R_E} v_i$$

$$v_o = -i_c R_L$$



$$(\beta + 1) i_b = i_e$$

$$v_i = i_b r_\pi + (\beta + 1) R_E i_b$$

$$i_b = \frac{v_i}{r_\pi + (\beta + 1) R_E}$$

$$\frac{v_o}{v_i} = \frac{-\beta R_L}{r_{\pi} + (\beta + 1) R_E}$$

$$= -\frac{\beta / r_{\pi} R_L}{1 + (\beta + 1) \frac{R_E}{r_{\pi}}}$$

$$\left. \begin{aligned} r_{\pi L} &= \beta / g_m \\ \Rightarrow \frac{\beta}{r_{\pi}} &= g_m \end{aligned} \right\}$$

$$\frac{v_o}{v_i} = \frac{-g_m R_L}{1 + g_m R_E}$$

$$\left. \begin{aligned} \beta + 1 &\approx \beta \end{aligned} \right\}$$

N.B. -  
 $\approx$


If  $\beta = \infty \Rightarrow r_{\pi} = \frac{\beta}{g_m} = \infty$




Small signal analysis of BJT

=

Small signal analysis of MOS

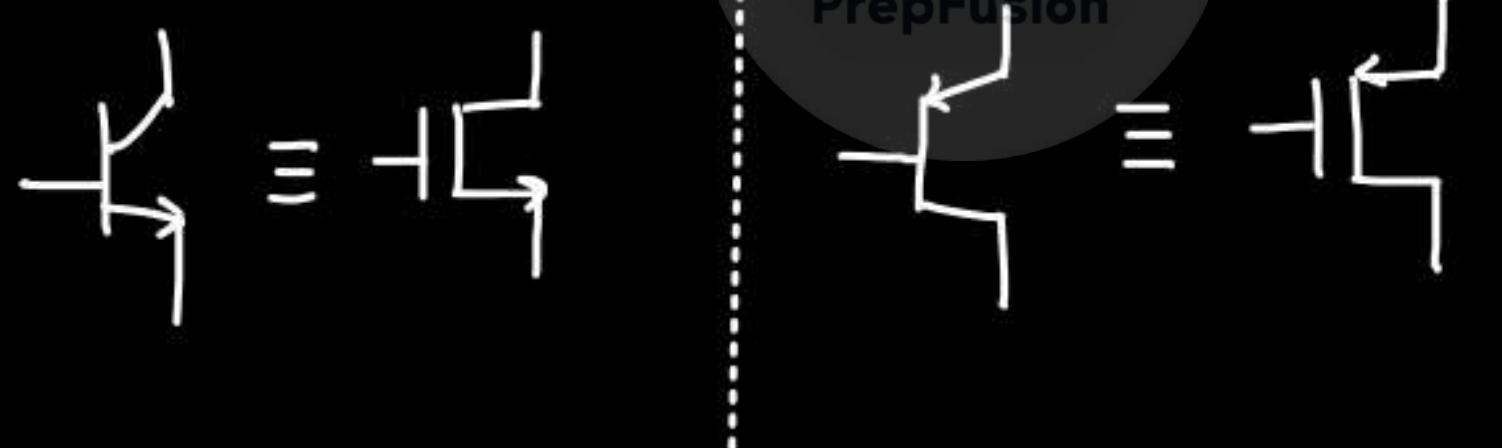


Q.

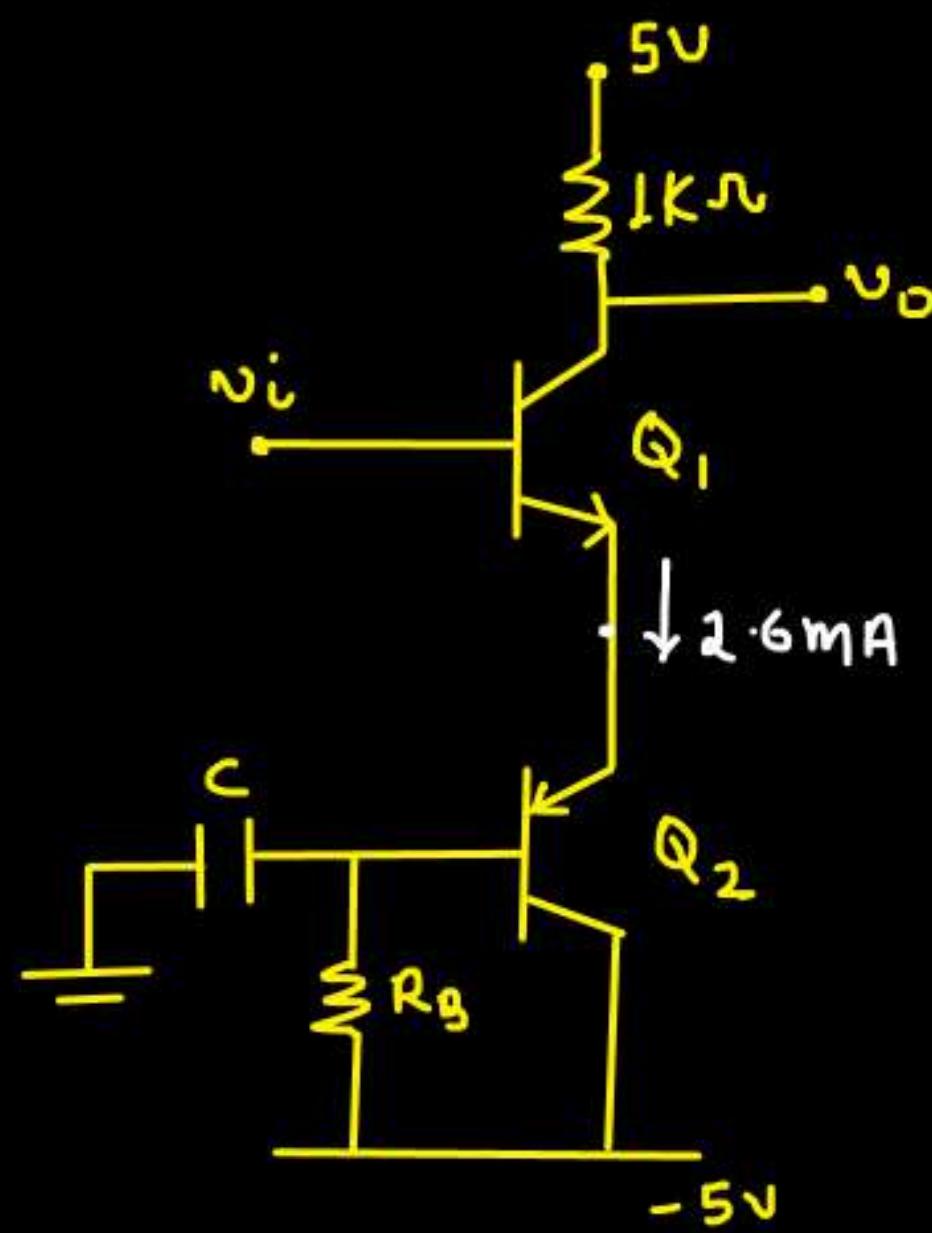

$Q_1$  and  $Q_2$  are biased  
with collector current of  
 $2.6\text{mA}$ .

$V_T = 26\text{mV}$ ,  $\beta = \infty$ ,  $V_A = \infty$   
Find small signal voltage  
gain.


PreFusion

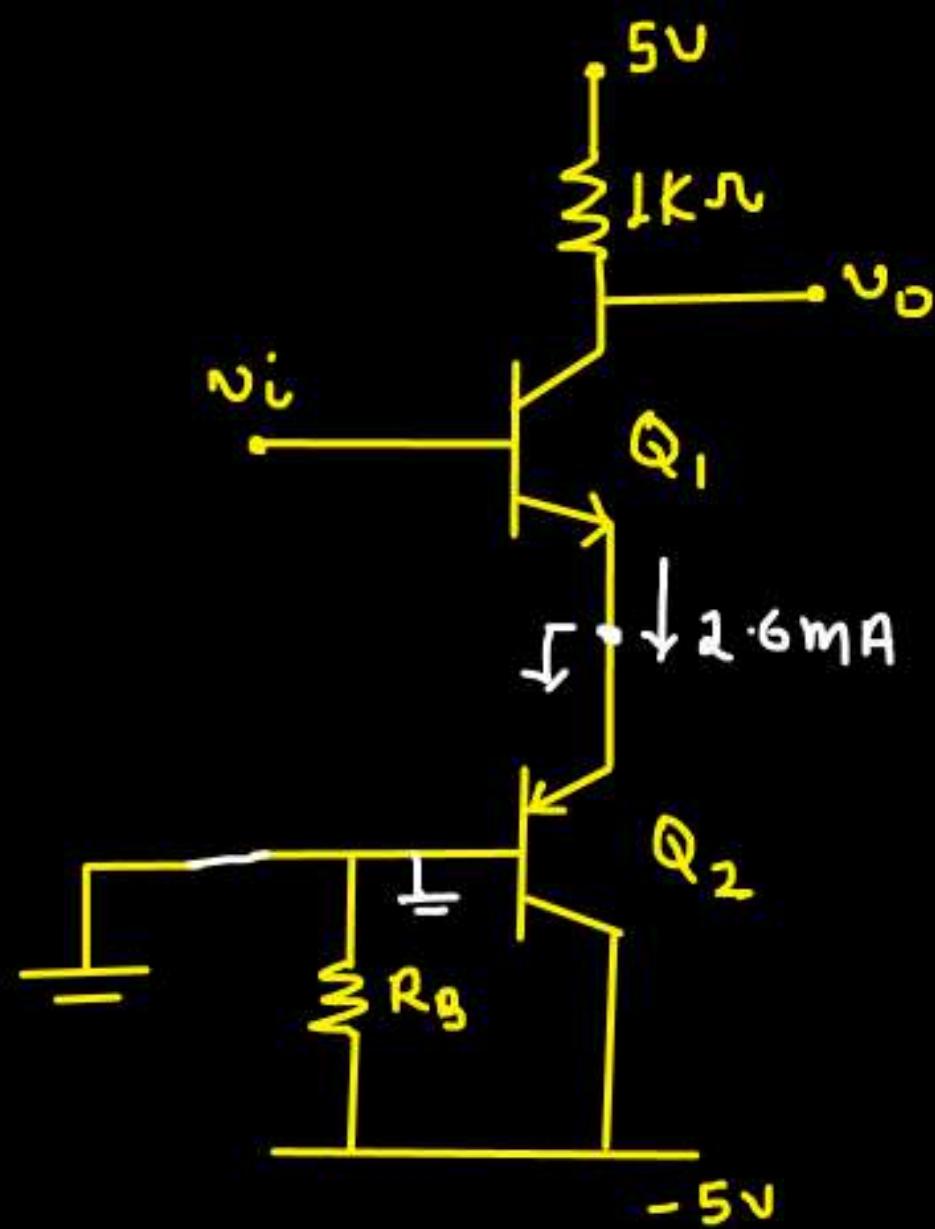

dc Analysis:-

$$\delta m = \frac{I_c}{V_T} = \frac{2.6m}{26m} = \frac{1}{10}$$


$$\gamma_D = \frac{V_A}{I_C} = \infty$$

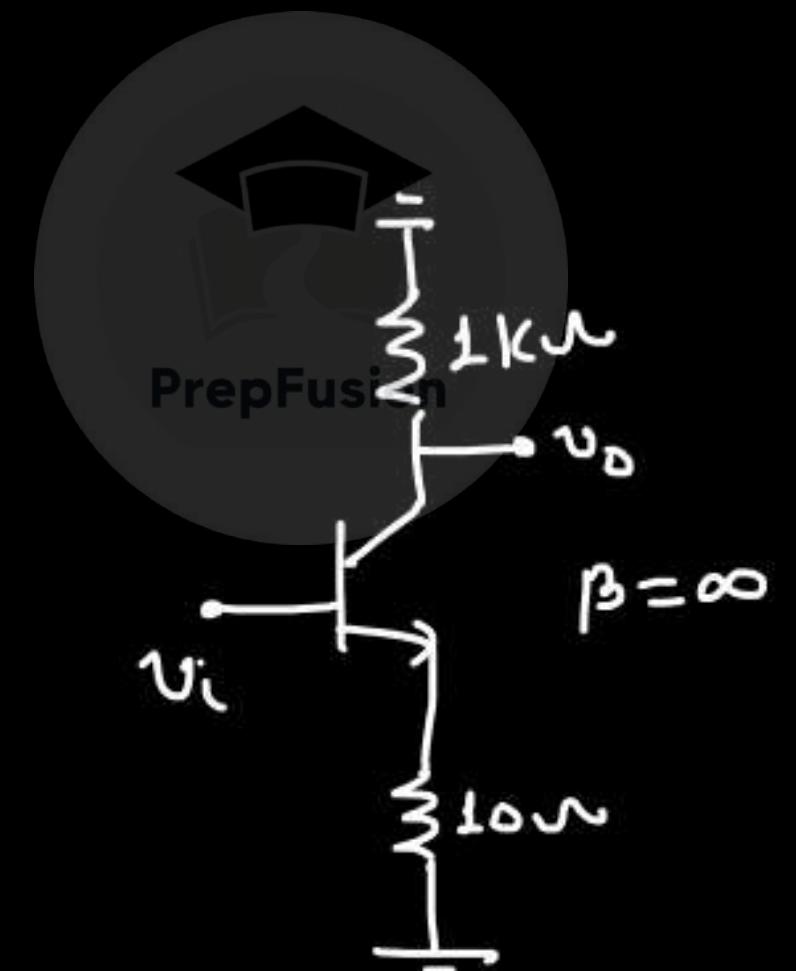

$$\begin{aligned} A_V &= -\frac{\delta m R_L}{(1 + \delta m R_S)} \\ &= -\frac{100}{(+1)} \end{aligned}$$

$$A_V = -50$$

Q.

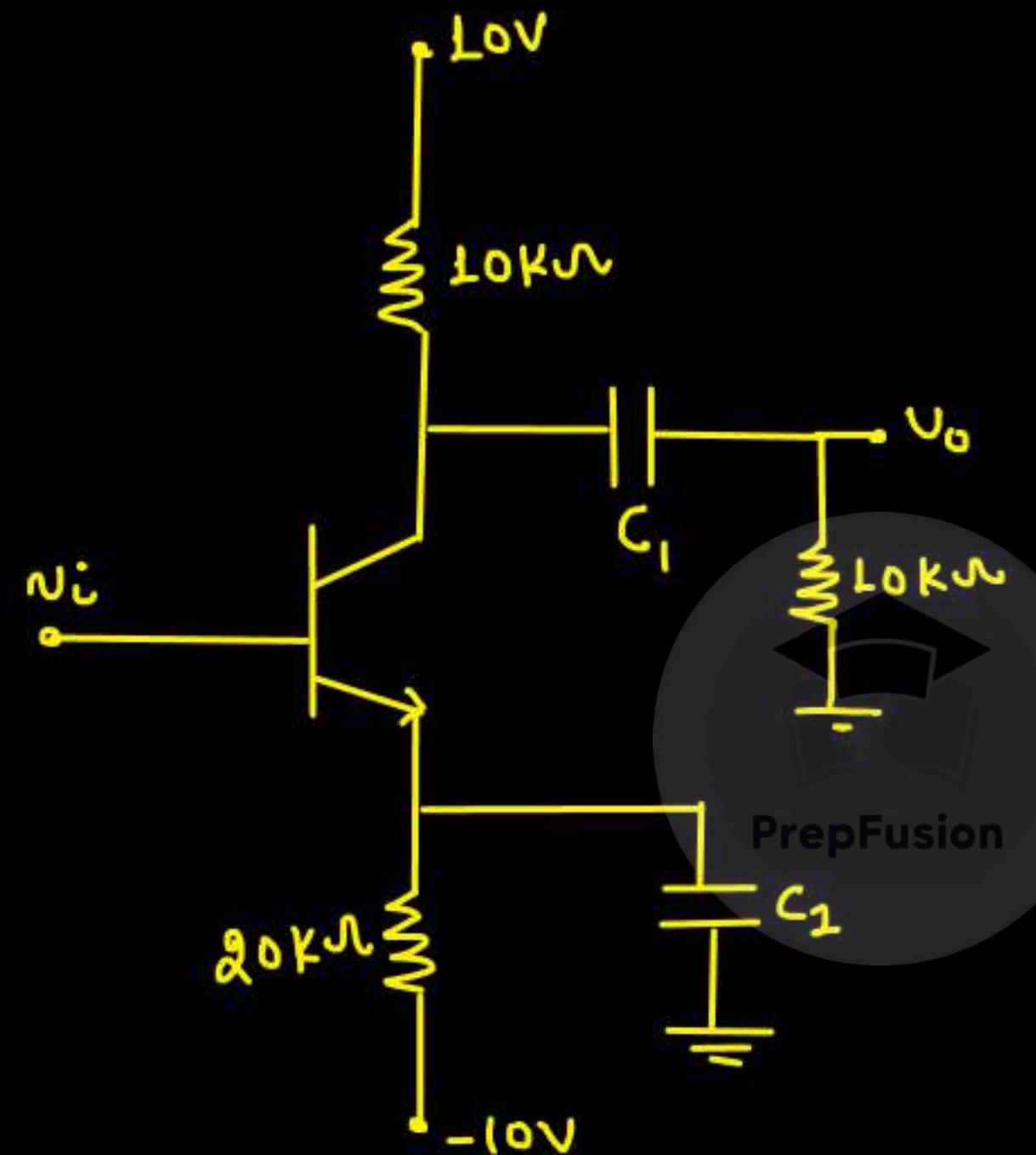

$$\gamma_D = \infty$$

$$\beta = \infty$$


$$V_{BE} = 0.7V$$

$$V_T = 26mV$$

Capacitors are shorted at  
Signal frequency.

Find Small Signal voltage gain.

## dc Analysis:-

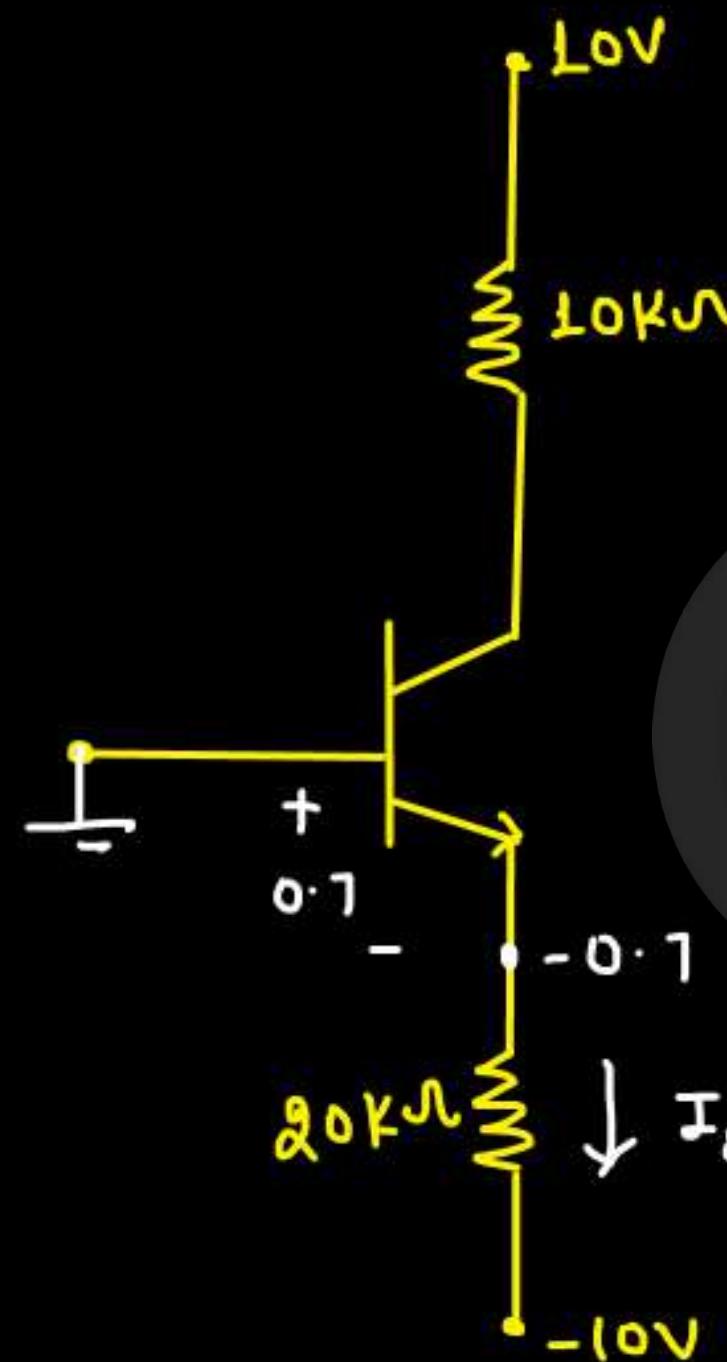


$$g_m = \frac{I_c}{V_T} = \frac{0.465\text{mA}}{26\text{mV}}$$

$$g_m = 17.88\text{mS}$$

$$\downarrow I_E = I_C = \frac{9.3}{20K} = 0.465\text{mA}$$

## Ac Analysis:-

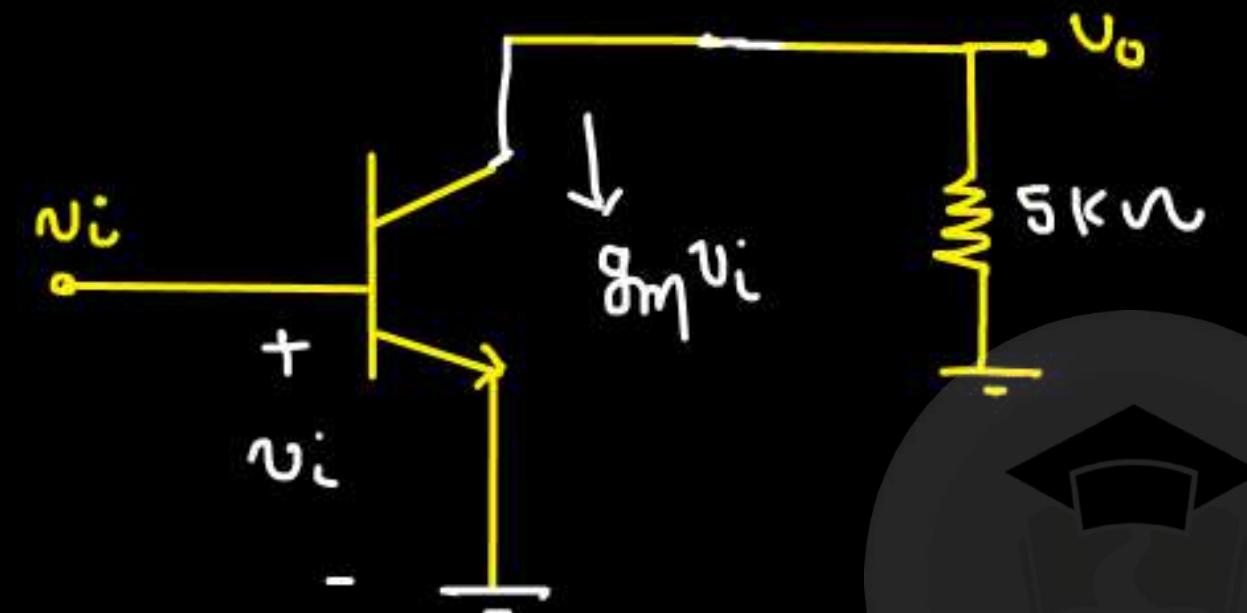

$$v_o = -g_m \times 5\text{k} v_i$$


$$\alpha_v = -17.08 \times 5$$

$$\alpha_v = -85.4 \text{ V/V}$$



## Assignment - 20

Q.

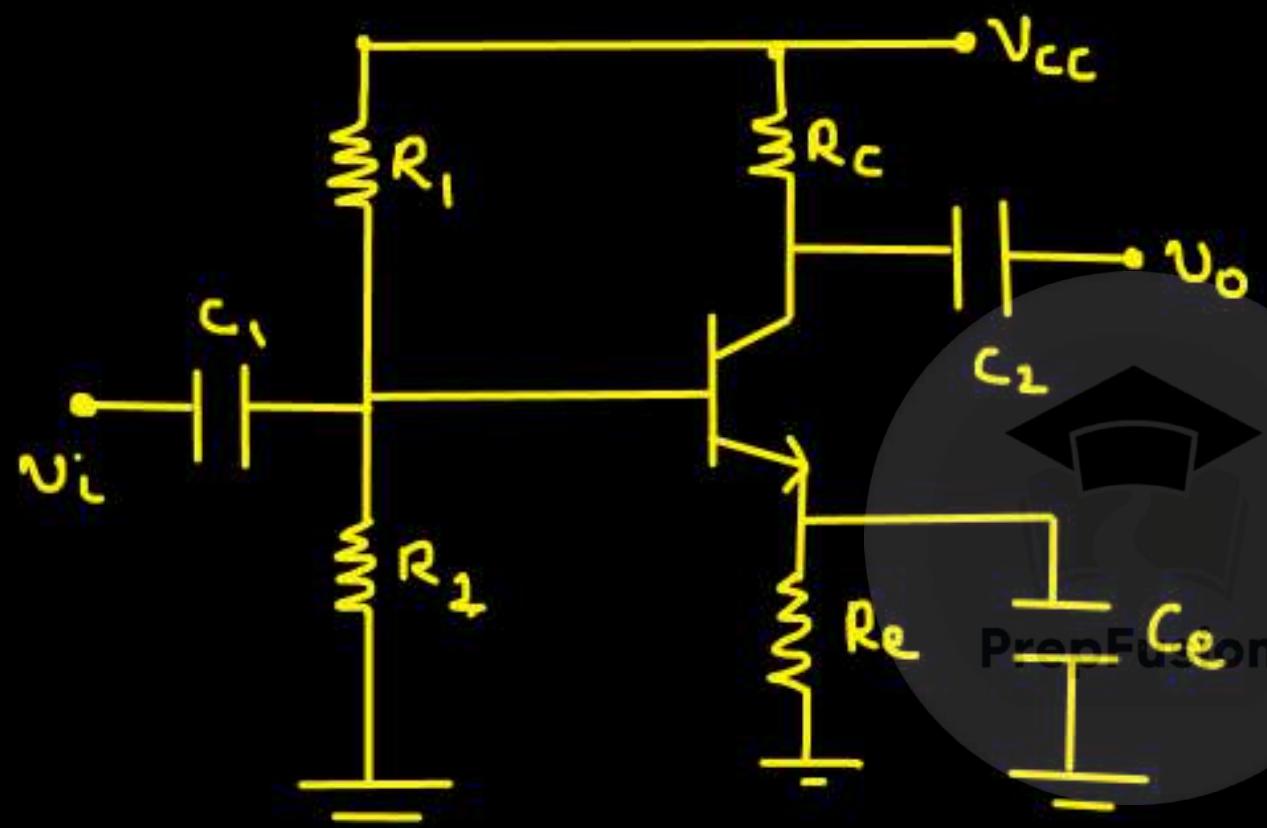

Find the ratio of small signal voltage gain when emitter resistance  $R_e$  is bypassed by  $C_e$  to when it's not bypassed.

$$h_{fe} = \beta$$

$$h_{ie} = r_\pi$$

$$h_{oe} = \frac{1}{r_o}$$


(a) L

(b)  $h_{fe}$

$$(c) \frac{(1+h_{fe})R_e}{h_{ie}}$$

~~$$(d) 1 + \frac{(1+h_{fe})R_e}{h_{ie}}$$~~

When  $R_E$  is bypassed :-

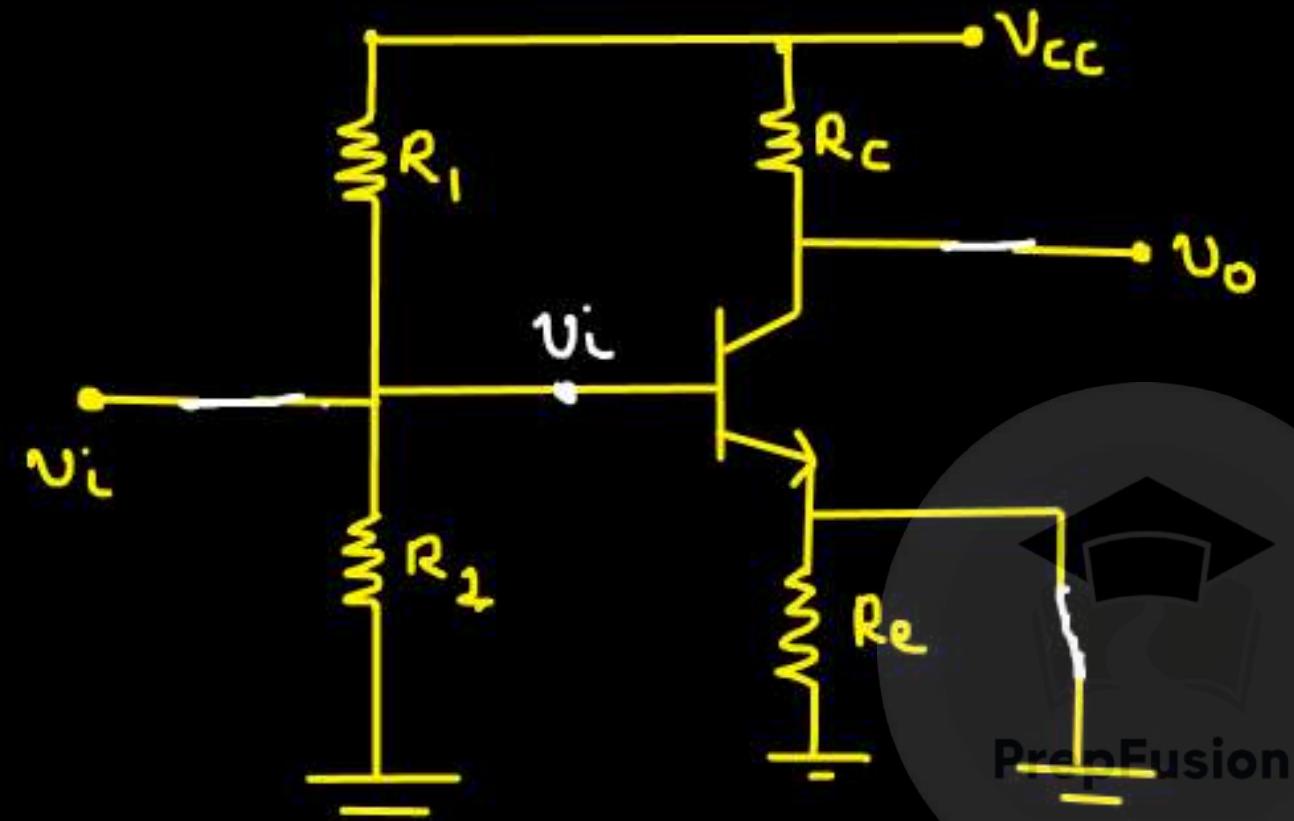



$$V_o = -g_m R_C V_i$$

$$\approx -\frac{\beta}{2\pi} R_C V_i$$

$$A_{Vi} = -\frac{h_{fe}}{h_{ie}} R_C$$

$$\tau_{\pi} = \frac{\beta}{g_m}$$

When  $R_E$  is not bypassed :-

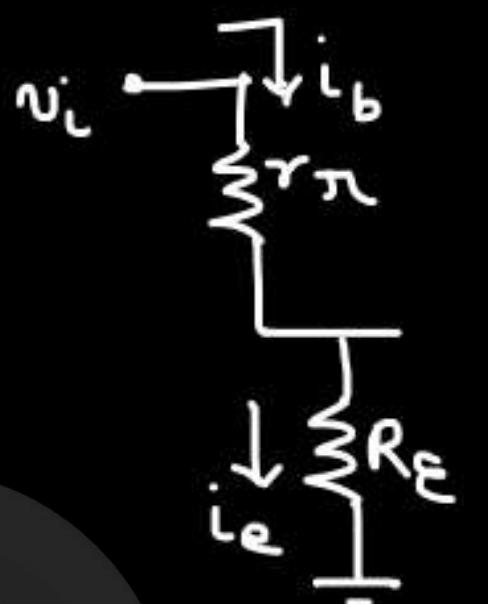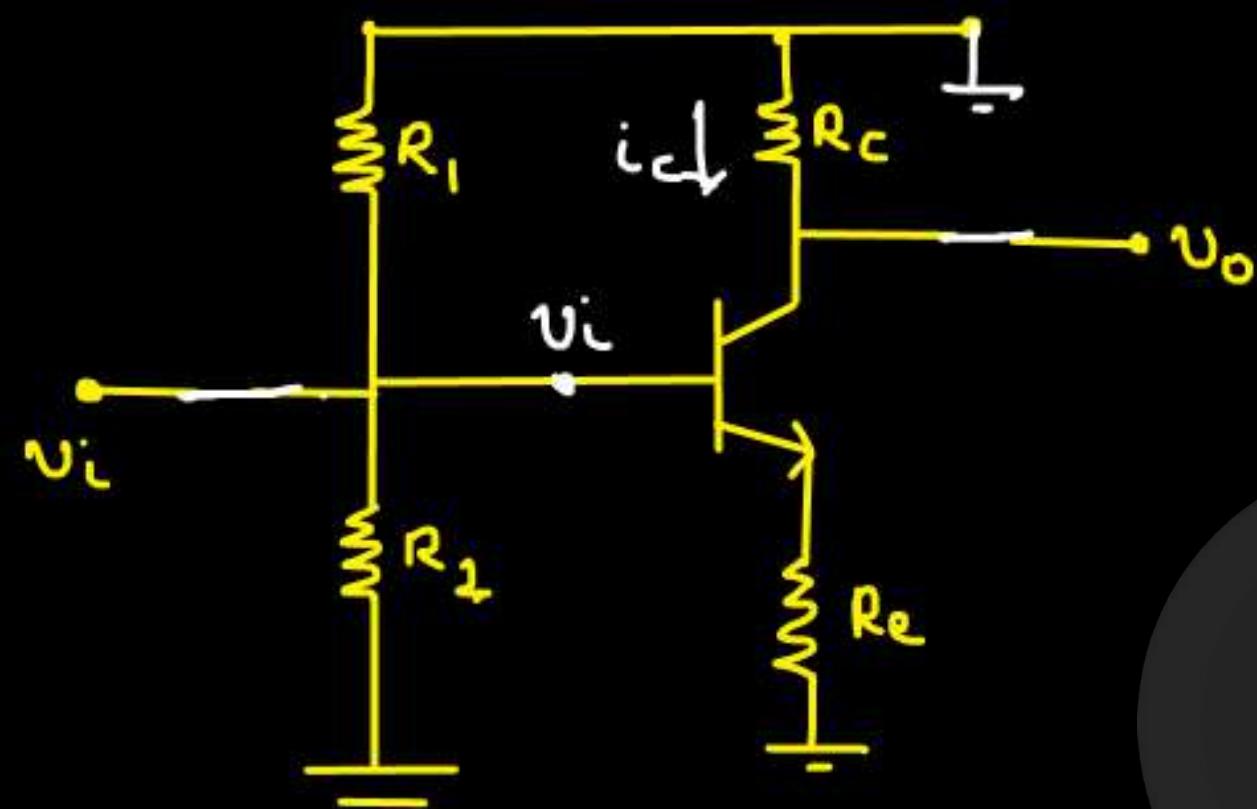

$$v_i = [r_\pi + (\beta + 1) R_E] i_b$$

$$i_c = \frac{\beta v_i}{r_\pi + (\beta + 1) R_E}$$


$$\frac{\Delta v_1}{\Delta v_2} = \frac{r_\pi + (\beta + 1) R_E}{r_\pi}$$

$$= 1 + \left( \frac{\beta + 1}{r_\pi} \right) R_E = \left[ 1 + \left( \frac{h_{fe} + 1}{h_{ie}} \right) R_E \right]$$


$$v_o = -i_c R_C$$

$$\Delta v_2 = \frac{-\beta R_C}{r_\pi + (\beta + 1) R_E}$$

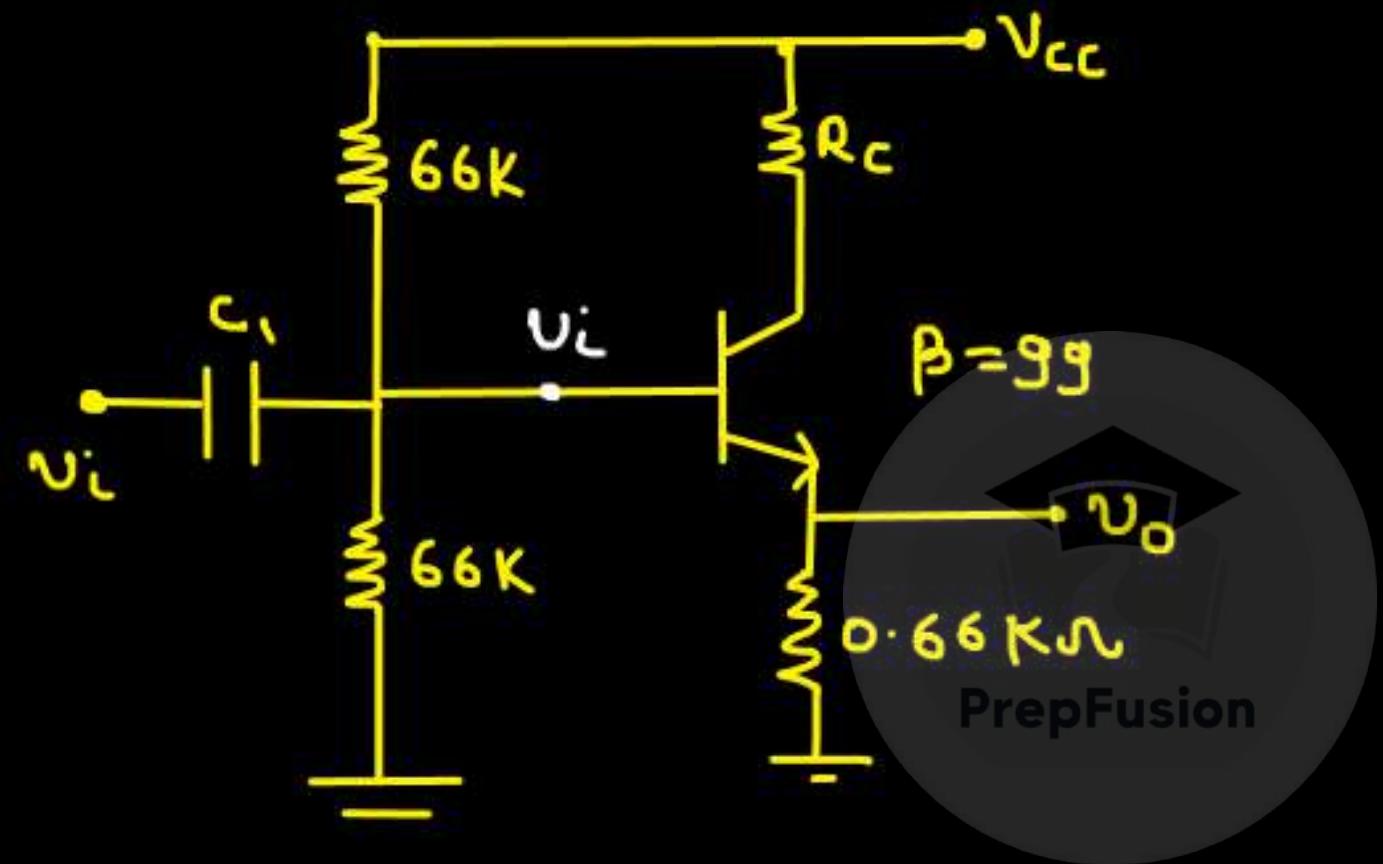Q. Find small signal voltage gain. [ $v_A = \infty$ ]



$$r_{\pi} = 1k\Omega$$

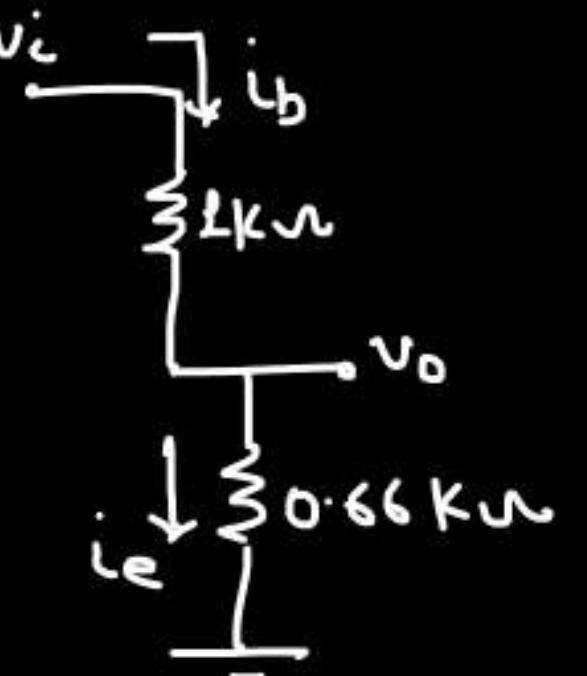

$$v_i = 1k i_b + 0.66k i_e$$


$$\begin{aligned} v_i &= 10 i_e + 660 i_e & \left\{ i_b = \frac{i_e}{100} \right\} \\ i_e &= \frac{v_i}{670} \quad \text{--- (2)} \end{aligned}$$

$$v_o = (0.66k) i_e \quad \text{--- (1)}$$

$$v_o = \frac{660 \times v_i}{670}$$

$$\approx v_o = 0.985$$

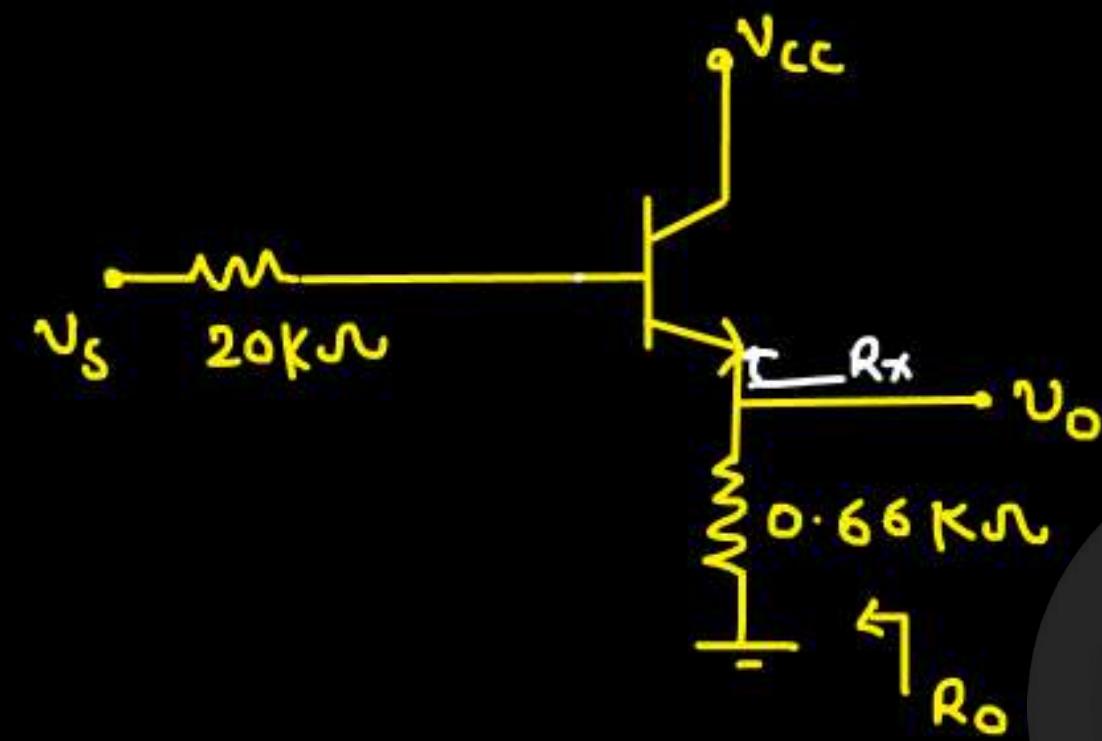Q. Find small signal output Resistance  $R_o$ .




$$h_{fe} = 99, h_{ie} = 2\text{k}\Omega$$


$$h_{oe} = 0$$

→  $r_o = \infty$   
 $\beta = 99$   
 $r_{\pi} = 2\text{k}\Omega$


PrepFusion

$$R_o = 660 \parallel R_x$$

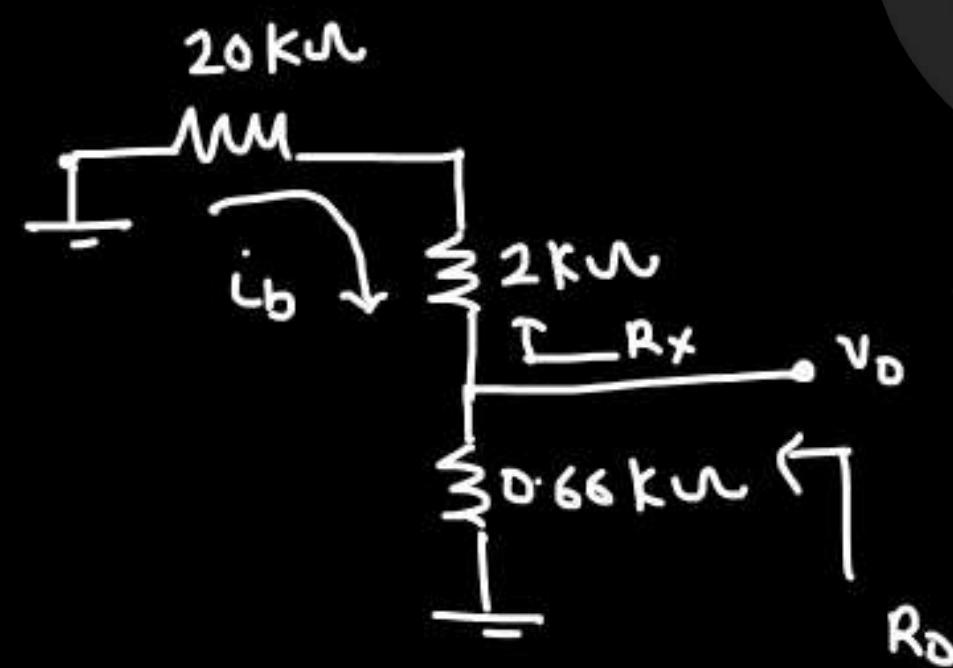

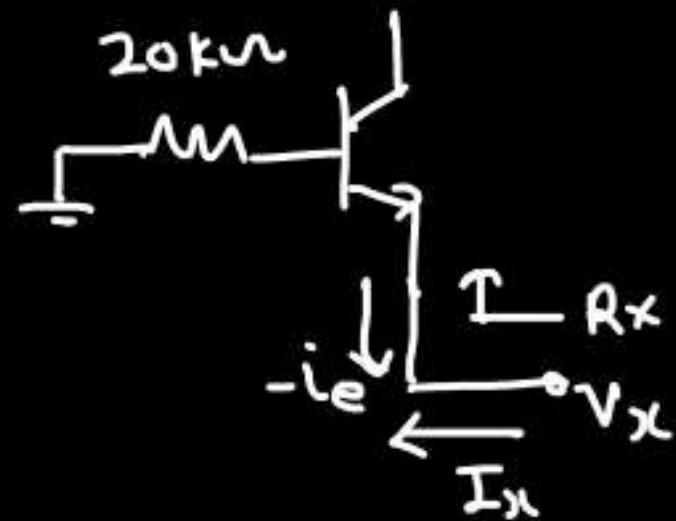
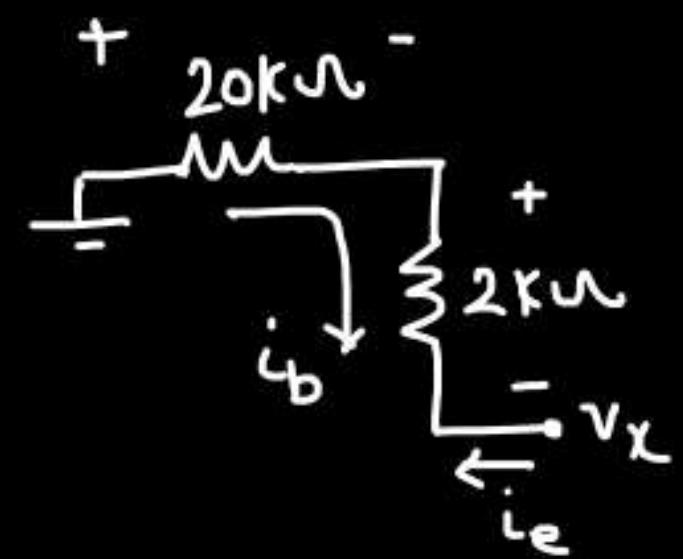
$$R_x = \frac{v_x}{i_x} = -\frac{v_x}{i_e}$$



$$\begin{aligned} v_x &= -22K i_b \\ &= -22K \times i_e \end{aligned}$$


$$v_x = -220 i_e$$

$$R_x = 220 \Omega$$

$$R_o = 220 \| 165 \Omega$$

$$R_o = 165 \Omega$$

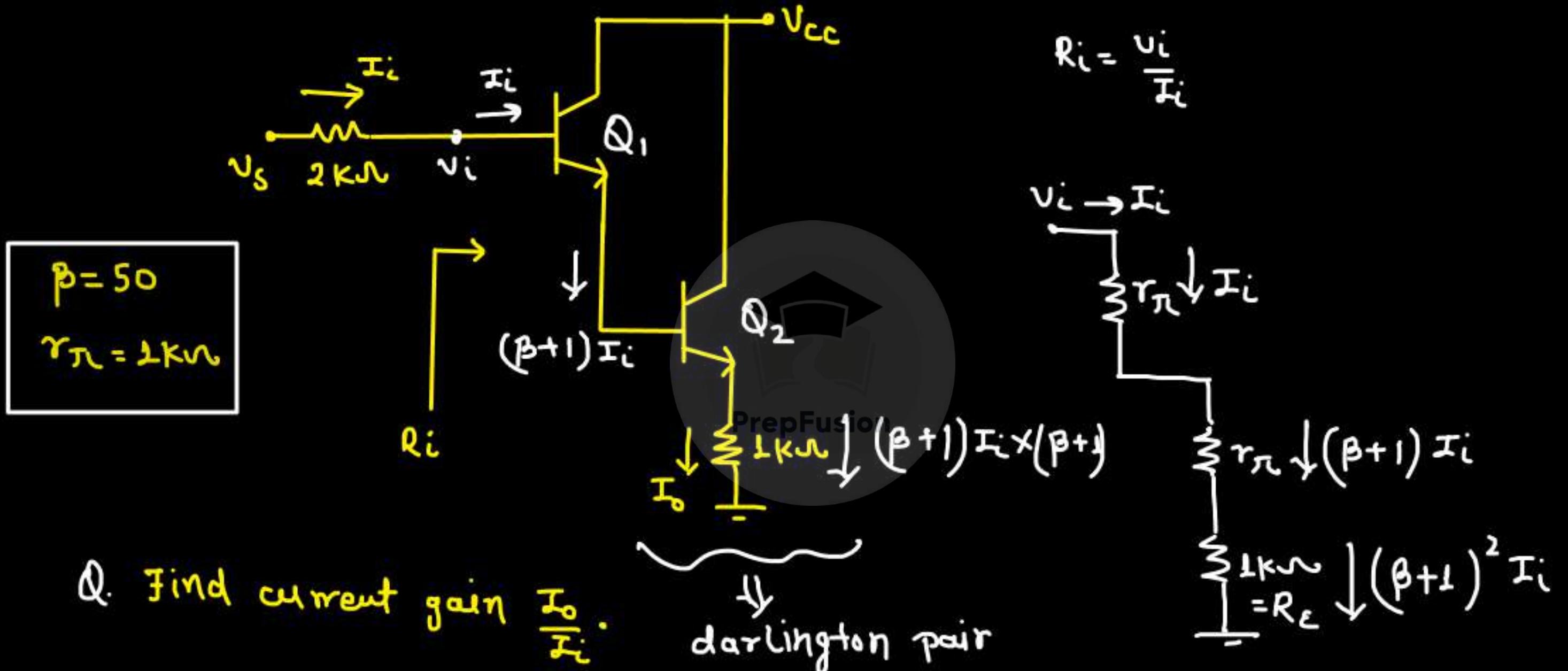**Q.** Find the value of input impedance. [CC-CC]



**Q.** Find current gain  $\frac{I_o}{I_i}$ .

$$V_i = r_{\pi} I_i + r_{\pi} (\beta + 1) I_i + (\beta + 1)^2 I_i \times R_E$$

$$R_i = r_{\pi} + r_{\pi} (\beta + 1) + (\beta + 1)^2 R_E$$

$$R_i = 1\text{k}\Omega + 51\text{k}\Omega + (51)^2 \times 1\text{k}\Omega$$

$$R_i = 2.653\text{ M}\Omega$$


$$I_o = (\beta + 1)^2 I_i$$

$$\frac{I_o}{I_i} = (51)^2 = 2601$$



PrepFusion

Q.

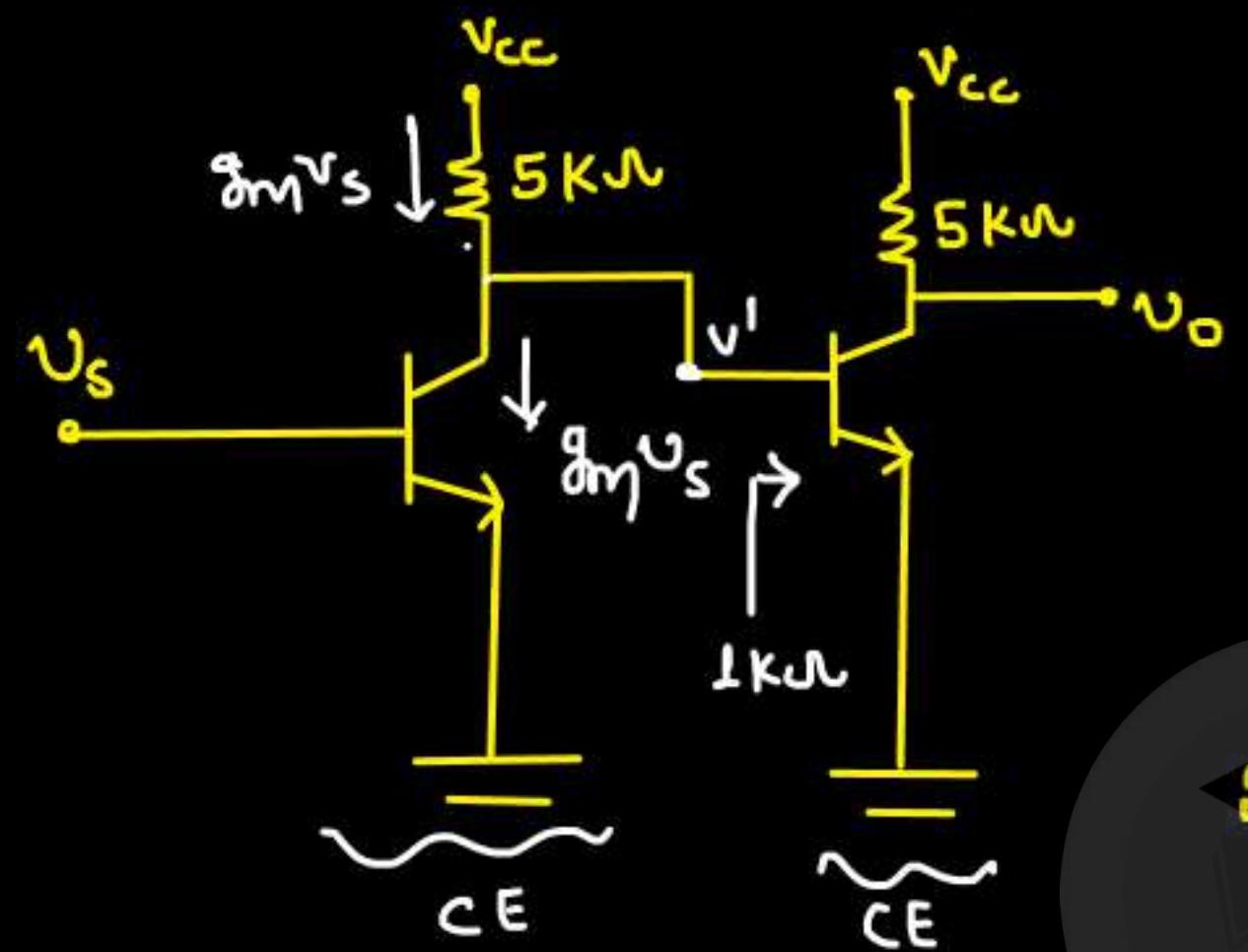

$$r_{\pi} = 1 \text{ k}\Omega$$


$$\beta = 100$$

Determine small signal voltage gain.

PrepFusion



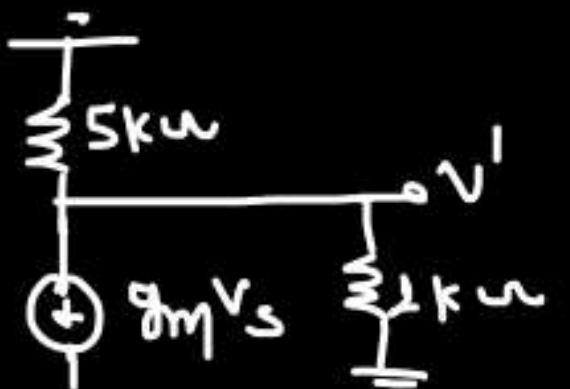
$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{1000} = 0.1 = 100 \text{ mV}$$



$$v^I = -g_m u_s \times \frac{5}{6} \text{ k} = -100 \text{ m} \times \frac{5}{6} \text{ k} \times u_s$$

$$v^I = -\frac{500}{6} u_s$$

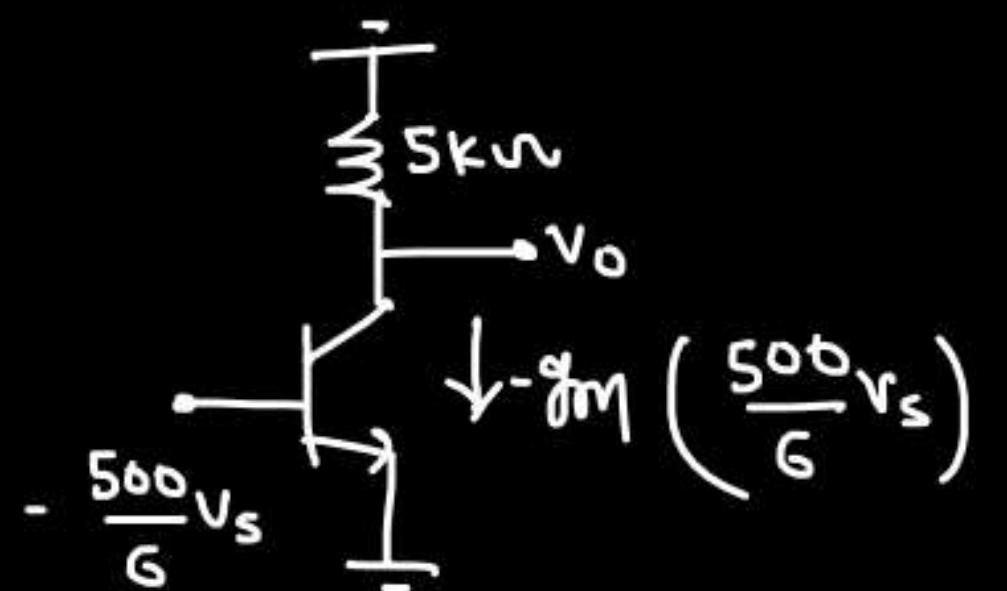

$$v_o = g_m \times 5k \times \frac{500}{6} v_s$$

$$\frac{v_o}{v_s} = 100 \times 5 \times \frac{500}{6}$$


$$A_v = 41666.67$$



Q. Find small signal voltage gain  $\frac{V_o}{V_s}$ .

\*

$$\beta = 100$$

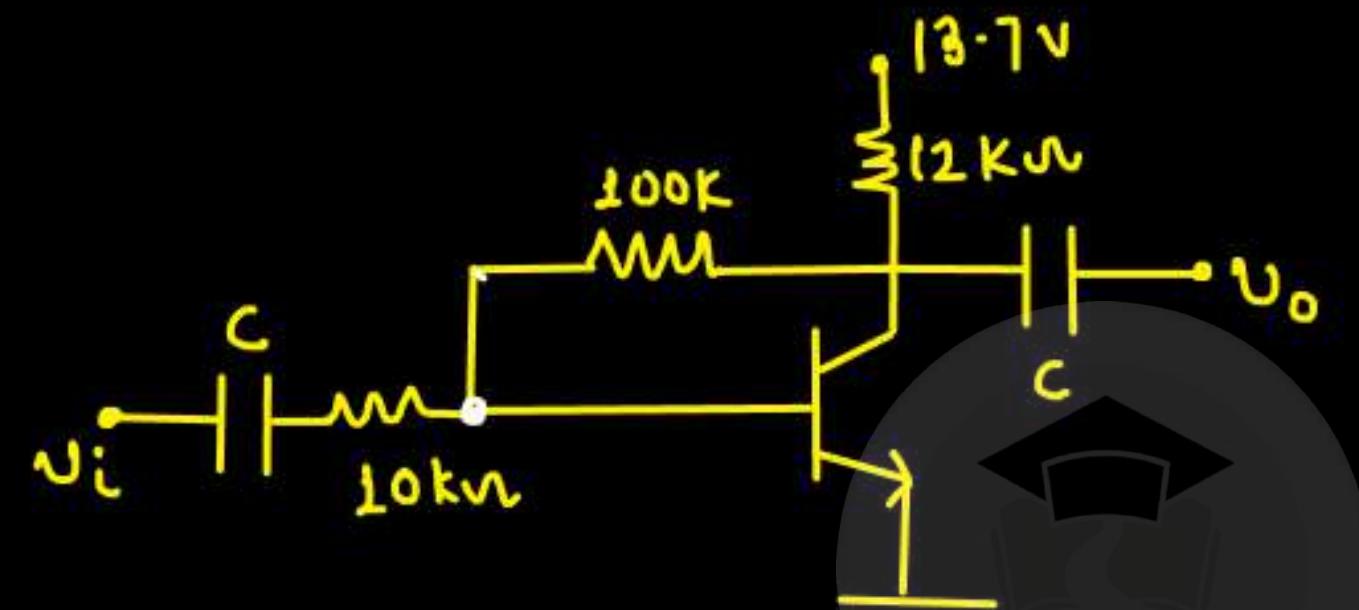


$$r_{\pi} = \frac{\beta}{g_m}$$

PrepFusion

- (a)  $\approx 200$  (b)  $\approx 100$  (c)  $\approx 20$  (d)  $\approx 10$

## DC Analysis:-

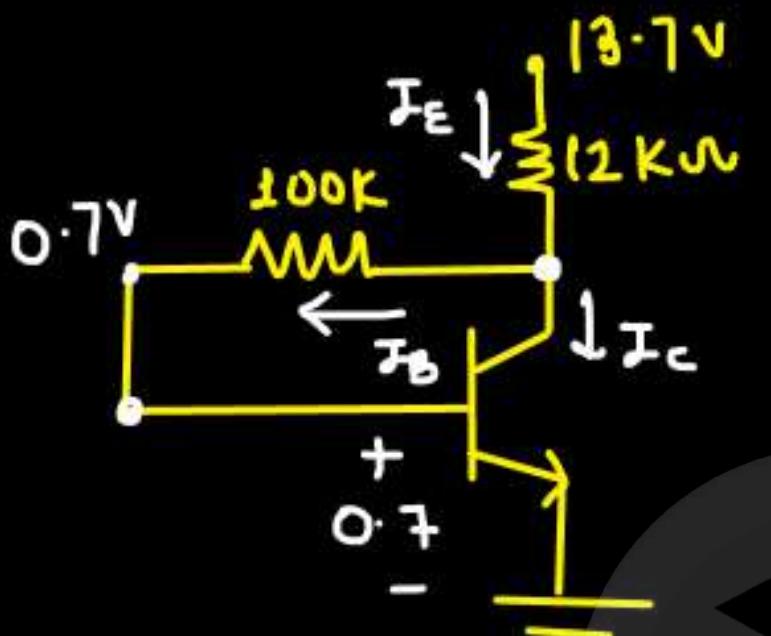

$$13.7 = 12k \times I_E + 100k \times I_B + 0.7$$

PrepFusion

$$13 = 12k \times 10I_B + 100k \times I_B$$

$$I_B = 9.9 \mu\text{Amp}$$


$$I_C = 0.99 \text{ mAmp}$$

$$\beta_m = \frac{0.99m}{25m} = 39.63m$$

$$\tau_{RL} = \frac{\beta}{\beta_m} = \frac{100}{39.63m}$$

$$\tau_{RL} = 2.52 \text{ k}\Omega$$

## Ac Analysis:-

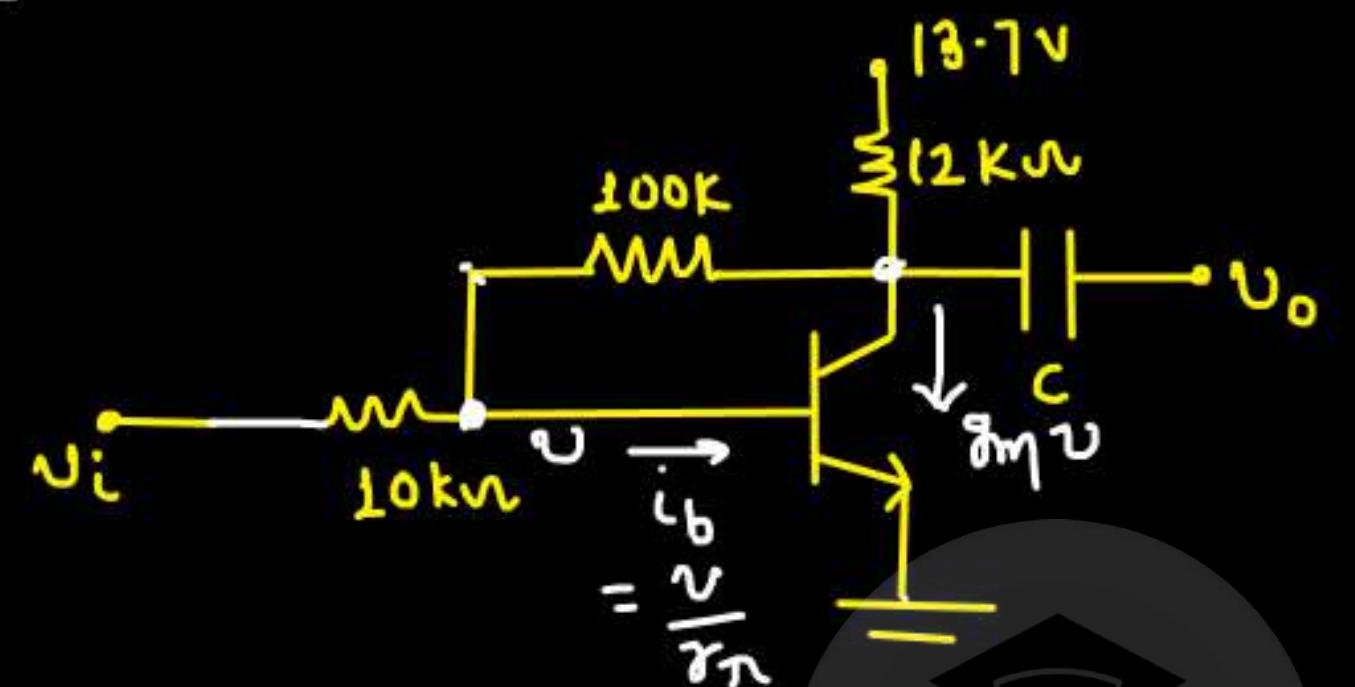

$$\frac{v - v_i}{10\text{k}} + \frac{v - v_o}{100\text{k}} + \frac{v}{r_\pi} = 0$$

$$\frac{v}{10\text{k}} + \frac{v}{100\text{k}} + \frac{v}{2.5\text{k}} = \frac{v_i}{10\text{k}} + \frac{v_o}{100\text{k}} \rightarrow \textcircled{1}$$

$$\frac{v_o - v}{100\text{k}} + \frac{v_o}{12\text{k}} + g_m v = 0$$

$$\frac{v_o}{100k} + \frac{v_o}{12k} = \frac{v}{100k} - \frac{v}{(1/g_m)}$$

$$1/g_m = 25$$

$$\frac{v_o}{|100k||12k|} = -\frac{v}{25}$$

$$v = -2.33m v_o \quad \text{--- (2)}$$

By eq<sup>n</sup> ① and ②

Preparation

$$\frac{-2.33m v_o}{10k||200k||2.5k} = \frac{v_i}{10k} + \frac{v_o}{100k}$$


$$-0.972 \times 10^{-6} v_o - v_o \times 10^{-5} = \frac{v_i}{10k}$$

$$-1.0572 \times 10^{-5} v_o = \frac{v_i}{10k}$$

$$\frac{v_o}{v_i} \approx -9.1$$

$$|A_v| \approx 10$$

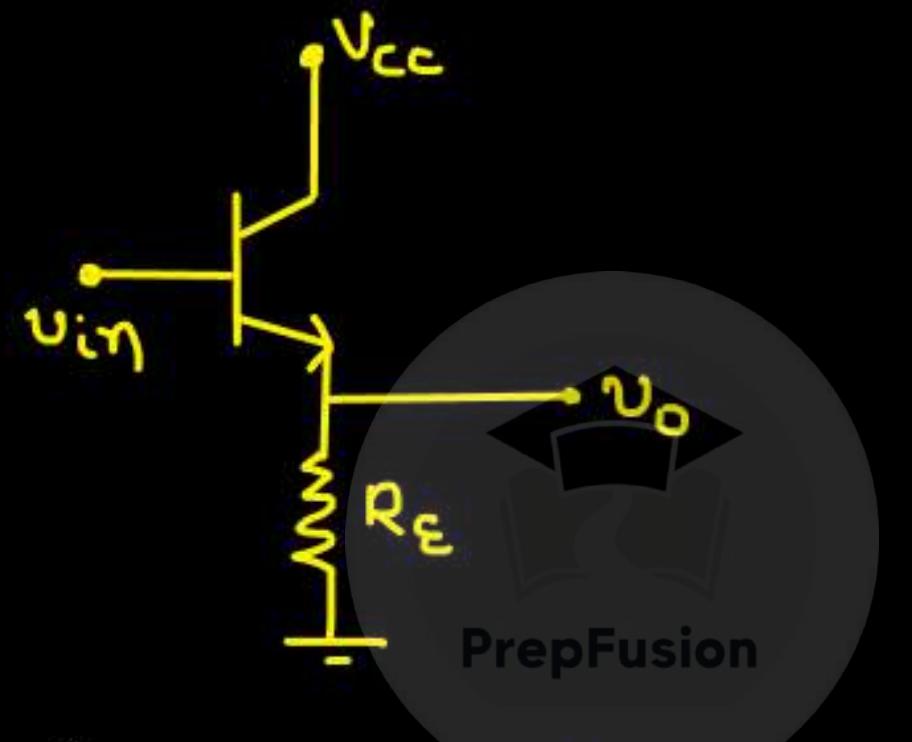Q. Which condition would ensure a nearly constant gain for large range of  $R_E$ ?



- (a)  $g_m R_E \ll 1$      (b)  $I_c R_E \gg V_T$     (c)  $g_m r_o \gg 1$     (d)  $V_{BE} \gg V_T$

→

$$v_o = i_e R_E \quad \text{--- (1)}$$

$$v_{in} = \frac{r_\pi \times i_e}{\beta + 1} + R_E i_e \quad \text{--- (2)}$$

$$V_o = \frac{V_{in} R_E}{\frac{r_\pi}{\beta+1} + R_E}$$

$$\text{Av} = \frac{R_E}{\frac{r_\pi}{\beta+1} + R_E}$$

For const. gain

$$\frac{r_\pi}{\beta+1} \ll R_E$$

$$\frac{1}{g_m} \ll R_E$$

$$g_m R_E \gg 1$$

$$I_C R_E \gg V_T$$

Q.

$$\beta = 80$$

$$V_A = \infty$$

$$V_{EB} (\text{PN}) = 0.7$$

$$V_T = 25.9 \text{ mV}$$


Find mid band voltage gain ( $\alpha_v$ ).

→ DC analysis

$$9V = 12k \times I_E + 0.7 + 2k \times I_B$$

$$8.3 = 12k \times 81 I_B + 2k I_B$$


$$I_C = 0.743 \text{ mA}$$

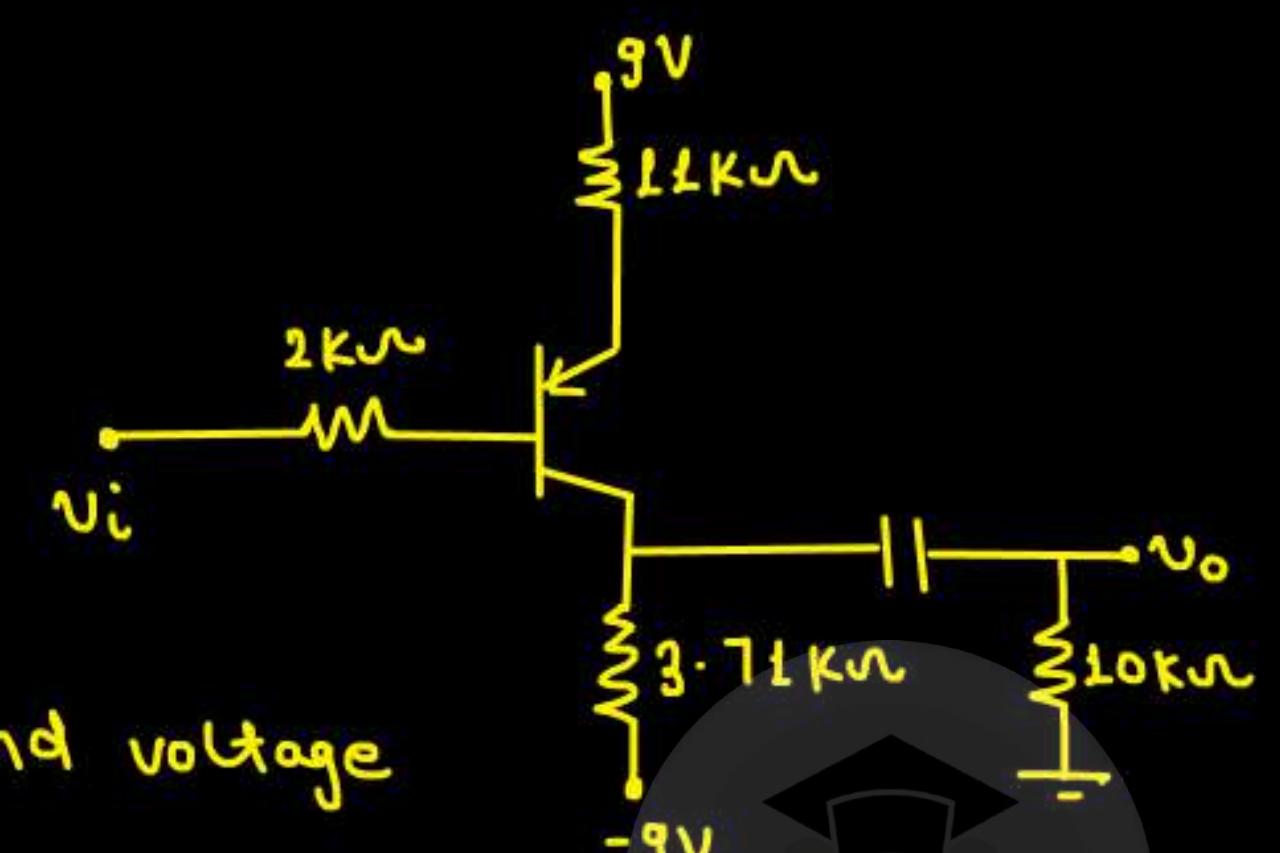


$$r_\lambda = \frac{80}{28.7 \text{ m}} = 2.78 \text{ k}\Omega$$

$$\alpha_v = 28.7 \text{ mV}$$

## AC Analysis :-

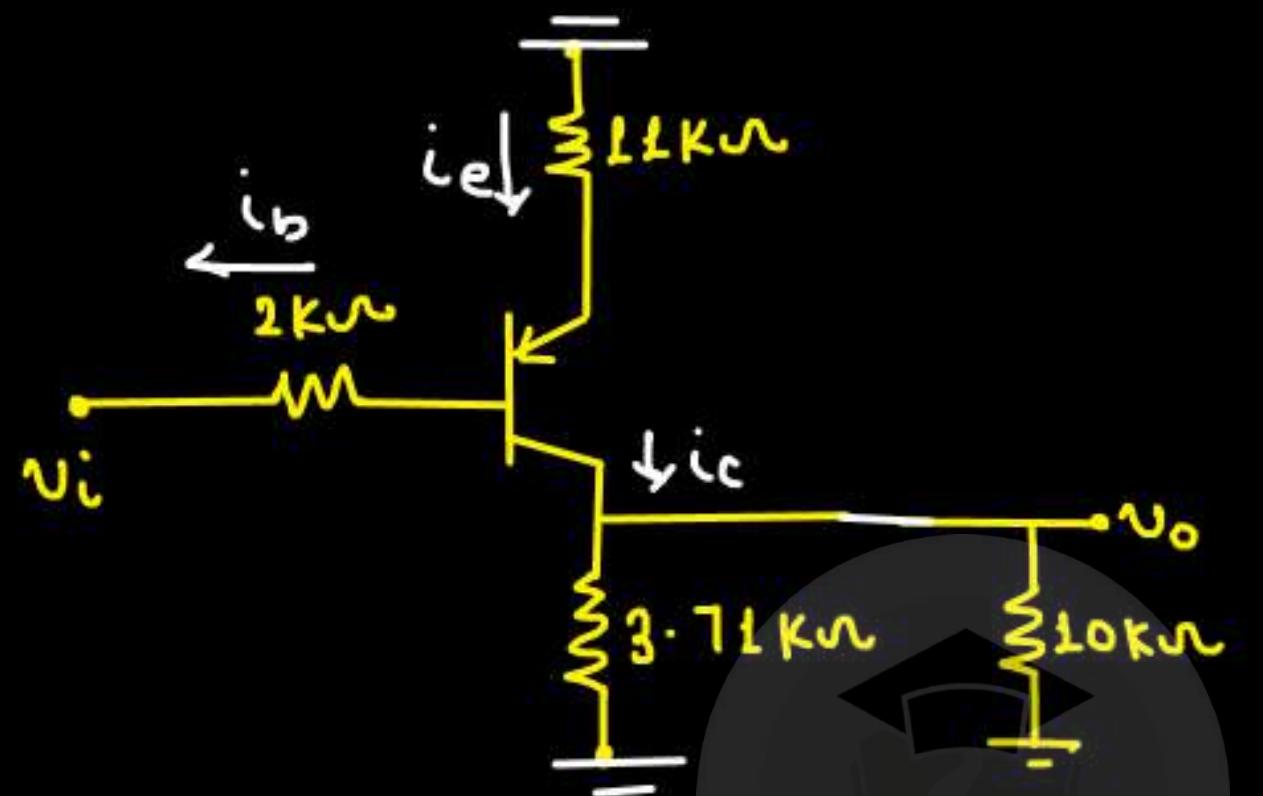
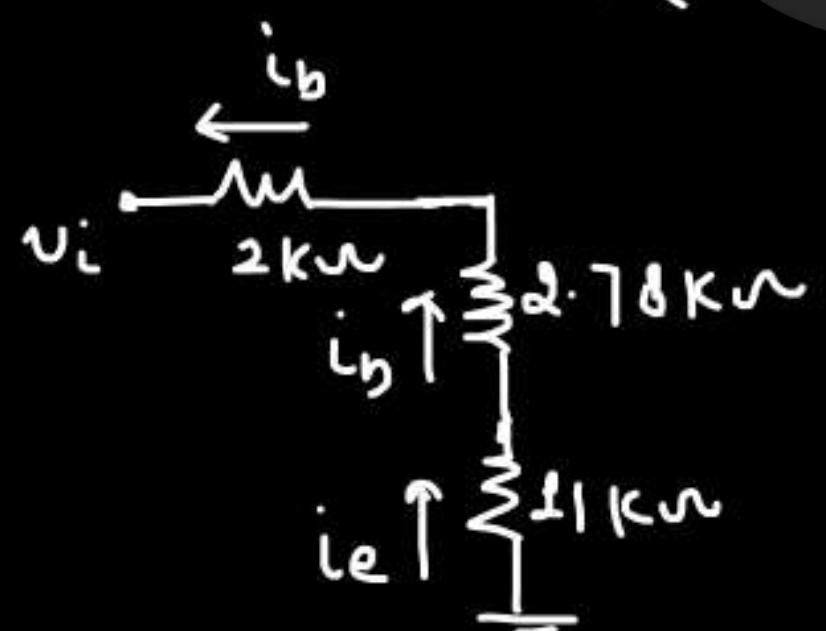
$$v_o = i_c (3.71k \parallel 10k) - 0 \quad \text{①}$$




$$\begin{aligned} -v_i &= 4.78k \times i_b + 1.1k \times i_e \\ i_c &= \frac{-v_i \times 80}{4.78k + 1.1k \times 81} \end{aligned}$$

$$\frac{v_o}{v_i} = \frac{-80 (3.71k \parallel 10k)}{4.78k + (1.1k \times 81)}$$

$$\frac{v_o}{v_i} = -0.24 \text{ V/V}$$


Q.

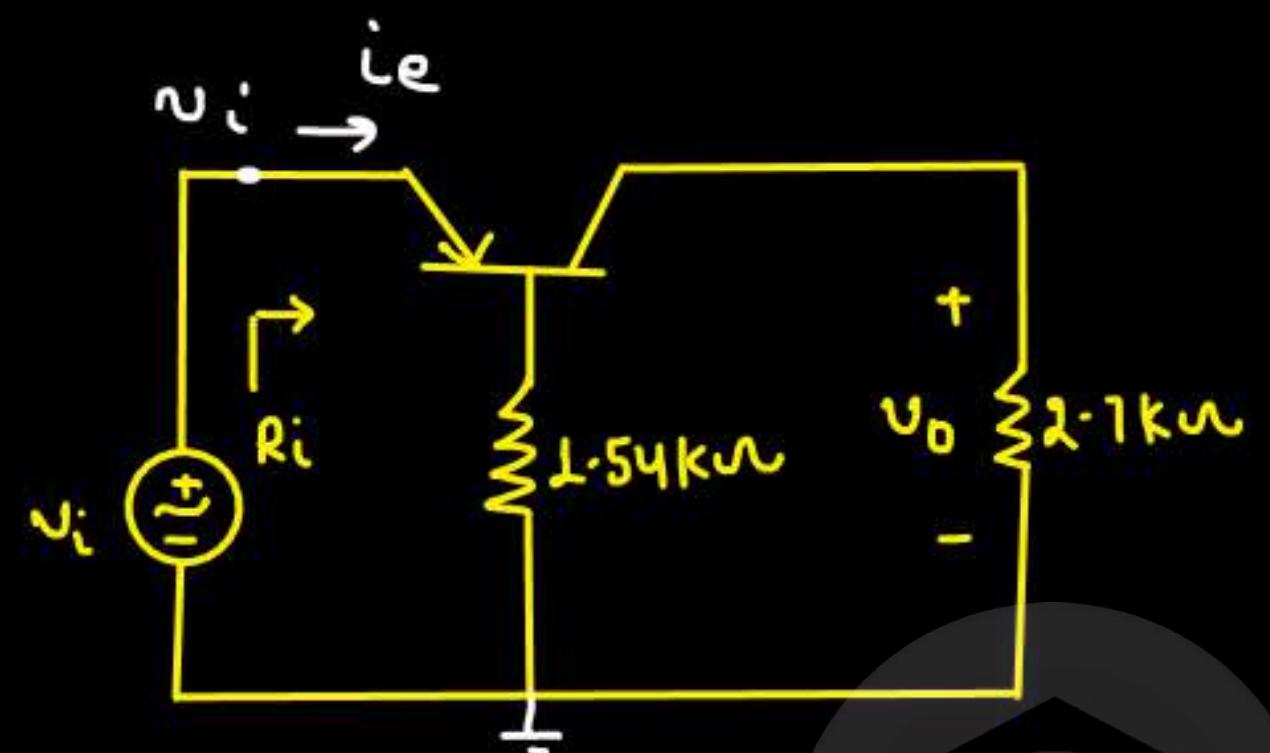

$$R_i = \frac{v_i}{i_e}$$

$$\begin{aligned} v_L &= 3.48k \times i_b \\ &= 3.48k \times i_e \end{aligned}$$

$$R_i = 45\Omega$$

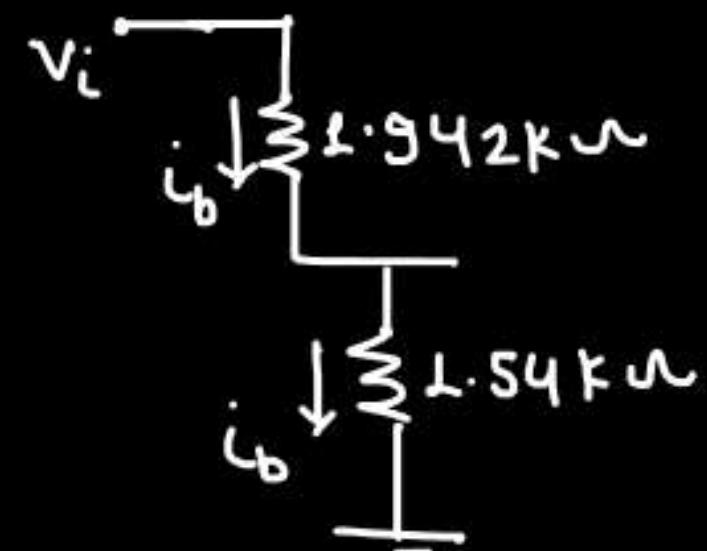

$$I_{CQ} = 1mA$$

$$\beta = 75$$


$$V_T = 25.9mV$$

Find input Resistance?

$$\begin{aligned} r_\pi &= \frac{\beta}{I_C} V_T \\ &= \frac{75 \times 25.9}{1} \\ &= 1.942k\Omega \end{aligned}$$

PrepFusion

Q.

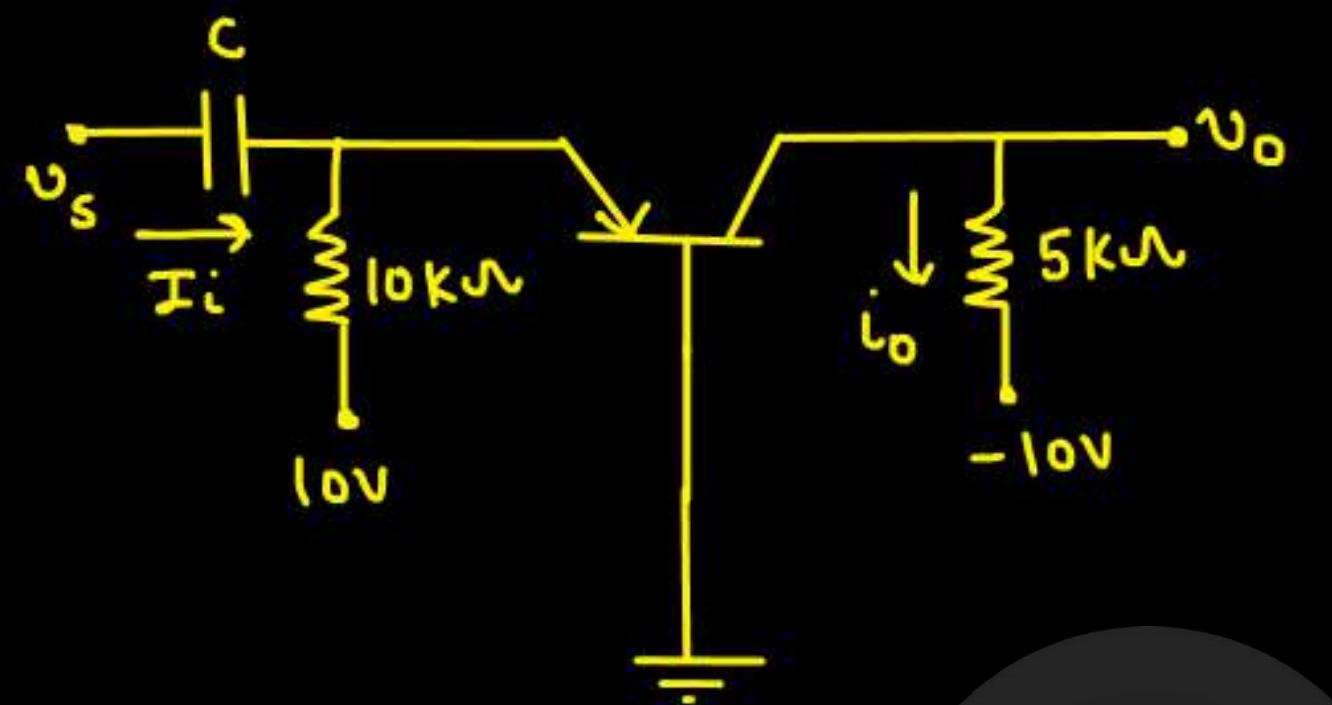

$$\beta = 100$$

$$V_{EB} = 0.7V$$

$$V_T = 26mV$$


$$V_A = \infty$$

(a) find current gain

(b) find voltage gain



PrepFusion

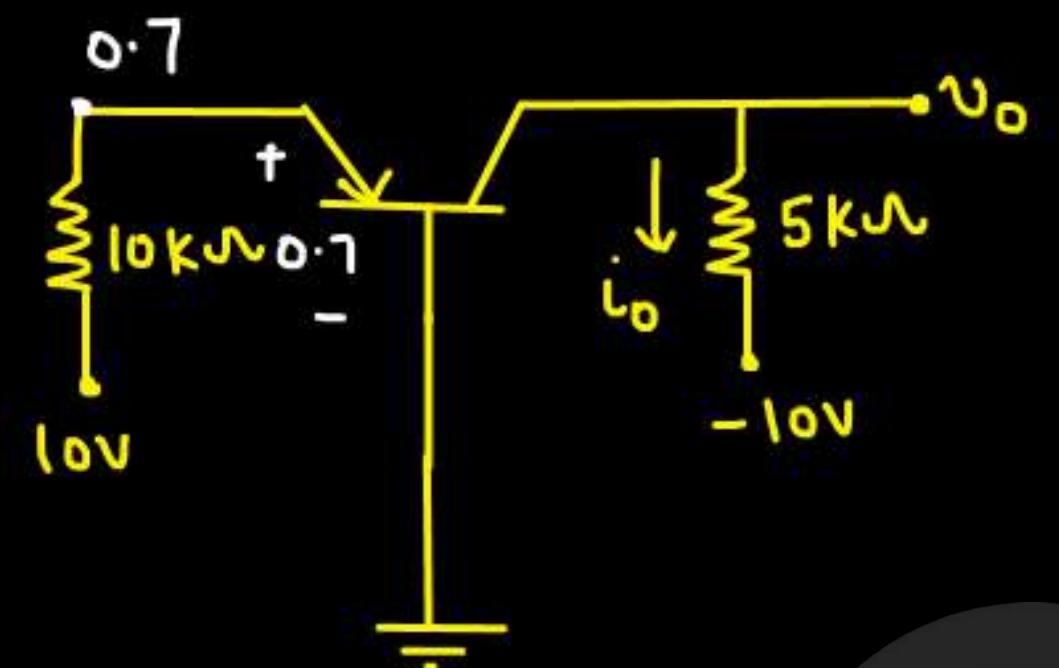


$$I_E = \frac{9.3}{10k}$$

$$I_E = 0.93mA$$

$$I_C = \frac{0.93 \times 100}{20} mA$$

$$\delta m = \frac{I_C}{V_T} = 35.41mV$$



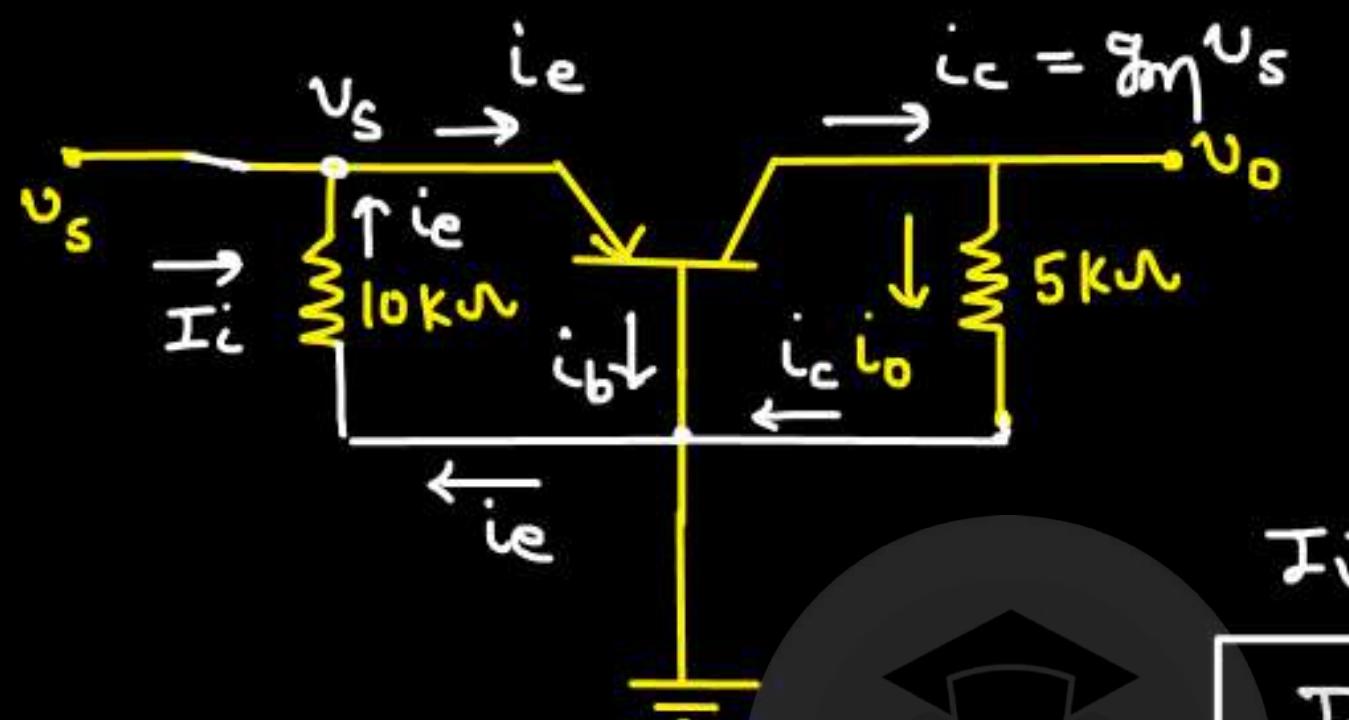



$$I_i = 0 \text{ Amp}$$

$$\frac{I_o}{I_i} = \frac{i_c}{0} = \infty$$

$$v_o = 5k\Omega \times g_m v_s$$

$$\frac{v_o}{v_s} = 35.41 \times 5k$$


$$A_V = 177.1 \text{ V/V}$$

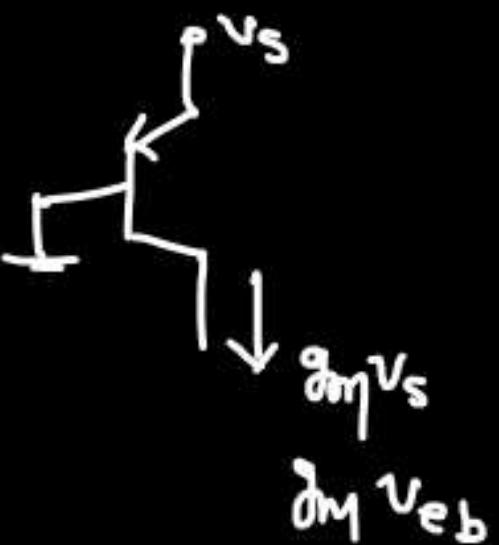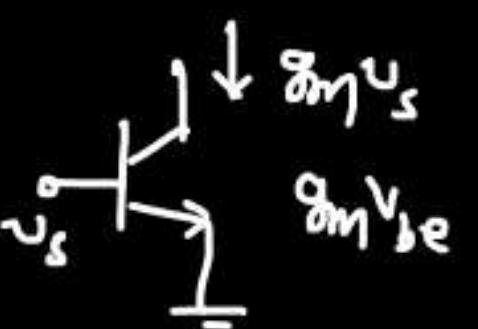

Q. Common Emitter stage has Transconductance  $g_m_1$ ,

Common base stage has Transconductance  $g_m_2$ .

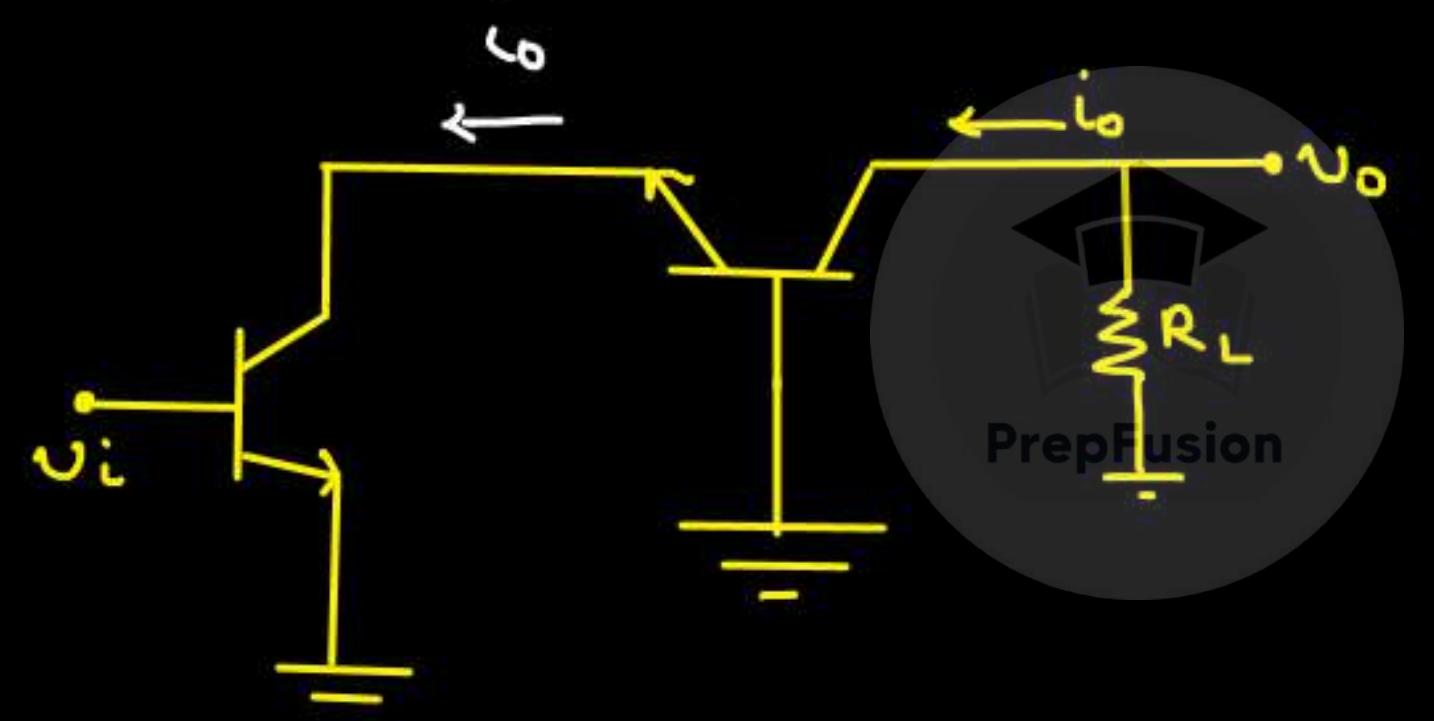Overall Transconductance ( $g_m$ ) of Cascaded Amp. is -



(c)  $g_m_1$

(b)  $g_m_2$

(c)  $\frac{g_m_1}{2}$

(d)  $\frac{g_m_2}{2}$

$$g_m = \frac{i_o}{u_i}$$


$$g_m_1 = \frac{i_o}{u_i}$$

$$g_m = g_m_1$$

Q. Transconductance of  $Q_1$  is  $\text{gm}_1$ .


Transconductance of  $Q_2$  is  $\text{gm}_2$ .

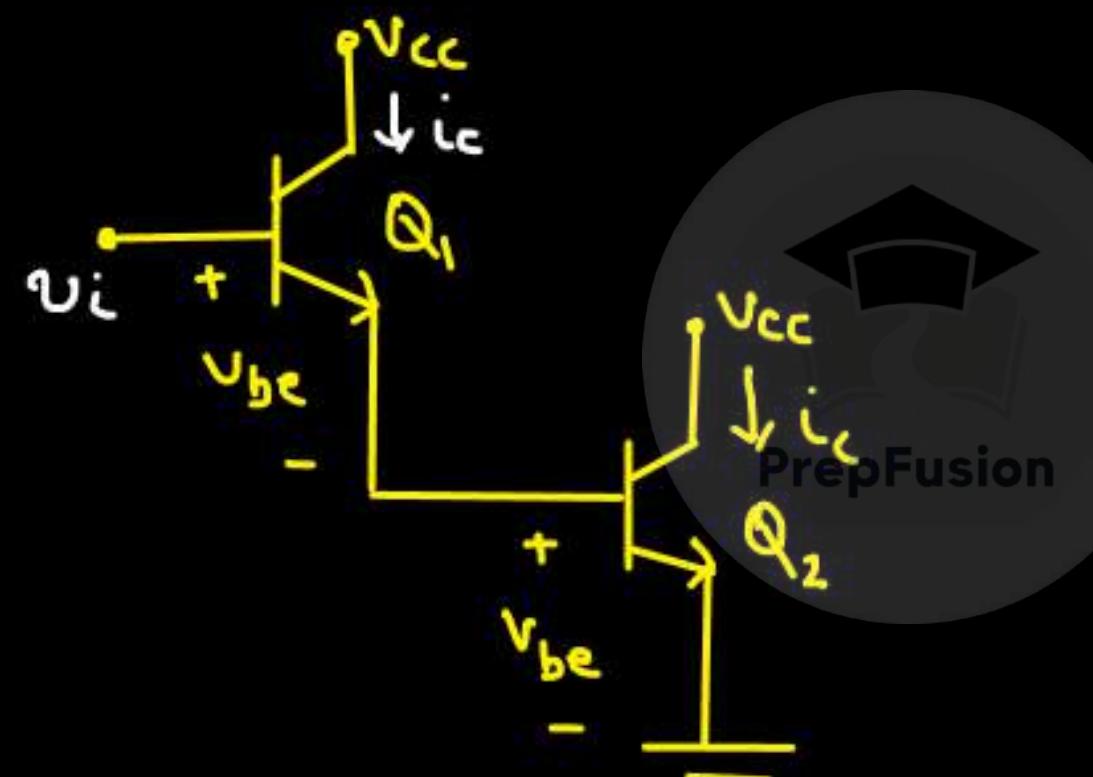Overall Transconductance ? [ $\text{gm}$ ]



$$\text{gm}_2 = \frac{i_c}{v_{be}}$$

$$\text{gm}_1 = \frac{i_c}{v_{be}}$$

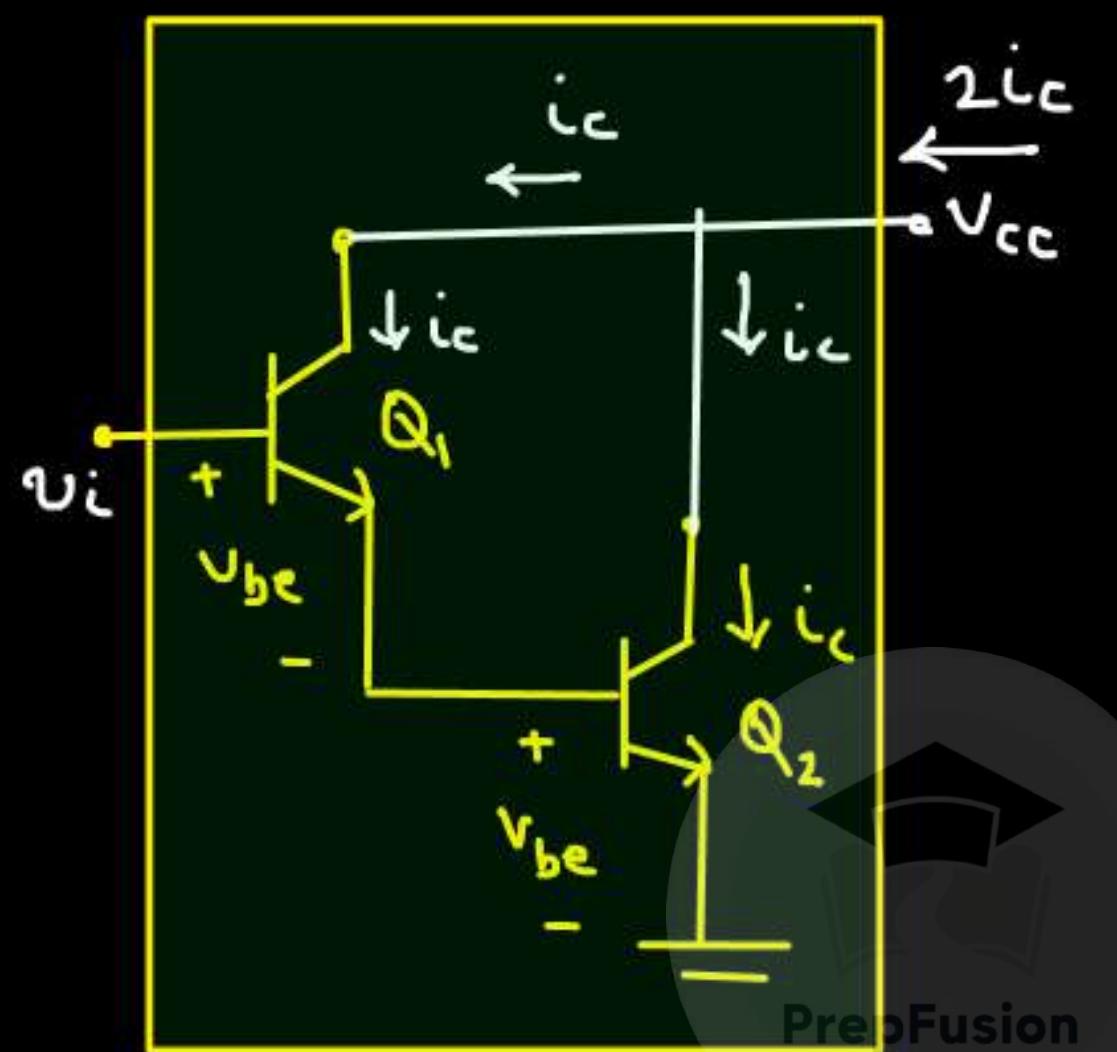


$$g_m = \frac{2i_c}{v_i}$$

$$v_i = 2v_{be}$$

$$g_m = \frac{2i_c}{2v_{be}} = \frac{i_c}{v_{be}}$$

$$g_m = g_{m1} = g_{m2}$$

Q. Find small signal voltage gain  $|\Delta_V|$  [ $V_A = \infty$ ]

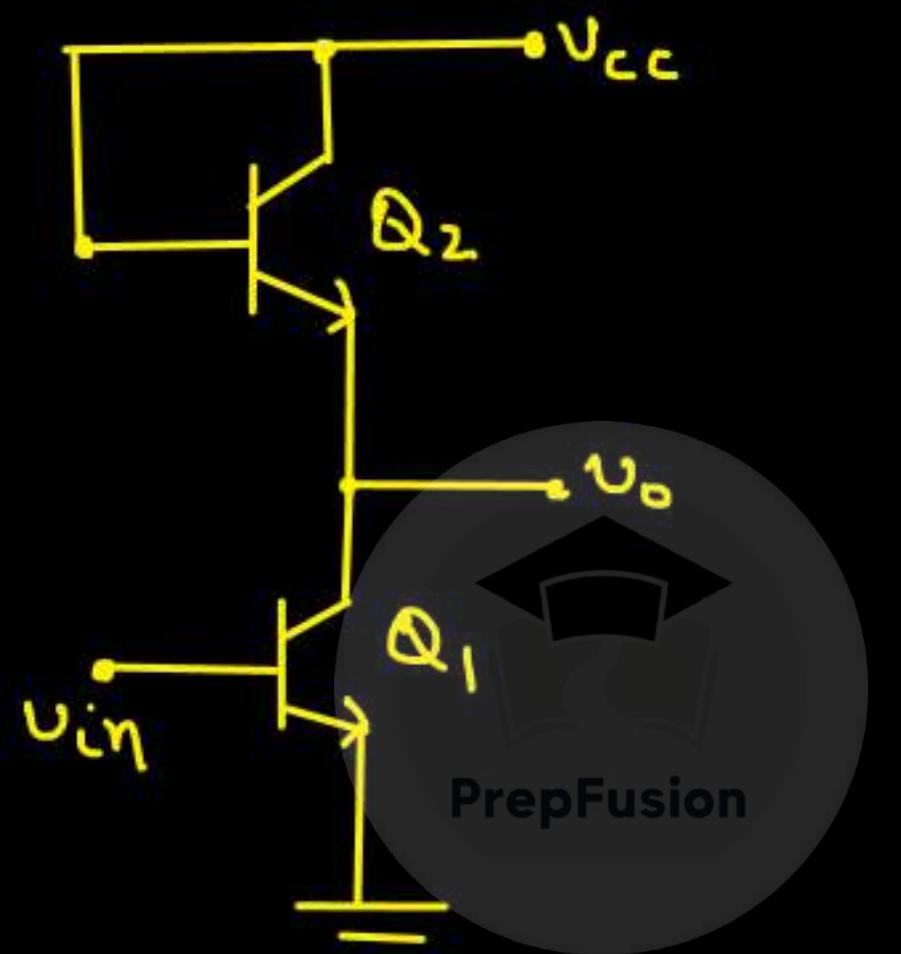


$$(a) \frac{\delta m_1 r_{\pi_2}}{1 + \delta m_2 r_{\pi_2}}$$

$$(b) \frac{\delta m_2 r_{\pi_2}}{1 + \delta m_2 r_{\pi_2}}$$

$$(c) \frac{\delta m_1 r_{\pi_1}}{\delta m_2 r_{\pi_2}}$$
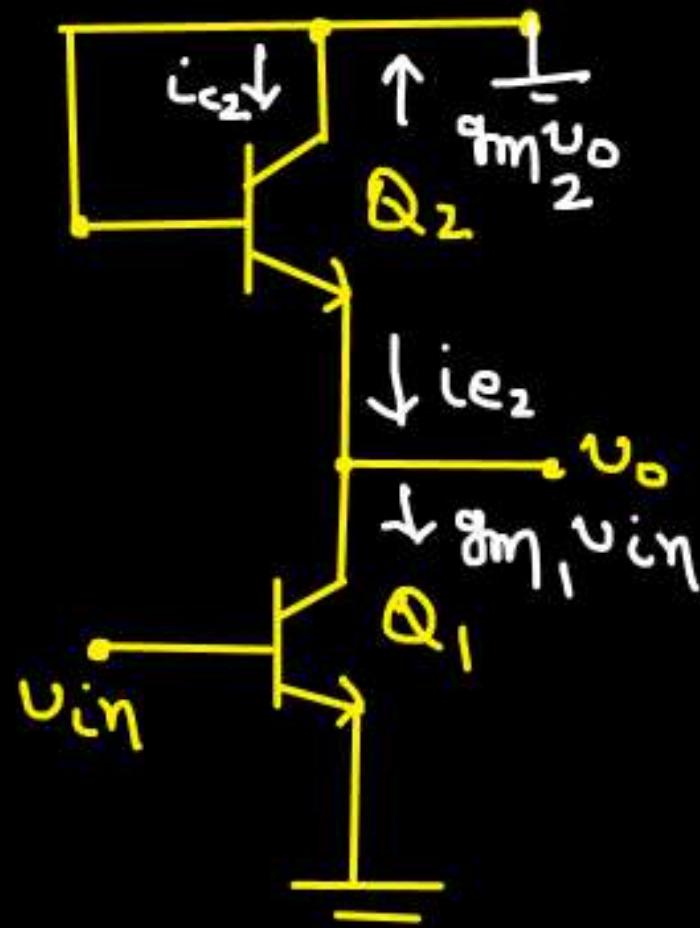
$$(d) \frac{\delta m_1 r_{\pi_1}}{1 + \delta m_2 r_{\pi_2}}$$



$$(V_{be})_2 = -V_0$$

$$i_{c2} = -g_m V_0$$

$$i_{e2} = -g_m V_0 \times \frac{(\beta_2 + 1)}{\beta_2}$$

$$g_m V_{in} = -g_m V_0 \frac{(\beta_2 + 1)}{\beta_2}$$

PrepFusion


$$\frac{V_0}{V_{in}} = \frac{-g_m \beta_2}{g_m (\beta_2 + 1)}$$

$$\gamma_\pi = \frac{\beta}{g_m}$$

$$\beta = \gamma_\pi g_m$$

$$A_V = \frac{-g_m \gamma_\pi \beta_2}{g_m \gamma_\pi \beta_2 + 1}$$


Q. Find overall voltage gain. ( $|A_{v1}|$ )

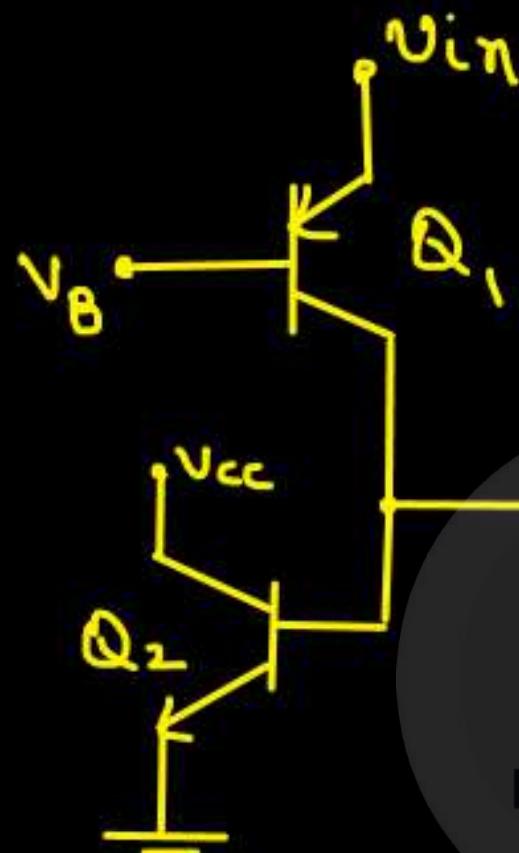

→

$$\text{gm}_1 v_{in} = \frac{v_o}{r_{\pi_2}}$$

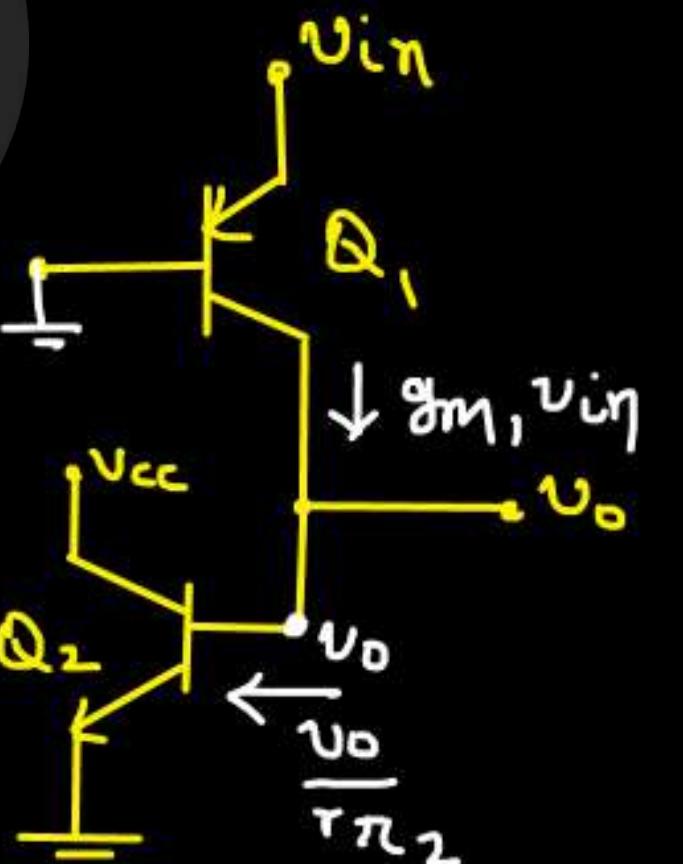
$$\frac{v_o}{v_{in}} = \text{gm}_1 r_{\pi_2}$$




# Differential Amplifier using BJT

## (Small Signal analysis)

1. Dual Input - balanced output:-

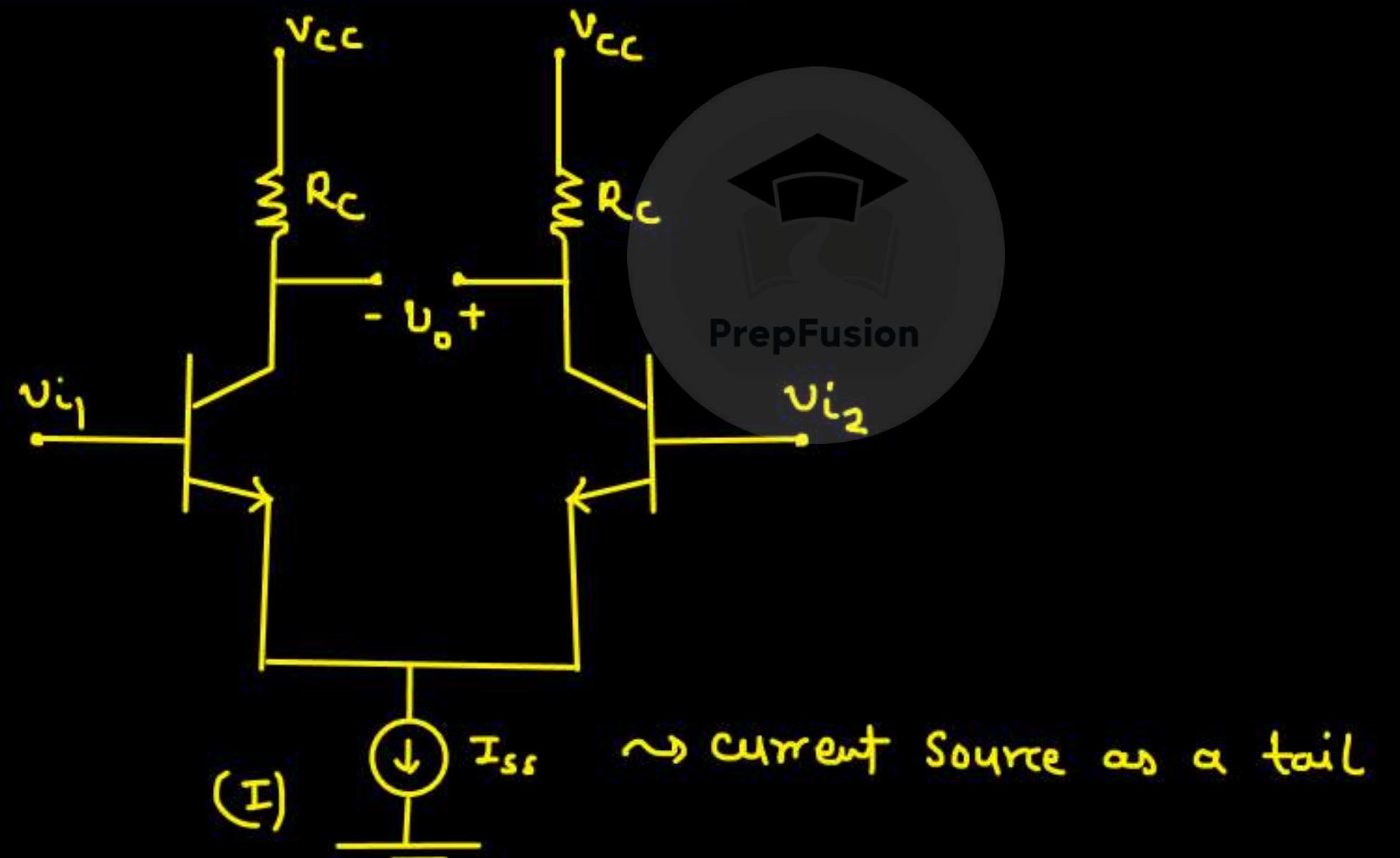

## (a) Differential Gain :-

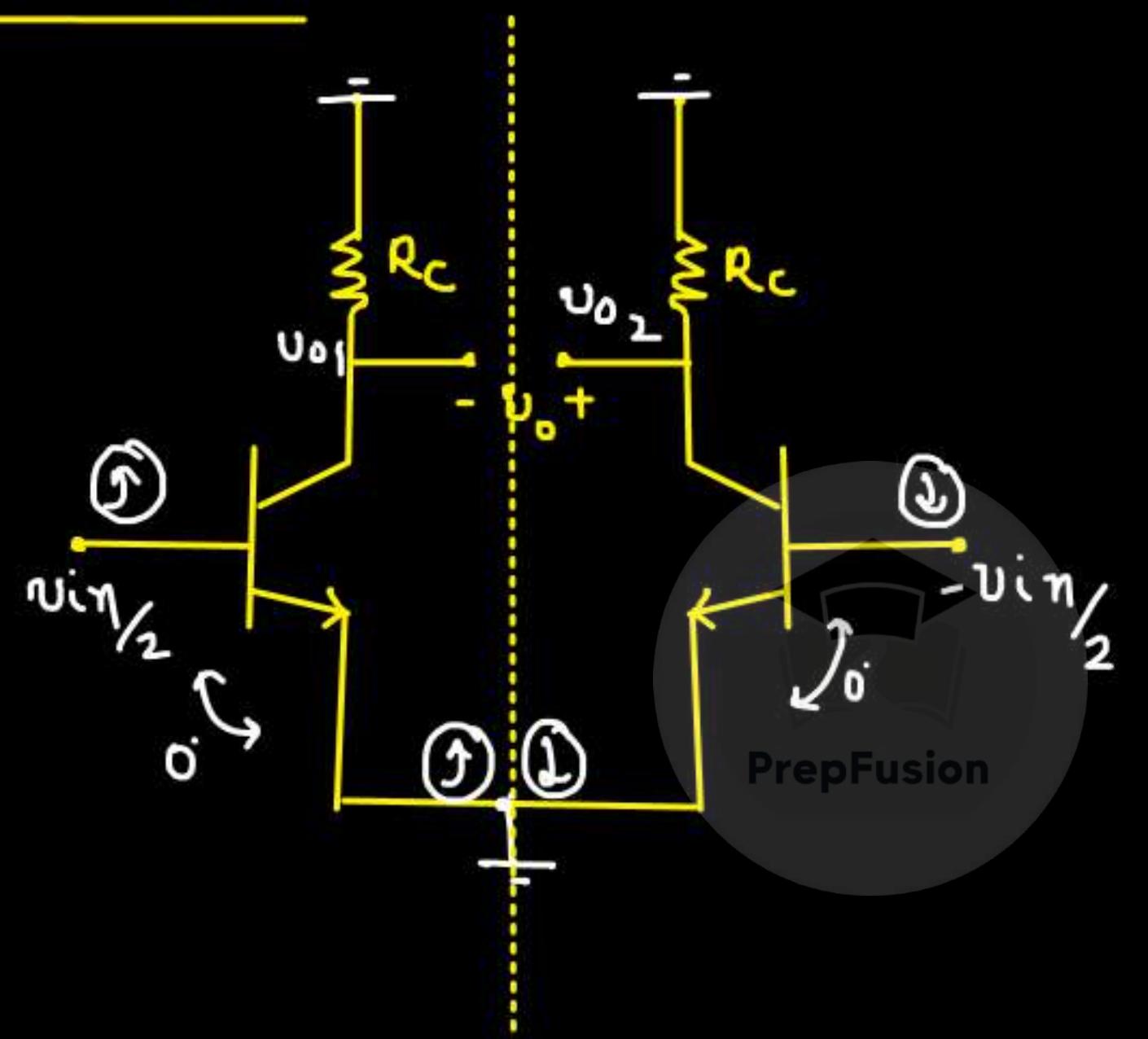

$$U_{o1} = -g_m R_C \frac{U_{in}}{2}$$

$$U_{o2} = -g_m R_C \left( -\frac{U_{in}}{2} \right)$$

$$= g_m R_C \frac{U_{in}}{2}$$

$$U_o = U_{o2} - U_{o1}$$


$$U_o = g_m R_C U_{in}$$

$$\text{Ad} = \frac{U_o}{U_i} = g_m R_C$$

## (b) Common Mode Differential Gain ( $\alpha_{CM-DM}$ ):-

$$CMRR = \frac{A_d}{\alpha_{CM-DM}}$$


\*   
  $CMRR = \infty$

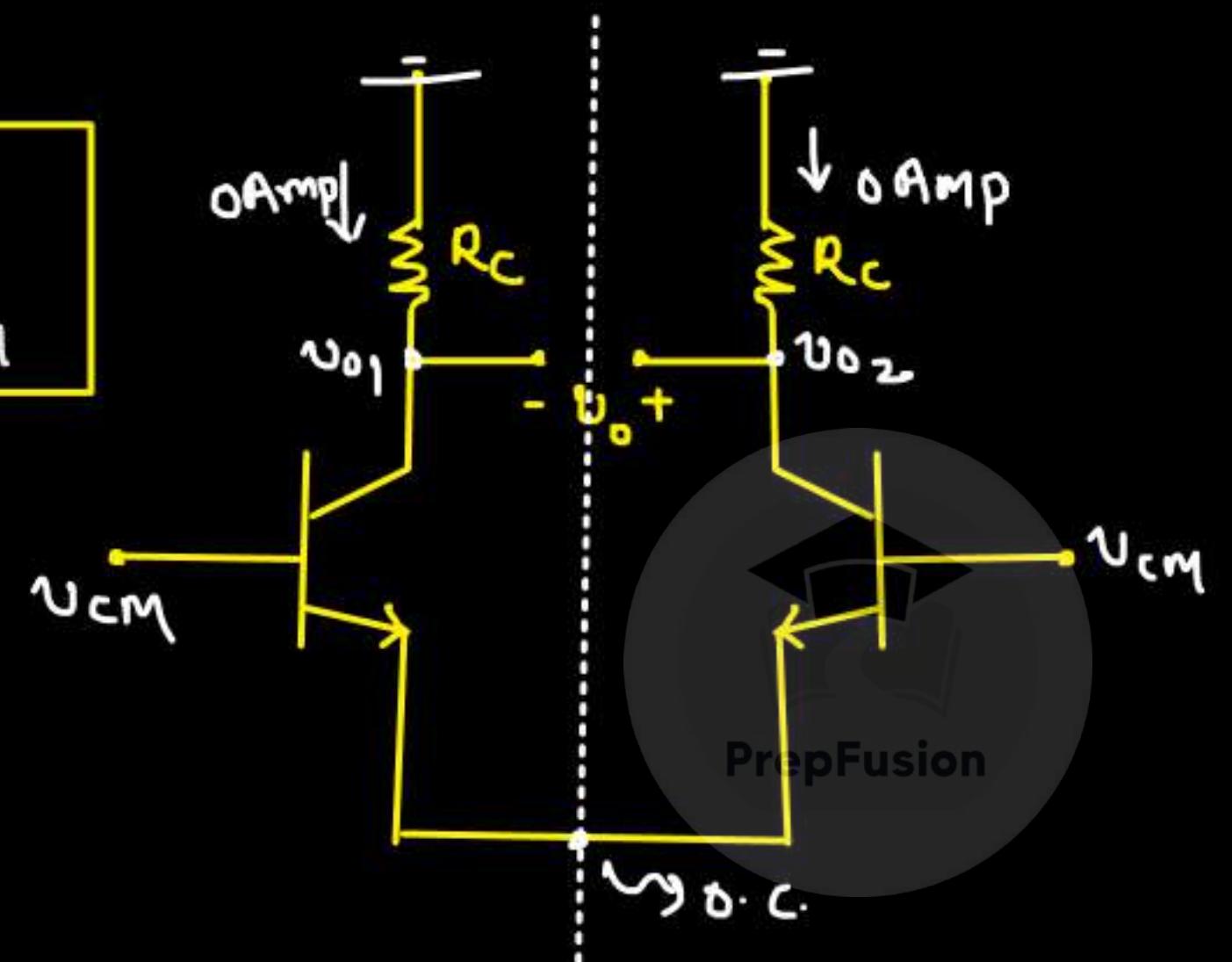


$$U_{O2} = U_{O1} = 0$$

$$\alpha_{CM-DM} = \frac{U_{O2} - U_{O1}}{U_{CM}}$$

$$\alpha_{CM-DM} = 0$$

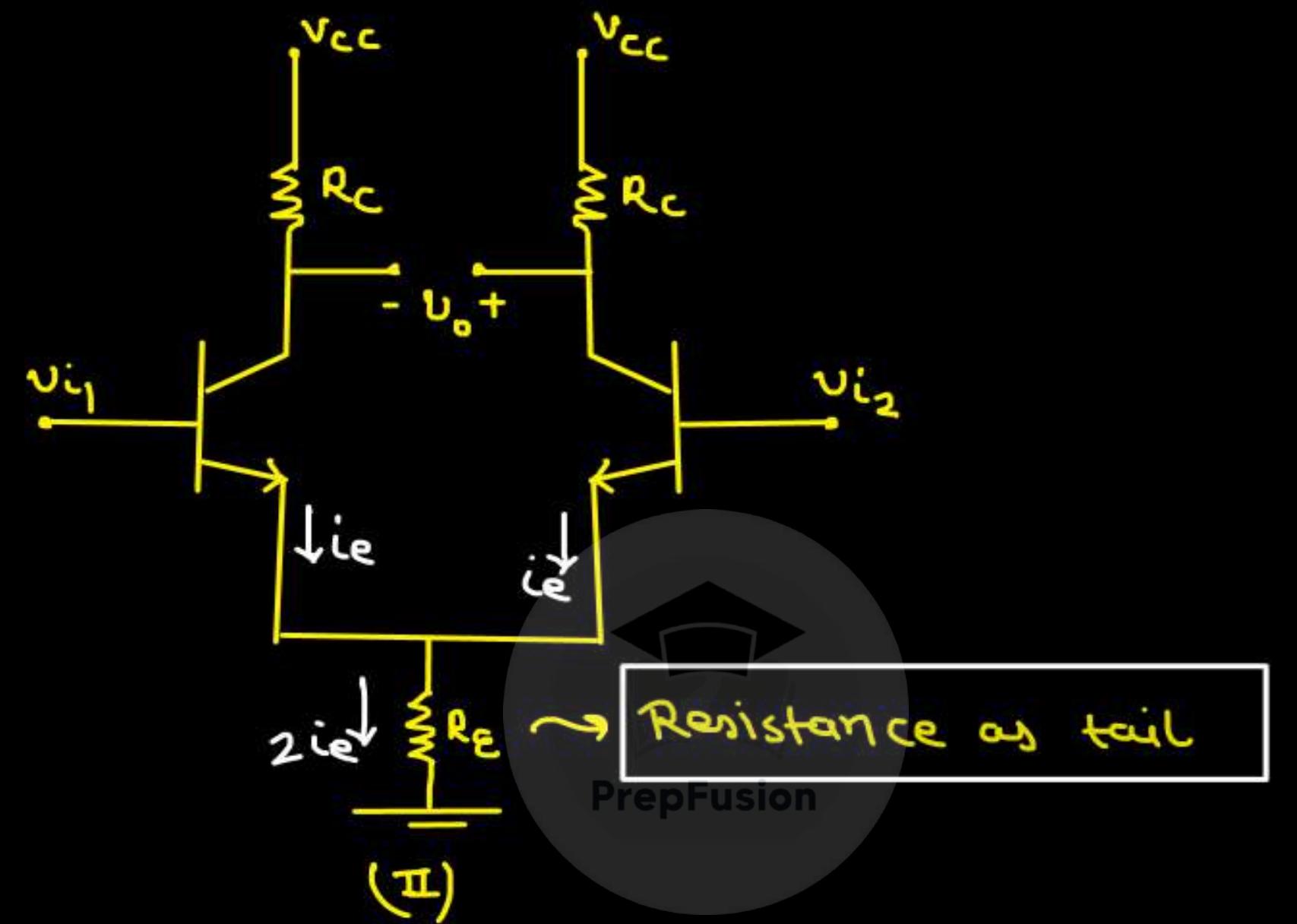
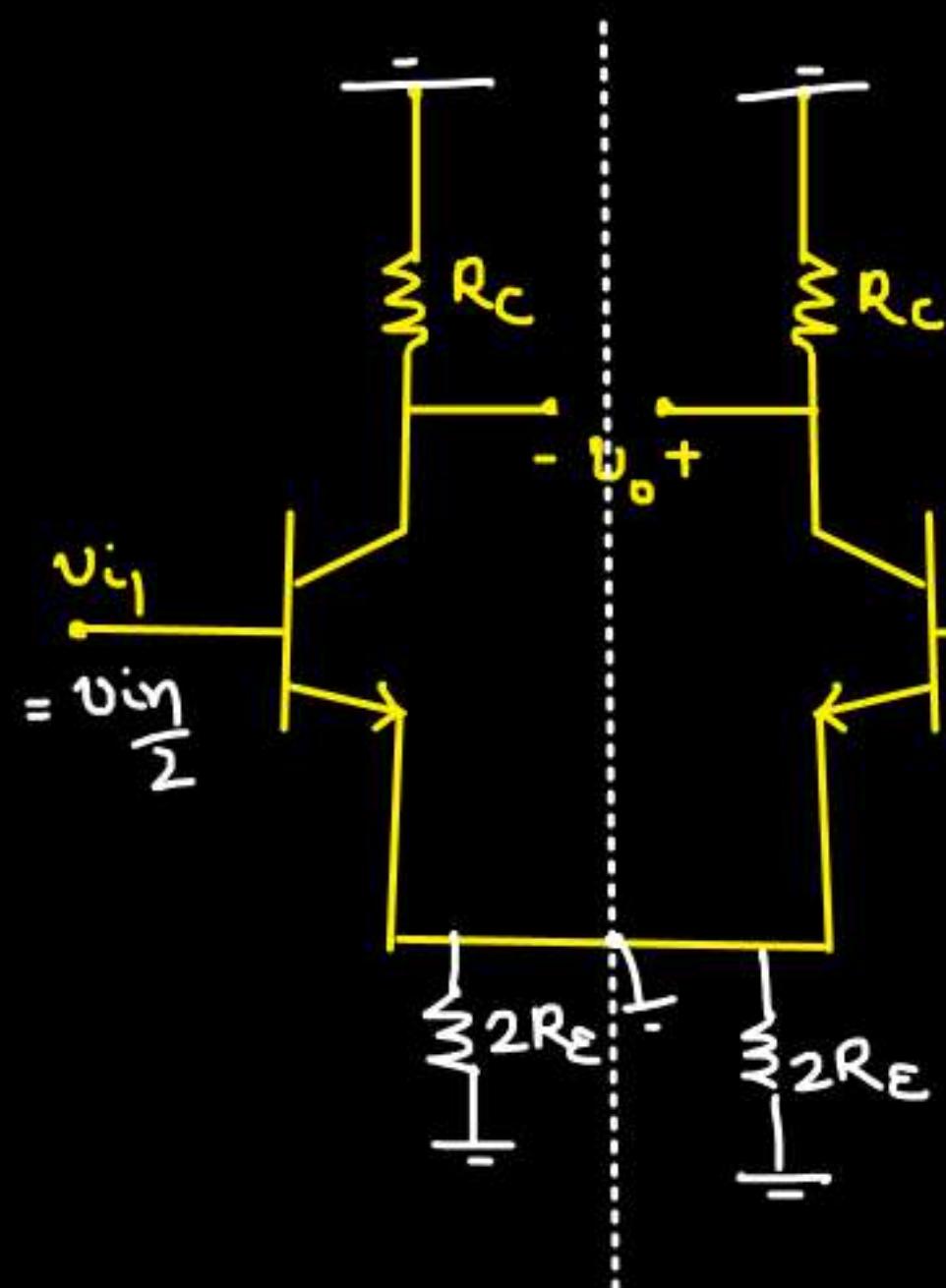
## (a) Differential Gain ( $\alpha_d$ ):-




$$v_{o_1} = -g_m R_C v_{in}/2$$

$$v_{o_2} = g_m R_C v_{in}/2$$

$$v_o = g_m R_C v_{in}$$

$$v_{in} = v_i$$

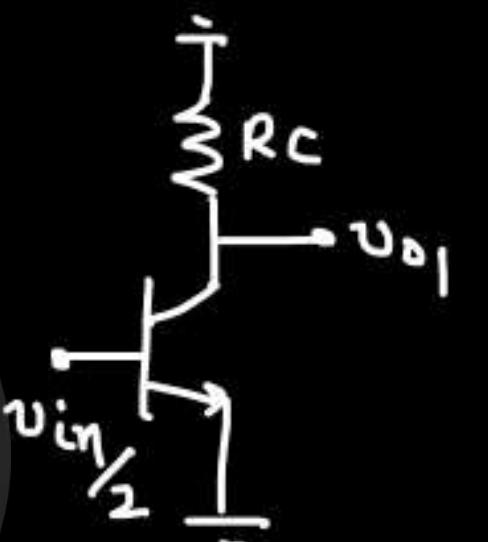


$$\alpha_d = g_m R_C$$


$$\alpha_d = g_m R_C$$

PrepFusion
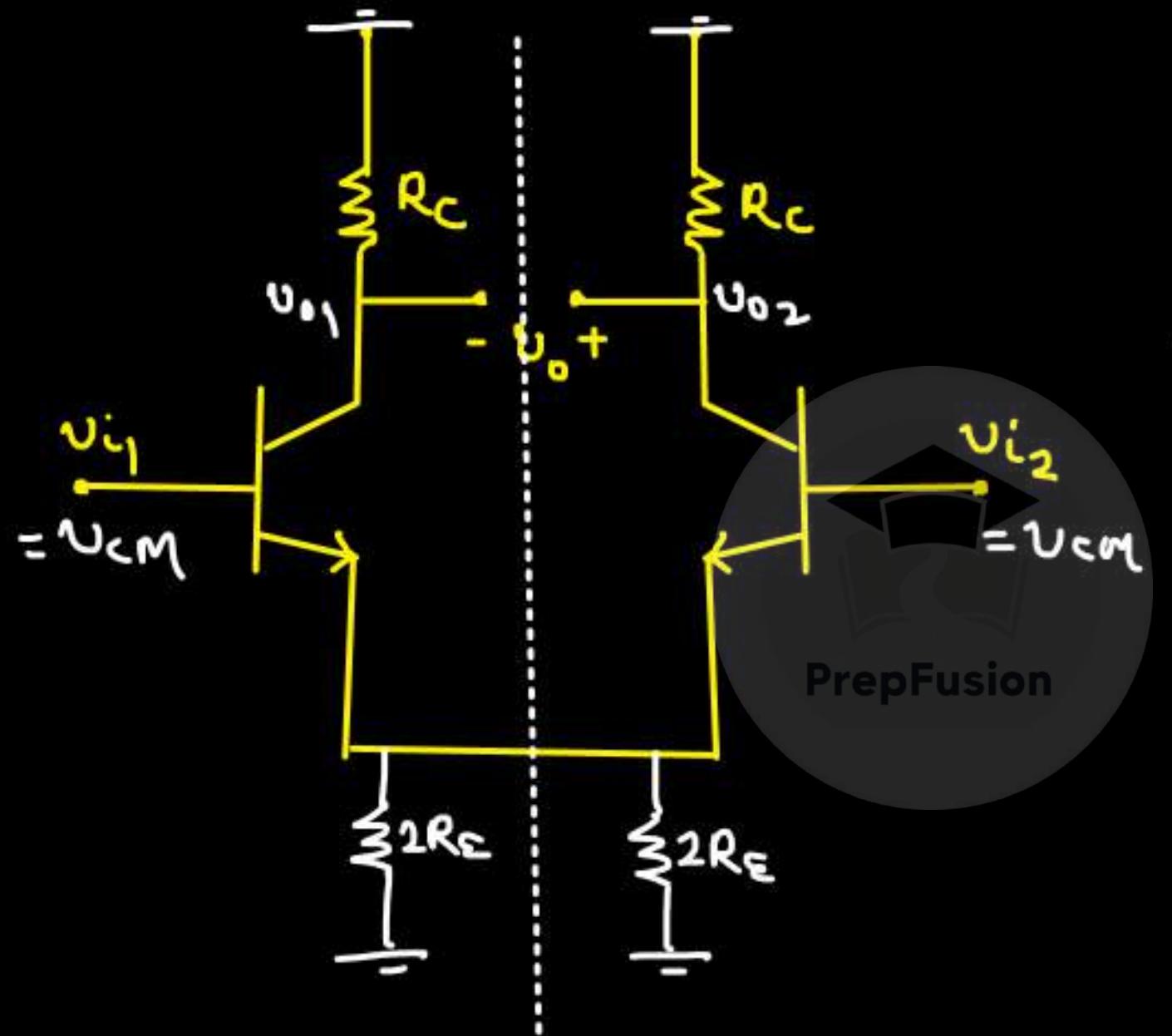
## (b) Common Mode Differential Gain ( $\alpha_{CM-DM}$ ): -


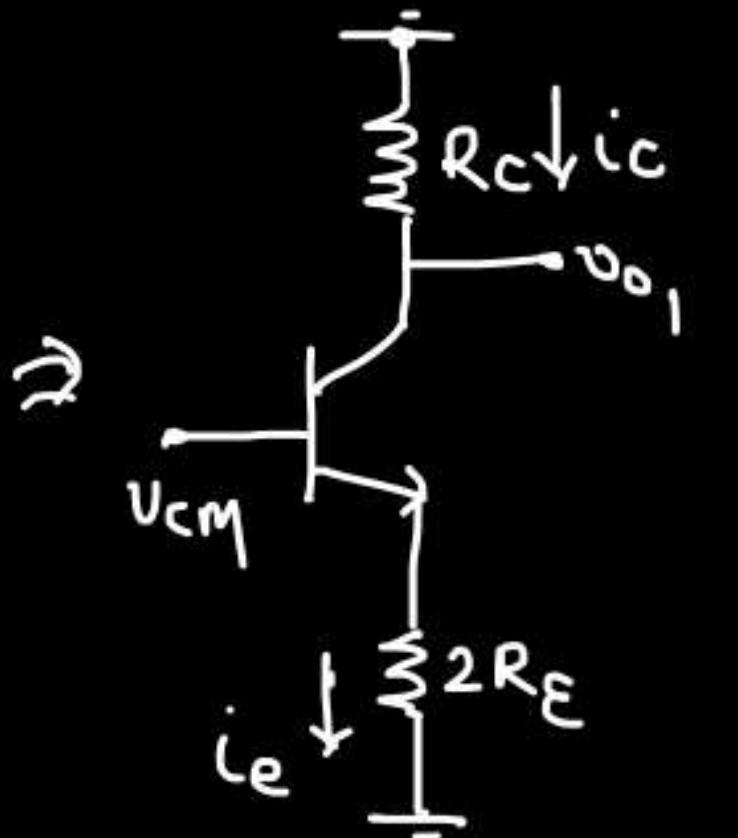
$$v_{o1} = \frac{-\beta R_C v_{cm}}{r_\pi + 2R_E (\beta + 1)}$$



$$v_{o1} = -i_c R_C$$

$$v_{cm} = r_\pi i_b + 2R_E \times (\beta + 1) i_b$$

$$i_c = \frac{\beta v_{cm}}{r_\pi + 2R_E (\beta + 1)}$$

$$v_{o_2} = \frac{-\beta R_C v_{CM}}{r_N + 2R_E(\beta + 1)}$$

$$(v_i)_{CM} = v_{CM}$$

$$(v_o)_{CM-DM} = v_{o_2} - v_{o_1} \\ = 0$$

$$A_{CM-DM} = 0$$



$$CMRR = \frac{\infty}{A_{CM-DM}} = \infty$$

$$(v_i)_{CM} = v_{CM}$$

$$(v_o)_{CM} = \frac{v_{o_1} + v_{o_2}}{2}$$


$$A_{CM} = \frac{-\beta R_C v_{CM}}{r_N + 2R_E(\beta + L)}$$

$R_E \uparrow \Rightarrow A_{CM} \downarrow$

if CMRR is defined as  $\frac{\infty}{A_{CM}}$


then  $R_E \uparrow \Rightarrow A_{CM} \downarrow \Rightarrow CMRR \uparrow$

## 2. Dual Input Unbalanced Output :-

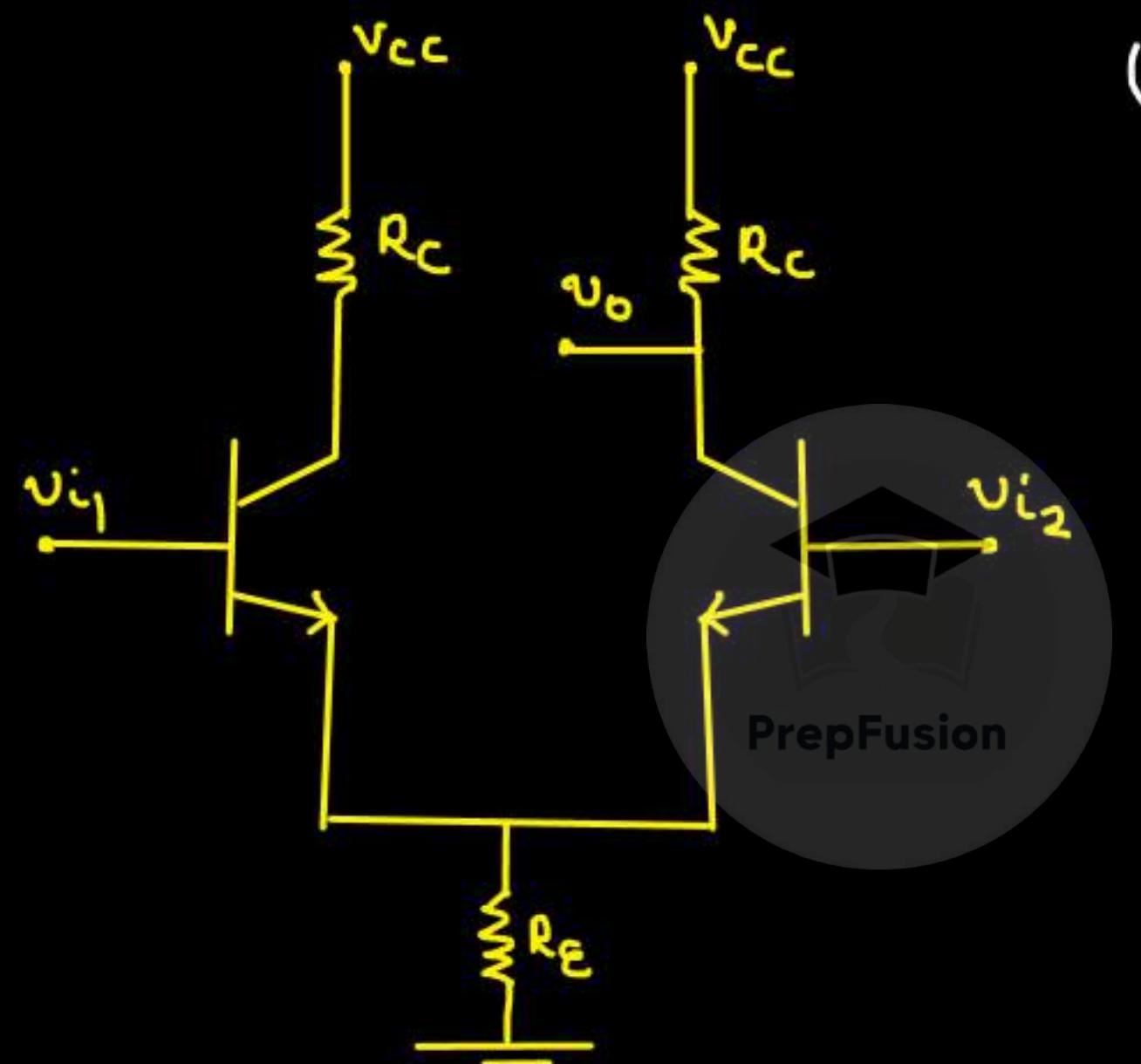

$$\begin{aligned}
 (V_o)_d &= (V_o)_{CM} \\
 &= (V_o)_{CM - DM} = V_o
 \end{aligned}$$

## (a) Differential Gain ( $A_d$ ) :-

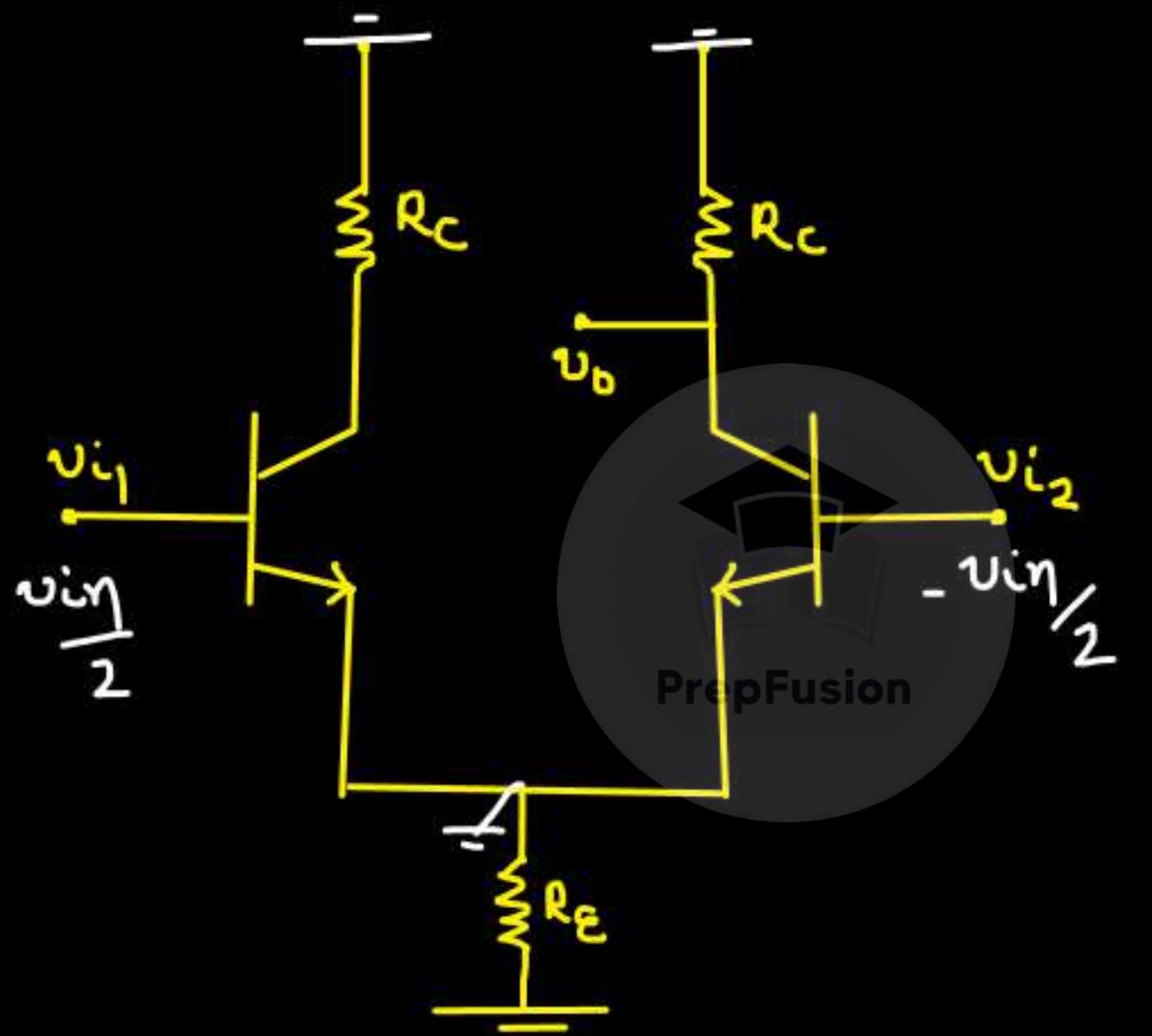


$$(v_o)_d = g_m R_C v_{i1}/2 = v_o$$

$$(v_i)_d = v_i$$

$$(\Delta v)_d = \frac{g_m R_C}{2}$$

$$= \frac{\beta R_C}{2 r_n}$$
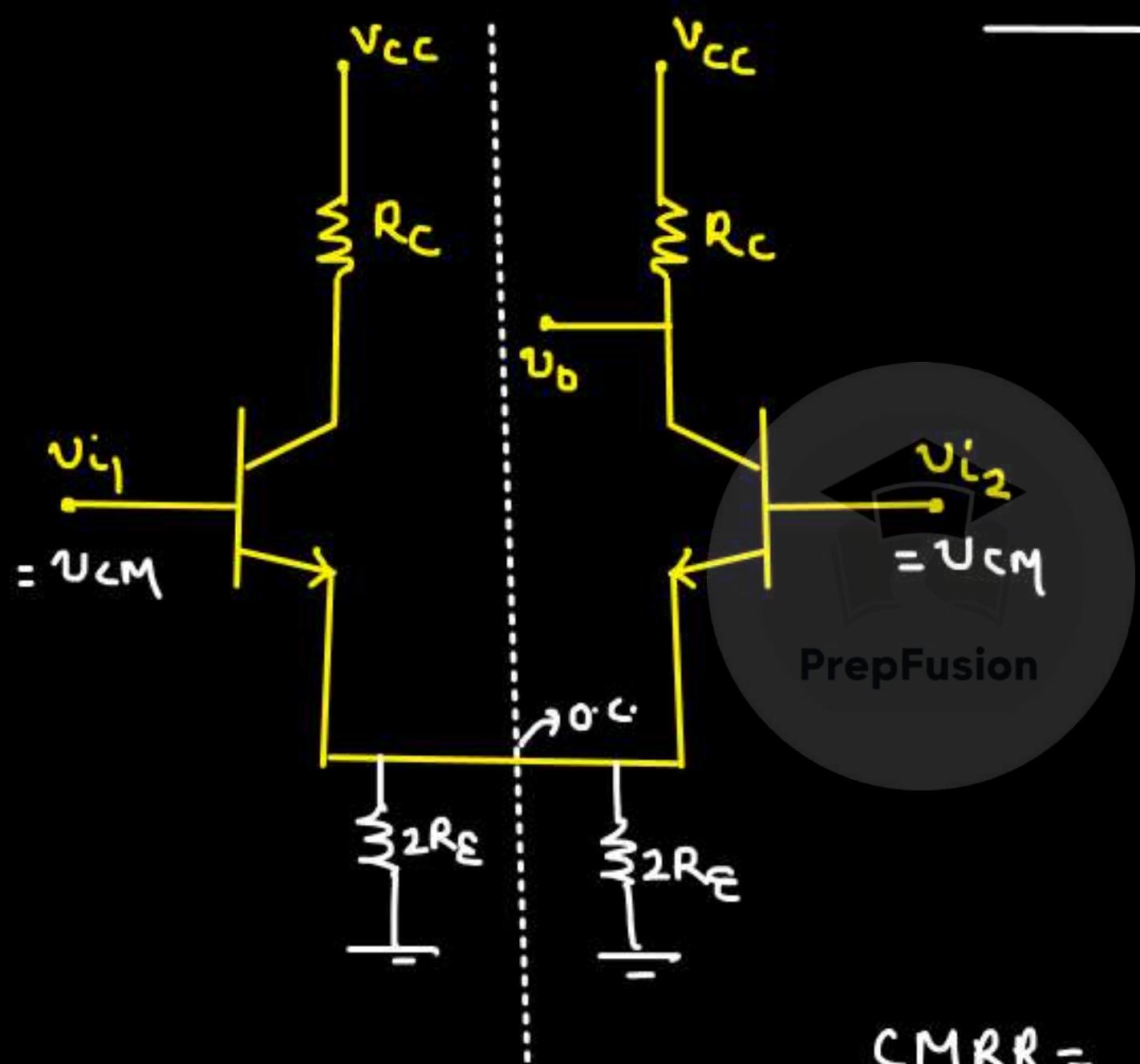
## (b) Common - Mode Differential Gain :- / Common Mode Differential Gain :-



$$U_o = \frac{\beta R_C U_{CM}}{r_{\pi} + 2R_E (\beta + 1)}$$

$$A_{CM} = A_{CM-DM} = \frac{\beta R_C}{r_{\pi} + 2R_E (\beta + 1)}$$

$$CMRR = \frac{A_d}{A_{CM-DM}} = \frac{\beta R_C}{2r_{\pi}} \times \frac{r_{\pi} + 2R_E (\beta + 1)}{\beta R_C}$$

$$CMRR = \frac{L}{2} + \frac{R_E}{r_N} (\beta + L)$$

$$\left\{ \frac{\beta}{r_N} = g_m \right\}$$

$$CMRR \approx \frac{L}{2} + g_m R_E$$

$$\beta + L \approx \beta$$


$$CMRR \approx g_m R_E$$

PrepFusion

**Q. 1**

In the differential amplifier shown in the figure, the magnitudes of the common-mode and differential-mode gains are  $A_{cm}$  and  $A_d$ , respectively. If the resistance  $R_E$  is increased, then

$$CMRR = \frac{\alpha q}{A_C}$$

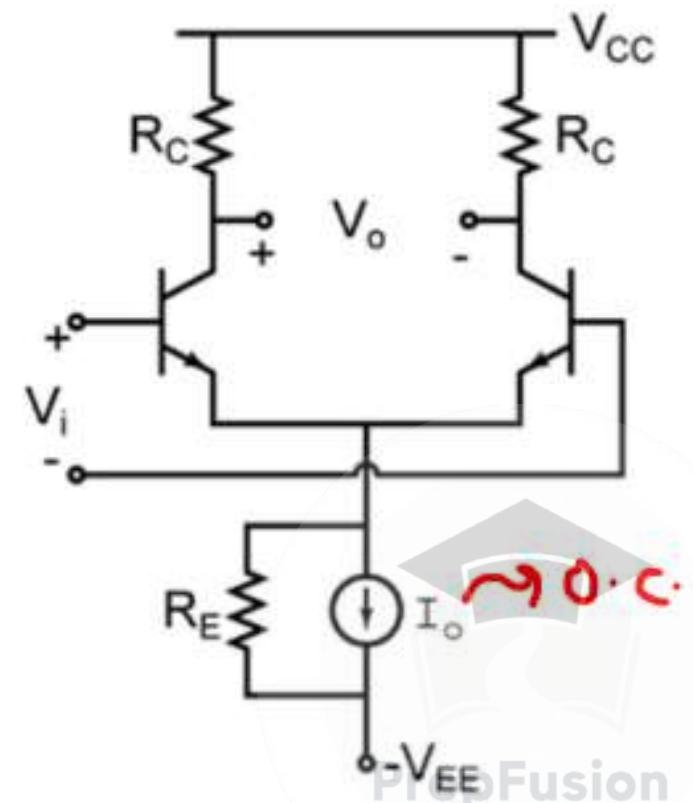

- (A)  $A_{cm}$  increases  
(C)  $A_d$  increases

- (B) common-mode rejection ratio increases  
(D) common-mode rejection ratio decreases

$$\rightarrow A_d = \alpha q R_C$$

$$A_C = \frac{\beta R_C}{r_\pi + 2(\beta + 1) R_E}$$

$R_E \uparrow \Rightarrow A_C \downarrow, A_d \sim$   
 $\downarrow$   
no change  
 $CMRR \uparrow$


### Common Data for Questions 53 and 54 :

The circuit shown in the figure uses three identical transistors with  $V_{BE} = 0.7 \text{ V}$  and  $\beta = 100$ .

Given  $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$ ,  $kT/q_e = 25 \text{ mV}$ . The collector current of transistor  $Q_3$  is 2 mA.

$$g_m = \frac{1 \text{ mA}}{25 \text{ mV}}$$
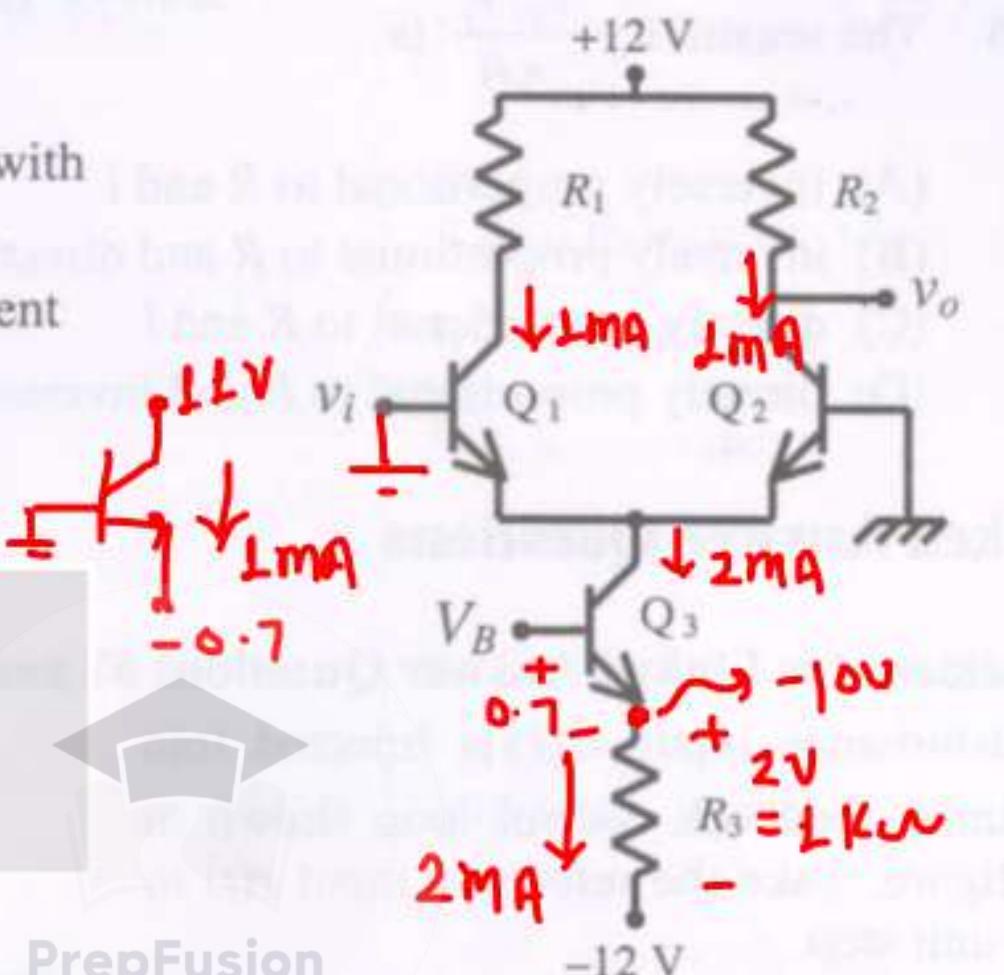
$$\begin{aligned} V_B &= -10 + 0.7 \\ &= -9.3 \text{ V} \end{aligned}$$





Q.53 The bias voltage  $V_B$  at the base of the transistor  $Q_3$  is approximately

- (A) -9.3 V      (B) -10.0 V      (C) -10.3 V      (D) -11.0 V

Q.54 The small-signal voltage gain of the circuit is

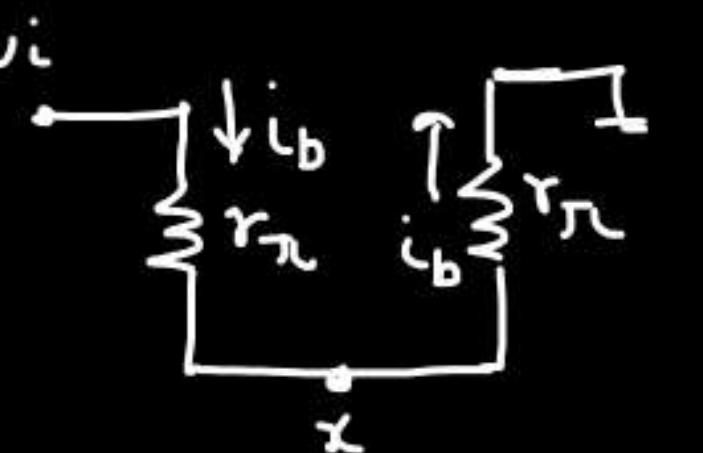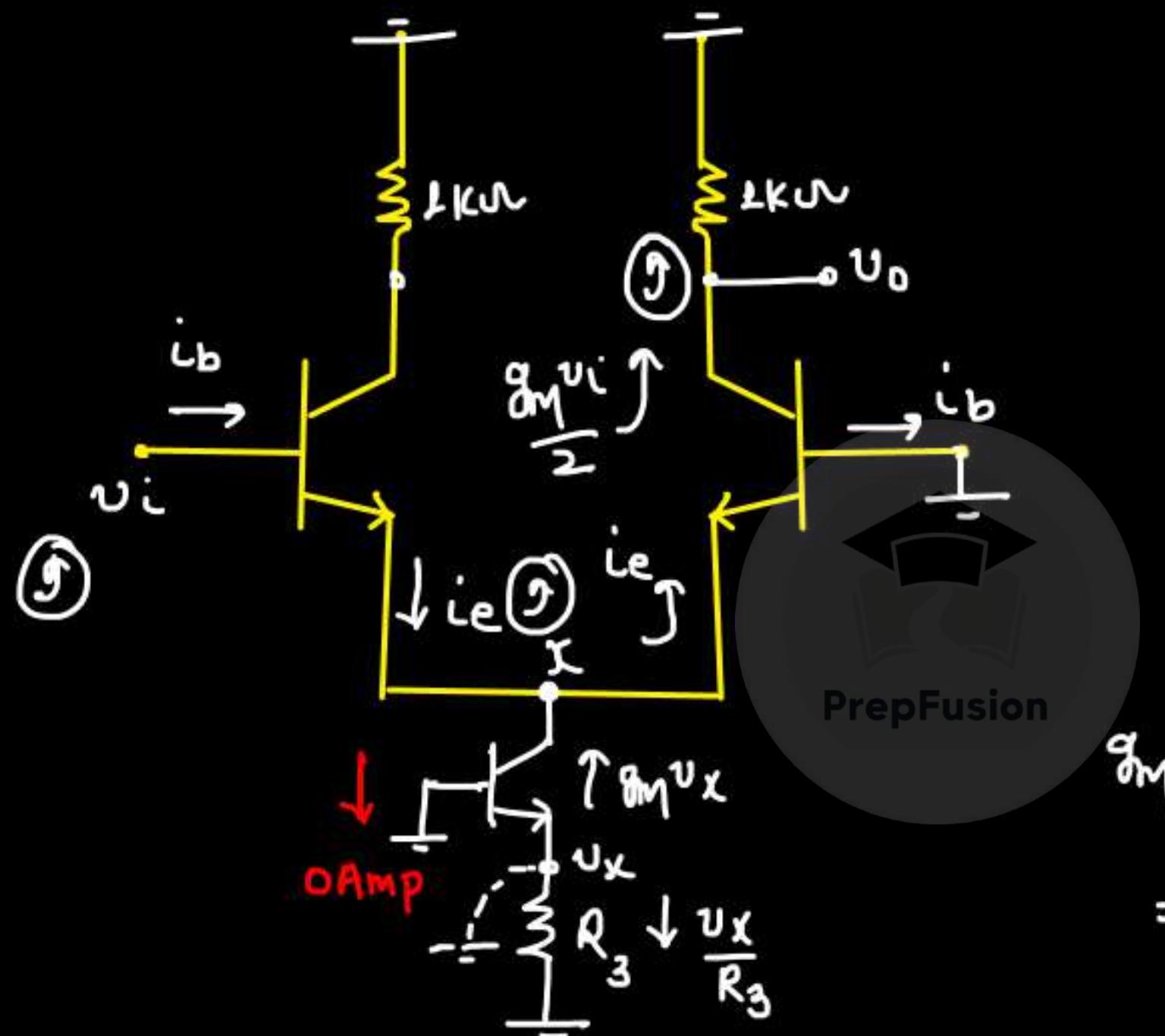- (A) -20      (B) -40      (C) 20      (D) 40



$$v_x = v_i / 2$$

$$g_m v_x = -v_x / 3$$

$$\Rightarrow v_x = 0$$

$$v_D = \frac{g_m v_i}{2} \times 1 \text{k}\Omega$$

$$\frac{v_D}{v_i} = \frac{1}{50} \times 1000$$

$$\therefore A_v = 20\%$$

## \* Feedback Topologies:-




Same as MOSFETs

I/P → mixing

O/P → Sampling

Q. Comment on Feedback Topology.

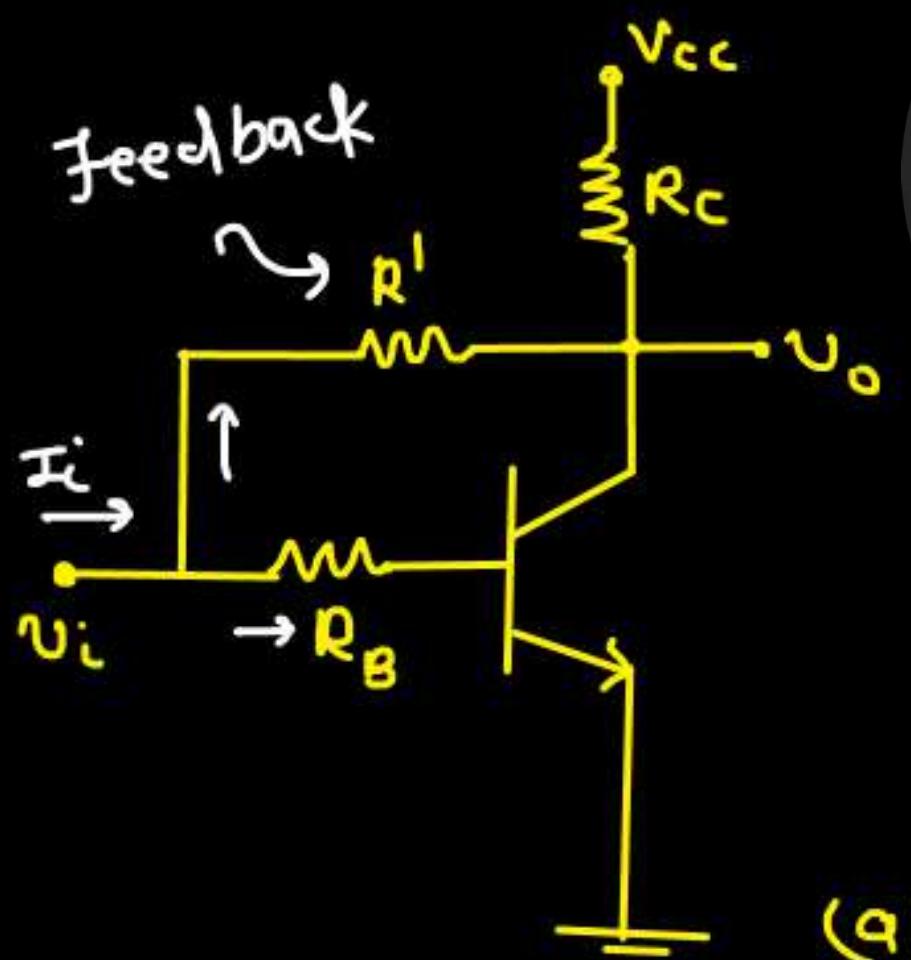


feedback ↳ output ⇒ connected

↳  
voltage sampling  
current mixing

Voltage - Current

Shunt - Shunt


Voltage - shunt

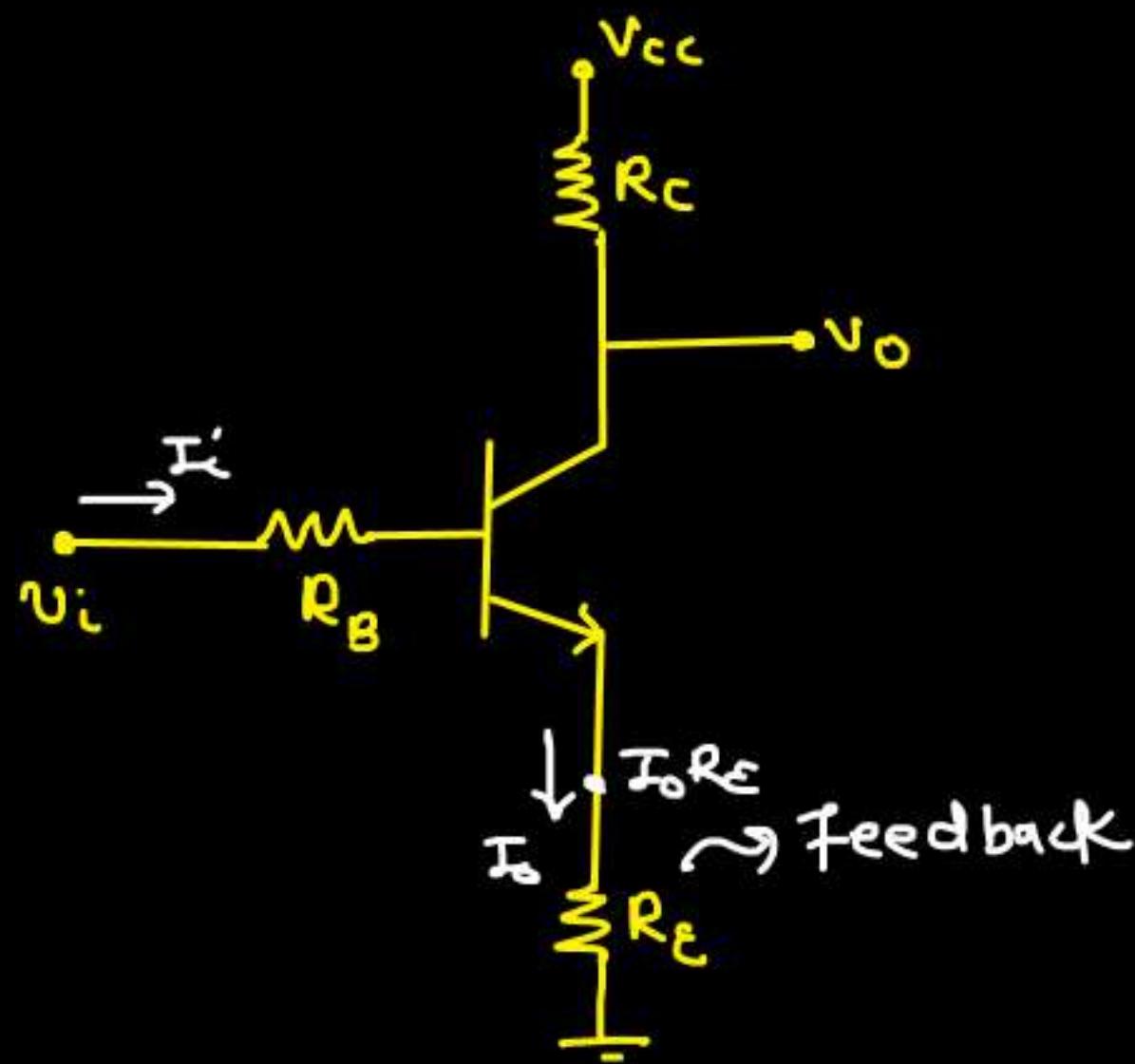

(b)

current sampling  
Voltage mixing

Current - Voltage

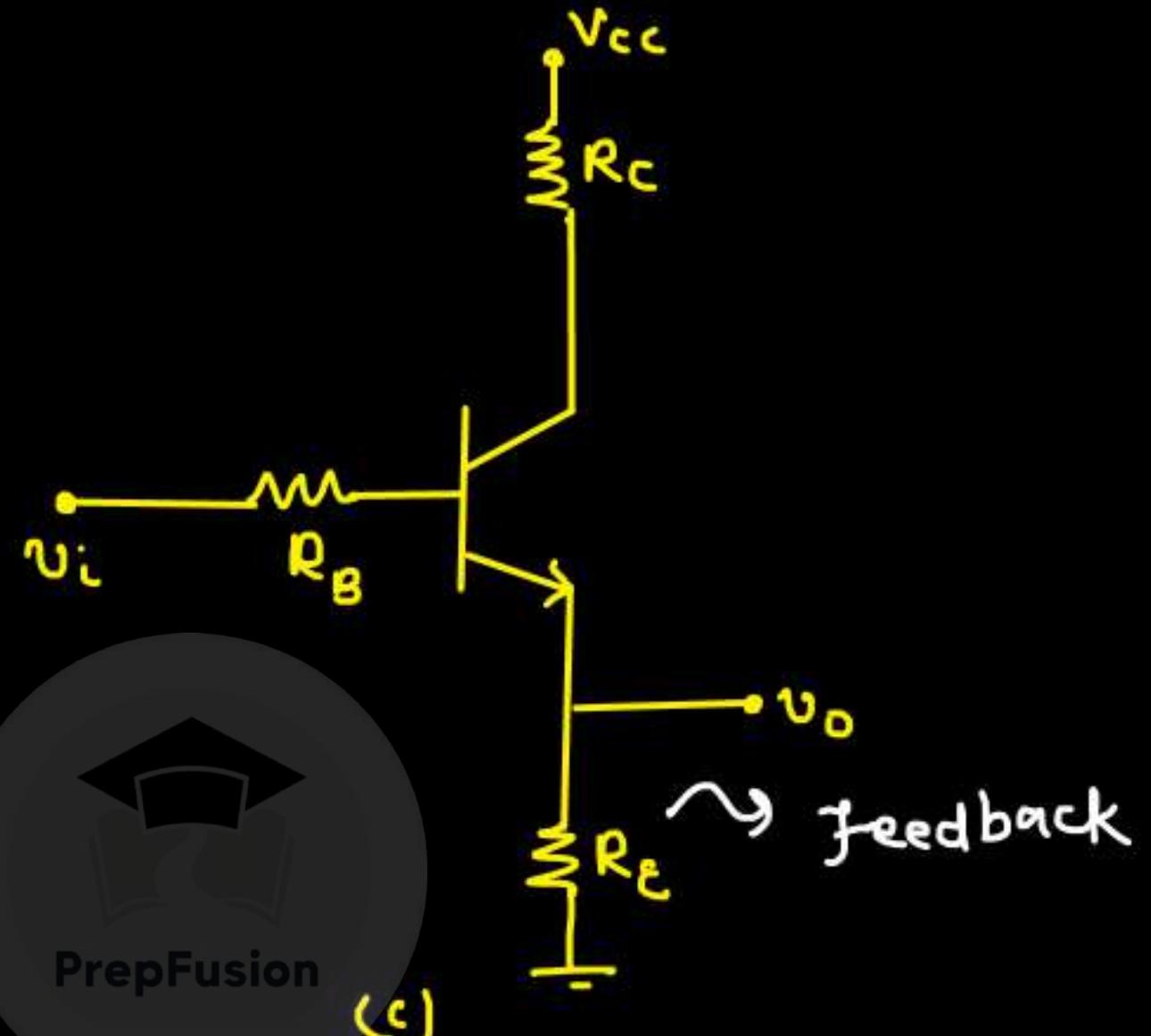


(c)

Voltage Sampling

Voltage mixing

Voltage - Voltage



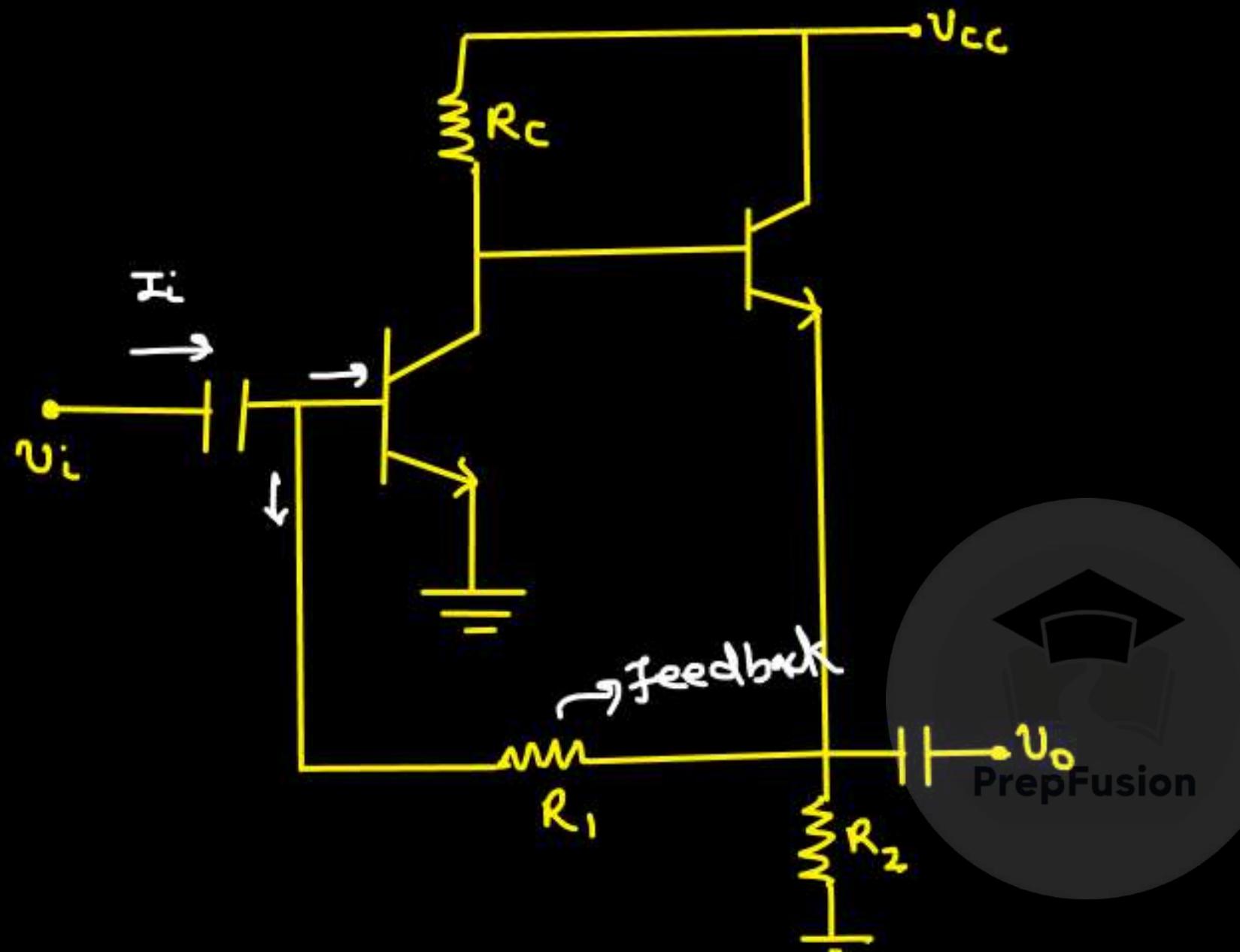


(d)

voltage sampling  
current mixing

voltage - current

## CMOS Inverter


\* Buffer :-

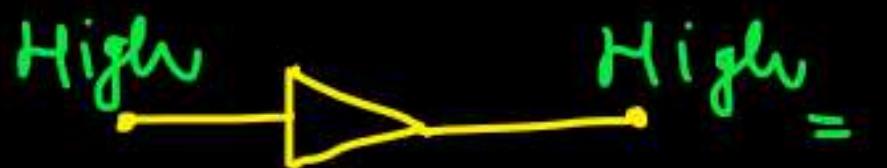

\* Inverter :-



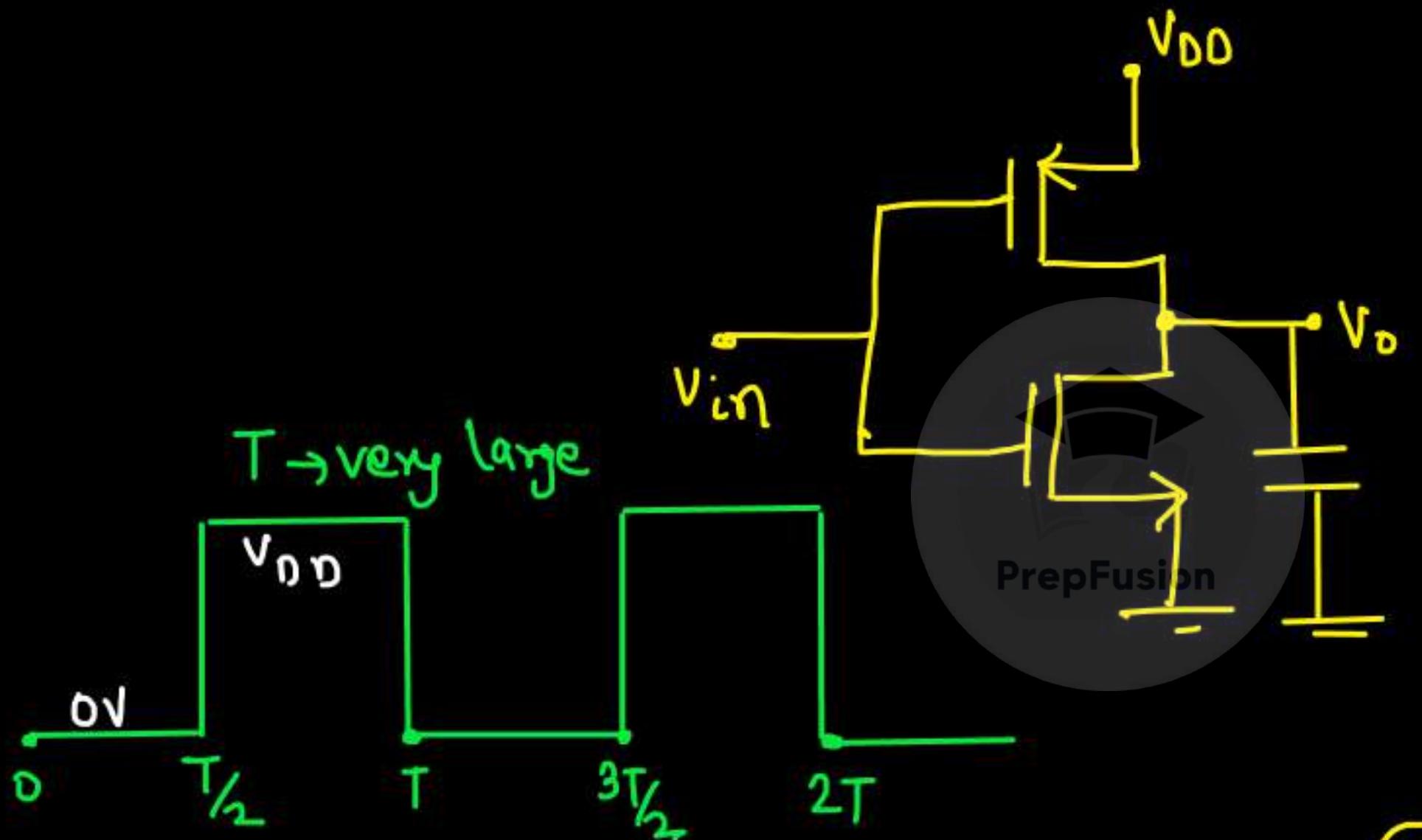CMOS inverter to pulse input :-  $V_{DD} = 5V, V$



$\rightarrow \text{for } 0 < t < T/2$

$$V_{in} = 0$$

@ PMOS  $\rightarrow$   
 $t=0$   
 $V_{sg} = V_{DD} > |V_{tp}|$

$V_{SD} = V_{DD}$   
ON, sat.

N MOS

@  $t=0$

$V_{gs} = 0$   
OFF

$\infty$ , for  $0 < t < T/2$



PMOS  $\rightarrow$  ON

NMOS  $\rightarrow$  OFF  $\rightarrow$  O.C.

initially,  $T$  in sat region



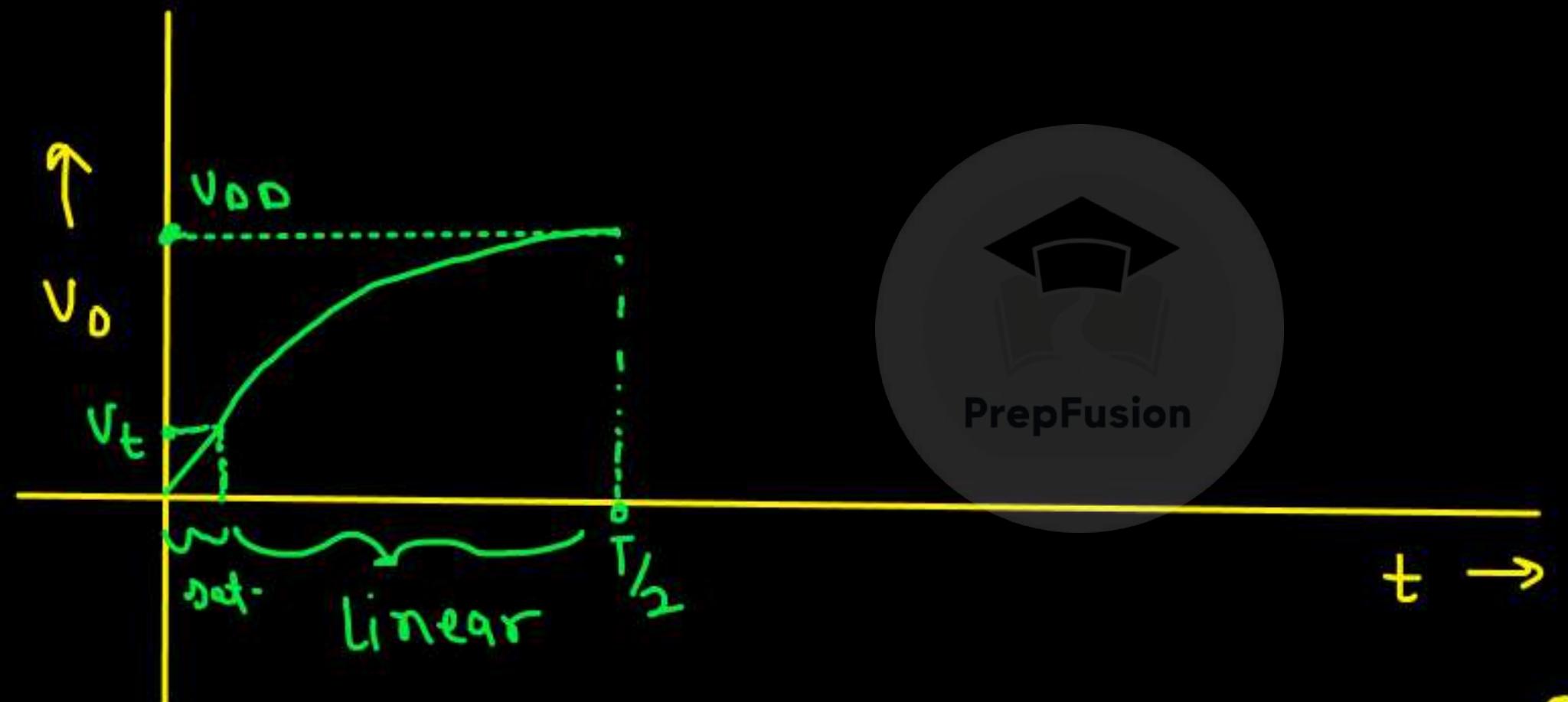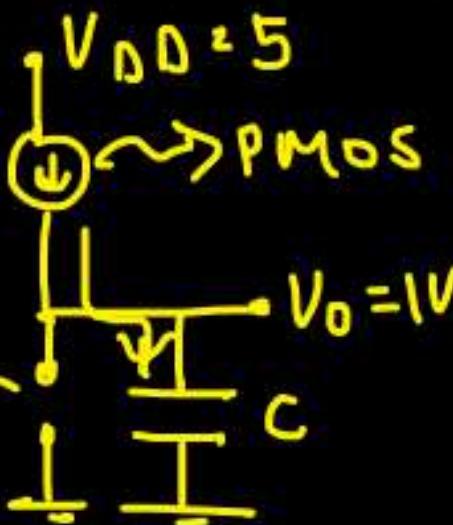PMOS can be replaced with a current source



Now,  $V_D$  is increasing  $\Rightarrow V_{SD}$  ↓

But  $V_{OV} = V_{SG} - V_{TPl} = 4V$  is fixed

$\Rightarrow$  PMOS is moving toward linear region

∴ @  $V_{SD} = V_{SG} - |V_{TP}|$

$$V_{DD} - V_0 = 4$$

$V_0 = \frac{1}{2}V$   $\Rightarrow$  when  $V_0 > |V| \Rightarrow V_{SD} < V_{SG} - |V_{TP}|$

$\Downarrow$   
Linear region  
 $\Downarrow$   
PMOS will be replaced with  $R_{ON}$



NMOS is still off

exponential charging

for  $T_1 < t < T$

$$V_{in} = 5V$$

for PMOS: -

$$V_{sg} \approx 0V \rightarrow \text{OFF} =$$

for NMOS

$$V_{gs} = 5V$$

$$V_{ov} = 4V$$

$$V_{ds} = V_o =$$


$$@ t=0 \quad V_{ds} = 5V$$

$$V_{ds} > V_{ov} \rightarrow \text{Sat. region}$$

↓  
NMOS  $\equiv$  Current Source



$V_{DD}$

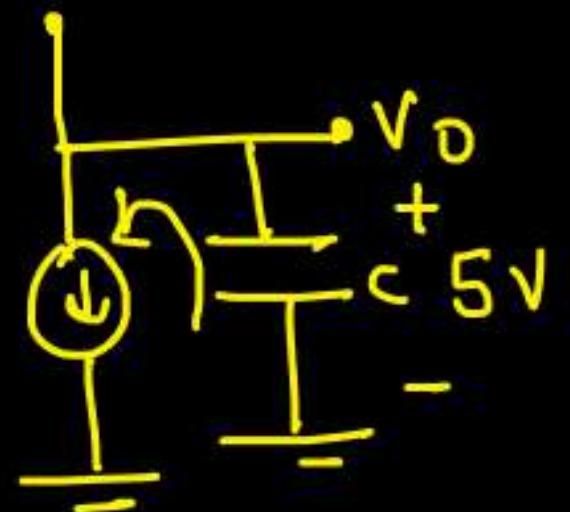

⇒ This discharges the cap. linearly



$V_0$  goes down


$(V_{DS})_N$  goes down

NMOS is moving towards  
linear region


$$V_{SD} < V_{DVS}$$

$$V_0 < 4V$$


$V_{DD}$

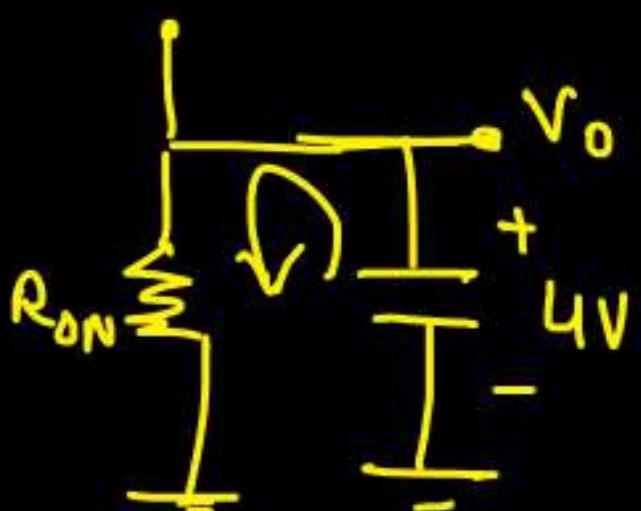

NMOS will be replaced  
with  $R_{ON}$

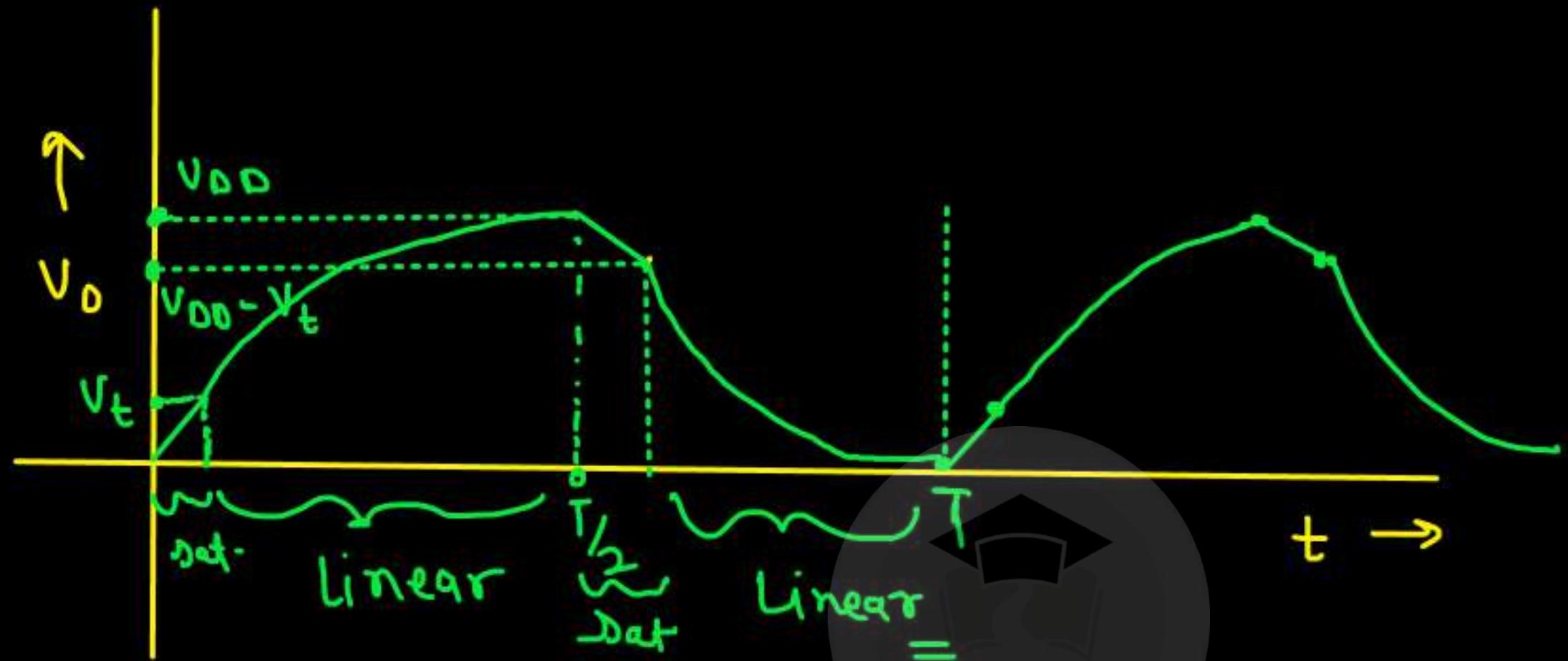

Q.

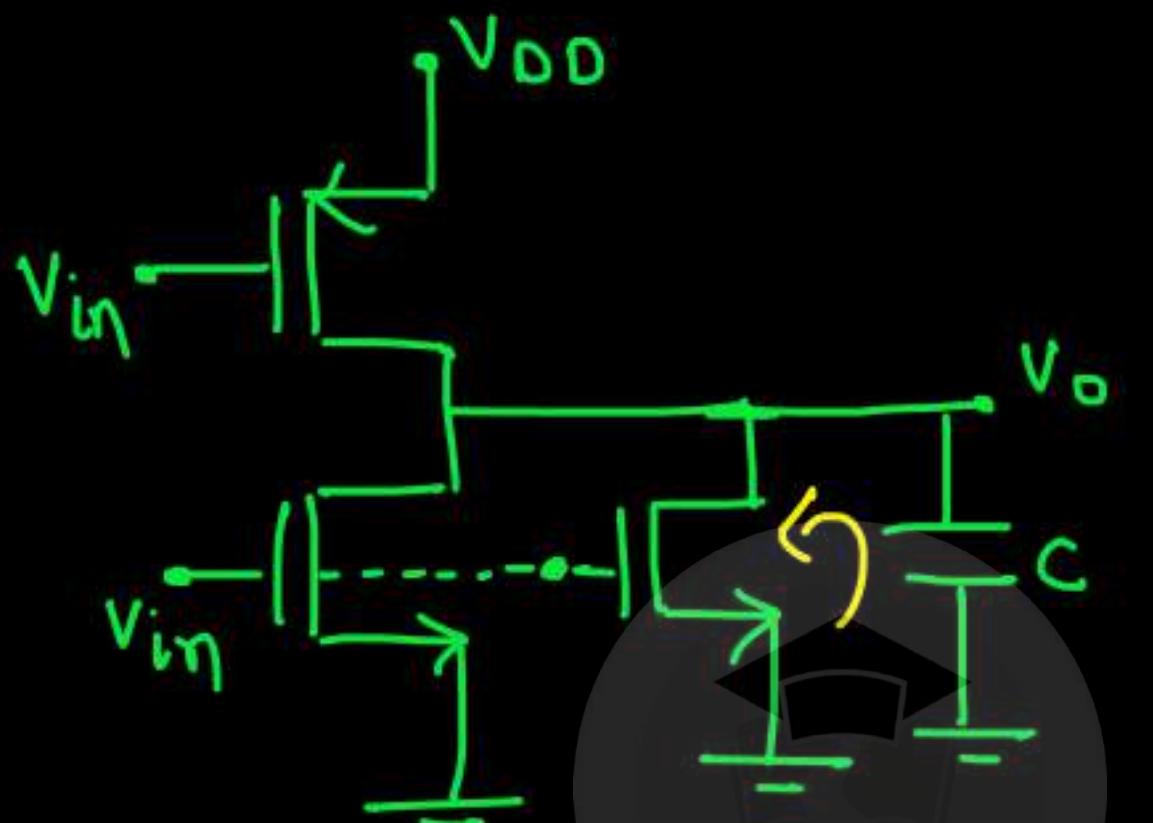


Comment on cap. speed  
of charging and  
discharging .

→ Speed of charging  
remains the same

$$(\tau)_{\text{dis.}} = \frac{R_{ON} C}{2}$$

Speed of  
discharging has  
increased.

## \* CMOS inverter with ramp input :-

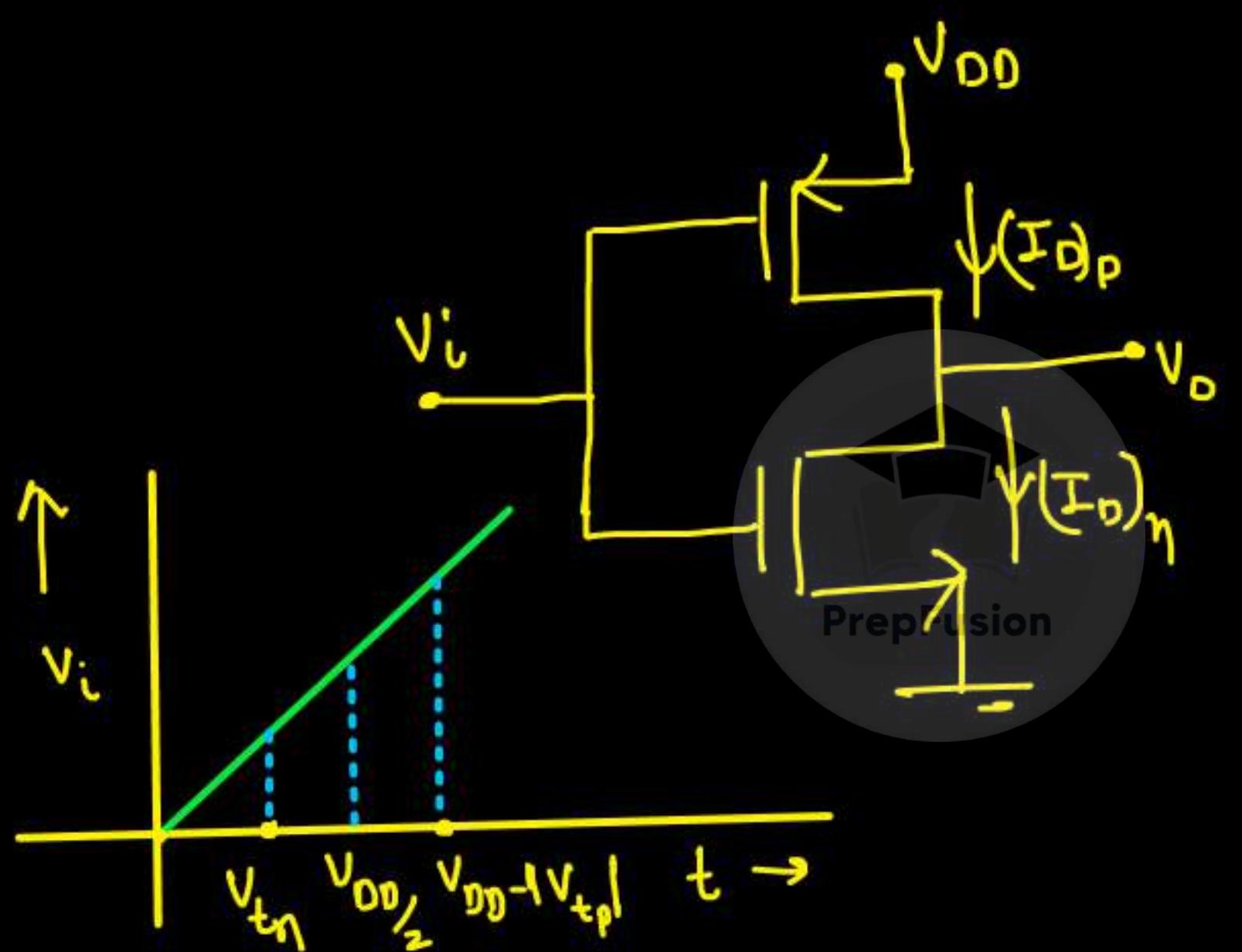

$$\text{Let } V_{DD} = 5V$$

$$V_{tn} = |V_{tp}| = 1V$$

$$V_{in} \equiv 0V \rightarrow 5V$$


(1) When  $0 < V_i < V_{t\eta}$

⇒ NMOS:-


$V_{GS} < V_{t\eta} \Rightarrow \text{off} \Rightarrow \text{cut-off}$

PMOS:-

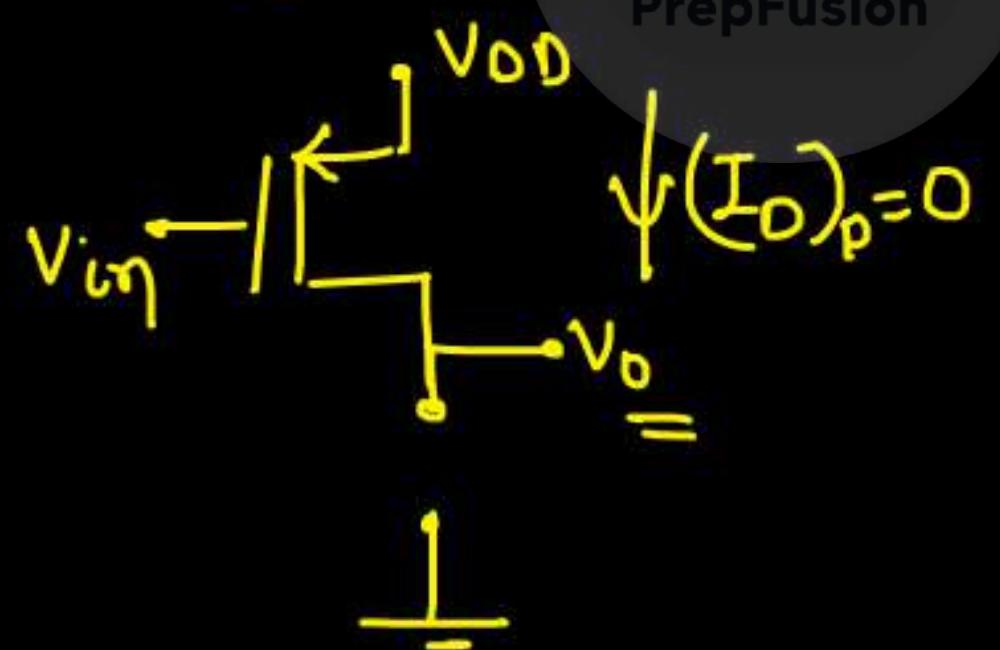$V_{SG} = V_{DD} - V_i > V_{DD} - V_t \Rightarrow \text{ON} \rightarrow \text{sat. or linear?}$




$$\Rightarrow V_o \approx V_{DD}$$

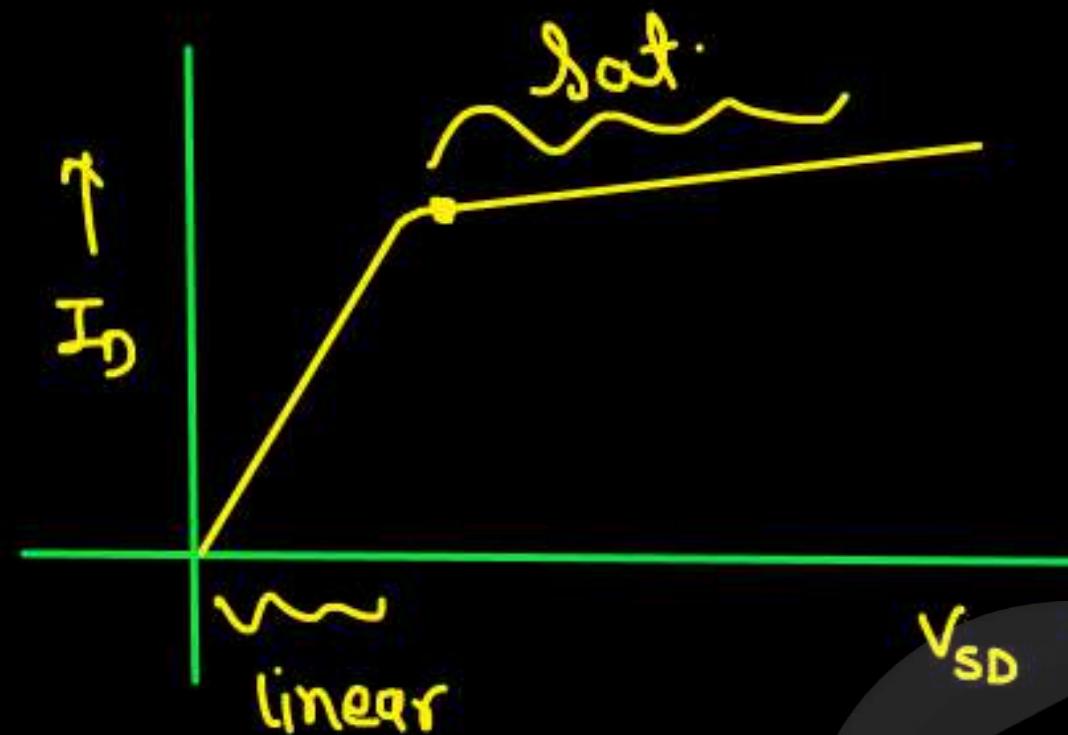

⇒ current can never go to zero in sat.  
 ⇒ it has to be in linear region =  
 (Because of zero current)

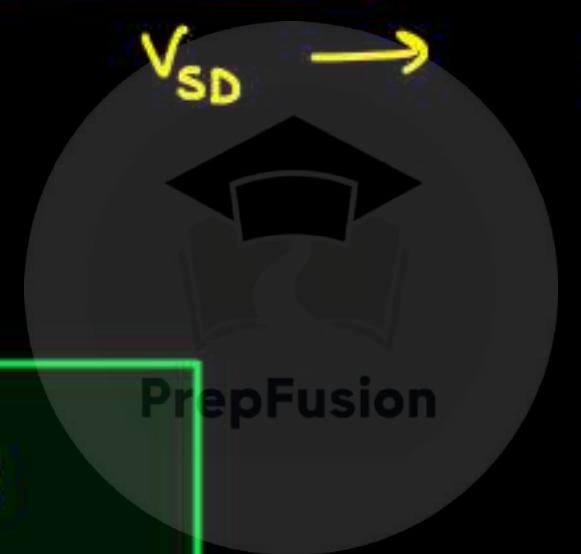$0 < V_i < V_{tn} : \quad V_o = V_{DD}$   
 pMOS → Linear  
 NMOS → Cut-off



$$(ii) V_t \leq V_i < V_{DD}/2$$

NMOS: -

$$V_{GS} = V_i > V_t \rightarrow ON \rightarrow Sat. or linear?$$


PMOS: -

$$V_{SG} = V_{DD} - V_i > |V_{tp}| \rightarrow ON \rightarrow Sat. or linear?$$

$$(5 - 2.5 > 1)$$

PrepFusion

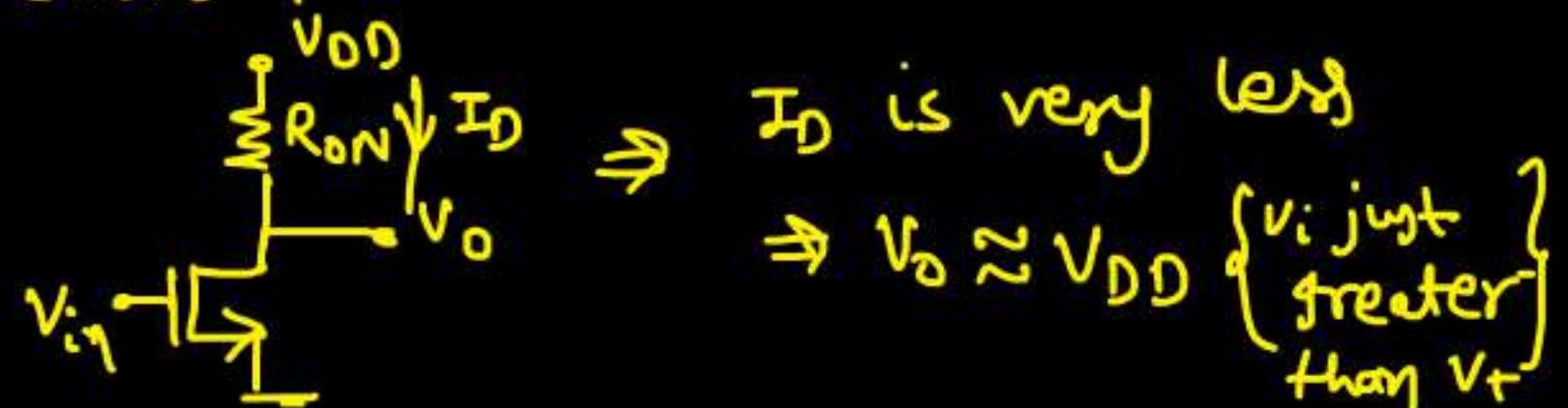→ whenever the MOS just turns on, it draws a very low amount of current.



So, for PMOS -

$V_{SD} \rightarrow$  very small  $\rightarrow$  it remains in linear region

for NMOS:-

$V_{DS} = V_o \approx V_{DD} \rightarrow$  very large

$$V_{GS} = V_{in}$$

$$V_{OV} = V_{in} - V_t$$

$\Rightarrow V_{DS} \gg V_{OV} \Rightarrow$  Sat. region

PrepFusion

$\rightarrow$  very low (Because  $V_{in}$  is just greater than  $V_t$ )

$V_{tn} < V_{in} < V_{DD}/2 \Rightarrow V_o \rightarrow$  goes down

PMOS  $\rightarrow$  Linear

NMOS  $\rightarrow$  Sat.

Now, your  $V_{in}$  is increasing

↓  
 $(V_{GS})_n$  is increasing.  
↓ NMOS in sat.

Current  $(I_D)_n$  is increasing

↓  
current in PMOS is also increasing  $((I_D)_p \uparrow)$

linear in  $(I_D)_p = 2k_p \left[ (V_{SG} - V_T) V_{SD} - \frac{V_{SD}^2}{2} \right]$

$$k_p = \frac{\mu_p C_o x W}{2L}$$

→  $V_{SG} \textcircled{1} \left\{ V_{SG} = V_{DD} - V_{in} \right\}$

→ But  $(I_D)_p \uparrow \Rightarrow (V_{SD})_p$  has to increase  
↓  
 $V_o$  starts going low

If  $(V_{SD})_P$  is increasing  $\Rightarrow$  PMOS in moving towards .  
at some point , both PMOS and NMOS will be in  
sat region =

$$(I_D)_{P_{sat}} = (I_D)_{n_{sat}}$$

$$k_p (V_{SG_p} - |V_{tp}|)^2 = k_n (V_{GS_n} - V_{tn})^2$$

$$V_{DD} - V_i - |V_{tp}| = \sqrt{\frac{k_n}{k_p}} (V_i - V_{tn})$$

$$V_{DD} - |V_{tp}| + \sqrt{\frac{k_n}{k_p}} V_{tn} = \sqrt{\frac{k_n}{k_p}} V_i + V_i$$

$$V_L = \frac{V_{DD} - |V_{tp}| + \sqrt{\frac{k_n}{k_p} V_{tn}}}{1 + \sqrt{\frac{k_n}{k_p}}}$$

if  $|V_{tp}| < V_{tn}$  and  $k_n = k_p =$

PrepFusion

$\Rightarrow V_L = V_{DD}/2$  → both NMOS & PMOS are in Sat. region.

@  $V_i = \frac{V_{DD}}{2} \Rightarrow$  Both PMOS & NMOS goes in sat.

only when  $k_n = k_p$

$$\mu_n C_{ox} \left( \frac{W}{L} \right)_n = \mu_p C_{ox} \left( \frac{W}{L} \right)_p$$

$$\Rightarrow \boxed{\frac{\left( \frac{W}{L} \right)_p}{\left( \frac{W}{L} \right)_n} = \frac{\mu_n}{\mu_p}}$$

generally,  $\mu_n > \mu_p \quad \{ \mu_n \approx 2.5 \mu_p \}$

$$\Rightarrow \left( \frac{W}{L} \right)_p = 2.5 \left( \frac{W}{L} \right)_n$$

if we want sat. region @  $V_i = V_{DD}/2$

$$\text{then } \left(\frac{W}{L}\right)_P > \left(\frac{W}{L}\right)_N \quad \left\{ \left(\frac{W}{L}\right)_P \approx 2.5 \left(\frac{W}{L}\right)_N \right\}$$

That's why the size of PMOS is larger than size of NMOS in CMOS inverter.

Since,  $V_{in} = V_{DD}/2 \rightarrow \text{sat.}$   
PMOS  $\rightarrow \text{sat.}$

$$V_{SD} = V_{DD} - V_0$$

$$V_{DS} = V_{SG} - |V_{TP}|$$

$$\leq V_{DD} - V_{in} - |V_{TP}|$$

@ Sat.  $\rightarrow$

$$V_{DD} - V_0 = V_{DD}/2 - |V_{TP}|$$

$$V_0 = V_{DD}/2 + |V_{TP}| =$$

PrepFusion

NMOS  $\rightarrow \text{sat.}$

$$V_{DS} = V_0$$

$$V_{DV} = V_{in} - V_{TP}$$

@ Sat.


$$V_0 \approx V_{DD}/2 - V_{TP} \approx$$

So, @  $V_{in} = V_{DD}/2$ , we are getting two op:-


$$V_o = \frac{V_{DD}}{2} + |V_{TP}| \quad \text{and} \quad V_o = \frac{V_{DD}}{2} - V_{TN}$$

↓ Take avg.

$$(V_o)_{avg} = \frac{V_{DD}}{2}$$

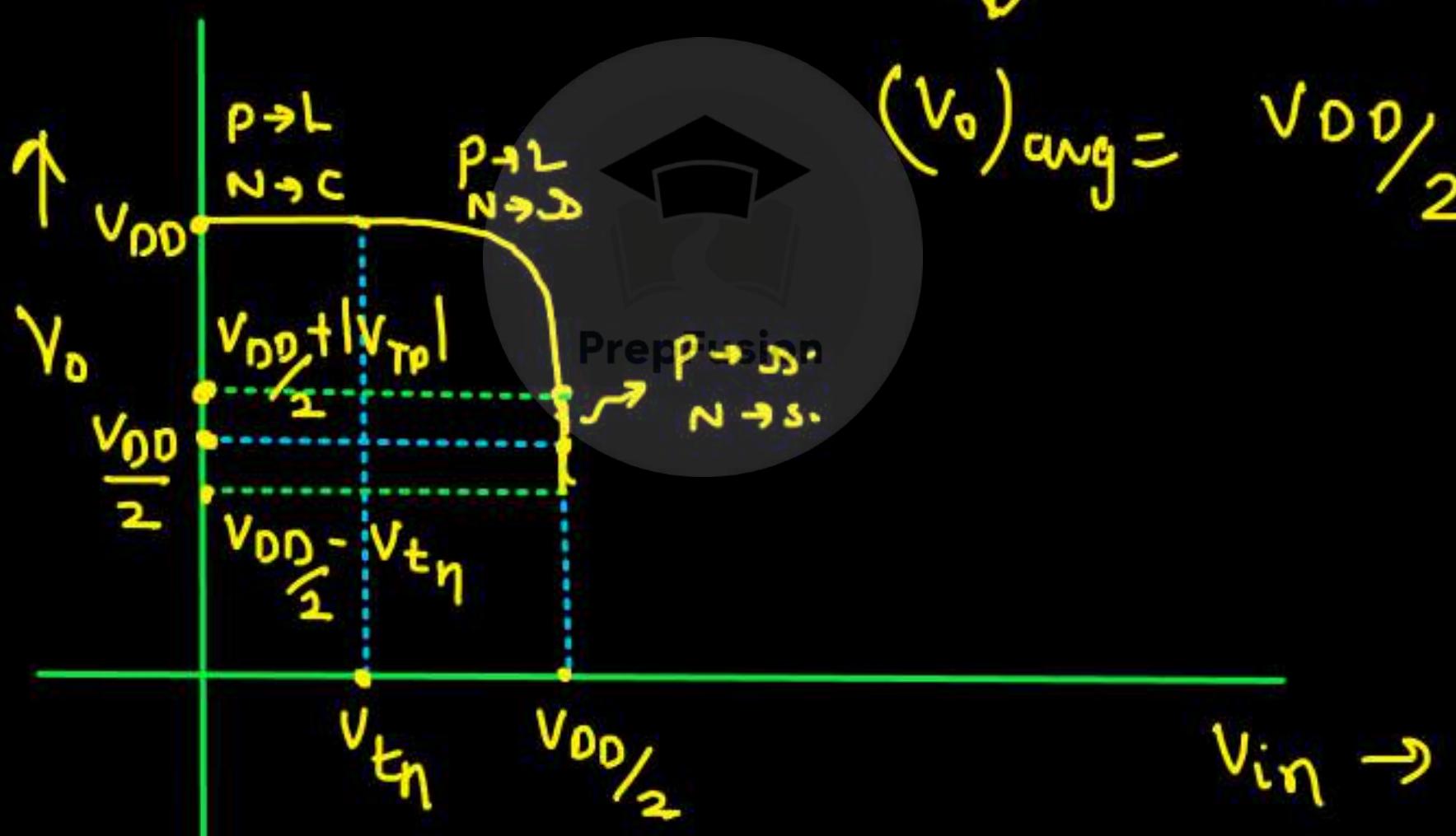

$$\text{now, } V_{DD/2} < V_i < V_{DD} - |V_{tp}| \Rightarrow 2.5 < V_i < 4$$

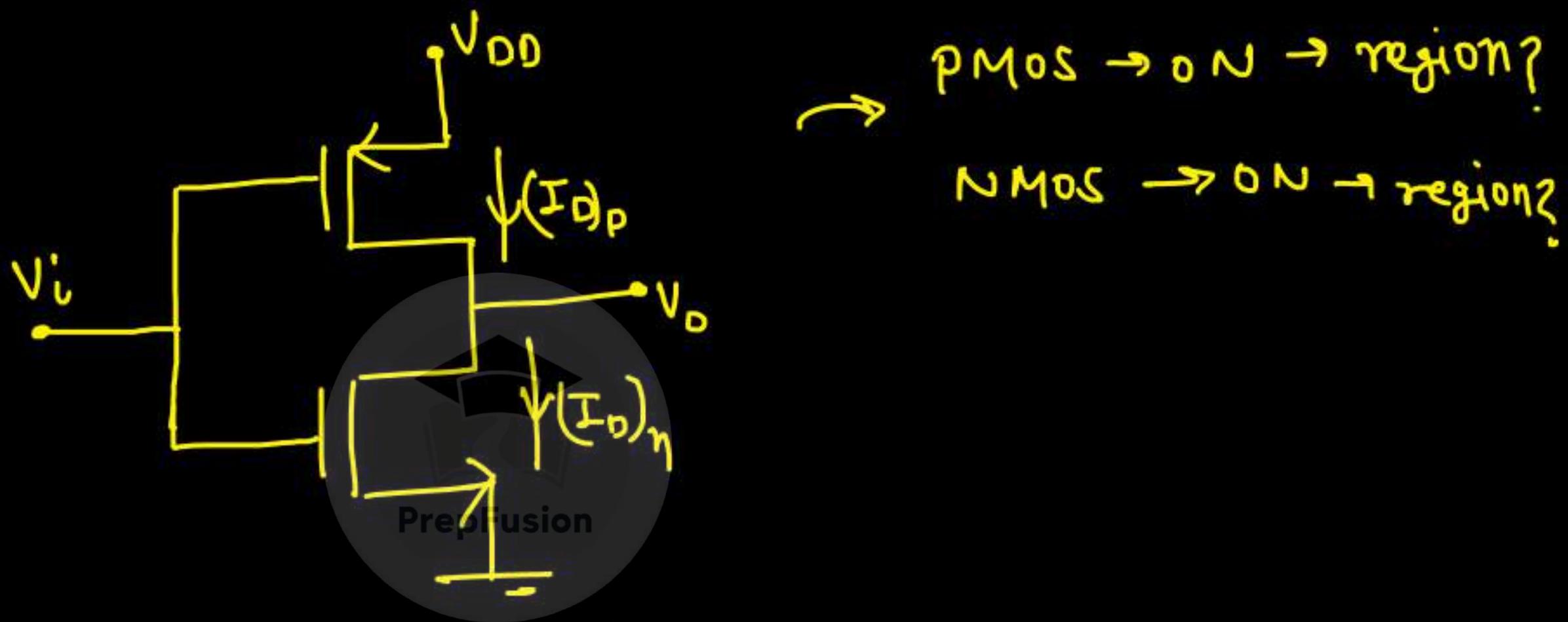

PMOS →

$$V_{SD} = V_{DD} - V_D$$

$$V_{SG} - V_T = V_{DD} - V_{DD/2} - V_T$$

PMOS → Jat.

Assume  $V_{in} = 4.1 \rightarrow 3.9$

@  $V_{in} = 4.1 \Rightarrow \text{PMOS off}$

@  $V_{in} = 3.9 \Rightarrow \text{PMOS just turns on}$

$I_D \rightarrow \text{less} \Rightarrow V_D \text{ is less} \Rightarrow (V_{SD})_P \downarrow$   
Jat.

NMOS →

$V_o$  goes low  $\Rightarrow (V_{DS})_n$  goes low  $\Rightarrow$  moves towards linear region

$\Rightarrow$  NMOS → Linear

$\frac{V_{DD}}{2} < V_i < V_{DD} - |V_{TP}| \Rightarrow V_o$  goes low

PMOS → Sat.

NMOS → Linear

PrepFusion

Now,  $V_{DD} - |V_{TP}| \leq V_i < V_{DD} \Rightarrow 4 \leq V_i < 5$

pMOS  $\rightarrow$  off

NMOS  $\rightarrow$  ON  $\Rightarrow$  linear {  $(I_D)_{n=0}$  is possible only in  
linear region }


$$V_{DD} - |V_{TP}| \leq V_i < V_{DD} \Rightarrow V_o \text{ nearly goes to zero}$$

$\Rightarrow$  pMOS  $\rightarrow$  cut off

NMOS  $\rightarrow$  linear

PrepFusion

## Voltage Transfer characteristics:-

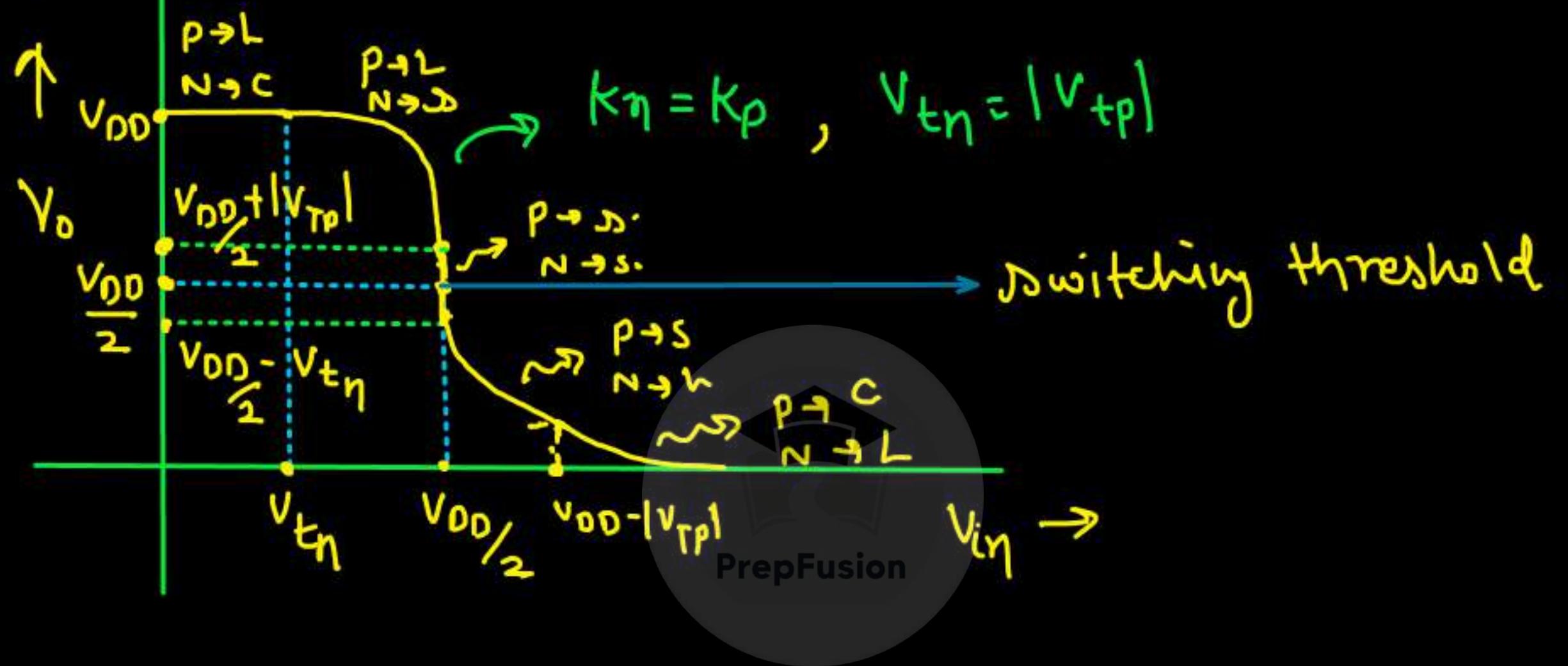

\*  $V_i$  for "sat. in both NMOS and PMOS"

$$(V_i)_{s.t.} = \frac{V_{DD} - |V_{TP}| + \sqrt{\frac{k_n}{k_p} V_{tn}}}{1 + \sqrt{\frac{k_n}{k_p}}} \rightarrow \text{Switching Threshold}$$

when  $k_n = 4k_p$  and  $|V_{TP}| = V_{tn}$

$$(V_i)_{s.t.} = \frac{V_{DD} + 2}{3} = \frac{5+2}{3} = 2.33 < 2.5V$$

↓  
Switching Threshold decreased

when  $k_n = 4k_p \rightarrow VTC$  moves towards origin.

When


$$k_n = \frac{k_p}{4}, \quad |V_{TP}| = V_{TN} = LV$$

$$(V_i)_{S-T} = \frac{V_{DD} + \frac{L}{2}}{\frac{L + \frac{L}{2}}{2}} = \frac{5.5}{1.5} = 3.66 > 2.5$$



S.T. increased

VTC move away from origin

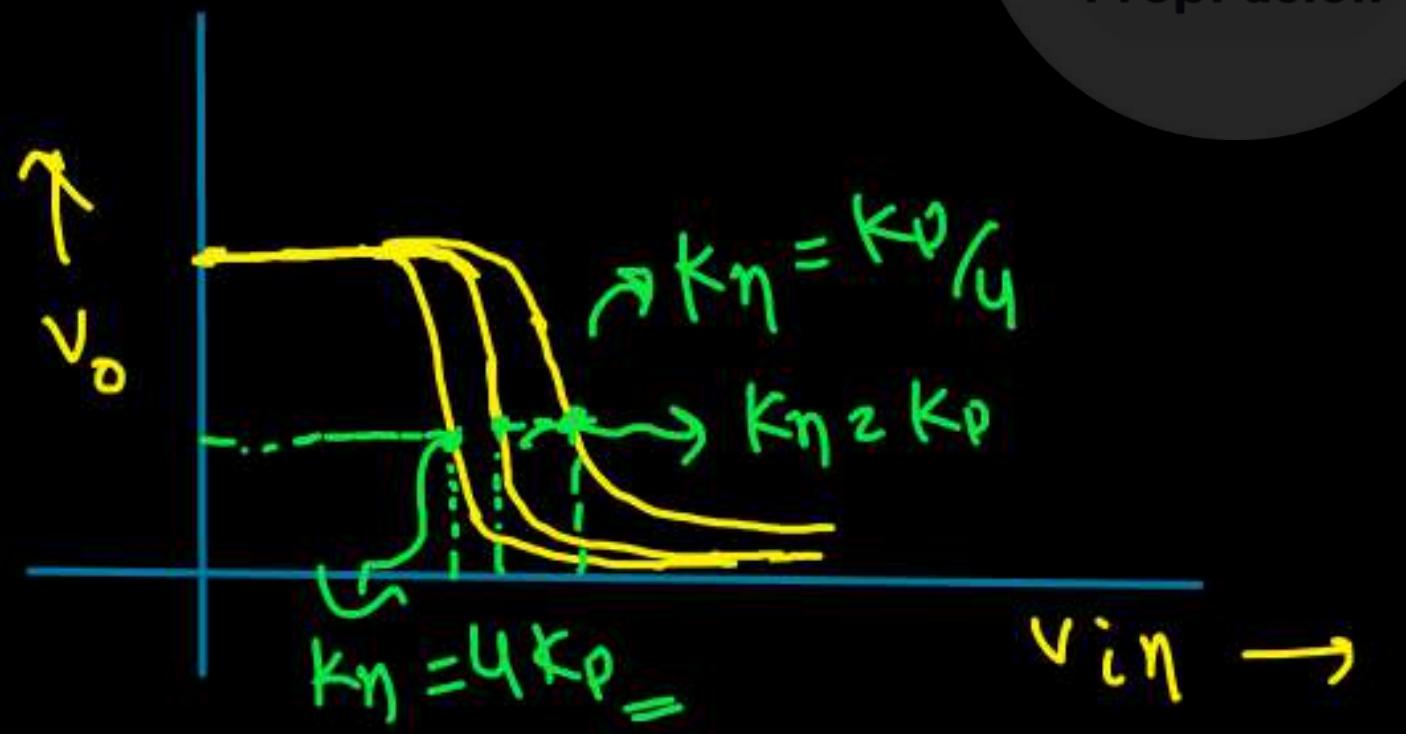


⇒ Interchanging PMOS & NMOS in CMOS inverter?

↳ Need of CMOS inverter?

- for a High i/p, we want output to go all the way down to zero.
- for a low i/p, we want output to go all the way up to 5V. (V<sub>t</sub> = 1V)


PrepFusion

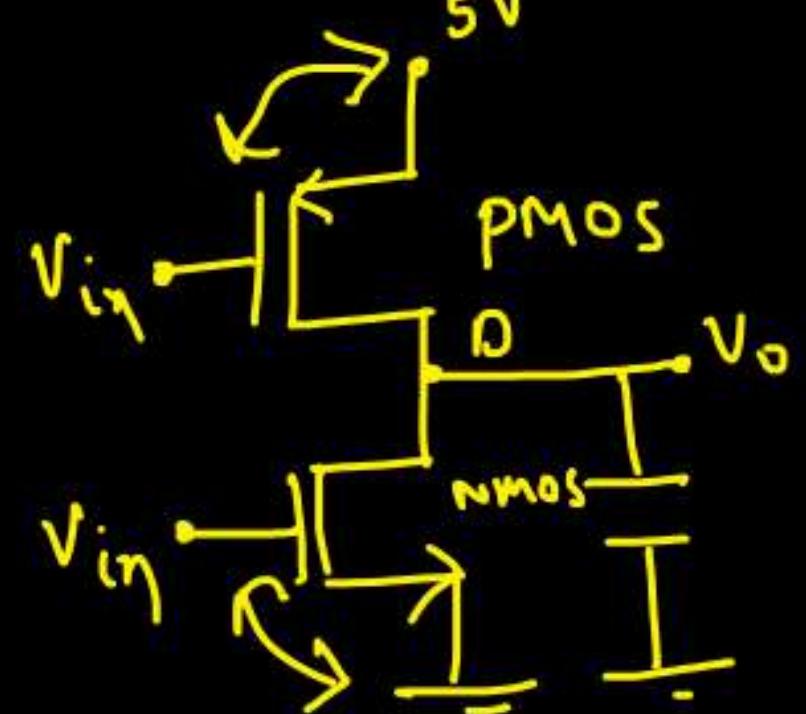

$$V_{in}=0 \Rightarrow (V_o)_{5.5} = 5V$$

$$V_{in}=5 \Rightarrow (V_o)_{5.5} = 0V$$

Interchanging:-

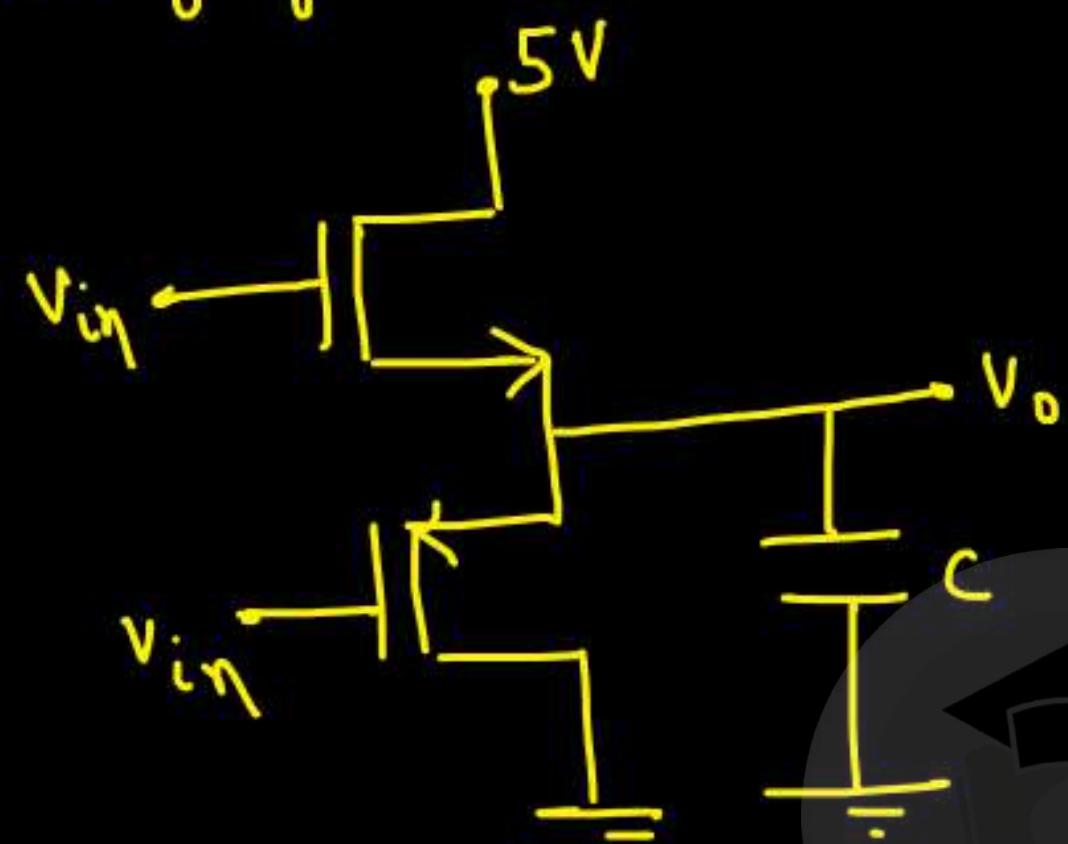

When  $V_{IN} = 5V =$   
 $N \rightarrow ON$   
 $P \rightarrow OFF$

$$(V_0)_{SS} = 4V$$

When  $V_{IN} = 0V$   
 $N \rightarrow OFF$   
 $P \rightarrow ON$

$$(V_0)_{SS} = 1V$$

- it's acting like a buffer, not inverter.
- your o/p doesn't go all the way up to 5V and doesn't come down all the way to 0V-