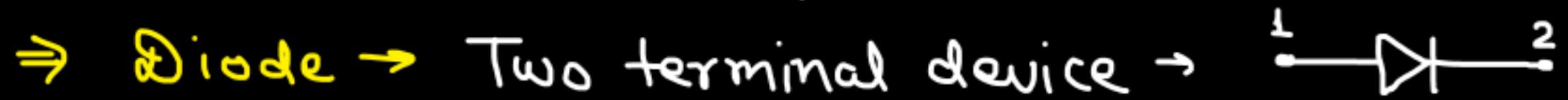



\* What we have studied ?


⇒ Diode → Two terminal device → 

\* What did we get from diode ?


- ① Clipper → clips off undesired part.
- ② Clamper → Sets a new dc value of the i/p.
- ③ Peak detector → detects peak value of i/p and gives dc o/p.
- ④ Voltage Multipliers → gives the o/p more than the max value of i/p signal (dc o/p)

## ⑤ Small signal Analysis :-

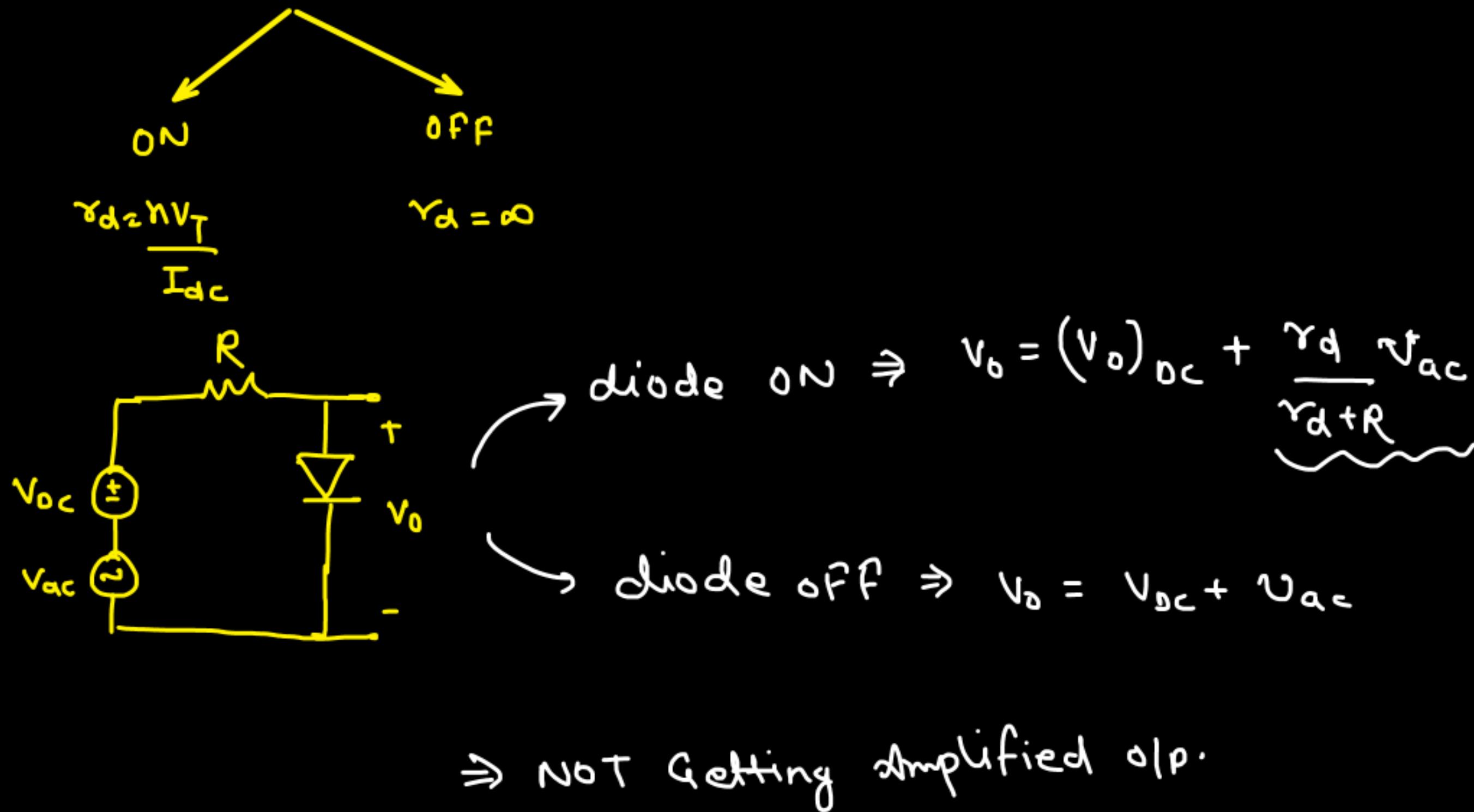


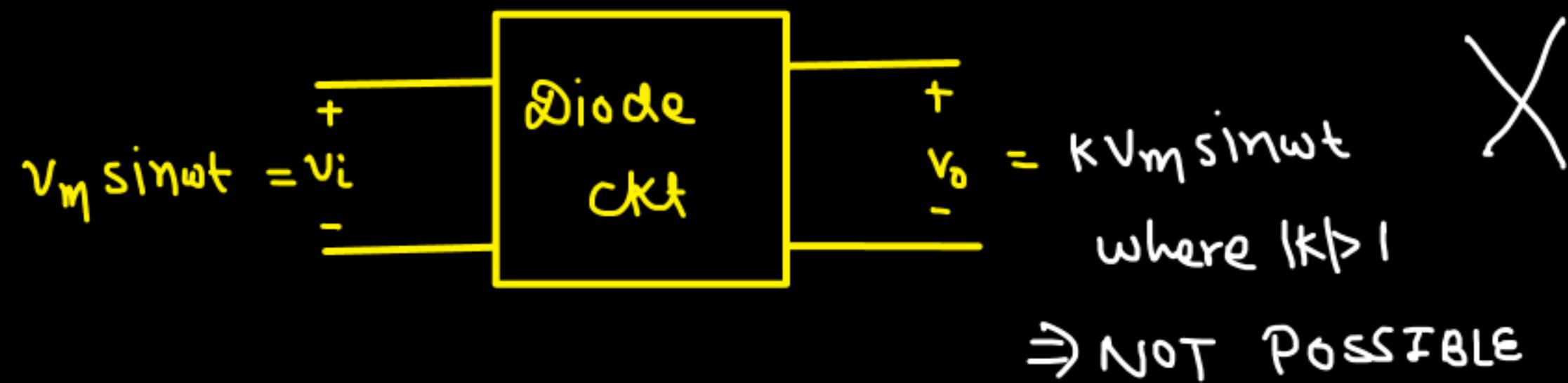

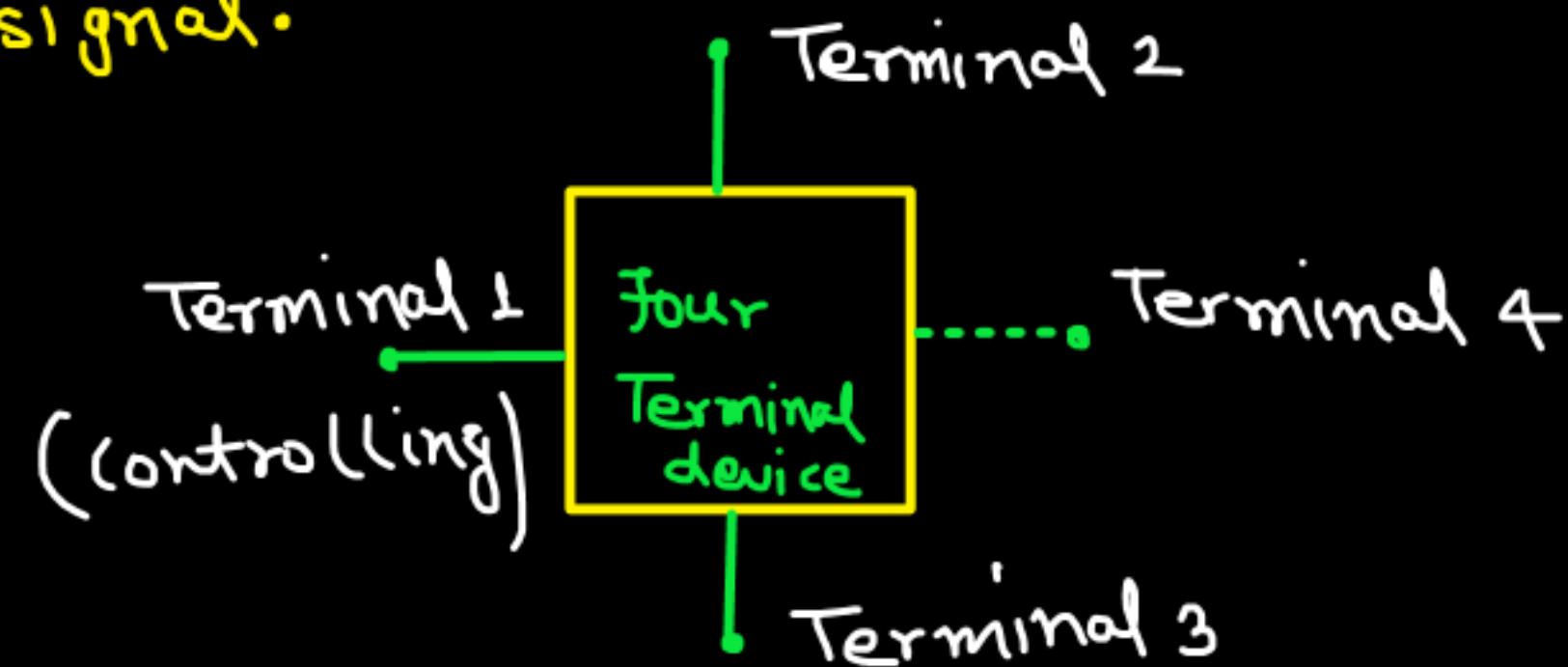⇒ You need some three / four terminal device for amplification of i/p ac signal.



## A Basic Amplifier :-

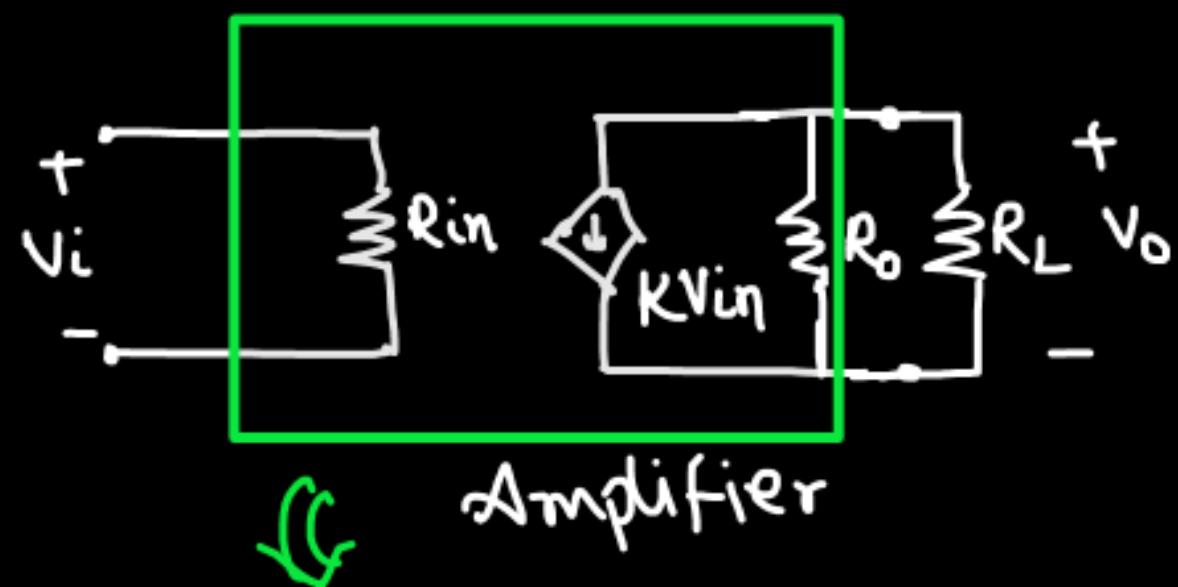

$$V_o = -K R_L V_{in}$$

↓

Amplification =

Gives Rise to Transistors



## Field Effect Transistors

(FET)



MOSFETs

(Metal oxide semiconductor)

Depletion Type

n-channel




p-channel

Enhancement type

n-channel

p-channel
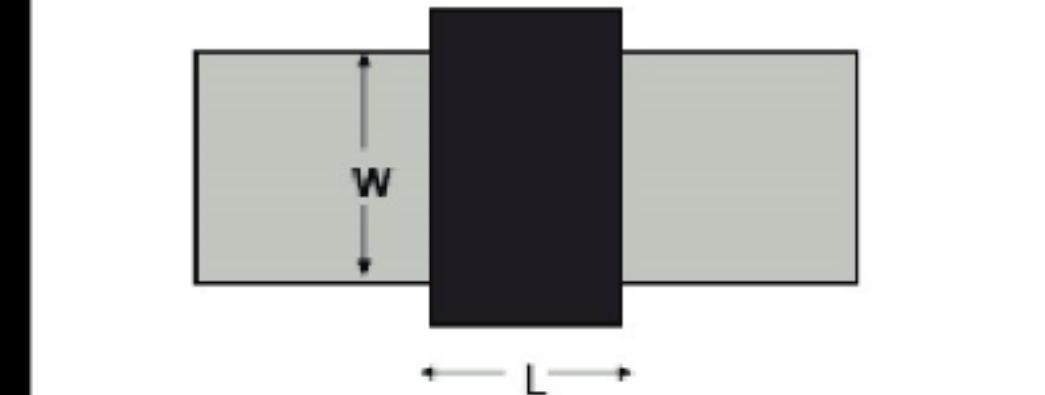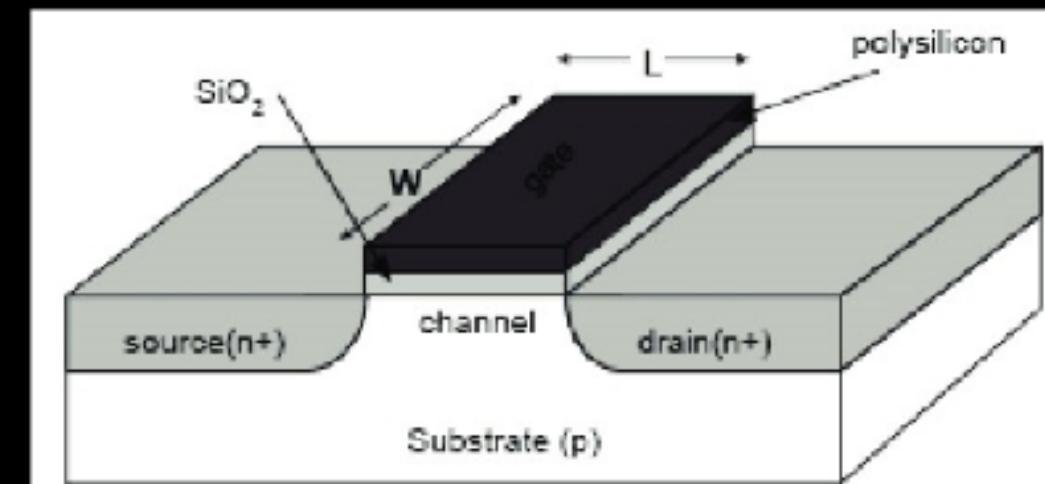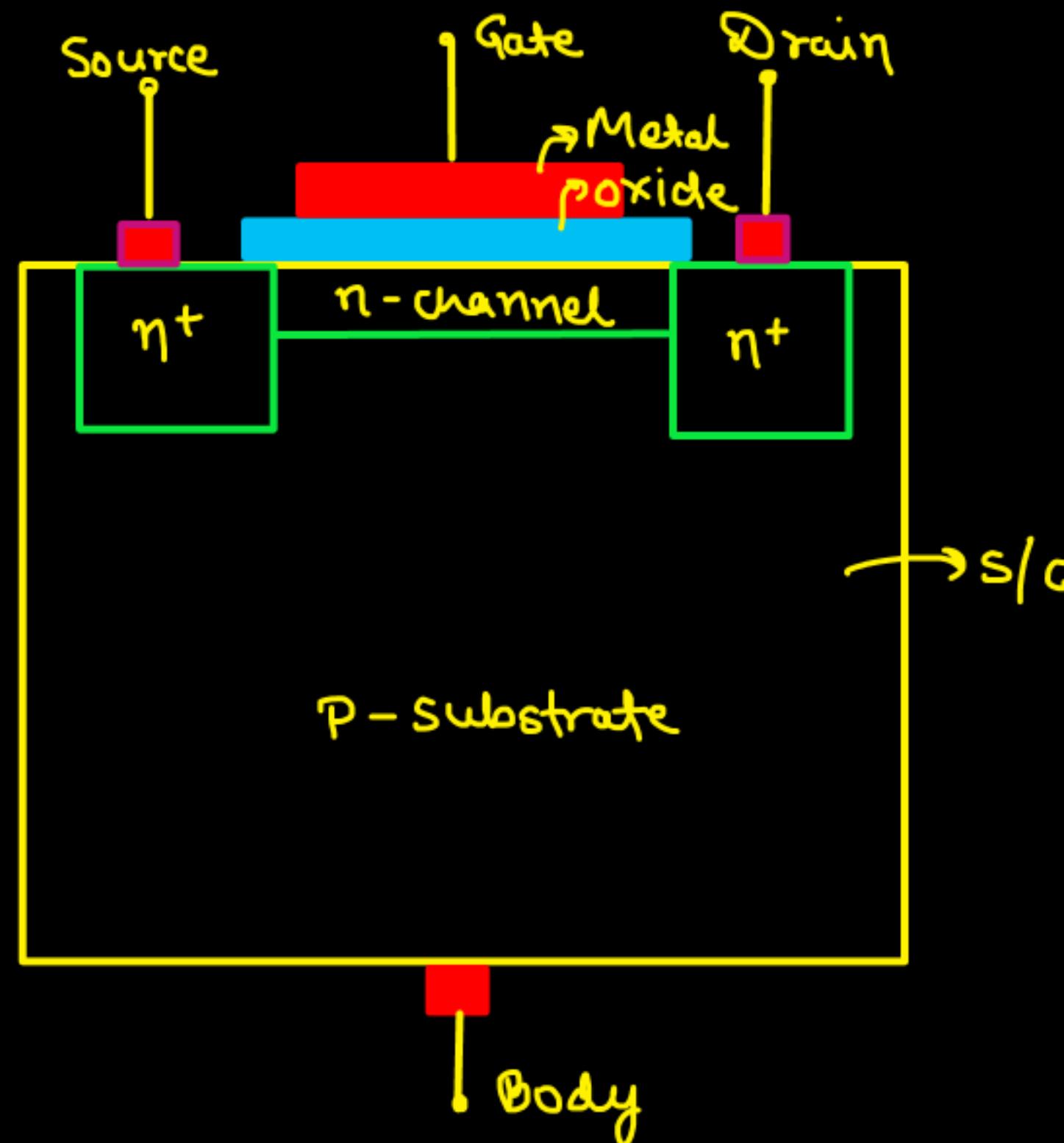
# ① n-type depletion MOSFETs: - [channel is already $n^+$ ]




[Photo from ResearchGate]

MOS  $\rightarrow$  4 terminal device

(Gate, Source, Drain, Body)

- ① Source:- Supplies the charge carrier to the channel.
- ② Drain:- Collects the charge carrier from the channel.
- ③ Gate:- Controls the flow of charge carriers.
- ④ Channel:- The path b/w drain and source from where the charge carrier travels.
- ⑤ JET (Field Effect Transistor):- The flow of current is modulated by applied voltage or electric field.

Analogy :-

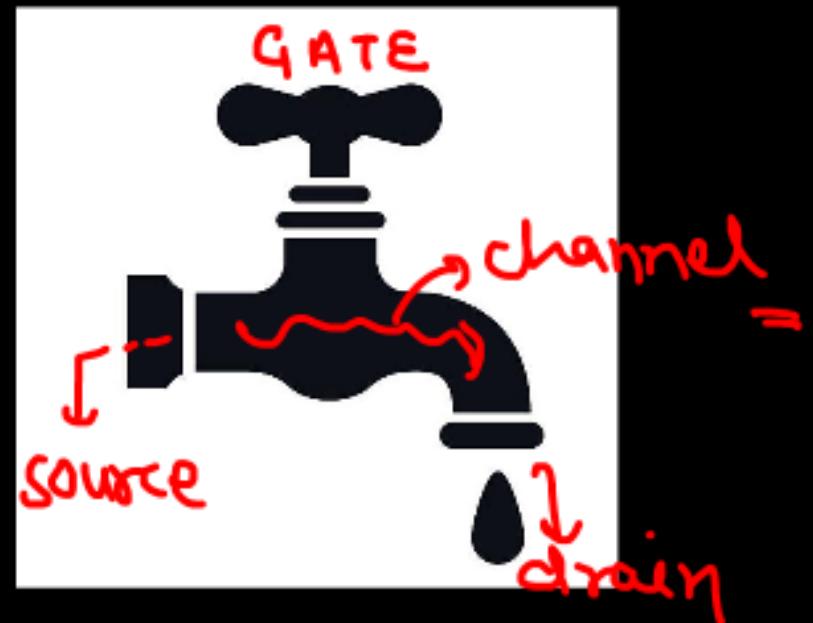


For n-channel depletion type MOSFET :-

Cod<sup>n</sup> L :-

(i)  $V_{GS} = 0V$

(ii)  $V_{DS} = +ve$

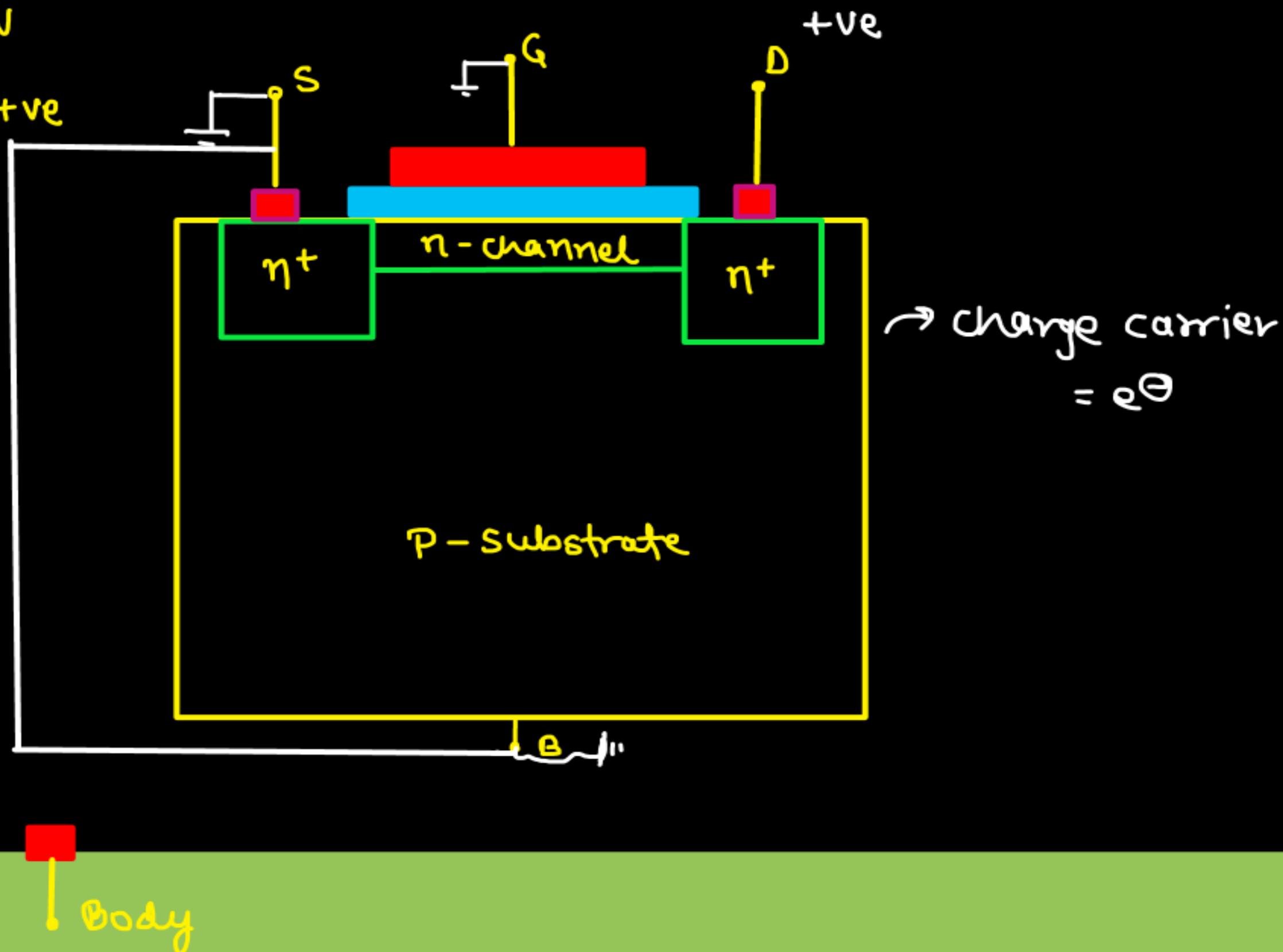

$n^+$  → Highly doped → more conductivity

↓  
less resistance

$n$  → lightly doped → less conductivity



↑  
More resistance



n-type





p-type

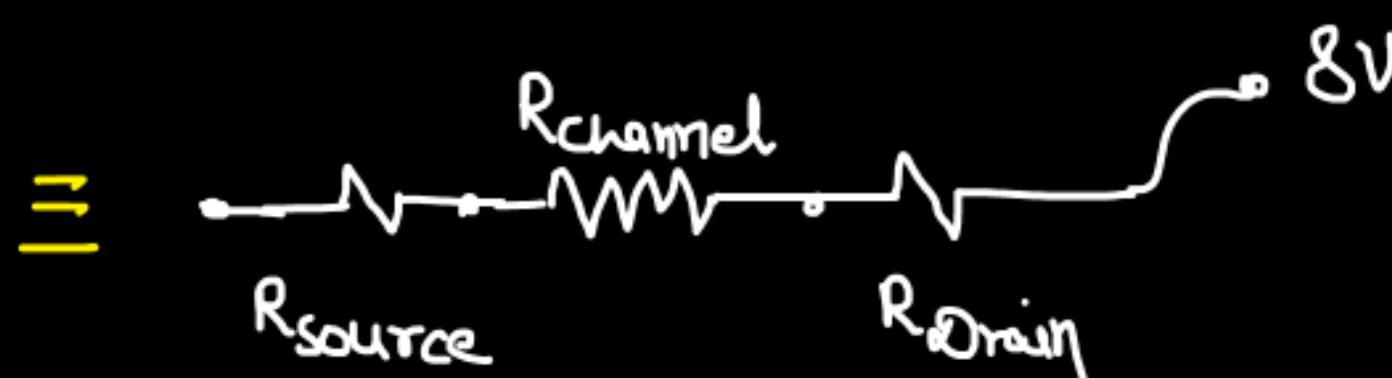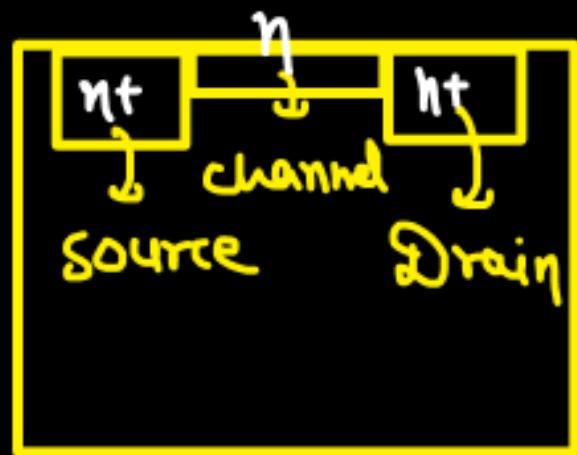


Assumption

$R_{channel} > R_{Drain}, R_{Source}$

$$R_{eq} = 2R_D = 2R_S$$

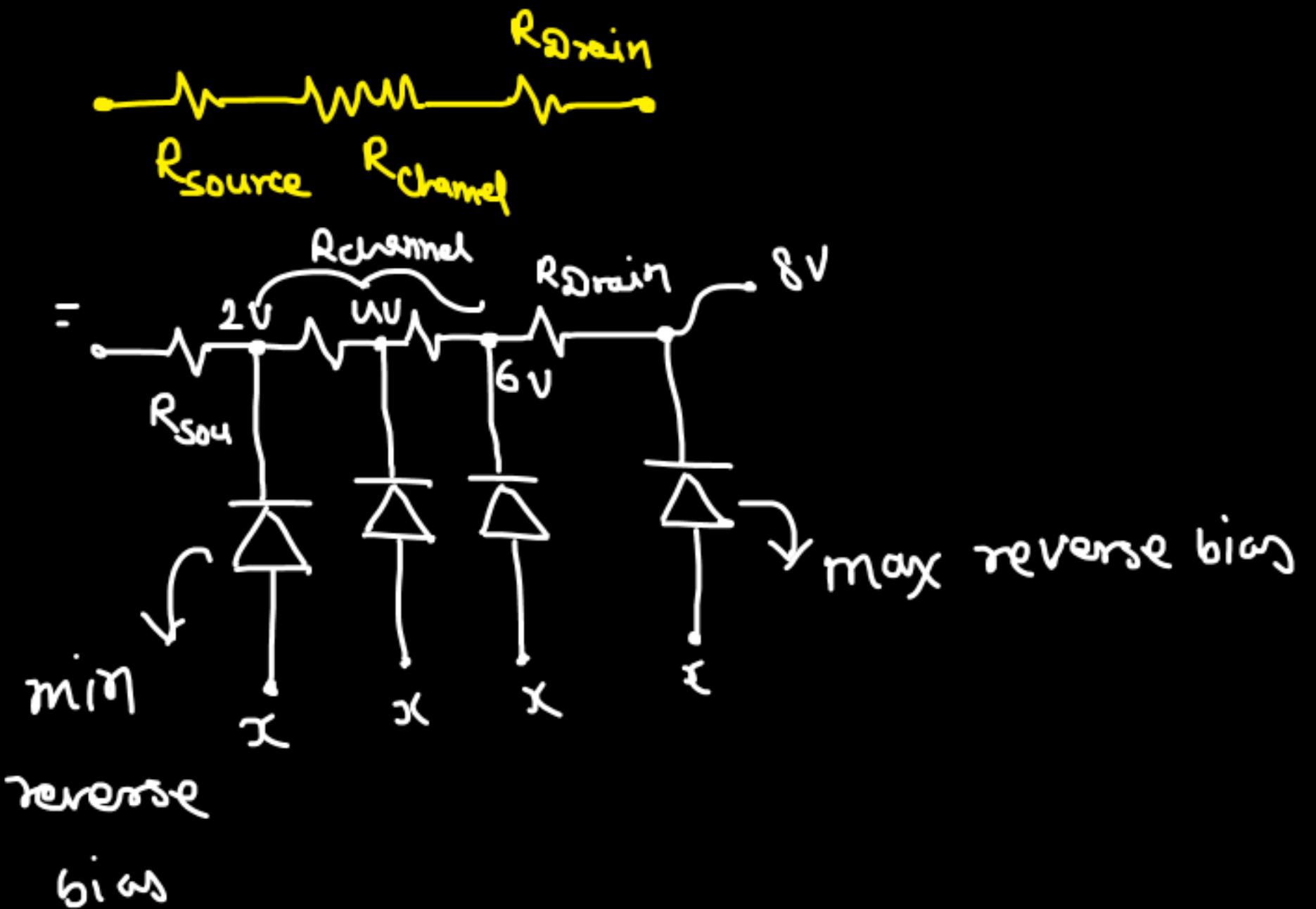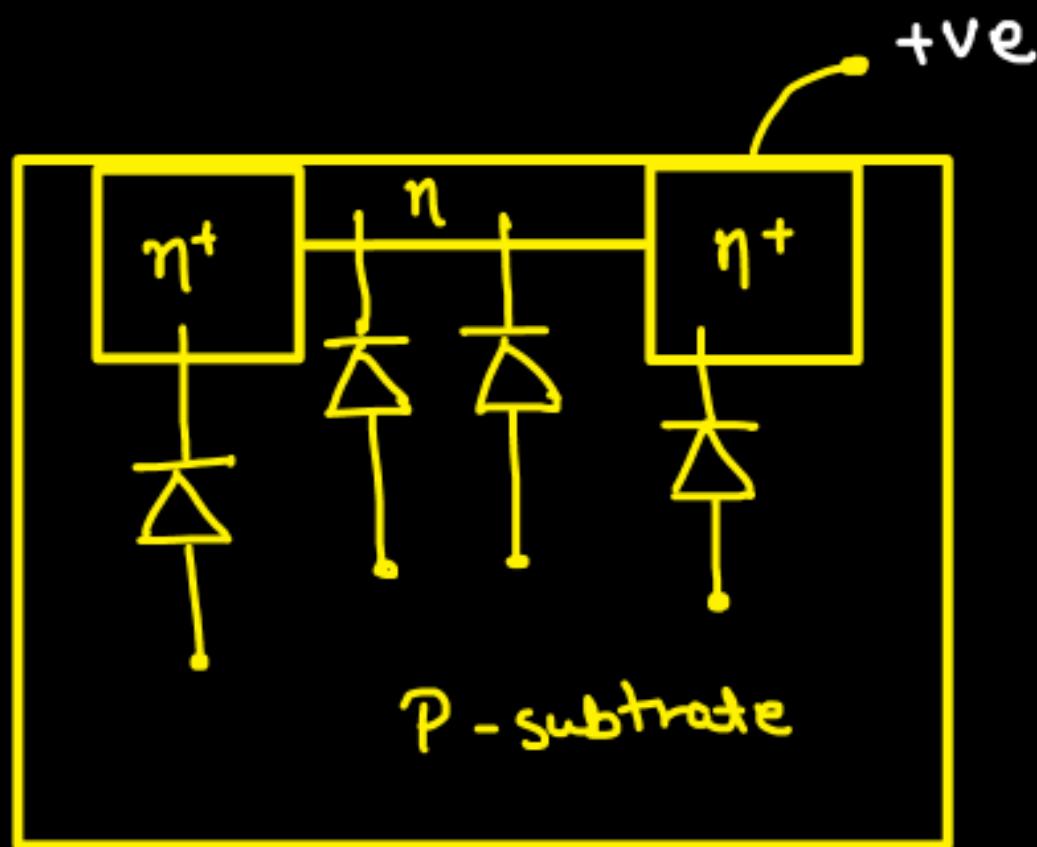

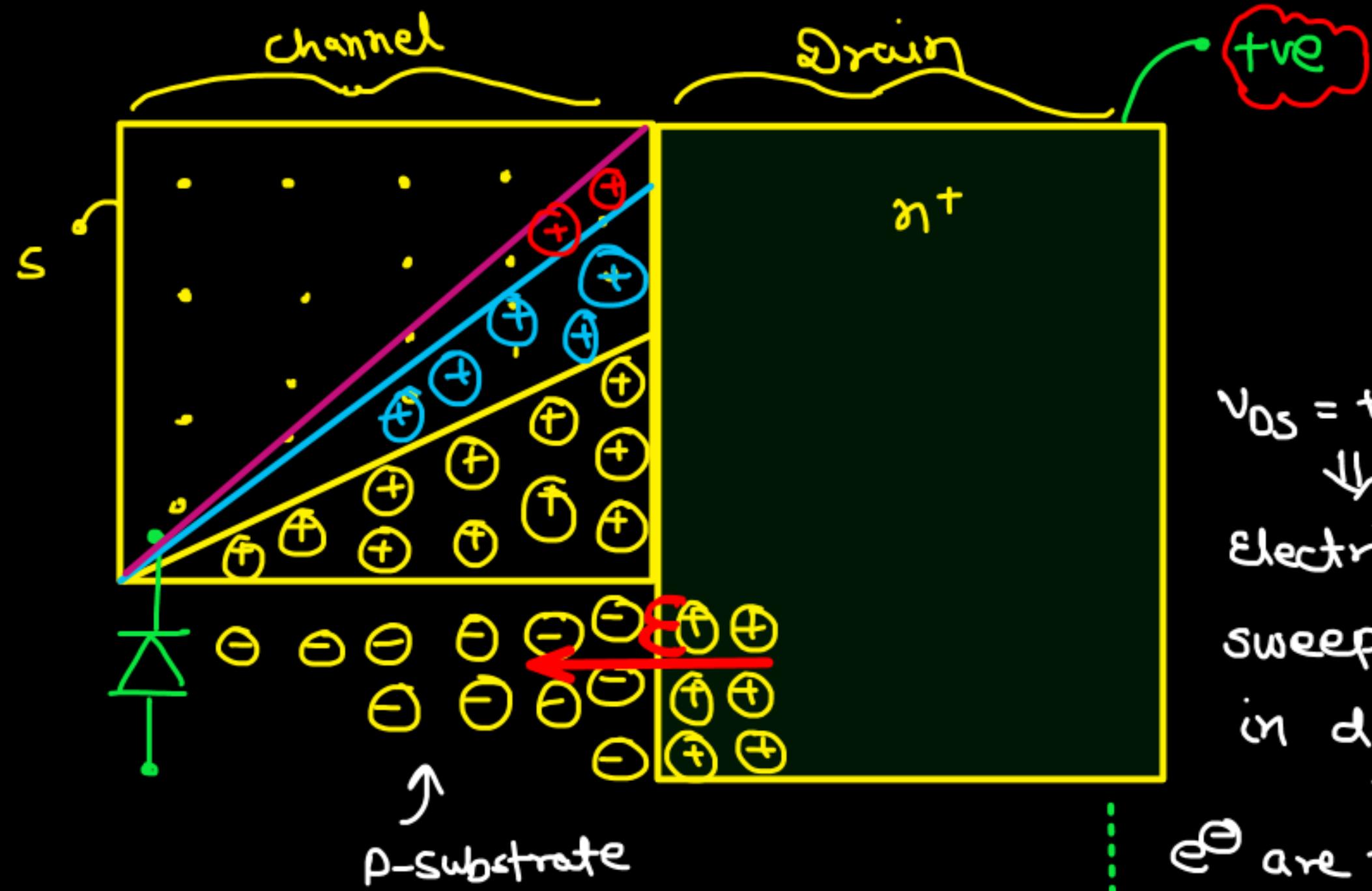
From drain to source , Reverse bias  $\downarrow \Rightarrow$  depletion width  $\downarrow$



What if  $V_{DS} \uparrow \uparrow \Rightarrow "E"$  will be strong  $\Rightarrow e^-$  will travel fast  $\Rightarrow$  current  $\uparrow$

$V_{DS} = +ve$   
 $\downarrow$   
 electric field  $E$  will sweep away the  $e^-$  in drain terminal  
 $\downarrow$

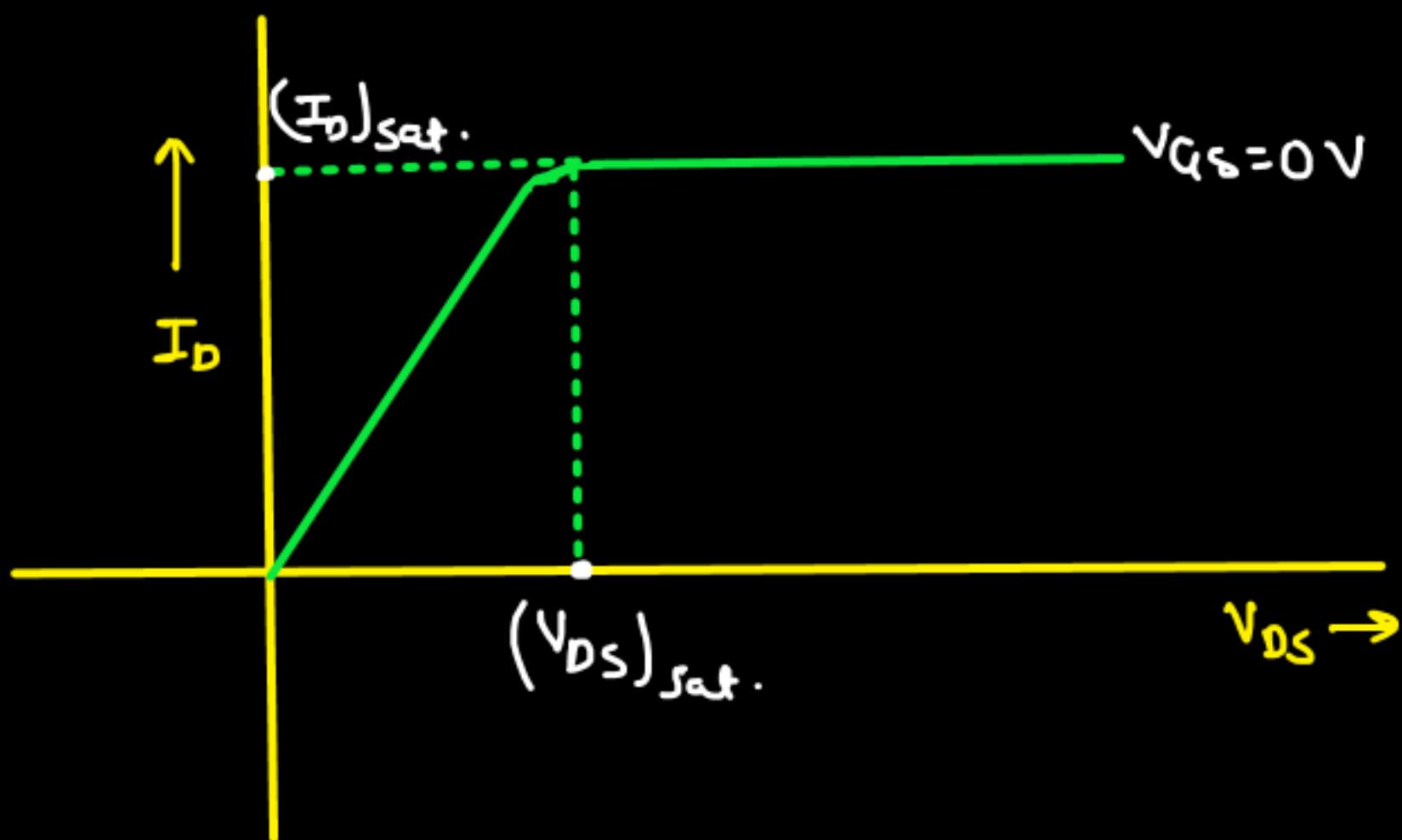$e^-$  are moving from source to drain  
 $\downarrow$   
 current will flow from drain to source.




But @ a certain value of  $V_{DS}$ , the channel will start having very less charge carriers. Although the "E" field is strong but the charge carriers are less and because of that current saturates.

cond<sup>n</sup> 2:-

$V_{DS} = +ve$  {Fixed}

$V_{GS} = \text{varying} [-ve \rightarrow +ve]$

①  $V_{GS} = -ve$

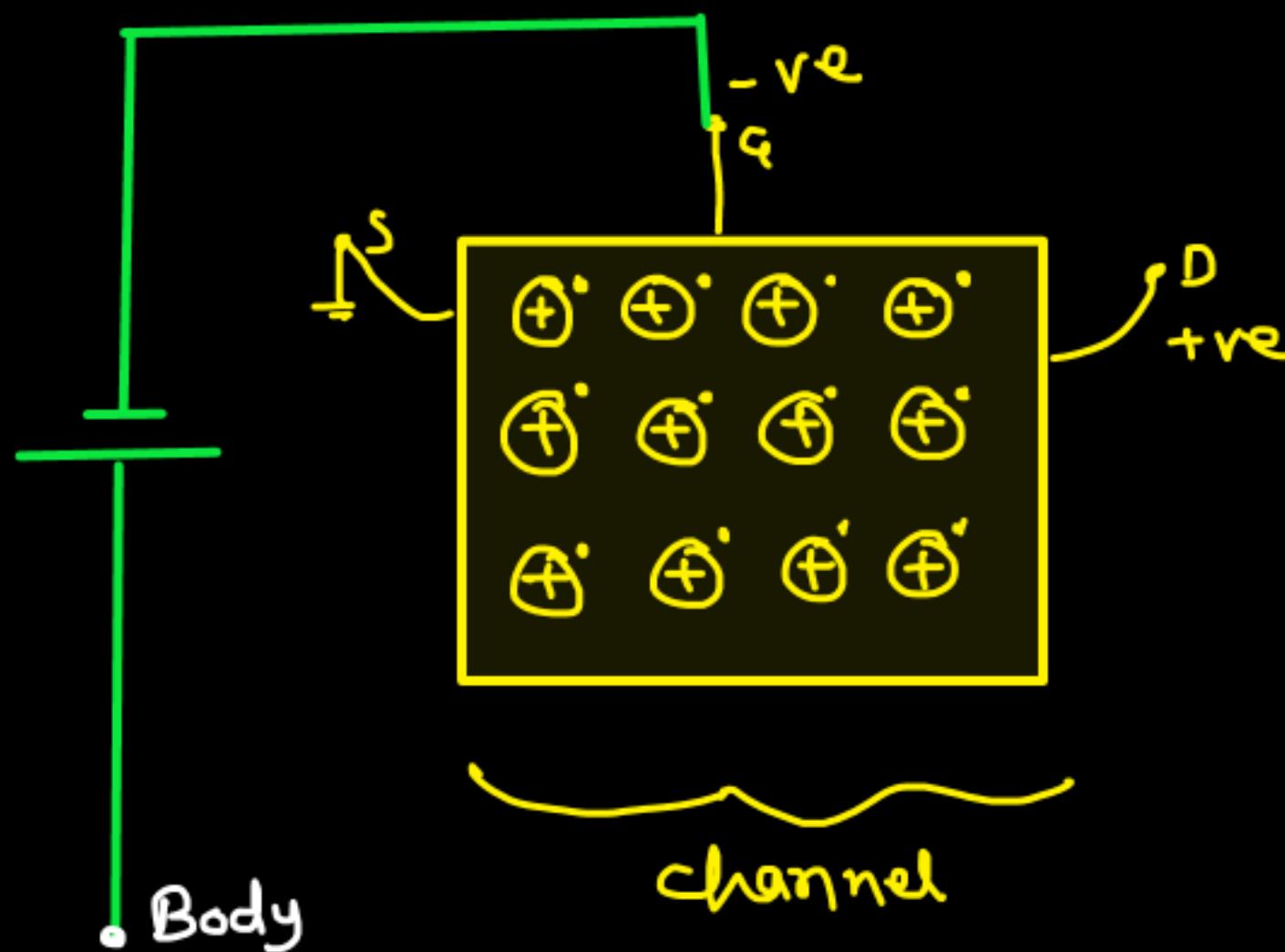


$V_G$  is increasing in negative dir<sup>n</sup>

↓  
channel is getting depleted of charge carrier

↓  
current is decreasing


if we keep on decreasing  $V_{GS}$  value, then

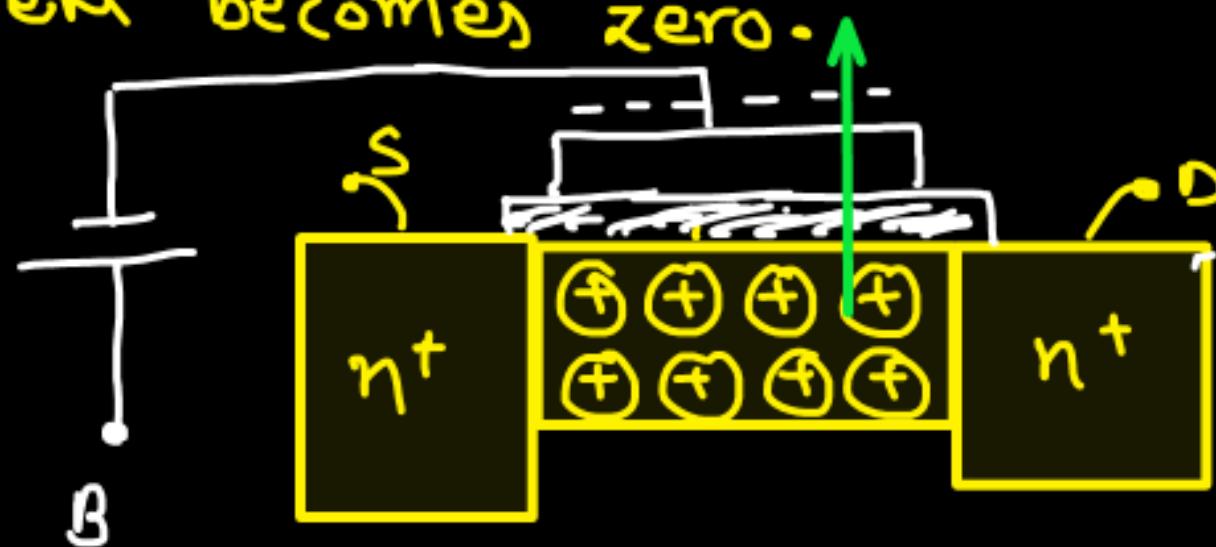@ Some -ve  $V_{GS}$  value, the channel will be depleted of charge carrier and the electric field in vertical direction will be so strong that the e $\Theta$  from source side will not be reaching the drain side and the current becomes zero.



⇒ Negative potential is known as pinch-off voltage.

②  $V_{GS} = +ve$

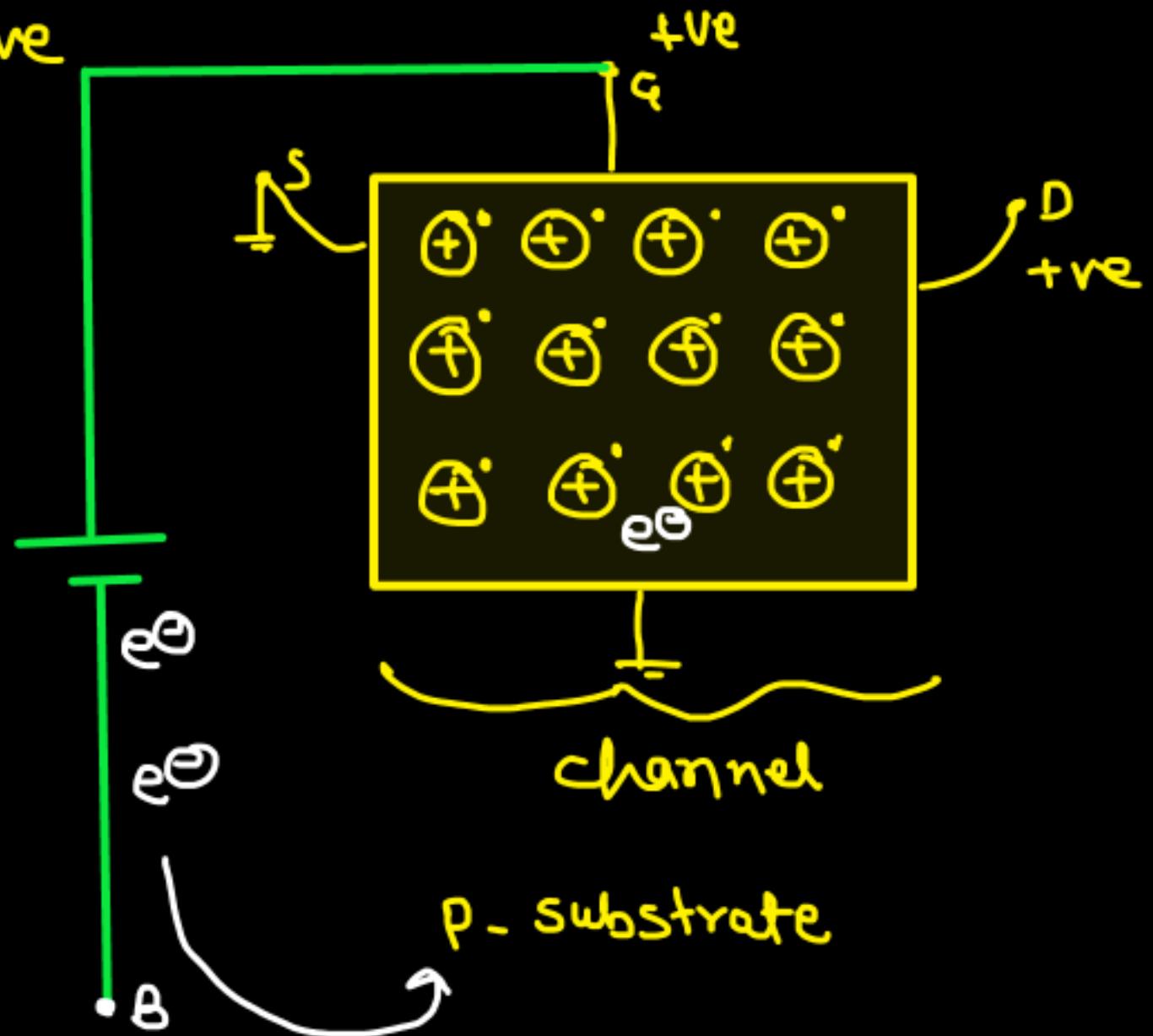


$V_G \uparrow \Rightarrow$  more  $e^-$  in channel




$I_D \uparrow$


$I_D$  v/s  $V_{DS}$  curve:-

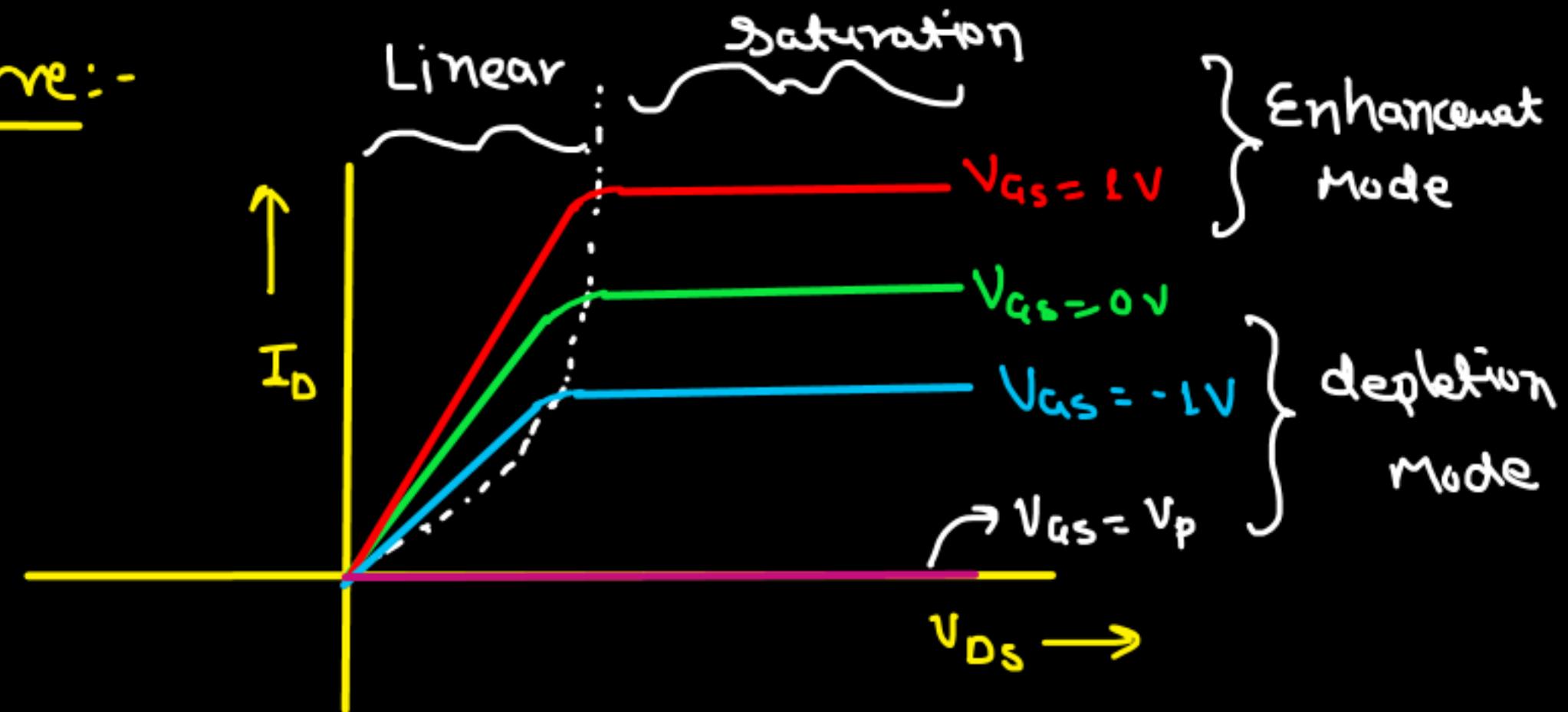

$I_D$  v/s  $V_{GS}$  curve:-

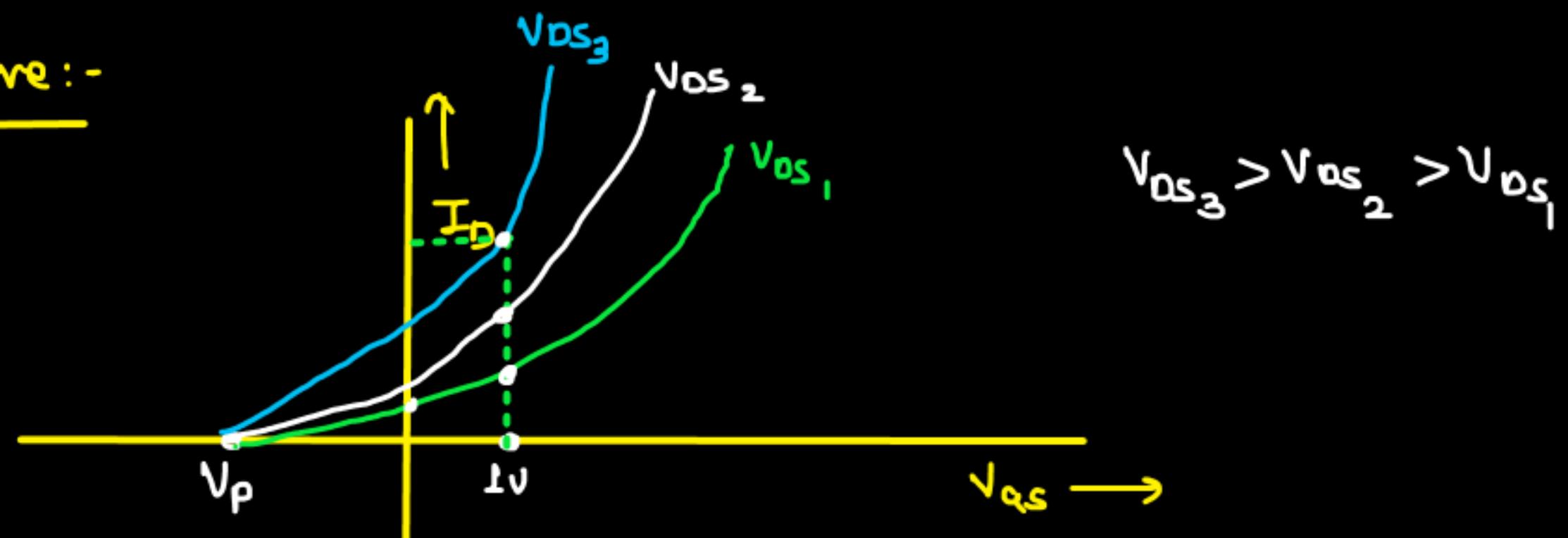


## P-channel depletion type MOSFET :-

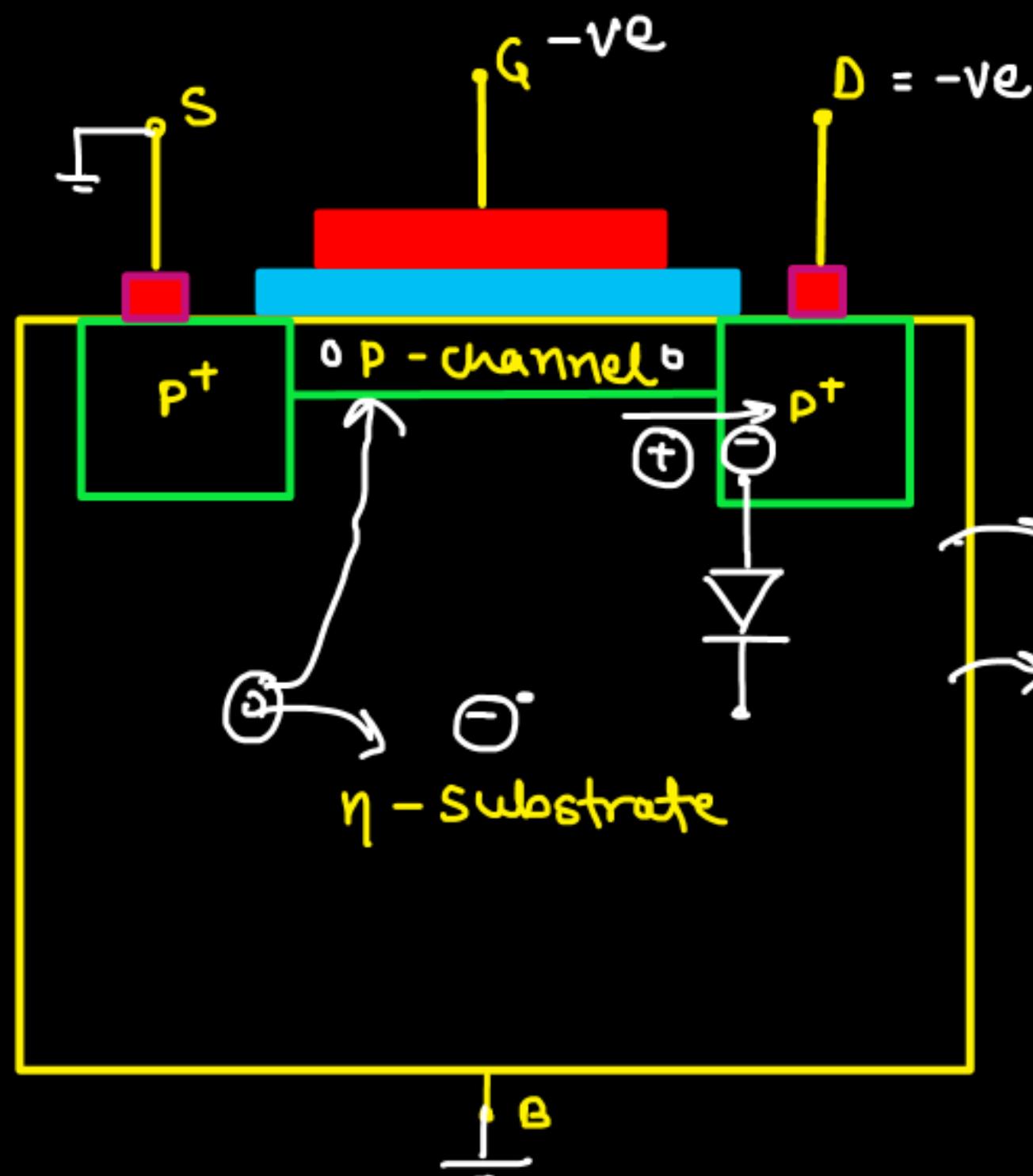


charge carrier = holes  
current dir<sup>n</sup>  $\Rightarrow$  Source to drain =

## $I_D$ v/s $V_{DS}$ curve :-

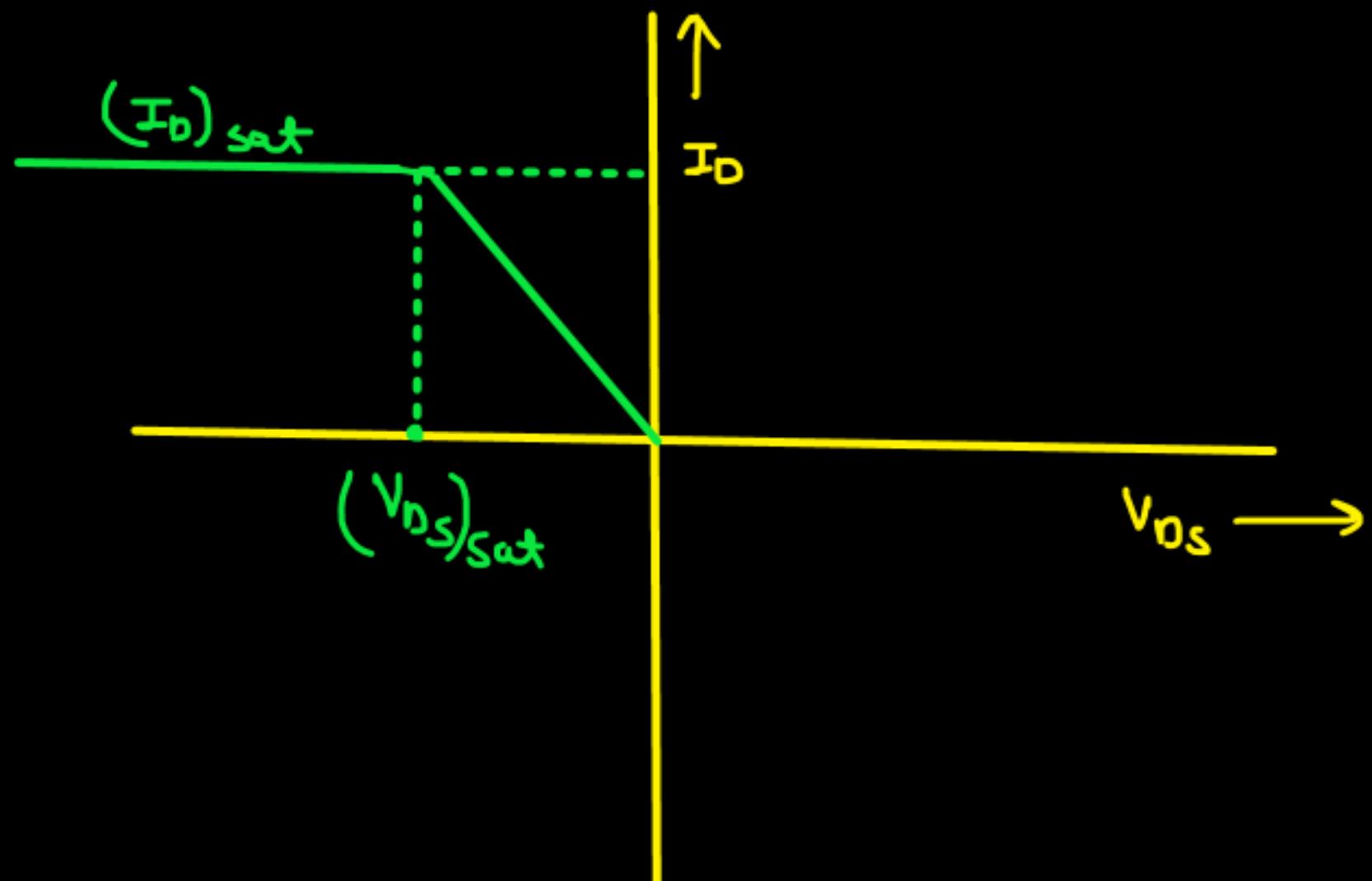

$I_D$  direction  $\Rightarrow$  Source to drain


$I_D$  v/s  $V_{GS}$  curve :-

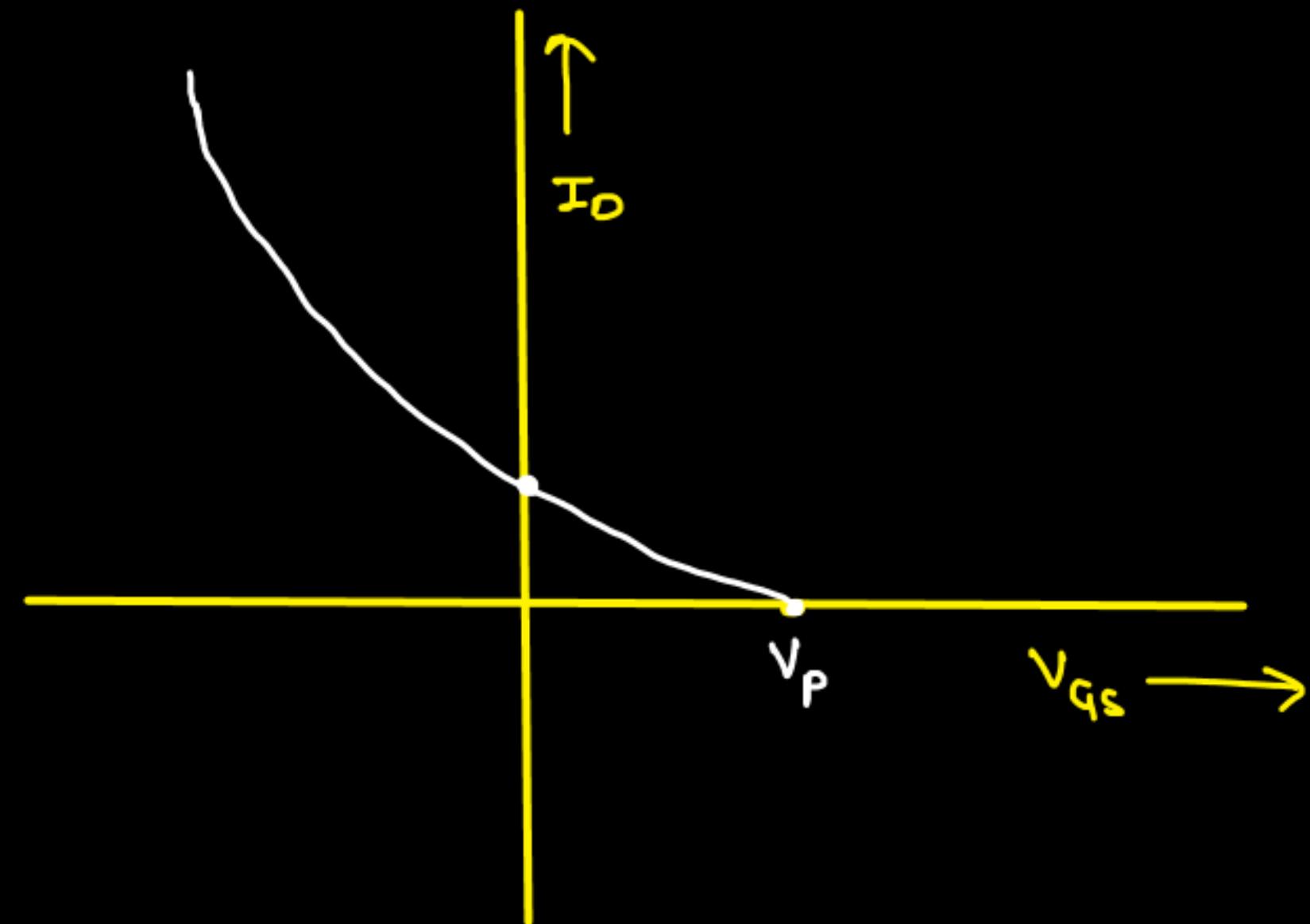

N.B. - In depletion type MOSFET, the channel (P or n) was already present. Even if you don't apply any controlling voltage @ gate terminal ( $V_{GS} = 0V$ ), still there will be some current flowing in the MOS and you will have some o/p @ the load.

For amplifier design, we need a input controlled energy source. That's why we can't use depletion type MOSFET for amplifiers.
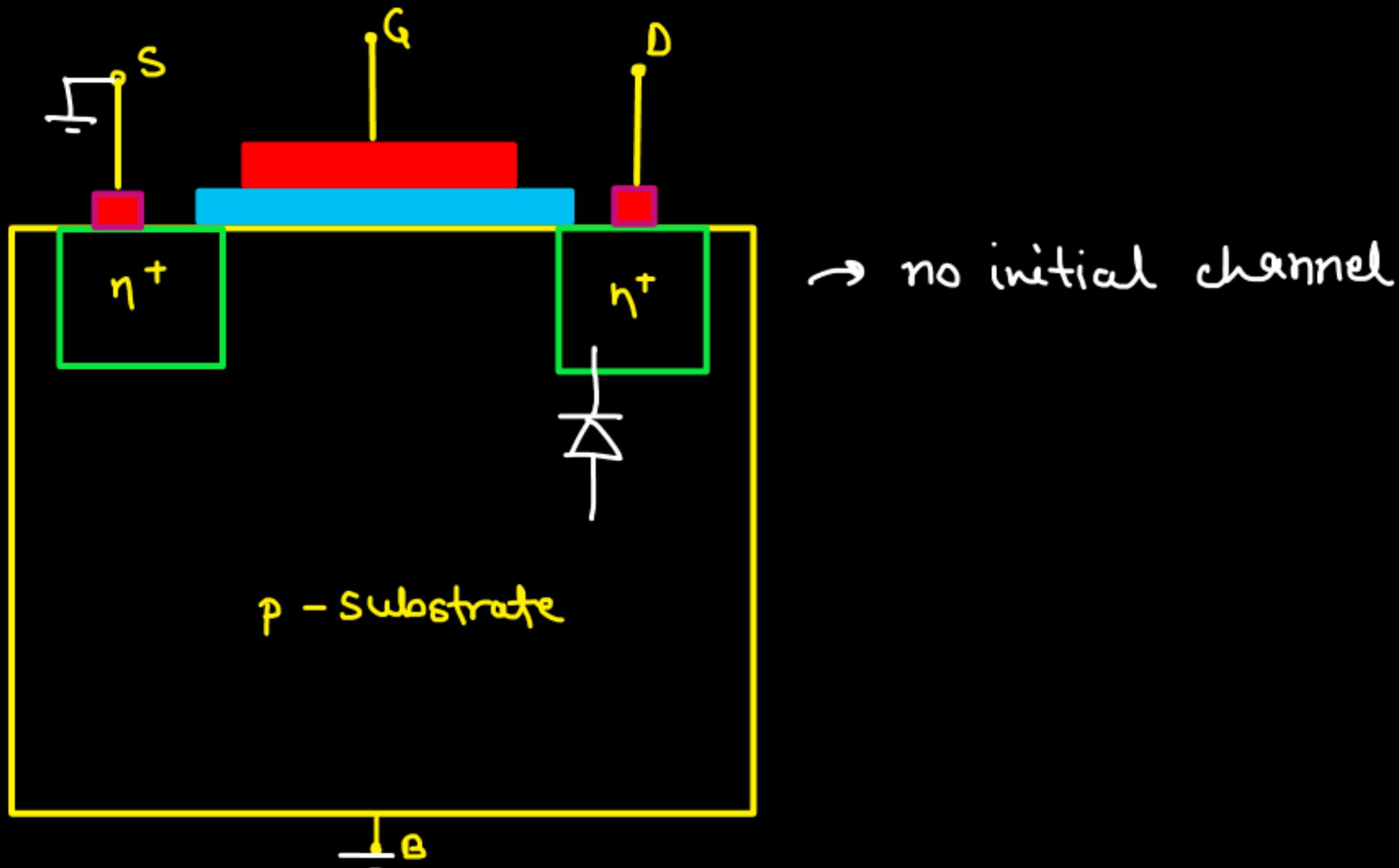
## \* $n$ -channel enhancement type MOSFET:- (NMOS)



Cod<sup>n</sup>-1

$$V_{GS} = 0 \text{ V} \Rightarrow I_D = 0 \text{ Amp}$$

$$V_{DS} = 0 \text{ V}$$

Cod<sup>n</sup>-2

$$V_{GS} = 0 \text{ V} \Rightarrow I_D = 0 \text{ Amp}$$

$$V_{DS} = -\text{ve}$$

Cod<sup>n</sup>-3


$$V_{GS} = 0 \text{ V} \Rightarrow I_D = 0 \text{ Amp}$$

$$V_{DS} = +\text{ve}$$

Cod<sup>n</sup>-4

$$V_{GS} = +ve \{ \text{very less} \}$$

$$V_{DS} = +ve$$

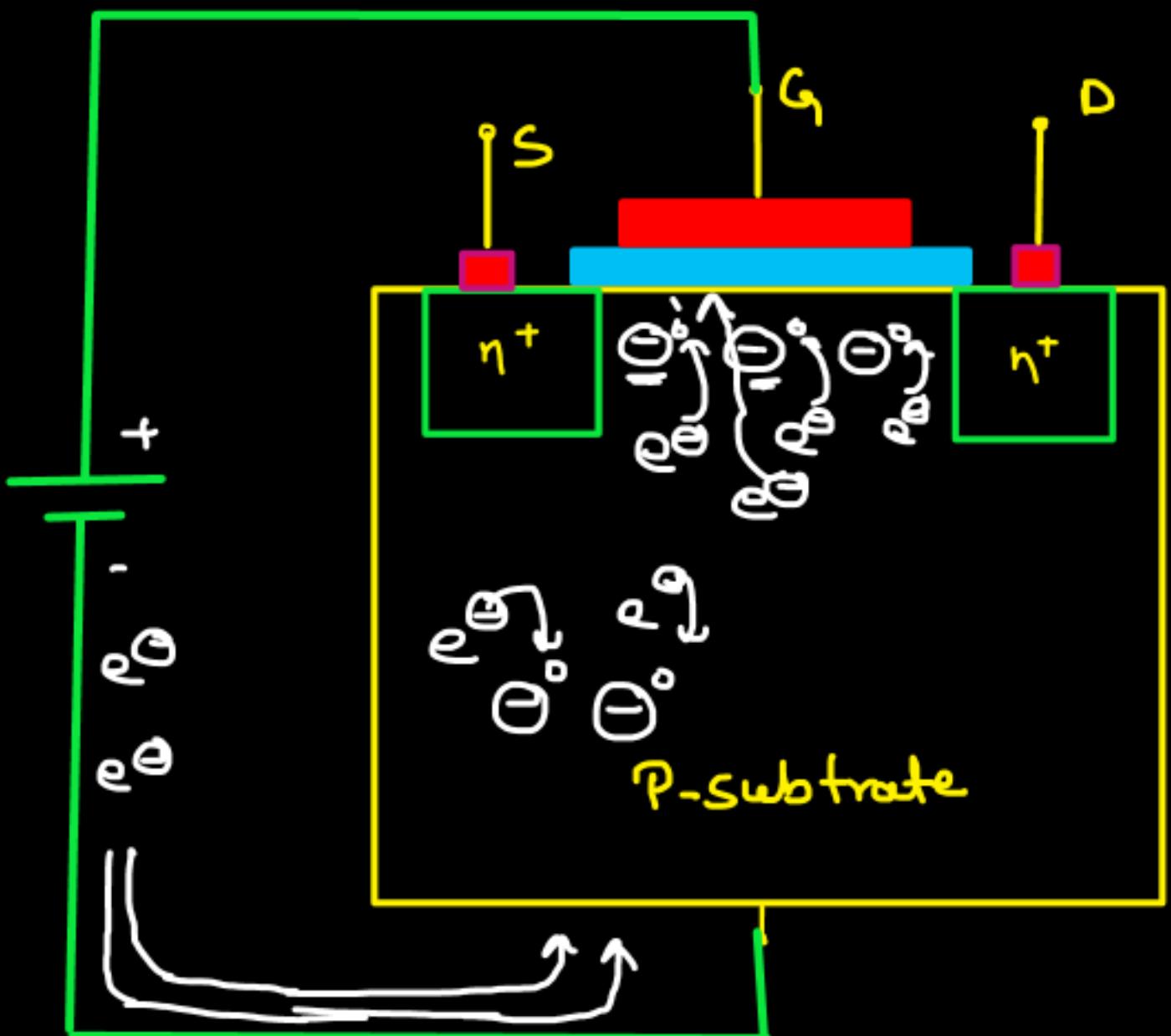

$V_G \uparrow \Rightarrow$  electron will come into substrate & recombine with hole



can't conduct current

still  $I_D = 0$  Amp



I have to increase  $V_g$  potential

@ some positive potential of  $V_g$ , the channel will be framed



Inversion layer

(P-substrate, we have framed  
n-channel)


since, the channel is present now, so the current  $I_D$  flows.  
direction of current is from drain to source.

\* The value of  $V_g$  at which the current flows, is known as threshold voltage ( $V_T$ ).

## Cod<sup>n</sup>-5


$V_{DS} = +ve$        $\Rightarrow I_D$  flows from drain to source.

$V_{GS} > V_T$

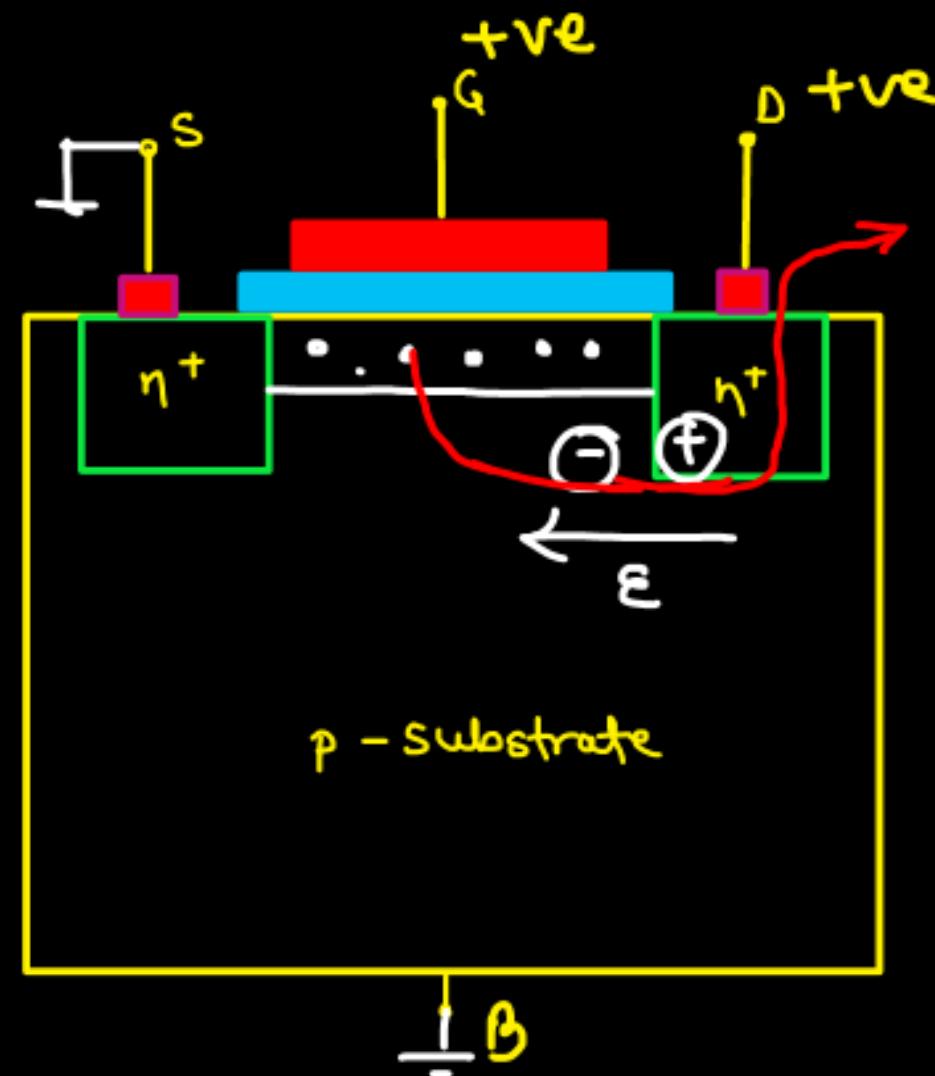

After  $V_{TH}$ , Increasing  $V_{GS} \uparrow \Rightarrow$  more  $e^-$  in channel


★ ★ ★  
 $I_D$  v/s  $V_{GS}$  Curve :-

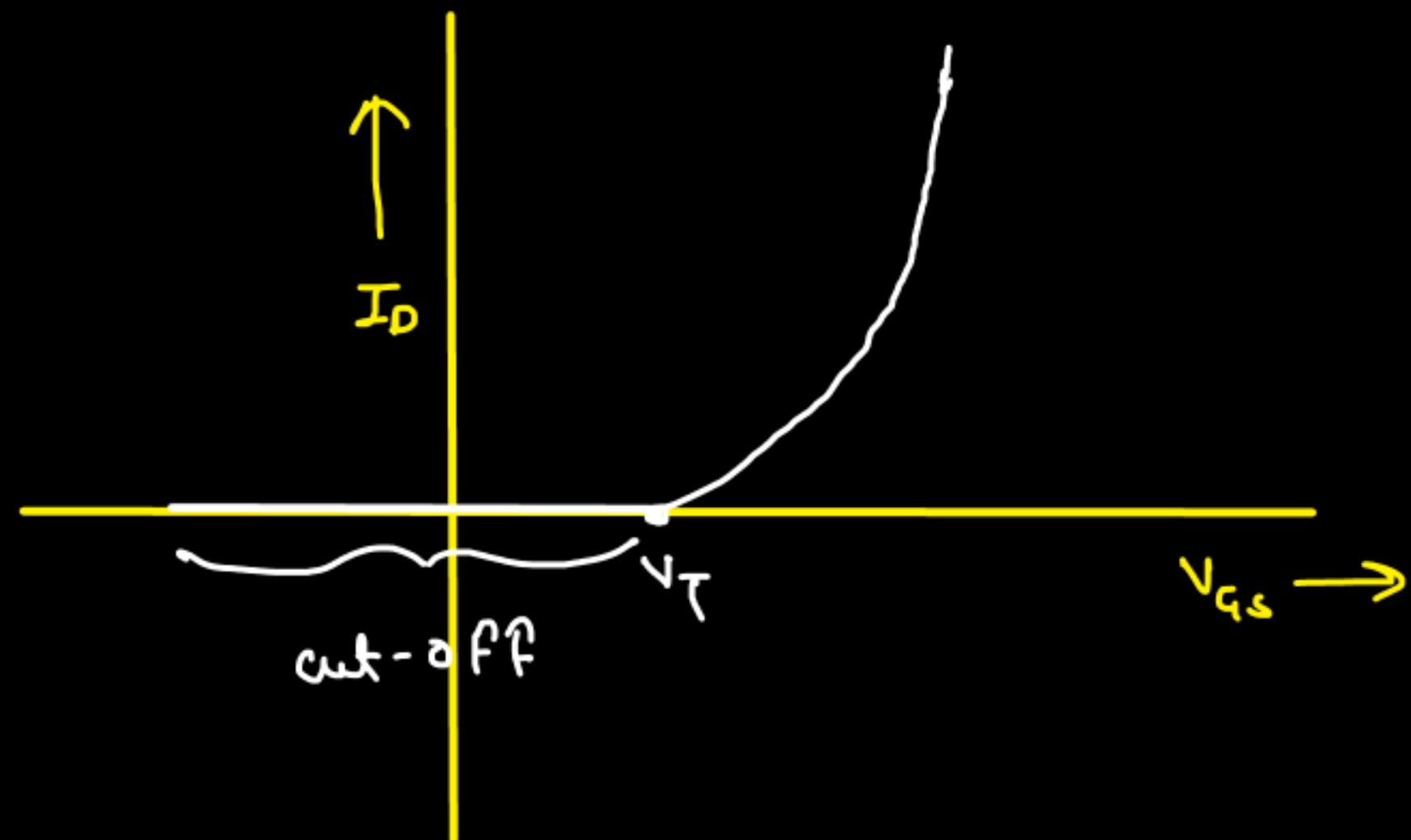

Cod<sup>n</sup>-6

$$V_{GS} > V_T \{ \text{fixed} \}$$


$$V_{DS} = +ve \{ \text{Increasing} \}$$

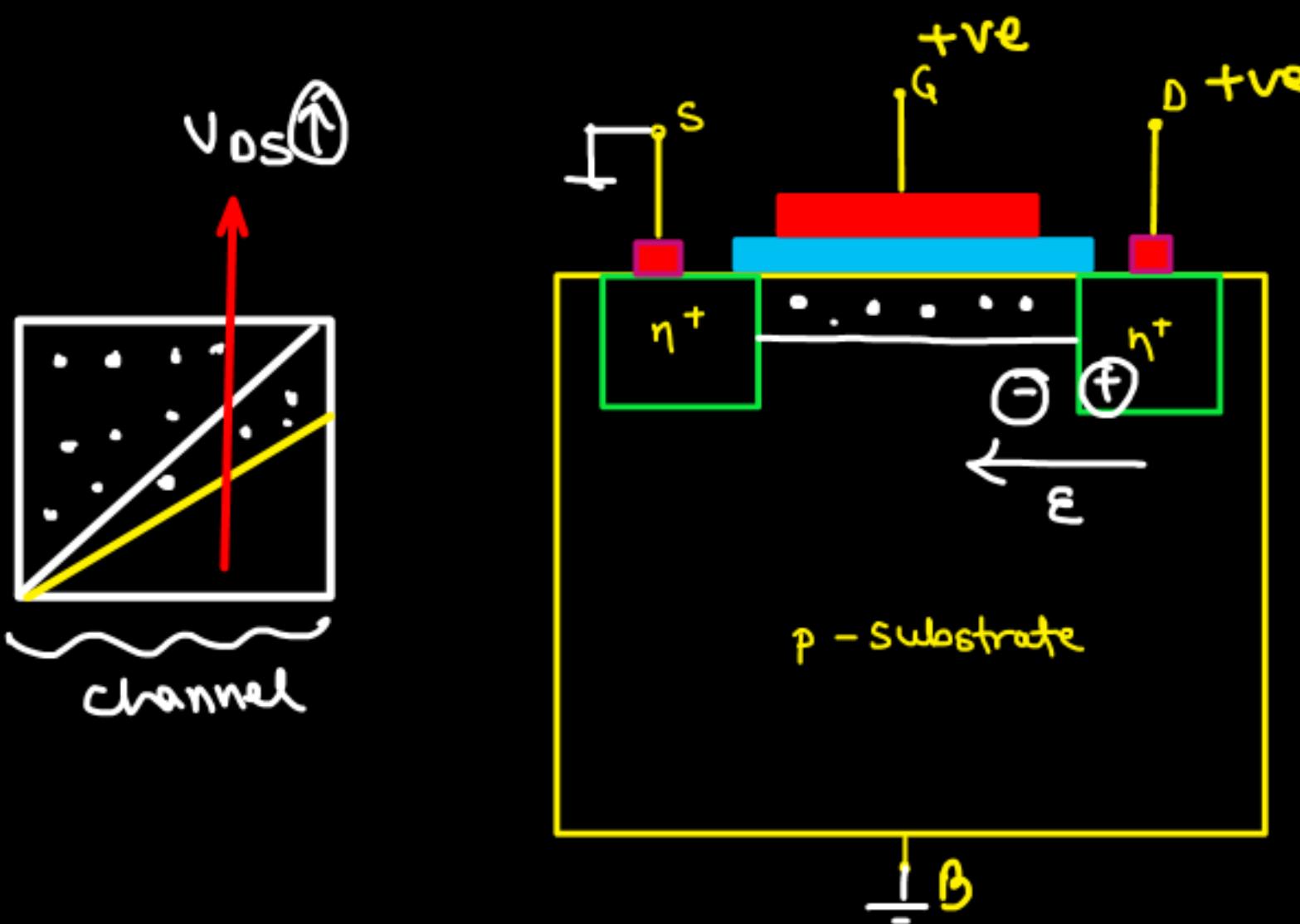

$V_{DS} \uparrow \Rightarrow \epsilon \uparrow \Rightarrow e^- \text{ gets more force} \downarrow \text{more current}$

@ some value of  $V_{DS}$ , the current will saturate.

$I_D$  v/s  $V_{DS}$  curve :-

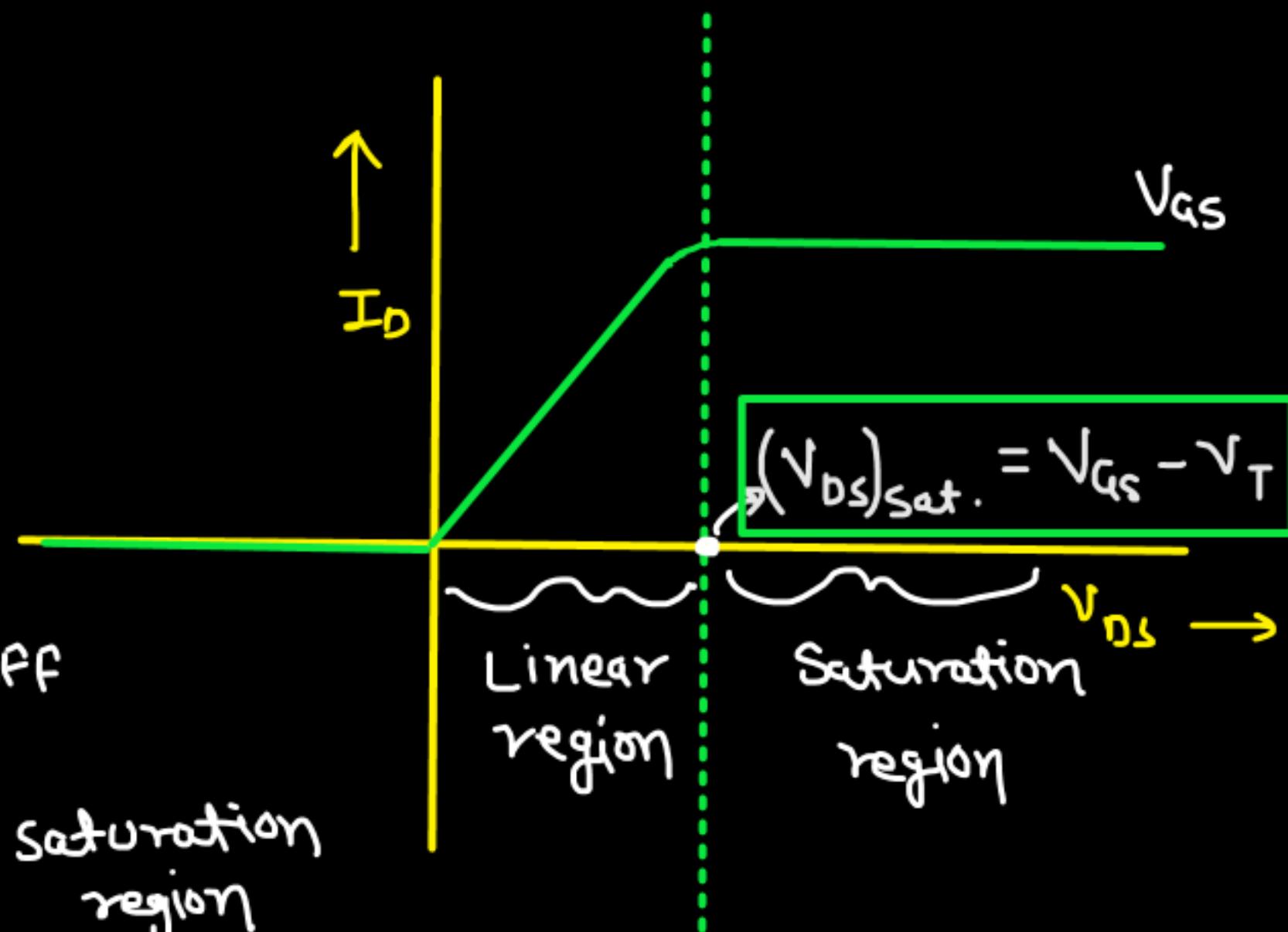


$V_{DS} < 0 \Rightarrow$  cut off

$V_{DS} > V_{GS} - V_T \Rightarrow$  saturation region

$V_{DS} < V_{GS} - V_T \Rightarrow$  linear

$I_D$  v/s  $V_{GS}$

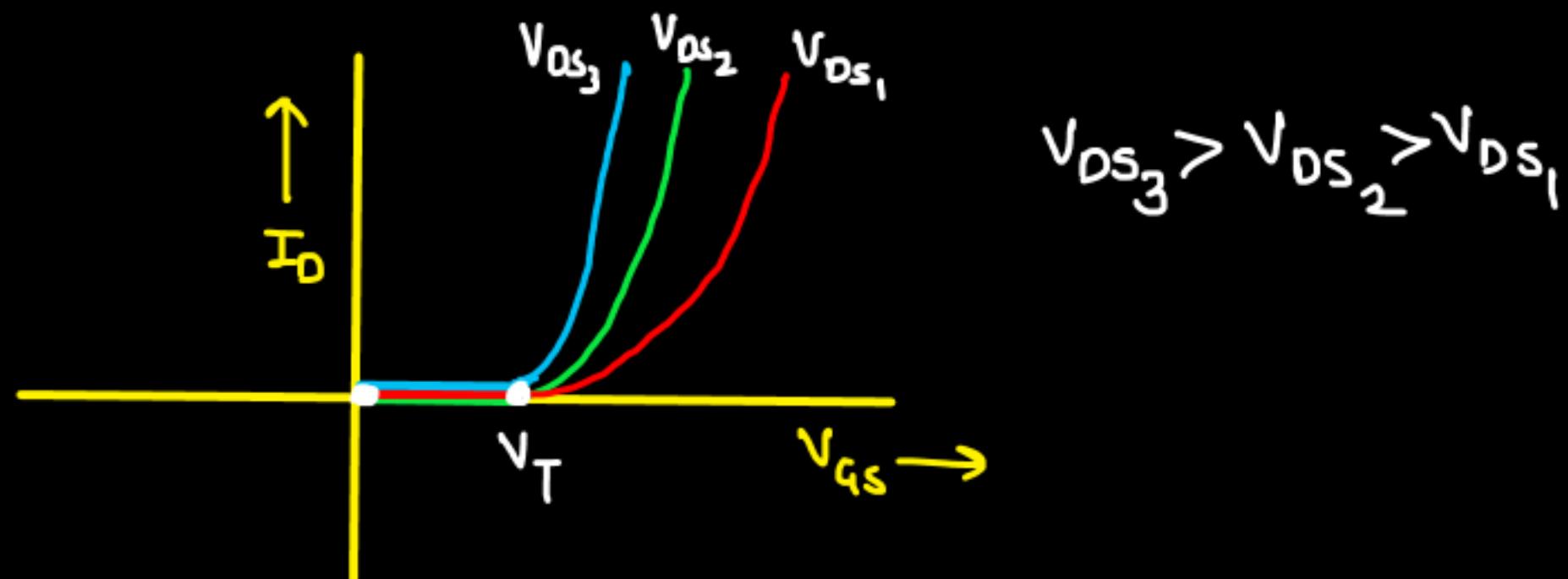

$$V_{DS_3} > V_{DS_2} > V_{DS_1}$$


$I_D$  v/s  $V_{DS}$

Sat. voltage

$$V_{DS_1} = V_{GS_1} - V_T$$



$$V_{DS_2} = V_{GS_2} - V_T$$

$$V_{DS_3} = V_{GS_3} - V_T$$

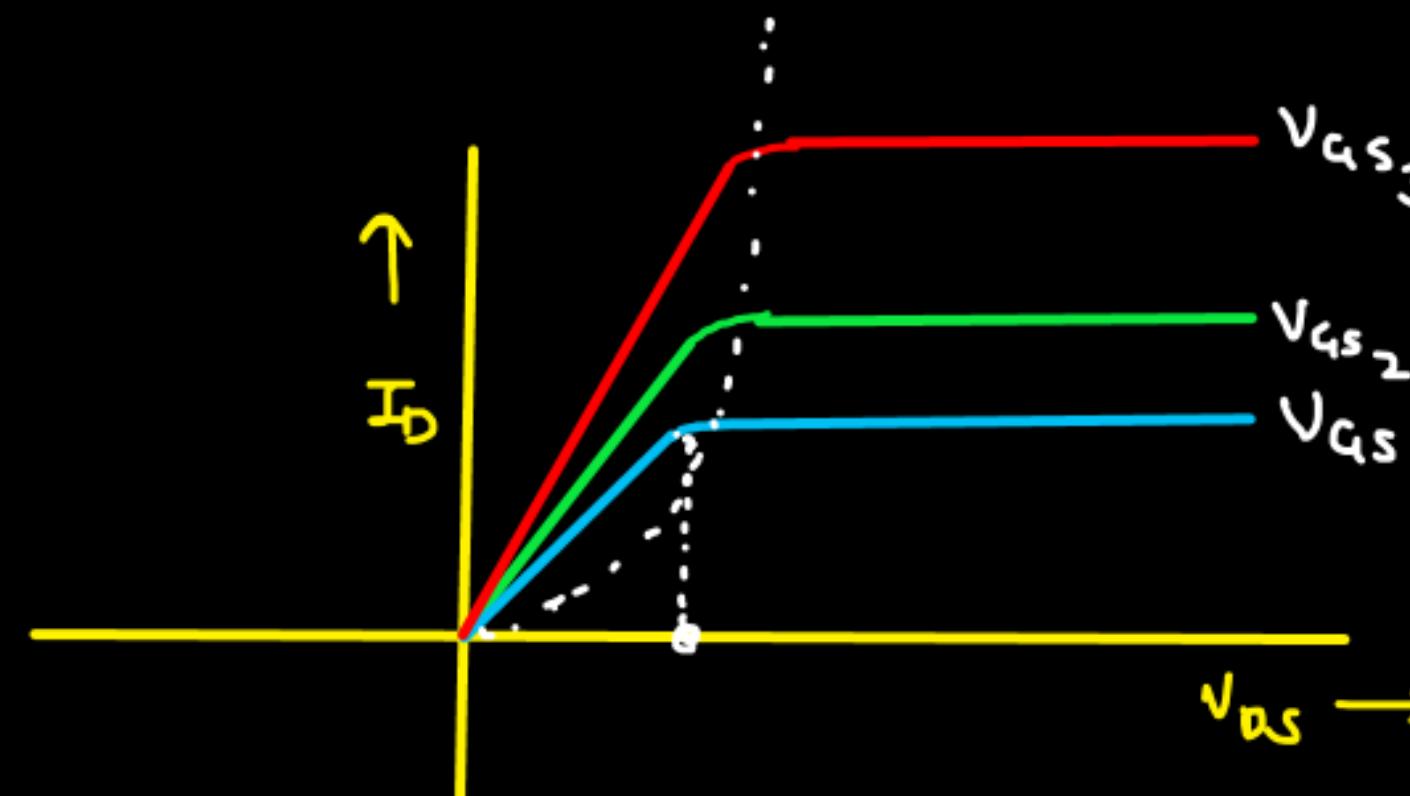

$$V_{GS_3} > V_{GS_2} > V_{GS_1}$$

## MOSFET Current Equation (N MOS) :-

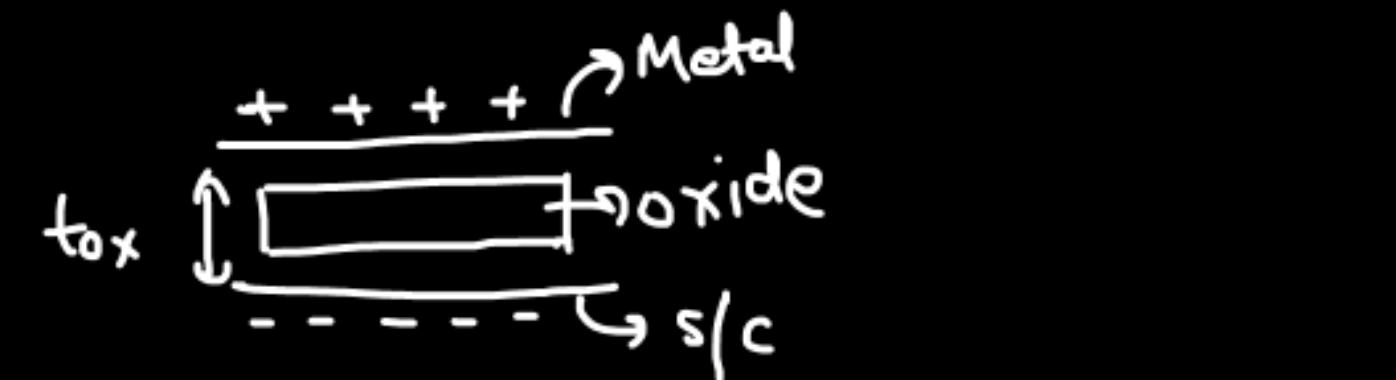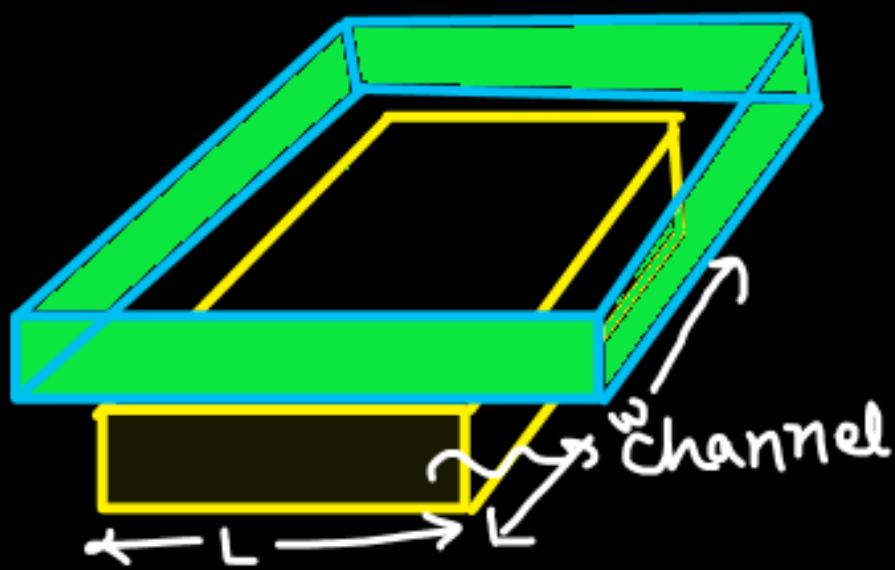

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \rightarrow \text{permittivity of oxide layer}$$

Current in Linear region :-  $[V_{DS} < V_{GS} - V_T]$

\*\*\*



$$I_D = \frac{m_n C_{ox} W}{L} \left[ (V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$m_n$  → mobility of e<sup>-</sup>

$L$  → channel length

$W$  → channel width

$V_{Tn}$  → Threshold voltage

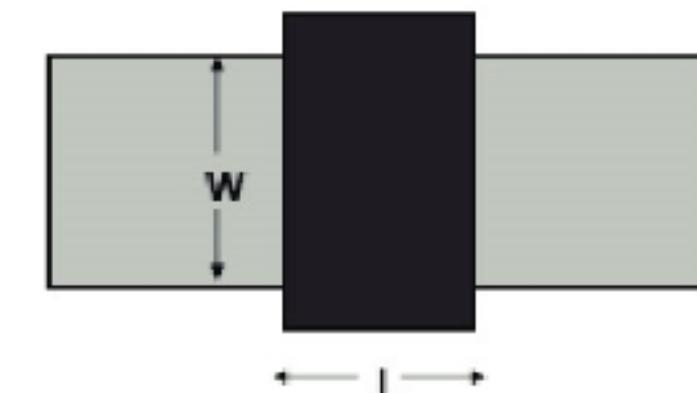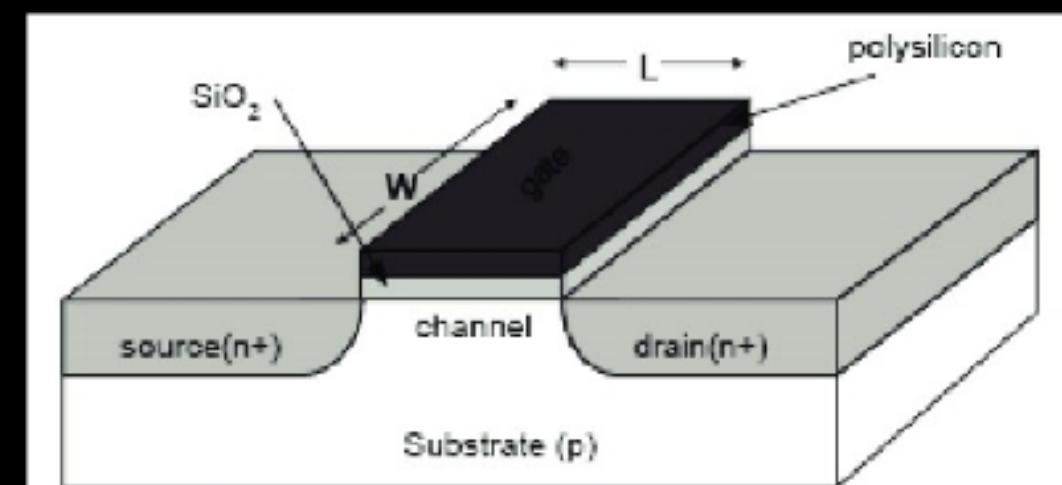


Current in saturation region:- [  $V_{DS} \geq V_{GS} - V_T$  ]

$$(I_D)_{Sat.} = \frac{\mu_n C_{OX} W}{2L} (V_{GS} - V_{Tn})^2$$

N.B:- In case NMOS ; Higher potential node  $\Rightarrow$  drain  
lower potential node  $\Rightarrow$  source  
current flow  $\Rightarrow$  drain to source

\* P-channel enhancement type MOSFET :-

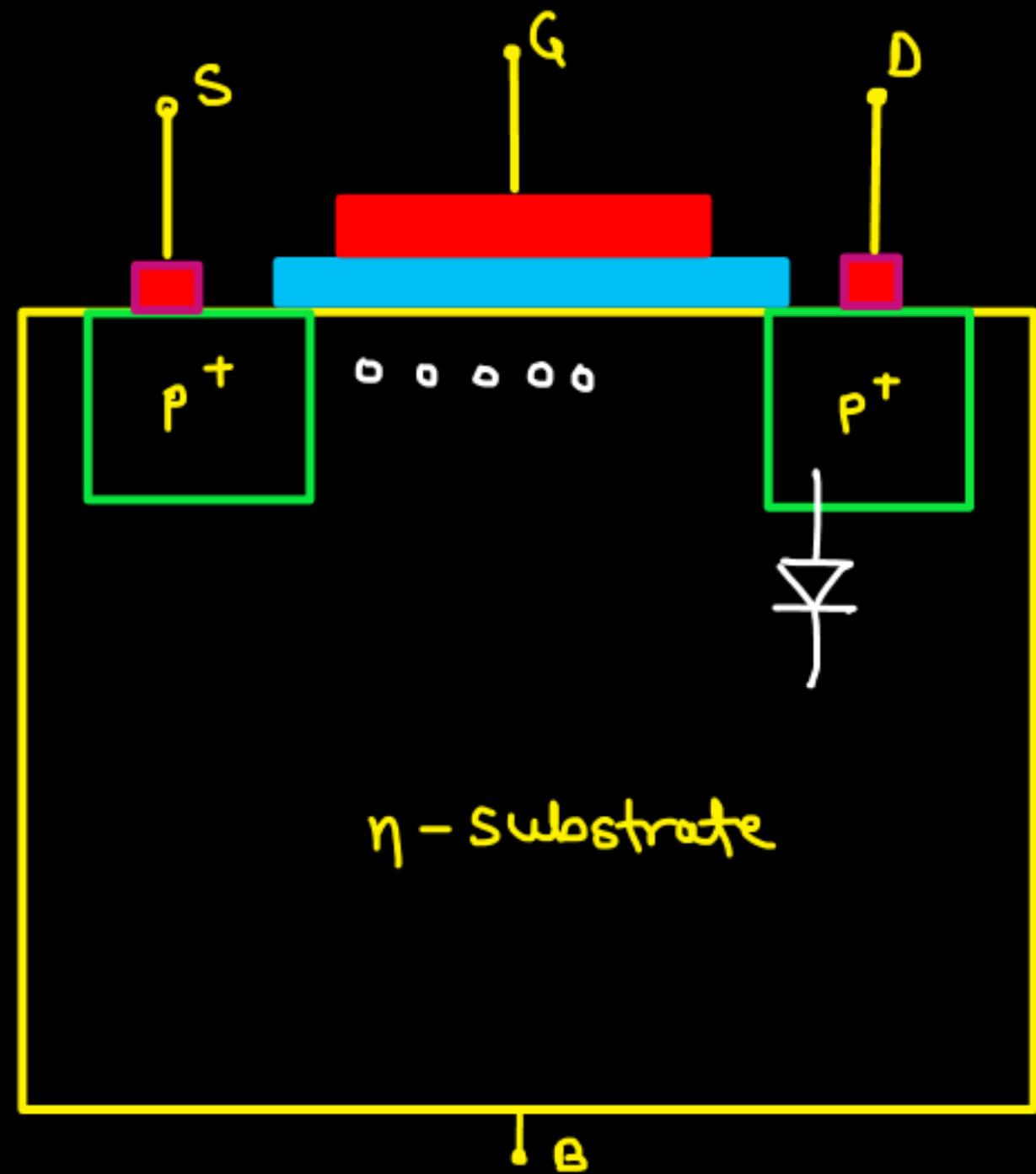

Cond<sup>n</sup> 1:-

$$V_{GS} = 0 = V_{DS} \Rightarrow I_D = 0$$

Cond<sup>n</sup> 2:-

$$V_{GS} = 0, V_{DS} = +ve \Rightarrow I_D = 0$$

Cond<sup>n</sup> 3:-

$$V_{GS} = 0, V_{DS} = -ve \Rightarrow I_D = 0$$

Cond<sup>n</sup> 4 ..


$$V_{GS} = -ve \text{ (very less)}$$

⇒ channel is not framed

$$V_{DS} = -ve$$



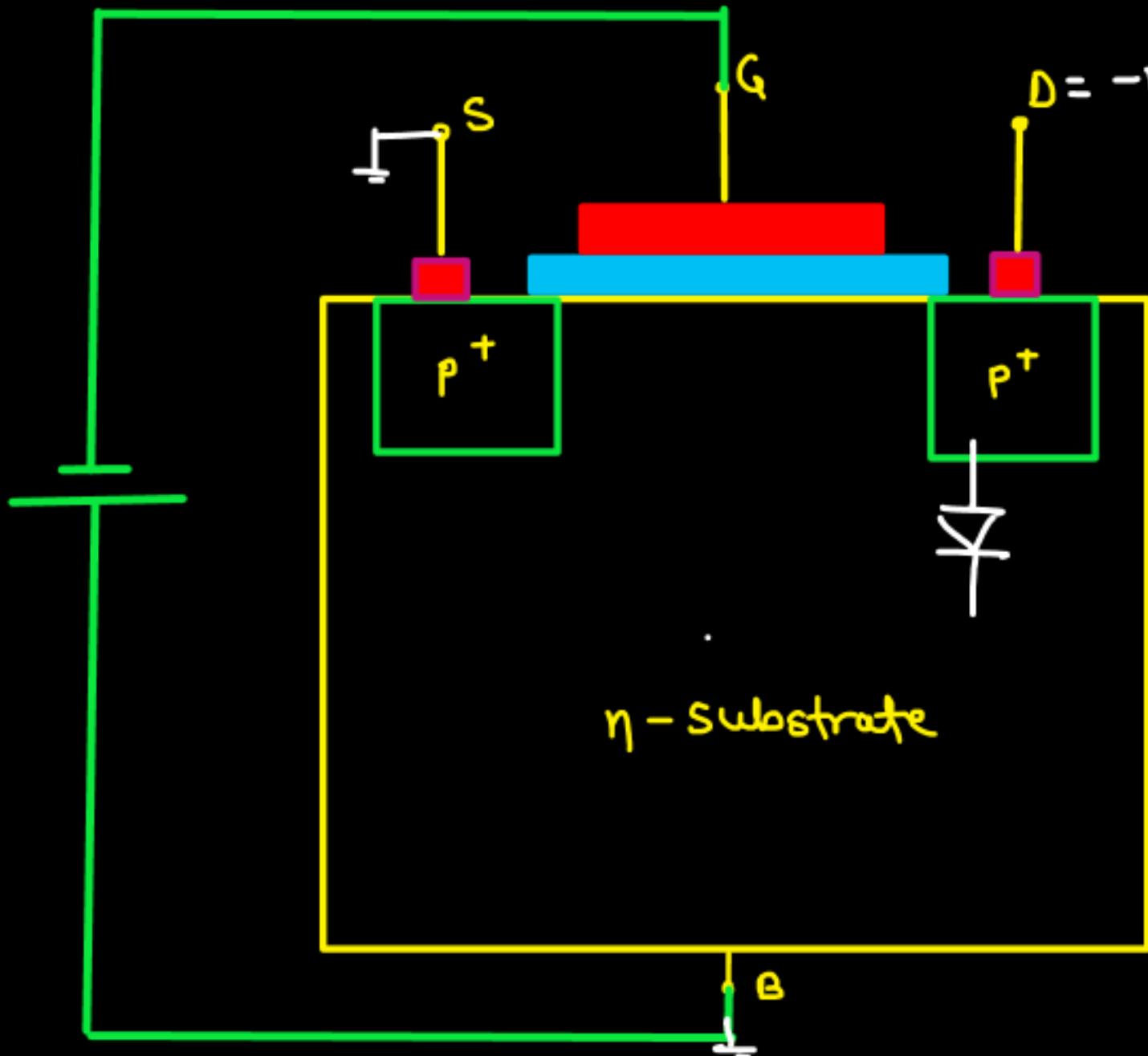You have to apply more negative potential.




$V_{GS} < V_{TP}$

↓

current flows

when  $V_{GS} < V_{TP}$

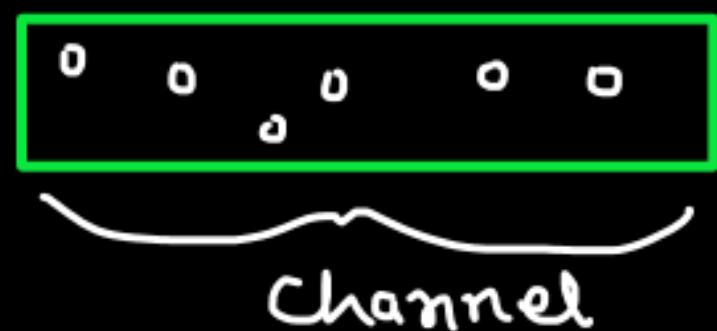

NMOS  $\rightarrow$  PMOS :-

$$V_{GS} \rightarrow V_{SG}$$

$$V_{DS} \rightarrow V_{SD}$$

$$V_{Tn} \rightarrow |V_{Tp}|$$


NMOS	PMOS
1) Cut-off $\Rightarrow V_{GS} < V_{Tn}$	$V_{SG} <  V_{Tp} $
2) ON $\Rightarrow V_{GS} > V_{Tn}$	$V_{SG} >  V_{Tp} $
3) Linear region $\Rightarrow$ $V_{DS} < V_{GS} - V_{Tn}$	$V_{SD} < V_{SG} -  V_{Tp} $
4) Saturation $\Rightarrow$ $V_{DS} > V_{GS} - V_{Tn}$	$V_{SD} \geq V_{SG} -  V_{Tp} $

Cond<sup>n</sup> 5:-


$$\begin{array}{l} \text{(i) } V_{GS} < V_{TP} \quad \underline{\text{OR}} \quad V_{SG} > |V_{TP}| \\ \text{(ii) } V_{DS} = -\text{ve} \quad \underline{\text{OR}} \quad V_{SD} = +\text{ve} \end{array} \Rightarrow I_D \text{ flows}$$



Source to drain

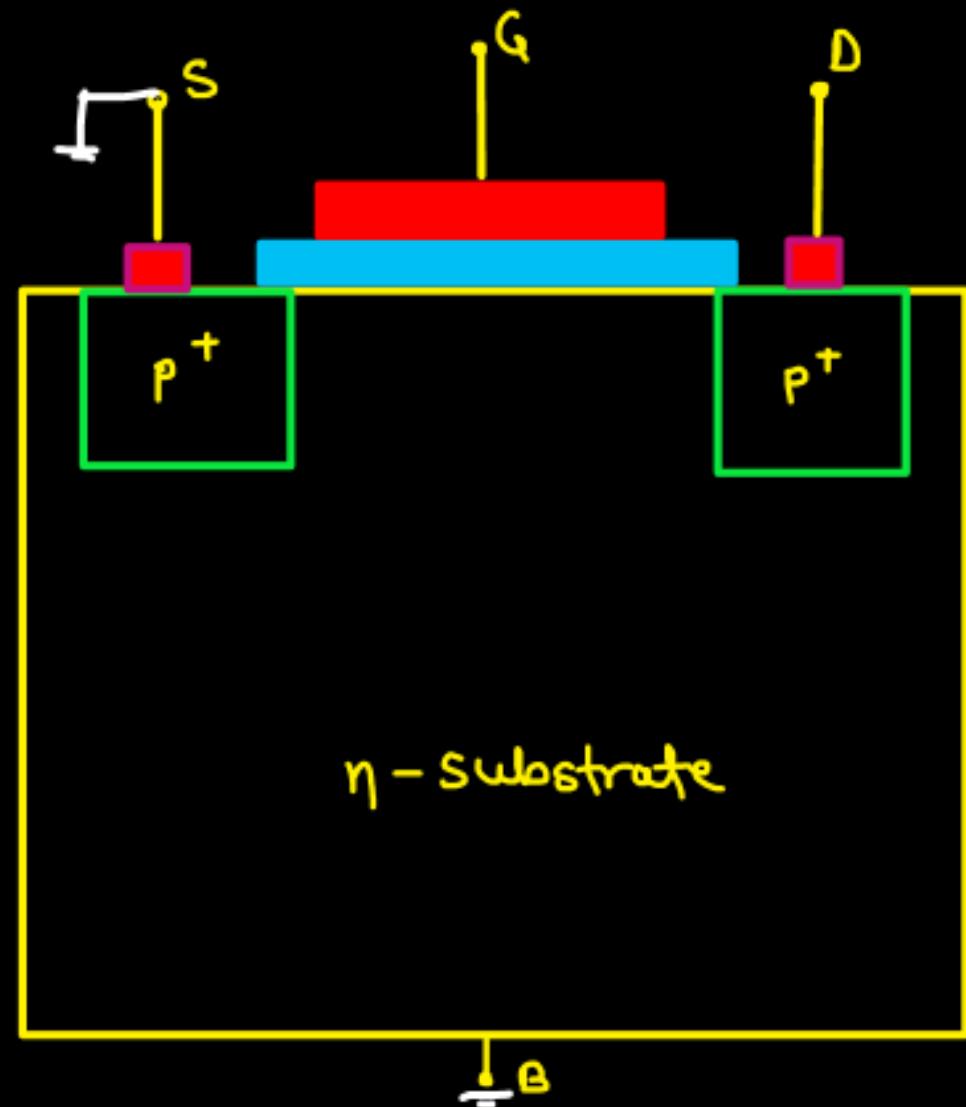


$I_D$  v/s  $V_{GS}$  curve:-

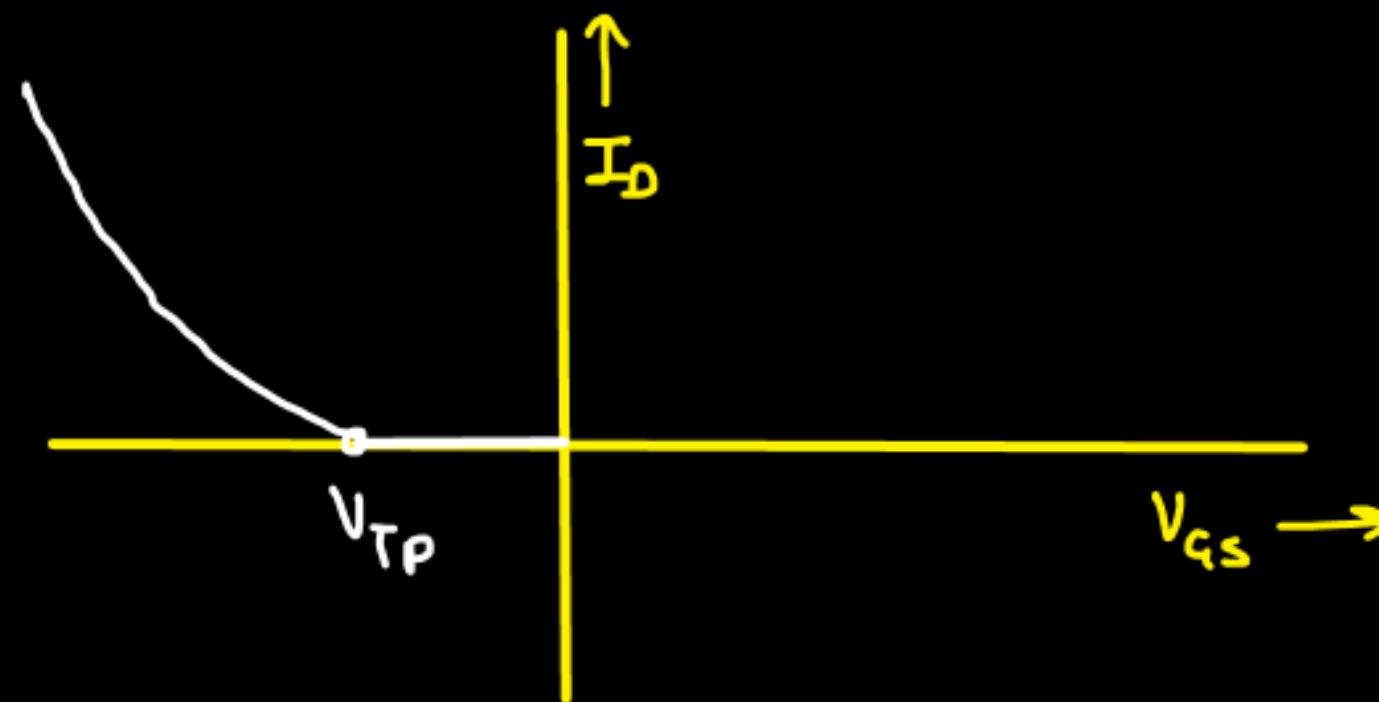

current dir<sup>n</sup>:-

$I_D$  v/s  $V_{SG}$  curve:-

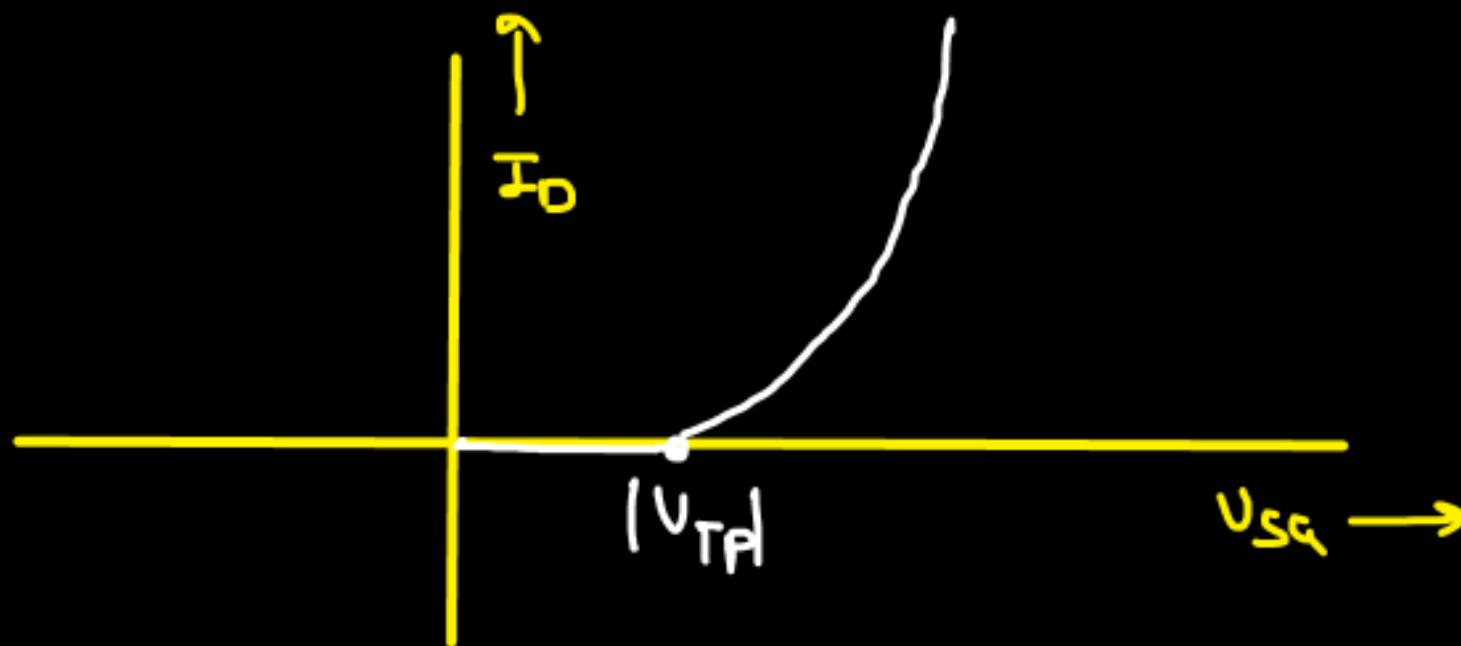

source to  
drain

$$V_{SG} > |V_{TP}|$$

Cool'n 6:-


$V_{QS} < V_T$  {fixed}

$V_{DS} = -ve$  {negative supply increasing}




current initially increases linearly  
and then saturates.

## $I_D$ v/s $V_{DS}$ Curve

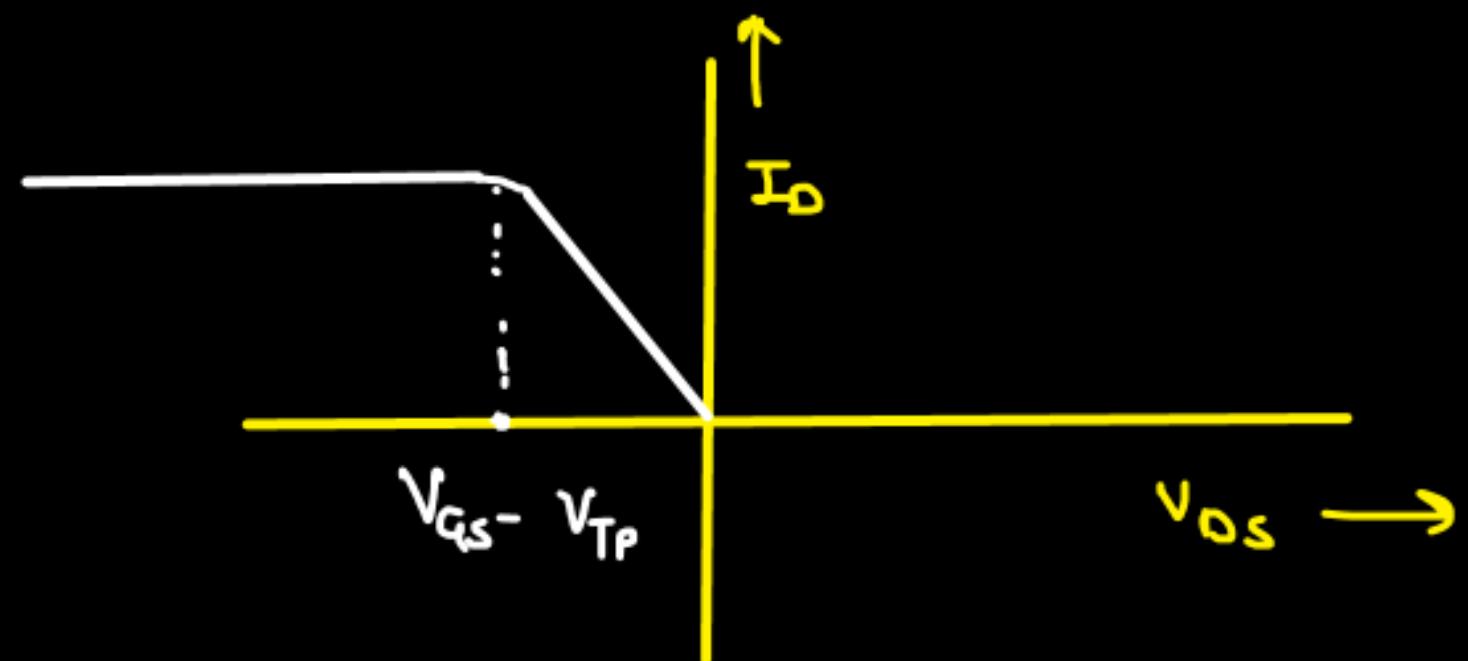


## $I_D$ v/s $V_{SD}$ Curve:-

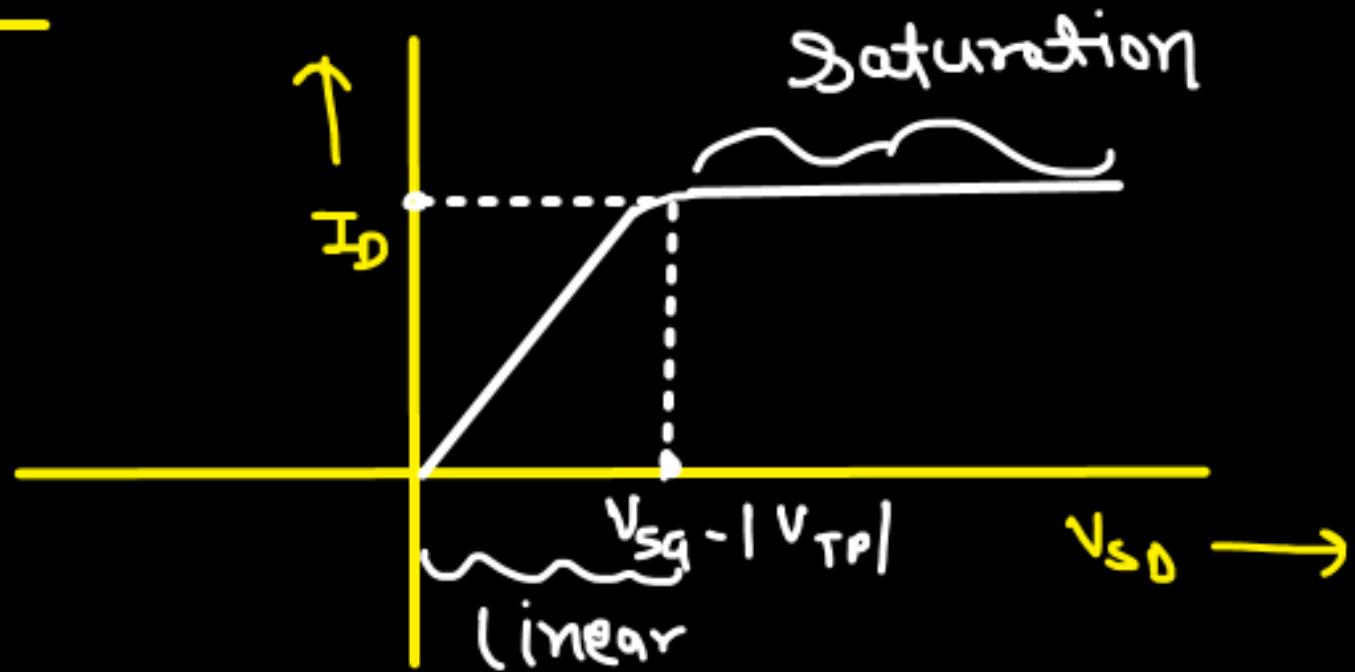


$$(V_{SD})_{sat} = V_{SG} - |V_{TP}|$$

$I_D$  v/s  $V_{SQ}$  Curve:-

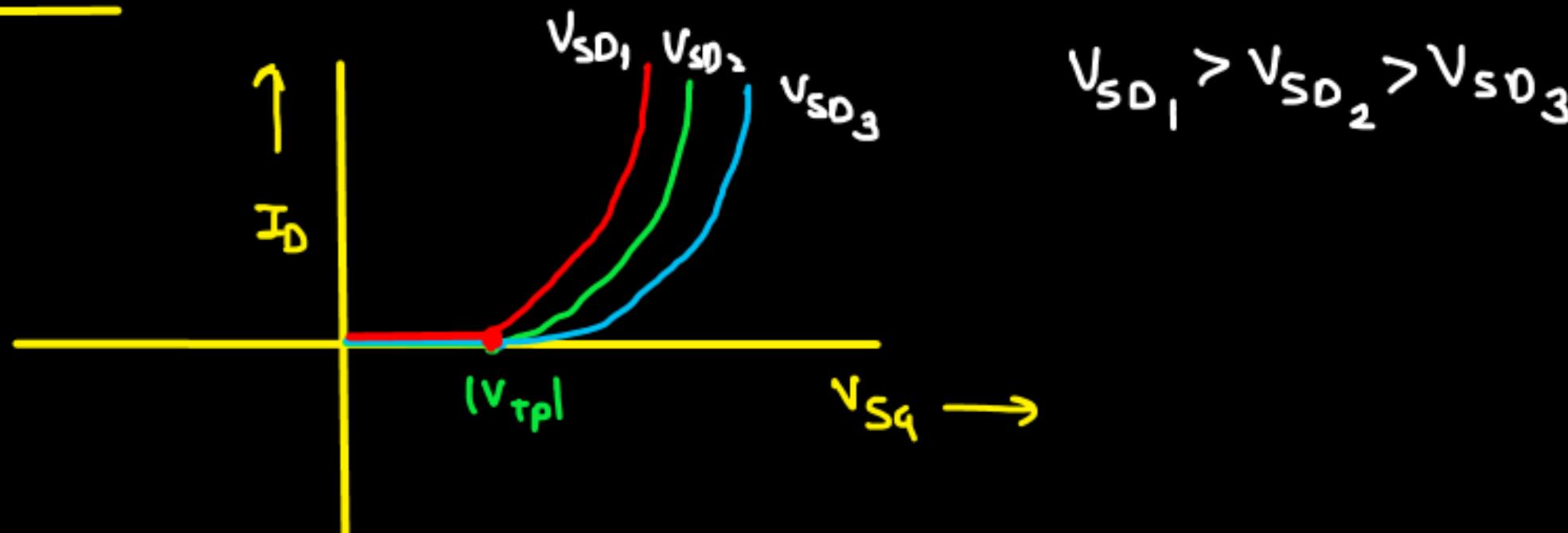

$I_D$  v/s  $V_{SD}$  Curve:-

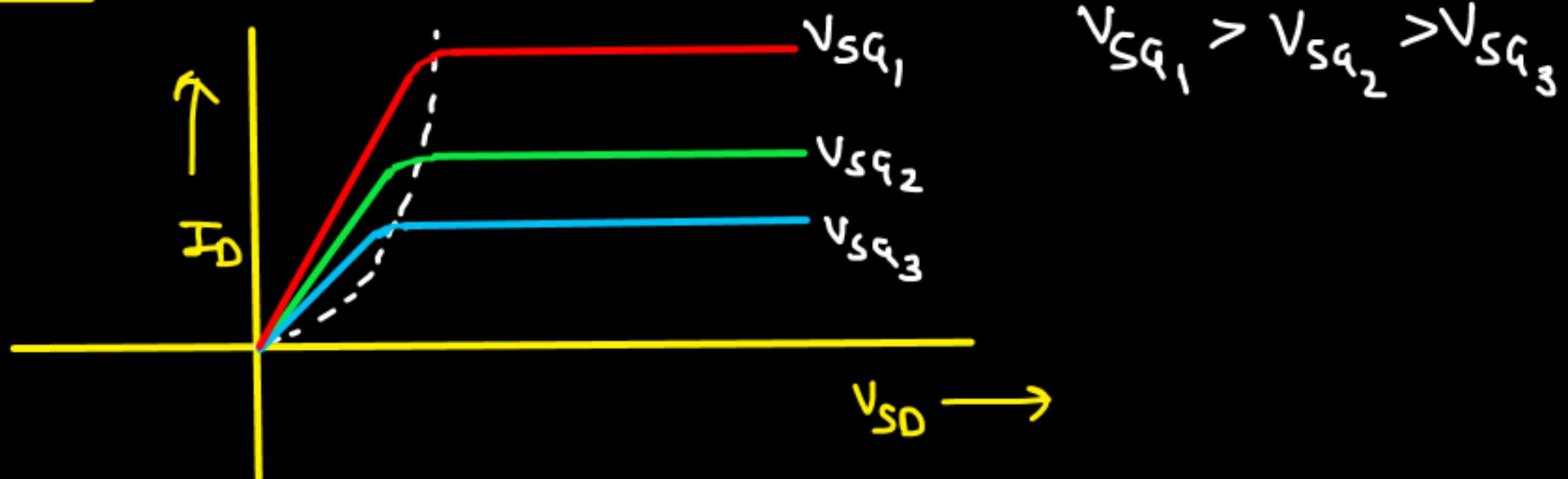

## Current equation:- (PMOS)

NMOS  $\rightarrow$  PMOS

$$V_{GS} \rightarrow V_{SG}$$

$$V_{DS} \rightarrow V_{SD}$$

$$V_{T\eta} \rightarrow |V_{TP}|$$

① Linear region :-  $[V_{SD} < V_{SG} - |V_{TP}|]$

$$I_D = \frac{\mu_p C_{ox} W}{L} \left[ (V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

② Saturation region :-  $[V_{SD} \geq V_{SG} - |V_{TP}|]$

$$I_D = \frac{\mu_p C_{ox} W}{2L} (V_{SG} - |V_{TP}|)^2$$

N.B.

= IN PMOS,

Higher potential = Source

lower potential = Drain

dir<sup>n</sup> of current = Source to Drain

IN NMOS,







Higher potential = Drain

lower potential = Source





dir<sup>n</sup> of current = Drain to Source

## \* MOSFET Circuit Symbol:-

H.P. → Higher potential  
L.P. → Lower potential

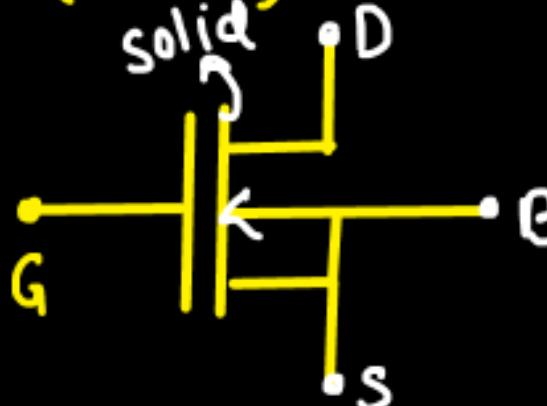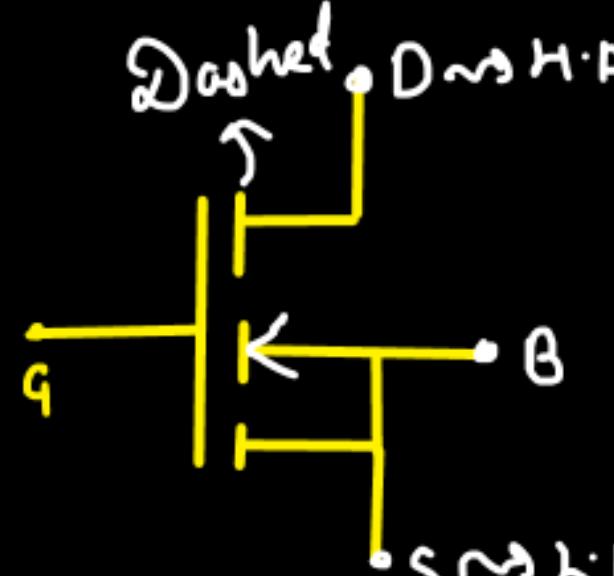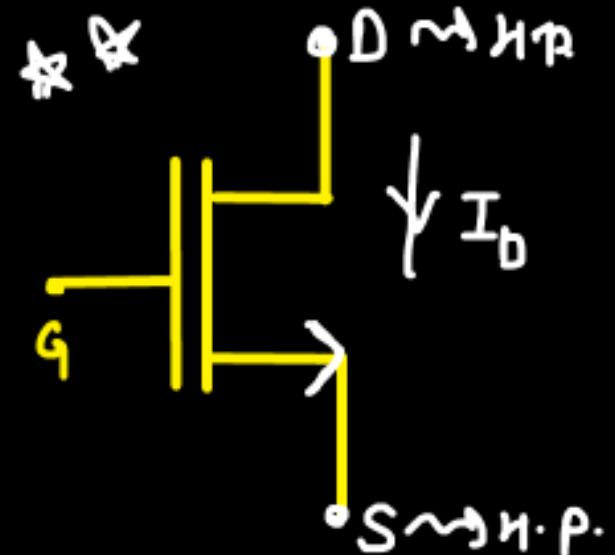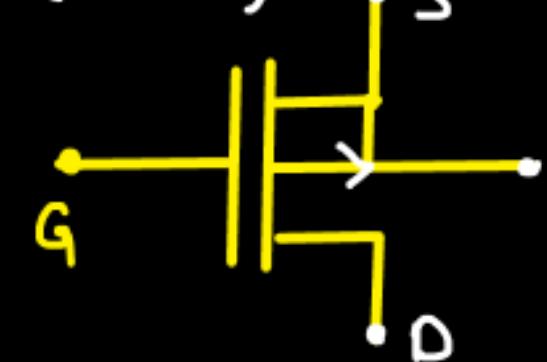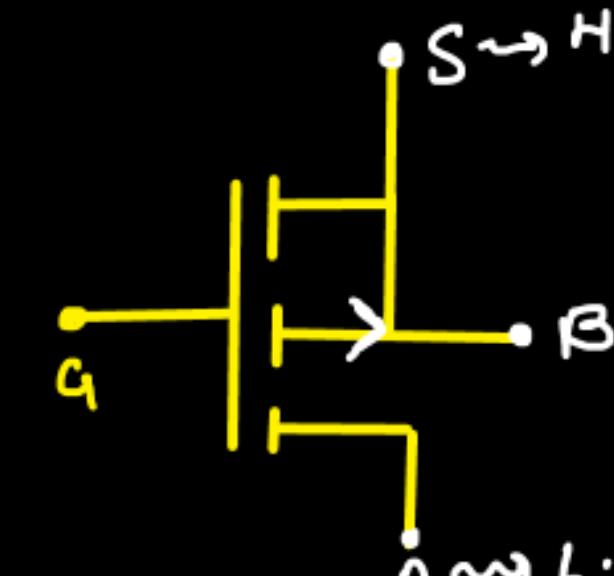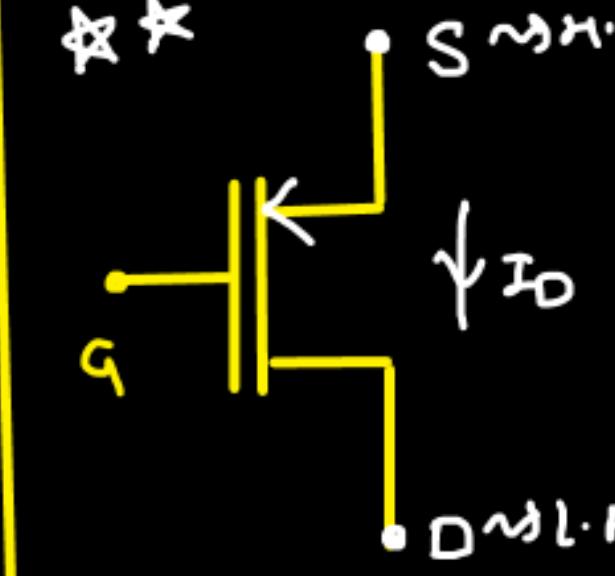Depletion type	Enhancement type	common for both
n-channel → (NMOS) 	 D ~ H.P. S ~ L.P.	 D ~ H.P. S ~ H.P. $I_D$
p-channel → (PMOS) 	 S ~ H.P. D ~ H.P.	 S ~ H.P. $I_D$ D ~ L.P.

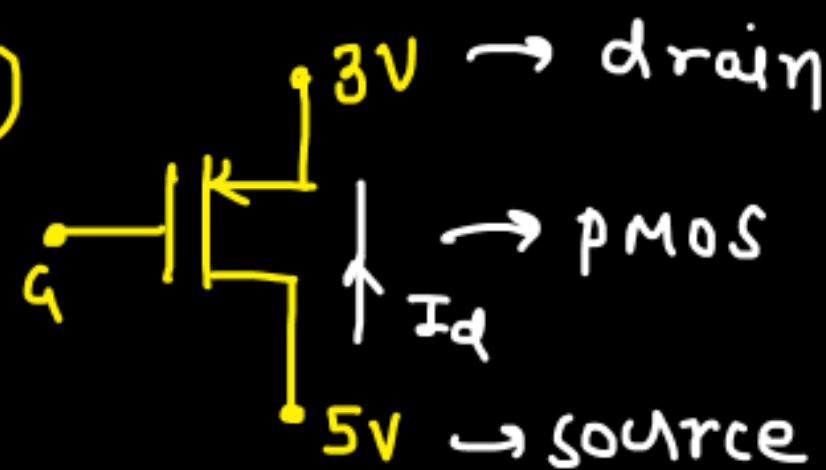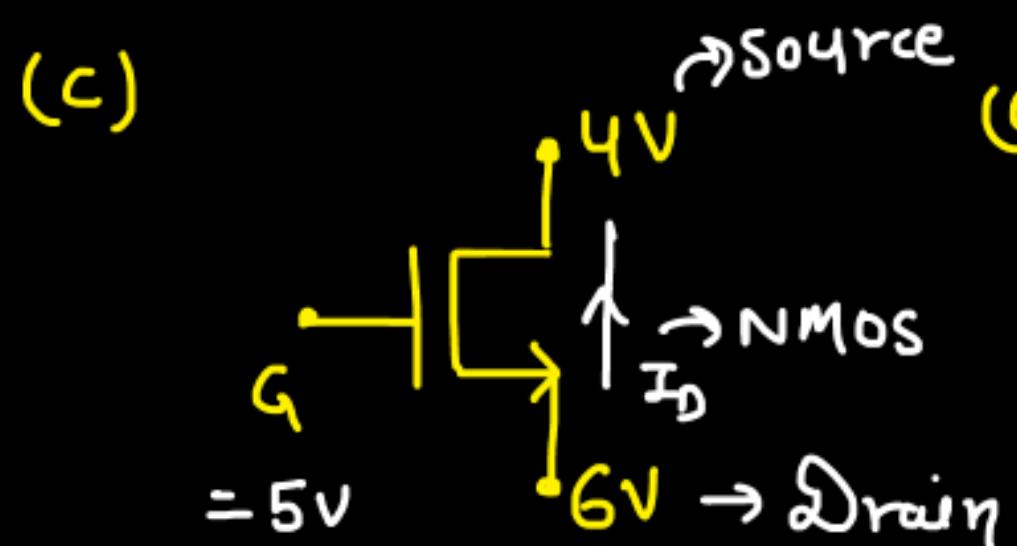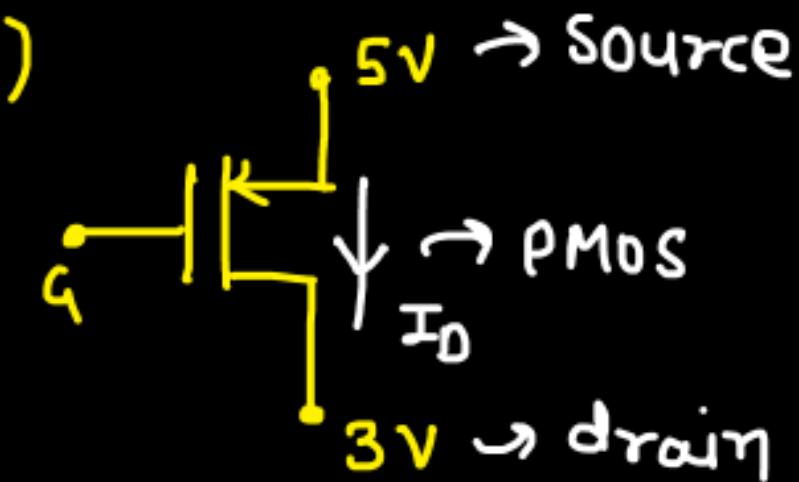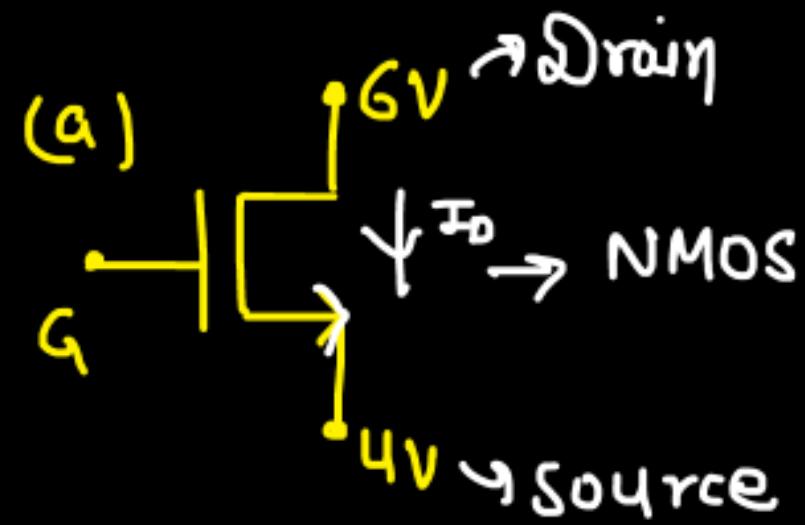Q. Mark Source and drain and the current dir<sup>n</sup>.



Q. Given  $\mu_p = 0.4 \mu_n$  -

What must be the relative width of n-channel and p-channel devices if they are to have equal drain currents when operated in the saturation mode with overdrive voltage of the same magnitude.



Overdrive voltage

$$V_{ov} = V_{GS} - V_{Tn}$$

↓  
NMOS

$$V_{ov} = V_{SG} - |V_{Tp}|$$

↓  
PMOS

$$(I_D)_p = (I_D)_n$$

$$\frac{\mu_p C_f \left(\frac{W}{L}\right)_p (V_{SG} - |V_{Tp}|)^2}{2} = \mu_n C_f \left(\frac{W}{L}\right)_n (V_{GS} - V_{Tn})^2$$

$$\mu_p \left( \frac{w}{L} \right)_p = \mu_\eta \left( \frac{w}{L} \right)_\eta$$

$$0.4 \left( \frac{w}{L} \right)_p = \left( \frac{w}{L} \right)_\eta$$

$$\left( \frac{w}{L} \right)_p = 4.5 \left( \frac{w}{L} \right)_\eta$$

Q: For n-channel MOSFET, if conduction parameter ( $k_n$ ) is  $0.249 \text{ mA/V}^2$ , Gate to Source voltage is  $2V_T$ .

where  $V_T = 0.75$ ,  $V_{DS} = 0.4V$ . Find drain current. Given:-

→

$$\left\{ k_n = \frac{\mu_n C_{ox} W}{2L} \right\}$$

$$\frac{\mu_n C_{ox} W}{2L} = 0.249 \text{ mA/V}^2$$

$$V_{GS} = 2V_T = 1.5V$$

$$V_T = 0.75V$$

$$V_{DS} = 0.4V$$

Drain current = ?  $\xrightarrow{\text{Sat. ?}}$   $\xrightarrow{\text{Linear. ?}}$

$$V_{ov} = V_{GS} - V_T = 0.75V$$

$$V_{DS} = 0.4V$$

$$V_{DS} < V_{ov} \text{ OR } V_{DS} < V_{GS} - V_T$$

$\underbrace{\hspace{2cm}}_{V_{DS}}$

Linear region =

MOS is working in linear region

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


$$= 2 \times 0.249 \left[ \frac{mA}{V^2} \left( 0.75 \times 0.4 - \frac{(0.4)^2}{2} \right) \times V^2 \right]$$

$$I_D = 0.109mA$$


Q. How many charge carriers are there in a MOS?

- One one. PMOS → Holes  
NMOS → Electrons


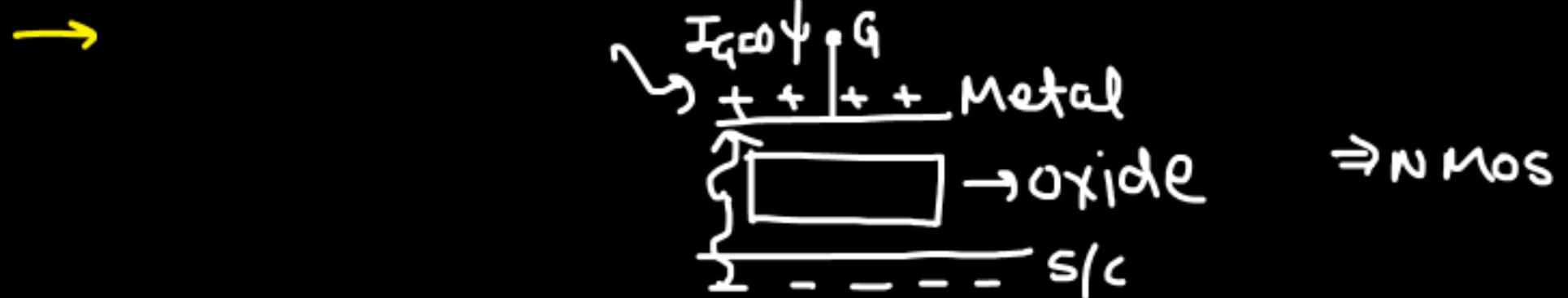
Q. What is the need of oxide Layer in MOS.



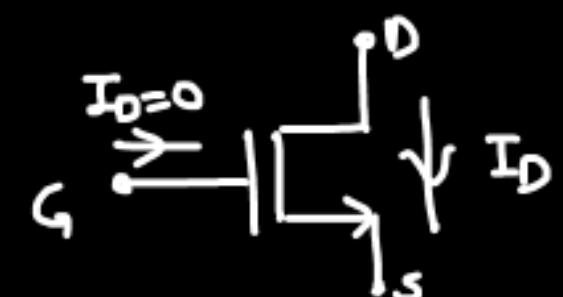Because of this oxide layer only, the  $e^-$  or the negative charge near the S/C is not reaching to the metal and we are able to form the channel and this channel helps in generating drain current.



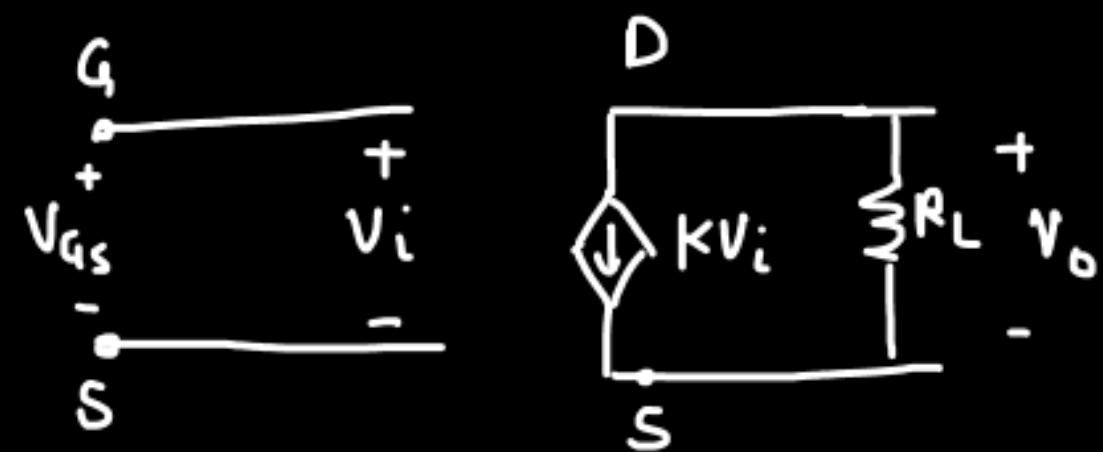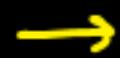Q. Why do we use MOSFET in enhancement mode for amplification?



Enhancement type MOSFETs doesn't conduct for zero i/p voltage.


For conduction,  $V_{GS} > V_T$

And the drain current depends on the applied i/p voltage.

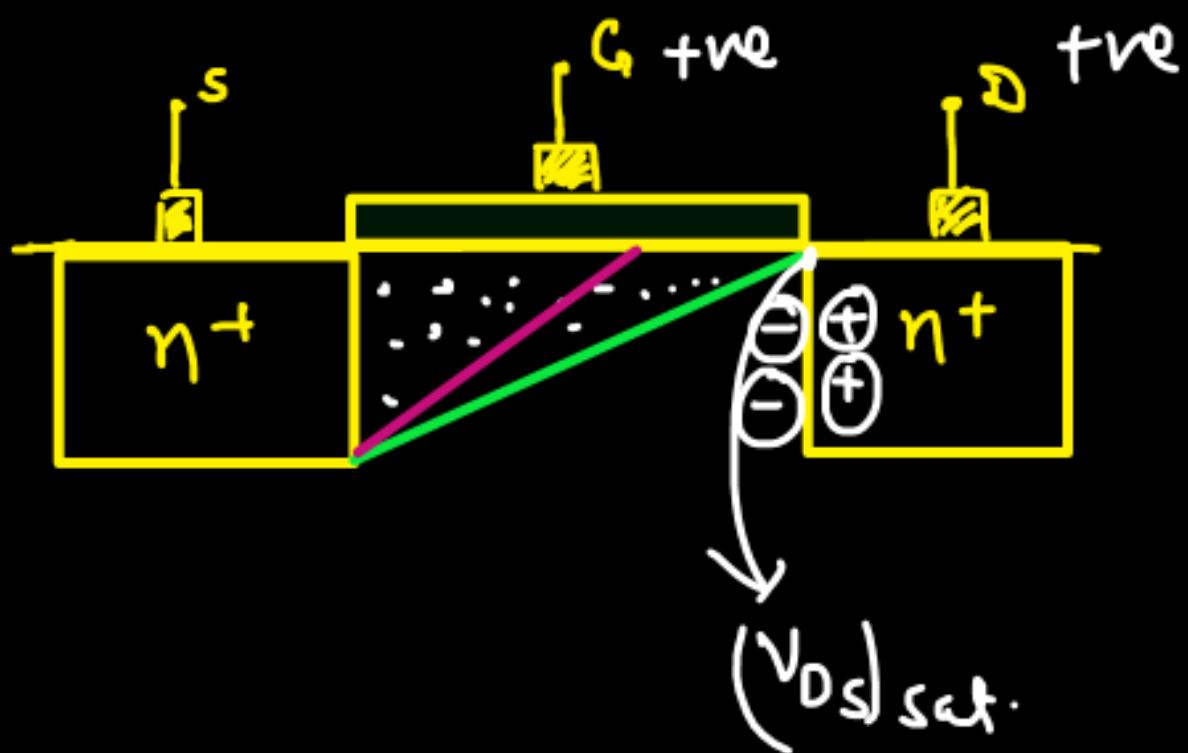
## Channel length Modulation (CLM):-

Ideally, For  $V_{DS} > (V_{DS})_{sat}$   $\Rightarrow$  Current saturates

Practically, For  $V_{DS} > (V_{DS})_{sat}$   $\Rightarrow$  Current rises slightly



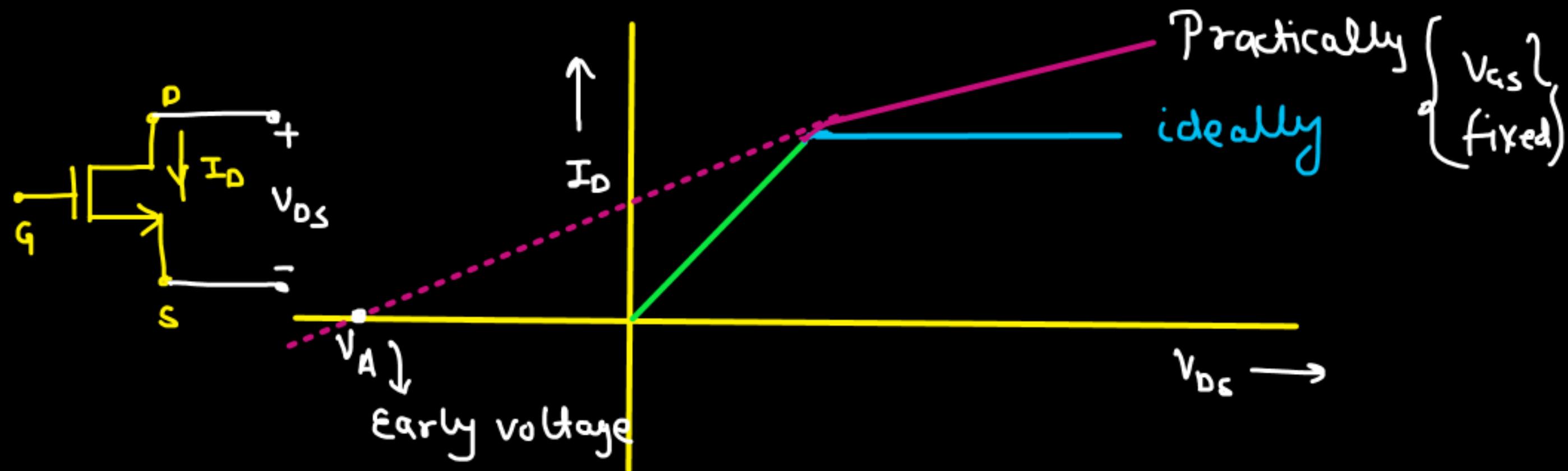$V_{DS} > (V_{DS})_{sat}$   $\Rightarrow$  depletion width  $\uparrow$   $\Rightarrow$  strong electric field  $\Rightarrow$  increases the current slightly.




Ideal case:- (Saturation)


$$(I_D)_{sat.} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 \Rightarrow \begin{matrix} \text{constant for fixed } V_{GS} \\ (\text{Independent of } V_{DS}) \end{matrix}$$

Drain-Source ON Resistance:- (Saturation)

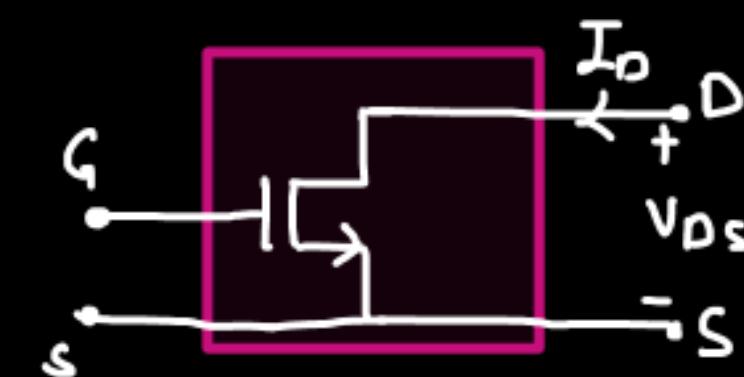
$$\frac{1}{r_{ds}} = \frac{\partial I_D}{\partial V_{DS}} = 0 \Rightarrow r_{ds} = \infty$$



Practically:-

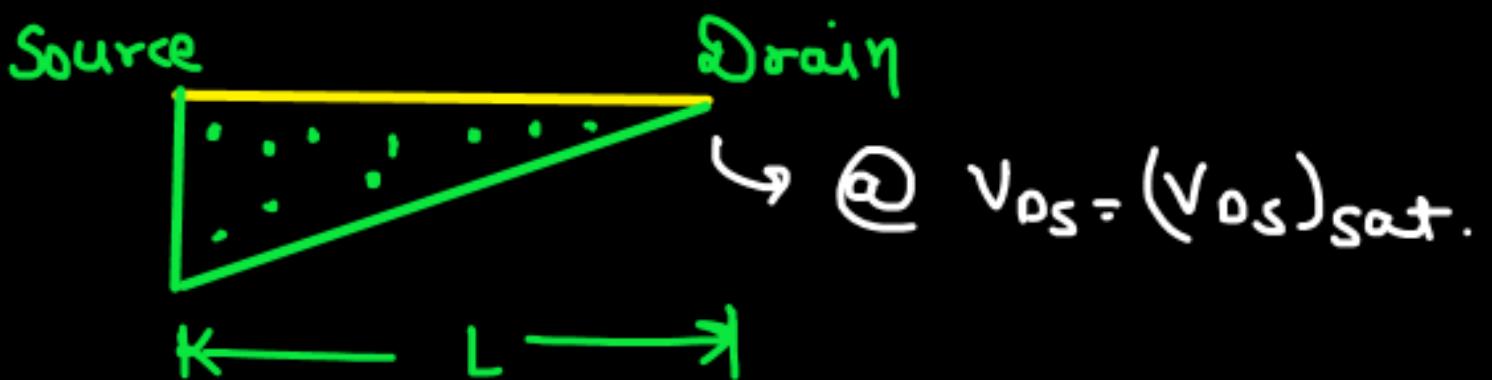

Further increasing V<sub>DS</sub>:-

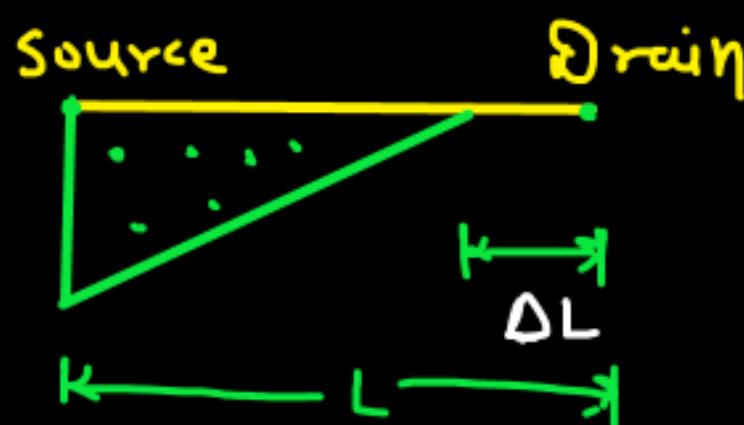

$$(I_D)_{Sat} = \frac{\mu_n C_{ox} W}{2(L - \Delta L)} (V_{GS} - V_T)^2$$

$$(I_D)_{sat} = \frac{\mu_n C_{ox} W}{2(L - \Delta L)} (V_{DS} - V_T)^2$$

$$= \frac{\mu_n C_{ox} W}{2L \left[ 1 - \frac{\Delta L}{L} \right]} (V_{DS} - V_T)^2$$

$$= \frac{\mu_n C_{ox} W}{2L} (V_{DS} - V_T)^2 \left[ 1 - \frac{\Delta L}{L} \right]^{-1}$$

$$\left[ (I_D)_{sat} \right]_{CLM} \sim \left[ (I_D)_{sat} \right]_{ideal} \left[ 1 + \frac{\Delta L}{L} \right] - \textcircled{O} \quad \left\{ \begin{array}{l} (1-x)^{-1} \\ = 1+x \end{array} \right\}$$

$$\Rightarrow \frac{\Delta L}{L} \propto V_{DS}$$

$$\Rightarrow \frac{\Delta L}{L} = \lambda V_{DS} - \textcircled{2}$$

\*  
\*\*

$$[(I_D)_{sat.}]_{CLM} = \underbrace{[(I_D)_{sat.}]_{ideal}}_{\lambda} [1 + \lambda V_{DS}]$$

$\lambda \rightarrow$  process technology  
parameter  
 $(V^{-1})$

Drain - Source ON resistance [Saturation] [CLM is present] :-

$$r_{ds} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\lambda [(I_D)_{sat.}]_{ideal}}$$

if  $\lambda = 0 \Rightarrow$  NO CLM  $\Rightarrow r_0 = \infty$   
ideal case

Early voltage -

$$[(I_D)_{sat}]_{CLM} = [(I_D)_{sat}]_{ideal} [1 + \lambda V_{DS}] \\ = 0$$

$$\Rightarrow 1 + \lambda V_{DS} = 0$$

$$V_{DS} = -\frac{1}{\lambda}$$


$\Rightarrow$  The value of  $V_{DS}$  @ which the drain current becomes zero,  
That is known as early voltage.

$$V_A = \frac{1}{\lambda}$$
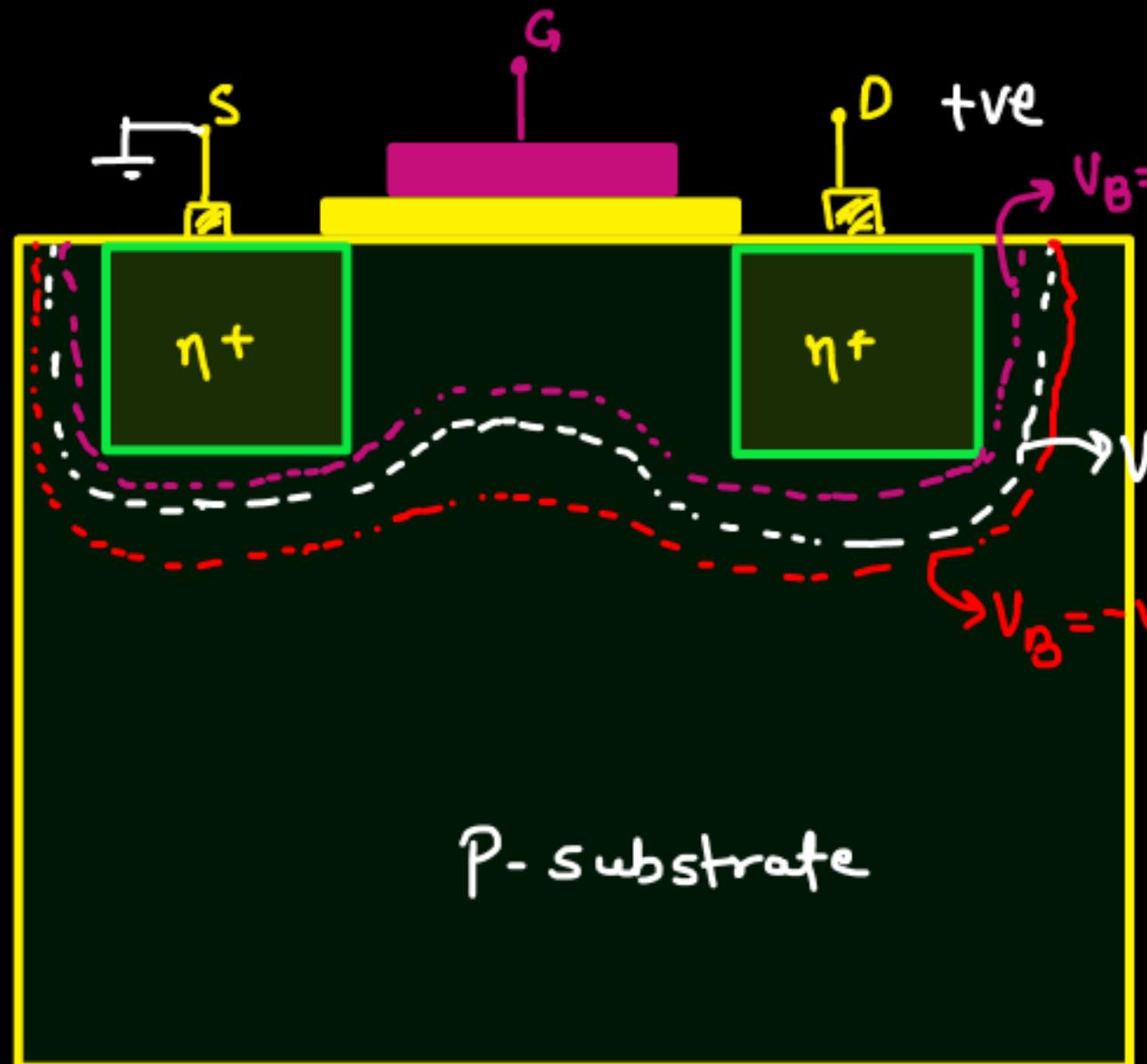
## Body Effect:-

Threshold voltage  
of NMOS

$$V_T = V_{T_0} + \gamma [\sqrt{2\Phi_f + V_{SG}} - \sqrt{2\Phi_f}]$$



$$\textcircled{1} \quad V_{SB} = 0$$

⇒ No change in  
Threshold voltage.

$$\textcircled{2} \quad V_{SB} = +ve ; V_B = -ve$$

Reverse bias @ source side  $\textcircled{1}$



e<sup>-</sup> from source will feel High  
electric field pushing them back  
into the source terminal



Higher V<sub>G</sub> required  $\Rightarrow V_T \uparrow$

③  $V_{SB} = -ve$ ,  $V_B = +ve$




Forward bias Towards source side  $\uparrow$



Source can supply more electrons @ lower  $V_g$




$V_T \downarrow$

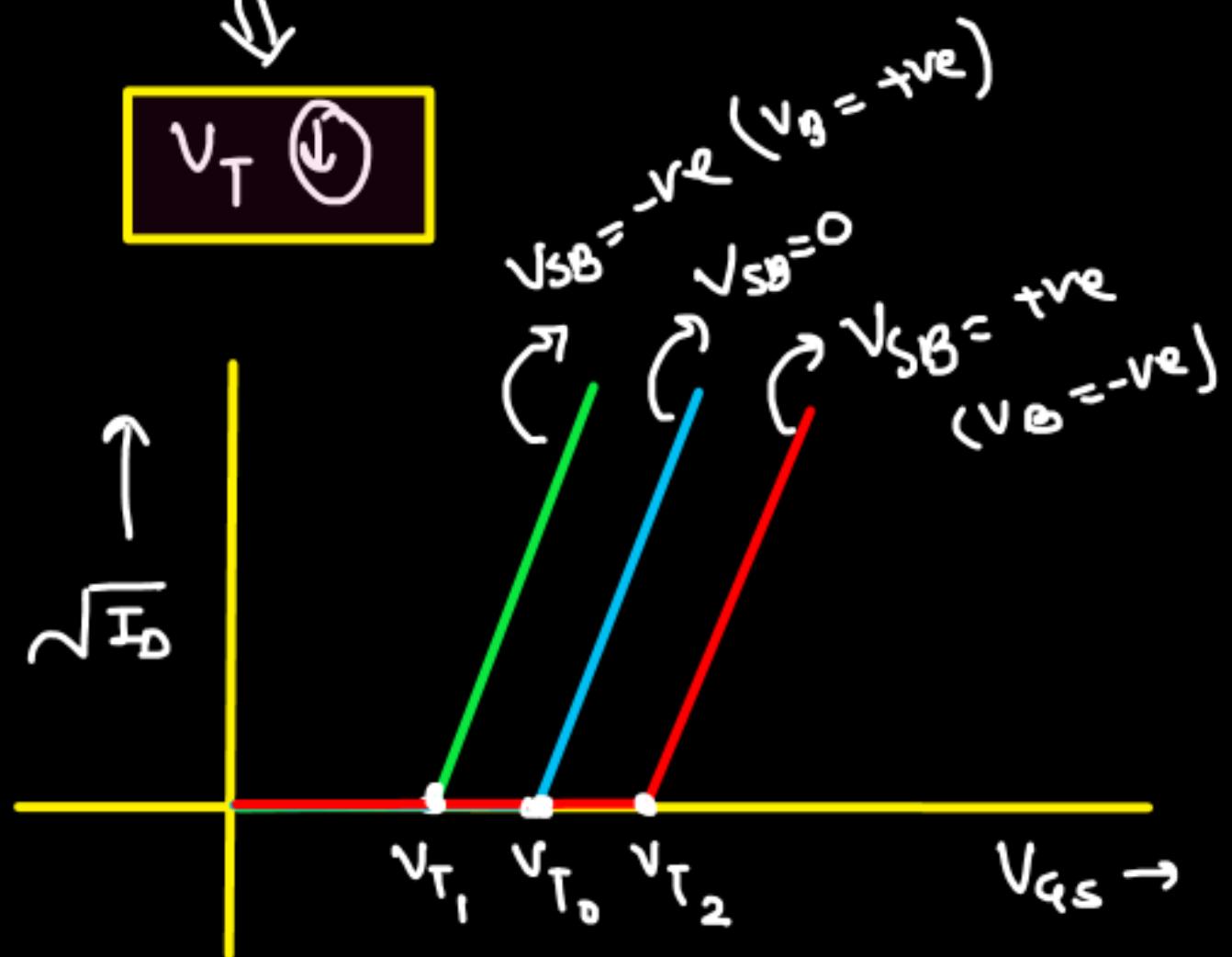

(i)  $V_{SG} = +ve$ ,  $V_B = -ve \Rightarrow V_T \uparrow$  (NOT Desirable)

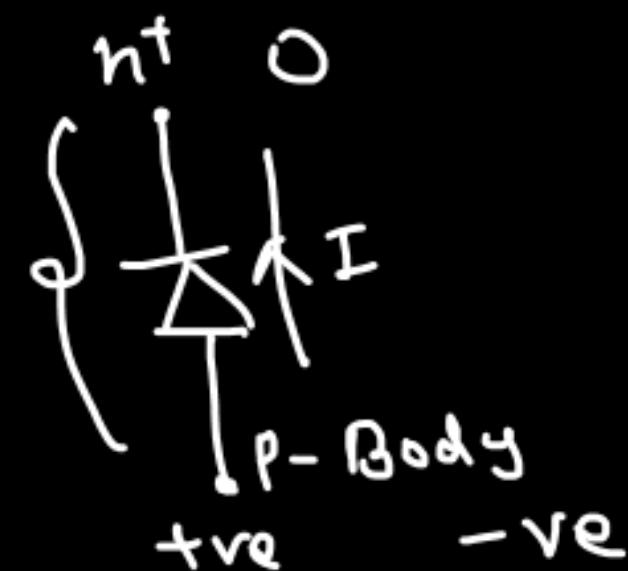(ii)  $V_{SG} = -ve$ ,  $V_B = +ve \Rightarrow$  Unwanted power consumption  
(NOT Desirable)




$\Rightarrow$  We always try to keep  $V_{SG}=0V$ ; Source- Body shorted

{ or at least source to body  
diode should be reverse  
biased }

## Assignment - 4

Q.

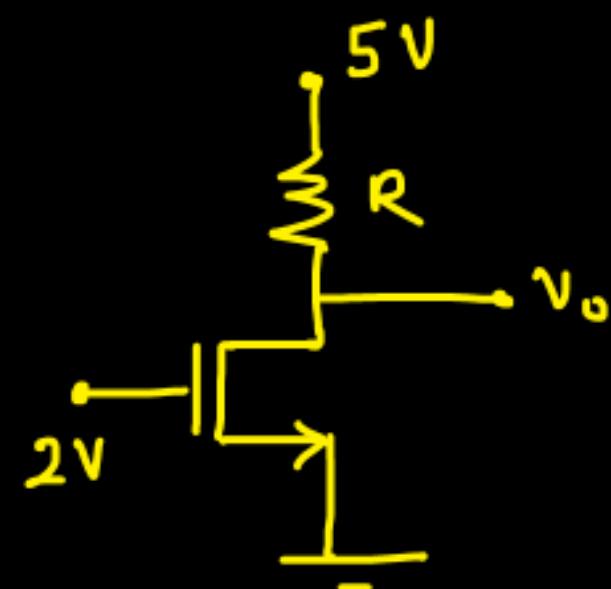

$$w_L = 10$$


$$\mu_n C_{ox} = 200 \mu A/V^2$$

$$v_T = 1V$$

Find  $v_o = ?$

(i)  $R = 1K\Omega$

(ii)  $R = 4.5K\Omega$

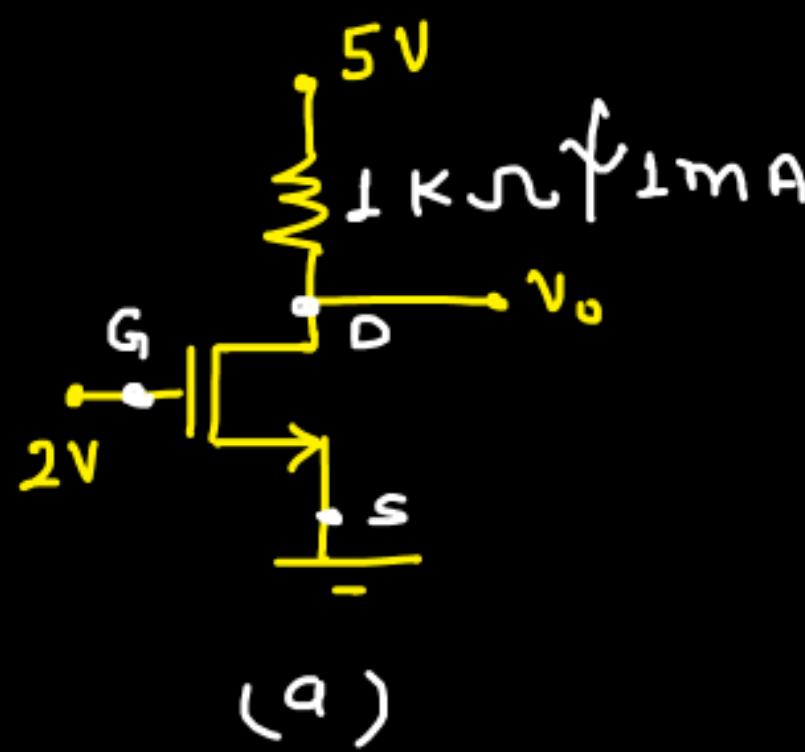

(a)

$$V_{GS} = 2 \text{ V}$$

$$V_{DS} = V_0$$

$$V_T = 1 \text{ V}$$

het., MOS is working in sat. region

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$= \frac{20 \times 10^{-4} \times 10}{2} (2 - 1)^2$$

$I_D = 1 \text{ mA}$

$V_o = 5 - 1 \text{ k} (1 \text{ mA}) = 5 - 1 = 4 \text{ V}$

$$V_{GS} = 2V, \quad V_T = 1V, \quad V_{DS} = V_{GS} - V_T \\ = 2 - 1 = 1V$$

$$V_{DS} = 4V$$

Here,  $V_{DS} > V_{GS} - V_T$


OR

$$V_{DS} > V_{DS} \Rightarrow \text{MOS is in sat.}$$

Assumption correct ✓

⇒

$$V_D = 4V$$

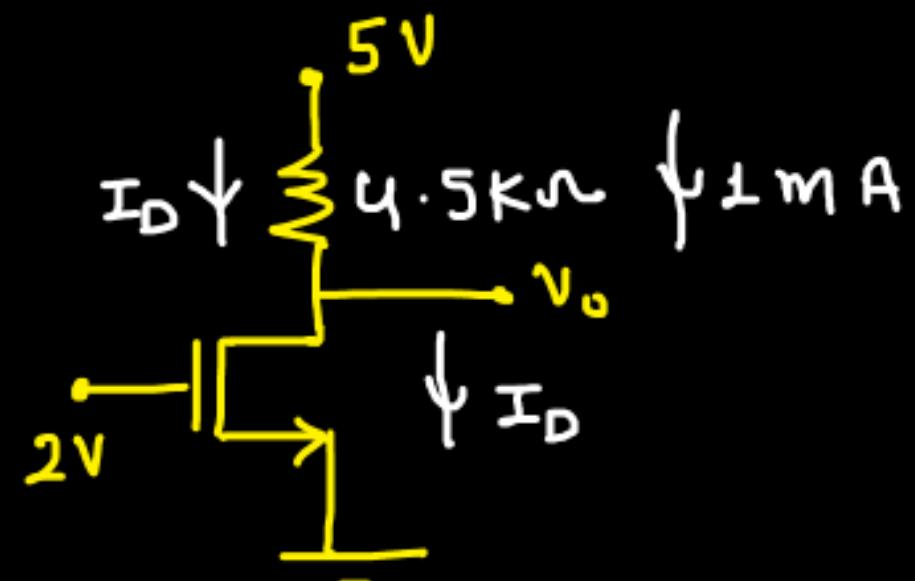

Assuming, Sat. region

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$= \frac{200 \mu A \times 20}{2} (2 - 1)^2$$

$$I_D = 1 \text{ mA}$$



$$V_o = 5 - 4.5 \text{ k}(\text{lm})$$

$$V_o = 0.5 \text{ V}$$



$$\text{Now, } V_{DS} = V_o = 0.5 \text{ V}$$

$$V_{GS} - V_T = 2 - 1 = 1 \text{ V}$$

Here,  $V_{DS} < V_{GS} - V_T \rightarrow$  linear region

Assumption wrong

Assuming, linear region;

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{5 - V_D}{4.5K} = \underbrace{\frac{200 \times 10}{2m}}_{\text{2m}} \left[ 1 \times V_D - \frac{V_D^2}{2} \right]$$

$$5 - V_D = 5 \left[ V_D - \frac{V_D^2}{2} \right]$$

$$4.5V_D^2 - 10V_D + 5 = 0$$

$$V_D = \frac{10 \pm \sqrt{100 - 90}}{9}$$

$$\begin{array}{c} \swarrow \searrow \\ 1.46V \quad 0.76V \end{array}$$

$$V_0 \rightarrow 1.46 V$$

$$V_0 \rightarrow 0.76 V$$

Let,  $V_0 = 1.4V = V_{DS}$

$$V_{DS} - V_T = 1V$$

Here  $V_{DS} > V_{DS} - V_T$

$\Rightarrow$  sat.

~~X~~

$$V_0 = 0.76 V = V_{DS}$$

$$V_{DS} - V_T = 1V$$

$$V_{DS} < V_{DS} - V_T$$

$\Rightarrow$  Linear ~~V~~






Assumption correct


$V_0 = 0.76 V$

Q. Given,  $\mu_n C_{ox} = 100 \mu A/V^2$ ,  $w/l = 1$ ,  $V_T = 1V$

Find region of operation.

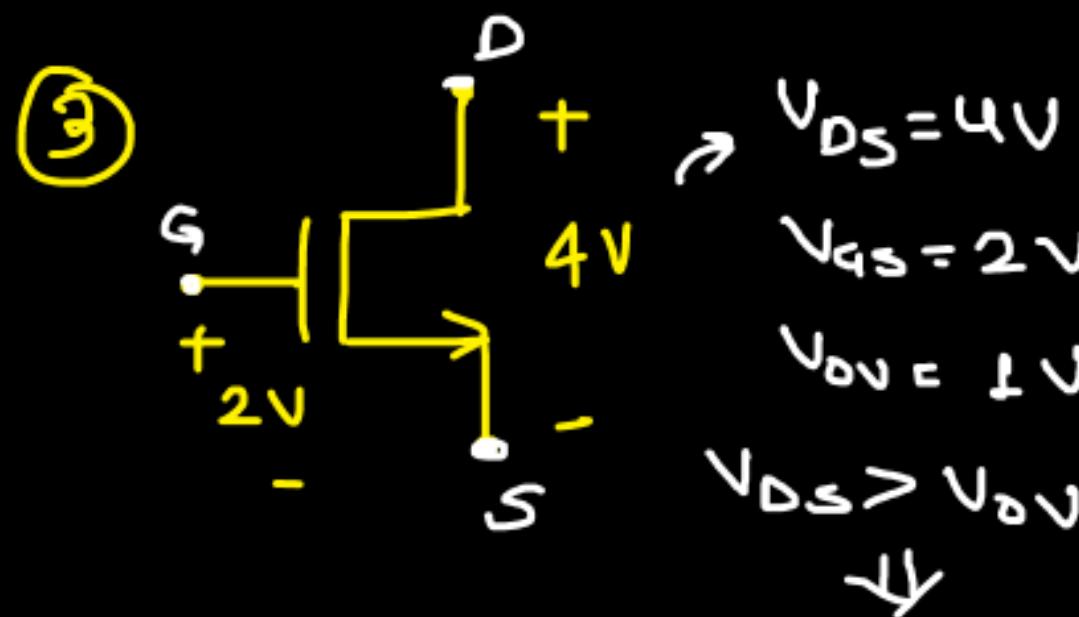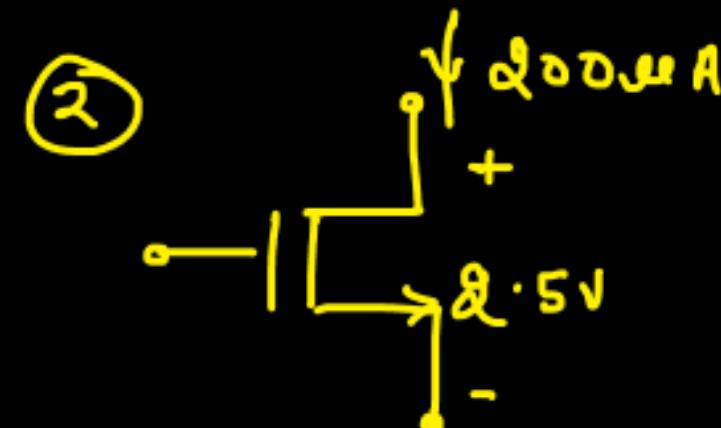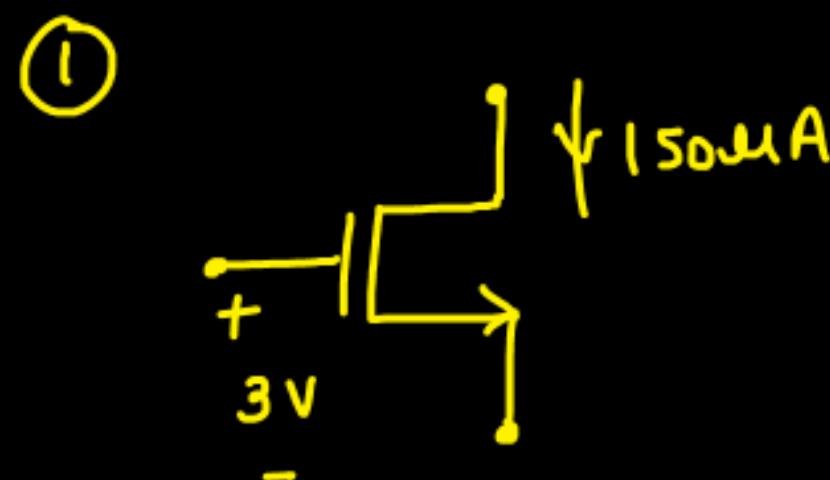


Sat. region

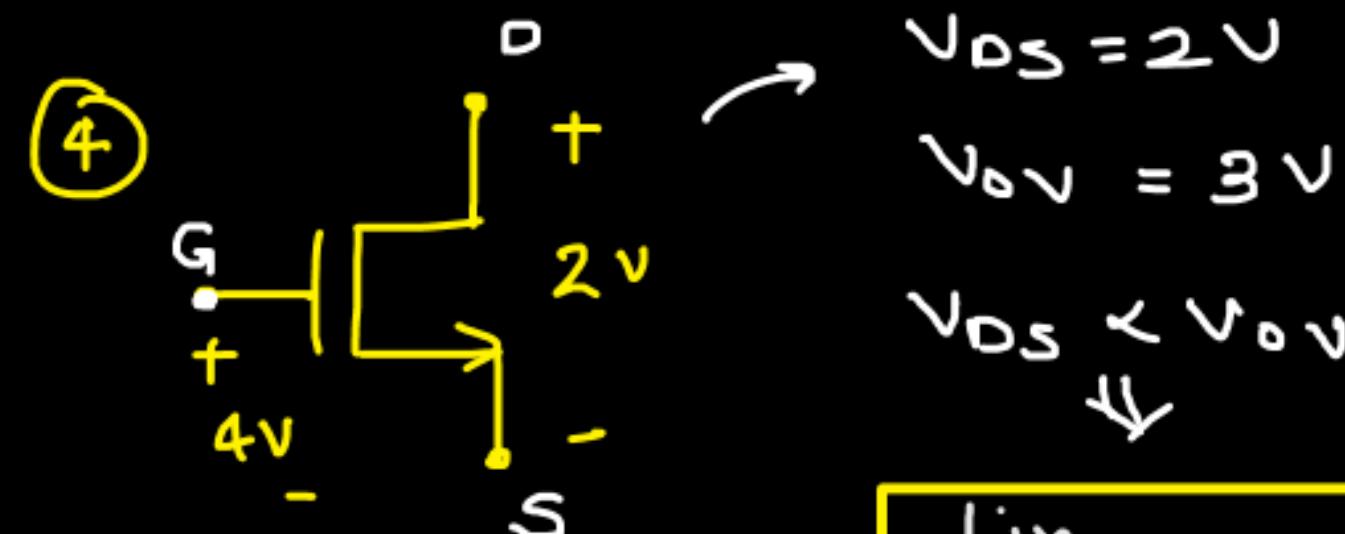

Linear region

⑤

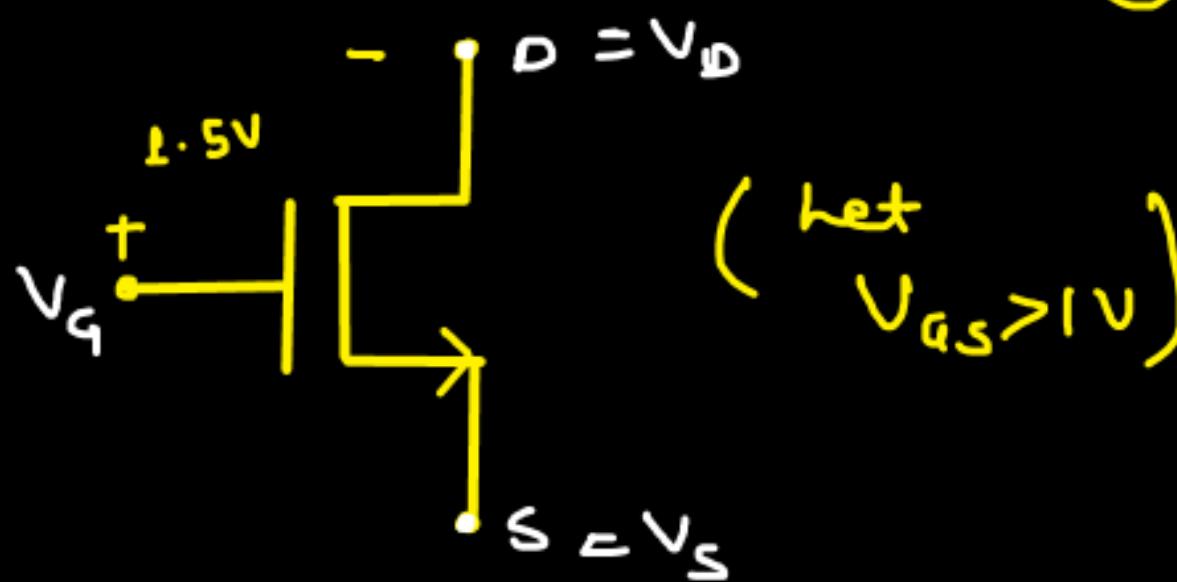

$$V_{DS} = V_D - V_S$$

$$V_{GS} = V_G - V_S$$

$$= V_D + 1.5 - V_S$$


$$V_{GS} = 1.5 + V_{DS}$$

$$V_T = 1V$$

$$V_{OV} = 0.5 + V_{DS}$$

$$V_{DS} < V_{OV} \Rightarrow \text{linear region}$$

⑥

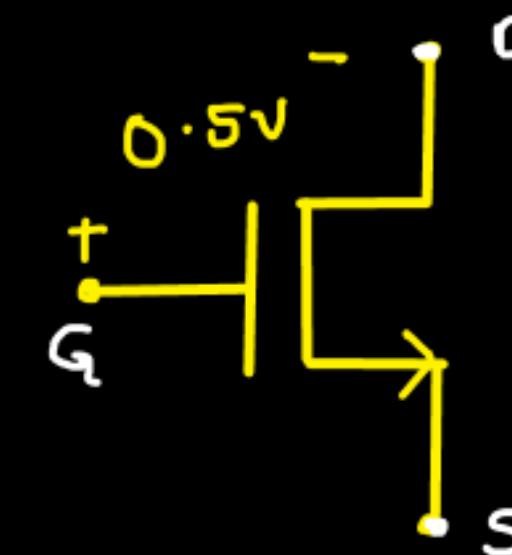

$$V_{DS} = V_D - V_S$$


$$V_{GS} = V_G + 0.5 - V_S$$

$$V_{GS} = V_{DS} + 0.5$$

$$V_T = 1V$$

$$V_{OV} = V_{DS} - 0.5$$
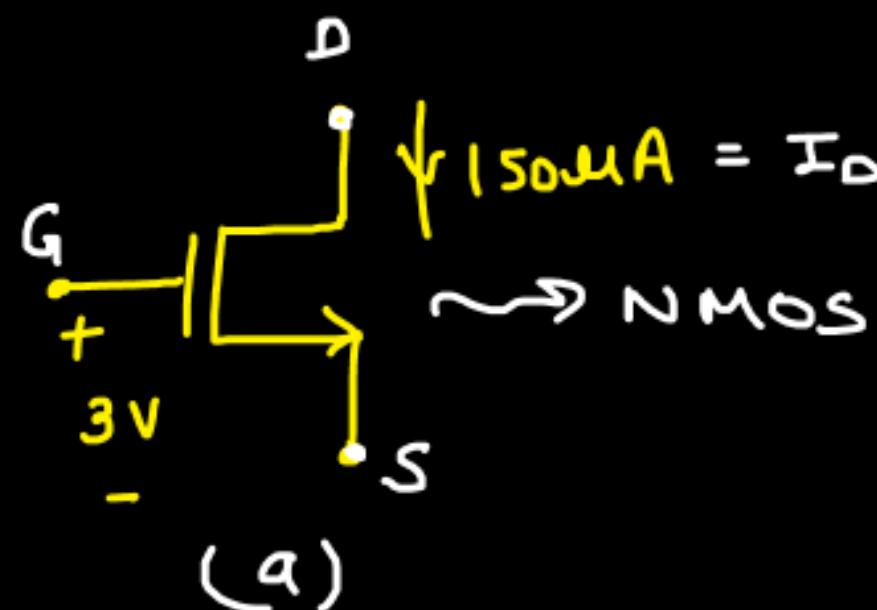
$$V_{DS} > V_{OV} \Rightarrow \text{sat. region}$$



$$V_{GS} = 3 \text{ V}$$

$$V_T = 1 \text{ V}$$


$$I_D = 150 \mu\text{Amp.}$$

het MOS is in sat. region


$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$= \frac{100 \times 10}{2} (3 - 1)^2$$

$$I_D = 200 \mu\text{A}$$

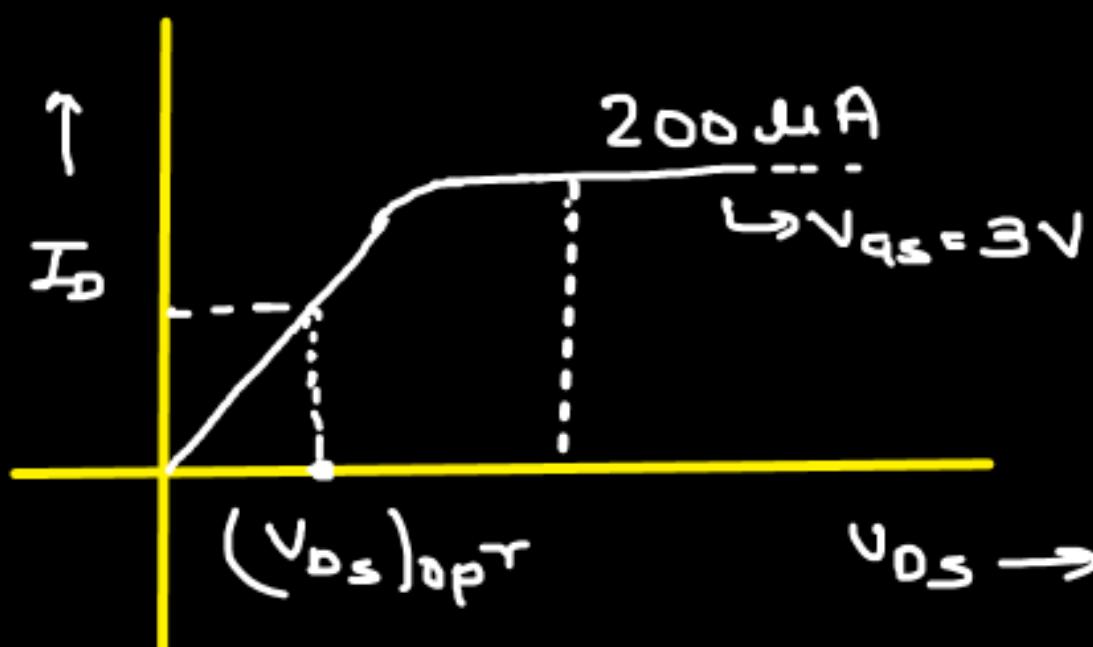

MOS is not in sat. but in linear

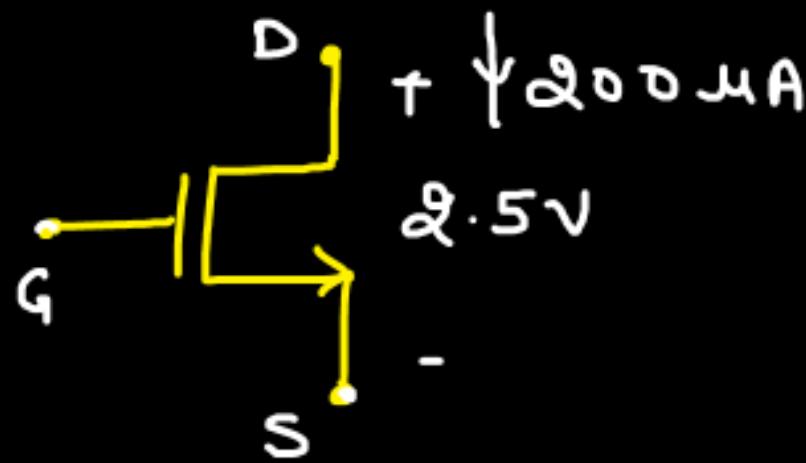

$$I_D = 200 \mu A$$

het, sat. region

$$I_D = \frac{4nC_{ox}W}{2L} (V_{GS} - V_T)^2$$

$$200 \mu A = \frac{100 \mu A \times 1}{2} (V_{GS} - 1)^2$$


$$V_{GS} = 3 V$$

$$V_{DS} = 2.5 V$$

$$V_{DV} = 3 - 1 = 2 V$$

Here  $V_{DS} > V_{DV} \Rightarrow$  sat. region  $\Rightarrow$  Assumption ~~W~~

Q.

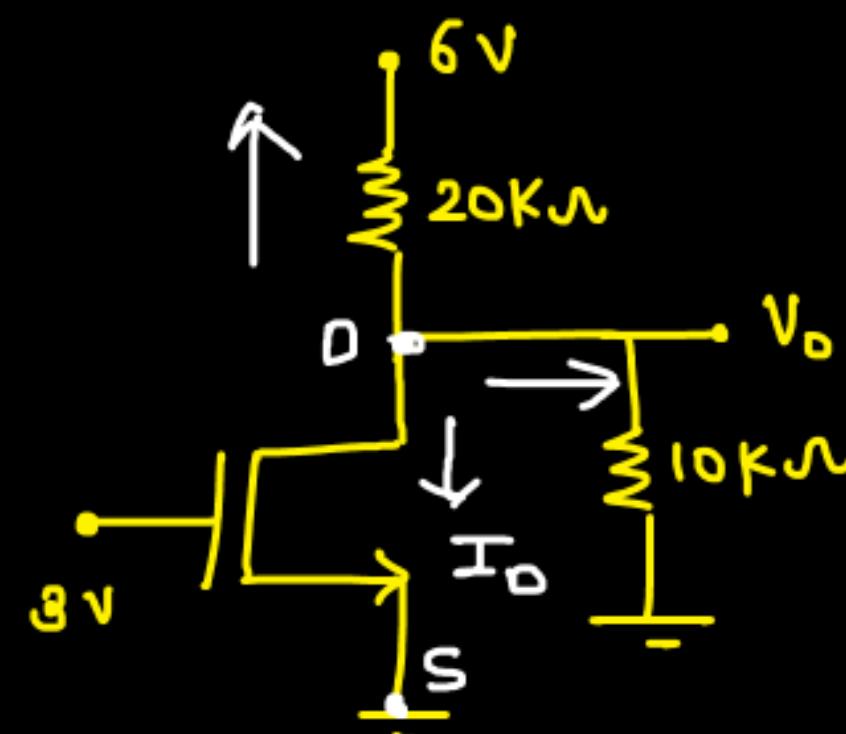

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$w/l = 1$$

$$V_T = 1V$$

$$\text{find } V_o = ?$$

$$V_{DS} = V_o$$

find drain current of Mos.

KCL @ node  $V_o$

→

$$I_D + \frac{V_o}{10k} + \frac{V_o - 3}{20k} = 0$$

$$I_D = \frac{6 - V_o}{20k} - \frac{V_o}{10k} \rightarrow \textcircled{1}$$

Let, MOS is in sat.

$$I_D = \frac{100 \mu}{2} (3-1)^2$$

$$I_D = 200 \mu A \quad \times$$

$$200 \mu = \frac{6 - V_o}{20k} - \frac{V_o}{10k}$$

$$4 = 6 - V_o - 2V_o$$

$$V_o = \frac{2}{3} = 0.67V \quad \times$$

$$V_{DS} = V_{GS} - V_T = 2V$$

$$V_o = V_{DS} < V_{DS} \Rightarrow \text{linear region} \Rightarrow \text{Assumption } \times$$

Assuming, MOS in linear region

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$\frac{6 - V_0}{20K} - \frac{V_0}{10K} = \text{Loosest} \left[ 2V_0 - \frac{V_0^2}{2} \right]$$

$$6 - V_0 - 2V_0 = 2 \left[ 2V_0 - \frac{V_0^2}{2} \right]$$

$$6 - 3V_0 = 4V_0 - V_0^2$$

$$V_0^2 - 7V_0 + 6 = 0$$

$$\Rightarrow V_0 \begin{cases} \rightarrow 1V \\ \rightarrow 6V \end{cases}$$

if  $V_0 = 1V$

$$V_{DS} = 2V$$

$$V_{DS} < V_{DS}$$

$\Rightarrow$  linear region

$$V_0 = 1V$$

if  $V_0 = 6V$

$$V_{DS} = 2V$$


$$V_{DS} > V_{DS}$$

$\downarrow$

Sat.

X  $\leq$

Q.

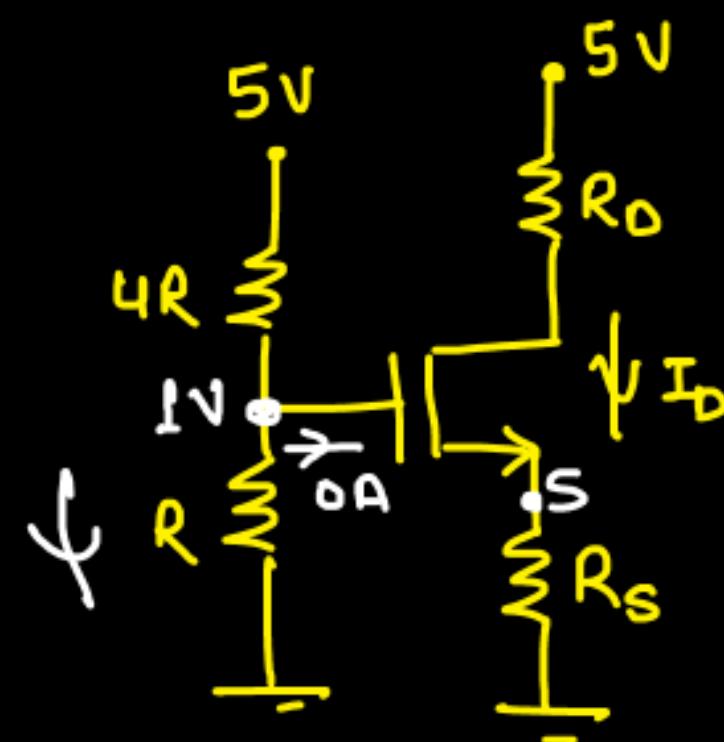

find  $R_S$  such that MOS works in saturation region.

Given

$$I_D = 119 \mu\text{Amp}, V_T = 0.5\text{V}$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = 4.12 \text{ mS/V}$$

$$V_G = 1\text{V}$$

$$V_S = I_D R_S$$

$$V_{GS} = 1 - I_D R_S$$

$$V_T = 0.5\text{V}$$


$$I_D = K_n (V_{GS} - V_T)^2$$

$$119\mu = 4.12m (1 - 119\mu \times R_S - 0.5)^2$$

$$0.17 = 0.5 - 119\mu \times R_S$$

$$\Rightarrow R_S = 2.71 \text{ k}\Omega$$

Q.

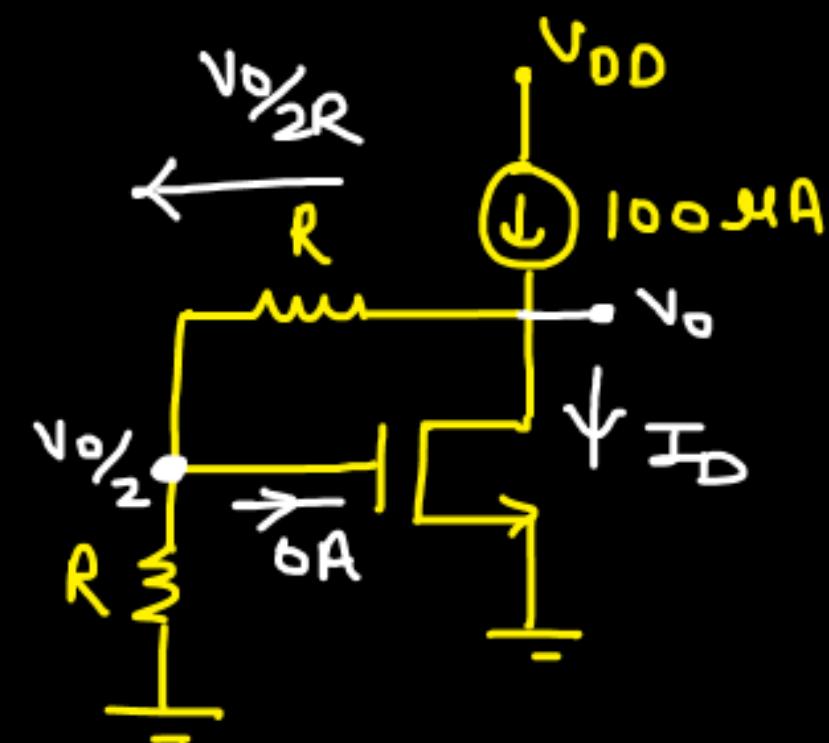

$$\frac{\mu_{nCOX} W}{L} = 100 \mu S/V$$

$$V_T = 1V, R = 40K\Omega$$

Find bias current in Transistor.

$$V_{DS} = V_D$$

$$V_{GS} = V_0/2$$

$$V_T = 1V$$

$$100 \mu A = \frac{V_0}{2R} + I_D$$

$$I_D = 100 \mu A - \frac{V_0}{80K}$$

$$I_D = 100 \mu A - \frac{1000}{80} V_0 \times \mu$$

$$I_D = 100\mu - 12.5V_o \mu \text{ A}$$

Let, MOS in sat,

$$I_D = \frac{100\mu}{2} \left( \frac{V_o}{2} - 1 \right)^2$$

$$100\mu - 12.5\mu V_o = 50\mu \left( \frac{V_o}{2} - 1 \right)^2$$

$$100 - 12.5V_o = 50 \left( \frac{V_o^2}{4} + 1 - V_o \right)$$

$$100 - 12.5V_o = 12.5V_o^2 + 50 - 50V_o$$

$$12.5V_o^2 - 37.5V_o - 50 = 0$$

$$V_o^2 - 3V_o - 4 = 0$$

$$\begin{aligned} &\rightarrow V_o = 4V \\ &\rightarrow V_o = -1V \end{aligned}$$

Let  $V_D = -V_U = V_{DS} \Rightarrow$  MOS goes into cut-off

Check:-

MOS cut-off

$$I_D = 0 \text{ Amp.}$$

$$\frac{V_0}{2R} = 100 \text{ mV}$$

$$V_D = 8V, V_{GS} = 4V$$

$$V_{DV} = \frac{V_0}{2} - V_T = 3V$$

$V_D > V_{DV}$   
also  $V_{GS} > V_T$   
also  $V_{DS} > 0V$

$\left. \begin{array}{l} \\ \\ \end{array} \right\} \Rightarrow$  MOS goes into sat.  
 $\downarrow$   
(Can't be cut-off)

$$\text{if } V_D = 4V$$

$$V_{DS} = 4V$$

$$V_{GS} = 2V$$

$$V_T = 1V$$

$$V_{OV} \approx 1V$$

$\Rightarrow V_{DS} > V_{OV} \Rightarrow$  Sat. region  $\supseteq$  Assumption ✓


$$V_D = 4V$$

$$I_D = 100\mu A = 12.5\mu A \times 4$$

$$\Leftarrow I_D = 50\mu A$$
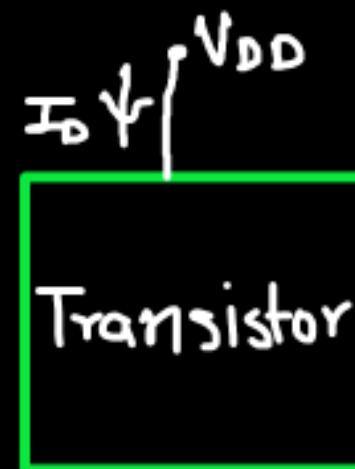
## Biasing:-

The process of setting a transistors DC operating voltage or current conditions to the correct level so that any AC input signal can be amplified correctly by the transistor.




Why biasing is required ?

↳ Why we needed MOSFET:-



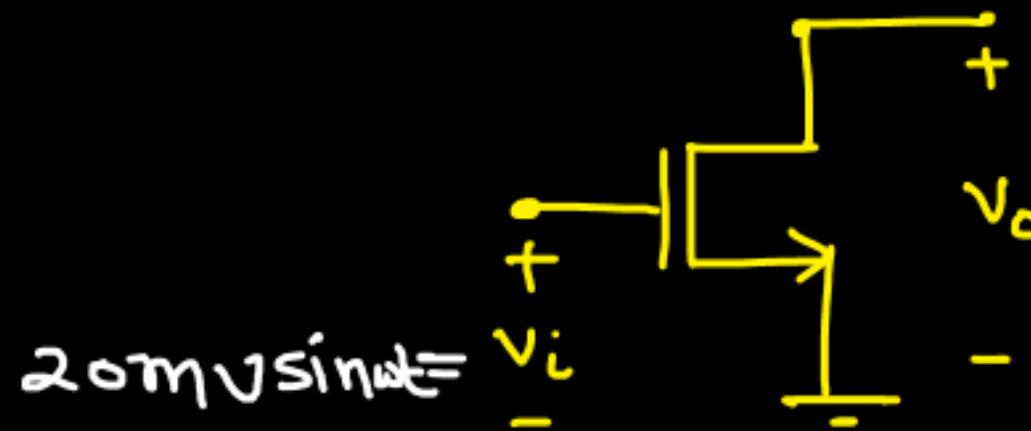\* Let I don't apply an dc bias to my amplifier and directly give small signal ac voltage.




$$20mV \sin \omega t = v_i$$

$$\Rightarrow v_{AS} = 20mV \sin \omega t$$

$$\text{max} = 20mV$$

$$\text{min} = -20mV$$

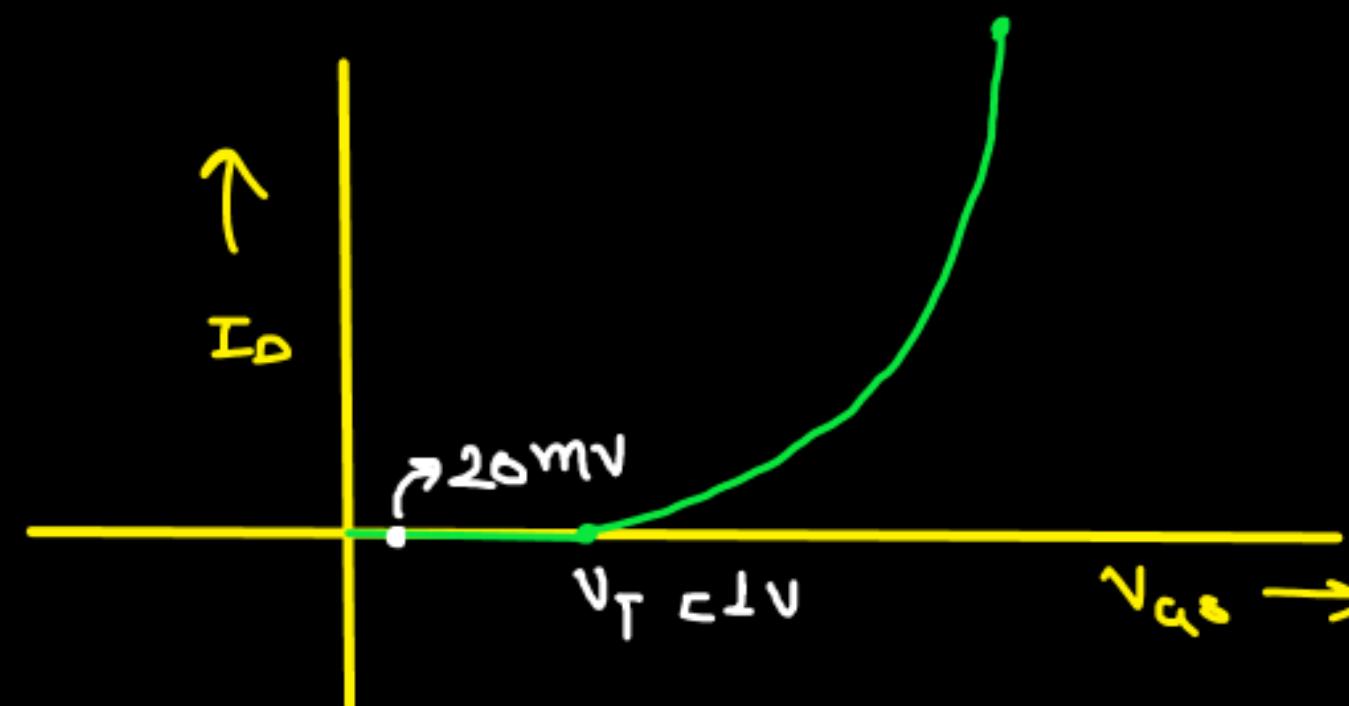


$\Rightarrow$  Transistor doesn't even turn on.


So, to make sure that the transistor is always in "ON condition", we give some dc bias to the MOS and apply small signal voltage (20mV, 10mV, 40mV) on it.

$$\Rightarrow V_{GS} = V_{QQ} + V_i$$

$$V_{GS} = 2V + 20mV \sin \omega t$$

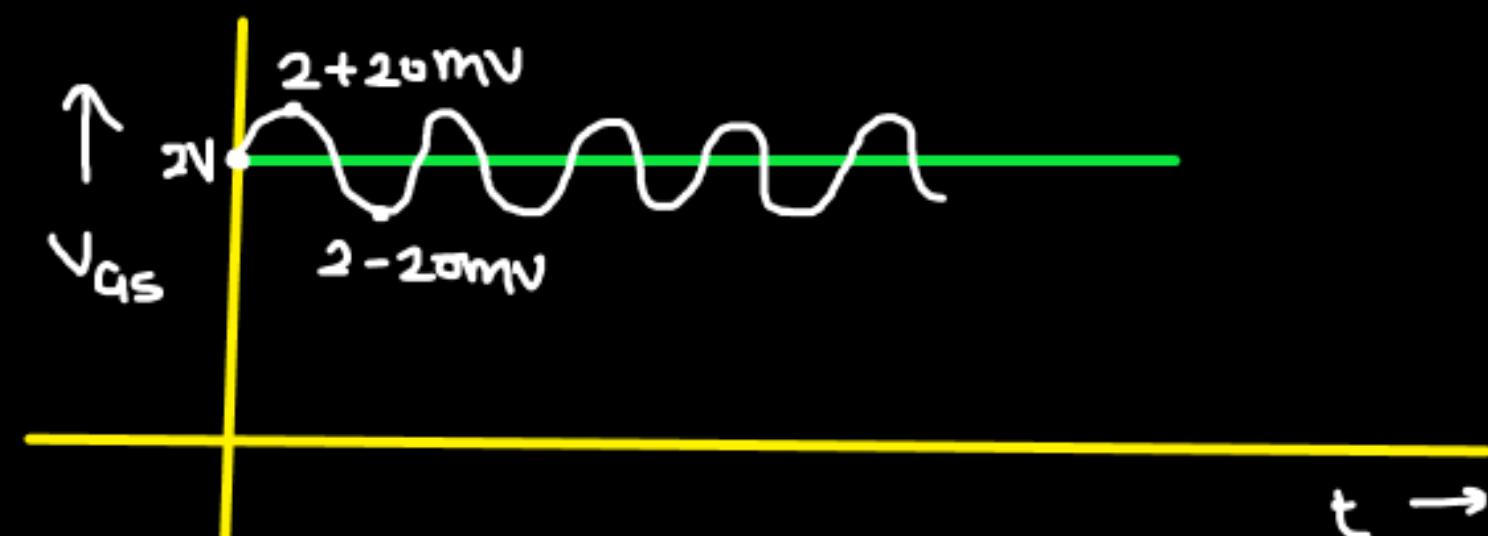

## Transfer Characteristics:-

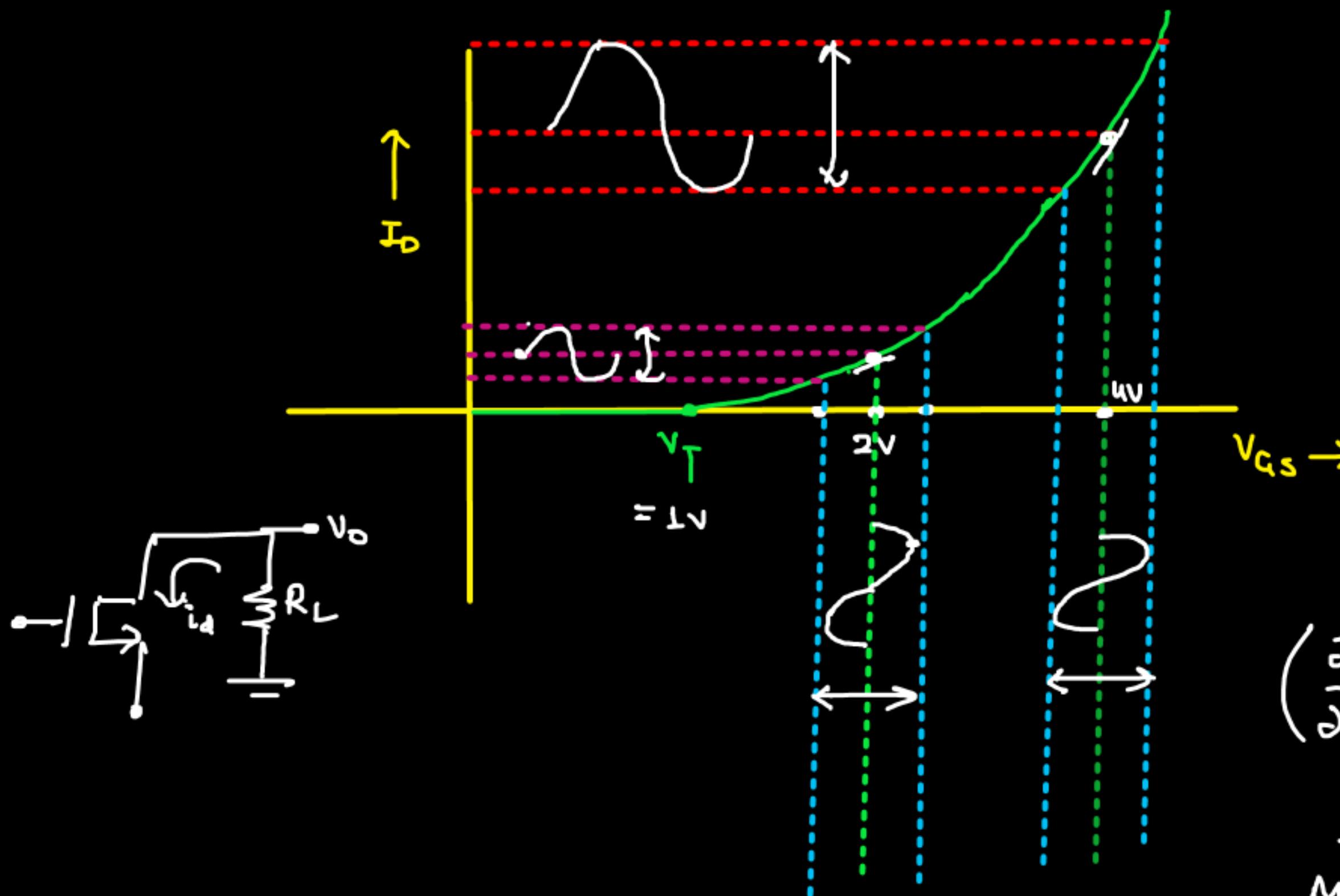

$$V_{GS_1} = 2 + V_i$$

$$V_{GS_2} = 4 + V_i$$

$$\left( \frac{\partial I_D}{\partial V_{GS}} \right)_{V_{GS_2}} > \left( \frac{\partial I_D}{\partial V_{GS}} \right)_{V_{GS_1}}$$

$\downarrow$   
MORE GAIN


@ Higher  $V_{GS}$ , you get Higher value of  $\frac{\partial I_D}{\partial V_{GS}}$

and that eventually gives more gain.

But, while using MOS as an amplifier, you can't keep  $V_{GS}(\text{dc})$  value to be very High. Why?


- (i) More power consumption
- (ii) MOS will fall out of saturation.
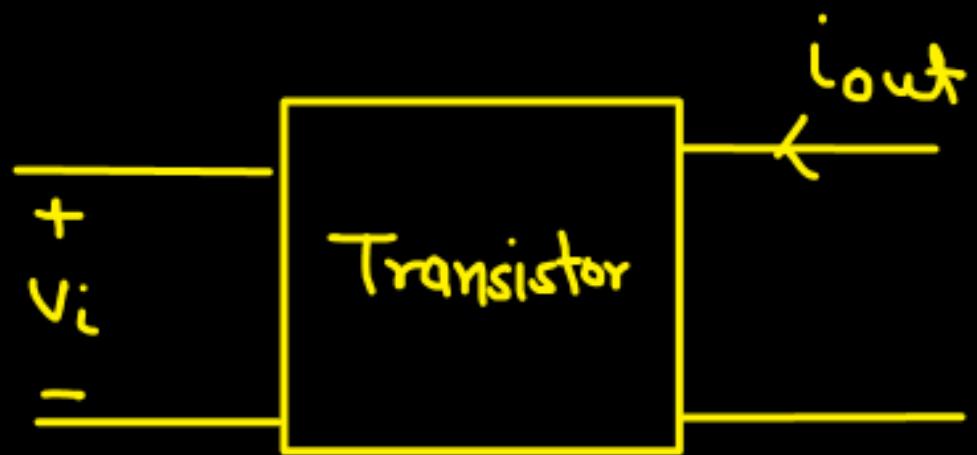
## Concept of Transconductance :- ( $g_m$ )



$$g_m = \frac{\partial i_{out}}{\partial V_{in}}$$

considering NMOS:-

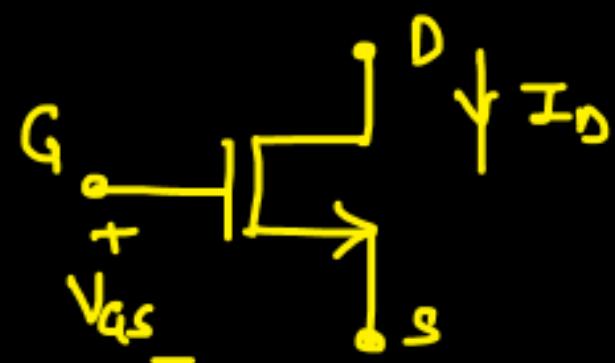

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

## Transconductance for Triode region:-

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\mu_n C_{ox} W}{L} [V_{DS} - 0]$$

$$(g_m)_{\text{Triode}} = \frac{\mu_n C_{ox} W}{L} \times V_{DS}$$

## Transconductance for Saturation region:-

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 \quad \text{--- (1)}$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$



$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T) \quad \checkmark \rightarrow (2)$$

From eqn (1)

$$\frac{\partial I_D}{V_{GS} - V_T} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T) = g_m$$

$$g_m = \frac{2 I_D}{V_{GS} - V_T} \quad \text{--- (3)}$$


$$I_D = \frac{\mu_n C_{ox} \omega}{2L} (V_{GS} - V_T)^2$$

$$2 \frac{\mu_n C_{ox} \omega}{L} I_D = \left( \frac{\mu_n C_{ox} \omega}{L} \right)^2 (V_{GS} - V_T)^2$$


$$\sqrt{2 \frac{\mu_n C_{ox} \omega}{L} I_D} = \frac{\mu_n C_{ox} \omega}{L} (V_{GS} - V_T) = g_m$$

$$g_m = \sqrt{2 \times \frac{\mu_n C_{ox} \omega}{L} I_D} \quad \text{--- (3)}$$

## Saturation region :-

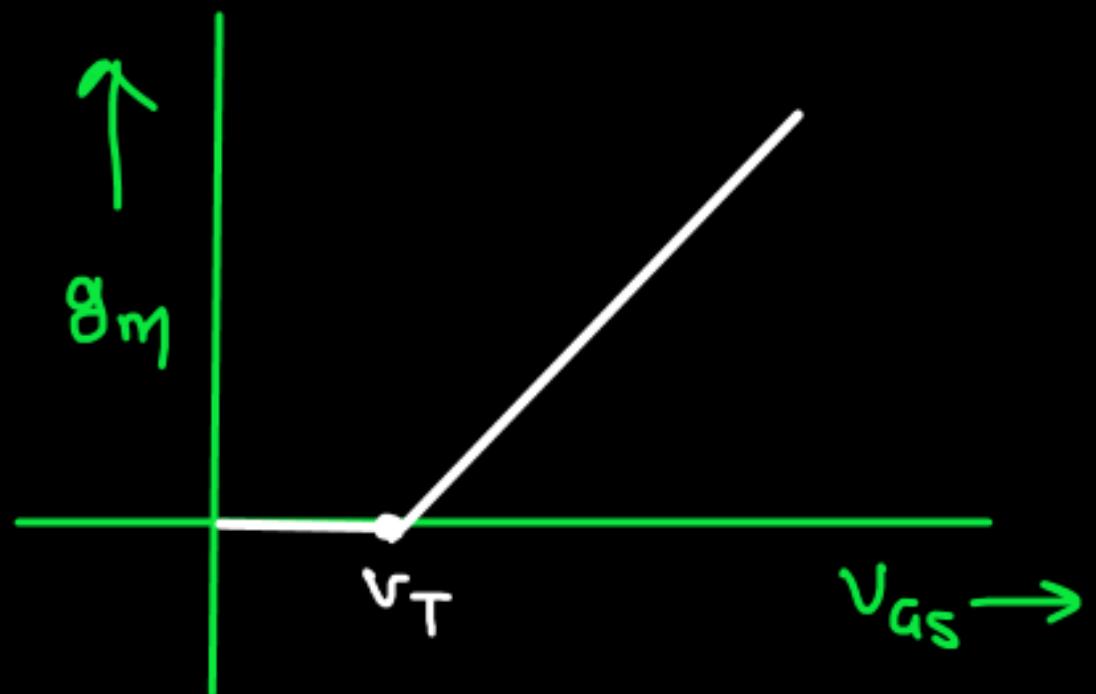

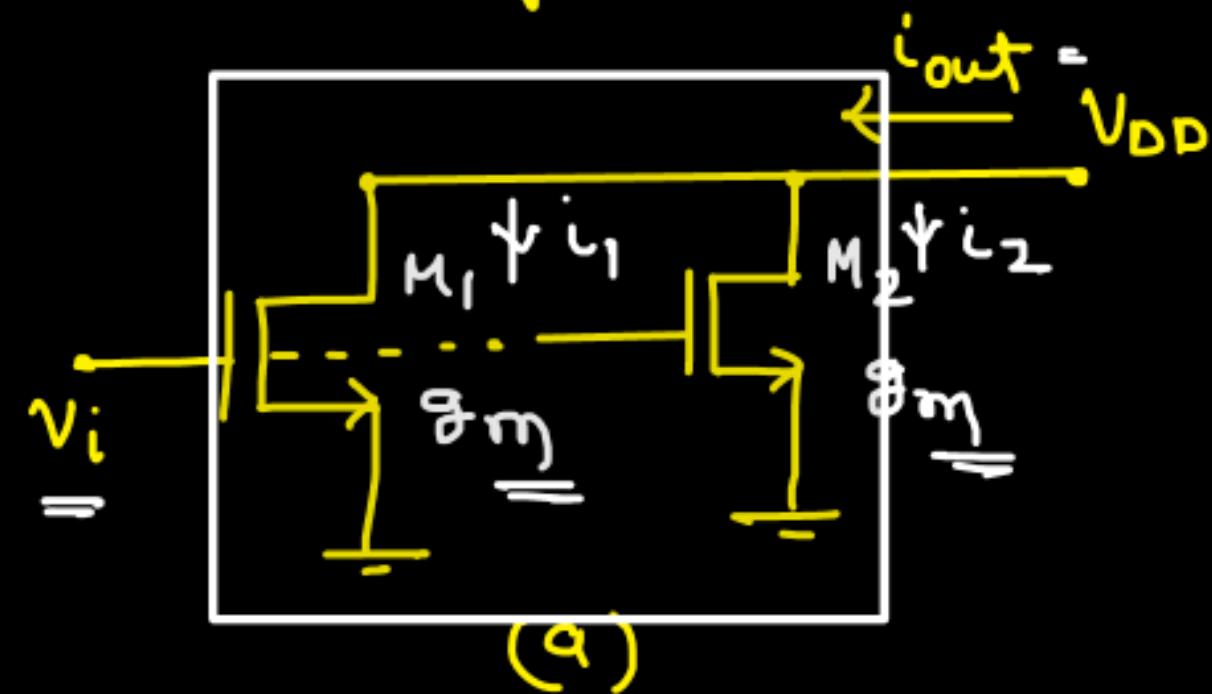- ① Find the overall Transconductance of the given fig.  $M_1$  and  $M_2$  are identical MOS with Transconductance  $g_m$ .



$$\Rightarrow \text{Overall Transconductance } G_m = \frac{\partial I_{\text{out}}}{\partial V_{\text{in}}} =$$

For M<sub>1</sub>,

$$\delta_m = \frac{\partial i_1}{\partial V_{in}}$$

For M<sub>2</sub>


$$\delta_m = \frac{\partial i_2}{\partial V_{in}}$$

$$G_m = \frac{\partial i_{out}}{\partial V_{in}} ; \quad i_{out} = i_1 + i_2$$

$$G_m = \frac{\partial (i_1 + i_2)}{\partial V_{in}}$$

$$G_m = \frac{\partial i_1}{\partial V_{in}} + \frac{\partial i_2}{\partial V_{in}}$$

$$G_m = 2\delta_m$$

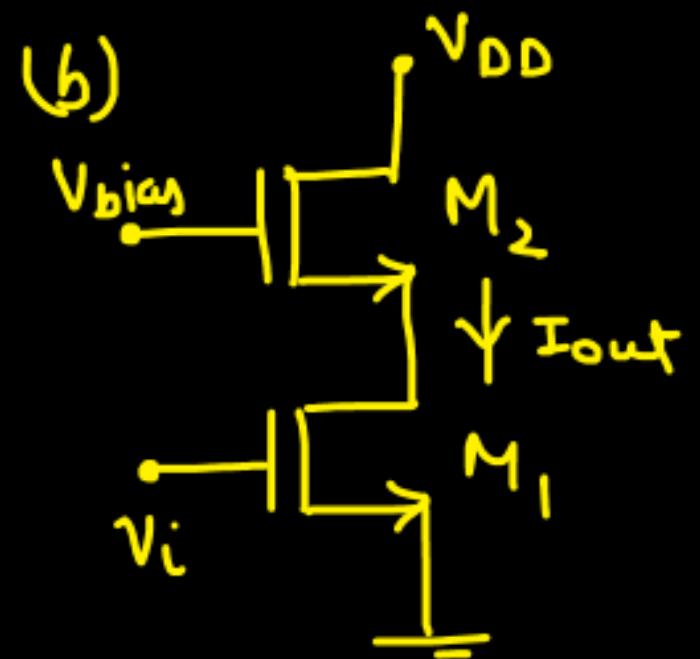

Transconductance of  $M_1$  and  $M_2$  is  $g_{m_1}$  and  $g_{m_2}$  respectively.



Find overall Transconductance of given ckt.

$$\rightarrow \text{Overall Transconductance} = \boxed{\frac{\partial I_{\text{out}}}{\partial V_{\text{in}}} = G_m}$$

$$g_{m_1} = \frac{\partial I_{\text{out}}}{\partial V_{\text{in}}} = G_m$$

$$G_m = g_{m_1}$$

## ★ O/P characteristics of MOS:-

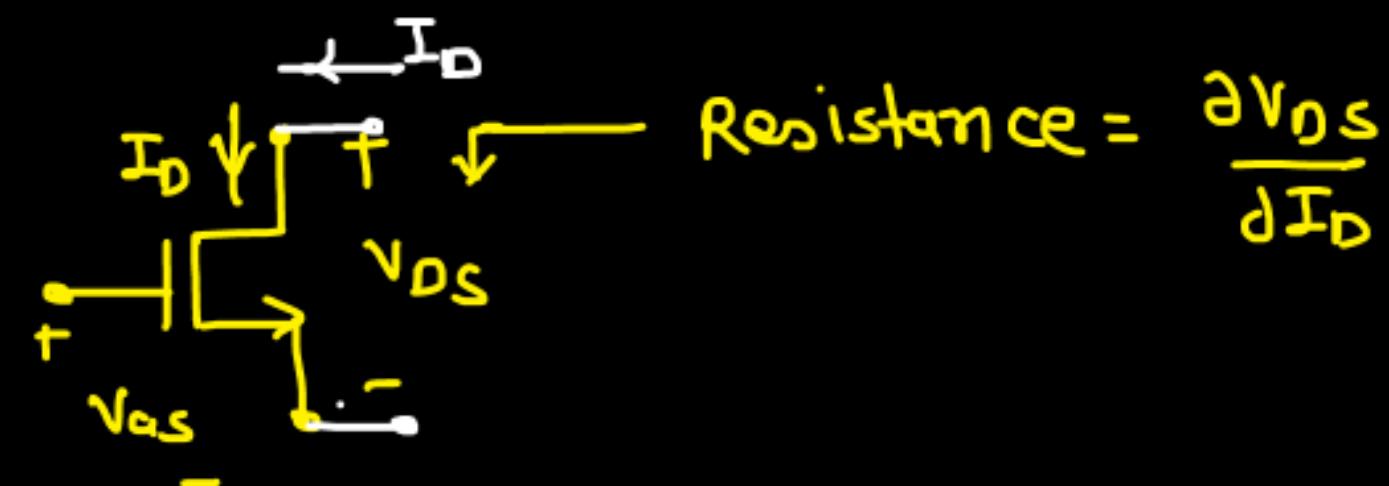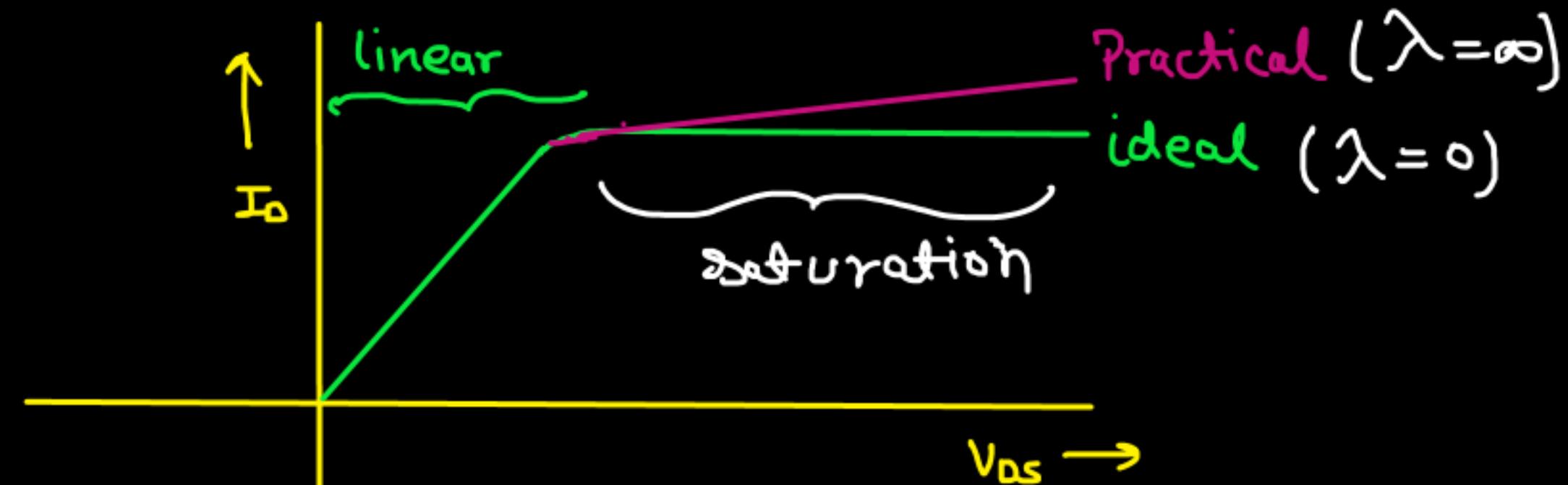

$$\downarrow (I_D)_{sat} = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$(I_D)_{linear} = \frac{\mu_n C_{ox} W}{L} [(V_{GS} - V_T) V_{DS} - V_{DS}^2 / 2]$$


For saturation region:-

$$\gamma_{ds} = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} \xrightarrow{\text{practical}} \gamma_{ds} = \frac{1}{\lambda [I_D]_{sat-ideal}}$$

$\xrightarrow{\text{ideal}}$


$$\gamma_{ds} = \infty$$

MOS in saturation region:-

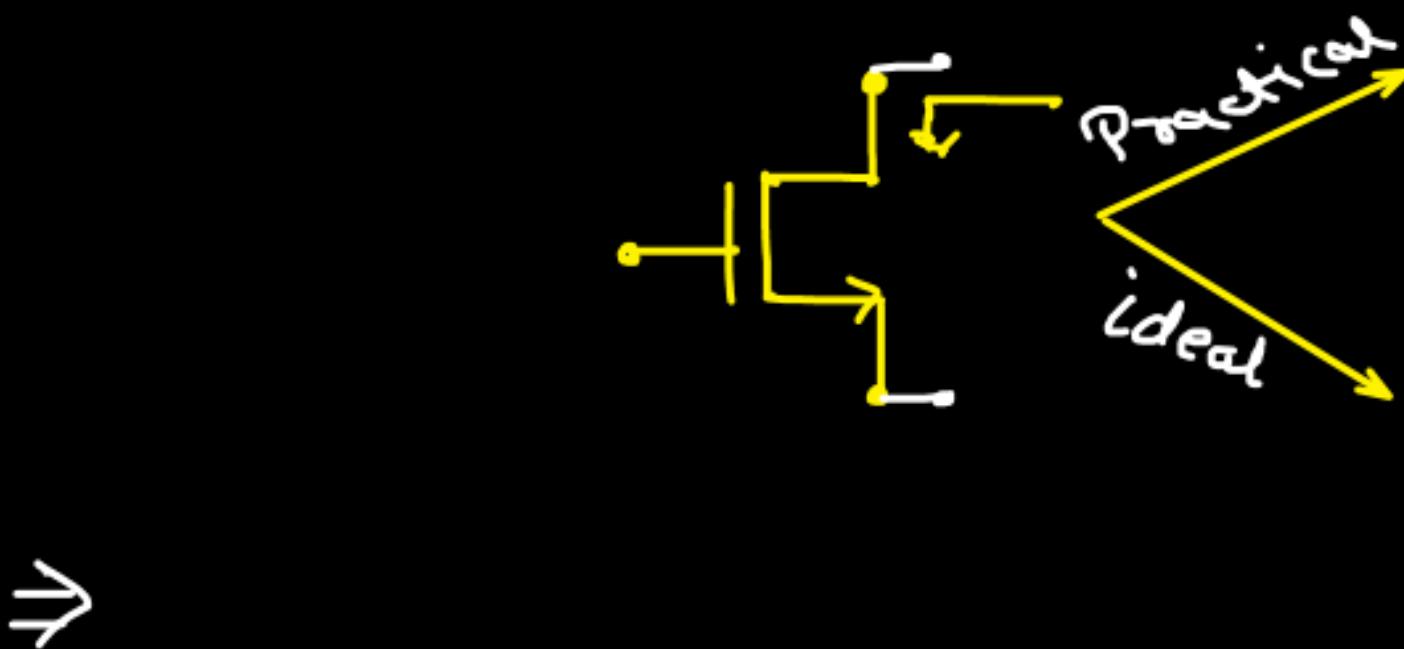

A circuit diagram of an NMOS transistor in saturation mode. The drain terminal (D) is at the top, the source terminal (S) is at the bottom, and the gate terminal (G) is on the left. A current source labeled  $I$  is connected between the drain and source terminals. A voltage source labeled  $V_{GS}$  is connected between the gate and source terminals. A feedback loop is shown from the drain terminal back to the gate terminal, consisting of a resistor labeled  $r_{ds}$  and a dependent current source labeled  $\lambda(I_D)$ . The equation for the drain-to-source voltage is given as:
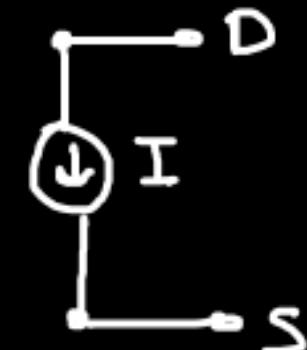
$$r_{ds} = \frac{1}{\lambda(I_D)_{sat-ideal}}$$



$$I = f(V_{GS})$$

For Triode region :-

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

for deep Triode region:-

$$I_D = \frac{\mu_n C_{ox} W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$


$$R_{ON} = \frac{\partial V_{DS}}{\partial I_D} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}}$$

For deep Triode region,

$V_{DS}$  is very small

$$\left[ V_{DS} < \frac{(V_{GS} - V_T)}{2} \right]$$

$$V_{DS} \approx 0$$

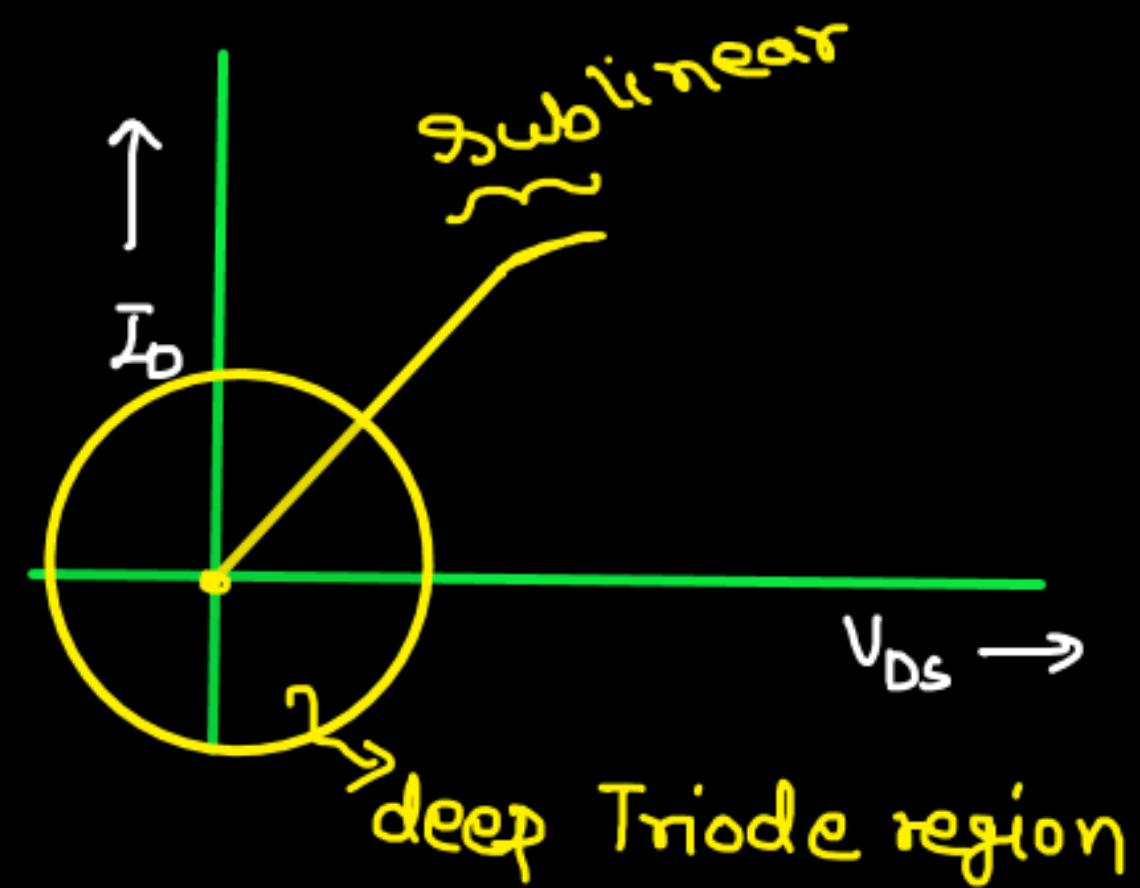


$$I_D = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T) V_{DS}$$

$$\frac{\partial I_D}{\partial V_{DS}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)$$

$$R_{on} = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)}$$

deep  
MOS in Triode region

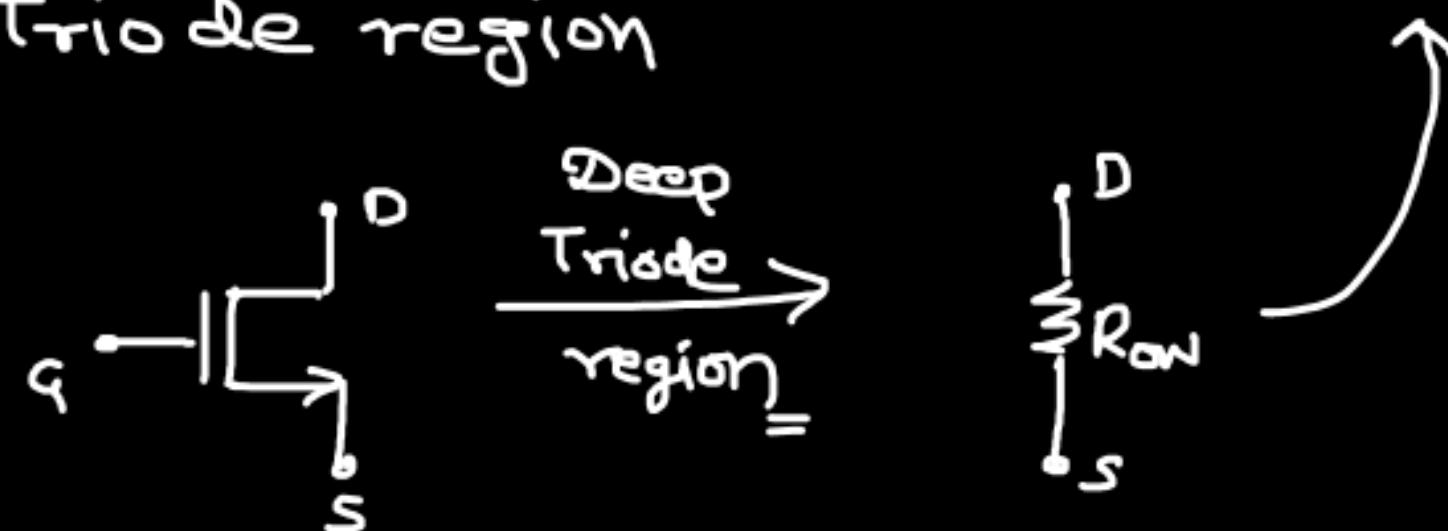


## Assignment - 5 (Fusion\_Special)

Q. 1  $V_X$  is varying from 0 to 3V.

Take  $V_{T\eta} = 0.7V = |V_{TP}|$


Plot  $I_Z v/s V_X$  and  $g_m v/s V_L$ .

(a)

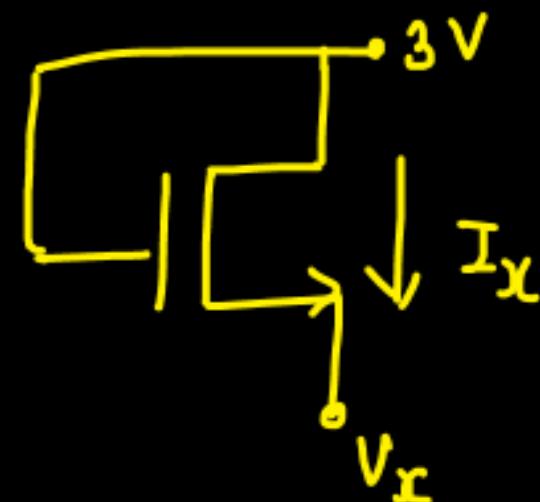

where  $g_m = \frac{\partial I_D}{\partial V_{GS}}$ ,  $\bar{g}_m = \frac{\partial I_D}{\partial V_{SG}}$

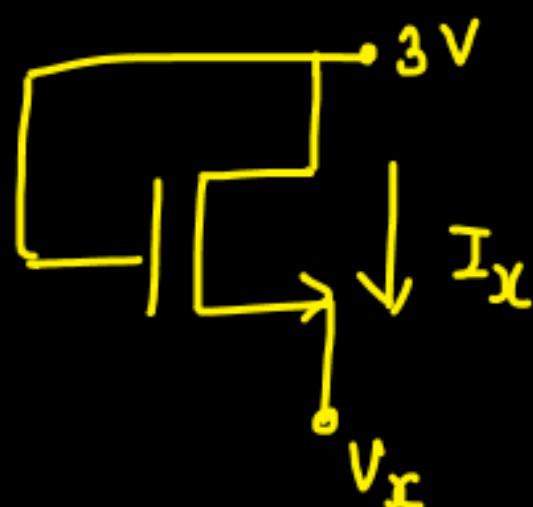$I_D \rightarrow$  Current from D to S (NMOS)  
 $\rightarrow$  Current from S to D (PMOS)



(a)

$$V_{DS} = 3 - V_x \quad \text{V}$$


$$V_{GS} = 3 - V_x$$

$$V_T = 0.7$$

$$V_{OV} = V_{GS} - V_T = 2.3 - V_x \quad \text{V}$$

$V_{DS} > V_{OV} \Rightarrow \text{always} \Rightarrow \text{sat.}$
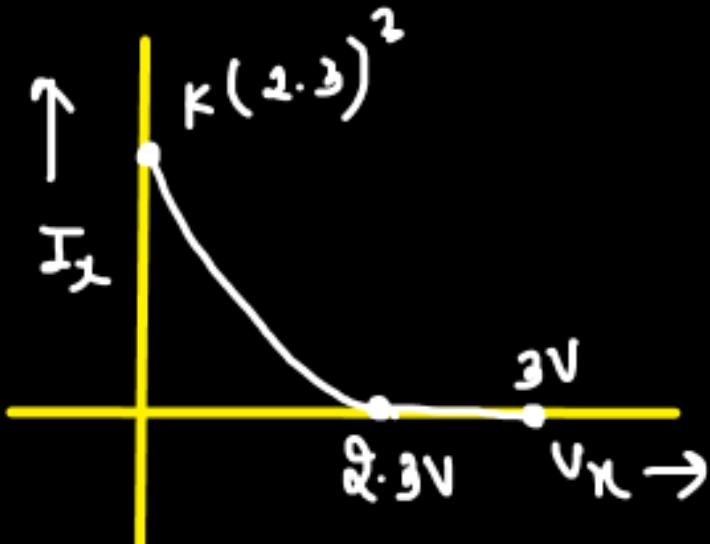
$$I_x = k (2.3 - V_x)^2 - 0 \quad \{ 0 < V_x < 2.3 \text{V} \}$$




For cut off :-

$$V_{GS} < V_T$$


$$3 - V_x < 0.7$$

$$\boxed{V_x > 2.3 \text{V}} \\ \Rightarrow I_x = 0 \text{ Amp}$$

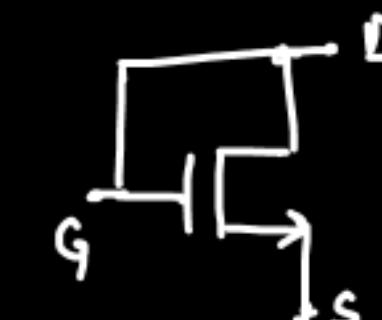If Gate and Drain are shorted, the MOS will always be in sat.



$$V_{DS} > V_{GS} - V_T$$

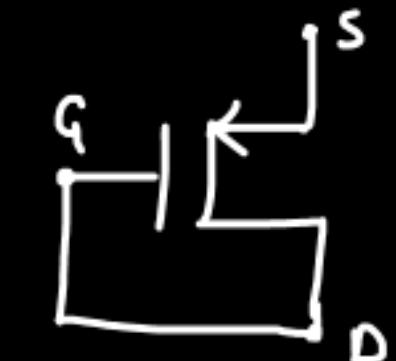

$$V_{SD} > V_{GS} - V_T$$


Talking about  $g_m$ :

MOS is always in sat.  $\{ 0 < v_x < 2 \cdot 3 \}$


$$(g_m)_{\text{sat}} = K' (v_{GS} - v_T)$$

$$g_m = K' (2 \cdot 3 - v_x)$$
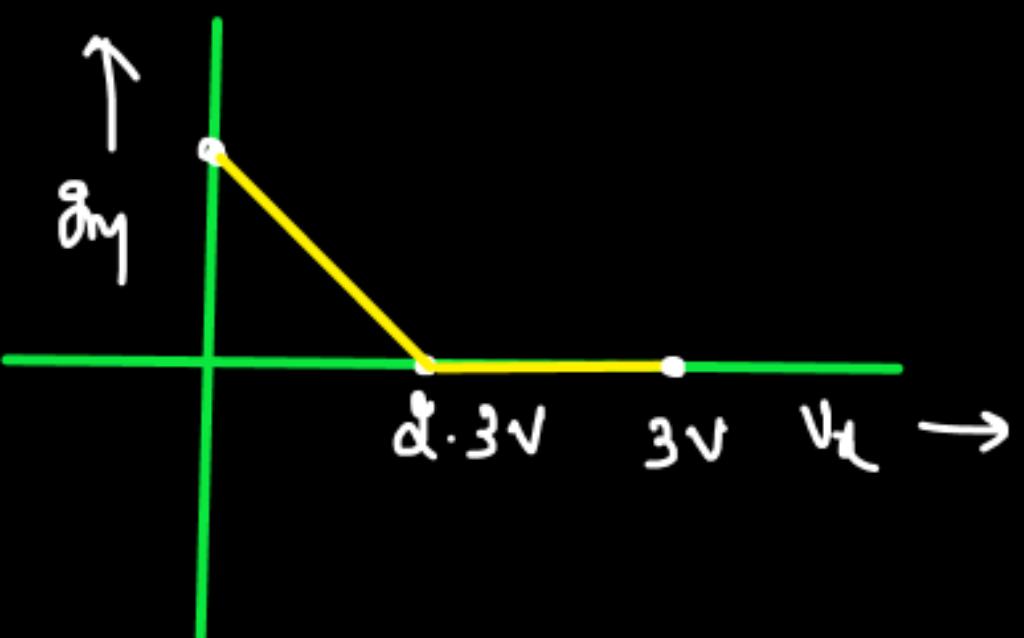
$$\text{when } v_x \geq 2 \cdot 3V \Rightarrow I_x = 0 \Rightarrow g_m = 0$$



(b)


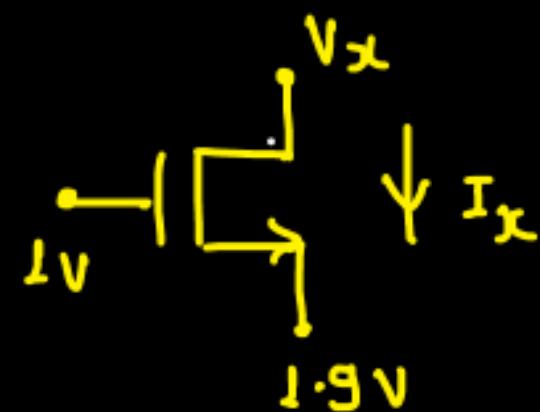


$$V_x = 0 \rightarrow 3V$$

$$V_T = 0.7V$$

→  $V_{GS} = 1 - 1.9V = -0.9V < V_T \Rightarrow I_x = 0 \text{Amp.}$  X X

$0 < V_x < 1.9V$

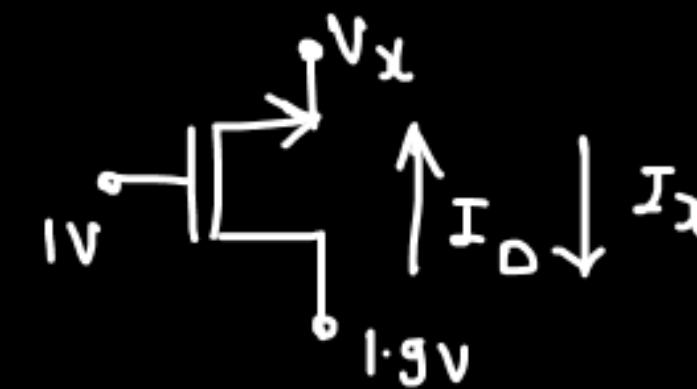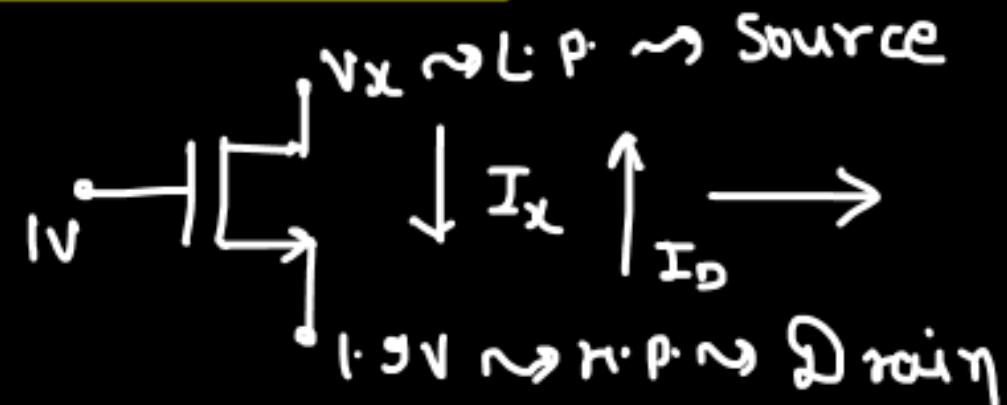

$$V_{DS} = 1.9 - V_x$$

$$V_{GS} = 1 - V_x$$

$$V_T = 0.7V$$

$$V_{OV} = 0.3 - V_x$$

For cut off  $\Rightarrow V_{GS} < V_T \Rightarrow V_{OV} < 0$

$$V_L > 0.3V$$

$\Rightarrow V_{DS} > V_{GS} - V_T \Rightarrow \text{Sat.}$

$0 < v_x < 0.3 \Rightarrow \text{Sat.}$

$$I_D = k (v_{GS} - v_T)^2$$

$$I_D = k (0.3 - v_x)^2$$

$$I_X = -k (0.3 - v_x)^2$$



$$\delta m = k' (v_{GS} - v_T)$$

$$\delta m = k' (0.3 - v_x)$$


$0.3 < v_x < 1.9V \Rightarrow \text{cut-off}$

$$I_X = 0 \text{ Amp.}$$

$$\delta m = 0$$

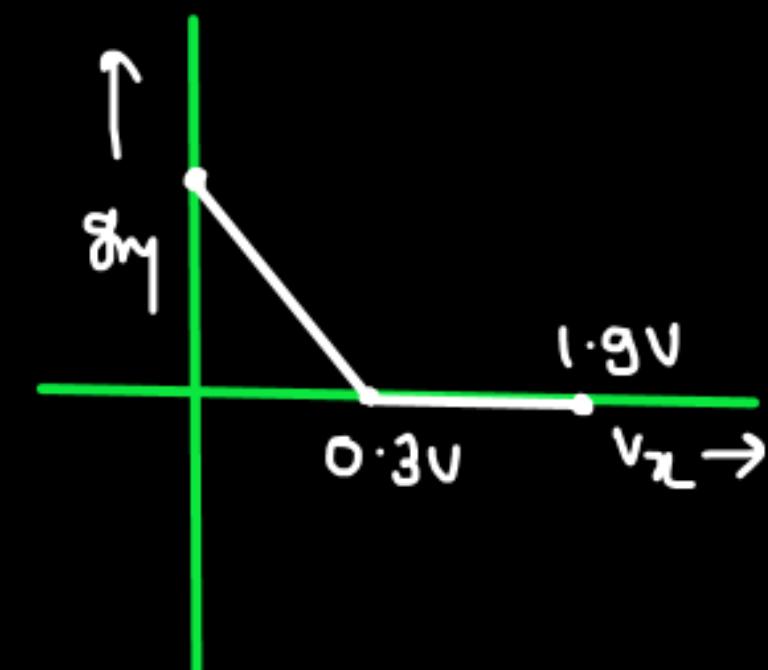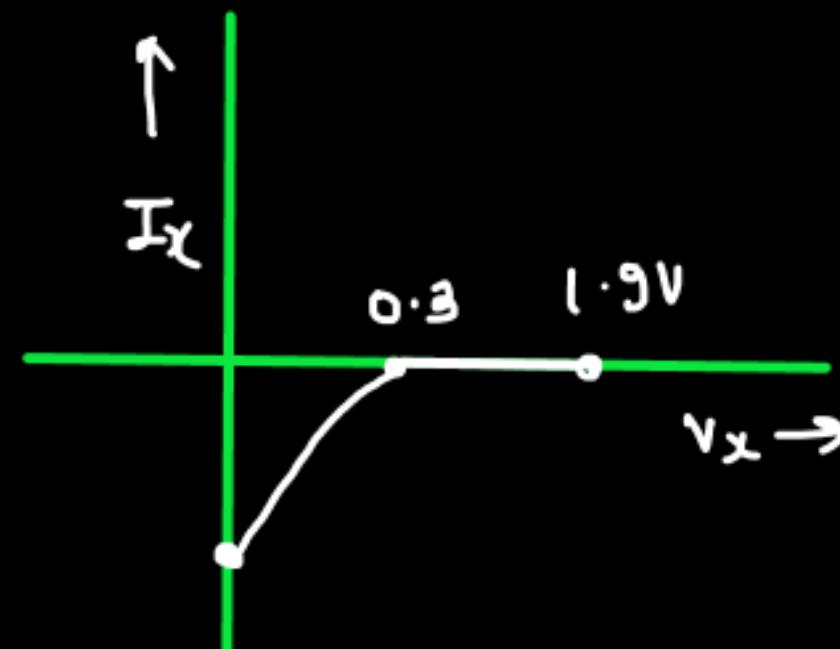



for  $V_x > 1.9V$

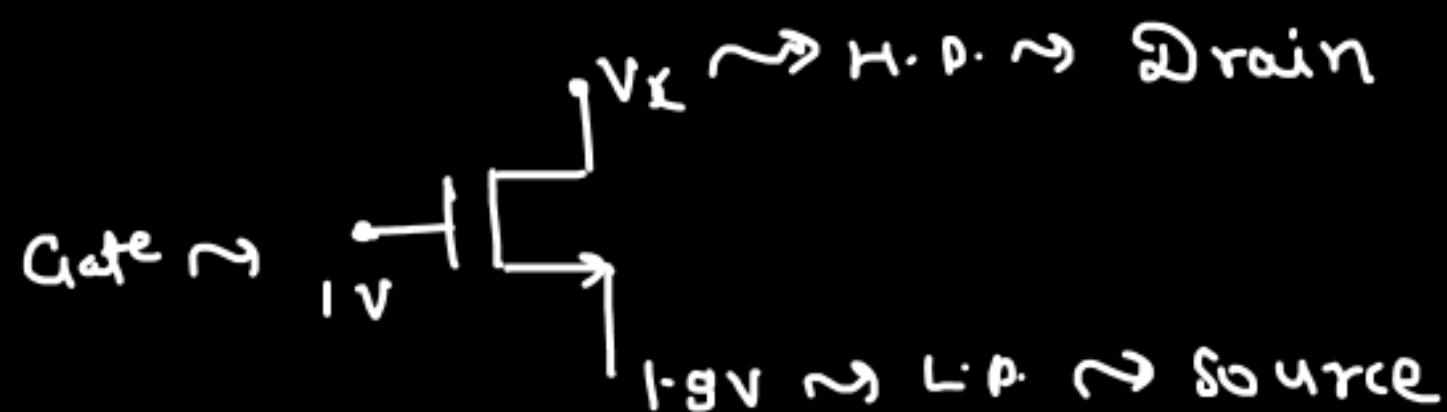


$V_{DS} = 1 - 1.9 = -0.9 < V_T \Rightarrow$  MOS is off

$$I_x = 0 \text{ Amp}$$

$$g_m = 0$$

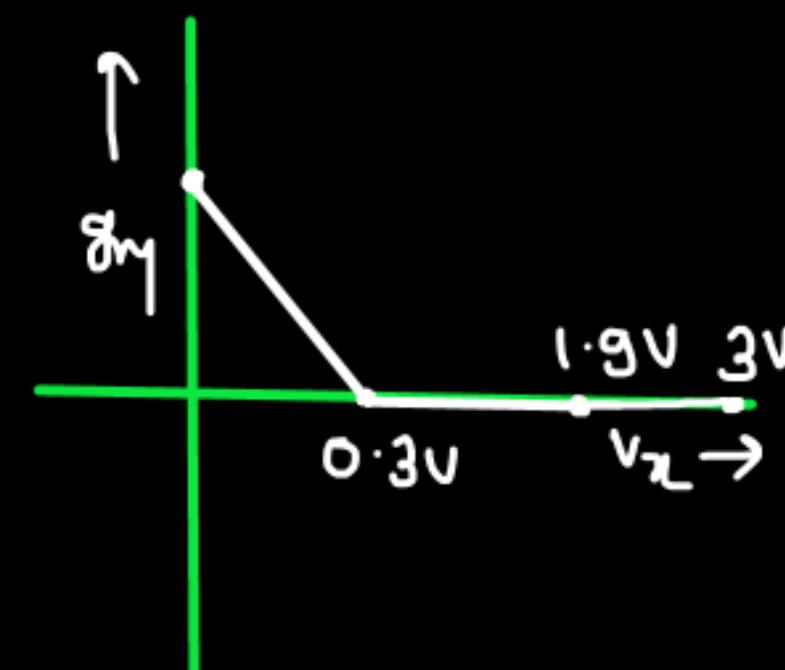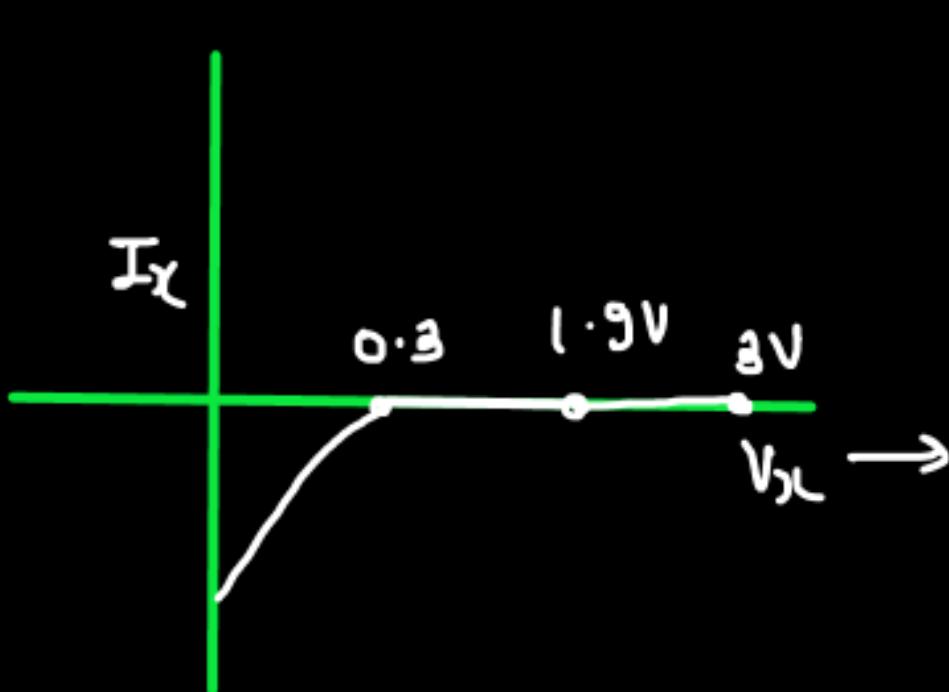


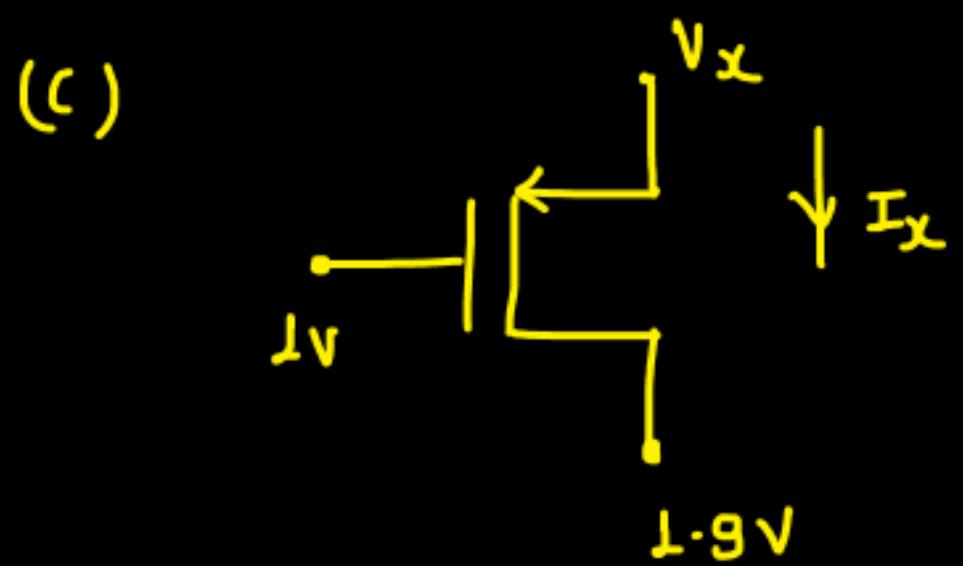

$$V_X \equiv 0 \rightarrow 3V$$

$$|V_{T_P}| = 0.7V$$

$\rightarrow 0 < V_X < 1.9V$

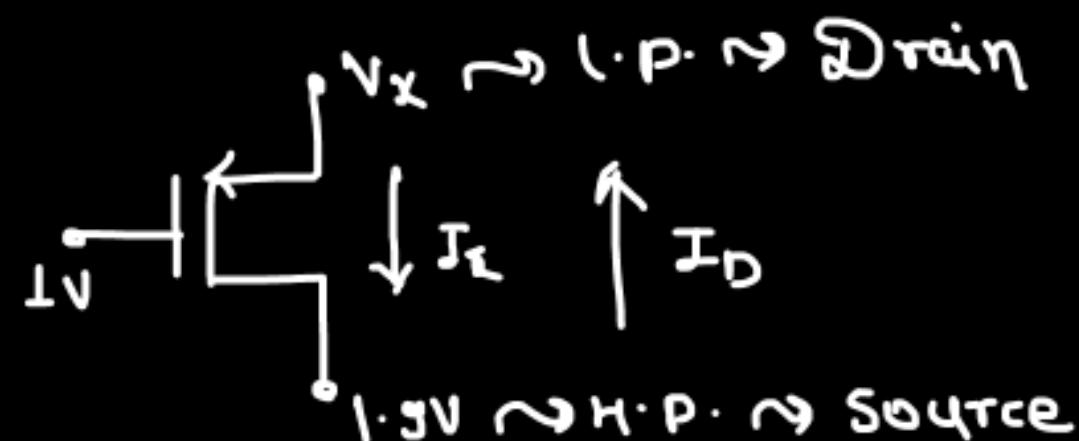

$$V_{SG} = 0.9V$$

$$V_{SD} = 1.9 - V_X$$

$$V_{OV} = 0.9 - 0.7 = 0.2V \rightarrow \text{MOS is ON}$$

for sat.

$$V_{SD} > V_{OV}$$

$$1.9 - V_X > 0.2V$$

$V_X < 1.7V$

$\Rightarrow V_X < 1.7 \Rightarrow \text{sat.}$

$1.9 > V_X > 1.7 \Rightarrow \text{linear}$

$$V_x < 1.7V$$

:-

$$I_D = k' (V_{SG} - V_T)^2$$

$$I_D = k' (0.2)^2$$

$$I_L = -I_D$$

$$I_L = -k' (0.2)^2 \sim \text{constant}$$

$$g_m = k (V_{SG} - V_T)$$

$$g_m = k (0.2) \sim \text{const.}$$

$$1.9V < V_x < 1.7V$$



:-

$$I_D = k'' [(V_{SG} - V_T) V_{SD} - \frac{V_{SD}^2}{2}]$$


$$I_L = -k'' [0.2 (1.9 - V_x) - \frac{(1.9 - V_x)^2}{2}]$$

$$(g_m)_{\text{linear}} = k''' \times V_{SD}$$

$$g_m = k''' \times (1.9 - V_x)$$

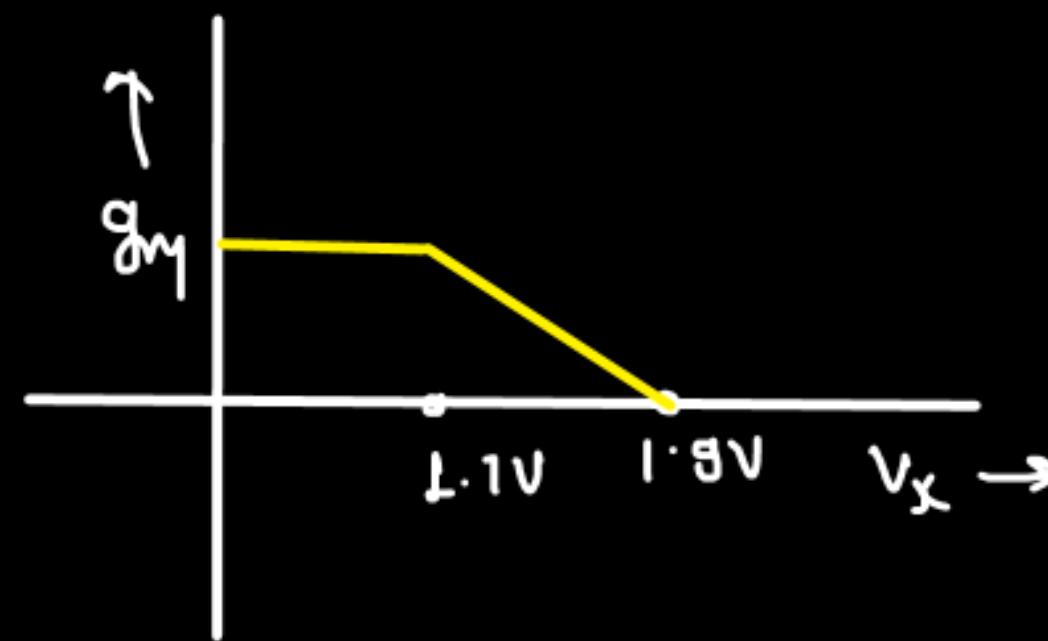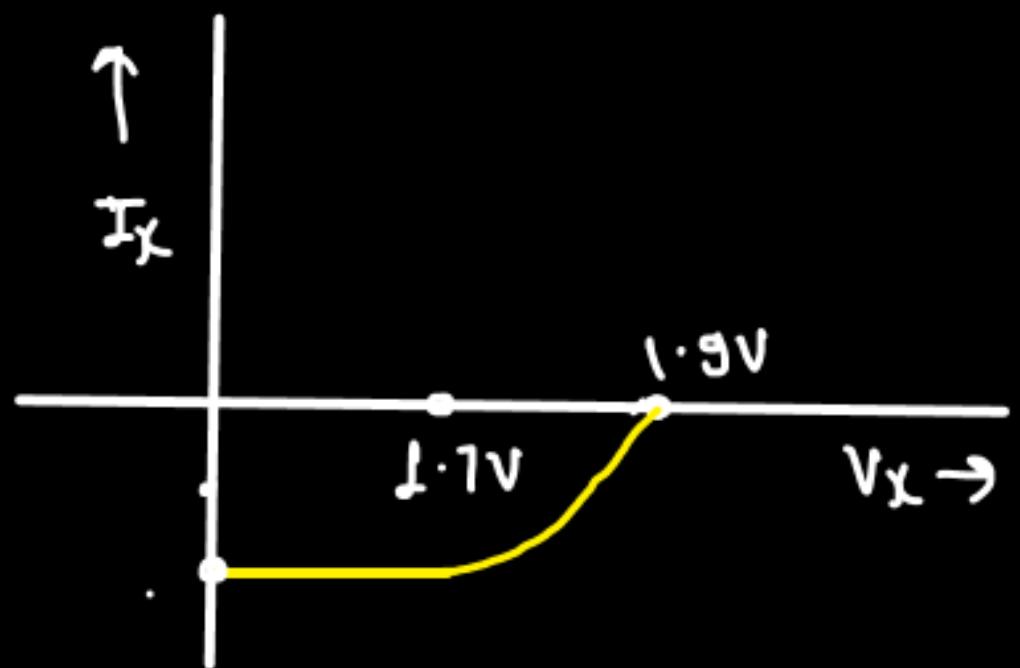

For  $V_x > 1.5V$

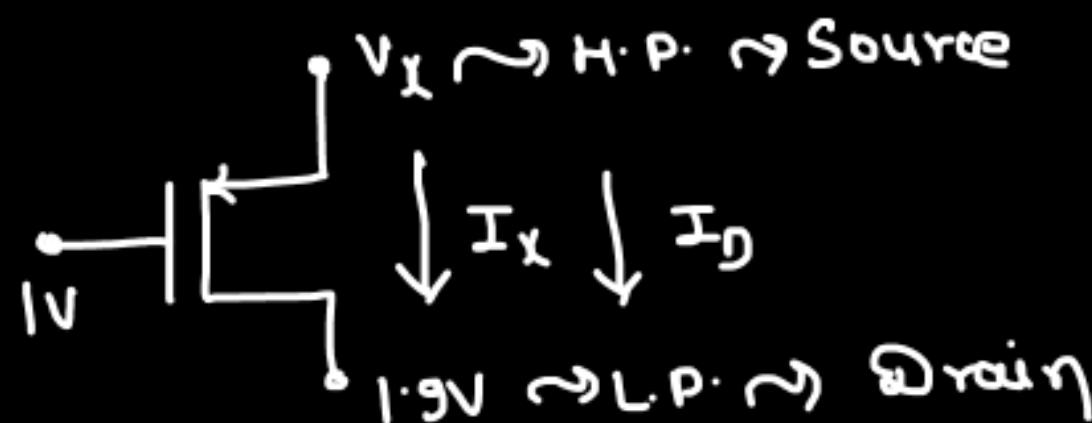

$$V_{SD} = V_x - 1.9V$$

$$V_{SG} = V_x - 1$$

$$V_T = 0.7V$$



$$V_{DS} = V_x - 1.1V$$

$\Rightarrow V_{SD} < V_{DS} \Rightarrow$  linear region


$$I_D = K \left[ (V_{SG} - V_T) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$I_D = I_L = K \left[ (V_L - 1.7) (V_L - 1.9) - \frac{(V_L - 1.9)^2}{2} \right]$$

$$\delta V = K' [V_L - 1.9]$$

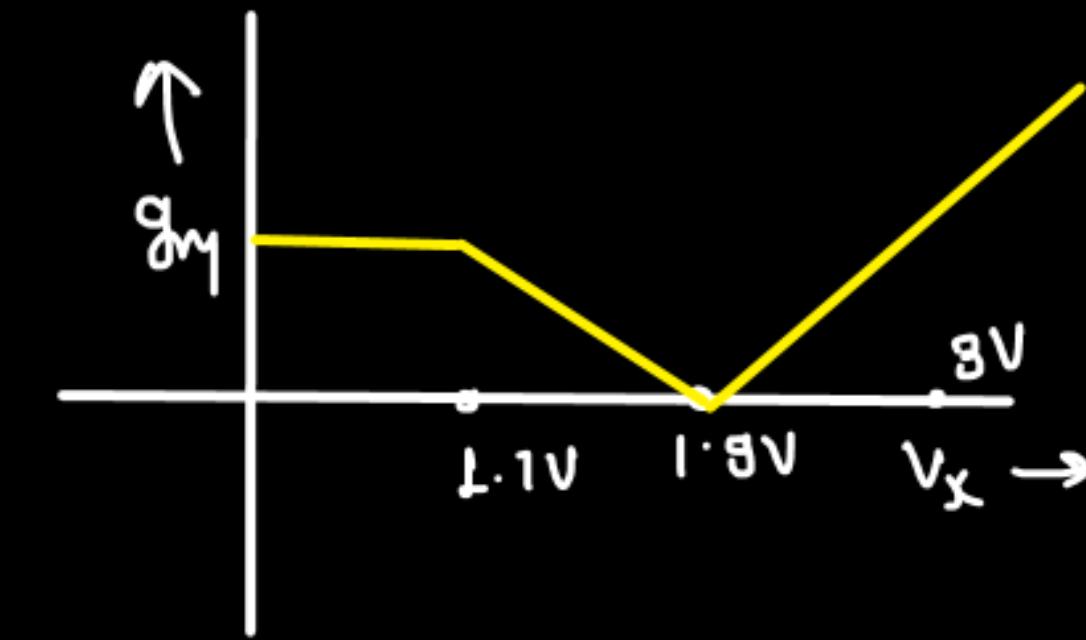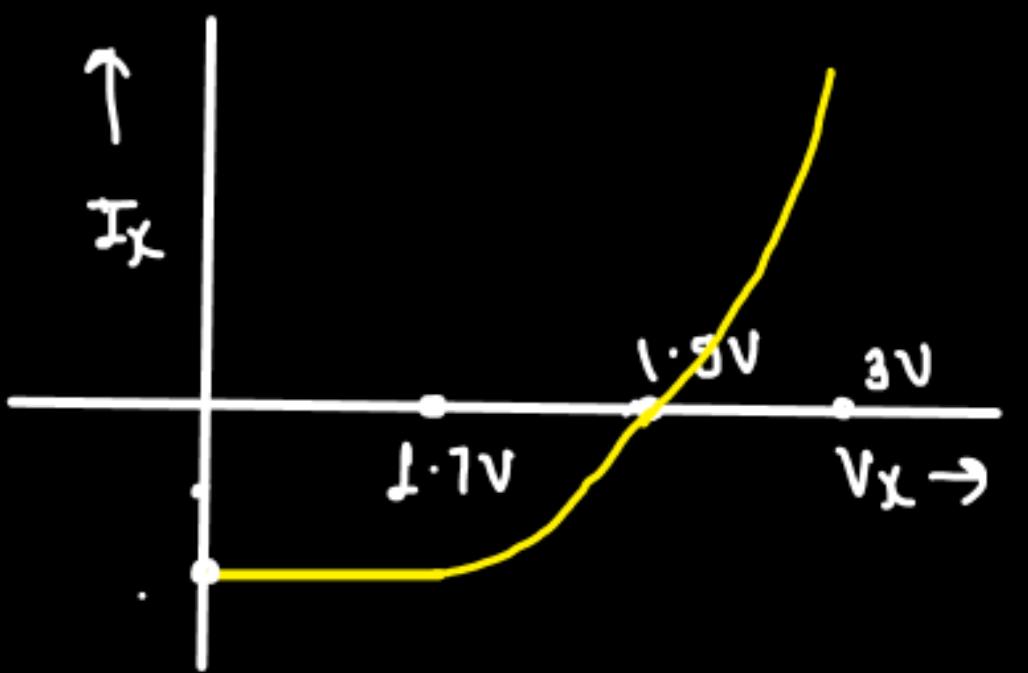

Q.

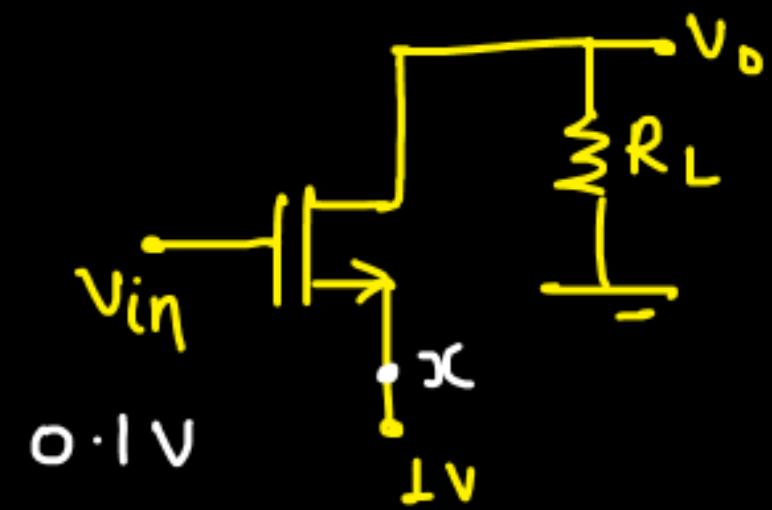

$$V_{in} \equiv 0 \rightarrow 3V$$

$$V_T = 0.7V$$

Plot  $V_o$  v/s  $V_{in}$ .

Given  $R_L \rightarrow$  very low

Find max value of  $V_o$ .


For  $V_i < 1.7V \Rightarrow$  MOS off XX

initially, Mos current = 0 A  $\Rightarrow V_o = 0V$

$\Rightarrow V_o \rightarrow$  Source

$V_s \rightarrow$  Drain

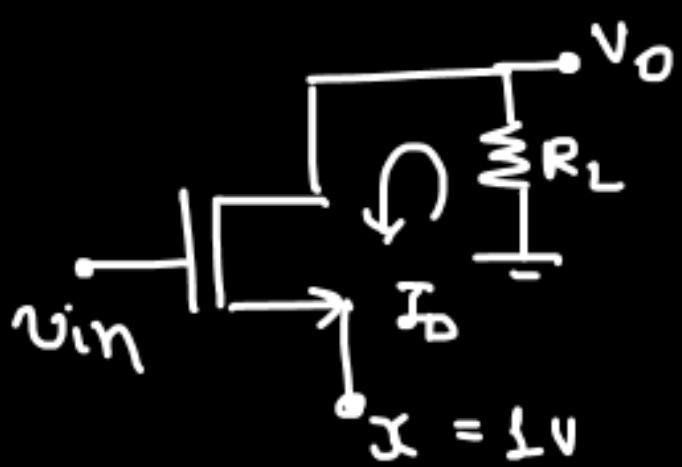Let's assume, potential  $x$  is source  $\Rightarrow V_0 = -ve$



↓


But  $V_S = V_x = Lv$

and  $V_0 = V_D = -ve$


↓

NOT POSSIBLE

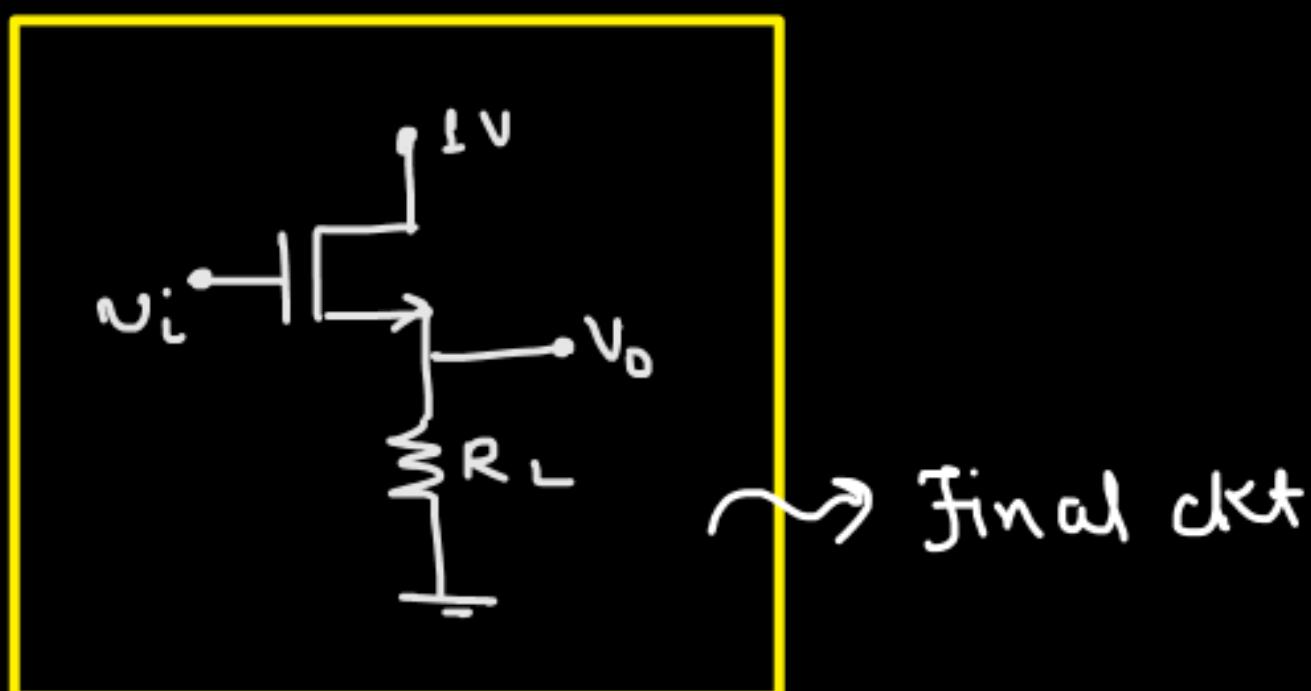$\Rightarrow x$  will always be drawn  
 $v_0$  will always be source



final ckt

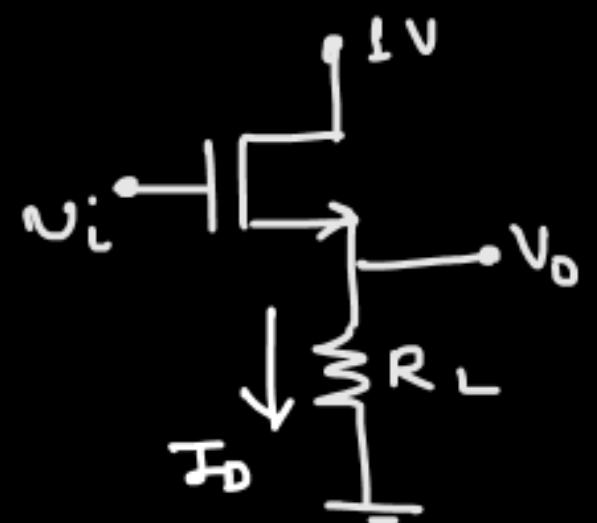

initially,  $V_o = 0V$

$V_{in} < V_T \Rightarrow V_{in} < 0.7V \Rightarrow \text{MOS OFF}$   
 $[V_{GS} < V_T]$

when  $V_{in} = 0.7V$

$\Rightarrow \text{MOS is ON}$

when MOS just turns on  $\Rightarrow I_D$  is very small

$$V_o = I_D R_L = \text{very small}$$

$$V_{DS} = 1 - V_o$$

$\Rightarrow$  for sat.

$$1 - V_o > V_i - 0.7 - V_o$$

$$V_{GS} = V_i - V_o$$

$$V_{DS} = V_i - 0.7 - V_o$$

$$V_i < 1.7V \Rightarrow \text{sat.}$$

$$V_i > 1.7V \Rightarrow \text{linear}$$

for  $0 < V_i < 1.7V$


$$I_D = k [V_i - 0.7 - V_0]^2$$

$$V_0 = I_D R_L$$

$$V_0 = k [V_i - 0.7 - V_0]^2 R_L$$

if we increase  $V_i \Rightarrow I \uparrow \Rightarrow V_0 \uparrow$


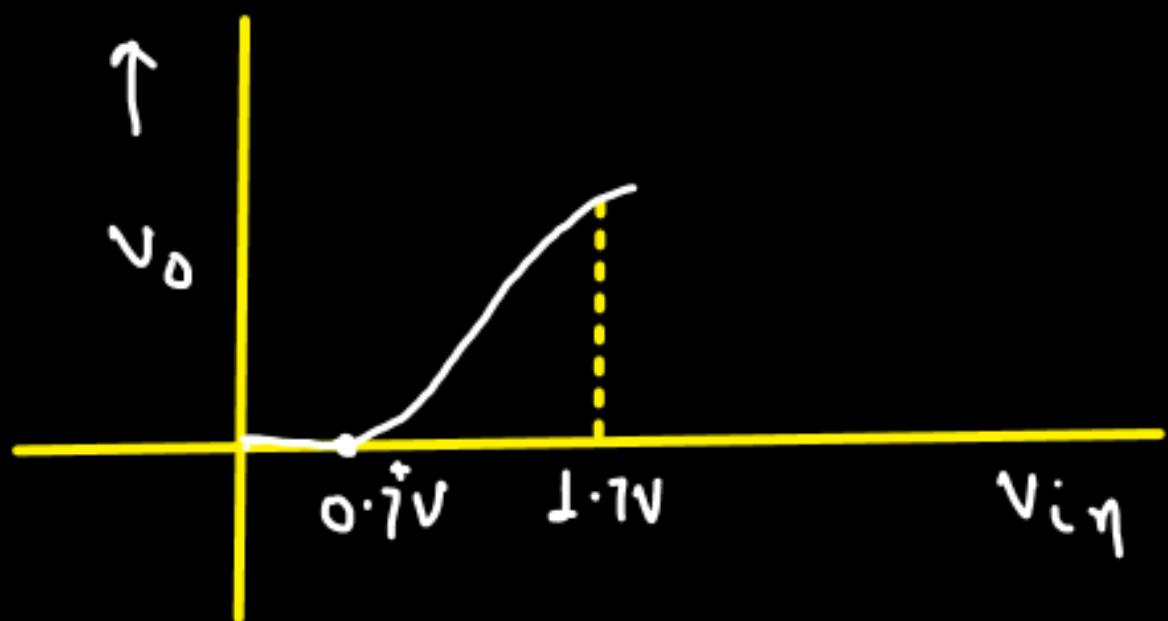
But  $V_0$  will not increase as much as  $V_i$ .




For  $V_i > 1.7V \Rightarrow$  diode Triode

$$I_D = K \left[ (V_i - 0.7 - V_0) (1 - V_0) - \frac{(1 - V_0)^2}{2} \right]$$

$$V_0 = I_D R_L$$

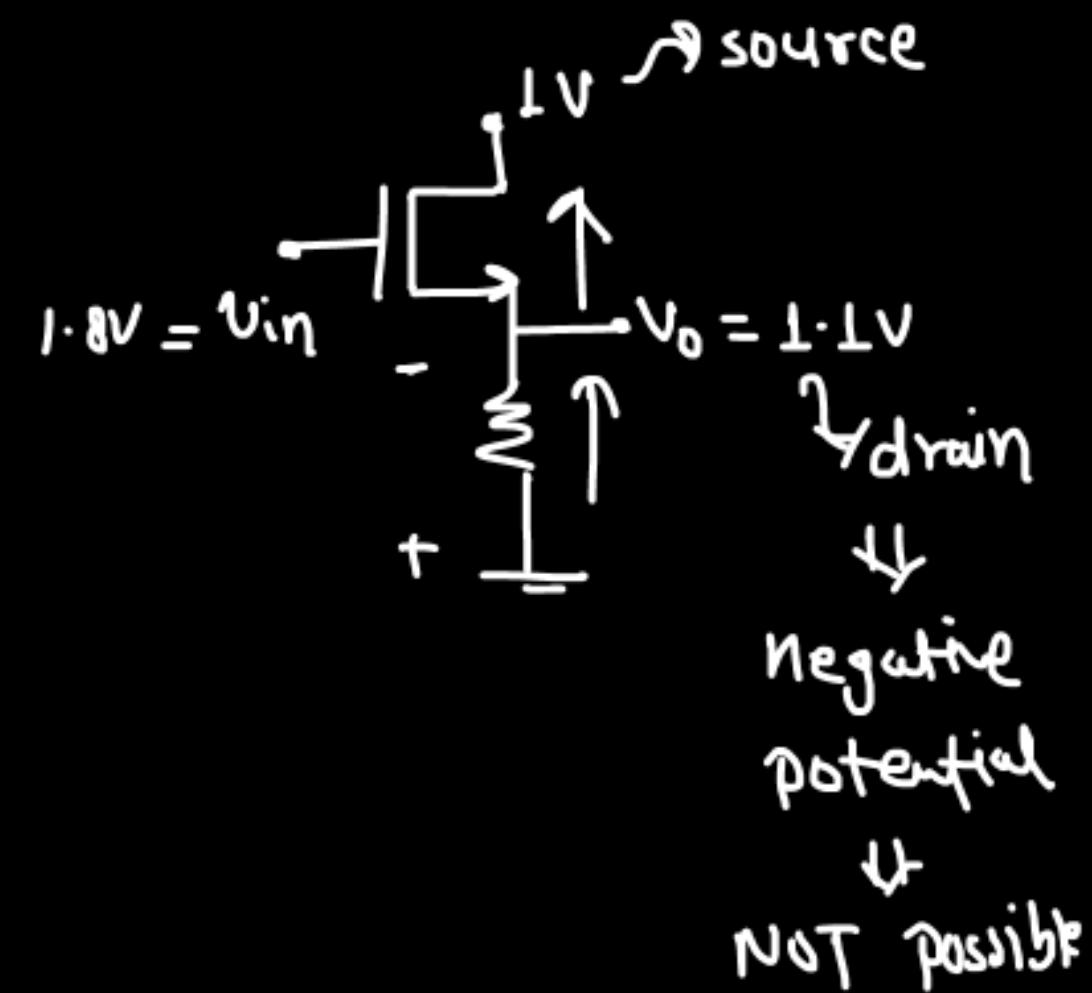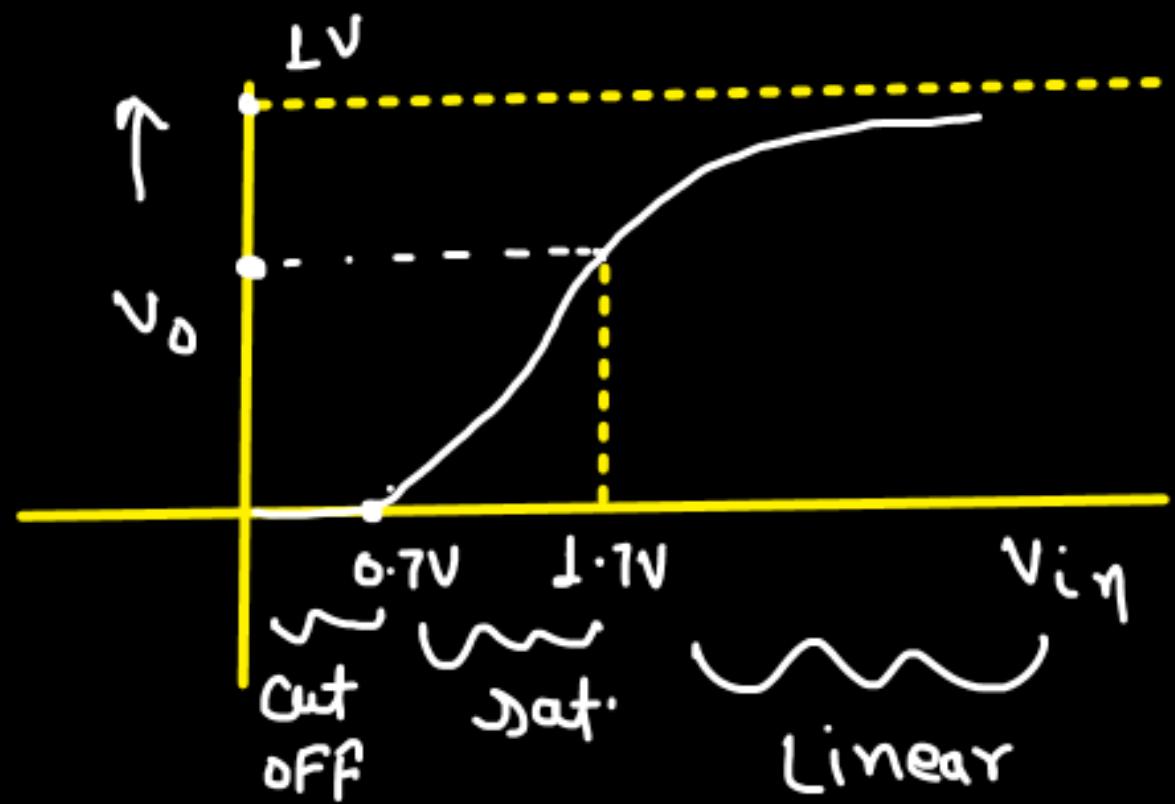

Q.

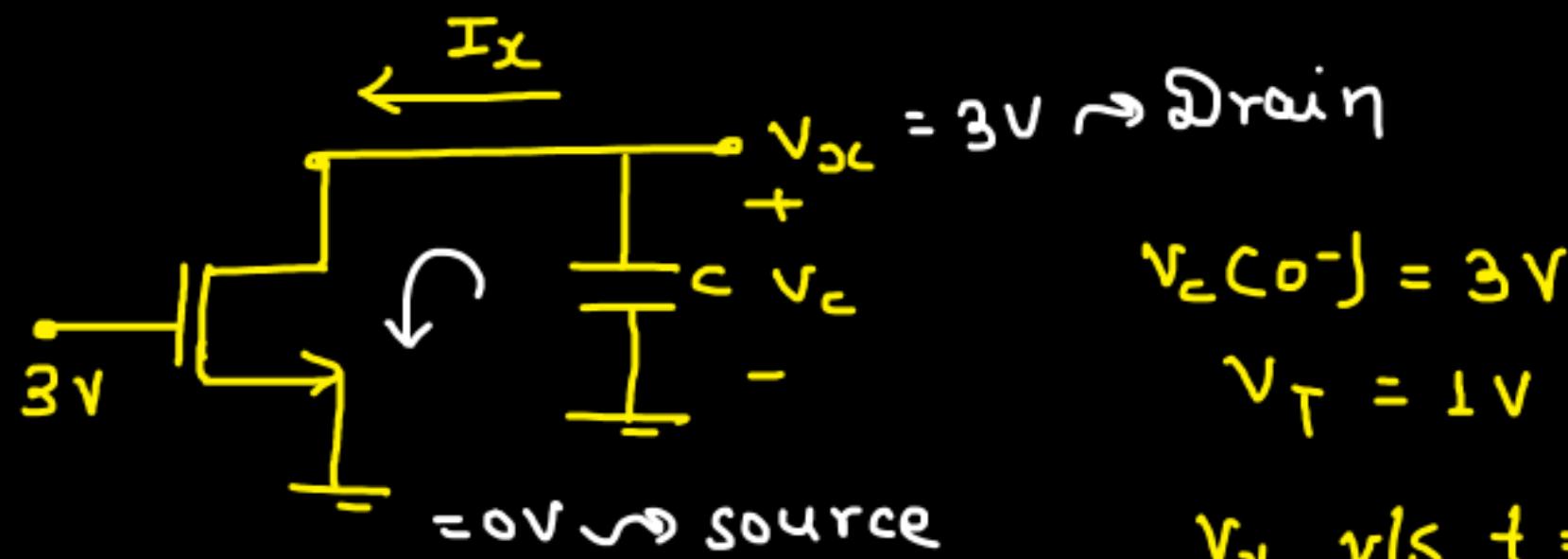

$$V_G(0^+) = 3V$$

$$V_T = 1V$$

$$V_{DS} \text{ v/s } t = ?$$

$$I_D \text{ v/s } t = ?$$

$$\rightarrow V_{GS} = 3V, V_{DS} = V_D = V_G$$

$$V_T = 1V$$

@  $t=0^+$


$$V_{DS} = 2V$$

$$V_{DS} = 3$$

@  $t=0^+$ ,  $V_{DS} > V_{DS}$   $\Rightarrow$  Sat. region



$$I_D = K[2]^2$$

@  $t=0^+$

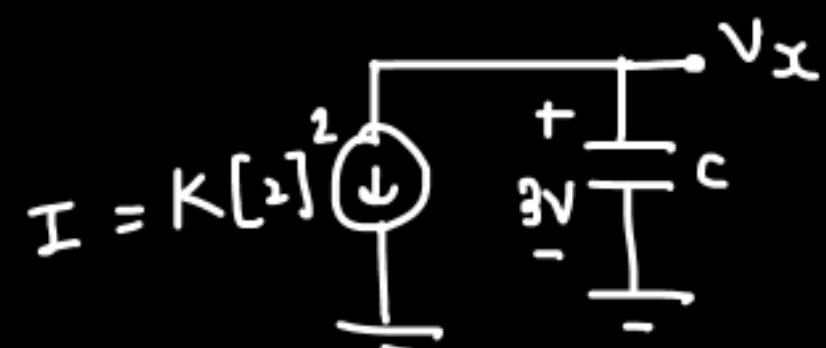

$\Rightarrow$  cap. will start discharging linearly.

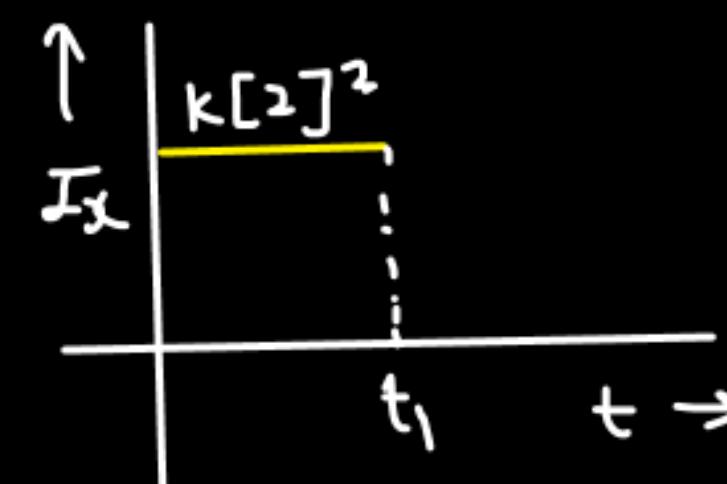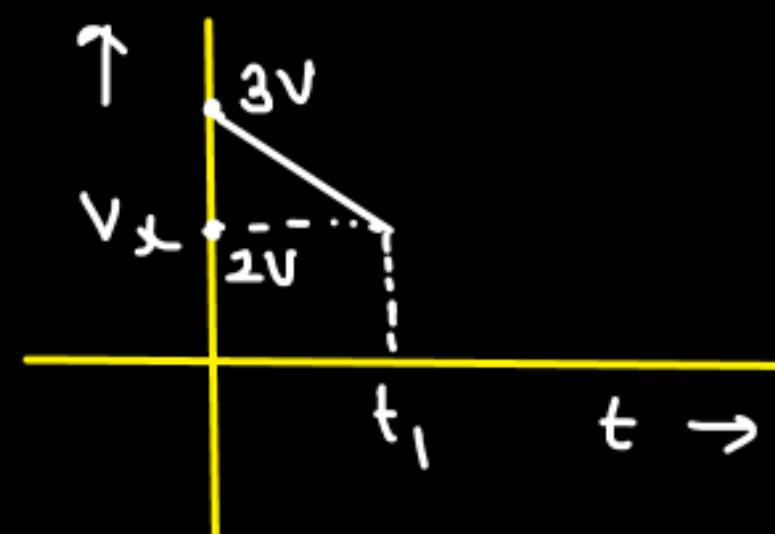
$$V_x = V_c(t) = 3 - \frac{1}{C} \int I \cdot dt \\ = 3 - \frac{I}{C} t$$



When  $V_{DS}$  or  $V_x < 2$

$\Rightarrow V_{DS} < V_{DN} \Rightarrow$  MOS will go into Triode  $\Rightarrow$  MOS acts as resistance


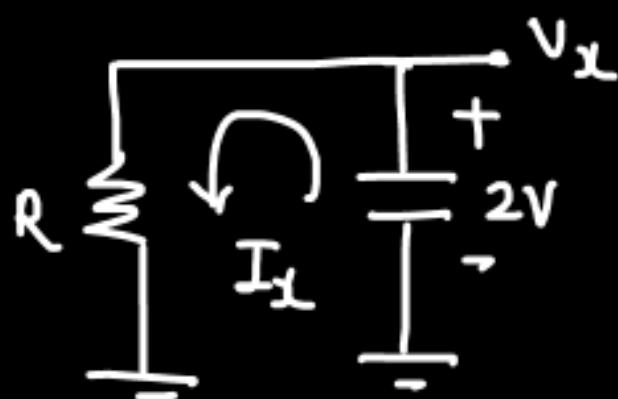
For  $t > t_1 \Rightarrow$  MOS goes into linear region.




$$\frac{1}{R_s} = \sum_s^D R_{DN} = R$$

$$I_x = k \left[ 2 \cdot V_x - \frac{V_x^2}{2} \right]$$

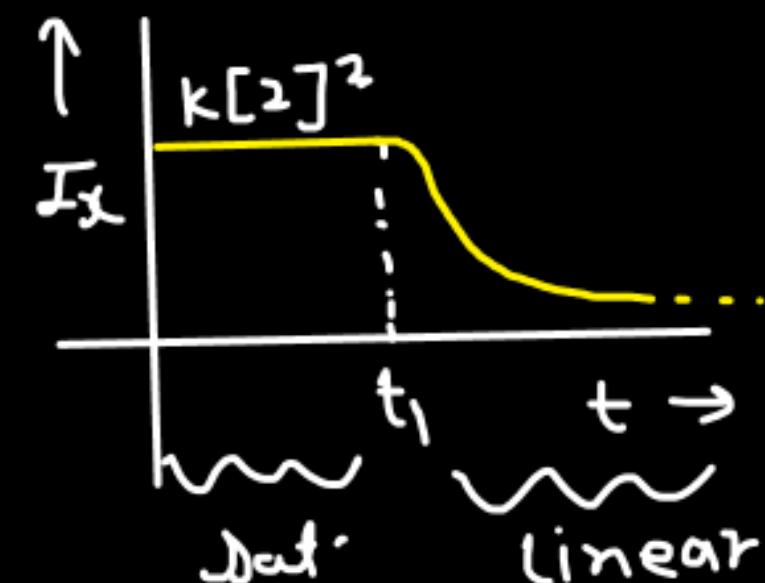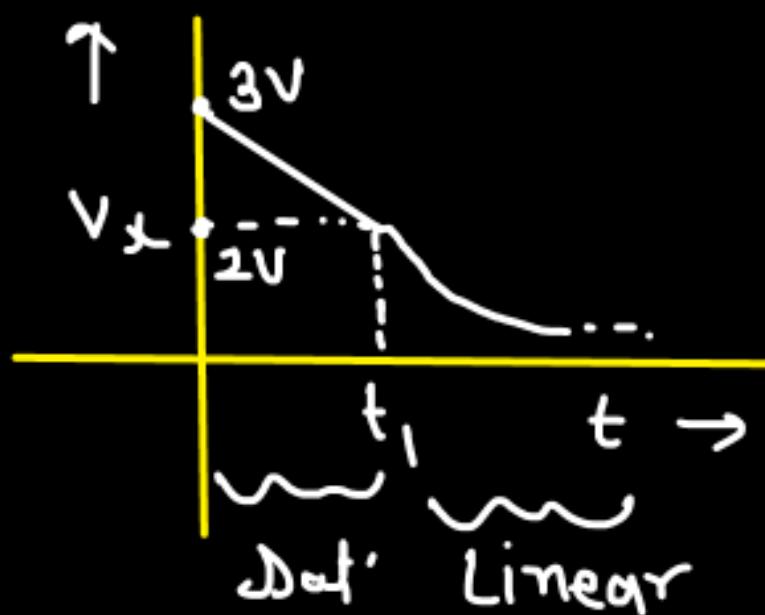$\Rightarrow$  Both  $V_x$  and  $I_x$  will go down to zero



Q.  
★★

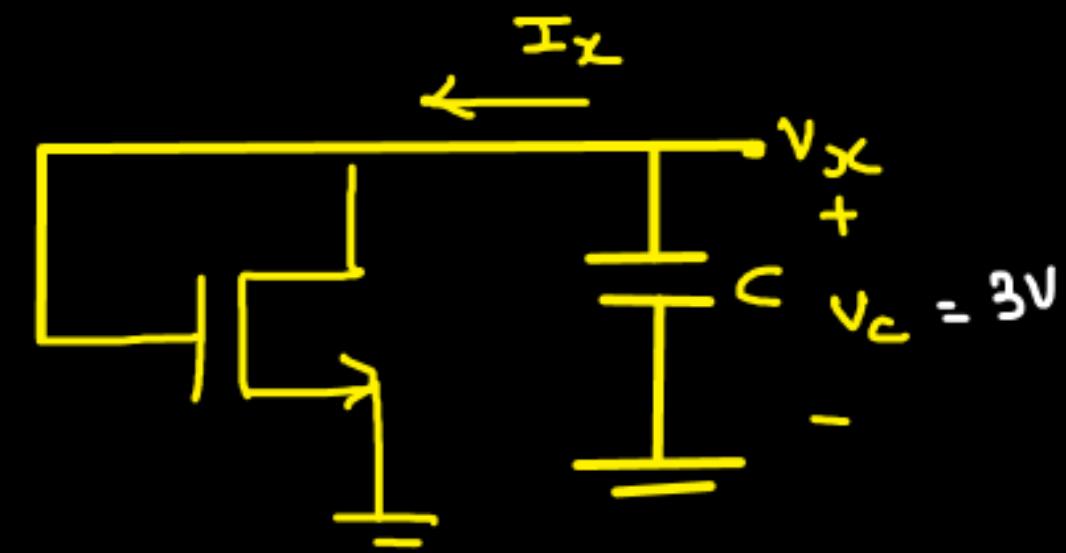

$$V_T = 1V$$

$$V_c(0) = 3V$$

$$V_x \text{ v/s } t = ?$$

$$I_x \text{ v/s } t = ?$$

Find min. value of  $V_x$


→ D and G are shorted  $\Rightarrow$  MOS always be in sat.

$$V_{GS} = V_x$$

$$V_{DS} = V_x \quad \Rightarrow \text{sat.}$$

$$V_{OV} = V_x - 1$$


$$I_x = k [V_x - 1]^2$$

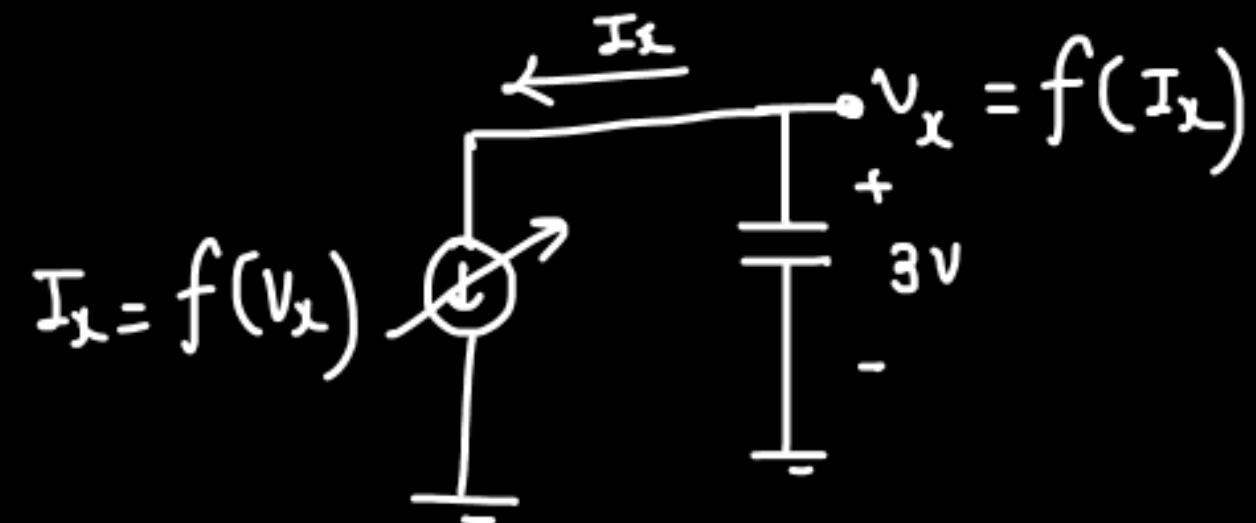


$$V_x = 3 - \frac{1}{C} \int |I_x(t)| dt$$

Here,  $V_x$  is going down. When  $V_{GS} < V_T \Rightarrow$  MOS will be off

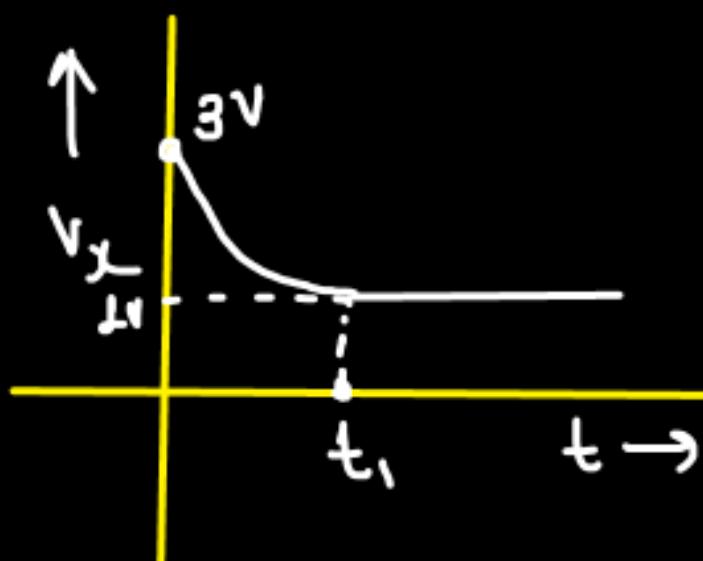$V_x < 1 \Rightarrow$  No current ( $I_x = 0$ )  
 ↓  
 NO further discharging



Q.

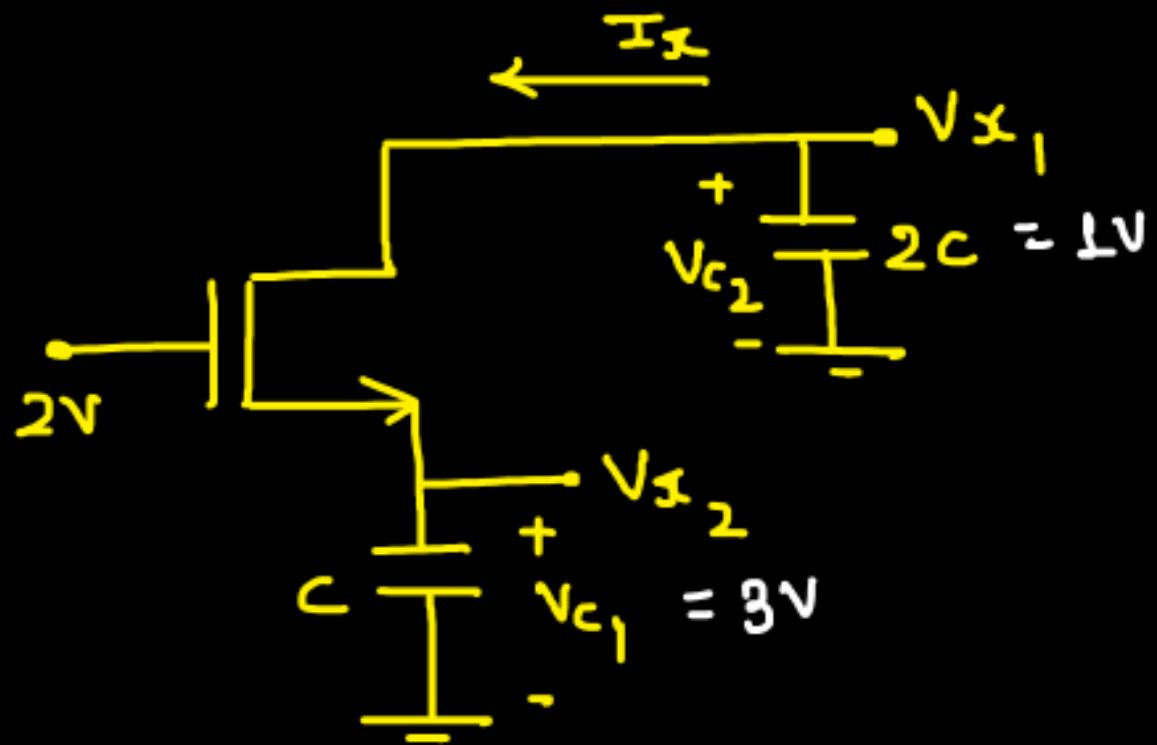

$$V_{C_1}(0^+) = 3V$$

$$V_{C_2}(0^+) = 1V$$

$$V_T = 0.7V$$

$$V_{X_1} \text{ v/s } t = ?$$

$$V_{X_2} \text{ v/s } t = ?$$

$$I_X \text{ v/s } t = ?$$

@  $t=0^+$

$$V_{X_2} = 3V, V_{X_1} = 1V$$

$\downarrow$


H.P.

$\downarrow$   
Drain

$\downarrow$

L.P.

$\downarrow$   
Source

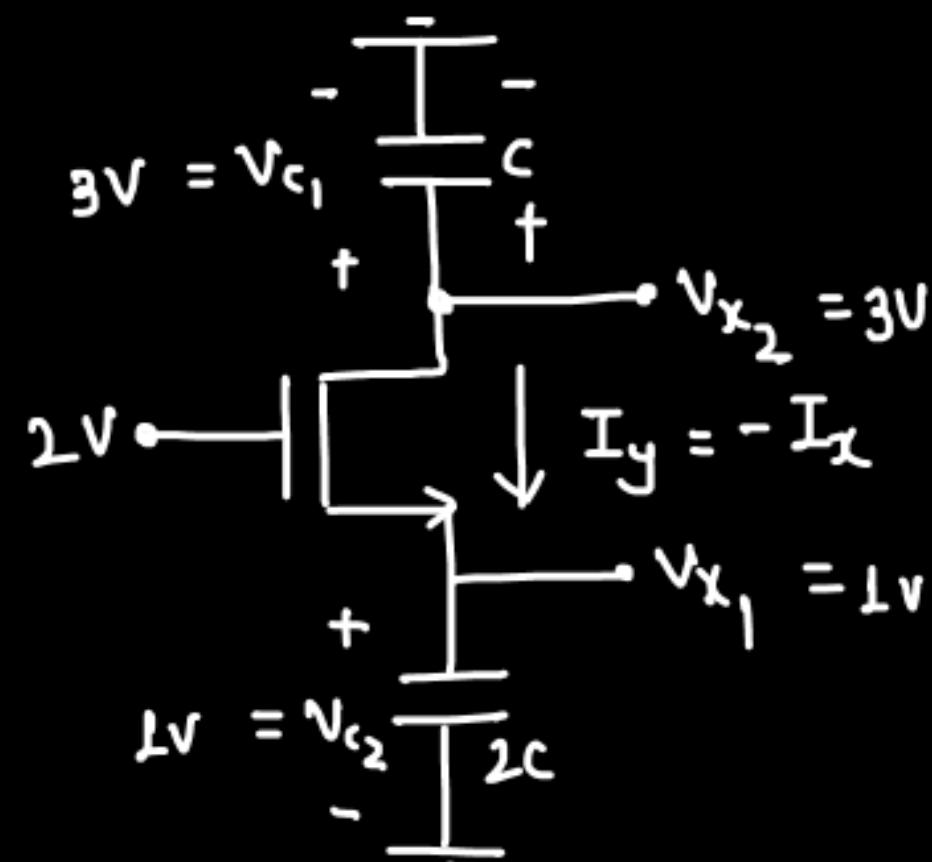

$C \rightarrow$  discharged

$2C \rightarrow$  charged

$$V_{DS} = 1V \Rightarrow V_{DS} = 0.3$$

$$V_T = 0.7V$$

$$V_{DS} = 2V$$

$$\Rightarrow V_{DS} > V_{DS} \Rightarrow \text{sat.}$$

$$I_y = f(v_{x_1})$$

$\Rightarrow$  Cap.  $2C$  can charge upto  $1.3V$  only.

Because, if  $2C$  charges above  $1.3V \Rightarrow$  MOS will be off

$$V_{x_1}(\text{ss}) = 1.3V$$

when  $V_{x_1}$  was increasing from 1V to 1.3V

↳

There was  $I_y$  current flowing out  
of cap. C

Both cap. C and  $2C$  are having same current

$$I_C = I_{2C}$$

$$\frac{\Delta Q_C}{\Delta t} = \frac{\Delta Q_{2C}}{\Delta t}$$

$$\Delta Q_C = \Delta Q_{2C}$$

$$C(\Delta V_C) = 2C(1.3 - 1)$$




$$\boxed{\Delta V_C = 0.6V}$$

⇒ change in capacitor C voltage would be 0.6V

Cap. C will discharge from 3V to 2.4V


$V_{x_2}$  will decay down from 3V to 2.4V

$$V_{C_1} (\text{S.S.}) = 2.4V$$

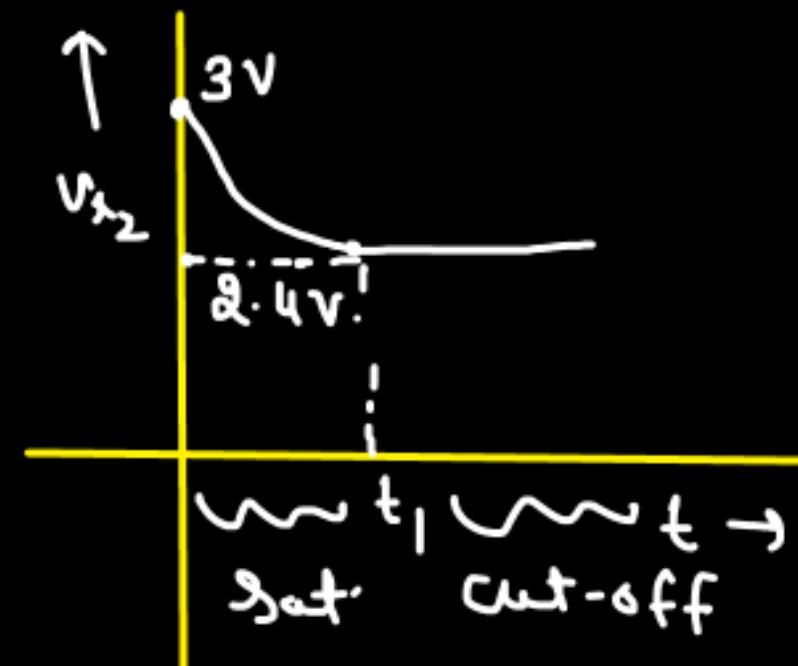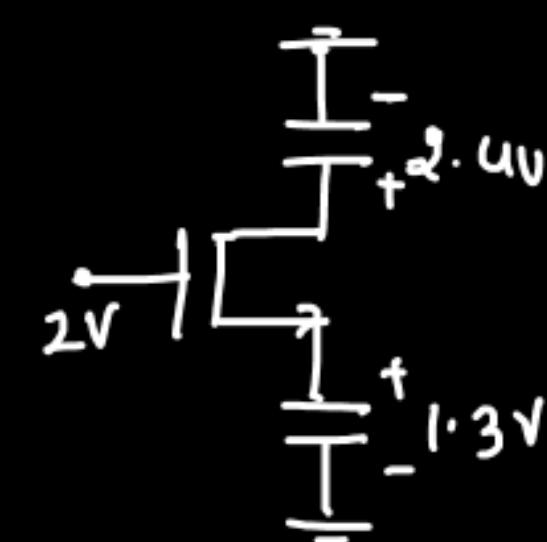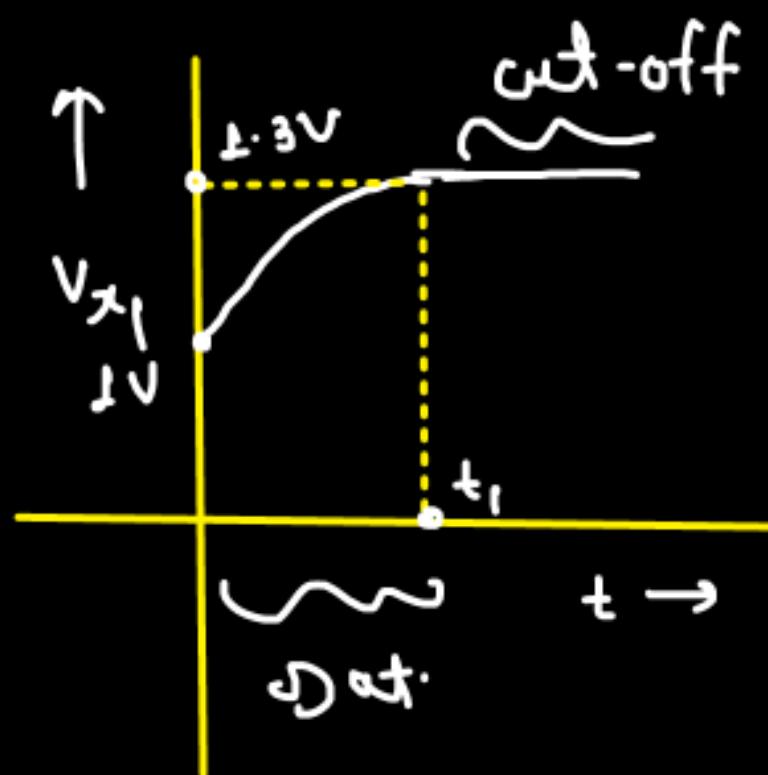


$$\begin{aligned} V_{DS} &= 1.1V \\ V_{GS} &= 0.7V \\ V_{OV} &< 0 \end{aligned} \quad \Rightarrow \text{sat.}$$

$V_{DS} > 0V$

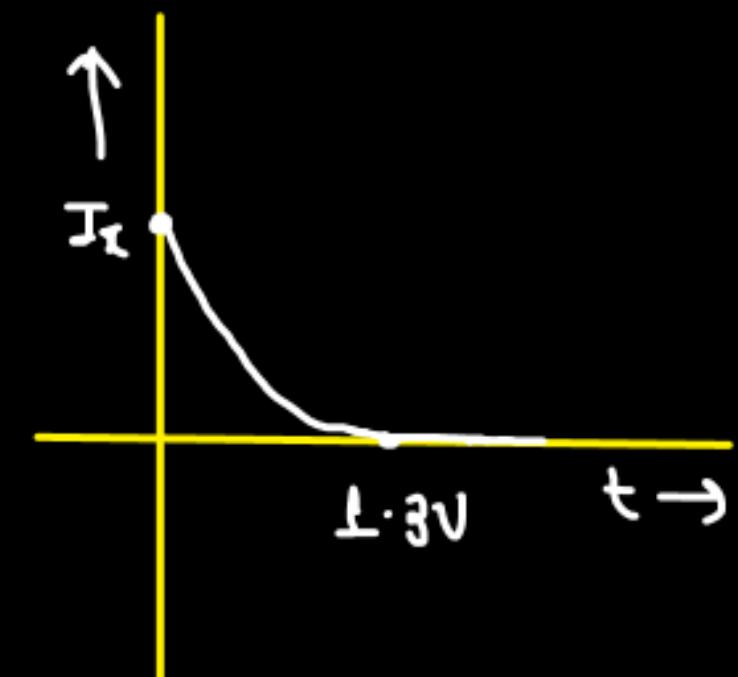

Q.

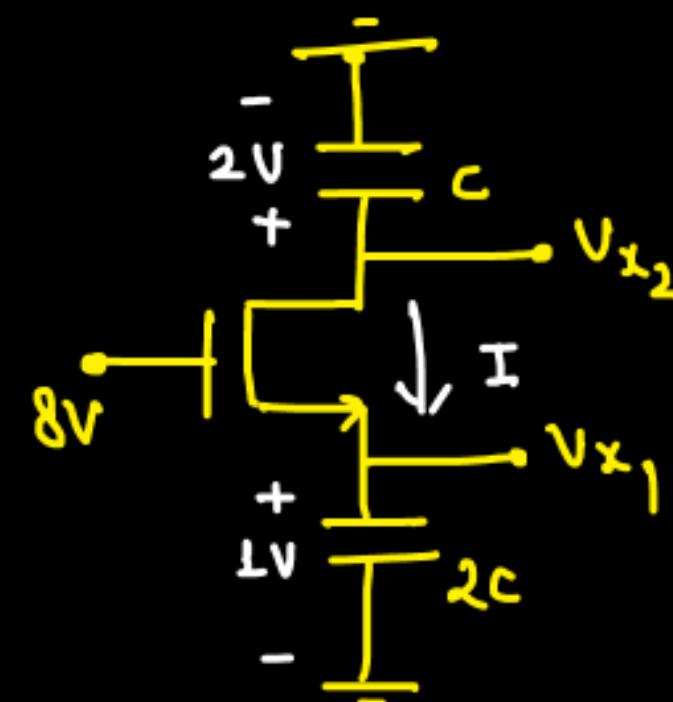

$$v_{x_2}(t=0^-) = 2V$$

$$v_{x_1}(t=0^-) = LV$$

$$v_T = Lv$$

Find s.s.  $v_{x_1}$  and  $v_{x_2} = ?$

$$v_{x_1}(s.s.) = 7V \quad \{ 1 \rightarrow 7 \}$$


$$\partial C(6V) = C(\Delta v_c)$$

$$\Delta v_c = 12V$$

C is discharging

$$v_{x_2}(s.s.) = 2 - 12 = -10V$$
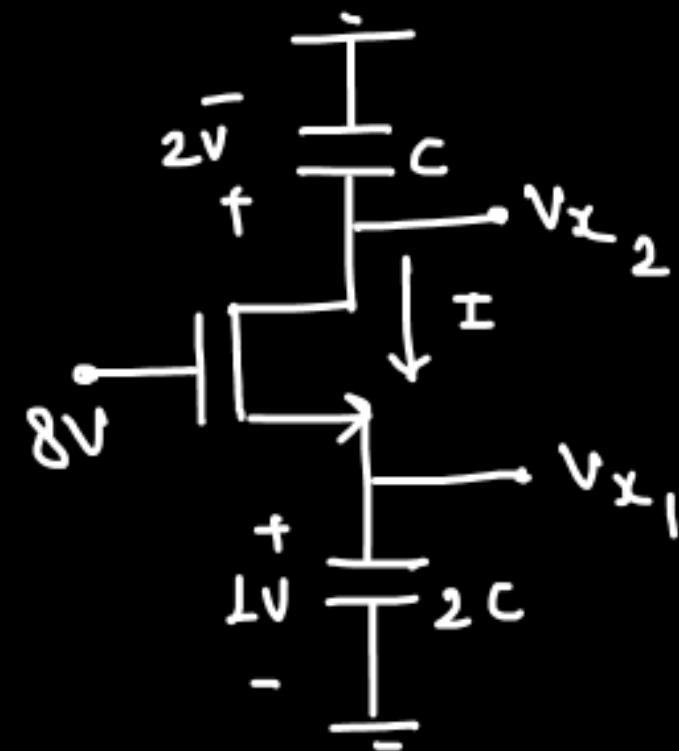
$$\Rightarrow v_{DS} = -10 - 7 = -17V \times$$



$C \rightarrow$  discharging  
 $2C \rightarrow$  charging

$$I_{2C} = I_C$$

$$\Delta Q_{2C} = \Delta Q_C$$

$$2C(\Delta V_{2C}) = C(\Delta V_C)$$

$$\Delta V_C = 2 \Delta V_{2C}$$

Let  $\Delta V_{2C} = x \Rightarrow 2C$  is gaining  $x$  voltage

$$V_{x1}(\text{ss}) = L + x$$

if 2c gains x voltage  $\Rightarrow$  c loses  $2x$  voltage

$$V_{X_2}(\text{S.S.}) = 2 - 2x$$

@ S.S.  $\Rightarrow V_{DS} = 0 \quad \{ I = 0 \}$

$$V_{X_2} - V_{X_1} = 0$$

$$V_{X_2} = V_{X_1}$$


$$2 - 2x = 1 + x$$

$$x = \frac{1}{3}V$$

$$V_{X_1}(\text{S.S.}) = 1.33V$$

$$V_{X_2}(\text{S.S.}) = 1.33V$$

Q.

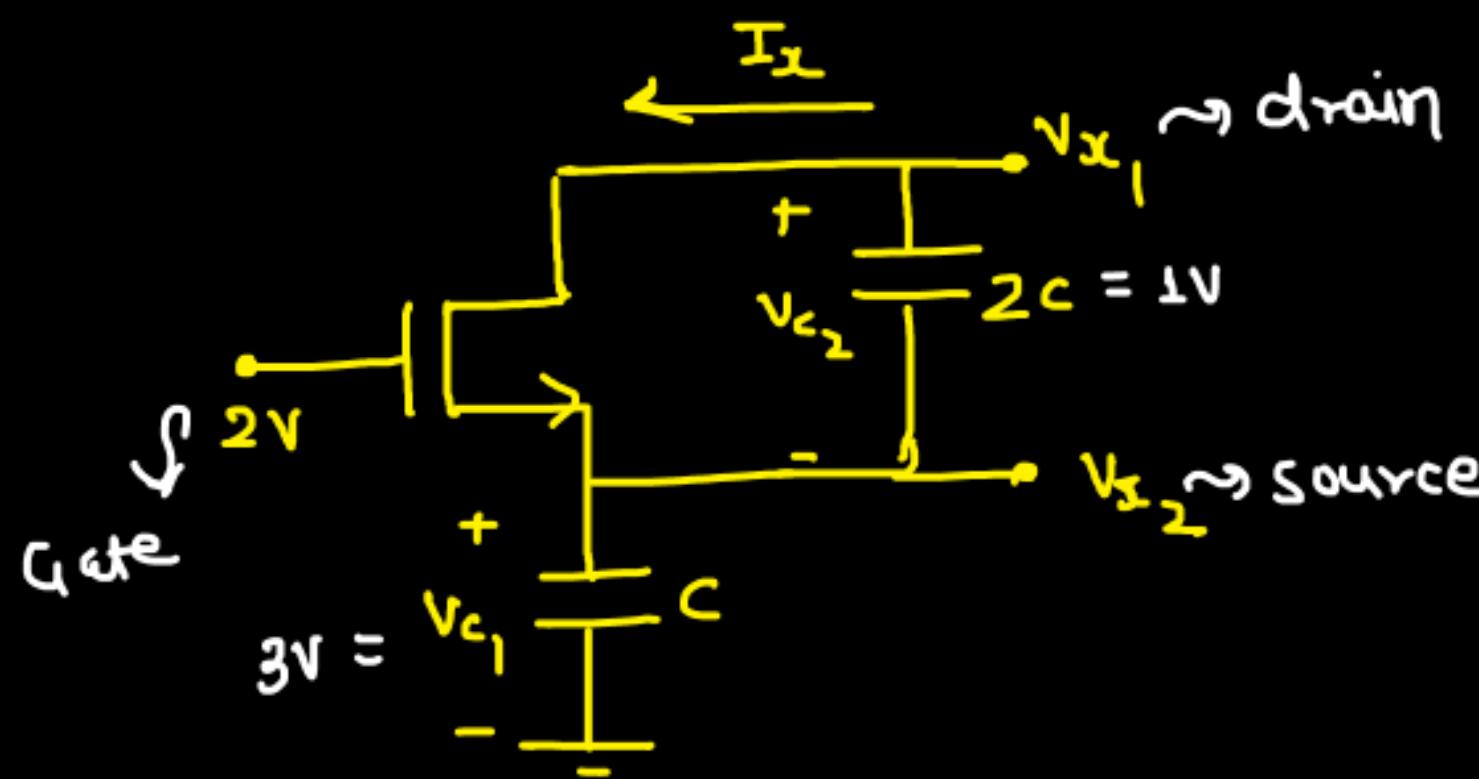

$$v_{x_1}(t=0^+) = 4V \rightsquigarrow \text{Drain}$$

$$v_{x_2}(t=0^+) = 3V \rightsquigarrow \text{source}$$

$v_{ds} = 2 - 3 = -1V < v_T \Rightarrow$  MOS doesn't even turn ON  $\Rightarrow I_x = 0 \Rightarrow \text{ss.}$




$$v_{c_1}(0^+) = 3V$$

$$v_{c_2}(0^+) = 1V$$


$$v_{x_1} \text{ vs } t = ?$$

$$v_{x_2} \text{ vs } t = ?$$

$$I_x \text{ vs } t = ?$$

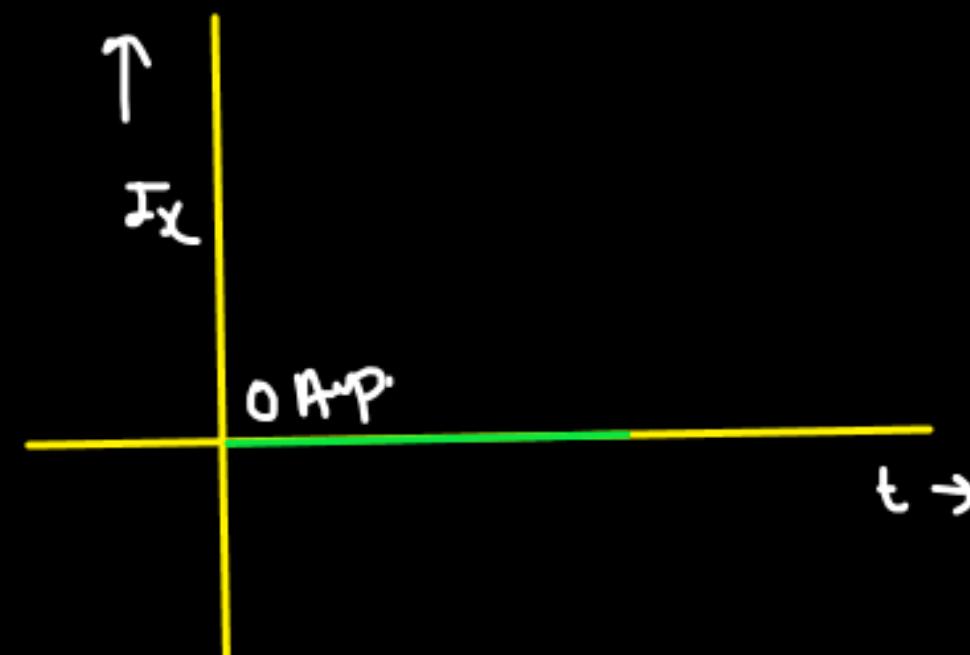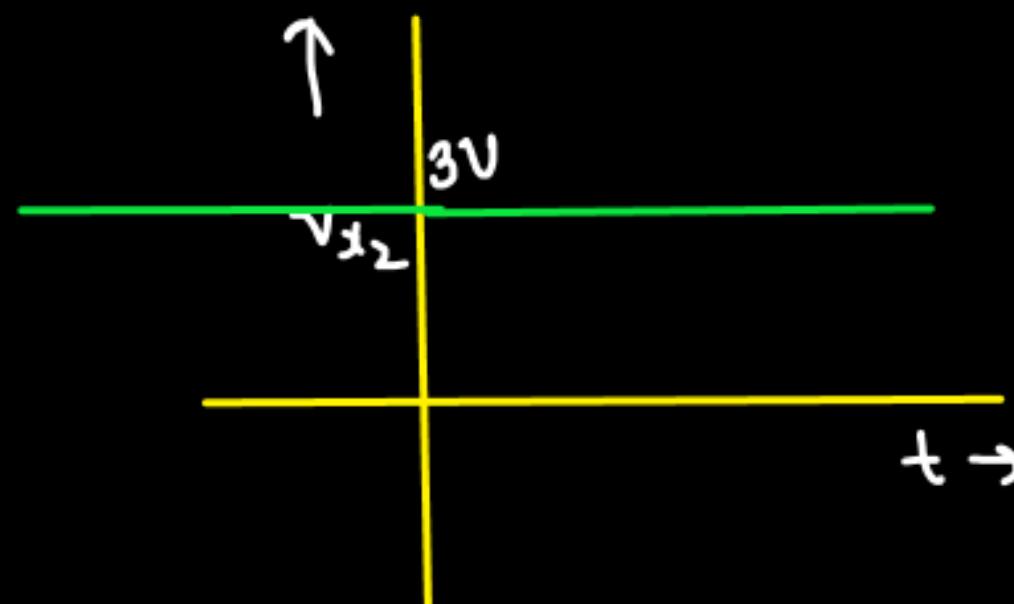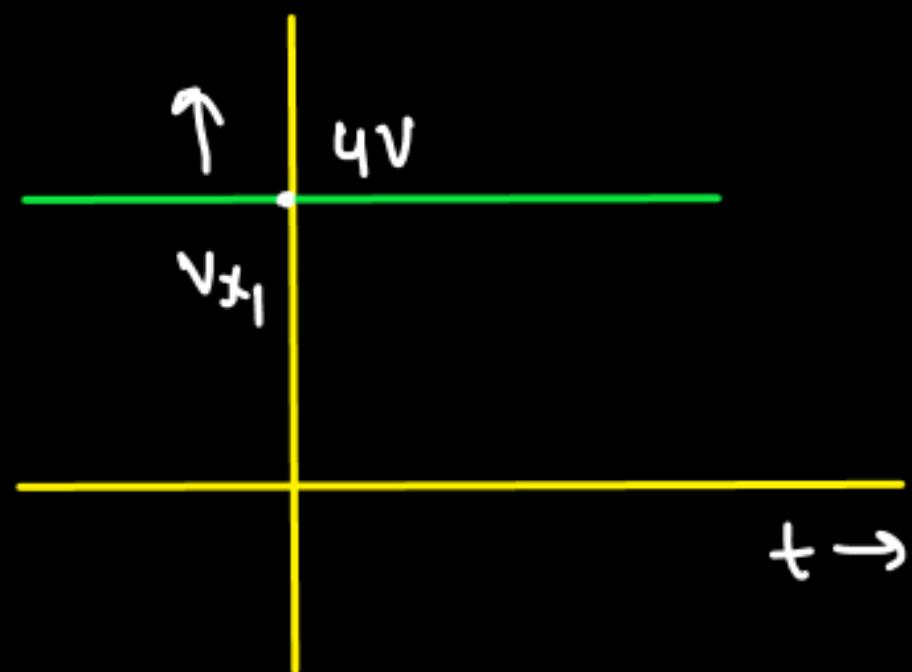

Q.

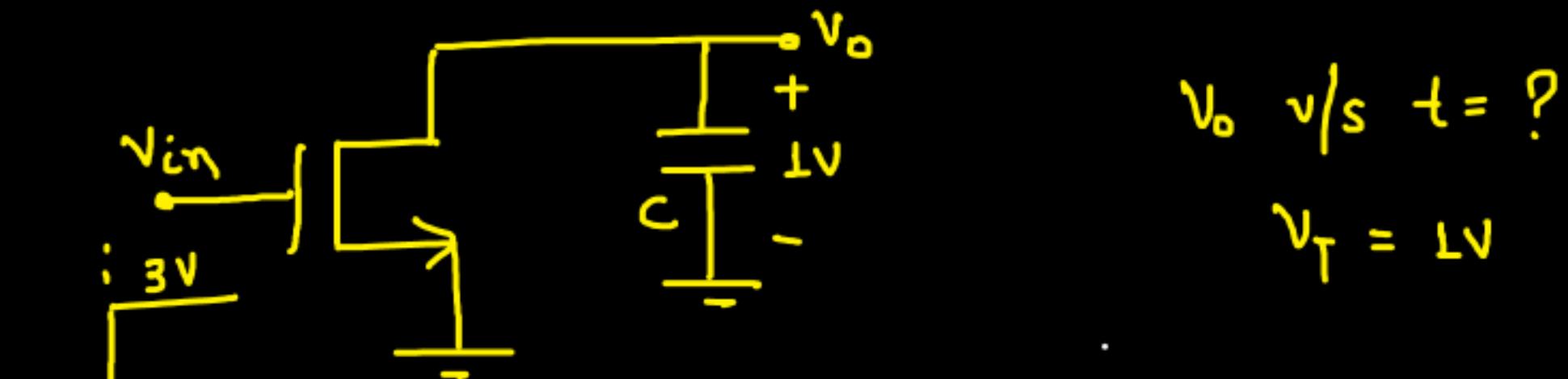

$$V_o \text{ v/s } t = ?$$

$$V_T = 1V$$

↳ for  $t < 0$  :-

$$V_{in} = 0V$$


$V_{QS} = 0V \Rightarrow \text{no current}$

$$V_o(t=0^-) = V_c(t=0^-) = 1V$$

for  $t > 0$  :-

@  $t=0^+$

$$V_{in} = 3V$$

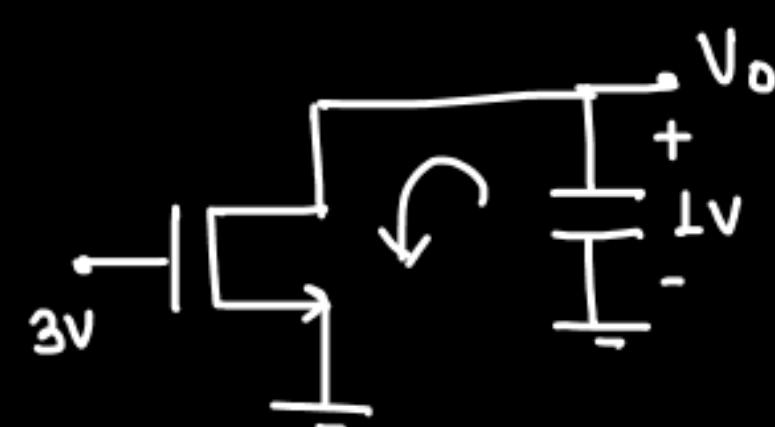

@  $t=0^+$



$$V_{DS} = V_D = 1V$$

$$V_{GS} = 3V$$


$$V_T = 1V$$

$$V_{OV} = 2V$$

$\Rightarrow$  linear region

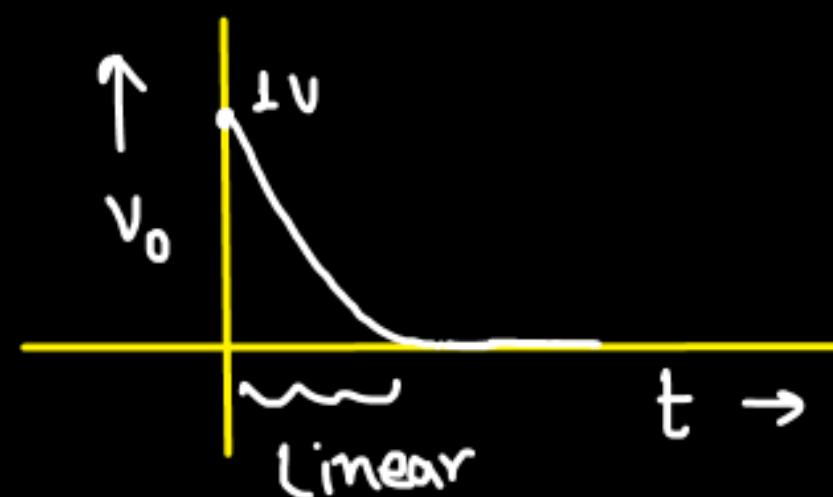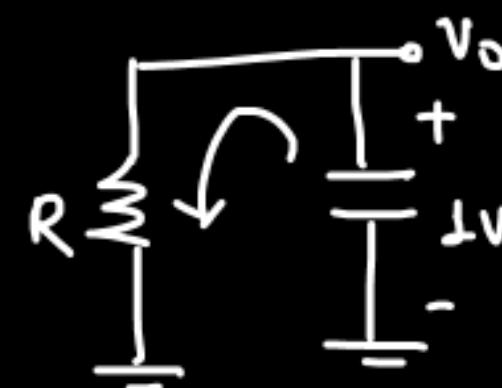


Q.

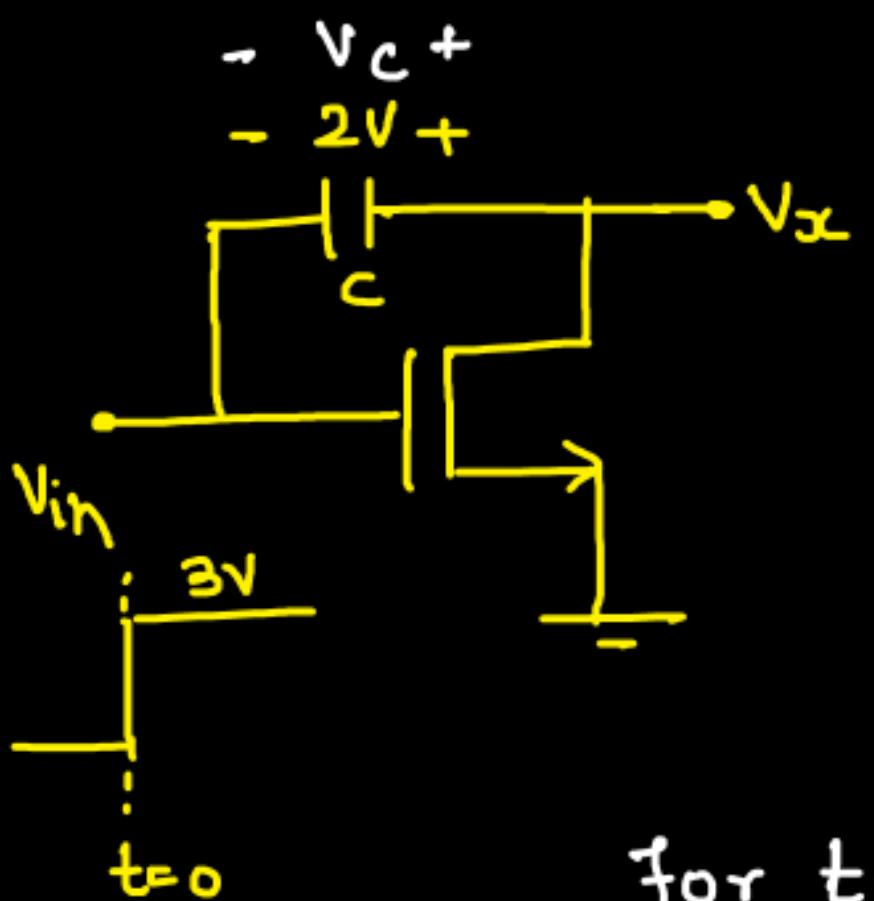

for  $t < 0$ :-
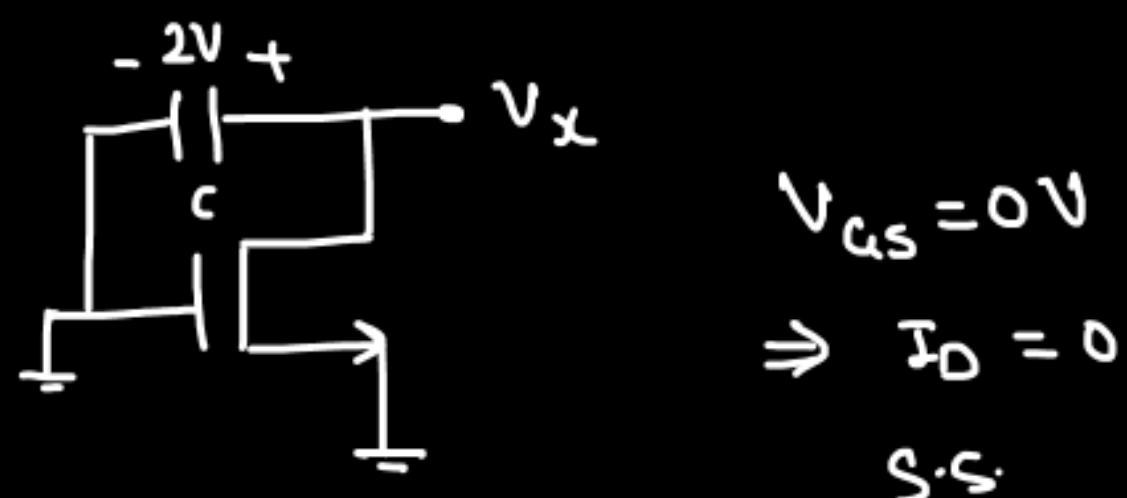
$$v_T = 1V$$
$$v_x \propto e^{-t/C} = ?$$



$$v_{as} = 0V$$


$$\Rightarrow I_D = 0$$

S.C.

$$v_c(t=0^+) = 2V = v_c(t=0^+)$$

$$v_x(t=0^+) = 2V$$

for  $t > 0$

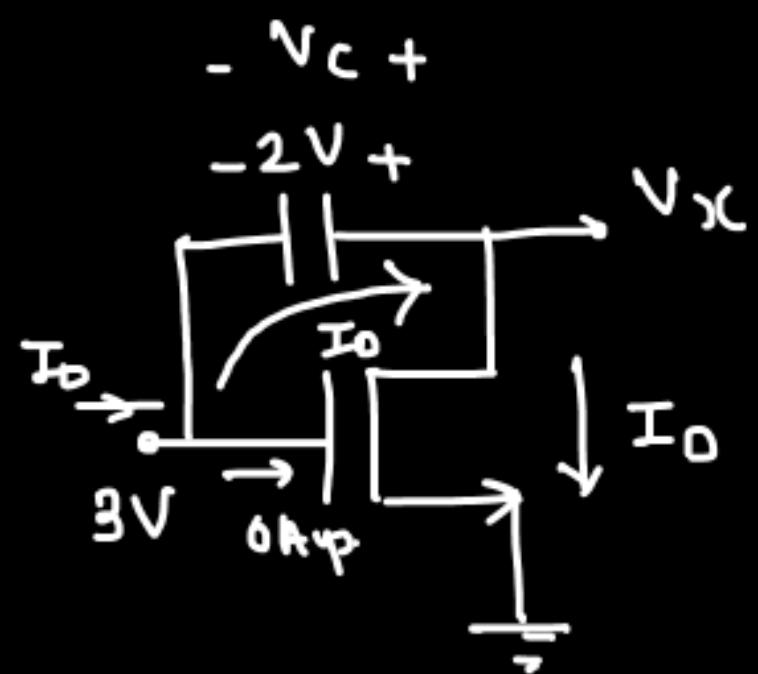

$$V_X(t=0^+) = 5V$$

$$V_{GS} = 3V, V_T = 1V \Rightarrow ON$$

$$V_{DS} = 5V$$

$$V_{UV} = 2V$$


$$V_{DS} > V_{UV} \Rightarrow sat.$$

$$(I_D) \propto K [2]^2$$

Cap. is getting charged in opposite direction.

$V_C$  value will decrease.
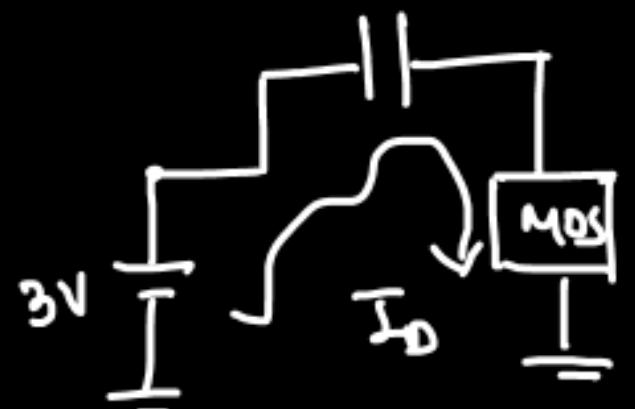
$$V_X = 3 + V_C \Rightarrow V_X \text{ goes down}$$





$$V_C = Q - \frac{1}{C} \int I \cdot dt$$

$$V_C = Q - \frac{I}{C} t$$

$$V_{DS} = V_X$$


$$V_{OV} = 2$$

$V_X < 2V \Rightarrow$  linear  
region

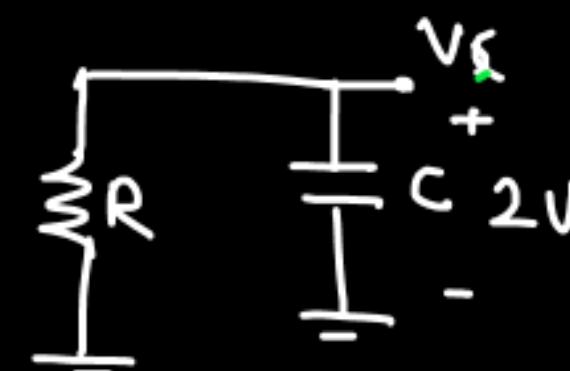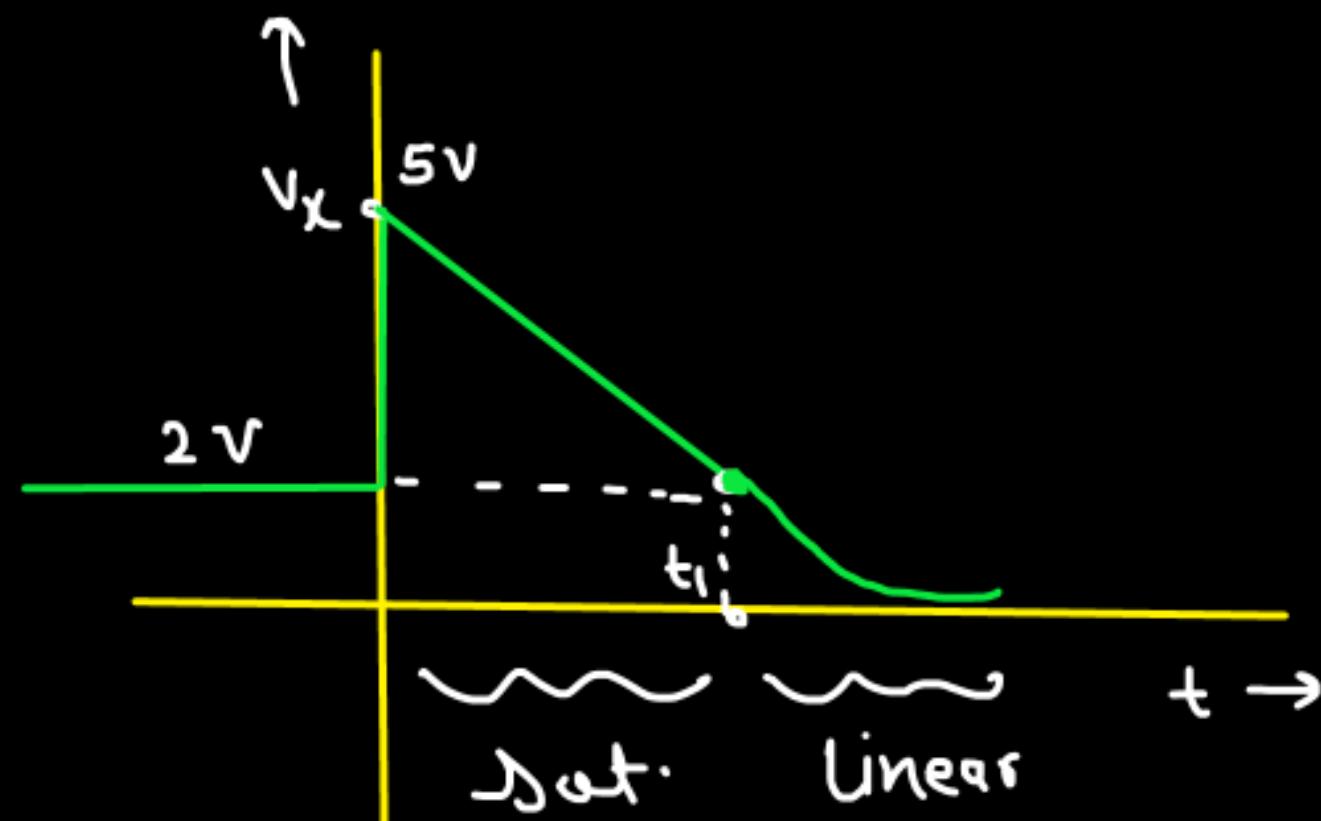

$$V_C(5 \cdot 5) = -3V$$

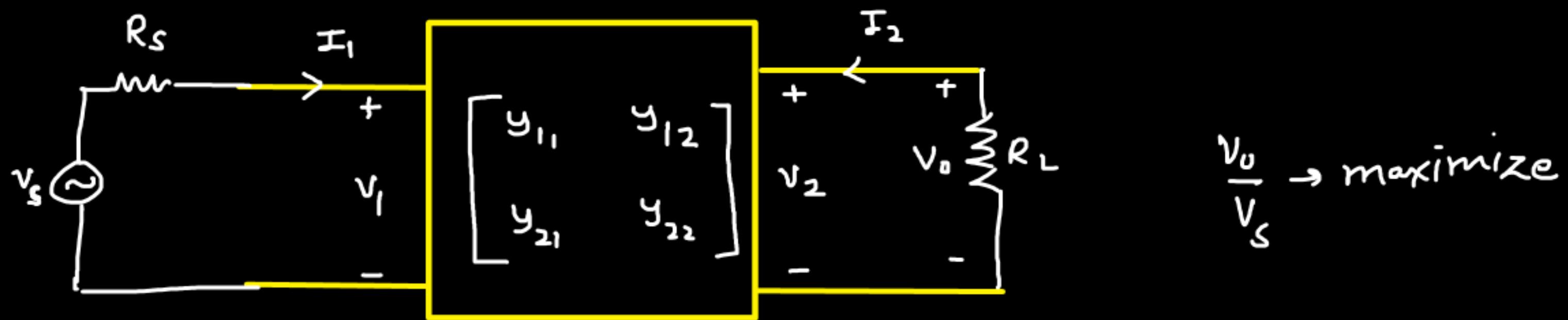Q. In a two port N/W, find the cond'n on  
y-parameter for which the voltage gain  
is maximum.




$$\frac{V_o}{V_s} \rightarrow \text{maximize}$$

→

$$I_1 = y_{11}v_1 + y_{12}v_2 \quad \text{--- (1)}$$
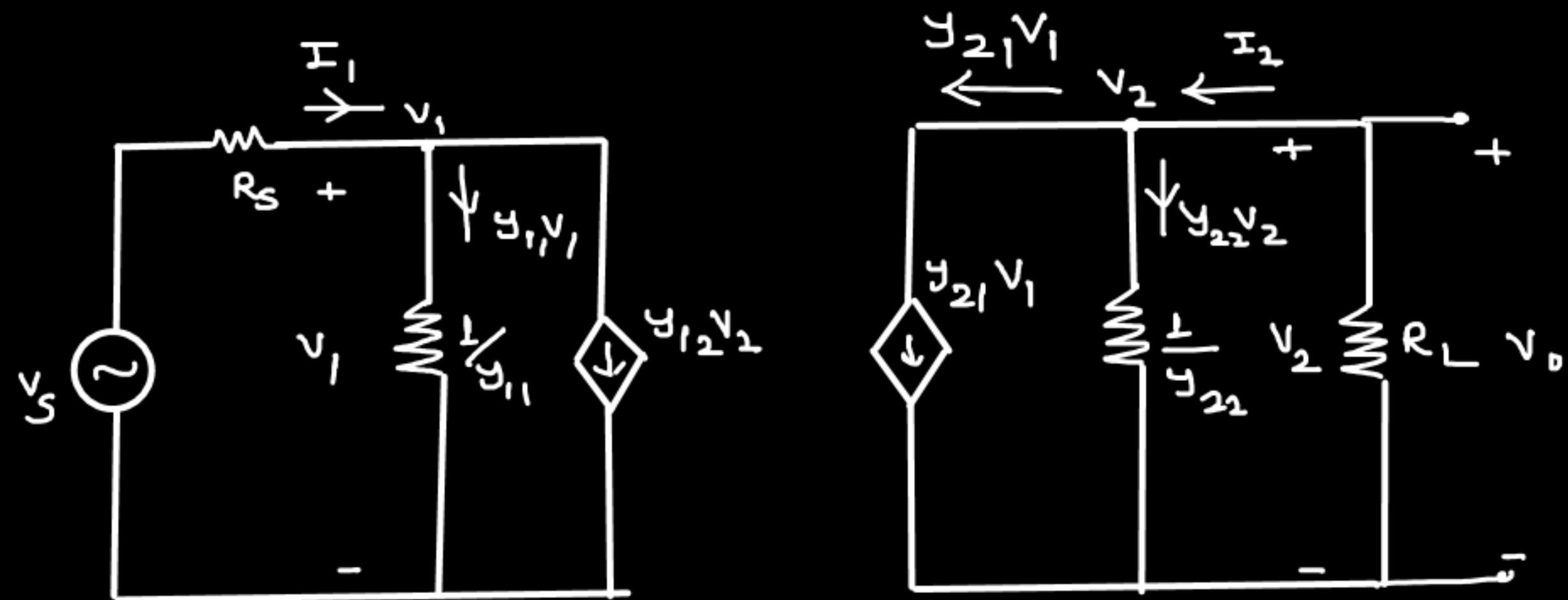
$$I_2 = y_{21}v_1 + y_{22}v_2 \quad \text{--- (2)}$$




$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad - \textcircled{1}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad - \textcircled{2}$$

$\frac{V_o}{V_s} \rightarrow \text{maximize}$

1. maximize  $v_1$

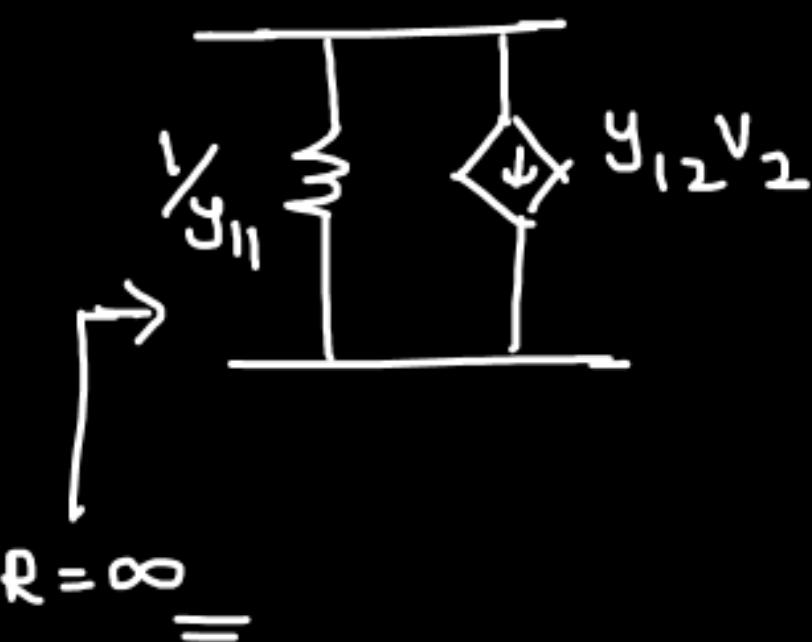

$$R = \infty =$$

if  $R = \infty$

$$v_1 = v_s$$

$$y_{11} = 0, y_{12} = 0$$

~~for~~  $\downarrow$

$$y_{11} = \min, y_{12} = \min$$

2. maximize  $v_o$  / minimize  $y_{22}v_2$

~~for~~

$$\Rightarrow y_{22} = 0$$

$$y_{22} = \min$$

$$V_o = -Y_{21} V_I R_L \quad \text{--- (1)}$$

$$V_I = V_S$$

$$\frac{V_o}{V_S} = -Y_{21} R_L$$

\*\*


To have  $\max^M$  gain

$$Y_{21} = \max^M$$

∴ 
$$Y_{11} = \min, Y_{12} = \min, Y_{22} = \min, Y_{21} = \max^M$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (2)}$$
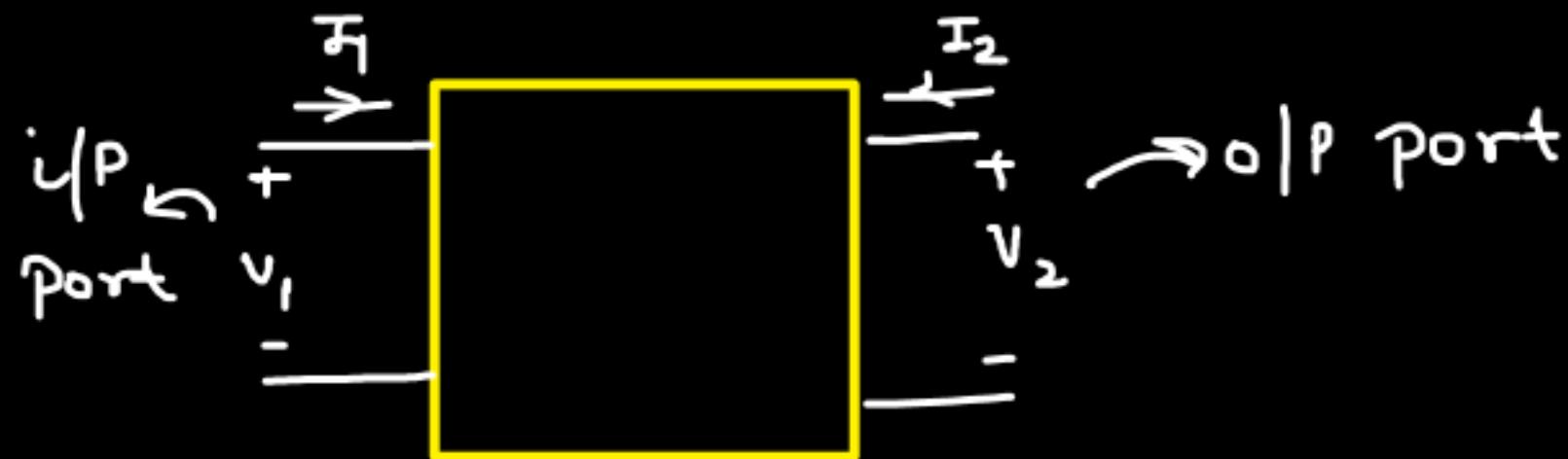
$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$




$$Y_{11} = \frac{\partial I_1}{\partial V_1} \Big|_{V_2=\text{const.}}$$

$$Y_{12} = \frac{\partial I_1}{\partial V_2} \Big|_{V_1=\text{const.}}$$

$$Y_{21} = \frac{\partial I_2}{\partial V_1} \Big|_{V_2=\text{const.}} = \frac{g_m}{m} = \text{large}$$

$$Y_{22} = \frac{\partial I_2}{\partial V_2} \Big|_{V_1=\text{const.}} = \frac{1}{\text{o/p resistance}} = \text{low}$$

Consider a MOS:-

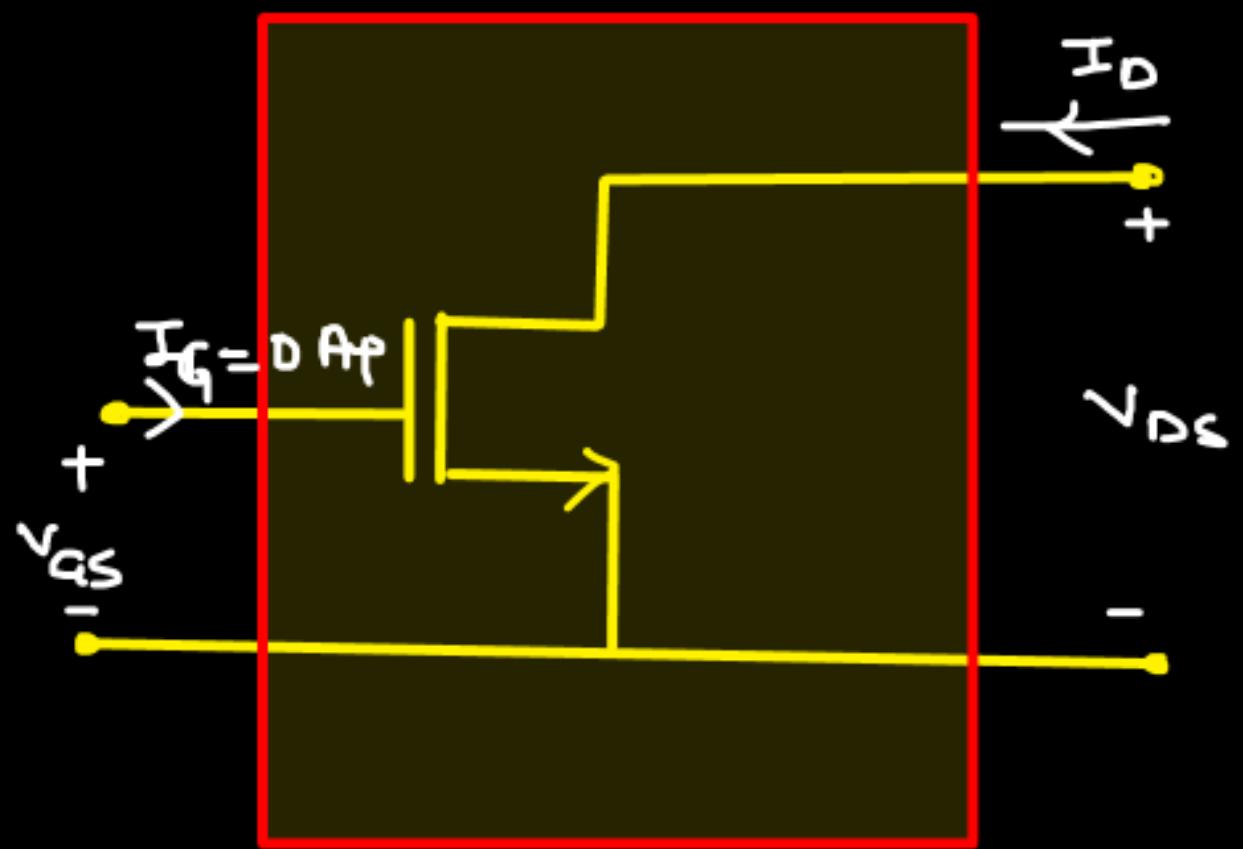

For both Triode and Sat. region

$$\frac{\partial I_D}{\partial V_{GS}} = g_{11} = 0$$

$$\frac{\partial I_D}{\partial V_{DS}} = g_{12} = 0$$

$\frac{\partial I_D}{\partial V_{GS}}$  for sat. and Triode

$$(g_m)_{\text{Triode}} = \frac{\mu n C_{ox} W}{L} (V_{DS})$$

In case of Triode region,  $V_{DS} < V_{GS} - V_T$

$\Rightarrow V_{DS}$  is very low



$g_m$  will be very low in Triode region


$$(\delta m)_{\text{sat.}} = \frac{\mu_n C_o x W}{L} (V_{GS} - V_T)$$

$$(I_D)_{\text{sat.}} = \frac{\mu_n C_o x W}{2L} \left[ (V_{GS} - V_T)^2 \right]$$

$I_D$  and  $V_{GS}$  follow square law relation  $\Rightarrow$  slope  $\frac{\partial I_D}{\partial V_{GS}}$  will be High

\*\*

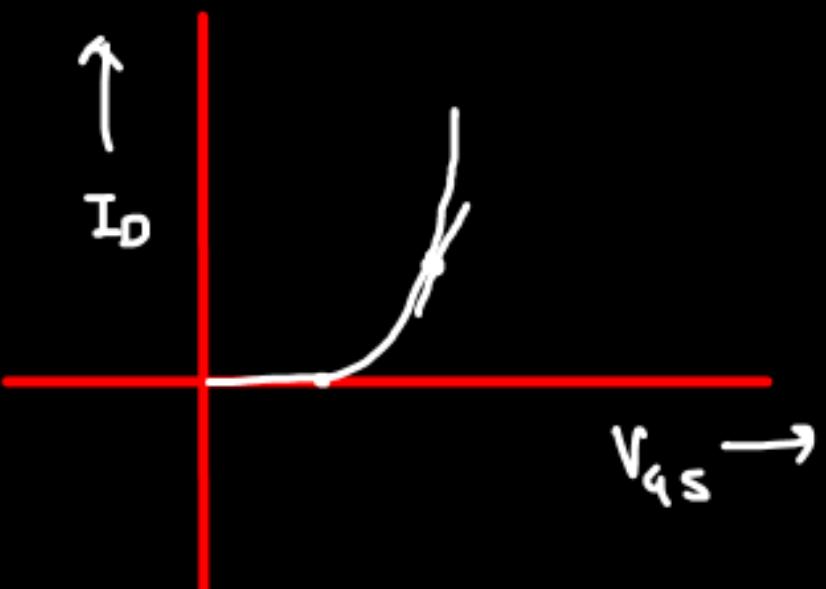
$$(\delta m)_{\text{sat.}} > (\delta m)_{\text{Triode}}$$



$\frac{\partial I_D}{\partial V_{DS}}$  for linear and sat. region :-

$$\left( \frac{\partial I_D}{\partial V_{DS}} \right)_{\text{deep-linear}} = \frac{\mu_n C_{ox} W}{L} (V_{GS} - V_T)$$
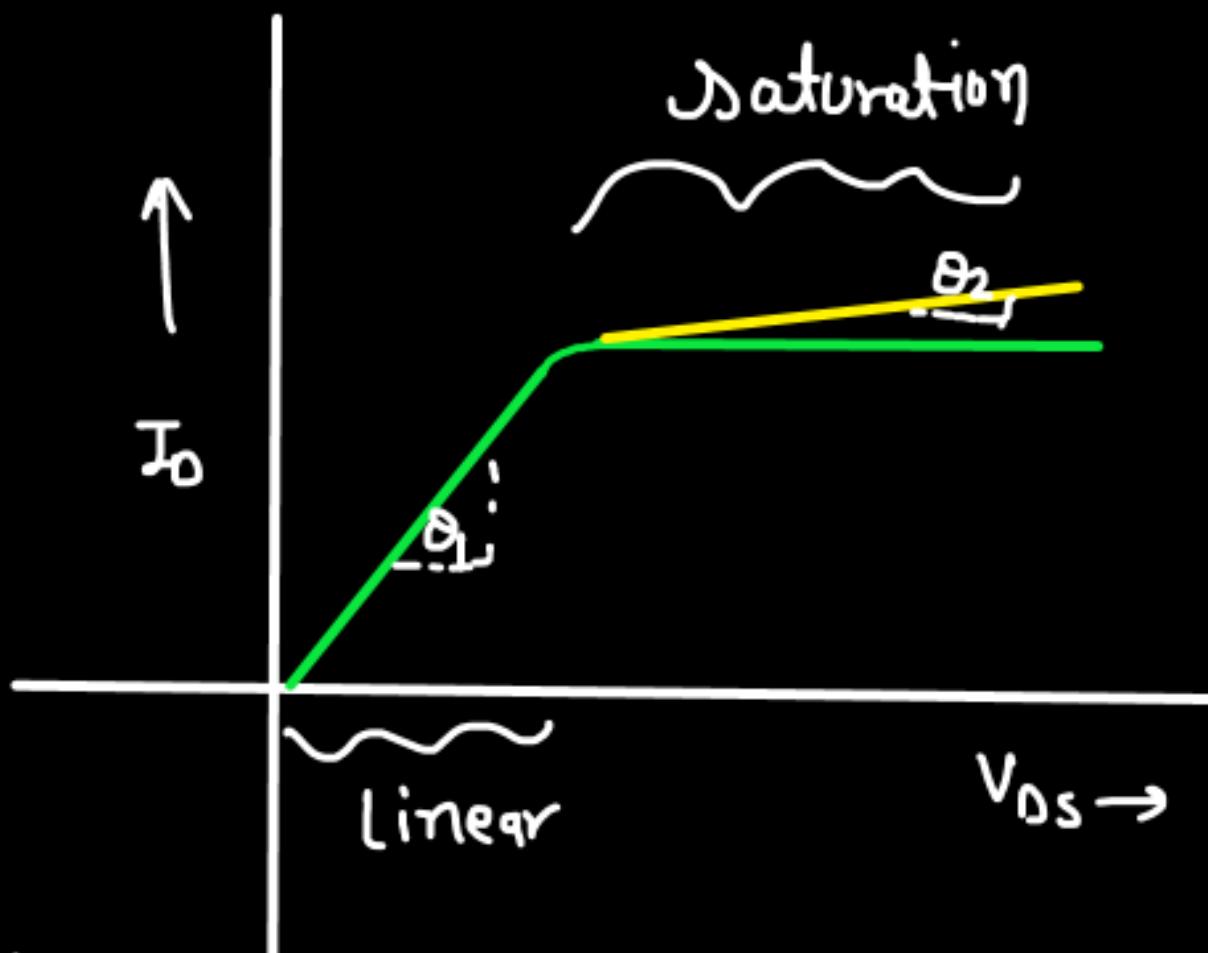
$$\left( \frac{\partial I_D}{\partial V_{DS}} \right)_{\text{sat.}} \begin{cases} \frac{1}{\lambda(I_D)} & (\lambda \neq 0) \\ \infty & (\lambda = 0) \end{cases}$$



For sat.  $\frac{\partial I_D}{\partial V_{DS}} \rightarrow \text{less} \Rightarrow \frac{\partial V_{DS}}{\partial I_D} \rightarrow \text{high}$

$$\theta_1 > \theta_2$$

For sat. region ,  
o/p resistance is High

⇒ Why we use MOSFET in sat. region for Amplification ?


- Because , in sat. region , we get Higher  $g_m$  and Higher o/p resistance that maximizes our voltage gain .

⇒ How to bias a MOS for amplification?

Try-1


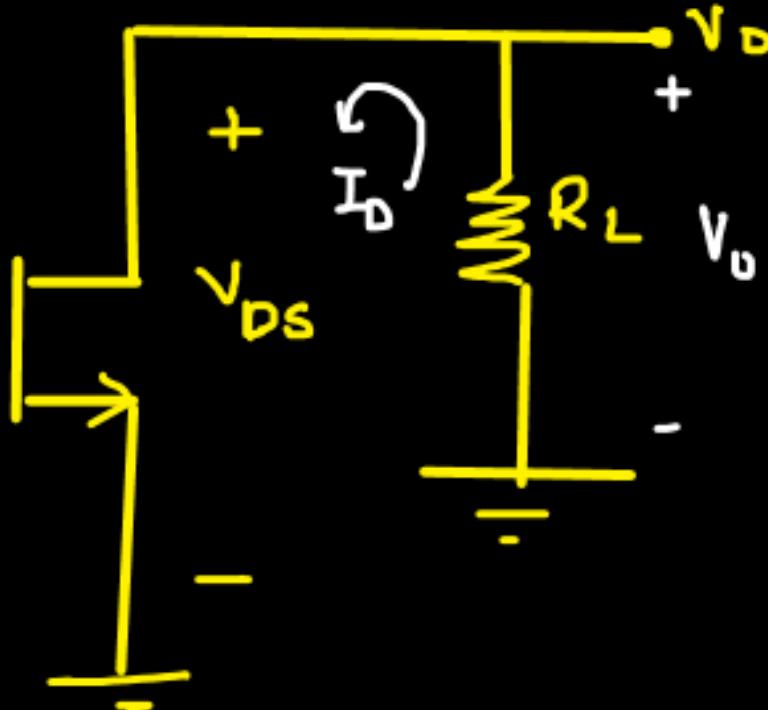
$$3V = V_{GS} \frac{I}{L}$$
$$20mV \sin \omega t = V_s$$



$$V_T = 1V$$

for sat.  $\rightarrow$

$$V_{DS} > V_{GS} - V_T$$

$$V_{DS} > 3 + 20mV \sin \omega t - 1$$

$$V_{DS} > 2V$$

$$V_{DS} = - I_D R_L$$

= negative




NOT DESIRED

[MOS will be in CUT-OFF]

Try-2

Fixing  $V_{DS}$

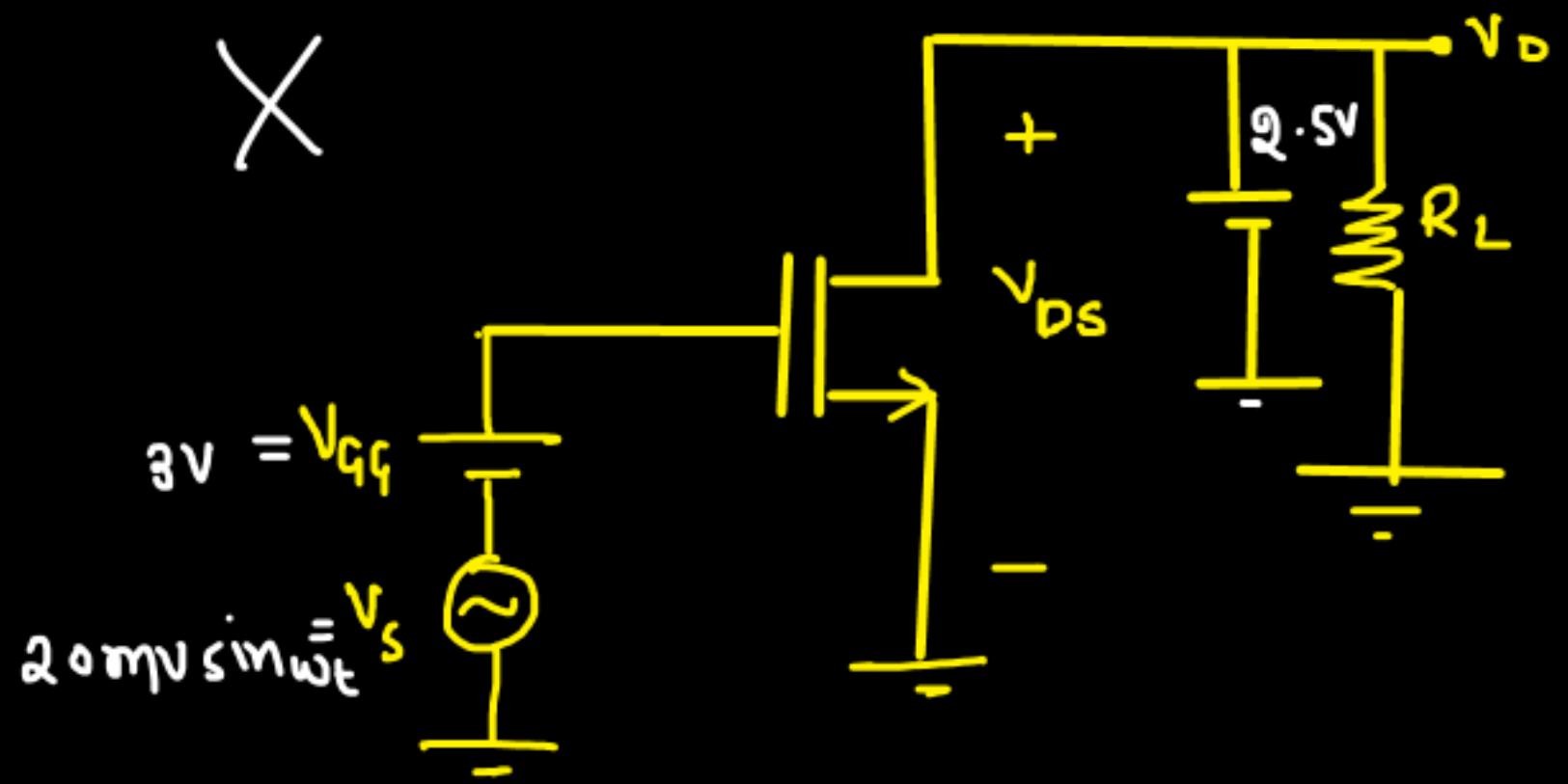

$$V_{DS} > 2V \rightarrow \text{for sat.}$$

Here ,



$$V_{DS} > V_{GS} - V_T \Rightarrow \text{sat. v.}$$

$$V_D = 2.5V \rightarrow \text{fixed}$$


↓

NOT working as  
an amplifier =

Try-3

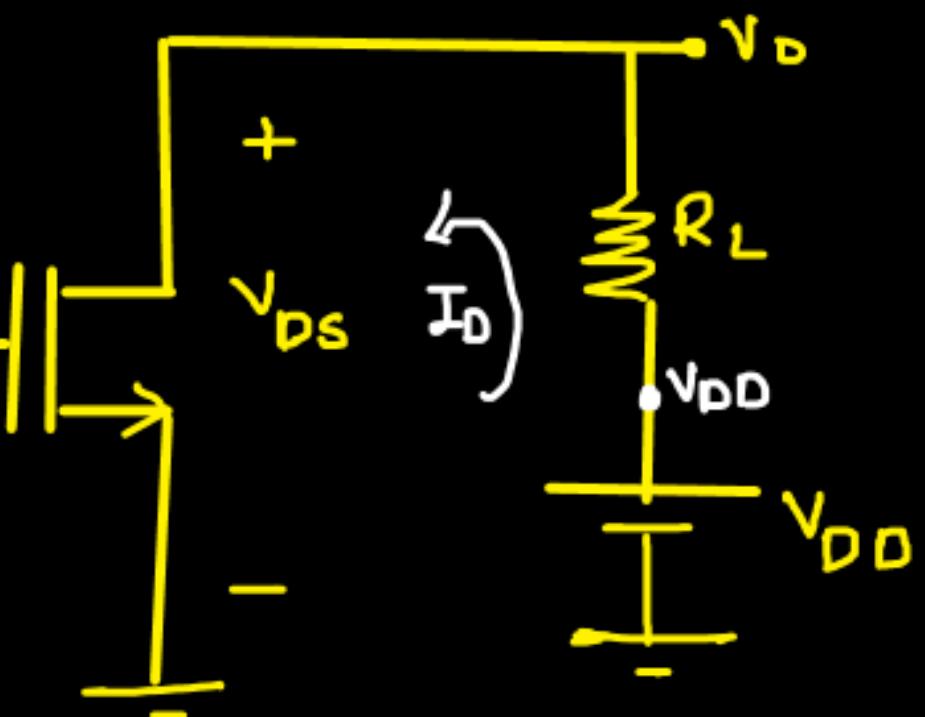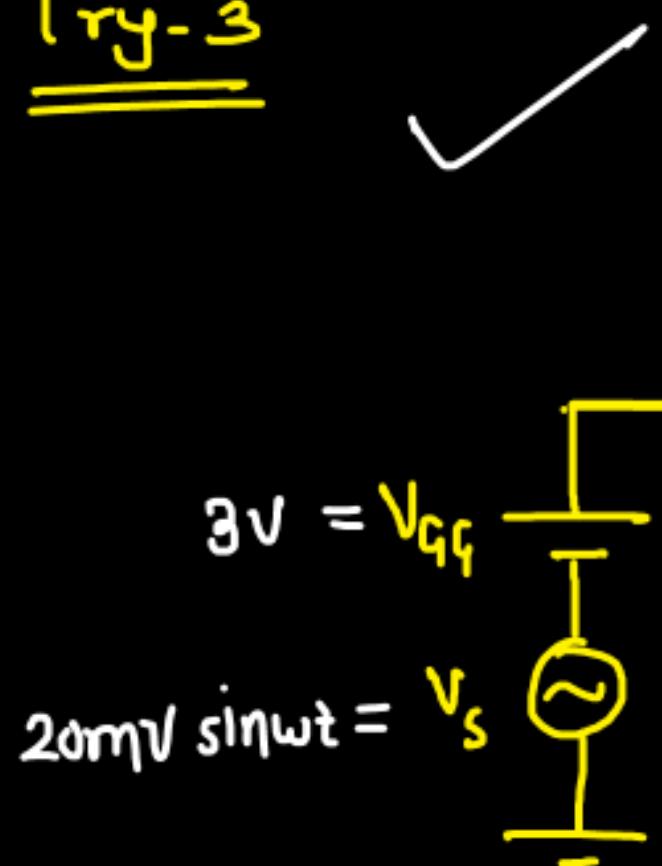

$$v_T = 1V$$

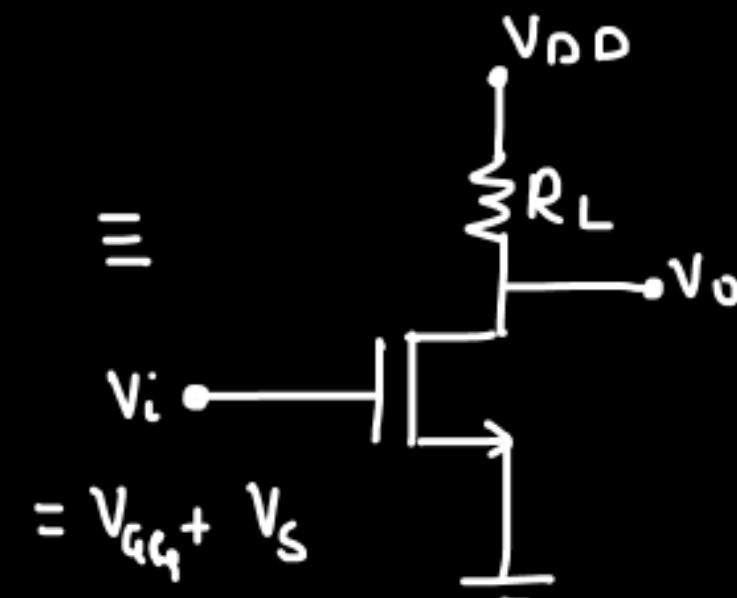


$$v_{DS} = v_{DD} - I_D R_L$$

You can adjust  $v_{DD}$  such that your MOS works in saturation region.

also, O/P is NOT fixed.

## Small Signal Analysis of MOS Amplifiers:-

## MOS in saturation

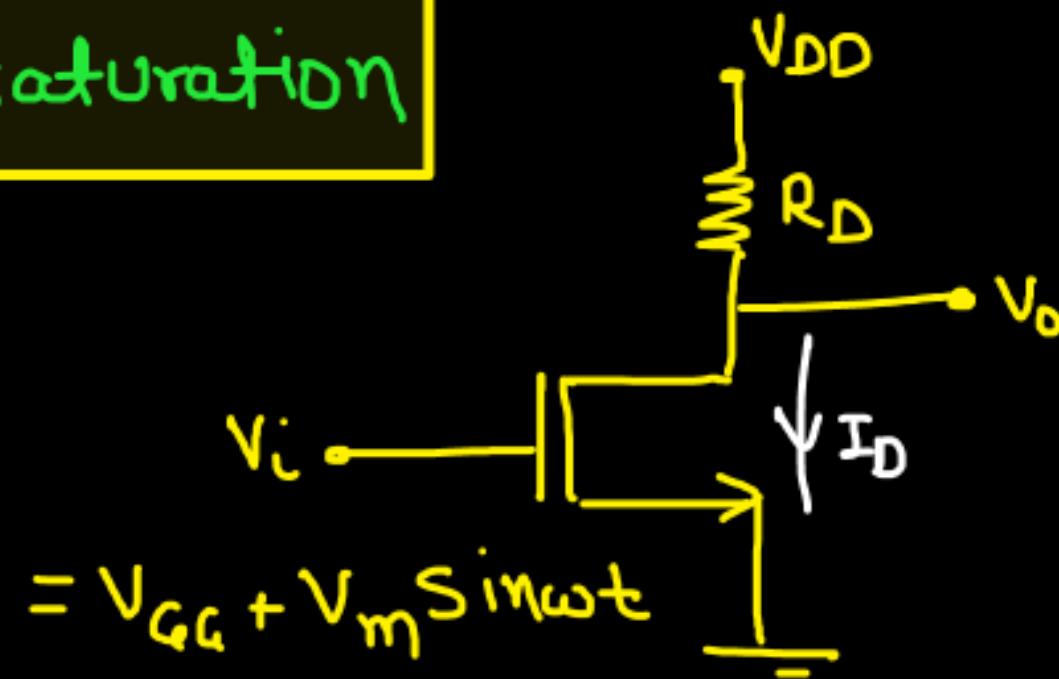

$$V_{gs} = V_m \sin \omega t \rightarrow \text{small signal ac input}$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T]^2$$

$$= \frac{M\eta C_w w}{2L} [V_{GQ} + V_m \sin \eta wt - V_T]^2$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T + V_m \sin \omega t]^2$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T]^2 \left[ 1 + \underbrace{\frac{V_m \sin \omega t}{V_{GS} - V_T}}_{\downarrow \text{small}} \right]^2$$

$\left\{ (1+x)^2 \approx 1+2x \right\}$

$$I_D = \frac{\mu_n C_{ox} W}{2L} [V_{GS} - V_T]^2 \left[ 1 + \frac{2V_m \sin \omega t}{V_{GS} - V_T} \right]$$

$$I_D = I_{DC} \left[ 1 + \frac{2V_m \sin \omega t}{V_{GS} - V_T} \right]$$

$\downarrow$

Current if only  $V_{GS}$  (dc) was applied

$$I_D = I_{Dc} + \frac{2I_{Dc}}{V_{Gg} - V_T} V_m \sin \omega t$$

$$I_D = I_{Dc} + g_m V_{gs}$$

↓      ↓  
dc component  
component

$$\left\{ \begin{array}{l} V_{gs} = V_m \sin \omega t \\ = \text{small signal ac} \end{array} \right.$$

*i(p)*

$$V_o = V_{DD} - I_D R_D$$

$$= V_{DD} - [I_{Dc} + g_m V_{gs}] R_D$$

$$V_o = \underbrace{V_{DD} - I_{Dc} R_D}_{\text{DC}} - \underbrace{g_m V_{gs} R_D}_{\text{AC}}$$

~~( $I_D$ )<sub>ac</sub> =  $\underline{g_m V_{gs}} = i_d$~~


$$(I_D)_{ac} = \underline{g_m V_{gs}} = i_d \neq f(V_{DD}, V_{Gg})$$

$$(V_o)_{ac} = - g_m V_{gs} R_D$$

## Method 2 (Understanding by Graph) :-

$$I_D = \underbrace{I_{Dc}}_{\text{DC}} + \underbrace{\text{AC signal}}_{\downarrow}$$

$$g_m V_{gs} = i_d$$


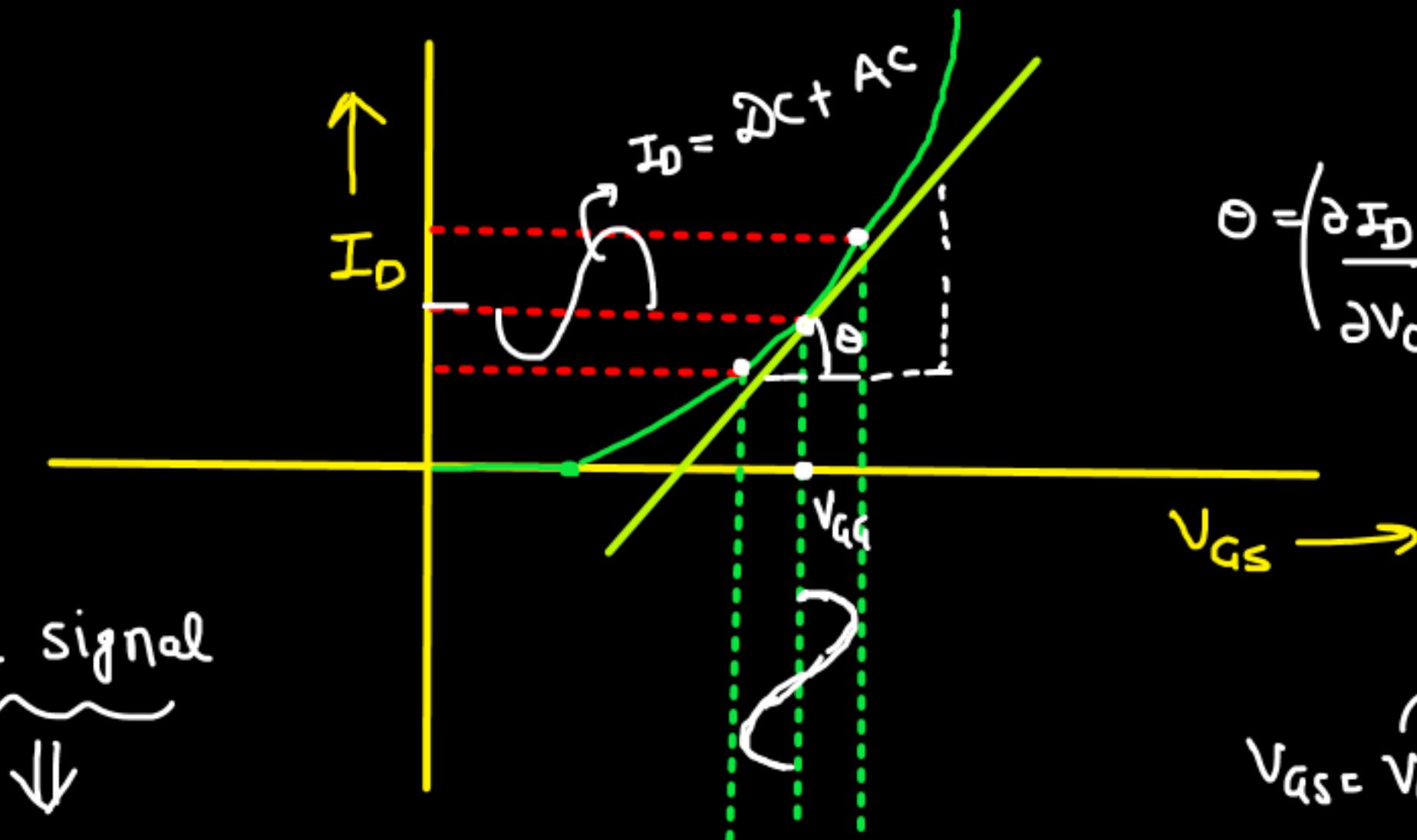


$$\Theta = \left( \frac{\partial I_D}{\partial V_{GS}} \right)_{V_{GS}} = g_m =$$

$$V_{GS} = V_{GE} + V_m \sin \omega t$$

$$= 2 + 20mV \sin \omega t$$



for Analysis Purpose :-

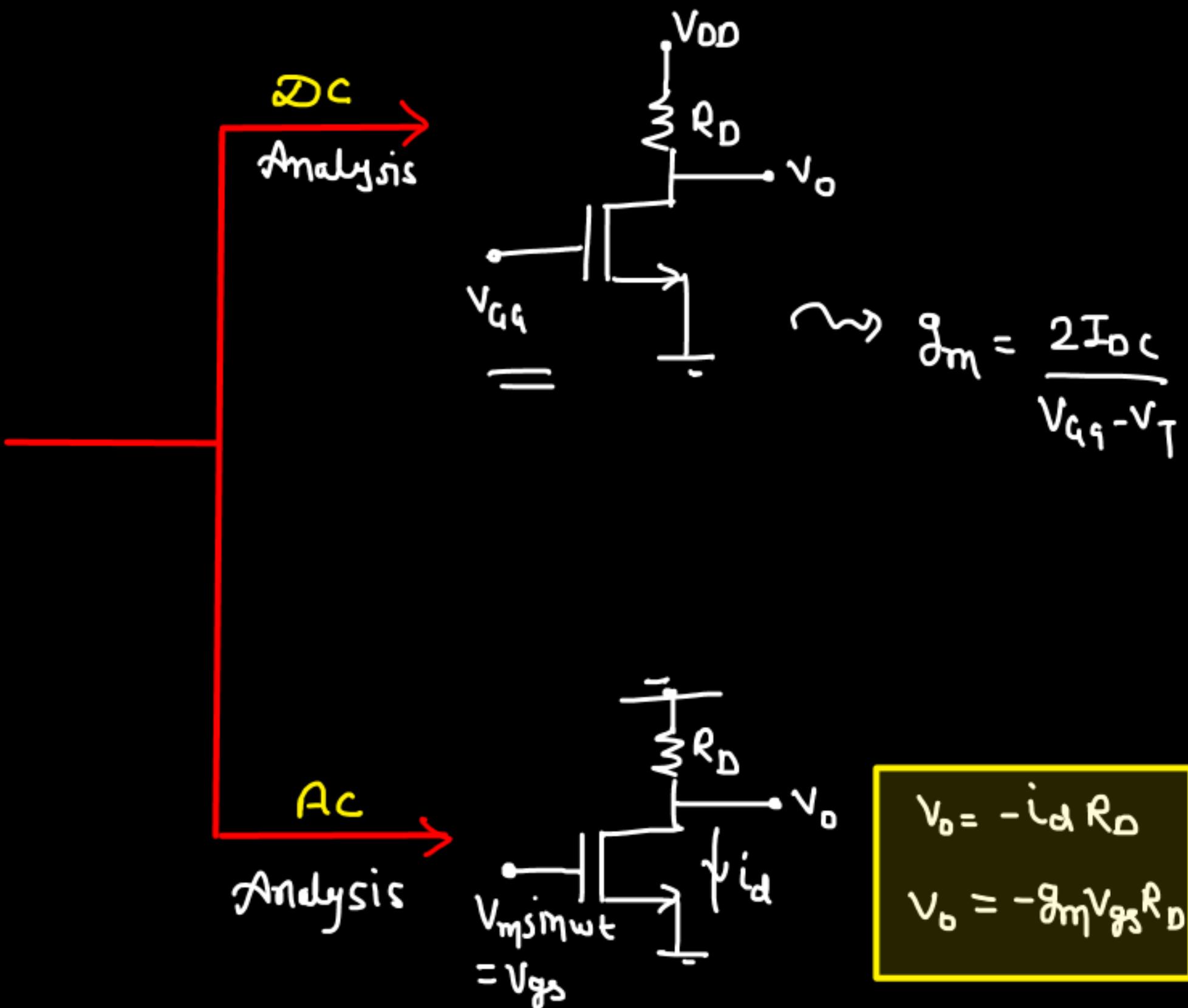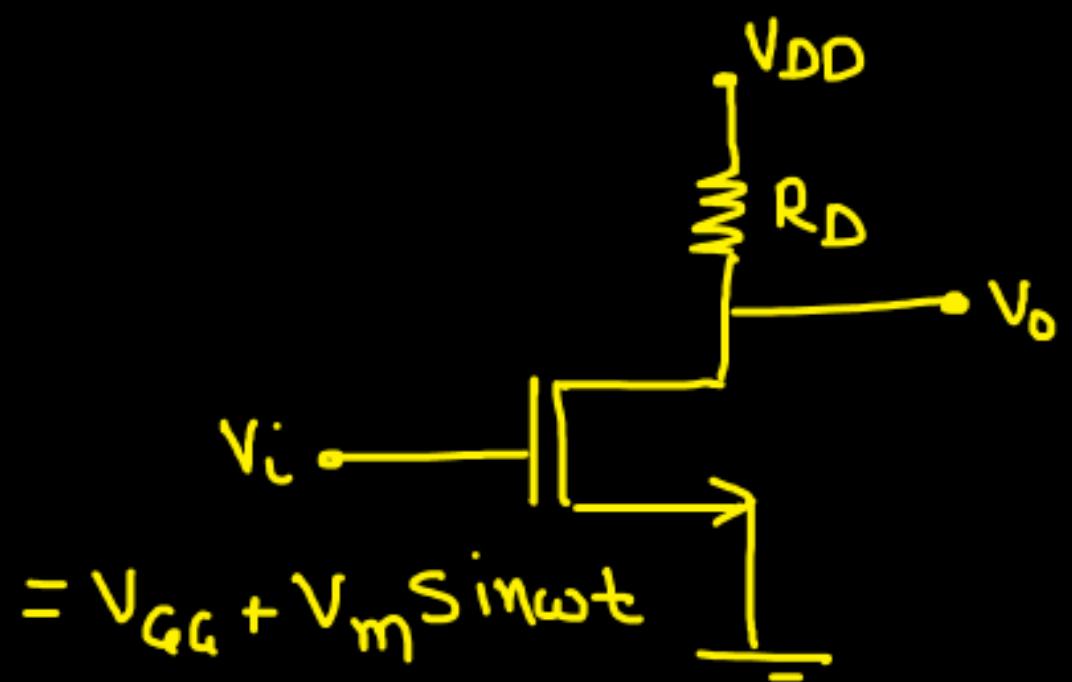


## Small Signal Model of MOSFET:-

### \* AC Analysis:-

① Nullify all the dc sources.

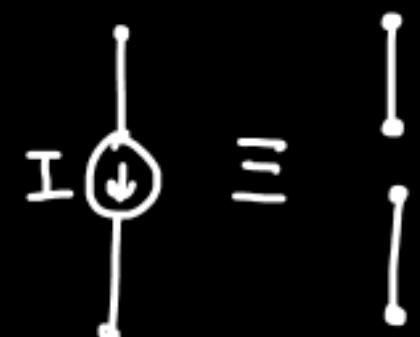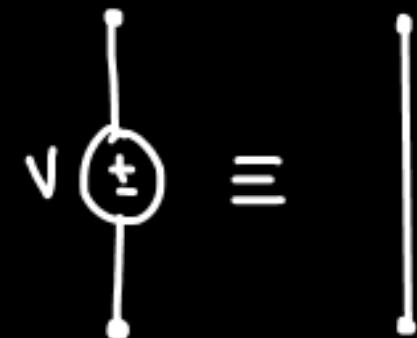

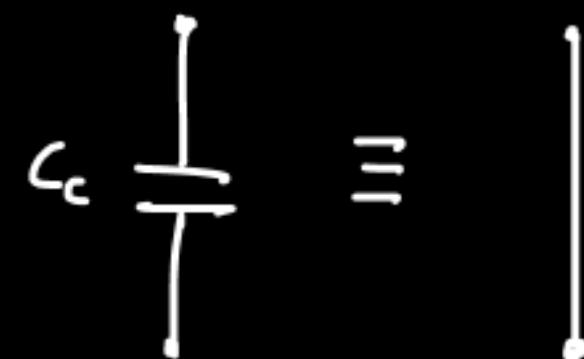② Coupling Cap. will be shorted. (Generally)




## DC Analysis:-


- ① Nullify all the ac sources.
- ② Coupling cap. will be open circuited.

$$C_c \frac{1}{T} \equiv \boxed{I}$$

## NMOS - (Small Signal Model)

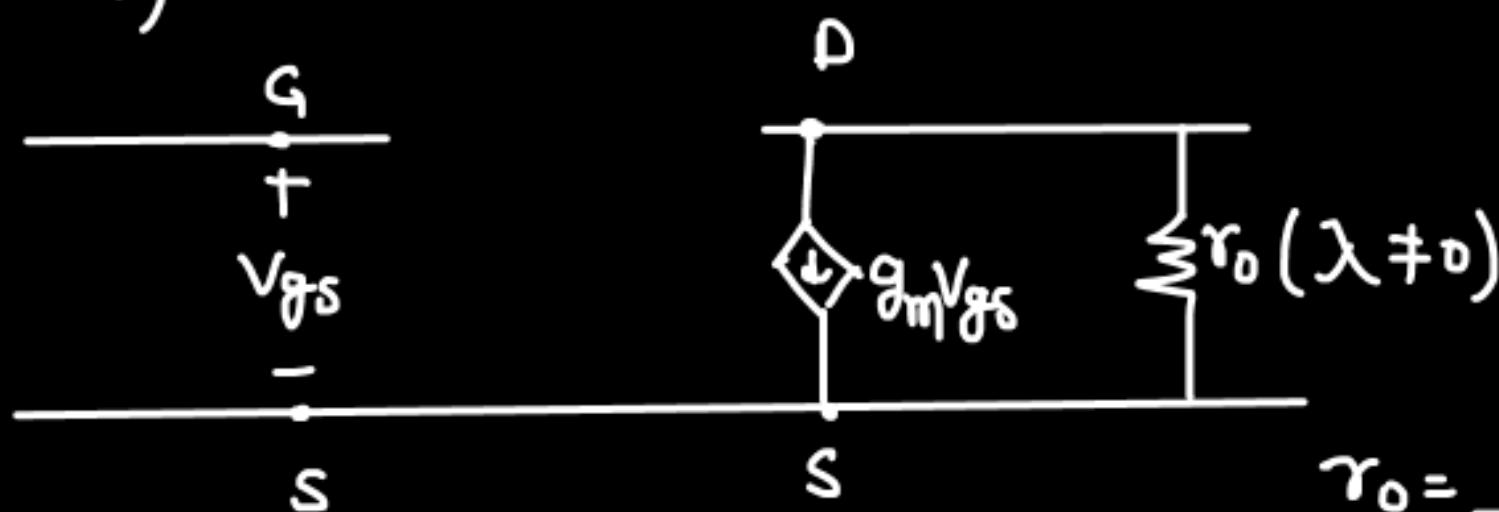

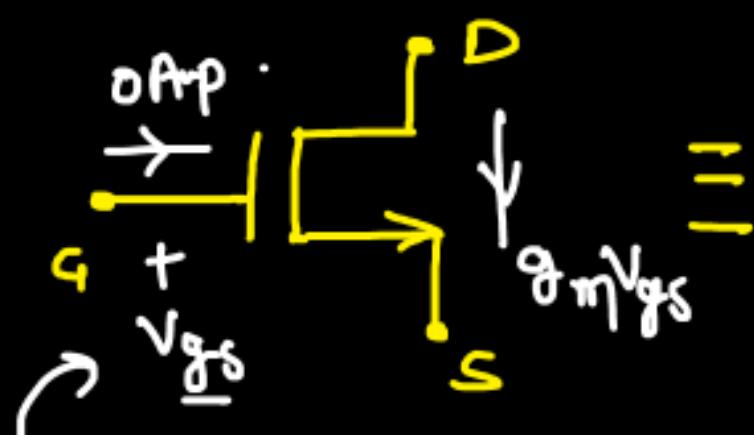
$$r_o = \frac{1}{\lambda(I_D)} \text{ Sat. - ideal}$$




Small signal voltage





$\pi$ -model

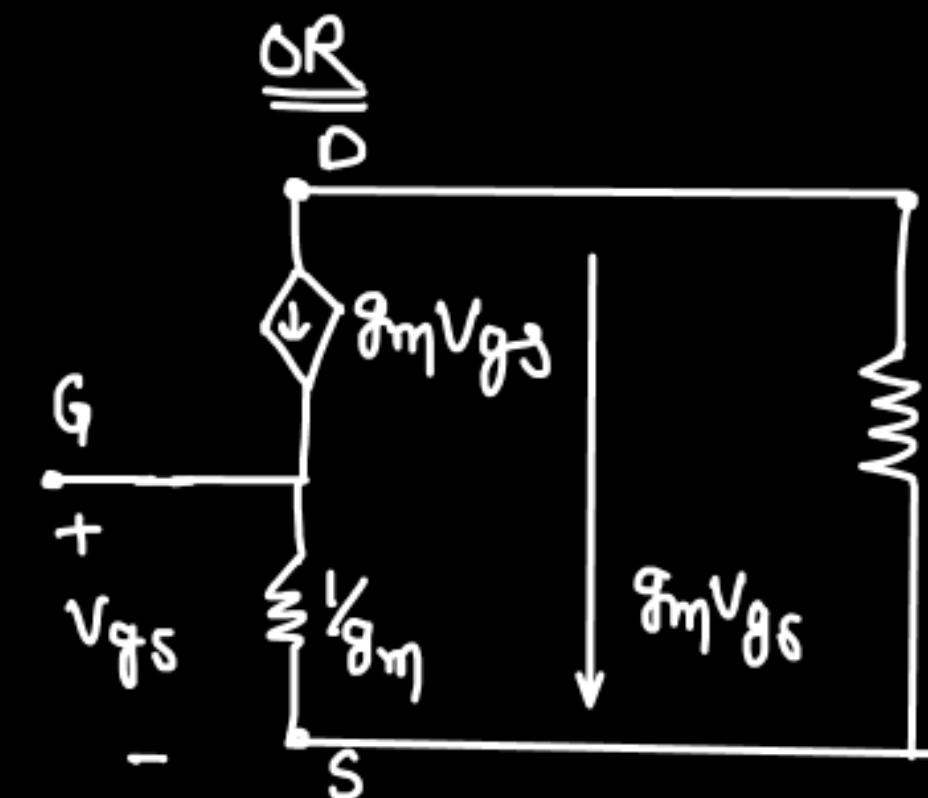


$\underline{\underline{OR}}$

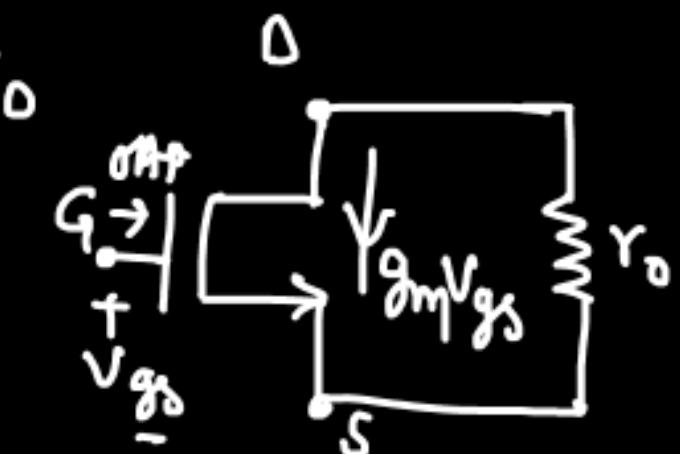

PMOS:-

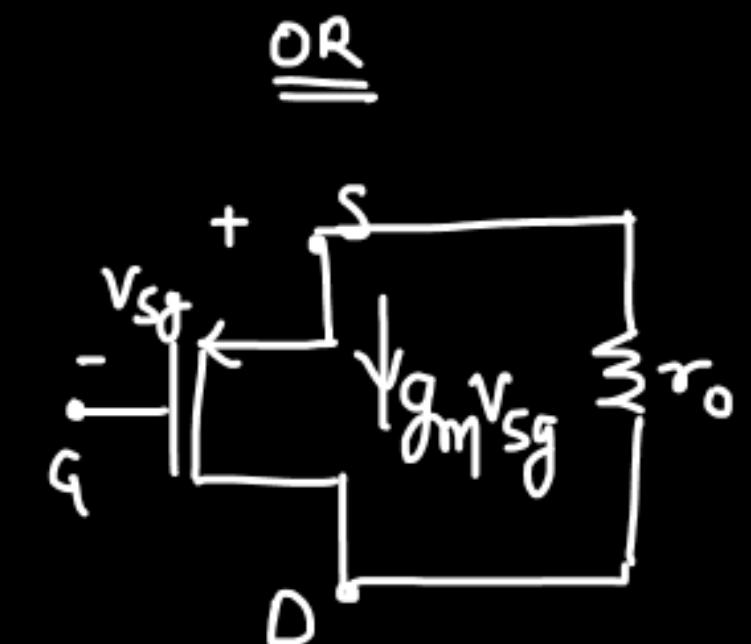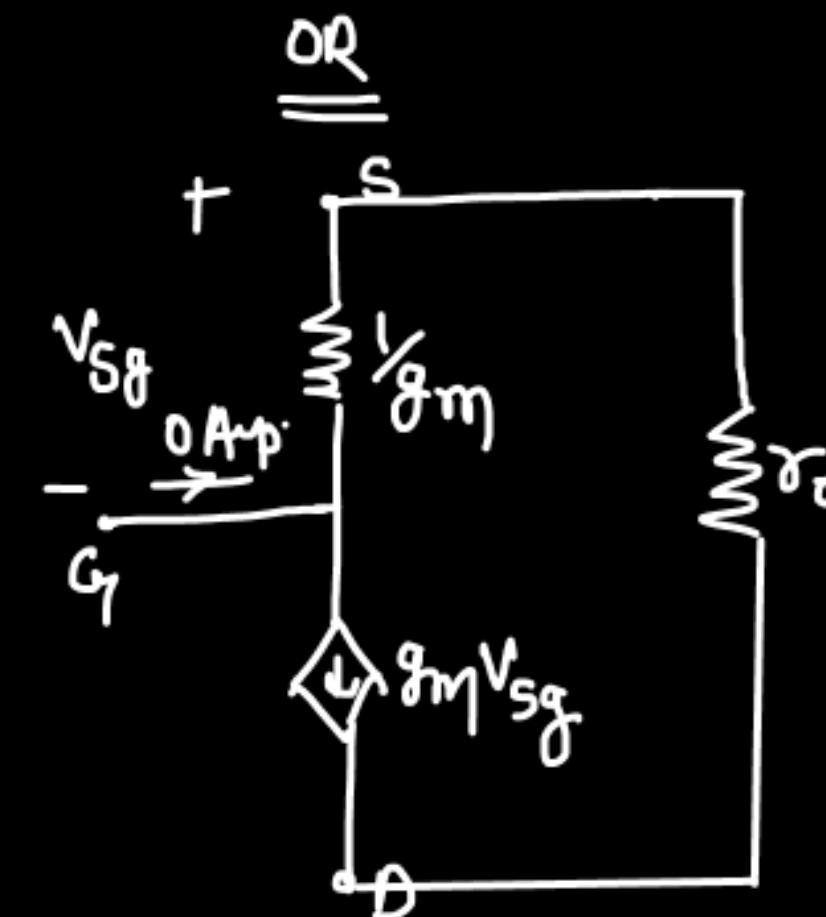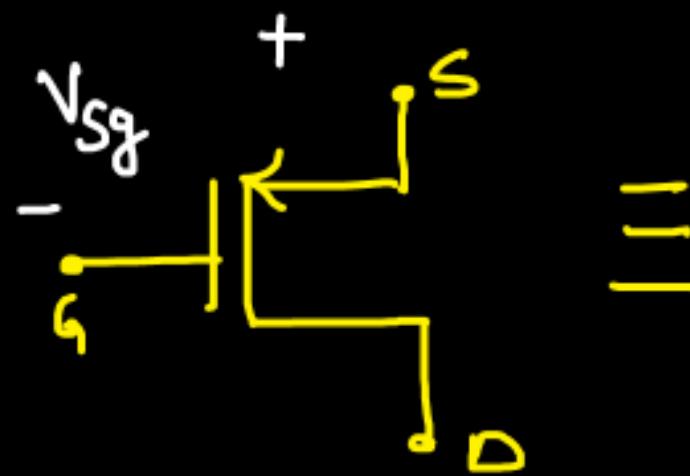
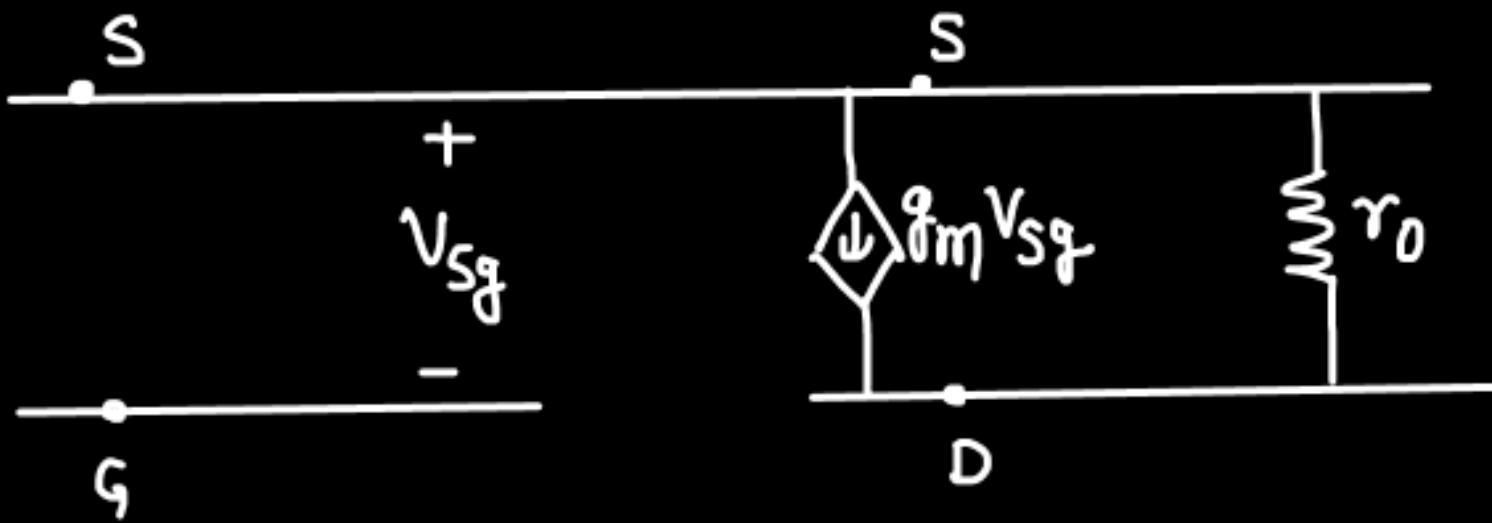


## Concept of port impedance:-

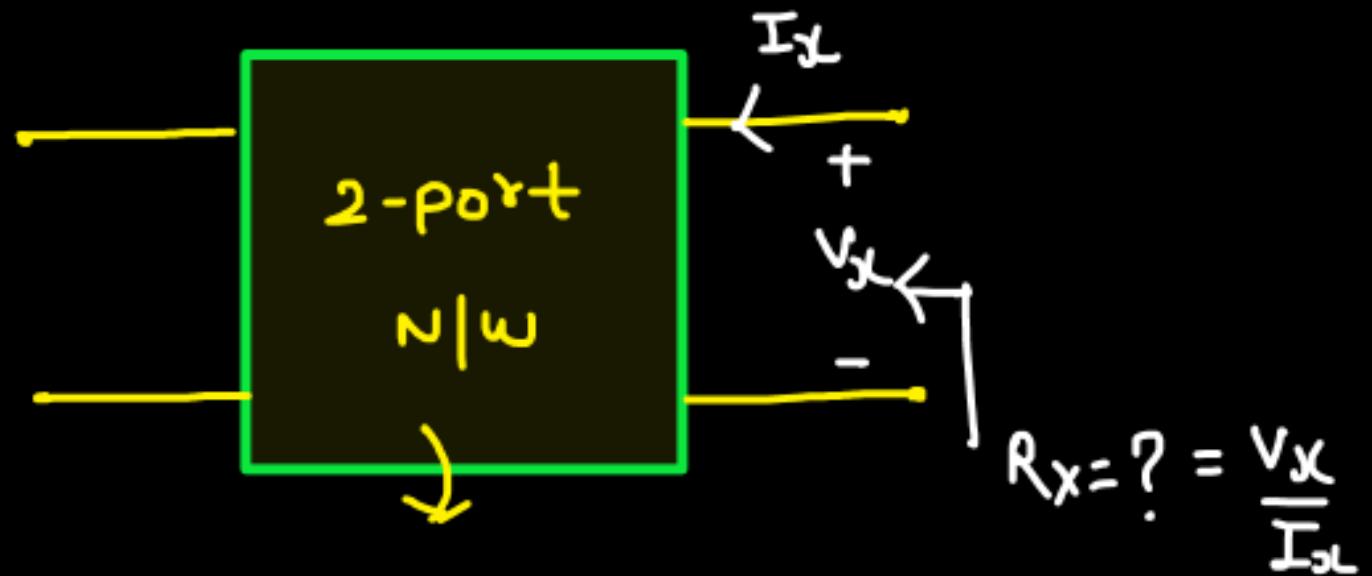

- (i) All independent source = 0
- (ii) Apply  $V_x$  and get  $I_x$  out of it, @ the port where you need to find the impedance.
- (iii)  $R_x = \frac{V_x}{I_x}$



Eg. →

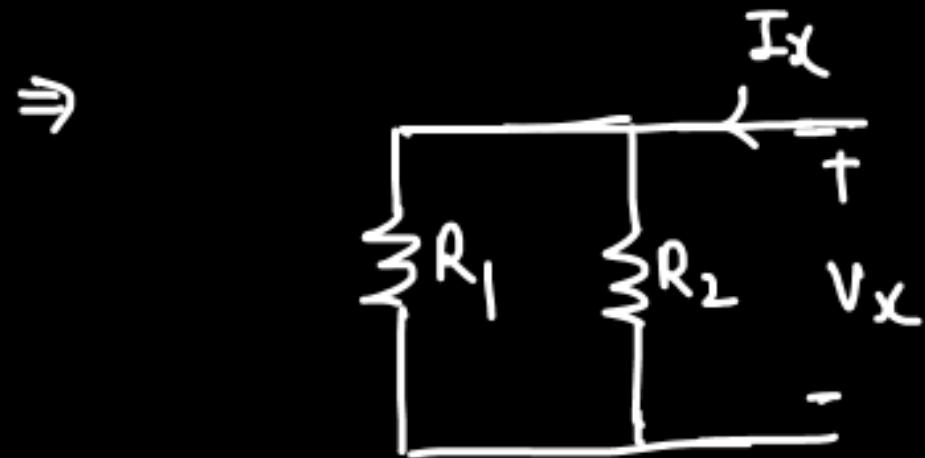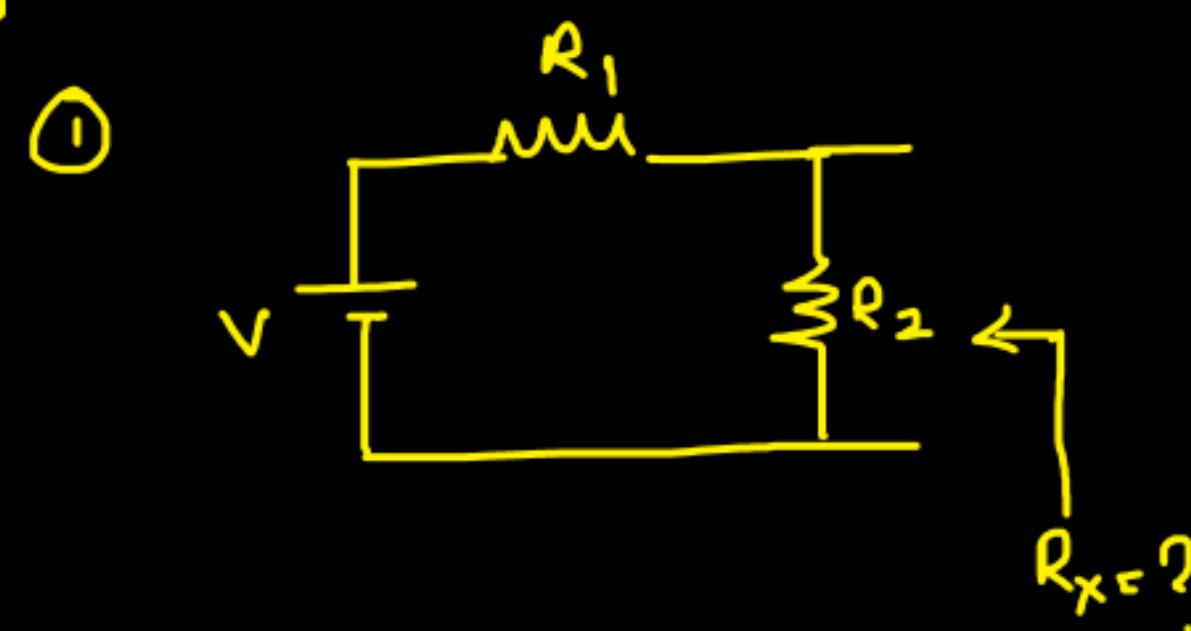


$$\frac{V_x}{R_2} + \frac{V_x}{R_1} = I_x$$

$$\frac{V_x}{I_x} = R_x = R_1 \parallel R_2$$


②

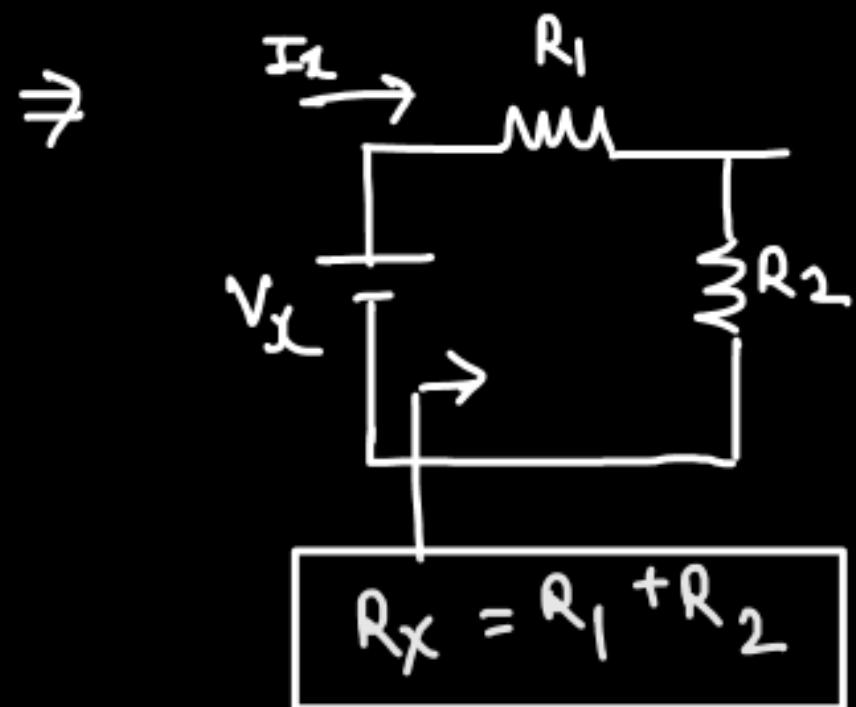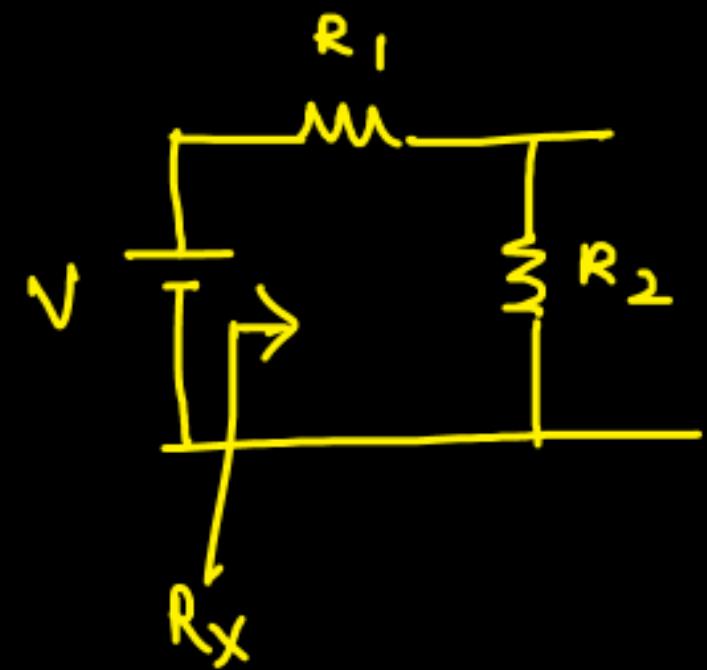

3

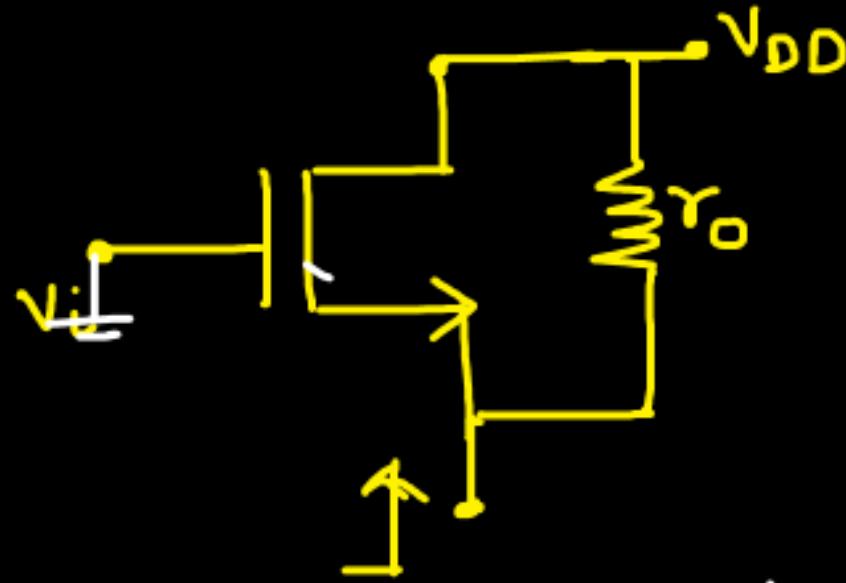


$r_x$  (Small signal resistance)

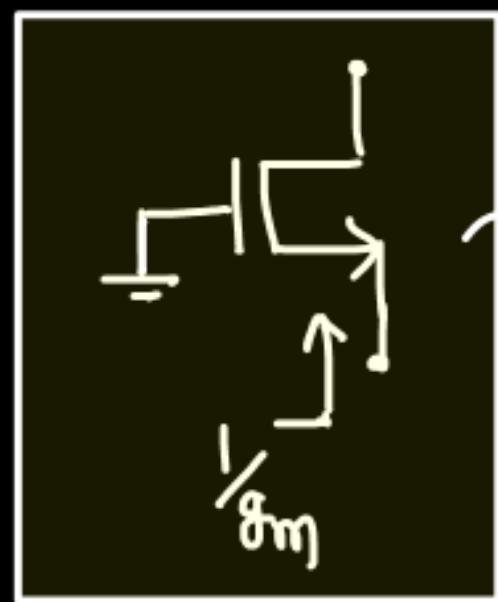

From source to ground, I see  $\frac{1}{gm}$

→

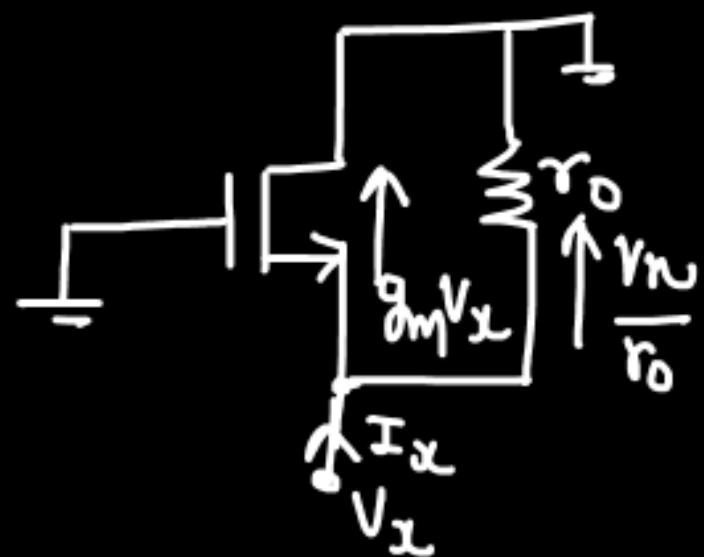

$$V_{gS} = -V_x$$

Nodal @  $V_x$

$$\frac{V_x}{r_o} + g_m V_x = I_x$$



$$V_x \left[ 1 + \frac{g_m r_o}{r_o} \right] = I_x$$

\*\*

$$R_x = \frac{1}{g_m} || r_o$$


$$R_x = \frac{r_o}{1 + g_m r_o}$$

4

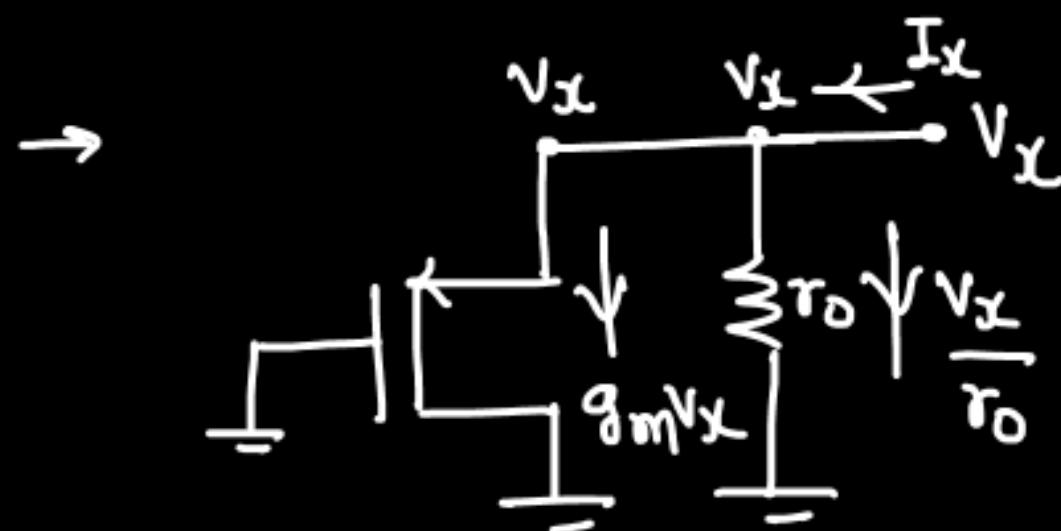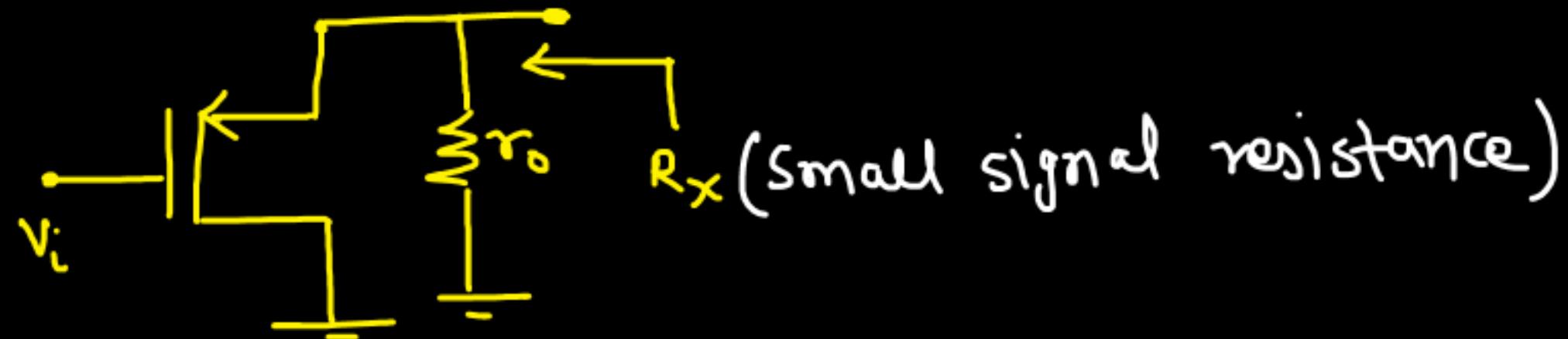


$$g_m V_L + \frac{V_x}{r_o} = I_x$$

\*  $R_x = \frac{1}{g_m} \parallel r_o$

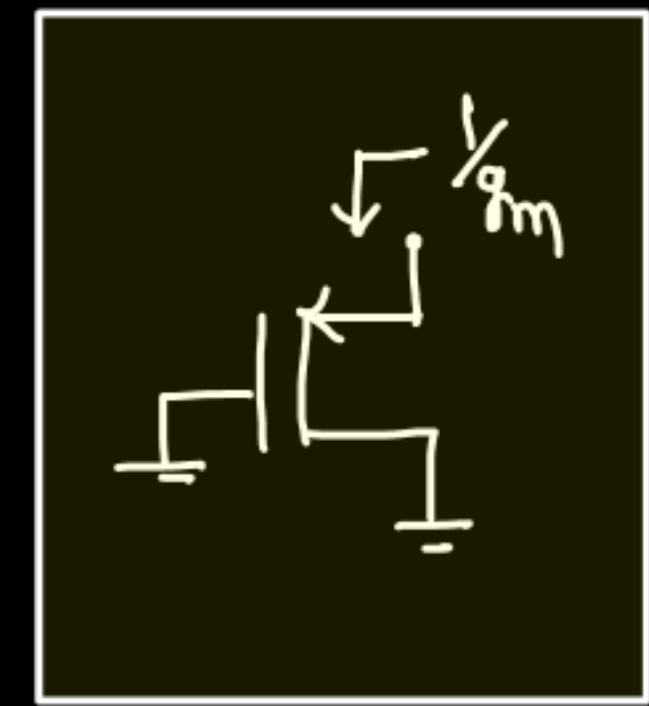

Q.

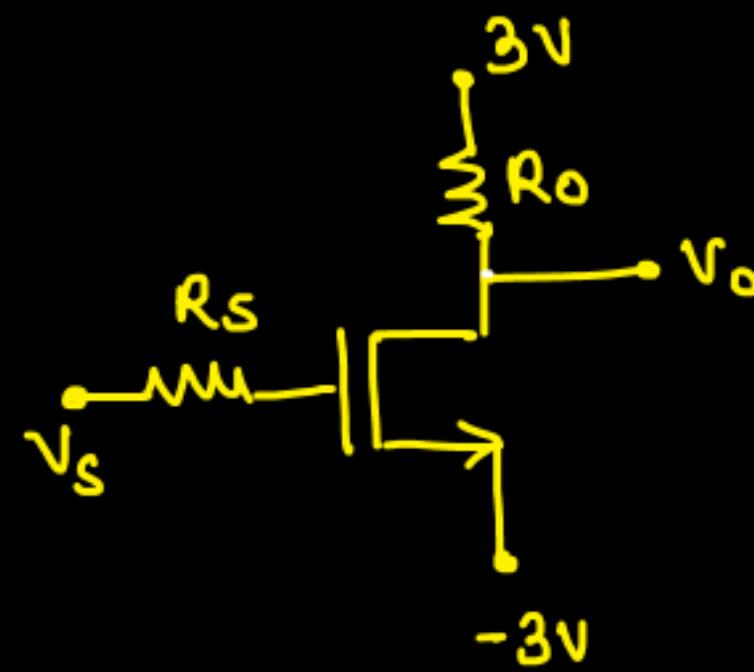

$$m_{nCox} = 100 \mu A/V^2$$

$$w/L = 1$$


$$V_T = 1V$$

$V_s \rightarrow$  small signal source (ac)

① Find  $R_o$  such that quiescent drain voltage is zero. (dc)

② Find small signal voltage gain. ( $\frac{V_o}{V_s}$ )

## DC Analysis

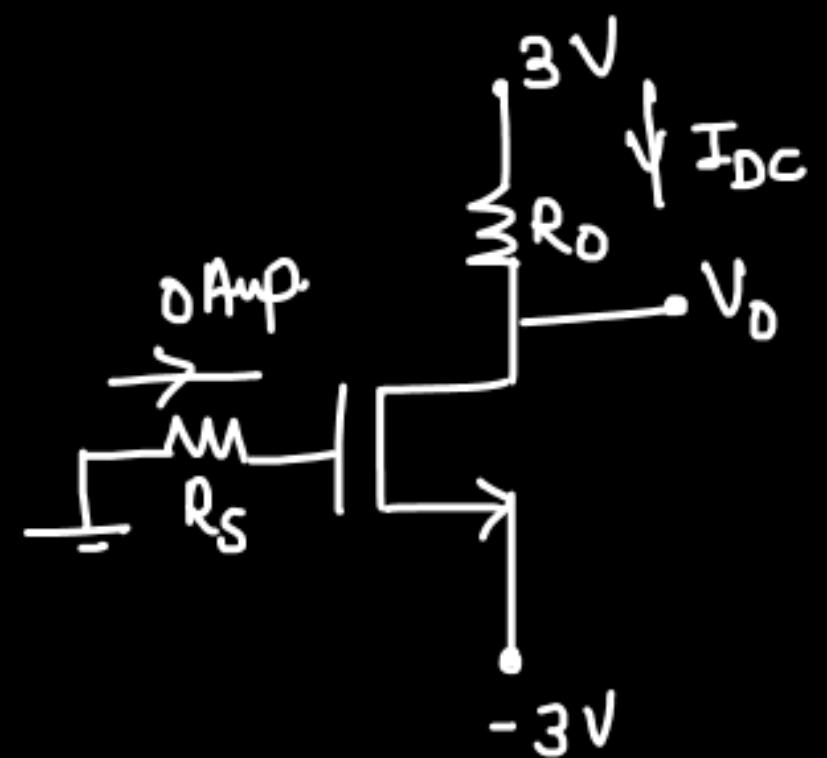

Target  $V_D = 0V$

$$I_{DC} = \frac{m n C_o k w}{2L} (V_{GS} - V_T)^2$$

$$I_{DC} = \frac{100\mu}{2} (3-1)^2$$

$$I_{DC} = 200 \mu \text{Amp}$$

$$V_{DS} = 3V$$

$$V_{GS} = 3V$$

$$V_T = 1V$$

$$V_{OV} = 2V$$

$$V_{DS} > V_{OV} \Rightarrow \text{Sat.}$$


$$V_D = 3 - I_{DC} R_D = 0$$

$$I_{DC} R_D = 3$$

$$R_D = \frac{3}{200\mu}$$

$$\Rightarrow R_D = 15k\Omega$$

## AC Analysis:-

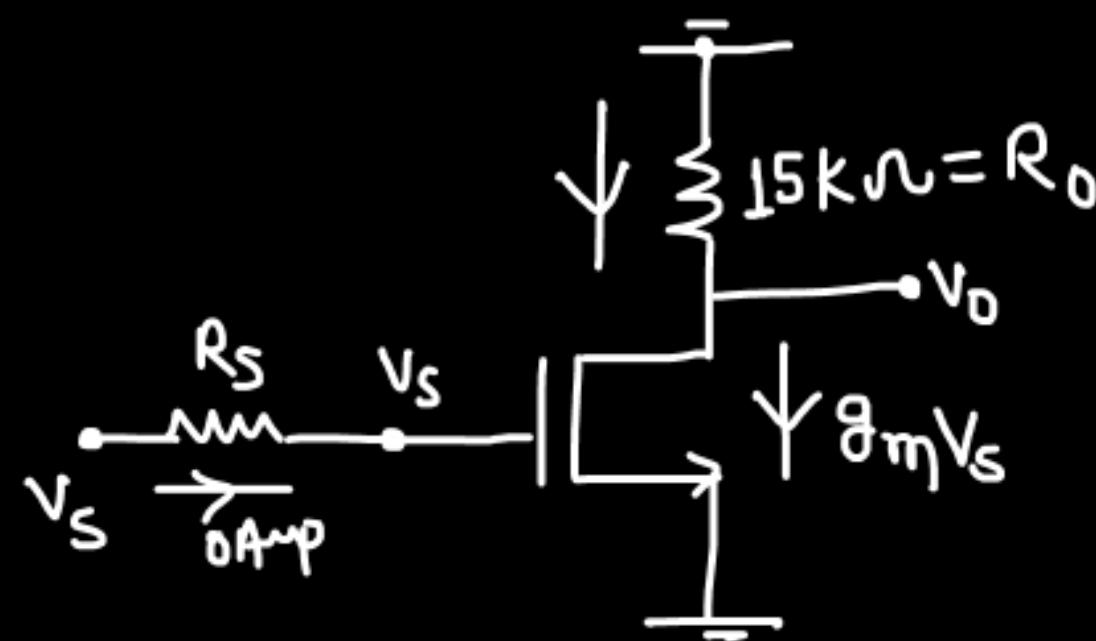

$$\frac{V_0}{V_s} = ?$$

$$V_0 = -g_m V_s \times R_0$$

$$\boxed{\frac{V_0}{V_s} = -g_m R_0}$$

$$R_0 \checkmark = 15k\Omega$$

$g_m$  ?

$$g_m = \frac{m \eta C_o \times W}{L} (V_{GS} - V_T)$$

$$= 100 \mu (3-1)$$

$$\boxed{g_m = 200 \mu \text{A}}$$

$$\frac{V_0}{V_s} = -200 \times 10^{-6} \times 1.5 \times 10^4$$

$$\boxed{\frac{V_0}{V_s} = -3 \text{ V/V}}$$


\* \*

$$g_m = \sqrt{2 \frac{\mu_n C_{ox} W}{L}} I_D = \sqrt{2 \times 100 \mu \times 200 \mu} = 200 \mu V$$

\* \*

$$g_m = \frac{2 I_{DC}}{V_{GS} - V_T} = \frac{2 \times 200 \mu}{2} = 200 \mu V$$


## Common Source Amplifiers:-

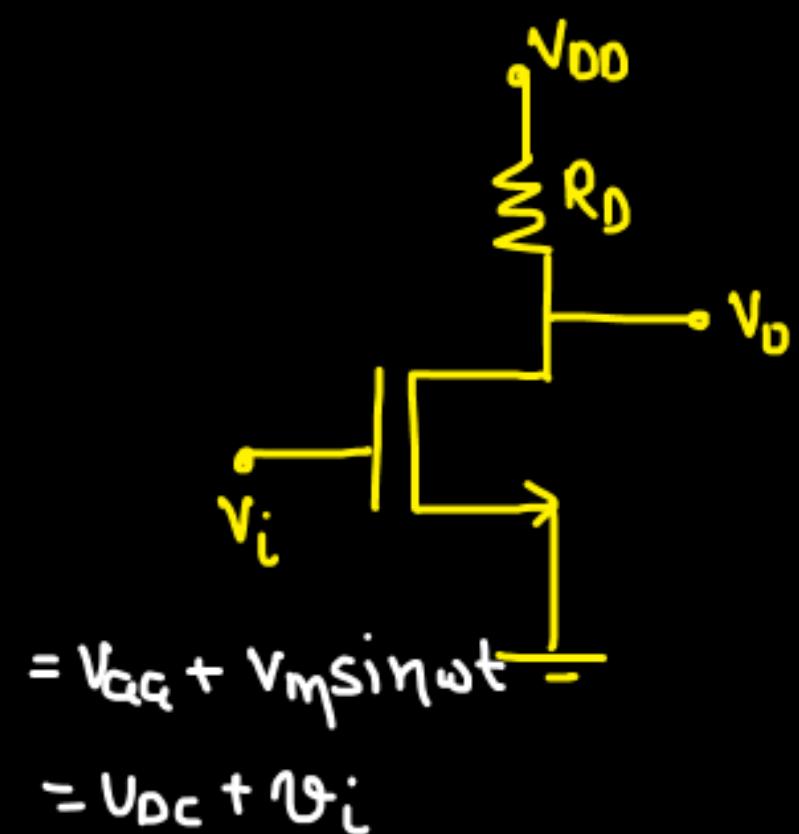

MOS is biased such that it's working in sat' region.

common source amplifier →  
input → Gate , o/p → Drain

## Small signal analysis (ac) :-

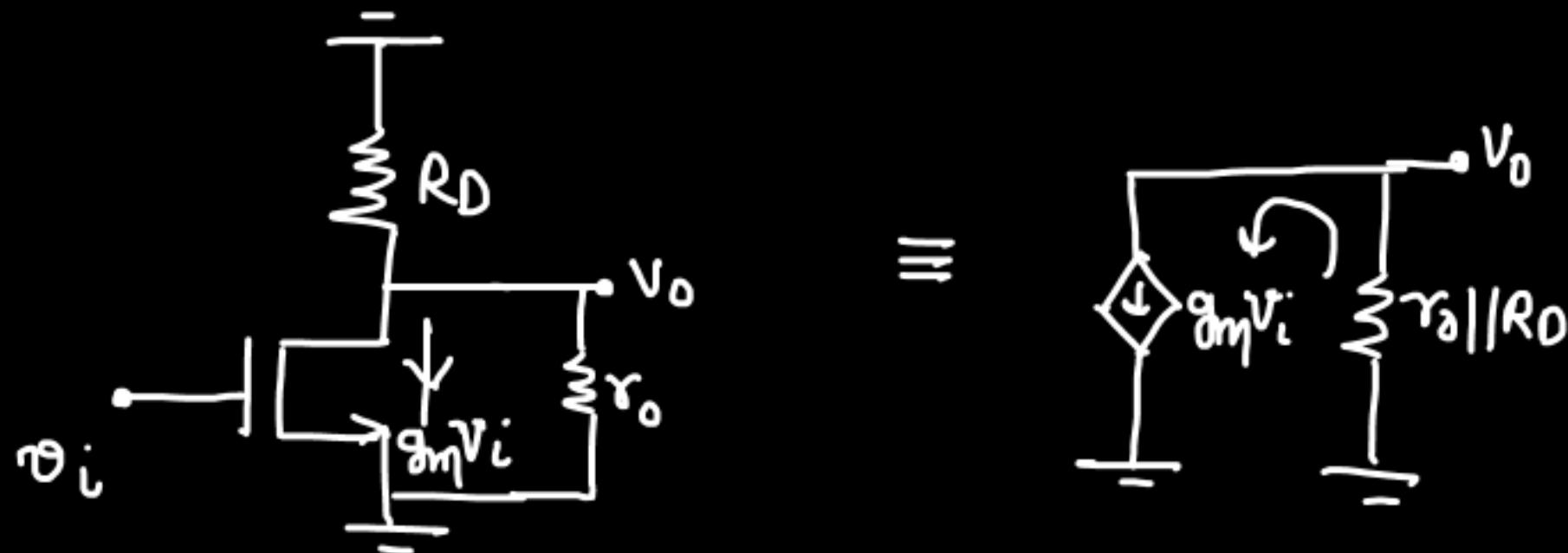


$$v_o = -g_m v_i [R_D || r_o]$$

$$\frac{v_o}{v_i} = -g_m [R_D || r_o]$$


→ small signal  
gain

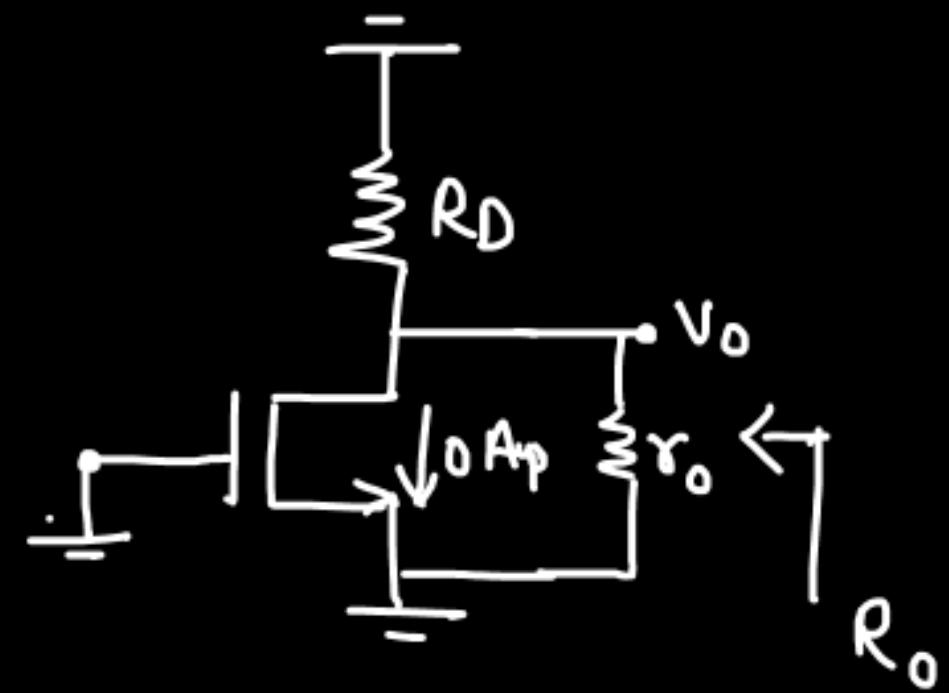② Small signal o/p resistance ( $R_o$ ): -



$$R_o = R_D || r_o$$


③ Small Signal Current gain :-

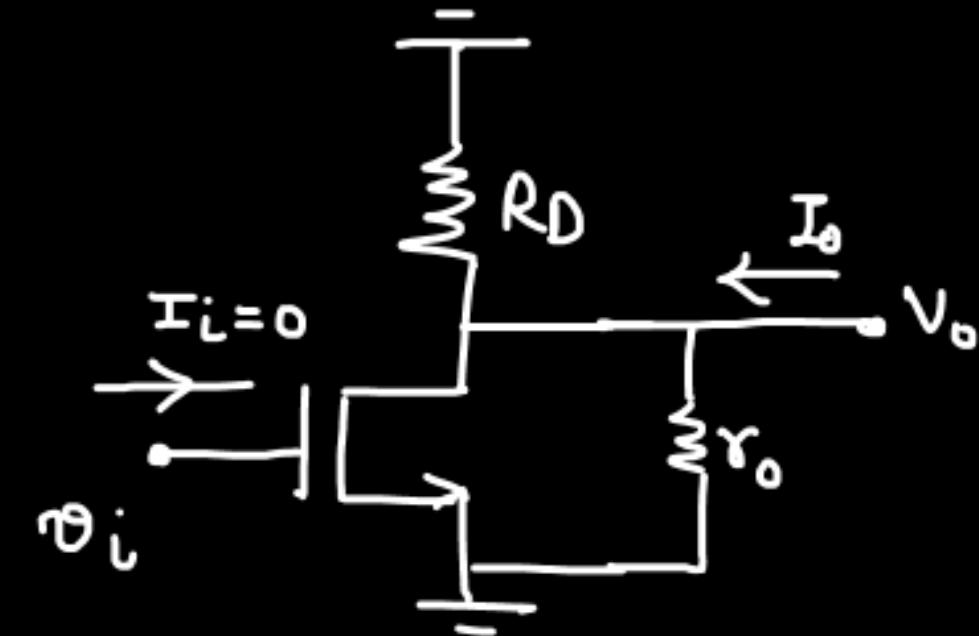

$$\text{Current gain} = \frac{I_o}{I_i} = \frac{I_o}{0}$$

$$A_I = \infty$$

④ Small signal i/p resistance :-

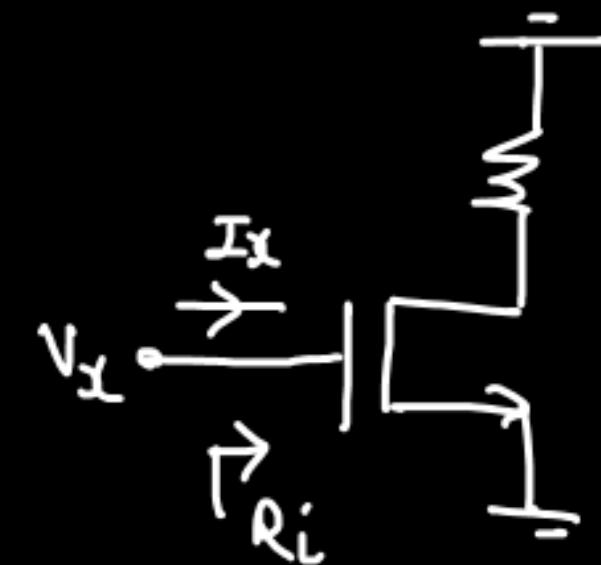

$$R_i = \frac{V_x}{I_x} = \frac{V_x}{0} = \infty$$

$$R_i = \infty$$

## Problem with common source amplifier:-

$$A_V = -g_m R_D \quad [\lambda = 0, \gamma_0 = \infty]$$

$$A_V = -\sqrt{2 \mu_n C_{ox} \omega \frac{L}{I_D}} \times R_D$$

$$T \uparrow \Rightarrow I_D \uparrow$$

$$A_V = f(I_D)$$

$$I_D = g(T)$$


$$A_V = h(T)$$

Because of Temp change, the gain can change  $\Rightarrow$  NOT Desirable

Using diode connected load in common Source


Amplifier:-

---

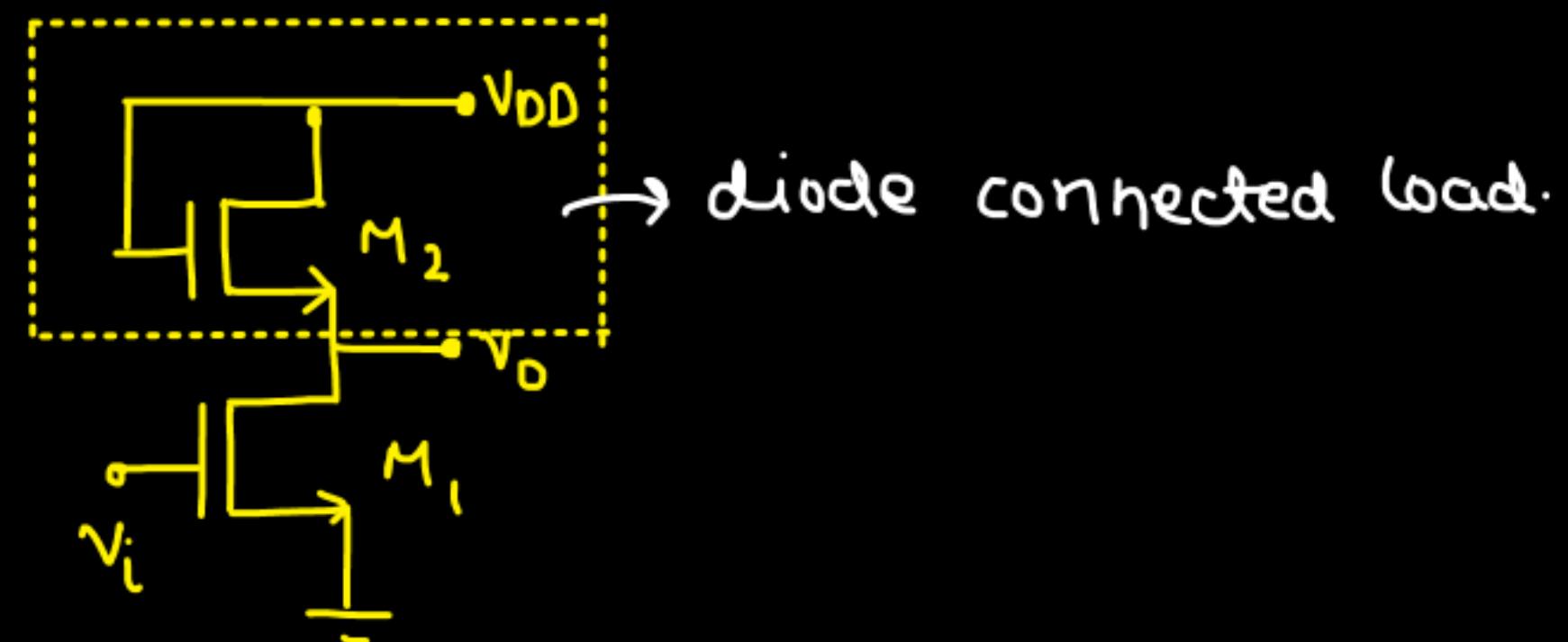

## Small Signal Analysis:-

Assuming [ $\lambda = 0$ ]

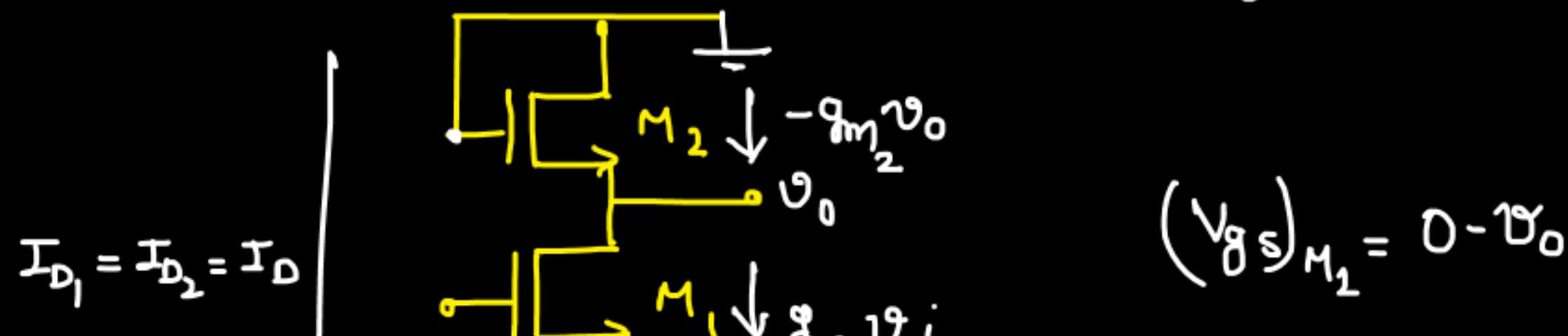

$$g_m v_i = - g_m v_o$$

$$\boxed{\frac{v_o}{v_i} = - \frac{g_m}{g_m}} \rightarrow \text{small signal gain}$$

$$A_V = - \frac{\delta m_1}{\delta m_2}$$


$$A_V = \frac{\sqrt{2(\mu_n \cos \omega) \frac{I_{D1}}{M_1}}}{\sqrt{2(\mu_n \cos \omega) \frac{I_{D2}}{M_2}}}$$

Here  $I_{D1} = I_{D2} = I_D$

$$A_V = \frac{\sqrt{(\frac{\omega}{L})_1}}{\sqrt{(\frac{\omega}{L})_2}} \rightarrow \text{constant gain}$$

$$\frac{\omega}{L} \neq f(\tau)$$

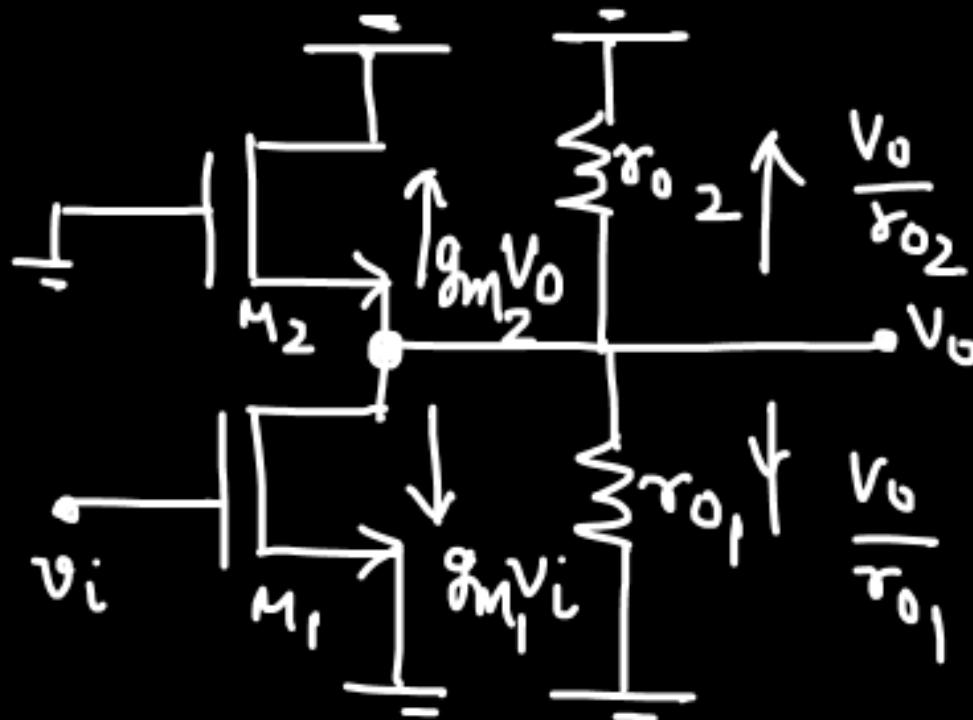$\Rightarrow$  Small signal gain considering  $\lambda \neq 0$



KCL @  $v_o$  :-

$$g_{m2}v_o + g_{m1}v_i + \frac{v_o}{r_{o2}} + \frac{v_o}{r_{o1}} = 0$$

$$\left[ \frac{v_o}{\frac{1}{g_{m2}} || r_{o1} || r_{o2}} \right] = -g_{m1}v_i$$

$$v_o \left[ g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}} \right] = -g_{m1}v_i$$


$$\frac{V_o}{V_i} = -g_m \left[ \frac{1}{g_m} || r_{o1} || r_{o2} \right]$$

→ small signal  
gain

if  $r_{o1} = r_{o2} = \infty$

$$\frac{V_o}{V_i} = -\frac{g_m}{g_m}$$


M-II

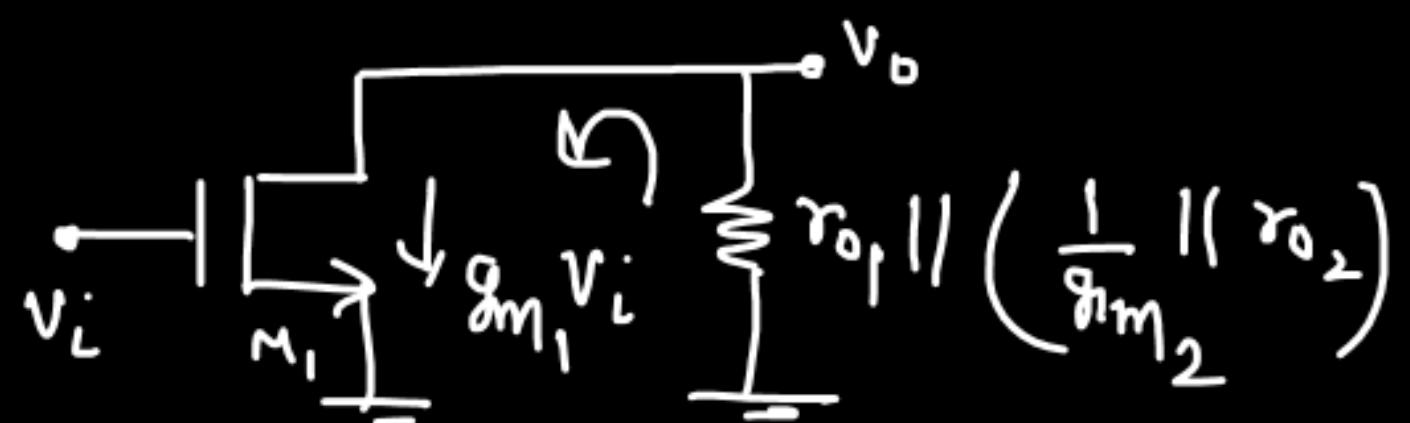

$$V_o = -g_m \left[ r_{o1} || \frac{1}{g_m} || r_{o2} \right] V_i$$

$$\frac{V_o}{V_i} = -g_m \left[ r_{o1} || r_{o2} || \frac{1}{g_m} \right]$$

O/p resistance :-

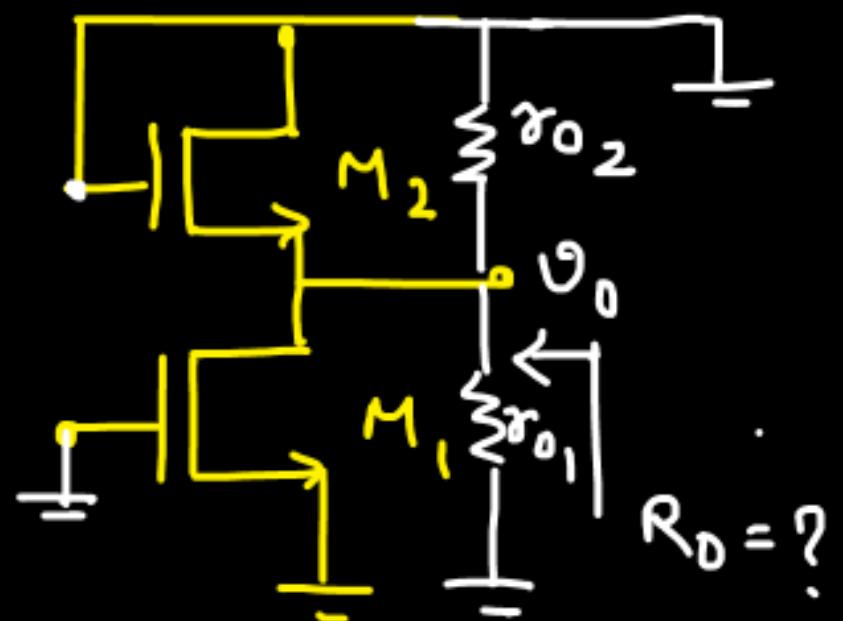


$$R_o = r_{o1} || r_{o2} || \frac{1}{g_m2}$$


if  $\lambda=0 \Rightarrow r_{o1} = r_{o2} = \infty$

$$R_o = \frac{1}{g_m2}$$
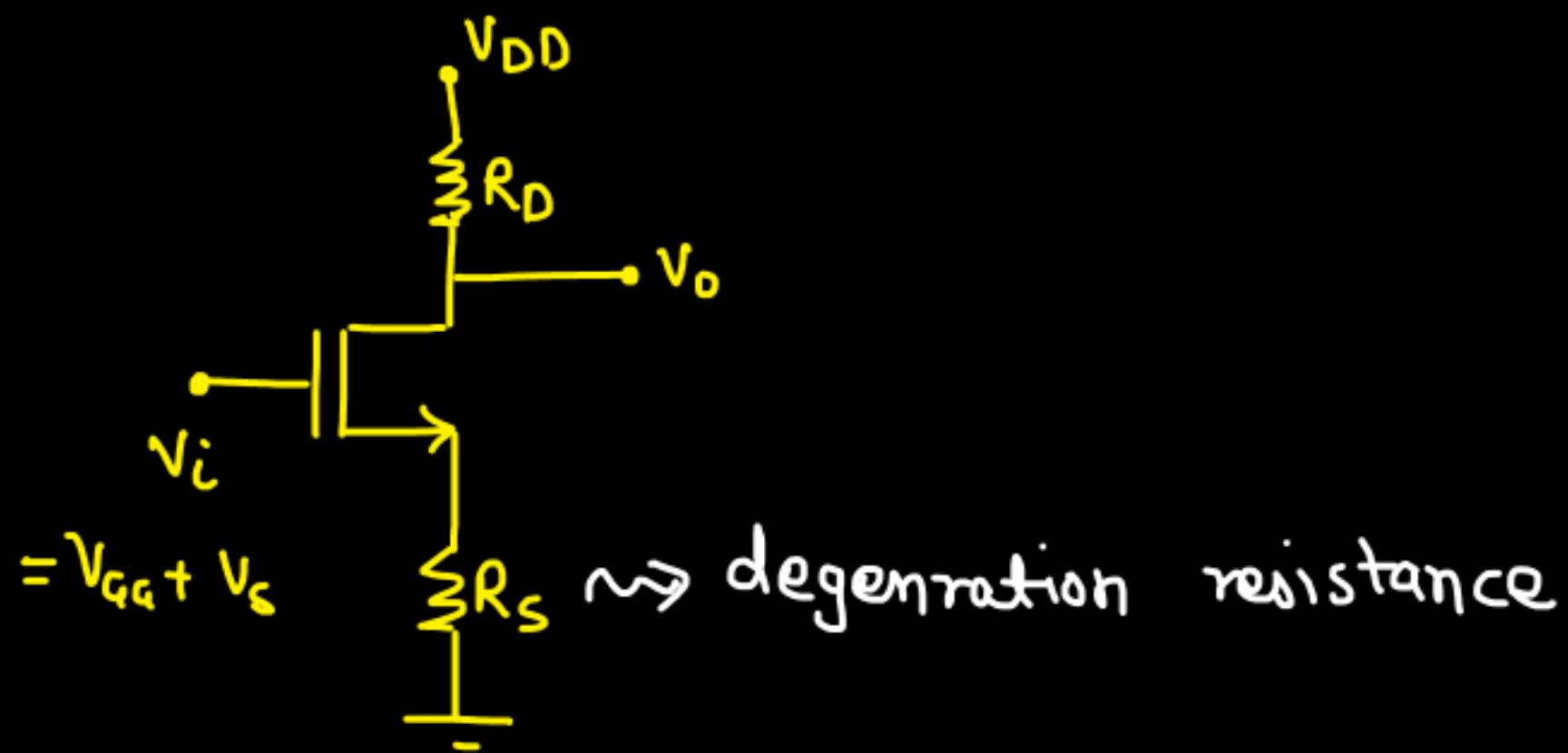
## Common source Amplifier with degeneration:-



## DC Analysis:-

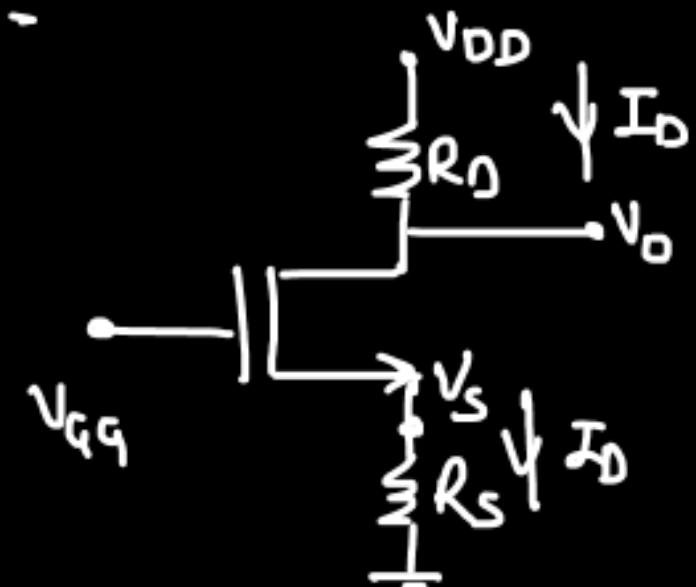


Let's assume, Because of Temp.  $I_D \uparrow$

$I_D \uparrow \Rightarrow V_S \uparrow \Rightarrow V_{GS} \downarrow \Rightarrow I_D \downarrow$

$\Rightarrow$  Stability achieved

## Small Signal Analysis:-

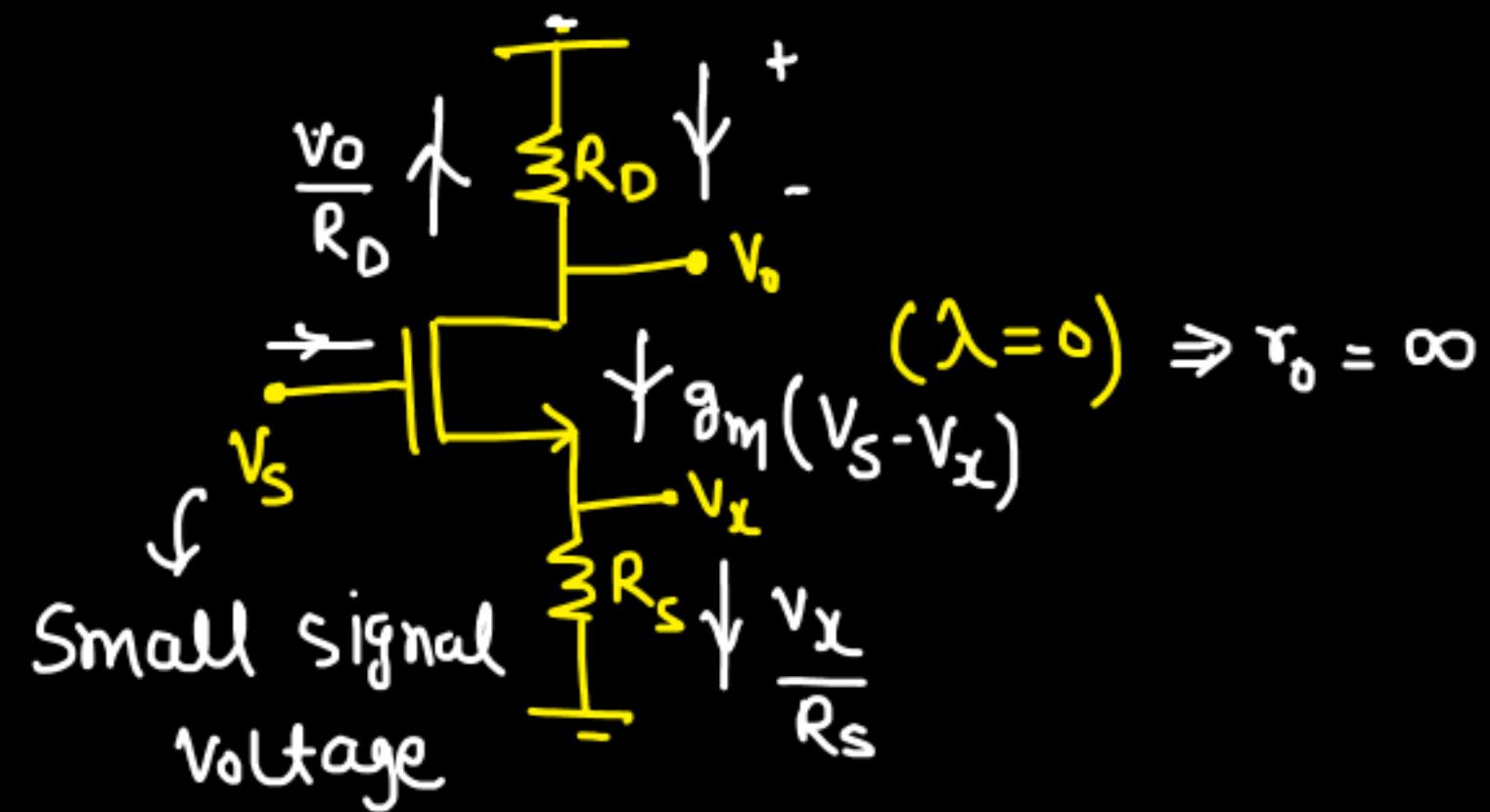

$$V_o = -g_m (V_s - V_x) \times R_D$$

$$V_o = -g_m R_D (V_s - V_x) \quad \textcircled{1}$$

$$\frac{V_o}{R_D} = -\frac{V_x}{R_s} \quad \Rightarrow \quad V_x = -\frac{R_s}{R_D} V_o \quad \textcircled{2}$$

By eqn ① and ②

$$V_o = -g_m R_D \left[ V_s + \frac{R_S}{R_D} V_o \right]$$

$$V_o = -g_m R_D V_s - g_m R_S V_o$$

$$V_o [1 + g_m R_S] = -g_m R_D V_s$$

$$\frac{V_o}{V_s} = \frac{-g_m R_D}{1 + g_m R_S} \rightarrow \text{small signal voltage gain}$$


Current gain:-

$$\alpha_I = \frac{I_o}{I_i} = \frac{I_o}{0} = \infty$$

Input Resistance:-

$$R_{in} = \frac{V_i}{I_i} = \frac{V_i}{0} = \infty$$

Voltage gain considering  $r_o$  :-

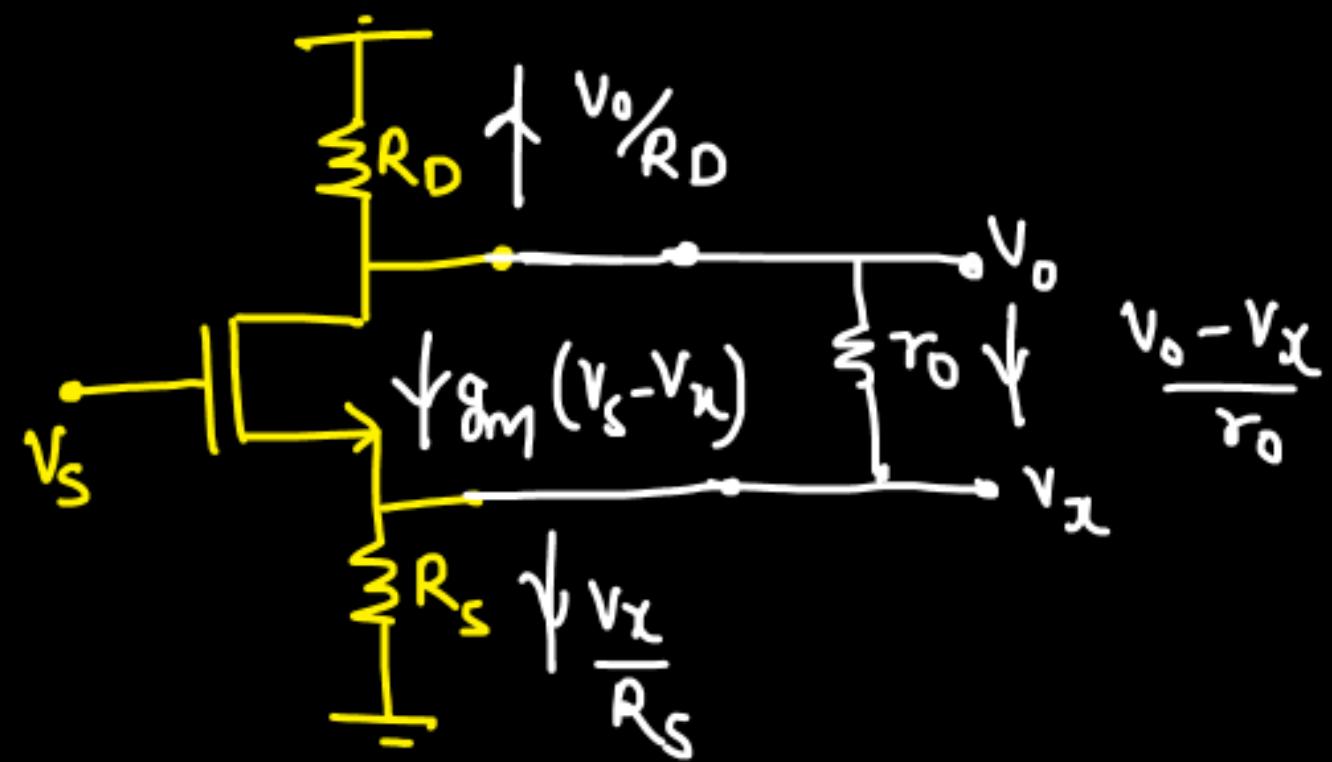

KCL @  $v_o$

$$g_m(v_s - v_x) + \frac{v_o}{R_D} + \frac{v_o - v_x}{r_o} = 0 \quad \textcircled{1}$$

$$\frac{v_o}{R_D} = -\frac{v_x}{R_s} \Rightarrow v_x = -\frac{R_s}{R_D} v_o \quad \textcircled{2}$$

By eq<sup>n</sup> ① and ②

$$g_m \left( V_S + \frac{R_S}{R_D} V_O \right) + \frac{V_O}{R_D} + \frac{V_O}{r_o} \left[ 1 + \frac{R_S}{R_D} \right] = 0$$

$$g_m V_S + V_O \left[ \frac{g_m R_S}{R_D} + \frac{1}{R_D} + \frac{1}{r_o} + \frac{R_S}{r_o R_D} \right] = 0$$

$$g_m V_S = - V_O \left[ \frac{g_m r_o R_S + r_o + R_D + R_S}{r_o R_D} \right]$$


$$\frac{V_O}{V_S} = - g_m R_D \left[ \frac{r_o}{g_m r_o R_S + r_o + R_D + R_S} \right]$$

if  $r_o = \infty$  [very large]


$$\frac{V_0}{V_S} = -g_m R_D \left[ \frac{\gamma_0}{g_m r_0 R_S + \gamma_0} \right]$$

$$\frac{V_0}{V_S} = -\frac{g_m R_D}{1 + g_m R_S}$$

O/P resistance :-

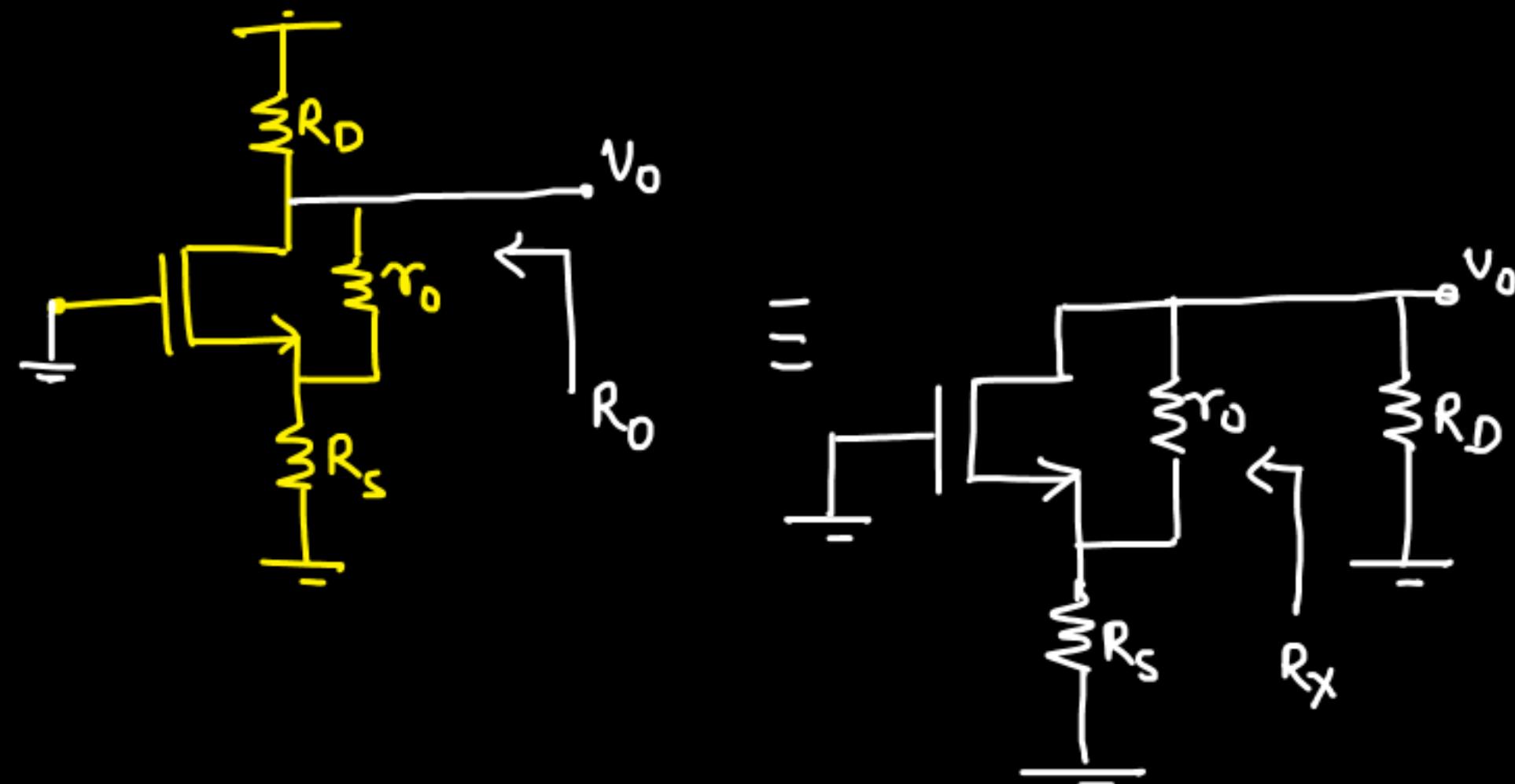

$$R_o = R_D \parallel R_X$$

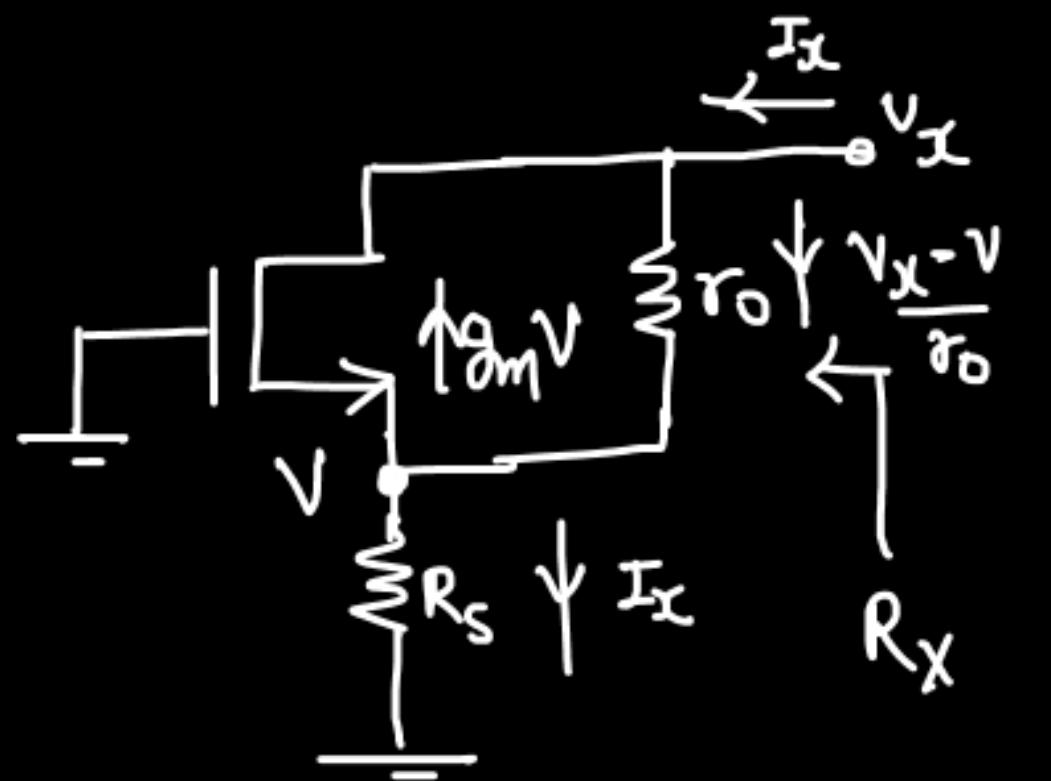

$$R_x = \frac{V_x}{I_x}$$

Nodal @  $V_x$  :-

$$I_x + g_m V = \frac{V_x - V}{r_0}$$

$$I_x r_0 + g_m r_0 V = V_x - V \quad \text{--- (1)}$$

$$V = I_x R_s \quad \text{--- (2)}$$

By eqn ① and ②

$$I_x r_0 + g_m r_0 [I_x R_S] = V_x - I_x R_S$$


$$I_x [r_0 + g_m r_0 R_S + R_S] = V_x$$

$$R_x = \frac{V_x}{I_x} = R_S + r_0 + g_m r_0 R_S \approx g_m r_0 R_S \quad \left\{ \begin{array}{l} g_m r_0 R_S \gg R_S \\ r_0 \end{array} \right\}$$

$$R_x = R_S + (1 + g_m R_S) r_0$$

$$R_x = r_0 + (1 + g_m r_0) R_S$$

To REMEMBER:-

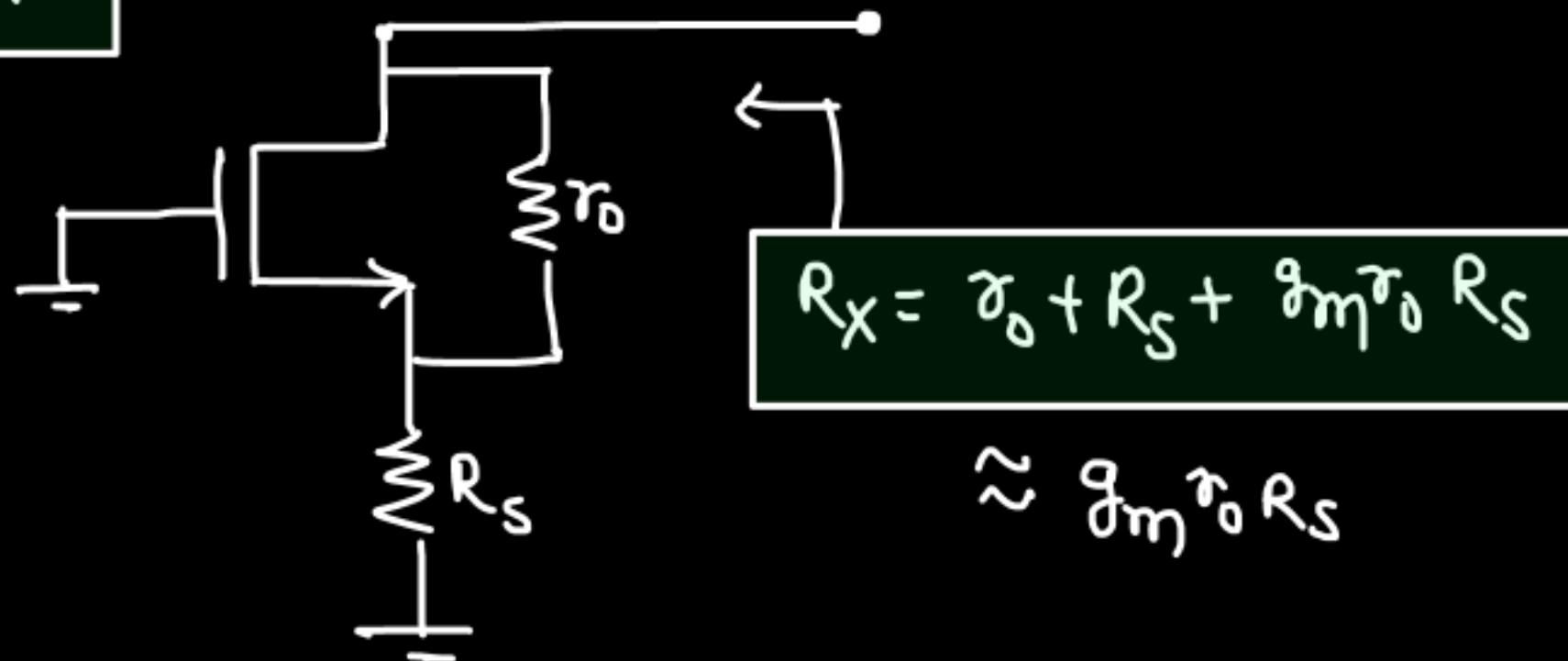

$$R_X = r_o + R_S + g_m r_o R_S$$


$$\approx g_m r_o R_S$$


O/P resistance:-

$$R_o = R_D \parallel R_X$$

$$R_o = \underbrace{R_D}_{\approx r_o} \parallel (r_o + R_S + g_m r_o R_S)$$
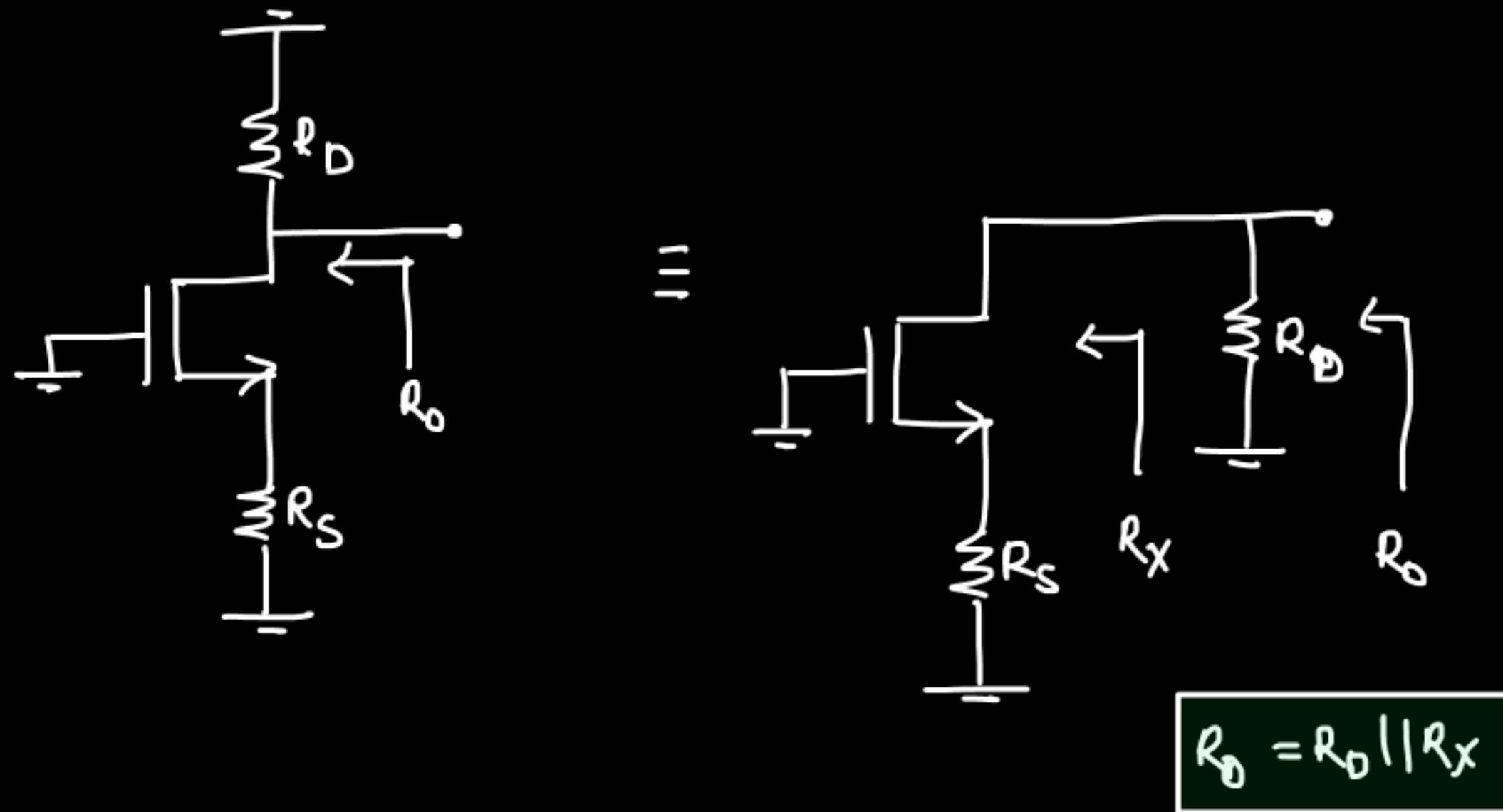
## \* O/P resistance of common source with degeneration ( $\lambda=0$ )



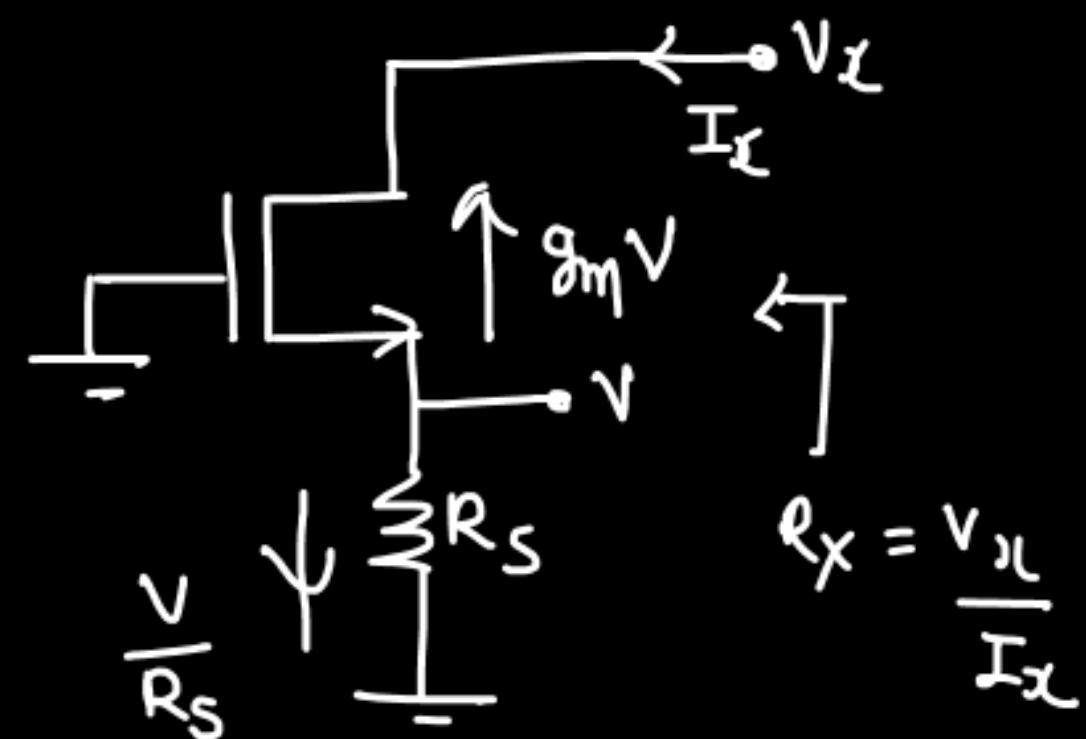

$$R_X = \frac{V_L}{I_L}$$

$$g_m V = -I_L \quad \textcircled{1}$$

$$\frac{V}{R_S} = I_L \quad \textcircled{2}$$

By eq<sup>n</sup> ① and ②

$$g_m I_X R_S = -I_L$$

$$I_X [g_m R_S + 1] = 0$$

$$I_X = 0$$

$$\Rightarrow R_X = \frac{V_L}{0} = \infty$$


$$R_o = R_D \parallel R_X$$

$$R_o = R_D \parallel \infty$$


$$\therefore R_o = R_D$$

## Common Source Amplifier:-

without degeneration

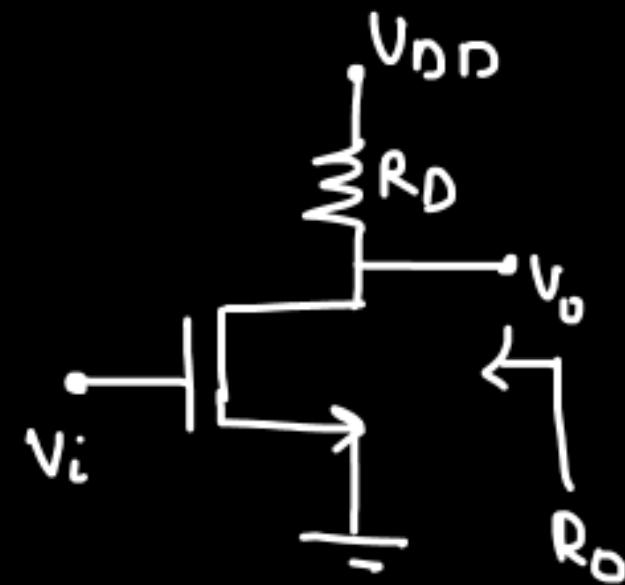

with degeneration

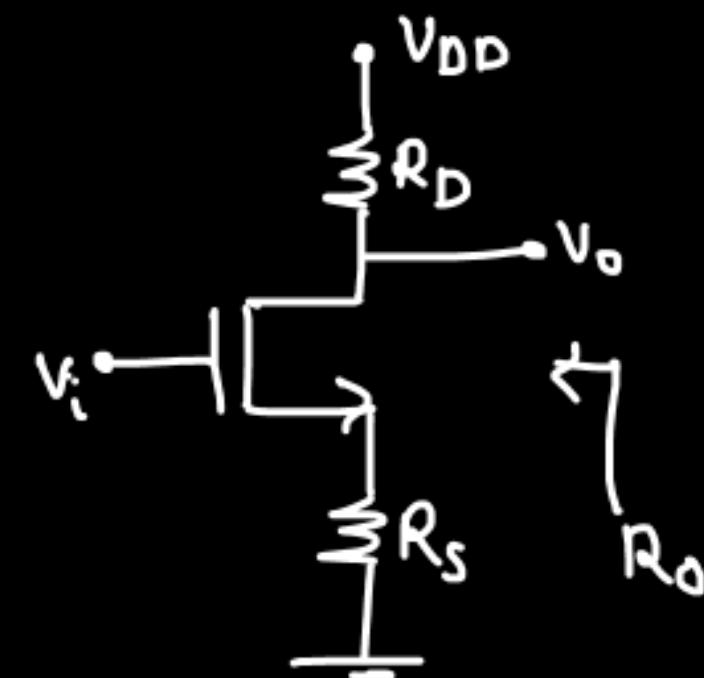


- ① less stability
- ②  $\frac{V_o}{V_i} = -g_m R_D \rightarrow$  more gain
- ③  $R_{out} = R_D \parallel r_o$

- ① Better stability
- ②  $\frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} \rightarrow$  less gain
- ③  $R_{out} = R_D \parallel (R_S + r_o + g_m R_S r_o)$

## Best way of biasing a Common Source Amplifier:-

### \* Previous biasing:-

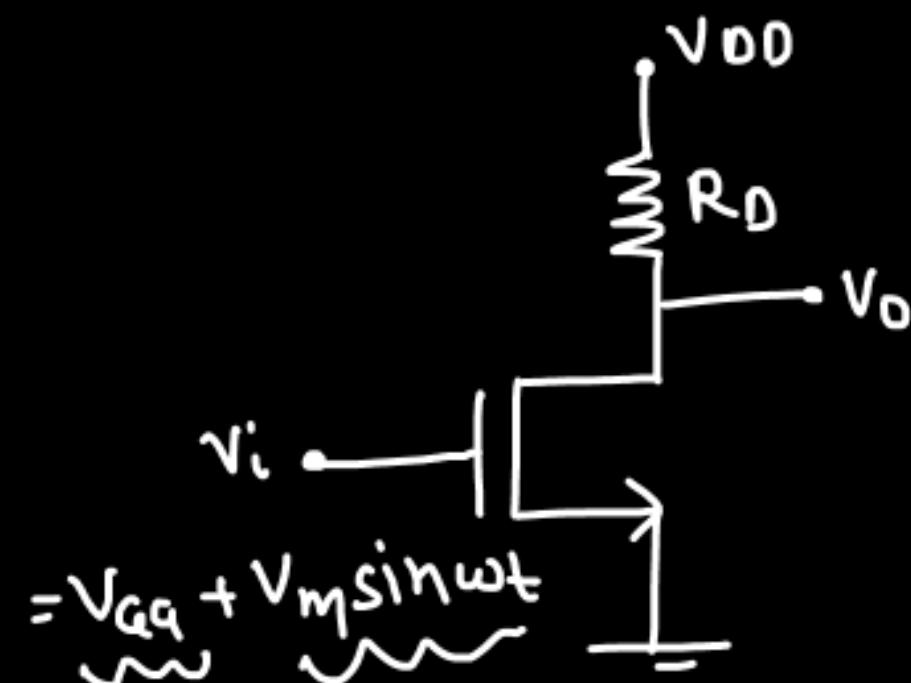


Here, for giving the dc bias, you need to use two supplies  $V_{DD}$  and  $V_{QQ}$

↓  
NOT DESIRABLE

⇒ I will use only one supply.


## New way of biasing:-

①

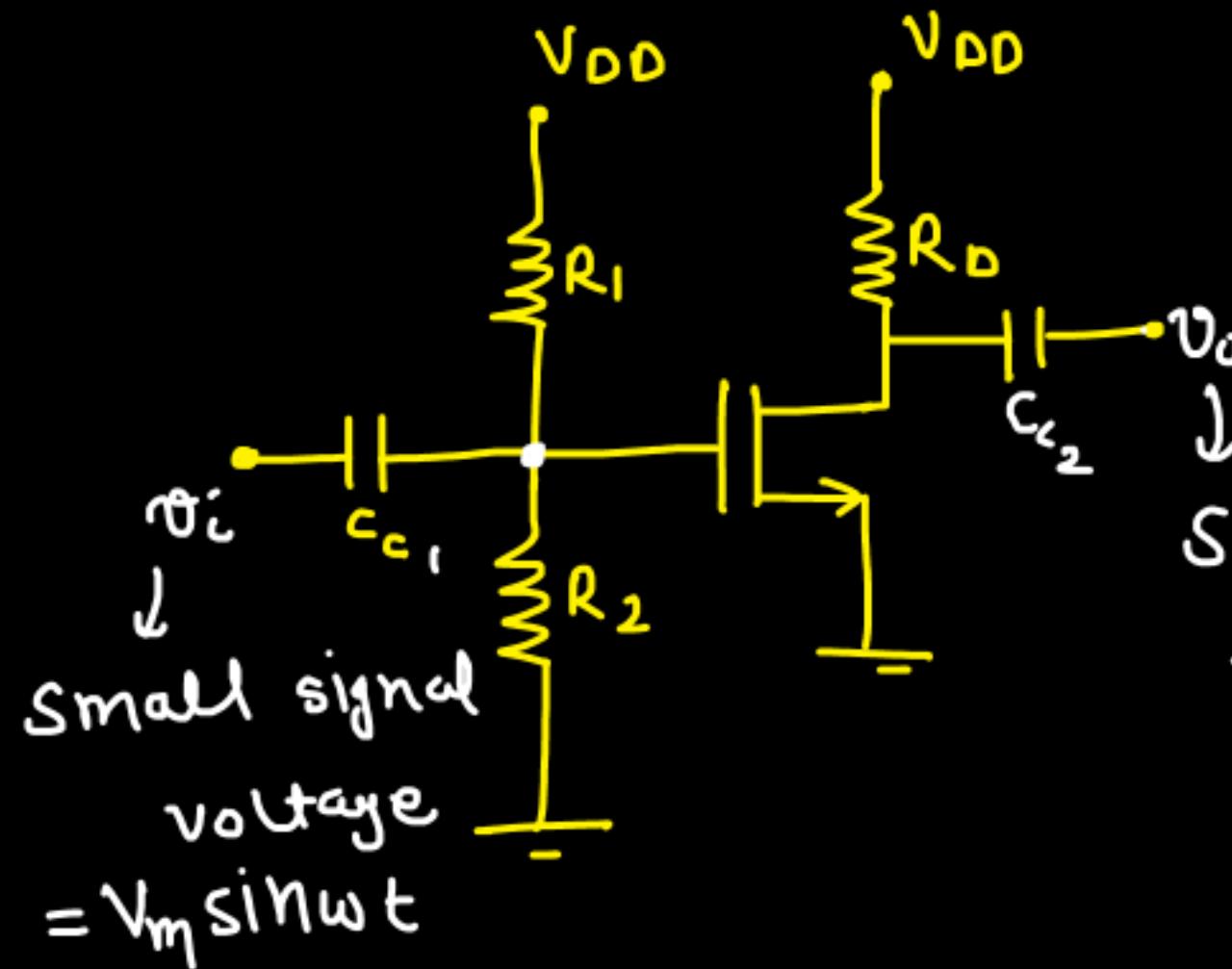

Small  
signal  
o/p

DC analysis:-

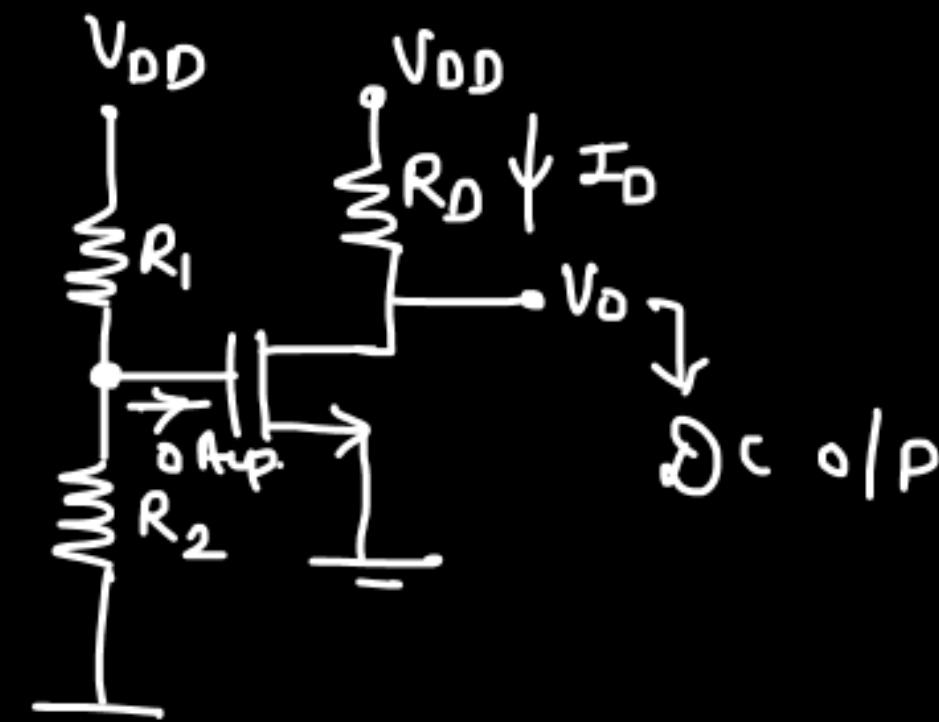

① Set  $R_1$  and  $R_2$ ; such that  $V_{GS} > V_T$

$$\frac{V_{DD} \times R_2}{R_2 + R_1} > V_T$$


$$V_{GS} = \frac{V_{DD} R_2}{R_2 + R_1}$$

$$I_D = \frac{4\pi \epsilon_0 \omega}{2L} (V_{GS} - V_T)^2$$

$$\Rightarrow V_o = V_{DD} - I_D R_D$$


② Set  $R_2$ ,  $R_1$  and  $R_D$  such that  $V_{DS} > V_{GS} - V_T$   $\rightarrow$  Ensuring sat. region

⇒ AC Analysis:-

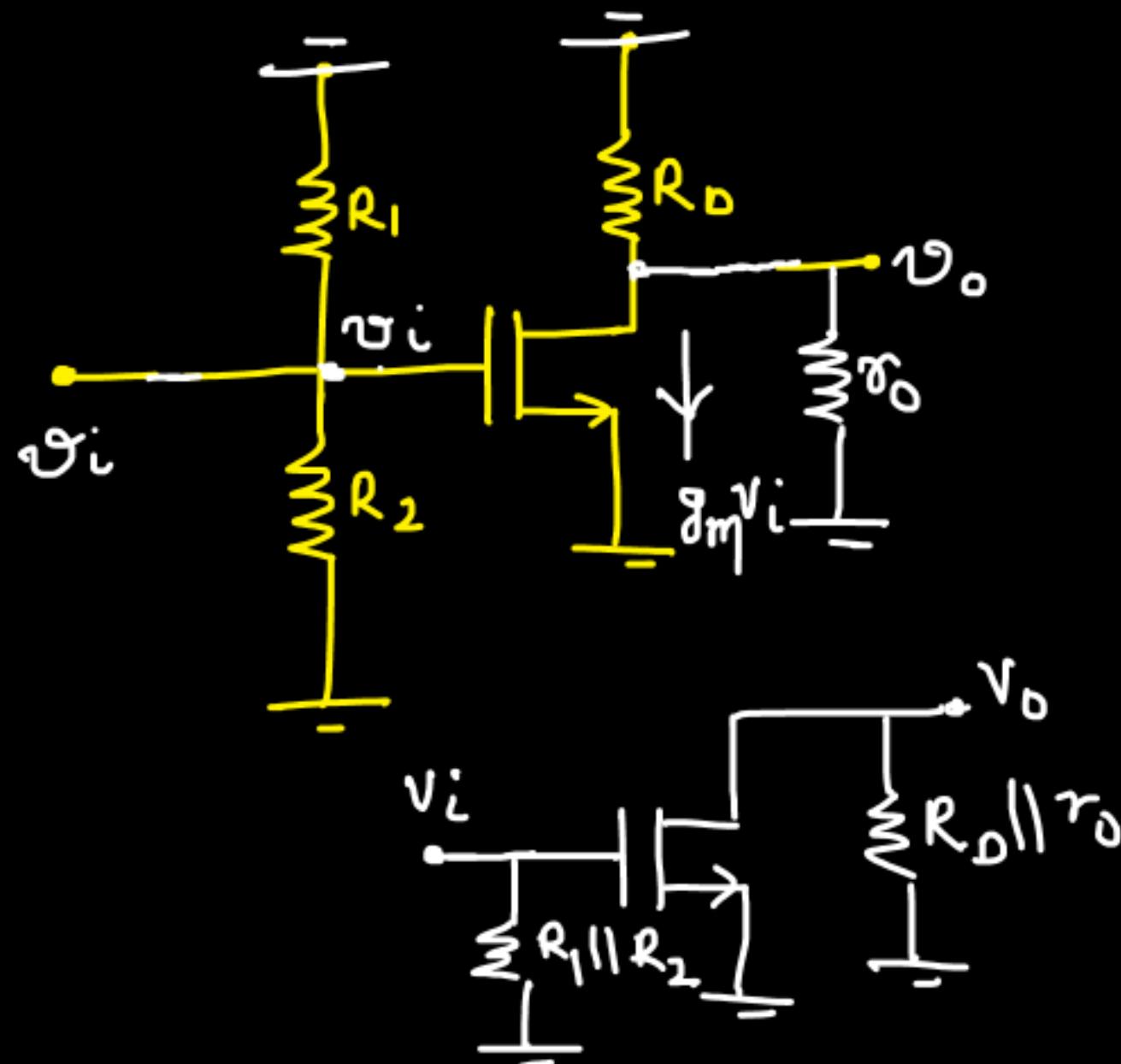


$$V_{GS} = V_i$$

$\Rightarrow$

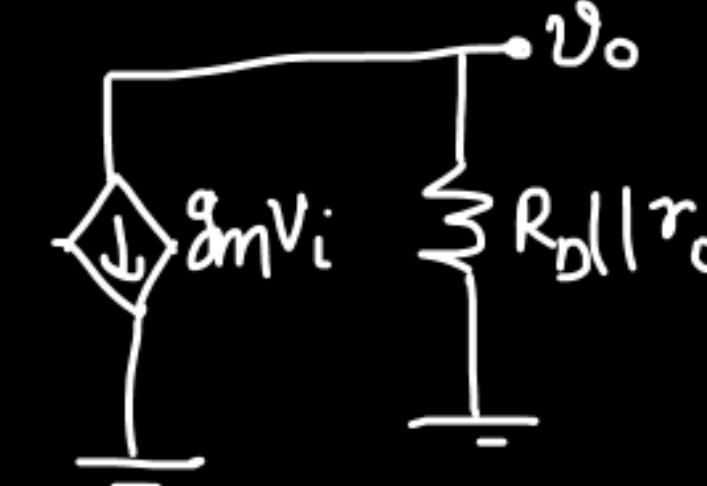

$$\frac{V_o}{V_i} = -g_m (R_D \parallel r_o) \rightarrow \text{Voltage gain} =$$

## Small Signal i/p resistance:-

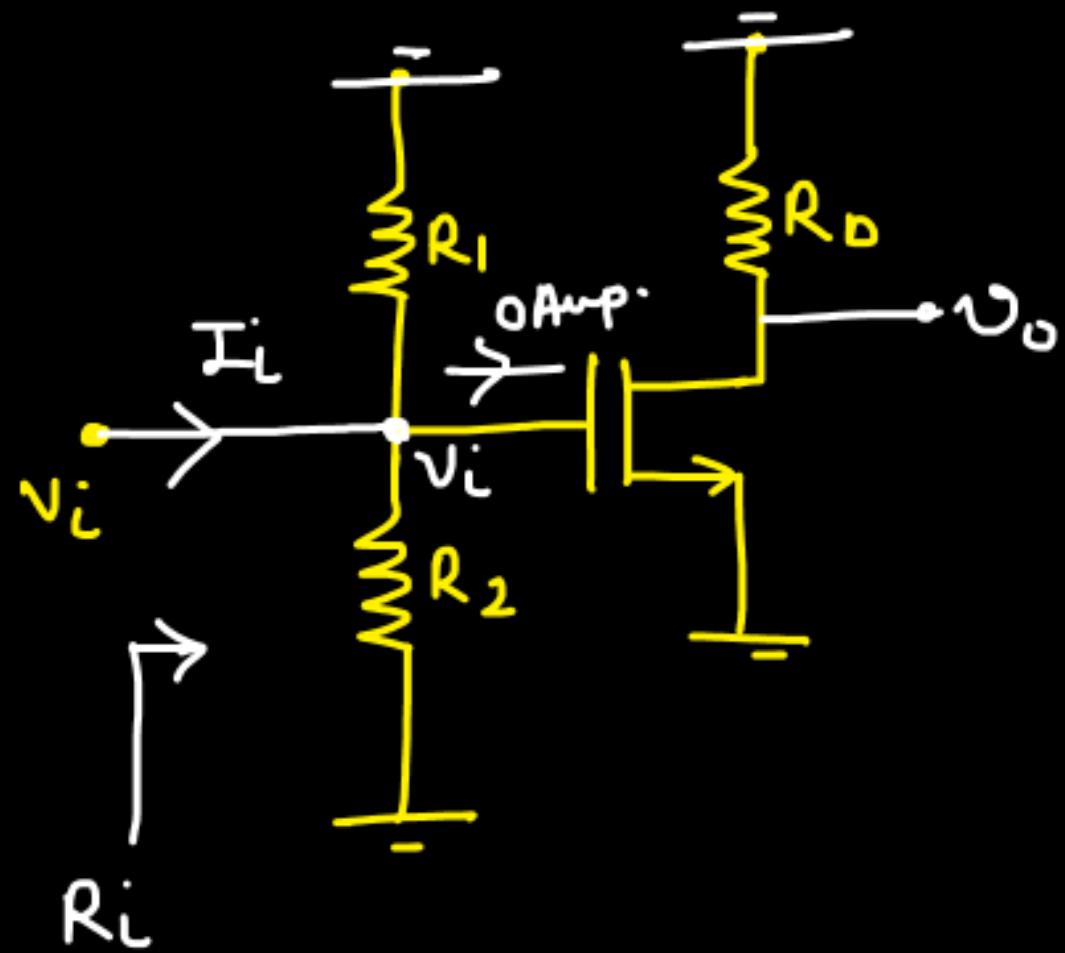

$$R_i = \frac{v_i}{I_i}$$


Nodal @  $v_i$

$$\frac{v_i}{R_1} + \frac{v_i}{R_2} = I_i$$

$$\frac{v_i}{I_i} = R_1 \parallel R_2$$

$$R_i = R_1 \parallel R_2$$

O/P resistance:-

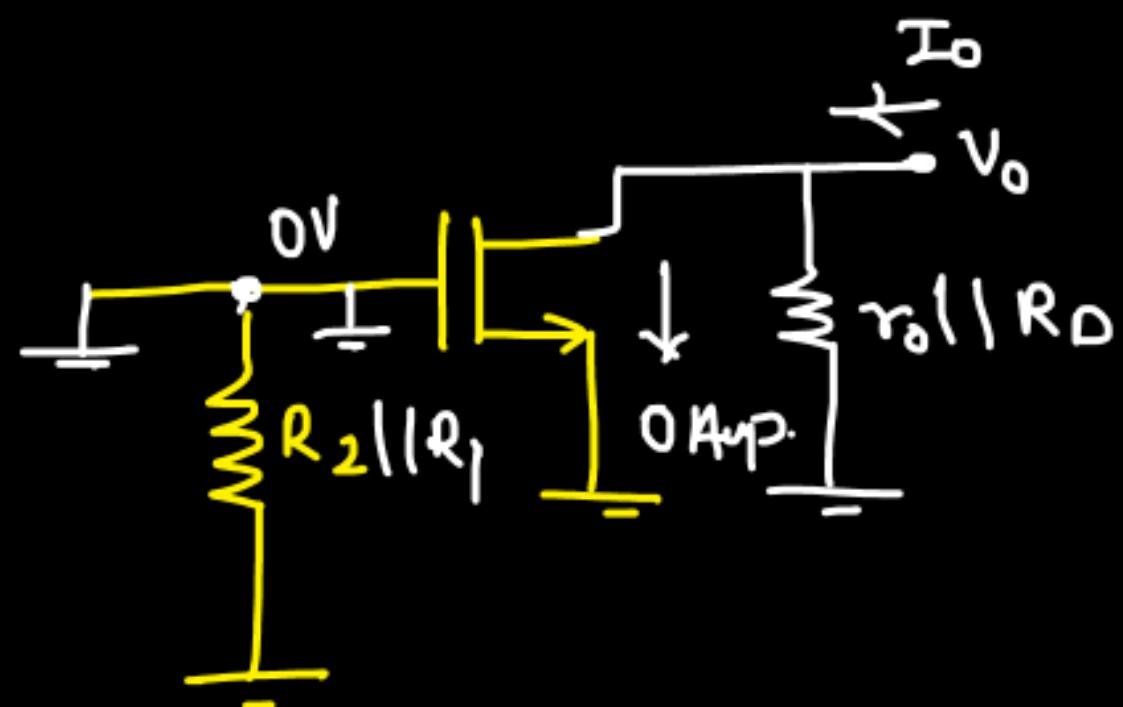


$$V_{gs} = 0V$$

$$R_{out} = r_o \parallel R_D$$


Why we use coupling capacitor ( $C_c$ ) ?

- ① Helps in isolating the dc bias setting.
- ② If you are cascading two or more stages, then only ac signal from the 1<sup>st</sup> stage will pass to the next stage while dc is blocked.

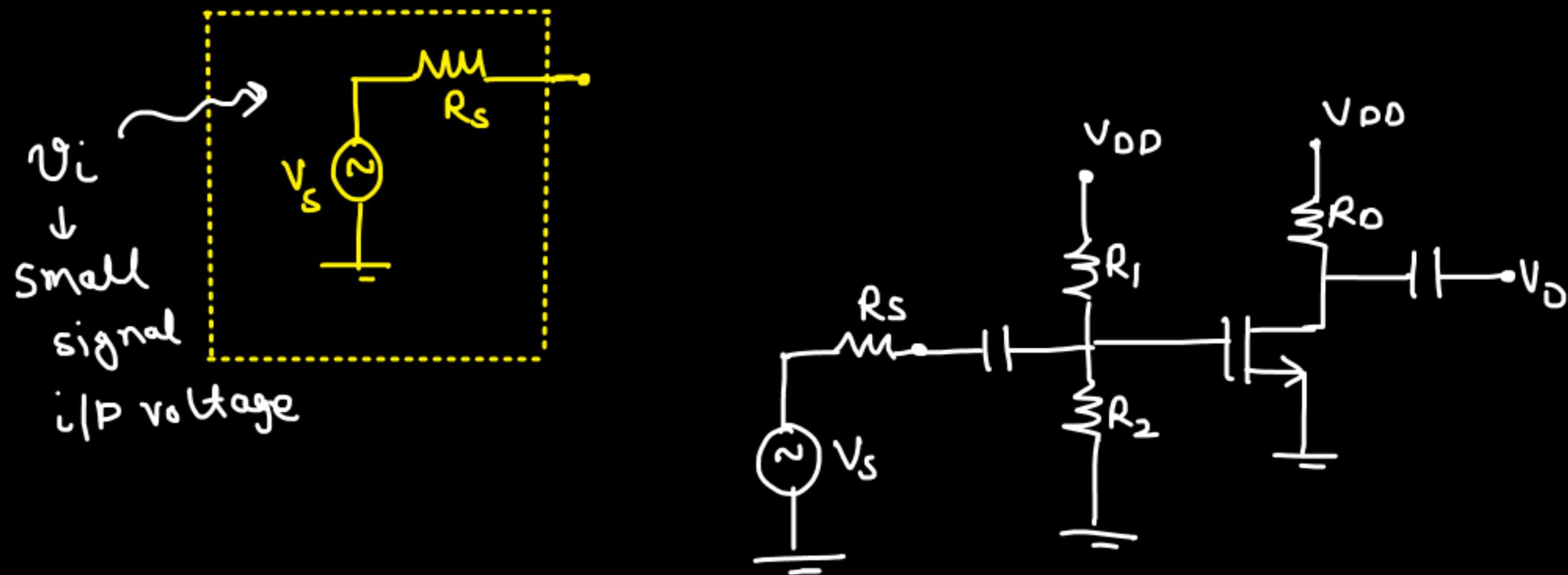If small signal input source has some  
Resistance  $R_s$ .



## Small Signal Analysis:-

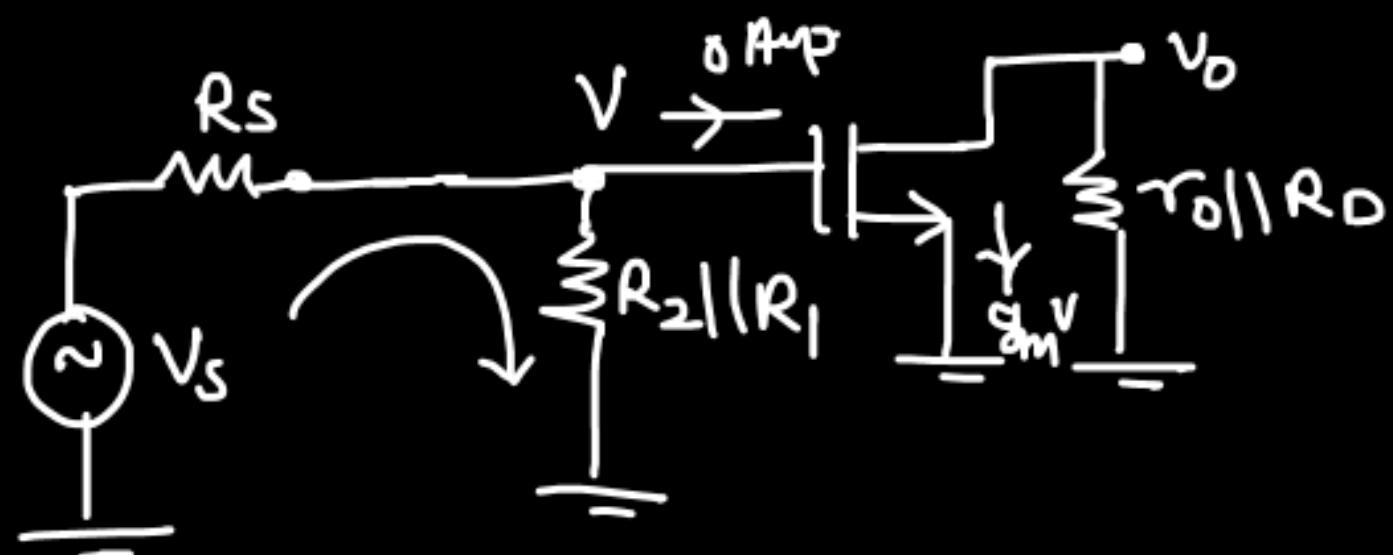

$$V_o = -g_m V [R_o || r_o]$$


$$V_o = -g_m [R_o || r_o] V = 0 \quad \text{--- (1)}$$

$$V = \frac{R_2 || R_1}{(R_2 || R_1) + R_s} \times V_s \quad \text{--- (2)}$$


$$\alpha_v = \frac{V_o}{V_s} = -g_m [R_o || r_o] \times \frac{[R_2 || R_1]}{[R_2 || R_1] + R_s}$$

→ Voltage gain

input resistance :-

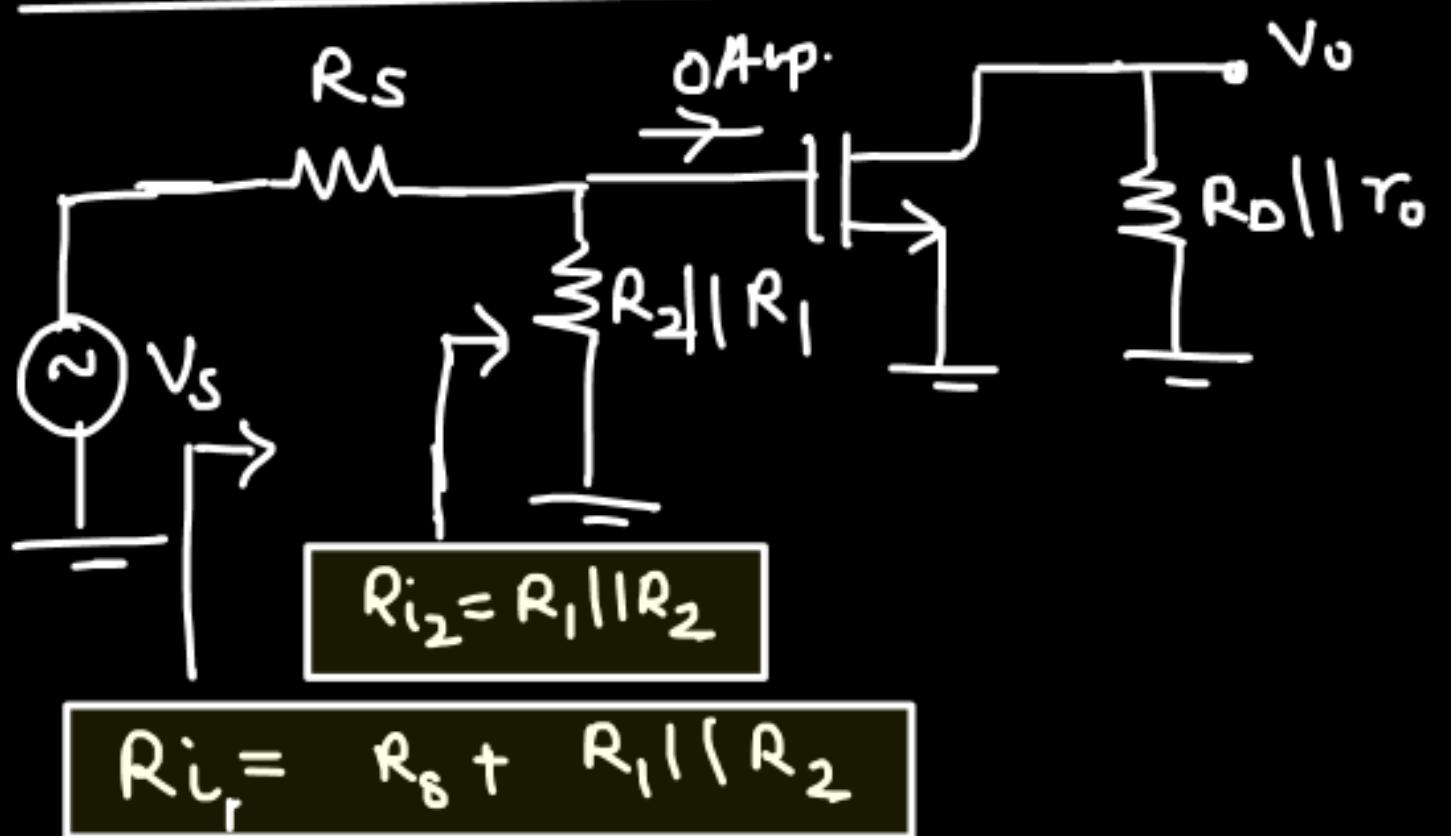


output resistance:-

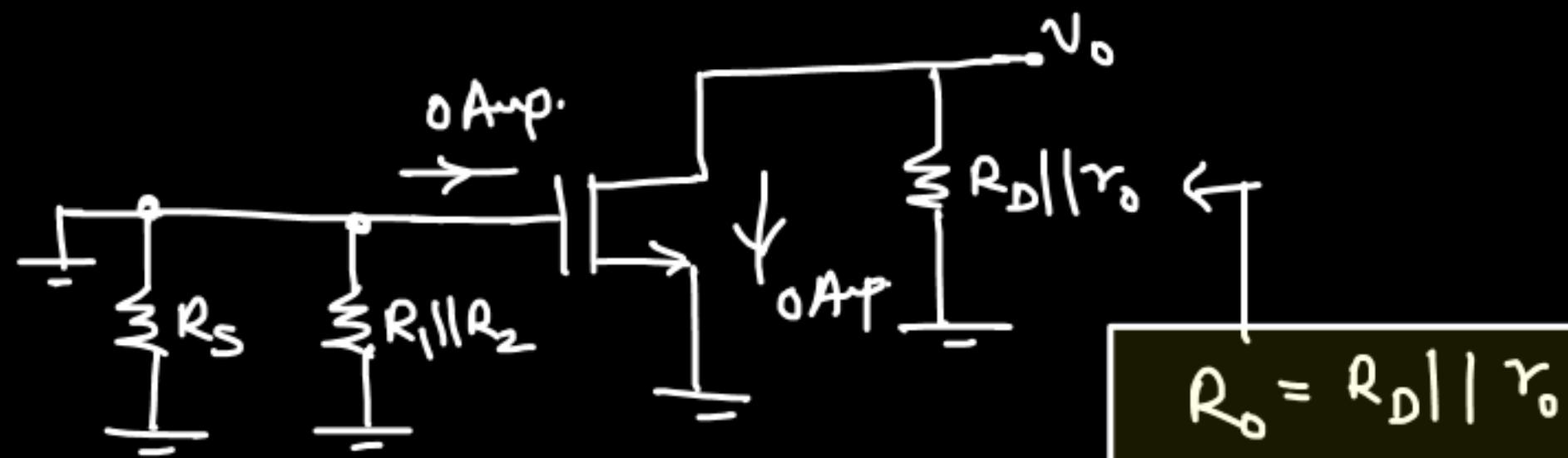

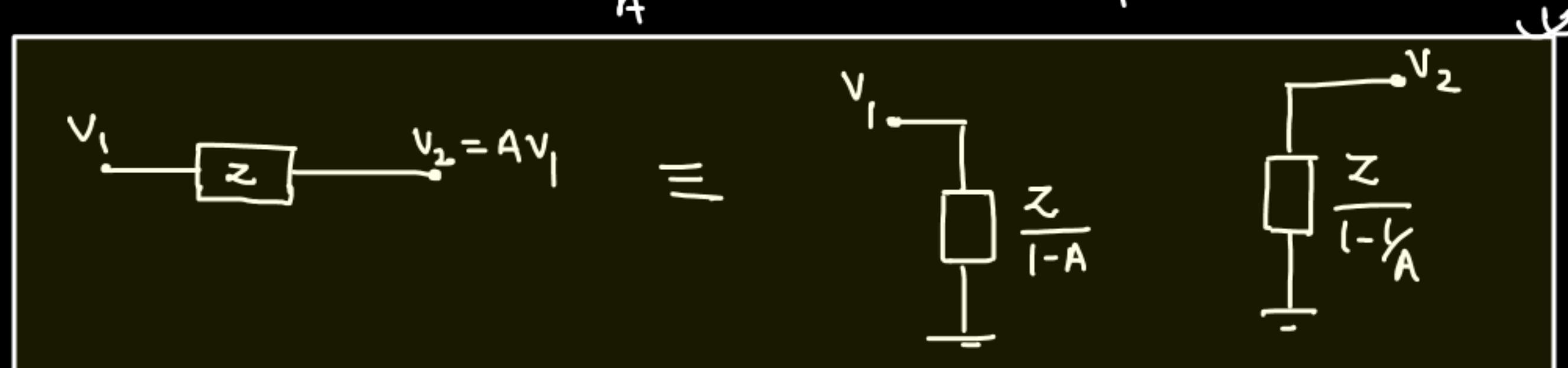
## Miller's Theorem :-


In a linear ckt, if there exist a branch with impedance  $z$ , connecting two nodes with nodal voltage  $v_1$  and  $v_2$ . We can replace this branch by two branches connecting the corresponding to ground by impedance respectively  $\frac{z}{1-A}$  and  $\frac{z}{1-\frac{1}{A}}$ ; where  $A = \frac{v_2}{v_1}$



Derivation:-

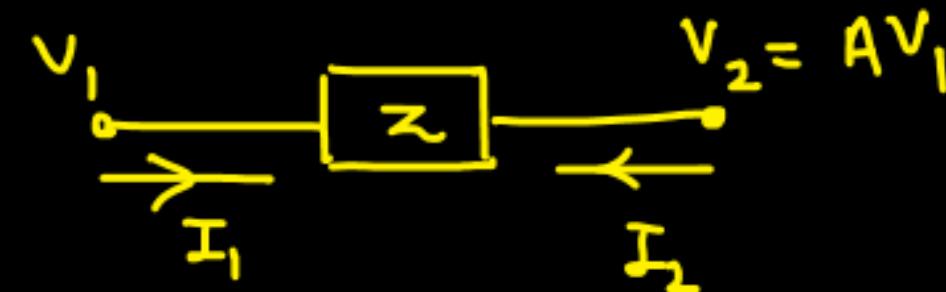

$$I_1 = -I_2$$

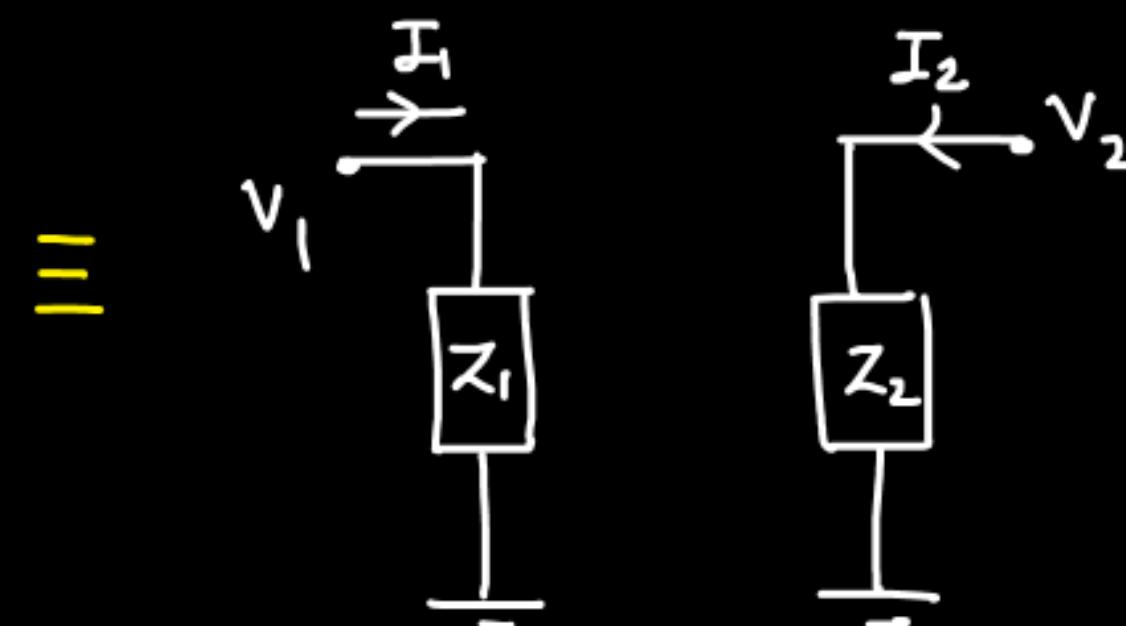

$$z_1 = \frac{V_1}{I_1}$$

$$\frac{V_1 - V_2}{z} = I_1$$

$$\frac{V_1 - AV_1}{z} = I_1$$


$$\frac{V_1}{I_1} = \frac{z}{1-A} = z_1$$

$$z_2 = \frac{V_2}{I_2}$$

$$\frac{V_2 - V_1}{z} = I_2$$

$$\frac{V_2 - V_1/A}{z} = I_2$$
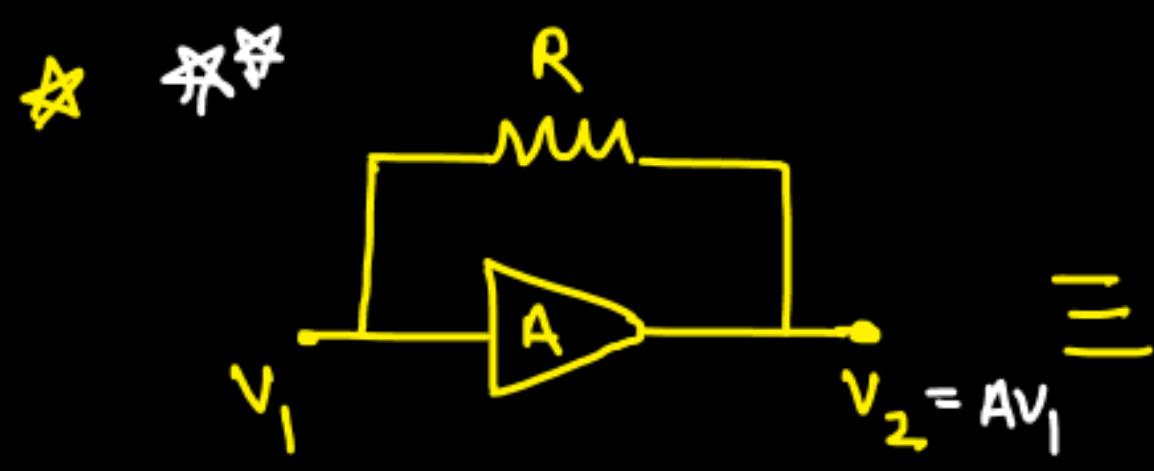
$$\frac{V_2}{I_2} = \frac{z}{1 - 1/A} = z_2$$




≡

$v_1$

$v_2$

$\frac{R}{(1-A)}$

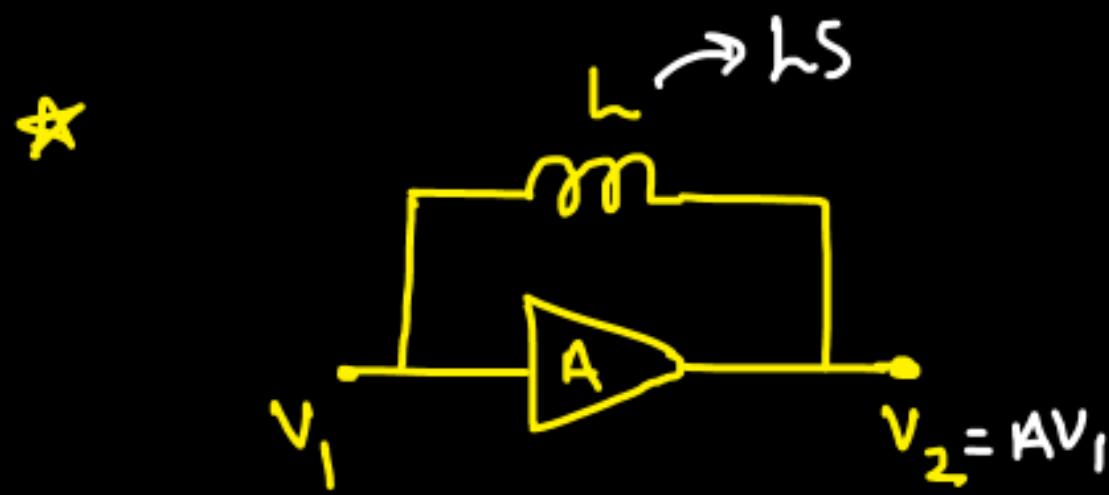


≡

$v_1$

$v_2$

$\frac{L}{(1-A)}$

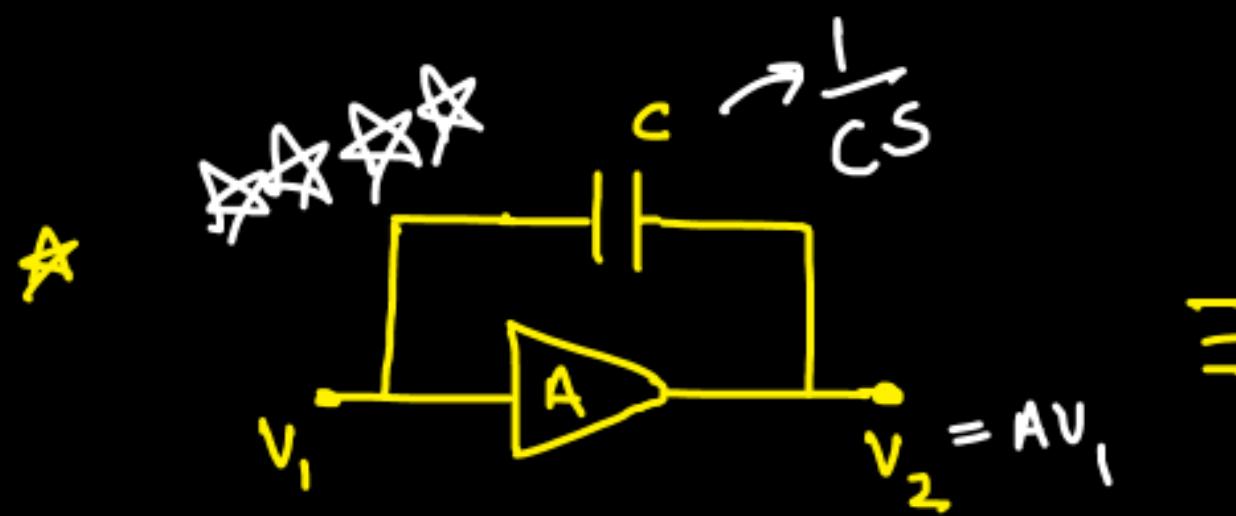



≡

$v_1$

$v_2$

$\frac{1}{C(1-A)}$

Eg.

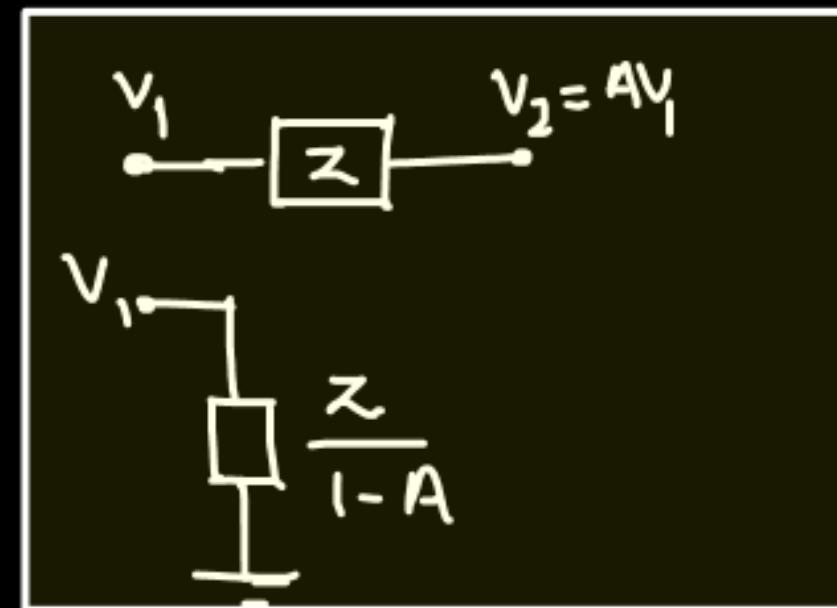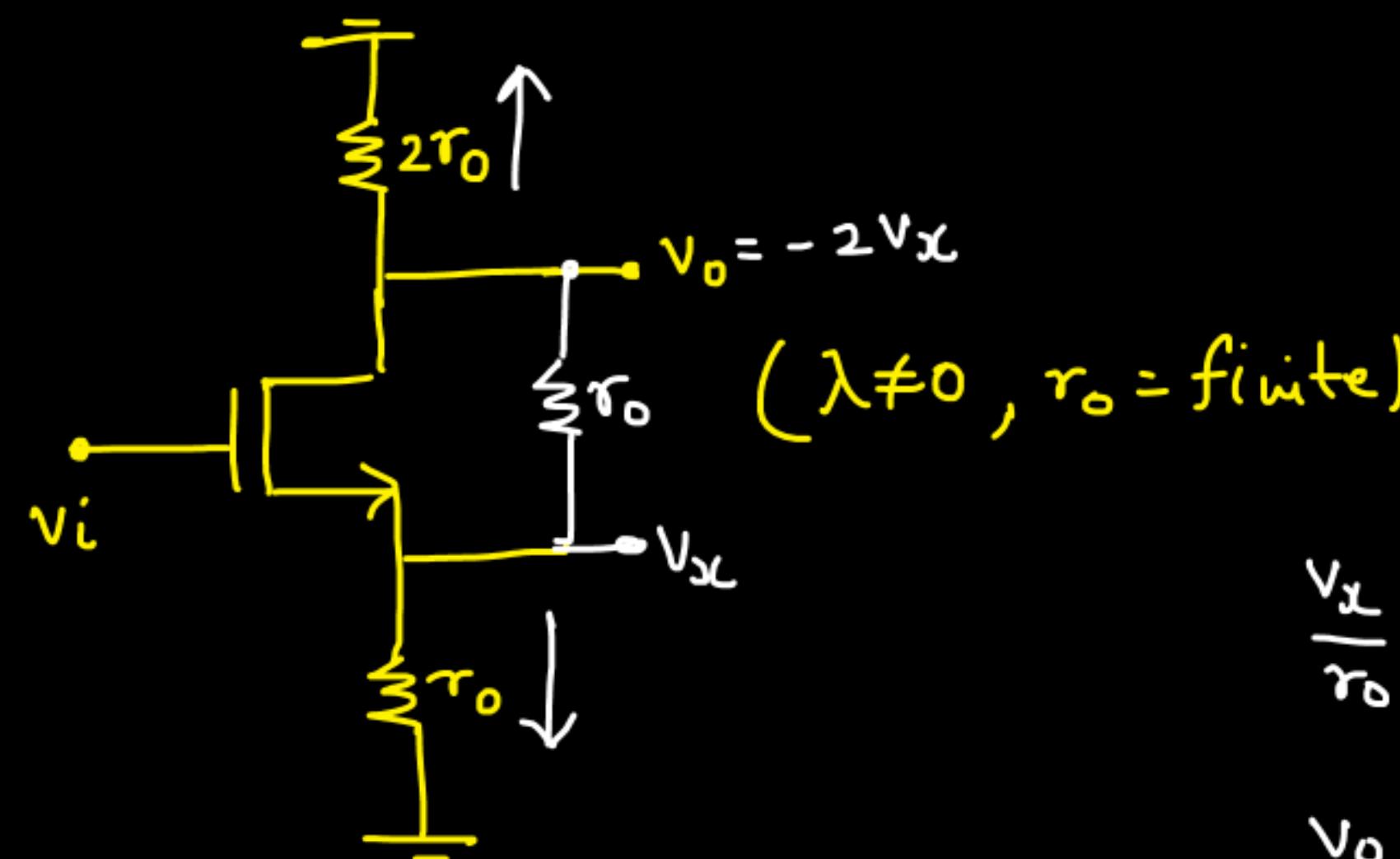


$$\frac{v_x}{r_o} = -\frac{v_o}{2r_o}$$

$$\frac{v_o}{v_x} = -2 \Rightarrow v_o = -2v_x$$

$$A = -2$$

$$\frac{v_x}{r_o / (1 + 2)} = \frac{r_o}{3}$$

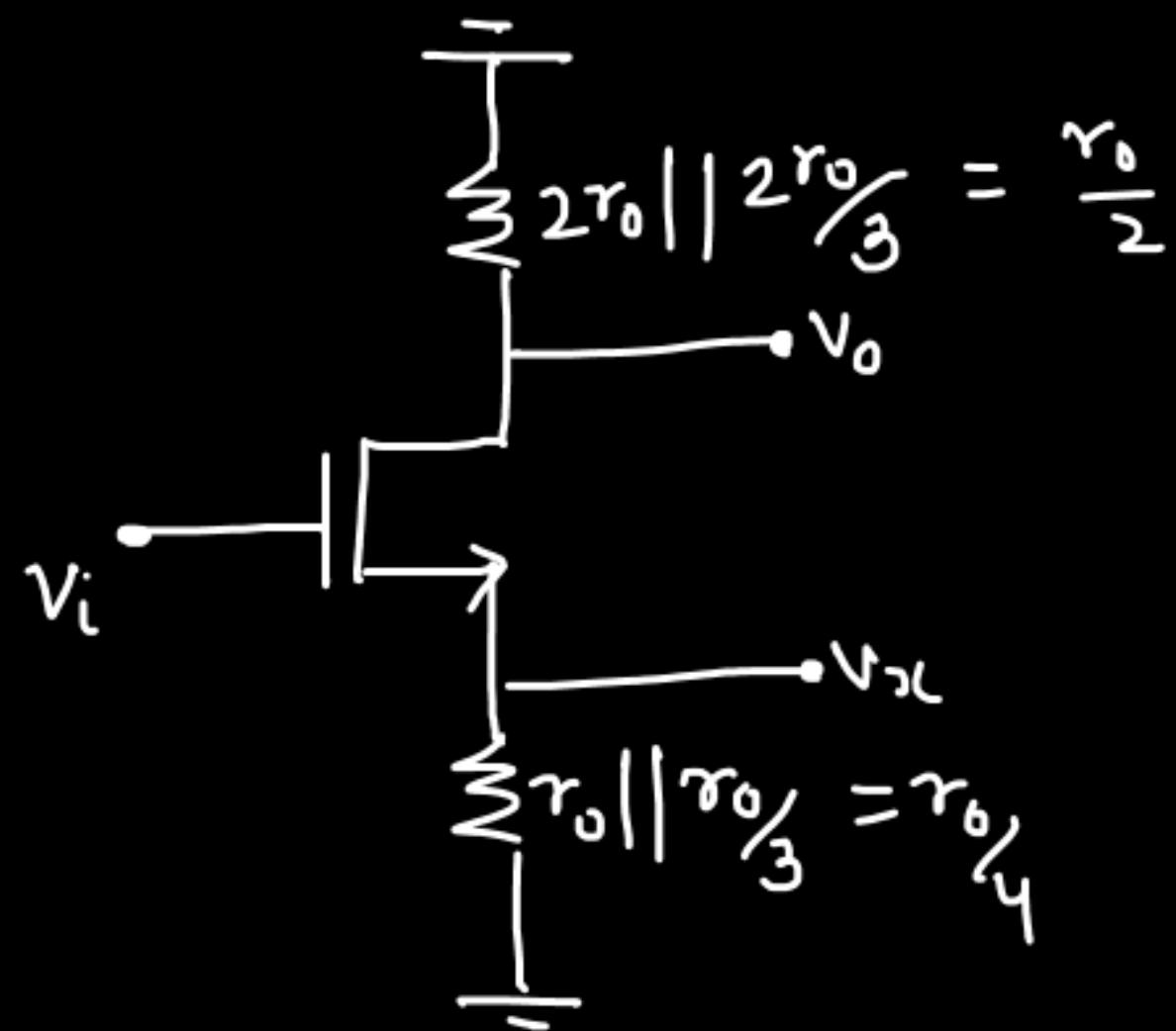
$$\frac{v_o}{r_o / (1 + 2)} = \frac{2r_o}{3}$$




$$\begin{aligned}
 \frac{V_o}{V_i} &= -\frac{g_m \left[ \frac{r_0}{2} \right]}{1 + g_m \left[ \frac{r_0}{4} \right]} \\
 &= -\frac{g_m r_0/2}{4 + g_m r_0}
 \end{aligned}$$

$$\boxed{\frac{V_o}{V_i} = -\frac{2g_m r_0}{4 + g_m r_0}}$$

## ② Self bias stage:-

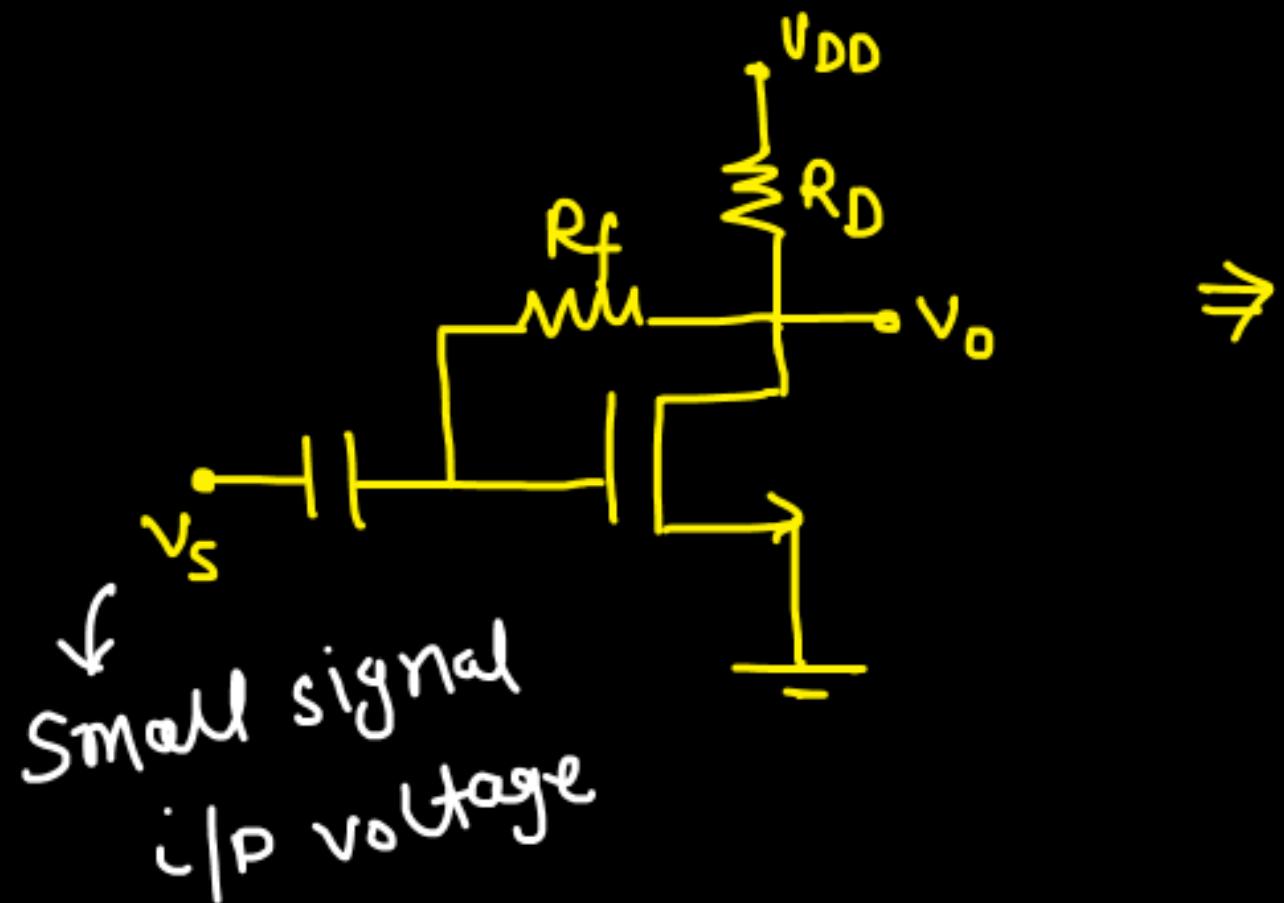

## DC Analysis:-

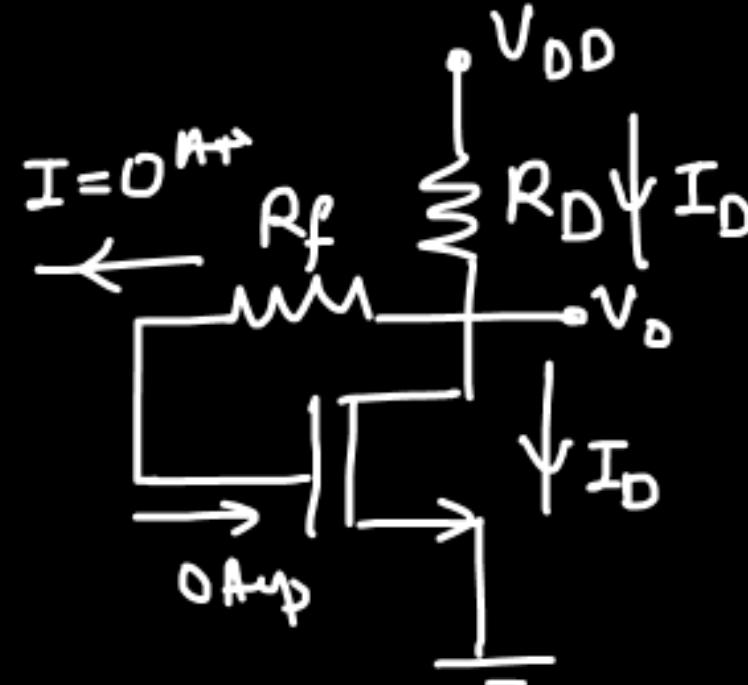




① Make sure that

$$V_{DD} - I_D R_D > V_T$$

ensuring  
MOS is ON

$\Rightarrow V_{DS} > V_{ov} \Rightarrow$  Always  
in Sat.  
=

## AC Analysis:-

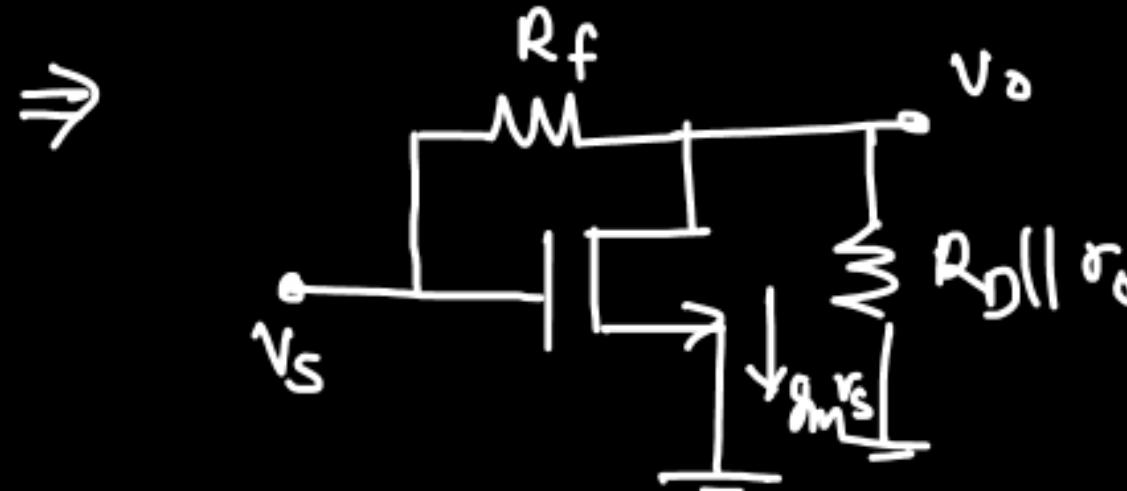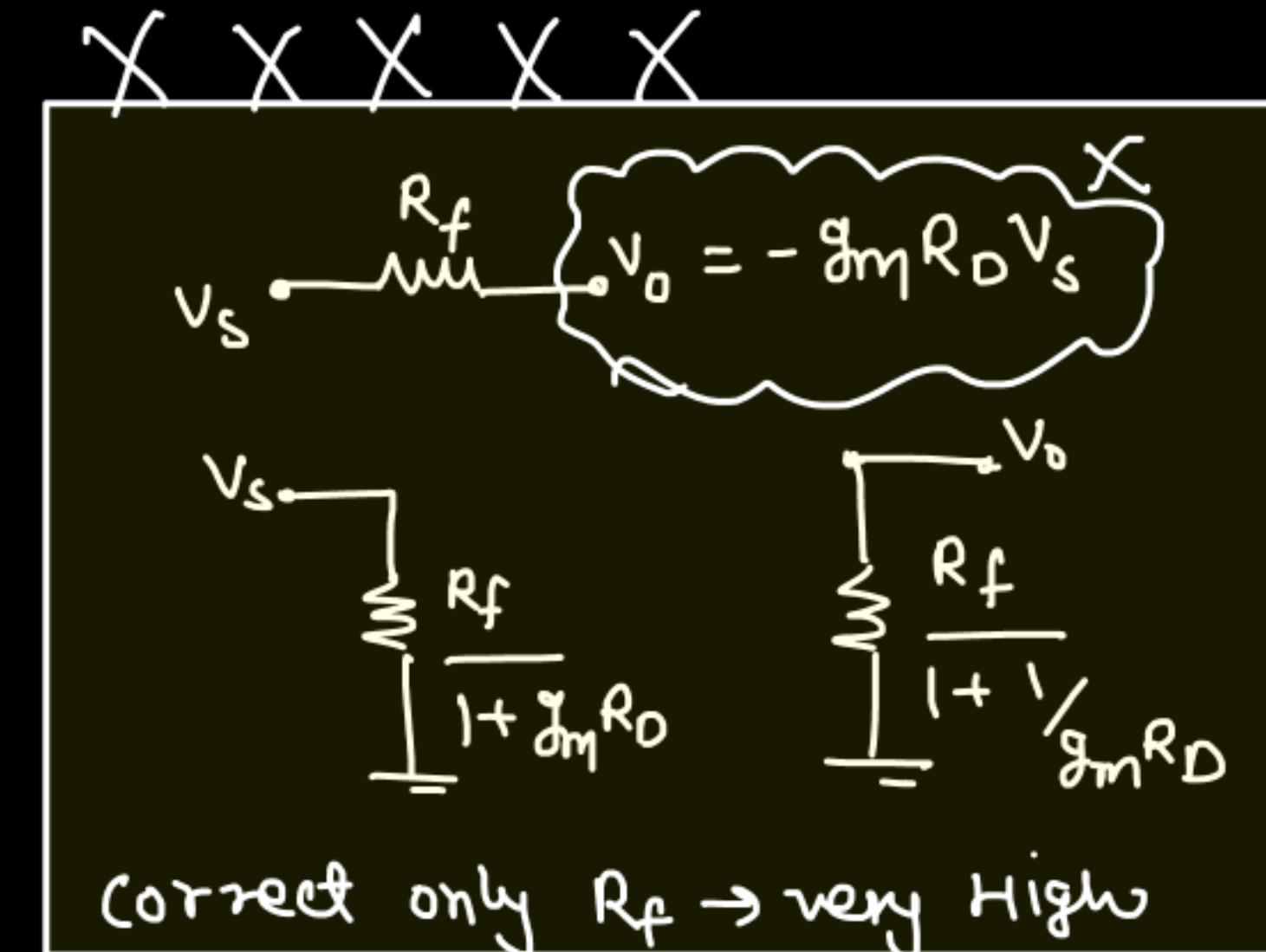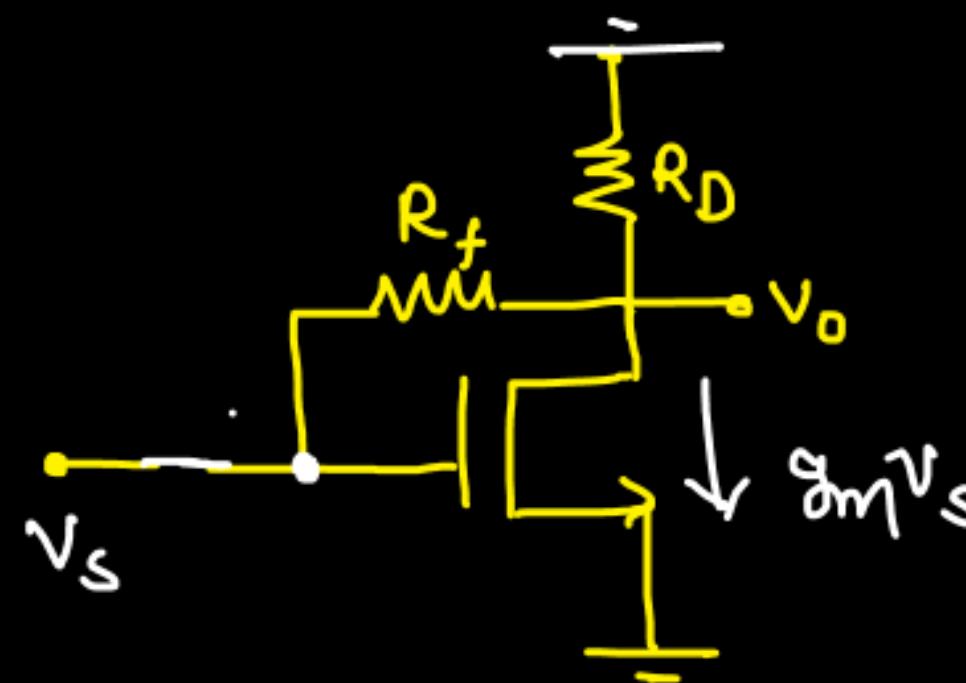

nodal @  $V_o$

$$\frac{V_o}{R_D || r_s} + g_m V_s + \frac{V_o - V_s}{R_f} = 0$$


$$\frac{V_o}{R_D || r_o} + \frac{V_o}{R_f} = \frac{V_s}{R_f} - g_m V_s$$

$$\frac{V_o}{R_f || R_D || r_o} = \frac{V_s}{(-g_m || R_f)}$$

$$\boxed{\frac{V_o}{V_s} = \frac{R_f || R_D || r_o}{-g_m || R_f}} = A$$

C


M - II :-

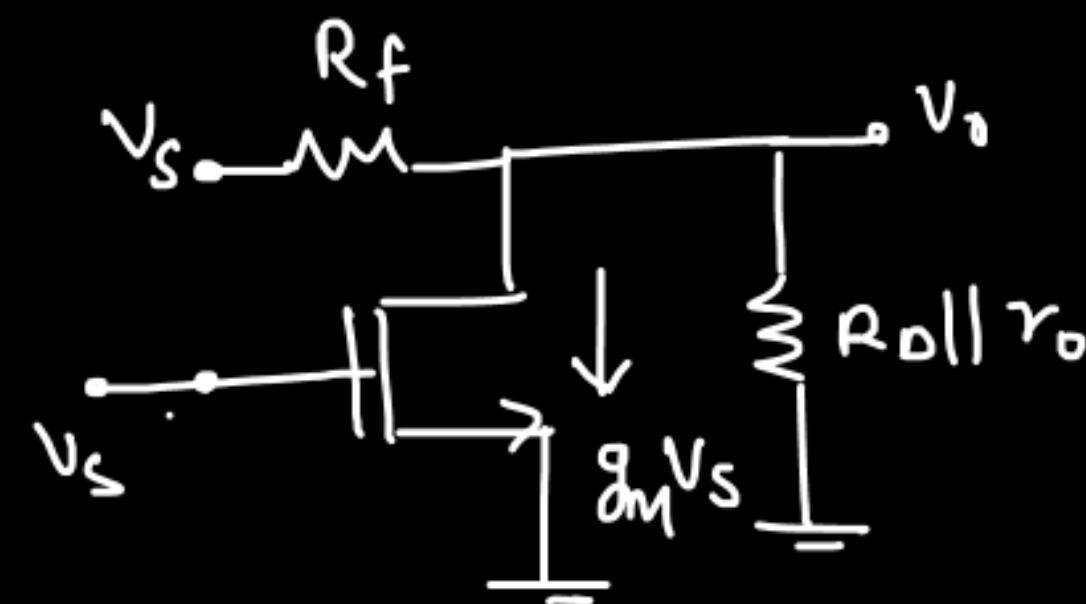

$$\rightarrow v_o = -g_m [R_D \parallel r_o \parallel R_f] v_s + \left[ \frac{R_D \parallel r_o}{R_f + (R_D \parallel r_o)} \right] v_s$$

$$\boxed{\frac{v_o}{v_s} = -g_m [R_D \parallel r_o \parallel R_f] + \frac{R_D \parallel r_o}{R_f + (R_D \parallel r_o)}} = A$$


★

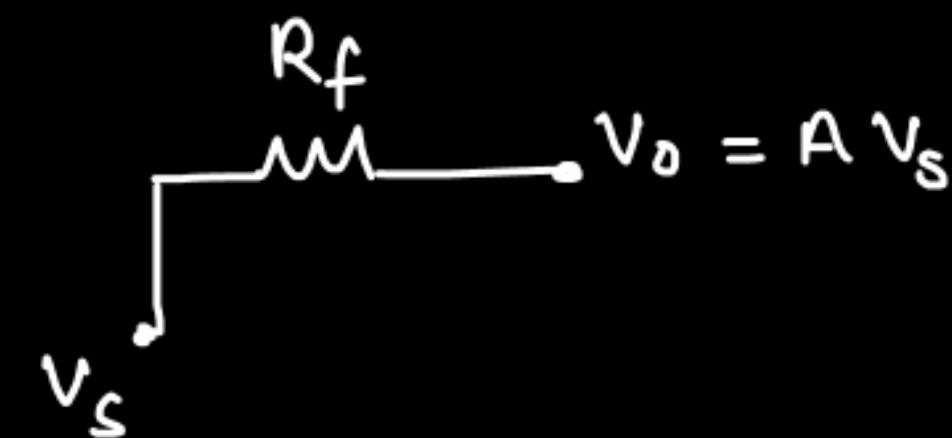

$$A = -g_m [R_D || r_o || R_f] + \frac{R_D || r_o}{R_f + (R_D || r_o)}$$



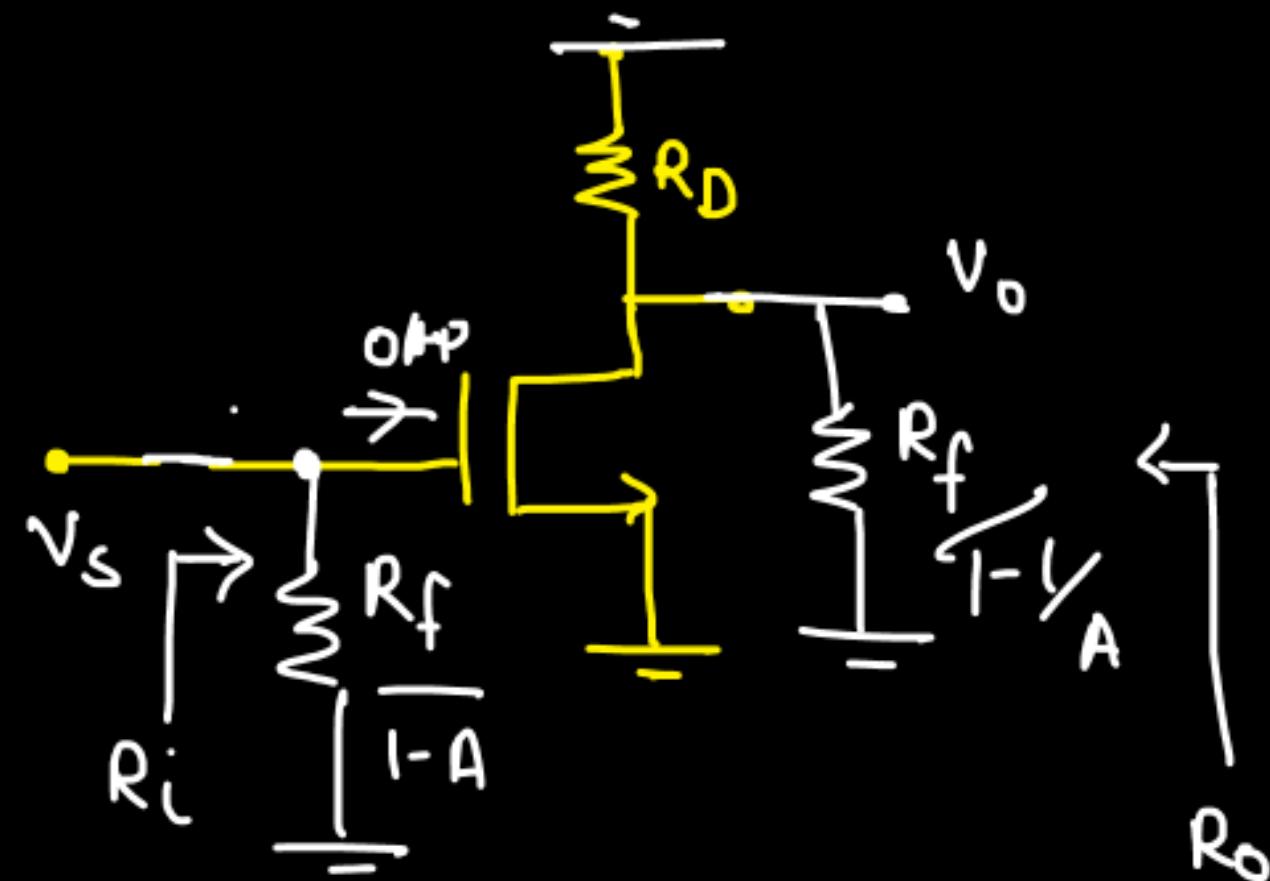input resistance :- / Output resistance :-




$$R_i = \frac{R_f}{1-A}$$

$$R_o = R_D || r_o || \frac{R_f}{1 - 1/A}$$

$$A = -g_m [R_D || R_f || r_o] + \frac{R_D || r_o}{(R_D || r_o) + R_f}$$

## Assignment - 6

Q.

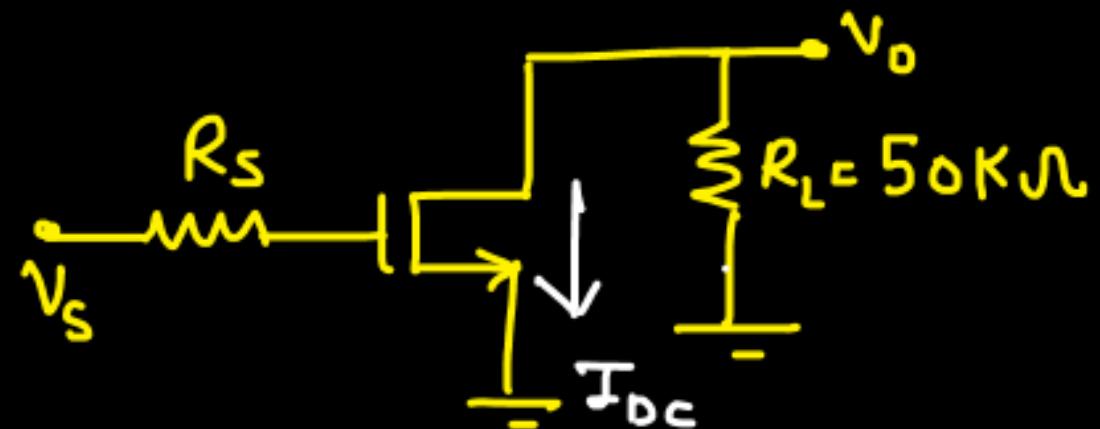

$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$w/l = L$$

$$V_T = 1\text{V}, \lambda = 0$$

Small signal model is drawn. The gain magnitude is 8.

Determine the bias current flowing through the mos.

$$\rightarrow |-g_m R_L| = 8 \quad \Rightarrow \quad g_m \times 50\text{K} = 8$$

$$g_m = 0.16\text{mS}$$


$$d\eta = \sqrt{\frac{2 \mu n C_o \times \omega}{L}} I_{Dc} = 0.16 m$$

$$\sqrt{2 \times 100 \times I_{Dc}} = 16 \times 10^{-5}$$

$$2 \times 10^{-4} \times I_{Dc} = 2.56 \times 10^{-10}$$

$$I_{Dc} = 128 \text{ microAmp.} \quad \checkmark$$

Q. 2

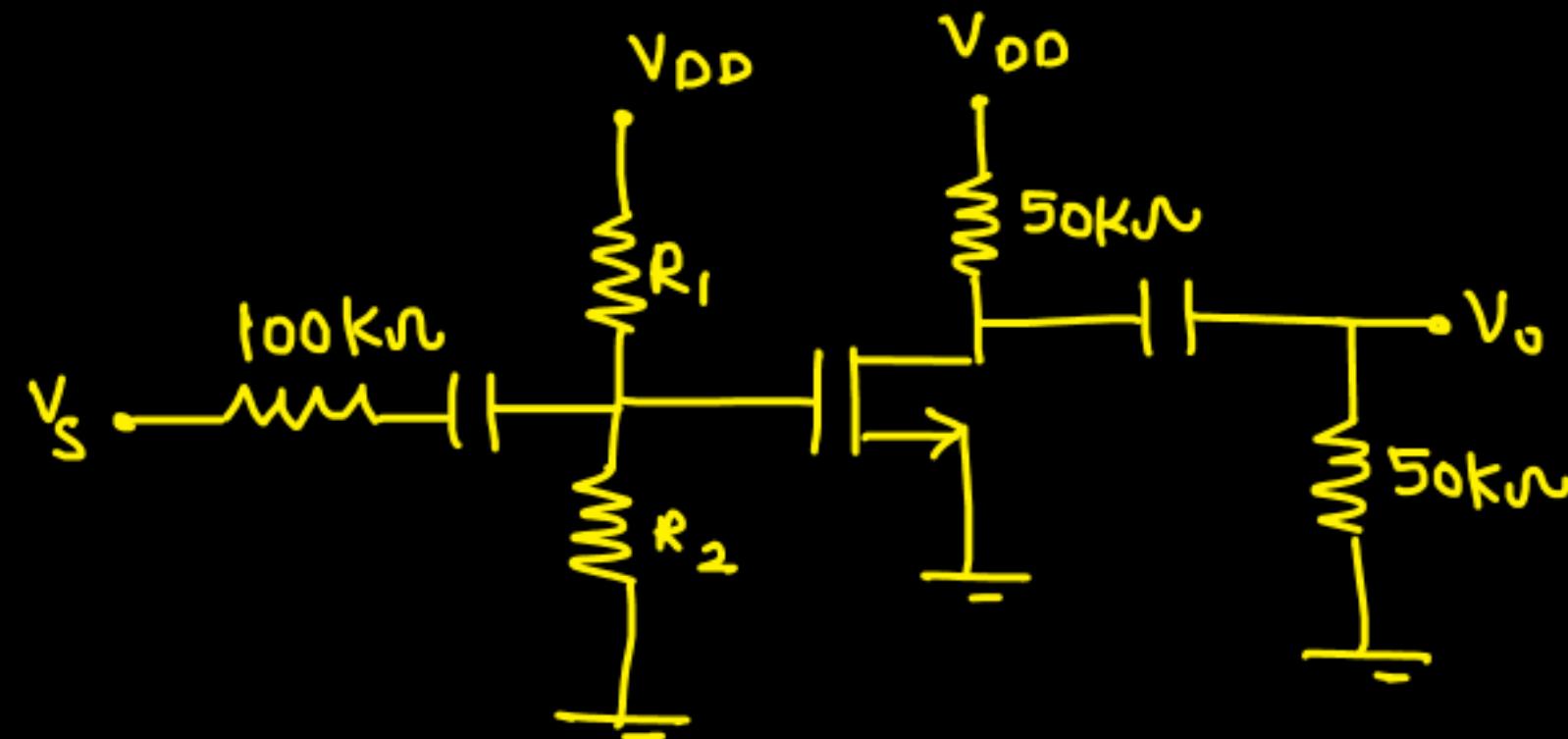


$\mu_n C_{ox} = 100 \mu A/V^2$  ,  $w_L = 1$  ,  $V_T = 1V$  • The transistor is biased @  $128 \mu A$ .

At operation point ;  $V_{DS} = V_{GS} + 1$

The bias current flowing through  $R_{1,2}$  is  $10 \mu A$ .

- ① Determine  $V_{DD}$ .
- ② Determine  $R_1$  &  $R_2$ .
- ③ Determine small signal gain  $\frac{V_o}{V_s}$ .

### ① DC Analysis :-

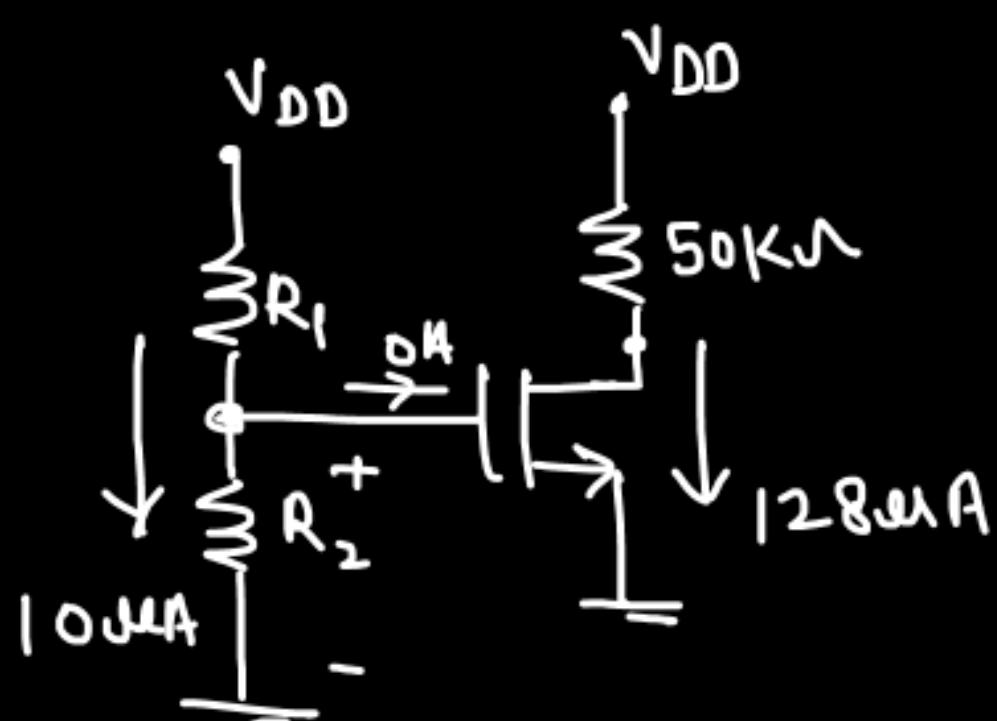

$$V_{DS} = V_{GS} + I \quad [\text{Given}]$$

$$V_{OV} = V_{GS} - V_T = V_{GS} - I$$

$V_{DS} > V_{OV} \Rightarrow$  Sat. region =

$$\Rightarrow V_{DS} = V_{DD} - 50K \times 128\mu$$

$V_{DS} = V_{DD} - 6.4$

— ①

$$I_D = 128 \mu A \quad [\text{Given}]$$

$$\frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 = 128 \mu$$

$$\frac{100\mu}{2} (V_{GS} - 1)^2 = 128 \mu$$

$$V_{GS} - 1 = \sqrt{2.56}$$

$$V_{GS} = 2.6 V \quad - \textcircled{2}$$

$$V_{DS} = V_{GS} + 1 \quad [\text{Given}]$$

$$V_{DD} - 6.4 = 2.6 + 1$$

$$V_{DD} = 10 V \quad \text{Ans.}$$

②  $R_1 = ?$ ,  $R_2 = ?$

Given,  $\frac{V_{DD}}{R_1 + R_2} = 10 \mu A$

$$\frac{10}{R_1 + R_2} = 10 \mu A$$



$$R_1 + R_2 = 1 M\Omega = 1000 k\Omega$$

Here,  $V_{GS} = 10 \mu A \times R_2 = 2.5$

$$R_2 = 260 k\Omega$$

$$R_1 = 740 k\Omega$$

③ Small signal voltage gain :-

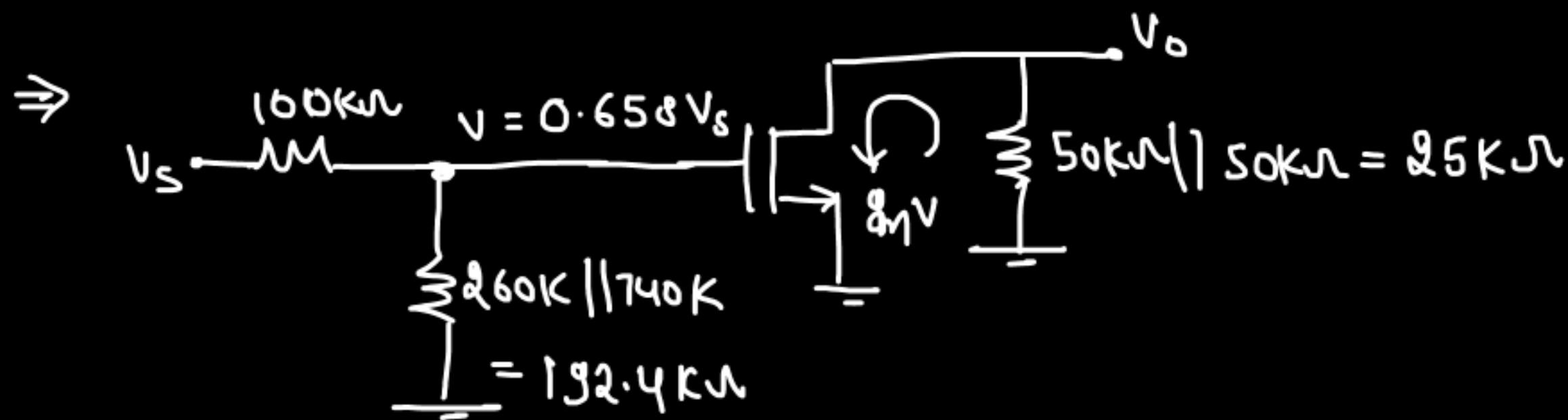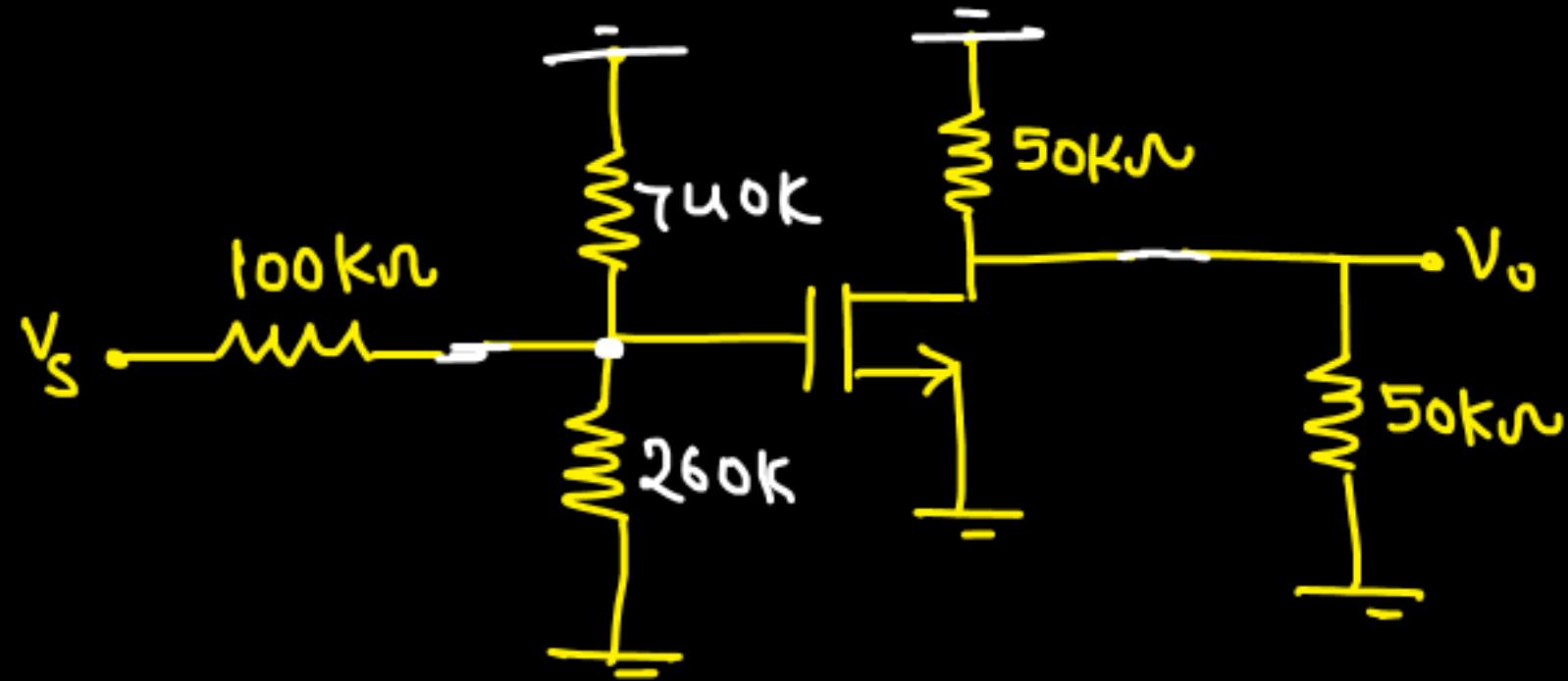

$$V_o = -g_m [25 \text{ k}\Omega] \times 0.658 V_s$$


$g_m = ?$

$$g_m = \frac{2 I_{DC}}{(V_{GS} - V_T)} = \frac{2 \times 128 \mu}{1.6} = 160 \mu S$$

$$V_o = -160 \times 10^{-6} \times 25 \times 10^3 \times 0.658 V_s$$

$$\boxed{\frac{V_o}{V_s} = -2.63 \text{ V/V}}$$

Q.

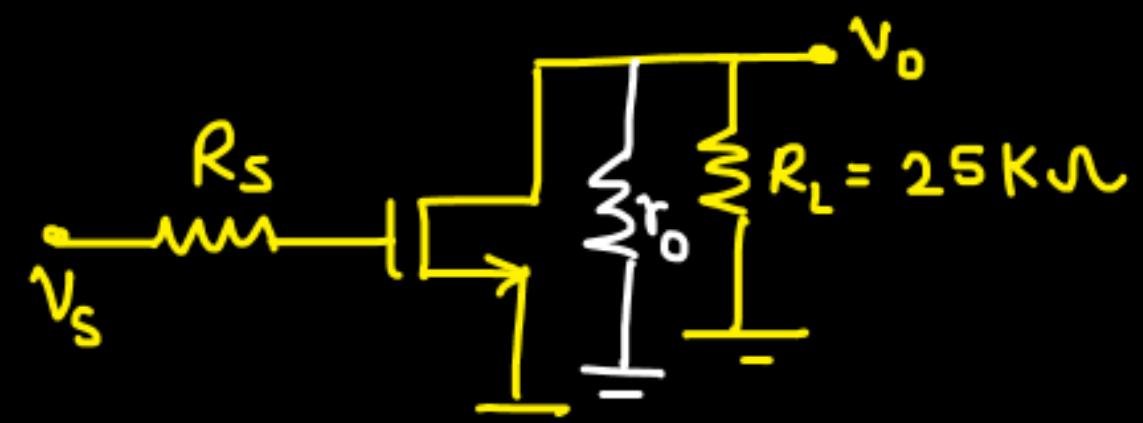

$$g_m C_{ox} = 100 \mu A/V^2$$

$$w_L = 1$$

$$V_T = 1V$$

considering  $\lambda=0$ , you calculated the gain to be -4.

Later, you realised that  $\lambda = 0.0625 V^{-1}$ .

Find the actual small signal gain.



$$-g_m \times 25k\Omega = -4$$

$$g_m = \frac{4}{25k\Omega} = 0.16mS$$

$$\text{Actual gain} = -g_m [\gamma_0 || 25\text{k}\Omega] \quad \textcircled{1}$$

$$\gamma_0 = ?$$

$$\gamma_0 = \frac{1}{\lambda [I_D]}_{\text{Sat. - ideal}}$$

$$g_m = 0.16 \text{ mS}$$

$$\sqrt{2 \times 100 \mu \times I_D} = 0.16$$

$$I_D = 128 \mu\text{A}$$

$$\Rightarrow \gamma_0 = \frac{1}{0.0625 \times 128 \mu}$$

$$\gamma_0 = \frac{10^6}{8}$$

$$\gamma_0 = 125 \text{k}\Omega$$

$$\text{Actual gain} = -0.16 \times 10^{-3} [125/(25)] \times 10^3$$

$$A_V = -3.33$$

N.B. -

Usually, we consider same  $g_m$  value for both of the cases

$$\lambda=0 \text{ & } \lambda \neq 0$$

$$[g_m]_{\lambda=0} = \frac{\mu_n C_o \omega}{L} (V_{GS} - V_T)^2$$

$$[g_m]_{\lambda \neq 0} = \frac{\mu_n C_o \omega}{L} (V_{GS} - V_T)^2 [1 + \lambda V_{DS}]$$


Since  $\lambda = \text{very small} \Rightarrow [g_m]_{\lambda=0} = [g_m]_{\lambda \neq 0}$

Q. All the transistor are identical with


$$\frac{MnC_oxW}{L} = 100 \mu A/V^2, V_T = 1V, \lambda = 0$$

(biased in sat. region)

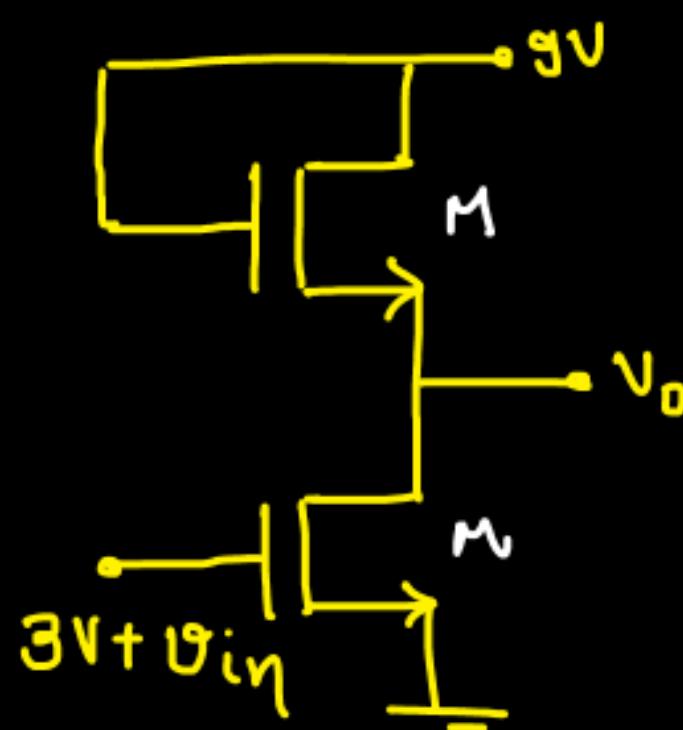Determine small signal voltage gain for (a) & (b).




(a)

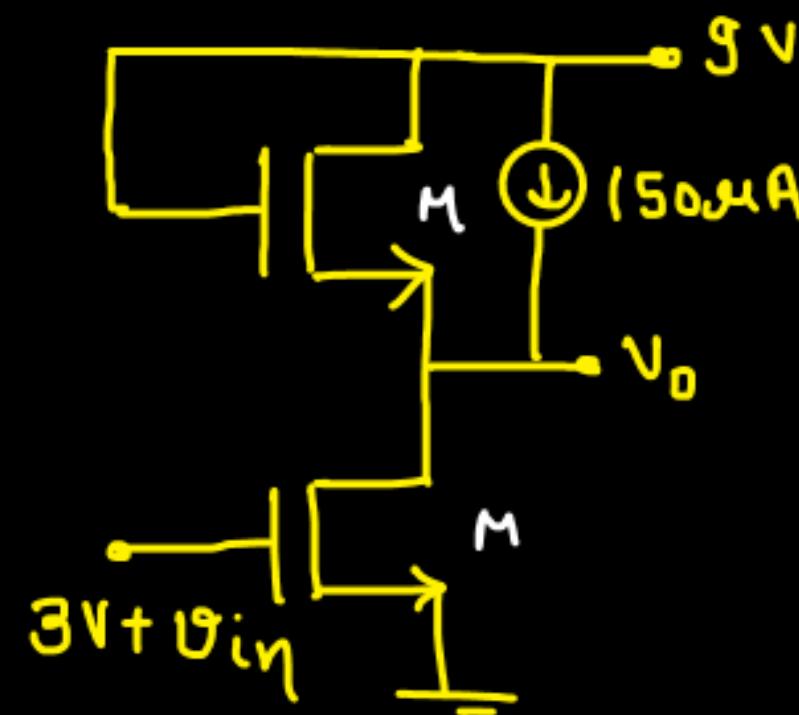

(b)

(i)

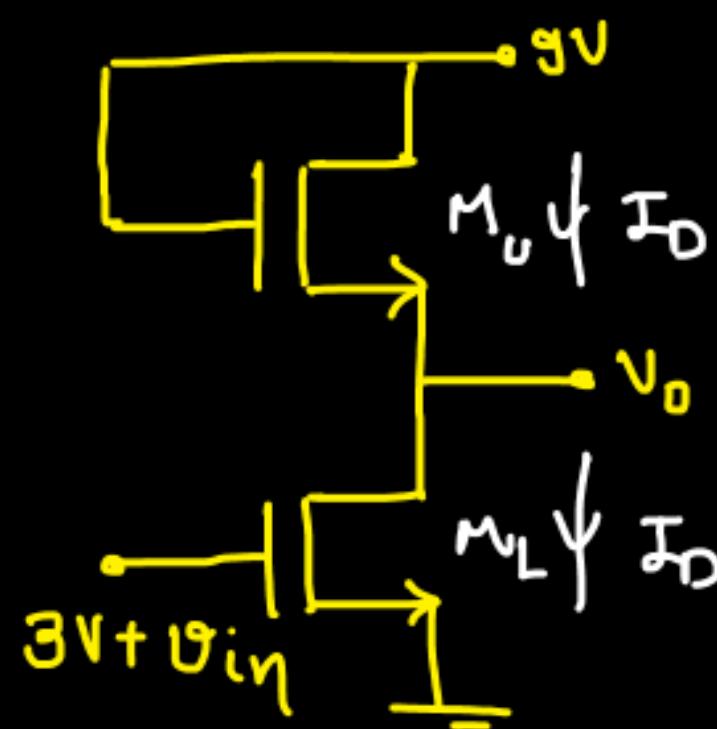


(a)

Both  $M_U$  and  $M_L$  will have same  $g_m$  value.


$$\left( g_m = \sqrt{2 \mu n C_{ox} W L} I_D \right)$$

⇒

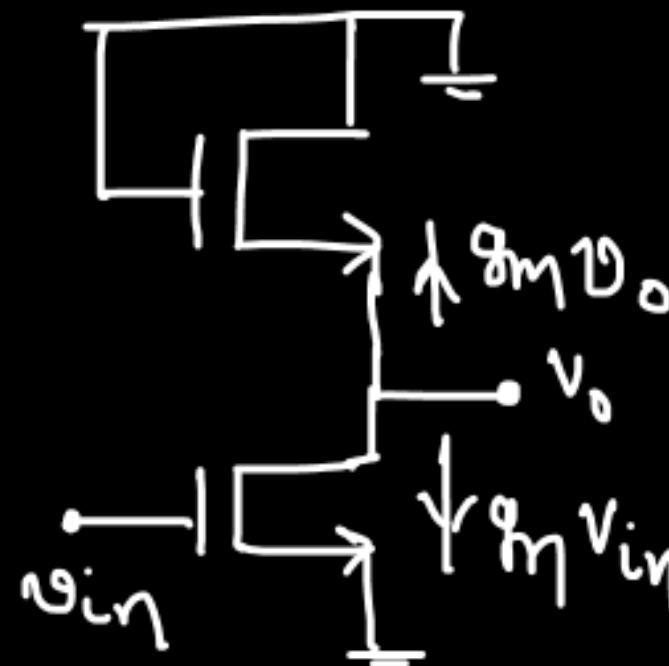

$$g_m v_{in} = -g_m v_o$$

$$\frac{v_o}{v_{in}} = -1$$

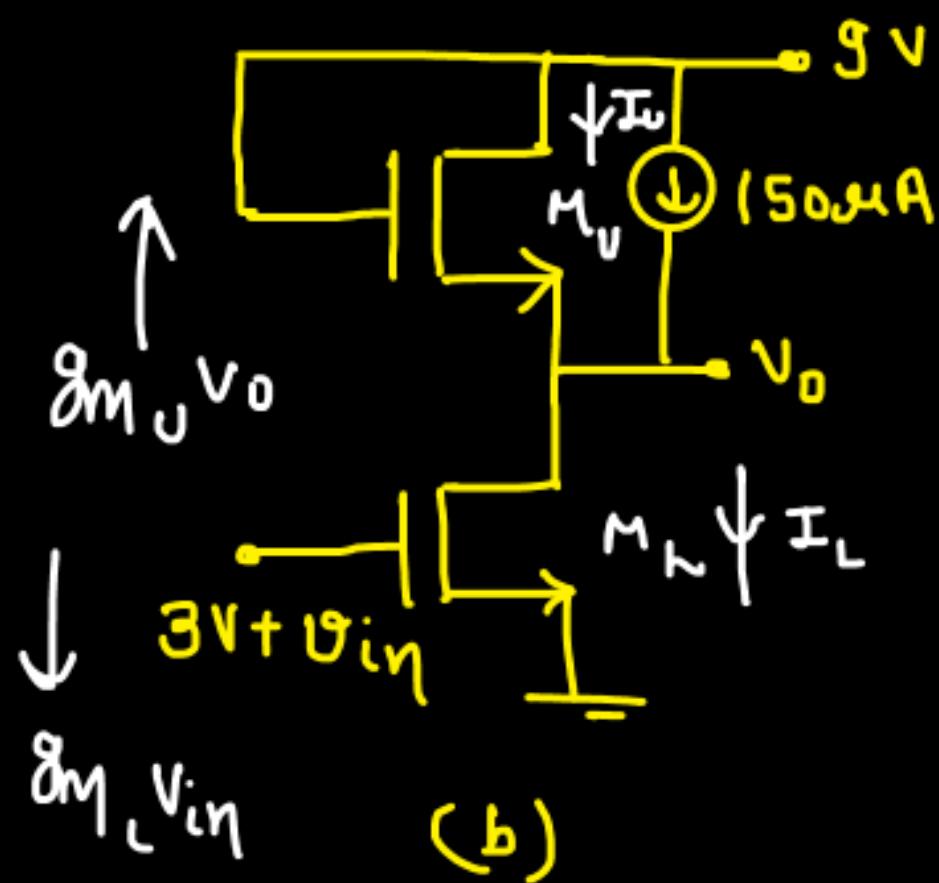

Small signal gain

$$A_V = -\frac{\delta m_L}{\delta m_U}$$
(2)

$$I_U = 150 \mu A - I_L$$

Here the dc current is not same in both transistors, so  
 $\delta m$  will be different.

$$I_L = \frac{100 \mu A}{2} (3-1)^2$$

$I_L = 200 \mu A$	$\rightarrow \delta m_L$
$I_U = 50 \mu A$	$\rightarrow \delta m_U$

$$\delta m = \sqrt{\frac{2m_n C_{ox} W}{L}} I_D$$
 $\Rightarrow \delta m \propto \sqrt{I_D}$


$$\frac{g_m L}{g_m U} = \frac{\sqrt{I_{D_L}}}{\sqrt{I_{D_U}}}$$

$$\frac{g_m L}{g_m U} = \frac{\sqrt{200 \mu}}{\sqrt{50 \mu}}$$

$$\frac{g_m L}{g_m U} = 2$$

$$\Rightarrow \boxed{m_v = -2}$$

Q.

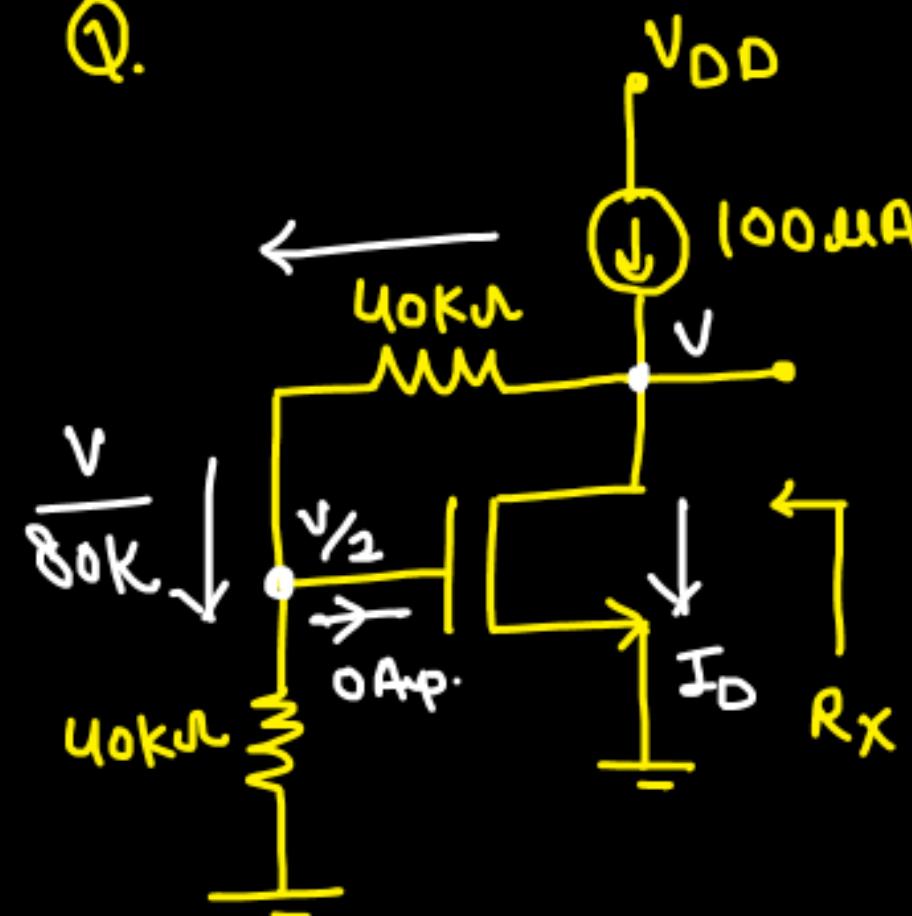

$$\frac{\mu_n C_{ox} W}{L} = 100 \mu\text{A}/V^2, V_T = 1\text{V}, \lambda = 0$$

- ① Determine the bias current in the transistor.
- ② Find small signal resistance  $R_X$ .

①  $V_{DS} = V$

$$V_{GS} = V_2$$

$$V_{OV} = V_2 - 1$$

$$\Rightarrow V_{DS} > V_{OV} \Rightarrow \text{Sat.}$$

$$100 \mu\text{A} = \frac{V}{80\text{K}} + I_D \quad \rightarrow \text{Q}$$

$$I_D = \frac{100 \mu\text{A}}{2} (V_2 - 1)^2 \quad \text{--- (1)}$$

$$100\mu = \frac{V}{0.08} \times \mu + 50\mu \left( \frac{V}{2} - 1 \right)^2$$

$$100 = (2.5V + 50 \left( \frac{V^2}{4} + 1 - V \right))$$

$$100 = 12.5V + 12.5V^2 + 50 - 50V$$

$$12.5V^2 - 37.5V - 50 = 0$$

$$V^2 - 3V - 4 = 0$$

$$V^2 - 4V + V - 4 = 0$$

$$\begin{matrix} V & \rightarrow & -1 \\ V & \rightarrow & 4 \end{matrix}$$


$$\Rightarrow V = 4V$$

$$V_{DS} = 4V, V_{GS} = 2V$$

$$I_D = \frac{100\mu}{2} (2-1)^2$$

$$I_D = 50\mu\text{Amp}$$

Small Signal Analysis:-

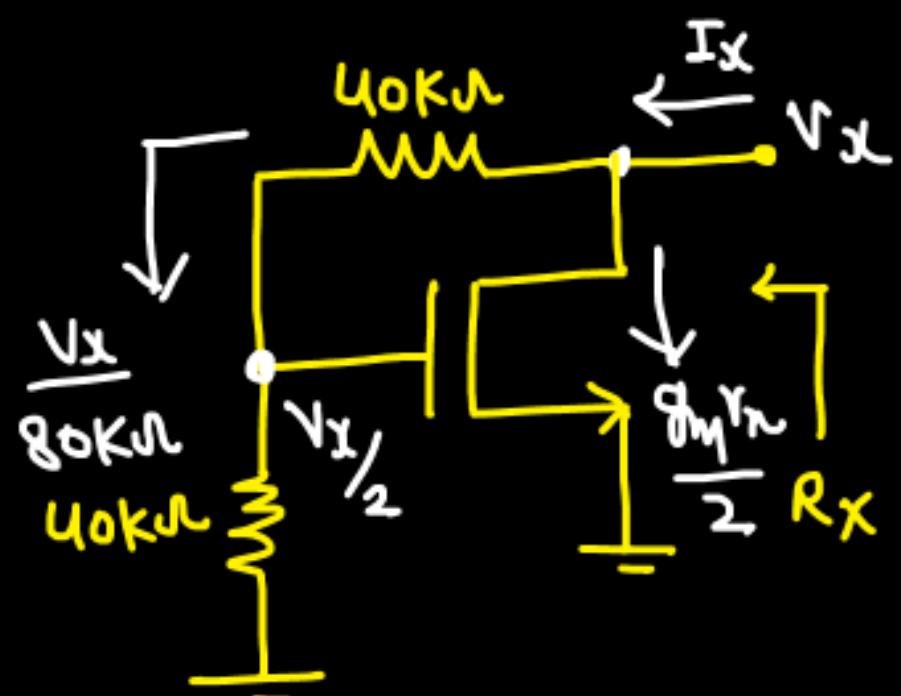

$$R_x = \frac{V_x}{I_x}$$

$$\frac{V_x}{80K} + \frac{g_m V_x}{2} = I_x$$

$$R_x = 80K \parallel \frac{1}{g_m}$$

$$g_m = ?$$

$$g_m = \sqrt{\frac{2MnC_{ox}\omega L}{L} I_D}$$

$$= \sqrt{2 \times 100 \times 50 \mu}$$

$$g_m = 100 \mu\text{s}$$


$$R_x = 80K \parallel \frac{2}{10^{-4}}$$

$$R_x = 80K \parallel 20K$$

$$R_x = 16K\Omega$$


ANS.

## Common Gate Amplifier:-

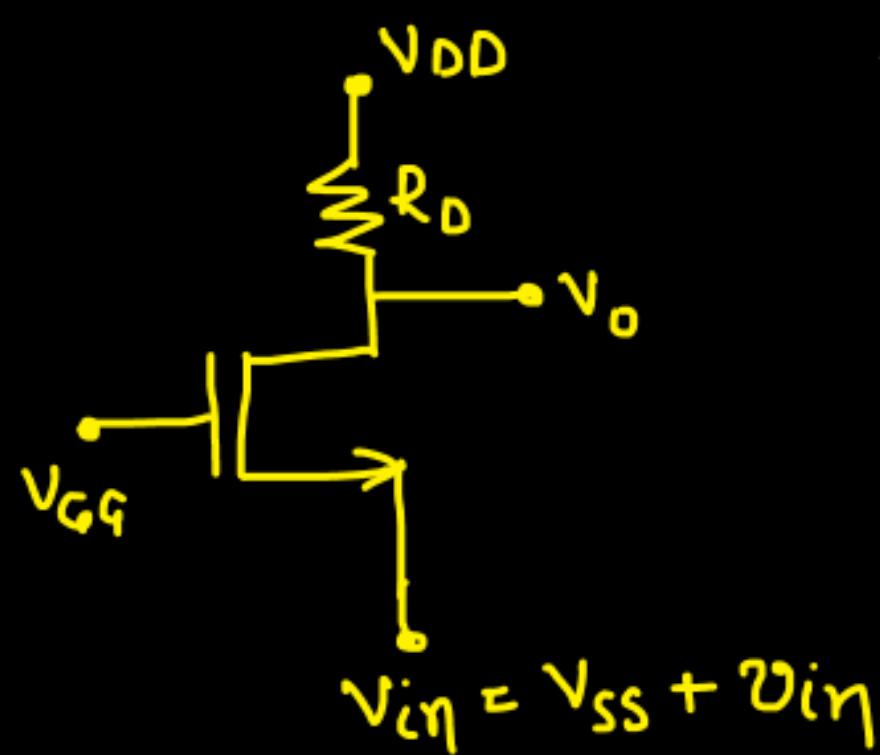


small signal i/p  $\rightarrow$  source  
" " o/p  $\rightarrow$  drain

## Small signal model:-

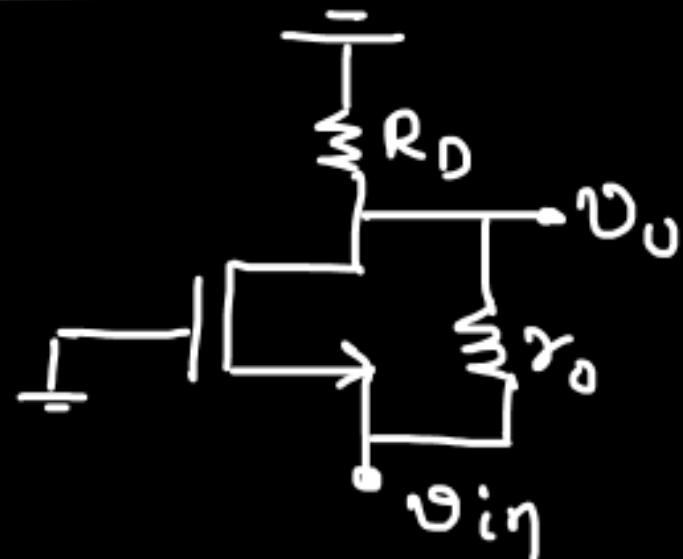

⇒ Voltage gain :-

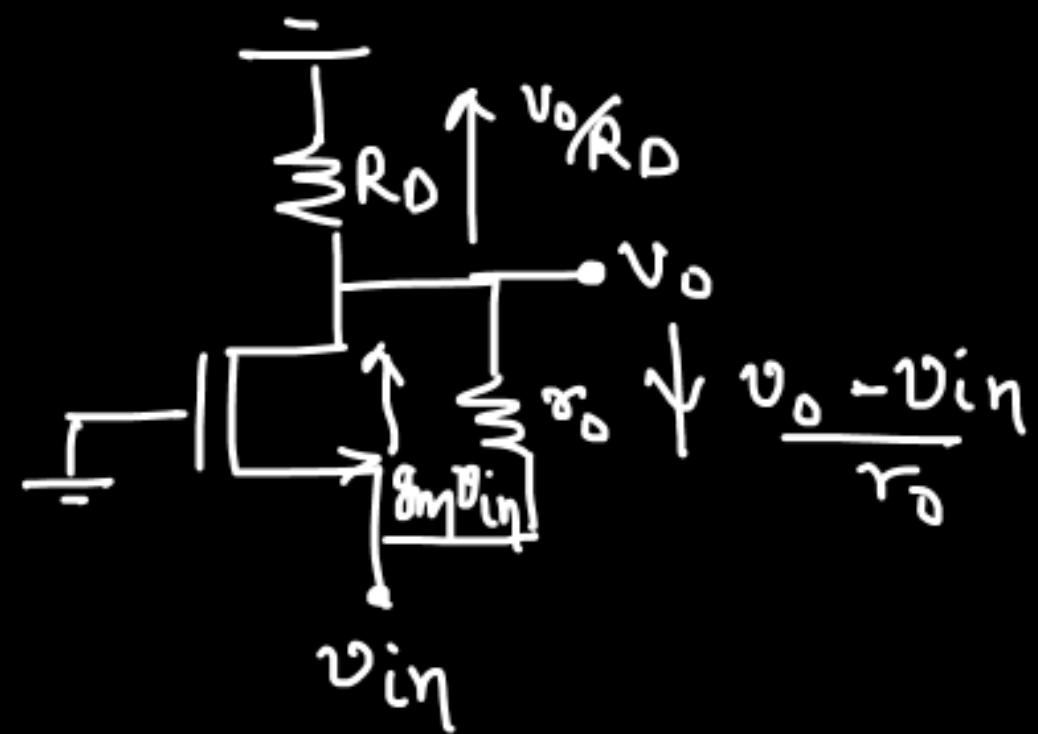$(\lambda \neq 0) \quad r_o = \text{finite}$




$$g_m v_{in} = \frac{v_o}{R_D} + \frac{v_o - v_{in}}{r_o}$$

$$v_{in} \left[ g_m + \frac{1}{r_o} \right] = v_o \left[ \frac{1}{R_D} + \frac{1}{r_o} \right]$$

$$v_{in} \left[ \frac{g_m r_o + 1}{r_o} \right] = v_o \left[ \frac{r_o + R_D}{R_D r_o} \right]$$

$$\boxed{\frac{v_o}{v_{in}} = \frac{R_D [g_m r_o + 1]}{r_o + R_D}}$$

Voltage gain ( $\lambda=0$ ):-

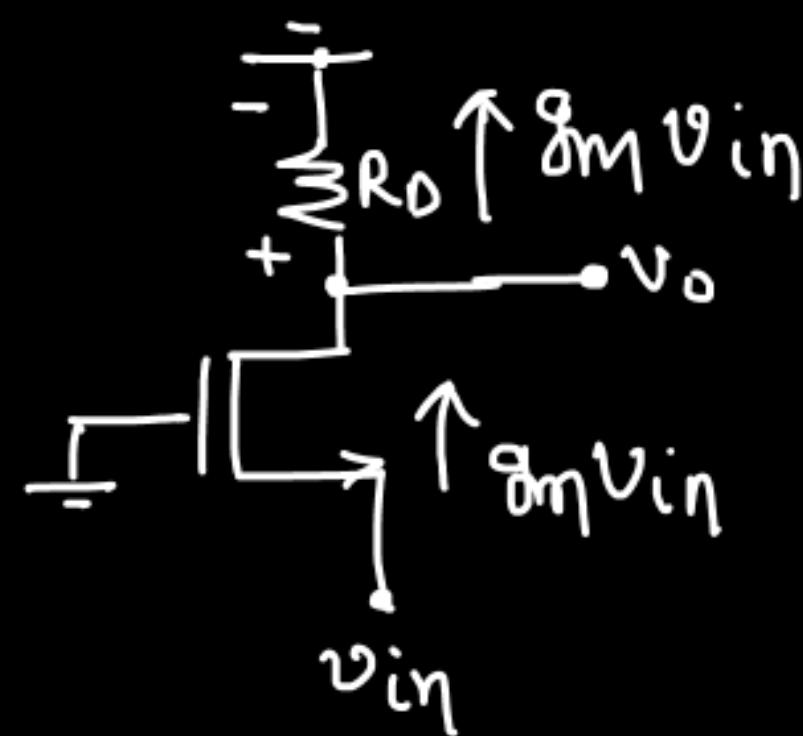


$$v_o = (g_m v_{in}) R_D$$

$$\frac{v_o}{v_{in}} = g_m R_D \quad \underline{\underline{=}}$$

B/w o/p and i/p there is 0°  
phase shift.

### ③ Input Impedance :-

( $\lambda \neq 0$ )

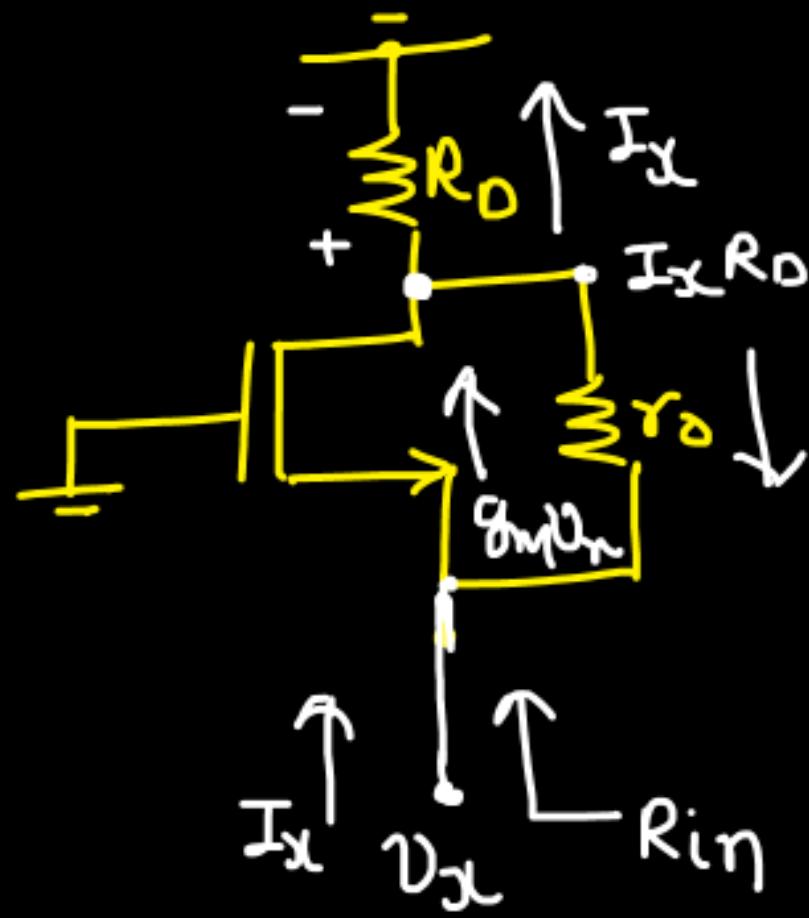

Nodal @  $I_X R_D$  :-

$$I_X + \frac{I_X R_D - V_X}{r_0} = g_m V_X$$



$$I_X \left[ \frac{r_0 + R_D}{g_m r_0} \right] = V_X \left[ g_m + \frac{1}{r_0} \right]$$

$$I_X \left[ r_0 + R_D \right] = V_X \left[ g_m r_0 + 1 \right]$$




$$R_X = \frac{V_X}{I_X} = \frac{r_0 + R_D}{1 + g_m r_0}$$

TO REMEMBER :-

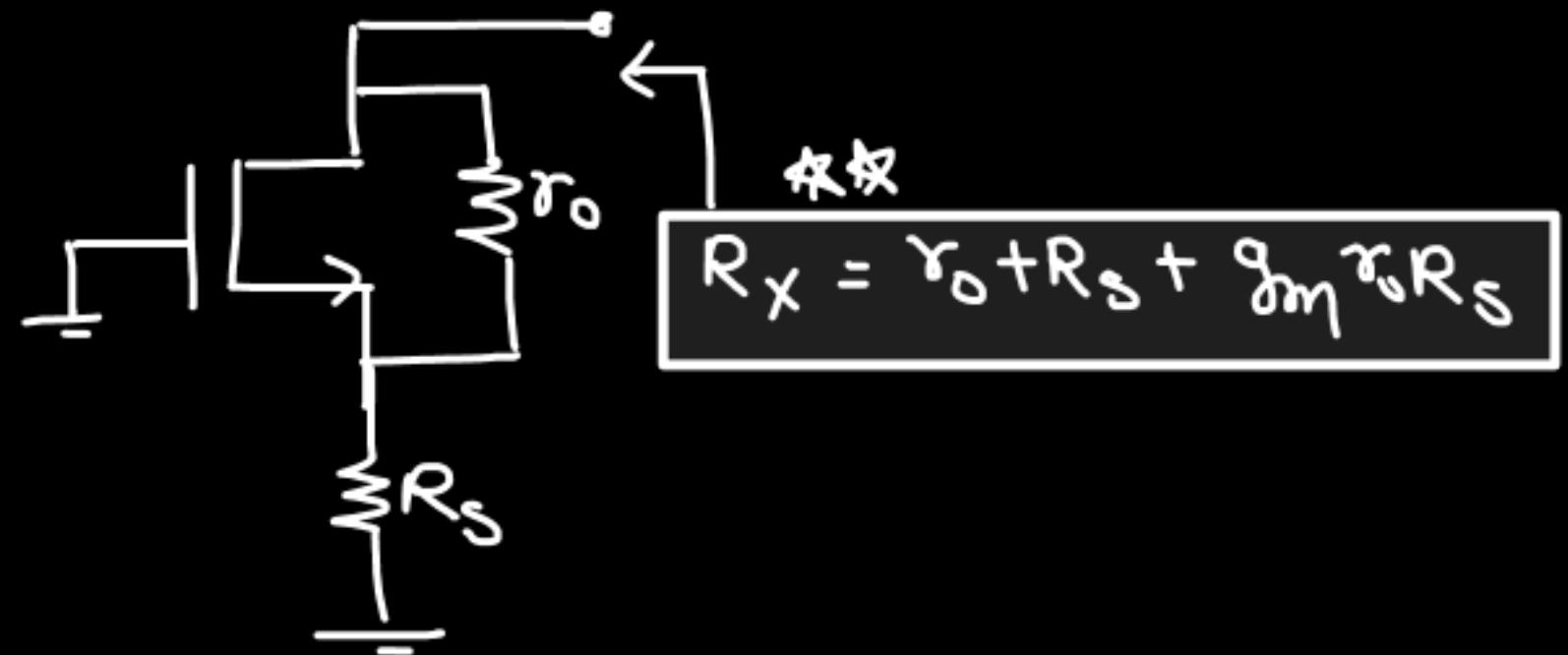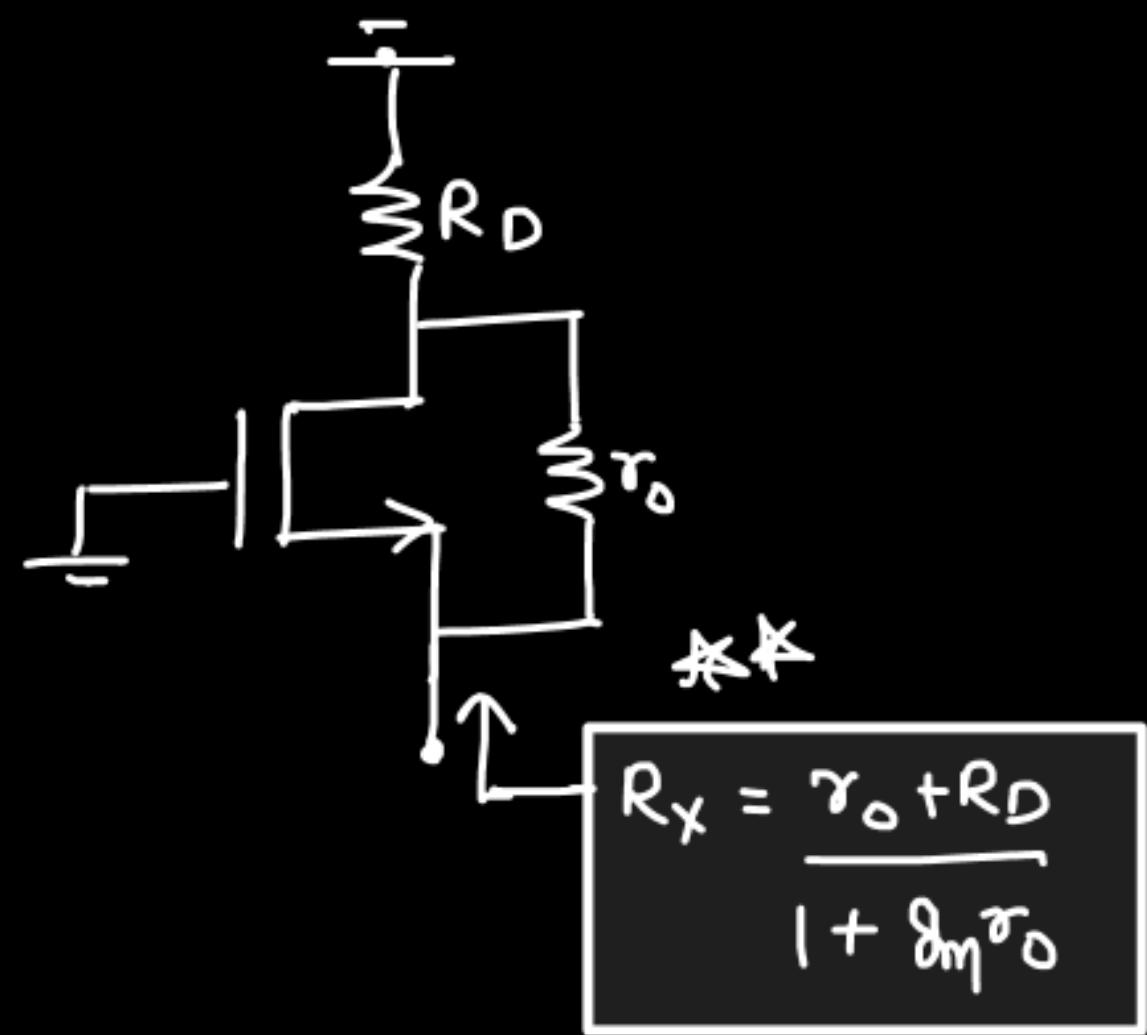

input impedance ( $\lambda=0$ ): -


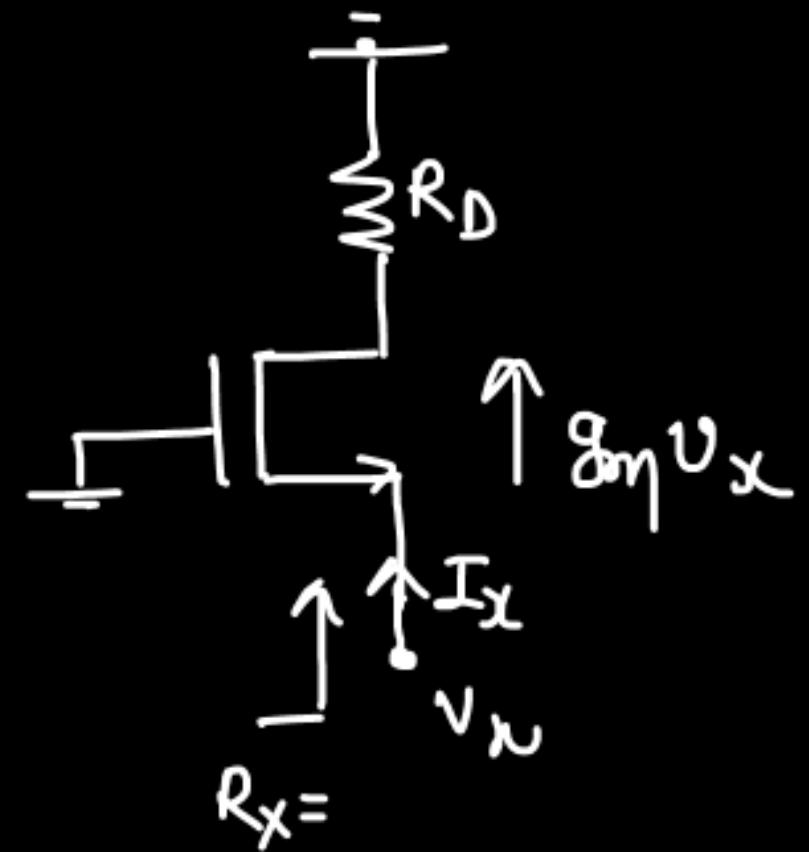


$$g_m v_x = I_x$$

$$\Rightarrow R_x = \frac{v_x}{I_x} = \frac{1}{g_m}$$
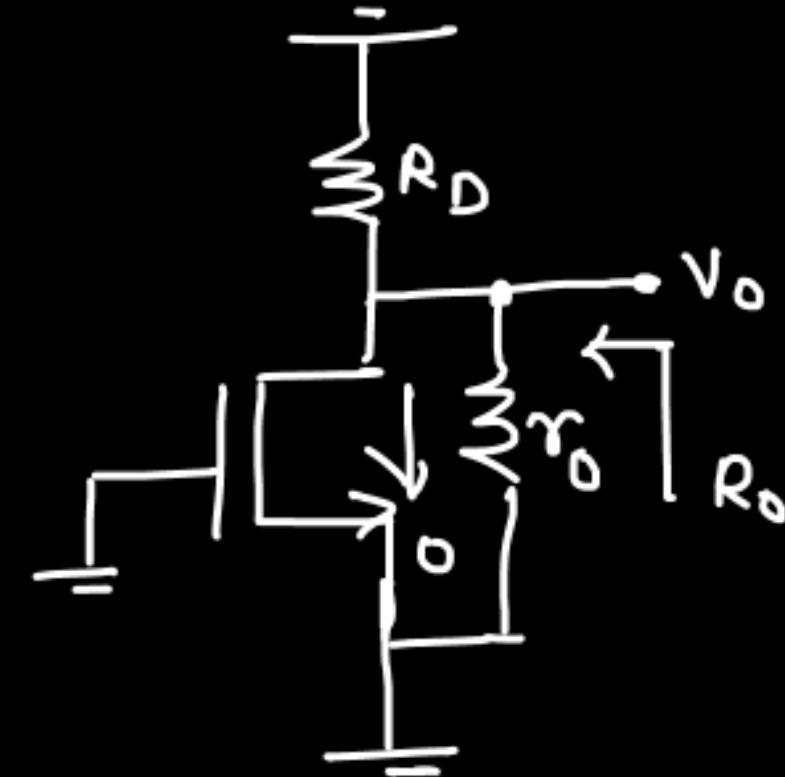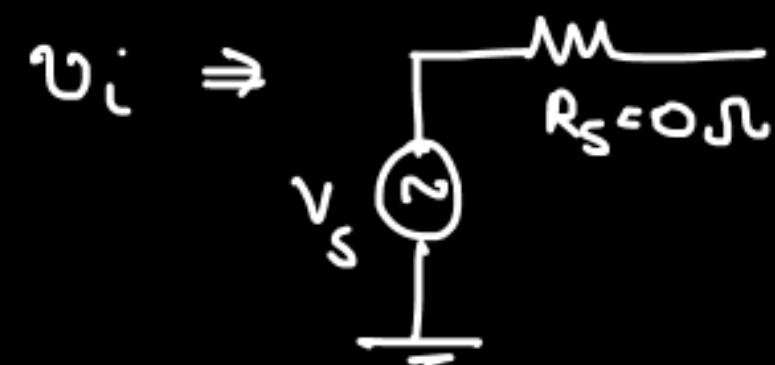
## Output impedance:-

(input source doesn't have any internal resistance)





\* \* \*

$$R_o = R_D \parallel r_o$$
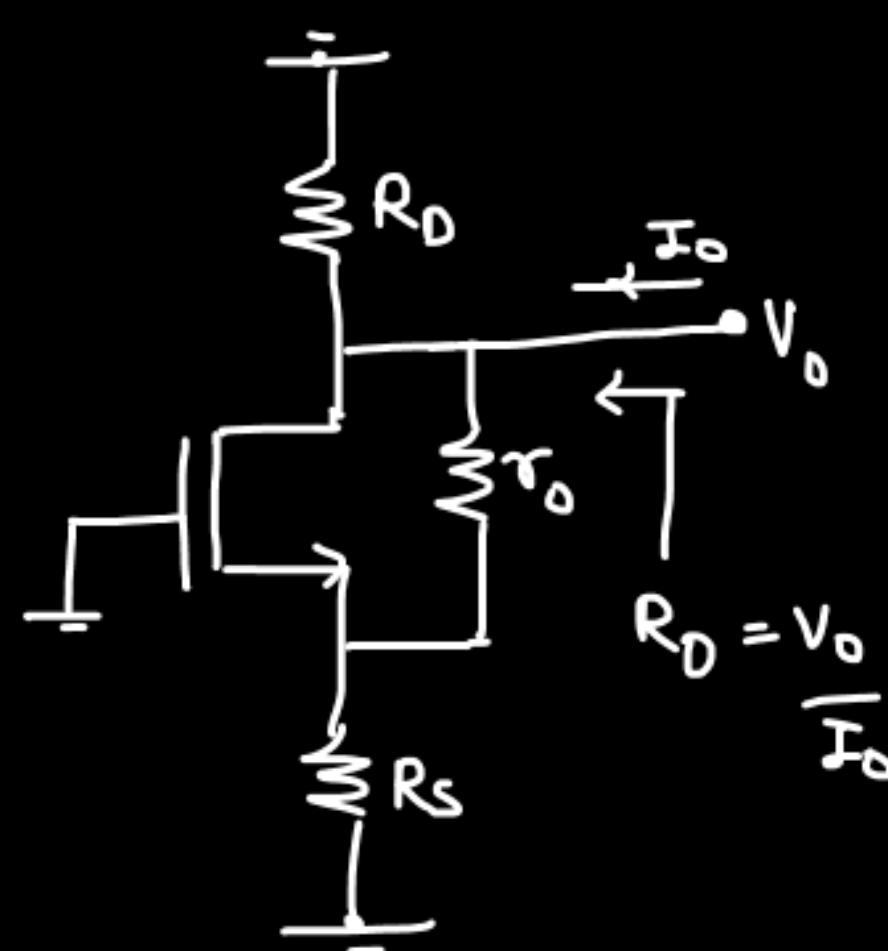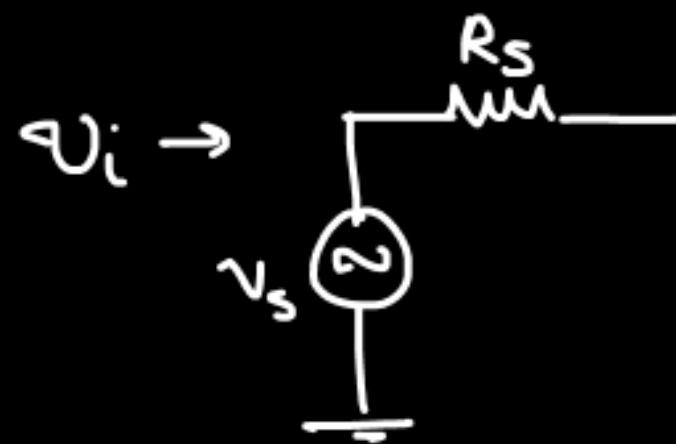
## Output resistance :-


(input source has some internal resistance)



$$R_o = R_D \parallel (r_o + R_s + g_m r_o R_s)$$

$$R_D = \frac{V_o}{I_o}$$

## Current - gain :-

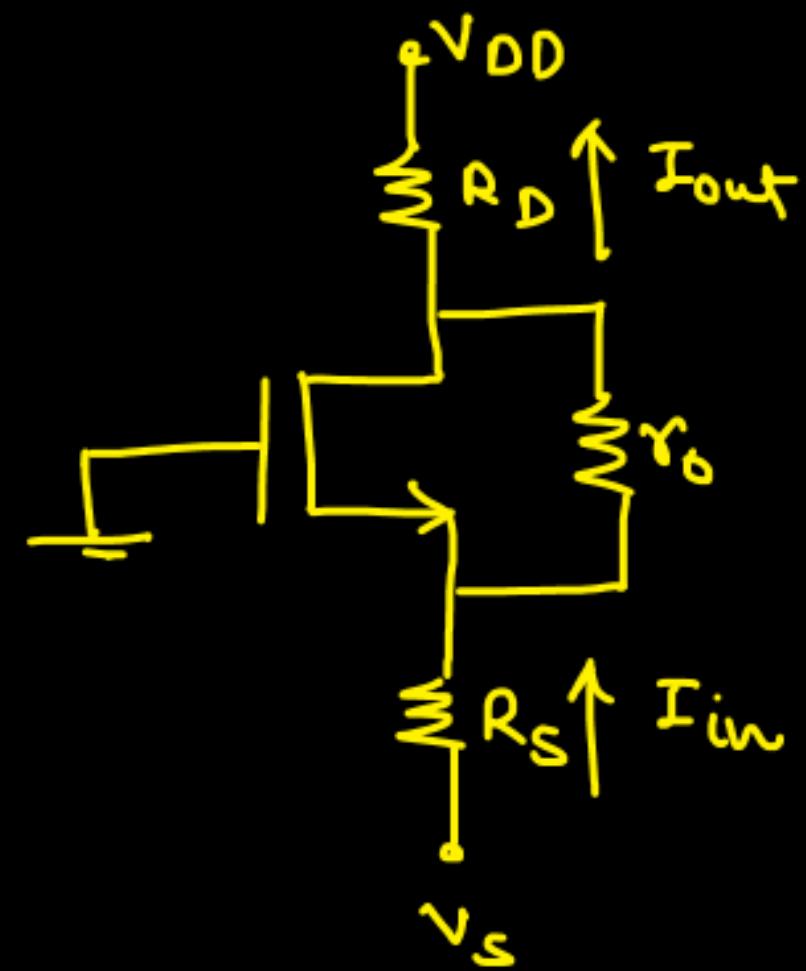


$$I_{in} = I_{out}$$

$$\frac{I_{out}}{I_{in}} = 1$$

$\Rightarrow$  CURRENT  
- BUFFER


COMMON GATE AMPLIFIER = C - BUFFER

## \* Common - drain amplifier :-

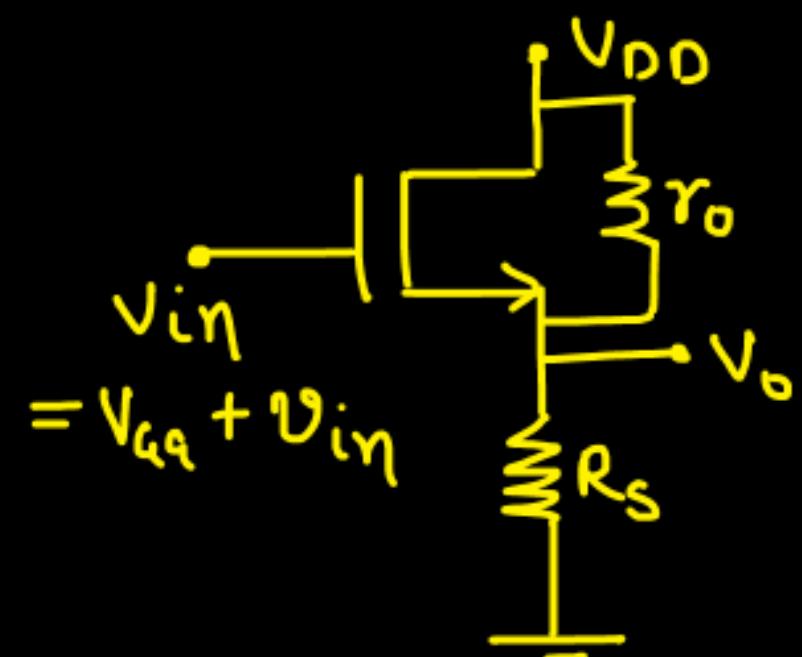


Small signal i/p  $\rightarrow$  Gate  
" " " o/p  $\rightarrow$  Source

## small signal Model :-

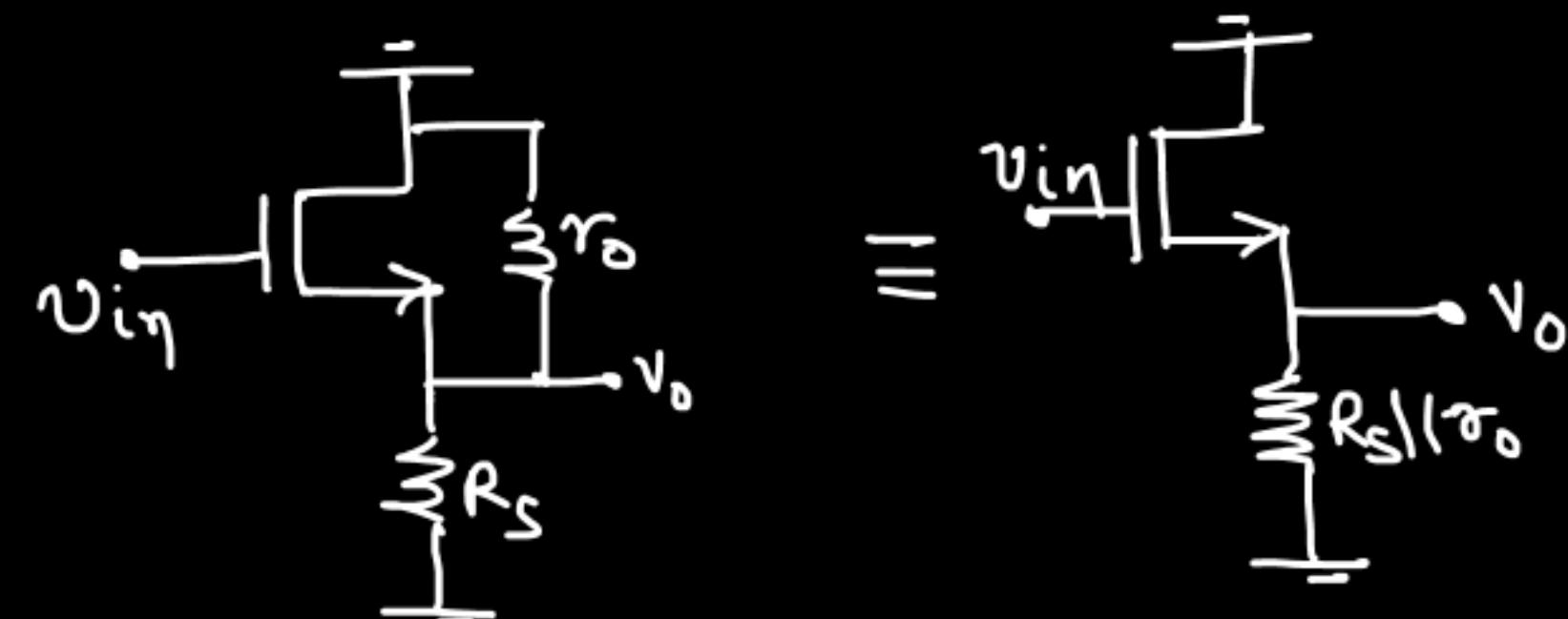

## Voltage gain:-

M-E

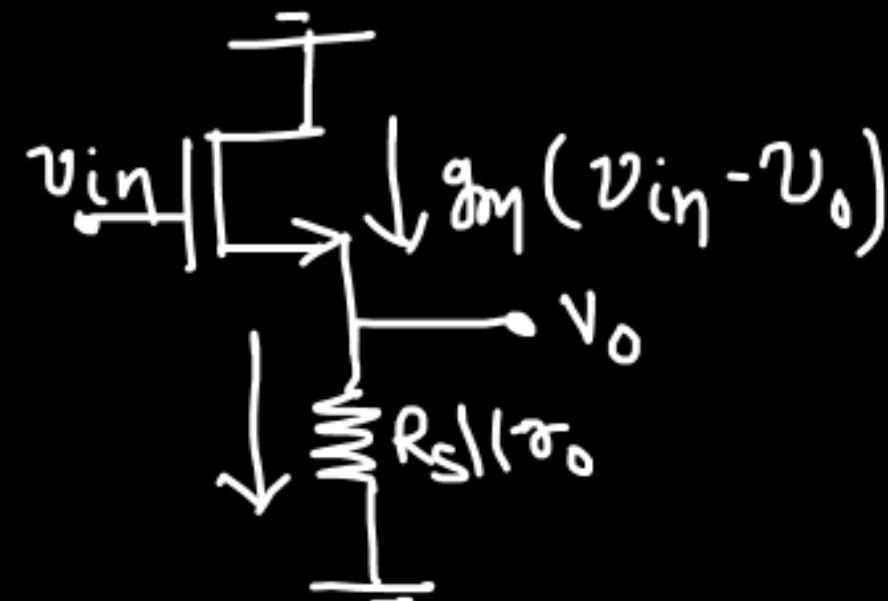

$$g_m(v_{in} - v_o) \times (R_S \parallel r_o) = v_o$$

$$g_m(R_S \parallel r_o) v_{in} = [L + g_m(R_S \parallel r_o)] v_o$$

$$\frac{v_o}{v_{in}} = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)}$$



★★

common - drain  $\equiv$  Source - follower

$$g_m(R_S \parallel r_o) \gg > 1$$

$$\frac{v_o}{v_{in}} = 1 \rightarrow \text{Source-follower}$$

M-II :-

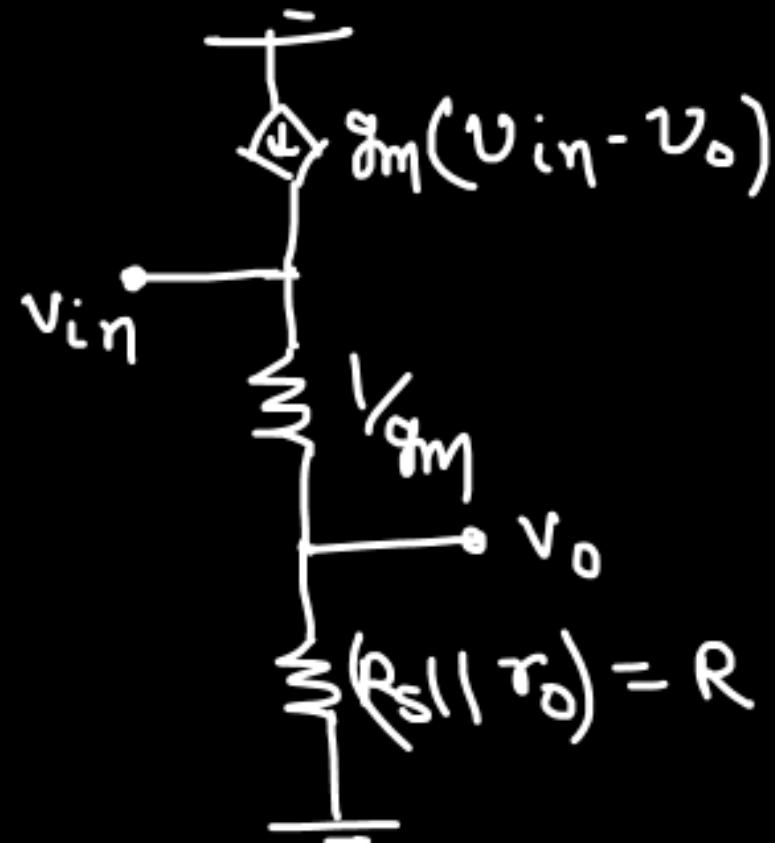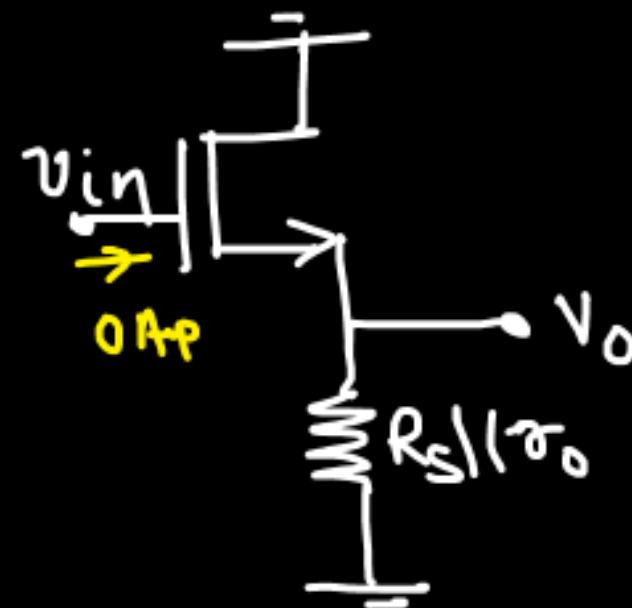

$$v_o = \frac{R}{R + \frac{1}{g_m}} v_{in}$$

$$\frac{v_o}{v_{in}} = \frac{g_m R}{1 + g_m R}$$

$$R = R_S \parallel r_o$$


Current gain :-

$$A_I = \frac{I_o}{I_{in}} = \frac{I_o}{0} = \infty$$

Input Impedance:-

$$R_i = \frac{V_i}{I_i} = \frac{V_i}{0} = \infty$$

Output Impedance:-

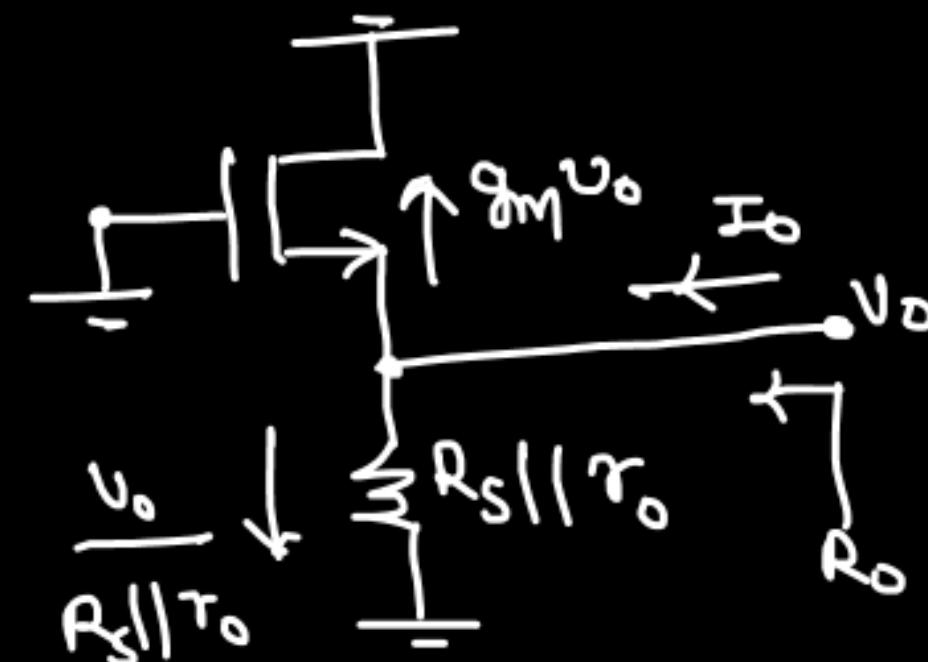


$$R_o = R_s // r_o // \frac{1}{g_m}$$

$$g_m V_o + \frac{V_o}{R_s//r_o} = I_o$$

## \* Summary:-

### ① Common Source Amplifier:-

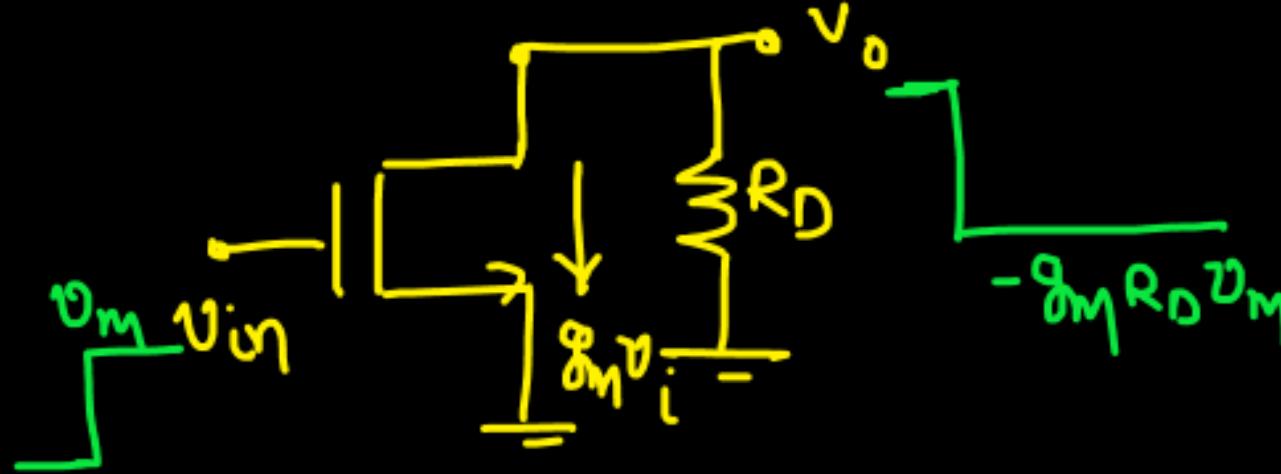


$$A_V = -g_m R_D$$

⇒ There is  $180^\circ$  phase shift  
b/w i(p) and o(p)

$$R_o = R_D // r_o$$

### ② Common GATE amplifier:-

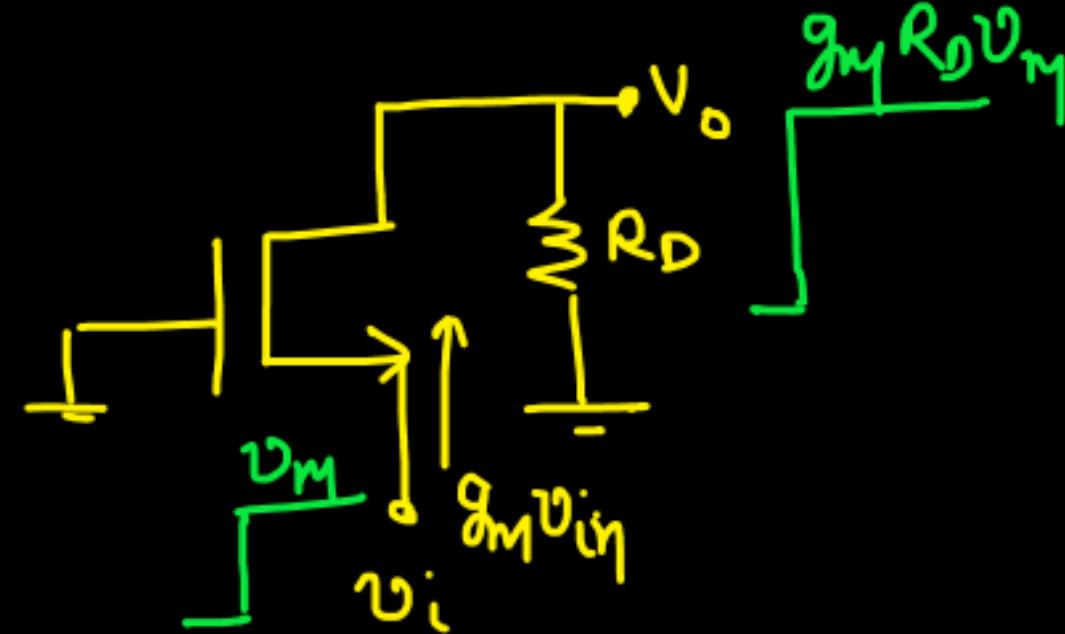


$$A_V = g_m R_D$$

⇒ b/w i(p) and o(p) there is zero degree phase shift

$$R_o = R_D // r_o$$

$$A_I = 1 \Rightarrow C-Buffer$$

### ③ Common - Drain Amplifier:-

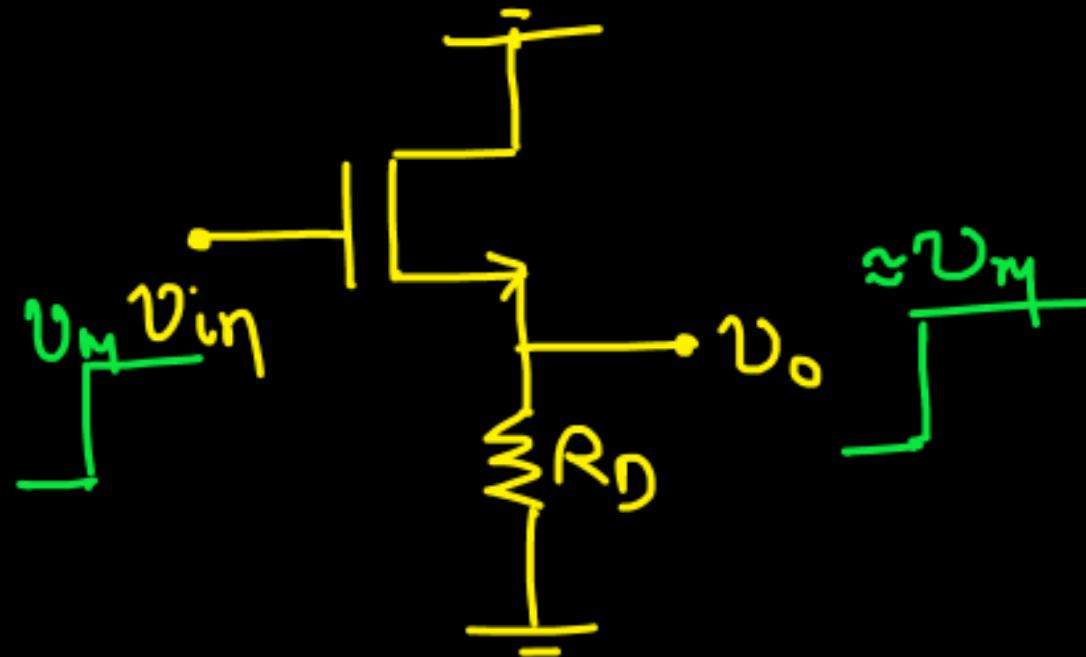


$$A_V = \frac{g_m R_D}{1 + g_m R_D} \approx 1 \Rightarrow \text{source-follower}$$

$\Rightarrow$  There is zero degree phase shift b/w i/p and o/p

$$R_o = R_D \parallel r_{o\parallel} \parallel \frac{1}{g_m}$$

Q.

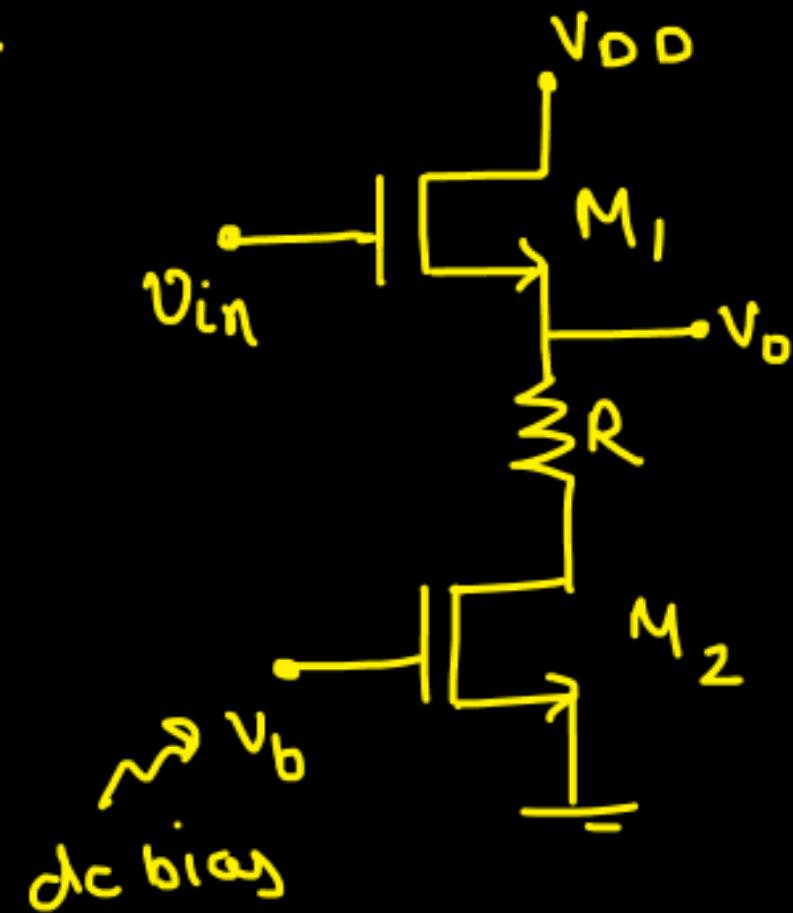

$$g_m_1 = 1.92 \text{ mS}$$

$$g_m_2 = 1.8 \text{ mS}$$



$$r_{ds1} = 20.63 \text{ k}\Omega = r_{o1}$$

$$r_{ds2} = 23.89 \text{ k}\Omega = r_{o2}$$

$$R = 4.6 \text{ k}\Omega$$

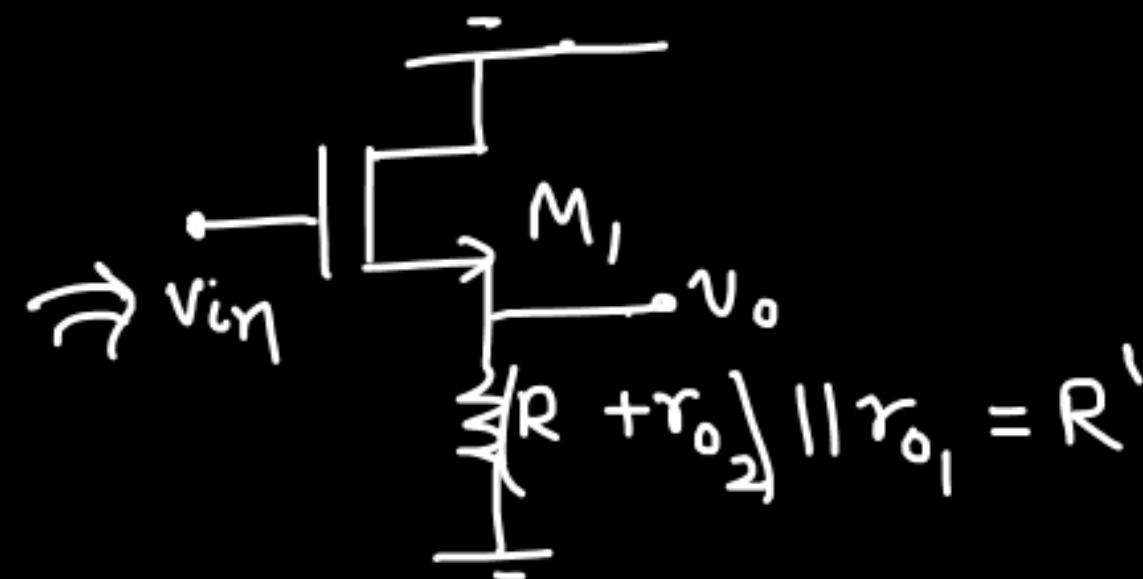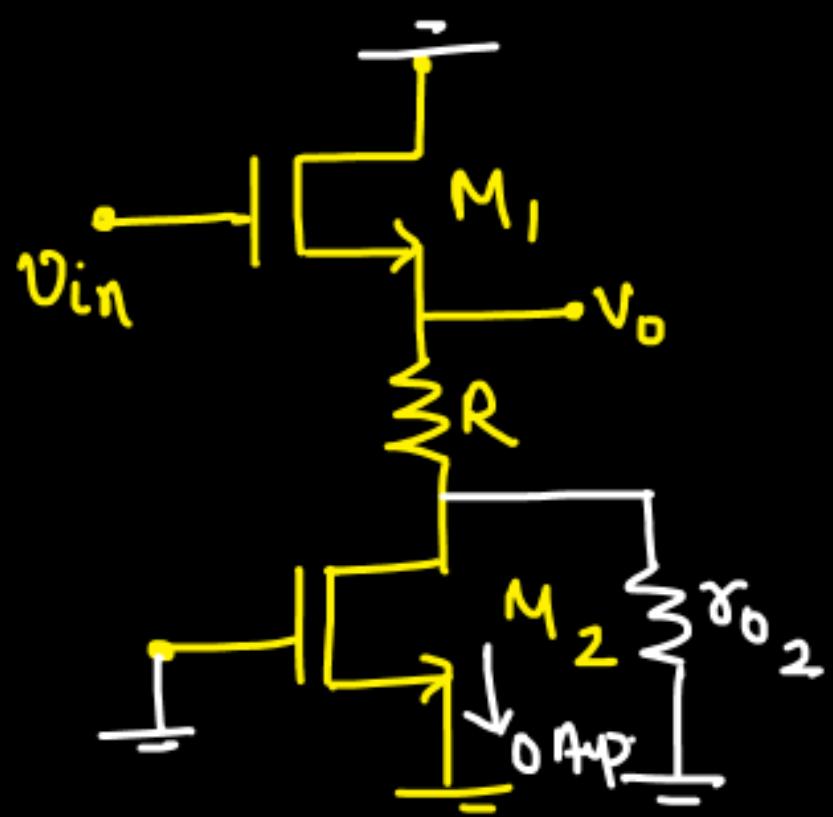Find small signal voltage gain  $\frac{v_o}{v_{in}}$ .






$$\frac{v_o}{v_{in}} = \frac{R'}{R' + \frac{1}{g_m 1}} = \frac{g_m R'}{1 + g_m R'}$$

$$R' = 28.49 \text{ k}\Omega \parallel 20.63 \text{ k}\Omega = 11.96 \text{ k}\Omega$$

$$g_m R' = 1.92 \text{ m} \times 11.96 \text{ k} = 22.97$$

$$\frac{v_o}{v_{in}} = \frac{22.97}{43.97} \approx 0.52$$

Q.

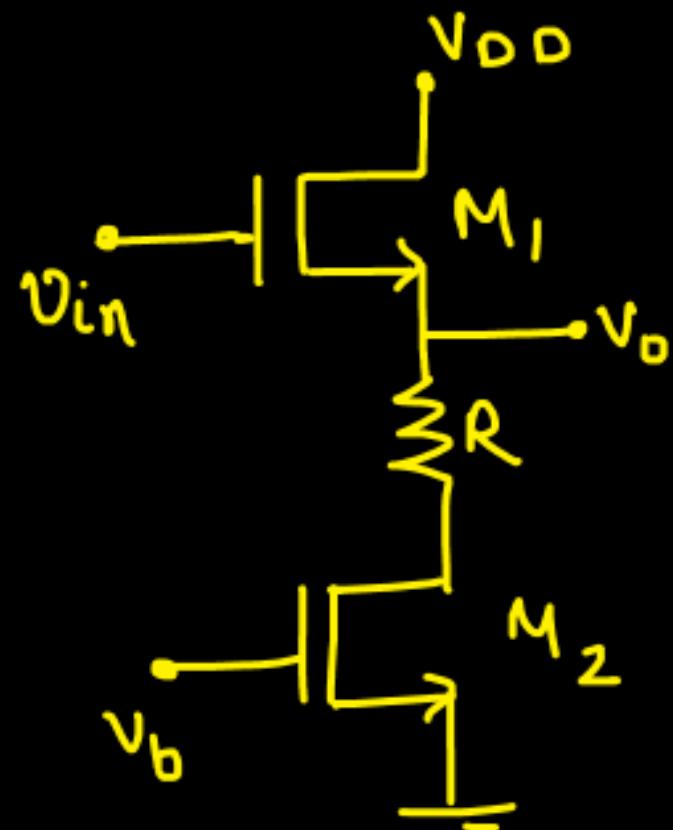

$$g_{m_1} = 1.92 \text{ mS}$$



$$g_{m_2} = 1.8 \text{ mS}$$

$$r_{ds1} = 20.63 \text{ k}\Omega$$

$$r_{ds2} = \infty$$

$$R = 4.6 \text{ k}\Omega$$

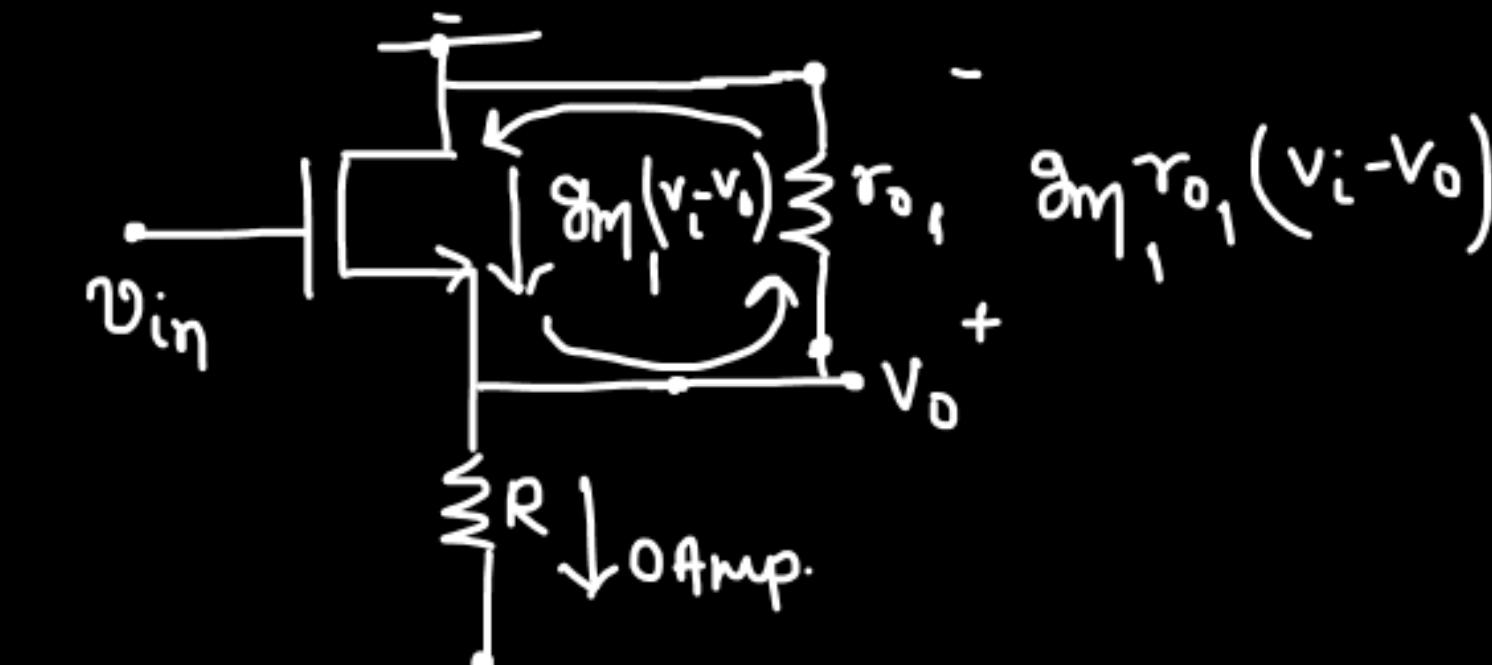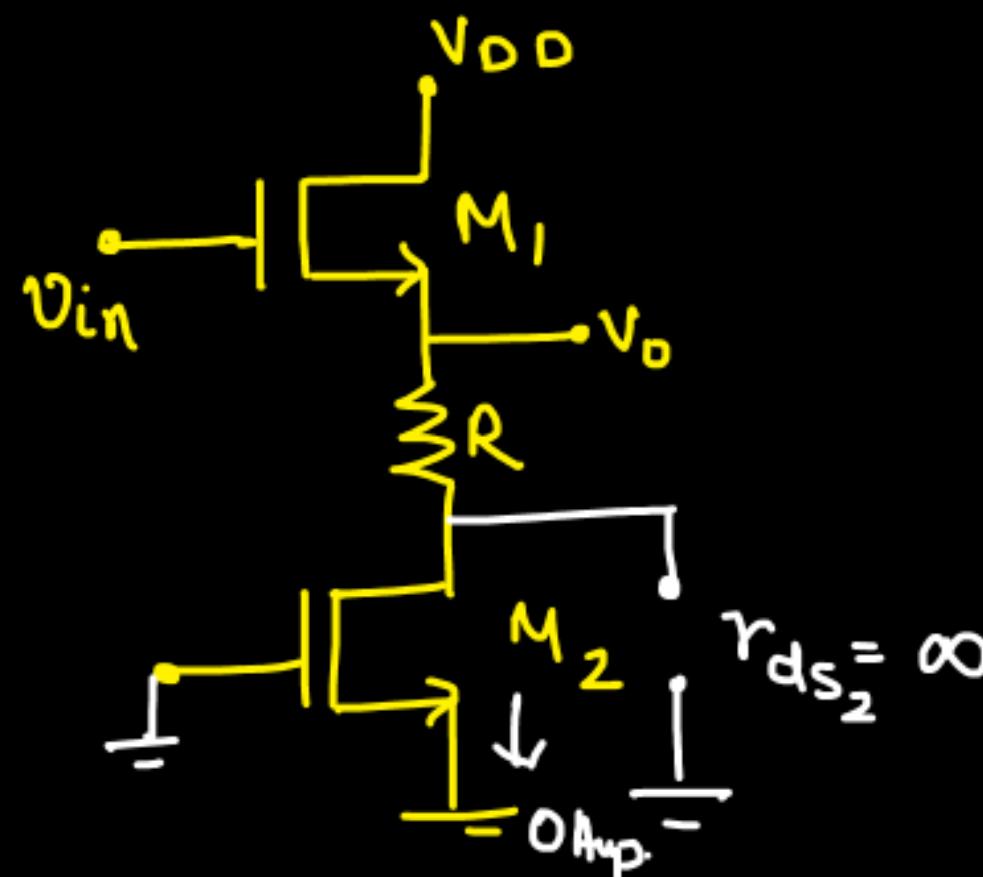small signal voltage gain  $\frac{v_o}{v_{in}} = ?$




$$g_m r_{ds1} (v_i - v_o) = V_o$$

$$g_m r_{ds1} v_i = (1 + g_m r_{ds1}) V_o$$

$$\frac{V_o}{V_i} = \frac{39 \cdot 6096}{40 \cdot 6096} = 0.975$$

$$\frac{V_o}{V_i} = \frac{g_m r_{ds1}}{1 + g_m r_{ds1}}$$

Q.

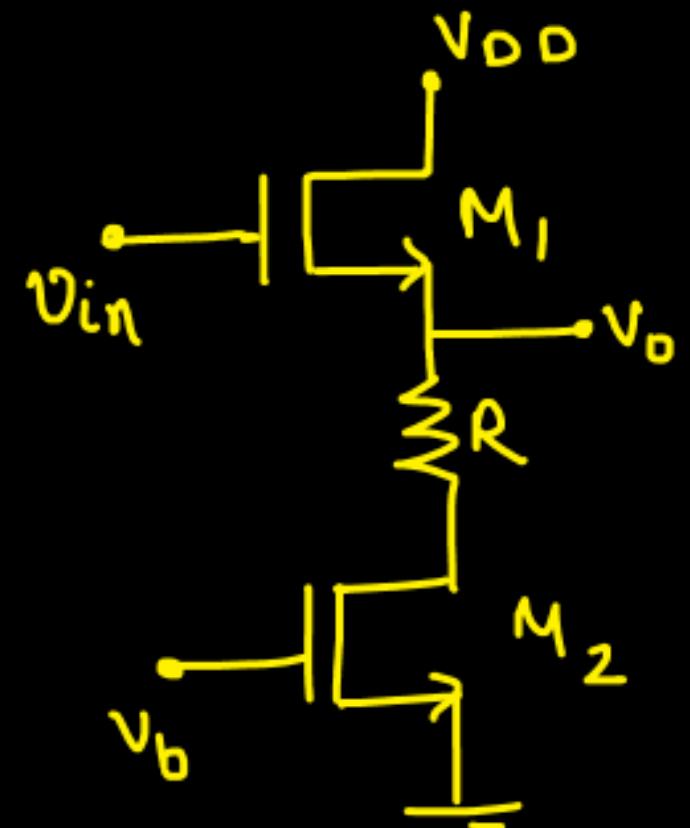

$$g_m_1 = 1.92 \text{ mS}$$



$$g_m_2 = 1.8 \text{ mS}$$

$$r_{ds1} = \infty$$

$$r_{ds2} = \infty$$

$$R = 4.6 \text{ k}\Omega$$

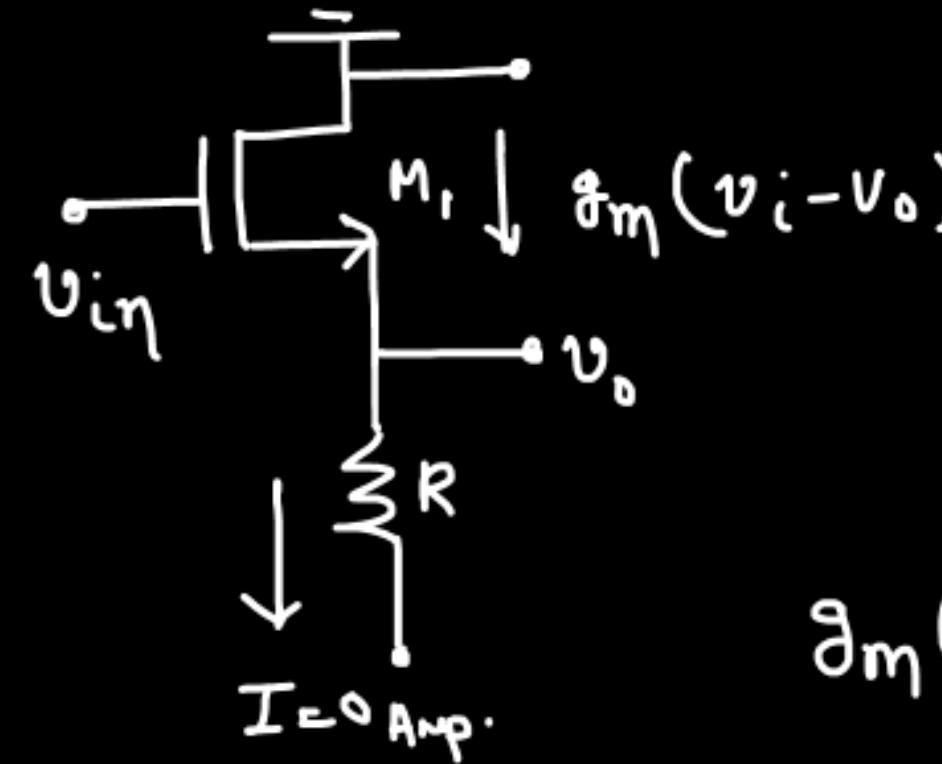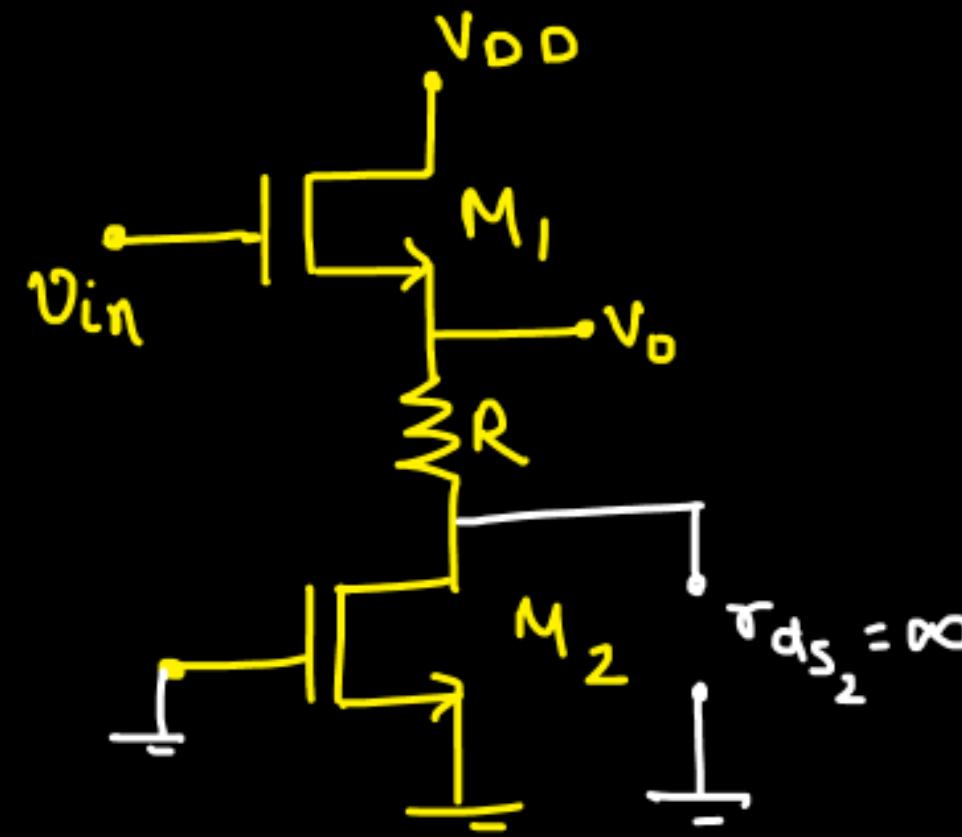small signal voltage gain  $\frac{V_0}{V_{in}} = ?$



$$\partial_m(v_i - v_o) = 0$$

$$v_i = v_o$$

★

$\frac{v_o}{v_i} = 1$
-----------------------

\* Interesting Method of finding voltage gain :.  
( $G_m R_{out}$  Method)

---

\* Small signal voltage gain of any configuration

$$A_V = G_m R_{out}$$

$$G_m \neq g_m$$



$$A_V = \frac{V_o}{V_s} = G_m R_{out}$$


①  $G_m \rightarrow$

Short ckt the opamp and find out the relation  
b/w  $I_{out}$  and  $V_s$ .




$$G_m = \frac{I_{out}}{V_s}$$

② Find small signal out resistance:-

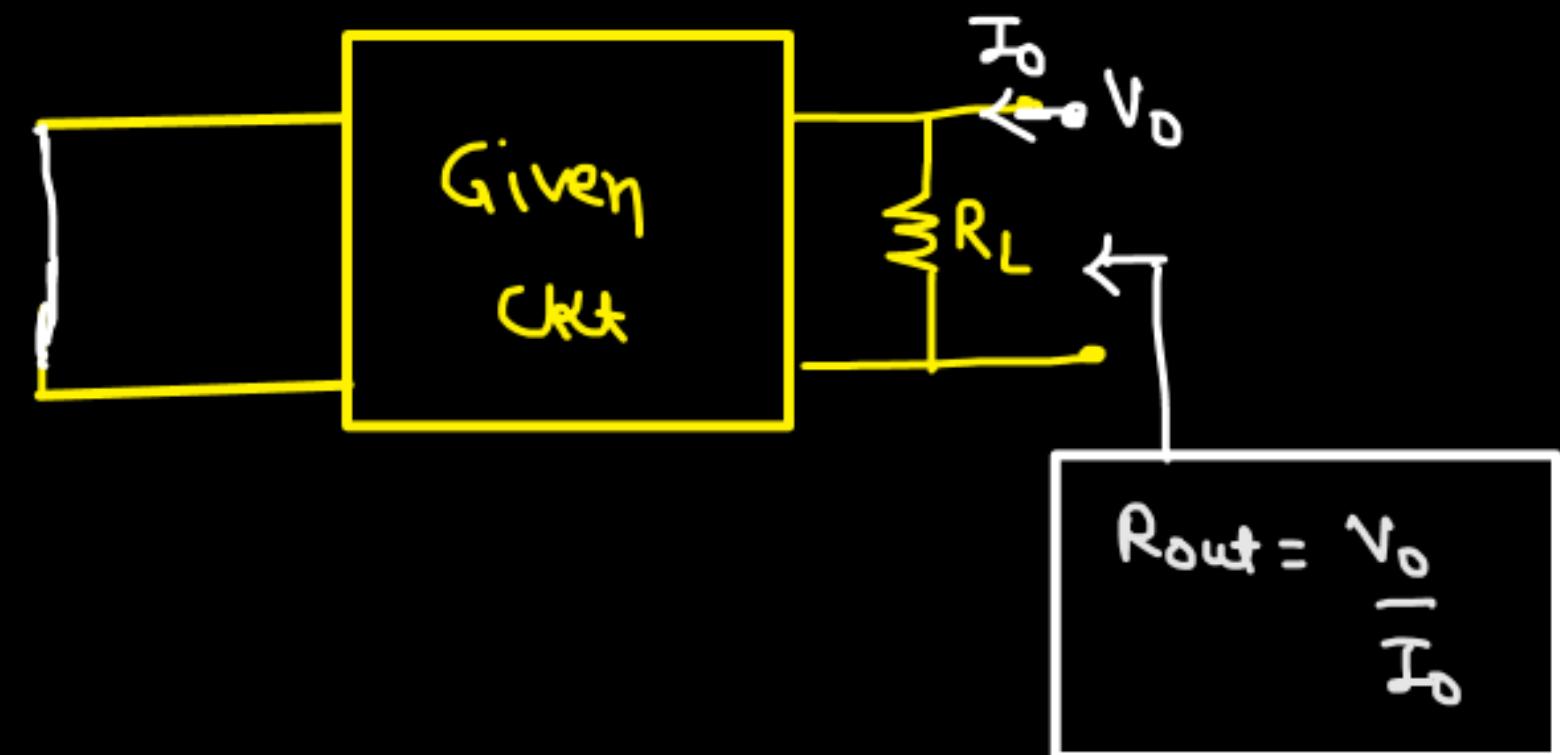


Eg → find small signal gain.


①

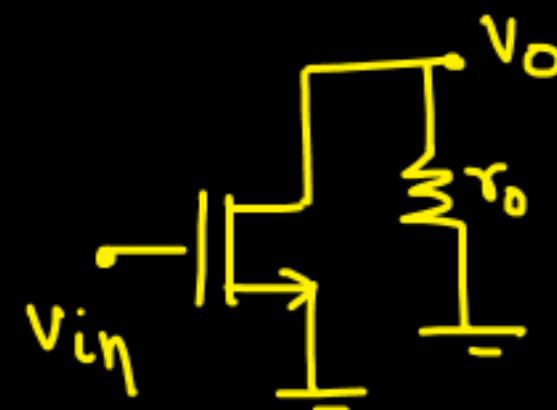

①  $G_m \rightarrow$

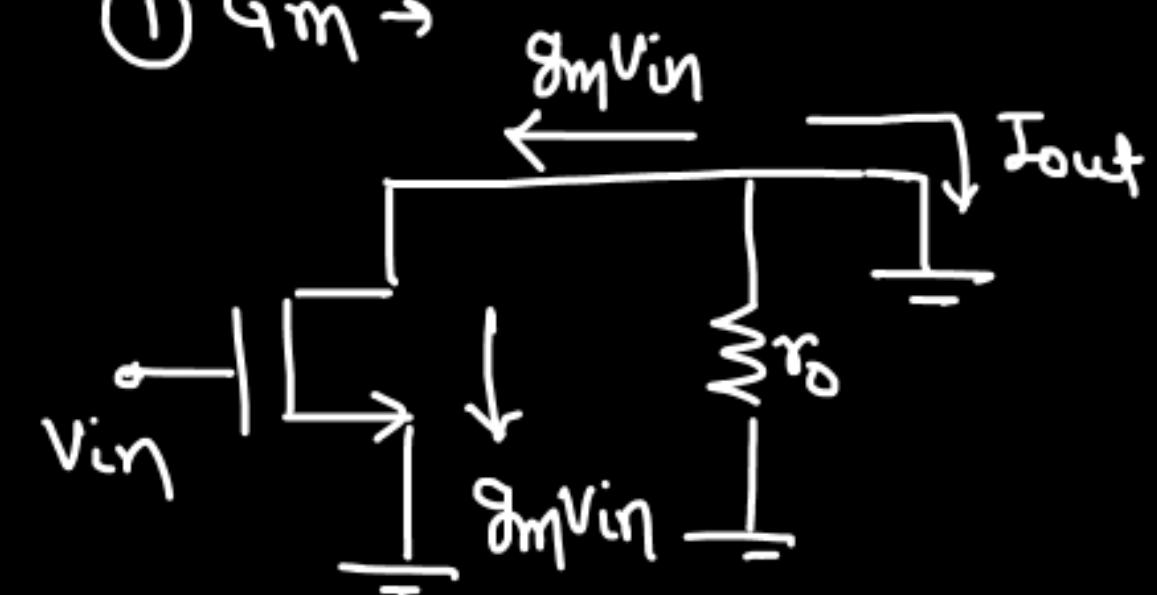

②  $R_{out} \rightarrow$


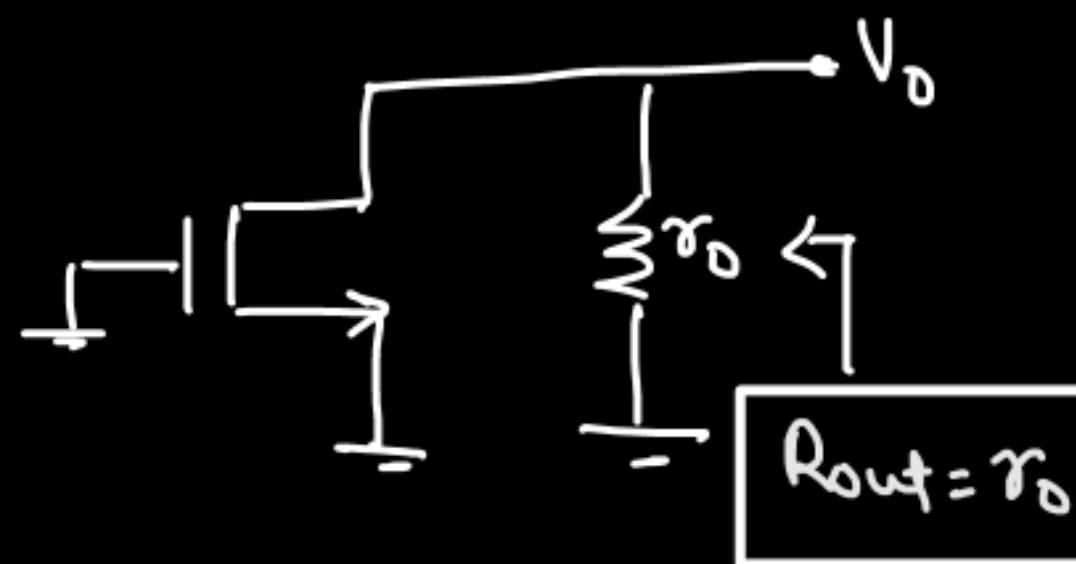


$$I_{out} = -\delta m V_{in}$$


$$G_m = \frac{I_{out}}{V_{in}} = -\delta m$$

$$\text{Gain} = -\delta m r_o$$

②

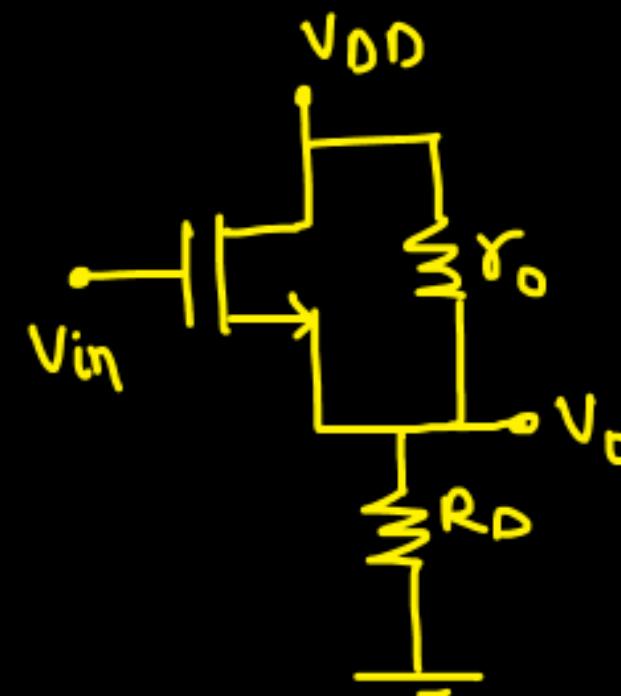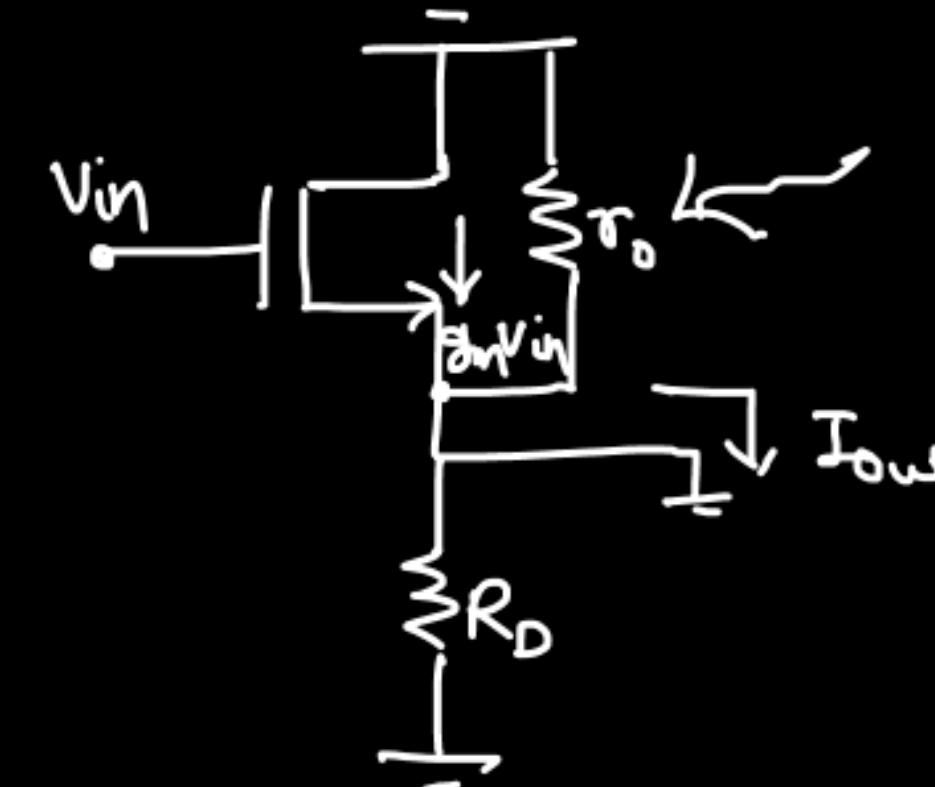 $\rightarrow \textcircled{1} \quad g_m \rightarrow$ 

②

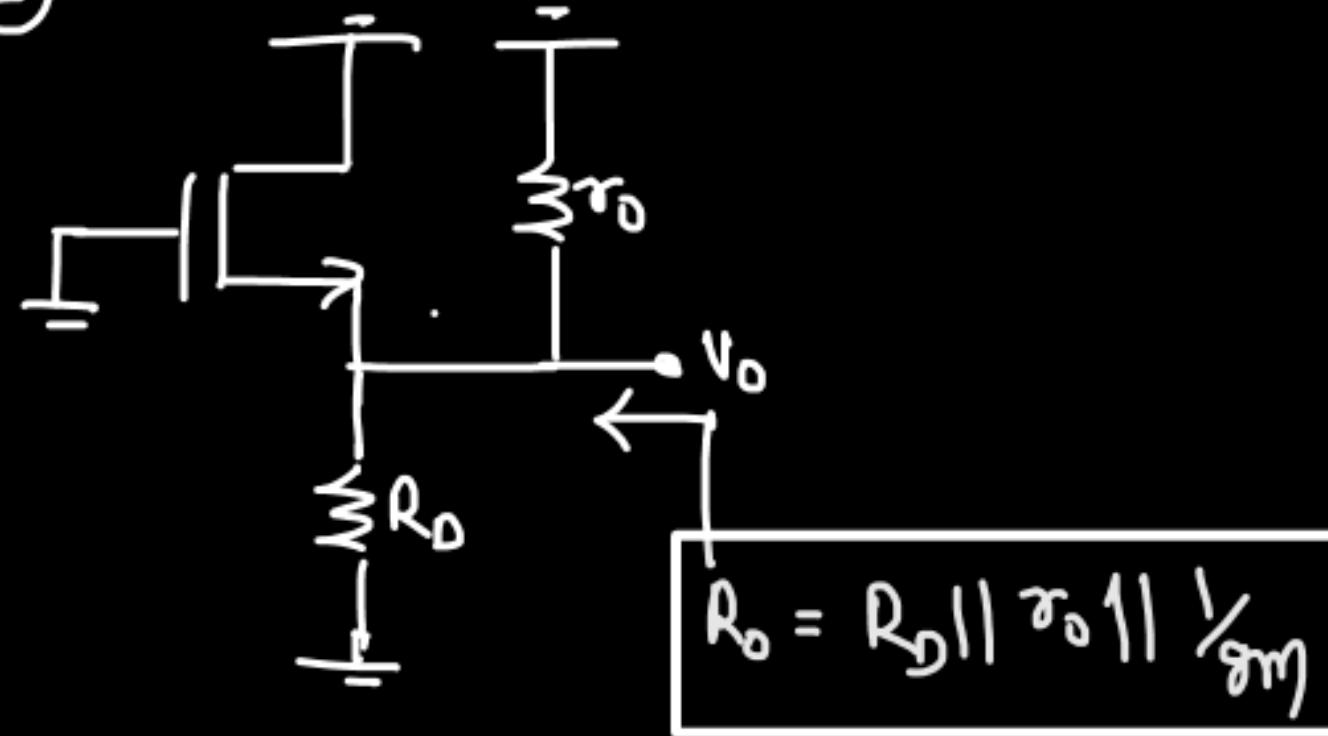


$$\Rightarrow I_{out} = g_m V_{in}$$

$$g_m = g_m$$


$$\Rightarrow A_V = g_m [R_D \parallel r_0 \parallel \frac{1}{g_m}]$$

③

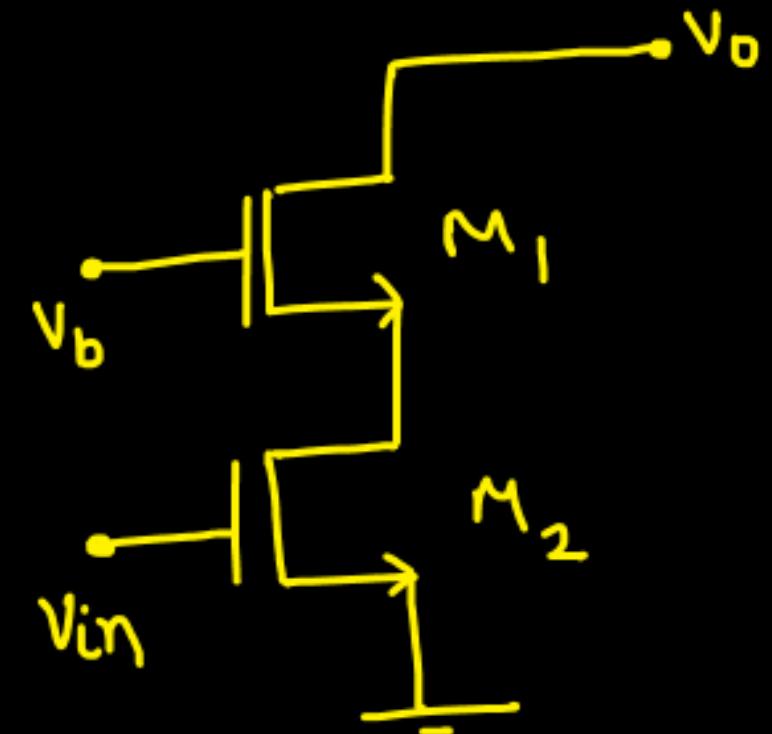

$\tau_{o1}$  and  $\tau_{o2}$  are very high


$$\Rightarrow G_m = ?$$

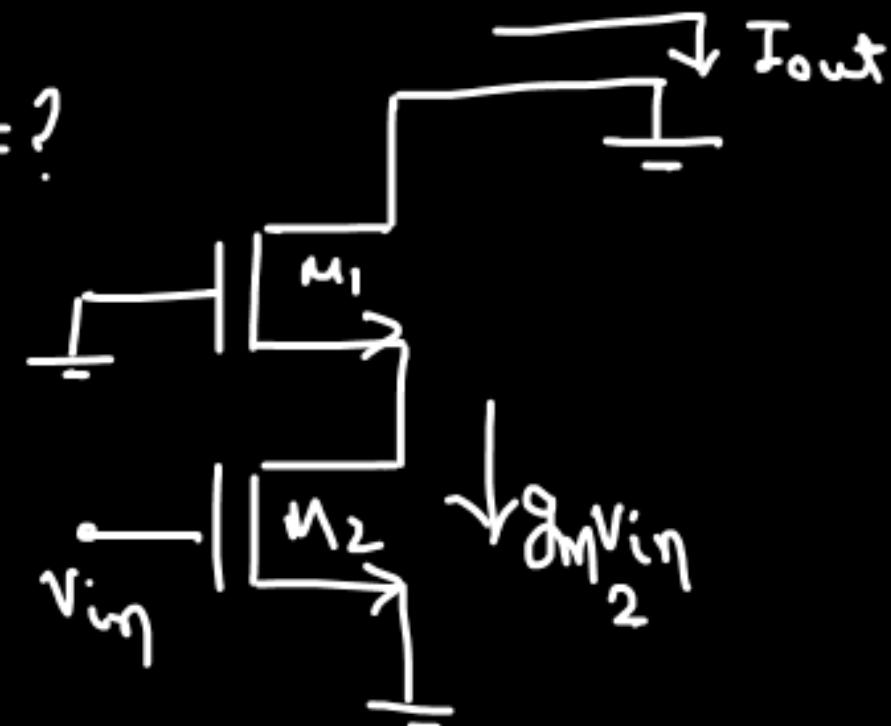

$$I_{out} = -g_m V_{in}$$

$$G_m = -g_m$$


$R_{out}$

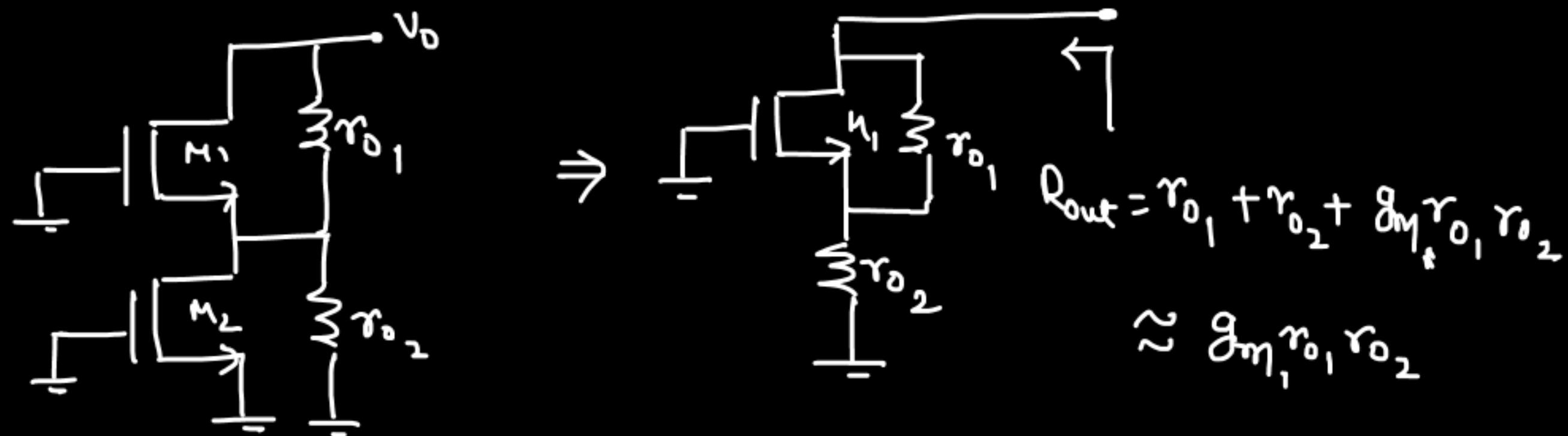

$$\Rightarrow \text{Gain} \approx -g_{m_2} [r_{o1} + r_{o2} + g_{m_1} r_{o1} r_{o2}]$$

$$\text{Gain} \approx -g_{m_2} g_{m_1} r_{o1} r_{o2}$$

Q.

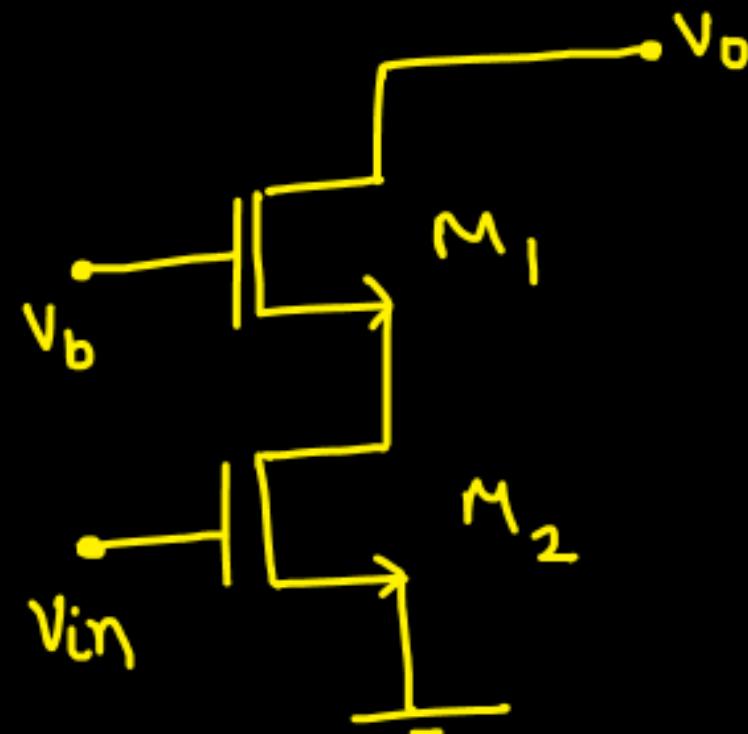

let's assume,


$$\frac{1}{g_m_1} = r_{o_1} = r_{o_2} = 2 \text{ k}\Omega$$

$$g_m_2 = 3 \text{ mS}$$

Find  $\frac{V_o}{V_{in}} = ?$

NOTE-

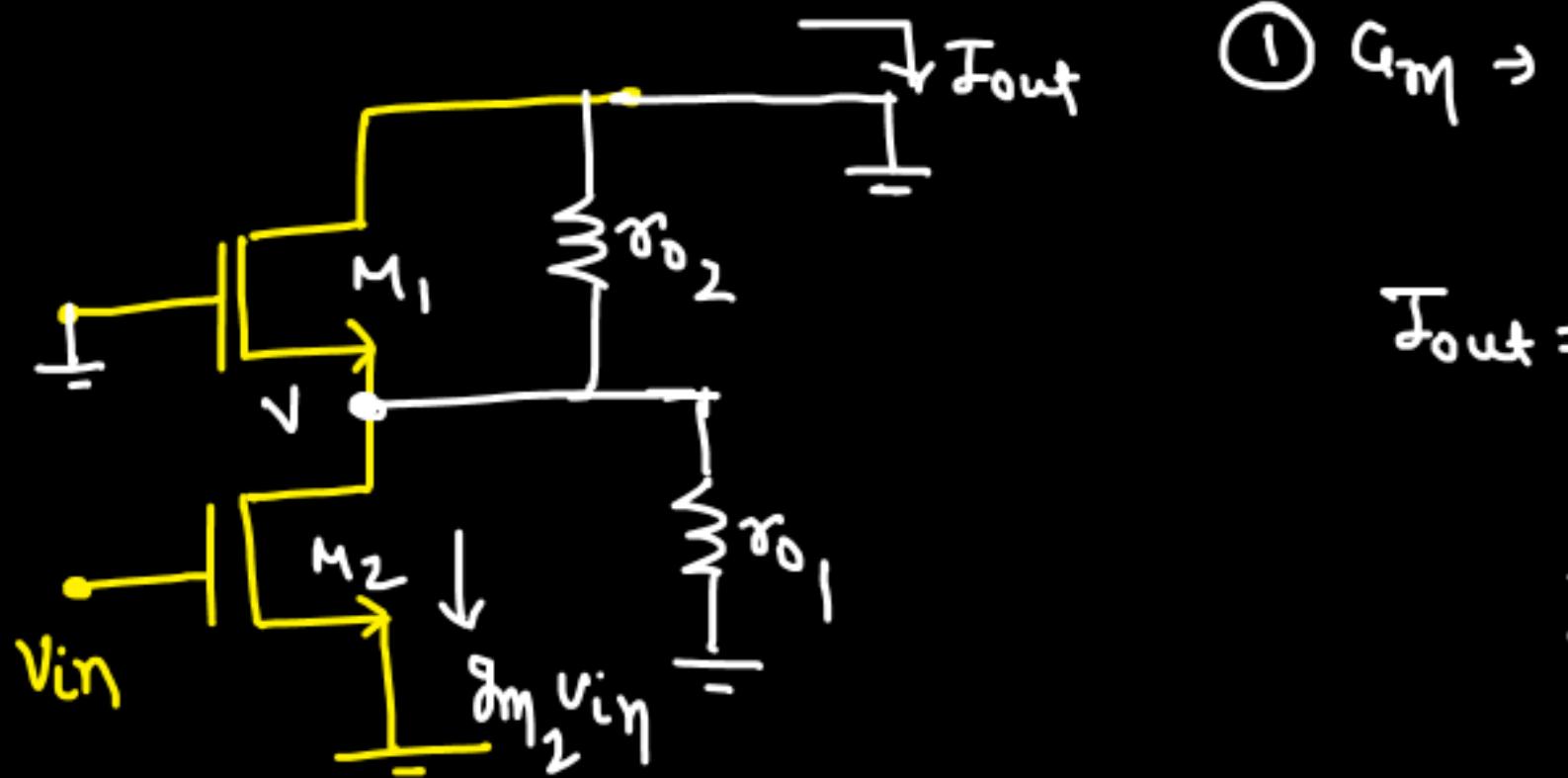
Generally  $g_m$  values are in  $\text{mS}$  and  $r_o$  values are in  $\text{M}\Omega$ . We took such values only for understanding purpose.



$$I_{out} = - \left[ \frac{g_m M_2 V_{in}}{3} + \frac{g_m M_2 V_{in}}{3} \right]$$

$$I_{out} = - \frac{2 g_m M_2 V_{in}}{3}$$

$$G_m = - \frac{2 g_m M_2}{3}$$

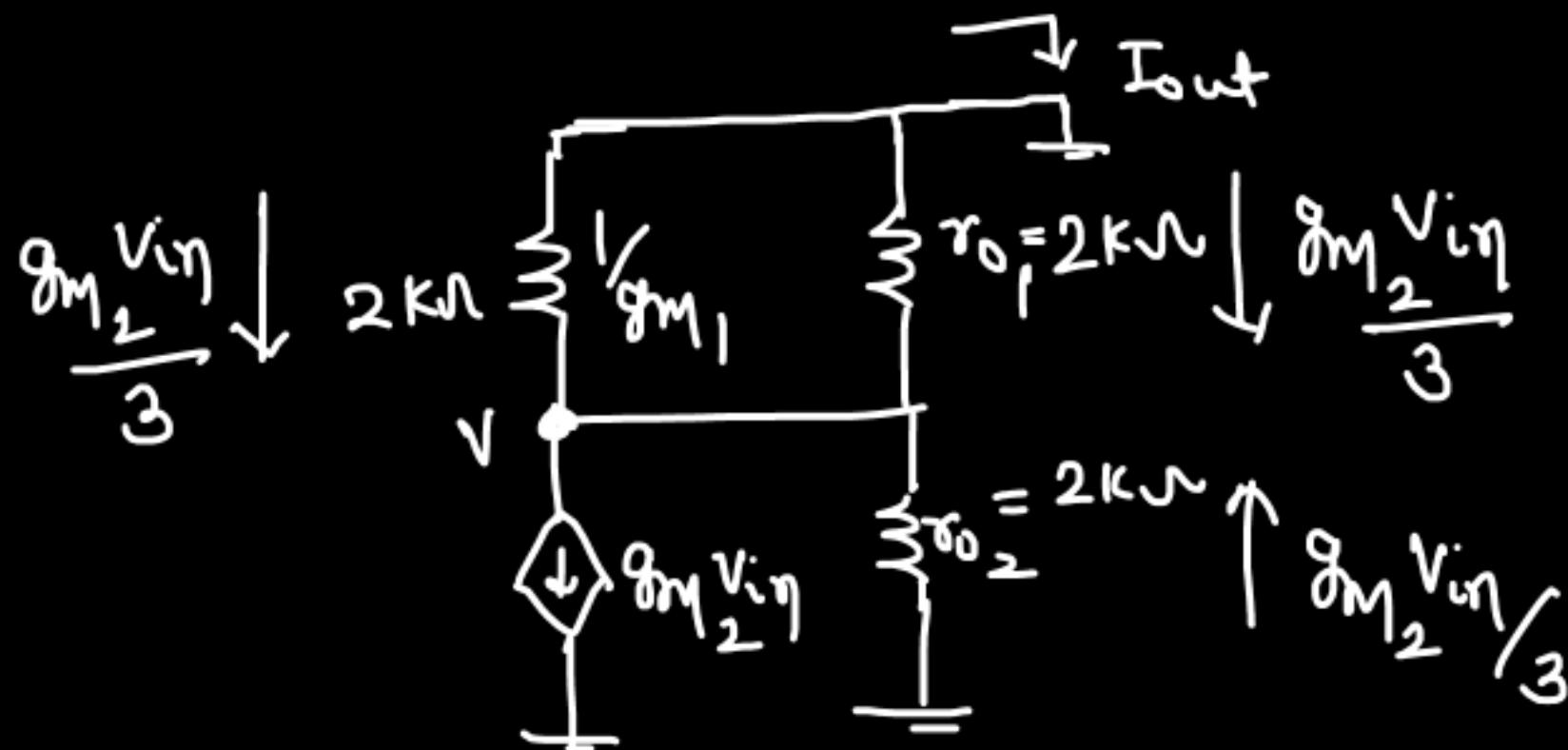

$$R_{out} = r_{o_1} + r_{o_2} + g_m r_{o_1} r_{o_2}$$
$$= 2k + 2k + \frac{1}{2k} \times 2k \times 2k$$


$$R_{out} = 6k\Omega$$

$$\alpha_v = -\frac{2}{3} \times 3mS \times 6k\Omega$$

$$\alpha_v = -12 \text{ v/v}$$

## MOS Amplifiers using PMOS:-


### ① Common Source Amplifier:-

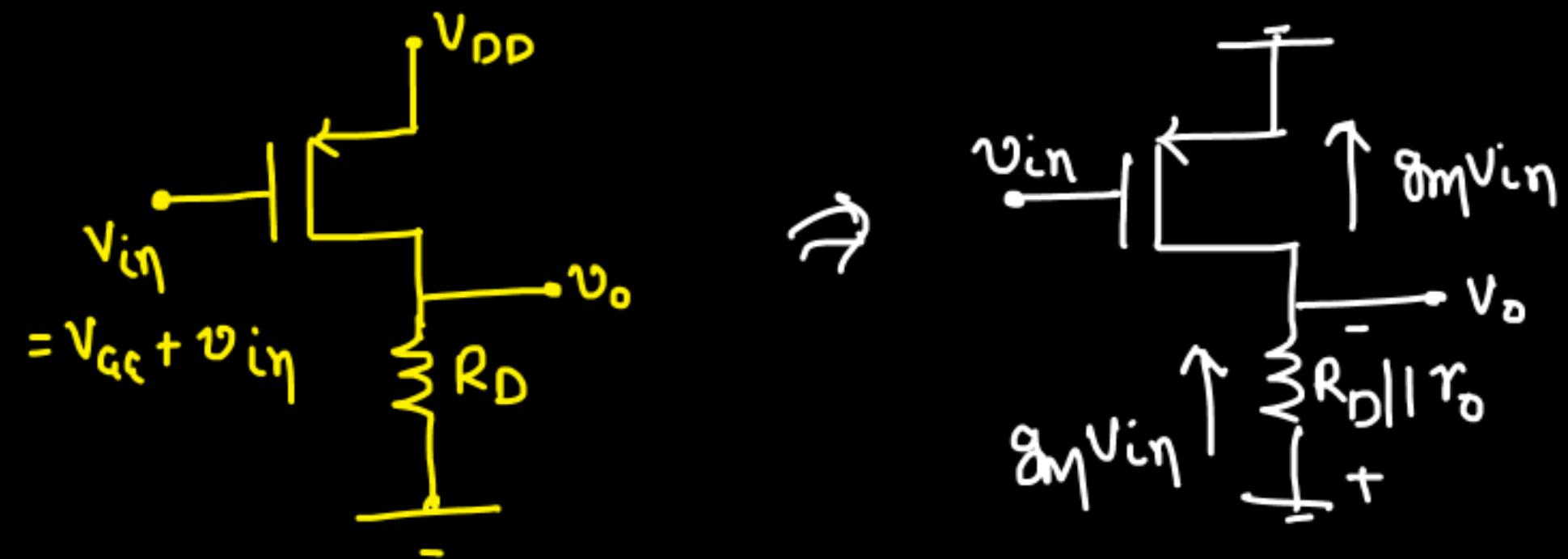

$$\frac{v_o}{v_{in}} = -g_m (R_D || r_o)$$


$\Rightarrow$  Current gain =  $I/P$  resistance  $= \infty$  ( $I/P$  current=0)

$\Rightarrow$  O/P impedance:-

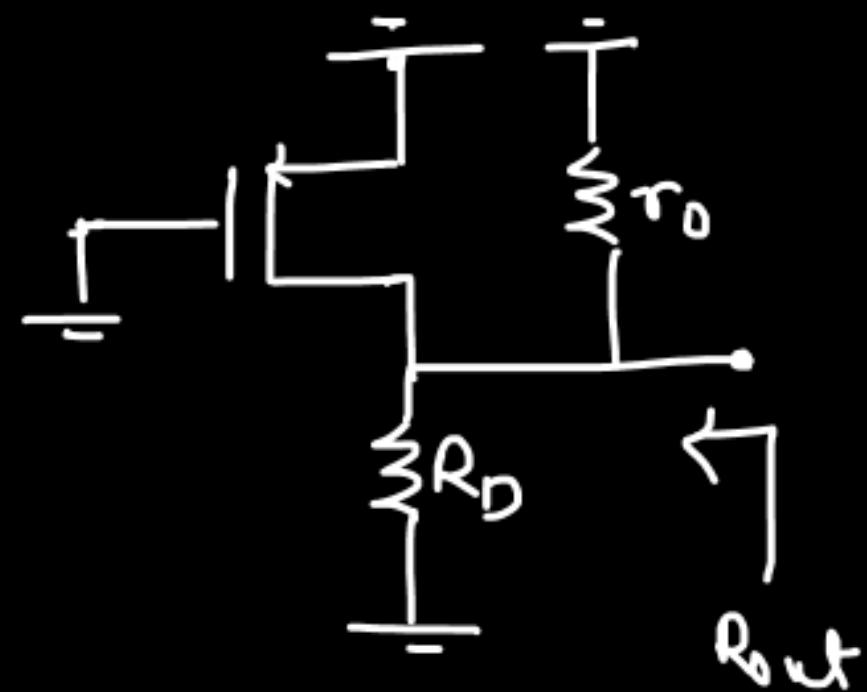

$$R_o = r_o \parallel R_D$$
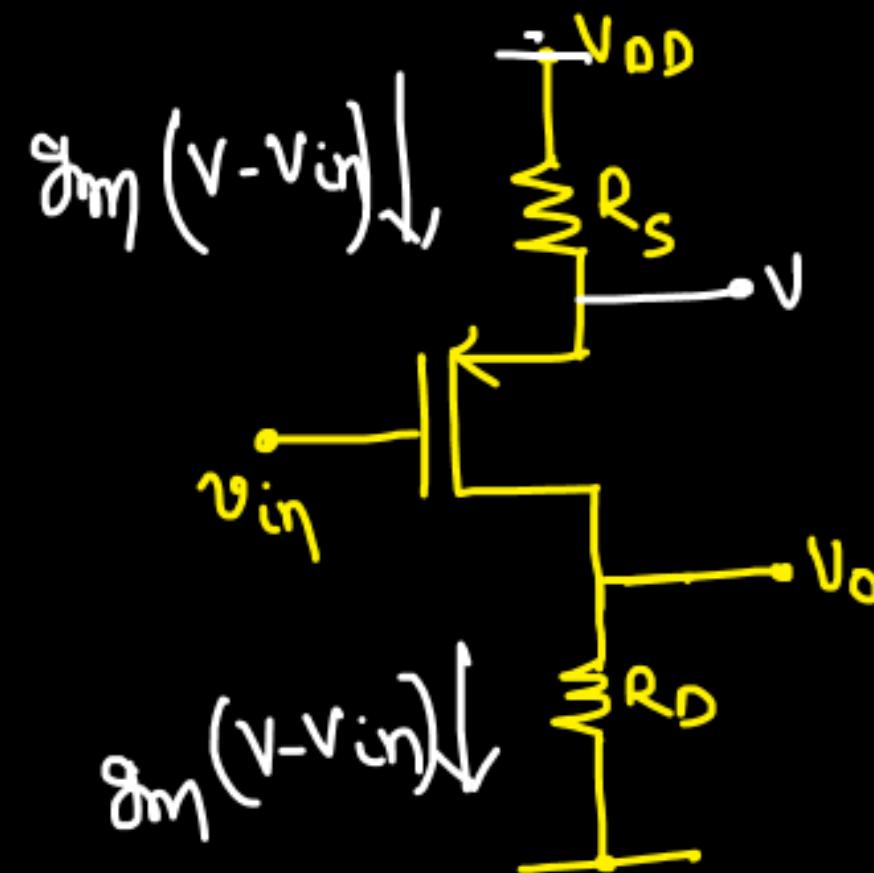
## Common Source Amplifier with degeneration:-



$$\lambda = 0$$

$$A_V = -\frac{g_m R_D}{1 + g_m R_S}$$

$$\Rightarrow \frac{V}{R_S} = -\frac{V_O}{R_D}$$

$$V_O = g_m R_D \left[ -\frac{R_S}{R_D} V_O - V_{IN} \right]$$

$$V = -\frac{R_S}{R_D} V_O$$

$$V_O [1 + g_m R_S] = -g_m R_D V_{IN}$$

$$\Rightarrow \frac{V_O}{V_{IN}} = -\frac{g_m R_D}{1 + g_m R_S}$$


$$A_V = -\frac{g_m R_D}{1 + g_m R_S}$$

$$g_m R_S \gg 1$$



$$A_V = -\frac{g_m R_D}{g_m R_S}$$

$$A_V = -\frac{R_D}{R_S} \rightarrow \text{constant gain (very stable)}$$

O/P impedance :-

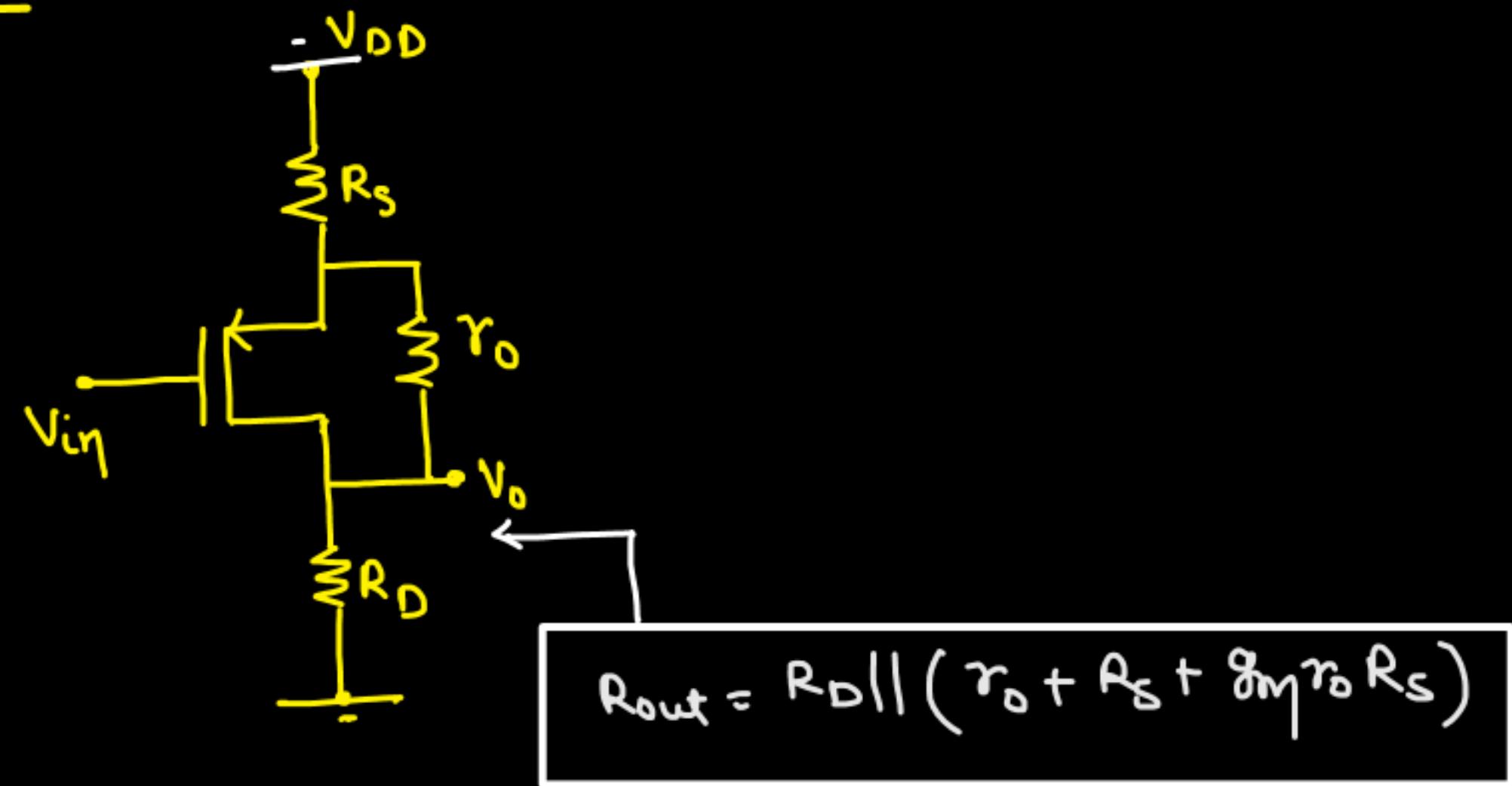


## ② Common Gate Amplifier:-

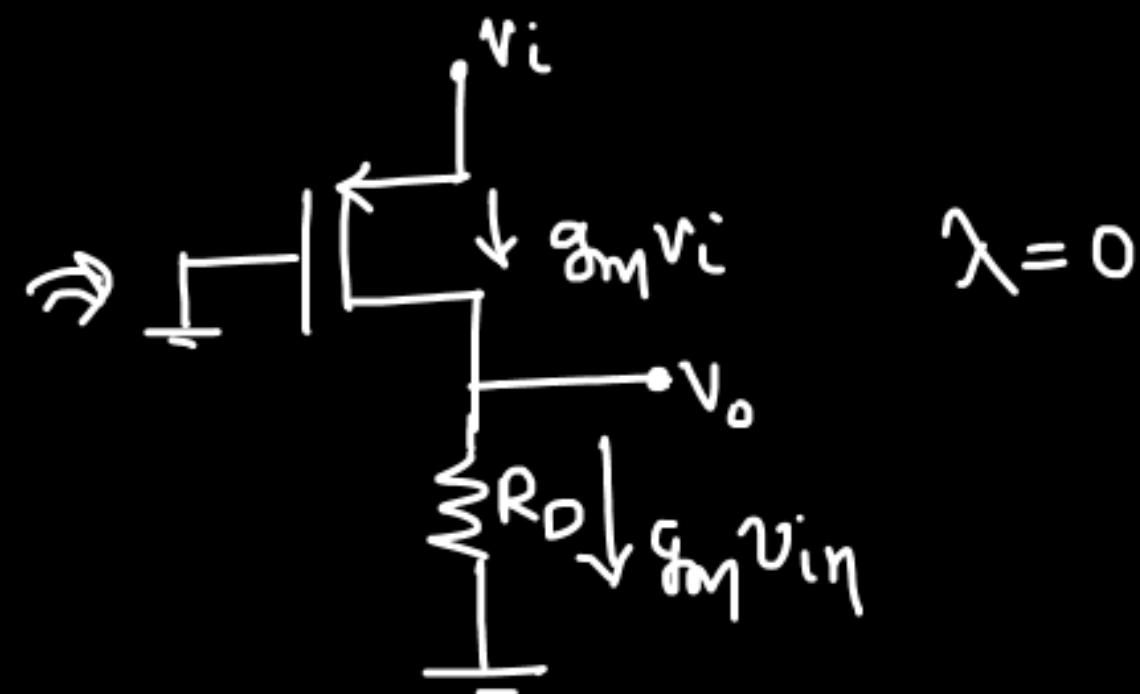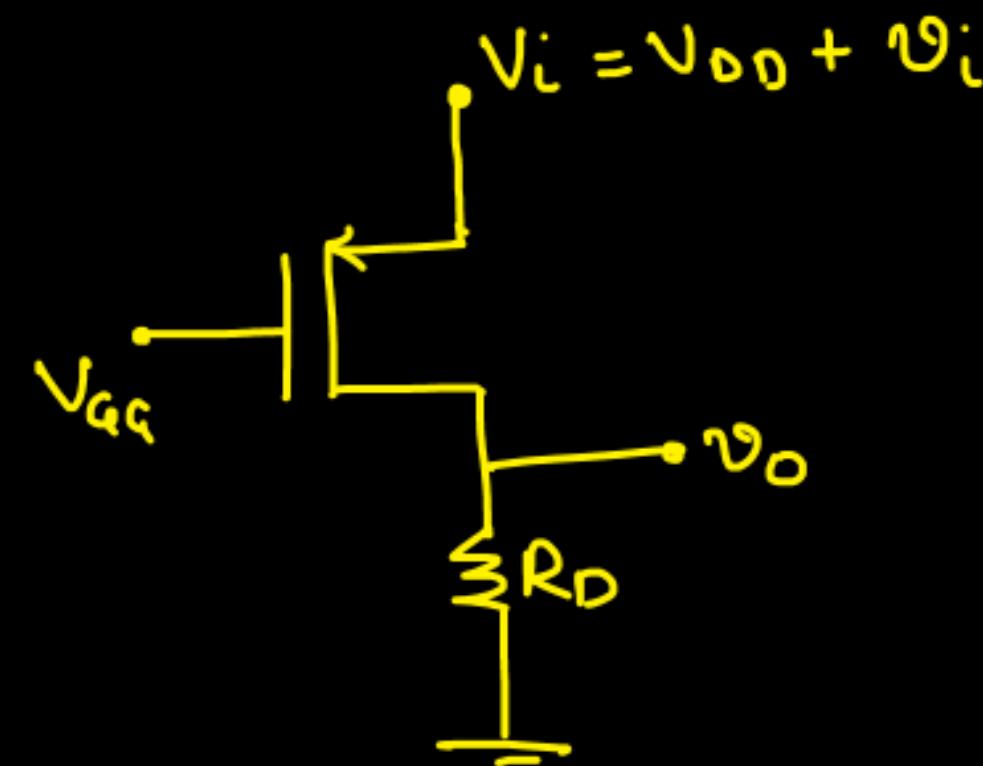


$$\frac{v_o}{v_i} = g_m R_D$$

## Input Impedance :-

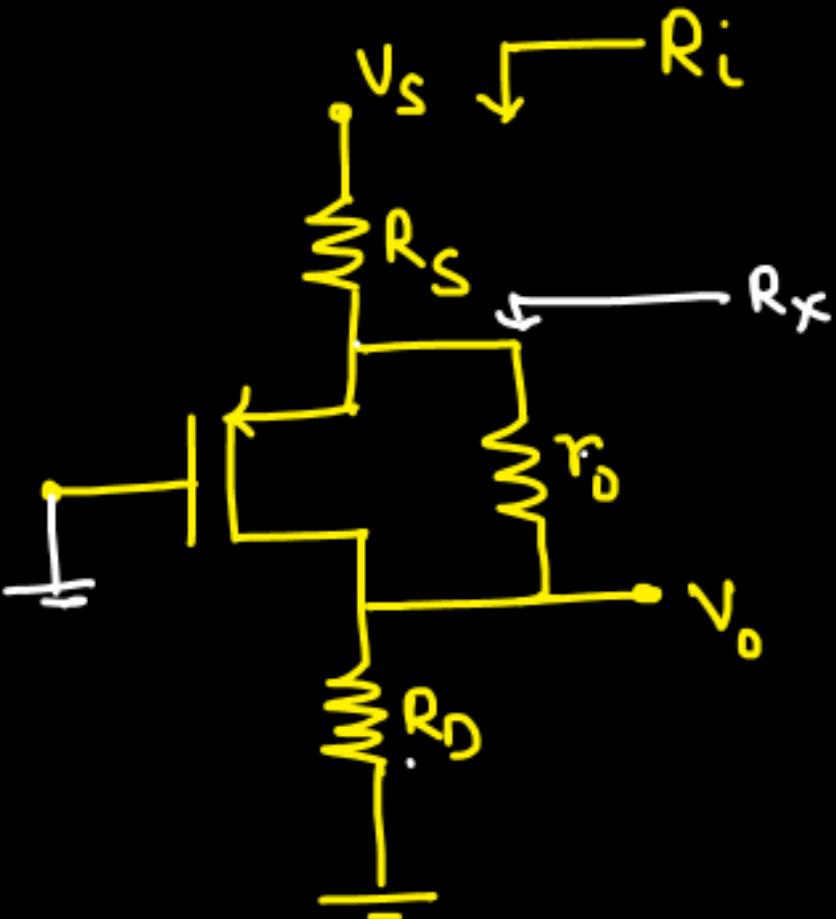

$$R_i = R_s + \frac{R_o + r_o}{1 + g_m r_o}$$


## Output Impedance:-

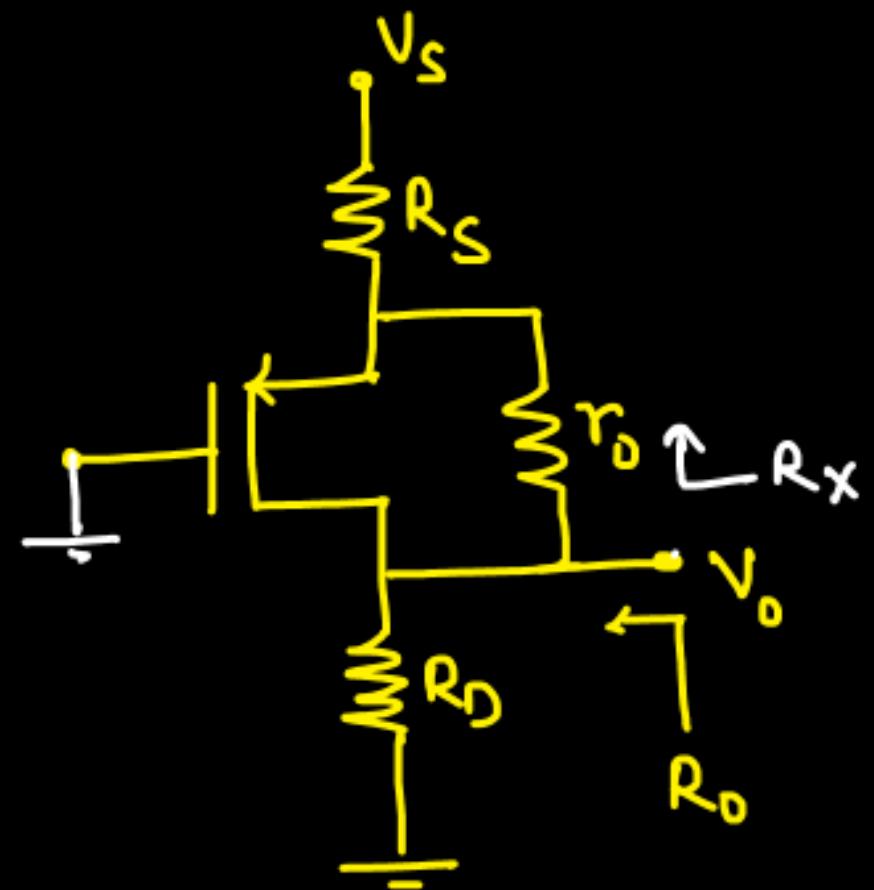

$$R_o = R_D \parallel R_X$$



$$R_o = R_D \parallel r_o + R_S + g_m r_o R_S$$

Current gain:-

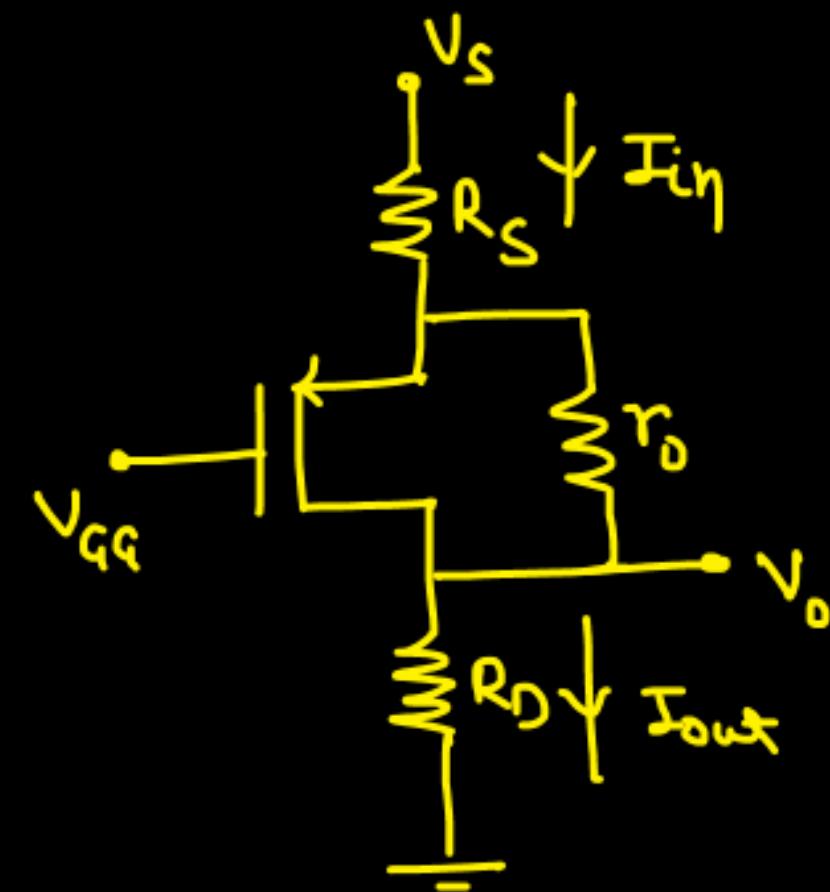

$$\frac{V_o}{I_{in}} = 1$$

### ③ Common-Drain Amplifiers:-

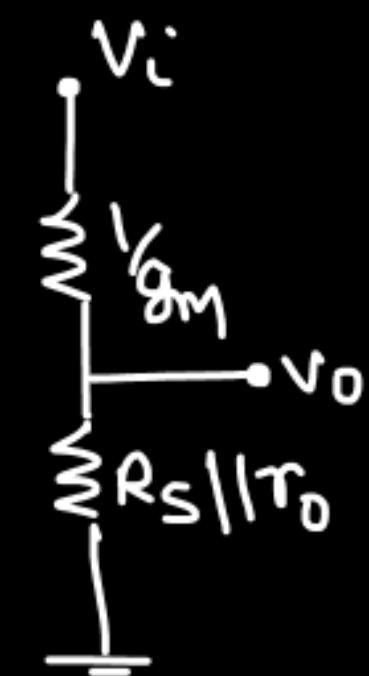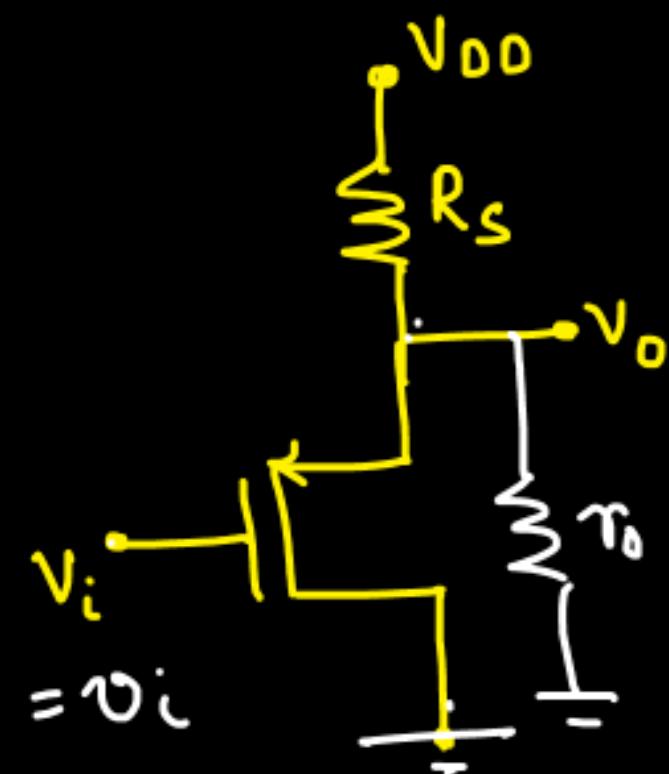

$$\frac{V_o}{V_i} = \frac{R_s}{R_s + 1/g_m}$$


$$\lambda = 0$$

$$\boxed{\frac{V_o}{V_i} = \frac{g_m R_s}{1 + g_m R_s}}$$

$$\lambda \neq 0$$


$$\boxed{\frac{V_o}{V_i} = \frac{g_m (R_s || r_o)}{1 + g_m (R_s || r_o)}}$$

## Output Impedance :-

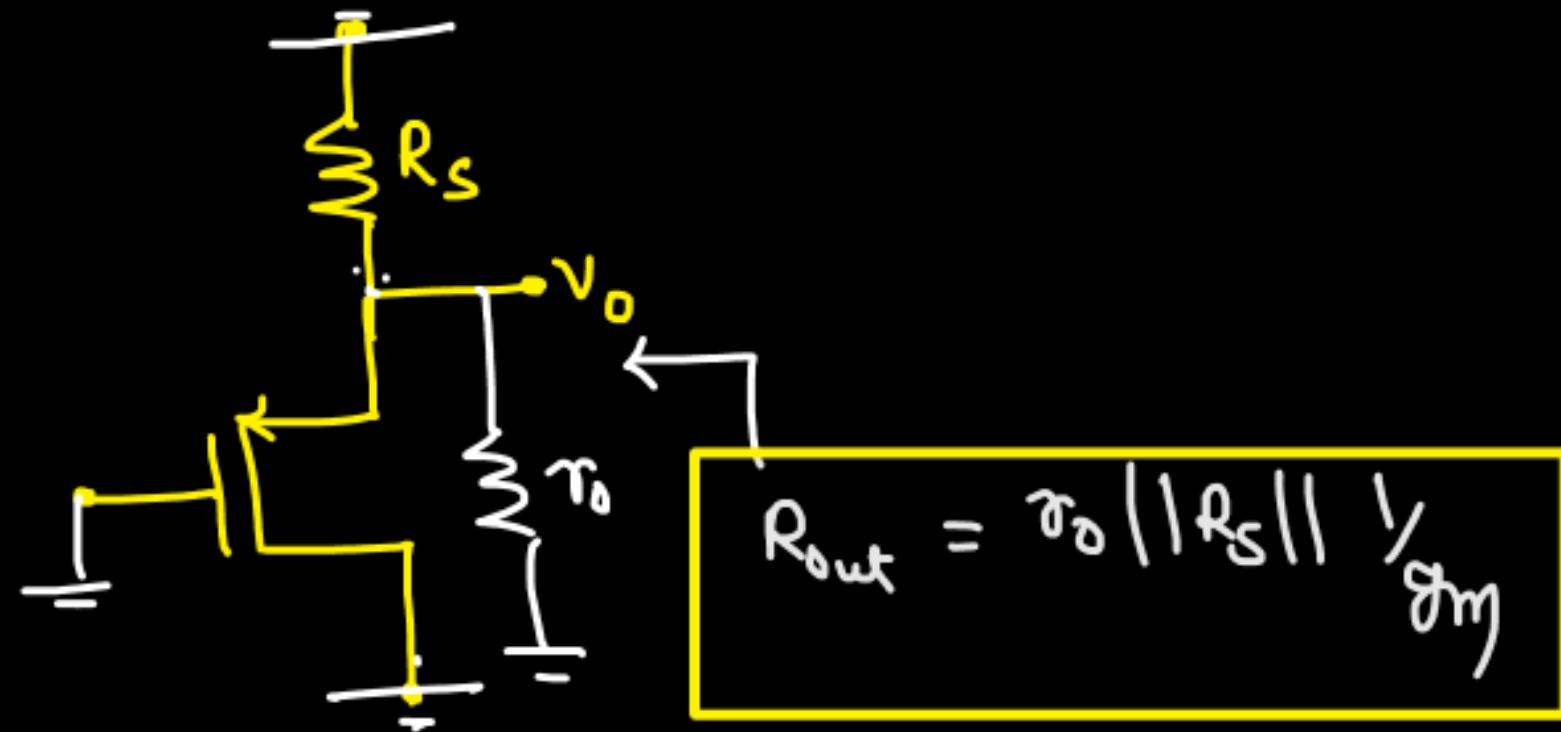

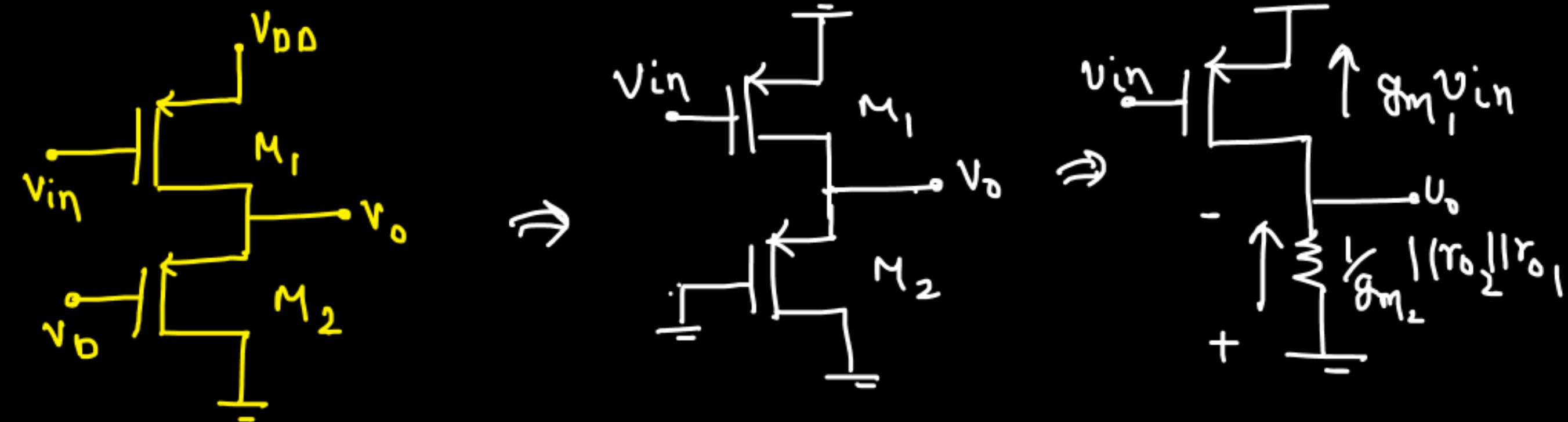
## Assignment - 7

Q. Find small signal voltage gain.  
 $(\lambda \neq 0)$




$$\frac{v_o}{v_i} = -g_{m1} \left[ \frac{1}{g_{m2}} || r_o_2 || r_o_1 \right]$$

Q.

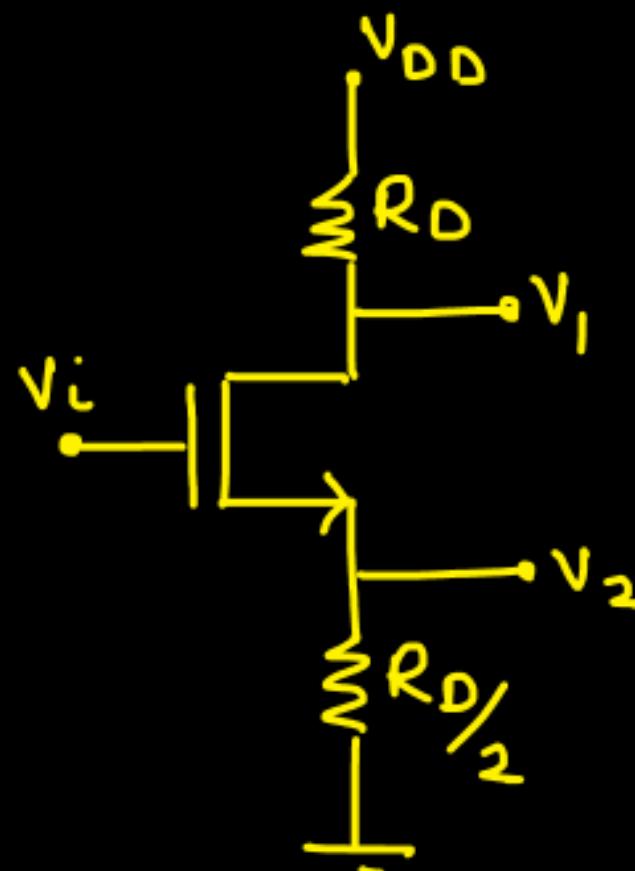

Find  $\frac{v_1}{v_2} = ?$  [small signal]  
( $\lambda \neq 0$ )

$\Rightarrow$

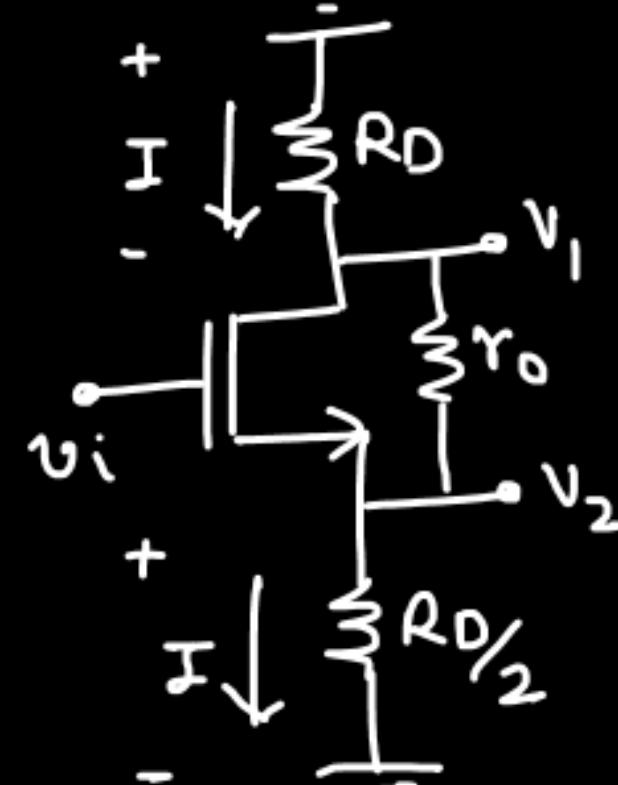


$$v_1 = -IR_D$$

$$v_2 = -I R_D/2$$

$$\boxed{\frac{v_1}{v_2} = 2}$$

Q.

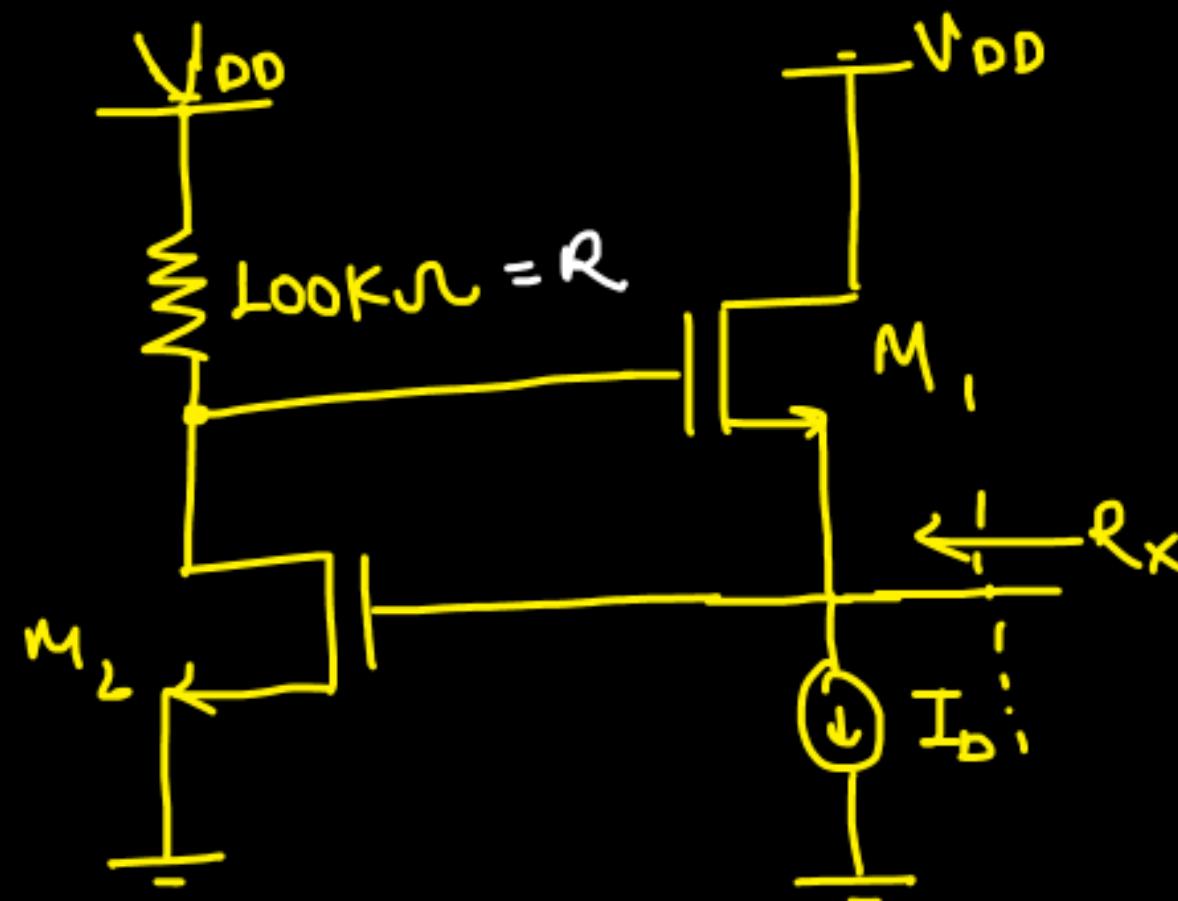

$$g_m = g_{m1} = g_{m2} = 100 \mu\text{s}$$


Determine small signal  $R_x = ?$

$$R = 100 \text{ k}\Omega$$

$$I_x = g_m(v_x - v) \rightarrow ①$$

$$v = -g_m v_x R \rightarrow ②$$

$$I_x = g_m (v_x + g_m v_R R)$$

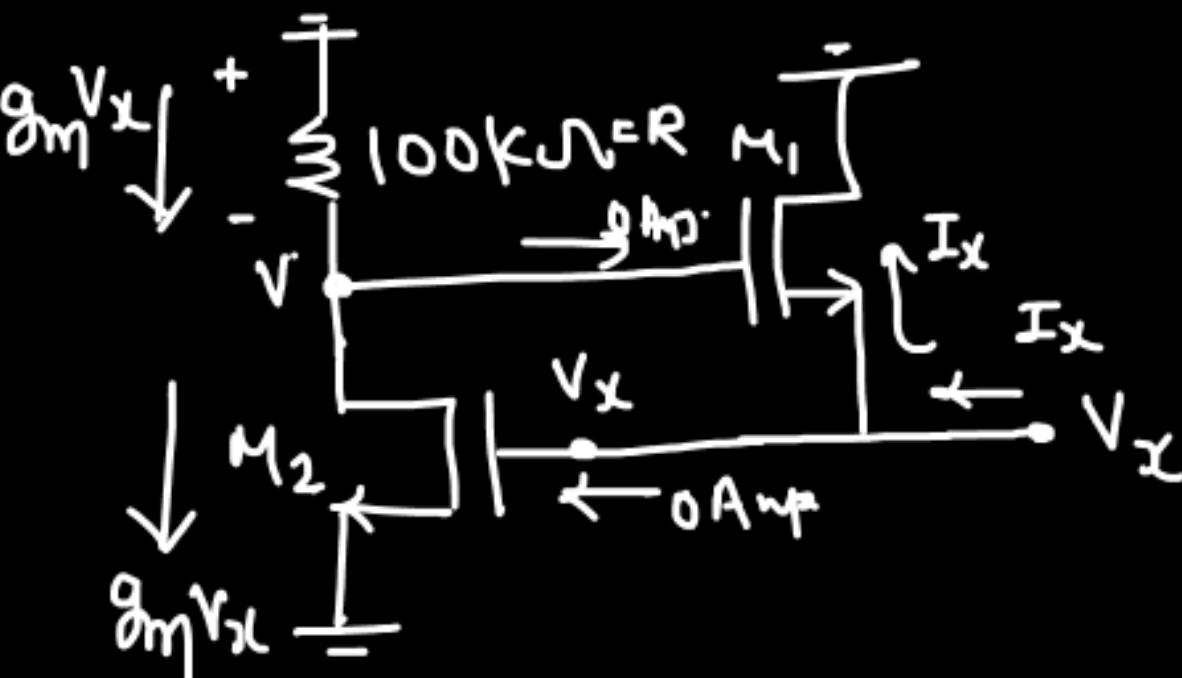

$$R_x = \frac{v_x}{I_x}$$


$$I_x = g_m [1 + g_m R] V_x$$

$$R_x = \frac{V_x}{I_x} = \frac{1}{g_m [1 + g_m R]} \\ = \frac{1}{10^{-4} [1 + 10^{-4} \times 10^5]}$$

$$R_x = \frac{1}{11} \times 10^4$$


\* Rx = 909.09 \Omega

Q.

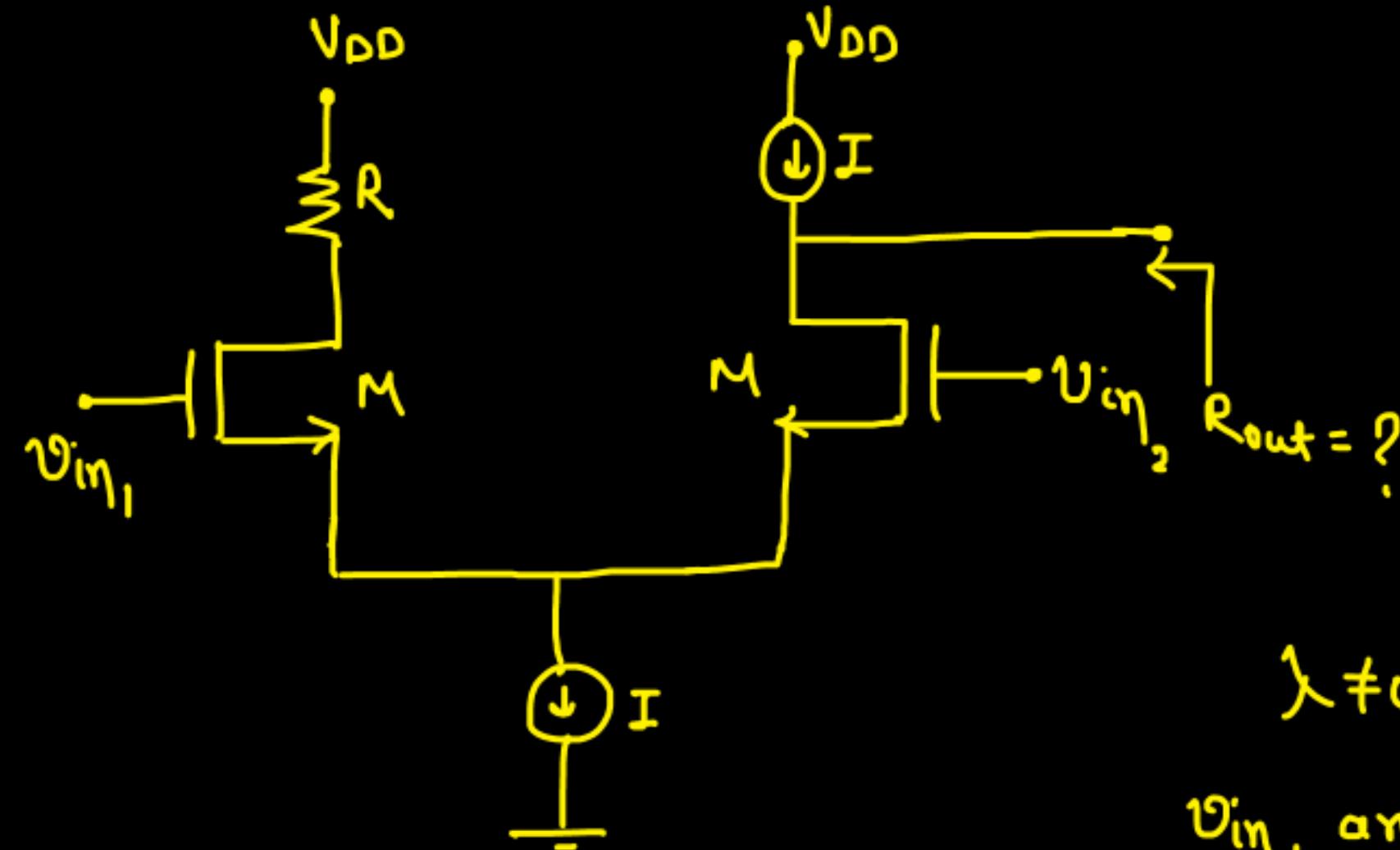


$$\lambda \neq 0$$

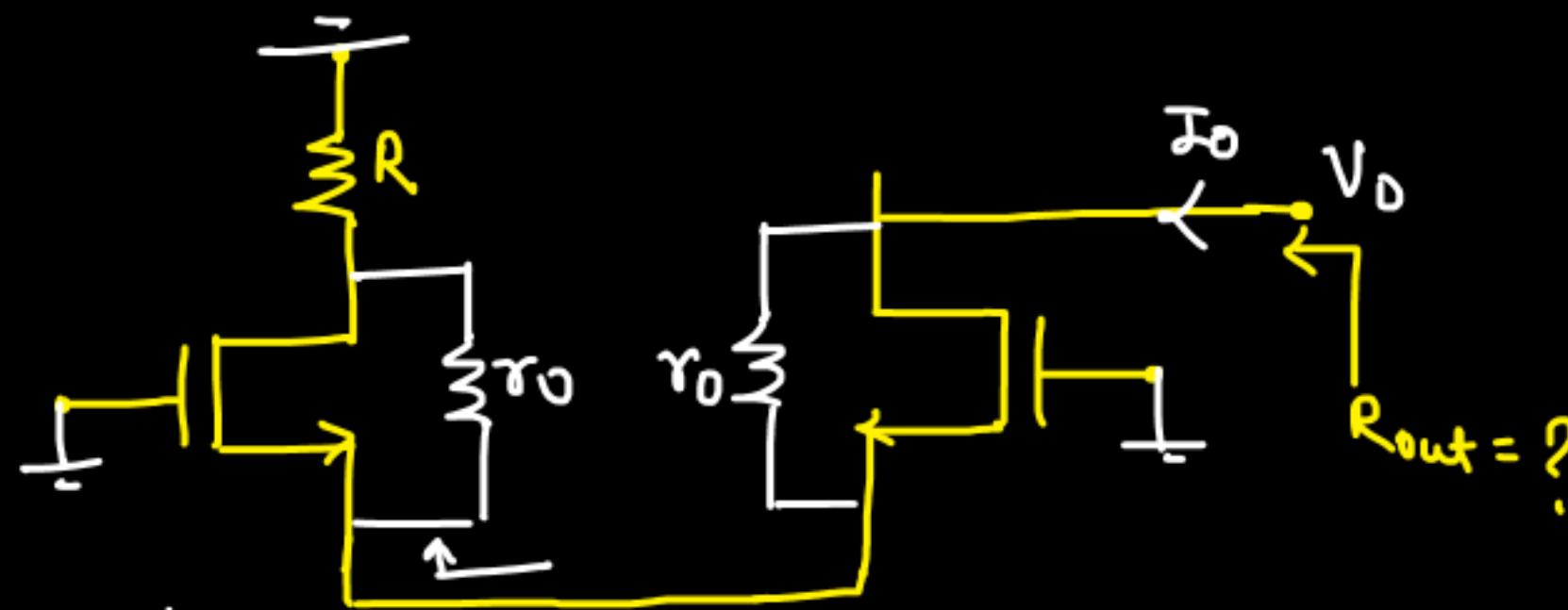$v_{in_1}$  and  $v_{in_2}$  are small signal if p.  
find small signal  $R_{out} = ?$



$$R_{out} = \frac{V_O}{I_0}$$

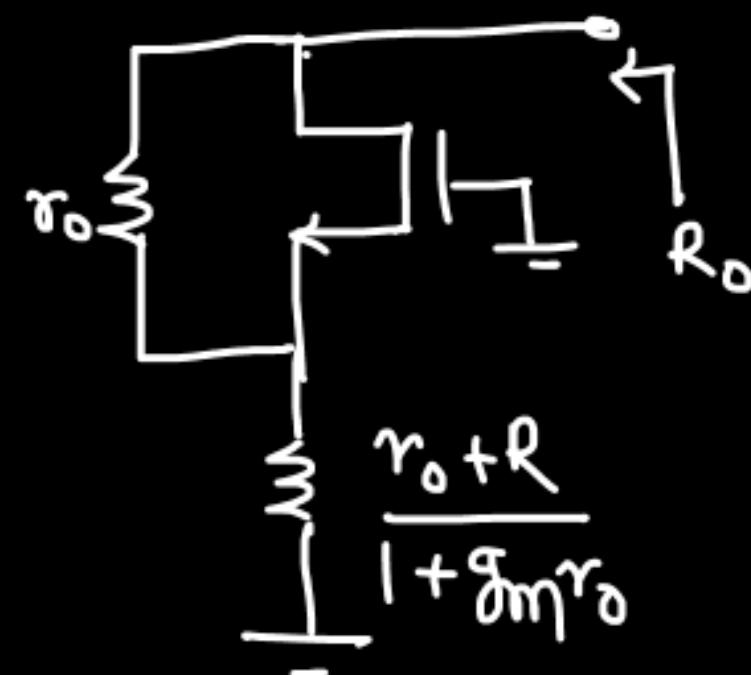



$$R_o = r_o + \frac{r_o + R}{1 + g_m r_o} + g_m r_o \left[ \frac{r_o + R}{1 + g_m r_o} \right]$$

$$= r_o + \left( \frac{r_o + R}{1 + g_m r_o} \right) [1 + g_m r_o]$$


\*   $R_{out} = 2r_o + R$

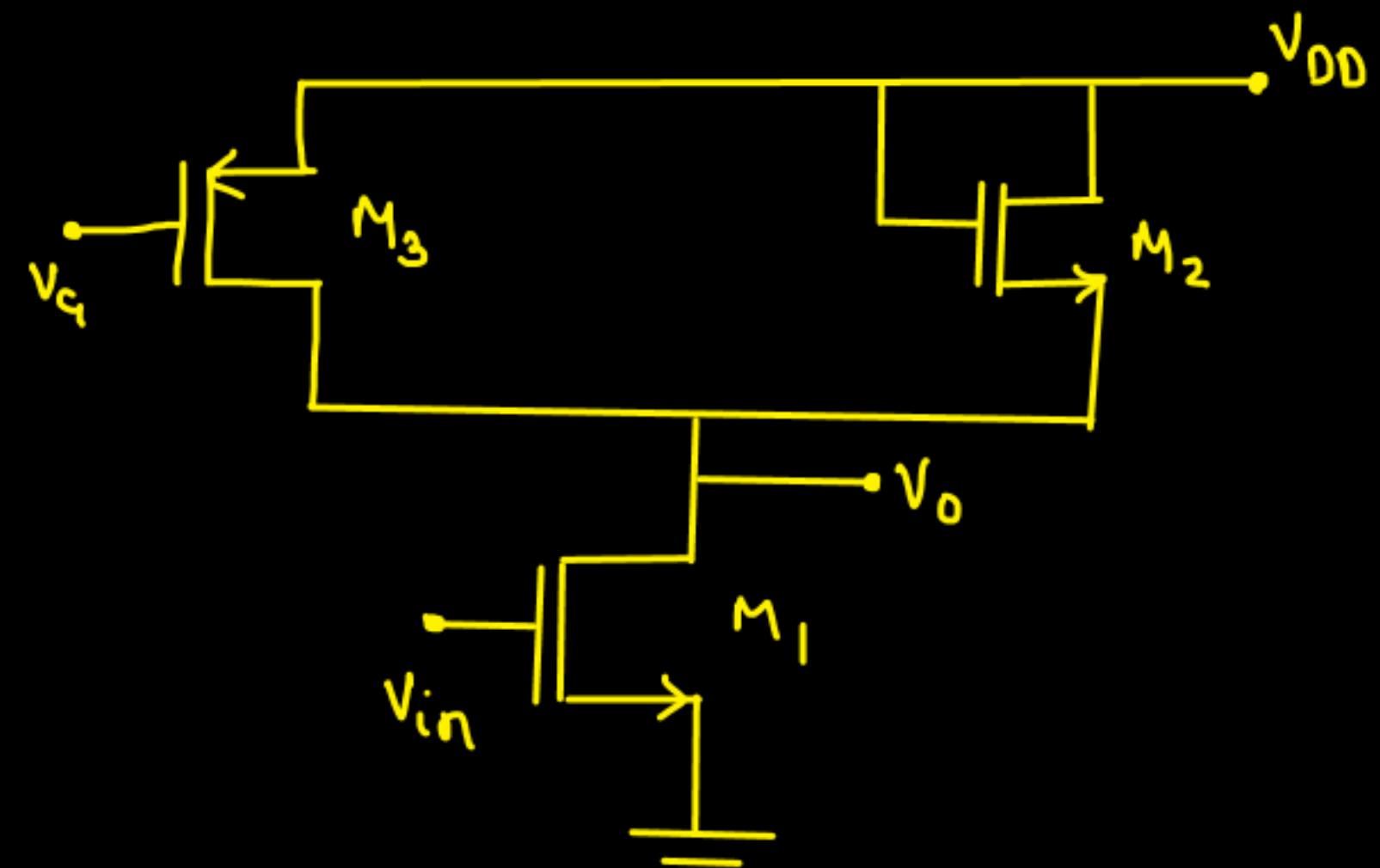Q. find small signal voltage gain. ( $\lambda \neq 0$ )



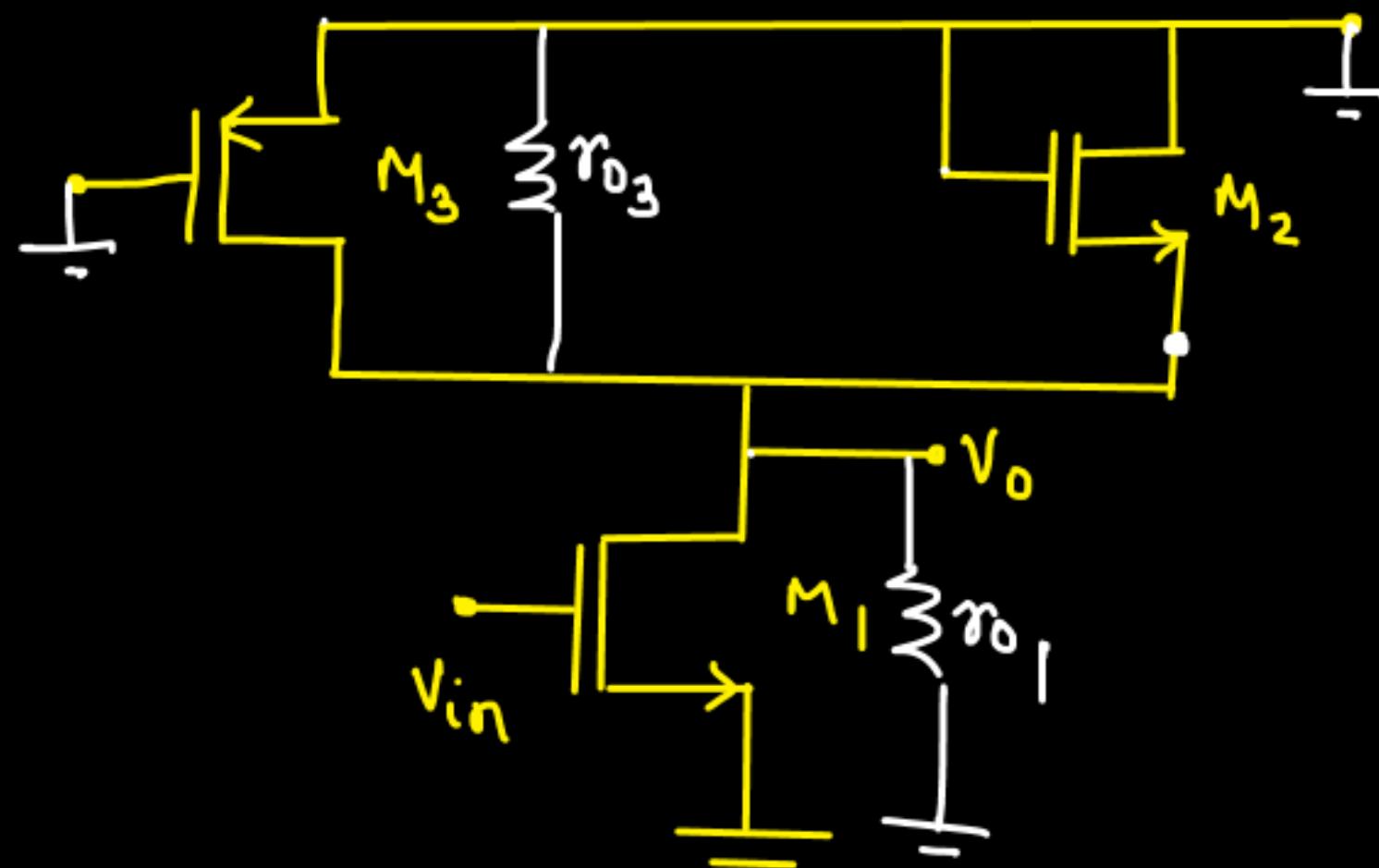


Δ\*

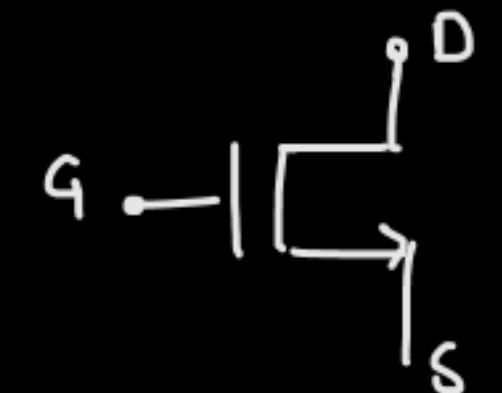

$$S \rightarrow Q \Rightarrow 1/g_m$$


$$S \rightarrow D \rightarrow r_o$$

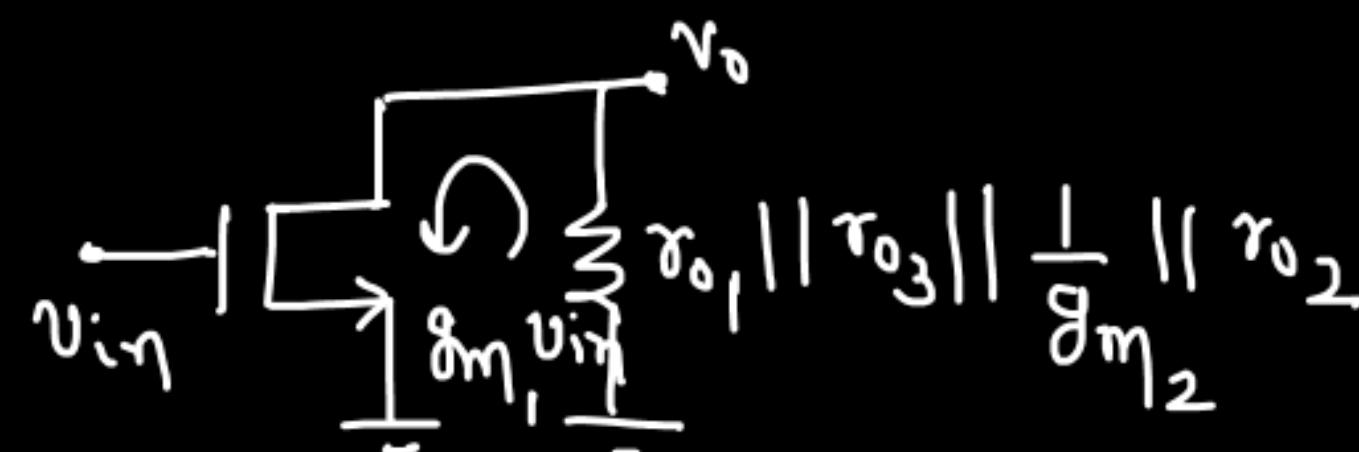

\*\*

$$\frac{v_o}{v_i} = -g_{m1} \left[ \frac{1}{g_{m2}} || r_{o2} || (r_{o1} || r_{o3}) \right]$$

Q.

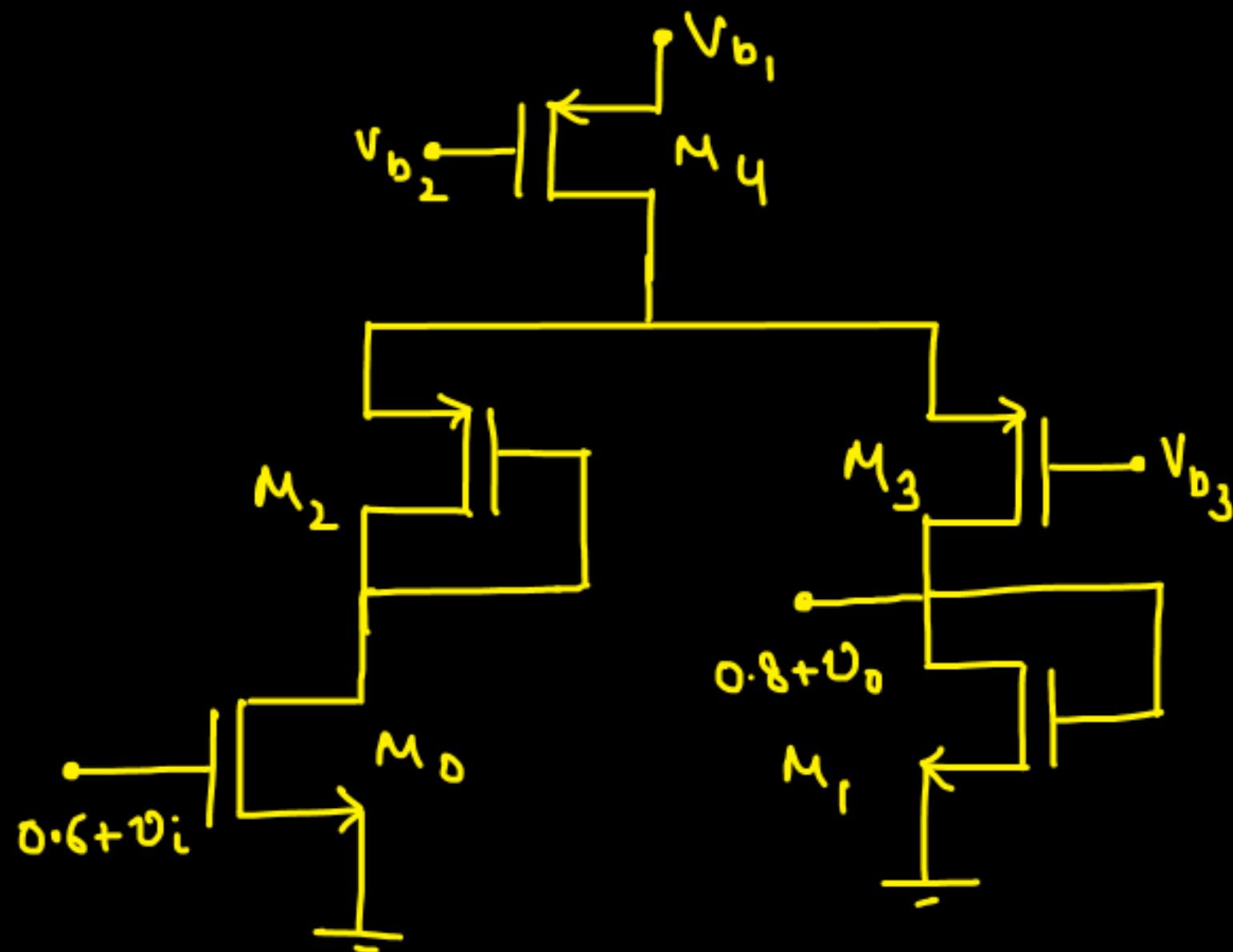


$$\lambda = 0$$

$$g_m = \frac{2I_{DC}}{V_{GS} - V_T}$$

Transistors are biased such that all Transistors are working in sat. region.  
 $M_0 - M_3$  are biased with  $\underline{5mA}$  current.  $V_T$  value for all the transistors is  $0.4V$ .

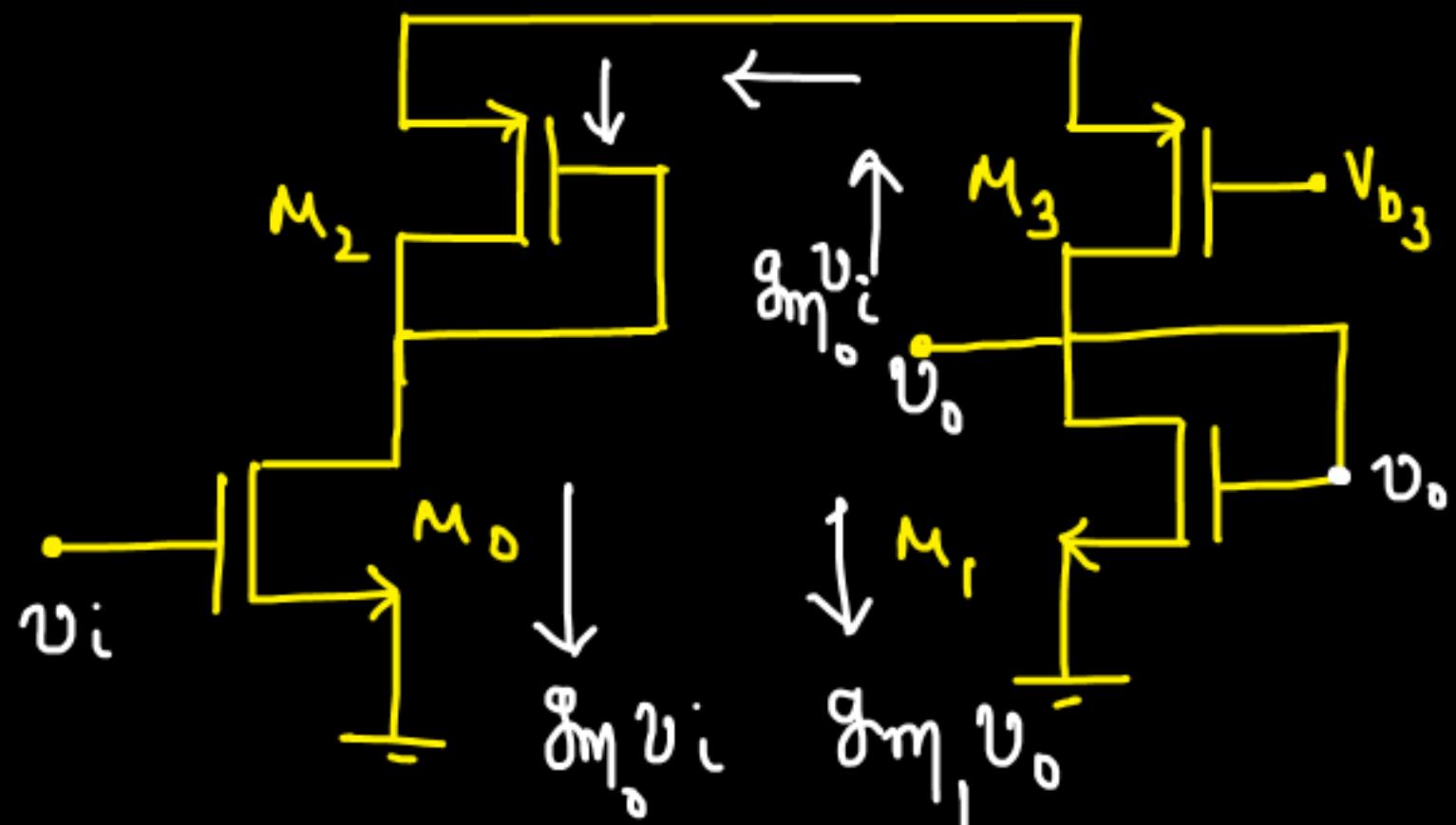find small signal voltage gain  $v_o/v_i$  ?



$$\partial m_0 v_i = - \partial m_1 v_o$$

$$\frac{v_o}{v_i} = - \frac{\partial m_0}{\partial m_1}$$


$$\begin{aligned} \partial m_0 &= (2 I_{DQ})_{M_0} \\ &= \frac{2 \times 5 \text{mA}}{0.6 - 0.4} = 50 \text{mS} \end{aligned}$$

$$\partial m_1 = \frac{2 \times 5 \text{mA}}{0.8 - 0.4} = 25 \text{mS}$$

★ ★


$$\frac{v_o}{v_i} = - \frac{50 \text{mS}}{25 \text{mS}} = -2 \text{V/V}$$

Q. Find small signal voltage gain.

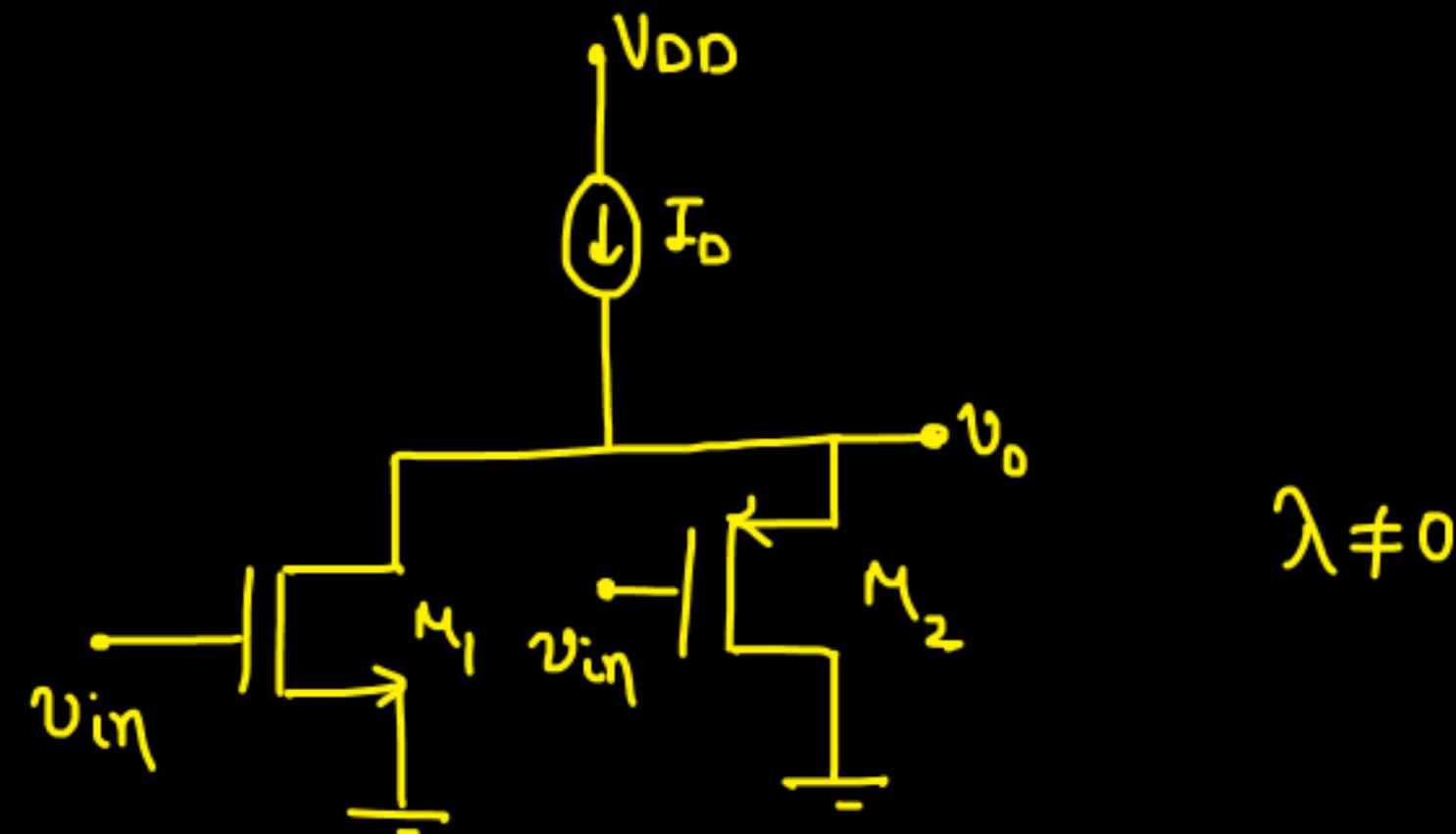

$$\lambda \neq 0$$
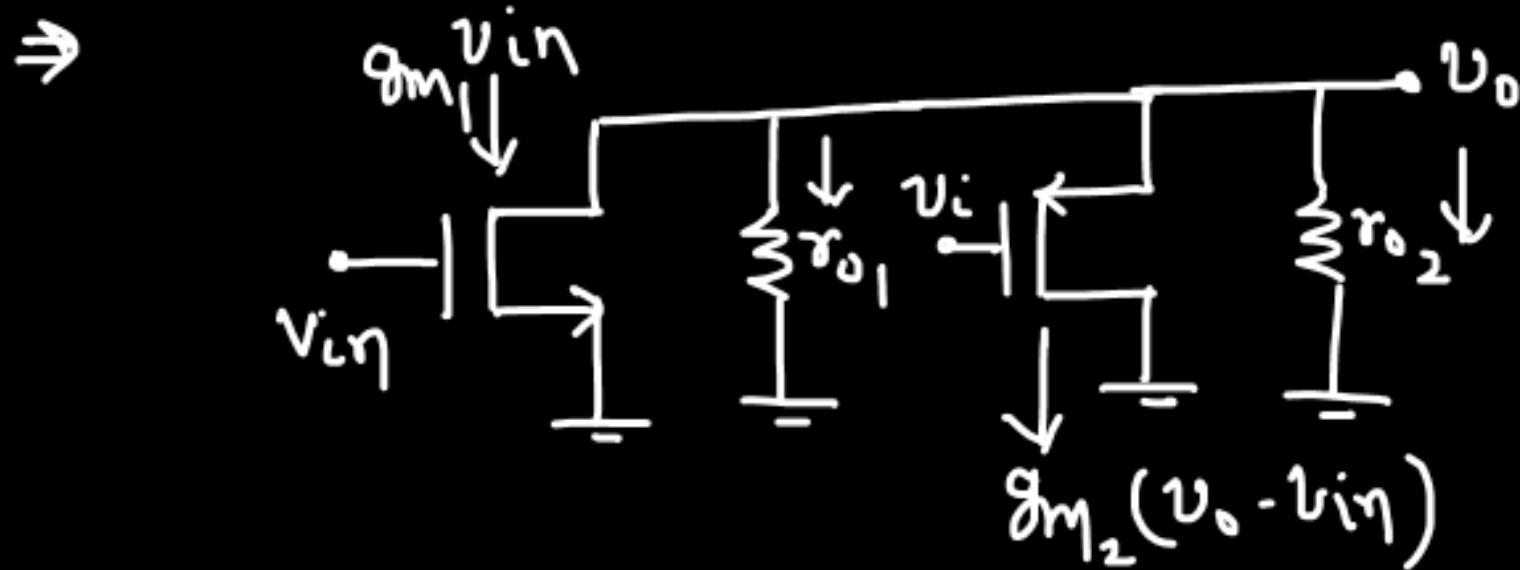
$$g_m1 v_{in} + \frac{v_o}{r_o1} + g_m2 (v_o - v_{in}) + \frac{v_o}{r_o2} = 0$$




$$\frac{v_o}{r_o1} + g_m2 v_o + \frac{v_o}{r_o2} = (g_m2 - g_m1) v_{in}$$

$$\frac{V_o}{r_{o_1} || r_{o_2} || \frac{1}{g_m_2}} = (g_m_2 - g_m_1) v_{in}$$

$$\boxed{\frac{V_o}{v_{in}} = (g_m_2 - g_m_1) \left( r_{o_1} || r_{o_2} || \frac{1}{g_m_2} \right)}$$

M-II  $\frac{G_m}{R_{out}}$  Mtd:-


$G_m \rightarrow$

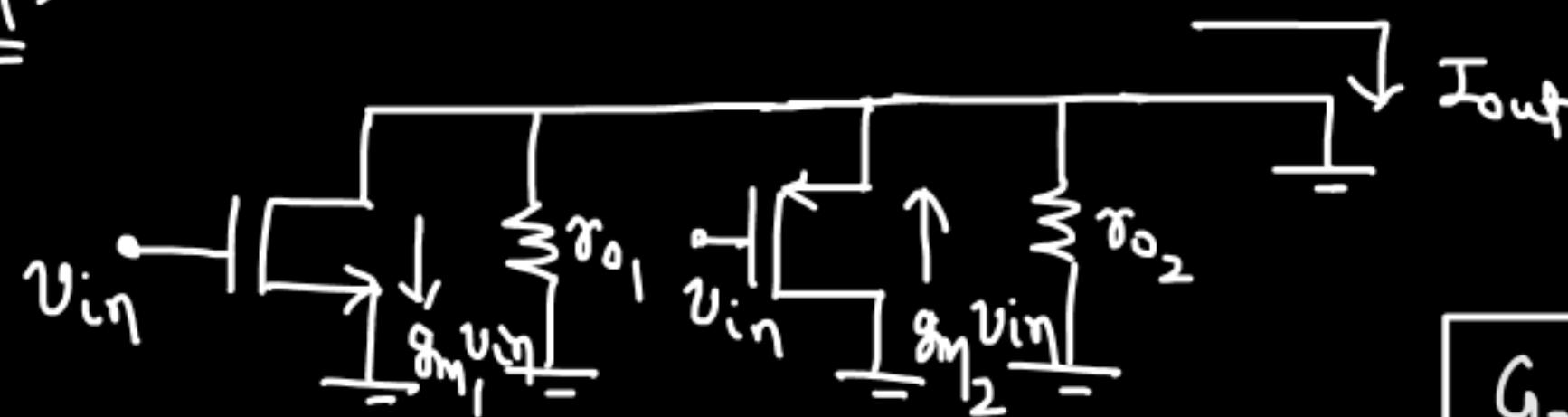

$$g_m_1 v_{in} + I_{out} = g_m_2 v_{in}$$

$$G_m = \frac{I_{out}}{v_{in}} = g_m_2 - g_m_1$$

$R_{out}$  →

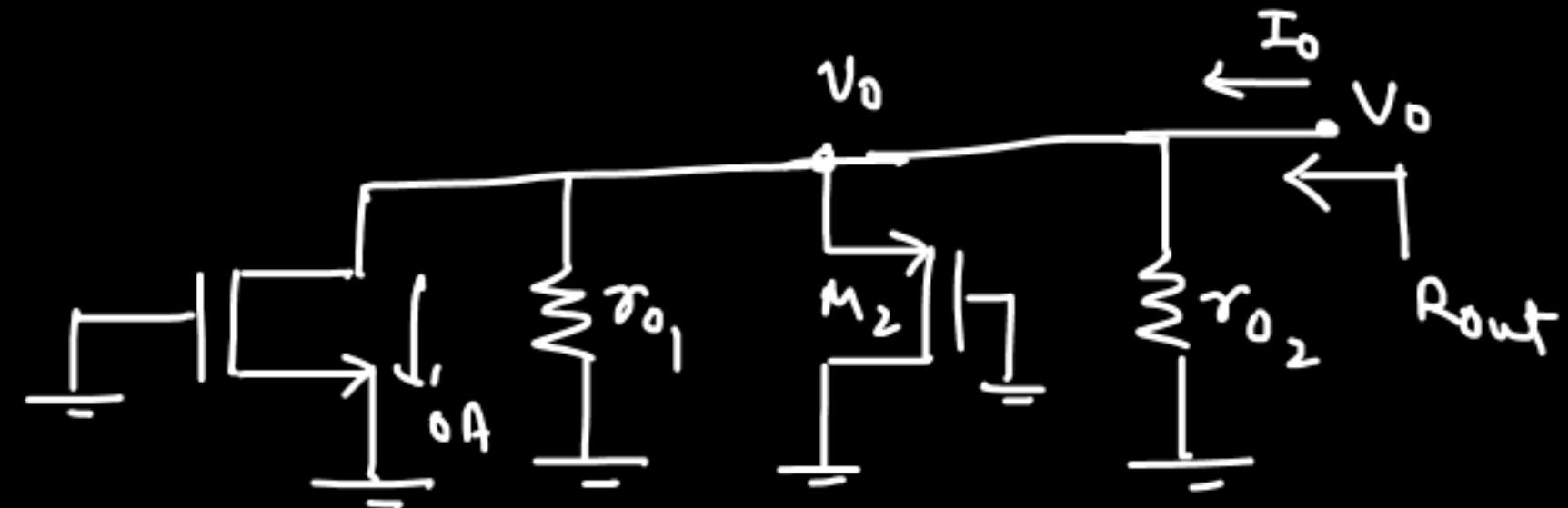


~~for~~

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m^2}$$


~~for~~

$$\Delta V = (g_m - g_m) \left( r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m^2} \right)$$

Q.

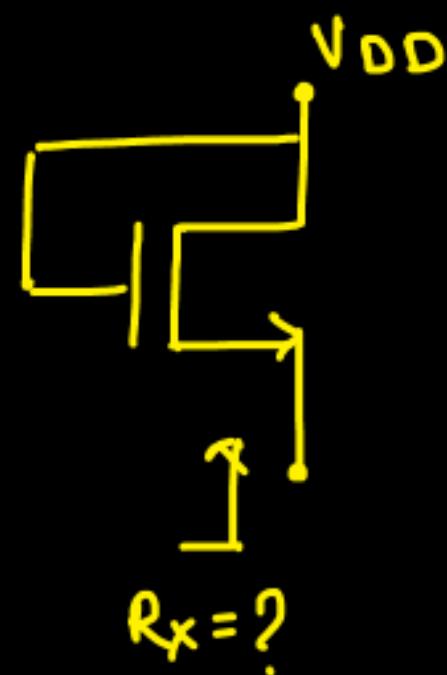






$\Rightarrow$

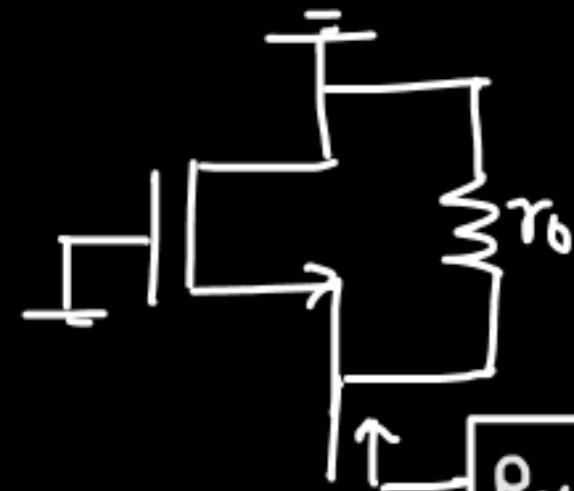


$$R_x = \frac{1}{g_m} || r_o$$

Q.

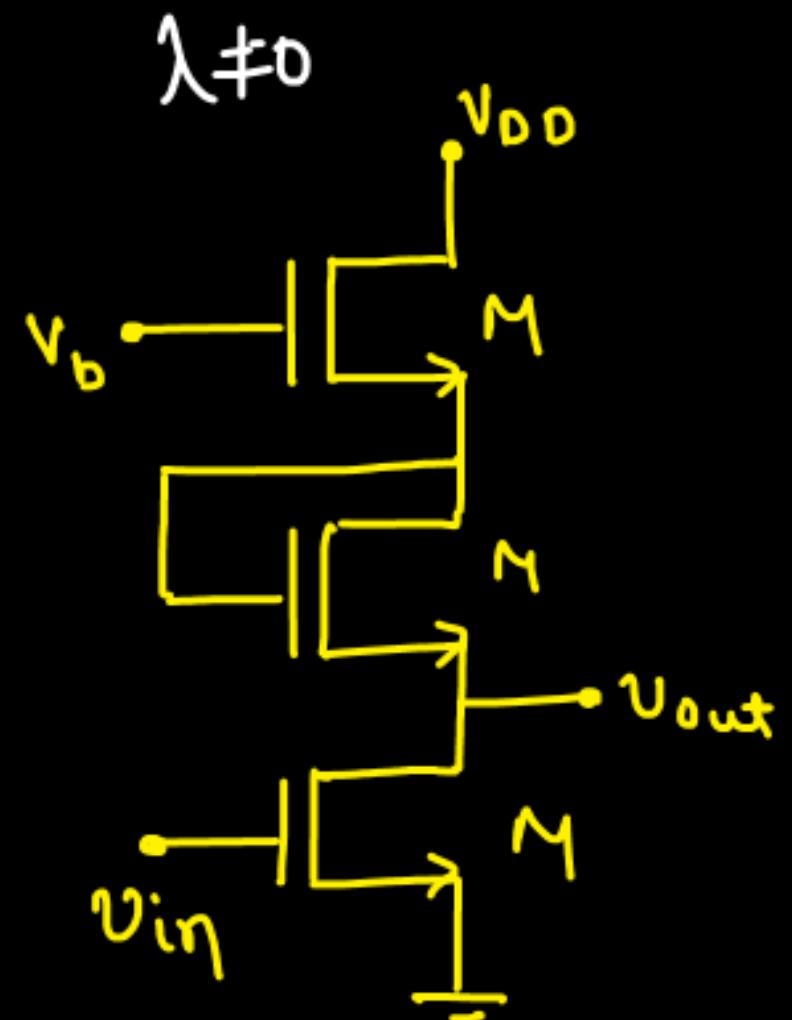


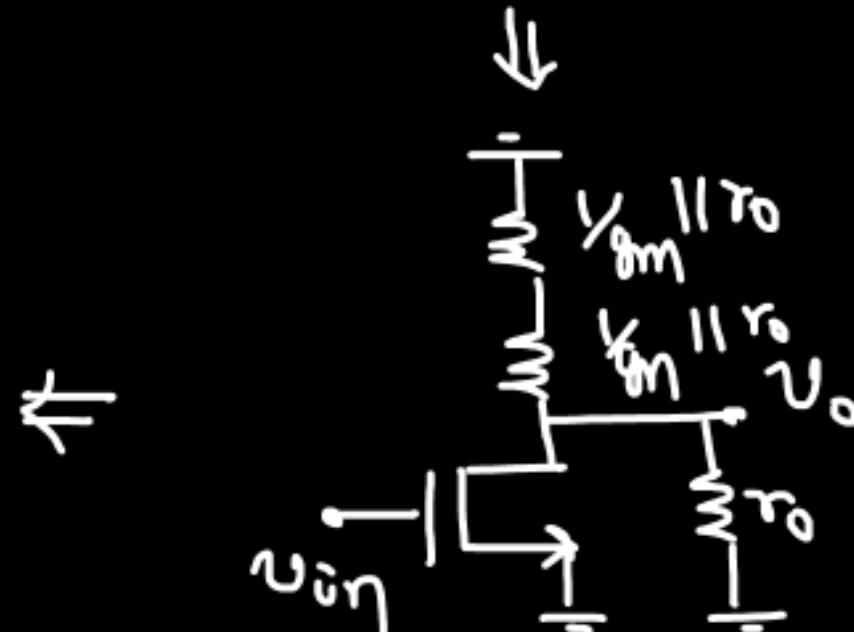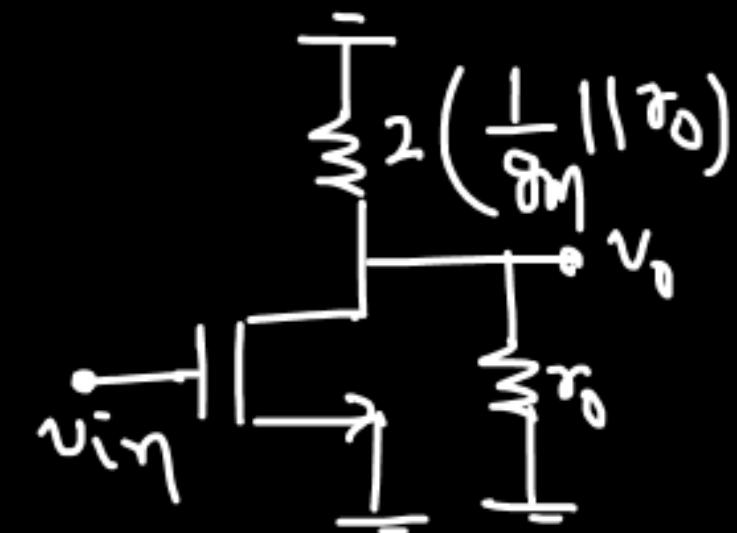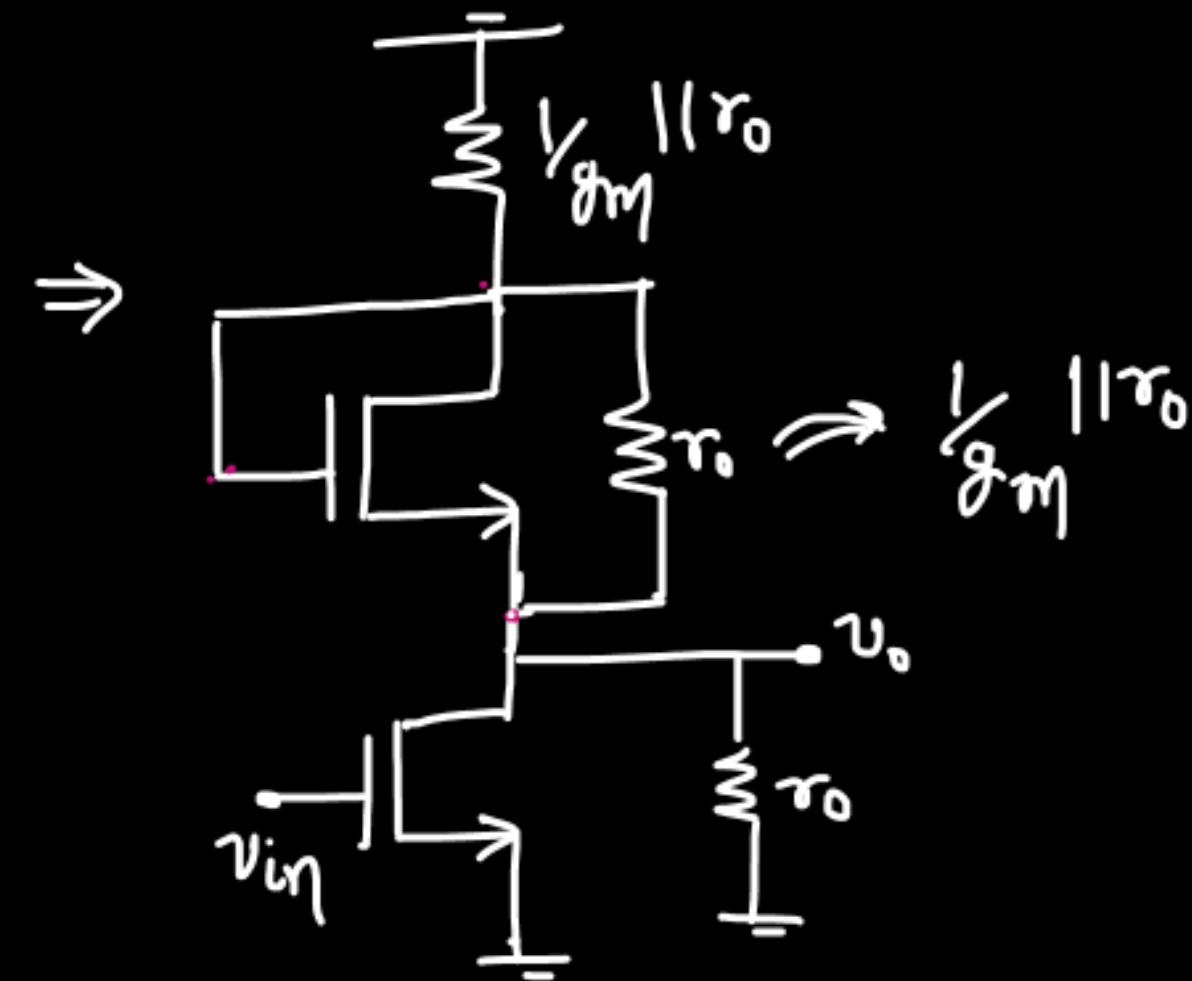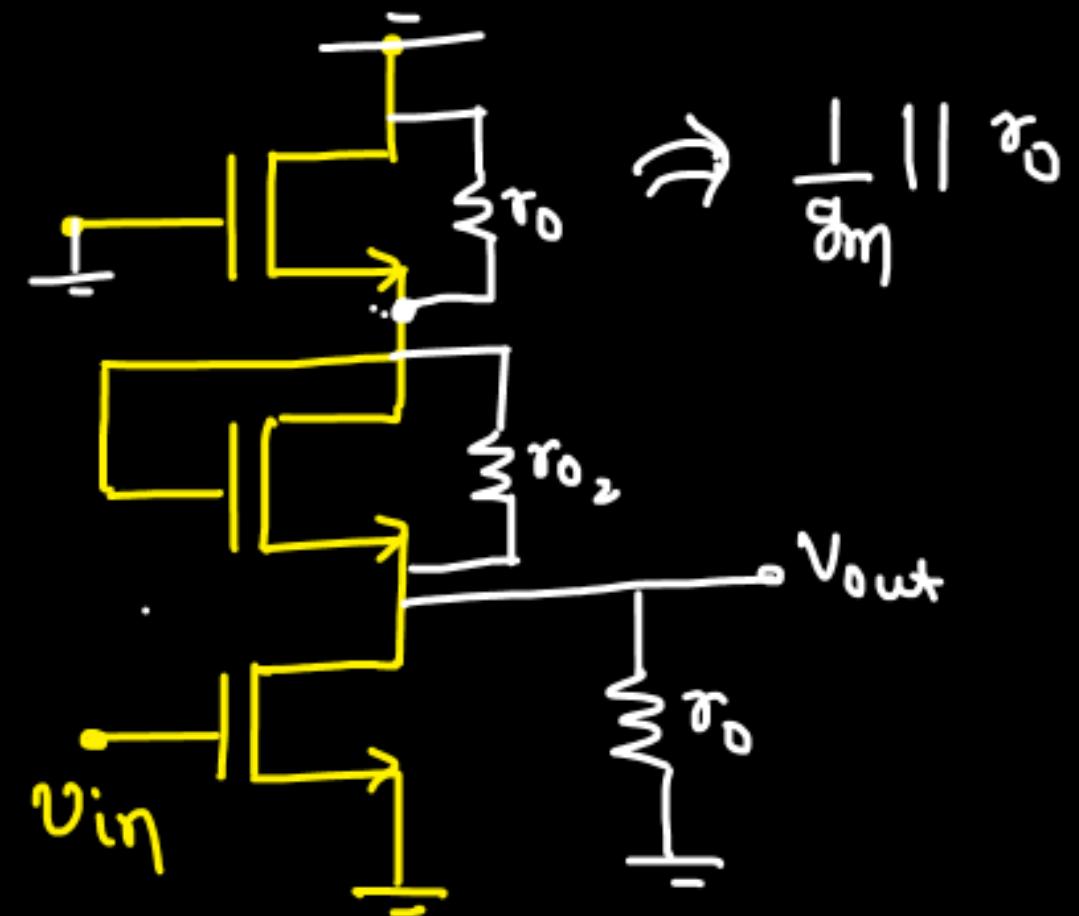

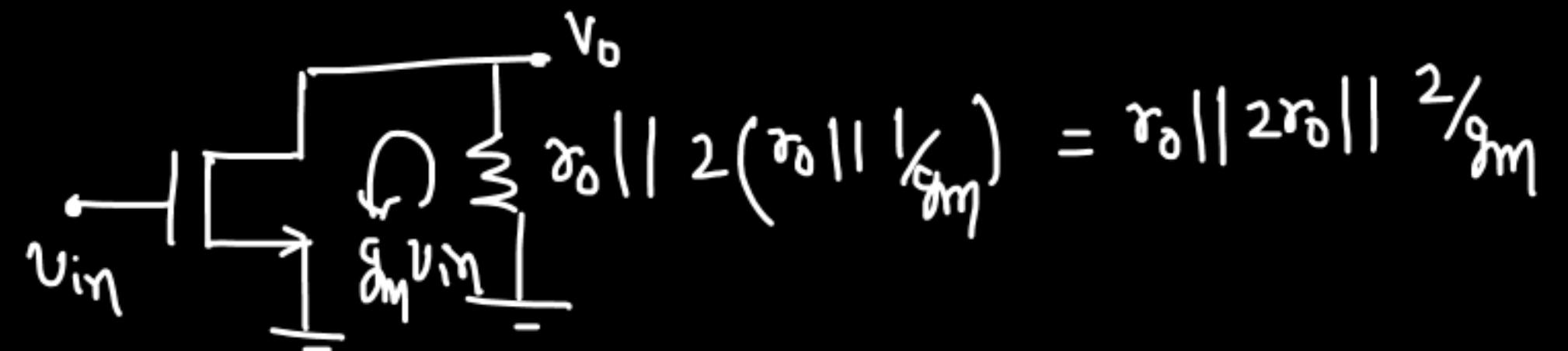

\*  $\frac{V_o}{V_{in}} = -g_m \left[ \frac{2}{g_m} \parallel \frac{2r_0}{3} \right]$

⇒ Current Source:-

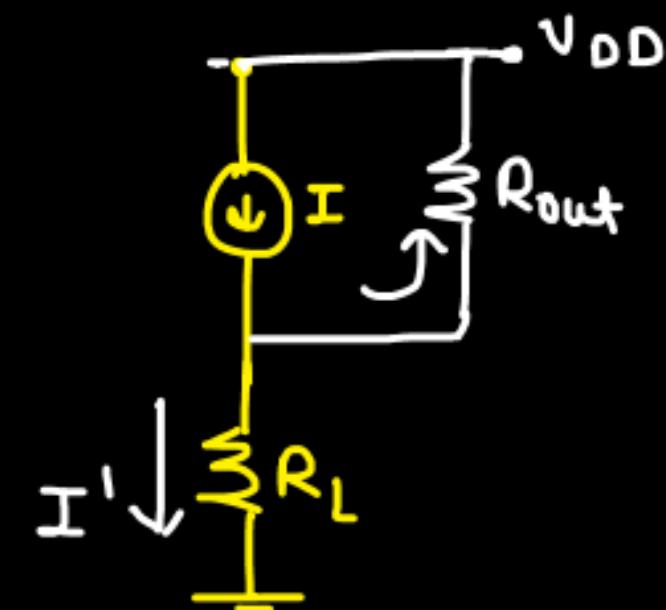


$$I' < I$$

if  $R_{out} \rightarrow \infty$

$$I' \rightarrow I$$

more  $R_{out} \Rightarrow$  better current source

## Making current source from MOS:-

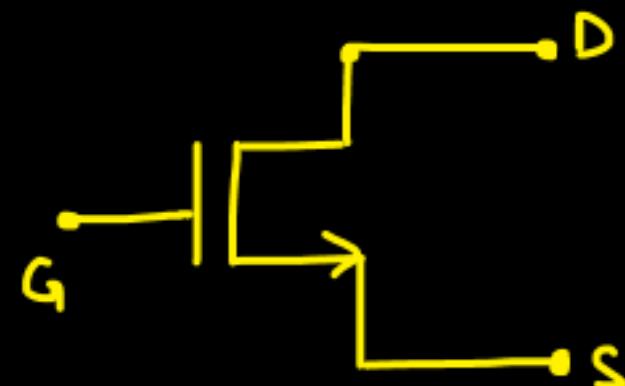


$$r_{o1} > r_{o2} > r_{o3}$$





↓

Bent current source

$M_1 \rightarrow$  Bent current source

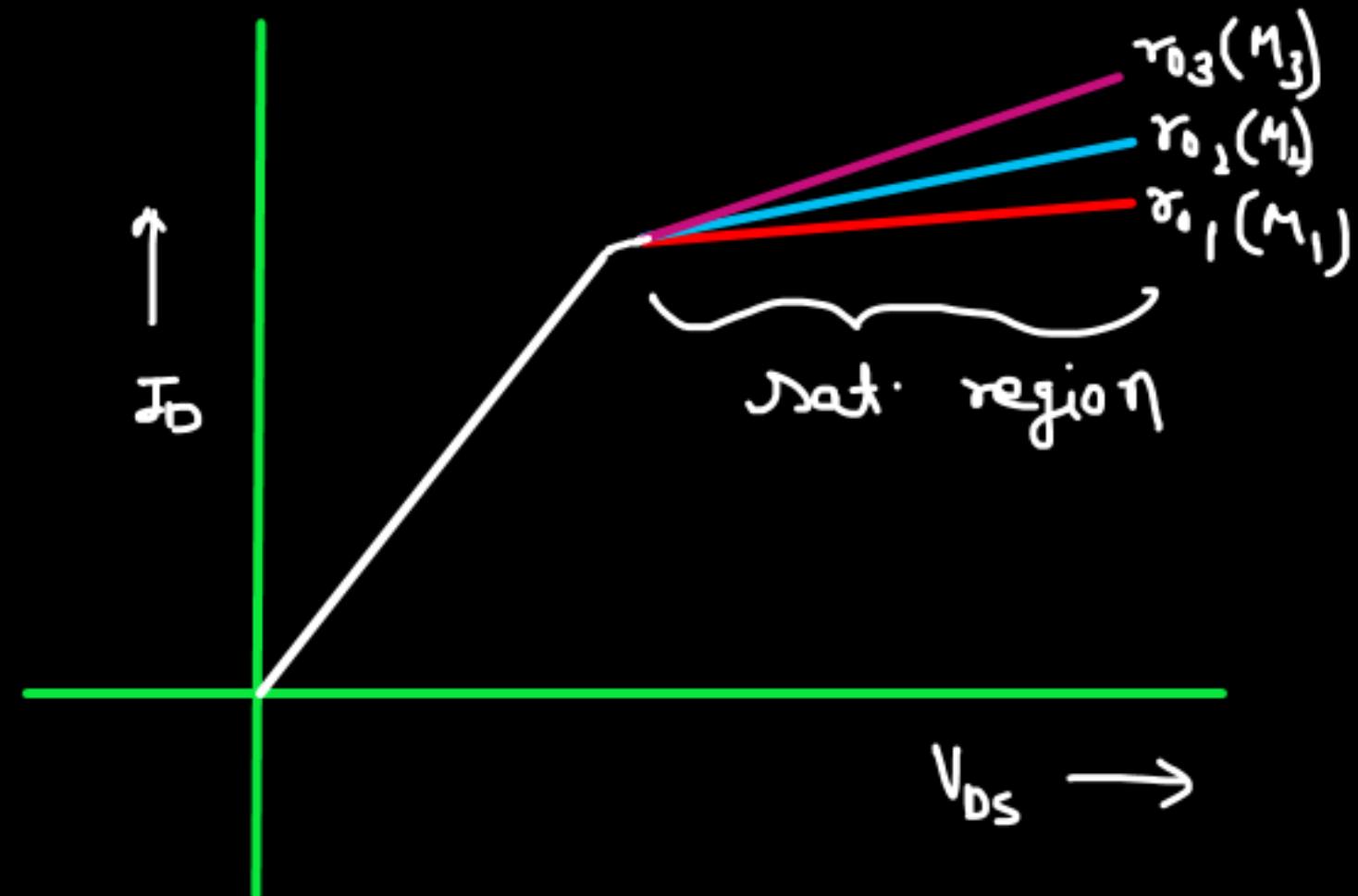

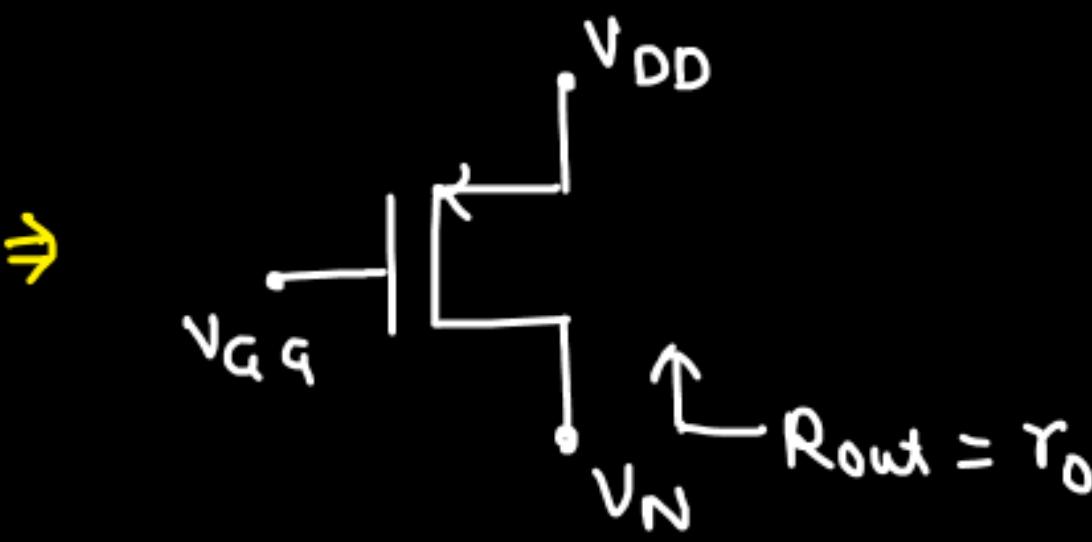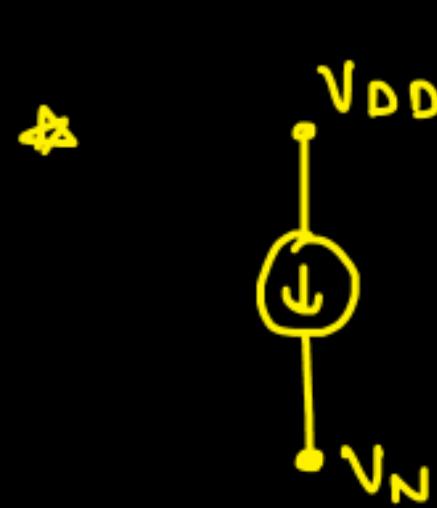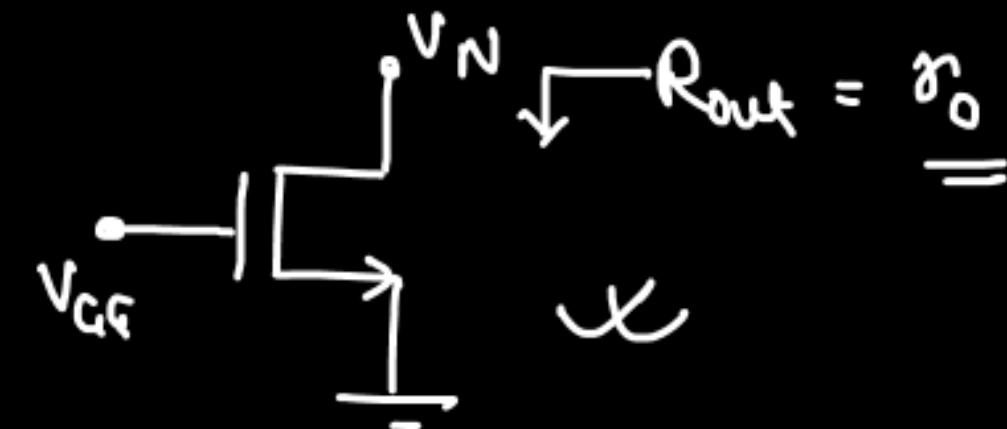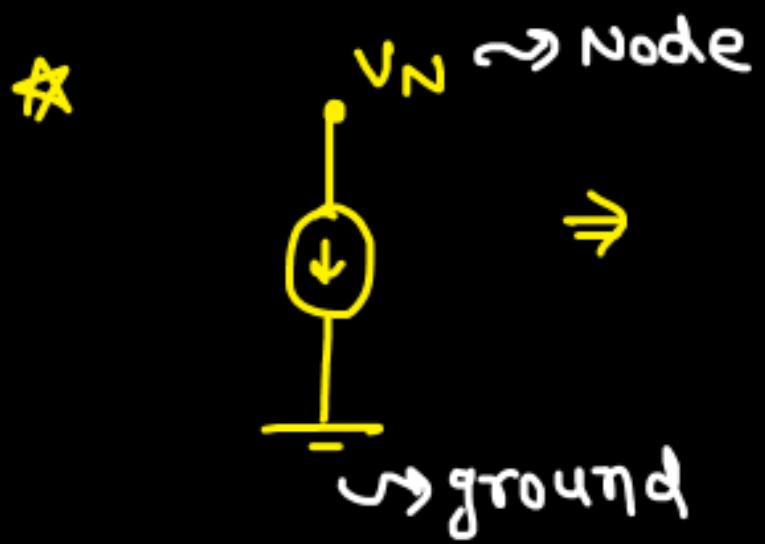
For using MOS as a current source,  
it should be biased in sat. region.




Node to ground  $\rightarrow$  NMOS  
 Supply to Node  $\rightarrow$  PMOS

$\Rightarrow$  What if I need a Higher o/p impedance?


★

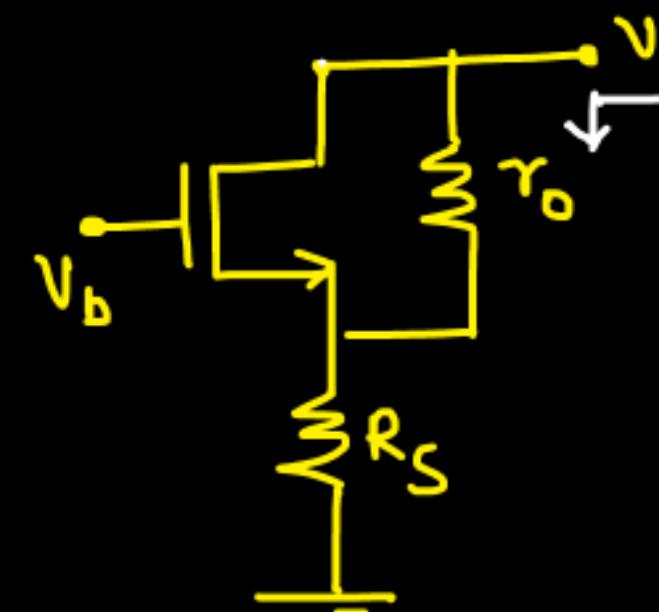

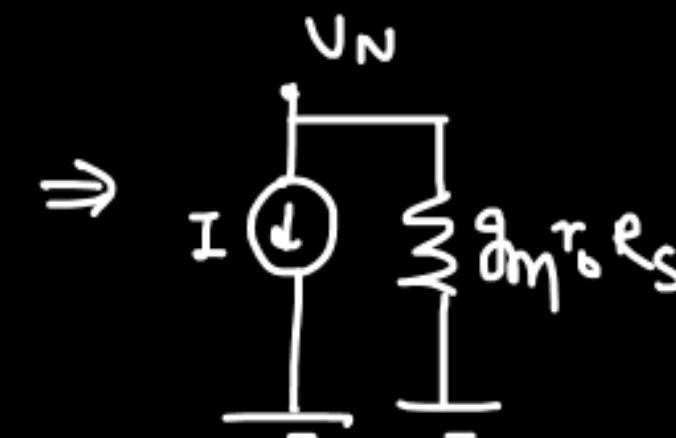
$$R_{\text{out}} = r_0 + R_S + g_m r_o R_S \\ \approx g_m r_o R_S$$





★

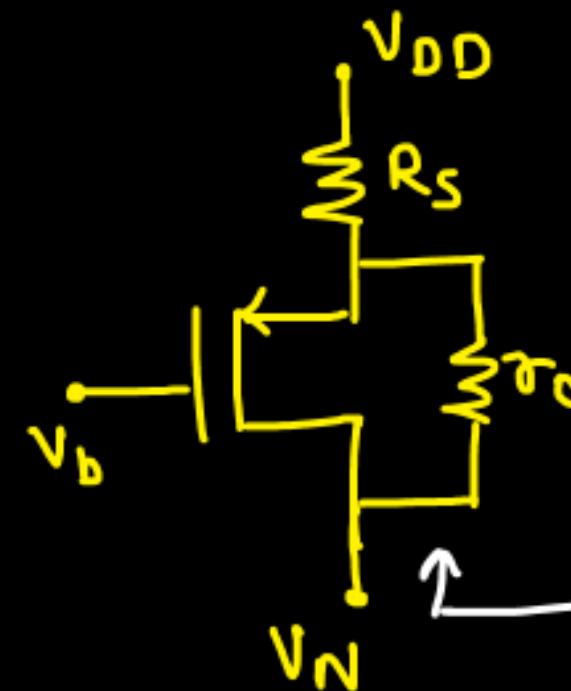
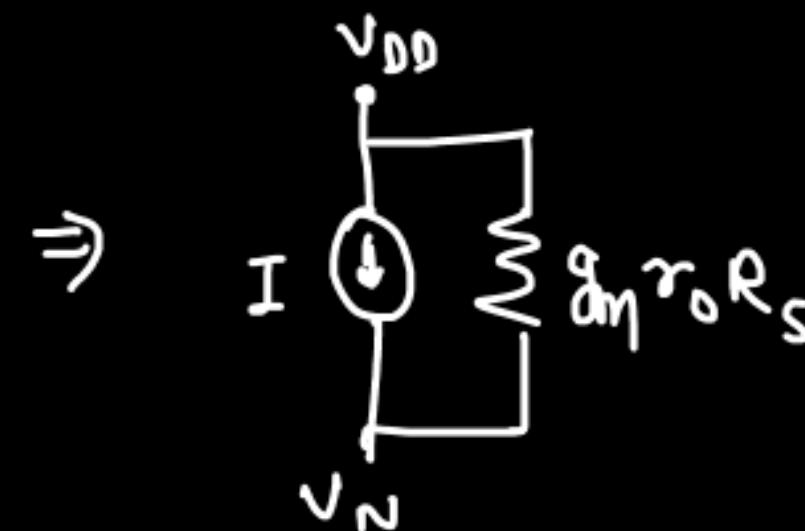
$$R_{\text{out}} = r_0 + R_S + g_m r_o R_S \\ \approx g_m r_o R_S$$



## Cascode Current Source:-

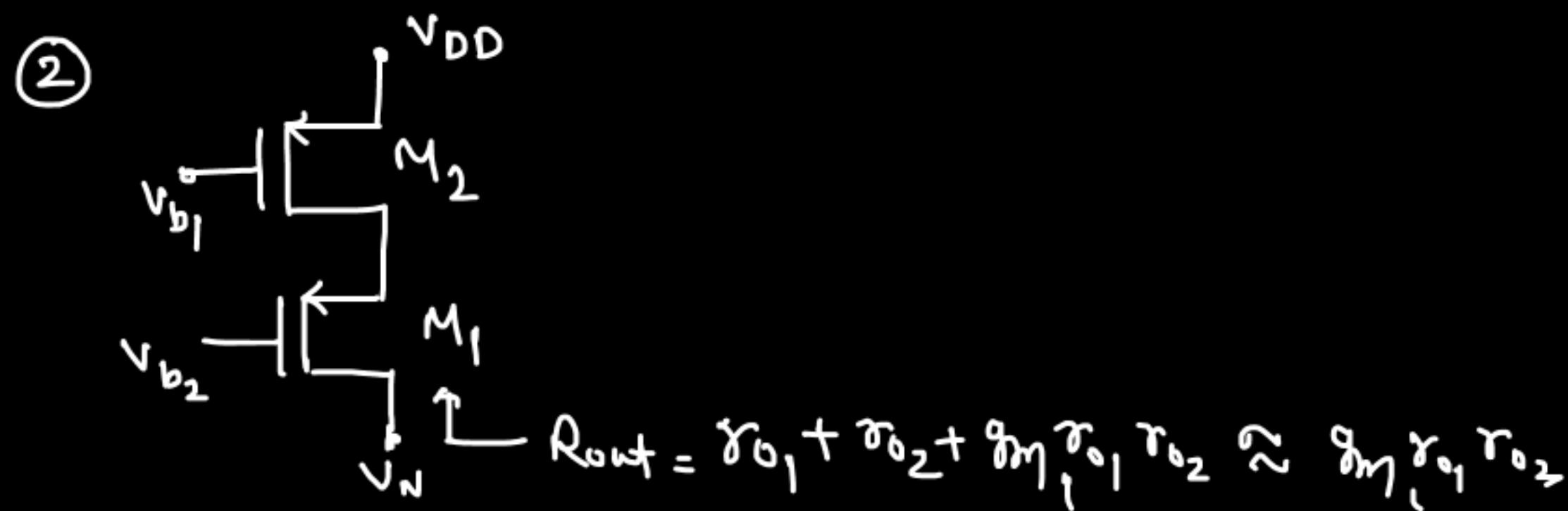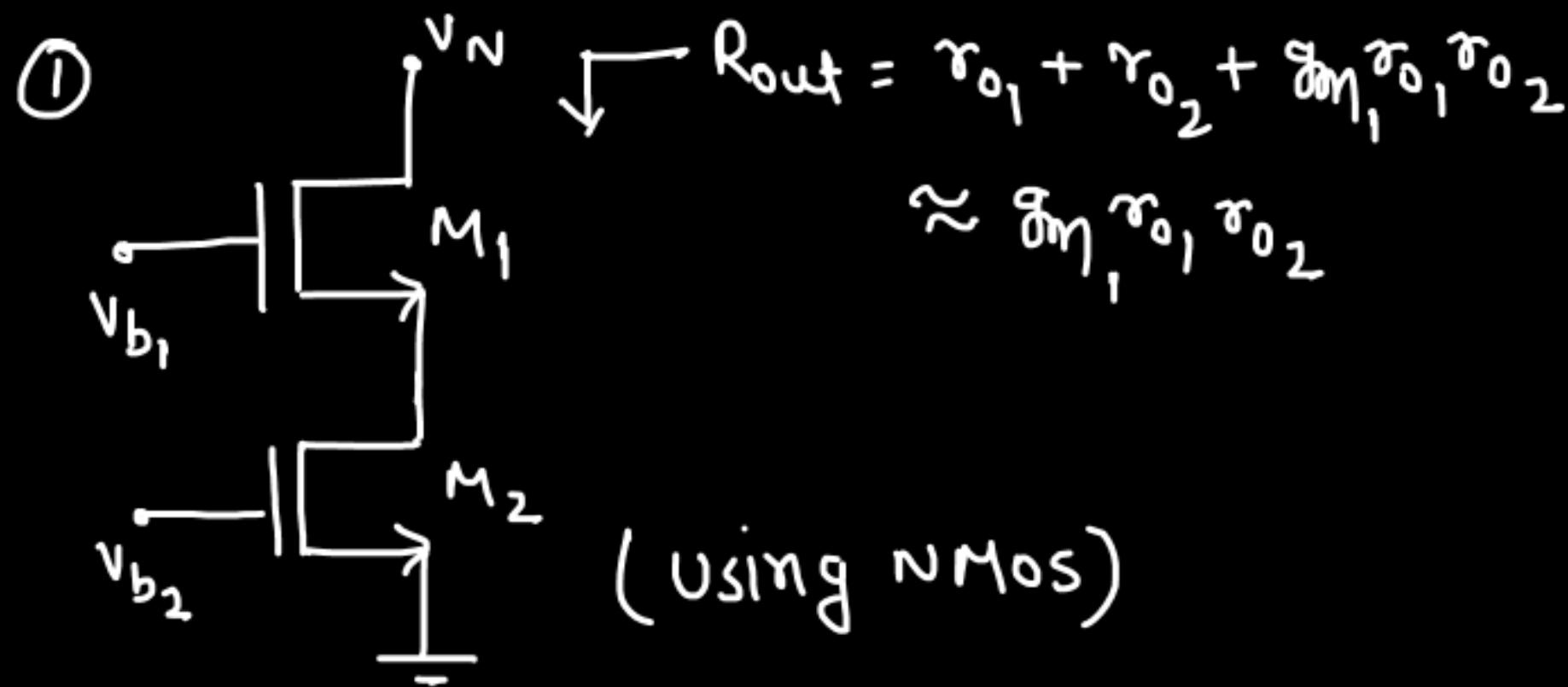


## Summary:-


①




$\Rightarrow$

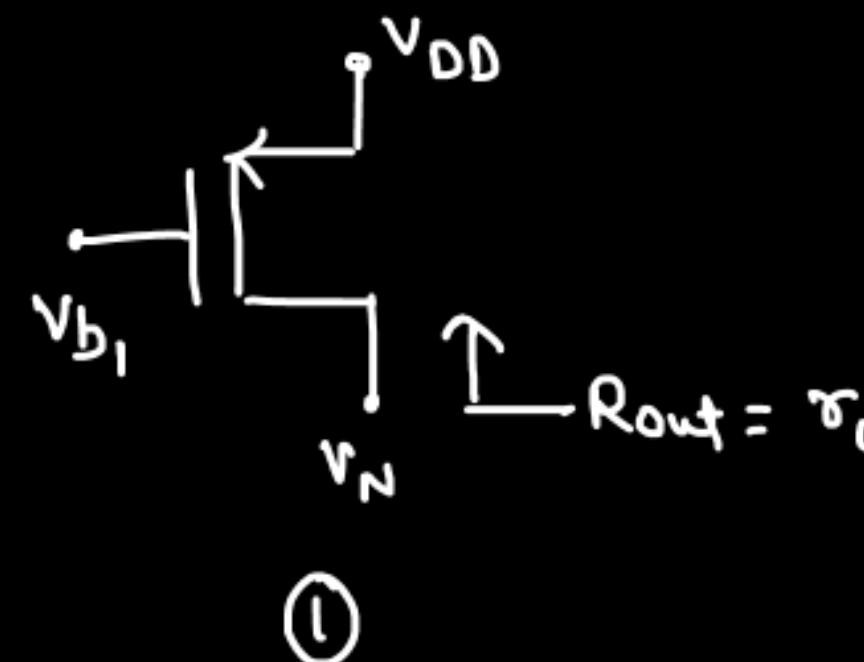

①

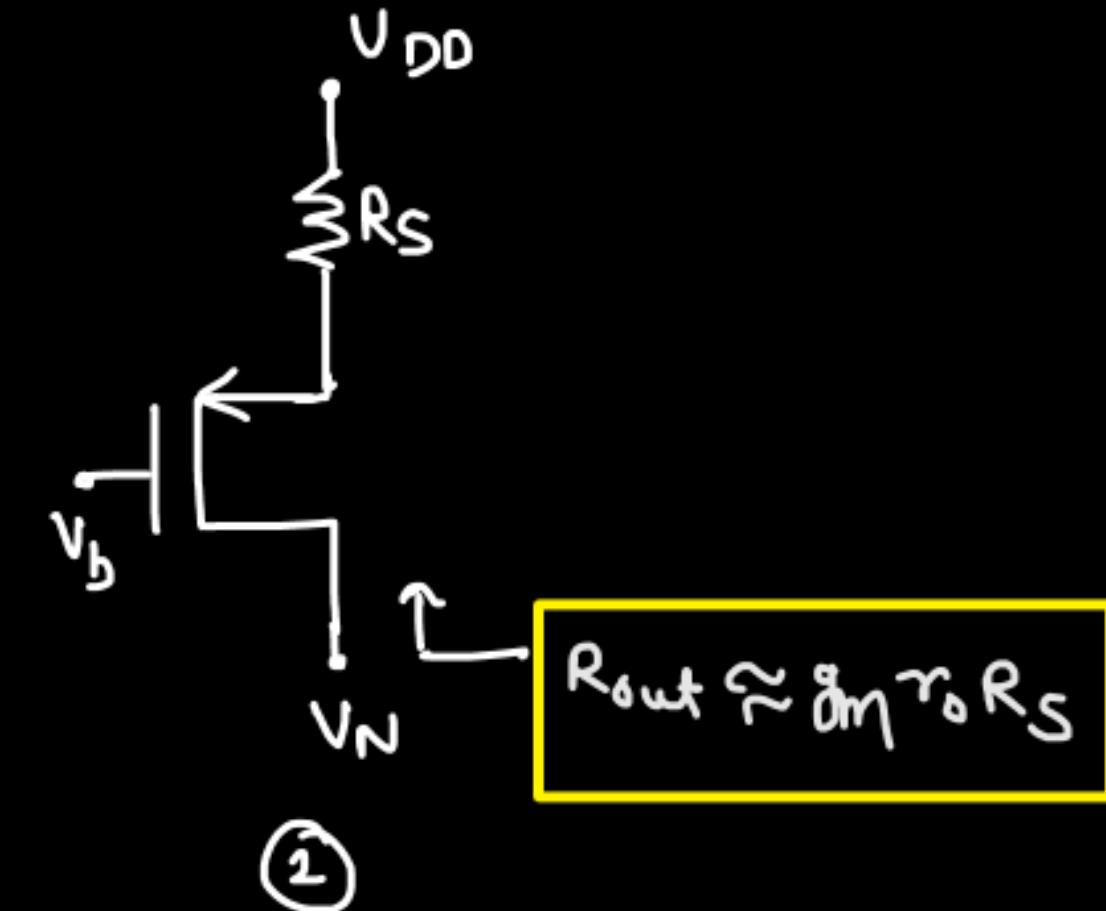

②

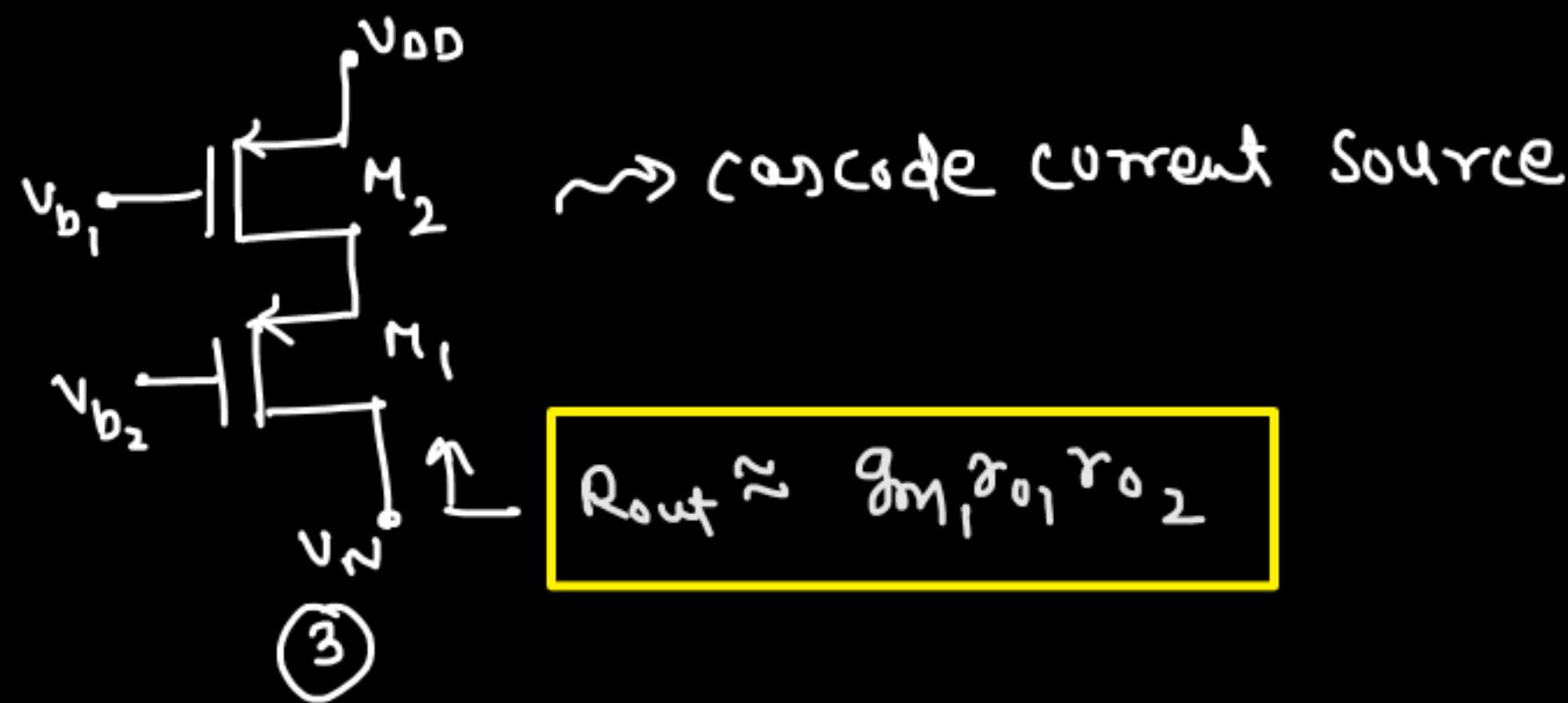


③


②




$\Rightarrow$

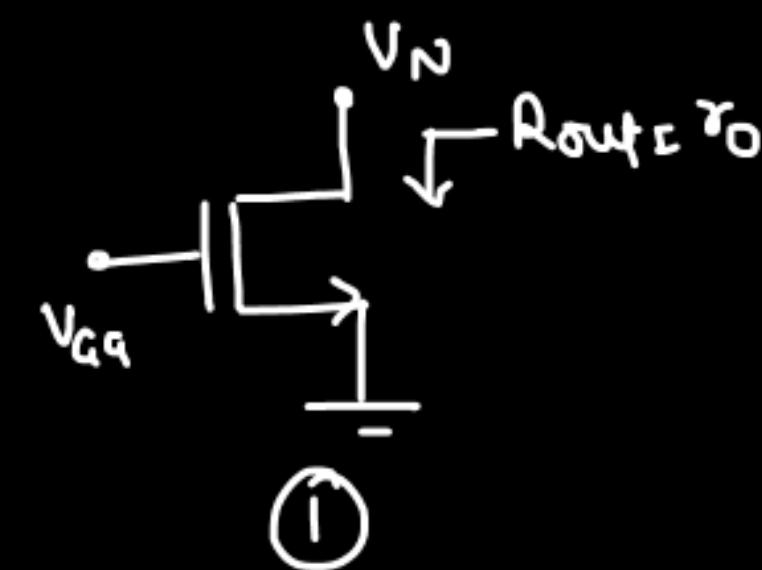

①

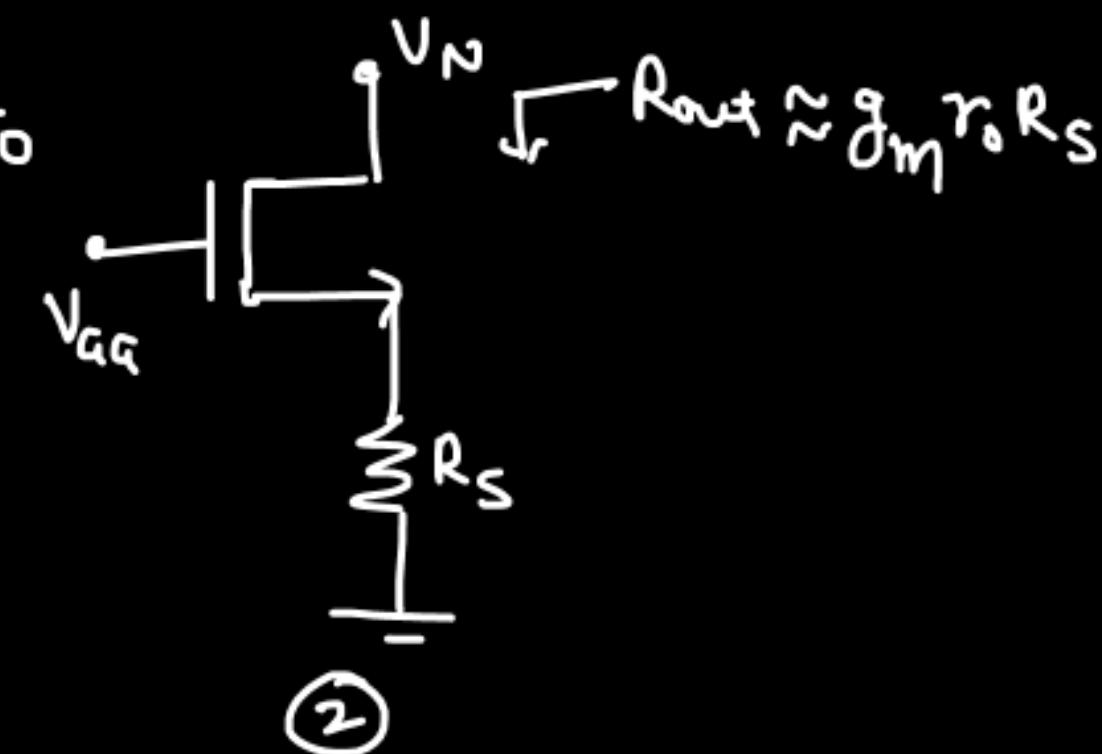



②

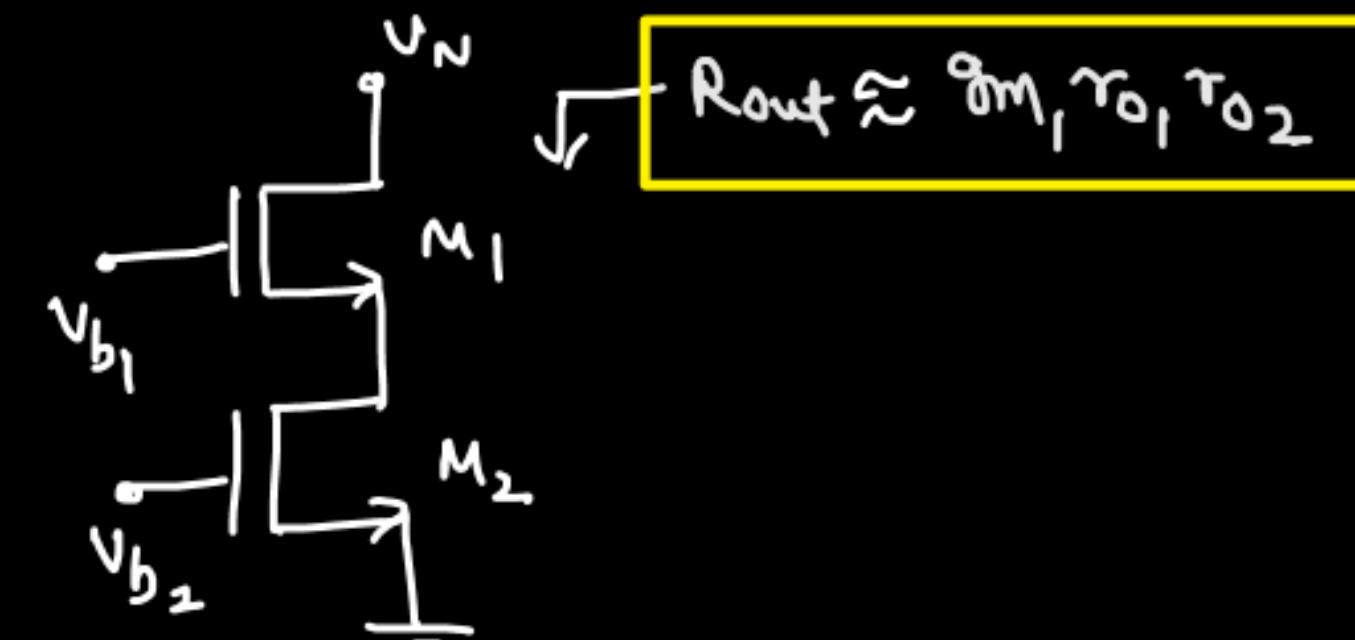

Q Design a common source amplifier with  
Cascode current source in load. Write the small  
[Using both PMOS & NMOS] signal gain.

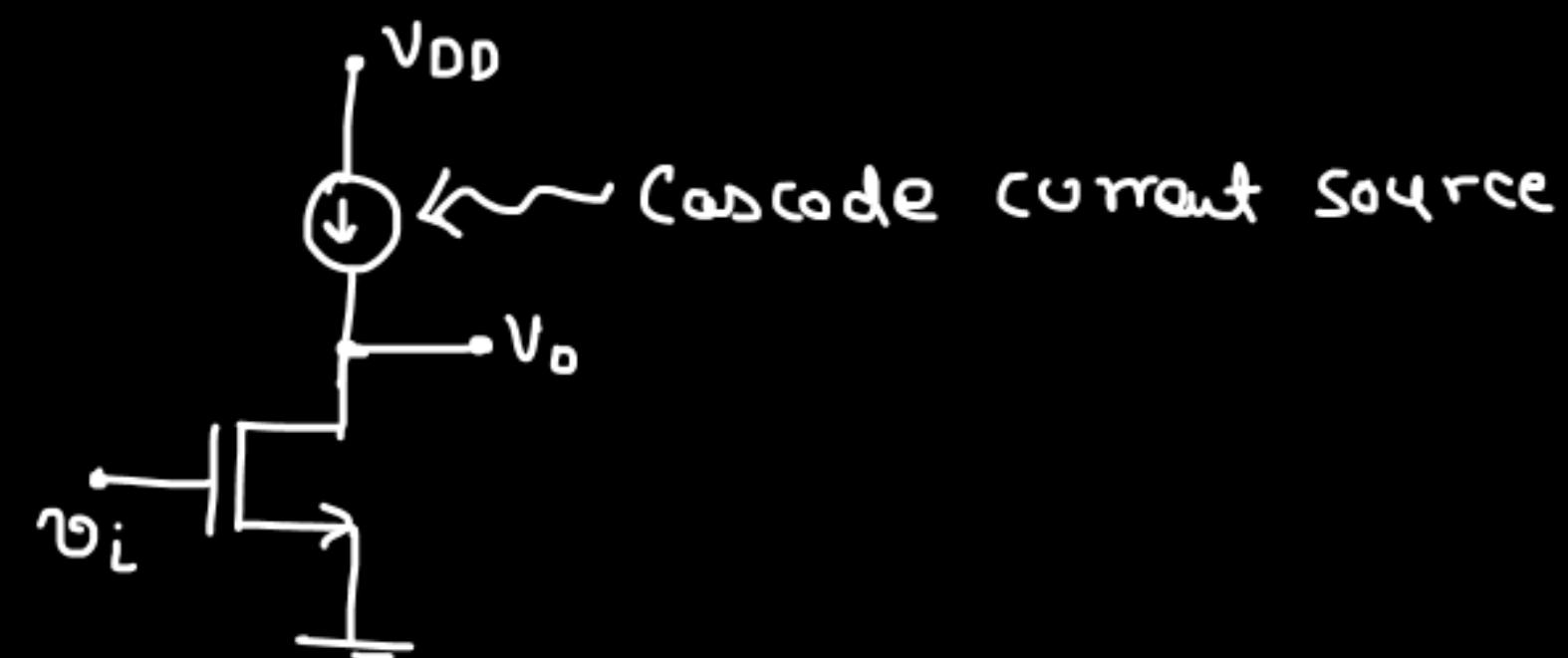→ CS Amplifier using NMOS, with current source in load:-



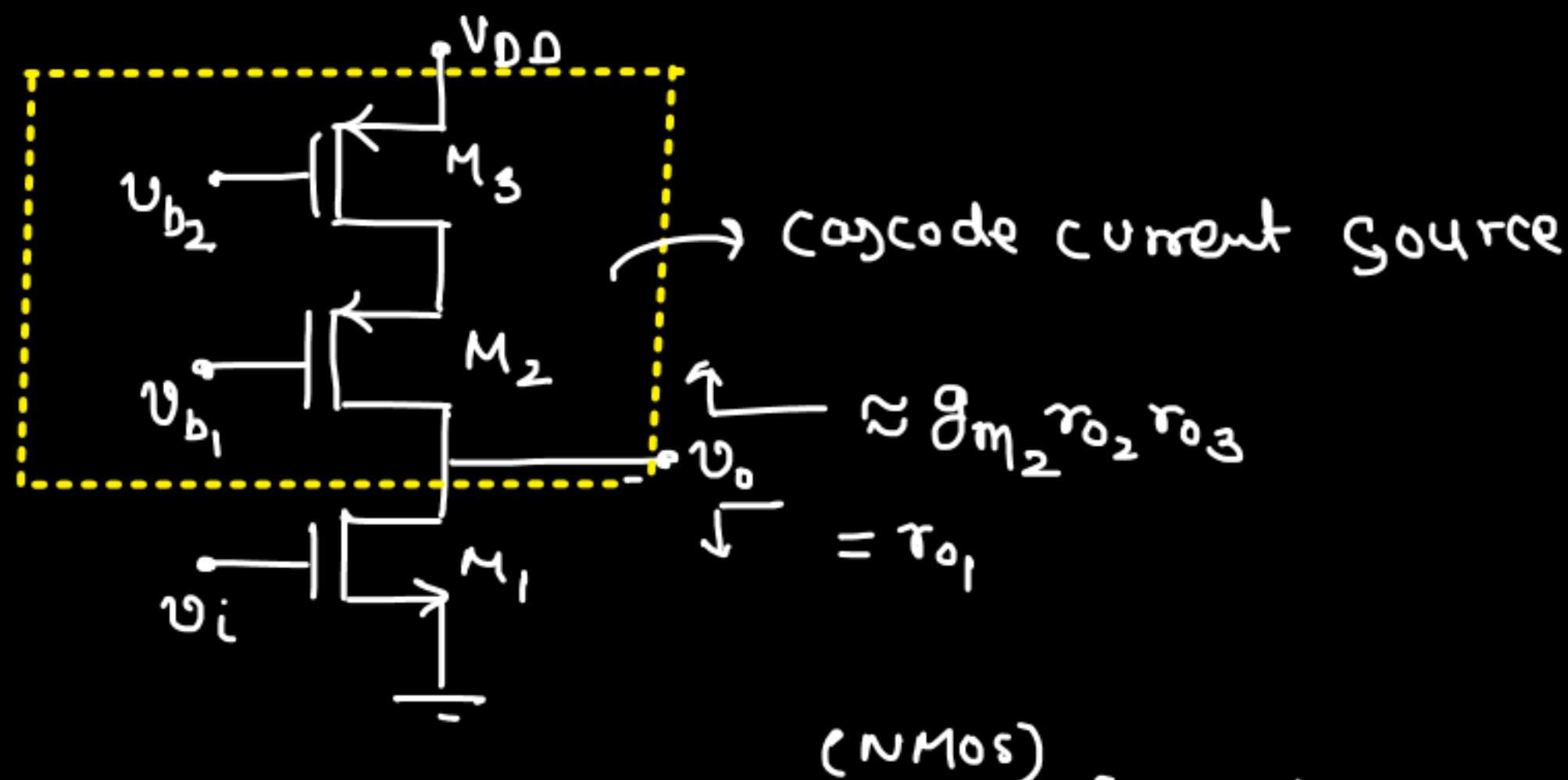


(NMOS)


fig → common source amplifier with cascode current source in (cascode PMOS)

$$\Delta V \approx -g_m [R_{o1} || g_m_2 R_{o2} R_{o3}]$$

$$\approx -g_m R_{o1}$$

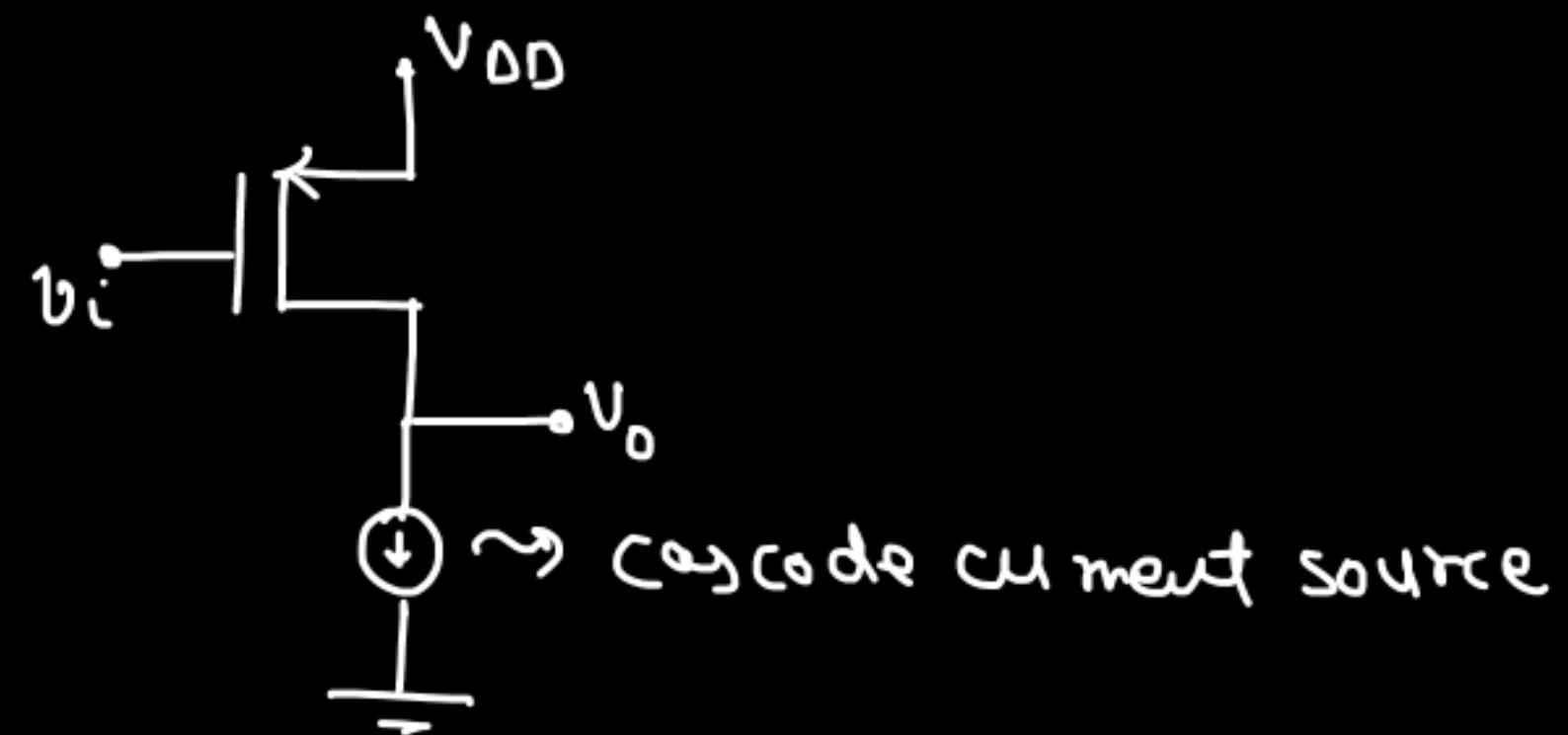⇒ CS amplifier using PMOS with current source in load.



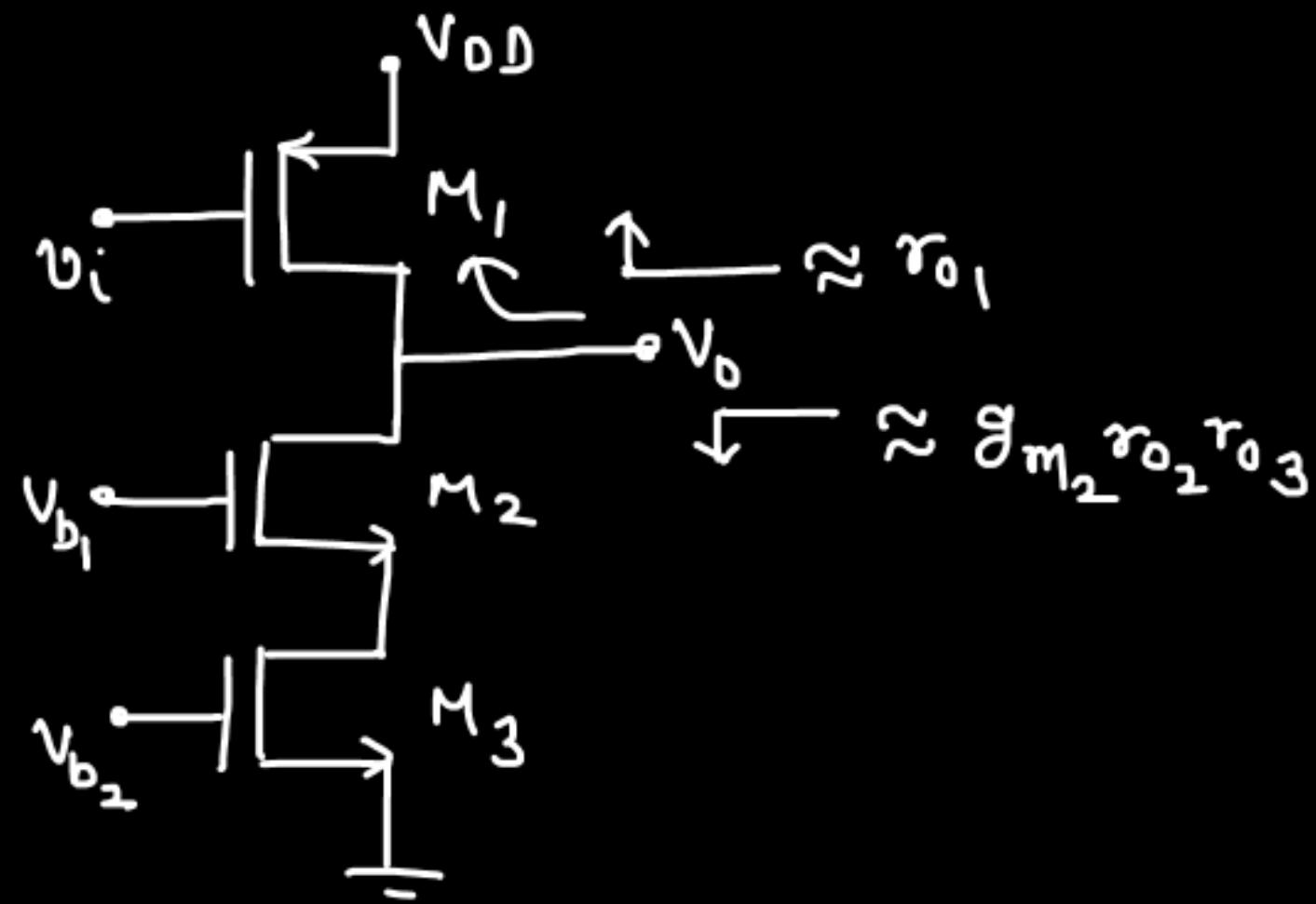

$$\Delta V = -g_m [r_o || g_m r_o r_o] \approx -g_m r_o$$

fig → common source amplifier with cascode current source  
 in load.  
 (PMOS) (NMOS)

Target :-

Building a High gain Amplifier.

$$A_V = G_m R_{out}$$

keeping  $G_m$  constant, increase  $R_{out}$



⇒ The design we made in the previous problem.

$$R_{out} = r_{o1} \parallel g_m r_{o2} r_{o3}$$





increase  $R_{out} =$

## Cascode Amplifier :-

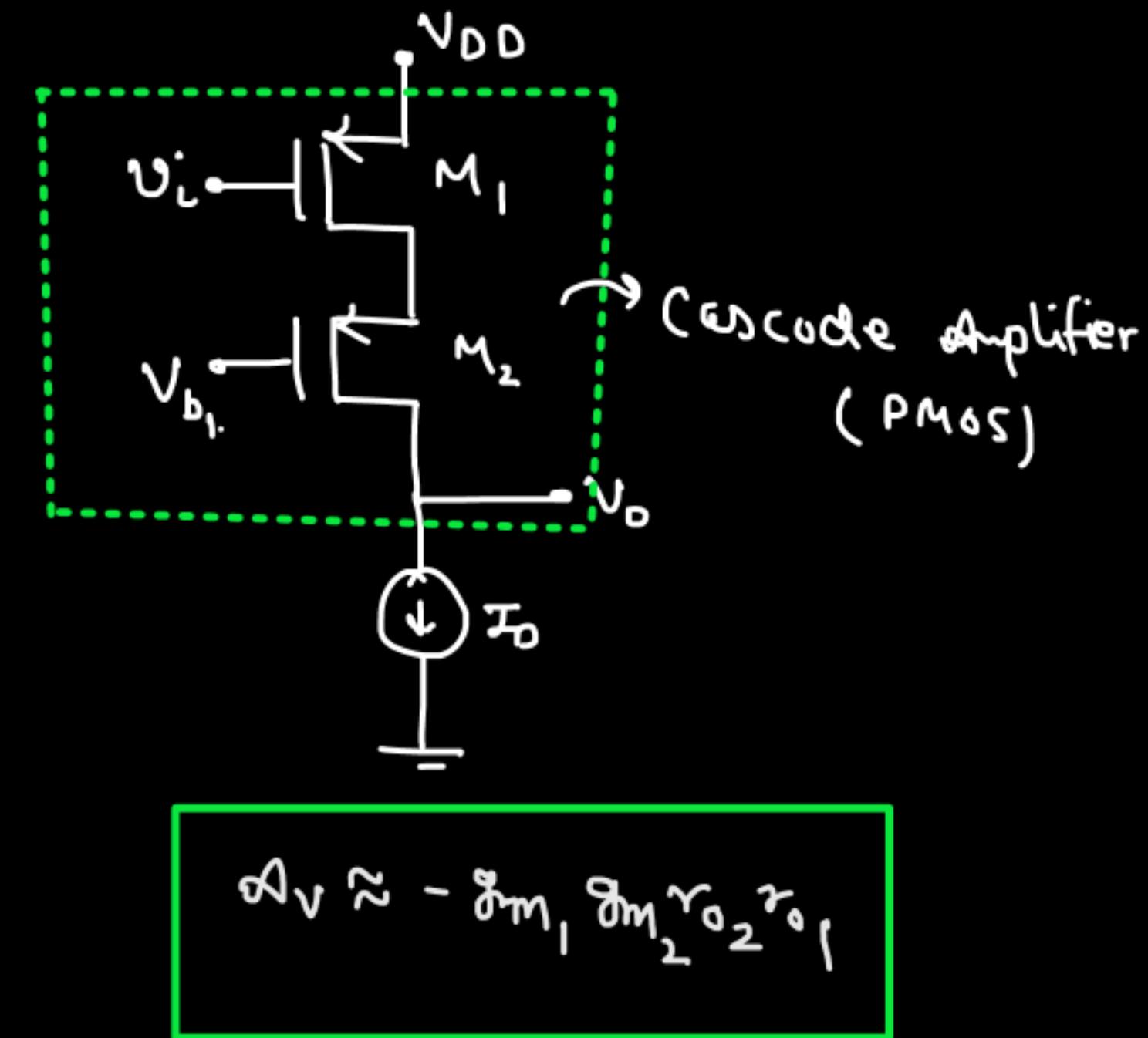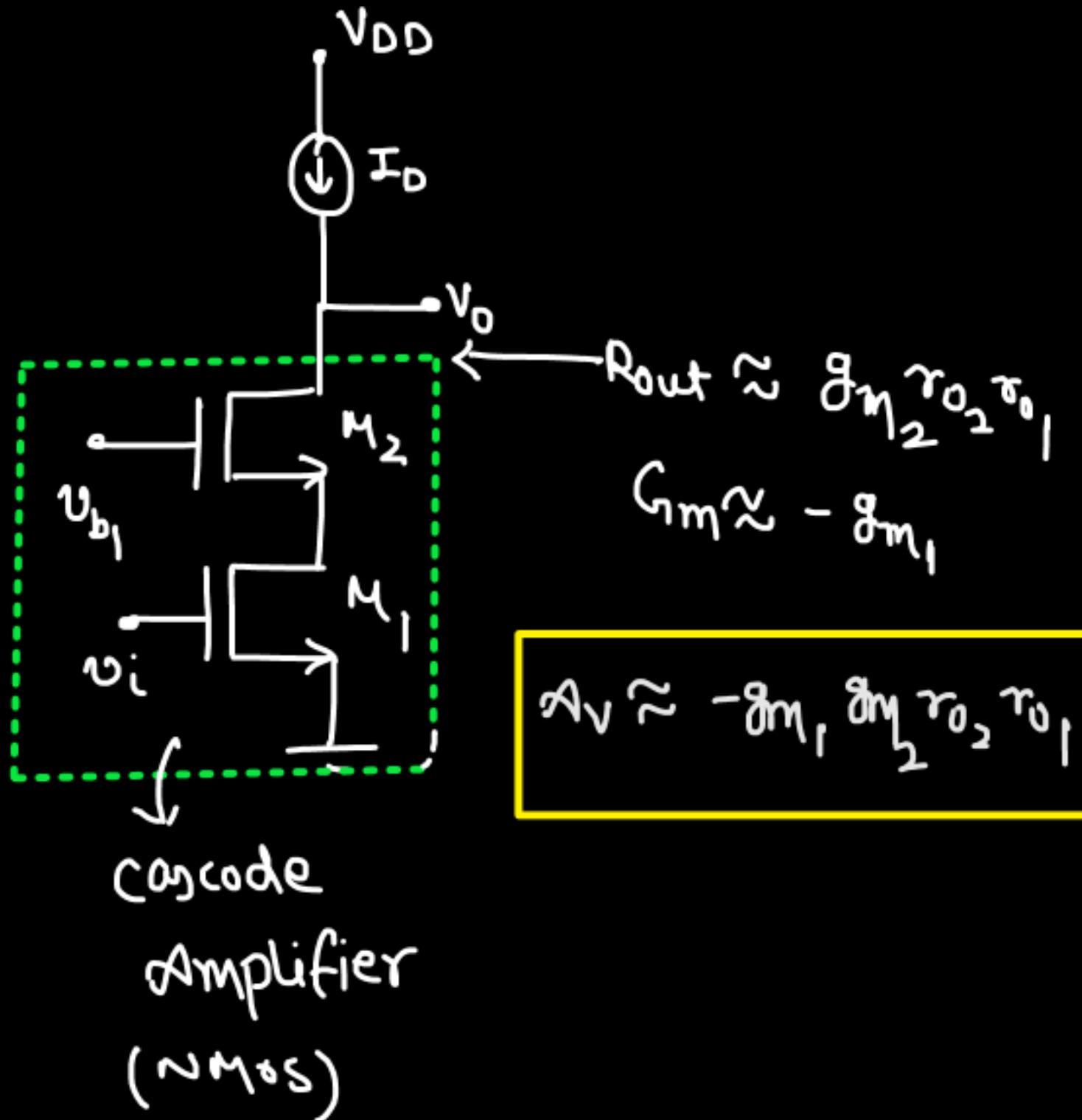

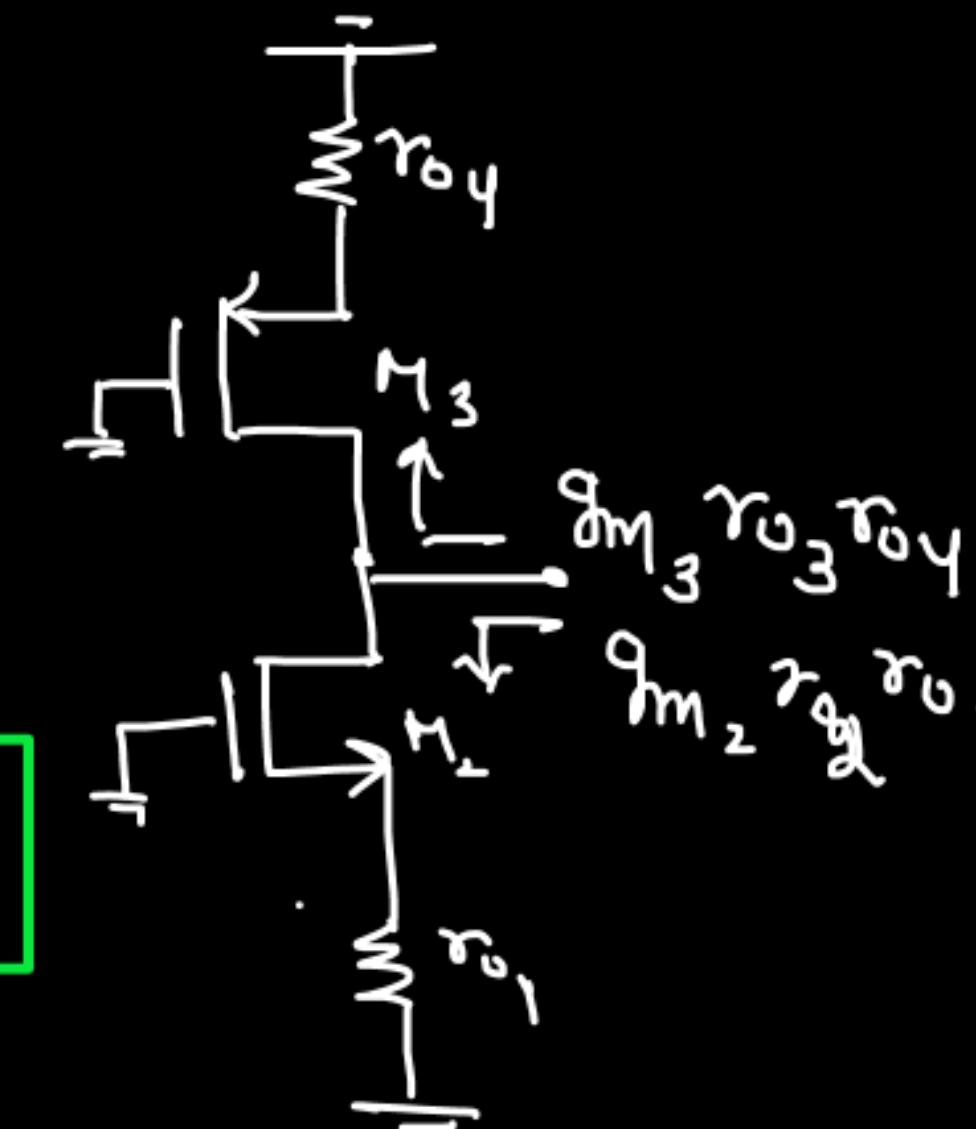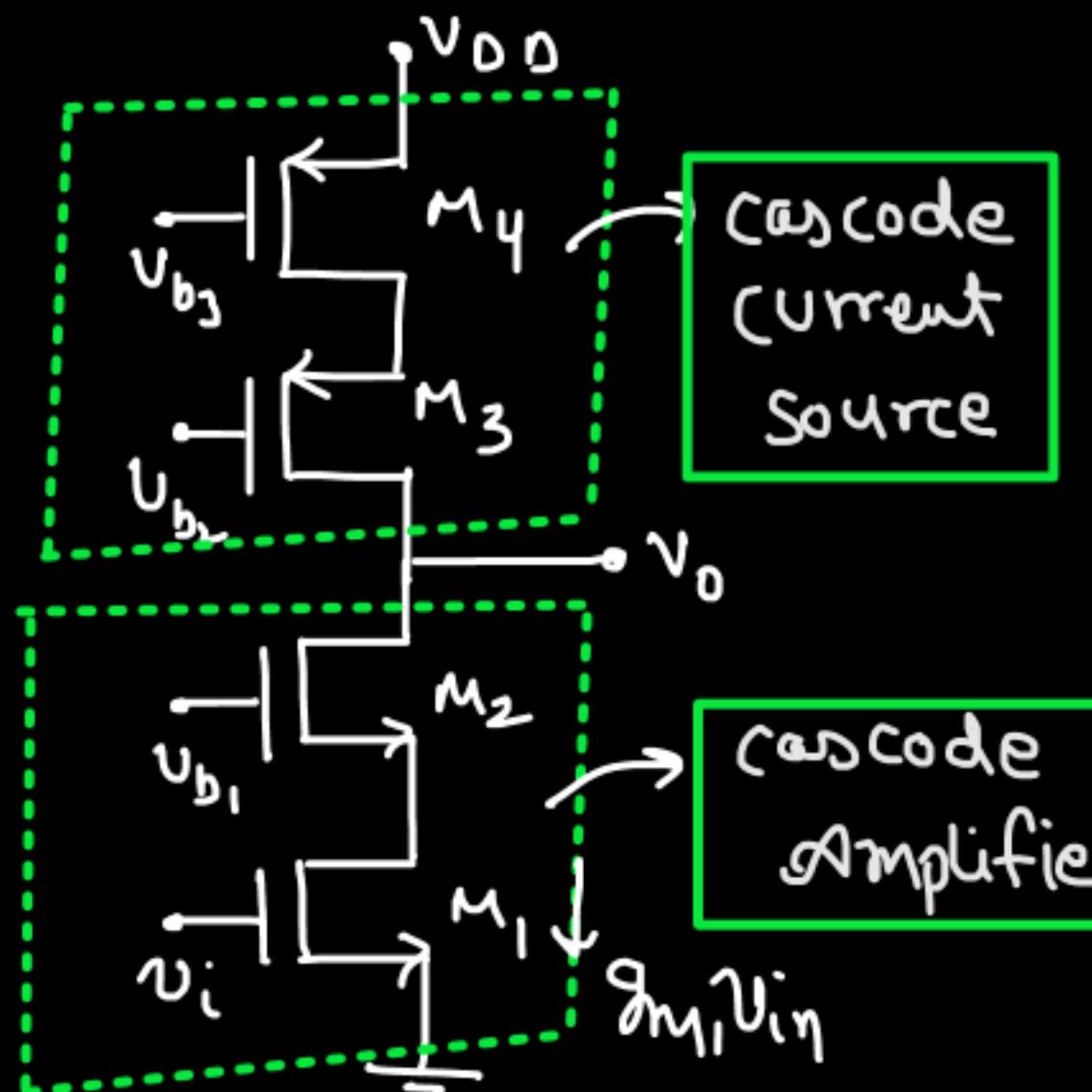
## Cascode amplifier with cascode current source:-



$$g_m \approx -g_{m1}$$

$$R_{out} \approx g_{m3} r_{o3} r_{o4} || g_{m2} r_{o2} r_{o1}$$

$$\Delta V \approx -g_{m1} [g_{m3} r_{o3} r_{o4} || g_{m2} r_{o2} r_{o1}]$$

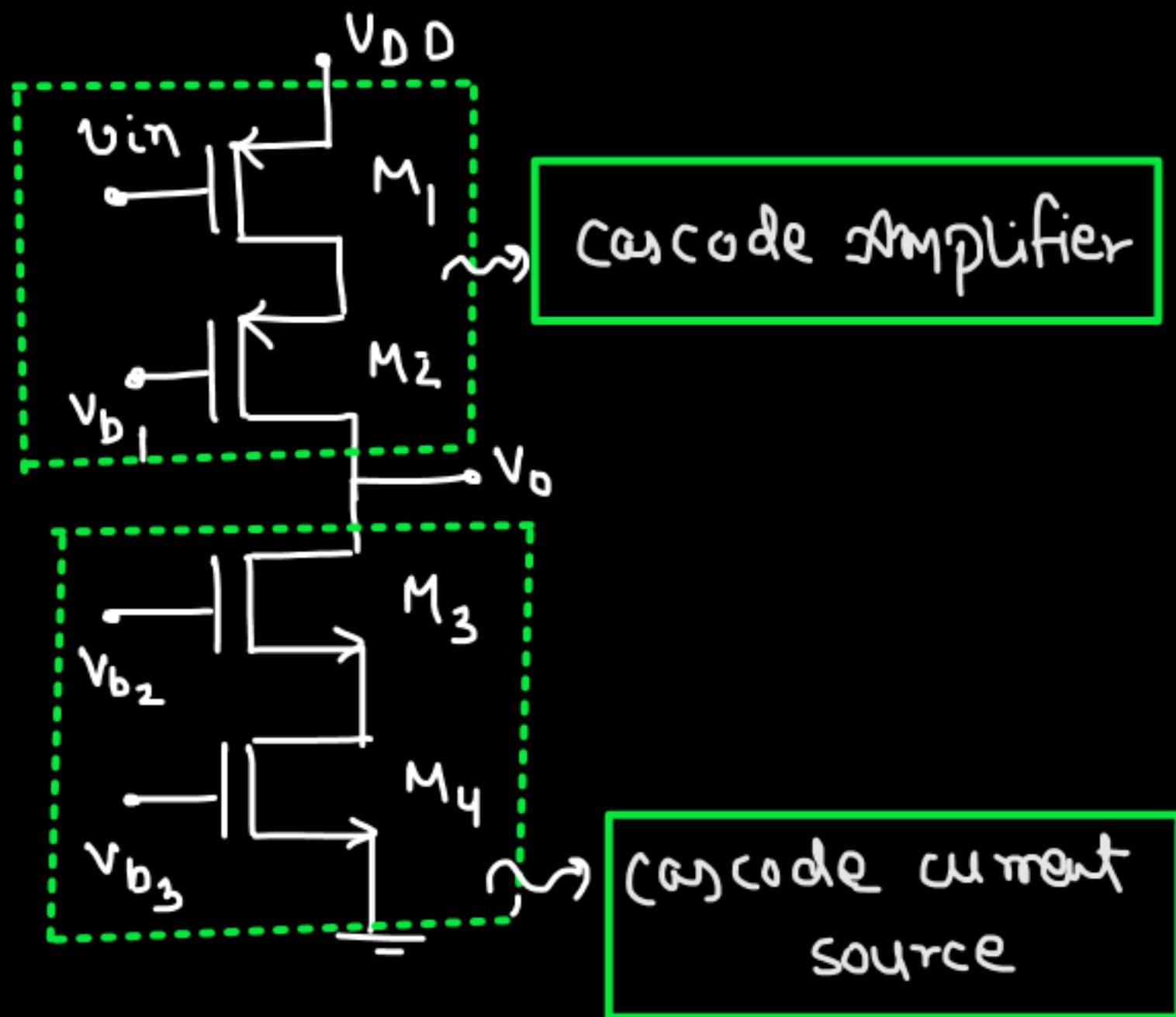


$$G_m \approx -g_{m_1}$$

$$R_{out} \approx g_{m_2} r_{o_2} r_{o_1} || g_{m_3} r_{o_3} r_{o_4}$$

$$\Delta V = -g_{m_1} [g_{m_2} r_{o_2} r_{o_1} || g_{m_3} r_{o_3} r_{o_4}]$$


What if :-

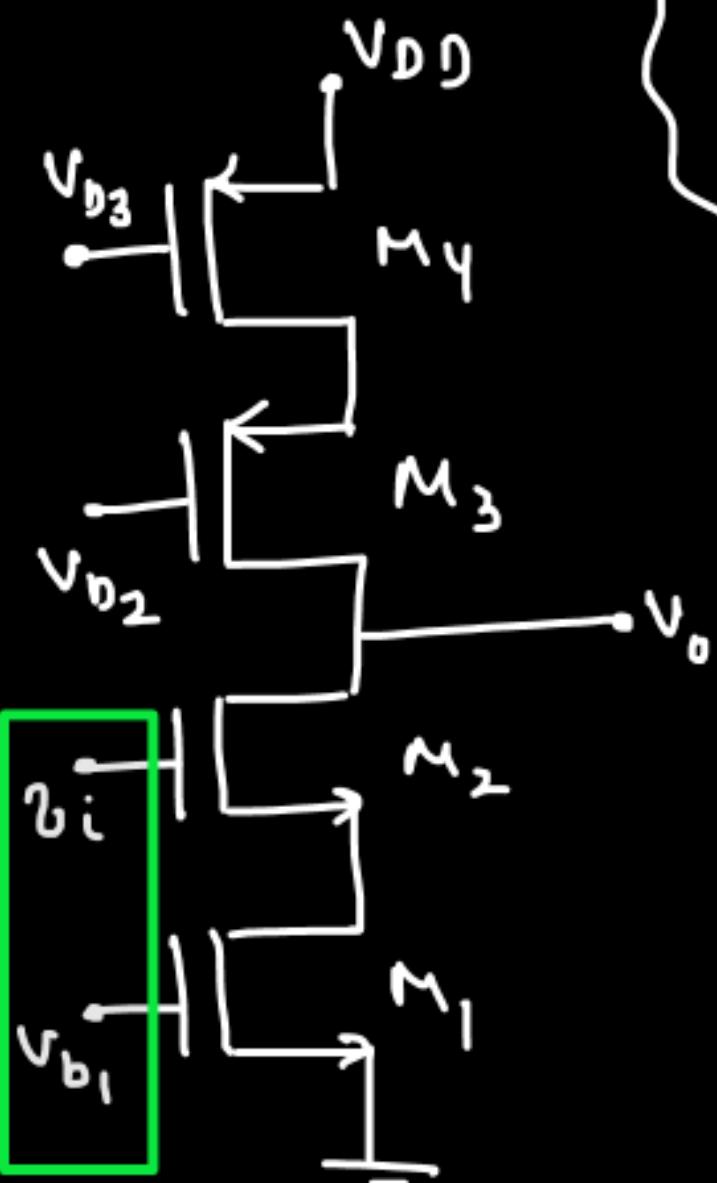


$$R_{out} \approx g_m r_{o3} r_{o4} || g_m r_{o2} r_{o1}$$

Same as before

$G_m = ?$

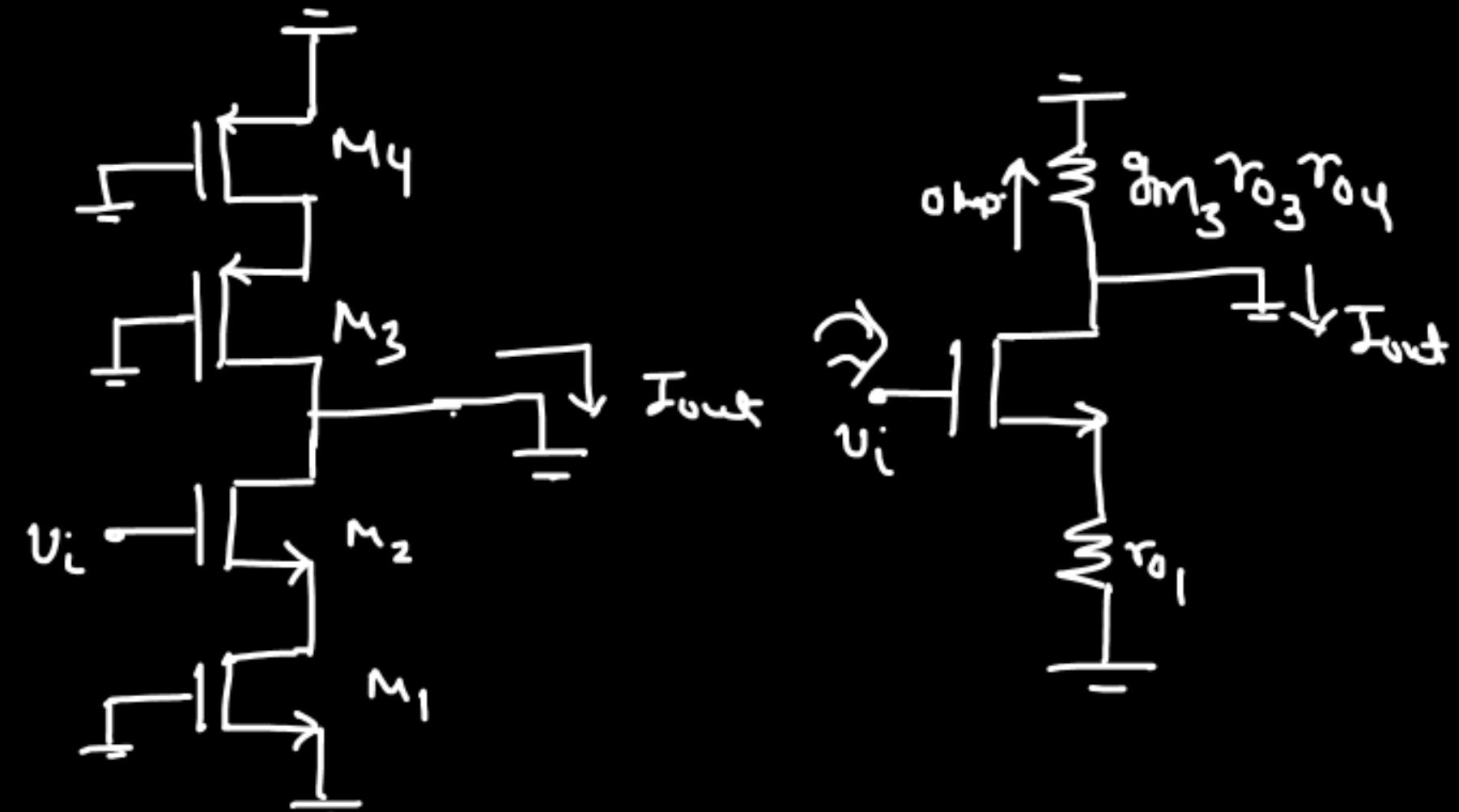

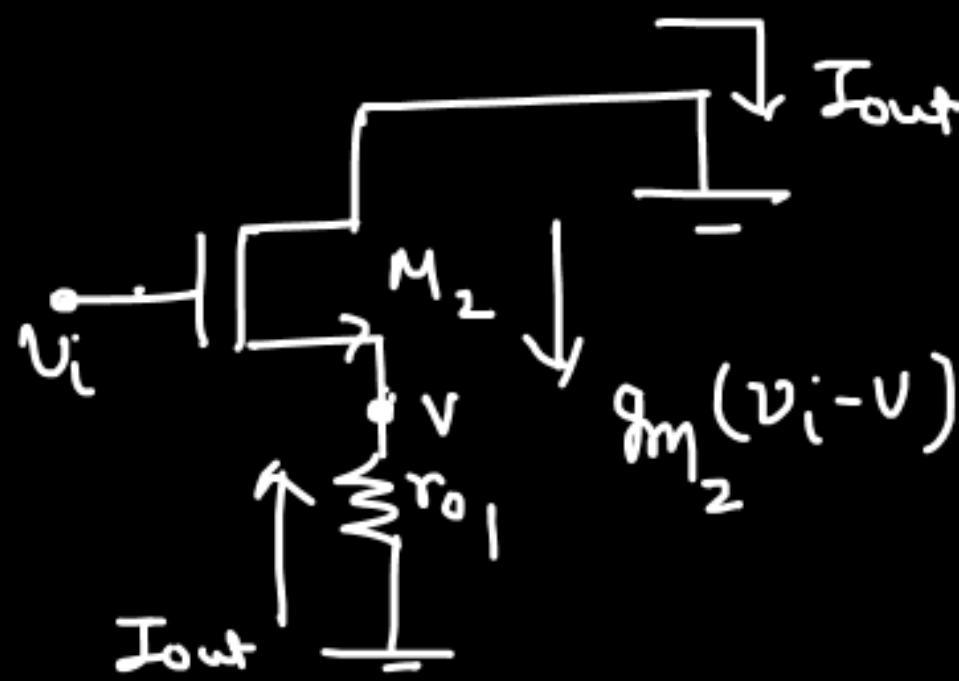

$$I_{out} = -g_m M_2 (V_i - V)$$

$$\frac{V}{r_{o1}} = -I_{out}$$

$$V = -I_{out} r_{o1}$$

$$I_{out} = -g_m M_2 (V_i + I_{out} r_{o1})$$

$$I_{out} = -g_m M_2 V_i - g_m M_2 r_{o1} I_{out}$$


$$\text{gain} \approx -\frac{g_m M_2}{1 + g_m M_2 r_{o1}} [g_m M_3 r_{o3} r_{o4} || g_m M_2 r_{o2} r_{o1}]$$

$$\frac{I_{out}}{V_i} = G_m = \frac{-g_m M_2}{1 + g_m M_2 r_{o1}} \rightsquigarrow G_m \text{ is reduced}$$


Gain is reduced [then cascode amplifier]

## Cascode Amp. v/s Common Source Amp. with degeneration:-


① Cascode Amp. (NMOS)

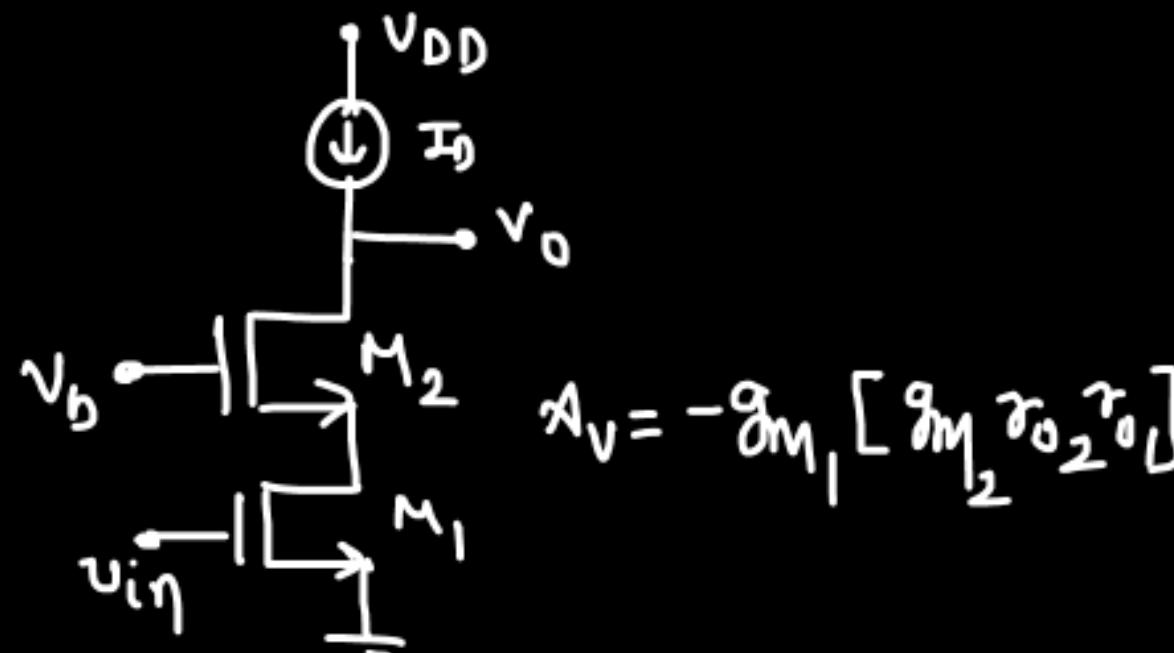


③ Cascode Amp. (PMOS)

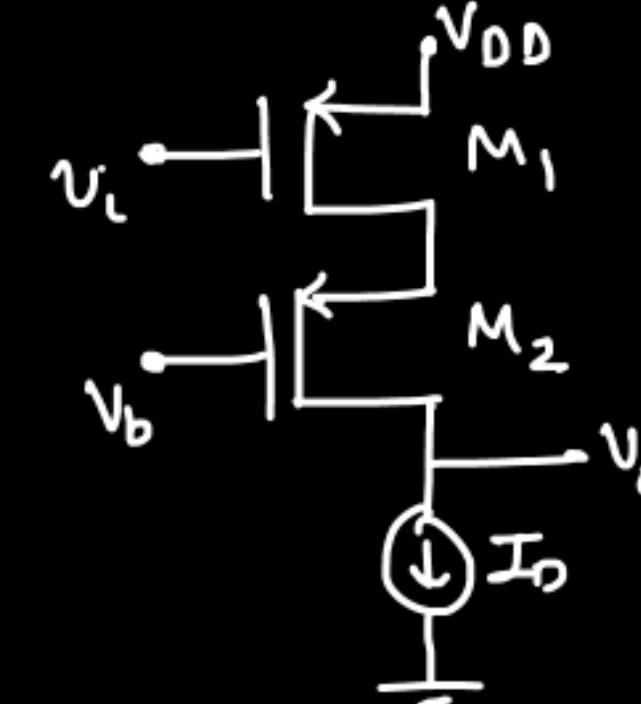

② CS with degen. amp. (NMOS)

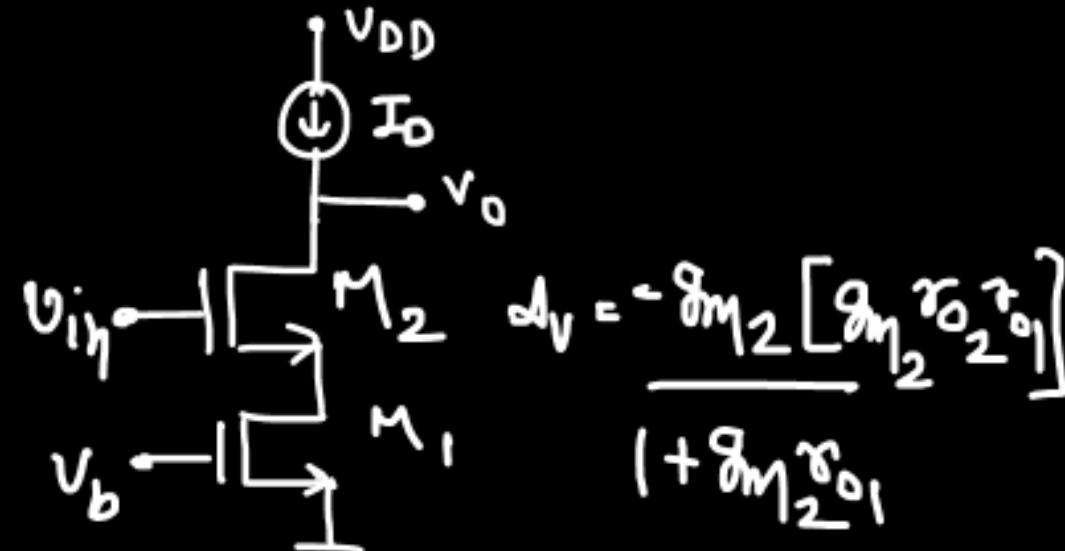


④ CS with degen. amp. (PMOS)

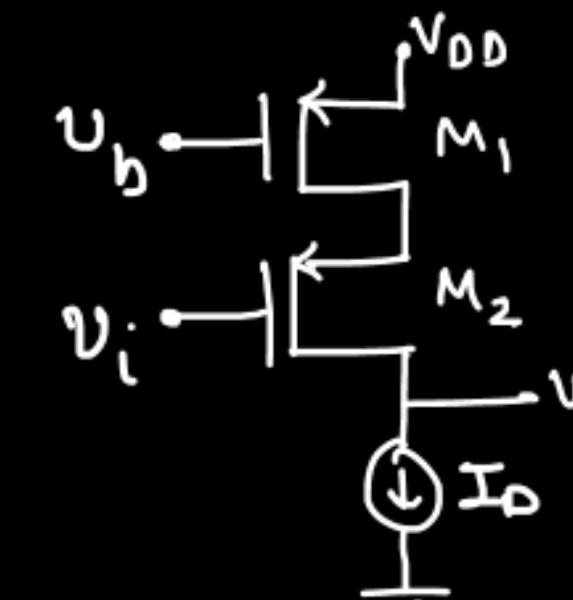

N.B.-

Cascode Amplifier :- Common Source Amp. in series  
with common Gate Amp.


## ⇒ Using MOS as a current source:-

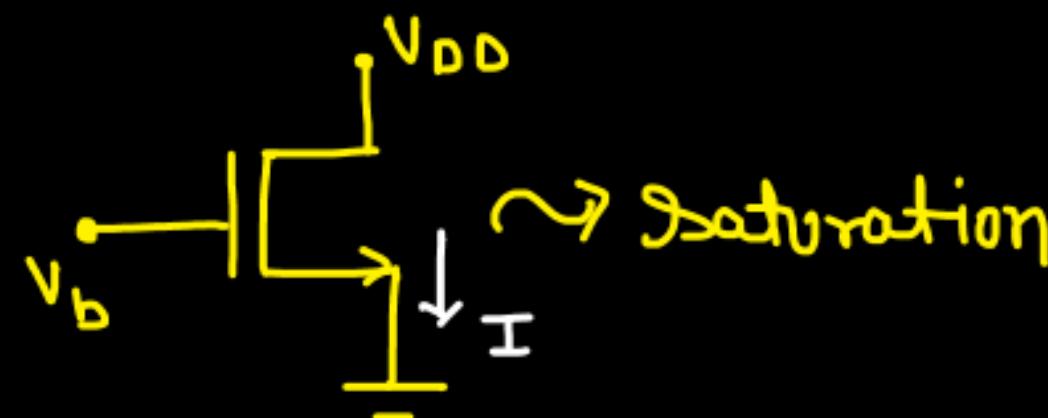

$$I = \frac{\mu_n C_{ox} W}{2L} (V_b - V_T)^2$$

$$I = \frac{\mu_n C_{ox} W}{2L} \left[ \frac{R_2}{R_2 + R_1} V_{DD} - V_T \right]^2$$

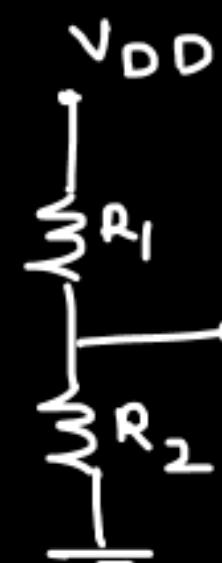Temp.  
dependent      Supply  
dependent      Temp.  
dependent



$$V_b = \frac{R_2}{R_2 + R_1} V_{DD}$$

⇒ I ≠ constant

⇒ for making a current source which is independent of supply and Temp., we need to use "Bandgap" circuit.

variation


[ OUT OF THE  
Scope of this  
course ]

Golden current source ⇒ Constant current Source


$$I_{\text{golden}} = I_{\text{ref}}$$

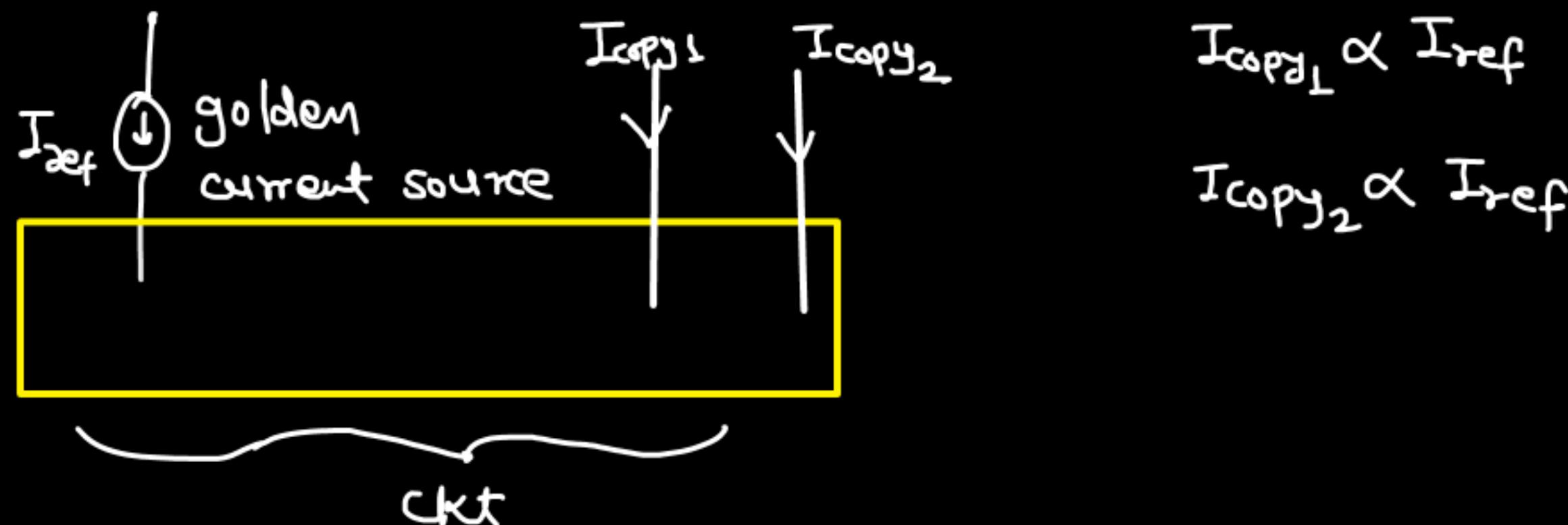
## Current Mirror ckt:-

With the help of golden current source , we will generate other current sources which are identical to golden current source.



Try-1:-

Using a resistor:-

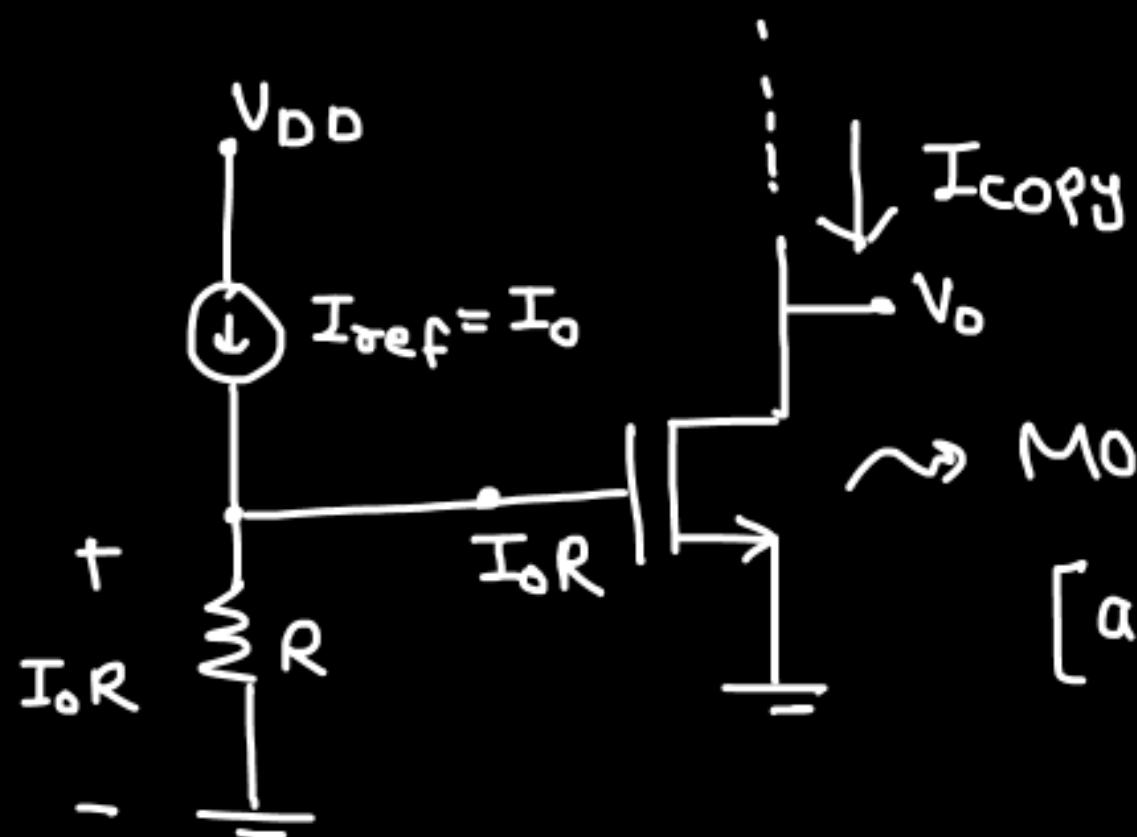

~ MOS is sat region


[adjust  $V_o$  such that Mos is working in sat.]

$$I_{\text{copy}} = \frac{I_0}{2L} \left[ I_0 R - \frac{V_o}{2} \right]^2$$

Temp dependent

Try-2:-

Using diode connected Transistor:-

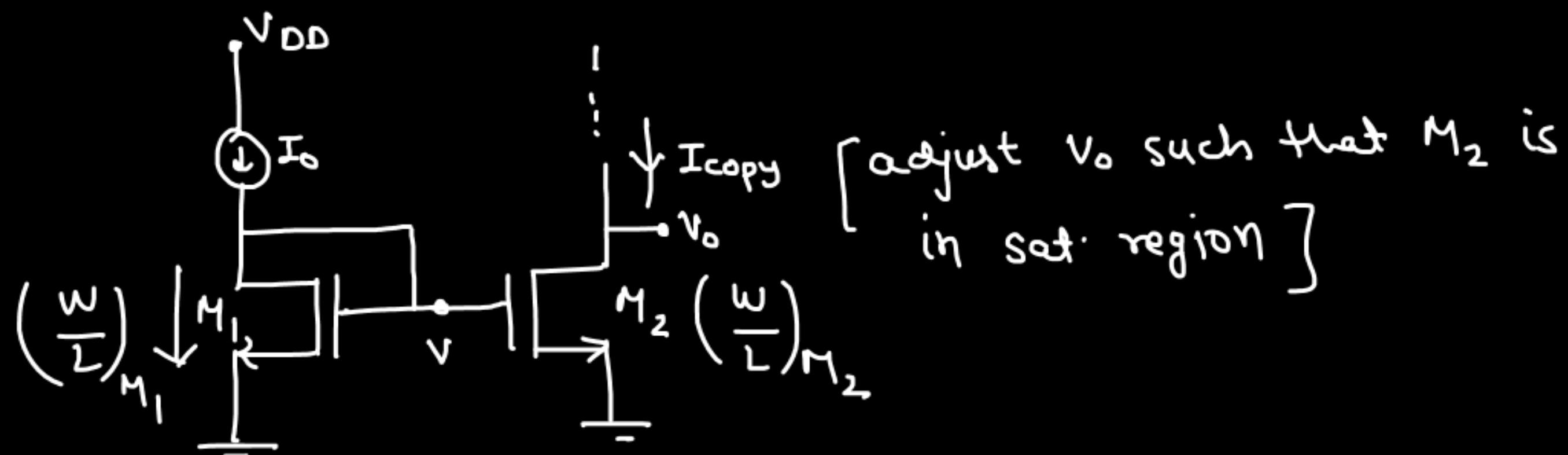

$$I_0 = \frac{\mu_n C_{ox}}{2} \left(\frac{w}{L}\right)_{M_1} (v - v_T)^2$$

$$v = \sqrt{\frac{2I_0}{\mu_n C_{ox} (\frac{w}{L})_{M_1}}} + v_T \quad \text{--- (1)}$$

$$I_{\text{copy}} = \frac{\mu_n C_{\text{ox}}}{2} \left(\frac{\omega}{L}\right)_{M_2} [V - V_T]^2$$


$$= \frac{\mu_n C_{\text{ox}}}{2} \left(\frac{\omega}{L}\right)_{M_2} \left[ \sqrt{\frac{2I_0}{\mu_n C_{\text{ox}} \left(\frac{\omega}{L}\right)_{M_1}}} + V_T - V_T \right]^2$$

$$I_{\text{copy}} = \frac{\left(\frac{\omega}{L}\right)_{M_2} I_0}{\left(\frac{\omega}{L}\right)_{M_1}}$$

$$I_{\text{copy}} \propto I_0$$

$\downarrow$   
independent of supply and Temp variation.
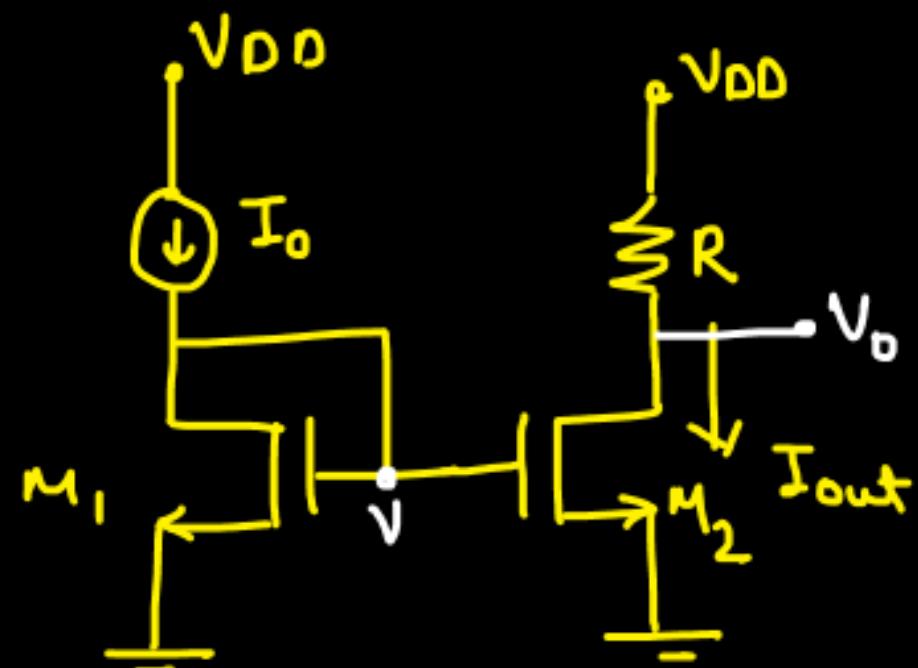
## Alternative Analysis of current Mirror ckt:-



$\Rightarrow$  Both  $M_1$  and  $M_2$  are in Sat. region.


$$(V_{GS})_{M_1} = (V_{GS})_{M_2} = V$$

$$I_0 = \mu_n C_{ox} \left( \frac{w}{L} \right)_{M_1} (V - V_T)^2 \quad \text{--- ①}$$

$$I_{out} = \mu_n C_{ox} \left( \frac{w}{L} \right)_{M_2} (V - V_T)^2 \quad \text{--- ②}$$

$$\text{②} \div \text{①} \Rightarrow \frac{I_{out}}{I_0} = \frac{\left( \frac{w}{L} \right)_{M_2}}{\left( \frac{w}{L} \right)_{M_1}} \Rightarrow I_{out} = \frac{\left( \frac{w}{L} \right)_{M_2}}{\left( \frac{w}{L} \right)_{M_1}} I_0$$

Eg.

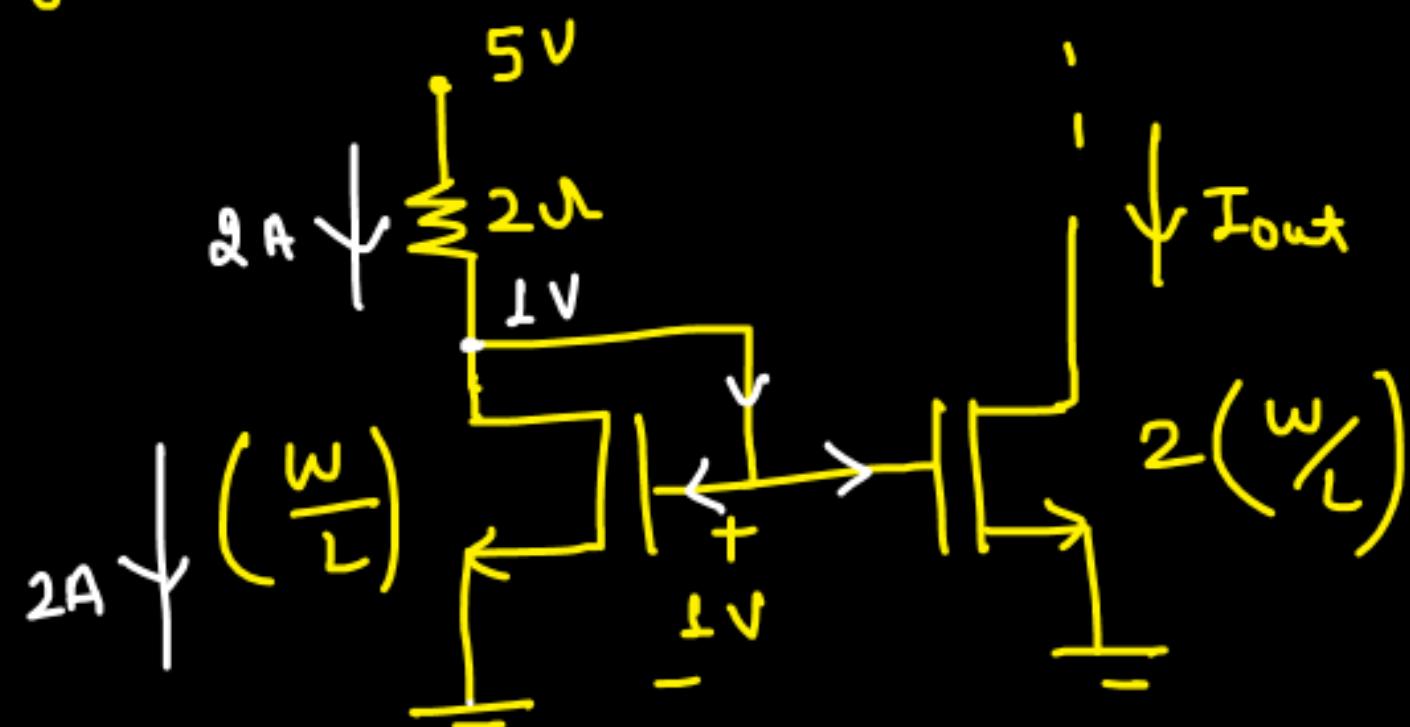


Both Transistors are working in Sat. region.  
Find  $I_{out} = ?$

$$I_{out} = \frac{2\left(\frac{w}{L}\right)}{\left(\frac{w}{L}\right)} \times 2 \text{ Amp.}$$

$$I_{out} = 4 \text{ Amp.}$$

## Current mirror using PMOS:-

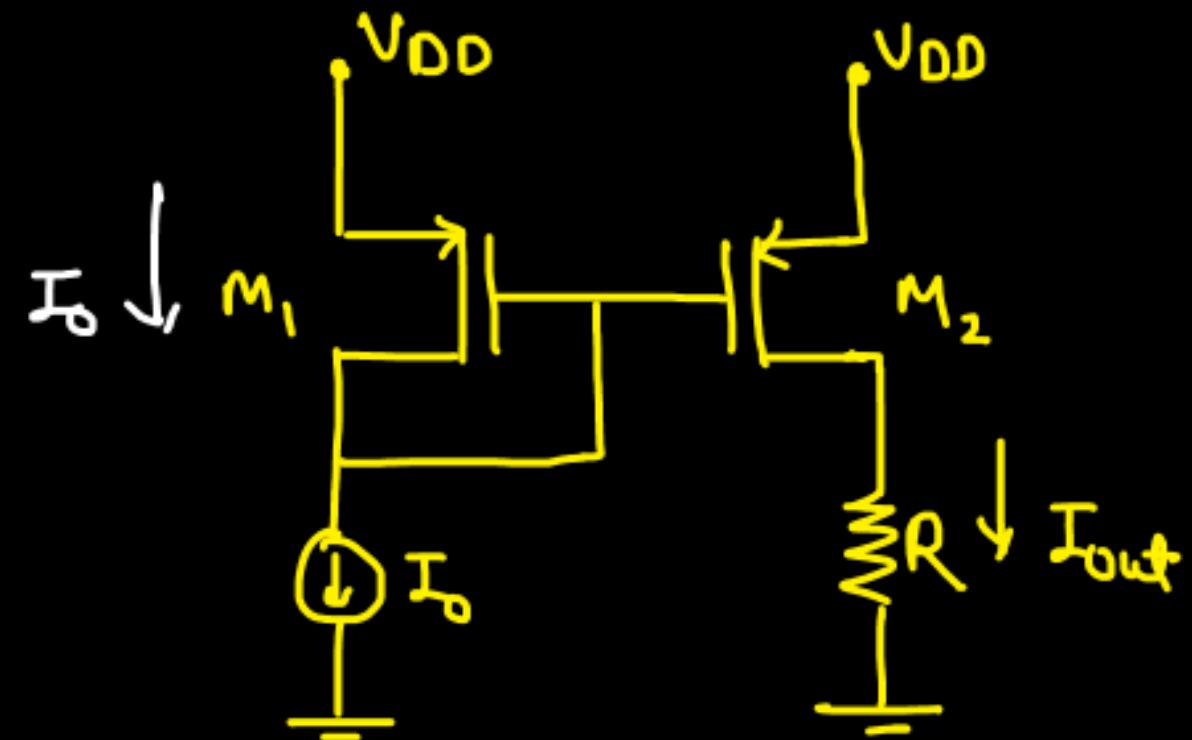


$$I_{out} = \frac{(w/L)_{M_2}}{(w/L)_{M_1}} I_0$$

Q. Both Transistors are perfectly matched.

$$m_n C_{ox} = 200 \mu A/\sqrt{V}, W/L = 10, V_T = 0.7V, \lambda = 0$$

Find the value of R to get 100μA o/p current.

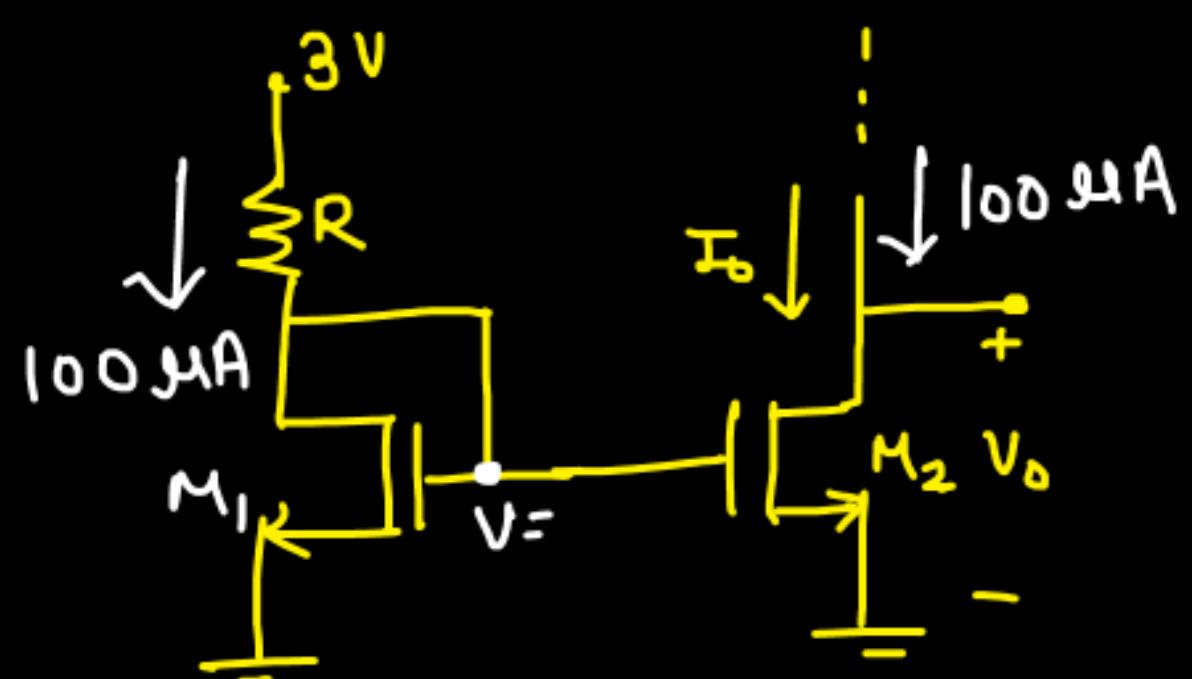
What is the lowest possible value of  $V_0$  such that  $M_2$  is working in sat. region.



$$100\mu A = \frac{200\mu N}{2} 10 [V - 0.7]^2$$

$$V - 0.7 = \sqrt{10}$$

$$V = 1V$$

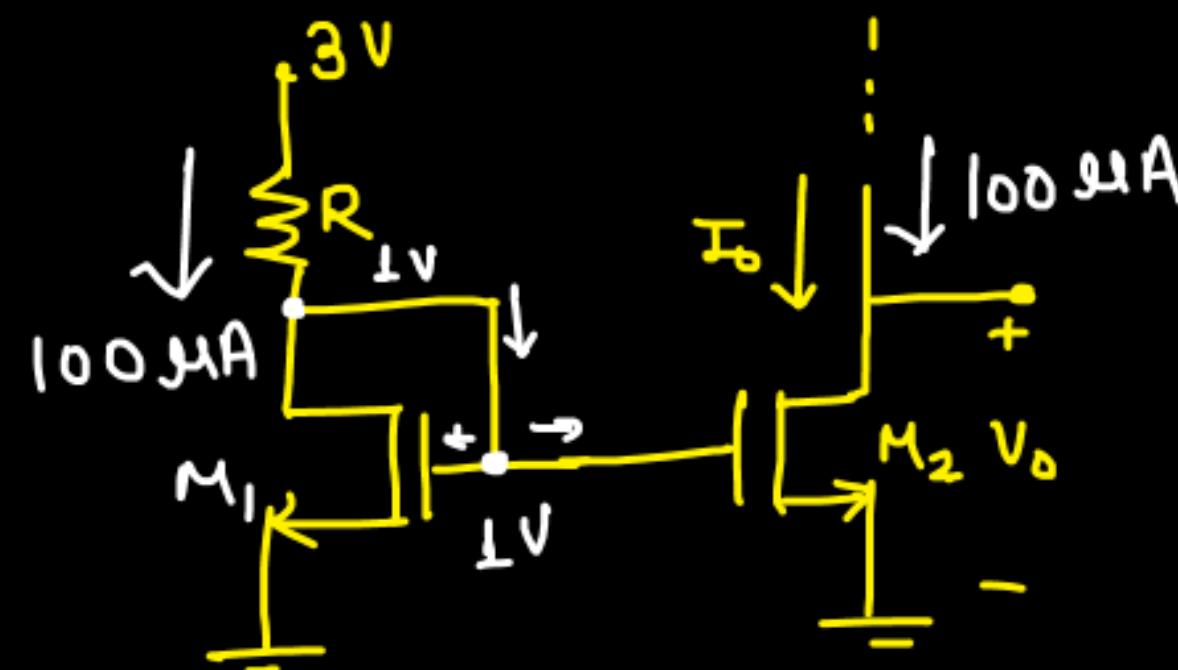

$$\frac{3-1}{R} = 100\mu A$$

$$R = 20k\Omega$$


ANS.

⇒ for sat. region

$$V_{DS} = V_{GS} - V_T$$

$$V_D = 1 - 0.7 = 0.3 \Rightarrow V_D = 0.3V$$

## ⇒ Building Multiple current sources:-

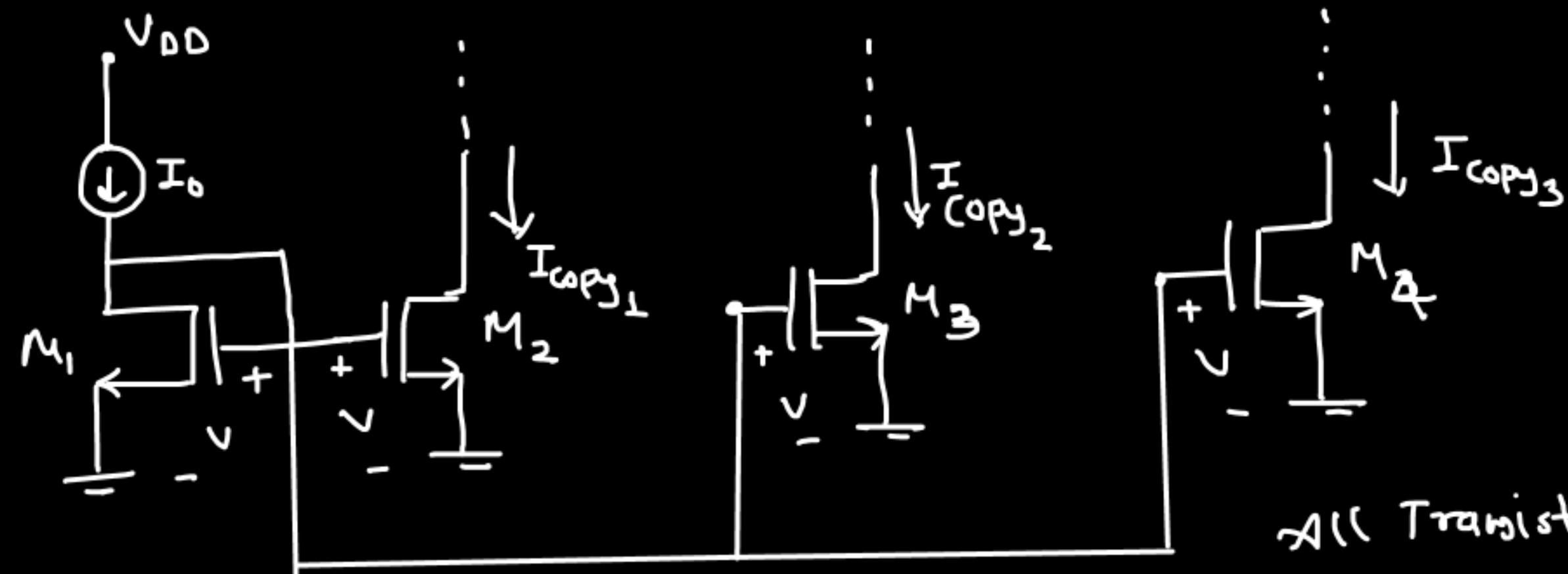


All Transistors are in sat.

$$I_{\text{copy}_1} = \frac{(w/L)_{M_2}}{(w/L)_{M_1}} I_0$$

$$I_{\text{copy}_2} = \frac{(w/L)_{M_3}}{(w/L)_{M_1}} I_0$$

Other way of showing the same cut:-

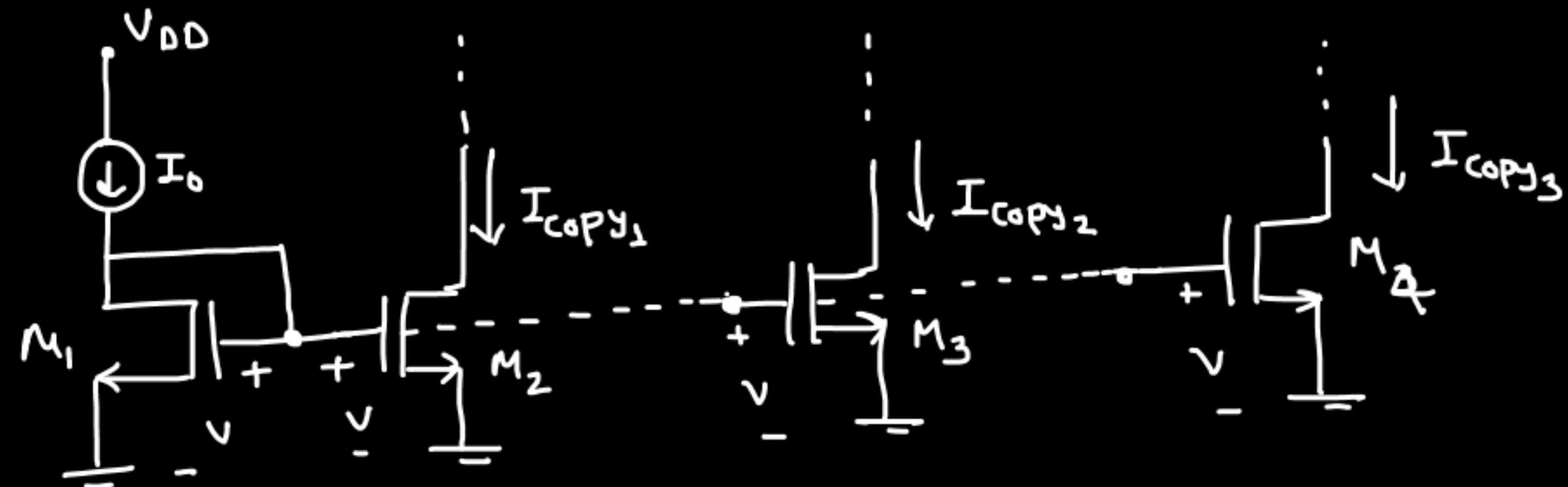

Q. Make a common source Amplifier (using NMOS)


with  $100\mu A$  current source in load. You have a reference current source of  $200\mu A$ .

You only have one supply  $V_{DD}$ .

Your small signal i(p)  $v_s$  has internal resistance  $R_S$ .


After designing the ckt, find the small signal voltage gain.

→

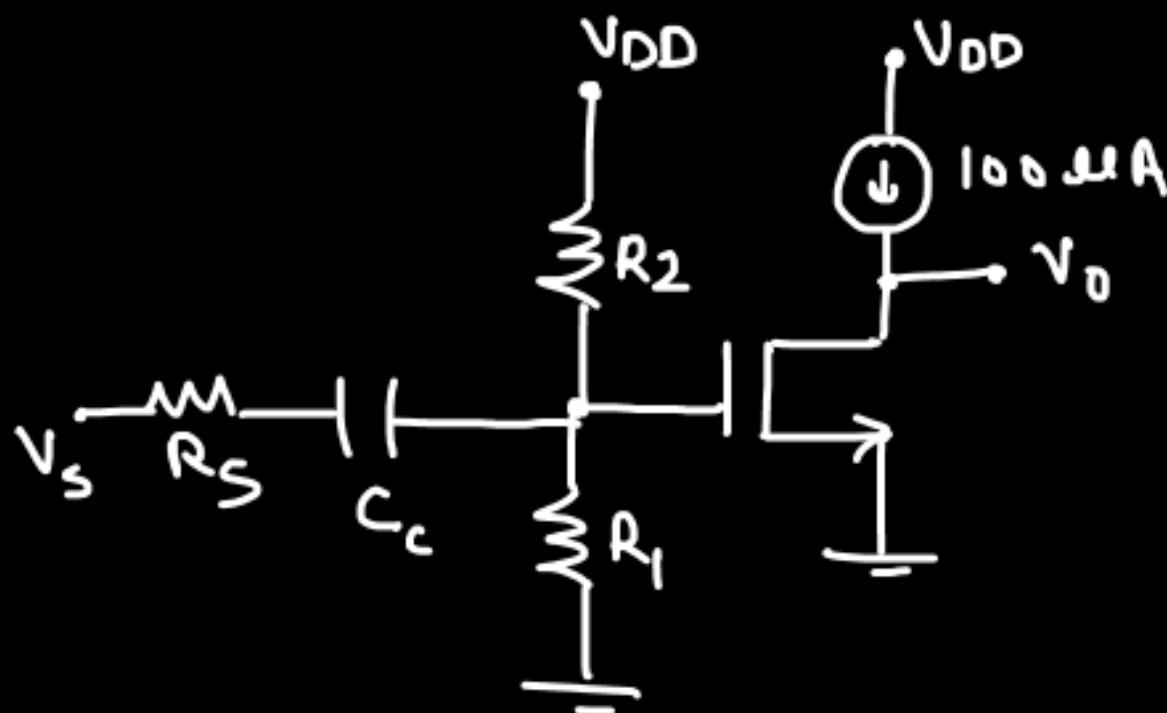


Next task:-

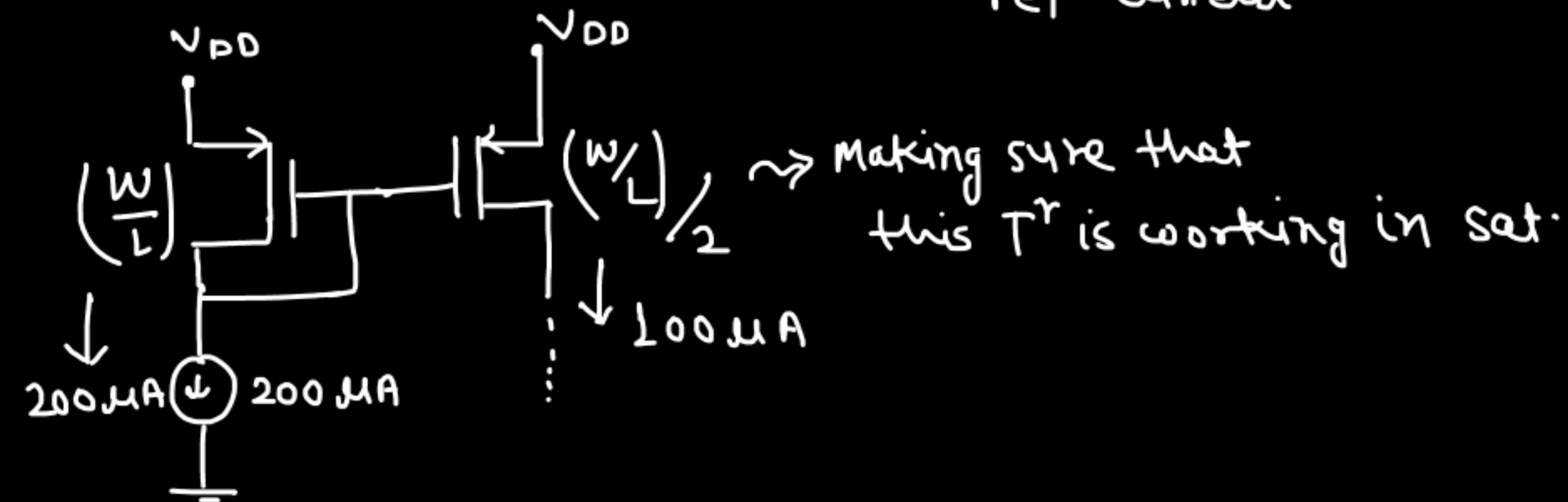designing 100 $\mu$ A current source from 200mA  
ref. current.






Final design :-

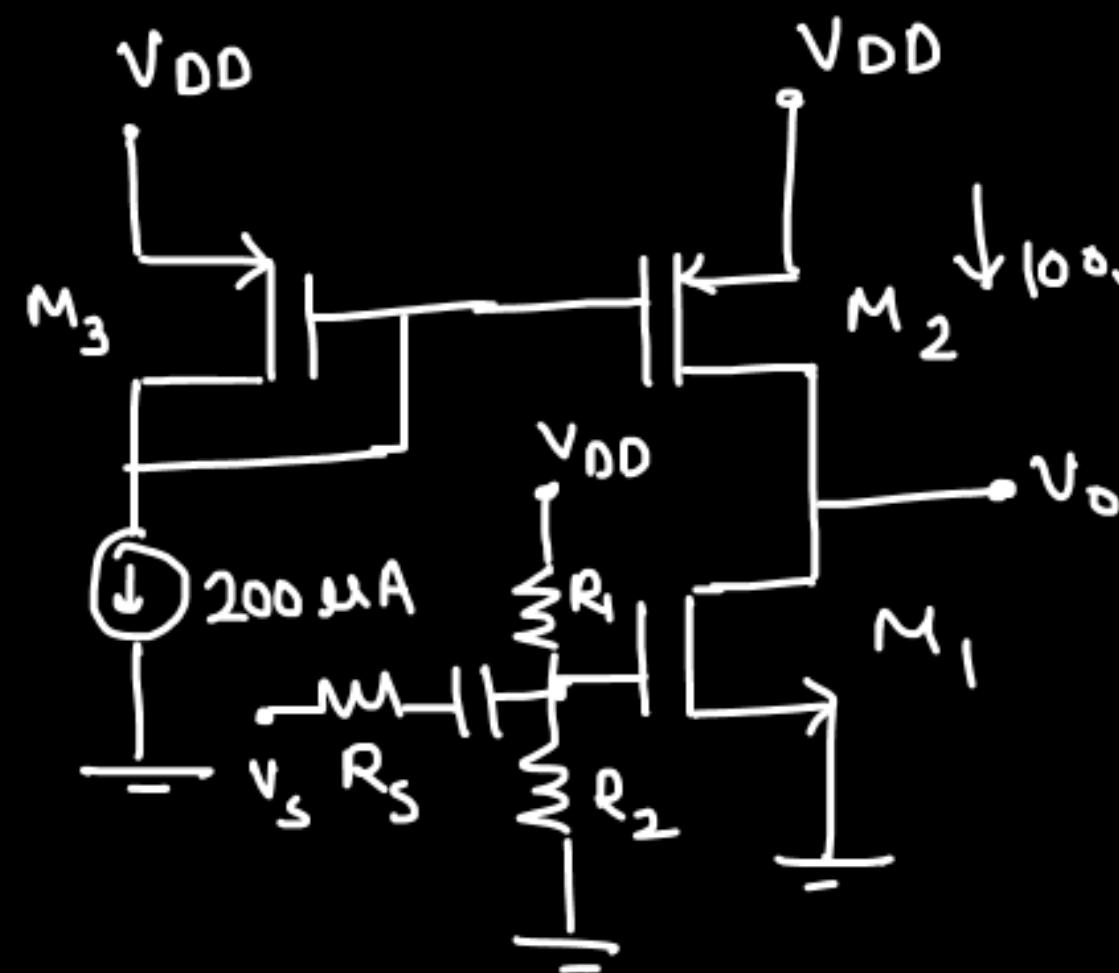

Adjust V<sub>DD</sub>, R<sub>1</sub>, R<sub>2</sub>  
such that all T's are  
working in sat.

$$\left(\omega_L\right)_3 = 2 \left(\omega_L\right)_2$$


Small signal Voltage gain :-

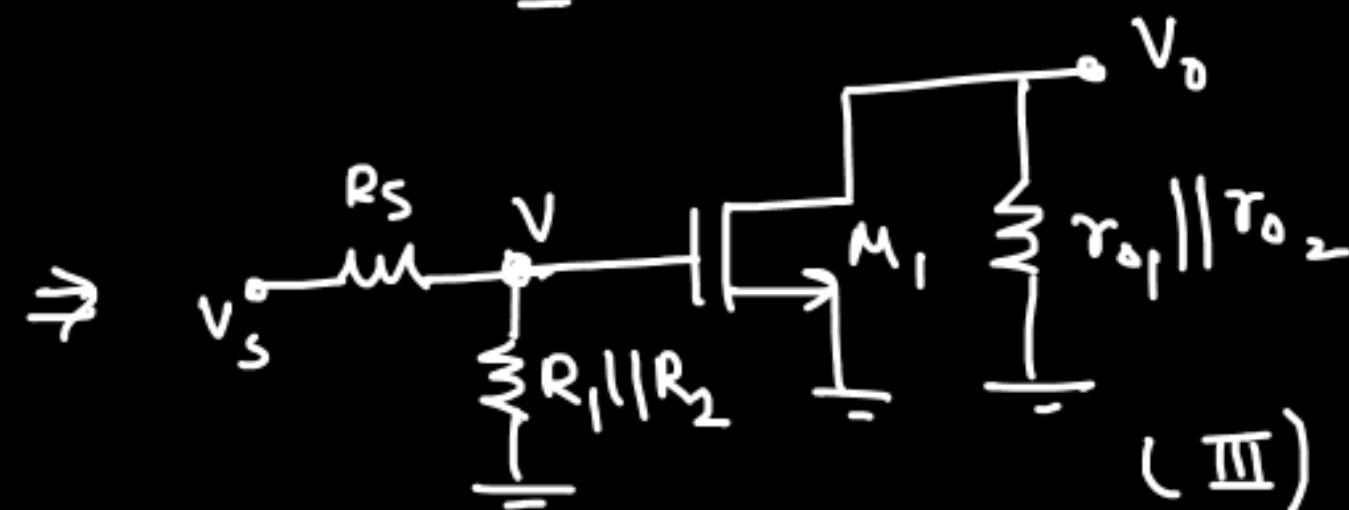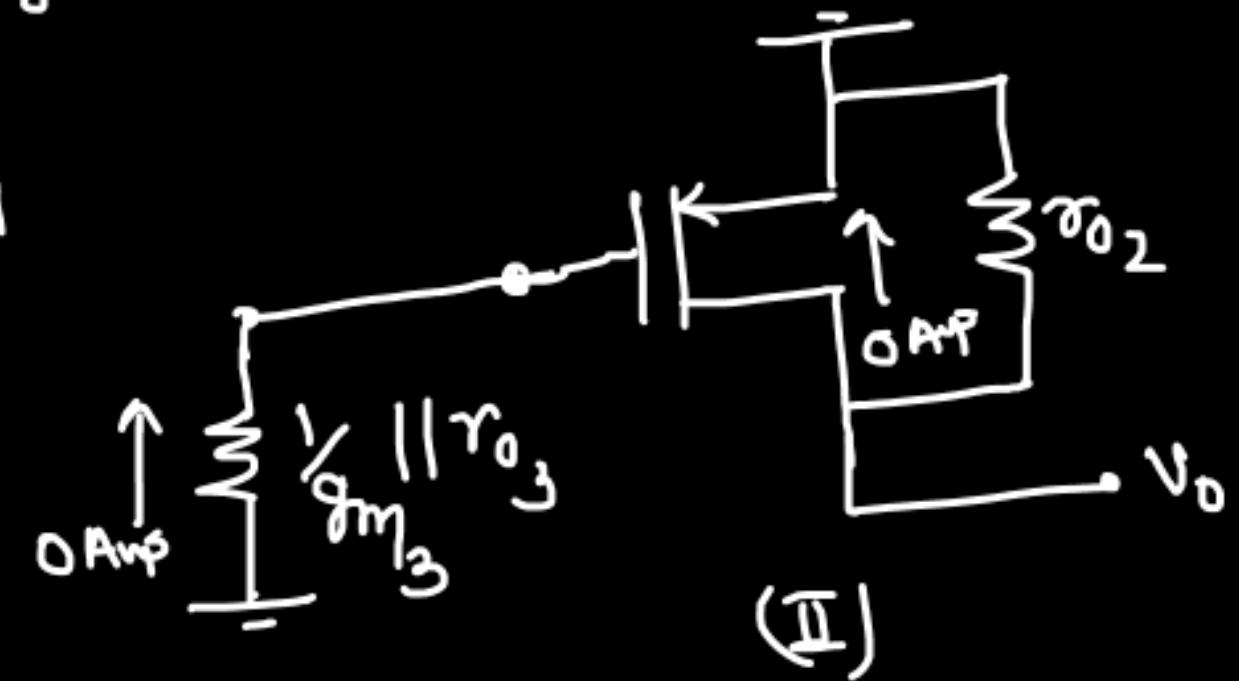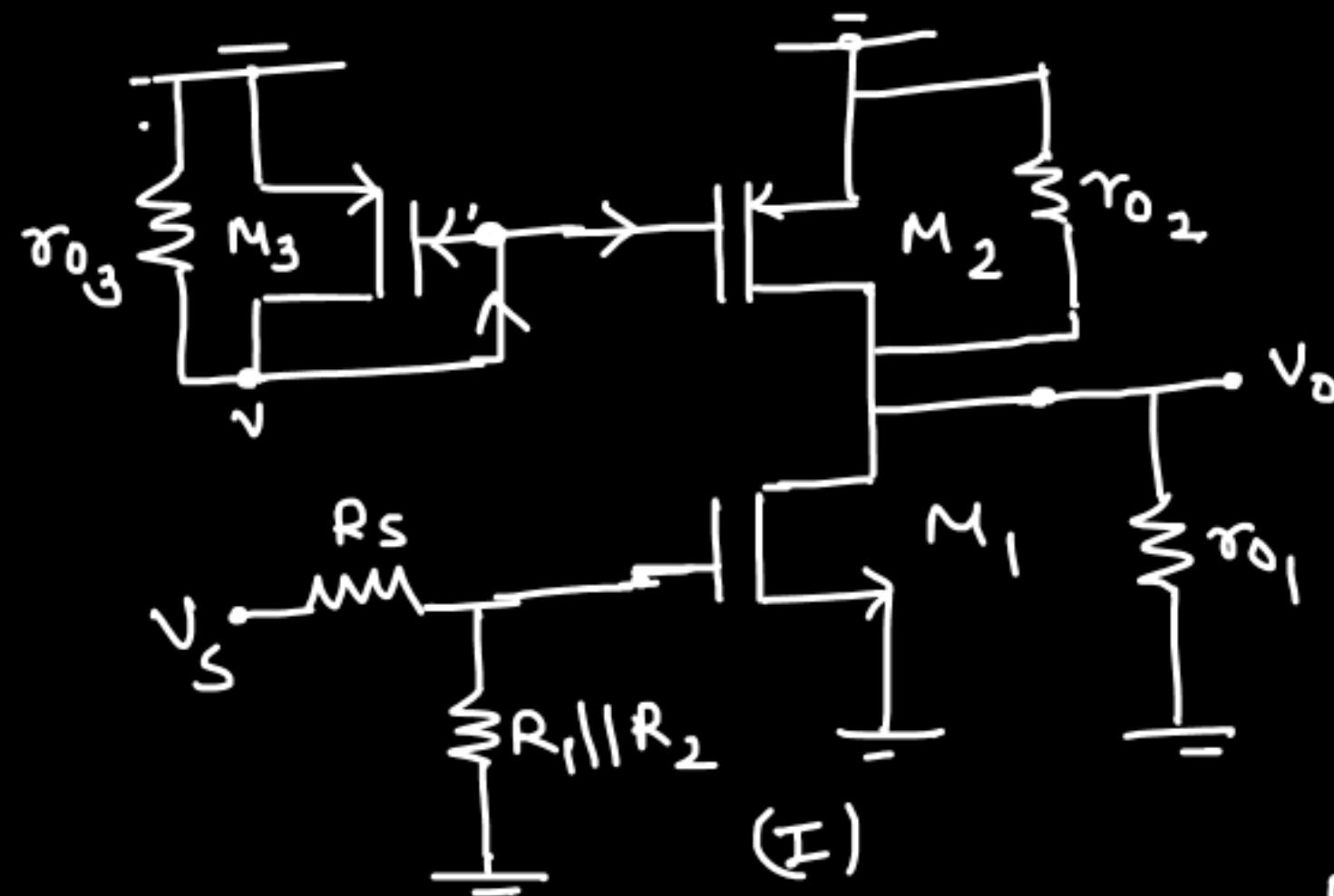

\*\*\*

$$\frac{V_o}{V_s} = -g_m [r_{o1} \parallel r_{o2}] \times \frac{(R_1 \parallel R_2)}{R_S + (R_1 \parallel R_2)}$$

M-II

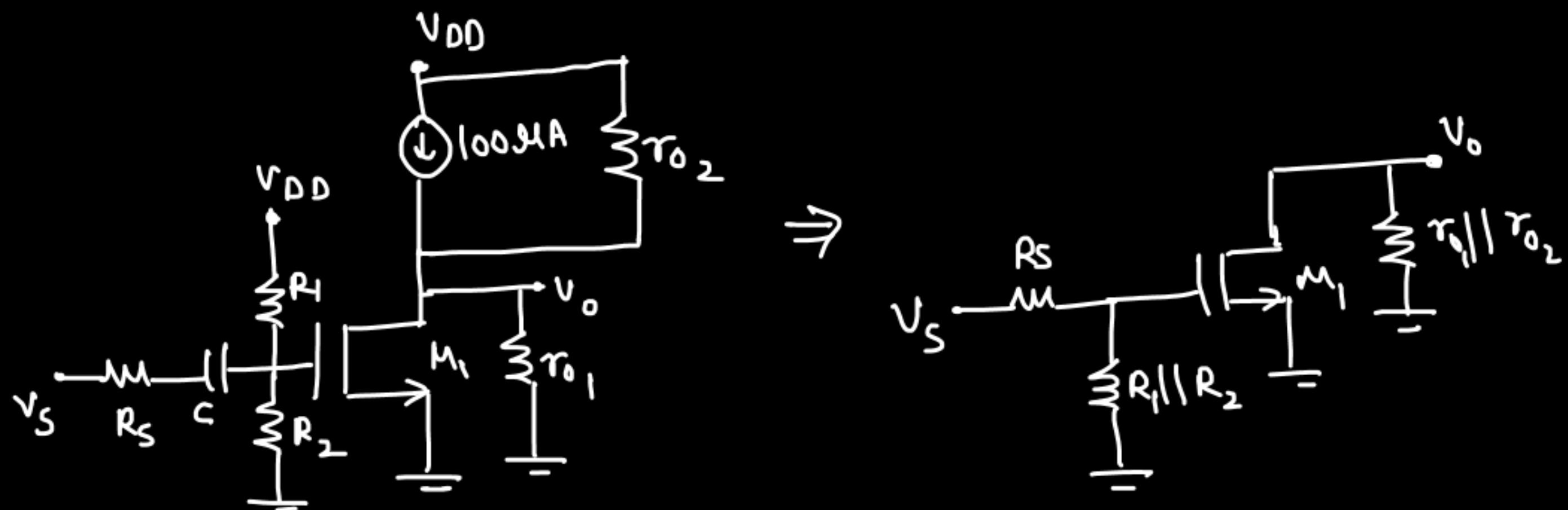


Q. Design a common drain amplifier (using NMOS)  
with  $100\mu A$  current source in load.

You have a reference current source of  $200\mu A$ .


[Note:- All the available transistor have same  $w_L$  ratios.]

→

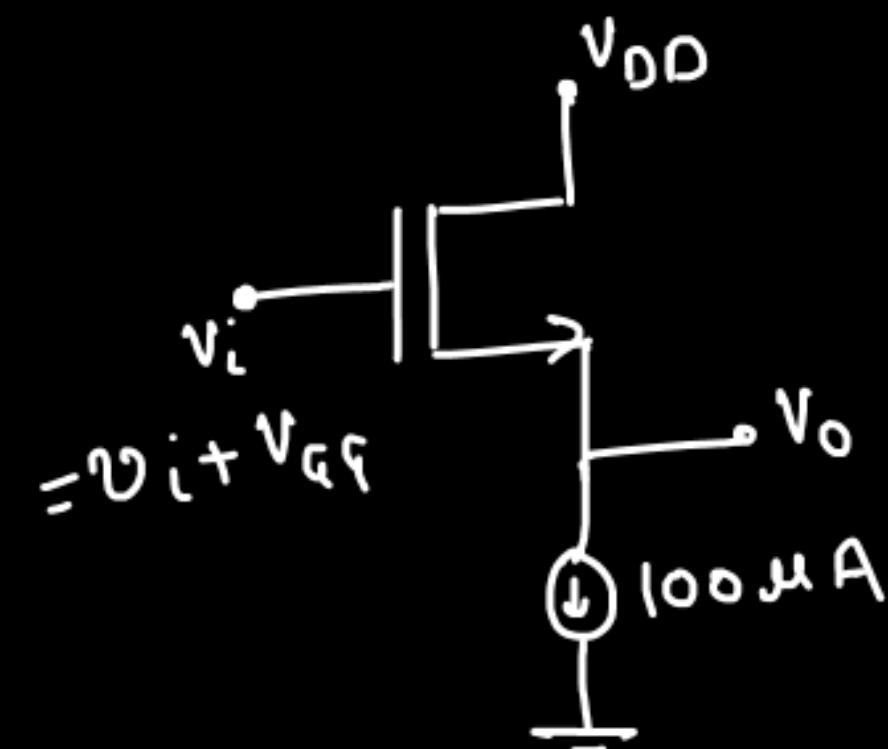


Task:-


designing 100  $\mu$ A current source:-

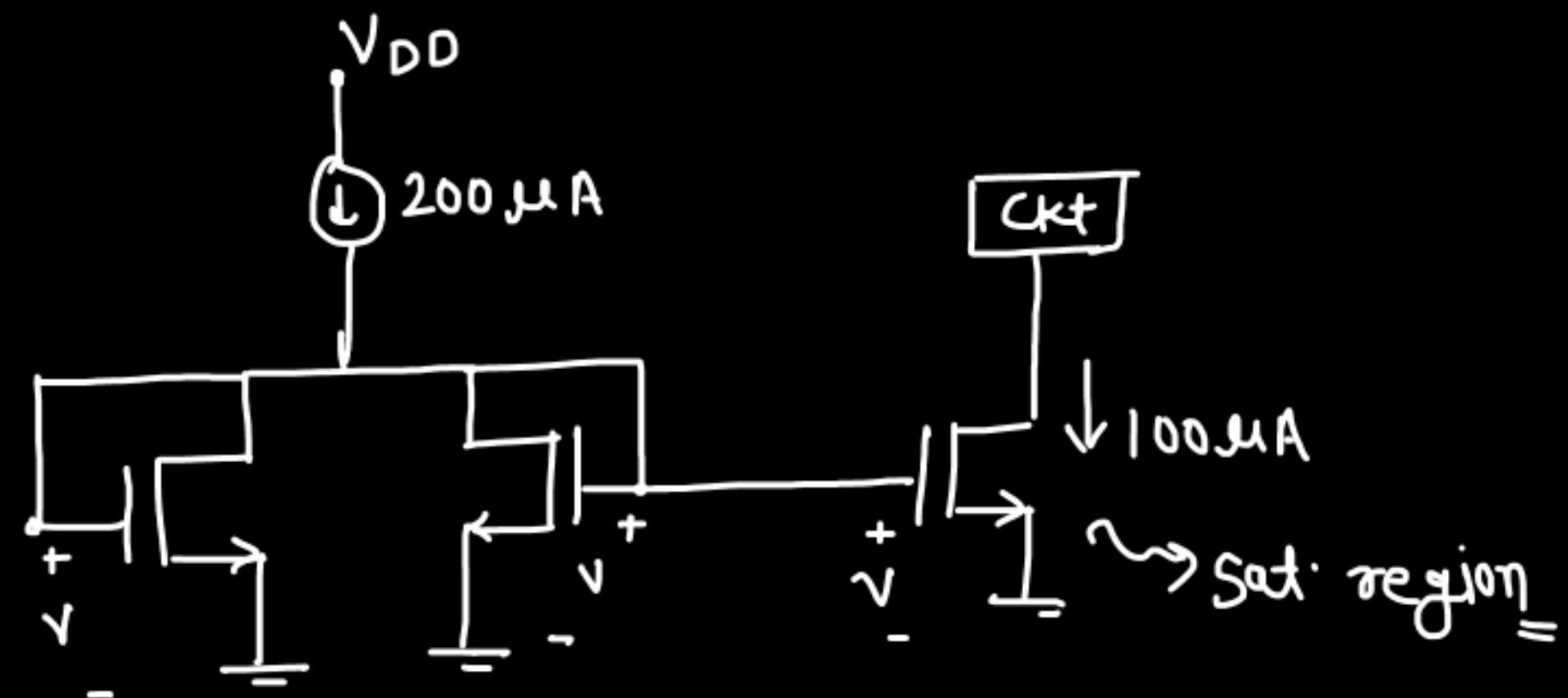

final design:-

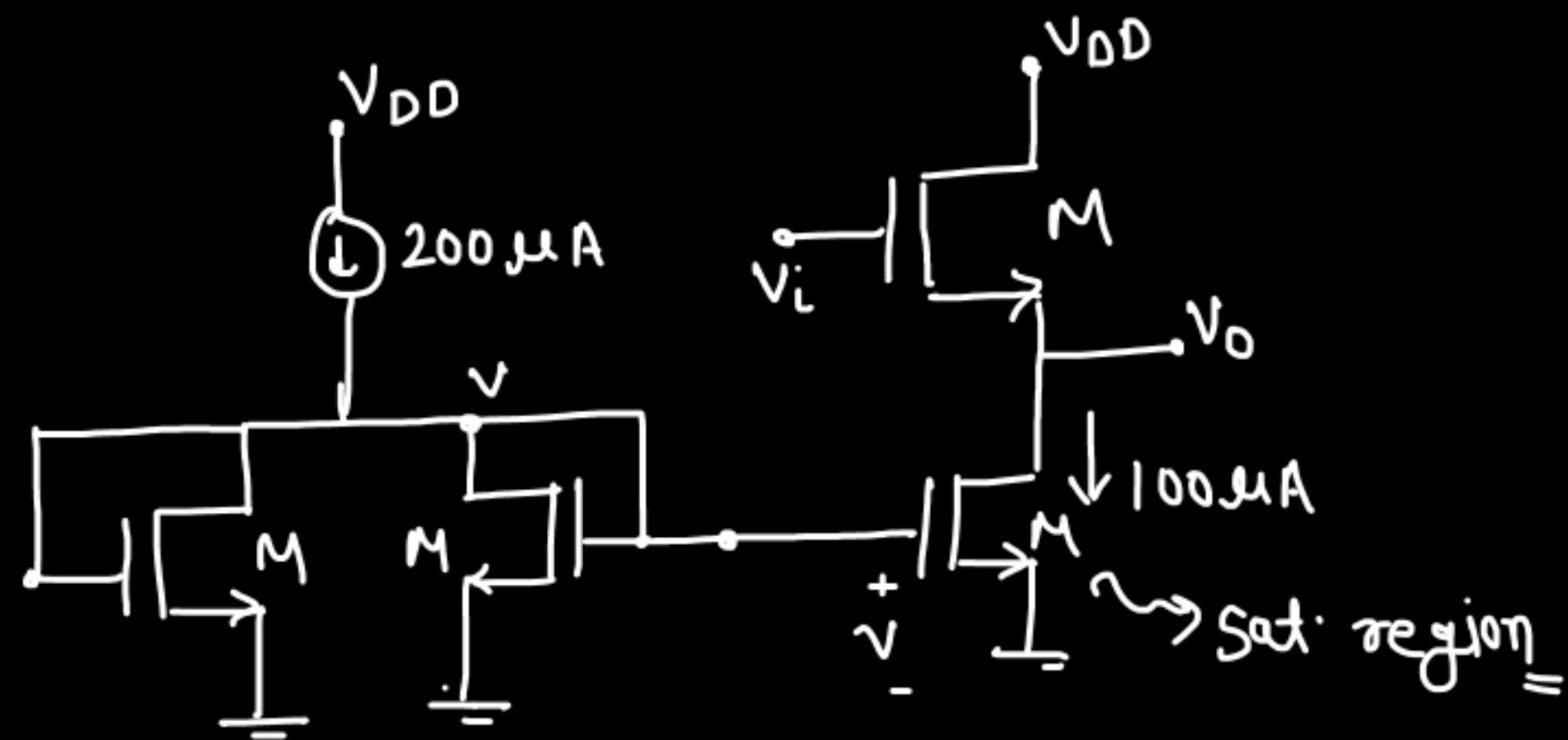

## small signal analysis:-

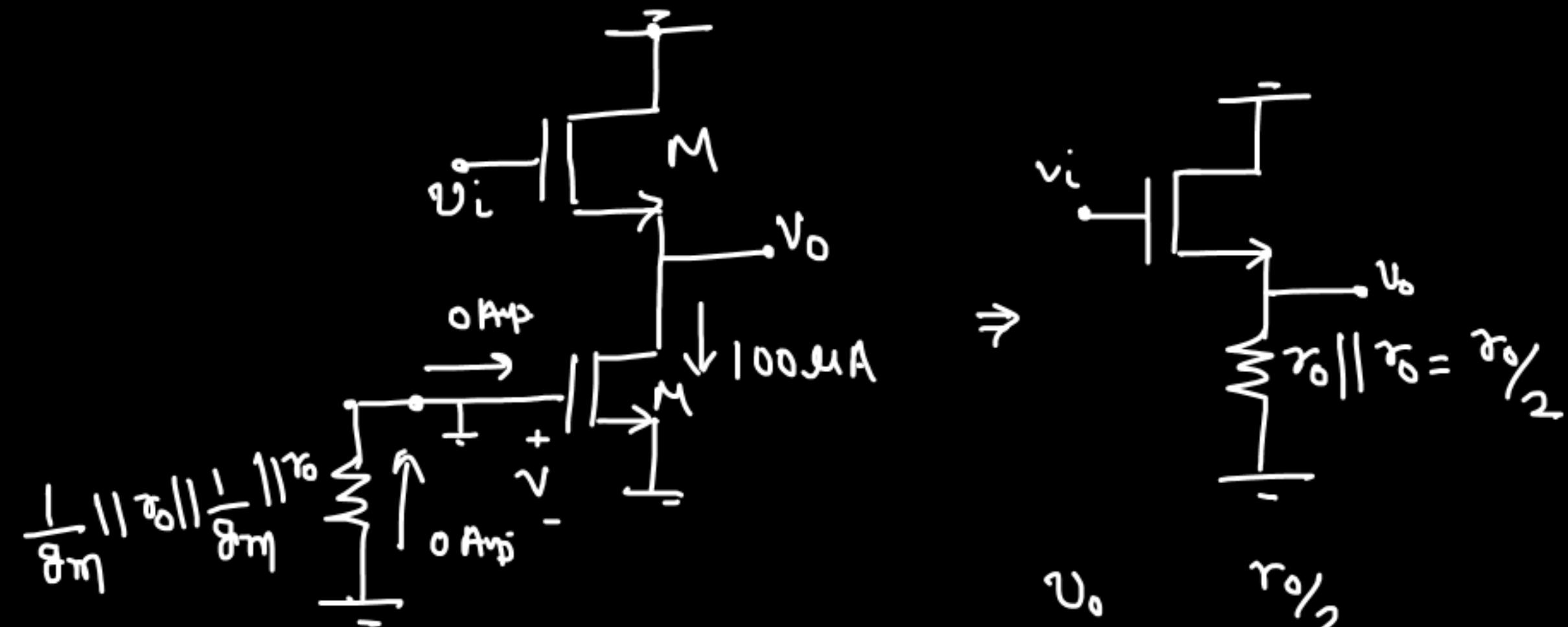


$$\frac{v_o}{v_i} = \frac{r_o/2}{1/g_m + r_o/2}$$




Ans

$$\frac{v_o}{v_i} = \frac{g_m r_o}{2 + g_m r_o}$$

Conclusion :-

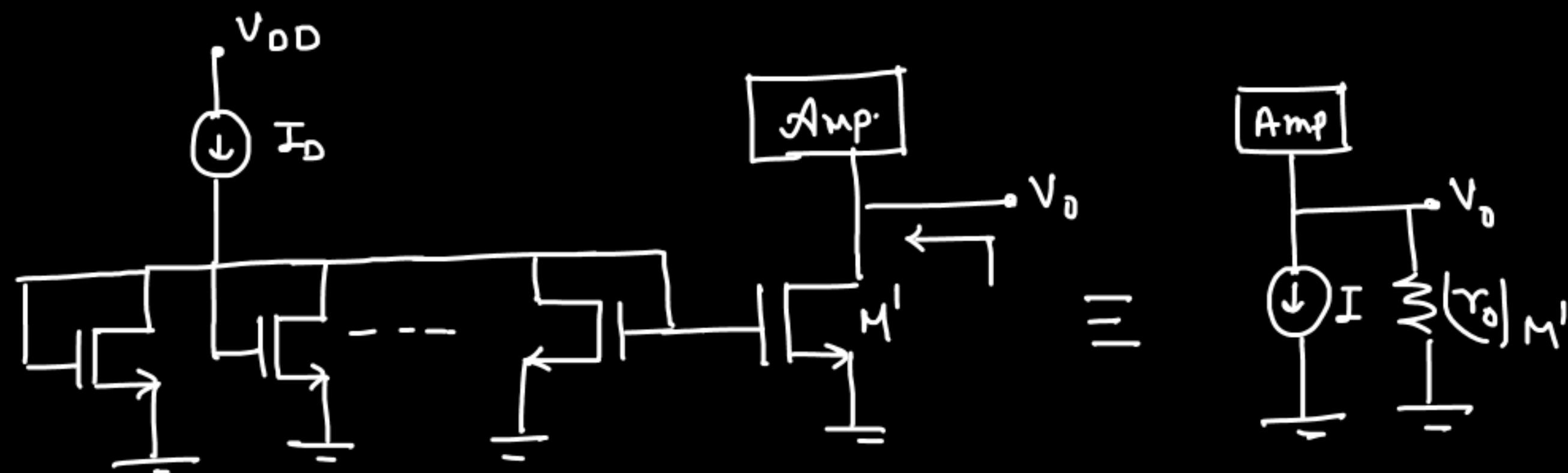

N.B. →

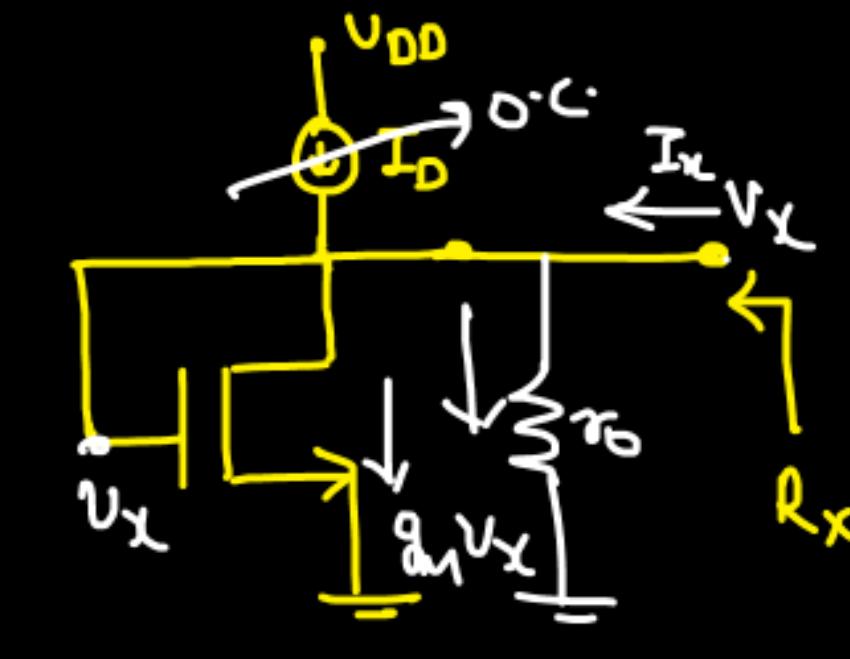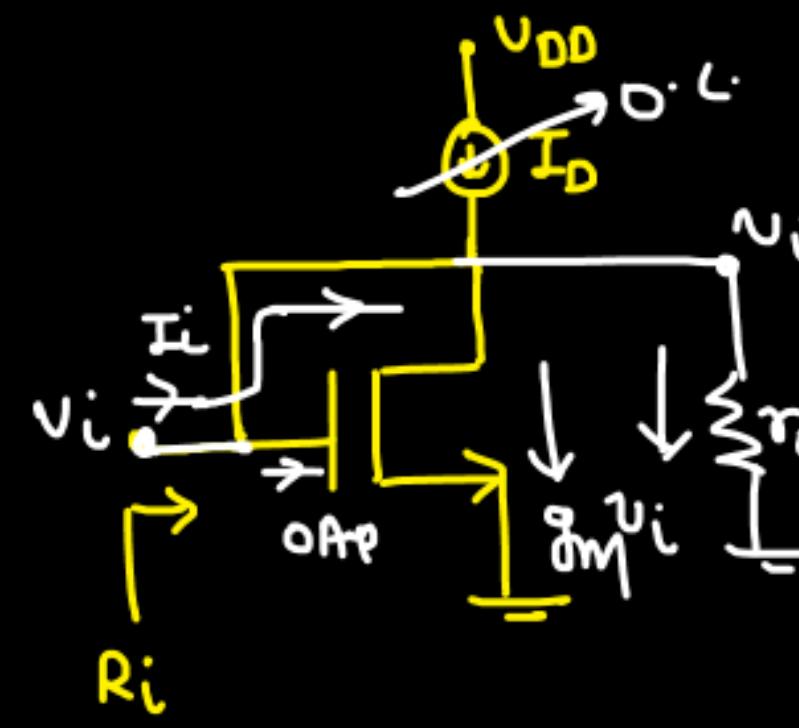
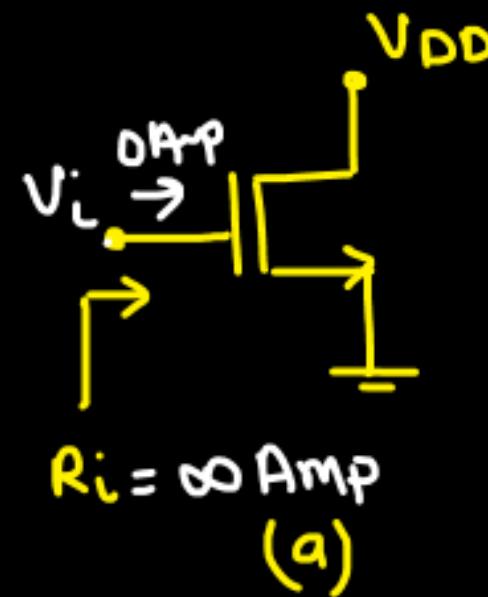


$$I_i = g_m V_i + \frac{V_i}{r_0}$$

$$\frac{V_i}{I_i} = R_i = \frac{1}{g_m} || r_0$$


$$\frac{V_x}{r_0} + g_m V_x = I_x$$

$$\frac{V_x}{I_x} = R_x = \frac{1}{g_m} || r_0$$

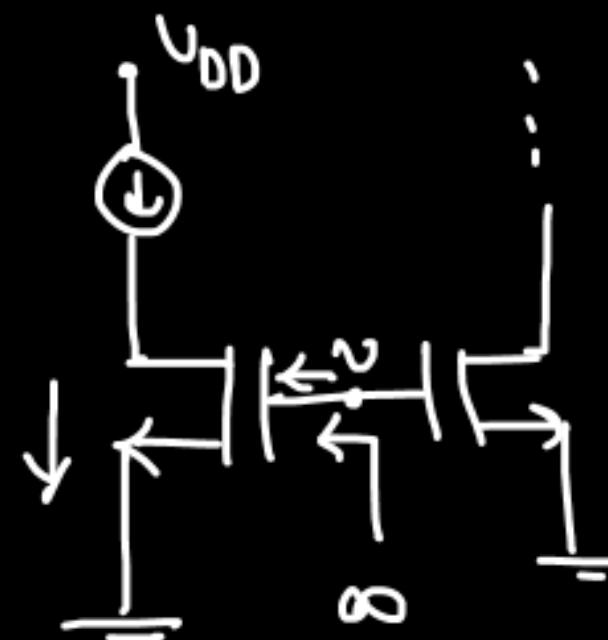
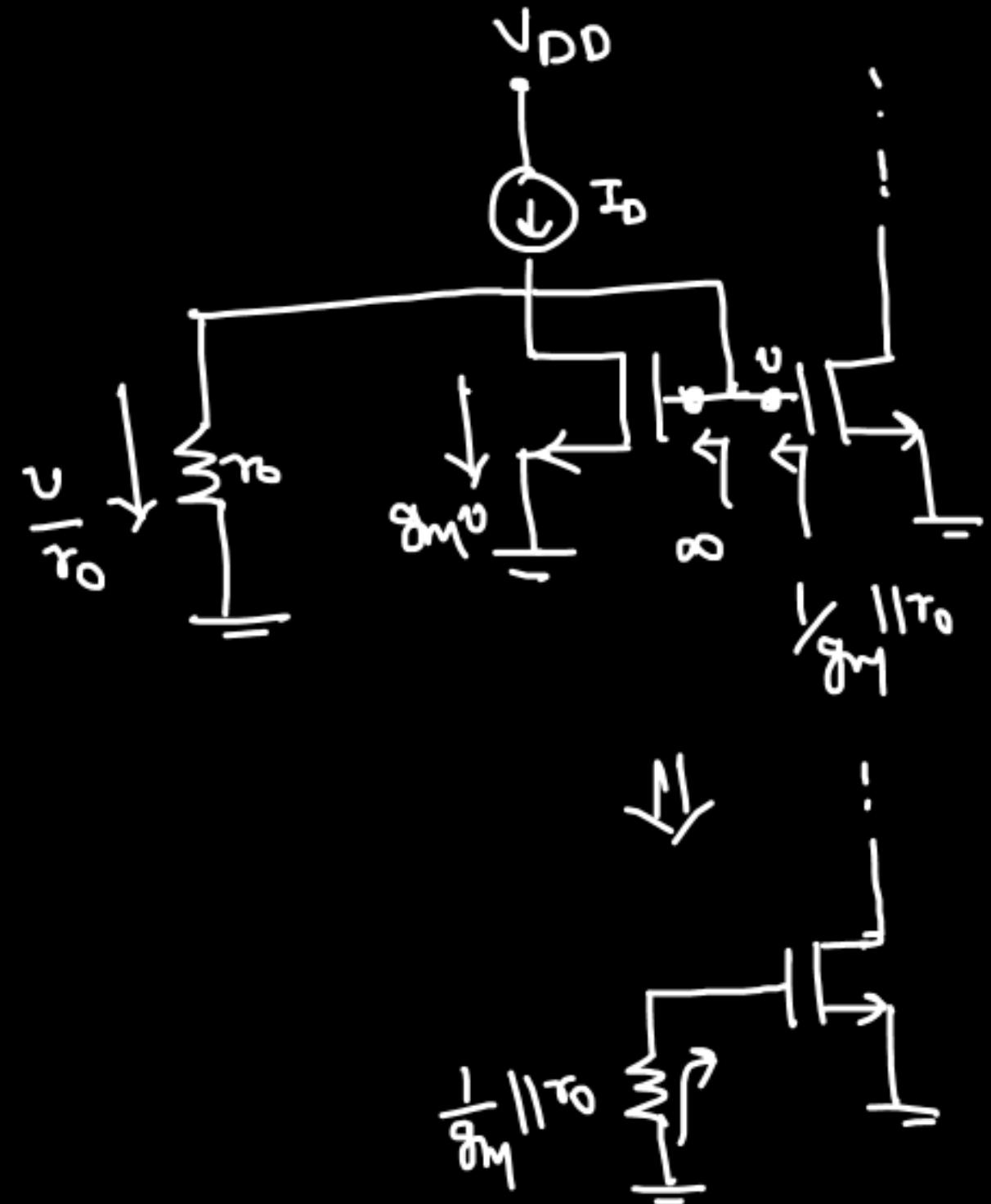




## Assignment - 8

Q.

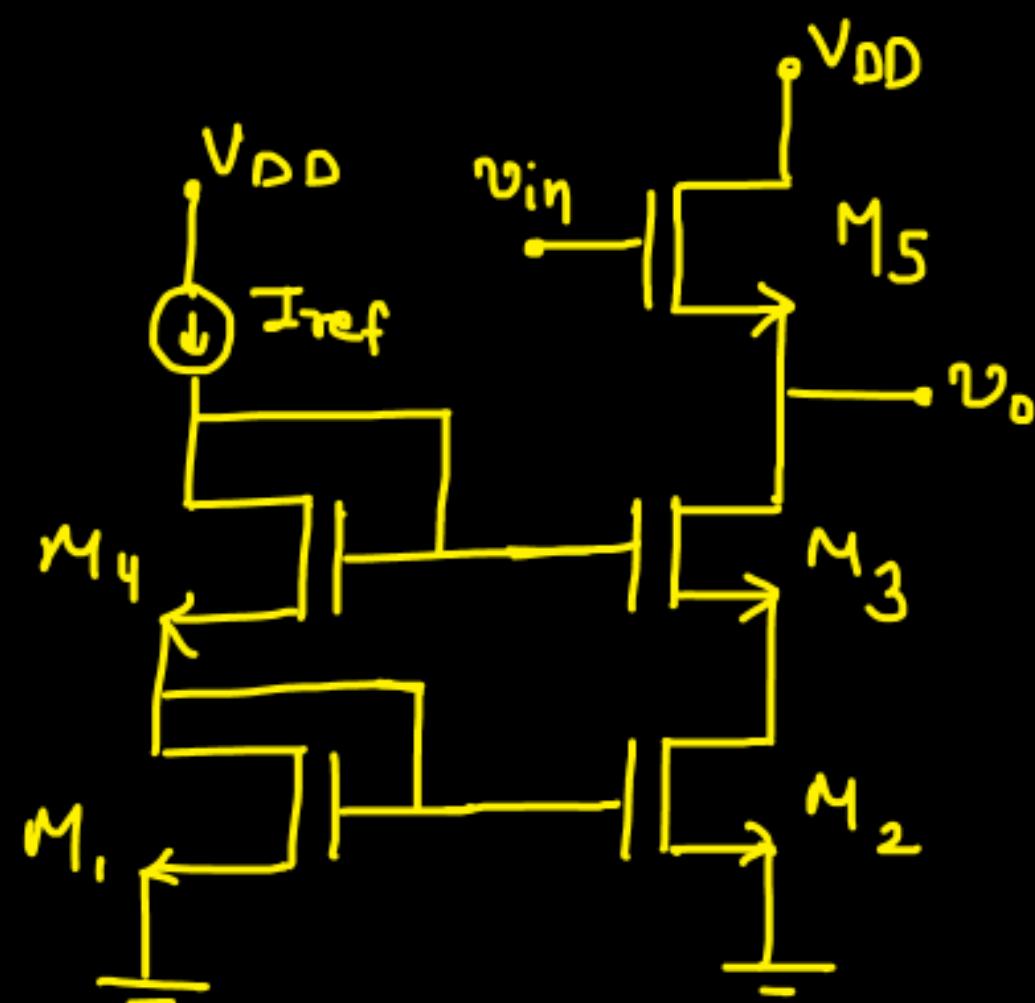

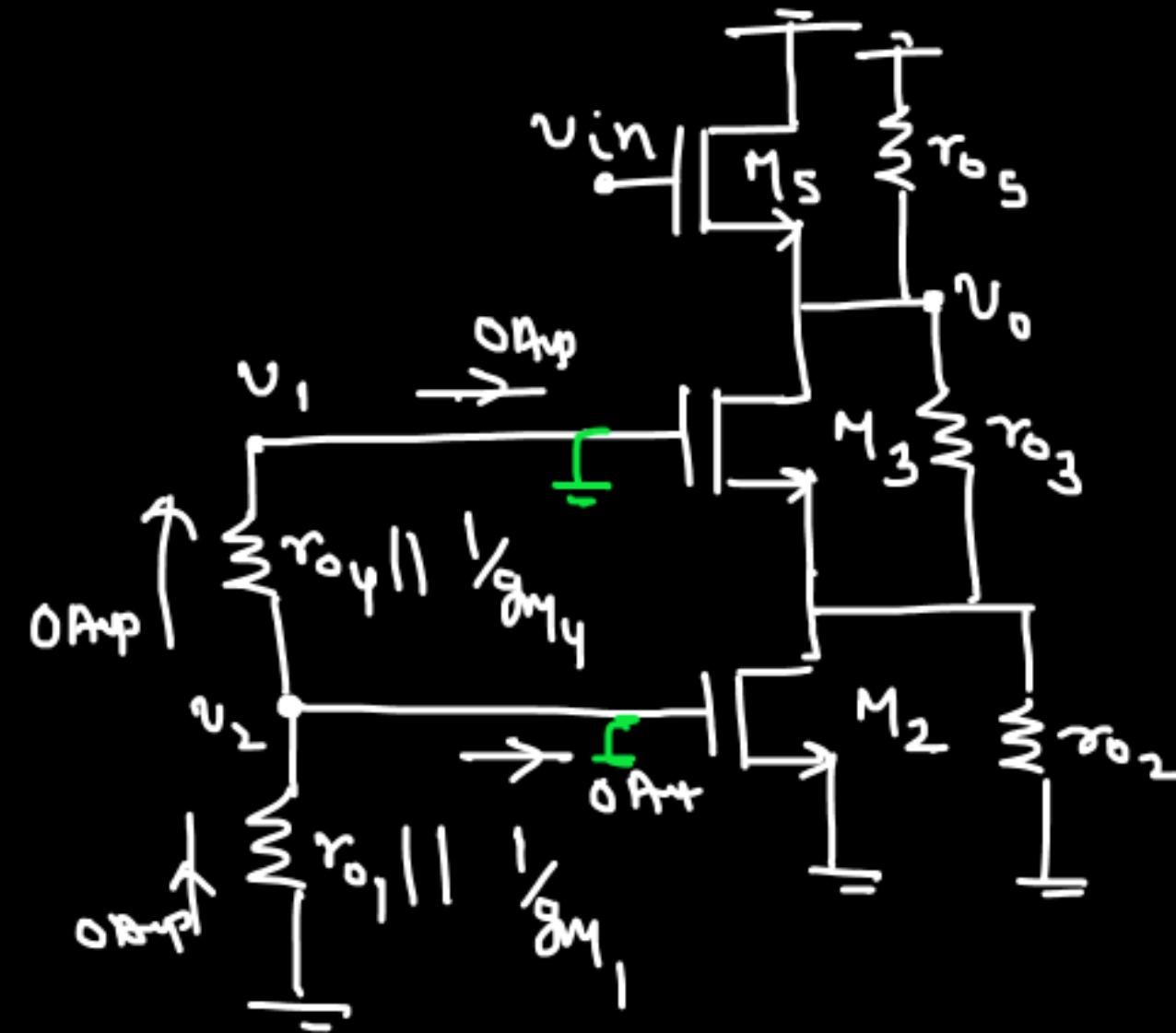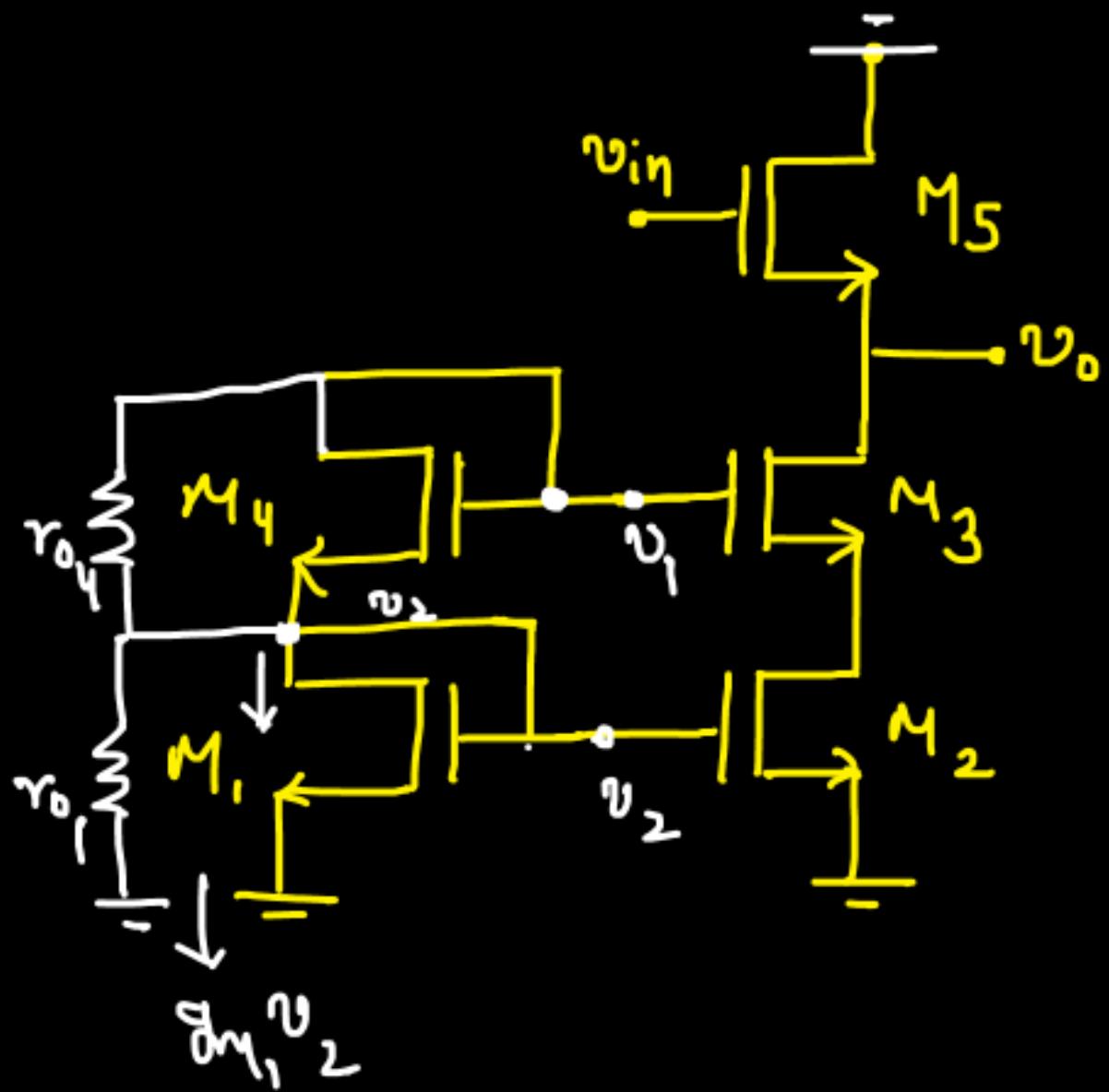Find small signal  
Voltage gain  $\frac{v_o}{v_i}$  ?




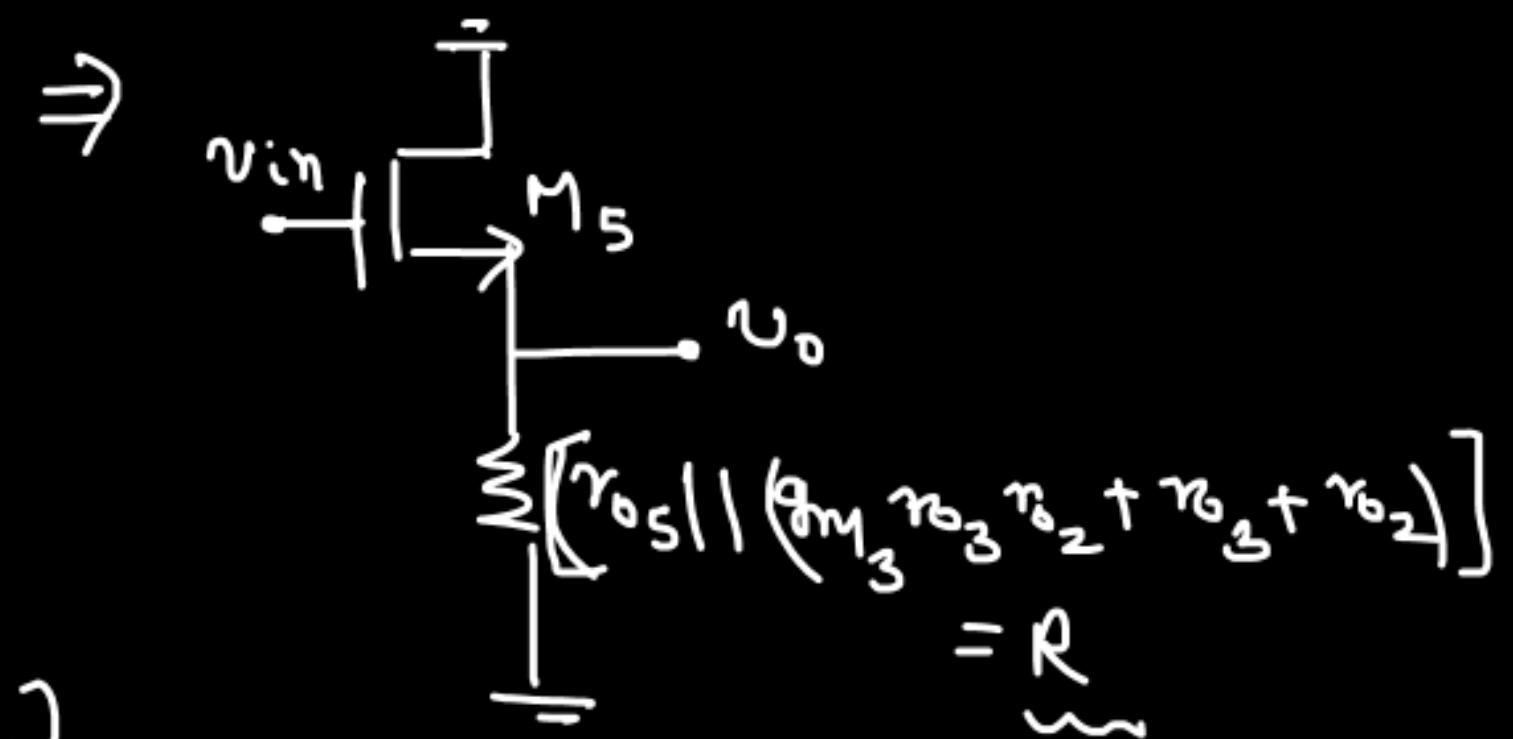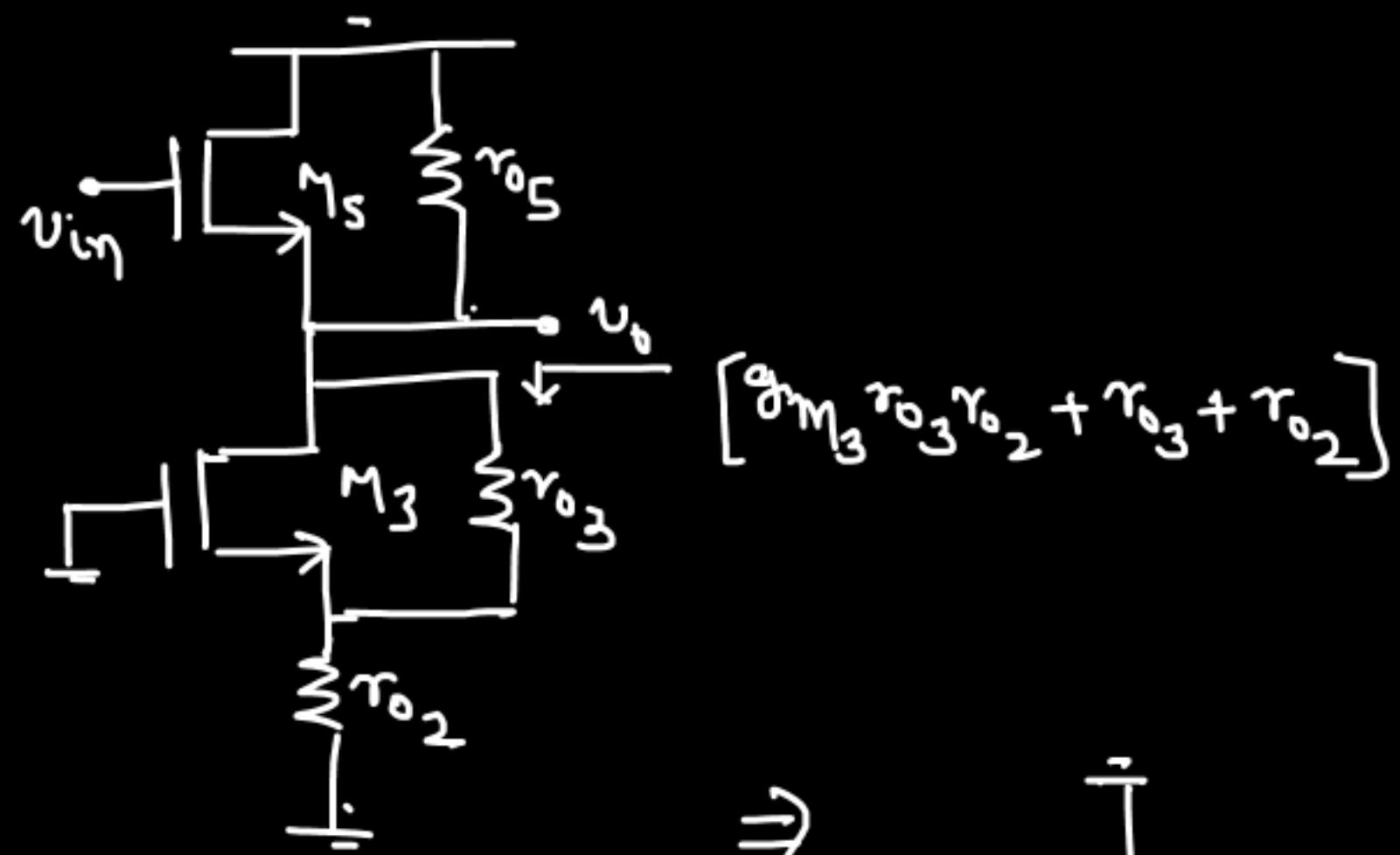

$$\frac{u_o}{v_{in}} = \frac{g_m M_5 R}{1 + g_m M_5 R}$$

$$R = r_{o5} \parallel (g_m M_3 r_{o3} r_{o2} + r_{o3} + r_{o2})$$

Q.

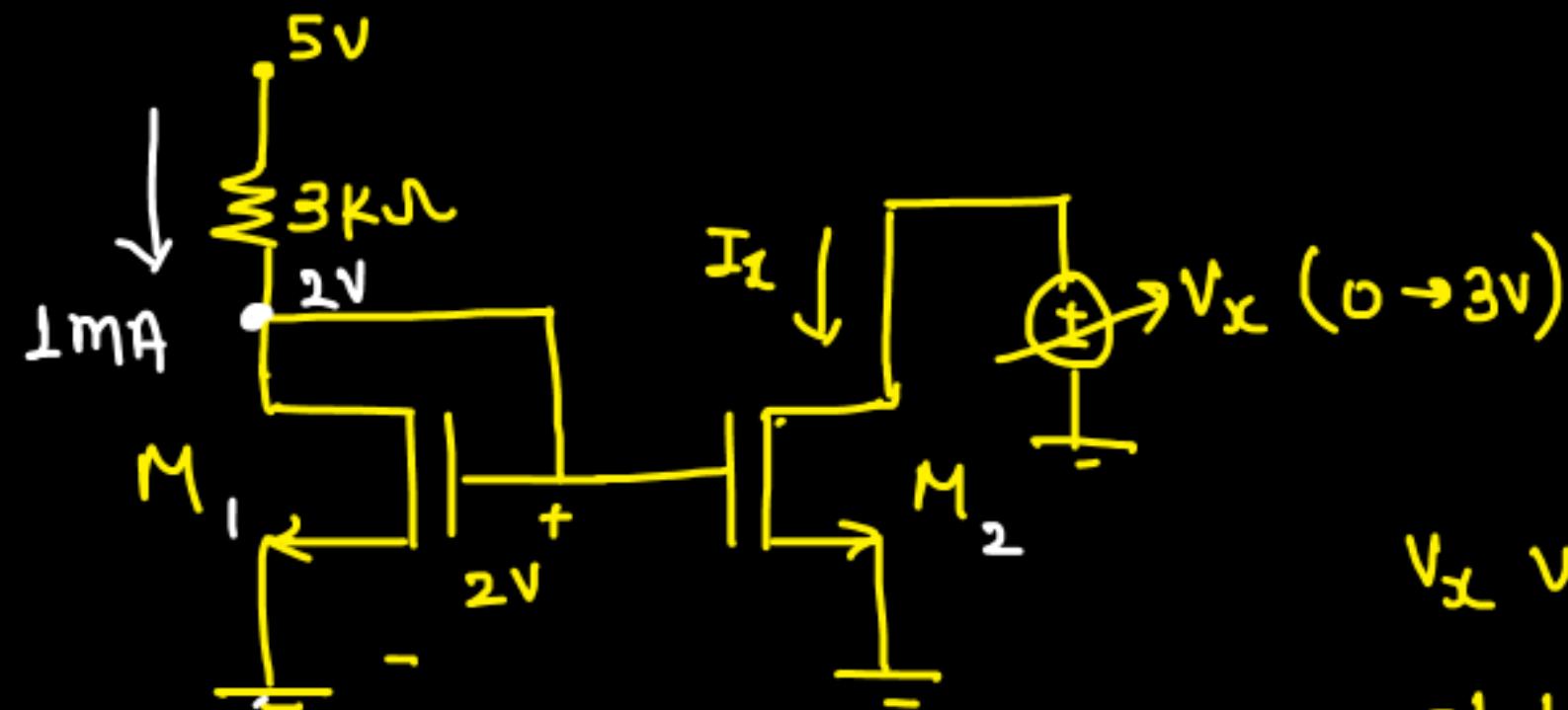

$$V_T = 1V$$

$V_x$  value is swept from  $0 \rightarrow 3V$ .  
plot  $V_x$  v/s  $I_x$ .

$$I_x = I_{MA} \quad [\text{when } M_2 \text{ is in sat.}]$$

$$V_x > 2 - 1 \Rightarrow V_x > 1V \Rightarrow M_2 \text{ is in sat}$$




$$I_x = I_{MA} \leftarrow M_1 \text{ & } M_2 \text{ are in current mirror}$$


$$\text{For } V_x > 1V \Rightarrow I_x = 1\text{mA}$$

For  $V_x < 1V \Rightarrow M_2$  is in linear region

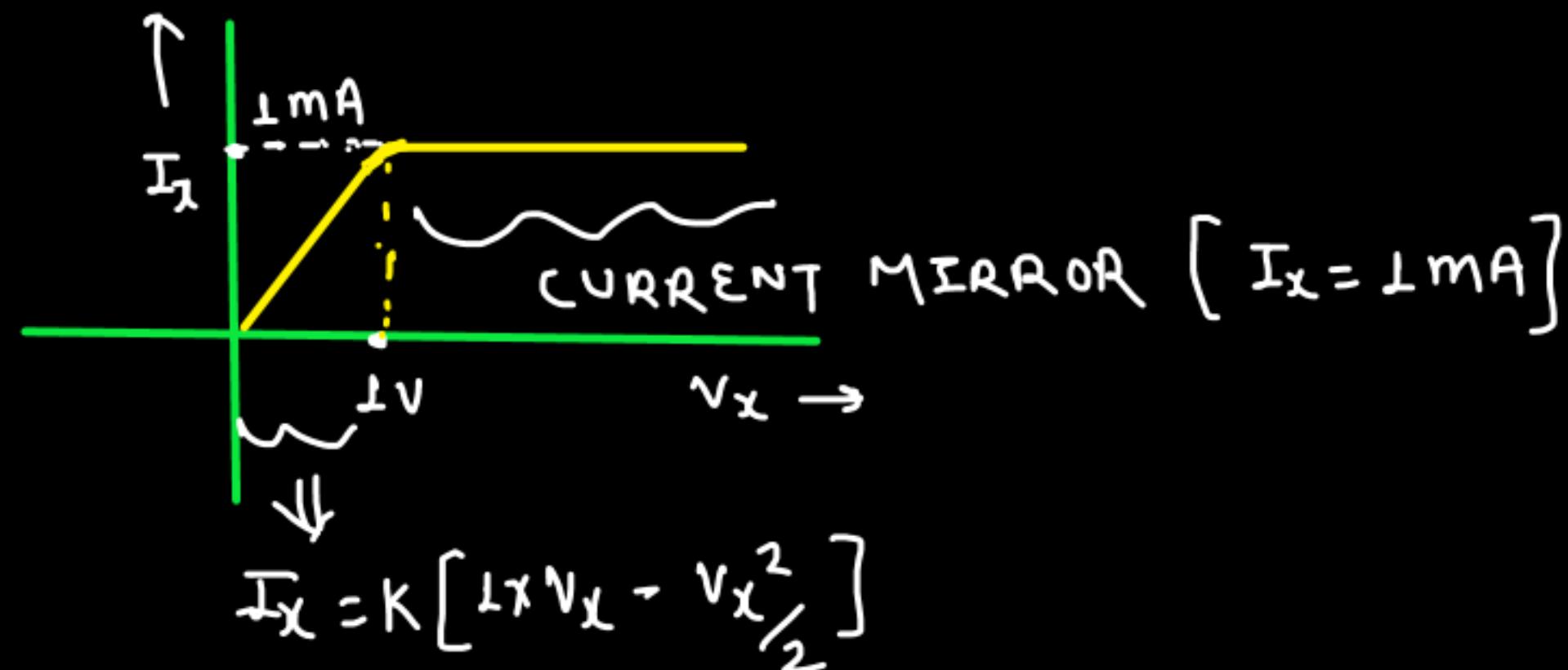current in linear region < current in sat. region  
(for fixed  $V_{Q_S}$ )




Q.

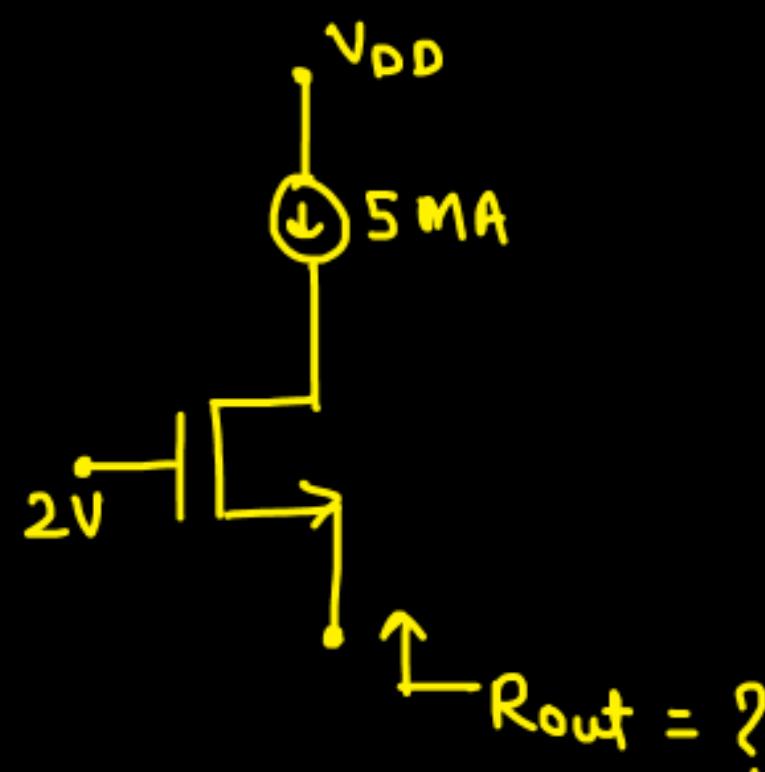


Find  $R_{out}$  for  $\lambda=0$ ,  $\lambda \neq 0$

$\Rightarrow \lambda=0$

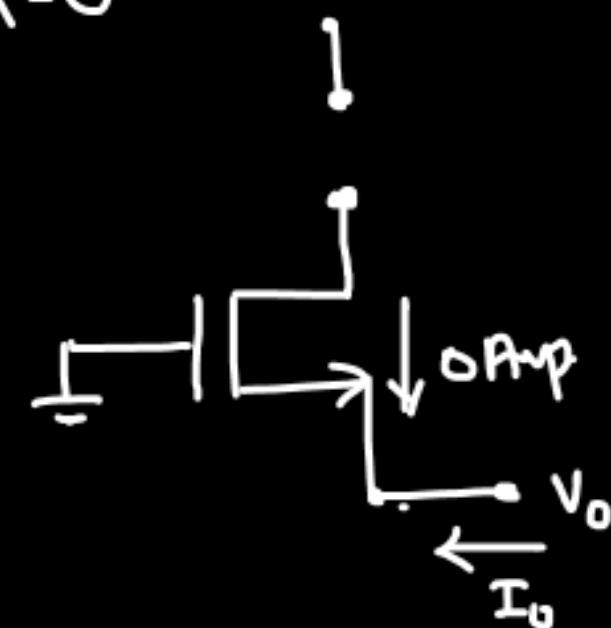

$$R_{out} \equiv \frac{V_o}{I_o} = \infty$$


$\lambda \neq 0$

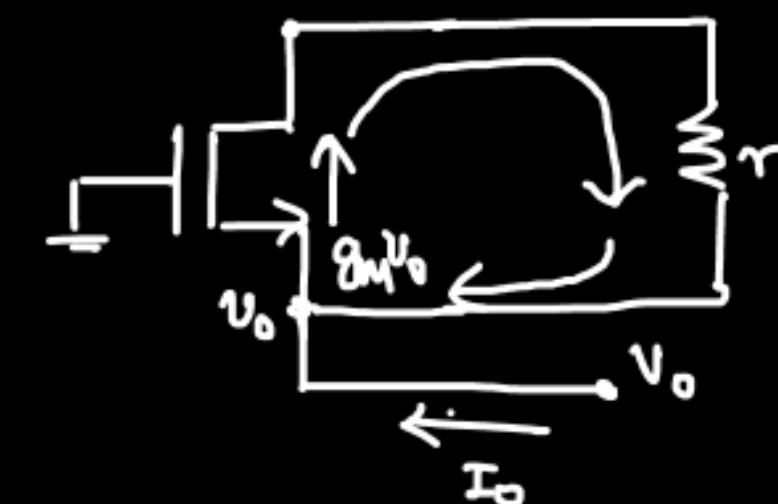

$$I_o = 0 \text{ Amp.}$$

$$R_o = \infty$$

Q.

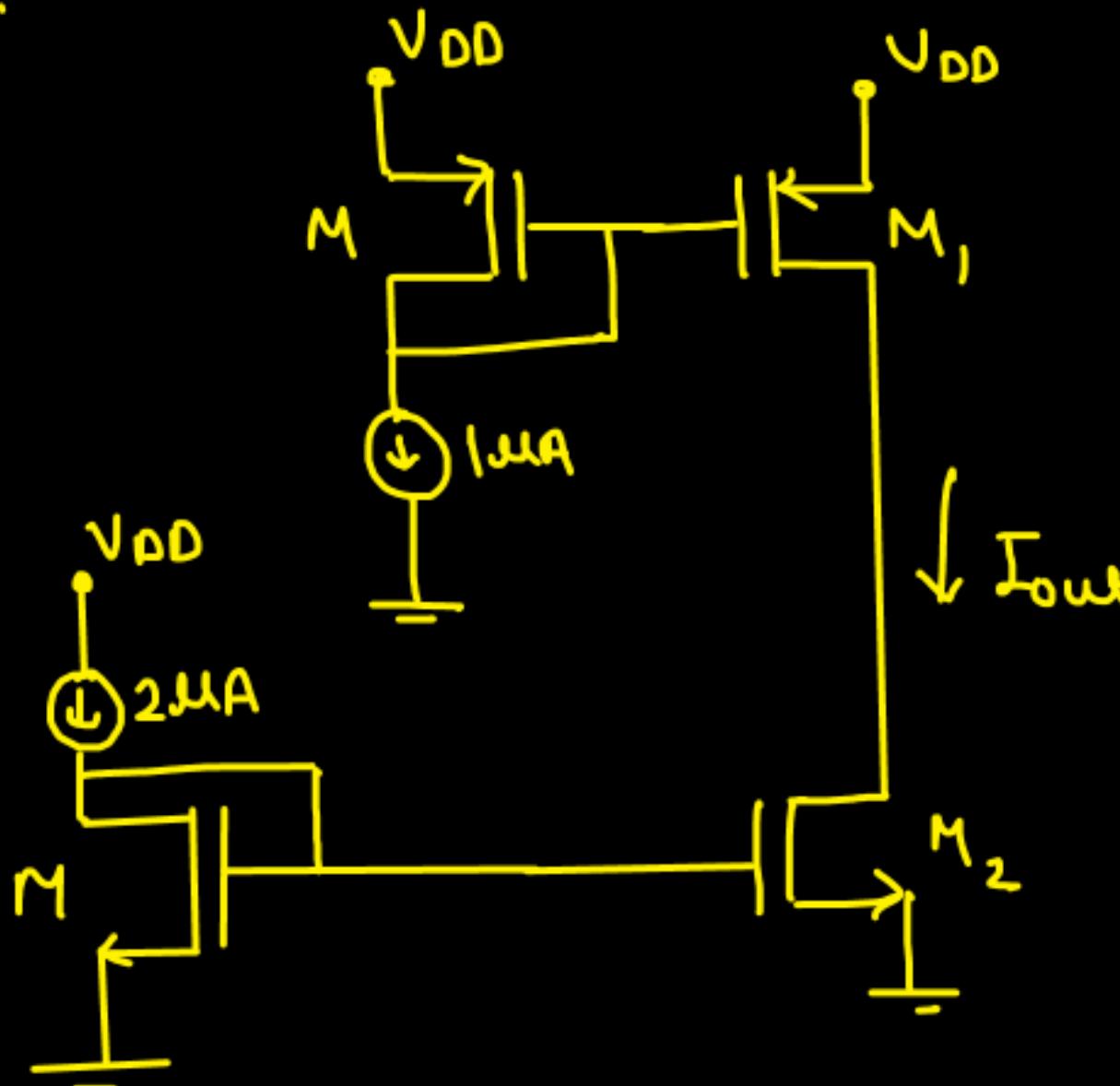

all Tr are identical.

Find I<sub>out</sub> ?

⇒ if M and M<sub>2</sub> are in c.M. ⇒ I<sub>out</sub> = 2 μA

if M and M<sub>1</sub> are in c.M. ⇒ I<sub>out</sub> = 1 μA

I<sub>out</sub> = 2 μA = 1 μA → NOT POSSIBLE

⇒ There will be only one current mirror working.

⇒ one of M<sub>1</sub> or M<sub>2</sub> will go into triode region and not in sat.

Let  $M_2$  is in sat. and  $M_1$  is in Triode.

$$I_{out} = 2\text{mA}$$



Same current is flowing through  $M_1$

[ if  $M_1$  was in sat., what is the max current it can take?  $\rightarrow 1\mu\text{A}$  ]

$\Rightarrow M_1$  can take max  $1\mu\text{A}$  current, but here even in Triode region, it's taking  $2\text{mA}$  current  $\Rightarrow$  which is not possible

$\Rightarrow$  Assumption is wrong

Let  $M_1$  is in sat.,  $M_2$  is in Triode

$$I_{out} = 1 \mu A$$




Same current is taken by  $M_2$

[ $M_L$  can drive max<sup>m</sup> current of  $2 \mu A$  in sat. so, it  
can certainly take  $1 \mu A$  current in Triode region]

$\Rightarrow$  Assumption is correct

$$I_{out} = 1 \mu A$$

Q.

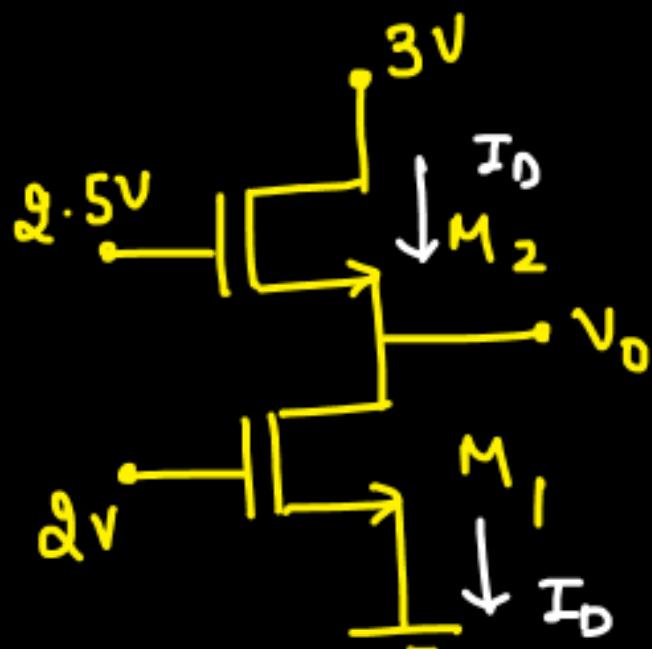

Both Transistors are identical.

$$V_T = 1V$$


Find operating cond'n of  $M_1$  &  $M_2$ .

→ Let both  $M_1$  and  $M_2$  are in sat.

$$(I_D)_{M_2} = (I_D)_{M_1}$$

$$\frac{\mu_n C_o x W}{2L} (2.5 - V_0 - 1)^2 = \frac{\mu_n C_o x W}{2L} (2 - 1)^2$$

$$V_0 = 0.5V \quad \boxed{X}$$

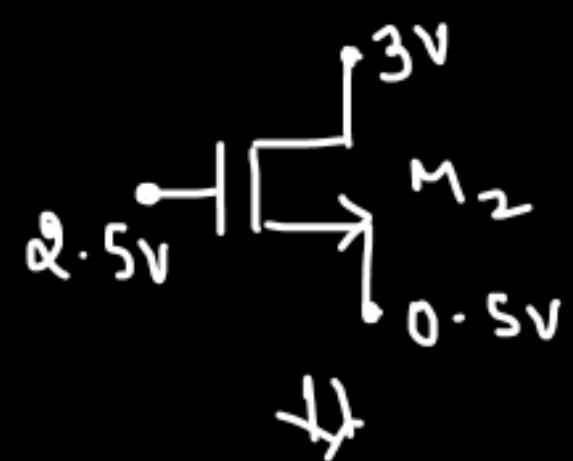


$$V_{DS} = 2.5V$$

$$V_{GS} = 2 - 1 = 1V$$

$V_{DS} > V_{GS}$   $\Rightarrow$  sat.

U

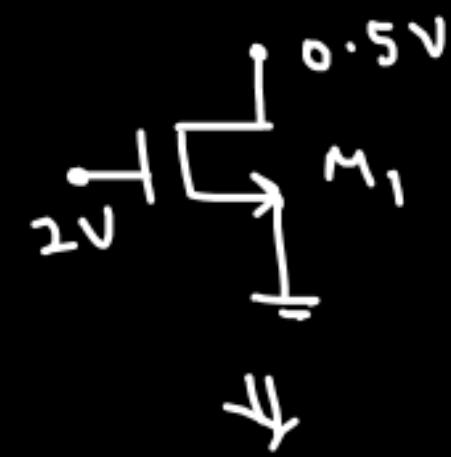

$$V_{DS} = 0.5V$$

$$V_{GS} = 1.5V$$

$V_{DS} < V_{GS}$   $\Rightarrow$  linear / Not in sat.

Let  $M_1$  is in linear,  $M_2$  is in sat.

$$(I_D)_{M_1} = (I_D)_{M_2}$$

$$\frac{\mu_n C_{ox} W}{L} \left[ (1)(V_o) - \frac{V_o^2}{2} \right] = \frac{\mu_n C_{ox} W}{2L} [2.5 - V_o - 1]^2$$


$$2V_0 - V_0^2 = [1.5 - V_0]^2$$

$$2V_0 - V_0^2 = 2.25 + V_0^2 - 3V_0$$

$$2V_0^2 - 5V_0 + 2.25 = 0$$

$$V_0 = \frac{5 \pm 2.64}{4}$$

$$V_0 = 1.9V \text{ OR } 0.6V$$

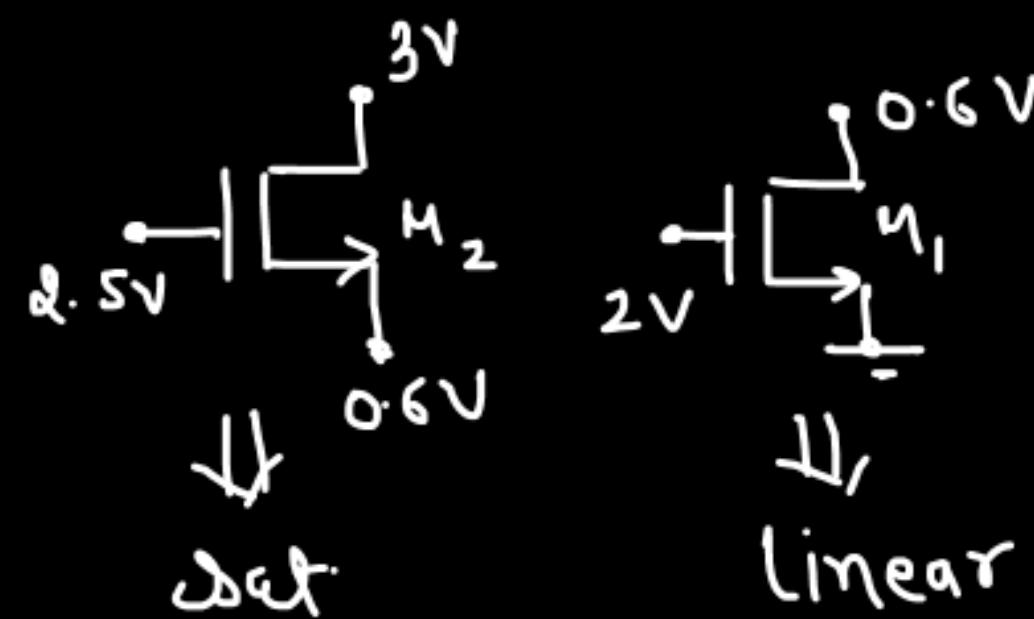

$V_0 = 0.6V$

M<sub>2</sub> is saturated  
M<sub>1</sub> is in linear


Q.




In the circuit shown, the threshold voltages of the pMOS ( $|V_{tp}|$ ) and nMOS ( $V_{tn}$ ) transistors are both equal to 1 V. All the transistors have the same output resistance  $r_{ds}$  of 6 M $\Omega$ . The other parameters are listed below:


$$\mu_n C_{ox} = 60 \mu A/V^2 ; \left(\frac{W}{L}\right)_{nMOS} = 5$$

$$\mu_p C_{ox} = 30 \mu A/V^2; \left(\frac{W}{L}\right)_{pMOS} = 10$$

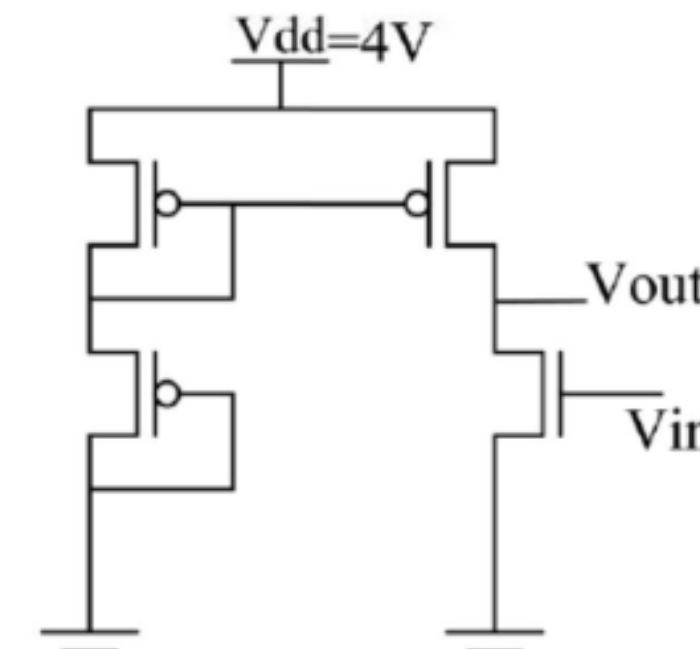$\mu_n$  and  $\mu_p$  are the carrier mobilities, and  $C_{ox}$  is the oxide capacitance per unit area. Ignoring the effect of channel length modulation and body bias, the gain of the circuit is \_\_\_\_\_ (rounded off to 1 decimal place).



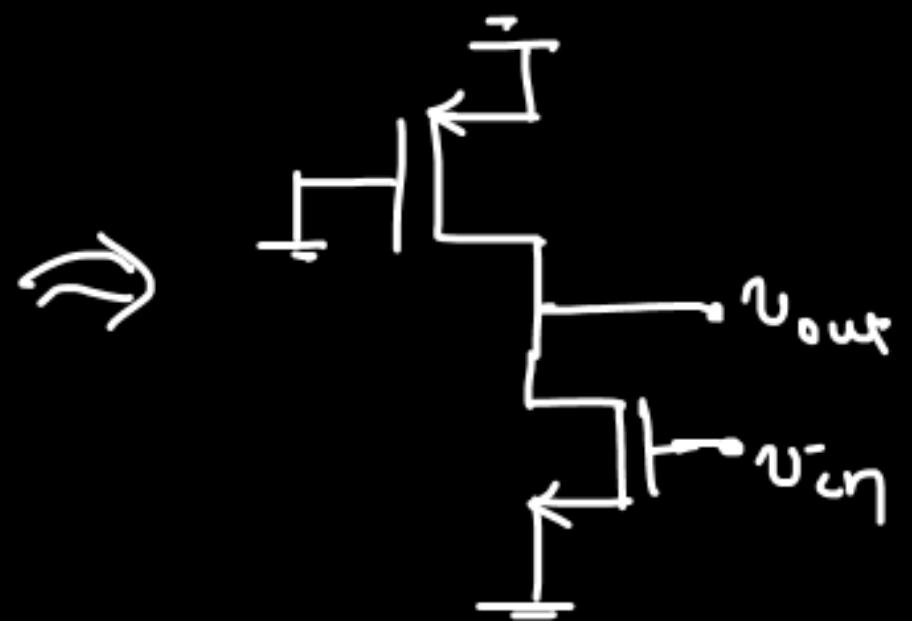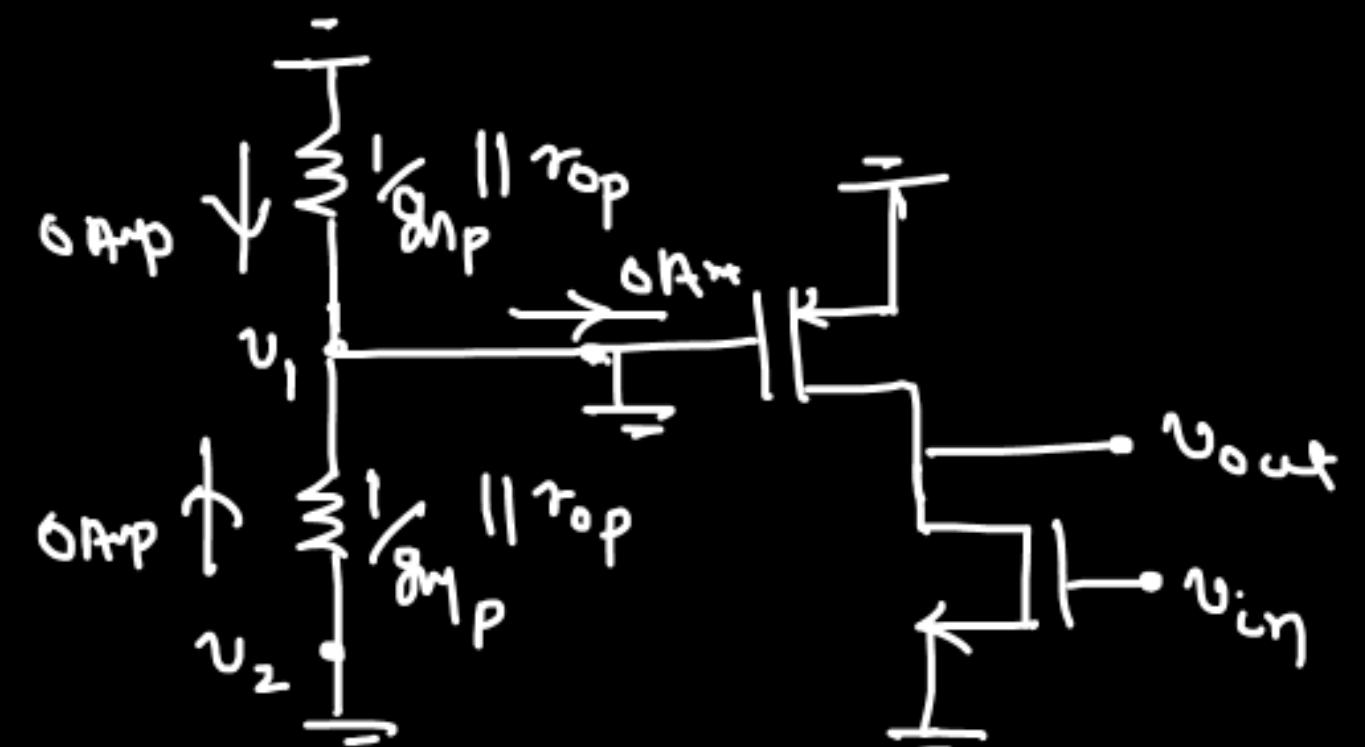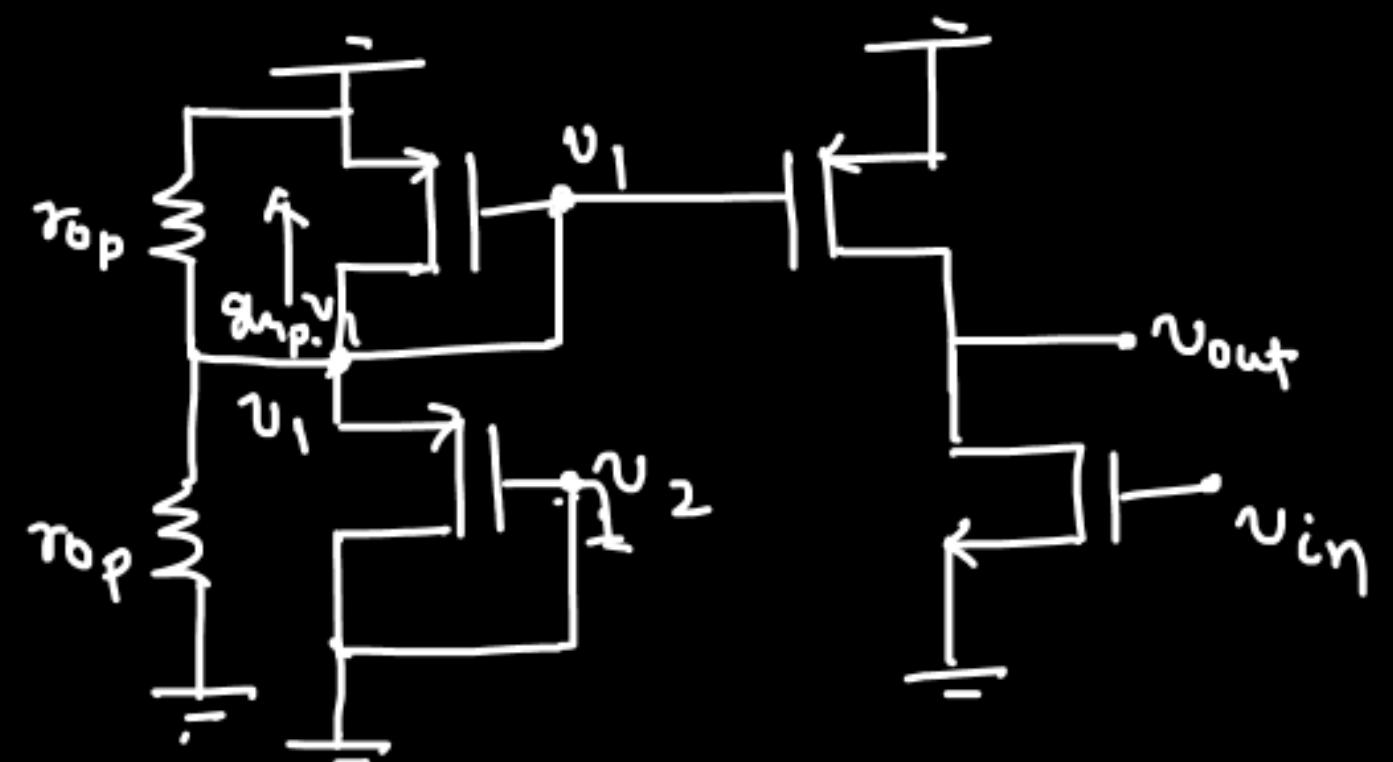

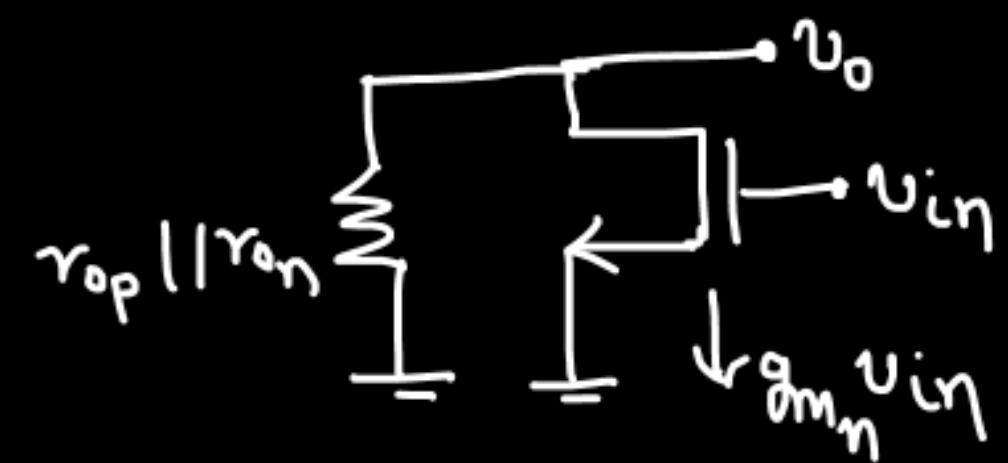


$$\frac{v_0}{v_i} = -g_m n [r_{op} || r_{on}]$$

$$r_{op} = r_{on} = GM \infty$$

$$g_m n = ?$$

$$g_m n = \sqrt{\frac{2 \mu_n C_{ox} W}{L} I_{D_N}}$$

$$I_{D_N} = ?$$

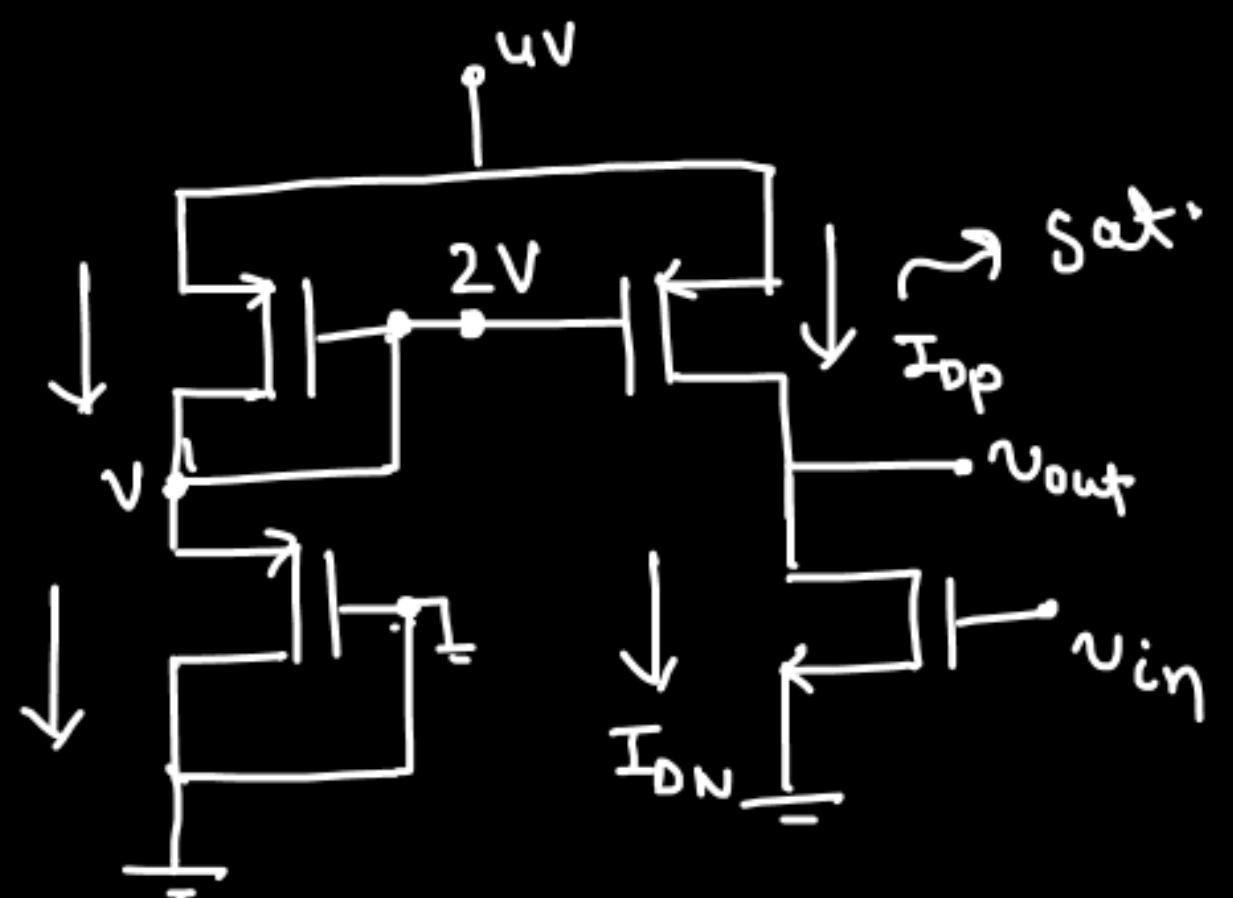

$$\frac{\mu_p C_{ox} W}{2L} [3 - V_a - 1]^2 = \frac{\mu_p C_{ox} W}{2L} [V_a - 1]^2 \quad \left\{ \lambda \rightarrow \text{very small} \right\}$$

$$3 - V_a = V_a - 1$$

$$V_a = 2V$$

$$I_{Dp} = \frac{\mu_p C_{ox} W}{2L} (V_{SG} - V_T)^2$$

$$I_{Dp} = \frac{300\mu}{2} (2-1)^2$$

$$I_{Dp} = 150\mu \text{Amp.} = I_{DN}$$

$$\delta m_\eta = \sqrt{2 \times 300\mu \times 150\mu} = 300\mu s$$


$$\alpha_V = -\delta m_p [\tau_{0p} || \tau_{0\eta}] \quad \tau_{0p} = 6 \text{ n.s}$$

$$= -300\mu \times [6 \text{ n.s} || 6 \text{ n.s}]$$

$$= -3 \times 10^{-4} \times 3 \times 10^6 = -900$$


$\alpha_V = -900 \text{ V/V}$   
 Ans.

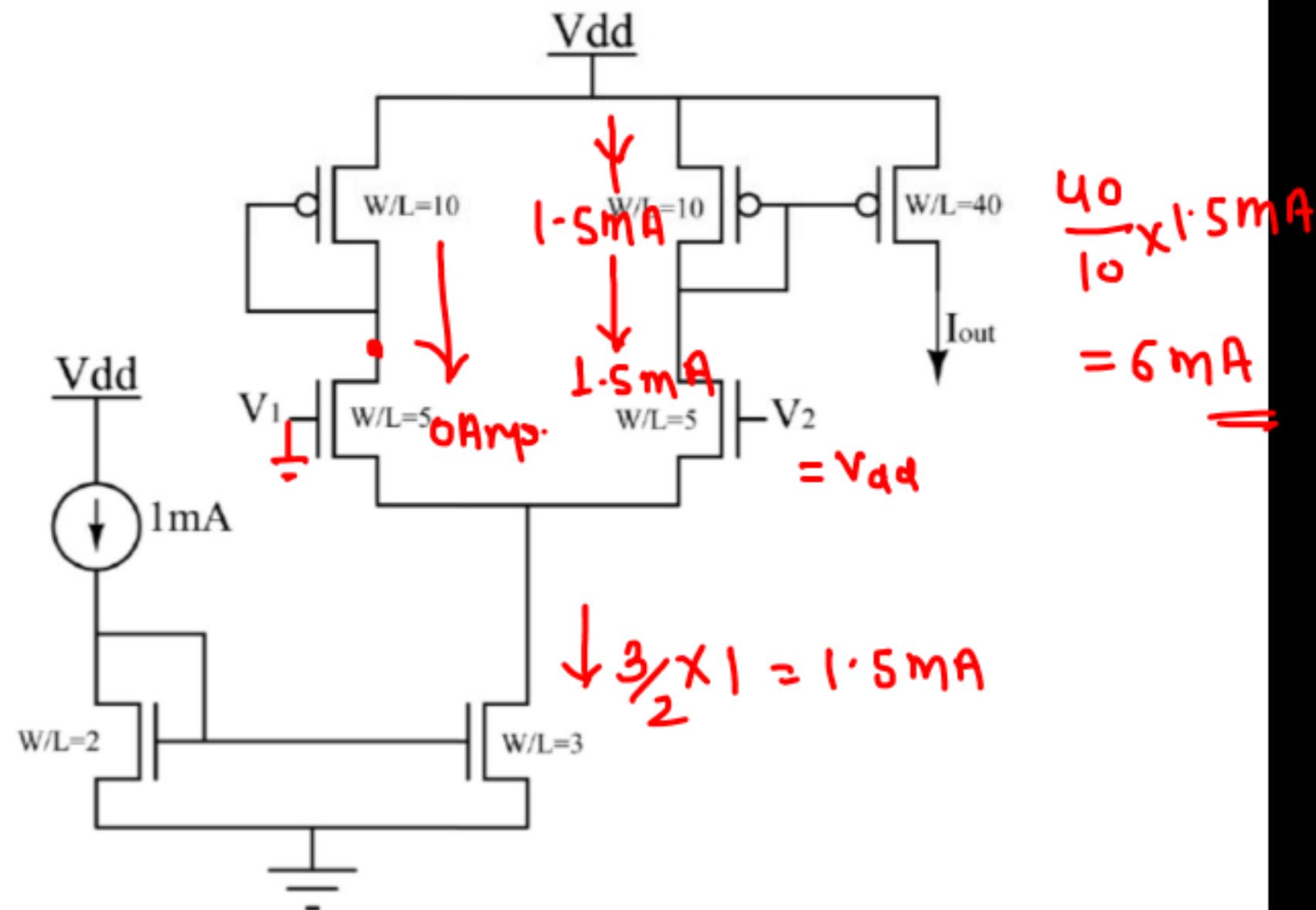In the circuit shown,  $V_1 = 0$  and  $V_2 = V_{dd}$ . The other relevant parameters are mentioned in the figure. Ignoring the effect of channel length modulation and the body effect, the value of  $I_{out}$  is \_\_\_\_\_ mA (rounded off to 1 decimal place).



## Assignment - 9 [Fusion - Special]

Q.

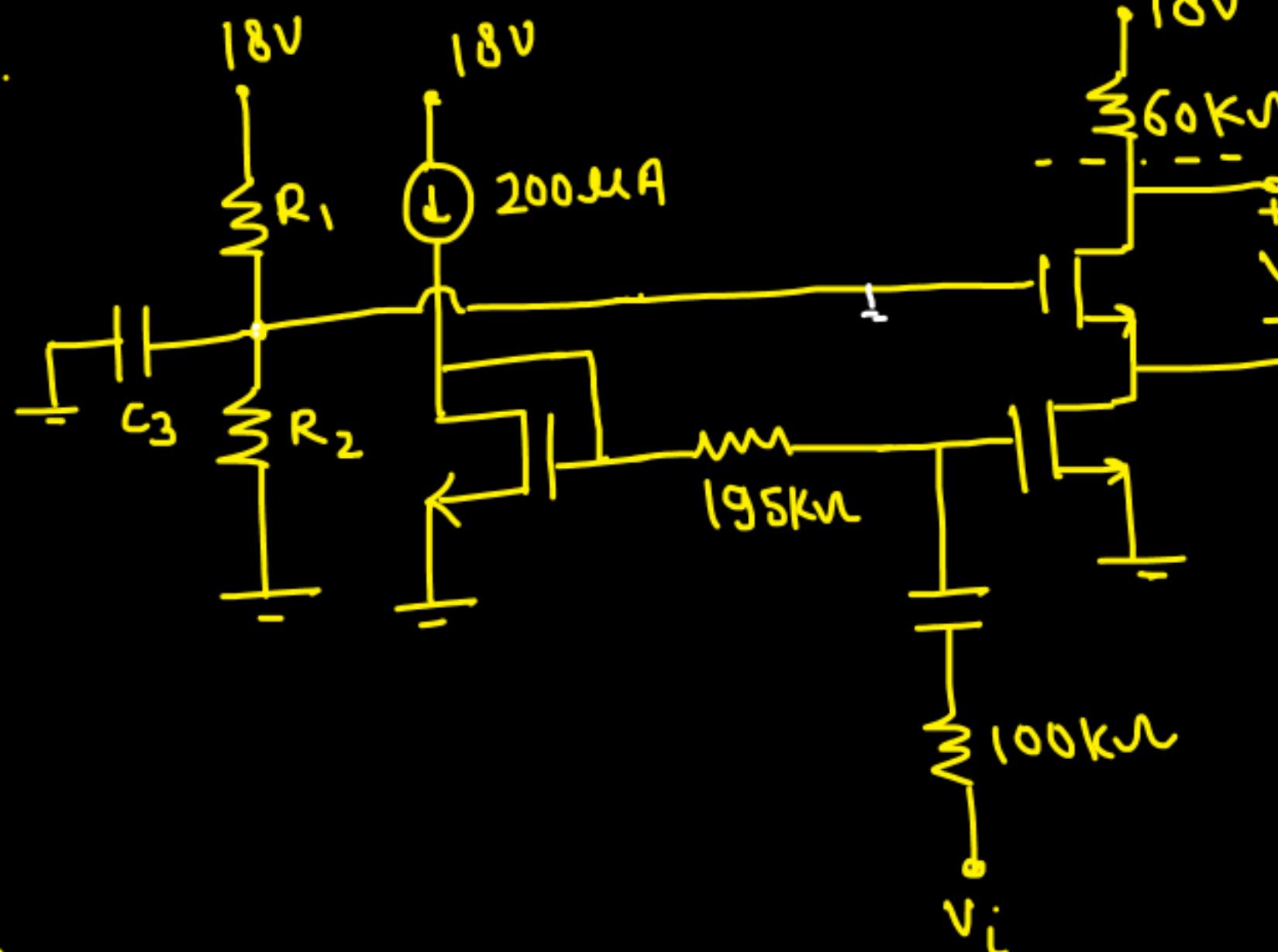

(a) Find small signal voltage gain  $\frac{v_o}{v_i}$ . ( $\lambda = 0$ )


(b) find small signal  $R_o$ . ( $\lambda = 0.05 \text{ V}^{-1}$ )

Given that all Tr are working in Sat. region.

$$\mu_n C_{ox} \frac{W}{L} = 100 \mu\text{A}/\text{V}^2$$

$$V_T = 1V$$

→ DC Analysis:-

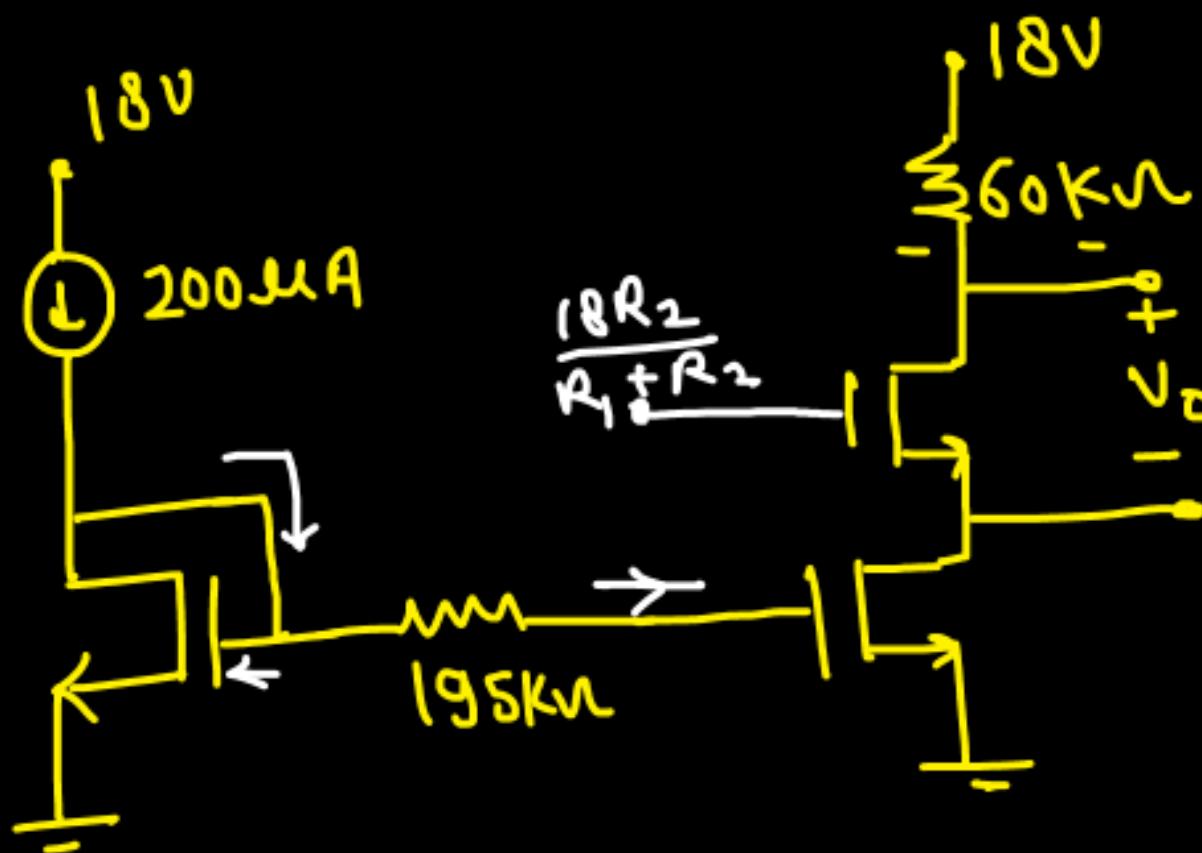

$$I_D = 200 \mu A$$


$$g_m = \sqrt{2 \mu_n C_{ox} W} I_D = 200 \mu S$$


⇒

$$g_m = 200 \mu S$$

$$\frac{1}{g_m} = 5 k\Omega$$

## AC analysis:-

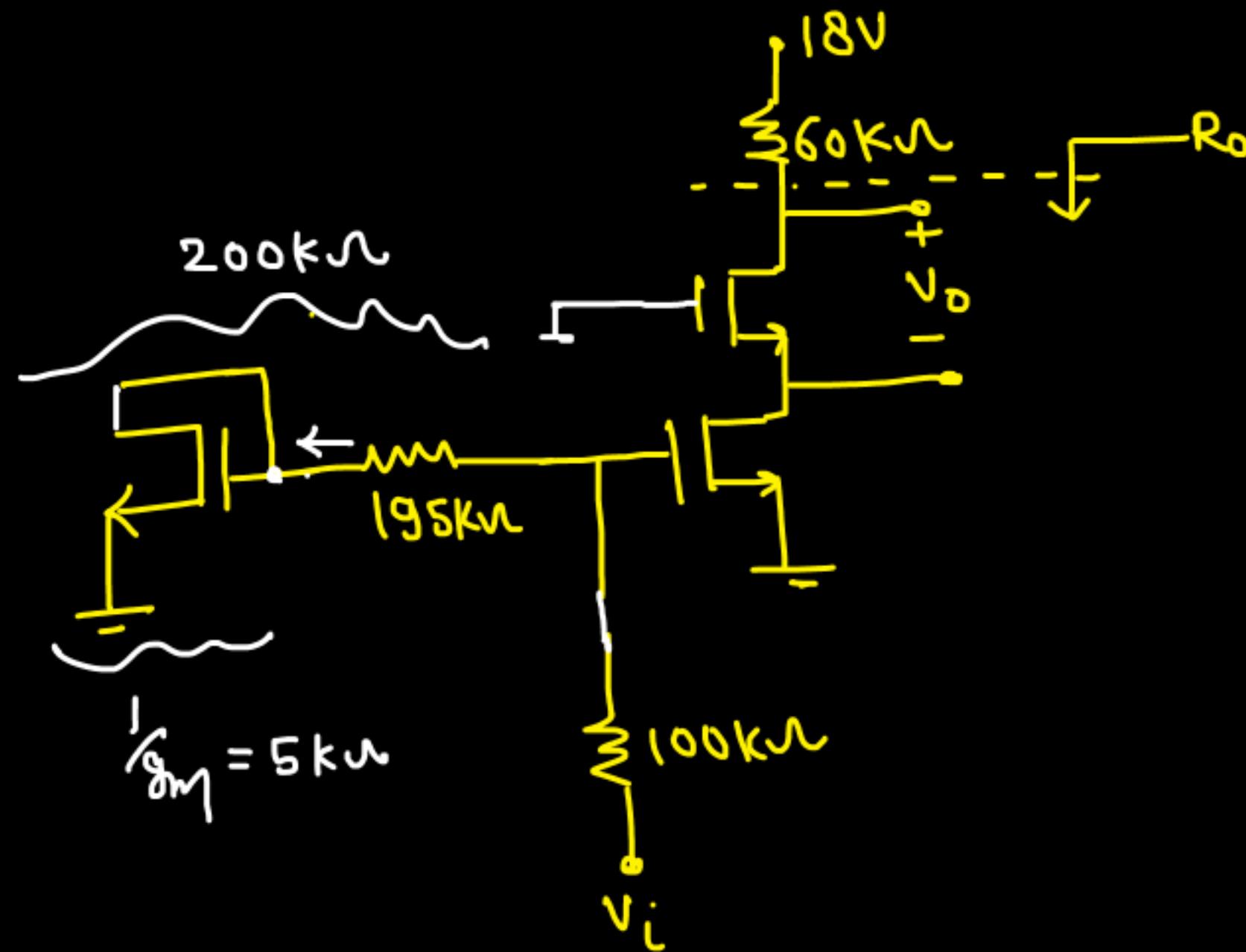


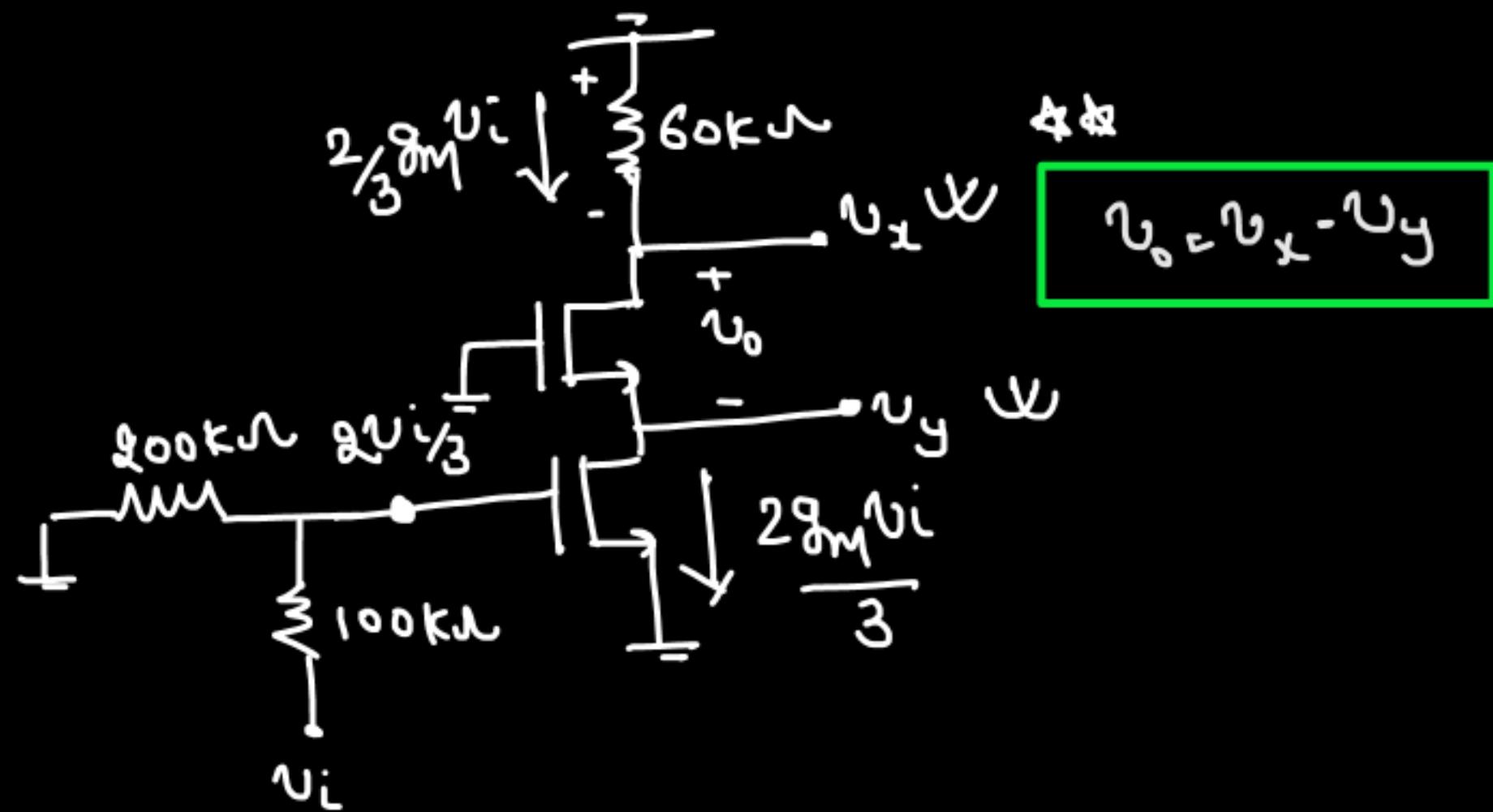

$$u_0 = -\frac{2}{3}8mVi \times 60k\Omega \quad \times$$

$$\begin{aligned}
 u_x &= -\frac{2}{3}8mVi \times 60k\Omega \\
 &= -\frac{2}{3} \times 200\mu \times 60k \times Vi
 \end{aligned}$$

$$u_x = -8Vi$$

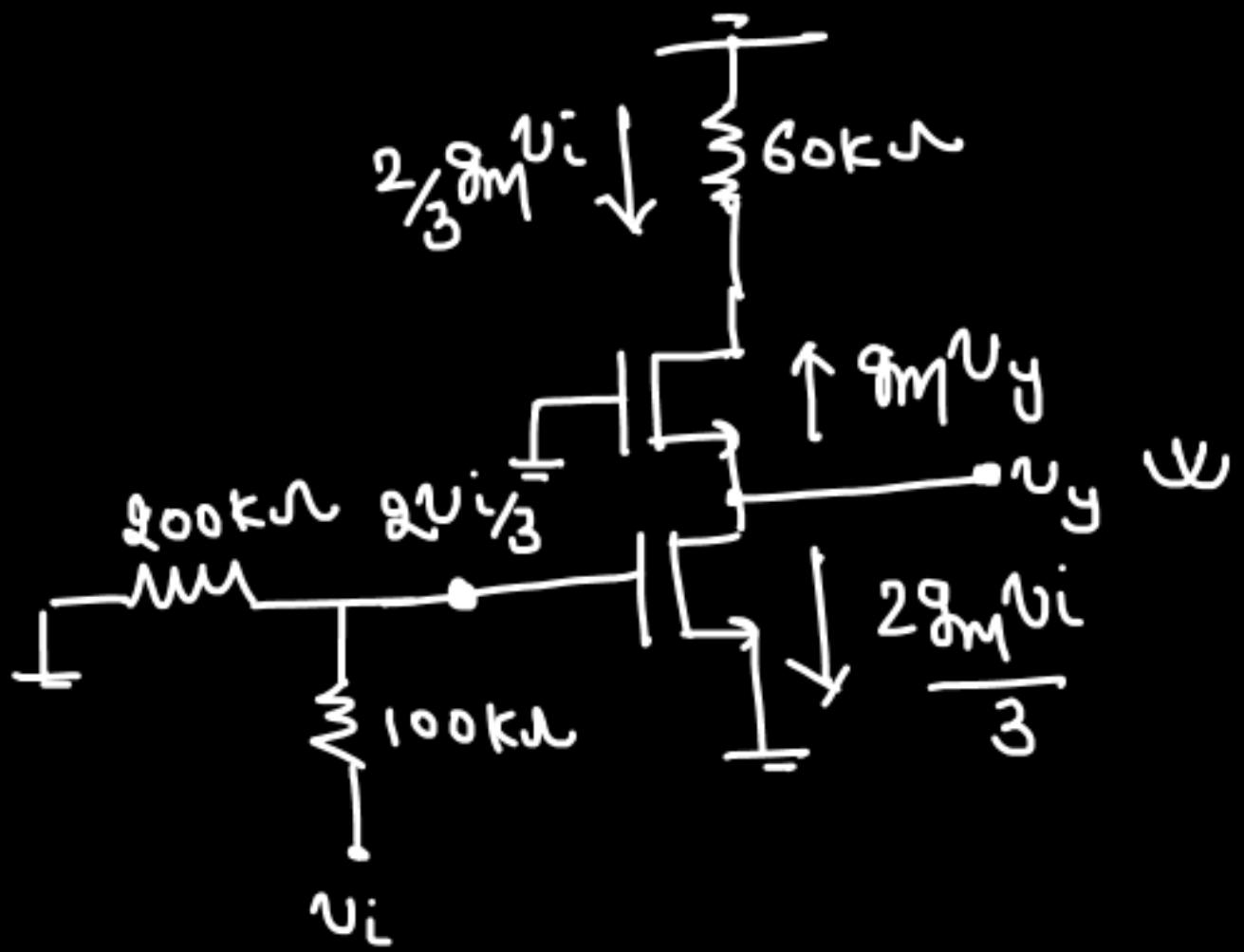

$$g_m u_y = - \frac{2}{3} g_m u_i$$


$$u_y = - \frac{2}{3} u_i$$

$$\begin{aligned} u_o &= u_x - u_y \\ &= -8u_i + \frac{2}{3} u_i \end{aligned}$$

$$u_o = -7.33 u_i$$

$$\frac{u_o}{u_i} = -7.33$$

$R_o$ :

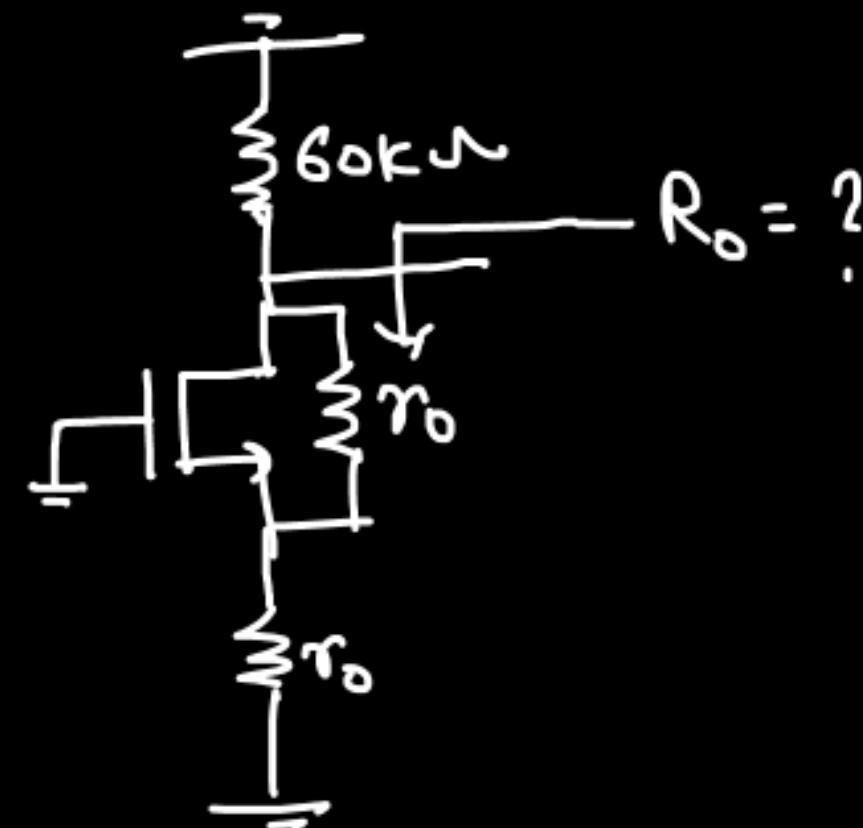


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.05 \times 200 \mu}$$

$$r_o = 100 \text{ k}\Omega$$

$$\begin{aligned} R_o &= g_m r_o r_o + r_o + r_o \\ &= g_m r_o^2 + 2r_o \\ &= 200 \mu \times 10^{-10} + 2 \times 10^5 \\ R_o &= 2.2 \text{ M}\Omega \end{aligned}$$


Q.  $M_0$  and  $M_1$  are perfectly matched.

(a) Determine current  $I_1$ .

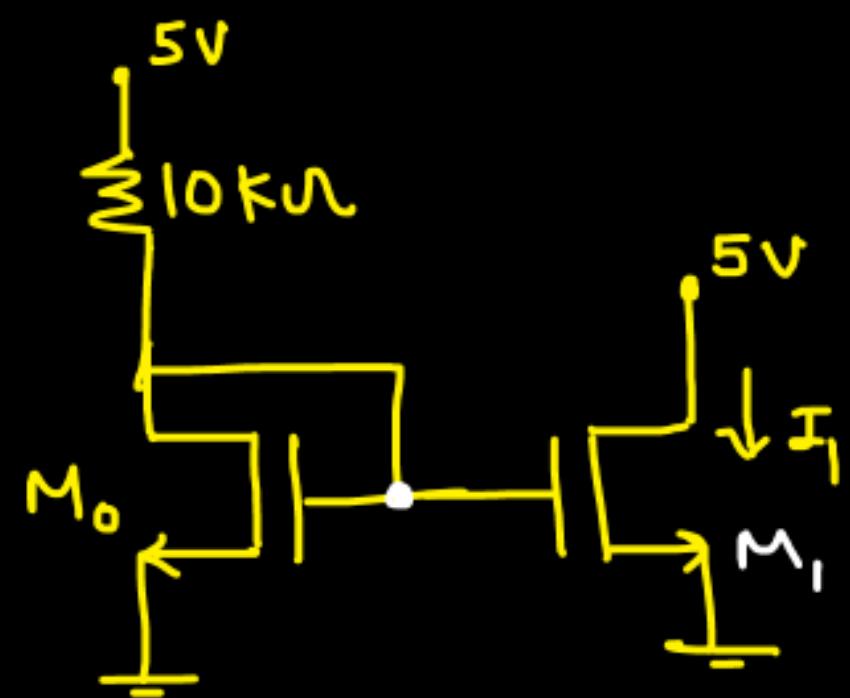

$$\mu n C_{ox} = 100 \text{ mA/V}^2, \quad W/L = 1, \quad V_T = 1 \text{ V}$$

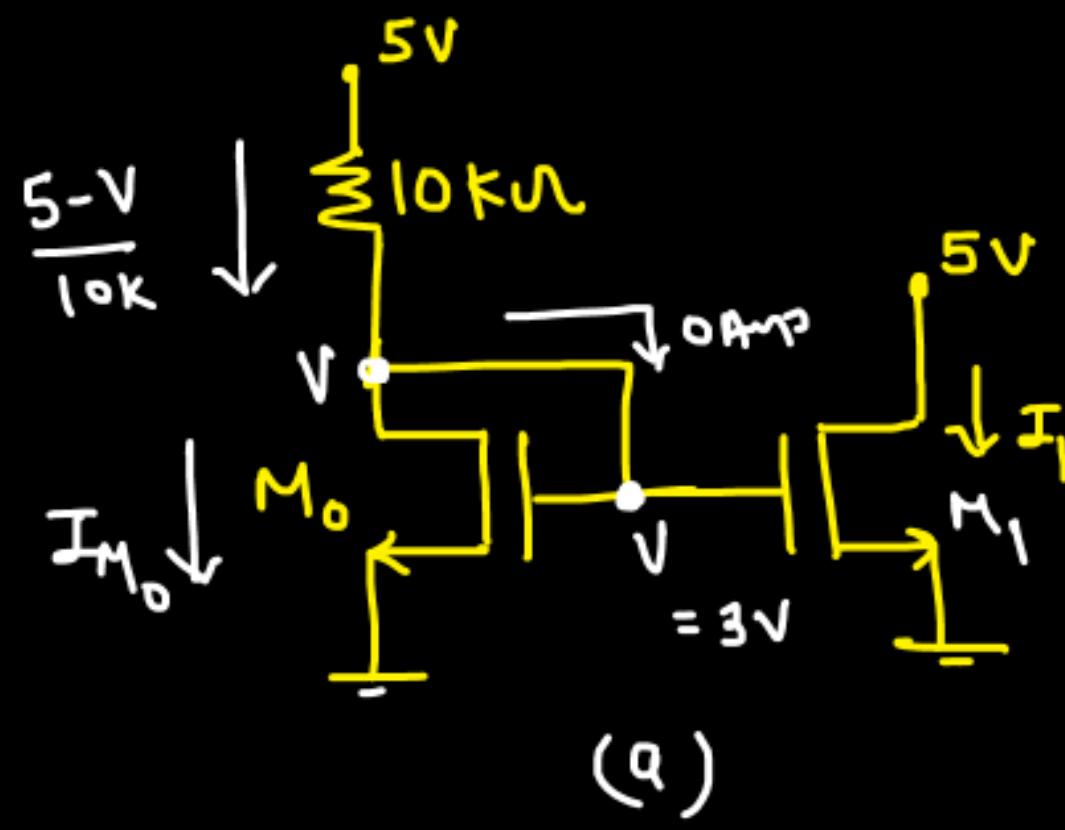(b)  $V_{DD}$  increases to 5.5V. Determine the increase in  $I_1$ .



$$I_{M_0} = \frac{4\pi C_o x \omega}{2L} (v_{ds} - v_T)^2$$

$$\frac{5-v}{10k} = \frac{100\mu}{2} (v-1)^2$$

$$5-v = (v-1)^2 / 2$$

$$10-2v = v^2 + 1 - 2v$$

V = 3V<sub>out</sub>

AA

I = 200 μA

Ans

$$M_1 \rightarrow \\ V_{DS} = 5V$$


$$V_{GS} = 3V$$

$$V_{DS} = 2V$$

$\Downarrow$   
Daf.

$$I_{M_0} = \frac{5-3}{10k} = \frac{2}{10k} = 200 \mu A = I_1$$

M-I

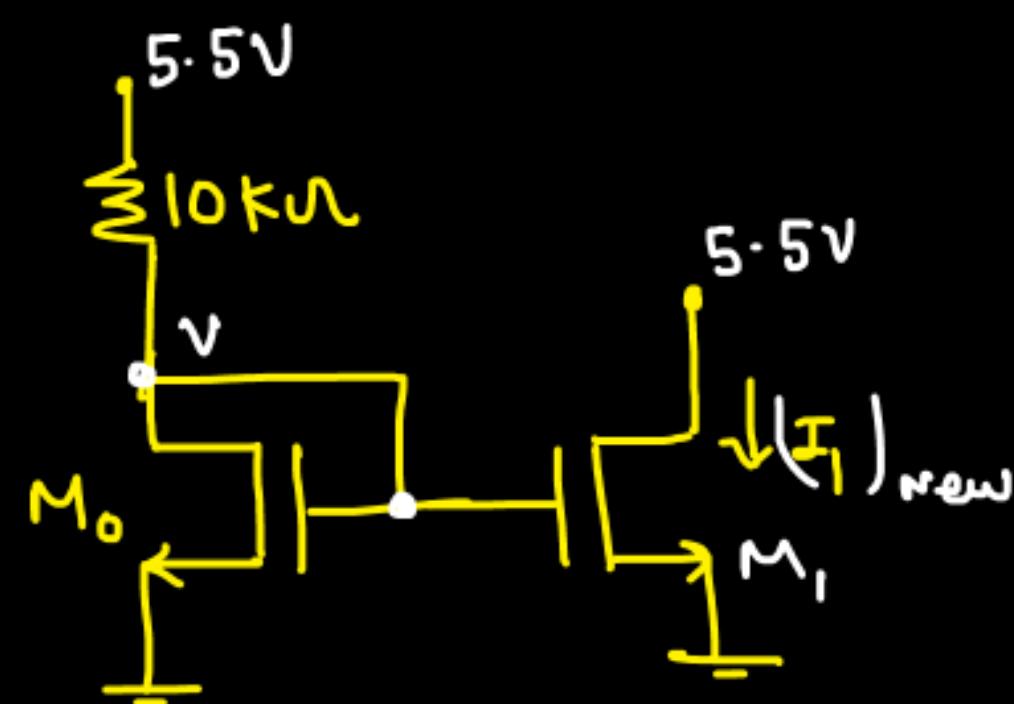

$$\Rightarrow \frac{5.5-V}{10k} = \frac{100\mu}{2} (V-1)^2$$

$$11-2V = V^2 + 1 - 2V$$

$$V^2 = 10$$



$$V = 3.16 \text{ Volt}$$

$$(I_{M_0})_{new} = (I_1)_{new} = \frac{5.5 - 3.16}{10k}$$

$(I_1)_{new} = 233 \mu A$

\*\*

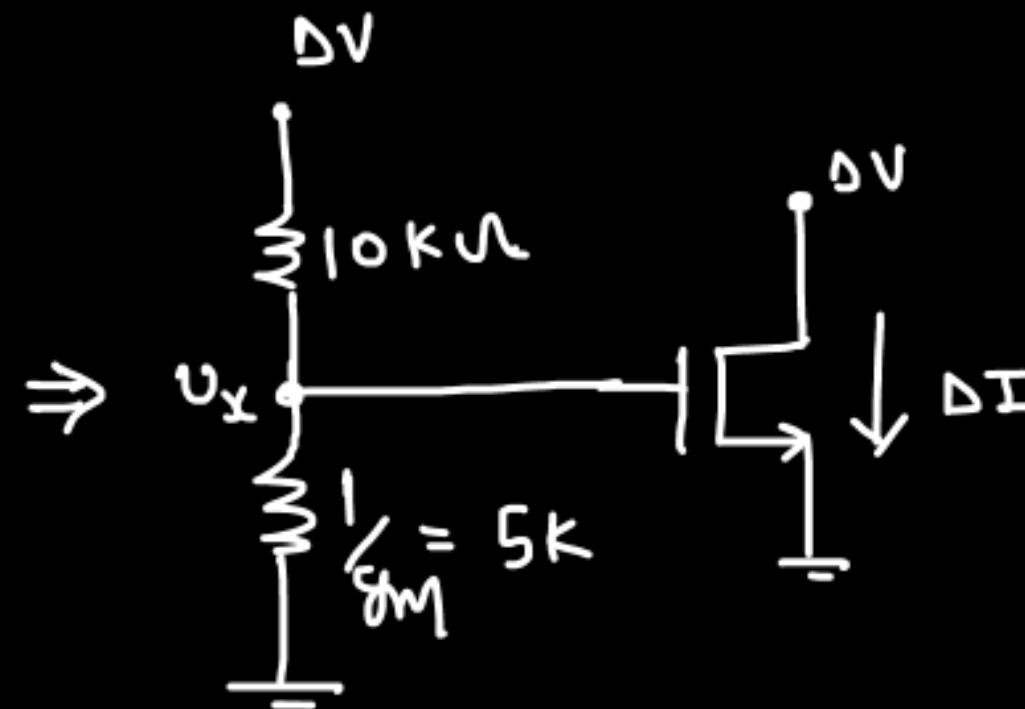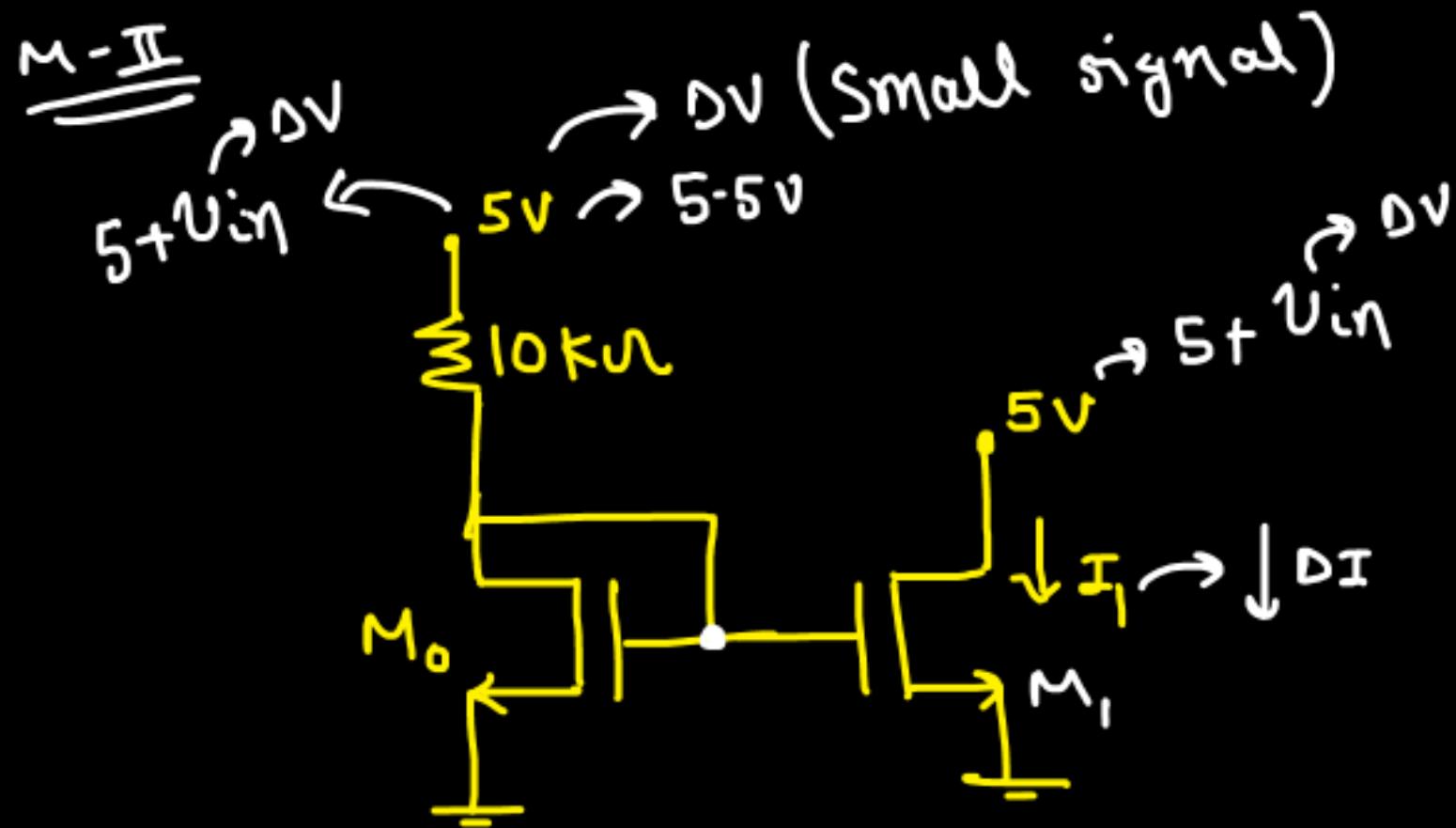$\Delta I = 233 \mu - 200 \mu = 33 \mu A \rightarrow$



$$g_m = \sqrt{\frac{2\mu n C_{ox} W}{L}} I_D$$

$$= \sqrt{2 \times 100 \mu \times 200 \mu S}$$

$$g_m = 200 \mu S$$

$$\frac{1}{g_m} = 5k\Omega$$

$$U_x = \frac{5k}{5k + 10k} \times DV = \frac{DV}{3}$$

$$DI = g_m U_x = \frac{g_m DV}{3} = \frac{200 \mu}{3} DV$$

\* \*

$DI = \frac{200 \mu}{3} DV$

$$\text{Here; } \Delta V = 5.5 - 5 = 0.5V$$

$$\Delta I = \frac{200\mu}{3} \times 0.5$$


$$\Delta I = 33.33 \mu\text{Amp}$$

For supply,

$$(i) 5.1V \Rightarrow \Delta I = \frac{200\mu}{3} \times 0.1 = 6.66 \mu\text{Amp.}$$

$$(ii) 5.3V \Rightarrow \Delta I = \frac{200\mu}{3} \times 0.3 = 20 \mu\text{Amp.}$$

Q.

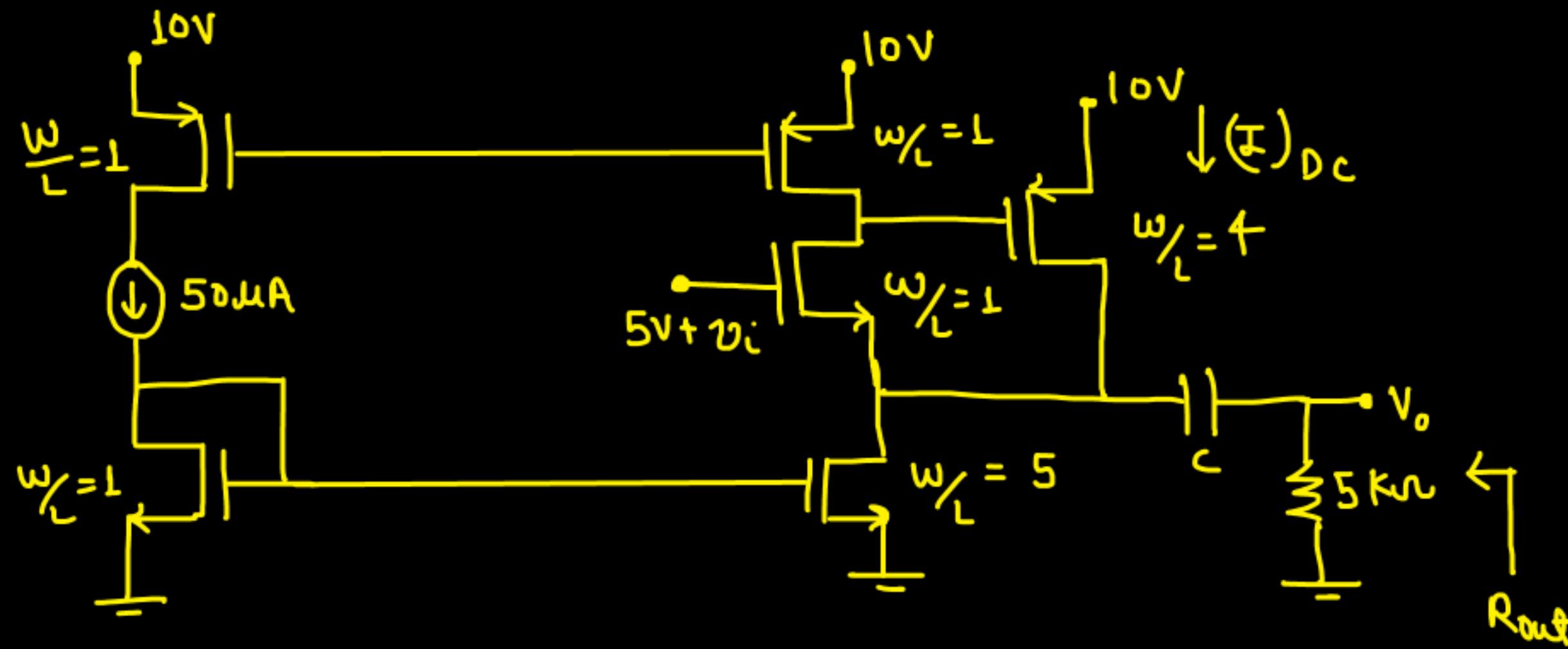


$$\mu_n C_{ox} = 100 \mu\text{A}/\sqrt{2}, \quad \mu_p C_{ox} = 25 \mu\text{A}/\sqrt{2}$$

$$V_{TH} = 1\text{V}$$

Given  $\rightarrow$  all Trs are biased in sat.


- Determine  $I_{DC}$
- Find small signal voltage gain
- Find small signal  $R_{out}$

## DC Analysis:-

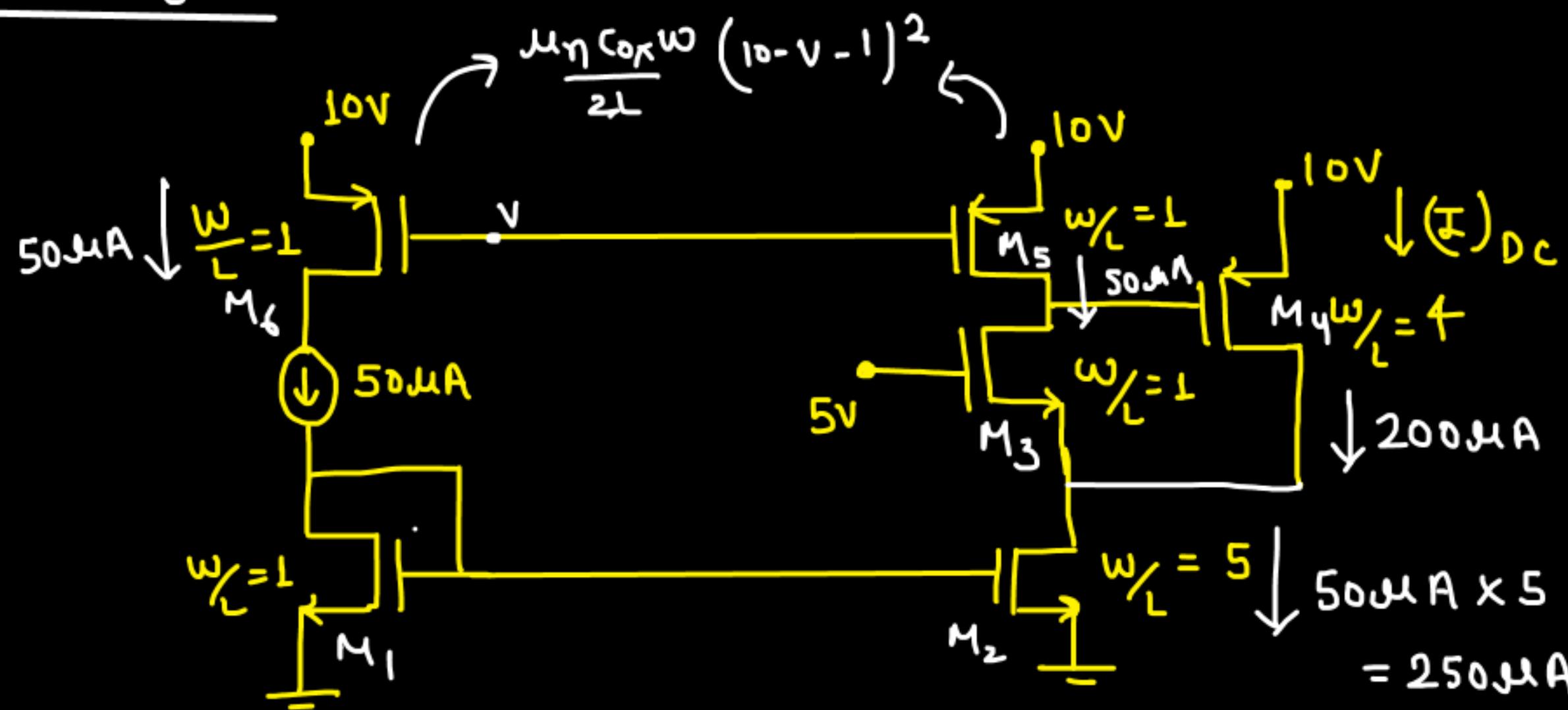


$$(I_{DC}) = 200\mu A$$

## AC Analysis:-

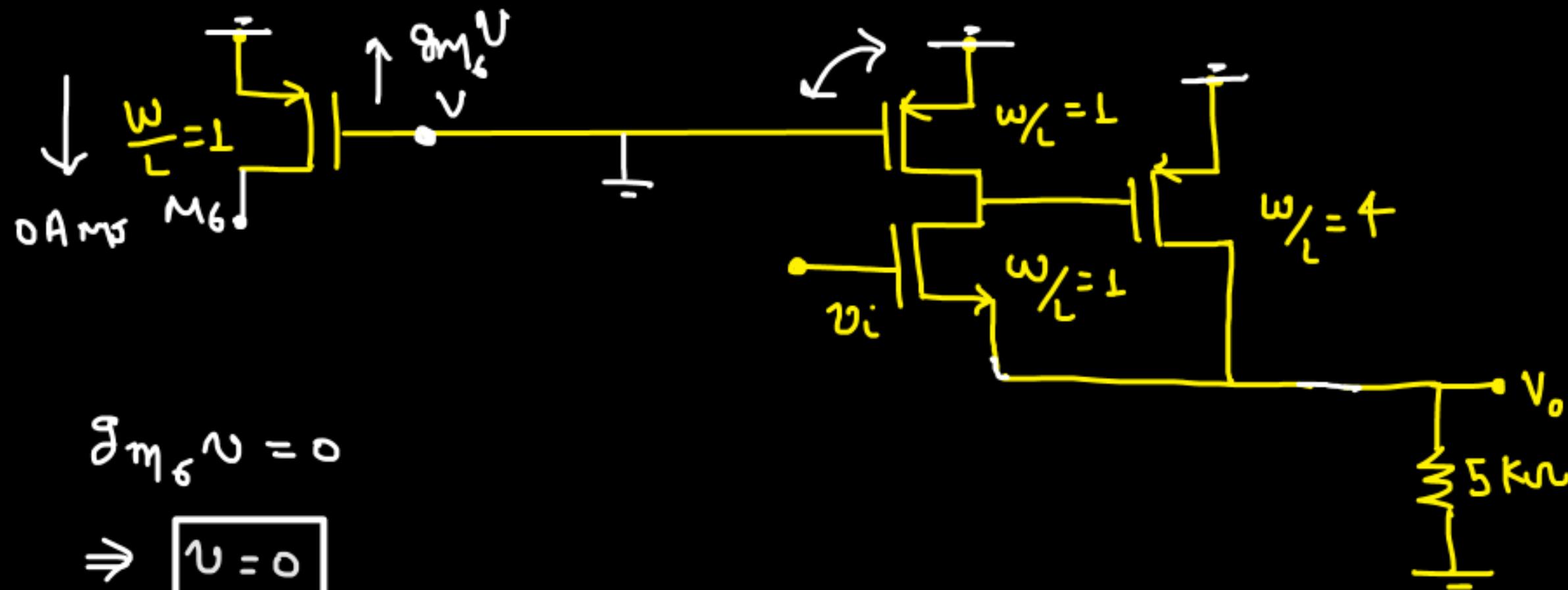

$$\frac{\partial m_6}{\partial} U = 0$$


$$\Rightarrow U = 0$$

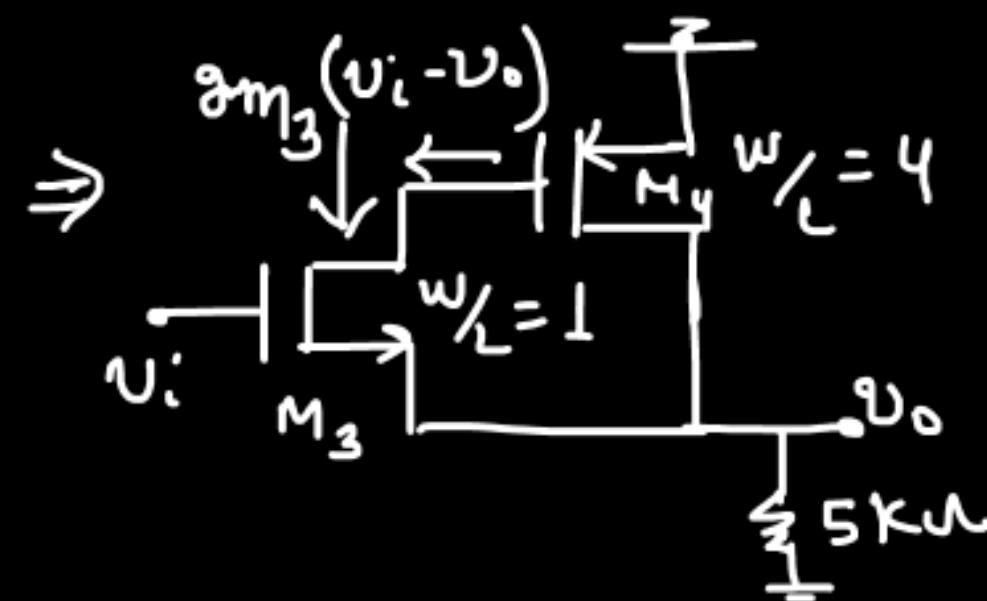

$$\frac{\partial m_3}{\partial} (U_L - U_o) = 0$$

$$U_o = U_i$$
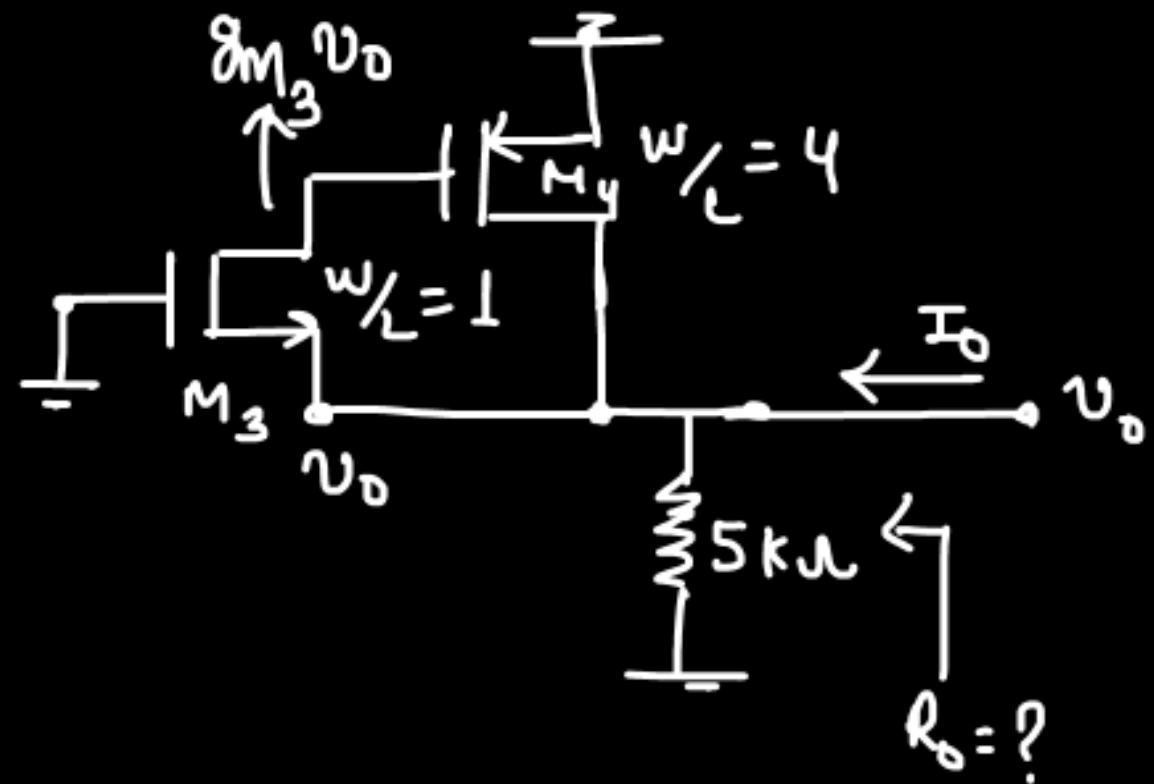
$$\frac{U_o}{U_i} = 1 \quad \text{Ans.}$$



$$\frac{v_D}{I_0} = R_0$$


$$\partial m_3 v_D = 0$$

$$v_D = 0$$

$$R_0 = \frac{0}{I_0} = 0 \Omega$$

15kΩ

Q.

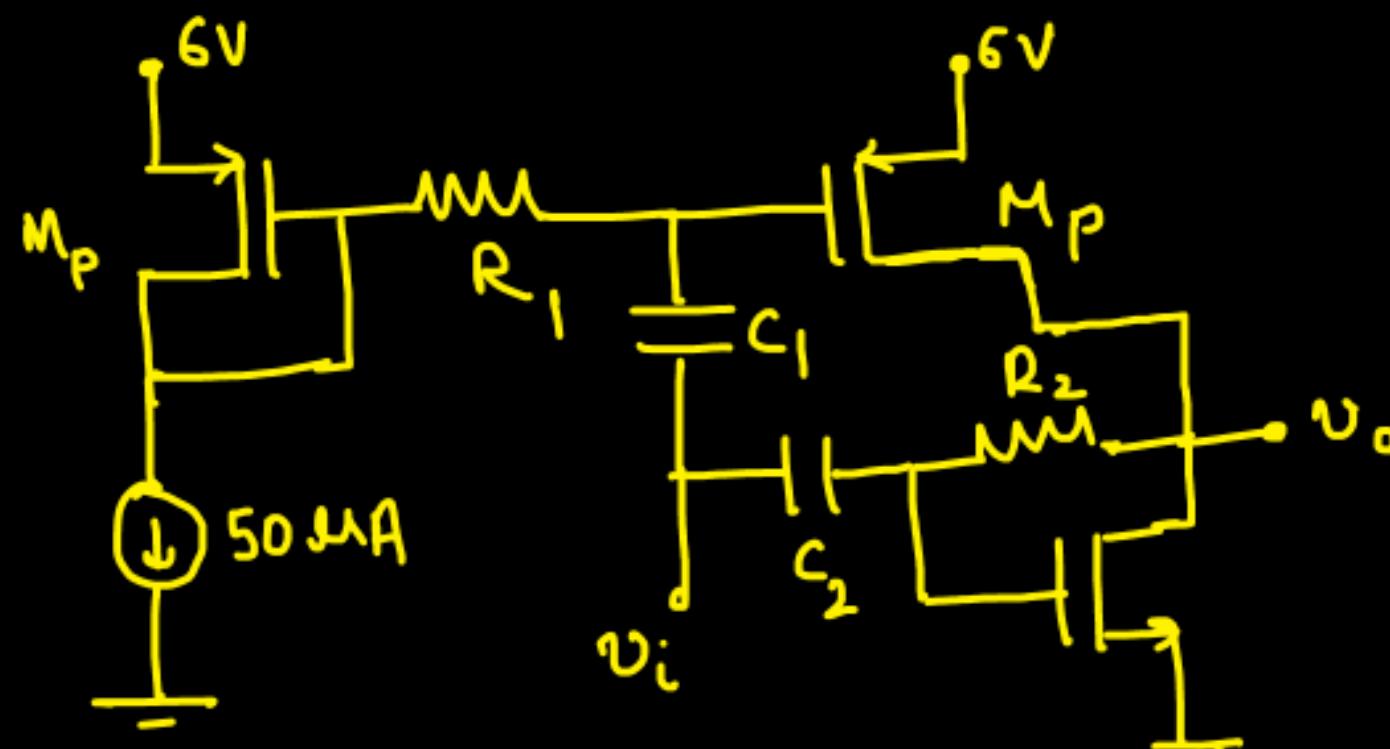


Given  $\rightarrow R_1, R_2$  values are very large.

$$M_P: \mu_P C_{ox} = 100 \text{ mA/V}^2, \frac{w_p}{L_p} = 4, V_{TP} = 0.5 \text{ V}, \lambda_p = 0.05 \text{ V}^{-1}$$

$$M_N: \mu_N C_{ox} = 400 \text{ mA/V}^2, \frac{w_n}{L_n} = 1, V_{TN} = 0.5 \text{ V}, \lambda_n = 0.05 \text{ V}^{-1}$$

Determine small signal voltage gain  $\frac{v_o}{v_i}$ ?

## DC Analysis :-

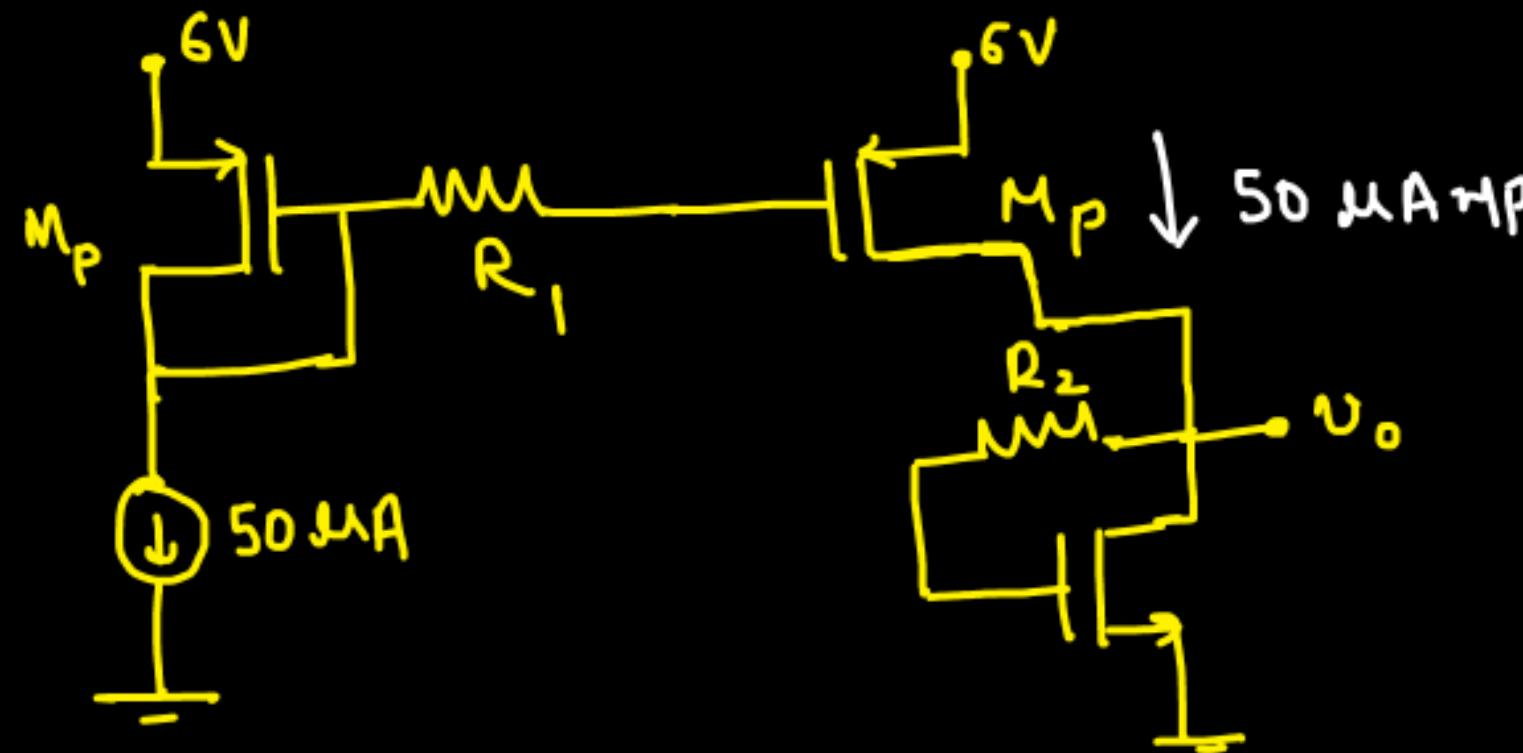

$$g_{m_P} = \sqrt{2 \times \frac{\mu_P C_{ox} W}{L}} I_D = \sqrt{2 \times 400 \mu A \times 50 \mu} = 200 \mu S$$

$$g_{m_\eta} = \sqrt{2 \times \frac{\mu_\eta C_{ox} W}{L}} I_D = \sqrt{2 \times 400 \mu A \times 50 \mu} = 200 \mu S$$



$$g_{m_P} = g_{m_\eta} = g_m = 200 \mu S$$

$$\gamma_{op} = \frac{1}{\lambda_p I_D} = \frac{1}{6.05 \times 50 \mu} = 400 \text{ kN}$$

$$\gamma_{o\eta} = \frac{1}{\lambda_n I_D} = \frac{1}{6.65 \times 50 \mu} = 400 \text{ kN}$$

$$\gamma_{op} = \gamma_{o\eta} = 400 \text{ kN} = \gamma_0$$

## AC analysis:-

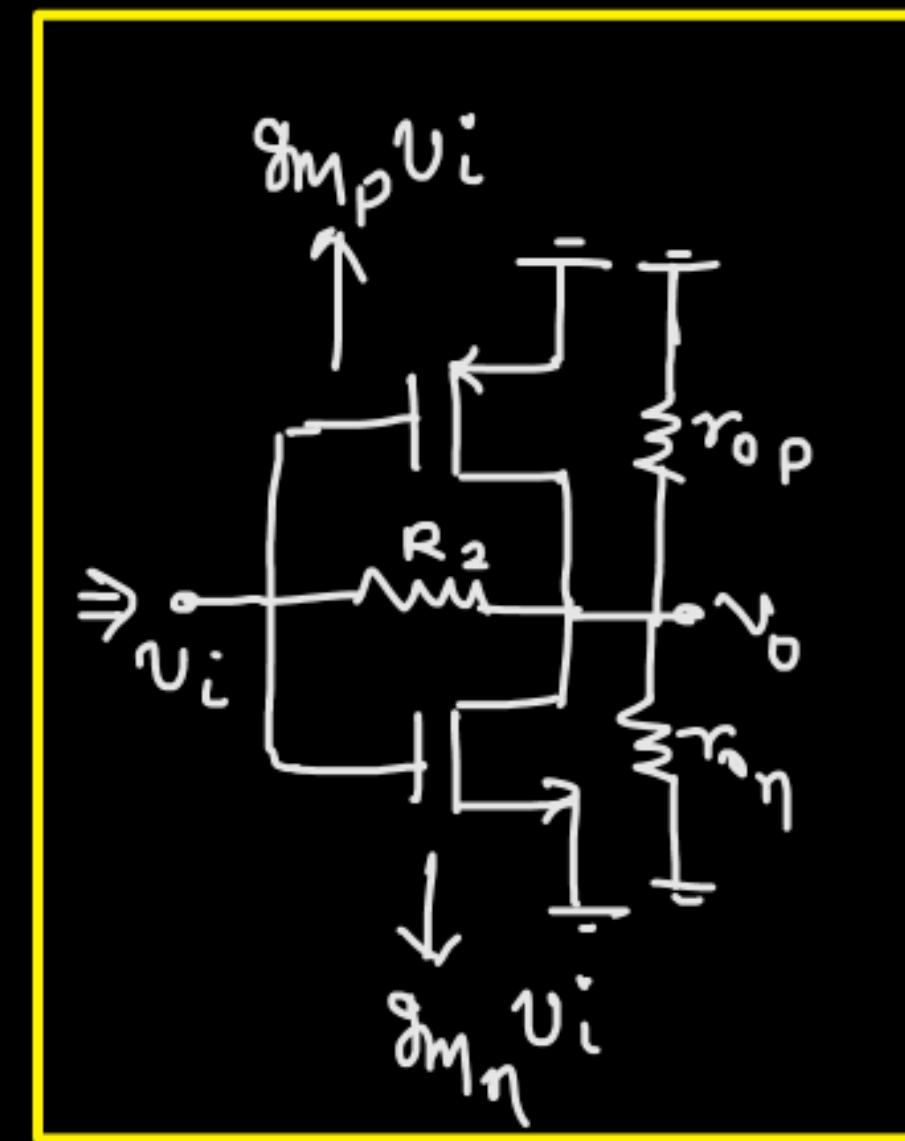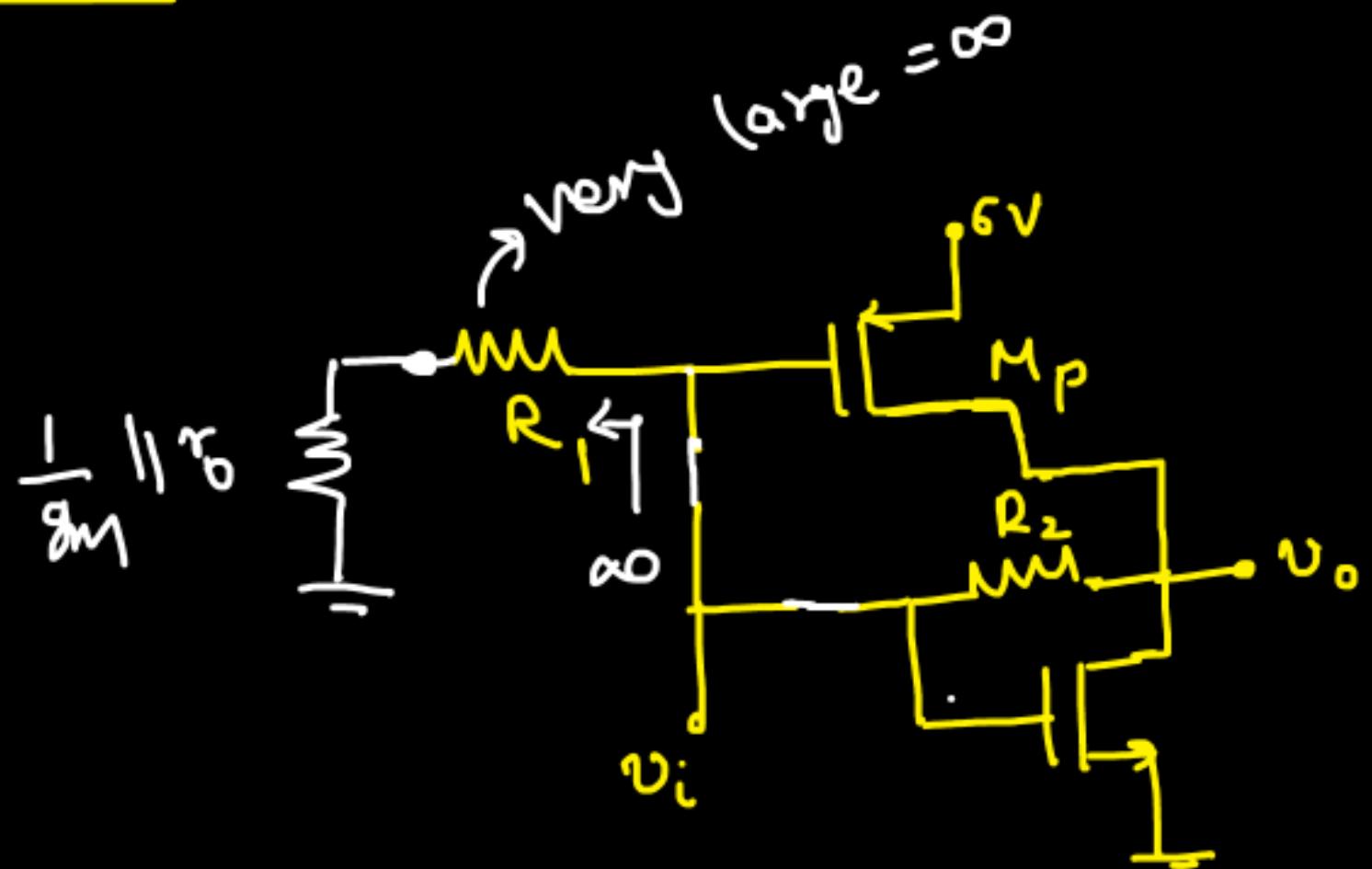


$$\frac{v_o}{r_{o_p}} + \frac{v_o}{r_{o_\eta}} + g_{m_p} v_i + g_{m_\eta} v_i = 0$$

$$\frac{v_o}{r_{o_p} \parallel r_{o_\eta}} = - (g_{m_p} + g_{m_\eta}) v_i$$

$$\frac{v_o}{v_i} = - (g_{m_p} + g_{m_\eta}) (r_{o_p} \parallel r_{o_\eta})$$

$$\Rightarrow \frac{v_o}{v_i} = - 400 \times 10^{-6} \times 200 \times 10^3 = -80$$

Q.

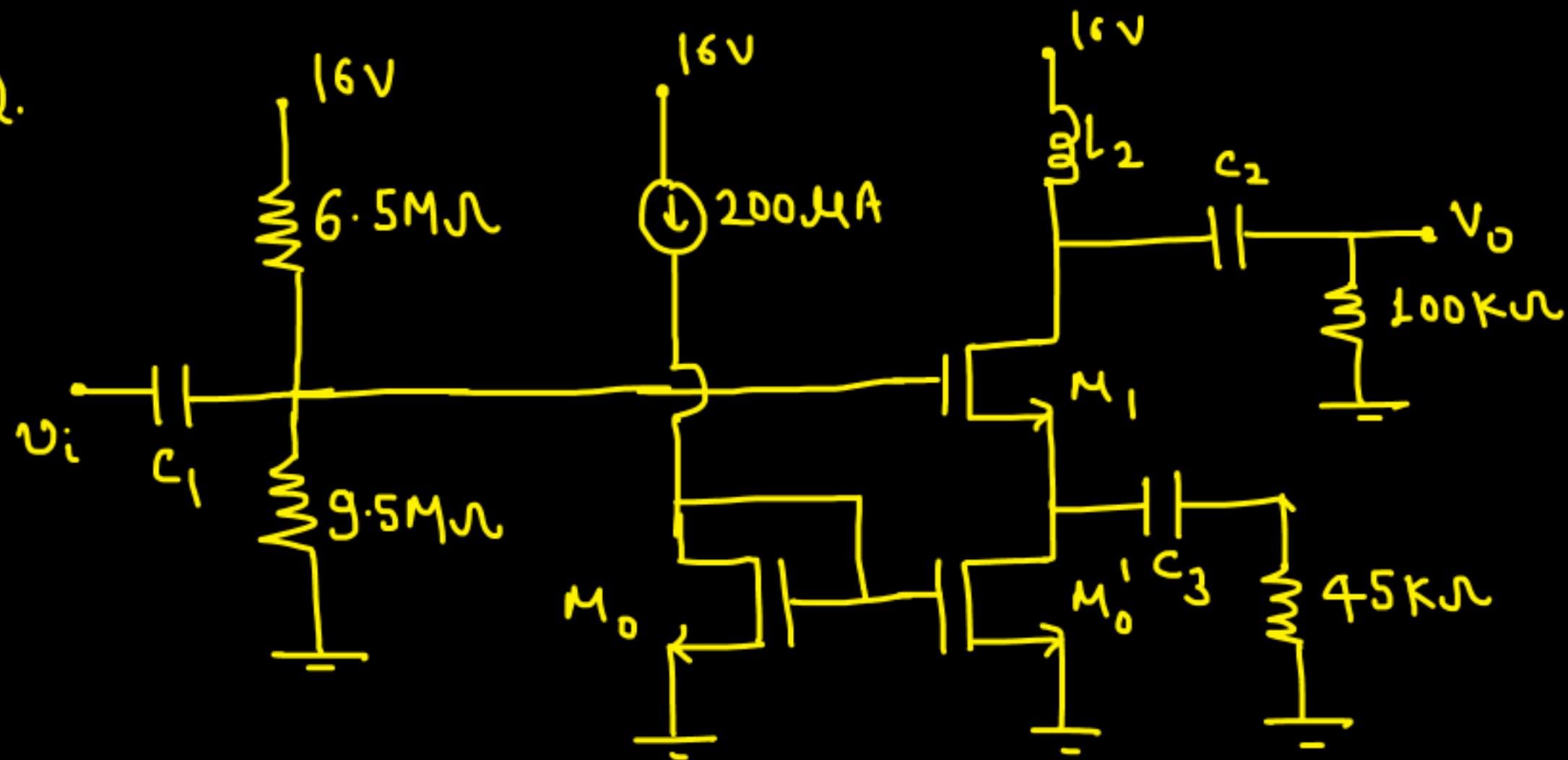


(a) Determine  $v_i$  for which  $M_1$  enters into Triode region.

(b) Determine  $v_i$  for which  $M_0'$  enters into Triode region.

$$\frac{I_{n\text{ox}}\omega}{L} = 100\mu A/V^2, \quad V_T = 1V$$

⇒ Considering  $M_1$  and  $M_0'$  are working in sat. region based on the given bias.

### DC Analysis:-

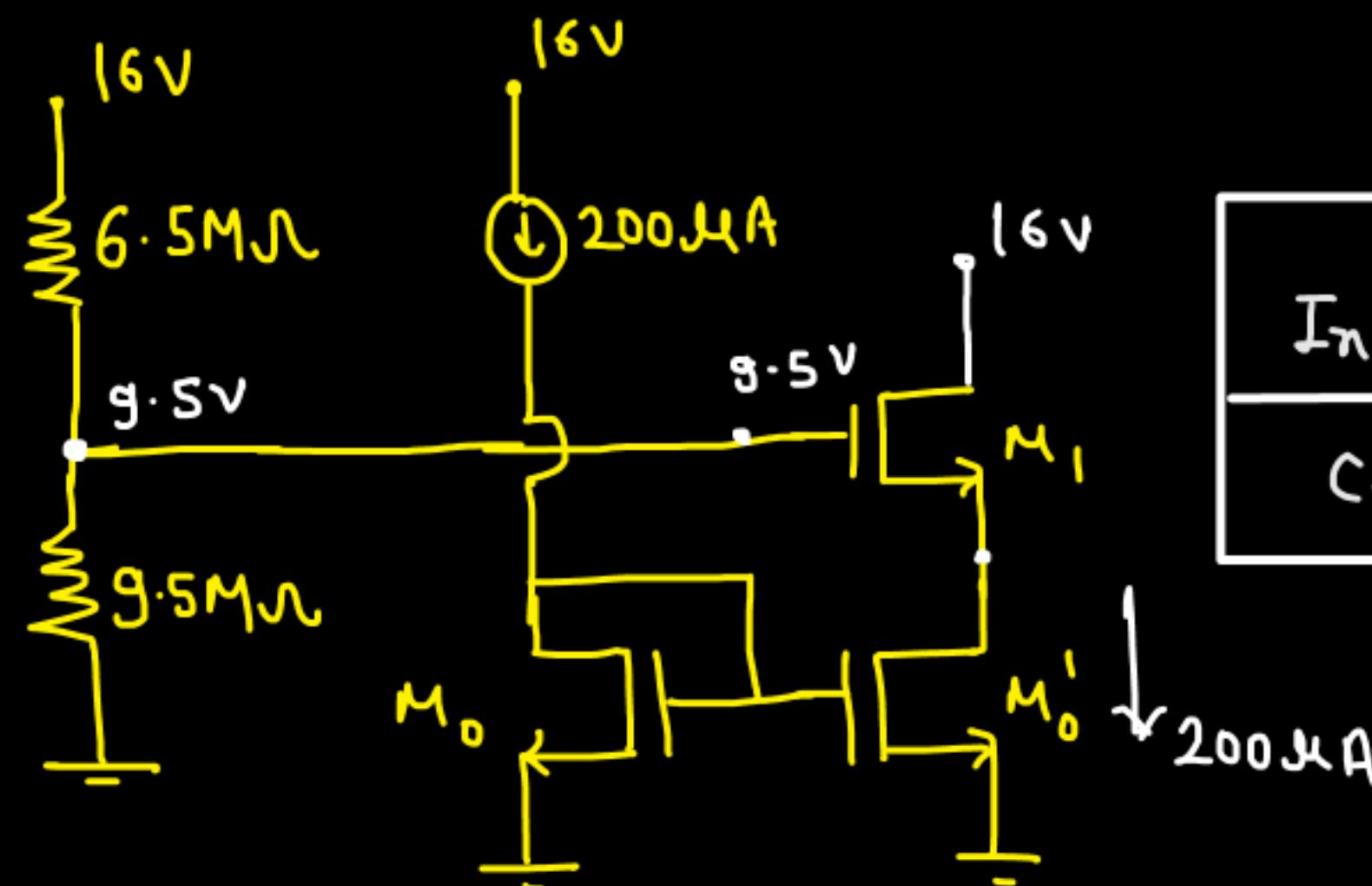

Inductor	DC S.C.	AC O.C.
Capacitor	0.C.	S.C.


$$I_{M_0'} = I_{M_1} = 200 \mu$$

$$200 \mu = \frac{100 \mu}{2} (V_{GS} - 1)^2$$


$$V_{GS} = 3V$$

For  $M_0'$  and  $M_1$   $V_{GS} = 3V$
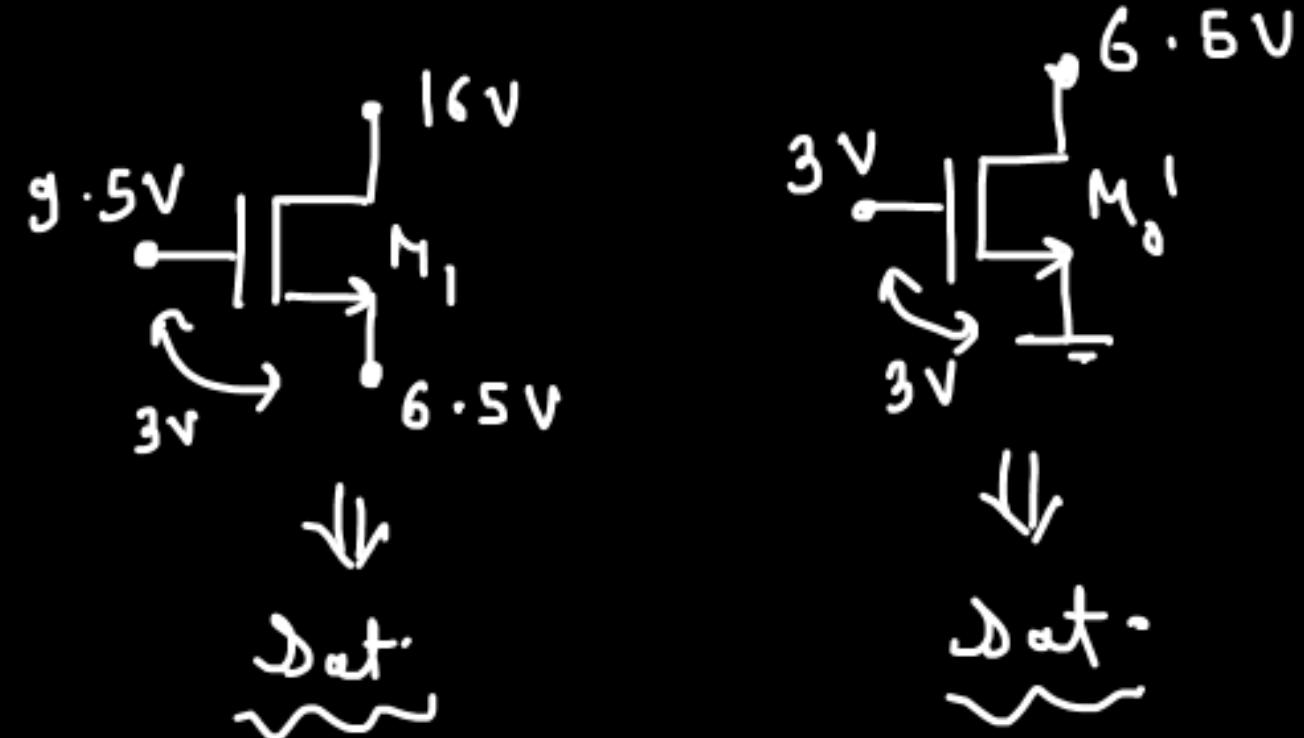
$$\delta t = \frac{2I_D}{V_{GS} - V_T} = \frac{9 \times 200 \mu}{3 - 1} = 200 \mu s$$





## AC Analysis:-

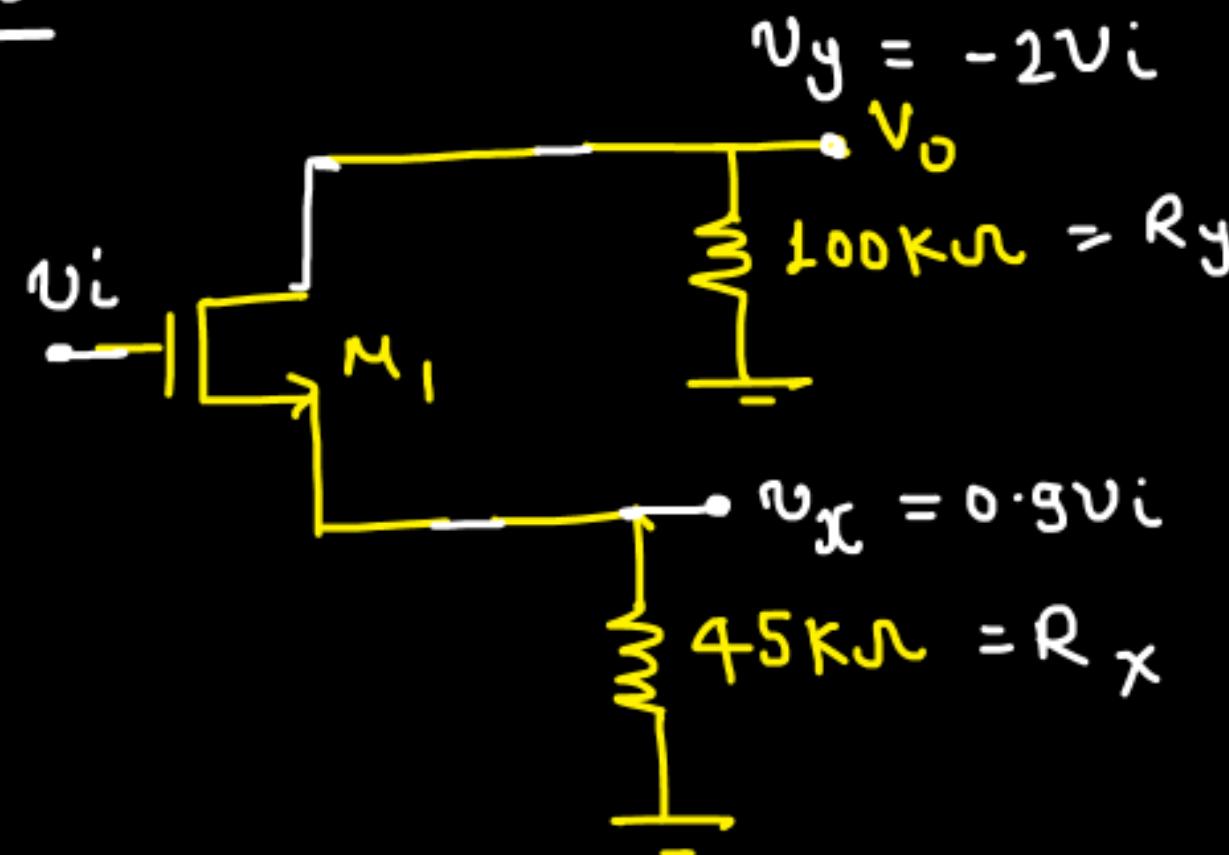

$$v_x = \frac{R_x}{R_x + 1/g_m} v_i = \frac{g_m R_x}{1 + g_m R_x} v_i = \frac{200\mu\text{A} \times 45\text{k}}{1 + 200\mu\text{A} \times 45\text{k}} v_i = 0.9 v_i$$
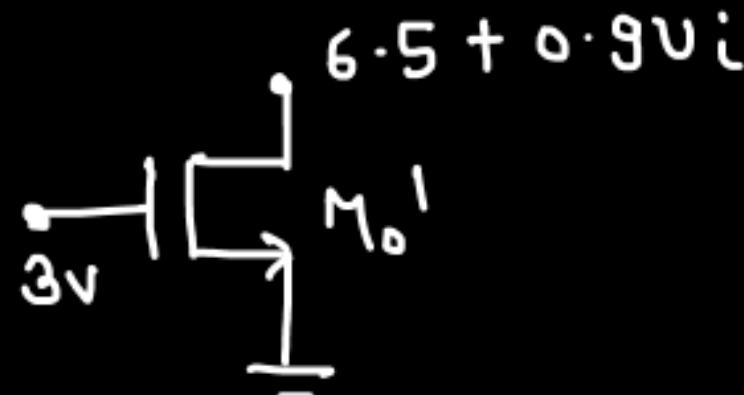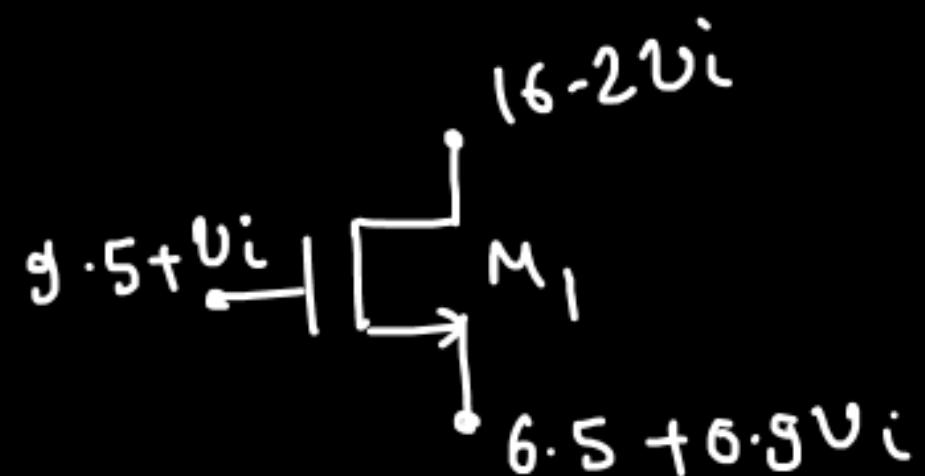
$$v_y = -\frac{g_m R_y}{1 + g_m R_x} v_i = \frac{-200\mu\text{A} \times 100\text{k}}{1 + 200\mu\text{A} \times 45\text{k}} v_i = \frac{-20}{10} v_i = -2 v_i$$



(a) For  $M_1$  to go into Triode:-

$$V_{DS} \leq V_{GS} - V_T$$

$$V_D - V_S \leq V_G - V_S - V_T$$

$$V_D \leq V_G - V_T$$

$$16 - 2V_i \leq 9.5 + V_i - 1$$


$$16 - 2V_i \leq 8.5 + V_i$$

$$\Rightarrow 7.5 \leq 3V_i$$

$$V_i \geq 2.5V$$

@  $V_i = 2.5V \Rightarrow Tr$  goes into triode.

(c) For  $M_o^1$

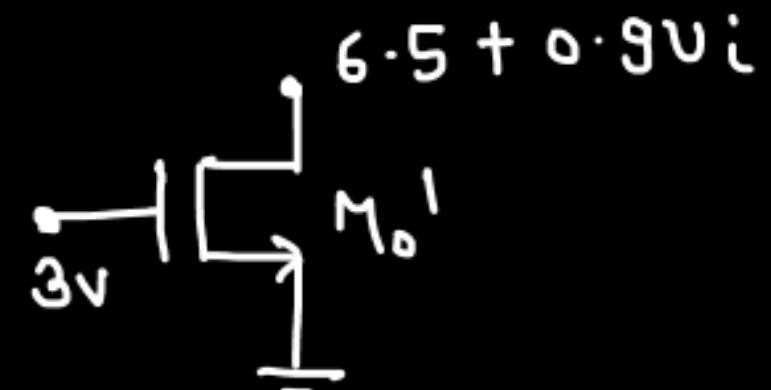

For cut off:-

$$v_{DS} \leq 0$$

$$6.5 + 0.9v_i \leq 0$$

$$0.9v_i \leq -6.5$$

$$v_i \leq -7.28V$$

For Triode ,


$$6.5 + 0.9v_i \leq 3 - 1$$

$$6.5 + 0.9v_i \leq 2$$

$$0.9v_i \leq -4.5$$

$$v_i \leq -5$$

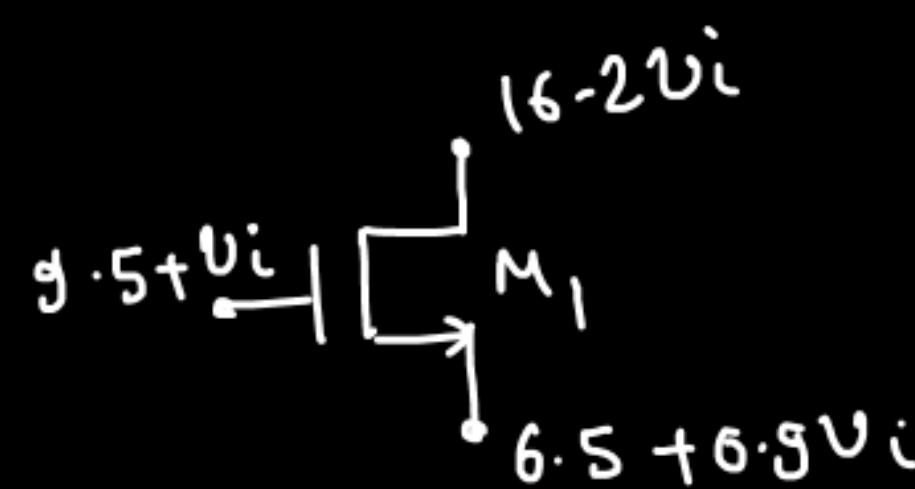@  $v_i = -5V \Rightarrow T_r M_o^1$  goes into Triode region



for cut off  $M_1$

$$\textcircled{1} \quad v_{DS} \leq 0$$

$$16 - 2v_i - 6.5 - 0.9v_i \leq 0$$

$$9.5 - 2.9v_i \leq 0$$

$$2.9v_i \geq 9.5$$


$$v_i \geq 3.21V$$

$$\textcircled{2} \quad v_{GS} \leq V_T$$


$$9.5 + v_i - 6.5 - 0.9v_i \leq 1$$

$$3 + 0.1v_i \leq 1$$

$$v_i \leq -20V$$

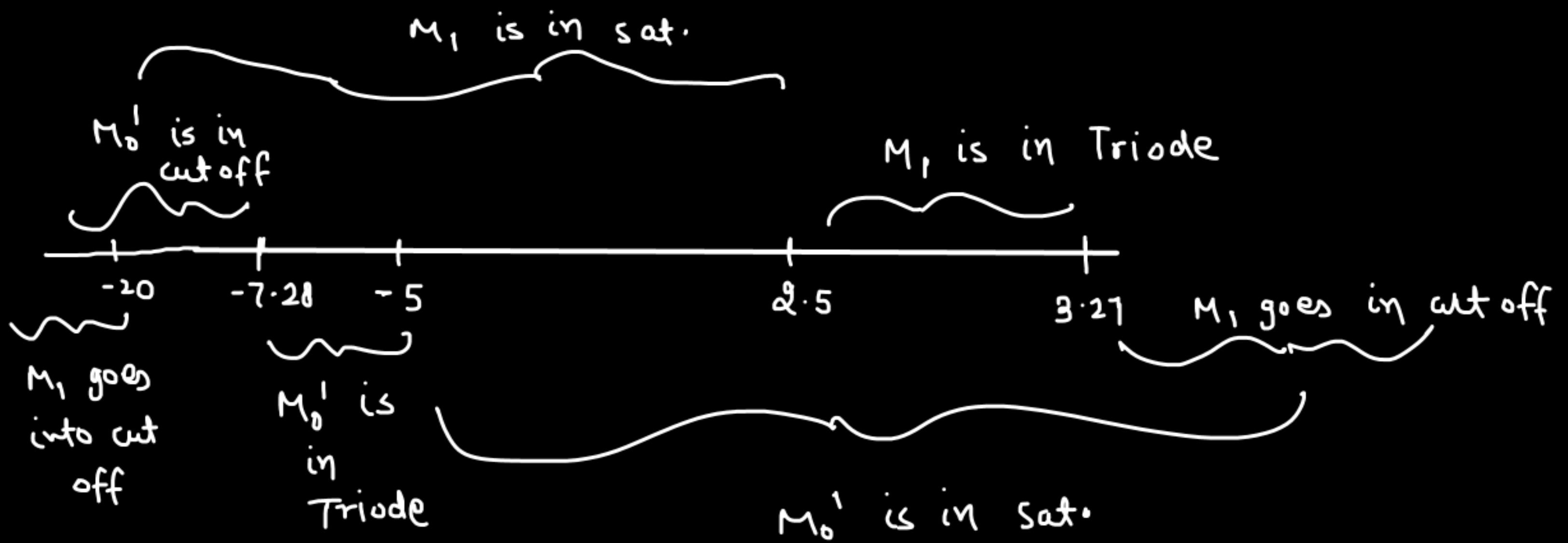

Q.

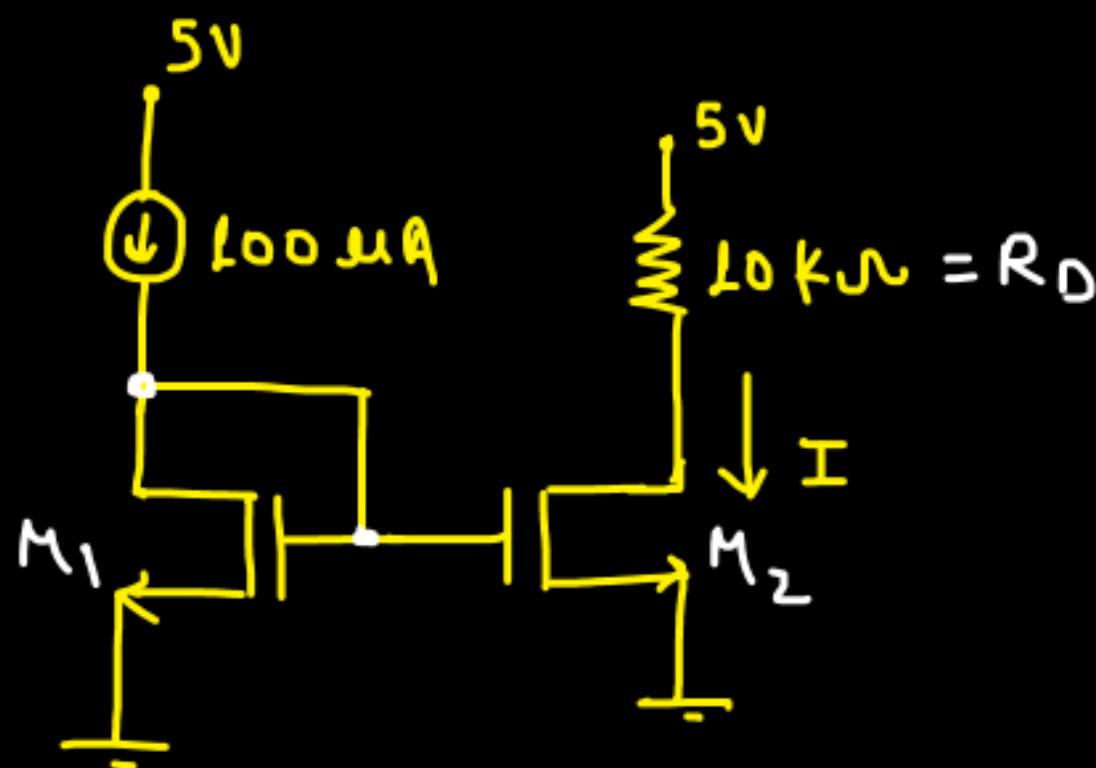

$$\frac{\text{UnCoax } \omega}{L} = \frac{50 \mu\text{A}}{V^2}$$

$$V_T = LV$$

$$\lambda = 0.01 \text{ V}^{-1}$$

find current  $I$  ?

~~(a)~~ 100  $\mu$ A

~~(b)~~ 100.96  $\mu$ Amp.

(c) 99.04  $\mu$ Amp

(d) 98.96  $\mu$ Amp

$$I = \frac{\mu_n C_{ox} \omega}{2L} (V_{DS} - V_T)^2 (1 + \lambda V_{DS})$$

$\lambda \neq 0$

$$I_{M_1} = \frac{\mu_n C_{ox} \omega}{2L} (V_{DS_1} - V_T)^2 (1 + \lambda V_{DS_1})$$

$$I_{M_2} = \frac{\mu_n C_{ox} \omega}{2L} (V_{DS_2} - V_T)^2 (1 + \lambda V_{DS_2})$$

{ let  $M_2$  is in sat }

$$\frac{I_{M_1}}{I_{M_2}} = \frac{1 + \lambda V_{DS_1}}{1 + \lambda V_{DS_2}}$$

For  $M_1$

$$100 \mu = \frac{50\mu}{2} (V_{GS} - 1)^2 (1 + \lambda V_{DS})$$

Since  $\lambda$  is very small, let  $\lambda V_{DS} \ll L$

$$V_{GS} = 3V$$

Here  $V_{GS} = V_{DS} = 3$

$$\lambda V_{DS} = 0.01 \times 3 = 0.03 \ll L \Rightarrow \text{considerable}$$



$$\frac{I_{M_1}}{I_{M_2}} = \frac{1 + \lambda(3)}{1 + \lambda[V_{DS_2}]}$$

$$V_{DS_2} = ? \quad , \quad I_M^{\text{net}} = x$$

$$V_{DS_2} = 5 - 10^4 x$$

$$\frac{100\mu}{x} = \frac{1+3x}{1+x[5-10^4x]}$$

$$10^{-4}[1+5x - x \times 10^4 x] = x + (3x)x$$

$$10^{-4} + 5 \times 10^{-4}x - x^2 = x + (3x)x$$

$$(10^{-4} + 0.05x)10^{-4} = x + 0.04x$$

$$1.05 \times 10^{-4} = 1.04 x$$


$$x = \frac{1.05 \times 10^{-4}}{1.04} = 100.96 \mu \text{Amp.}$$

if  $R_D = 20 \text{ k}\Omega$   $\Rightarrow I_{M_2} = 100 \mu\text{Amp}$ .  
[Perfectly matched  $V_{DS}$ ]

if  $R_D = 10 \text{ k}\Omega$   $\Rightarrow I_{M_2} > 100 \mu\text{Amp}$ .  
 $[V_{DS_2} > V_{DS_1}]$

if  $R_D = 25 \text{ k}\Omega$   $\Rightarrow I_{M_2} < 100 \mu\text{Amp}$ .  
 $[V_{DS_2} < V_{DS_1}]$

Q.

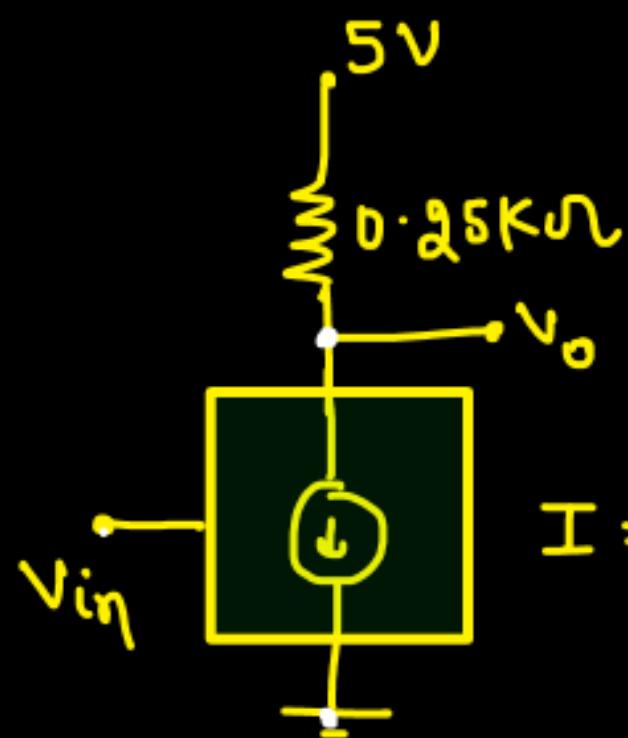

$$I = [v_{in}^2 + 2v_{in} + 1] [1 + 0.05v_o] \text{ mA}$$

Yellow-box is a three terminal element.  $V_{in-Q} = 1V$

find small signal voltage gain  $\frac{V_{in}}{V_o} = ?$  (approx)

~~(a)~~ -0.95

(b) -19.5

(c) -49.5

(d) -99.5

→ for MOS:-

$$I_D = k_n [V_{GS} - V_T]^2 [1 + \gamma V_{DS}]$$


for given problem,

$$I = [V_{in}^2 + 2V_{in} + 1] [1 + 0.05 V_0] \text{ mA}$$


$$g_m = \frac{\partial I}{\partial V_{in}} = 2V_{in} + 2 \text{ mA} \quad \left\{ \text{Assuming } 1 + 0.05 V_0 \ll 1 \right\}$$

$$\boxed{(g_m)_{V_{in}=1V} = 4 \text{ mS}}$$
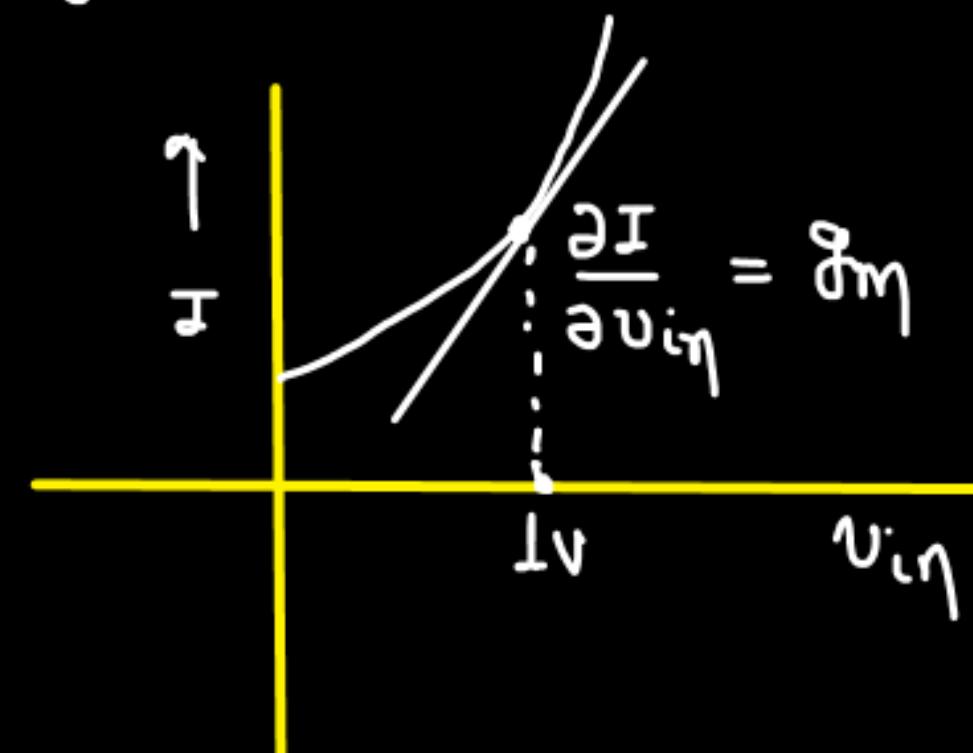
$$\gamma_0 = \frac{1}{\frac{\partial I}{\partial V_0}} = \frac{10^3}{(V_{in}^2 + 2V_{in} + 1)(0.05)}$$


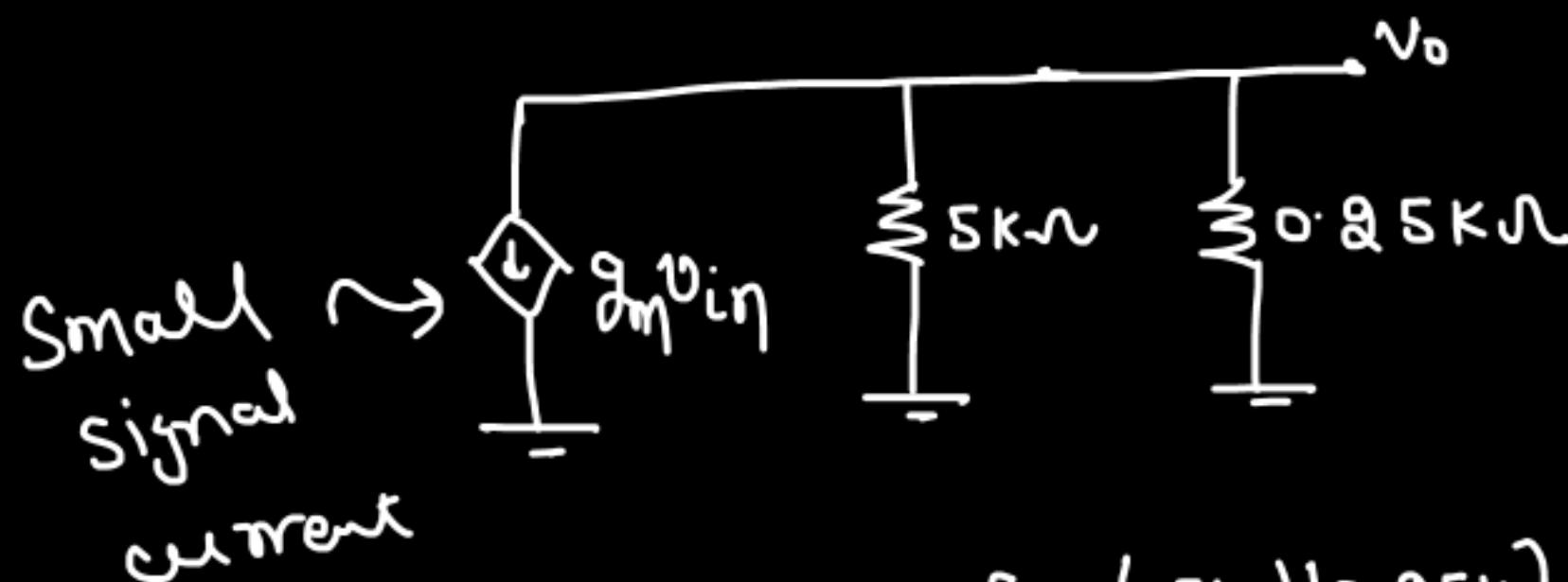
$$(r_d)_{V_{in-Q}=1} = \frac{10^3}{44005} = 5 \text{ k}\Omega$$




$$\begin{aligned} V_o &= -g_m (5k \parallel 0.25k) V_{in} \\ &= -4m \times 0.238k \times V_{in} \end{aligned}$$

$$\frac{V_o}{V_{in}} = -0.95 \text{ V/V}$$

Ans =

Q.

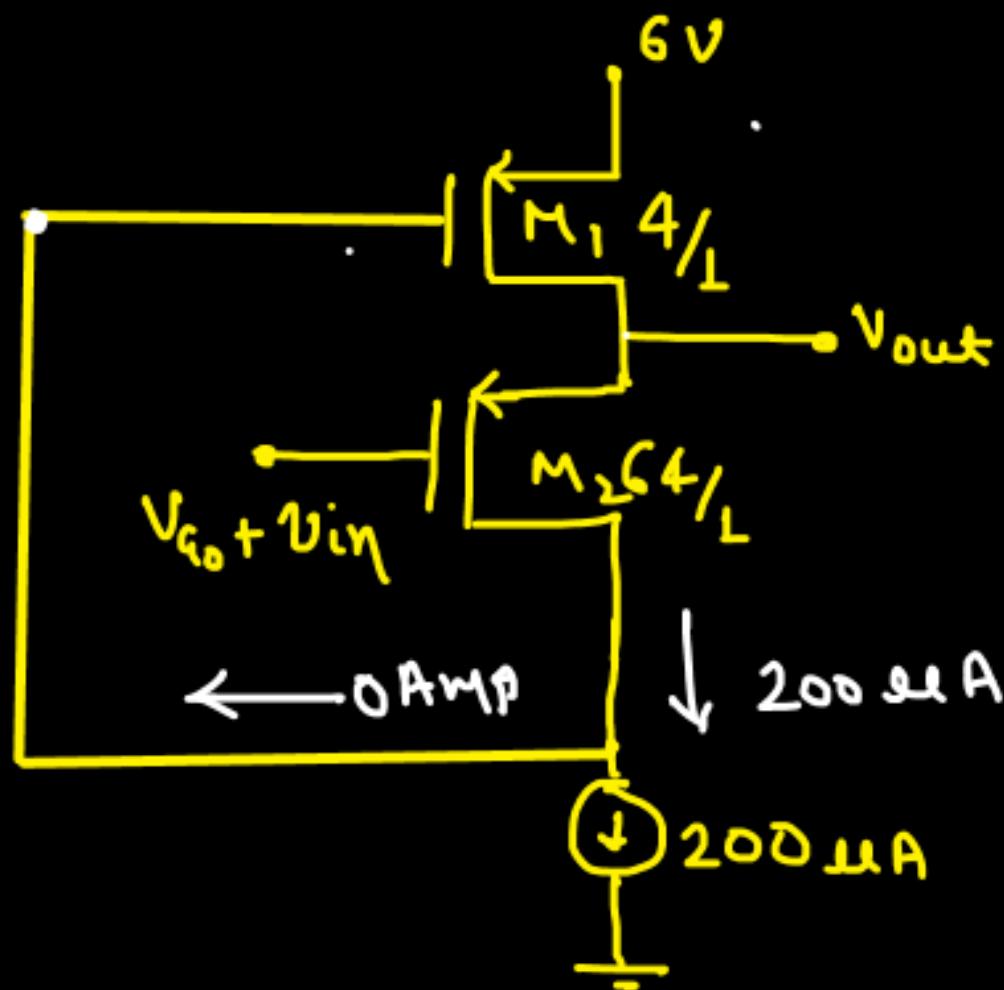

$$\mu_{pox} = 25 \mu A/V^2$$

$$V_T = 1V$$

$$V_{in} = V_p \cos(\omega t)$$


V<sub>g<sub>o</sub></sub> is set such that it maximizes V<sub>p</sub> that can be applied while keeping all the Tr. in sat. region.

- (a) Find optimum value of V<sub>g<sub>o</sub></sub>      (b) find max value of V<sub>p</sub>.

$$I_{M_1} = 200 \mu A$$

$$\Rightarrow 200\mu = \frac{25\mu \times 4}{2} (V_{SG_{M_1}} - 1)^2$$


$$V_{SG_{M_1}} = 3V$$

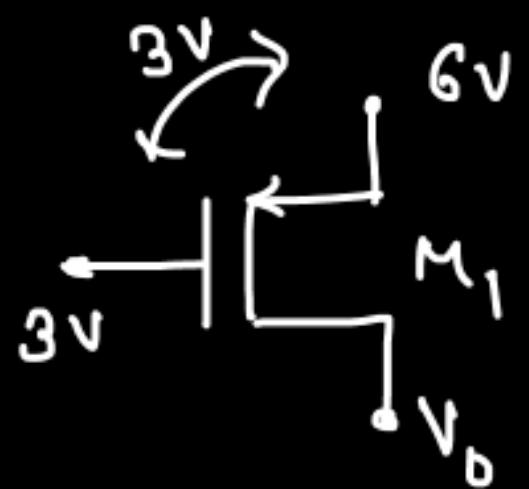

$$I_{M_2} = 200 \mu A$$



$$\Rightarrow 200\mu = \frac{25\mu \times 64}{2} (V_{SG_{M_2}} - 1)^2$$

$$V_{SG_{M_2}} = 1.5V$$

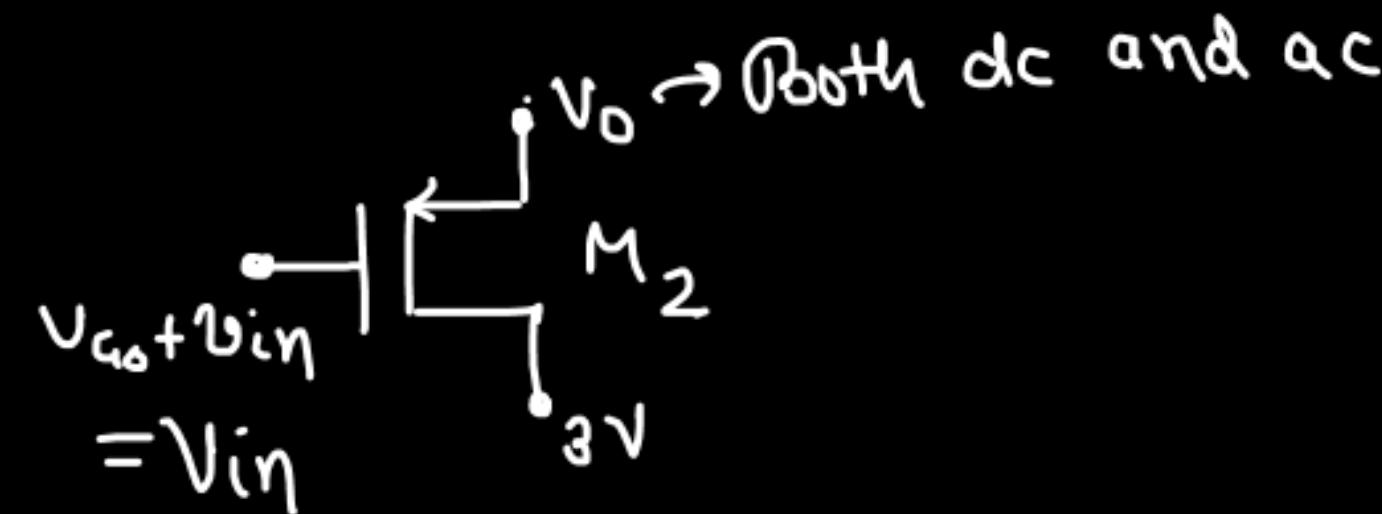

$$V_o - V_{in} = 1.5$$

$$V_o = 1.5 + V_{in}$$

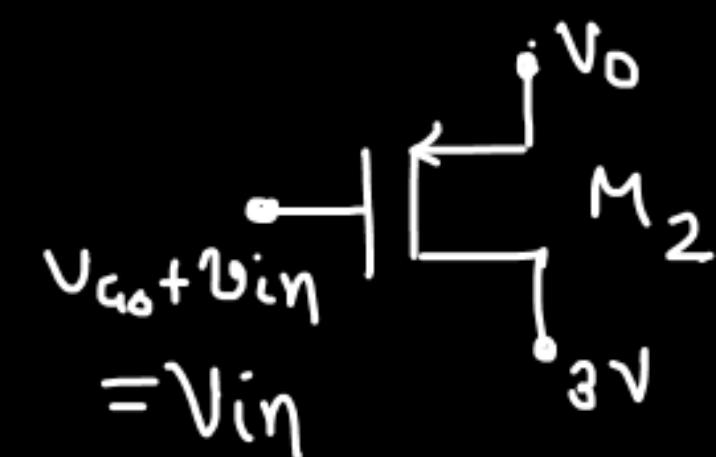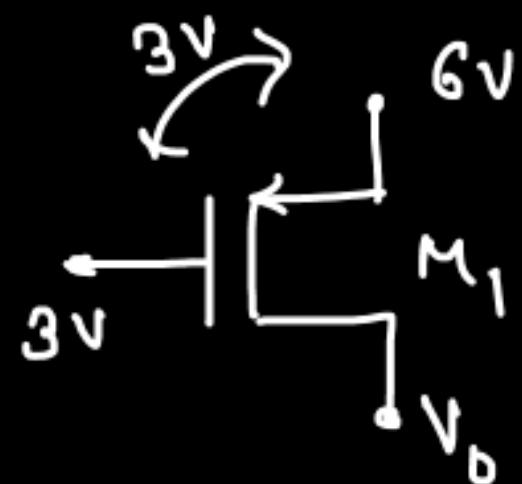

For sat.

$$6 - V_o \geq 6 - 3 - 1$$

$$6 - V_o \geq 2$$

$$V_o \leq 4$$

$$1.5 + V_{in} \leq 4$$

$$V_{in} \leq 2.5V$$

$$V_o - 3 \geq V_o - V_{in} - 1$$

$$-3 \geq -V_{in} - 1$$

$$V_{in} \geq 2$$

~~sat~~

$$2.3 \quad 0.2$$

$$V_{in} = V_{co} + V_{in}$$

$$= V_{co} + V_p \cos \omega t$$

$$(V_{in})_{\max} = V_{co} + V_p, \quad (V_{in})_{\min} = V_{co} - V_p$$

$$V_{Q_0} - V_p = 2$$


$$V_{Q_0} + V_p = 2 \cdot 5$$

$$V_{Q_0} = 2 \cdot 2.5 V$$

$$V_p = 0 \cdot 25 V$$

Aus

aus

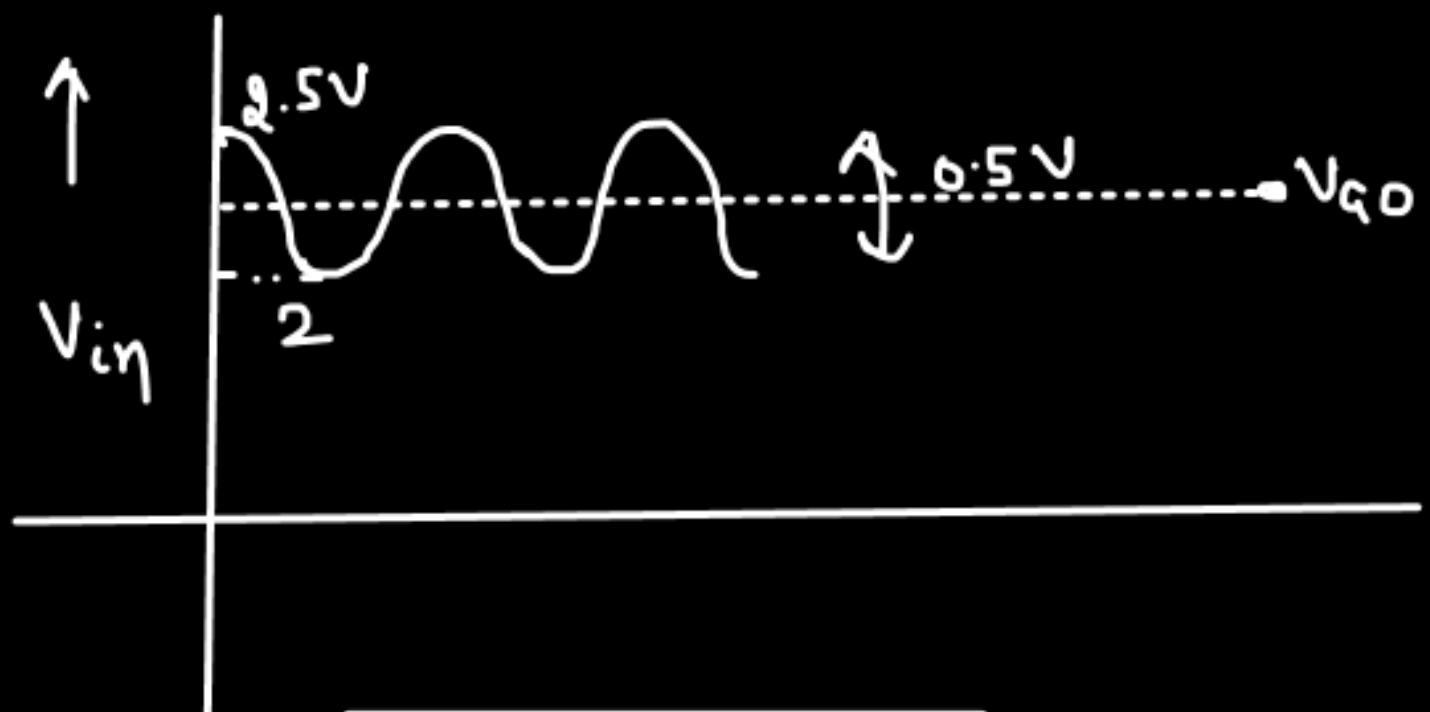


$$\begin{array}{c} 2 < V_{Q_0} < 2.5 \\ \downarrow \quad \downarrow \\ 0.5 > V_p > 0 \end{array}$$


## ⇒ Some Miscellaneous Topics :-
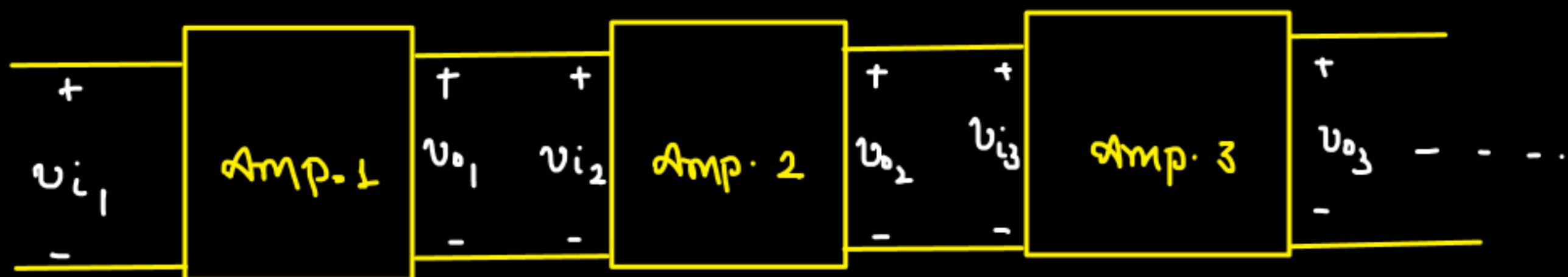
### \* Multi-stage Amplifiers (Cascade Amplifiers) :-

A series of amplifier in which each amplifier connects its o/p to the i/p of next amplifier in the chain.



Eg. →

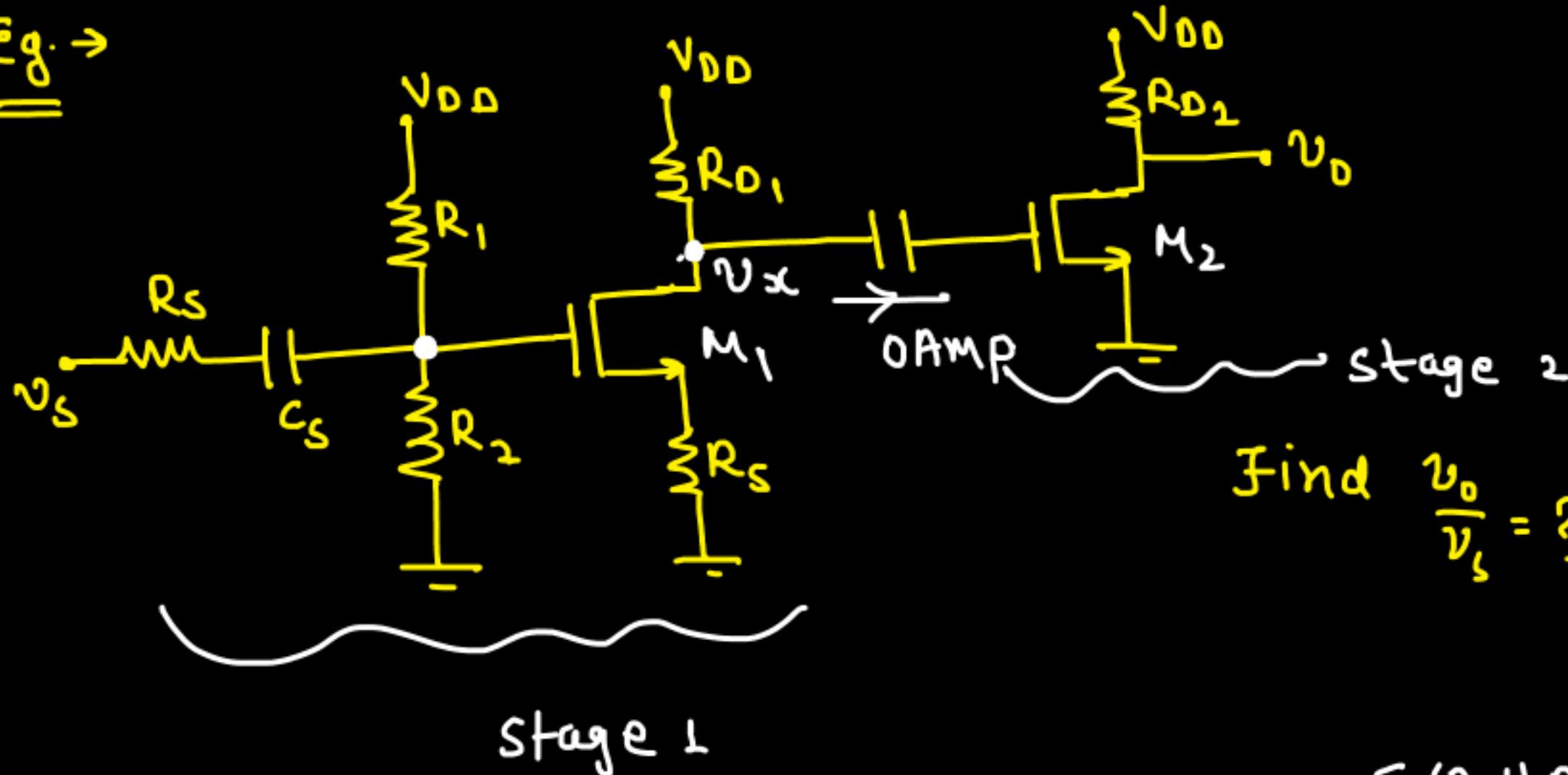

Find  $\frac{v_o}{v_s} = ?$

$$\frac{v_x}{v_s} = -\frac{g_m R_{D1}}{(g_m R_s + g_m R_{D1})} \left[ \frac{(R_1 || R_2)}{(R_1 || R_2) + R_s} \right] \quad \textcircled{1}$$


$$\frac{v_o}{v_x} = -g_m R_{D2} \quad \textcircled{2}$$

multiply eqn ① with eqn ②

$$\frac{v_s}{v_b} \times \frac{v_0}{v_s} = \boxed{\frac{v_0}{v_s} = \left[ g M_2 R_D 2 \right] \left[ \frac{g M_1 R_D 1}{1 + g M_1 R_S} \right] \left[ \frac{(R_1 || R_2)}{(R_1 || R_2) + R_S} \right]}$$

\* \* \*

②

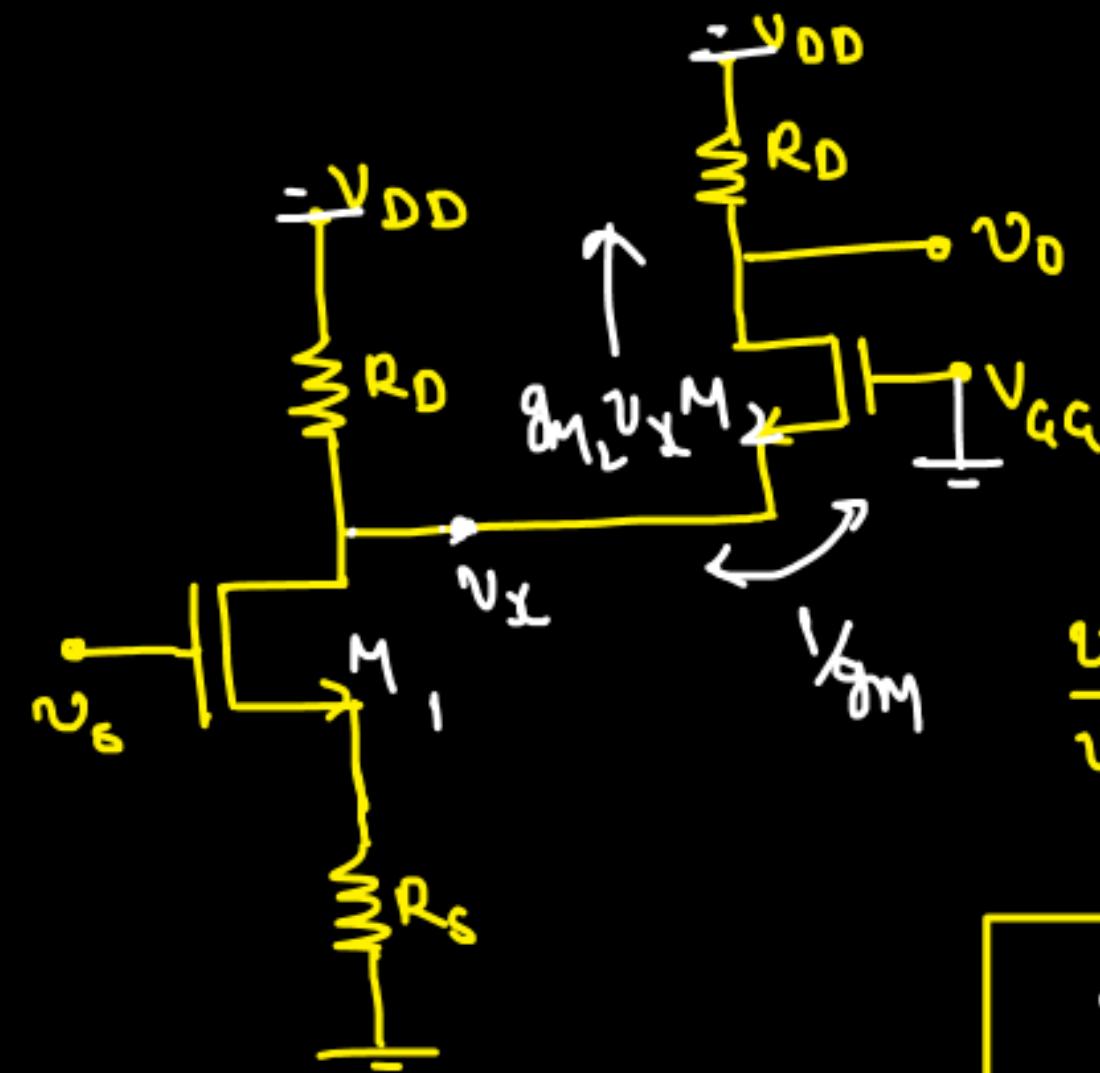

$$\frac{v_o}{v_s} = ? \quad [\text{Small signal voltage gain}]$$

$$\boxed{\frac{v_o}{v_s} = -\frac{g_m R_D}{1 + g_m R_S}} \quad \times$$

$$\frac{v_o}{v_s} = \frac{-g_{m_1} [R_D \parallel \frac{1}{g_{m_2}}]}{1 + g_{m_1} R_S} \rightarrow 0$$

$$\frac{v_x}{v_0} = ?$$

$$v_0 = g_m v_x R_D$$


$$\frac{v_0}{v_x} = g_m R_D - \textcircled{2}$$

\* \* \*

$$\frac{v_0}{v_x} = -g_m R_D \times \frac{g_m [R_D || \frac{1}{g_m}]}{1 + g_m R_S}$$
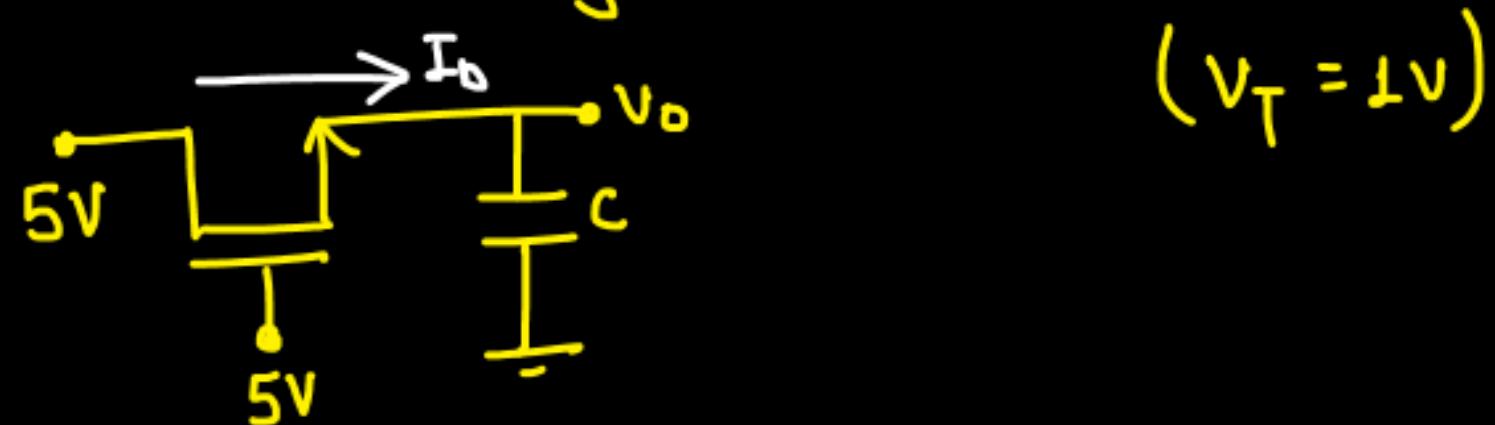
## Concept of Pass Transistor Logic:-

Q. Find the steady state value of  $V_o$ .



(a)

@  $t=0^+$ ,  $V_o = 0V$

$$V_{DS} = 5V$$

$V_{GS} = 5V \Rightarrow T_r \text{ is ON}$

$$V_T = 1V$$

if  $T_r$  is ON  $\Rightarrow 5V$  from drain  
will charge the capacitor

When  $I_D = 0 \text{ Amp} \Rightarrow$  No charging  
on cap.

↓  
Steady state

$I_D > 0 \Rightarrow$  cap. will be charging




$$\textcircled{1} \quad V_{DS} > V_T \Rightarrow 5 - V_D > 1 \Rightarrow V_D \leq 4 \Rightarrow V_D \leq 4V$$


$$\textcircled{2} \quad V_{DS} > 0 \Rightarrow 5 - V_D > 0 \Rightarrow V_D \leq 5$$




$$(V_D)_{\text{req}} = 4V$$

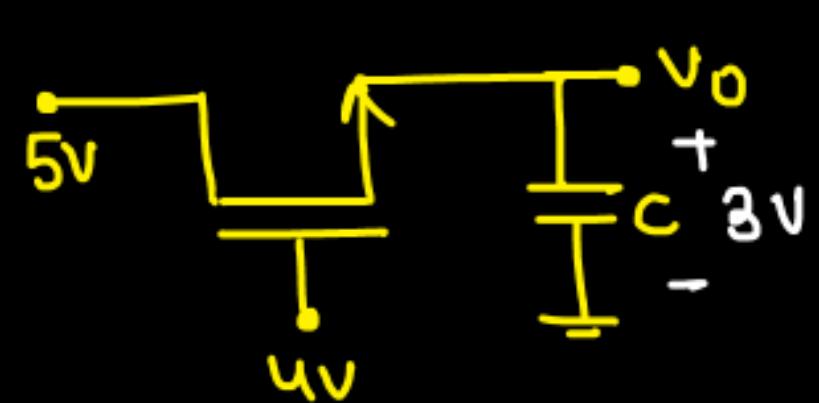


(b)

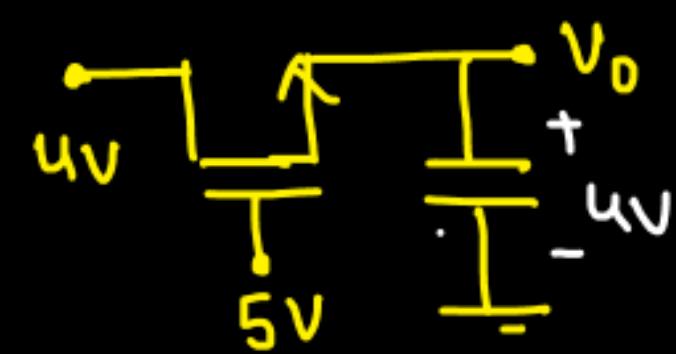

(c)

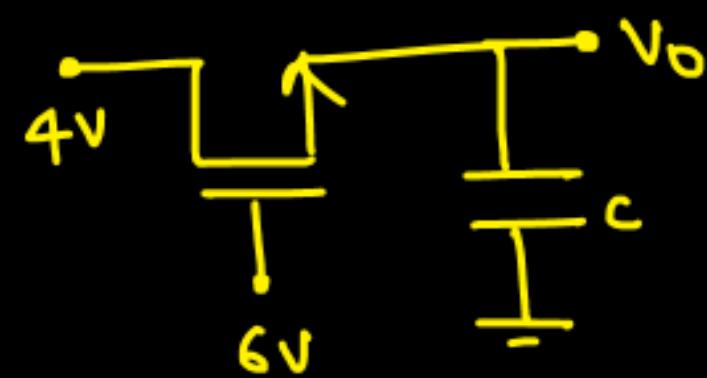

(D)

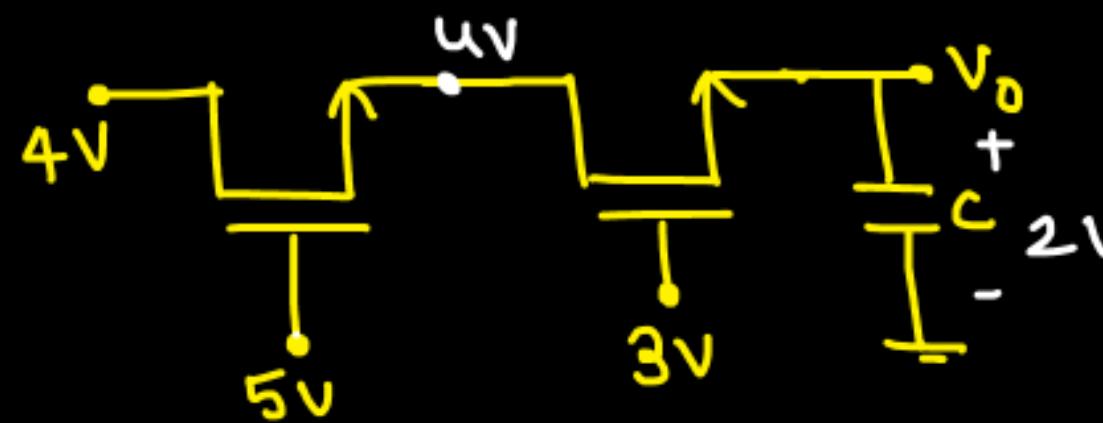

(E)

$$v_{ds} > v_T - \textcircled{1}$$


$$6 - v_o > 1$$

$$v_o \leq 5V$$


$$v_{ds} > 0 - \textcircled{2} \Rightarrow v_o = 4V$$

$$4 - v_o > 0$$



$$v_o \leq 4V$$


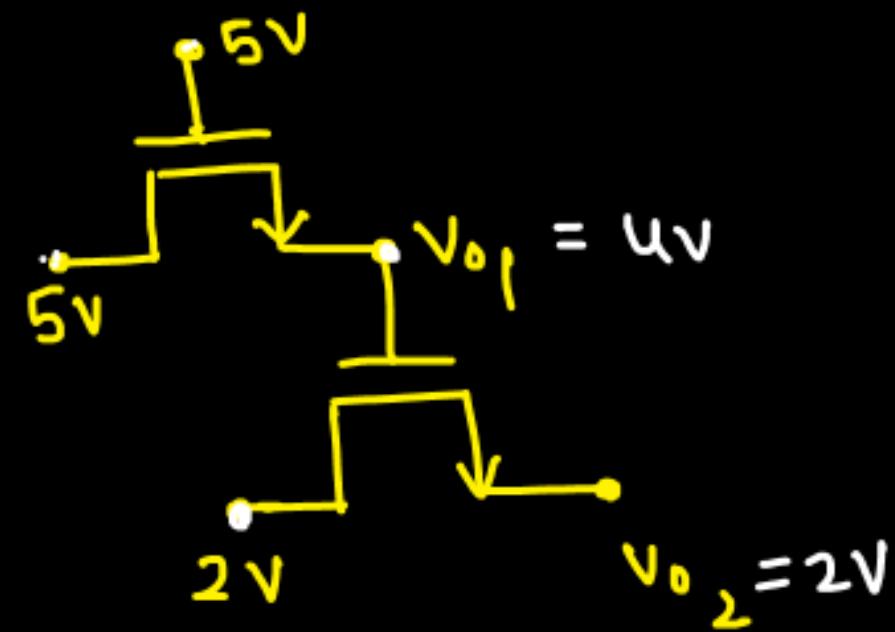


(F)

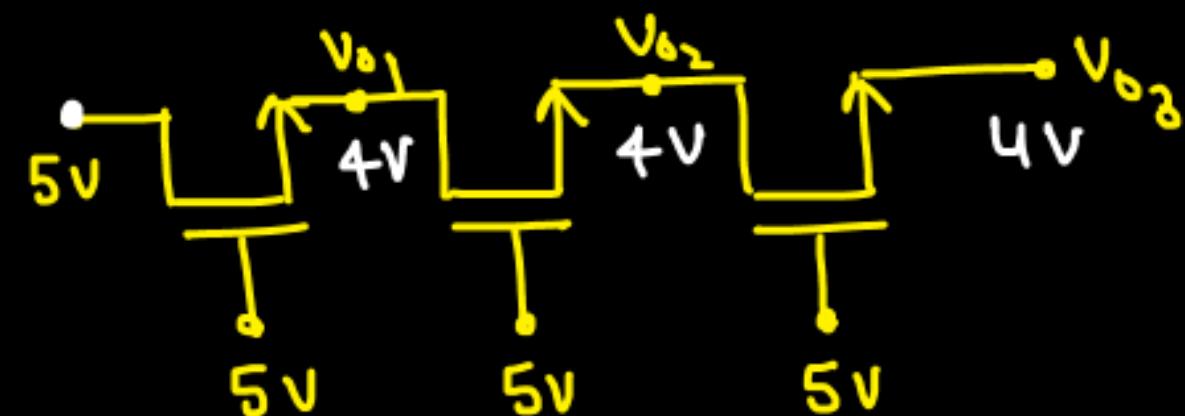

(G)

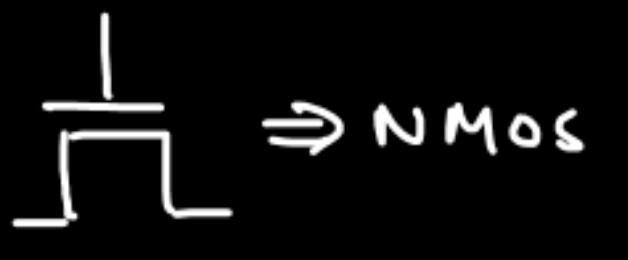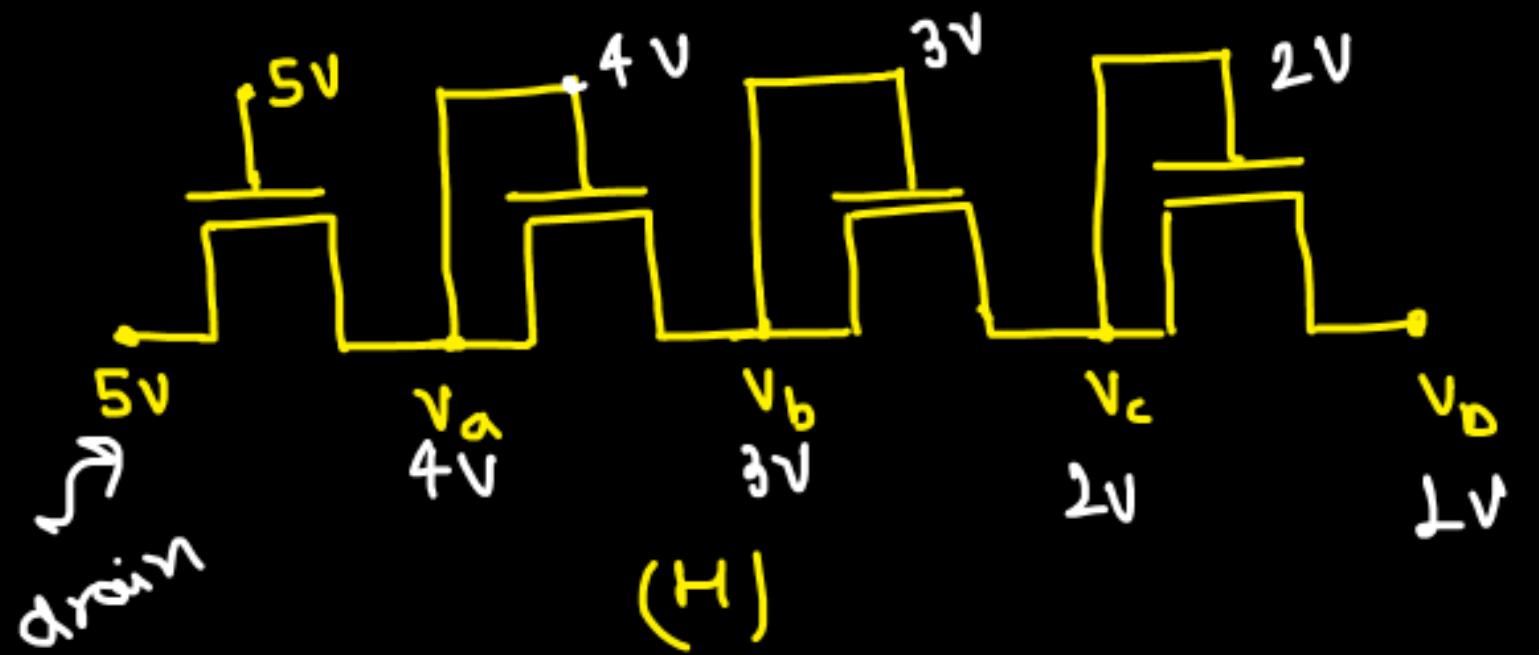

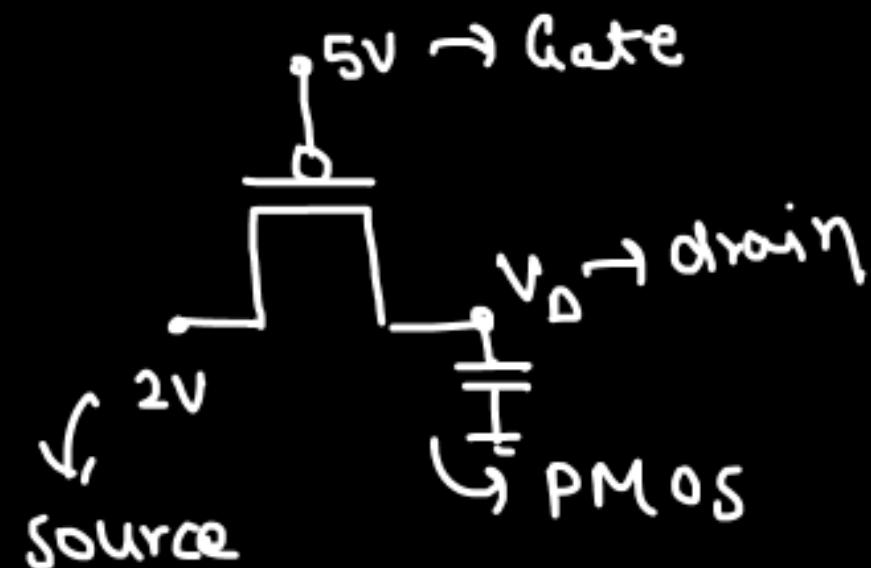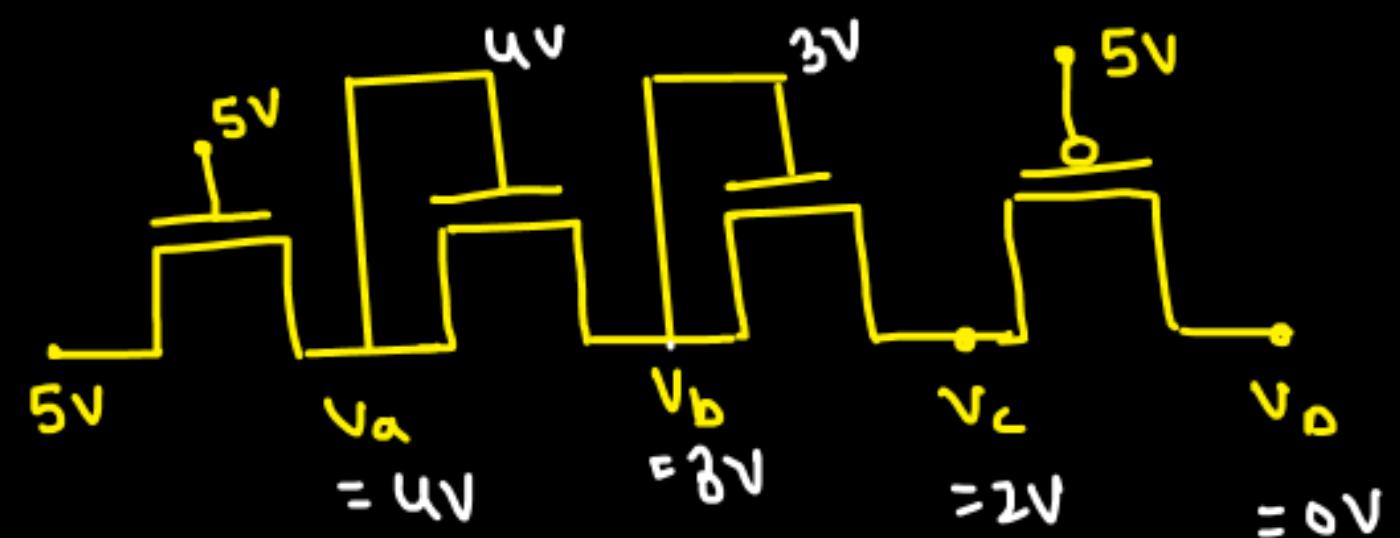


H·P → Source  
L·P → Drain

$$V_{SG} = 2 - 5 = -3V$$

↓  
MOS is off

↖  
No charging for  $V_D$

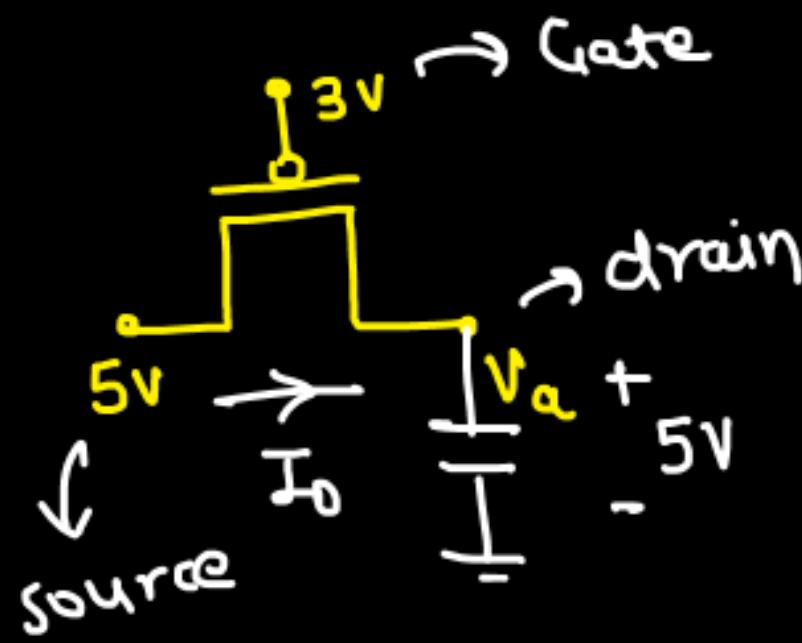

$$V_{SG} = 5 - 3 = 2V > V_T \Rightarrow \text{always}$$


$T_r$  can turn off only when

$$V_{SD} = 0$$

$$5 - V_0 = 0$$

$$(V_0)_{S.S.} = 5V$$

Q

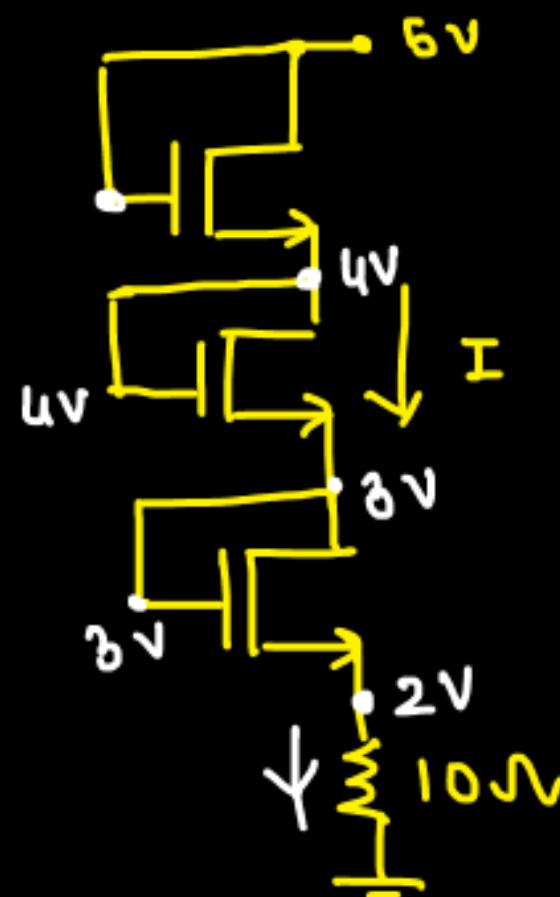


steady state  $I = ?$

$$I = \frac{2}{10} = 0.2 \text{ Amp.}$$

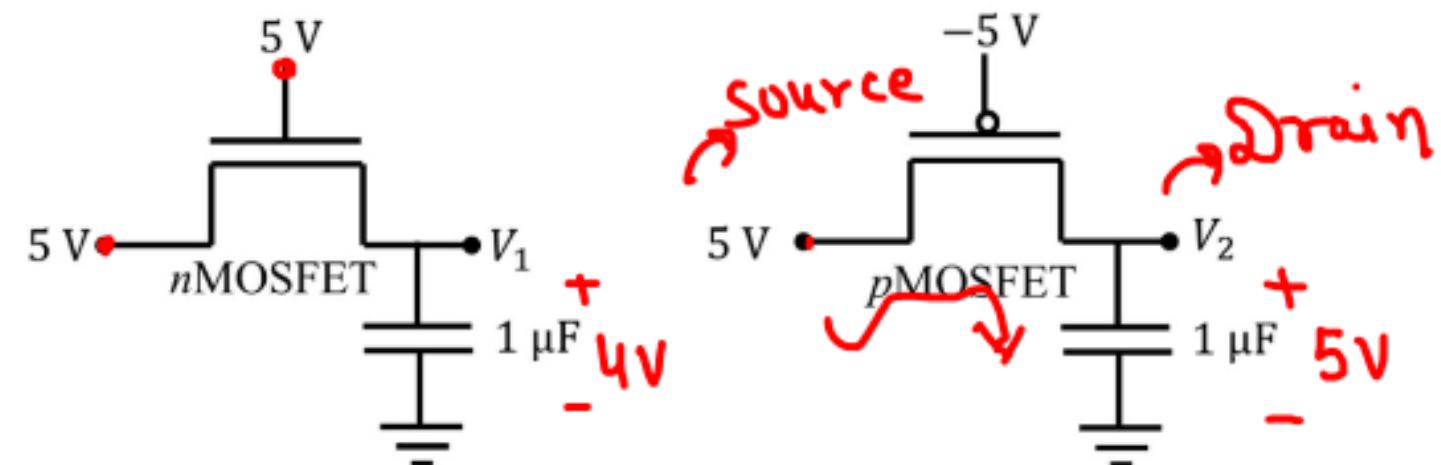Q.20

The ideal long channel *n*MOSFET and *p*MOSFET devices shown in the circuits have threshold voltages of 1 V and  $-1$  V, respectively. The MOSFET substrates are connected to their respective sources. Ignore leakage currents and assume that the capacitors are initially discharged. For the applied voltages as shown, the steady state voltages are \_\_\_\_\_.



(A)  $V_1 = 5 \text{ V}, \quad V_2 = 5 \text{ V}$

$$V_{SG} = 5 - (-5) = 10 \text{ V}$$

(B)  $V_1 = 5 \text{ V}, \quad V_2 = 4 \text{ V}$

4

(C)  $\checkmark V_1 = 4 \text{ V}, \quad V_2 = 5 \text{ V}$

 $T_r = 0 \text{ N}$ 

(D)  $V_1 = 4 \text{ V}, \quad V_2 = -5 \text{ V}$

# Frequency Response of MOS

## Pre-requisites:-

Transfer f<sup>n</sup>, pole, zero, Bode plot.

LAUNCHING  
**ANALOG VLSI MASTERY : COHORT (0-10)**

60 HRS OF VIDEO CONTENT ✓  
COMPLETE CLASS NOTES ✓  
ASSIGNMENTS ✓  
DOUBT SOLVING GROUP ✓

▶ PLAY ALL

FREE YOUTUBE COURSE!!



HIMANSHU AGARWAL  
ANALOG

Analog VLSI Mastery : Cohort (0-10) || Himanshu Agarwal || PrepFusion  
Himanshu Agarwal · Playlist  
Analog VLSI Mastery : Cohort (0-10) || Free YouTube Course || Himanshu Agarwal || @PrepFusion\_GA... • 12:03  
Day to Day Roadmap to Complete Analog VLSI Mastery : Cohort (0-10) • 10:21  
VIEW FULL PLAYLIST

42

NETWORK ANALYSIS  
TRANSIENT ANALYSIS

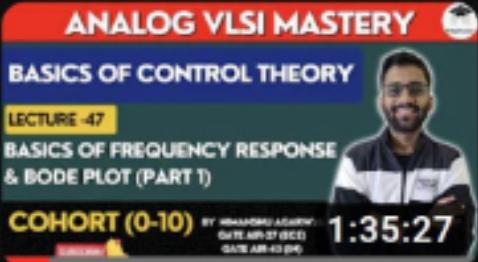
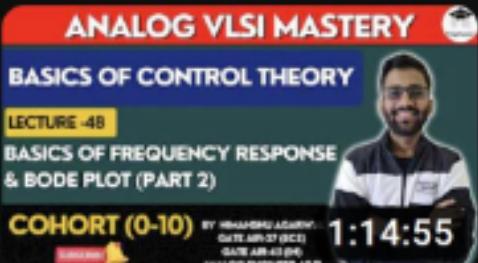
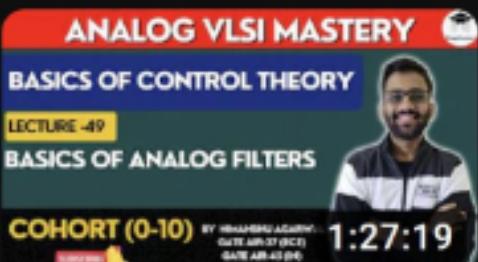
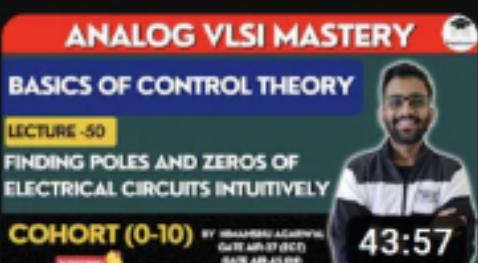
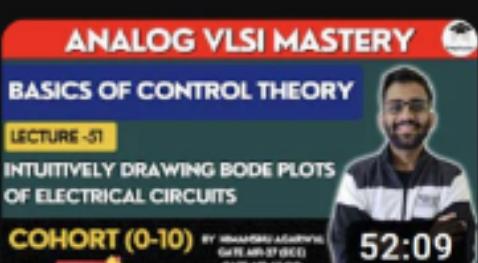
LECTURE-40  
BASICS OF CONTROL SYSTEMS  
IN ELECTRICAL CIRCUITS

GATE 2025-26 BY HIMANSHU AGARWAL  
50:26


Basics of Control Systems in Electrical Circuits || Network Analysis || GATE  
2025-26 || PrepFusion

PrepFusion - GATE • 493 views • 2 months ago

: v

- 19  **Basics of Frequency Response & Bode Plot (Part 1) || Analog VLSI Mastery (Cohort 0-10)**  
Himanshu Agarwal • 708 views • 2 months ago  
**LECTURE -47**  
**BASICS OF FREQUENCY RESPONSE & BODE PLOT (PART 1)**  
**COHORT (0-10)** BY HIMANSHU AGARWAL  
1:35:27
- 50  **Basics of Frequency Response & Bode Plot (Part 2) || Analog VLSI Mastery (Cohort 0-10)**  
Himanshu Agarwal • 323 views • 2 months ago  
**LECTURE -48**  
**BASICS OF FREQUENCY RESPONSE & BODE PLOT (PART 2)**  
**COHORT (0-10)** BY HIMANSHU AGARWAL  
1:14:55
- 51  **Basics of Analog Filters || Analog VLSI Mastery (Cohort 0-10) || Himanshu Agarwal**  
Himanshu Agarwal • 688 views • 2 months ago  
**LECTURE -49**  
**BASICS OF ANALOG FILTERS**  
**COHORT (0-10)** BY HIMANSHU AGARWAL  
1:27:19
- 52  **Finding Poles and Zeros of Electrical Circuits Intuitively || Analog VLSI Mastery (Cohort 0-10)**  
Himanshu Agarwal • 418 views • 2 months ago  
**LECTURE -50**  
**FINDING POLES AND ZEROS OF ELECTRICAL CIRCUITS INTUITIVELY**  
**COHORT (0-10)** BY HIMANSHU AGARWAL  
43:57
- 53  **Intuitively Drawing Bode Plots of Electrical Circuits || Analog VLSI Mastery (Cohort 0-10)**  
Himanshu Agarwal • 364 views • 2 months ago  
**LECTURE -51**  
**INTUITIVELY DRAWING BODE PLOTS OF ELECTRICAL CIRCUITS**  
**COHORT (0-10)** BY HIMANSHU AGARWAL  
52:09

Q. Draw the bode plot for given RC ckt.

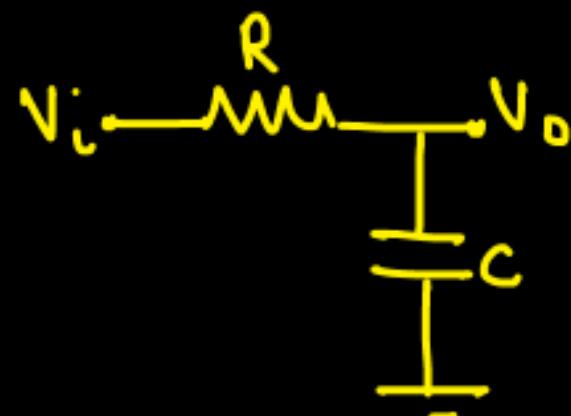

$$R = 2 \Omega$$


$$C = 1 F$$

For which value of  $V_i$  ckt will have the max<sup>m</sup> attenuation?

$$V_i = 50mV \sin\left(\frac{t}{4}\right) \rightarrow 0.25 \text{ rad/sec}$$

$$V_i = 50mV \sin(2t) \rightarrow 2 \text{ rad/sec}$$

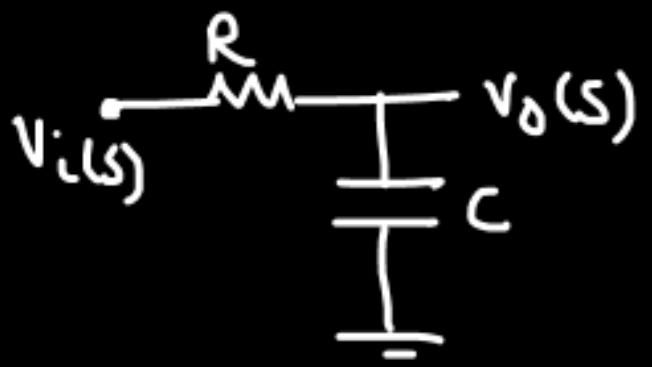
$$V_i = 50mV \sin(20t) \rightarrow 20 \text{ rad/sec}$$




$$\frac{v_o(s)}{v_i(s)} = \frac{1}{1 + RCS}$$

$$\omega_p = -\frac{1}{RC}, \quad \omega_L = \infty$$
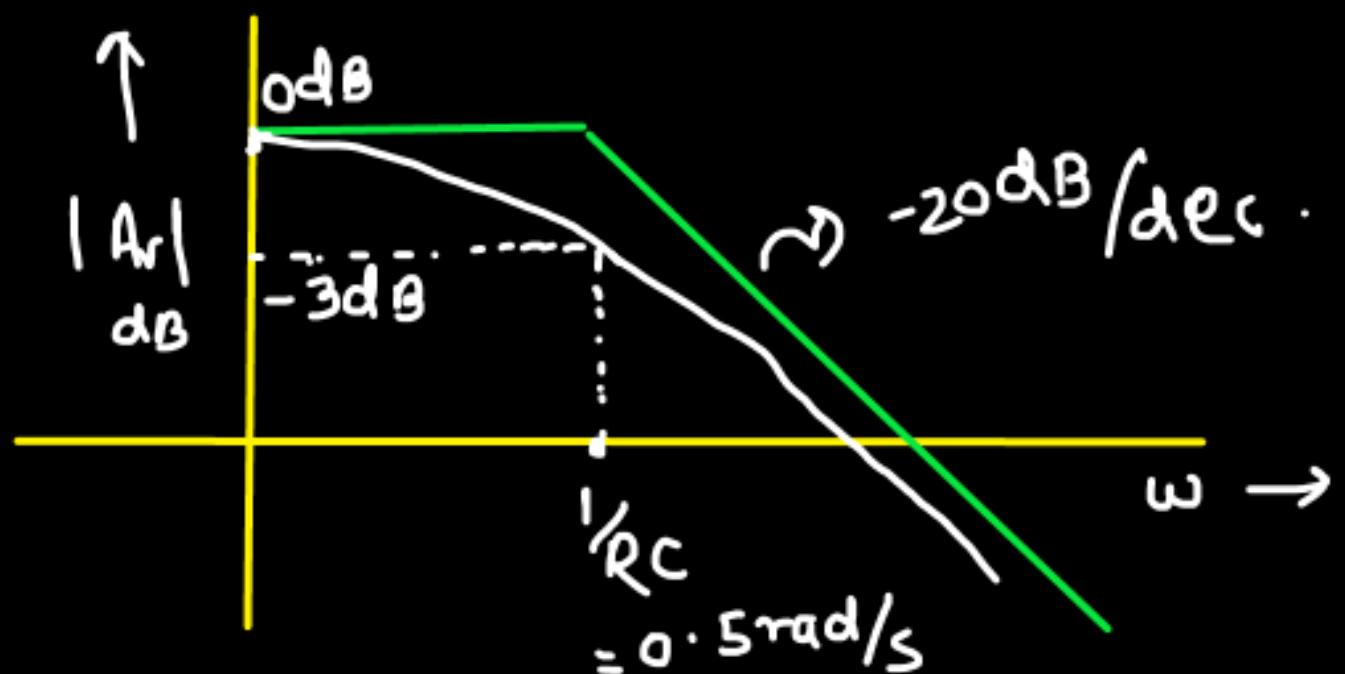
$$\omega_p = -\frac{1}{2\pi f} = -0.5 \text{ rad/sec}$$



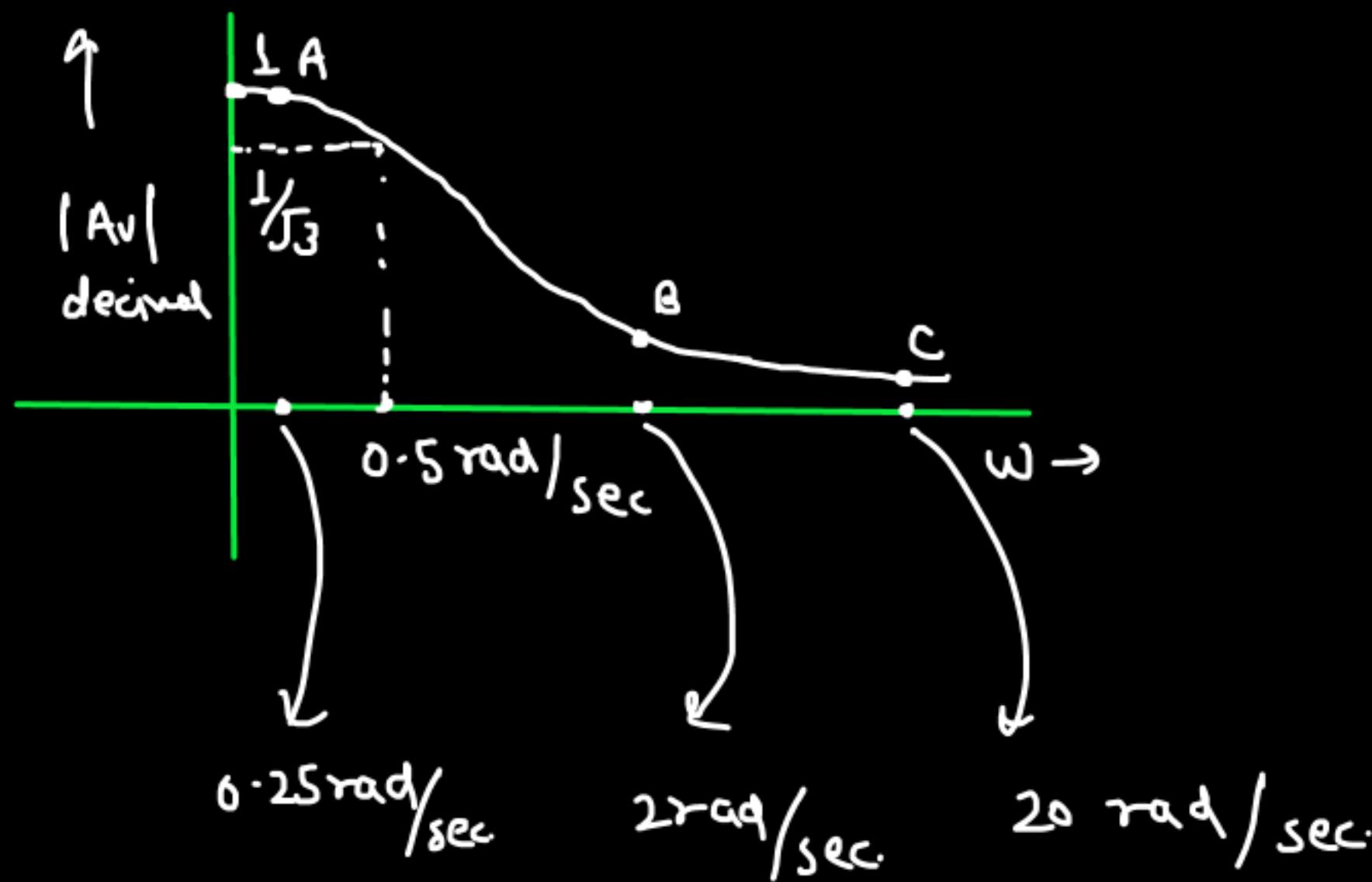


$$\left(\frac{V_o}{V_i}\right)_{0.25 \text{ rad/sec.}} > \left(\frac{V_o}{V_i}\right)_{2 \text{ rad/sec.}} > \left(\frac{V_o}{V_i}\right)_{20 \text{ rad/sec.}}$$

$\Downarrow$   
max gain  $\Rightarrow$  min attenuation


$\Downarrow$   
min gain = max<sup>m</sup> attenuation

Q. Plot the frequency response.

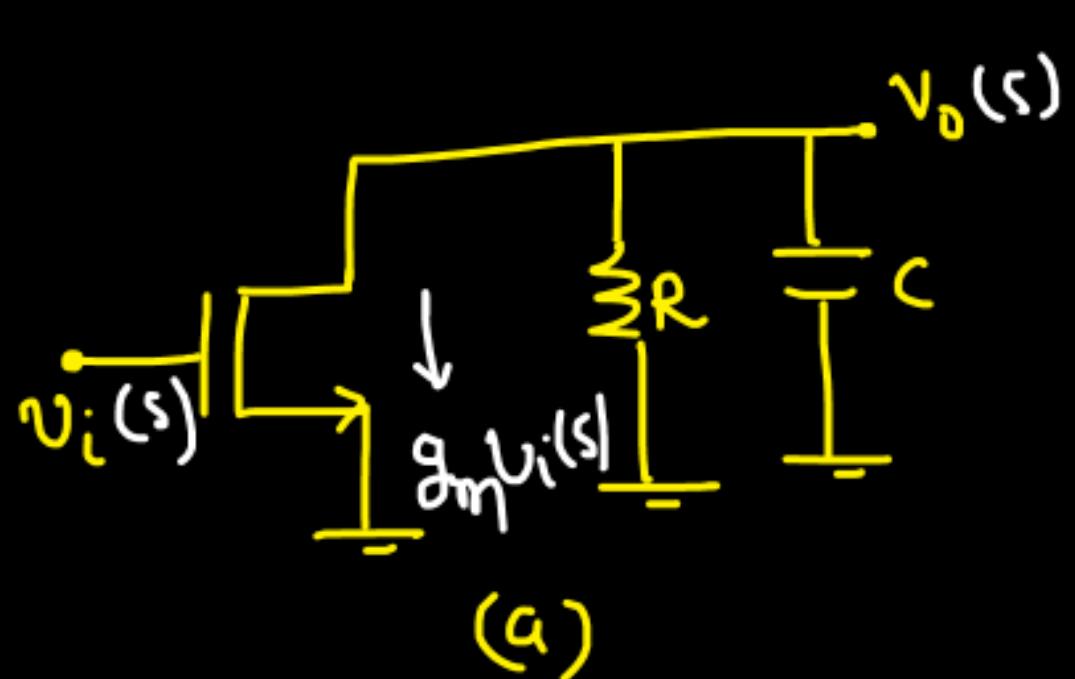

$$\frac{V_o(s)}{V_i(s)} = ?$$


→

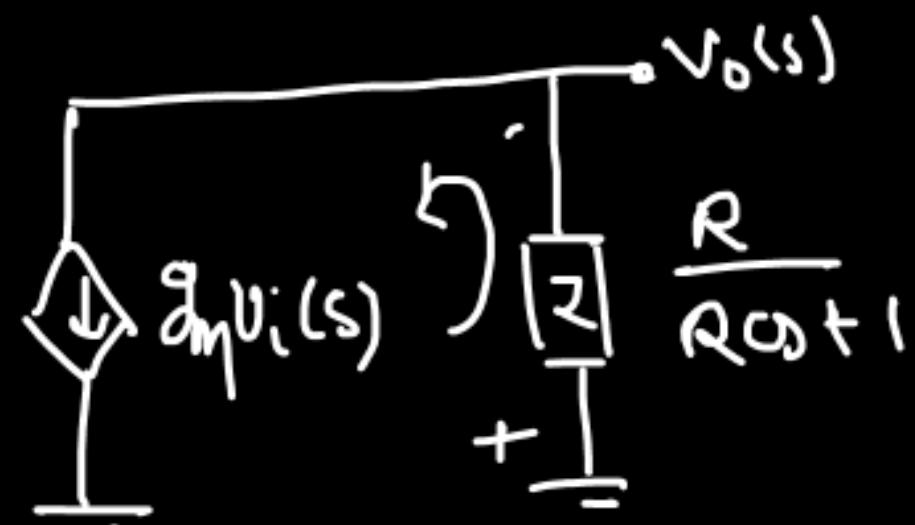

$$V_o(s) = - \frac{g_m \times R}{RCs + 1} V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = - \frac{g_m R}{RCs + 1}$$


$$\omega_p = -\frac{1}{RC} \quad |\alpha(\text{DC gain})| = g_m R$$

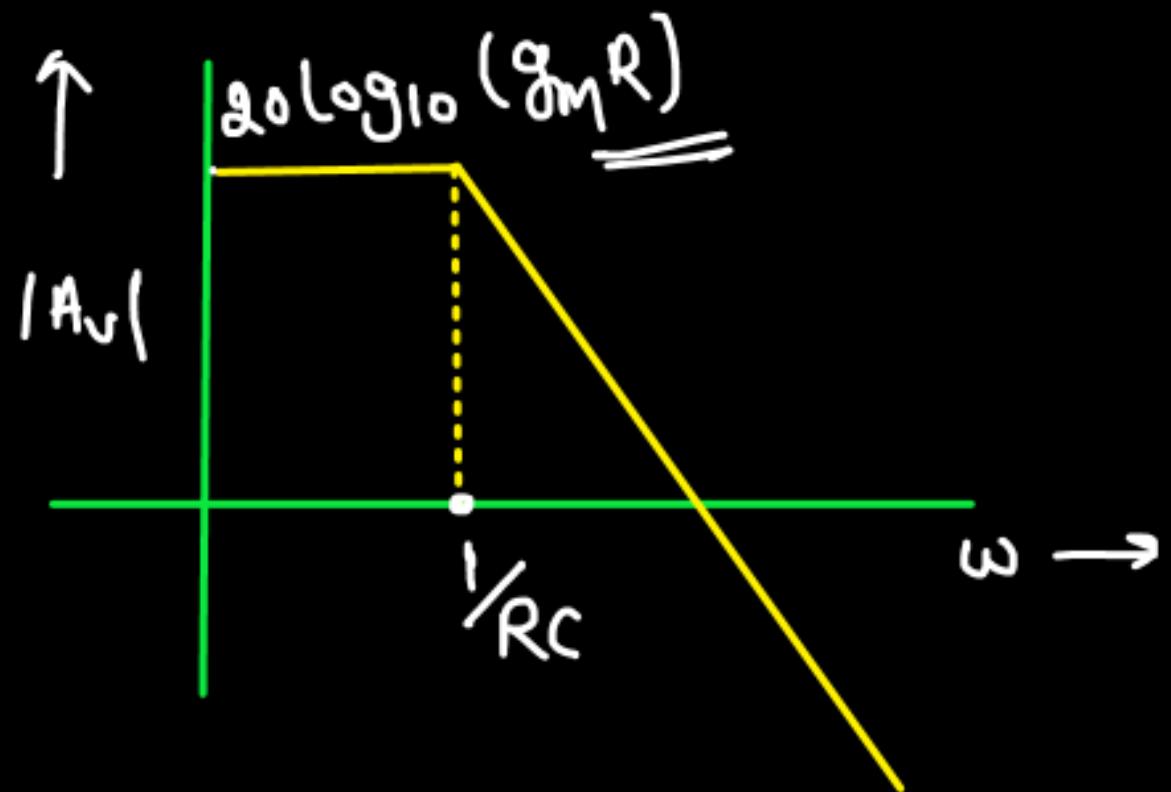

Let's assume  $V_{i(s)} = 20mV \sin(\omega t)$

For better amplification,


$$\omega_i \ll \frac{1}{RC}$$

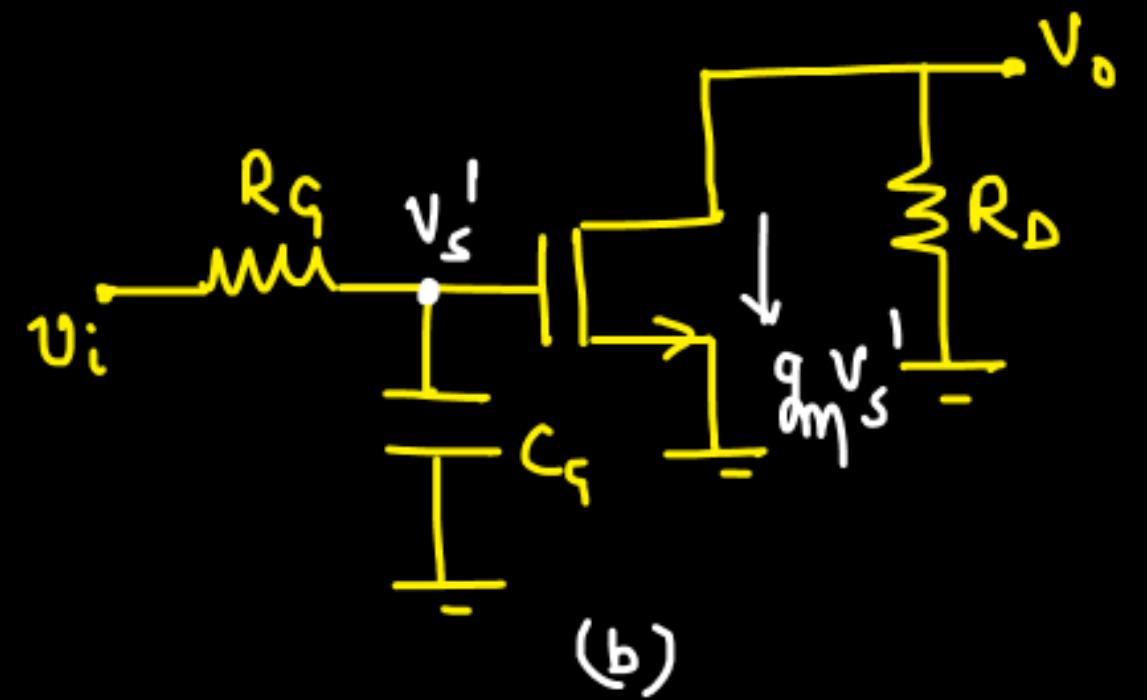

$$v_o = -g_m R_D v_s' \quad \text{---} \textcircled{1}$$

$$v_s' = \frac{\frac{1}{C_Q s}}{\frac{1}{C_Q s} + R_Q} v_i = \frac{1}{R_Q C_Q s + 1} v_i$$
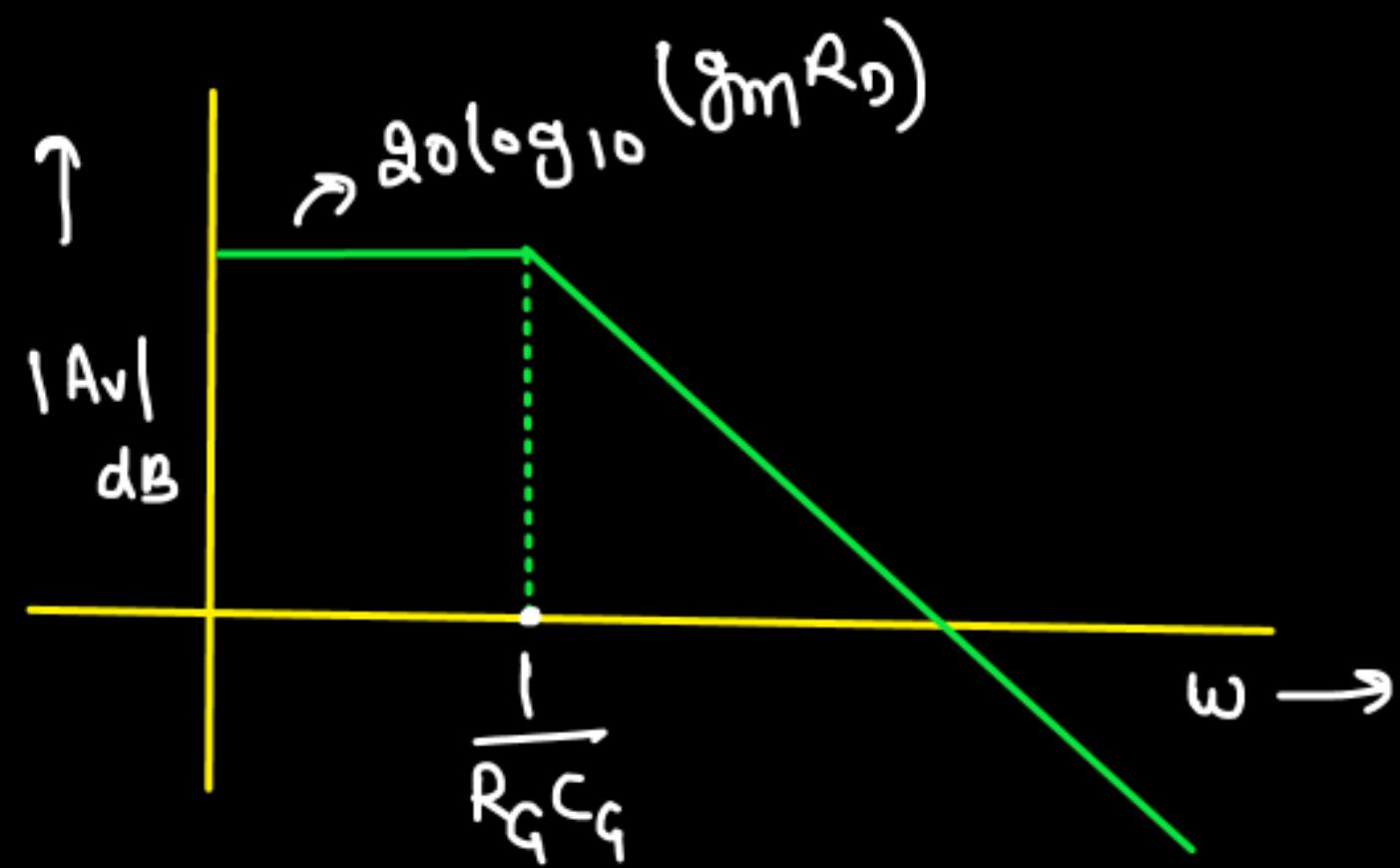
$$\frac{v_o}{v_i} = \frac{-g_m R_D}{R_Q C_Q s + 1}$$




$$V_i = V_m \sin(\omega_i t)$$

$$\omega_i \ll \frac{1}{R_Q C_Q}$$

⇒ For better amplification =

Q.

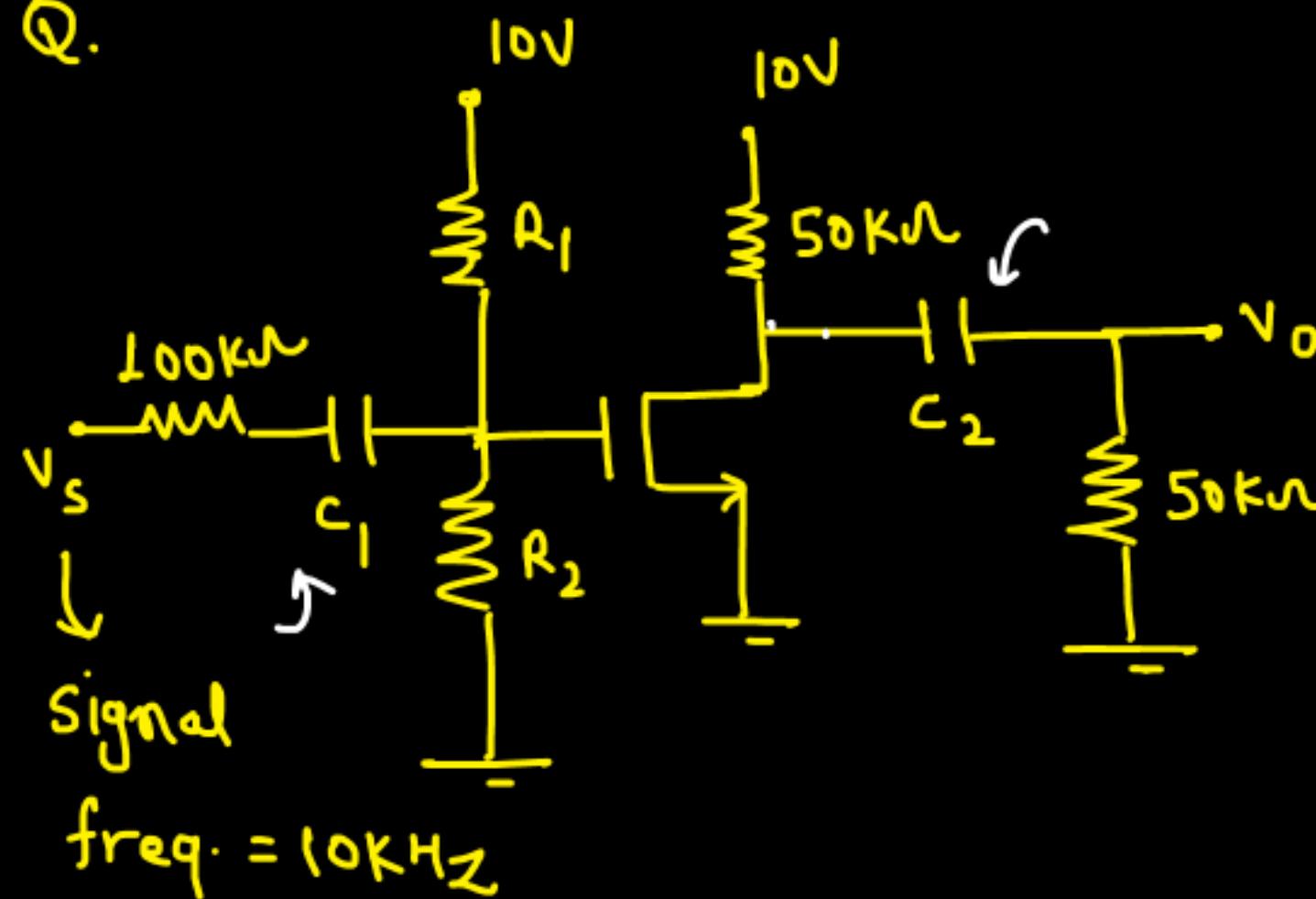

$C_1, C_2 \rightarrow$  coupling cap.

$$R_1 = 260\text{k}\Omega$$


$$R_2 = 740\text{k}\Omega$$

How large you should choose  $C_1$  and  $C_2$  such that both cap. acts as short ckt @ signal freq. =

$$C_1 \gg C_{o1}$$

$$C_2 \gg C_{o2}$$

Determine  $C_{o1}$  and  $C_{o2}$ .

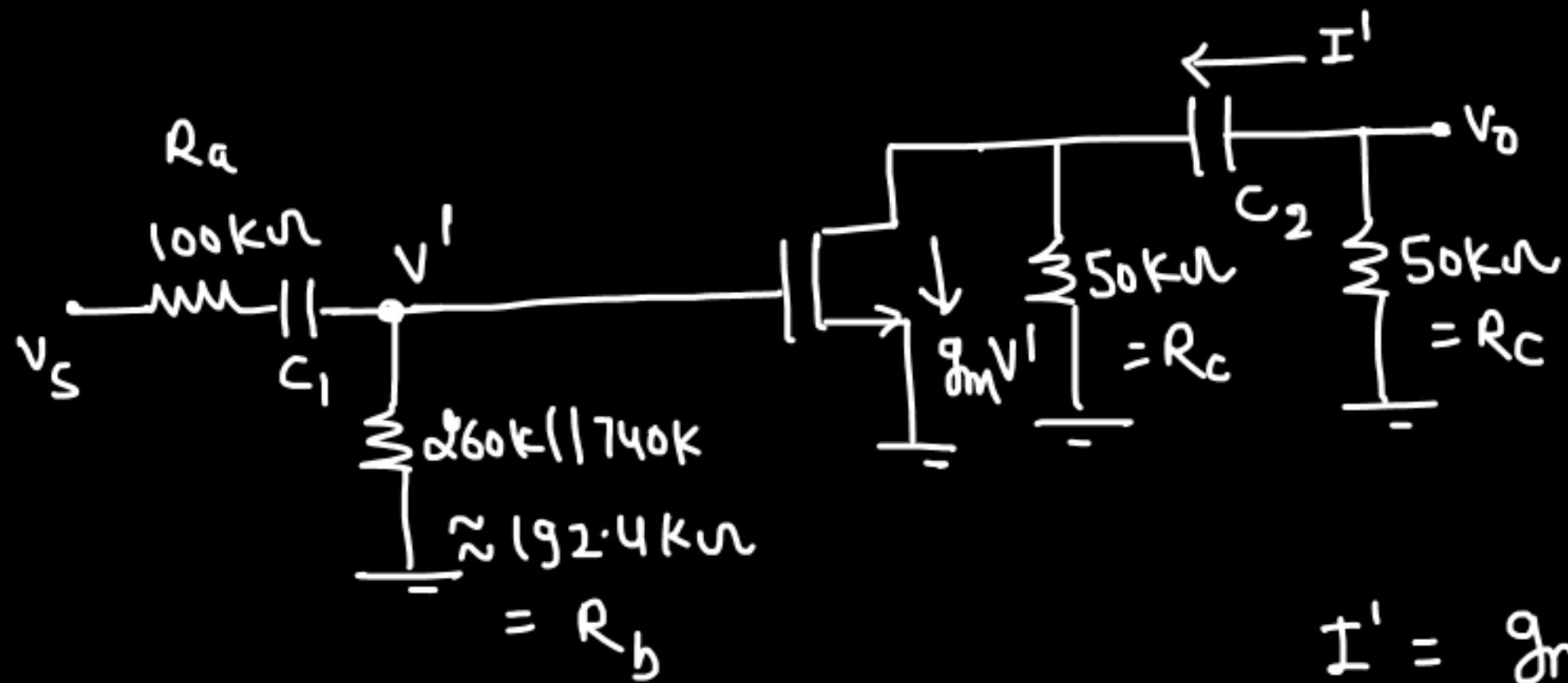

$$I' = g_m v' \times \frac{R_C}{R_C + R_b + \frac{1}{C_2 s}}$$

$$I' = g_m v' \times \frac{R_C C_2 s}{2R_C C_2 s + 1} \quad \textcircled{2}$$

$$v' = \frac{R_b}{R_b + R_A + \frac{1}{C_1 s}} v_s(s) \quad \textcircled{1}$$

$$v' = \frac{R_b C_1 s}{(R_b + R_A) C_1 s + 1} v_s(s)$$

$$v_o = -I' R_C \quad \textcircled{3}$$

$$V_o(s) = - \frac{g_m R_c C_2 s}{2 R_c C_2 s + 1} \times \frac{R_b C_1 s}{(R_b + R_q) C_1 s + 1} V_i(s)$$


$$A_v(s) = \frac{V_o(s)}{V_i(s)} = \frac{-g_m R_c R_b C_1 C_2 s^2}{(2 R_c C_2 s + 1)[(R_b + R_q) C_1 s + 1]} \quad \text{Ans.}$$

$$\omega_{Z_1} = \omega_{Z_2} = 0$$

$$\omega_{P_1} = \frac{-1}{2 R_c C_2}, \quad \omega_{P_2} = \frac{-1}{(R_b + R_q) C_1}$$

$$\omega_p = \frac{-1}{100k \times C_2}$$
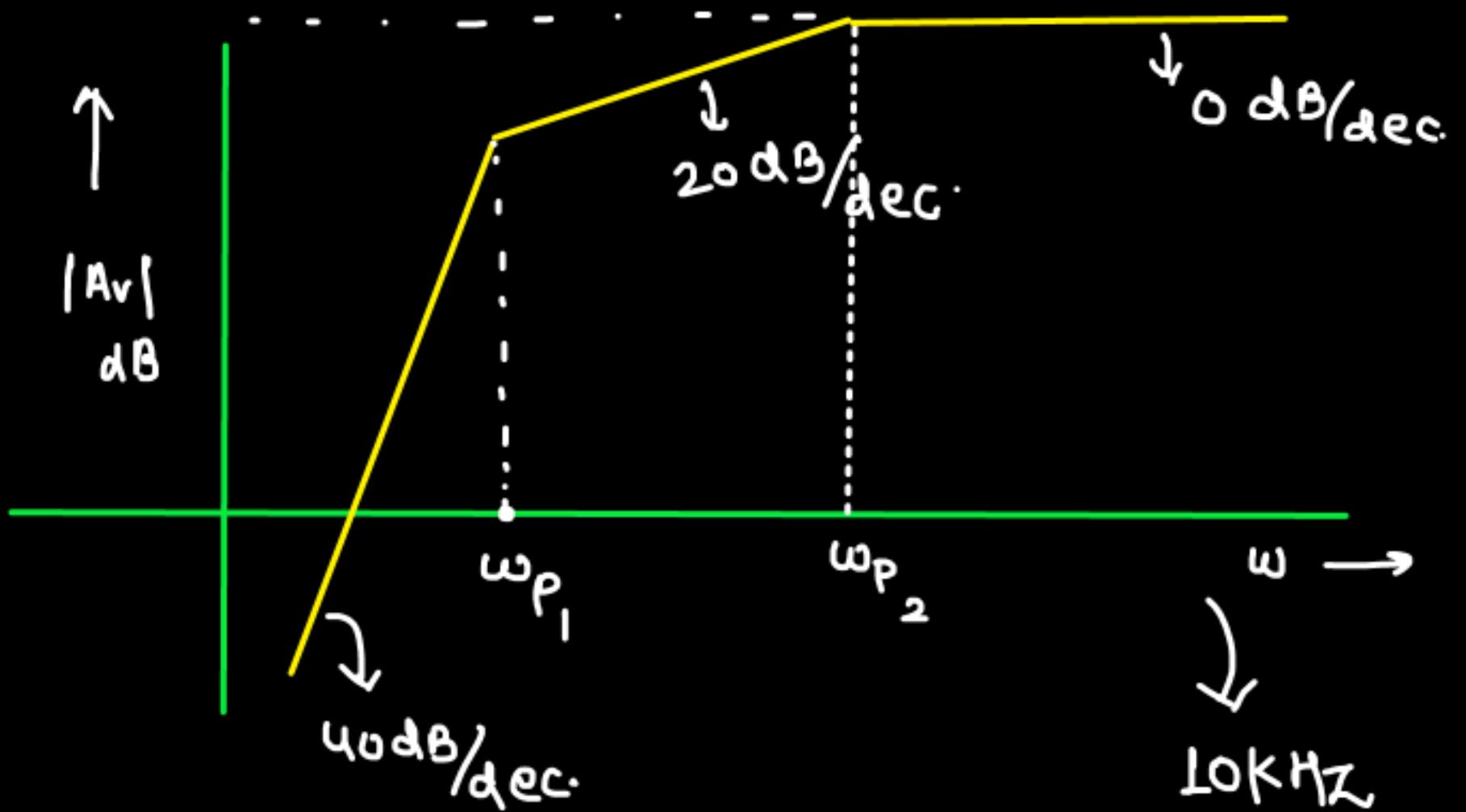
$$\omega_p = \frac{-1}{292.4k \times C_1}$$



$$\omega_{P_1} < 20k\pi$$

$$\frac{1}{100k \times C_2} < 20k\pi$$

$\Rightarrow C_2 > 159 \text{ pF}$

$$\omega_{P_2} < 20k\pi$$

$$\frac{1}{292.4k \times C_1} < 20k\pi$$



$\Rightarrow C_1 > 54.4 \text{ pF}$

$$= 20k\pi \text{ rad/sec}$$


Generally  $c_2$  should be 1590 pF  
 $c_1$  should be 544 pF  $[c_1, c_2 = 10c_0]$

NOT Imp.

## ⇒ High Freq. Model of MOS:-

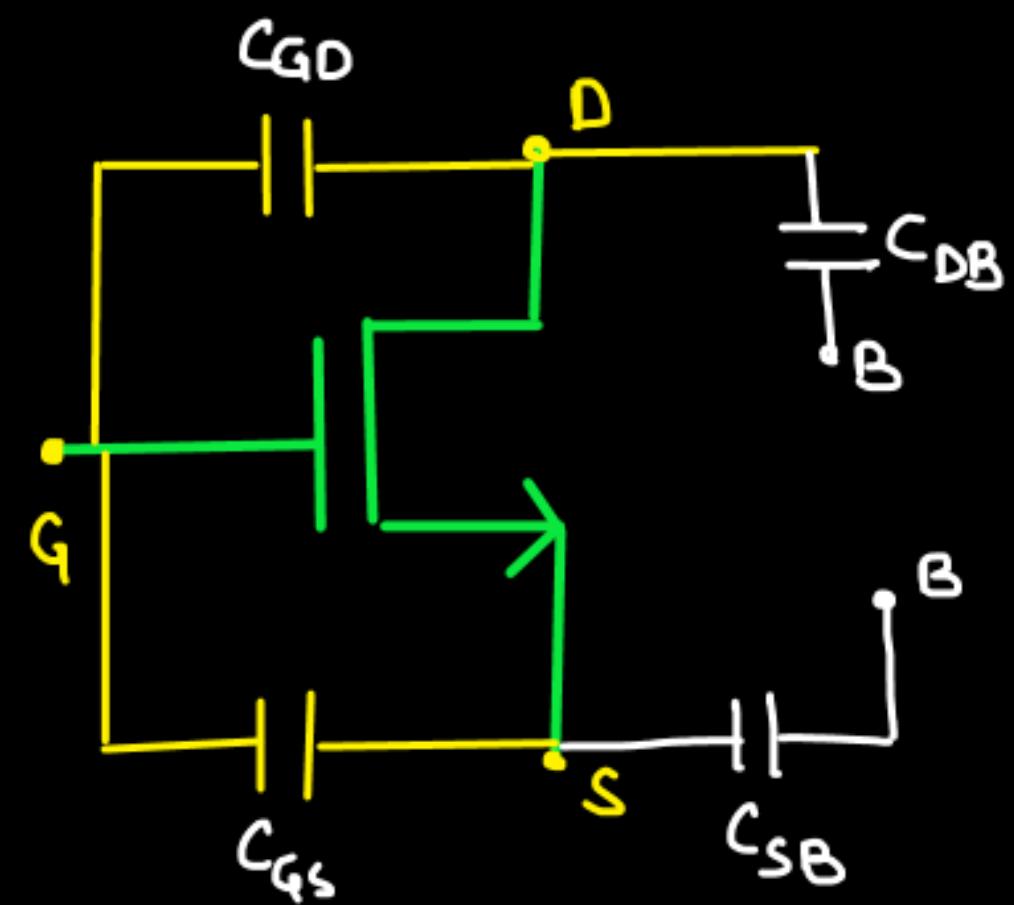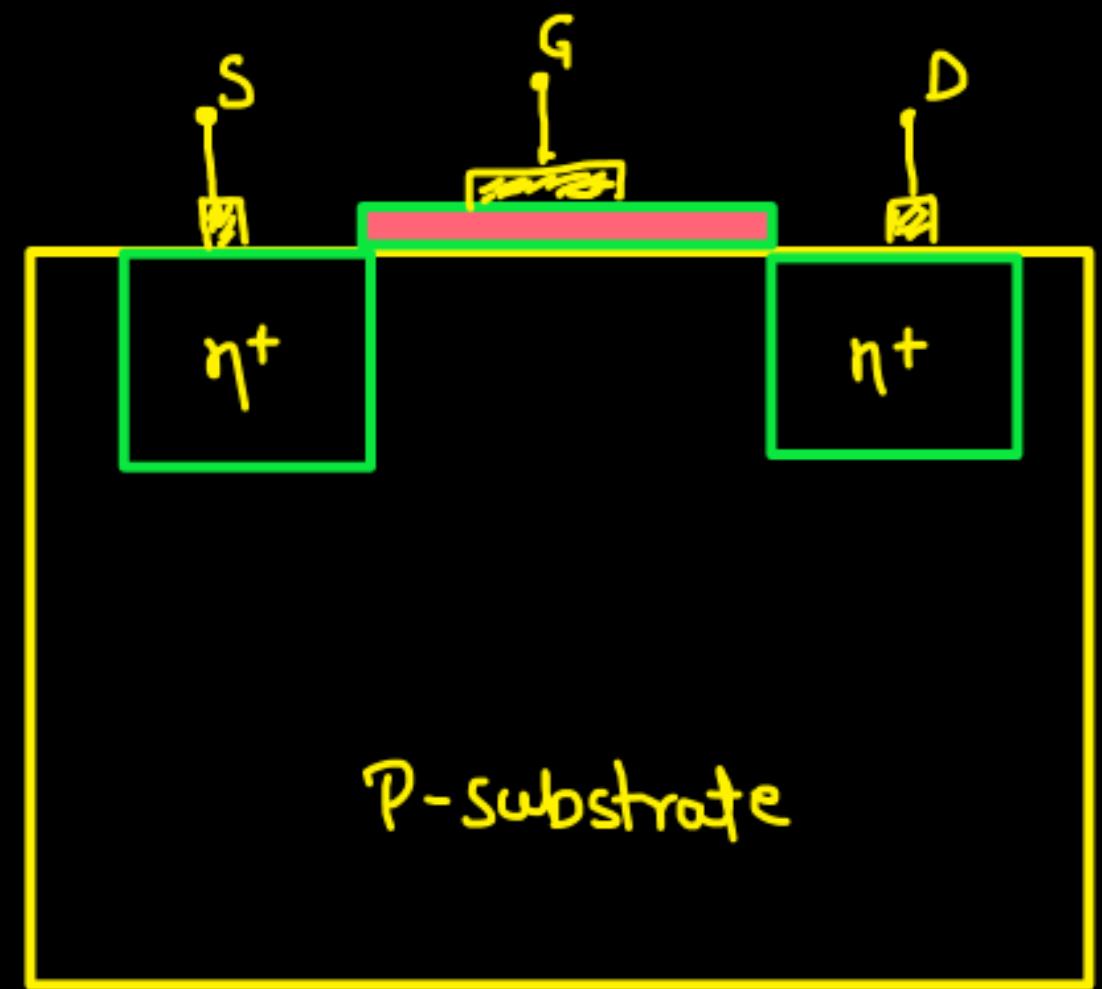

~~not~~  $\Rightarrow$

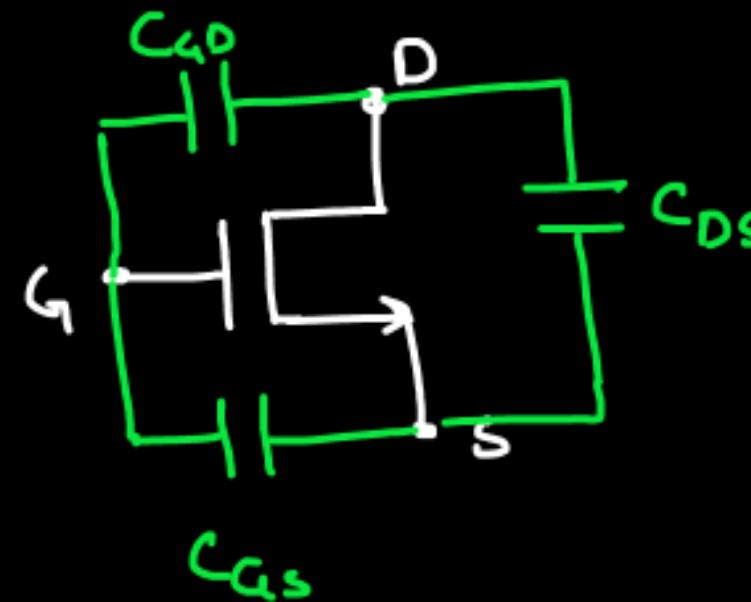

+nt @ Higher freq.

$C_{GS}, C_{QD}, C_{DS} \sim PF, fF$   
(small) Range


$$@ \text{low freq.} \Rightarrow \frac{1}{C_{QDS}} = \frac{1}{\text{very low} \times \text{very low}} = \frac{1}{0} = \infty \Rightarrow 0 \cdot C$$

$$@ \text{High freq.} \Rightarrow \frac{1}{C_{QDS}} = \frac{1}{\text{very low} \times \text{very high}} = \frac{1}{\text{considerable}} \Rightarrow \text{stays in action}$$

$\Rightarrow$  @ low and Mid freq., Parasitic / Internal / J<sup>n</sup> cap are open ckt.

@ High freq., They come in action

Q.

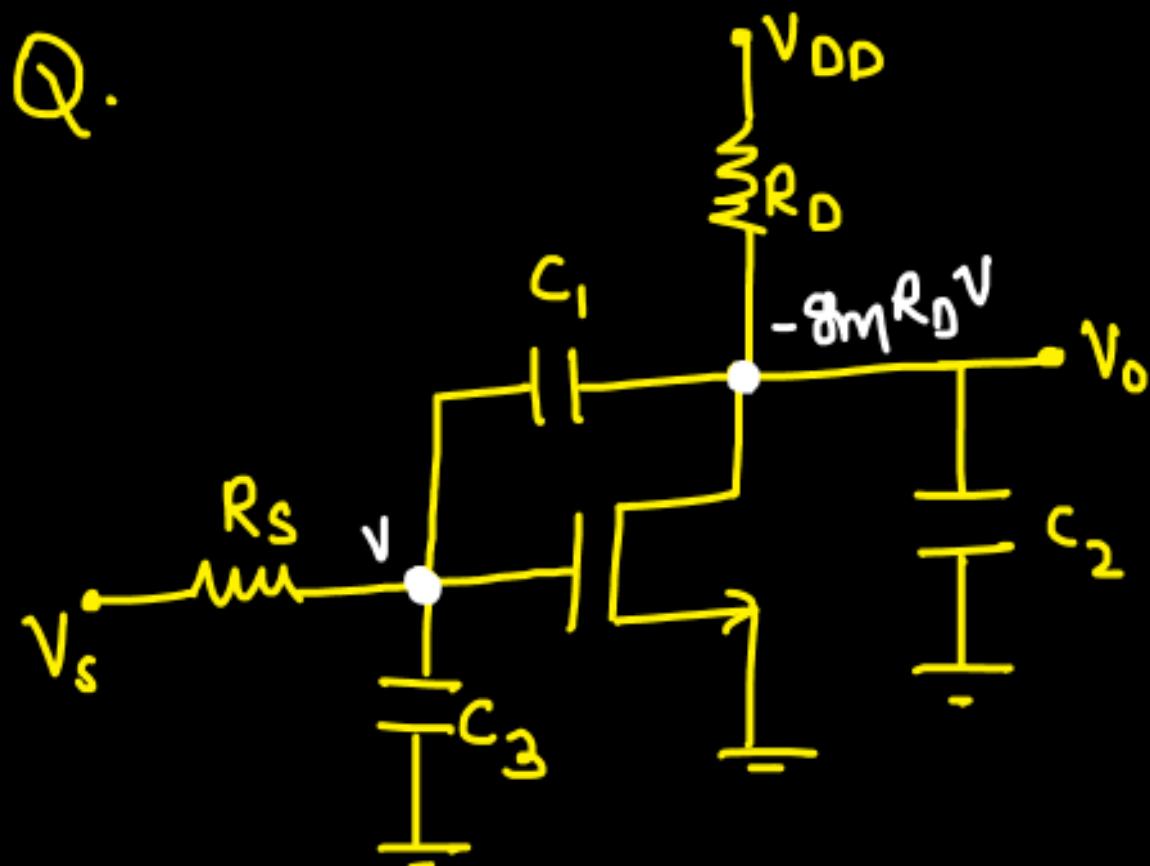


Given that  $C_1, C_2$  &  $C_3$   
are parasitic cap.

[ $C_1, C_2, C_3 \rightarrow$  very low value  
pf]



Draw the freq. response.

DC gain :-

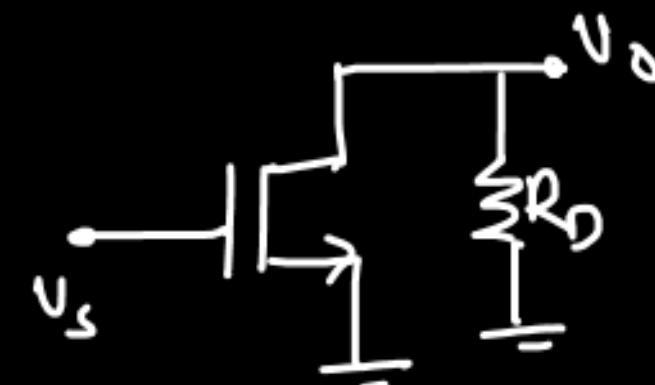

$$\frac{v_o}{v_s} = -g_m R_D$$

Applying Miller's Theorem :-

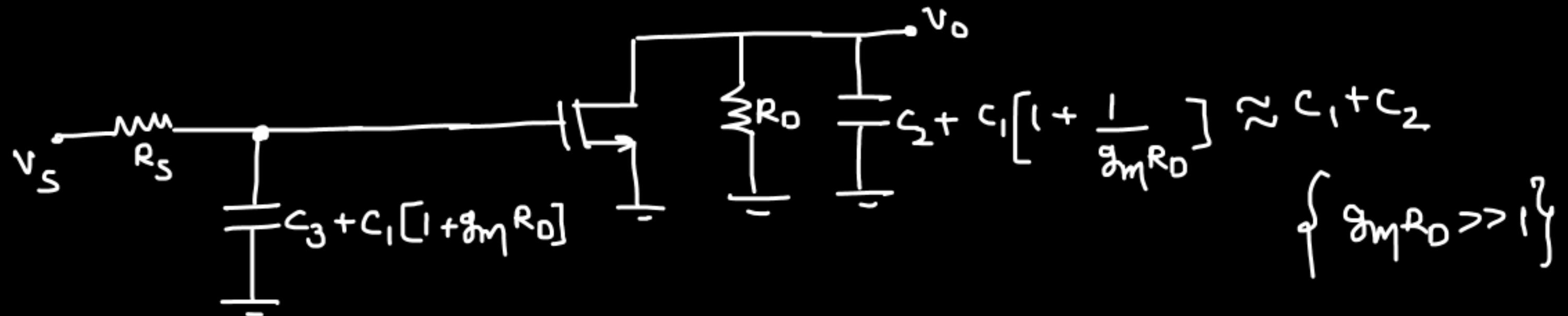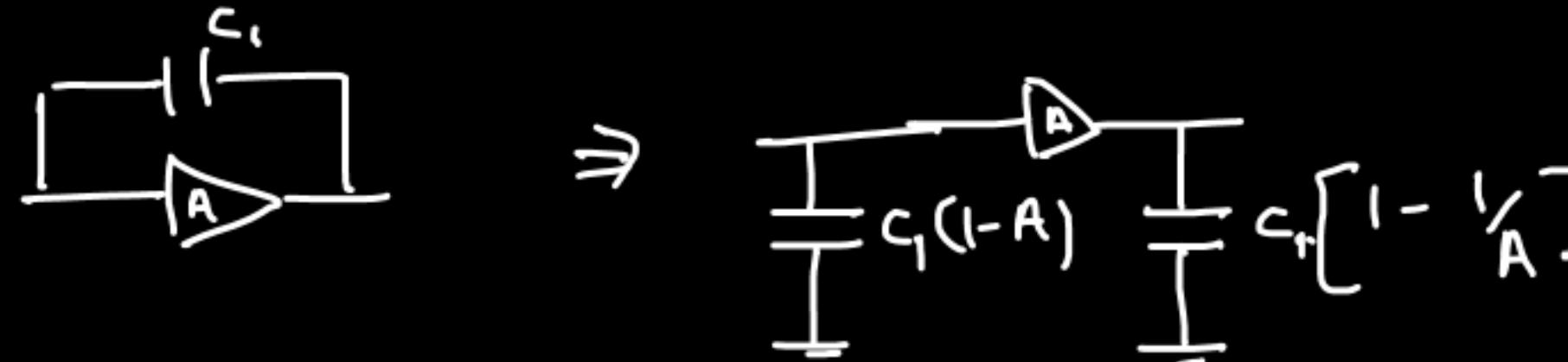


$$\frac{v_o(s)}{v_s(s)} = \frac{-g_m R_D}{\left[ [C_3 + C_1(1 + g_m R_D)] R_s s + 1 \right] \left[ R_D (C_1 + C_2) s + 1 \right]}$$

$$\omega_{Z_1} = \infty$$


$$\omega_{Z_2} = 0$$

$$\omega_p = \frac{-1}{R_0(C_1 + C_2)}$$
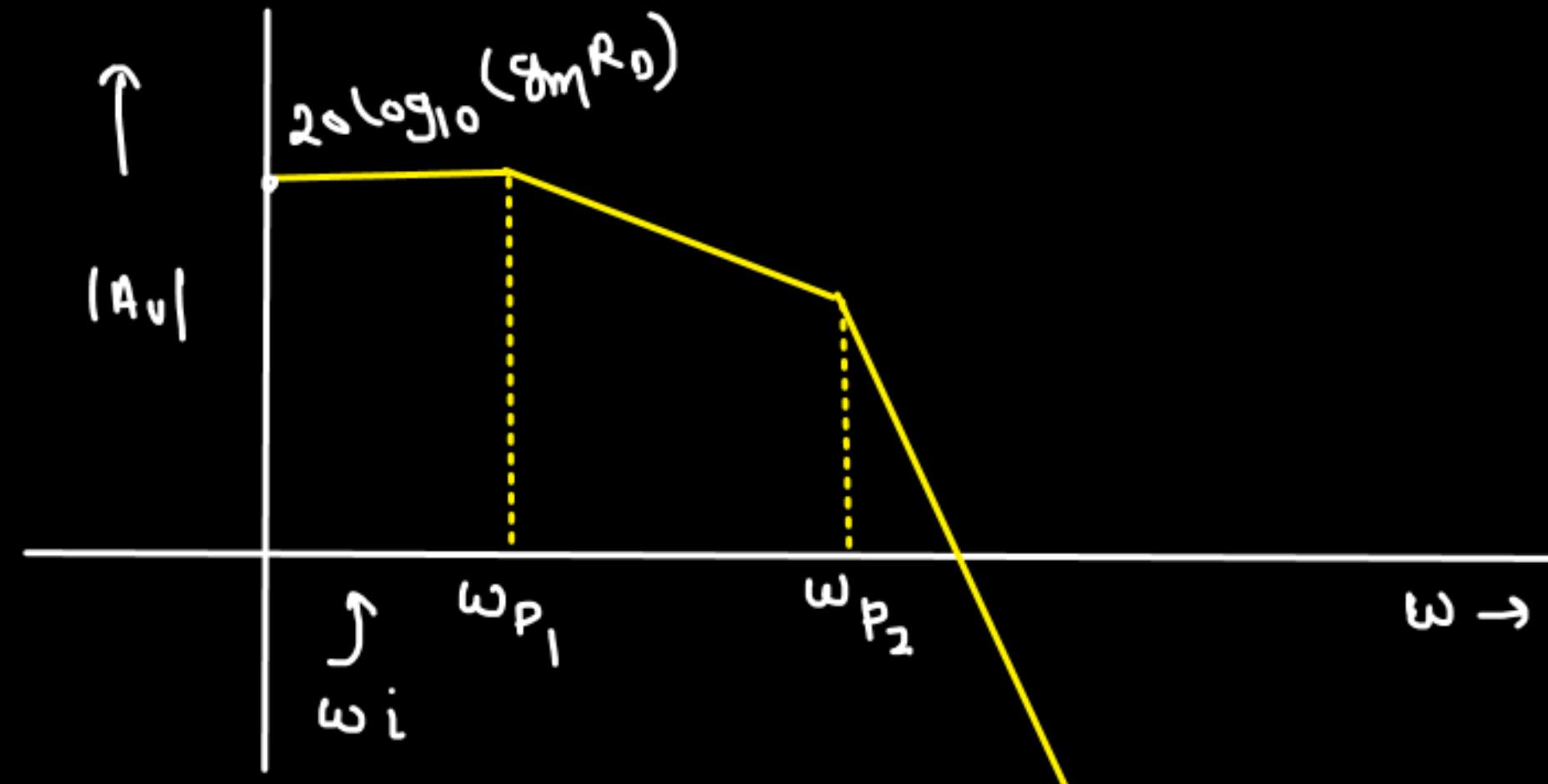
$$\omega_p = \frac{-1}{[C_0 + C_1(1 + g_m R_0)] R_S}$$




N.B. →

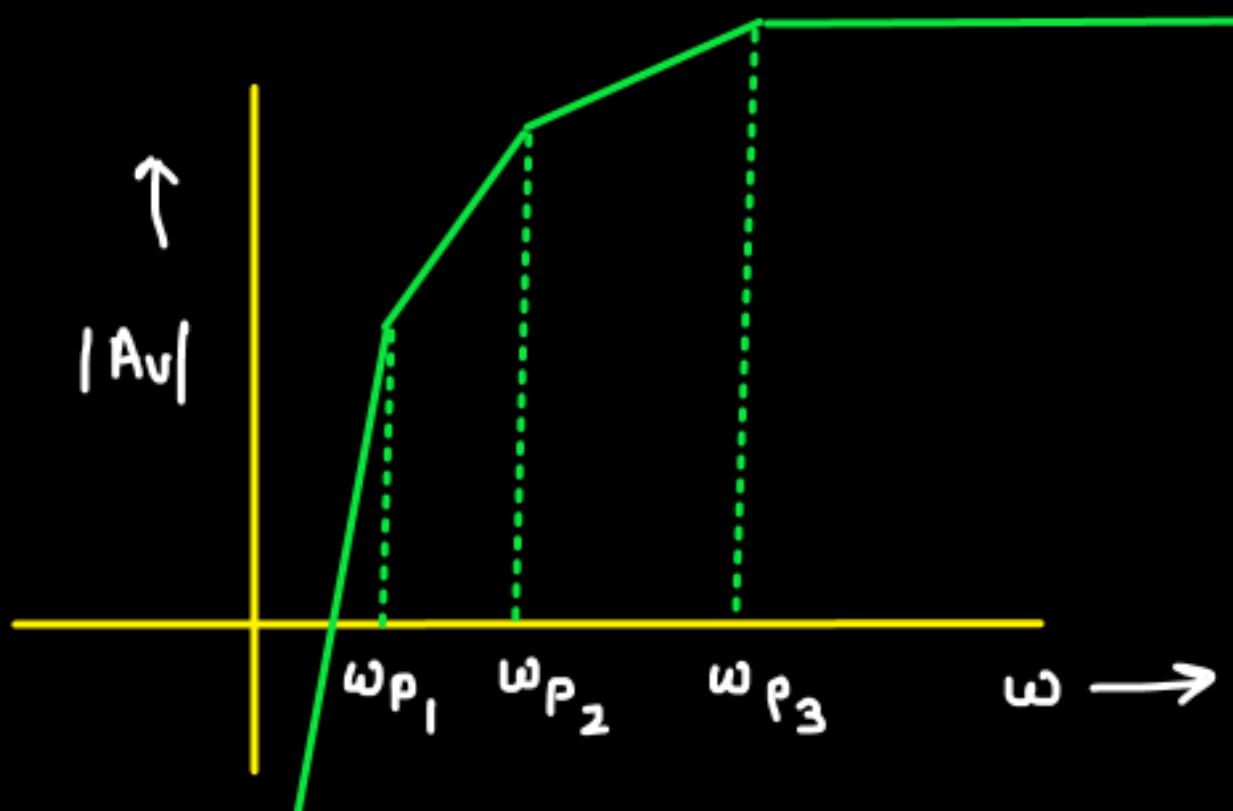

↓

3-dB cut-off freq. =  $\omega_{P_3}$

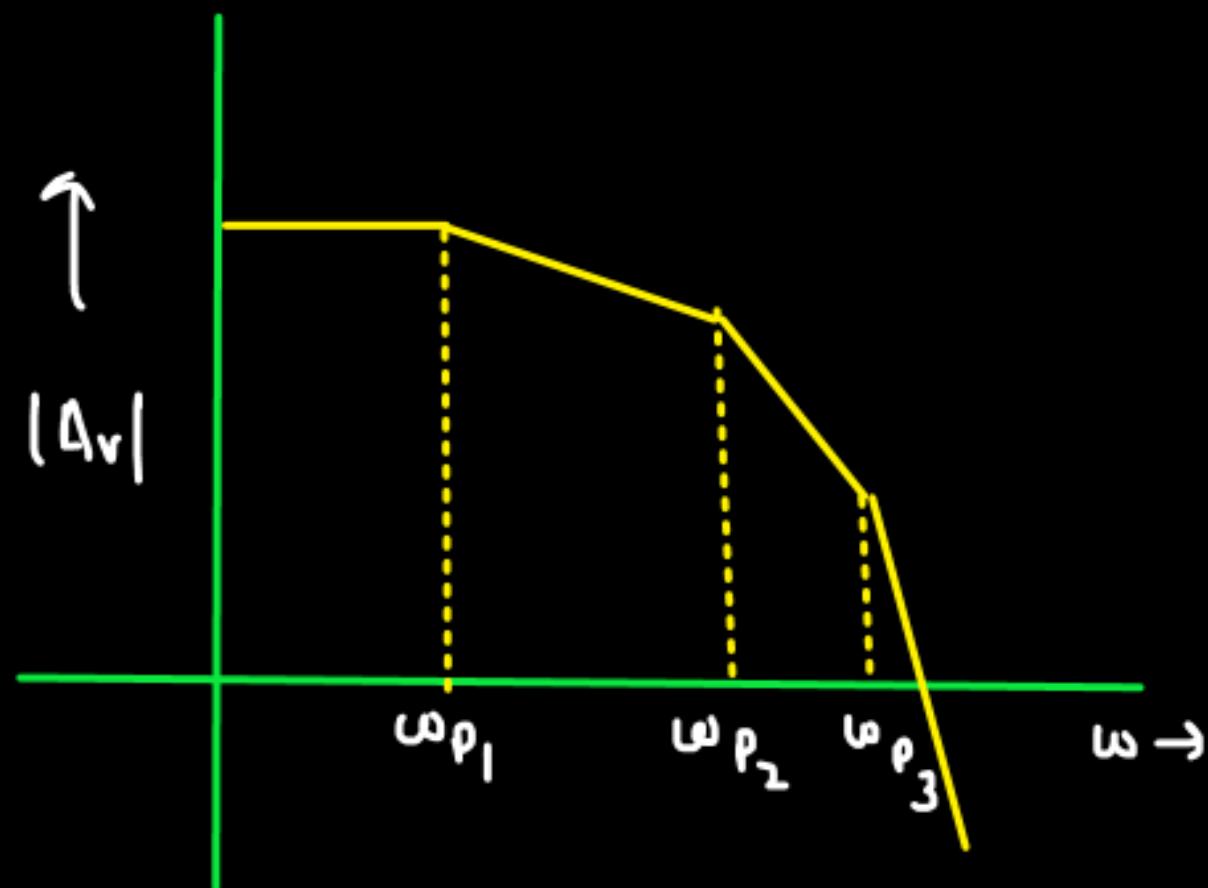

3-dB cut-off freq. =  $\omega_{P_1}$

## Low Freq. Model of MOS:-

↓  
coupling cap. will be in action

↓  
( $\eta_f$  or  $\mu_f \rightarrow \underline{\text{High}}$ )

@ low freq.  $\Rightarrow \frac{1}{c_c s} = \frac{1}{\text{High} \times \text{low}} = \frac{1}{\text{consider}} =$  will be in action

@ High freq.  $\Rightarrow \frac{1}{\text{High} \times \text{High}} = \frac{1}{\infty} = 0 =$  cap. will act as S.C.

$\Rightarrow$  @ low freq.  $\Rightarrow$  coupling cap. are in action


$\Rightarrow$  @ High freq. & Mid freq.  $\Rightarrow$  coupling cap. is S.C.

## Conclusion:-
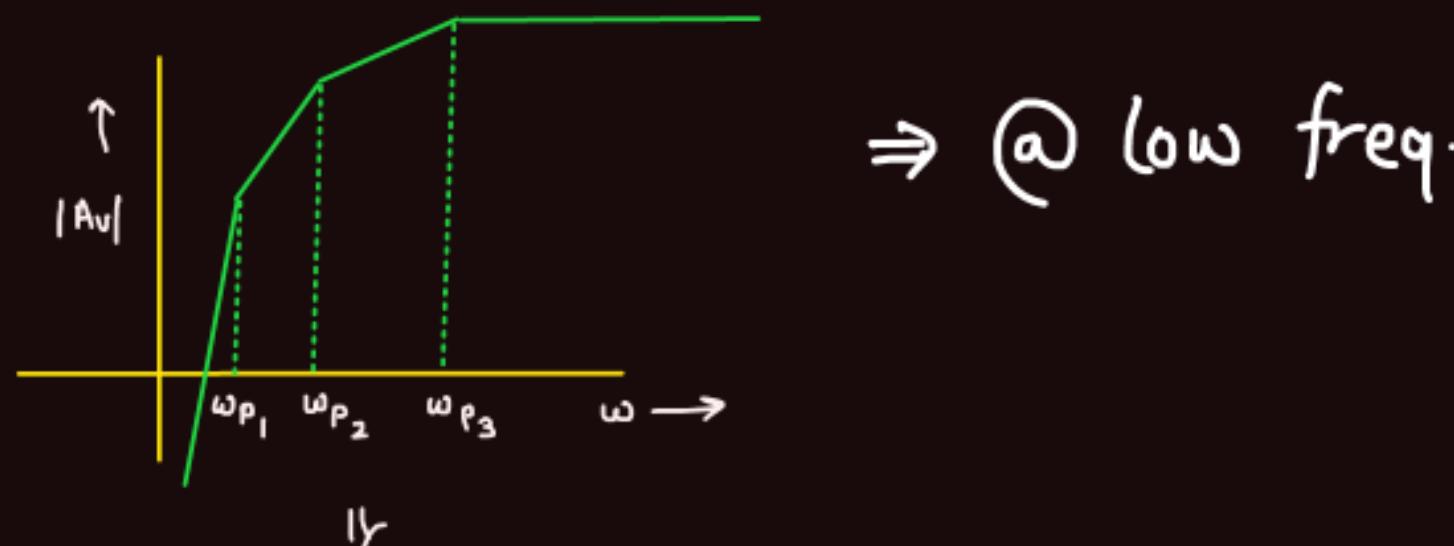
### (a) Coupling cap:-

- ↳ Will be in action @ low freq.
- ↳ Response will be of HPF.
- ↳ Will act as S.C. @ High and Mid freq.


Coupling  $\Rightarrow$  Low freq.  $\Rightarrow$  H.P.F.  $\Rightarrow$  3-dB cut off freq. will be Highest pole



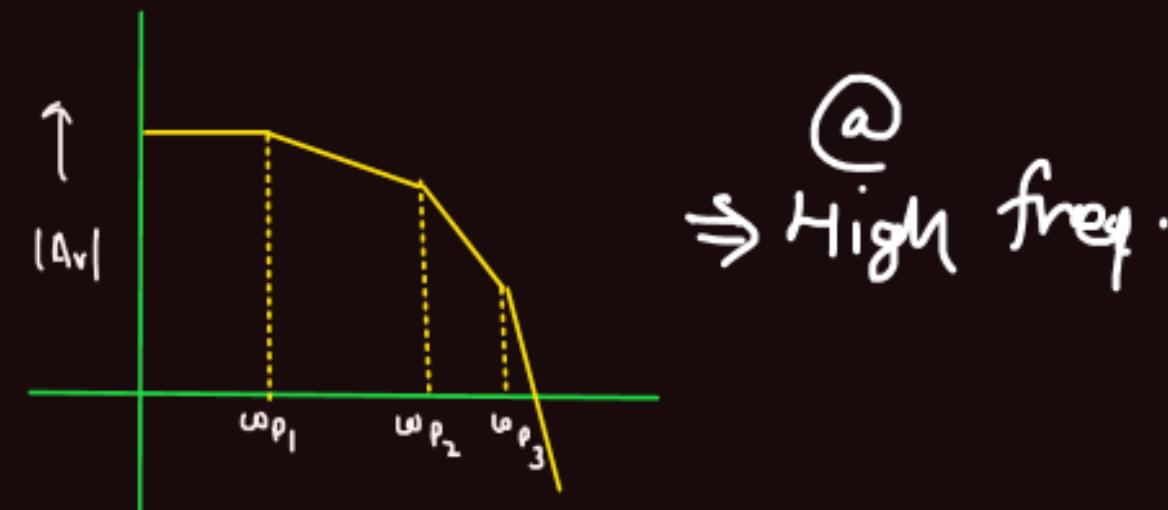
## (b) Parasitic / Internal / J<sup>n</sup> cap.

- ↳ will be in action @ High freq.
- ↳ Response will be of LPF
- ↳ will act as o.c. @ low and Mid freq.

Parasitic / Internal / J<sup>n</sup> cap.  $\Rightarrow$  High freq.  $\Rightarrow$  LPF  $\Rightarrow$  cut-off freq. will be min pole.


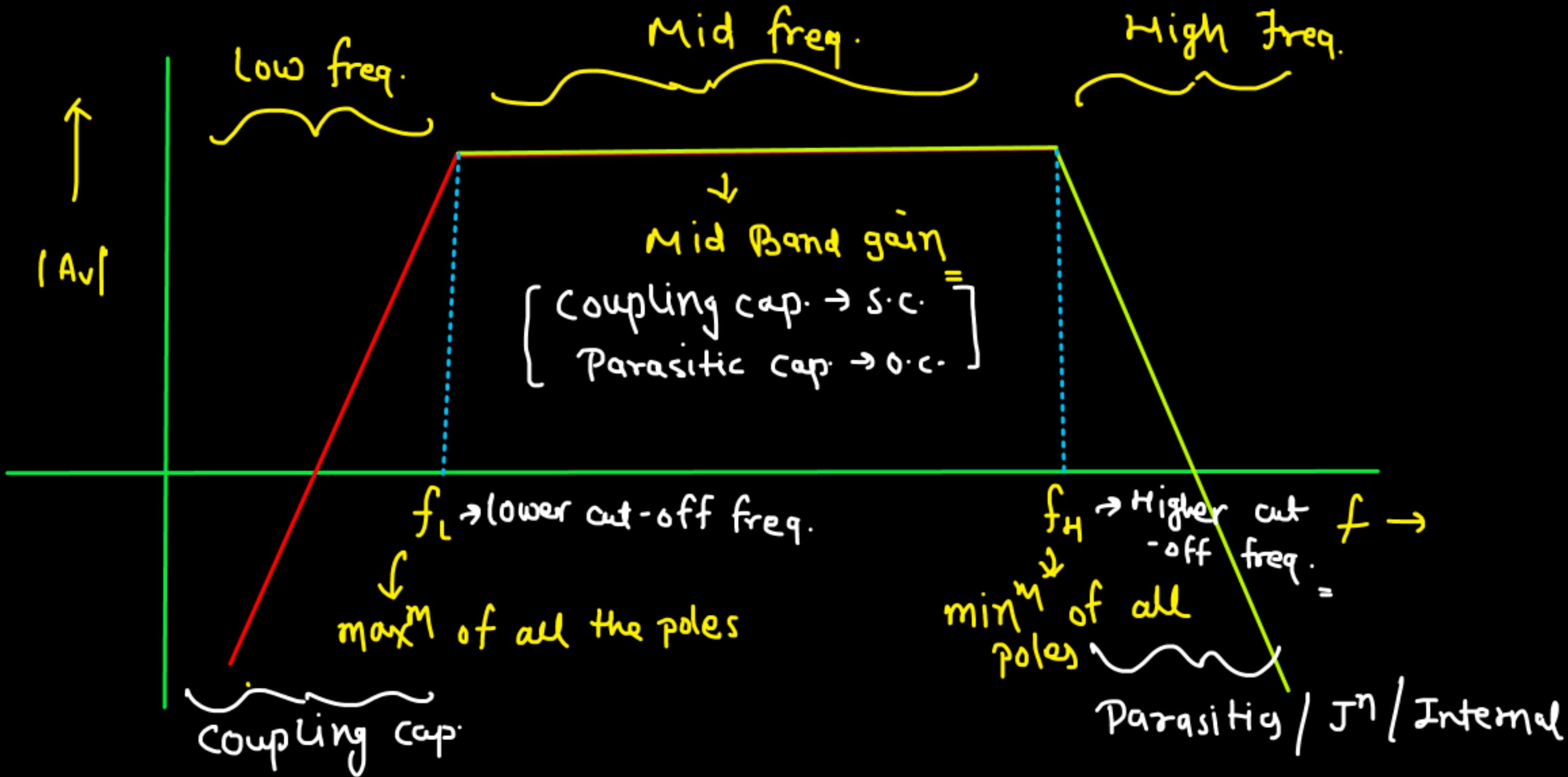
## ⇒ Freq. Response of a RC Coupled MOS Amp:-



$\Rightarrow$  How to find a pole in MOS ckt.

- ① find the order of the ckt.
- ② Nullify the i/p and find equivalent resistance across cap. [consider the other cap. shorted]

$$\omega_p = \frac{1}{C R_{eq}}$$

$\Rightarrow$  How to find a zero in MOS ckt:-


- ① NO Hard and fast rule. Do intelligent analysis.

$$T(s) = \frac{A \left( \frac{s}{z_1} + 1 \right) \left( \frac{s}{z_2} + 1 \right) \dots \left( \frac{s}{z_n} + 1 \right)}{\left( \frac{s}{R_1} + 1 \right) \left( \frac{s}{R_2} + 1 \right) \dots \left( \frac{s}{R_n} + 1 \right)}$$

$\Rightarrow A = dc$   
gain  
 $(\omega=1)$


@  $s = -z_1 \Rightarrow T(s) = 0$

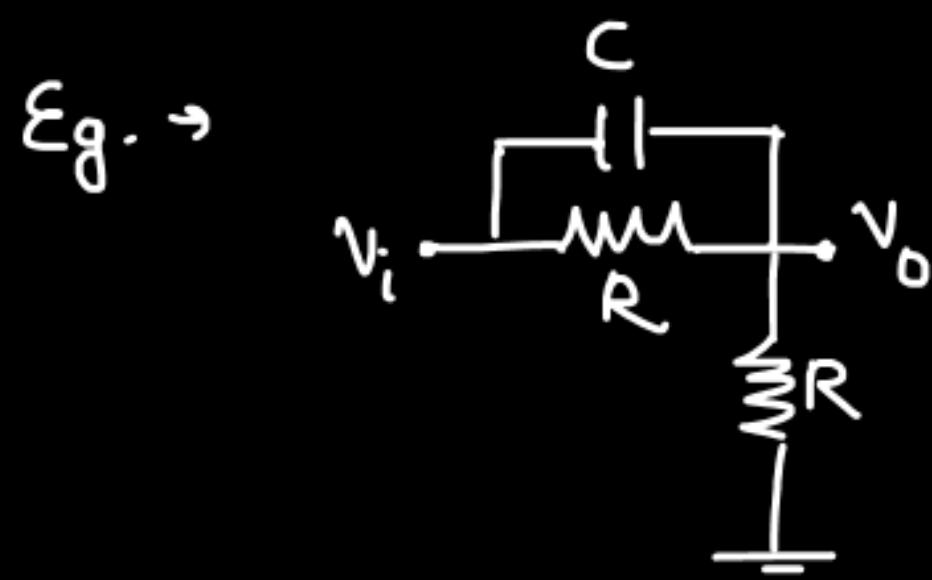@ zero, T.F. becomes zero.  $\frac{V_o(s)}{V_i(s)} \rightarrow 0 \Rightarrow V_o(s) \rightarrow 0$



① order = 1<sup>st</sup>

② Poles →

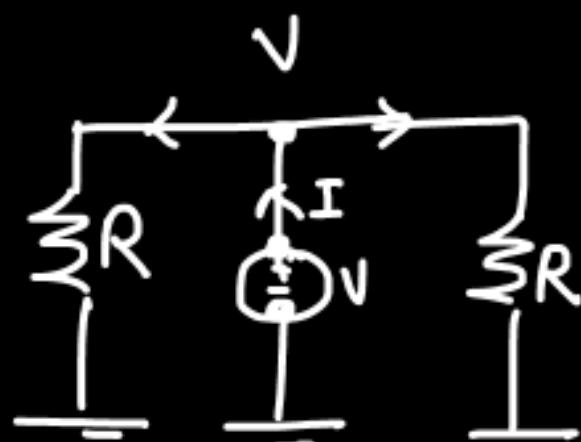


$$\Rightarrow R_{eq} = R/2$$

$$C_{eq} = C$$

$$\omega_p = \frac{-1}{R/2 C} = \frac{-2}{R C}$$

③ zero →

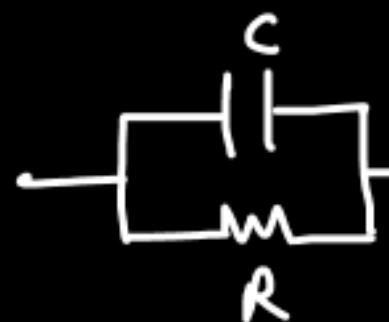

$$= \frac{R}{RCj+1} = 0$$


$$\Rightarrow s_z = -\frac{1}{RC}$$

$$T.F. = \frac{A(sRC + L)}{\left(\frac{sRC}{2} + 1\right)} = \frac{2A(sRC + L)}{(sRC + 2)}$$

@  $\omega=0$   $T.F. = A$

in the given ckt


@  $\omega=0$

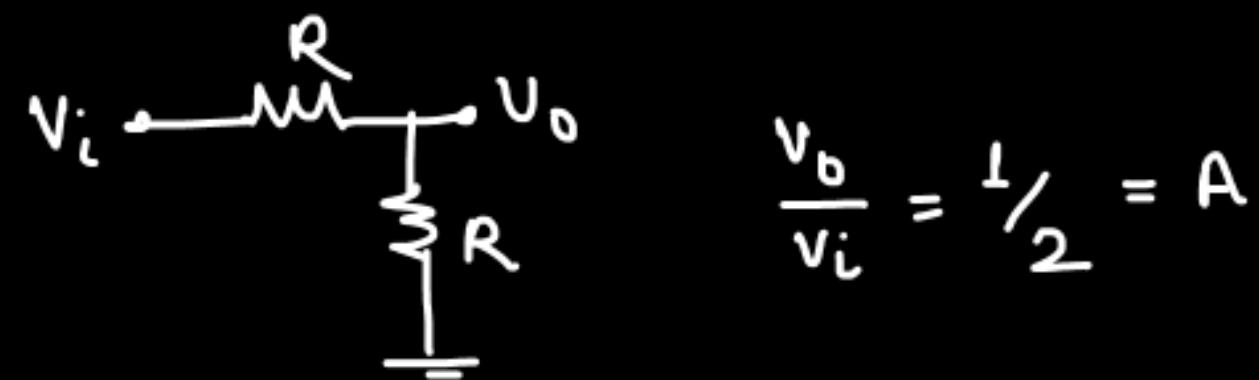

$$\frac{V_o}{V_i} = \frac{1}{2} = A$$

$T.F. = T(s) = \frac{sRC + 1}{sRC + 2}$
---

Q.

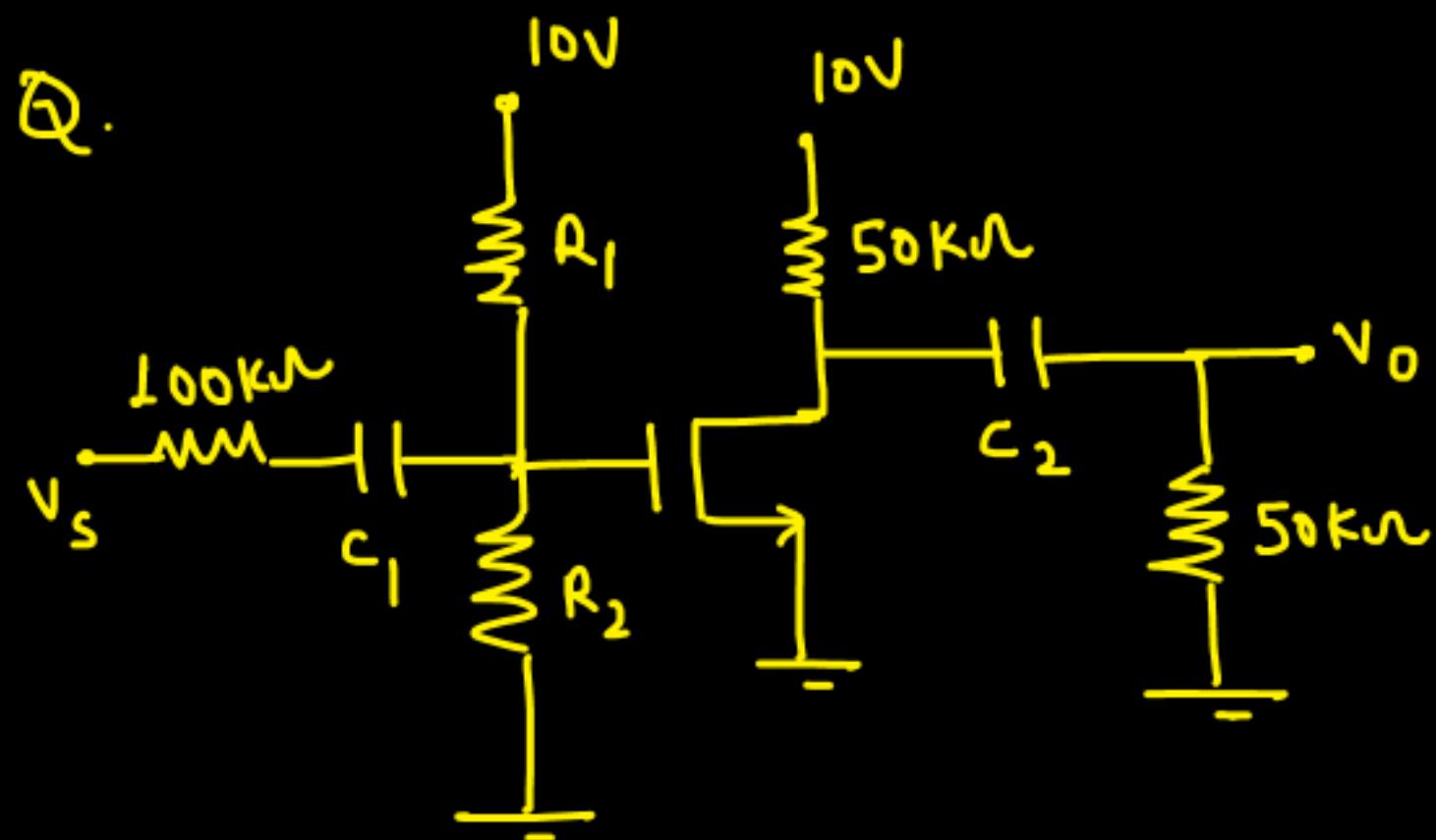

how freq. operation

(a) Determine the order of ckt.

(b) Find the location of poles.

(c) Determine 3-dB cut-off


$$\text{freq. } (\text{kHz}) =$$

$$R_1 = 260 \text{ k}\Omega$$

$$R_2 = 740 \text{ k}\Omega$$

$$C_1 = 100 \text{ pF}$$

$$C_2 = 200 \text{ pF}$$


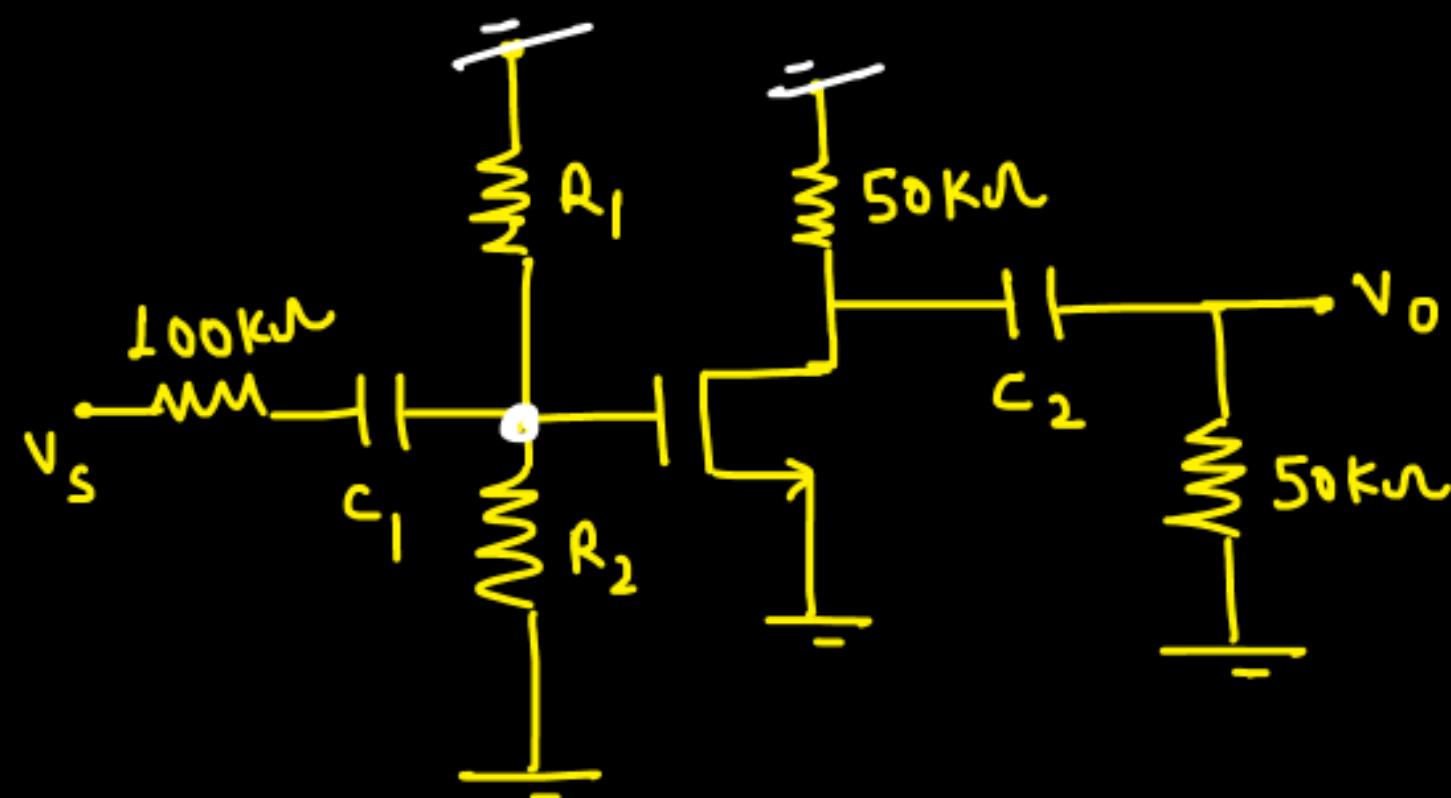


① order = 2<sup>nd</sup>

② poles :-

pole because of  $C_1$

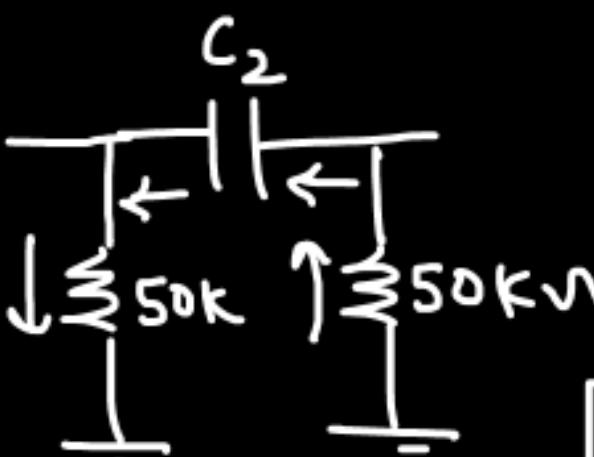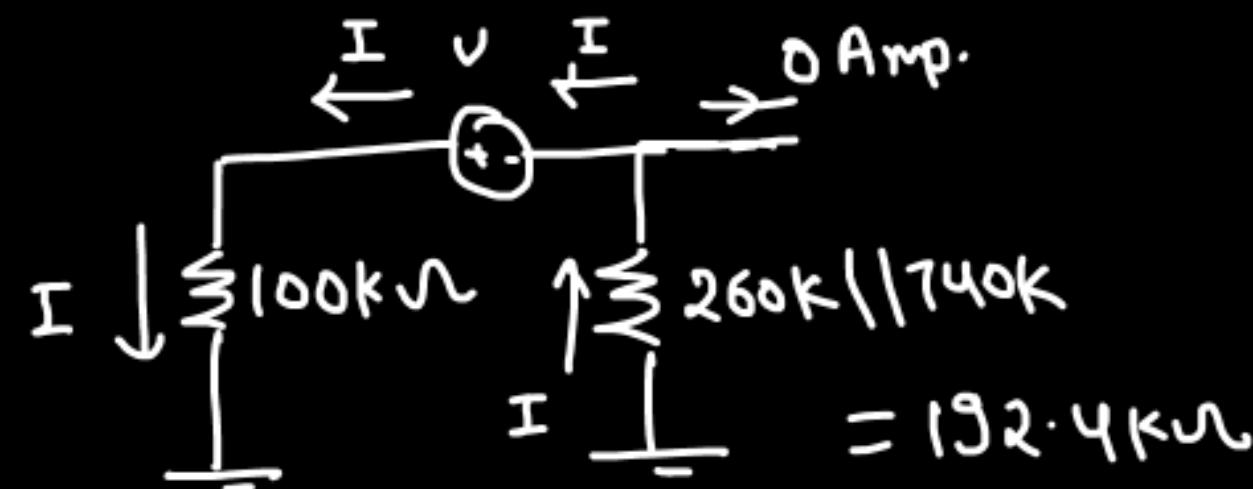$\rightarrow$  S.C.  $C_2$ , S.C. input  $v_s$



$$R_{eq} = 100k\Omega$$

$$C_2 = 100 \mu F$$

$$\omega_{P_2} = \frac{1}{R_{eq} C_2} = 100 \text{ Krad/sec.}$$

$$C_{eq} = C_1 = 100 \mu F = 10^{-10} F$$

$$R_{eq} = 192.4 + 100 = 292.4 \text{ k}\Omega$$

$$\omega_{P_1} = \frac{1}{R_{eq} C_1} = 34.2 \text{ Krad/sec.}$$

$$3\text{-dB cut-off freq.} = \max(\omega_{p_1}, \omega_{p_2}) \\ = 100 \text{ k rad/sec}$$


$$\omega_{dB} = 15.91 \text{ kHz}$$

@  $\omega=0$ , Because of  $C_2$ ,  $v_o$  is zero


@  $\omega=0$ , Because of  $C_1$ ,  $v_o$  is zero

$\Rightarrow$  you have two zeros @  $\omega=0$
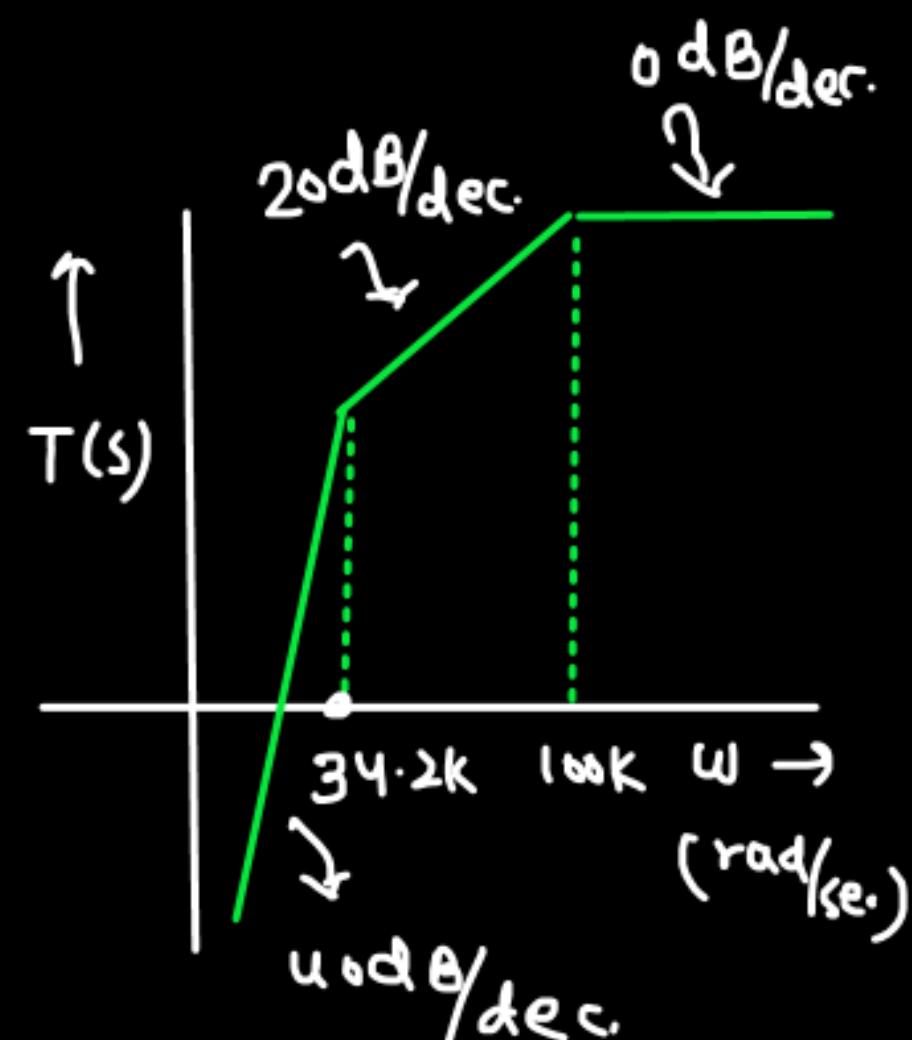
$$T(s) = \frac{K s^2}{\left(\frac{s}{34.2k} + 1\right)\left(\frac{s}{100k} + 1\right)}$$





Q.

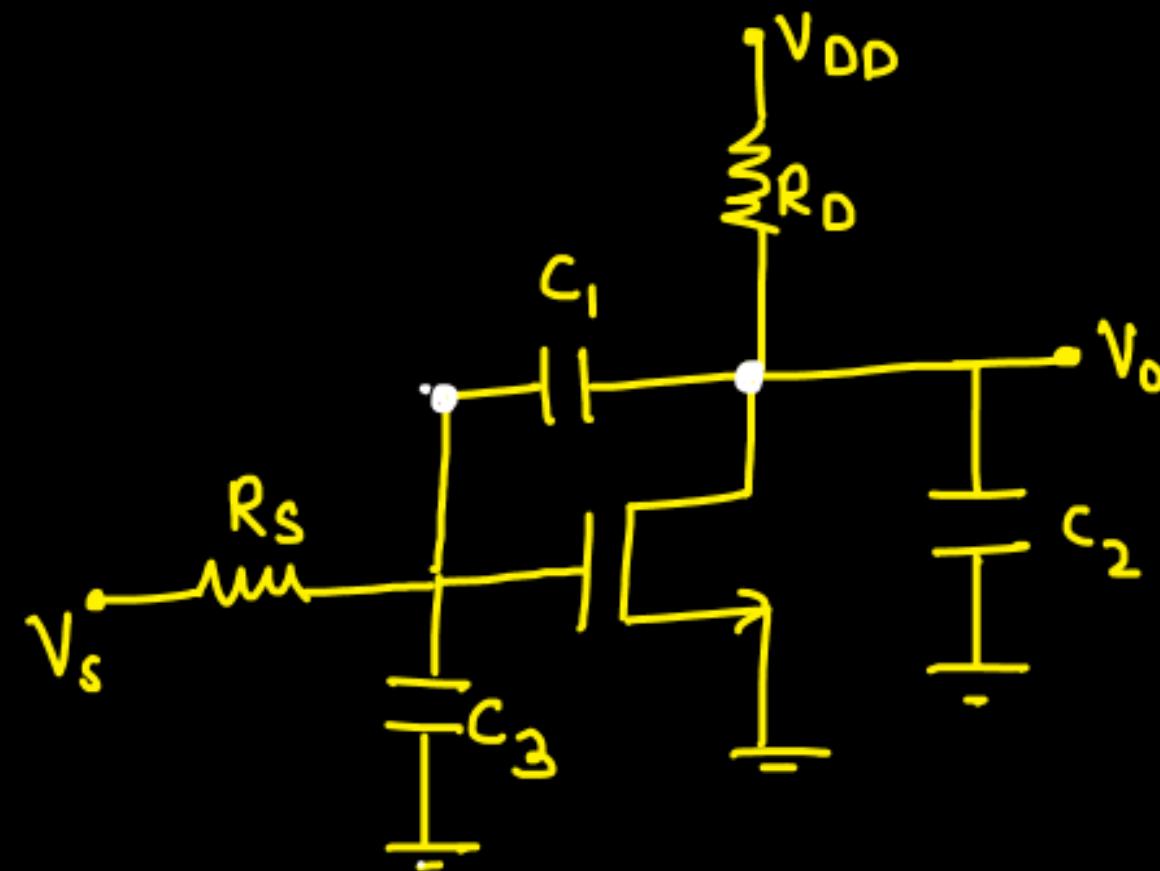

Given that  $C_1, C_2$  &  $C_3$   
are parasitic cap.

[ $C_1, C_2, C_3 \rightarrow$  very low value  
pf]

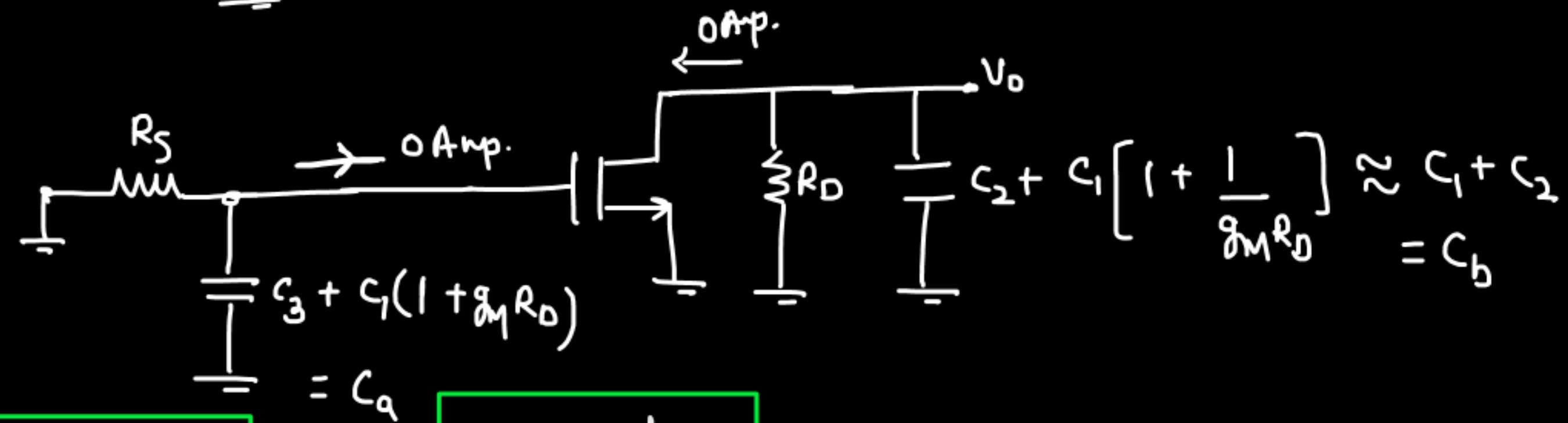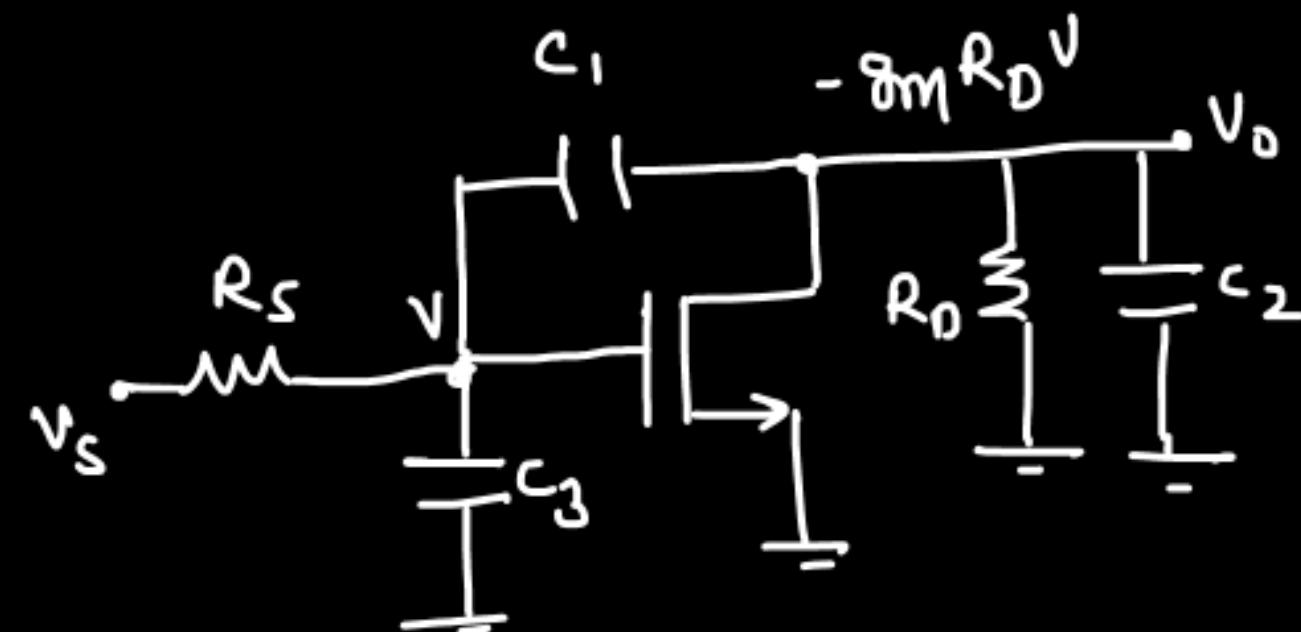- Determine the order of the ckt.
- Determine the location of poles.
- Draw freq. response.
- Tell 3-dB cut-off freq.



$$\omega_{P1} = \frac{1}{R_s C_q}$$


$$\omega_{P2} = \frac{1}{R_D C_b}$$

Because of  $C_2$ , @  $\omega = \infty, V_0 = 0 \Rightarrow \text{zero} @ \infty$

Because of  $C_3$ , @  $\omega = \infty, V_0 = 0 \Rightarrow \text{zero} @ \infty$


$$T.F. = \frac{-g_m R_D}{\left\{ SR_S [C_3 + C_1(1 + g_m R_D)] + 1 \right\} \left\{ SR_D (C_1 + C_2) + L \right\}}$$

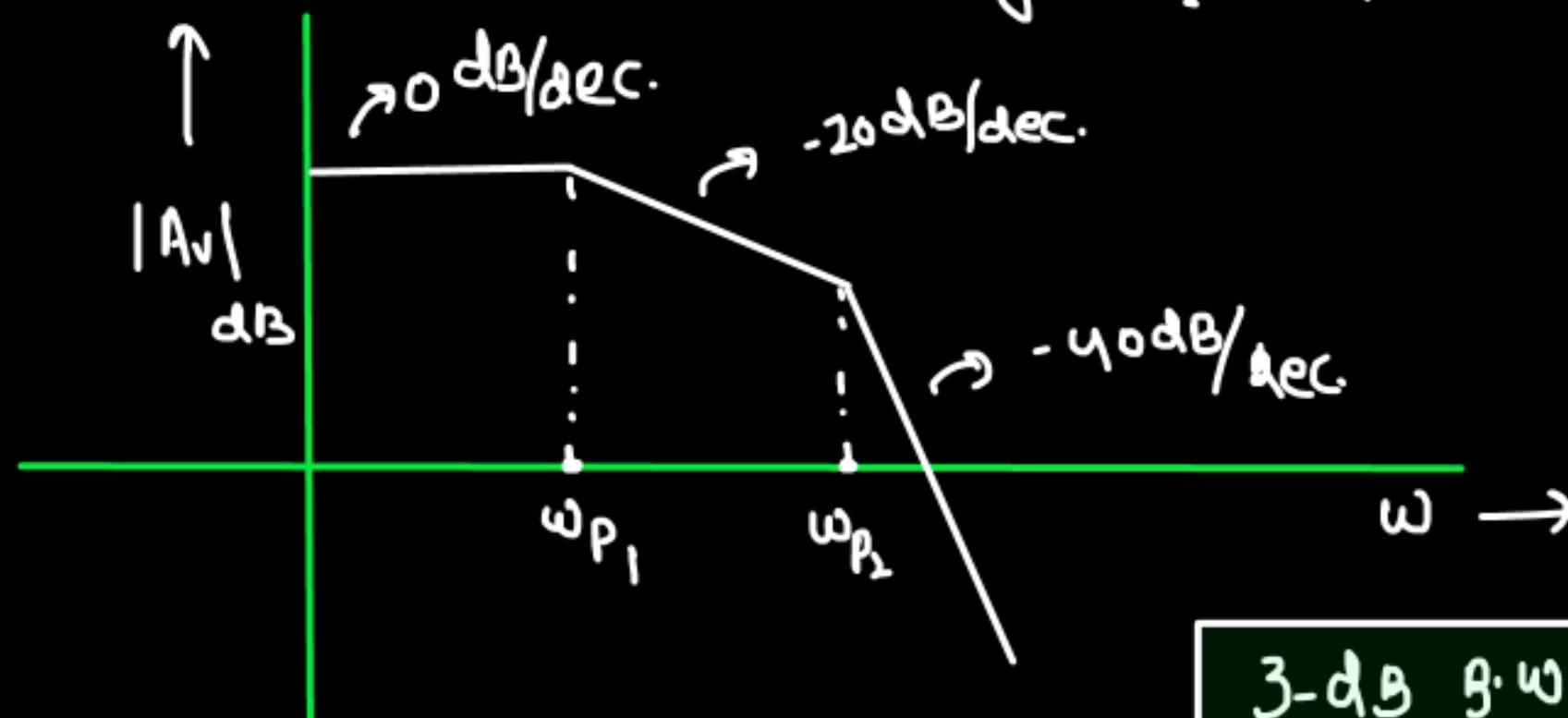considering  $\omega_{p_2} > \omega_{p_1}$



$$3-\text{dB} \text{ } g \cdot w = \omega_{p_1}$$

③

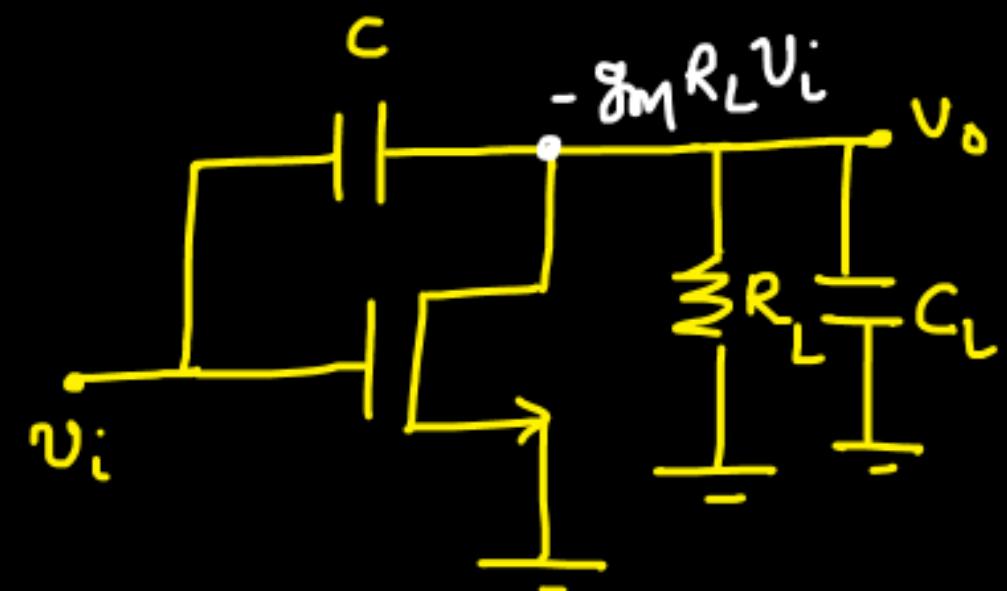

Q. Draw Bode plot. Considering

(a)  $R_L C_L \gg \frac{C}{g_m}$


(b)  $N O C o d i n g$

$\Rightarrow 1^{\text{st}}$  order

$\Rightarrow$  Compare your results.

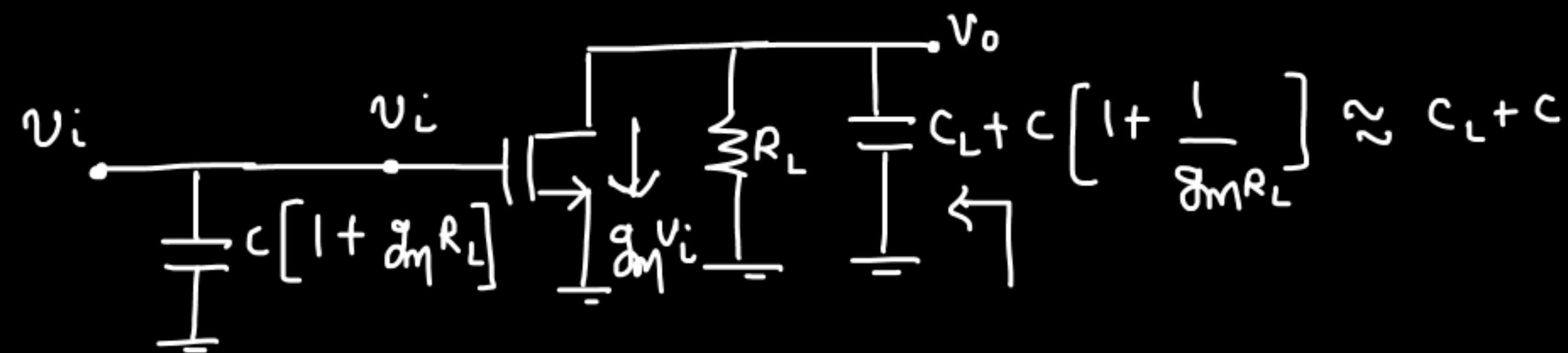(a) Since,  $C$  is very low

$\Rightarrow$  I can apply millers Theorem



$$A_V = G_m R_{out}$$

$$G_m = -g_m$$


$$R_{out} = R_L \left( 1 + \frac{1}{(C_L + C)s} \right)$$

$$A_V = -g_m \left[ R_L \left( 1 + \frac{1}{(C_L + C)s} \right) \right]$$


$$A_V = \frac{-g_m R_L}{R_L [C_L + C] s + L}$$

$$\omega_p = \frac{-L}{R_L [C_L + C]}$$

$$\omega_z = \infty$$

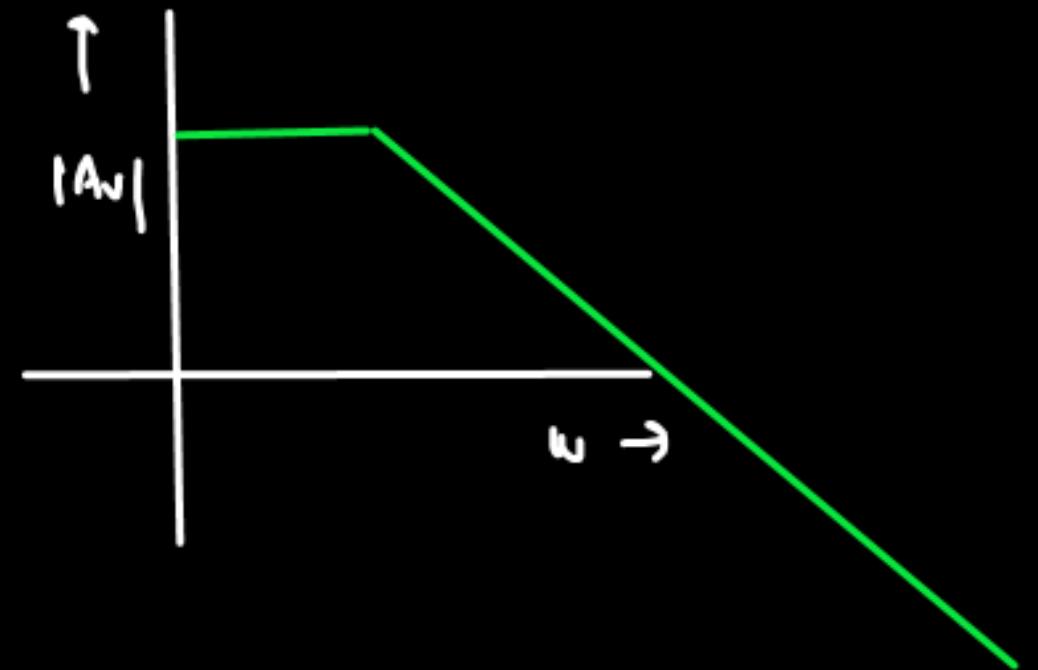

(b)

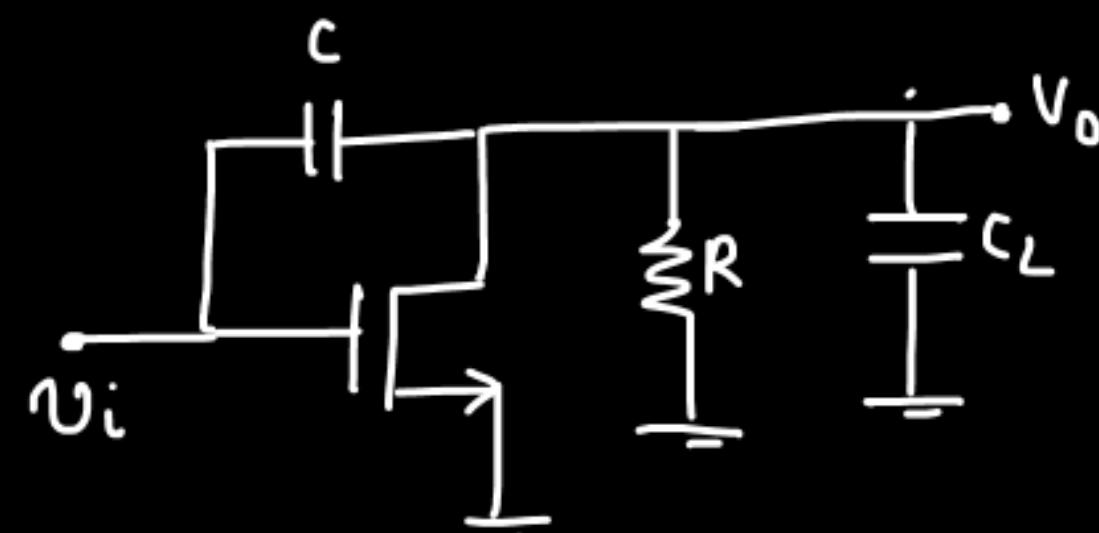

$$G_m = ?$$

$$I_{out} = -[g_m V_i - V_i \omega]$$

$$\frac{I_{out}}{V_{in}} = G_m = -[g_m - \omega]$$


$$R_{out} = R_L \parallel \frac{1}{(C_L + C)s}$$

$$A_V = \left[ -g_m + CS \right] \left[ \frac{R_L}{R_L(C_L + C)S + 1} \right]$$

$$A_V = \frac{-[g_m - C]}{R_L(C_L + C)S + 1}$$


$$\omega_p = \frac{1}{R_L(C_L + C)}$$

$$\omega_z = \frac{g_m}{C}$$

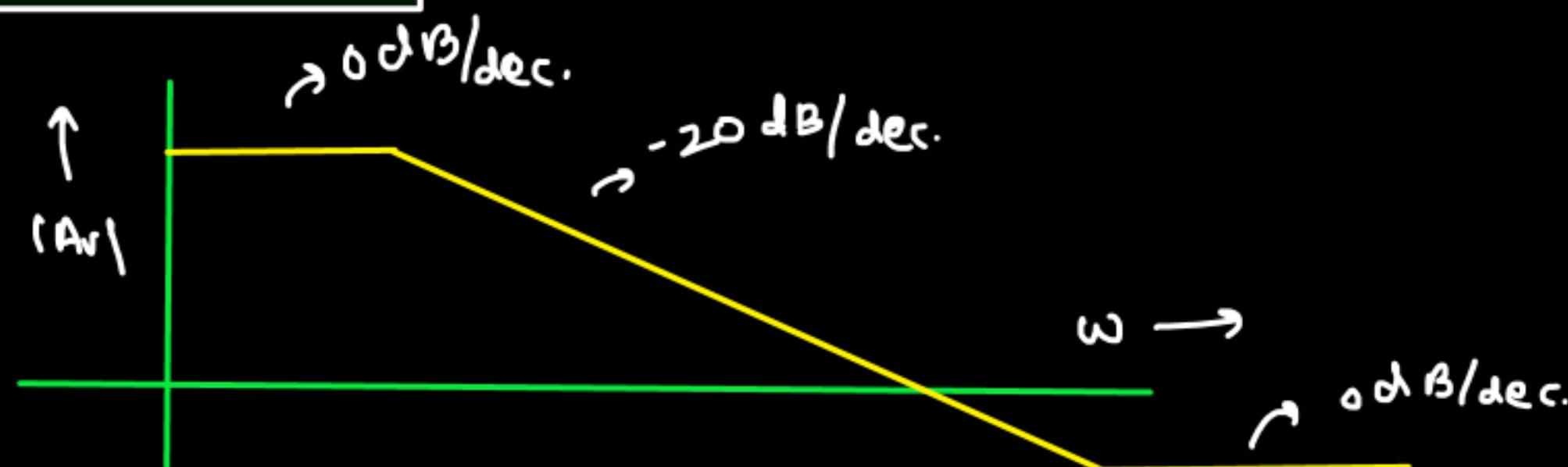


## Frequency Response for Common Gate Amplifiers:-

(High frequency)

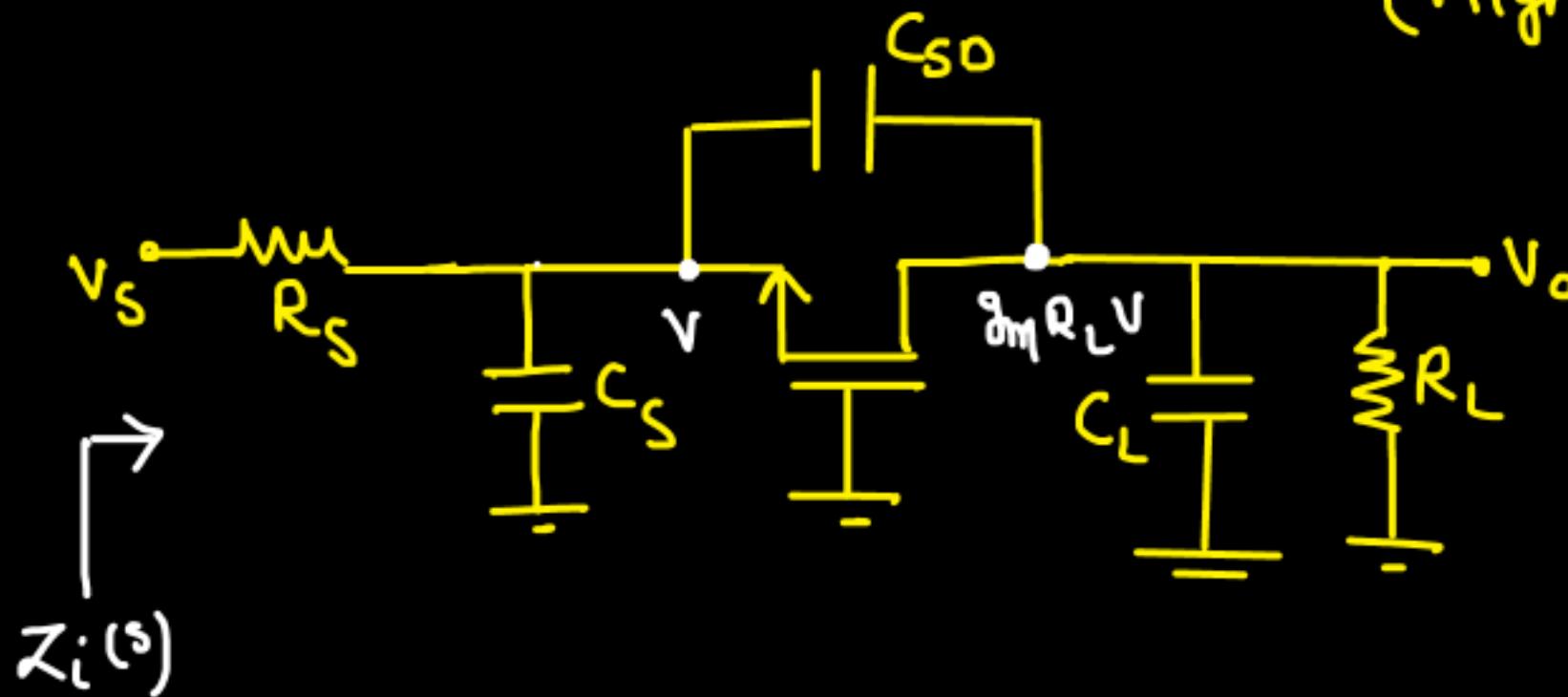


order = 2<sup>nd</sup>

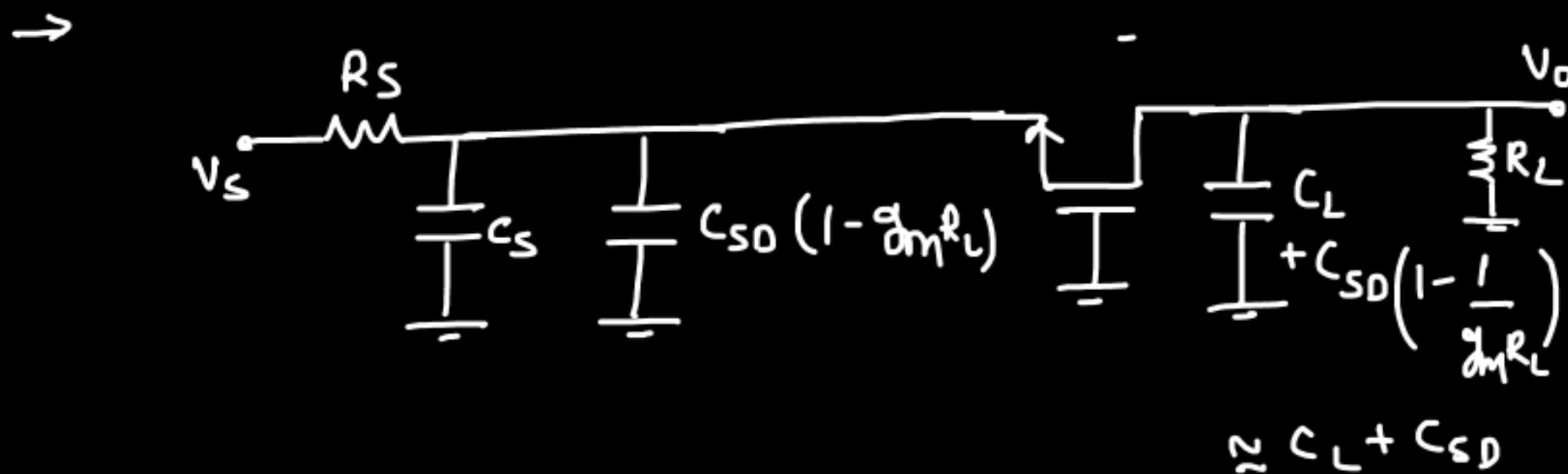$C_{SD}, C_s, C_L \rightarrow$  Parasitics



$$A = g_m R_L$$


$$\approx C_L + C_{SD}$$

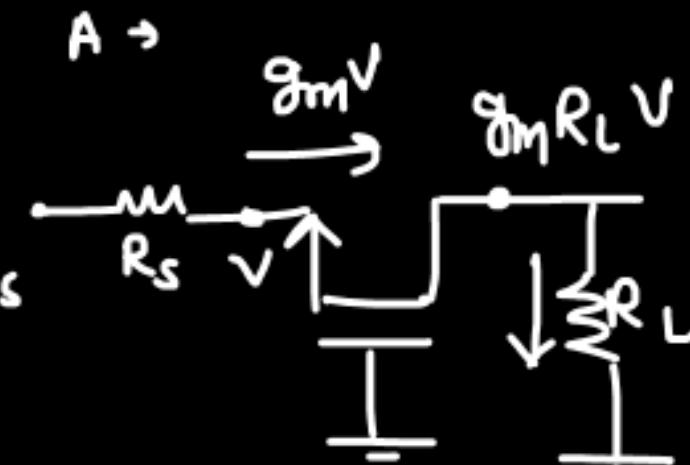

$$\omega_{Z_1} = 0 \quad , \quad \omega_{Z_2} = \infty$$

Poles:-

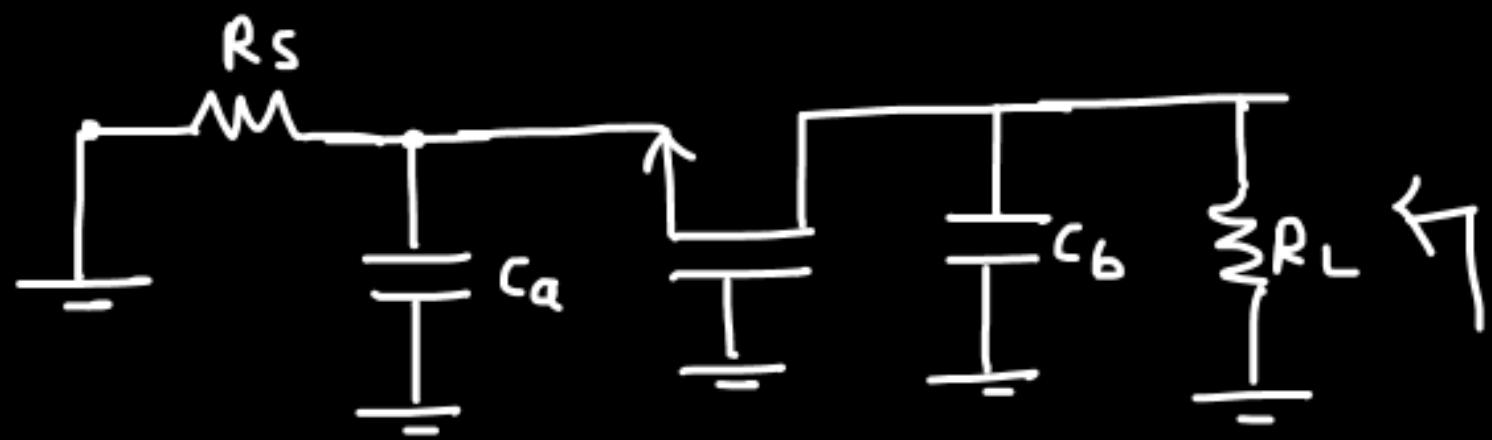

Equivalent resis. across

$$C_b \rightarrow R_L$$

$$\omega_{P_2} \text{ or } \omega_{P_1} = \frac{1}{C_b R_L}$$

$$C_a = C_S + C_{SD} \left[ 1 - \frac{1}{g_m R_L} \right]$$

$$C_b = C_S + C_{SD} \left[ 1 - \frac{1}{g_m R_L} \right] \approx C_S + C_{SD}$$



Equivalent res' across  $C_a \rightarrow R_S \parallel \frac{1}{g_m}$

DC gain:-

$$K = ? = \frac{V_o(\omega=0)}{V_S(\omega=0)}$$

$$\omega_{P_1} \text{ or } \omega_{P_2} = \frac{1}{C_a [R_S \parallel \frac{1}{g_m}]}$$


$\Rightarrow$

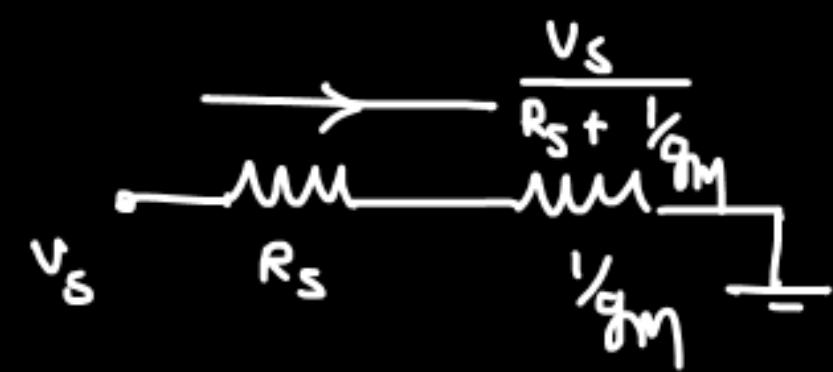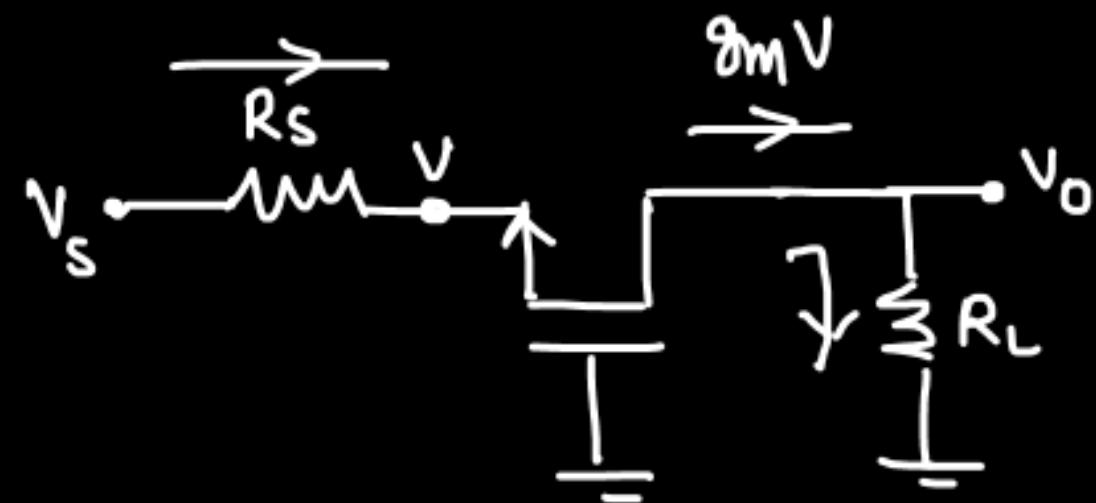

$$V_o = \frac{V_s}{R_s + \frac{1}{g_m}} \times R_L$$

$$\boxed{\frac{V_o}{V_s} = \frac{g_m R_L}{1 + g_m R_s}} = k$$

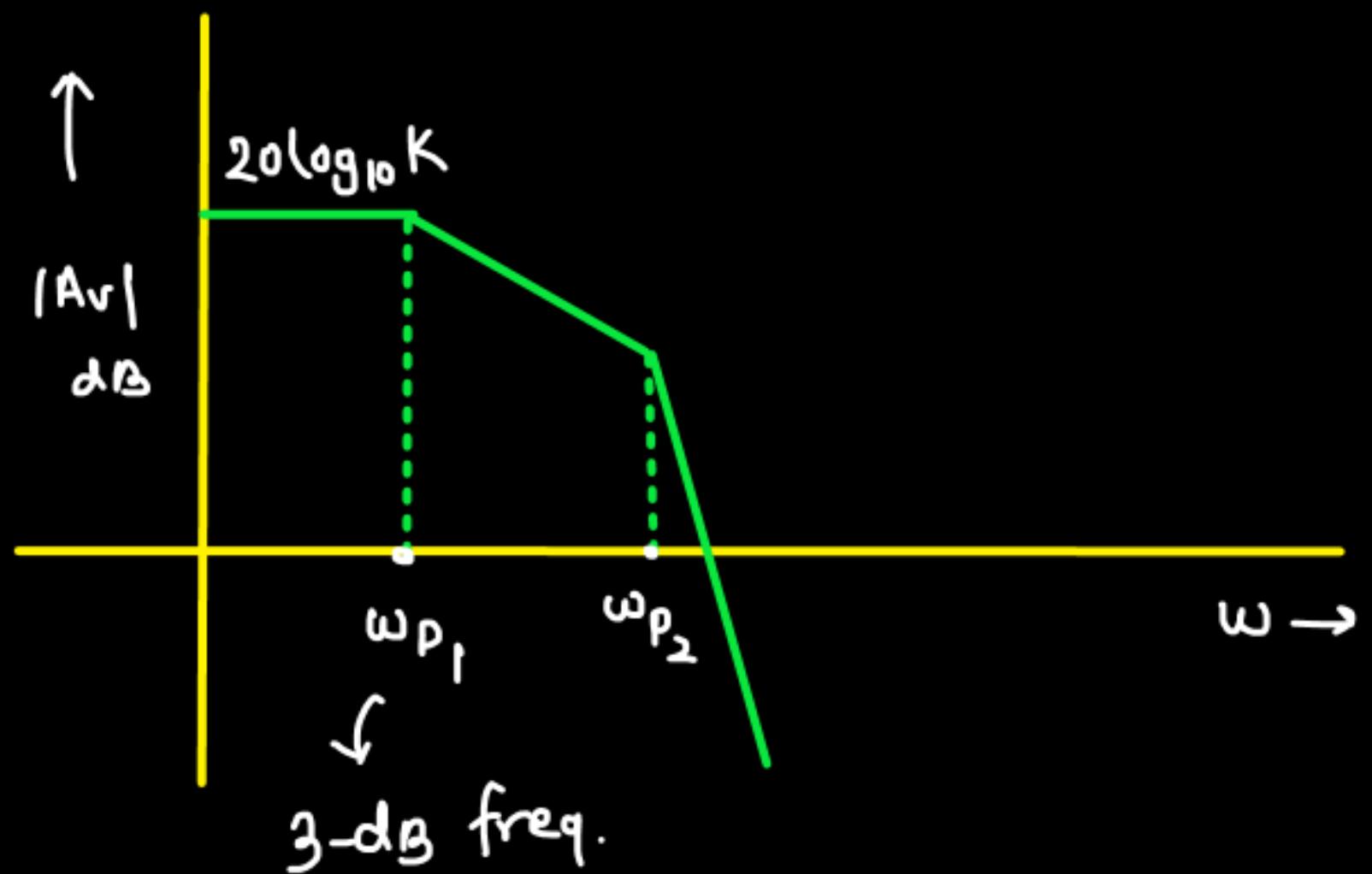
$$T(s) = \frac{K}{\left(\frac{s}{\omega_{P_1}} + 1\right) \left(\frac{s}{\omega_{P_2}} + 1\right)}$$



input resistance:-

$$Z_i(s) = R_s + \frac{1}{C_{as}} \parallel \frac{1}{g_m}$$

output impedance:-

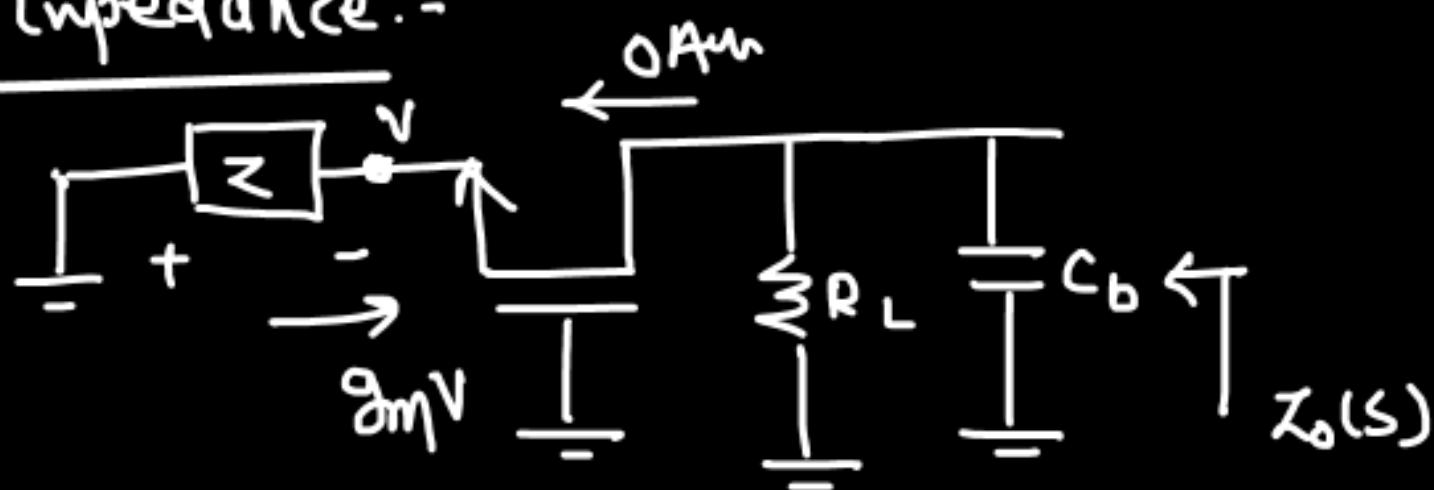

$$-g_m ZV = V$$

$$V[1 + g_m z] = 0$$


$$V=0$$

Ans

$$Z_o(s) = \frac{1}{C_b s} \parallel R_L$$

## Assignment - 10

Q.

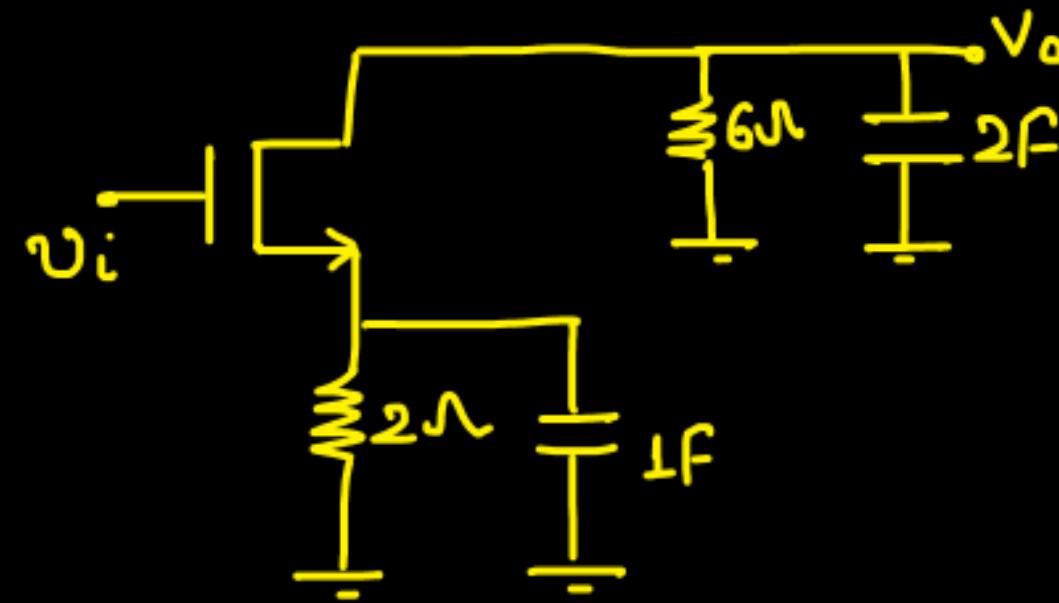

Given,  $g_m = 0.5 \text{ s}$

N.B.  $\rightarrow$  These are not the typical values of  $g_m$ , resistance and cap.

- ① Find 3-dB B.W. and freq. response.
- ② Tell the location of poles and zeros.
- ③ If small signal  $i_P$


$$V_i = 20mV \sin\left(\frac{3}{4}t\right)$$

Find  $V_o$ ?

→


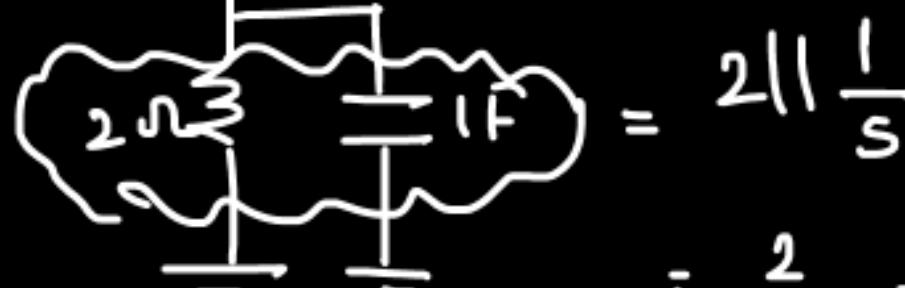
$$Z_L(s) = 6 \parallel \frac{1}{2s} = \frac{6}{(2s+1)}$$



$$= 2 \parallel \frac{1}{s}$$

$$= \frac{2}{2s+1} = Z(s)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-g_m Z(s)}{1 + g_m Z(s)}$$


$$= -0.5 \left( \frac{6}{2s+1} \right)$$

$$= \frac{1}{1 + 0.5 \left( \frac{2}{2s+1} \right)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-1 \cdot s (2s+1)}{(2s+1)(s+1)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-\frac{3}{(2s+1)}}{1 + \frac{1}{2s+1}} = \frac{-3(2s+1)}{(2s+1)(2s+2)}$$

M-II

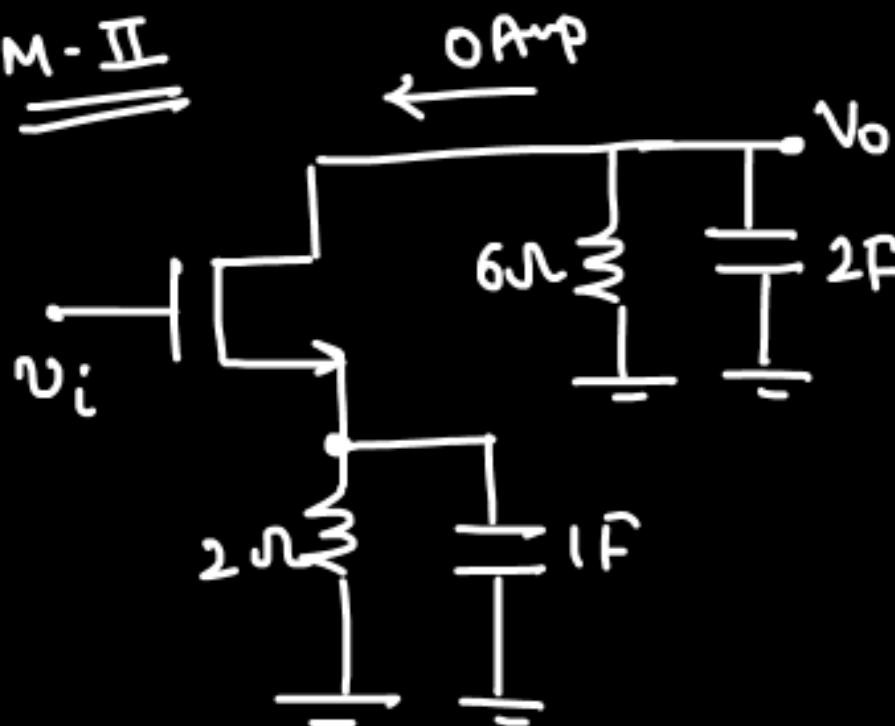

order = 2<sup>nd</sup>

Poles:-

$$\omega_{P_2} = \frac{1}{1F \left( 2\Omega || \frac{1}{8\eta} \right)} = \frac{1}{1F (2\Omega || 2\eta)} = 1 \text{ rad/sec.}$$

$$\omega_{P_1} = \frac{1}{2F(\epsilon)} = -\frac{1}{18} \text{ rad/sec.}$$

DC gain:-

$$K = -\frac{g_m R_L}{1 + g_m R_S} = -\frac{3}{1+1} = -1.5$$

Zeros:-


$$\omega_{Z_1} = \infty \quad (2F)$$

$$\omega_{Z_2} = ? \Rightarrow 2\Omega || \frac{1}{1S} = \infty \Rightarrow \frac{2}{2S+1} = \frac{1}{0}$$

$$T(s) = \frac{-1.5(2s+1)}{(12s+1)(s+1)}$$

$$\omega_{Z_2} = -1/2$$

Freq. response:-

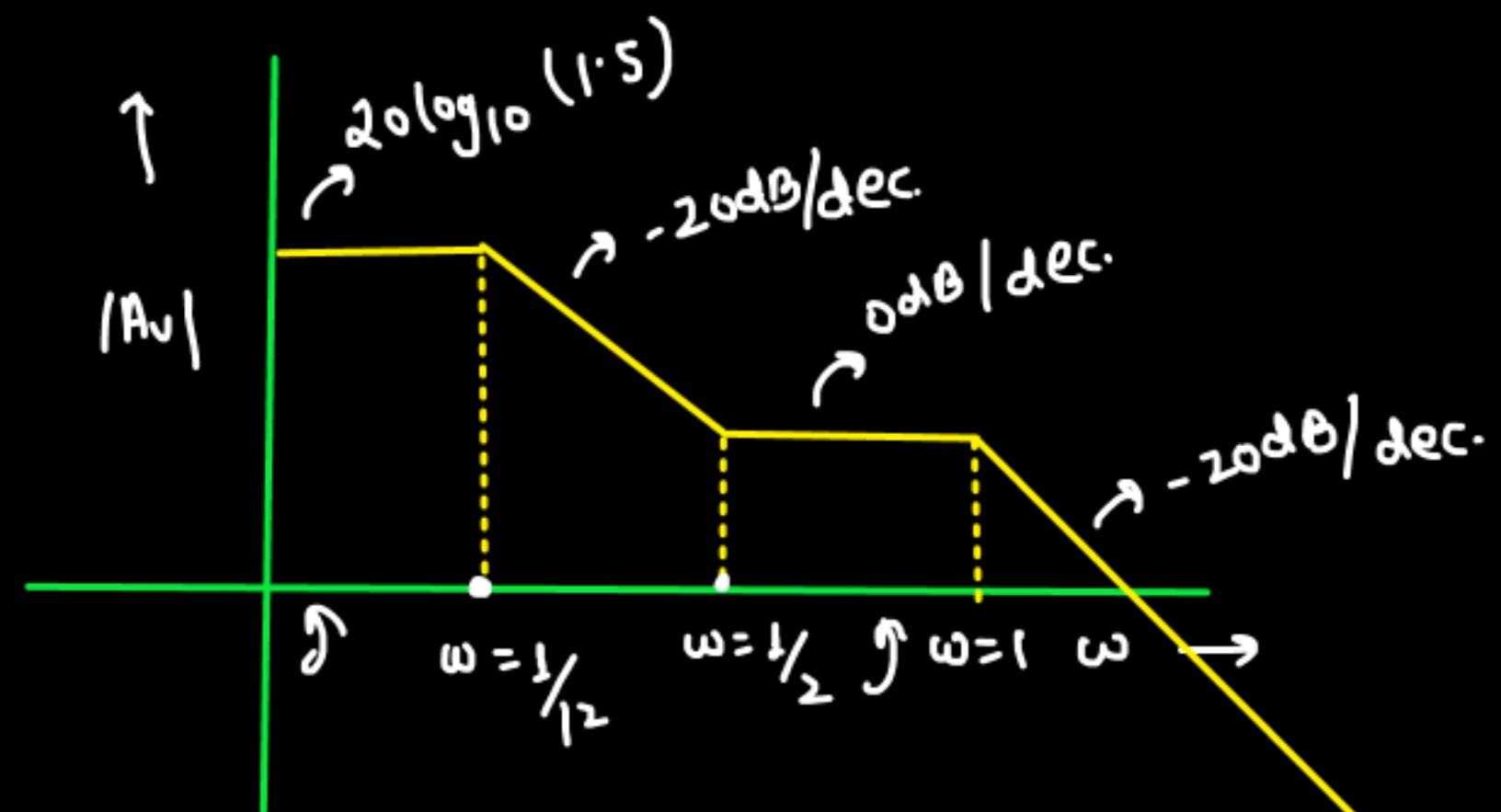

$$3-\text{dB B.W.} / \text{cut-off freq} = \frac{1}{12} \text{ rad/sec.}$$

(iii)  $V_i = 20mV \sin\left(\frac{3}{4}t\right); \omega_i = \frac{3}{4} \text{ rad/sec.}$

$$\frac{V_o(s)}{V_i(s)} = \frac{-1.5(2s+1)}{(12s+1)(s+1)}$$

$$20mV \sin\left(\frac{3}{4}t\right) \rightarrow \boxed{\frac{-1.5(2s+1)}{(2s+1)(s+1)}} \rightarrow ?$$

$$\rightarrow T(j\frac{3}{4}) = \frac{-1.5\left(2j \times \frac{3}{4} + 1\right)}{\left(1 \times j\frac{3}{4} + 1\right)\left(j\frac{3}{4} + 1\right)} = \frac{-1.5\left(6j + 4\right) \times 4}{(j36 + 4)(j3 + 4)}$$

$$|T(j\frac{3}{4})| = -0.24$$


$$\angle T(j\frac{3}{4}) = -244.2^\circ$$

$$\left[ -(180 + \tan^{-1}\left(\frac{6}{4}\right)) - \tan^{-1}\left(\frac{36}{4}\right) - \tan^{-1}\left(\frac{3}{4}\right) \right]$$

$\frac{3}{4}t$

$$\Rightarrow v_o(t) = 4.8mV \sin\left(\frac{3}{4}t - 244.2^\circ\right)$$


Q.

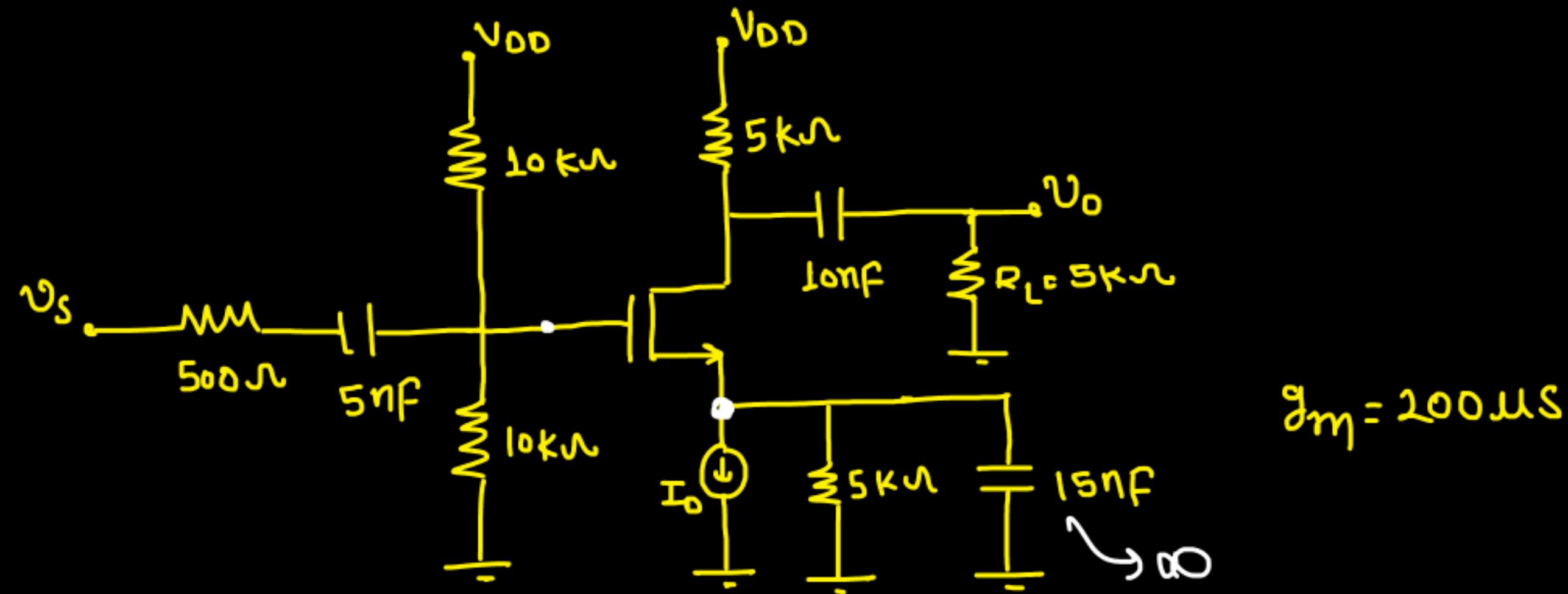

- (a) Find the location of poles and zeros.
- (b) Find the 3-dB cut-off frequency.


$$\rightarrow \omega_{z_1} = 0, \omega_{z_2} = 0 \quad \omega_{z_3} = \frac{-1}{15\eta \times 5K} = -13.33 \text{ K rad/sec.}$$

Req. across 5nF :-

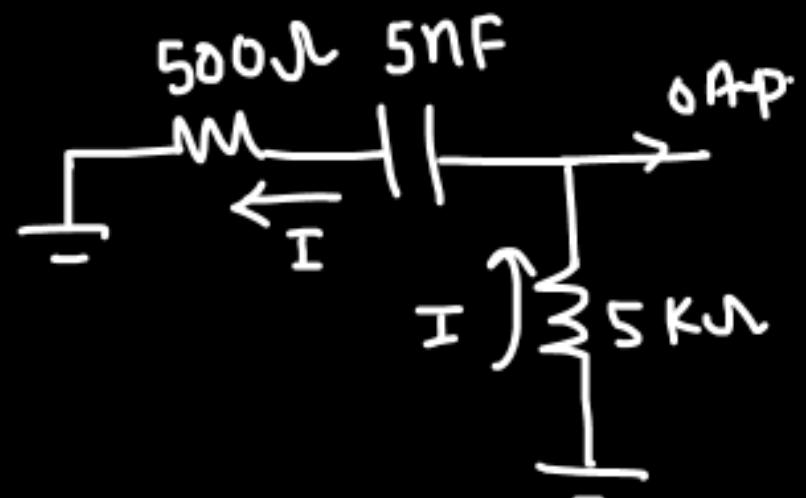

$$\omega_{P_3} = \frac{L}{5n \times 5.5K} = -36.36 \text{ Krad/sec.}$$

15nF :-

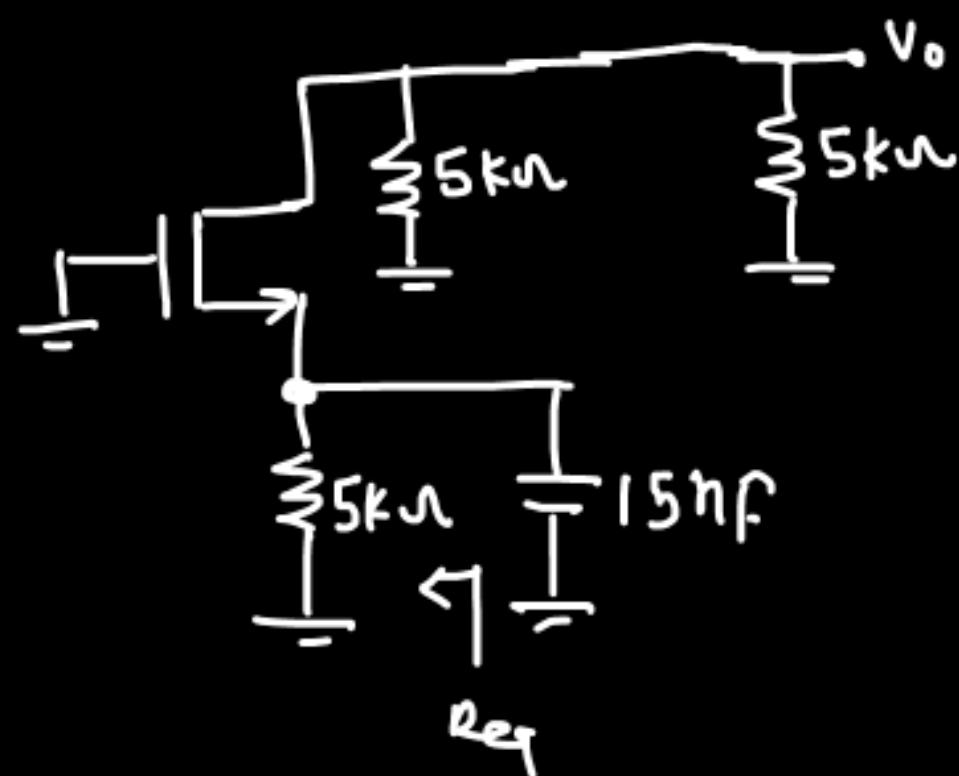


$$R_{eq} = 5K \parallel \frac{1}{g_m} = 5K \parallel 5K = 2.5K$$

$$\omega_{P_1} = \frac{1}{15n \times 2.5K} \quad [g_m = 200\mu S]$$

$$\omega_{P_2} = -26.67 \text{ Krad/sec.}$$


loopf :-

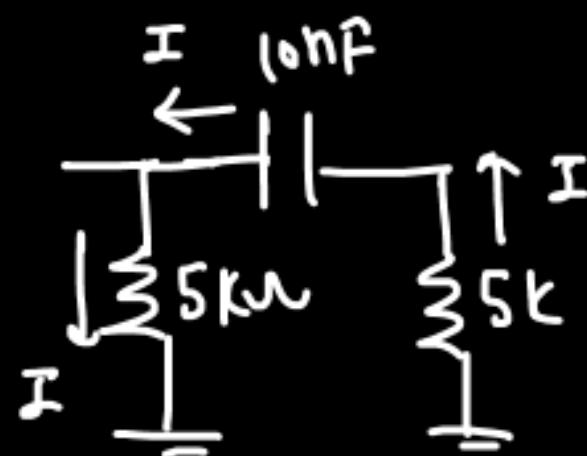


$$\omega_p = \frac{1}{10\eta \times 10K} = -10\text{krad/sec}$$

$$T(s) = \frac{A s^2 \left( \frac{s}{13.33K} + 1 \right)}{\left( \frac{s}{10K} + 1 \right) \left( \frac{s}{26.67K} + 1 \right) \left( \frac{s}{36.36K} + 1 \right)}$$

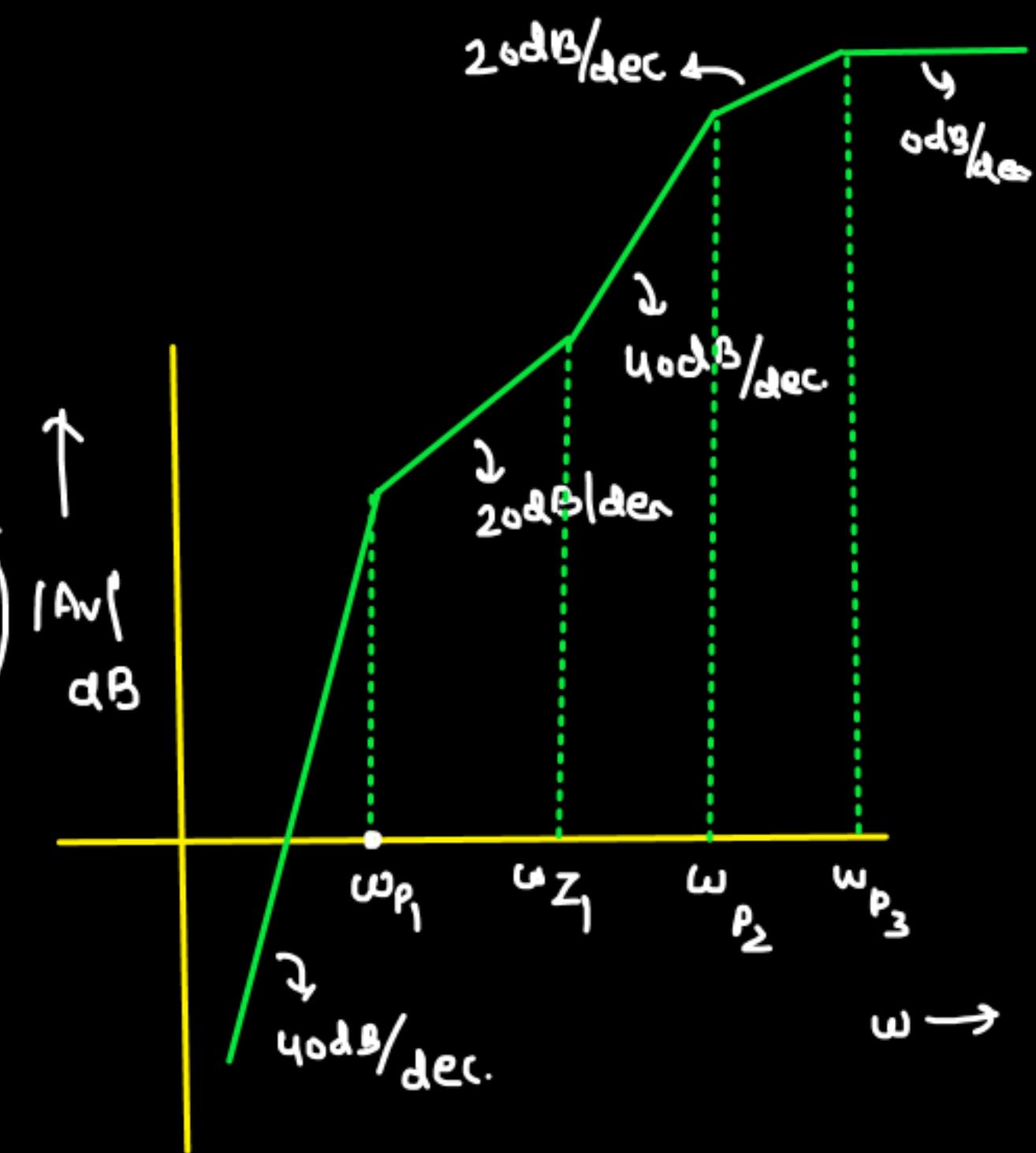3-dB cut-off freq. =  $36.36\text{krad/sec.}$




Q.

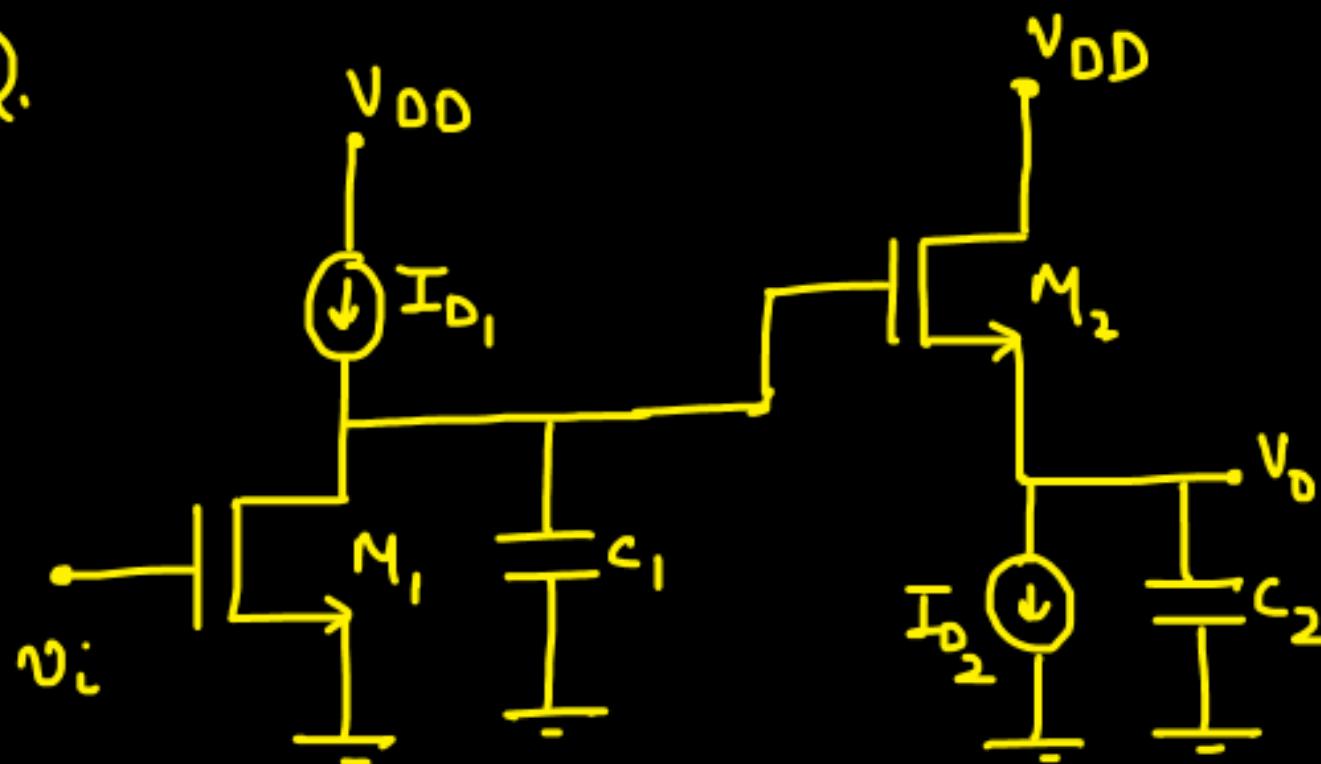

Write down the frequency response intuitively.


→ order = 2<sup>nq</sup>

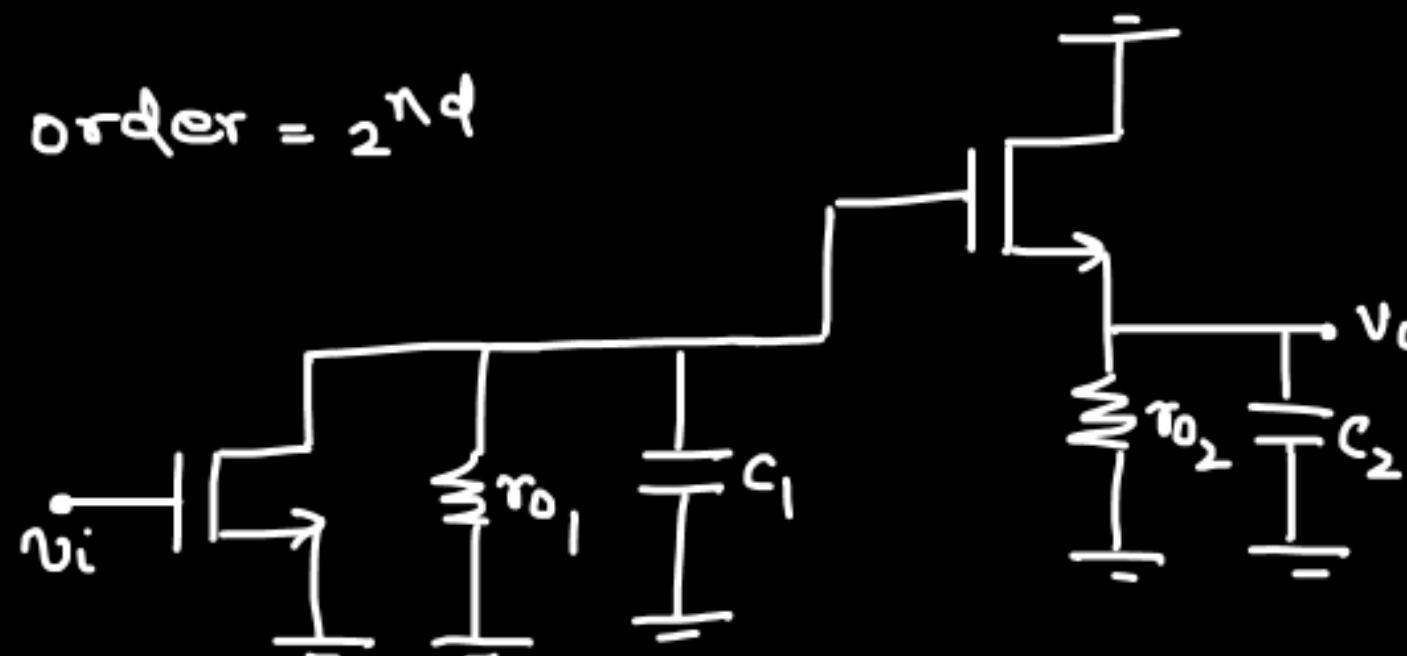

$$\omega_{p_1} \text{ or } \omega_{p_2} = \frac{-1}{r_{o1} C_1}$$


$$\omega_{p_2} \text{ or } \omega_{p_1} = \frac{-1}{C_2 \left[ \frac{1}{r_{o2}} || r_{o1} \right]}$$
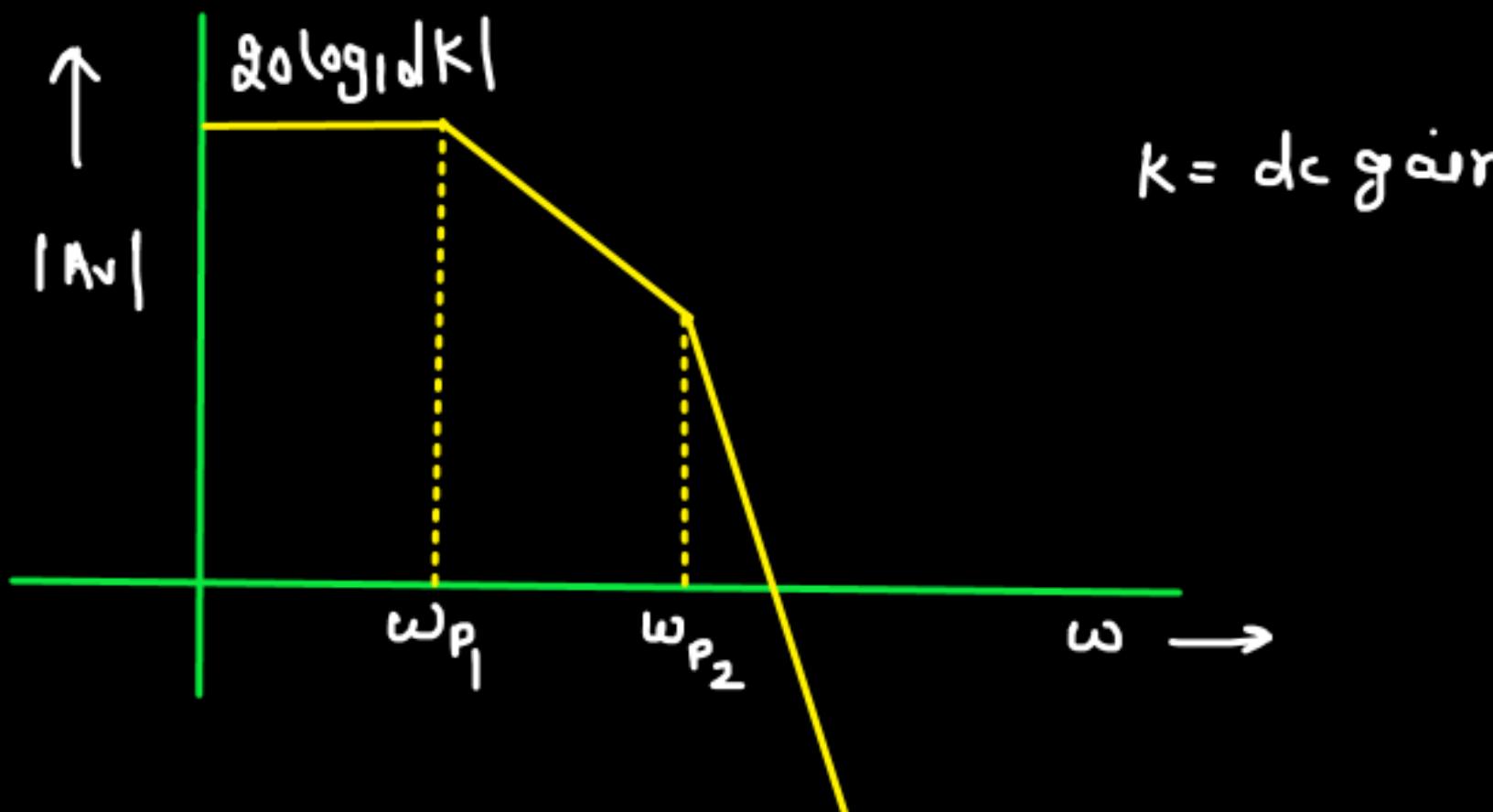
$$\omega_{z_1} = \infty, \omega_{z_2} = \infty$$



$k = \text{dc gain}$
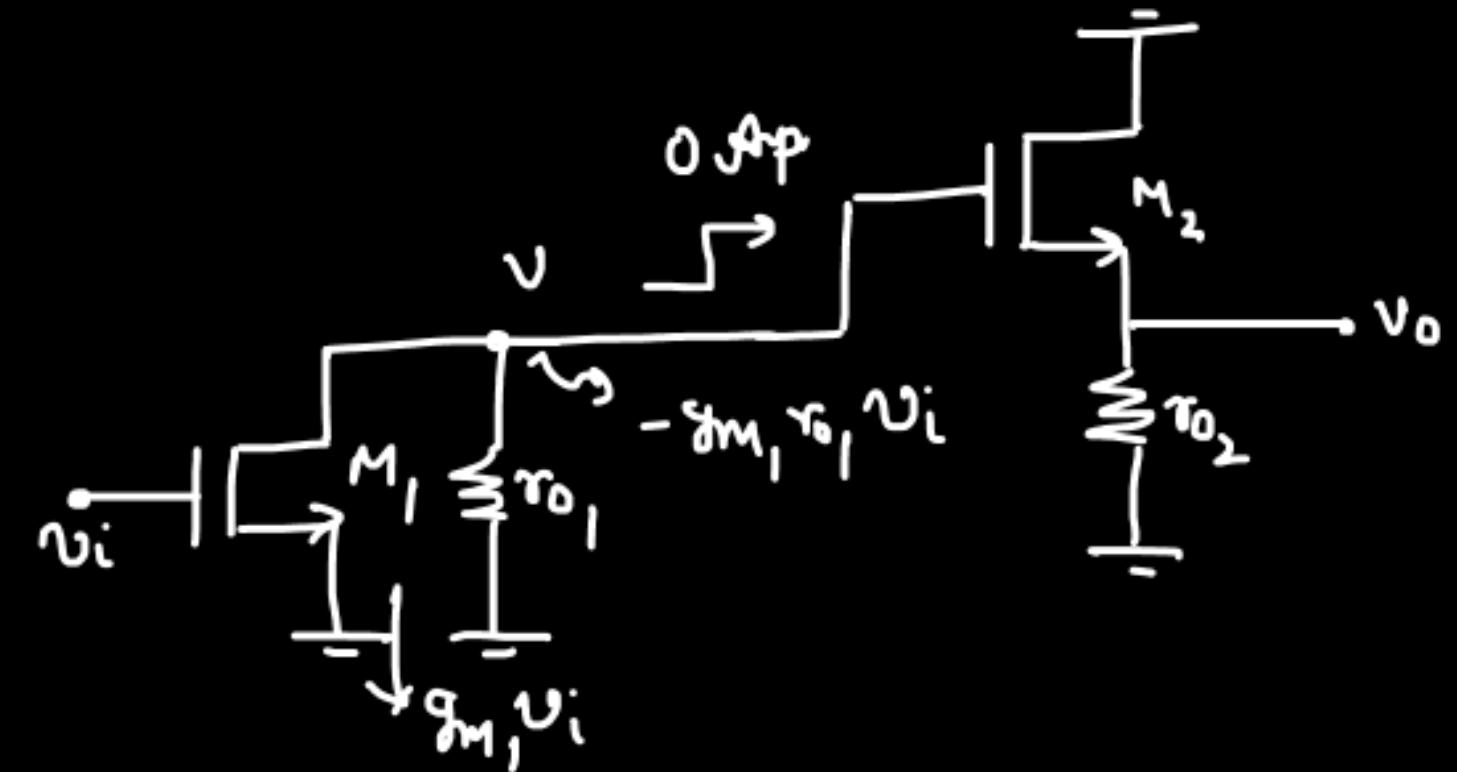
$$V_o = -\frac{\delta M_2 r_{02}}{1 + \delta M_2 r_{02}} \times \delta M_1 r_{01} = k$$




Q. Find (a) DC gain


(b) 3-dB Bandwidth ( $\omega_{3\text{-dB}}$ )

(c) 3-dB Unity gain Bandwidth ( $\omega_{\text{UgB}}$ )

[Make Necessary Approximations]

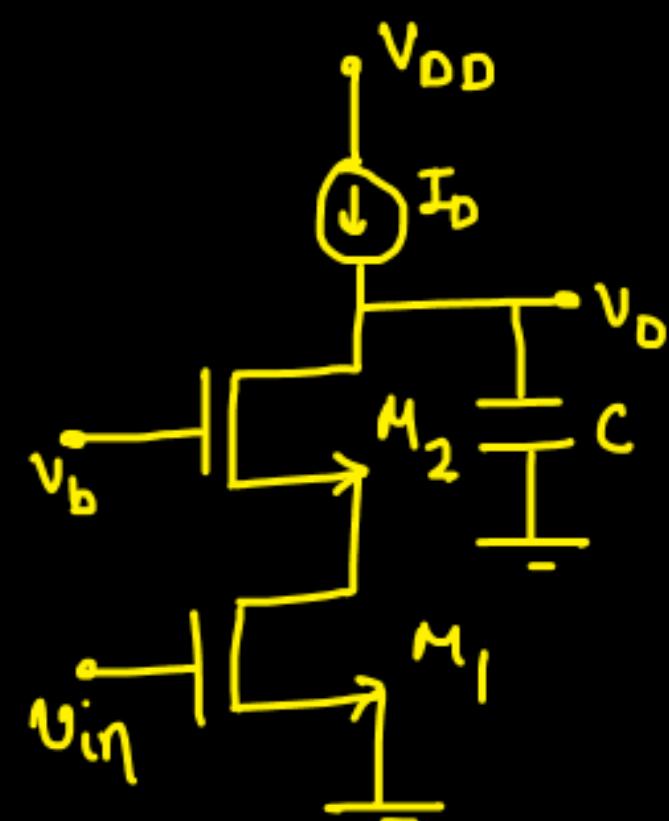

(a) Dc gain (Small signal gain) :-

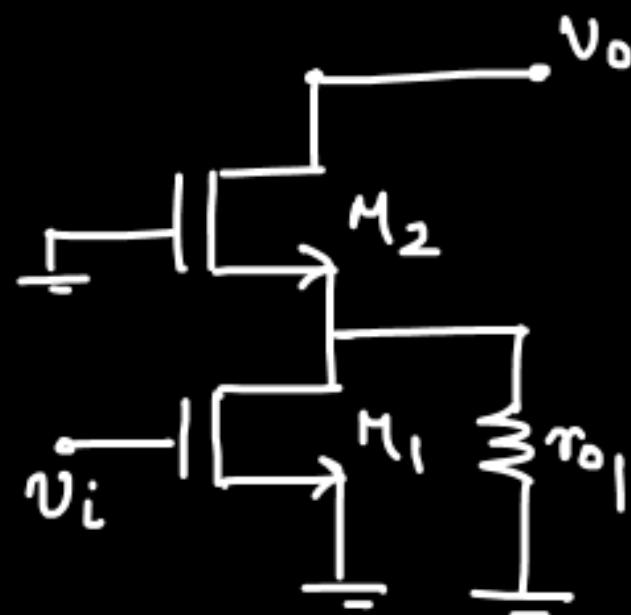

$$\Delta V = -G_m R_{out}$$

$$\Delta V \approx -g_m g_m r_{o_2} r_{o_1}$$


$$R_{out} = g_m r_{o_2} r_{o_1} + r_{o_2} + r_{o_1}$$

(ii) 1<sup>st</sup> order :-

$$\omega_z = \omega$$

$$\omega_p = \frac{1}{C[g_m r_{o_2} r_{o_1}]}$$
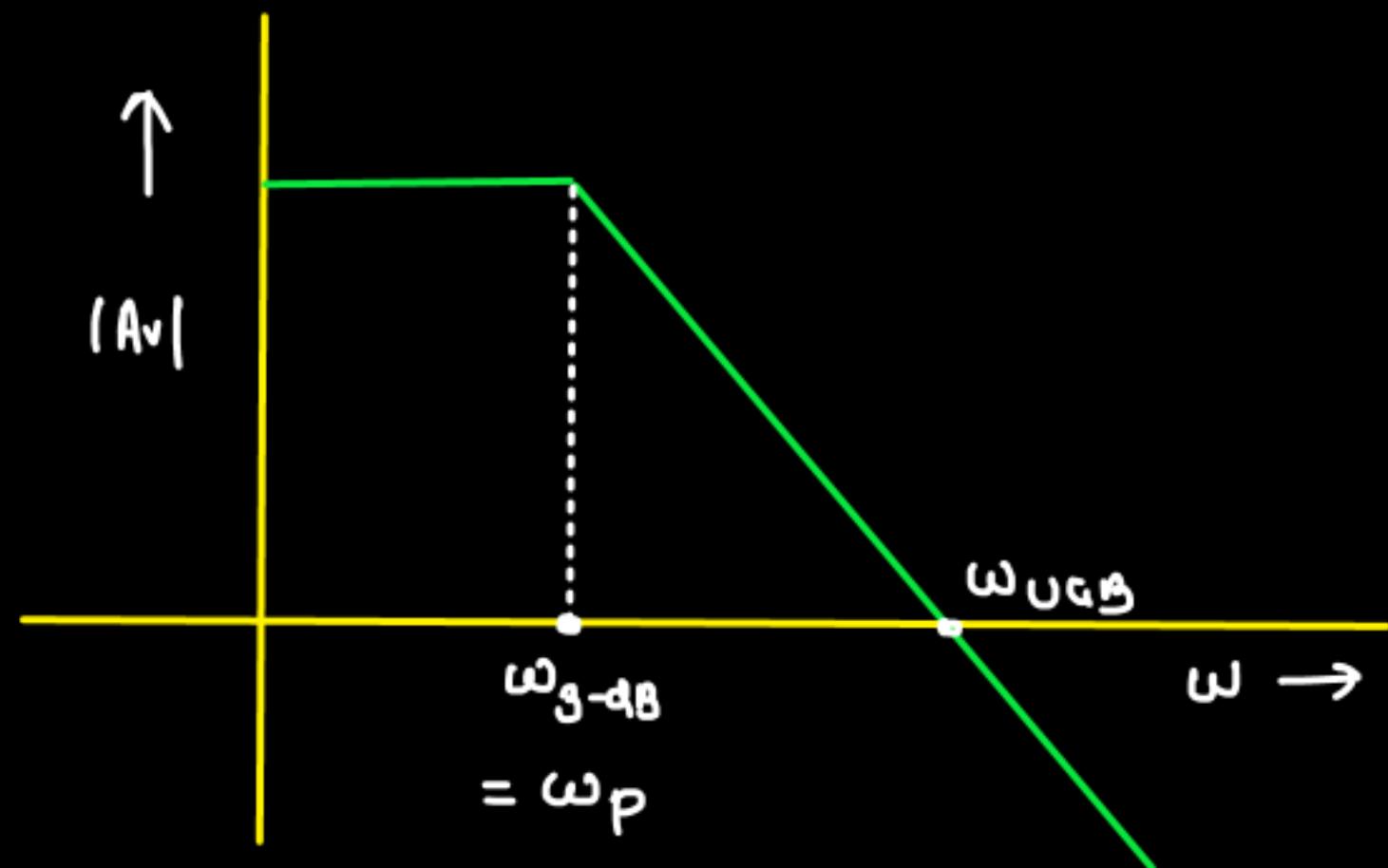
$$T(s) = \frac{-g_m g_m r_{o_1} r_{o_2}}{1 + s C g_m r_{o_2} r_{o_1}}$$



$$3\text{-dB freq. } \omega_c = \omega_p = \frac{-1}{C [g_m r_o_1 + r_o_2 + r_o_1]} \approx \frac{-1}{C g_m r_o_2 r_o_1}$$

Unity gain B.W.  $\rightarrow$  For a low Pass filter, the freq. @ which the gain is unity (0 dB).

$$@ \omega = \omega_{UAB}$$

$$|T(j\omega_{UAB})| = 1$$

$$\frac{g_m_1 g_m_2 r_{02} r_{01}}{\sqrt{1 + \omega_{UAB}^2 c^2 g_m_2^2 r_{02}^2 r_{01}^2}} = 1$$

$$g_m_1^2 g_m_2^2 r_{02}^2 r_{01}^2 = \omega_{UAB}^2 c^2 g_m_2^2 r_{02}^2 r_{01}^2$$

$$\omega_{UAB} = \frac{g_m_1}{c}$$

For a stable config. →

Gain Bandwidth product is constant.


3-dB Bandwidth × DC gain = Unity gain BW ×  $\times L$

$$\omega_{UGB} = A_v \times \omega_{3-dB}$$

For the given problem,

$$\omega_{UGB} = \frac{g_m_1 g_m_2 r_o_2 r_o_1}{C g_m_2 r_o_2 r_o_1} = \frac{g_m_1}{C}$$

Q.

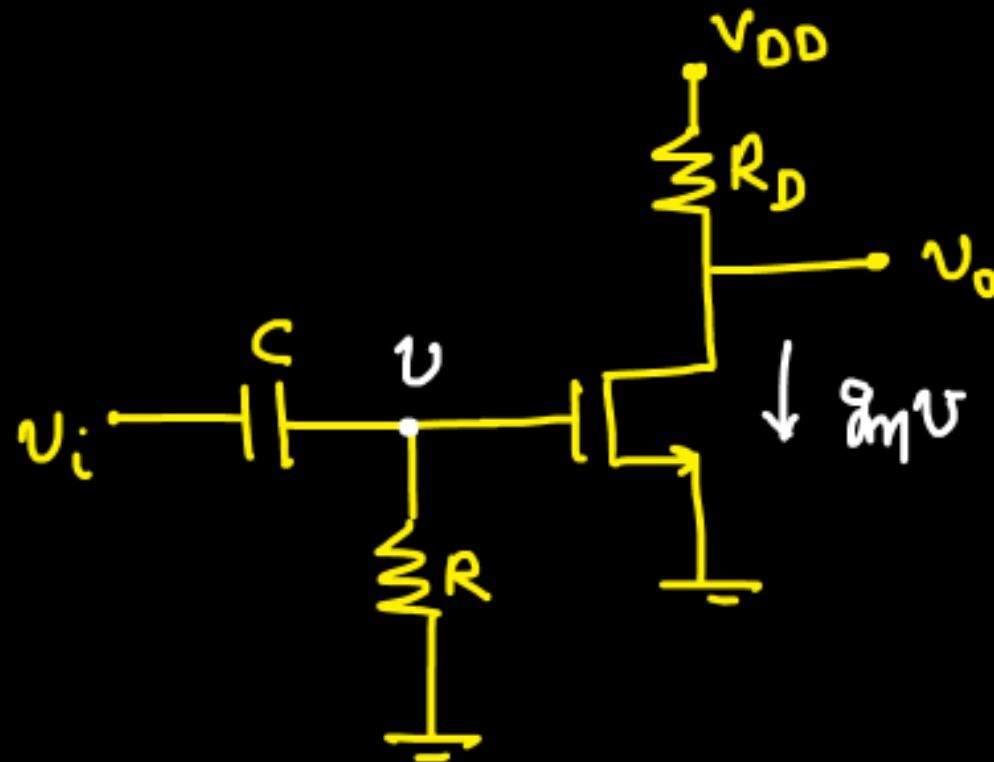

$$v_o = -g_m R_D v \rightarrow ①$$

$$v = \frac{R_C}{1 + R_C} v_i \rightarrow ②$$

$$\frac{v_o}{v_i} = -g_m R_D \left( \frac{R_C}{R_C + 1} \right)$$


Q. (a) Find 3-dB B.W.

(b) Find 3-dB cut-off freq.

(c) Find the freq. @ which the gain is unity.

$$\omega_Z = 0$$

$$\omega_P = -\frac{1}{RC}$$

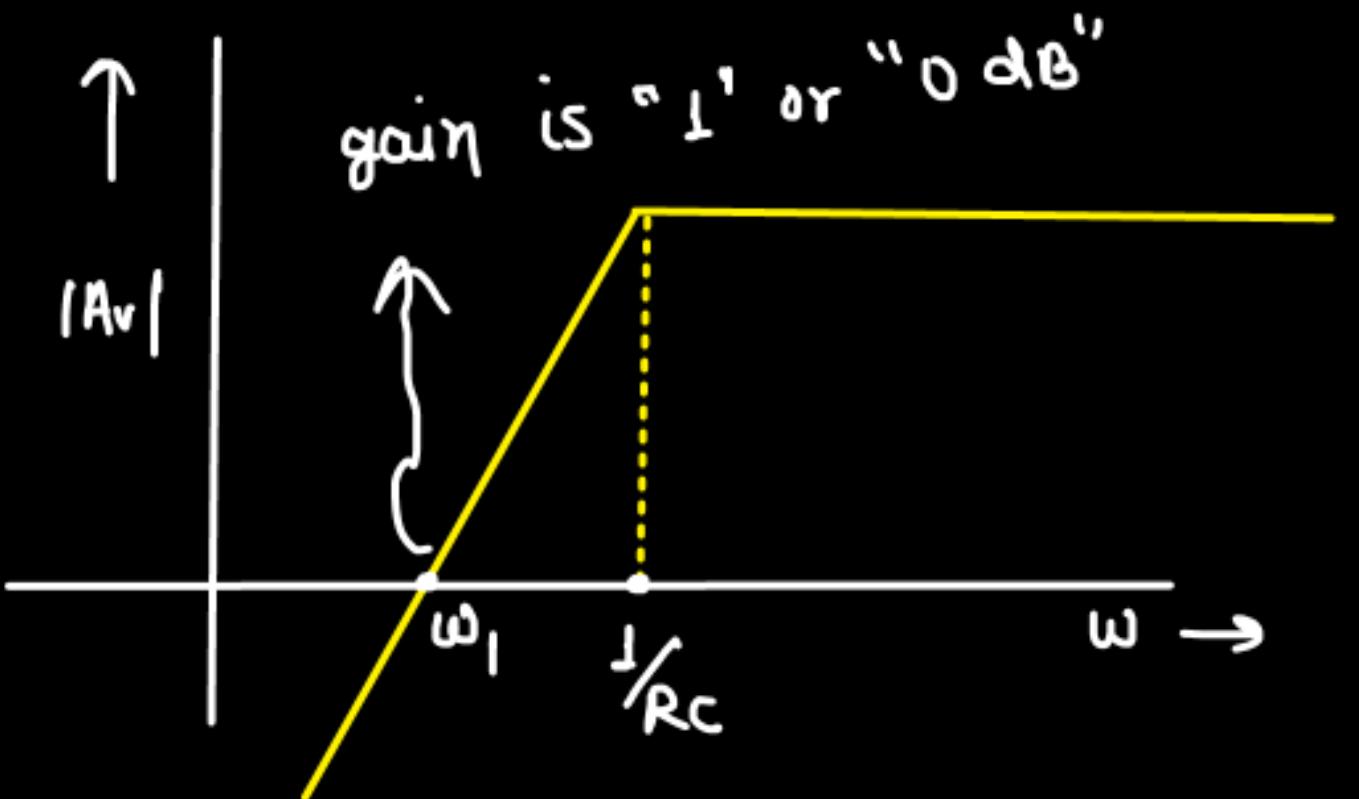

$$\textcircled{1} \quad \text{3-dB cut-off freq.} = \frac{1}{R_C} = \omega_p$$

$$\textcircled{2} \quad \text{3-dB B.W.} = \infty - \frac{1}{R_C} = \infty$$

$$\omega_1 = ?$$

$$@ \omega = \omega_1$$

$$|T(j\omega_1)| = L$$

$$\frac{g_m R_D \times R_C \omega_1}{\sqrt{1 + \omega_1^2 R^2 C^2}} = 1$$

$$\frac{g_m^2 R_D^2 R^2 C^2 \omega_1^2}{1 + \omega_1^2 R^2 C^2} = 1 + \omega_1^2 R^2 C^2$$

$$\omega_1^2 [g_m^2 R_D^2 R^2 C^2 - 1] = 1$$

$$\omega_1 = \frac{1}{R_C \sqrt{g_m^2 R_D^2 - 1}}$$



generally  $g_m R_D \gg L$

$$\omega_1 \approx \frac{1}{R_C \times g_m R_D}$$
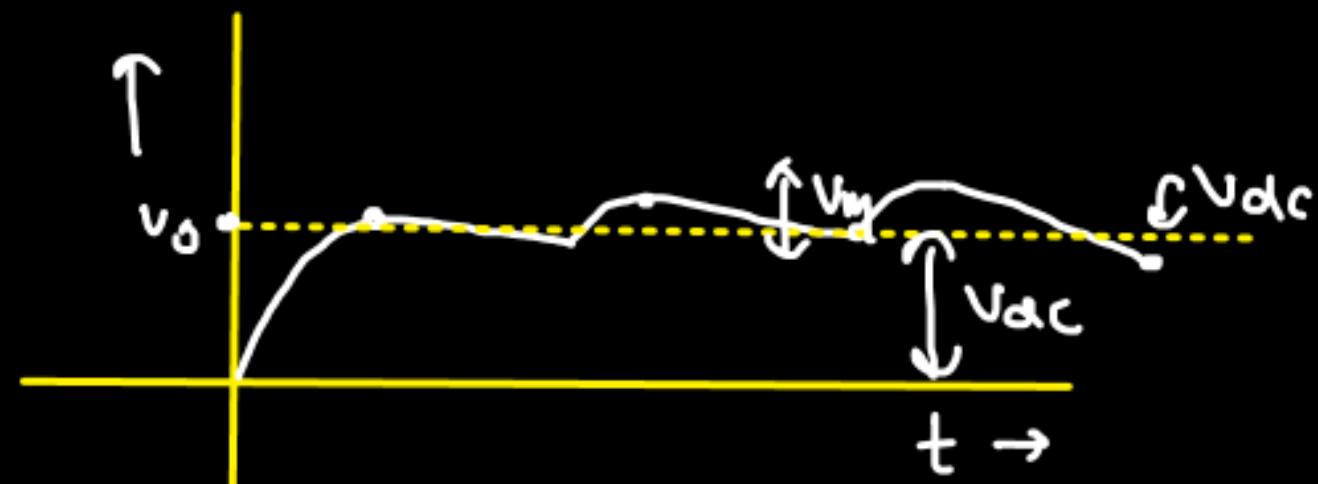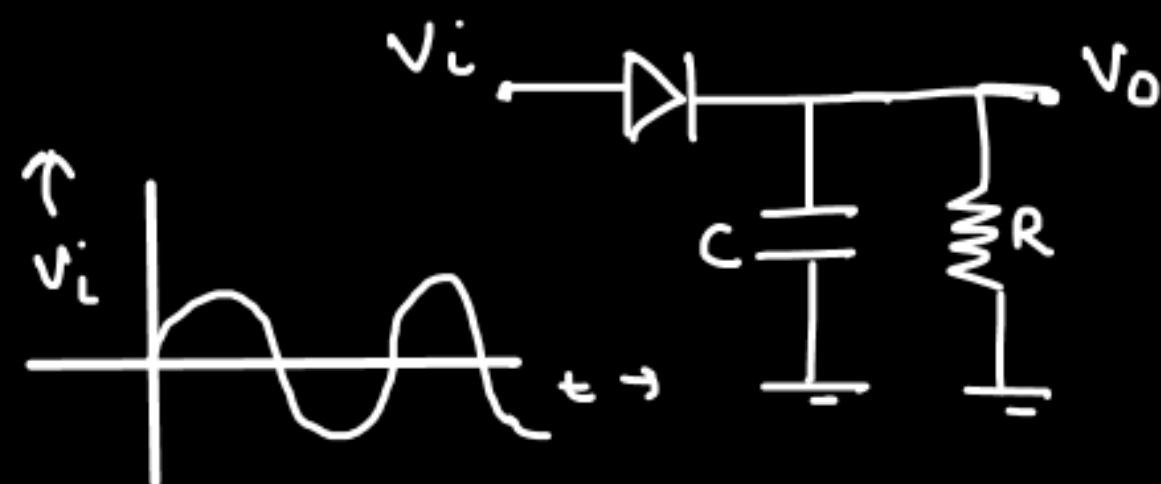
## Differential Amplifier


↳ Why do we need differential Amplifier?

\* Generally the dc supply we use , have some small ripple.



This supply  $v_o = V_{dc} + v_{ac}$   
will be fed to the Transistors. dc o/p ripple (small signal noise)

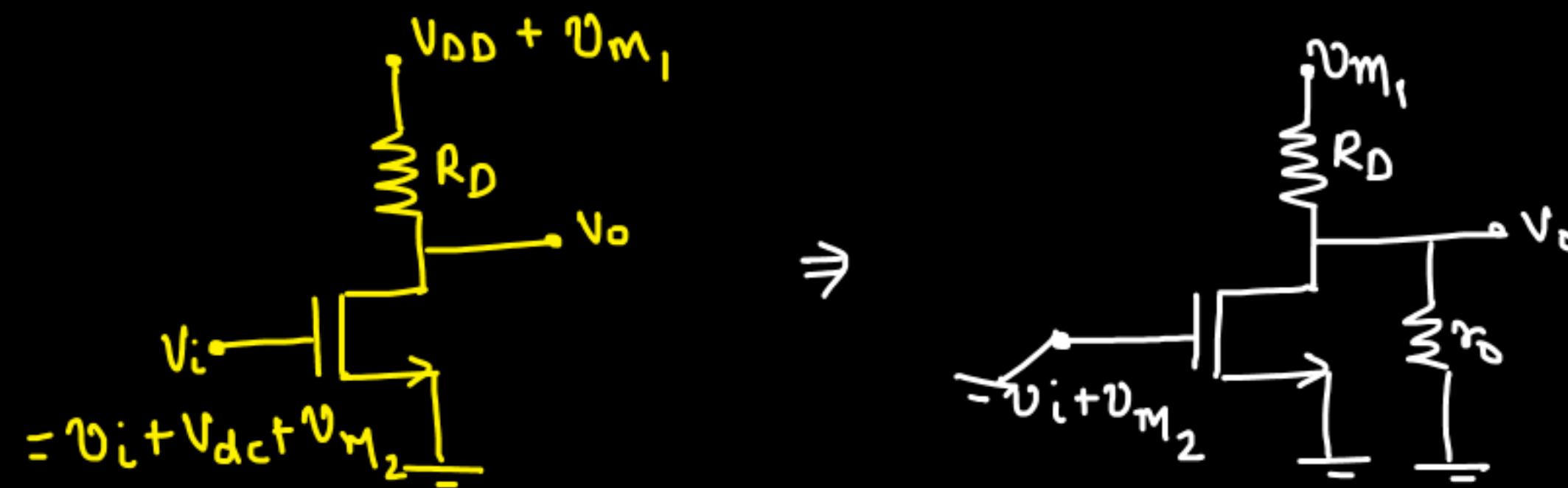Q. all the supplies have some ripples ( $V_{M_1}, V_{M_2}$ ) .  
Find small signal o/p.



$$V_o = -g_m (V_i + V_{M_2}) (R_D \parallel r_o) + \frac{r_o}{r_o + R_D} V_{M_1}$$

$$V_o = -g_m (R_D \parallel r_o) V_i - g_m (R_D \parallel r_o) V_{M_2} + \frac{r_o}{r_o + R_D} V_{M_1}$$


$$v_o = \underbrace{g_m (R_D || r_o) v_i}_{\text{desired}} - \underbrace{g_m (R_D || r_o) v_{m_2} + \frac{r_o}{r_o + R_D} v_{m_1}}_{\text{NOISE}}$$

To eradicate the noise part, we use differential amp.


## Basic Idea:-

- ↳ At input, you have "signal + noise"
  - ↳ At output, you have "signal + noise"
- you want amplified o/p, but no noise  $\Rightarrow$

$$[v_o = \underline{A} v_i]$$

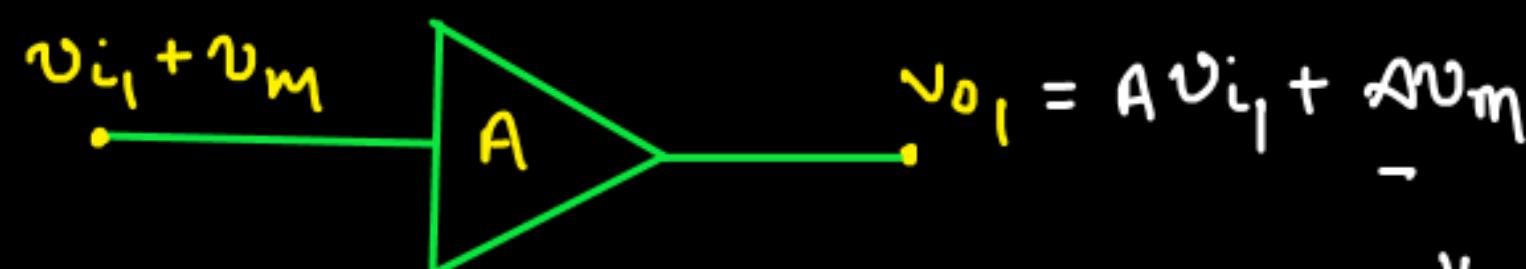
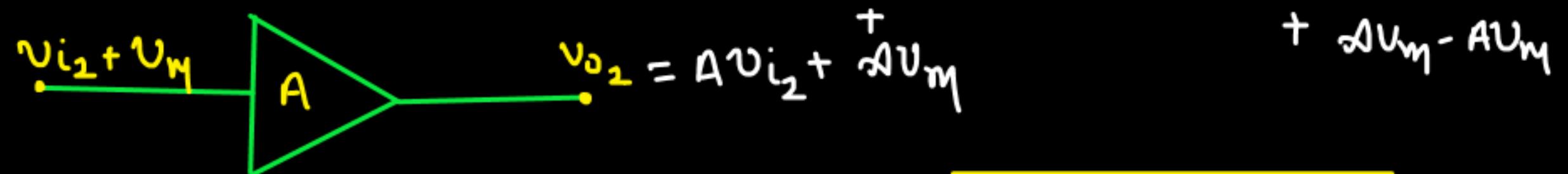
$$v_o = v_{o2} - v_{o1} = A(v_{i2} - v_{i1})$$






$$v_o = A(v_{i2} - v_{i1})$$

if  $v_{i_2} = v_{i_1}/2$  and  $v_{i_1} = -v_{i_2}/2$

$$v_o = Av_i \rightarrow \text{desired o/p}$$

Here  $v_{i_2}$  and  $v_{i_1}$  are differential signals.

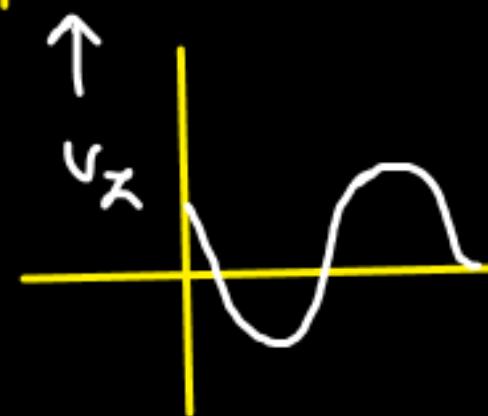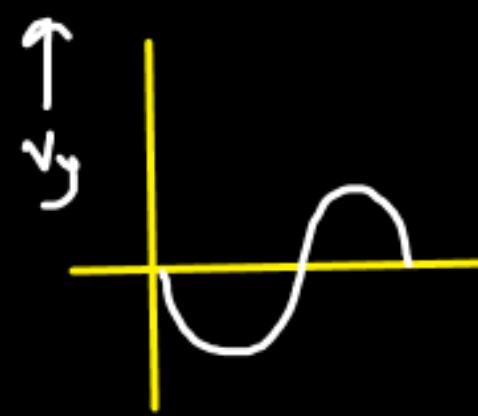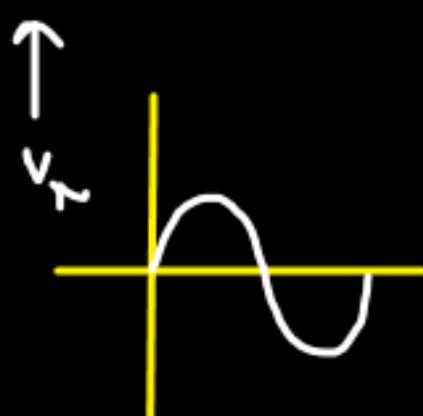
- same amplitude
- same dc level
- opposite in phase



→  $v_x$  &  $v_y$  are differential signals.


→  $v_x$  &  $v_z$  are not differential signals.

## How to generate differential Signal:-

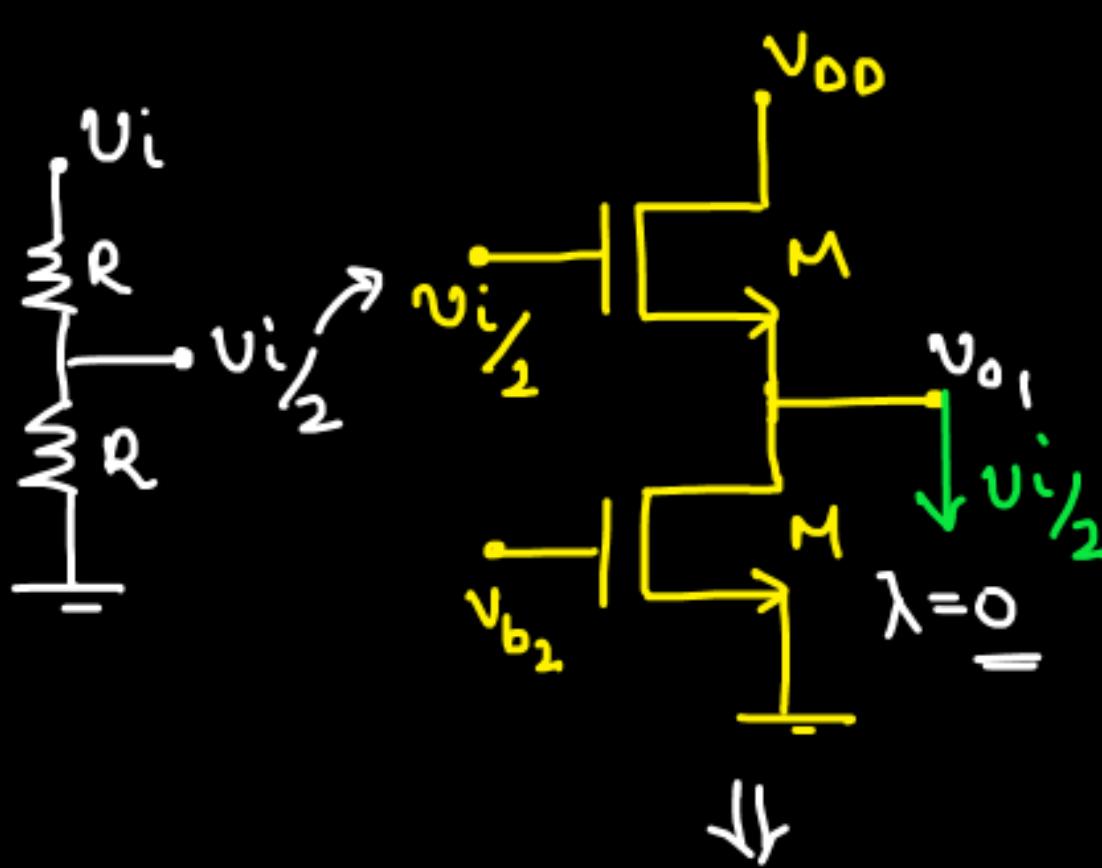


$$g_m \left( \frac{v_i}{2} - v_{o1} \right) = 0$$

$$v_{o1} = \frac{v_i}{2}$$

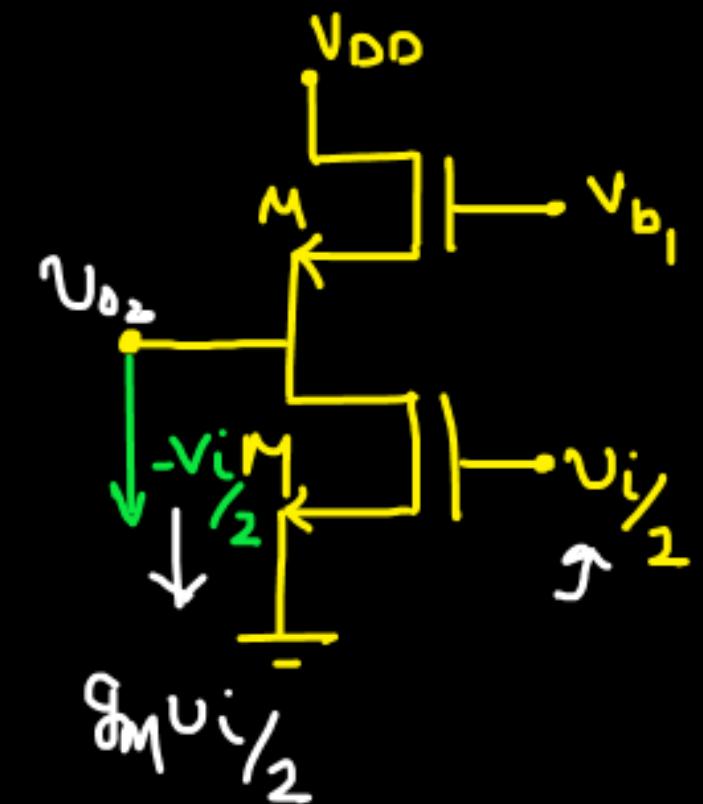


$$v_{o2} = - g_m \frac{v_i}{2} \left[ \frac{1}{g_m} \right]$$

$$v_{o2} = - \frac{v_i}{2}$$

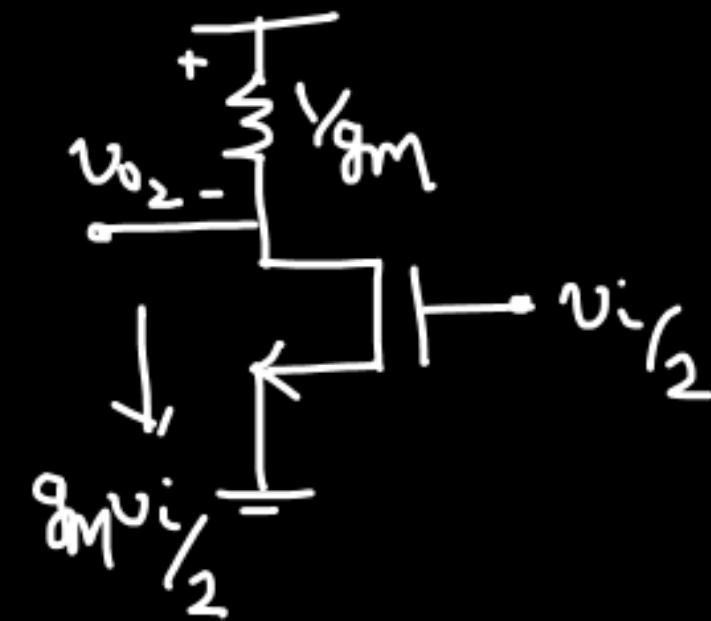

## Differential Amplifier:-

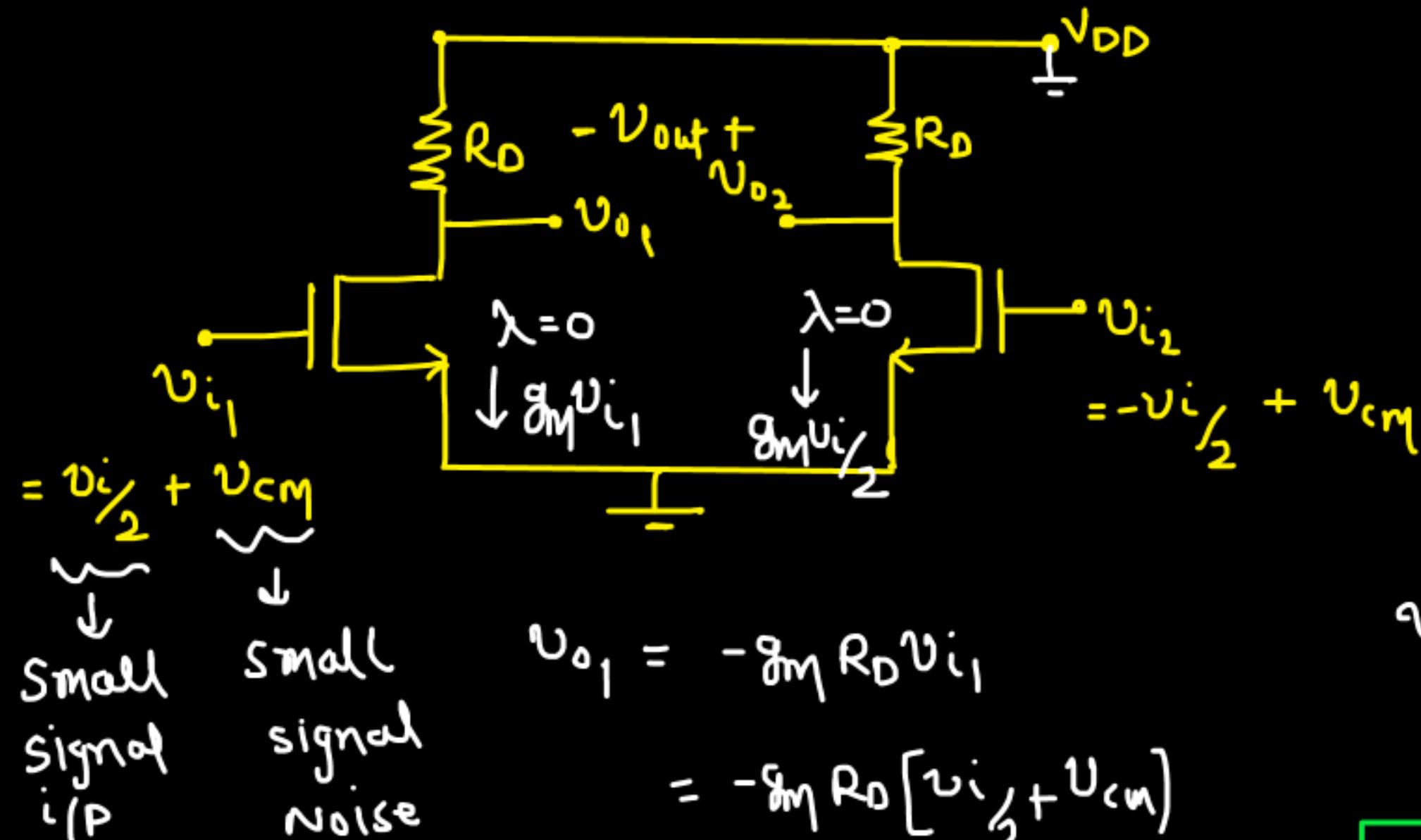

$$V_{o1} = -g_m R_D \frac{V_i}{2} - g_m R_D V_{cm}$$


$$V_{o2} = g_m R_D V_{i1} - g_m R_D V_{cm}$$

$$V_o = V_{o_2} - V_{o_1}$$

$$= g_m R_D \frac{V_i}{2} - g_m R_D V_{cm} - \left[ -g_m R_D \frac{V_i}{2} - g_m R_D V_{cm} \right]$$

$$V_o = g_m R_D V_i$$

$$\frac{V_o}{V_i} = g_m R_D$$

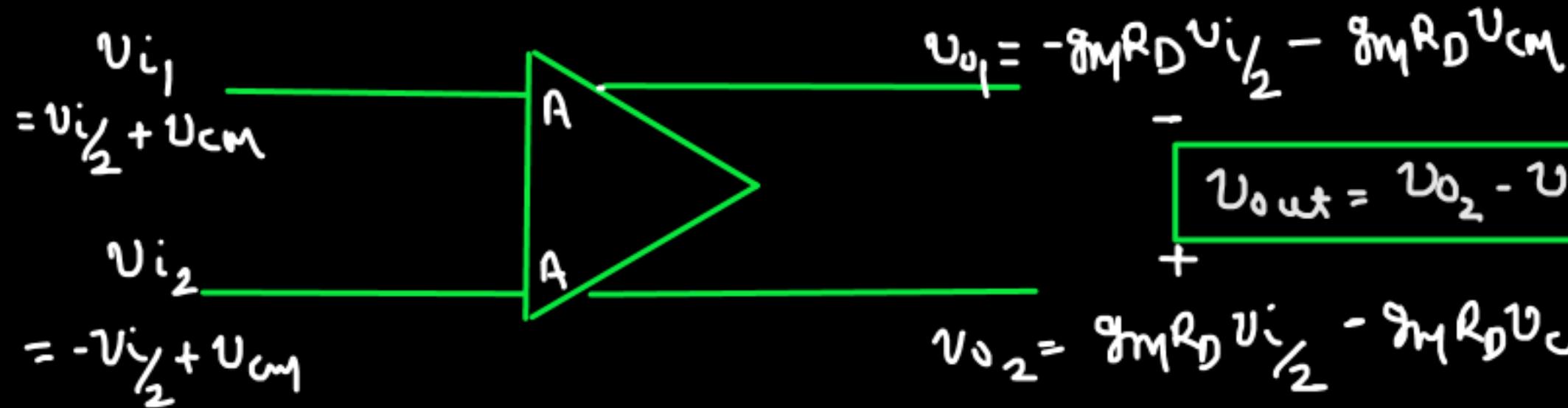


$$V_{o_1} = -g_m R_D V_{i_1}/2 - g_m R_D V_{cm}$$

$$V_{out} = V_{o_2} - V_{o_1} = g_m R_D V_i$$

$$V_{o_2} = g_m R_D V_{i_1}/2 - g_m R_D V_{cm}$$

## Some Common Terms:-

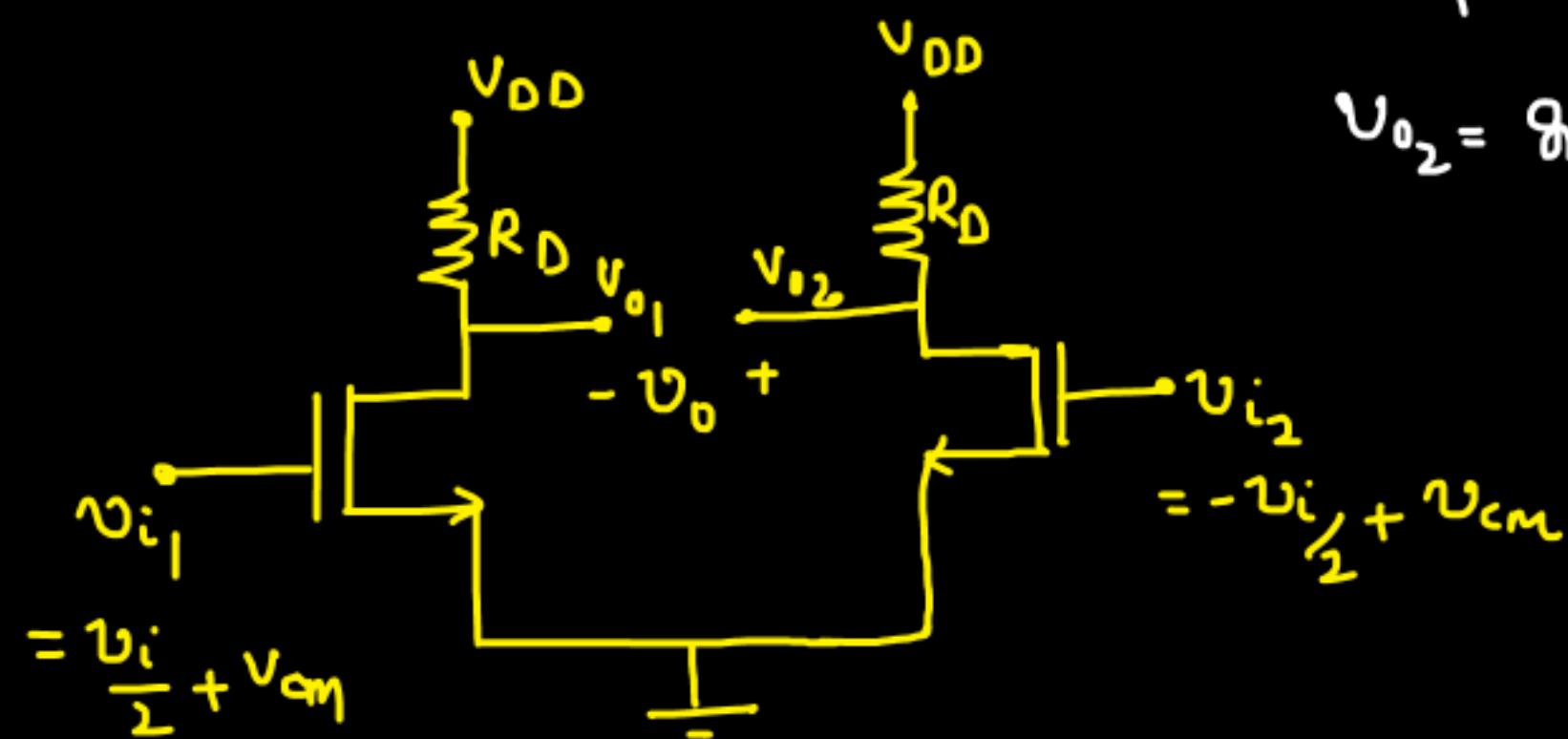

$$v_{o1} = -g_m R_D \frac{v_i}{2} - g_m R_D v_{cm}$$

$$v_{o2} = g_m R_D \frac{v_i}{2} - g_m R_D v_{cm}$$

$$= -\frac{v_i}{2} + v_{cm}$$

\* differential input  $(v_i)_d = v_{i1} - v_{i2} = v_i$


\* differential output  $(v_o)_d = v_{o2} - v_{o1} = g_m R_D v_i$

\* differential gain  $(\Delta v)_d = \frac{(v_o)_d}{(v_o)_i} = g_m R_D$

⇒ HOW TO FIND Differential Gain :-

Put  $v_{i_1} = v_{i/2}$  and  $v_{i_2} = -v_{i/2}$  {if  $v_{i_1} - v_{i_2} = v_i$ }

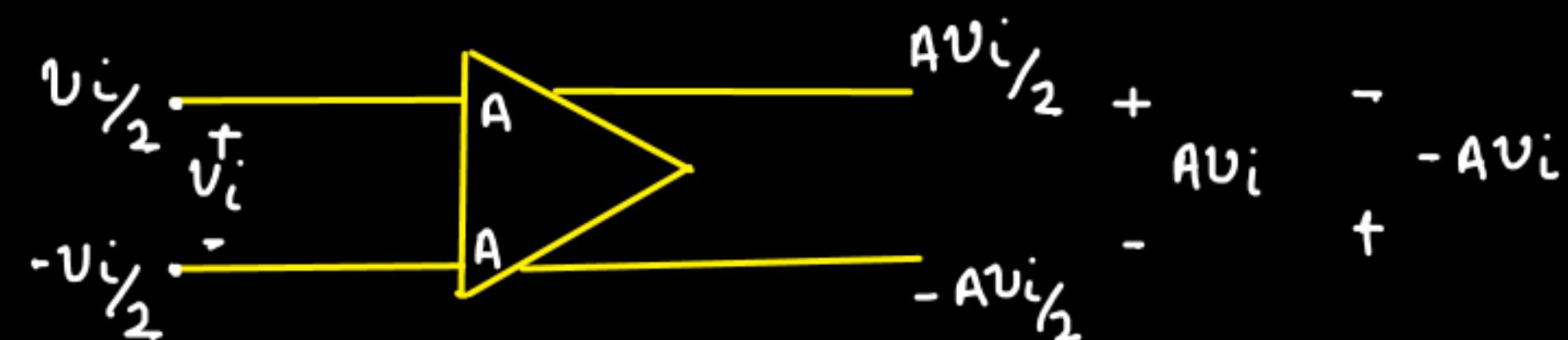Calculate  $v_o = v_{o_2} - v_{o_1}$  OR  $v_{o_1} - v_{o_2}$



Here  $A = -g_m R_D$

\* Common mode input  $(V_i)_{CM} = \frac{V_{i1} + V_{i2}}{2} = \frac{2V_{CM}}{2} = V_{CM}$

\* Common mode output  $(V_o)_{CM} = \frac{V_{o1} + V_{o2}}{2} = -\frac{2g_m R_D V_{CM}}{2} = -g_m R_D V_{CM}$


\* Common mode gain  $(A_v)_{CM} = \frac{(V_o)_{CM}}{(V_i)_{CM}} = -g_m R_D$

How To FIND common mode gain :-

→ Apply  $V_{i1} = V_{i2} = V_{CM}$

Find  $V_{o1}$  and  $V_{o2}$  and take average  $\rightarrow (V_o)_{CM}$
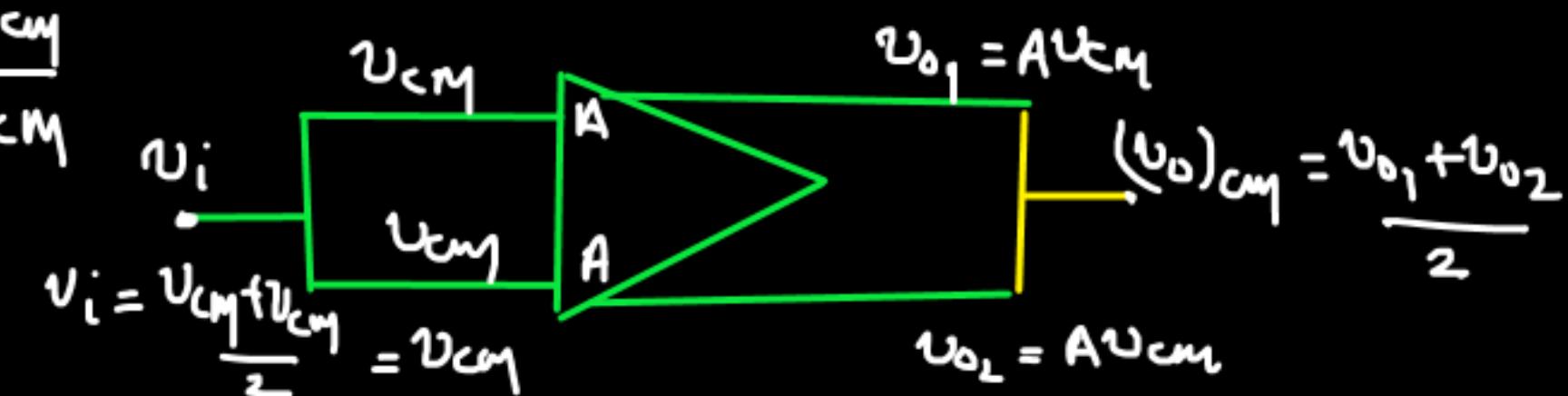
$$\text{gain} = \frac{(V_o)_{CM}}{V_{CM}}$$




HOW TO FIND [Common-Mode Differential gain] :-

$$[(A)_{CM-DM}]$$

Apply  $V_{i_1} = V_{i_2} = V_{CM}$

Find  $V_{o_1}$  &  $V_{o_2}$  and  $(V_o)_{CM-DM} = V_{o_2} - V_{o_1}$  or  $V_{o_1} - V_{o_2}$
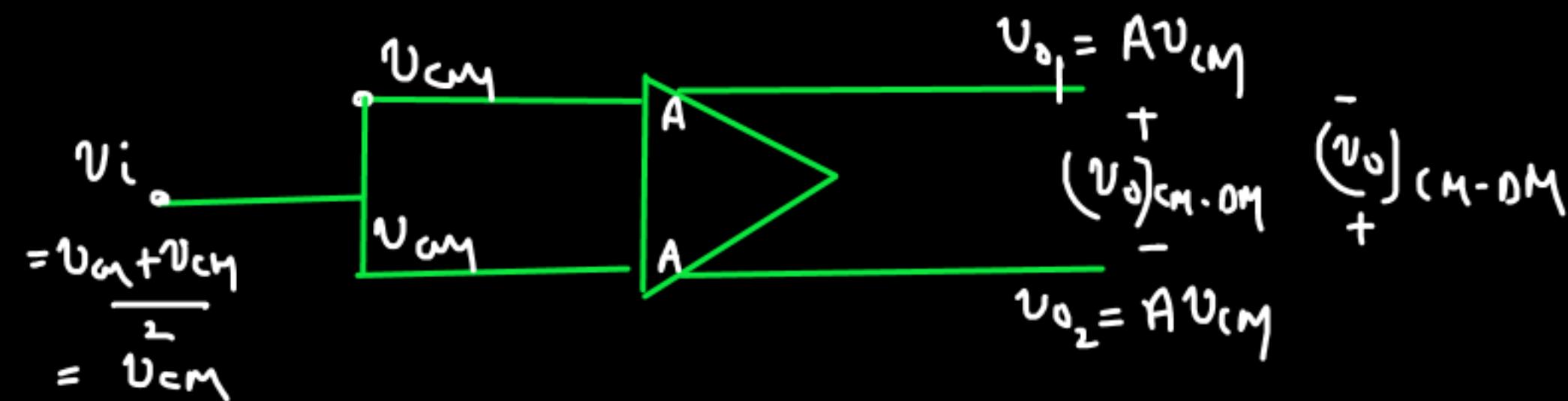
$$(A)_{CM-DM} = \frac{(V_o)_{CM-DM}}{V_{CM}}$$



## Common Mode Rejection Ratio:-

(CMRR)

Shows the ability of rejecting  
common mode input.

\*\*

$$CMRR = \left| \frac{A_{\text{d}}}{A_{\text{CM-DM}}} \right| = \left| \frac{\text{Differential gain}}{\text{Common-Mode differential gain}} \right|$$


MORE CMRR  $\Rightarrow$  Less sensitive to noise

CMRR  $\rightarrow \infty$   $\Rightarrow A_{\text{CM-DM}} = 0 \Rightarrow$  No noise in the o/p


Q. for the given config (a) and (b). Find

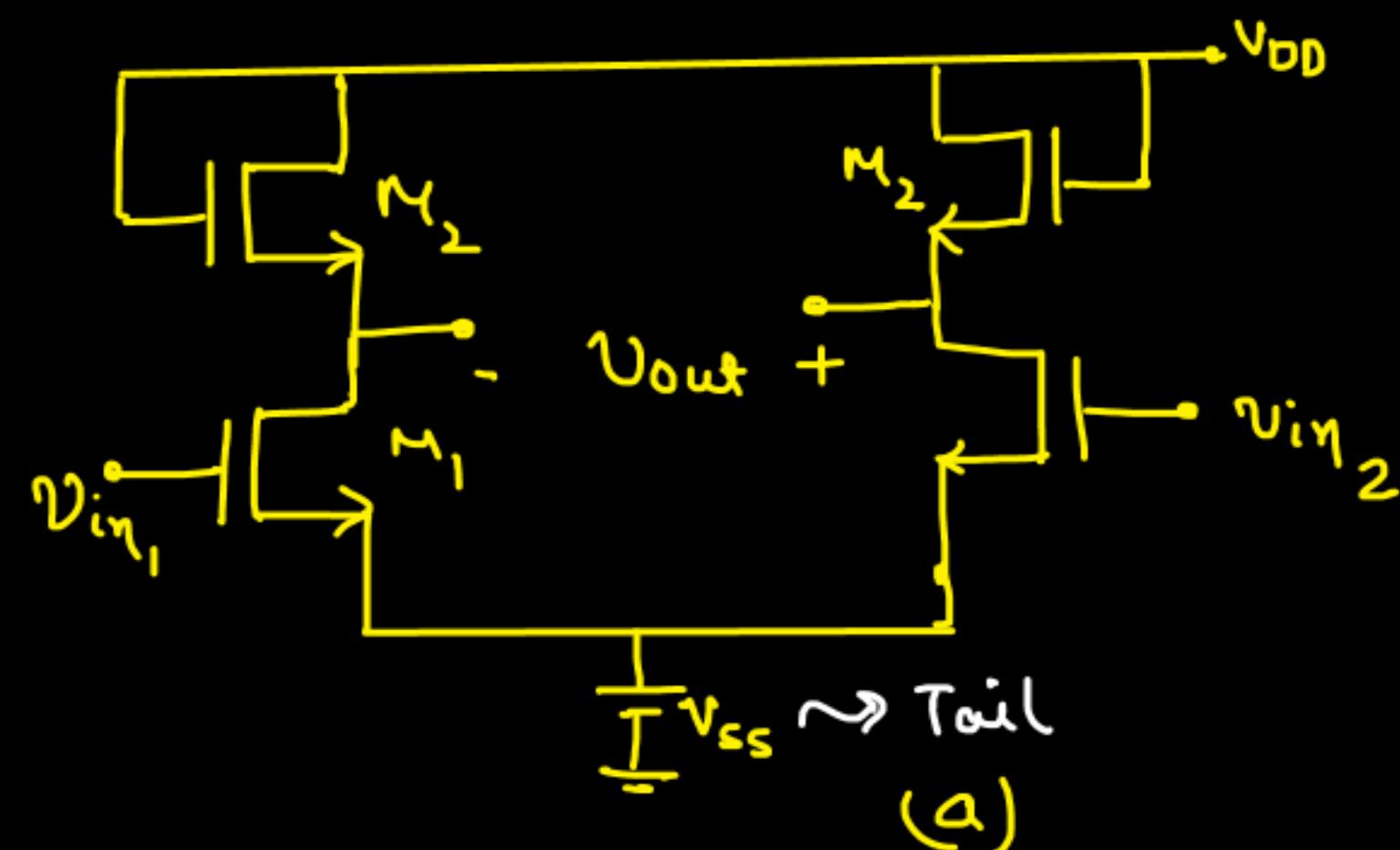- (i) Differential Gain
- (ii) Common-Mode Gain
- (iii) Common-Mode Differential Gain
- (iv) CMRR

N.B. -  $\lambda \neq 0$  for  $M_2$   
 $\lambda = 0$  for  $M_1$




$$v_{in} = v_{in1} - v_{in2}$$

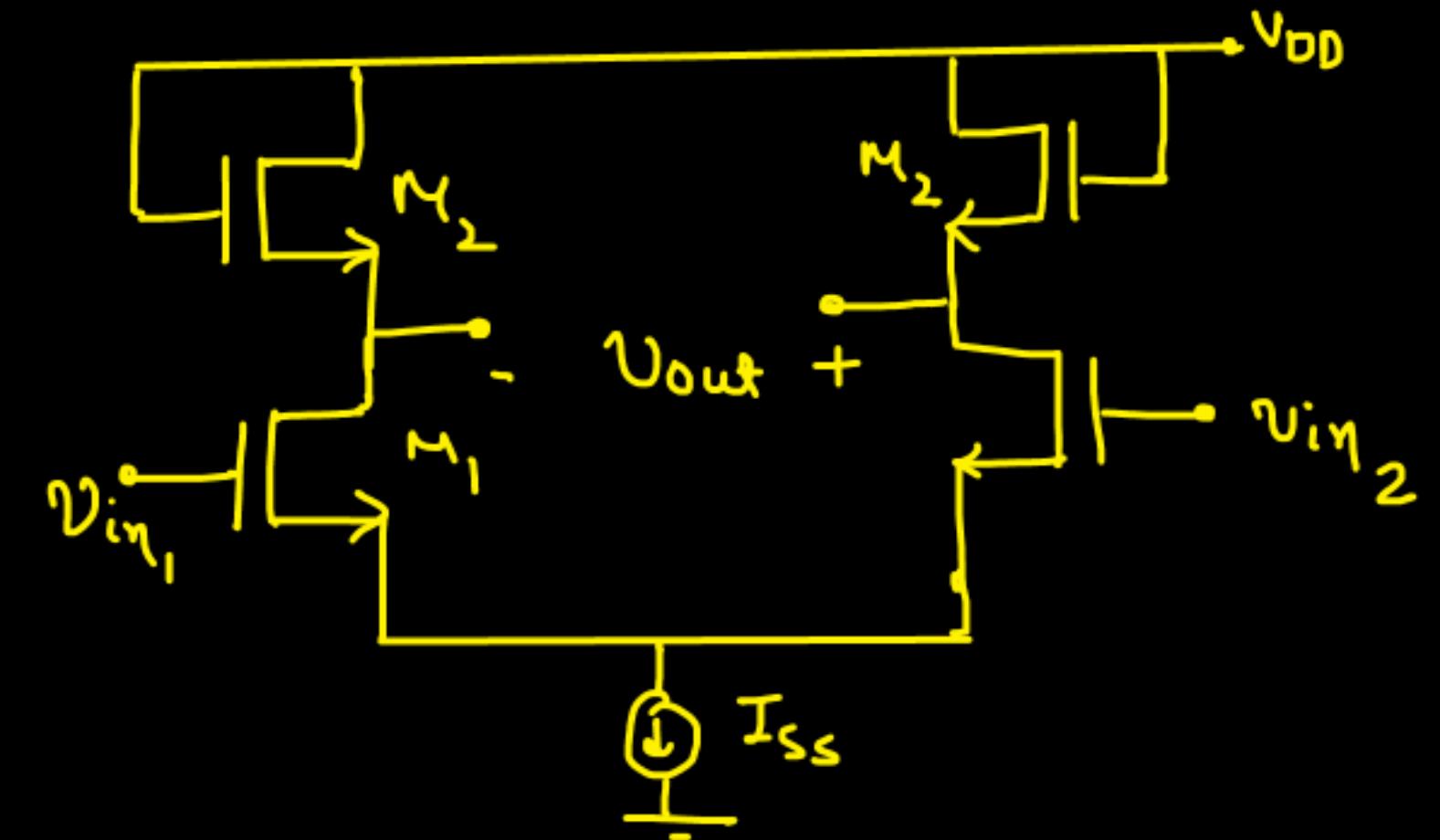


(b)

$$v_{in} = v_{in_1} - v_{in_2}$$

→

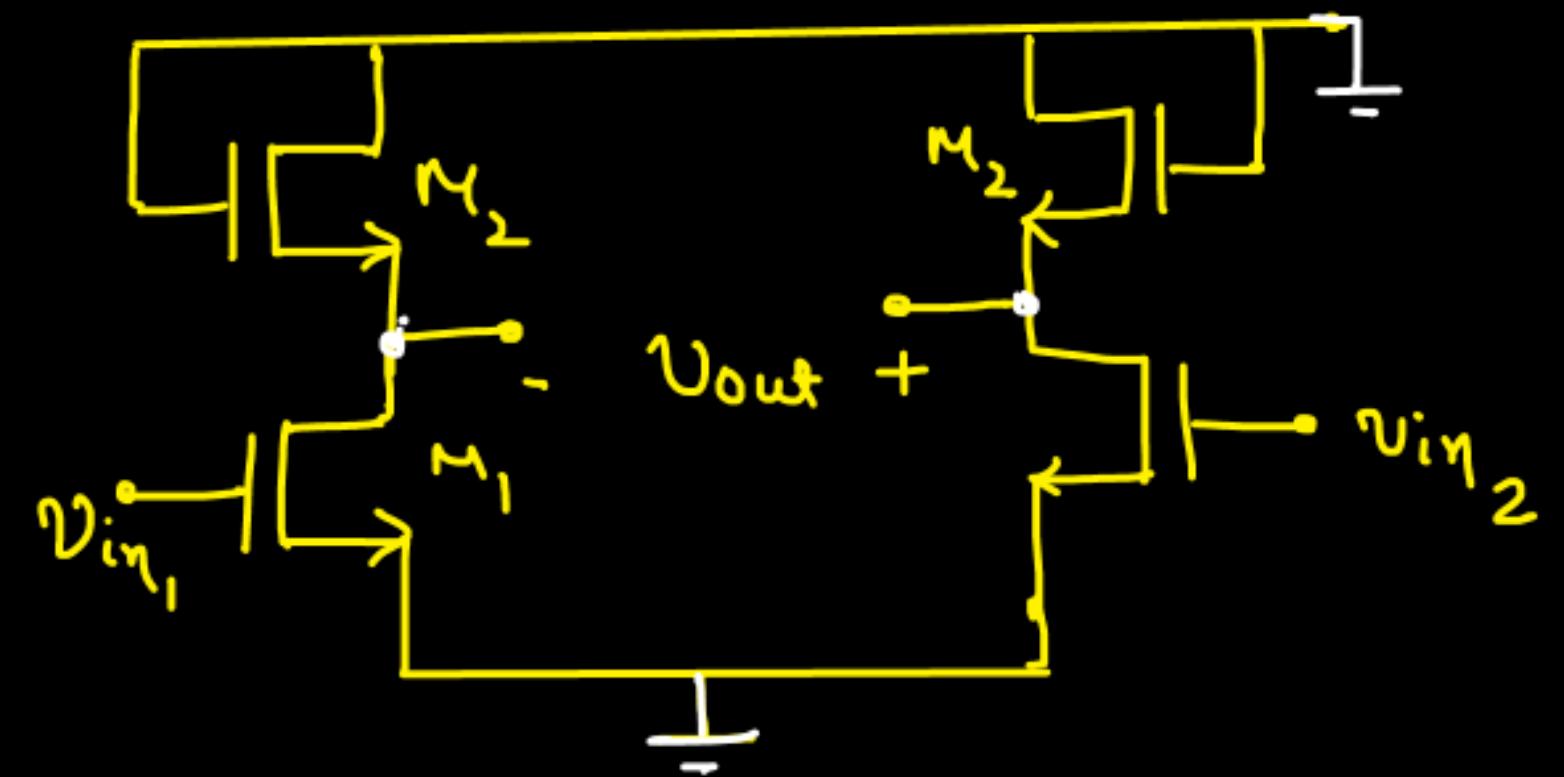


(a)

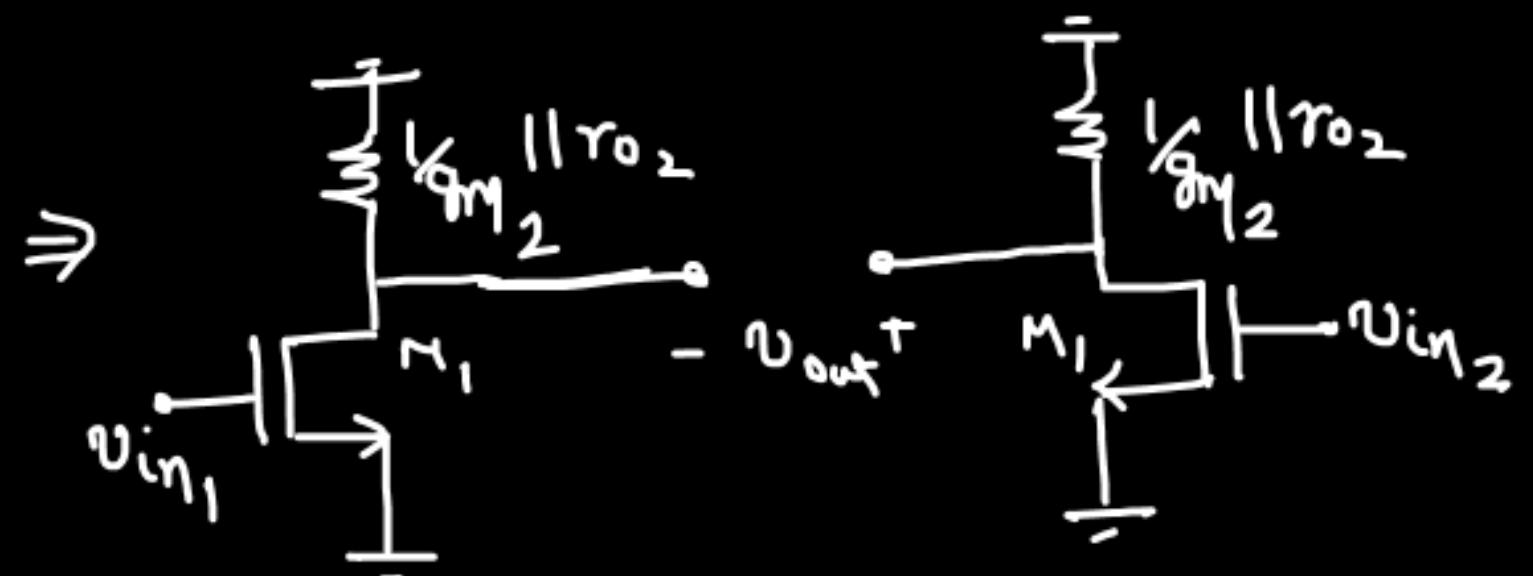

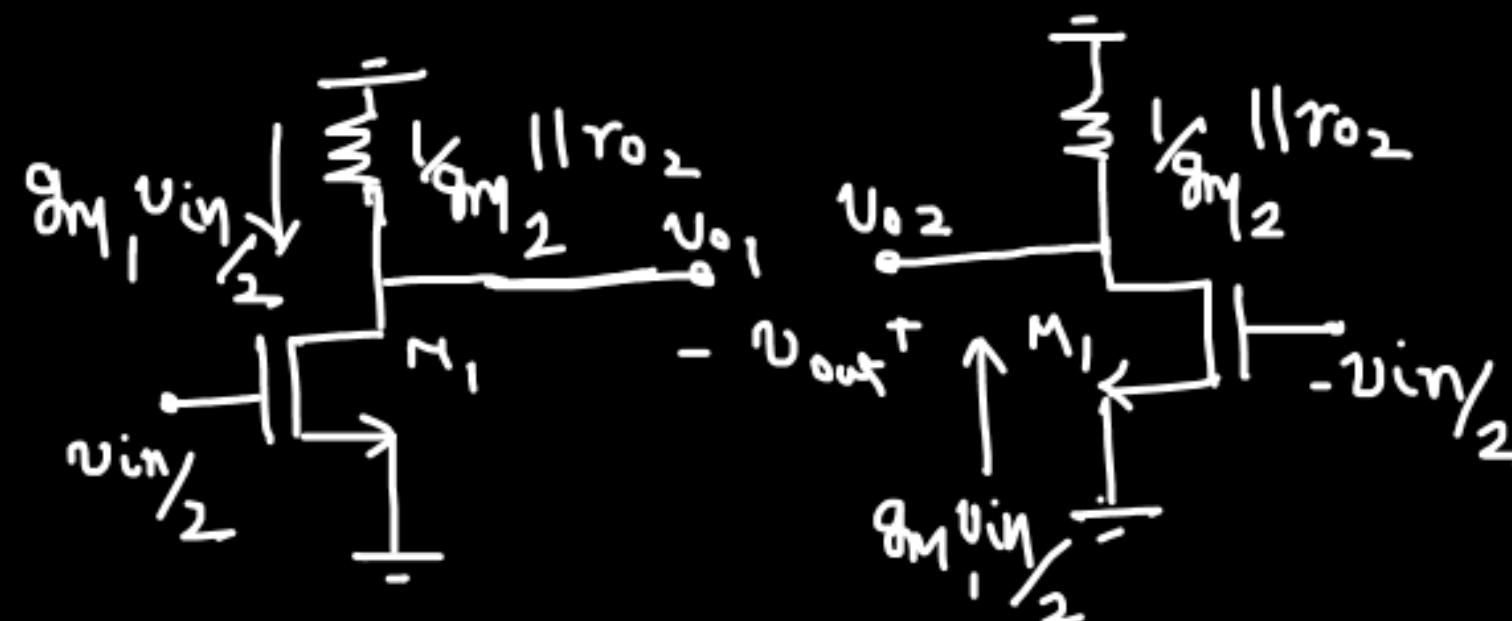(I) Differential gain:-

$$U_{i_1} = \frac{U_{in}}{2}, \quad U_{i_2} = -\frac{U_{in}}{2} \quad [U_{in_1} - U_{in_2} = U_{in}]$$



$$U_{o_1} = -g_{M_1} \left[ \frac{1}{g_{M_2}} || r_{o_2} \right] \frac{U_{in}}{2}$$

$$U_{o_2} = g_{M_1} \left[ \frac{1}{g_{M_2}} || r_{o_2} \right] \frac{U_{in}}{2}$$


$$\Rightarrow (U_o)_d = g_{M_1} \left[ \frac{1}{g_{M_2}} || r_{o_2} \right] U_{in}$$

$$\Rightarrow (U_i)_d = \frac{U_{in}}{2} - \left( -\frac{U_{in}}{2} \right) = U_{in}$$

$$(\Delta V)_d = g_{M_1} \left[ \frac{1}{g_{M_2}} || r_{o_2} \right] U_{in}$$

(II) Common - Mode gain :-

$$V_{i_1} = V_{i_2} = V_{CM}$$

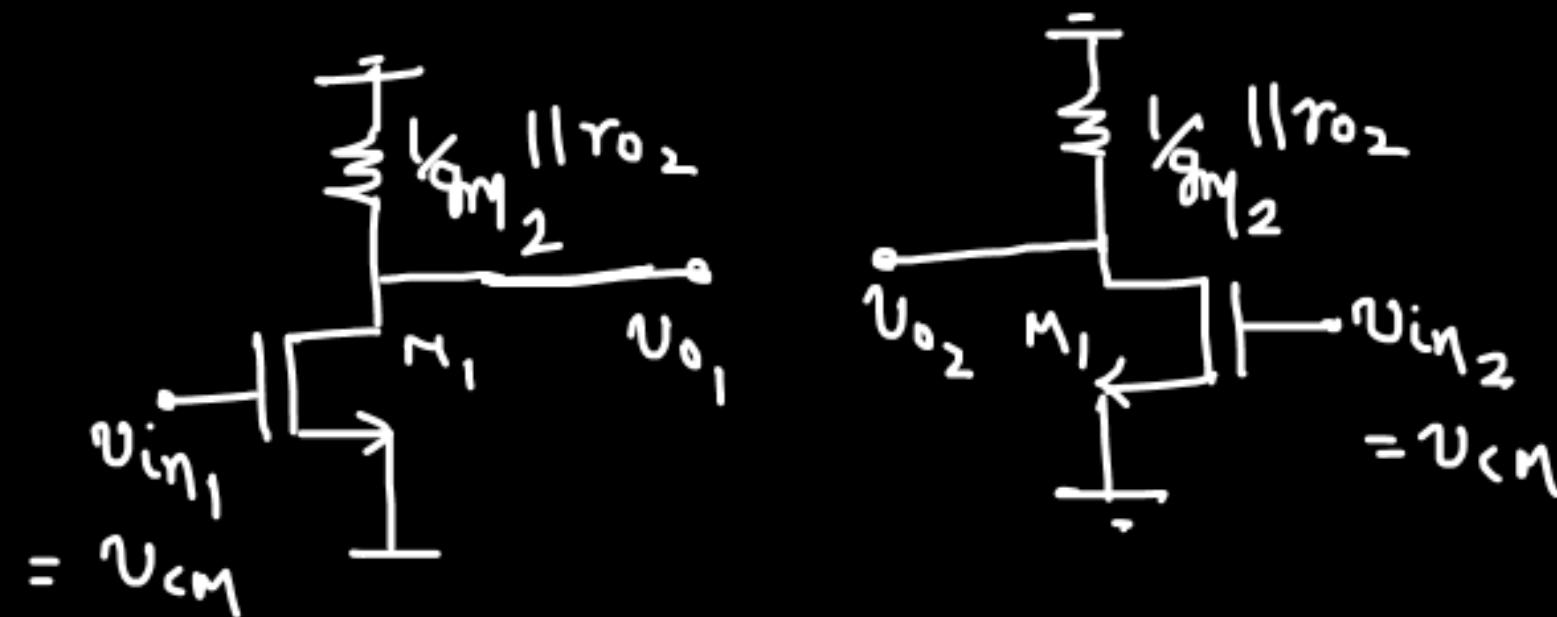

$$V_{o_1} = -g_{m_1} \left[ \frac{1}{g_{m_2}} || r_{o_2} \right] V_{CM}$$

$$(V_o)_{CM} = \frac{V_{o_1} + V_{o_2}}{2}$$

$$V_{o_2} = -g_{m_1} \left[ \frac{1}{g_{m_2}} || r_{o_2} \right] V_{CM}$$

$$(V_o)_{CM} = -g_{m_1} \left[ \frac{1}{g_{m_2}} || r_{o_2} \right] V_{CM}$$

$$(\alpha_v)_{CM} = -g_{m_1} \left[ \frac{1}{g_{m_2}} || r_{o_2} \right]$$

$$(V_i)_{CM} = \frac{V_{CM} + V_{CM}}{2} = V_{CM}$$

Common Mode Differential gain:-

$$V_{i_1} = V_{i_2} = V_{CM}$$

$$V_{o_1} = -g_m \left[ \frac{1}{g_m} || r_o \right] V_{CM}$$

$$V_{o_2} = -g_m \left[ \frac{1}{g_m} || r_o \right] V_{CM}$$

$$(V_o)_{CM-DM} = V_{o_2} - V_{o_1} = 0$$


$$(V_i)_{CM-DM} = V_{CM} + \frac{V_{CM}}{2} = V_{CM}$$

$$\boxed{(A_v)_{CM-DM} = \frac{0}{V_{CM}} = 0}$$

CMRR :-

$$\begin{aligned} CMRR &= \left| \frac{(A)_d}{(A)_{CM-DM}} \right| \\ &= \left| \frac{(A)_d}{0} \right| \end{aligned}$$



$$\boxed{CMRR = \infty}$$

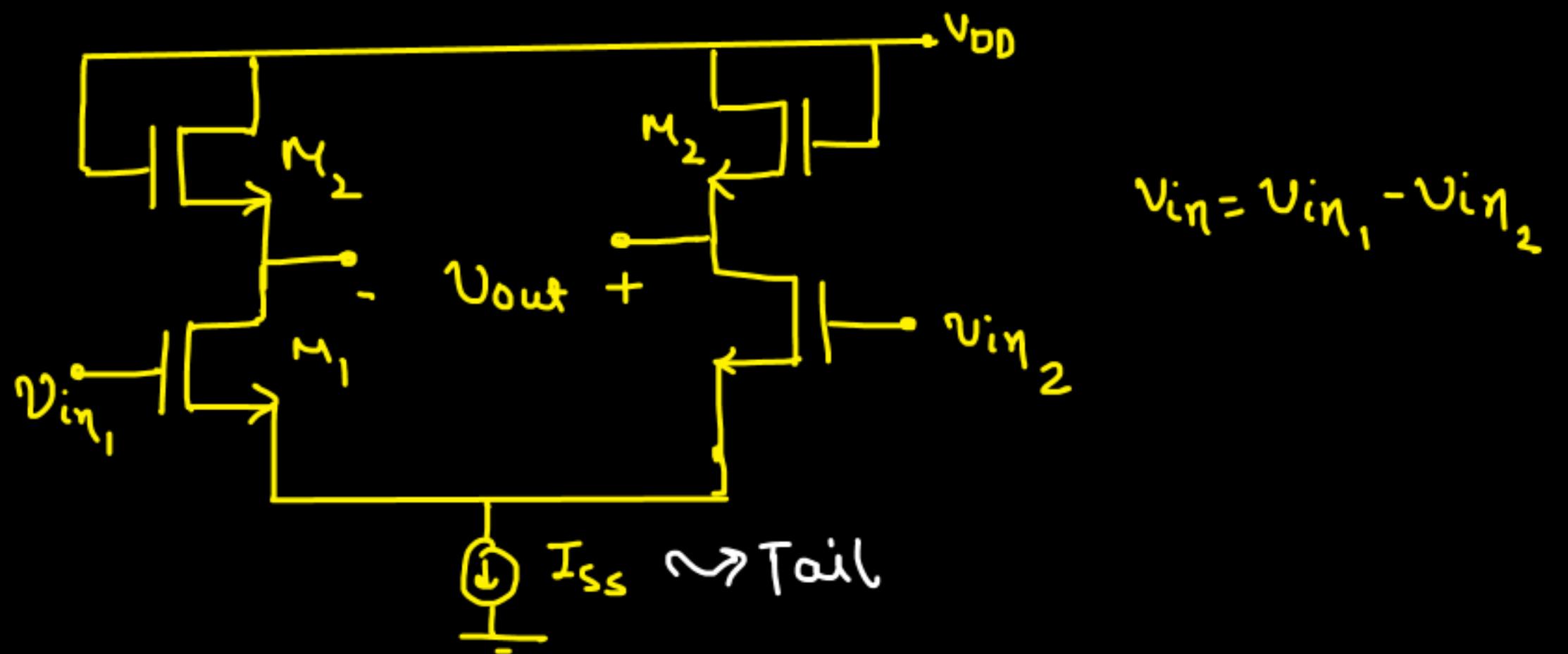

$$V_{in} = V_{in1} - V_{in2}$$


(b)

## (I) Differential gain :-

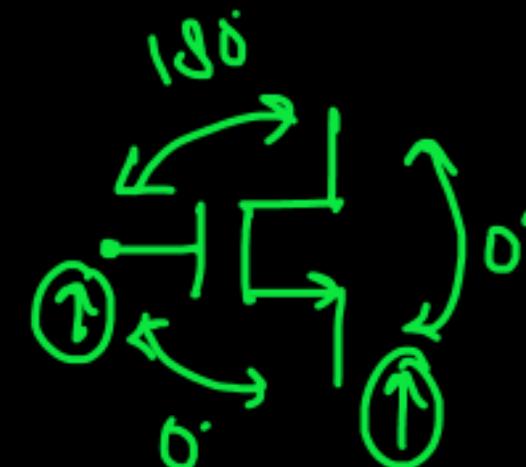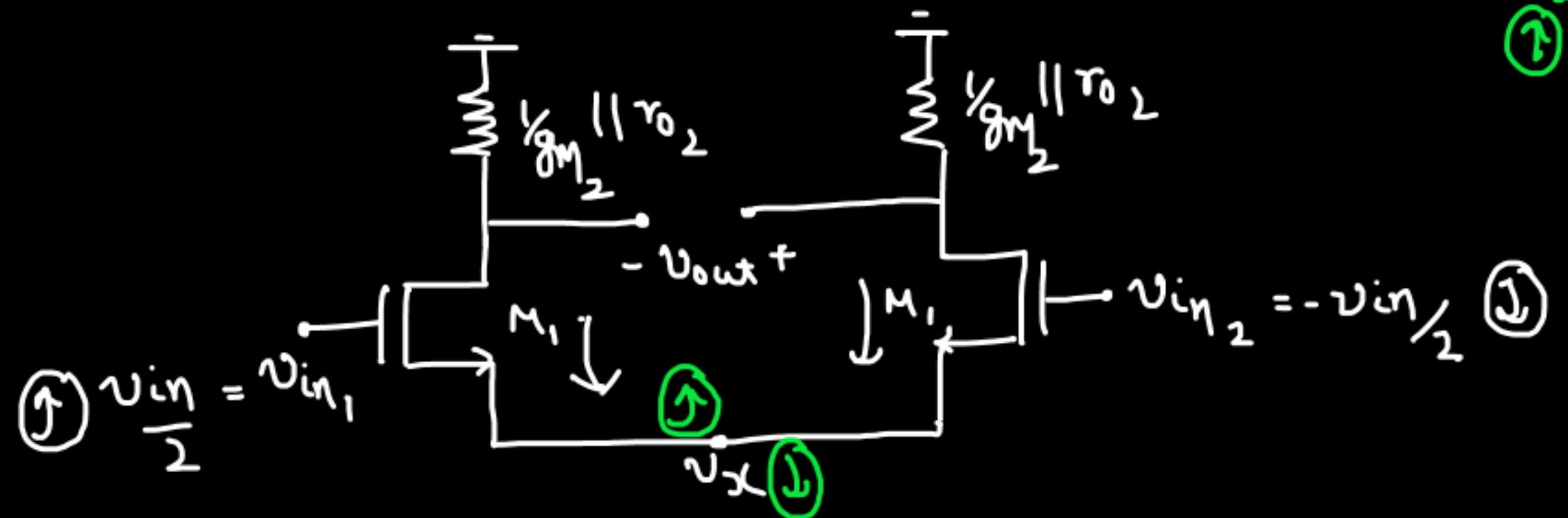

$$g_m(V_{in} - V_x) = - g_m(-\frac{V_{in}}{2} - V_x)$$

$$V_x = 0$$

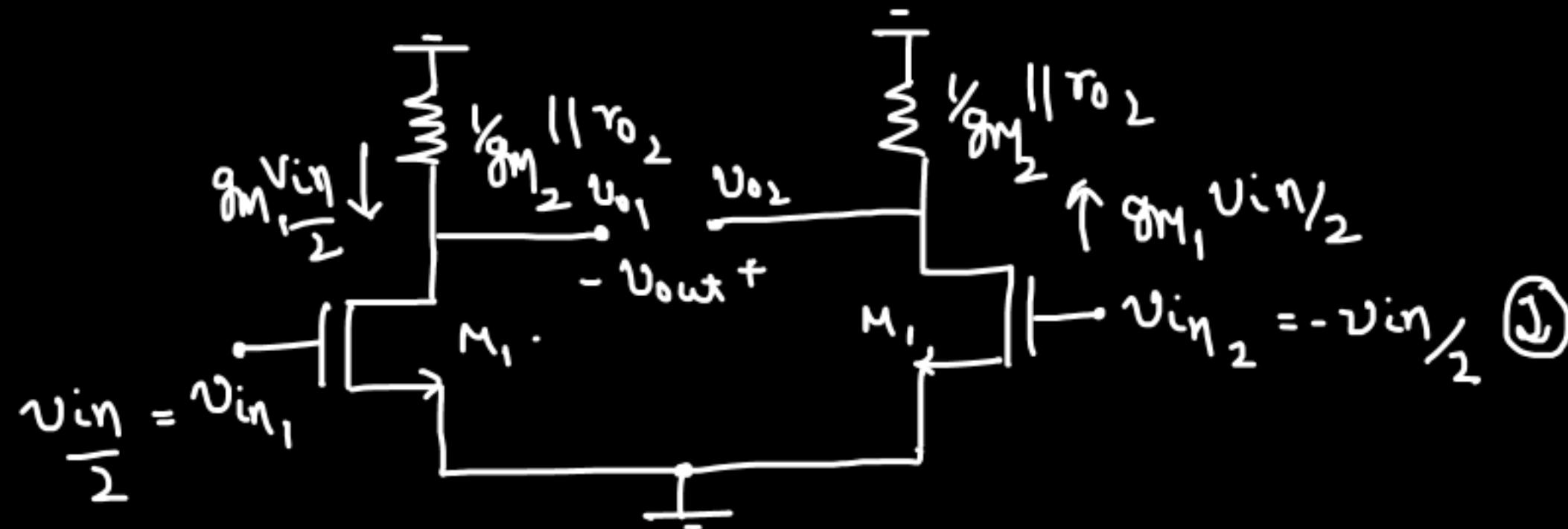

$$v_{o_2} = g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_{o_2} \right] v_{in} \frac{1}{2}$$


$$v_{o_1} = -g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_{o_2} \right] v_{in} \frac{1}{2}$$

$$A_V = g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_{o_2} \right] v$$

$$(v_{out})_d = g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_{o_2} \right] v_{in}$$

$$(v_{in})_d = v_{in}$$

(II) Common Mode Gain:-

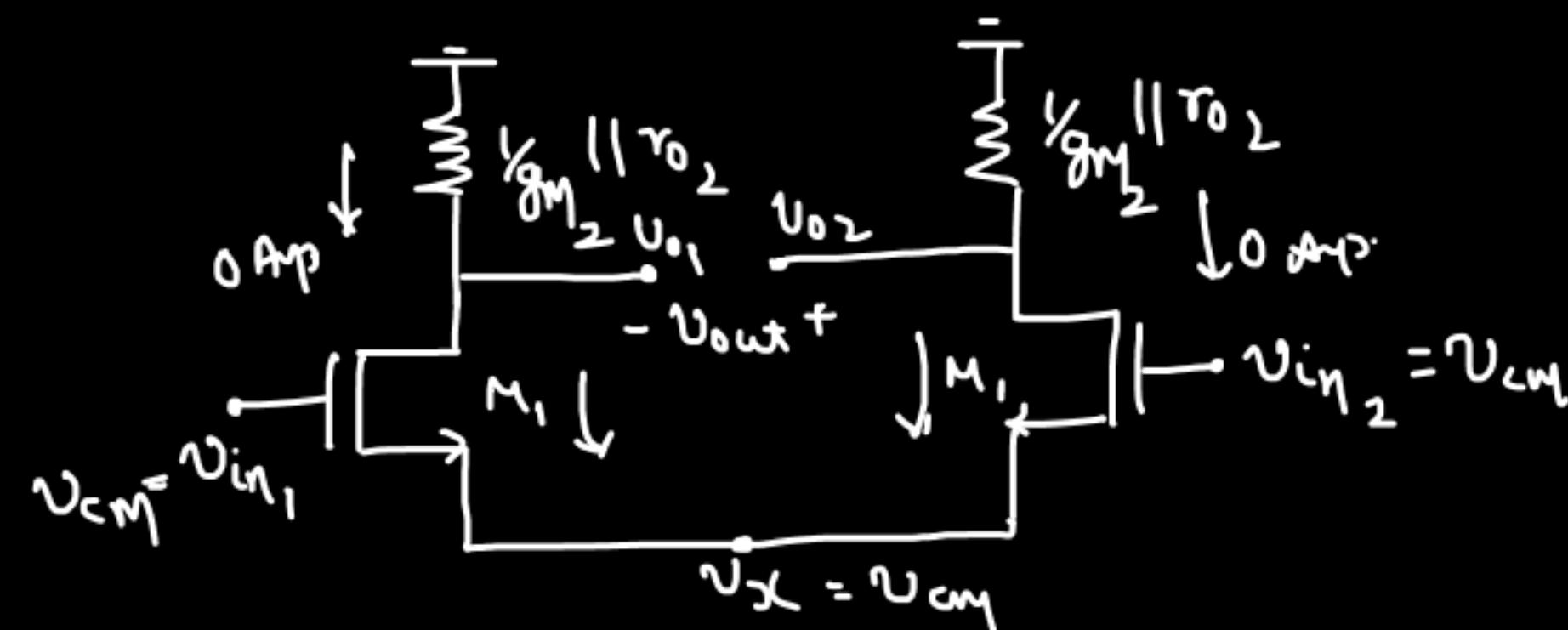

$$g_m_1 (V_{cm} - V_x) = - g_m_1 (V_{cm} - V_n)$$

$$2g_m_1 (V_{cm} - V_n) = 0$$

$$V_x = V_{cm}$$

$$V_{o_1} = V_{o_2} = 0$$

$$(V_o)_{cm} = \frac{V_{o_1} + V_{o_2}}{2} = 0$$

$$(\Delta v)_{cm} = \frac{0}{V_{cm}} = 0$$

N.B. Common Mode gain shows the amount of noise present in the ckt.

It's good to have as low as common mode gain.

### (III) Common - Mode Differential gain :-

$$V_{o_1} = 0$$

$$V_{o_2} = 0$$

$$(V_o)_{CM-DM} = V_{o_2} - V_{o_1} = 0$$

$$\boxed{(A)_{CM-DM} = 0}$$

N.B. - When there is no Mismatch in Transistors

Voltage source as tail

$$\textcircled{1} \quad (\Delta V)_d = g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_o \right]$$

$$\textcircled{2} \quad (\Delta V)_{CM} = -g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_o \right]$$

$$\textcircled{3} \quad (\Delta V)_{CM-DM} = 0$$

Current source as tail


$$\textcircled{1} \quad (\Delta V)_d = g_{m_1} \left[ \frac{1}{g_{m_2}} \parallel r_o \right] \rightarrow \underline{\text{Same}}$$

A\*


$$\textcircled{2} \quad (\Delta V)_{CM} = 0 \rightarrow \boxed{\text{Advantage}}$$

$$\textcircled{3} \quad (\Delta V)_{CM-DM} = 0 \rightarrow \boxed{\text{Same}}$$

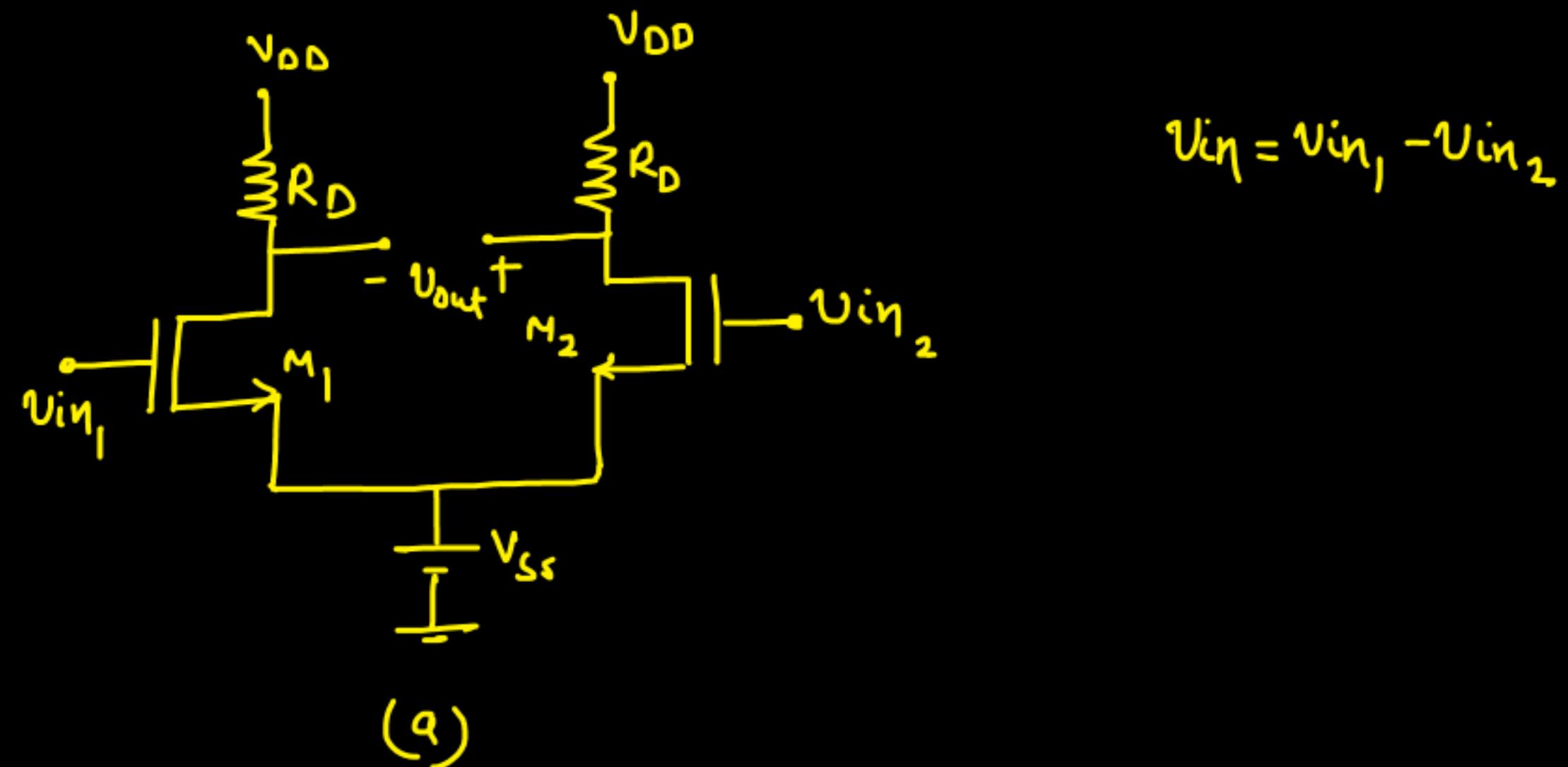⇒ finding the same parameters when there is mismatch:-



(a) Differential gain :-

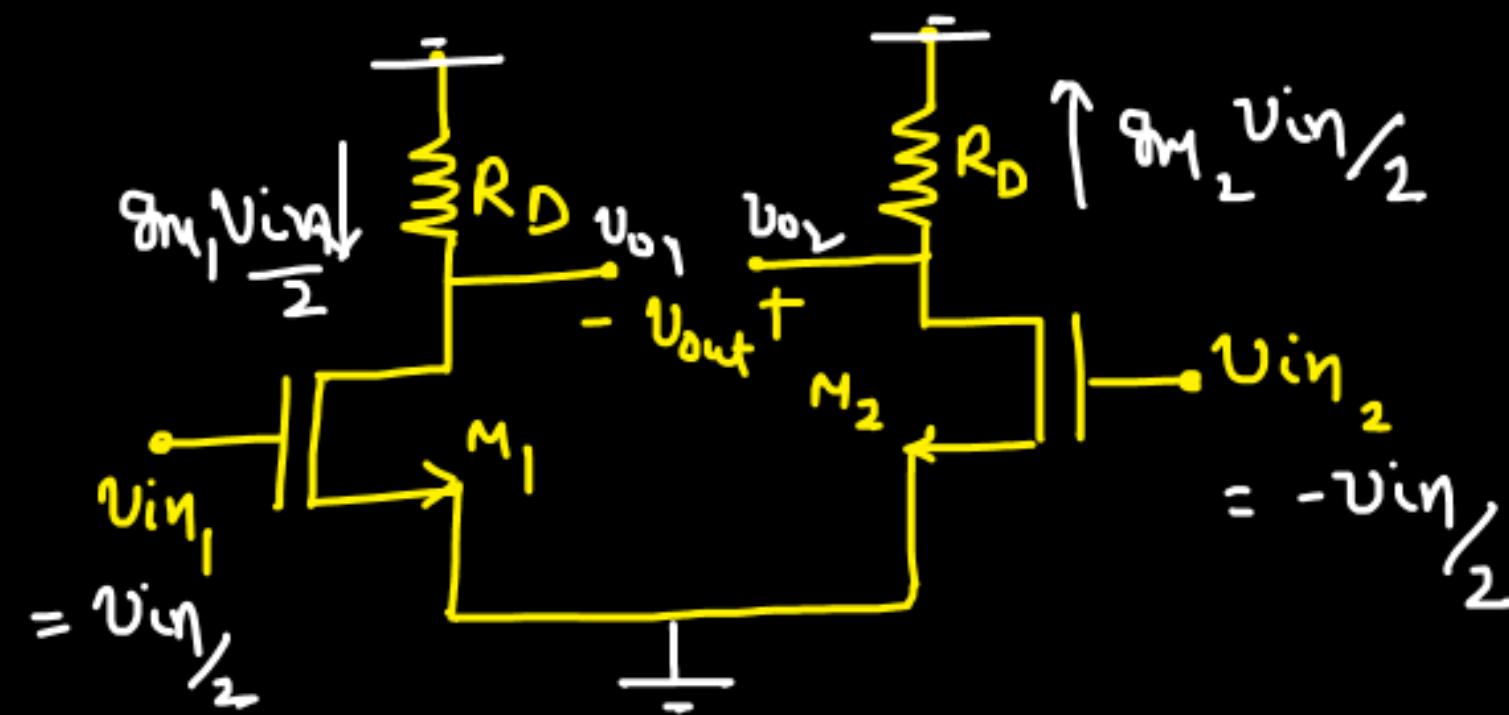

$$V_{02} = g_m R_D \frac{V_{in}}{2}$$

$$V_{01} = -g_m R_D \frac{V_{in}}{2}$$


$$(V_o)_d = V_{02} - V_{01} = (g_m + g_m) R_D \frac{V_{in}}{2}$$

$$(V_i)_d = V_{in}$$

A

$$(A_v)_d = \left( \frac{g_m_1 + g_m_2}{2} \right) R_D$$

(b) Common - Mode Gain :-

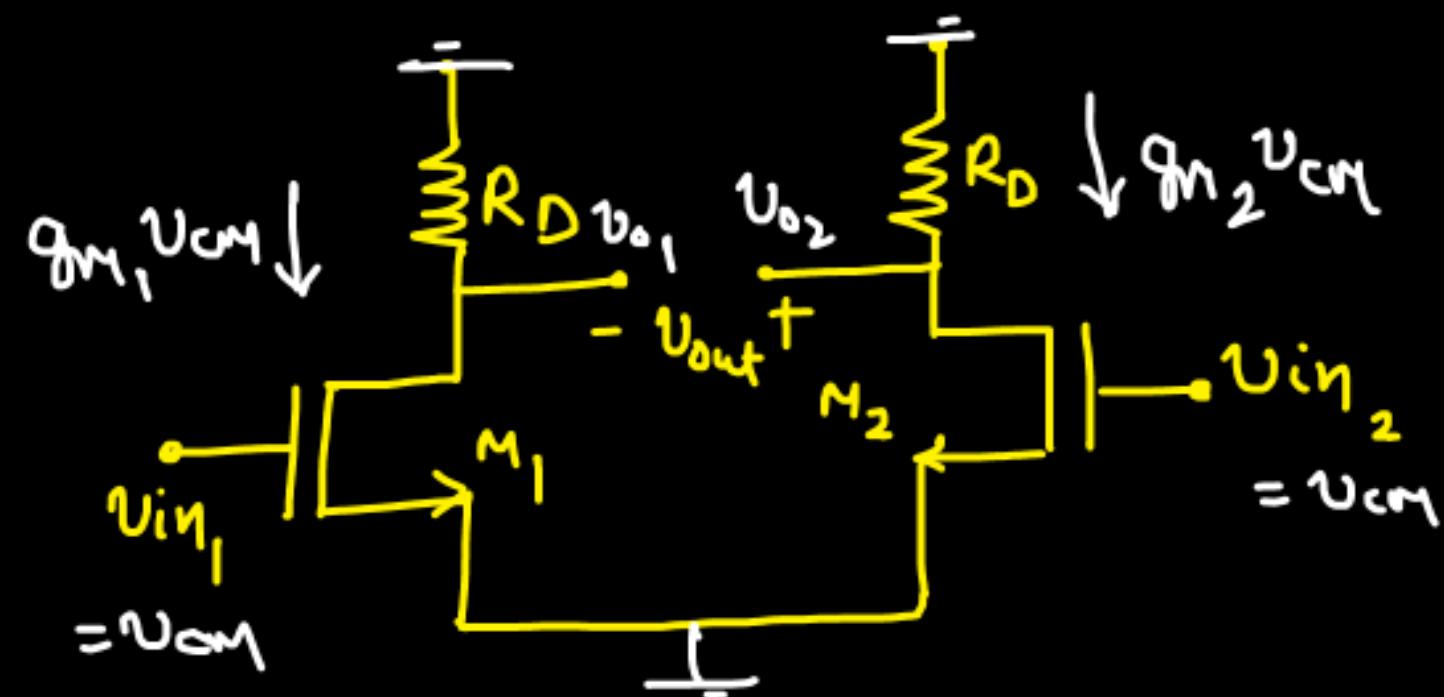

$$v_{o2} = -q_m v_{cm} R_D$$

$$v_{o1} = -q_m v_{cm} R_D$$


$$(v_o)_{cm} = -\left(\frac{q_m_1 + q_m_2}{2}\right) R_D v_{cm}$$

$$(v_i)_{cm} = v_{cm}$$

4

$$(v_o)_{cm} = -\left(\frac{q_m_1 + q_m_2}{2}\right) R_D$$

### (c) Common Mode Differential Gain:-

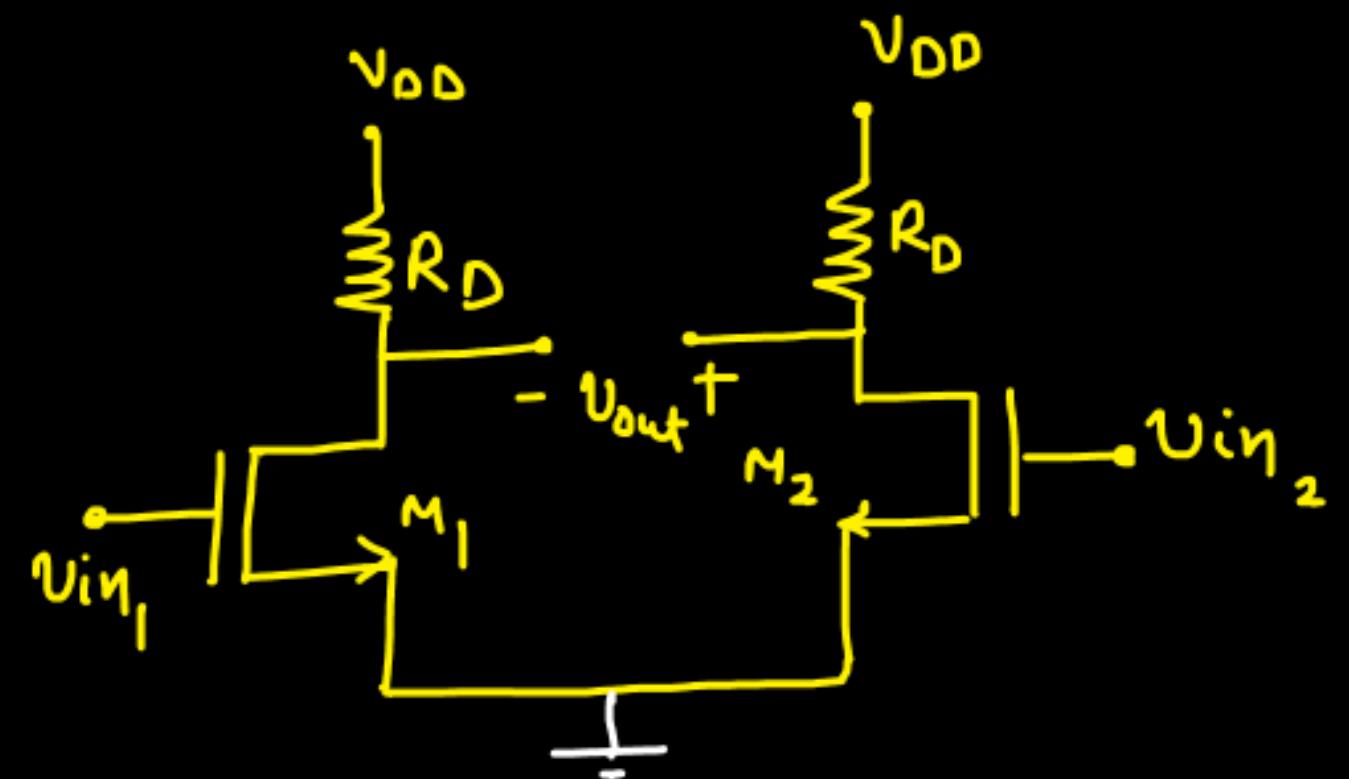


$$(v_o)_{CM-DM} = (g_m - g_m) R_D v_{CM}$$


$$(v_i)_{CM} = v_{CM}$$

↗

$$(\Delta v)_{CM-DM} = (g_m - g_m) R_D$$

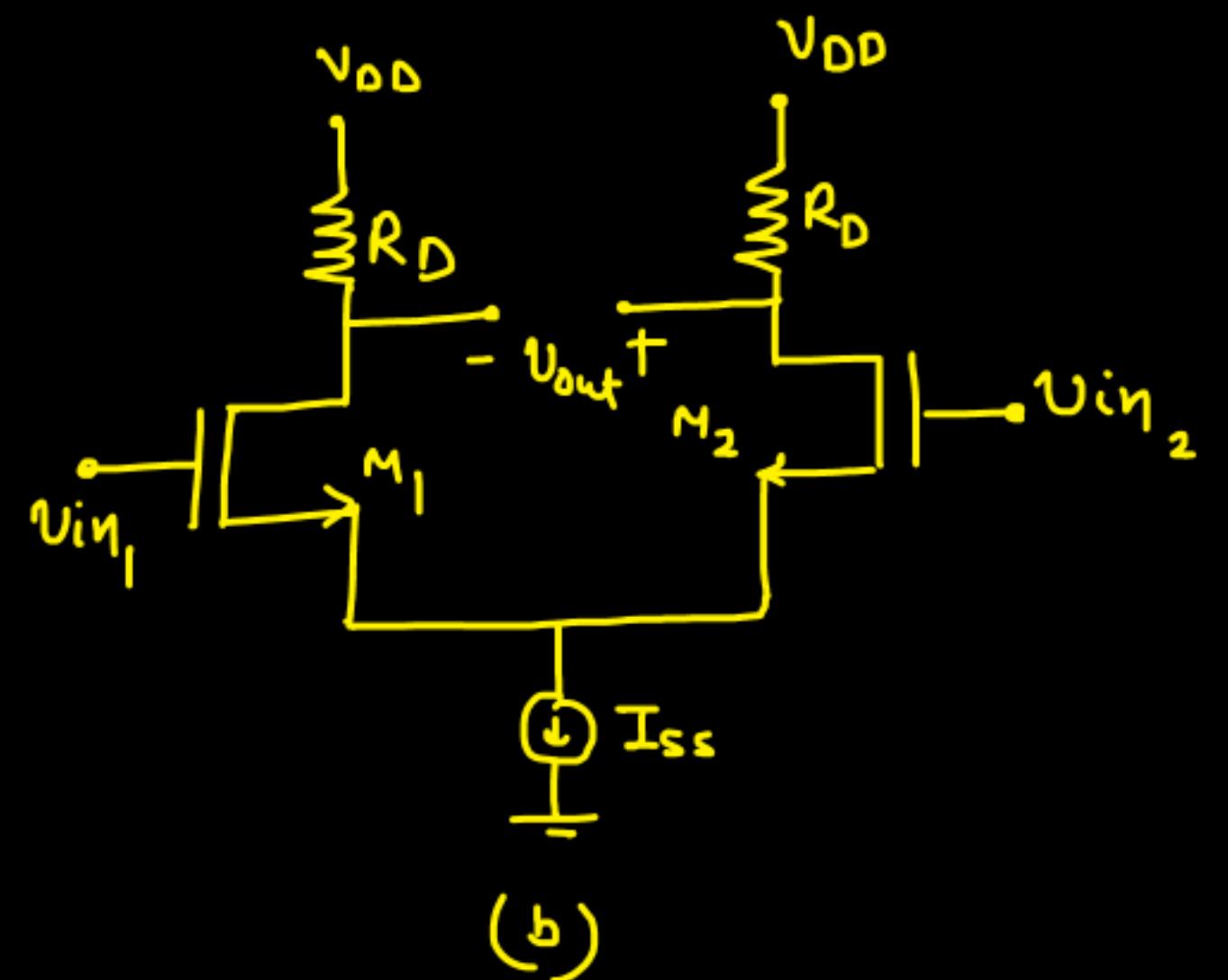

(q) Differential Gain :-

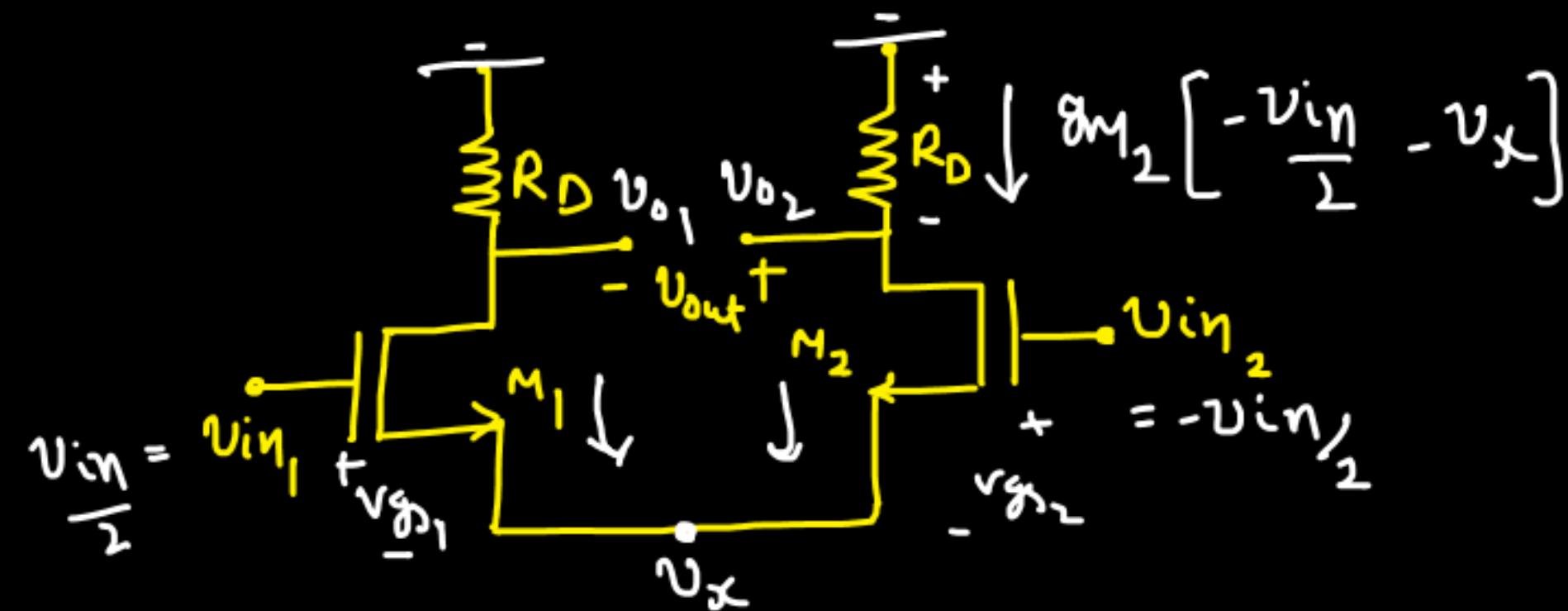

$$g_m1 \left[ \frac{u_{in}}{2} - v_x \right] = -g_m2 \left[ -\frac{u_{in}}{2} - v_x \right]$$

$$g_m1 \frac{u_{in}}{2} - g_m1 v_x = g_m2 \frac{u_{in}}{2} + g_m2 v_x$$

$$\frac{(g_m1 - g_m2)}{g_m2 + g_m1} \frac{u_{in}}{2} = v_x \quad \text{--- (1)}$$

$$v_{o2} = \frac{g_m}{2} R_D \left[ \frac{v_{in}}{2} + v_x \right]$$

$$v_{o1} = -\frac{g_m}{2} R_D \left[ \frac{v_{in}}{2} - v_x \right]$$

$$(v_o)_d = \frac{g_m}{2} R_D \left[ \frac{v_{in}}{2} + v_x \right] + \frac{g_m}{2} R_D \left[ \frac{v_{in}}{2} - v_x \right]$$

$$(v_o)_d = \left[ \frac{g_m}{2} + \frac{g_m}{2} \right] R_D v_{in} + \left[ \frac{g_m}{2} - \frac{g_m}{2} \right] R_D v_x$$

$$= \left[ \frac{g_m}{2} + \frac{g_m}{2} \right] R_D v_{in} + \left[ \frac{g_m}{2} - \frac{g_m}{2} \right] R_D \frac{\left[ \frac{g_m}{2} - \frac{g_m}{2} \right] v_{in}}{\left[ \frac{g_m}{2} + \frac{g_m}{2} \right]} \frac{v_{in}}{2}$$

$$= \frac{\left[ \frac{g_m}{2} + \frac{g_m}{2} \right]^2 R_D - \left[ \frac{g_m}{2} - \frac{g_m}{2} \right]^2 R_D}{g_m} \frac{v_{in}}{2}$$

$$= \frac{[4g_m_1 g_m_2]}{g_m_1 + g_m_2} R_D \frac{V_{in}}{2}$$

$$(V_o)_d = \left[ \frac{2g_m_1 g_m_2}{g_m_1 + g_m_2} \right] R_D V_{in}$$

$$(V_i)_d = V_{in}$$

$$(\Delta V)_d \approx \frac{2g_m_1 g_m_2}{g_m_1 + g_m_2} R_D$$

Current source as a tail :-


$$(\Delta V)_d = \frac{2g_m_1 g_m_2}{g_m_1 + g_m_2} R_D$$

Voltage source as a tail :-

$$(\Delta V)_d = \left( \frac{g_m_1 + g_m_2}{2} \right) R_D \xrightarrow{\text{Advantage}}$$

$$(\Delta V)_d_{V.S.} > (\Delta V)_d_{C.S.} \rightarrow \begin{matrix} \text{In case of} \\ \text{mismatch} \end{matrix}$$

(b) Common mode gain :-

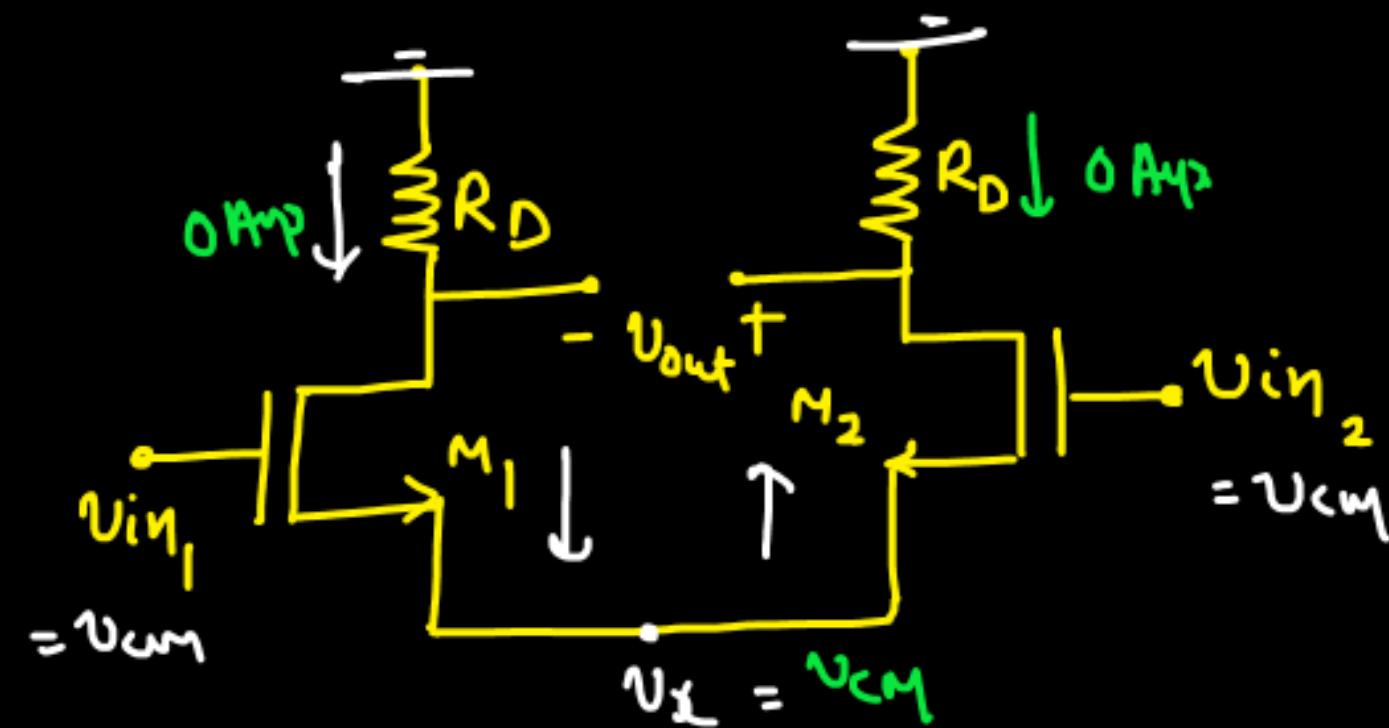

$$g_m_1 (V_{cm} - V_x) = - g_m_2 (V_{cm} - V_x)$$

$$(g_m_1 + g_m_2) V_{cm} = (g_m_2 + g_m_1) V_x$$

\*  $V_x = V_{cm}$  &

$(\partial V)_{cm} = 0$

$$(A_v)_{cm \rightarrow v.s.} = - \left( \frac{g_m_1 + g_m_2}{2} \right) R_D$$

$$(A_v)_{cm \rightarrow c.s.} = 0$$

Advantage =

### (c) Common-Mode Differential Gain :-

$$V_{o_1} = V_{o_2} = 0$$


$$(A_v)_{CM-DM} = 0$$

$$(A_v)_{CM-DM \rightarrow V.S.} = (g_m 1 - g_m 2) R_D$$

$$(A_v)_{CM-DM \rightarrow C.S.} = 0$$


↓  
Advantage

## ★ Some important concepts :-


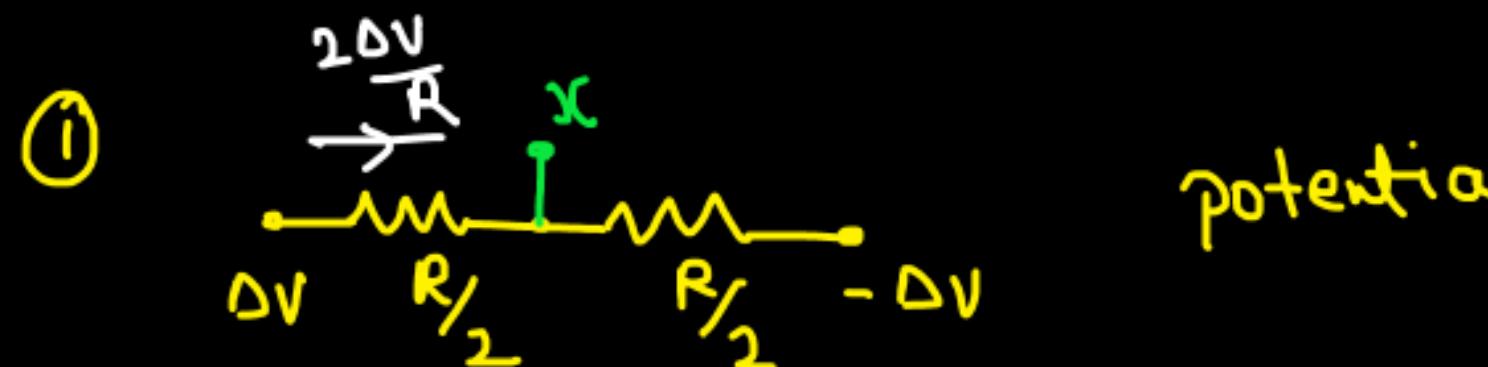


potential @ node x ?

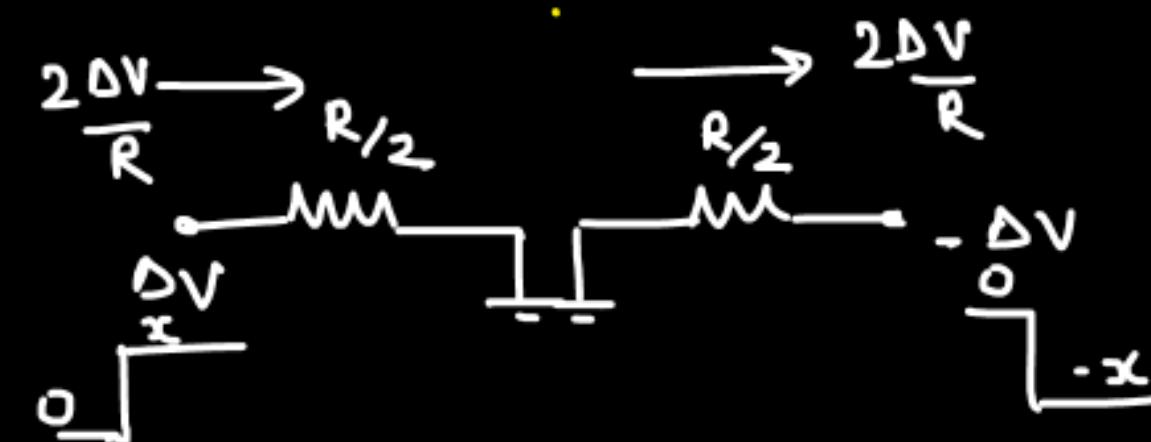
$$\rightarrow v_x = \frac{\Delta V (R/2) + (-\Delta V) (R/2)}{R}$$



$v_x = 0$

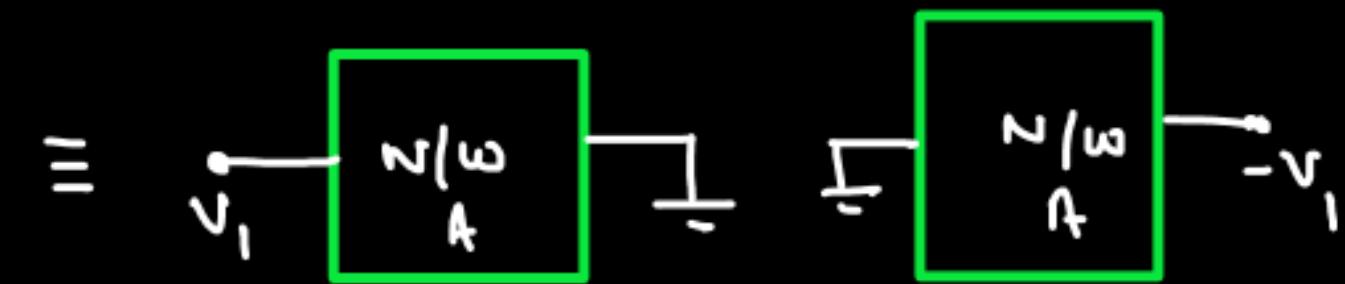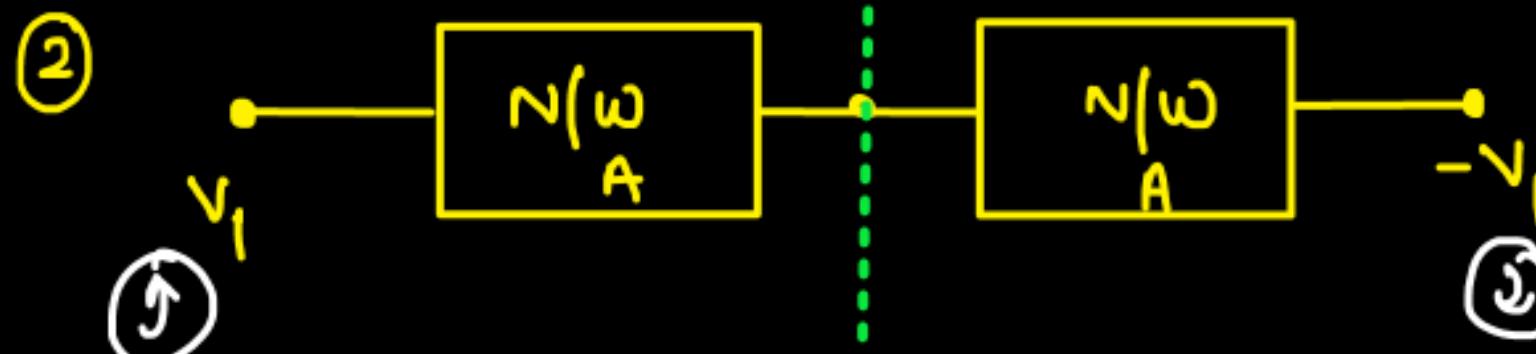


③

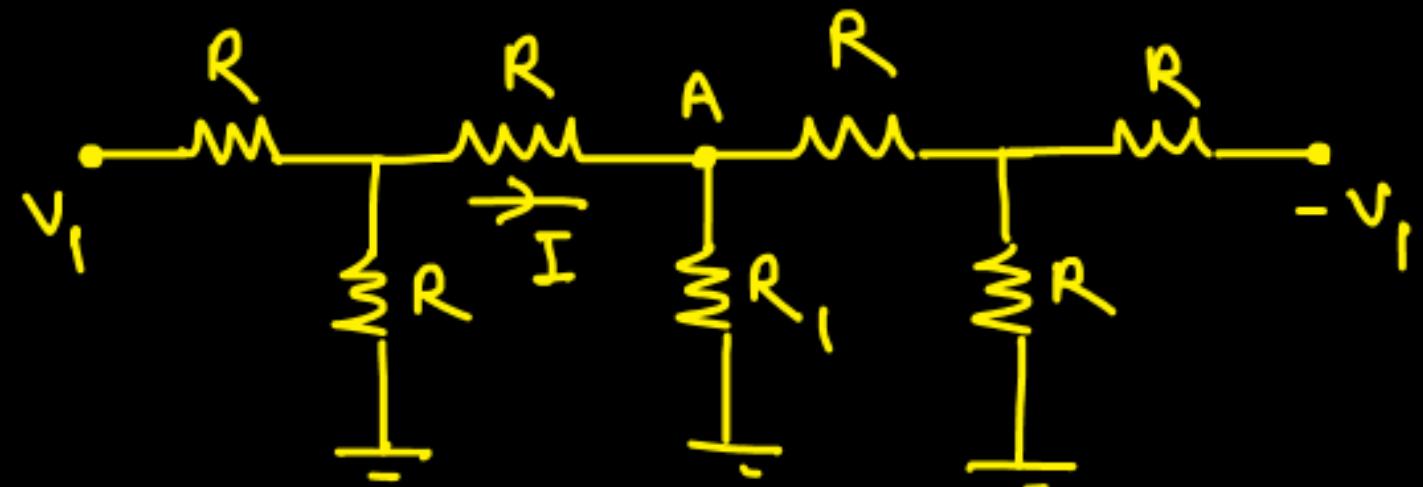


Find the potential @ node A.

Find current  $I$ .

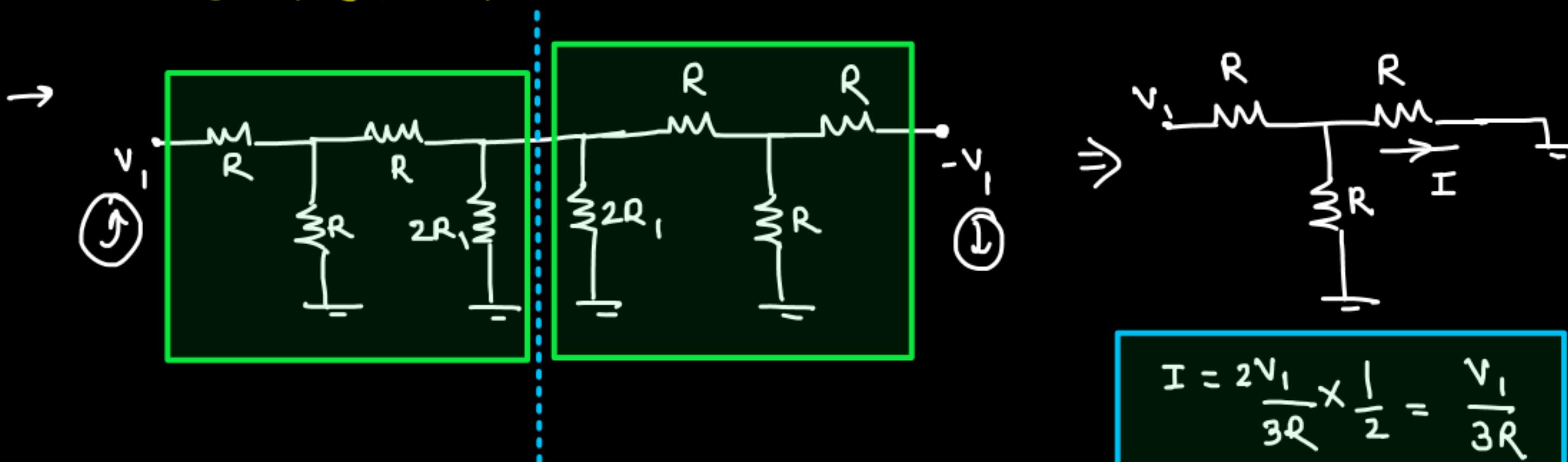


④

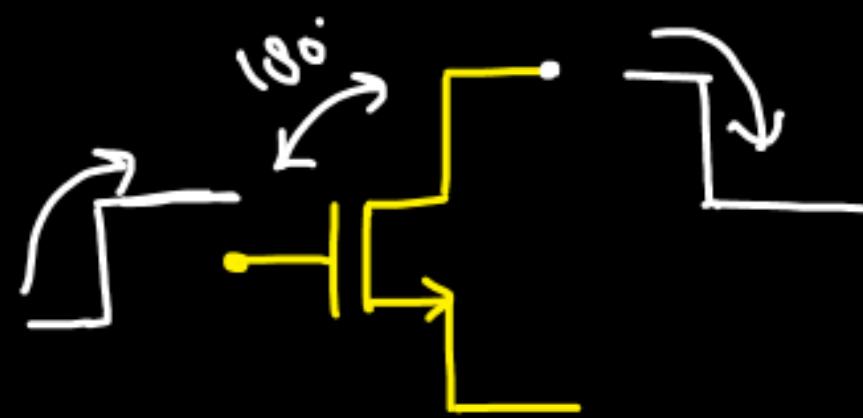


$$A_V = -g_m R_D$$

⑤

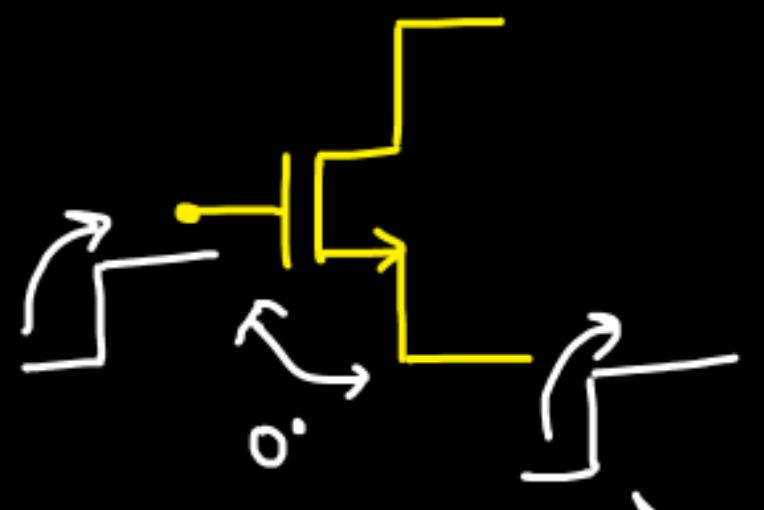

$$A_V = \frac{g_m R_S}{1 + g_m R_S}$$

⑥

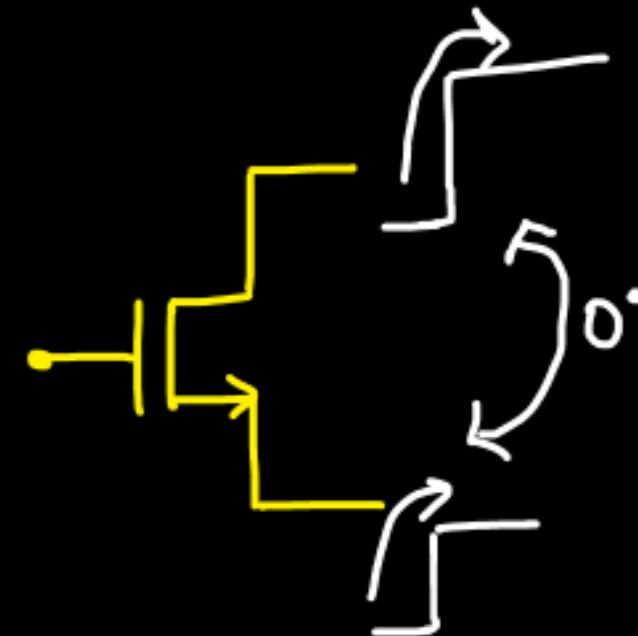


$$A_V = g_m R_D$$

⑦




≡

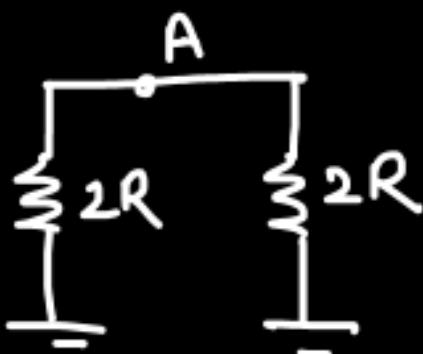


⑧




≡

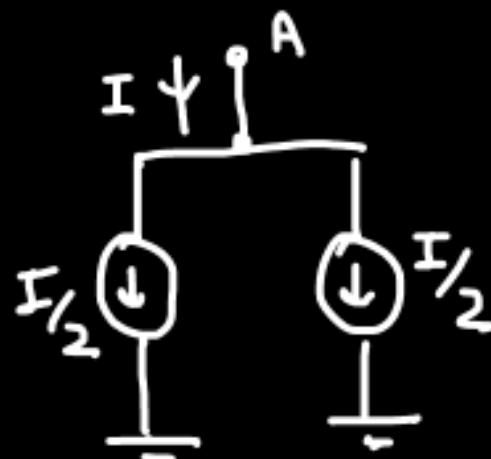


⑨

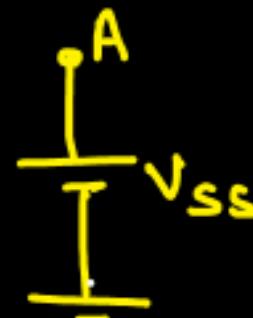


≡

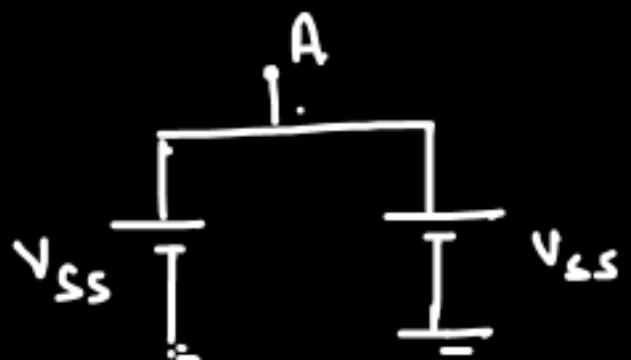


⑩

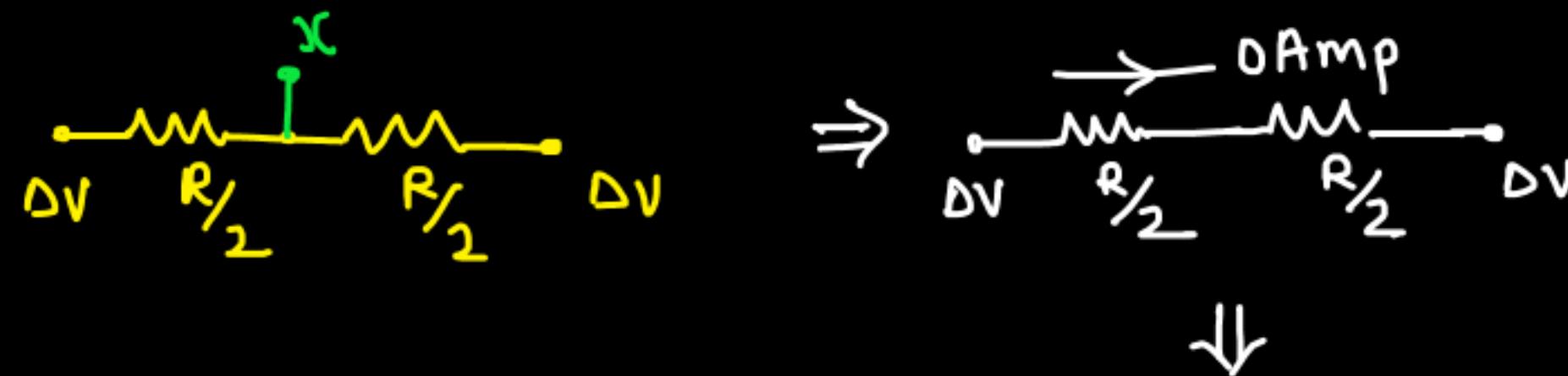

⑪

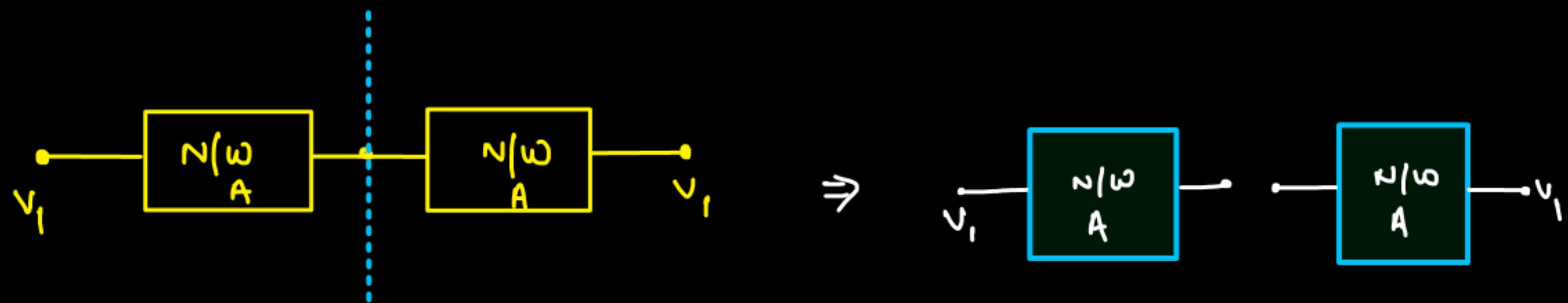


(12)

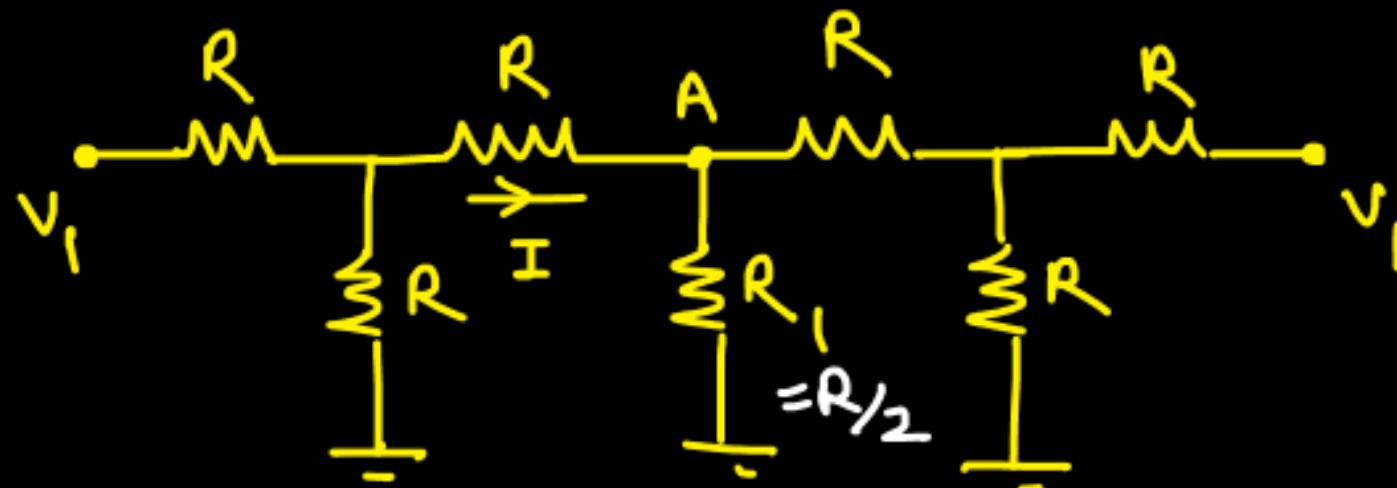

$$R_1 = R/2$$


Find current  $I = ?$

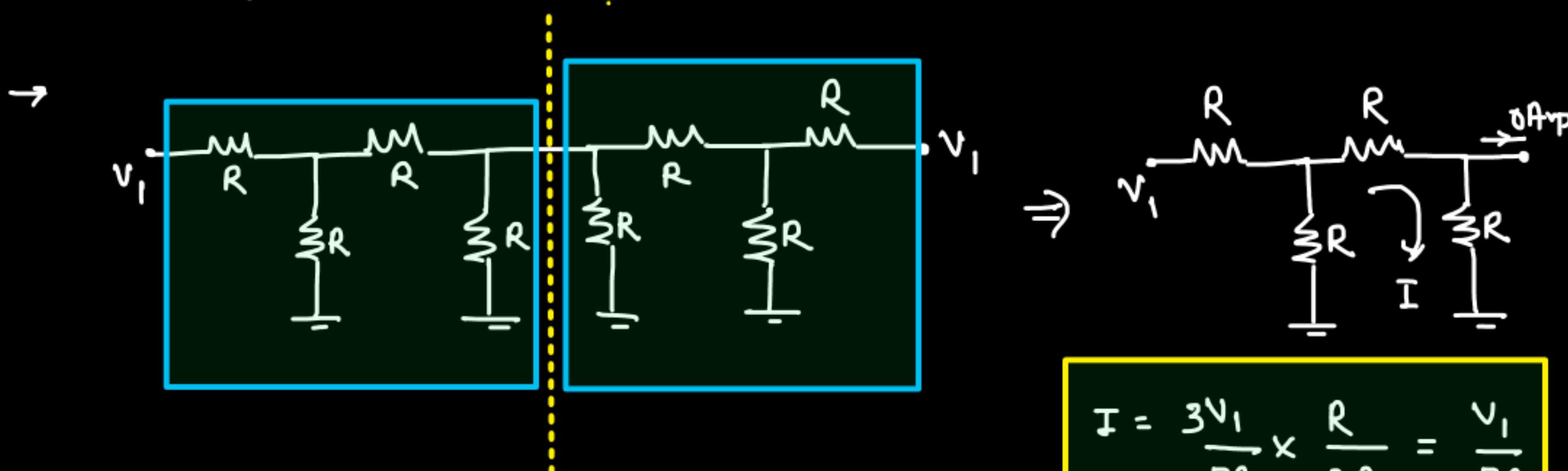

$$I = \frac{3v_1}{5R} \times \frac{R}{3R} = \frac{v_1}{5R}$$



⇒ Concept of Half Ckt:-

(a) For Differential Gain:-

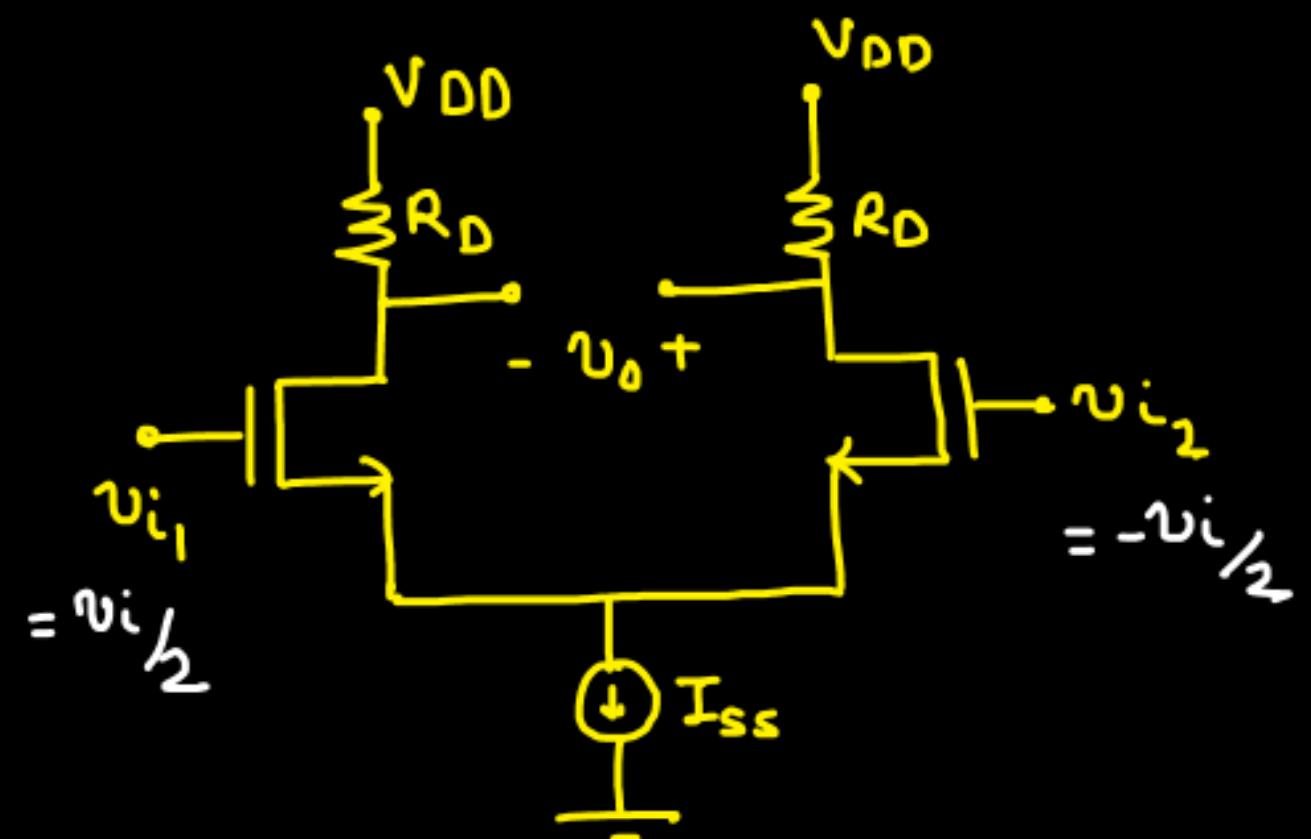

$$v_{i_1} - v_{i_2} = v_{in}$$

## Small signal Model :-

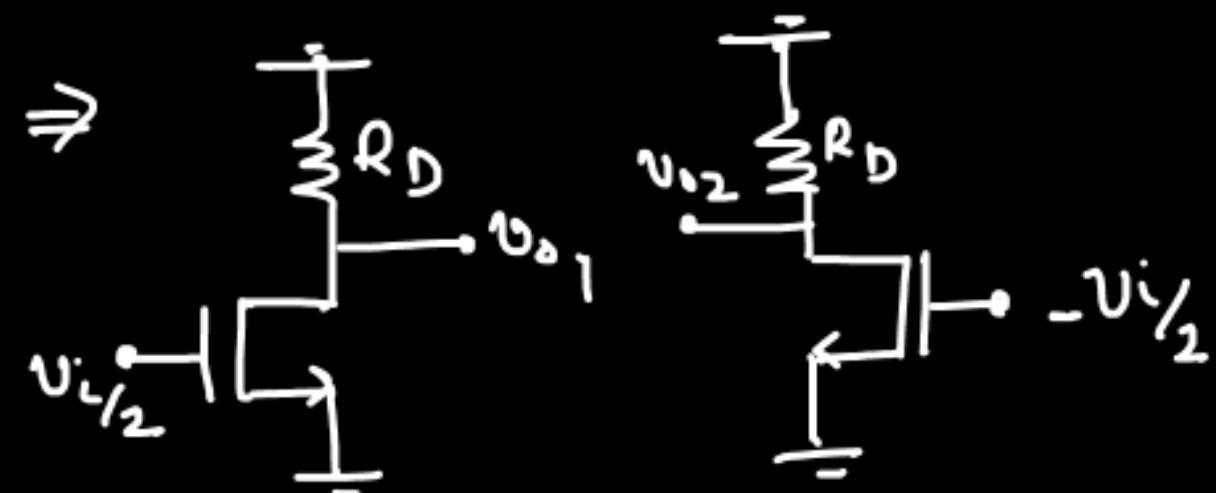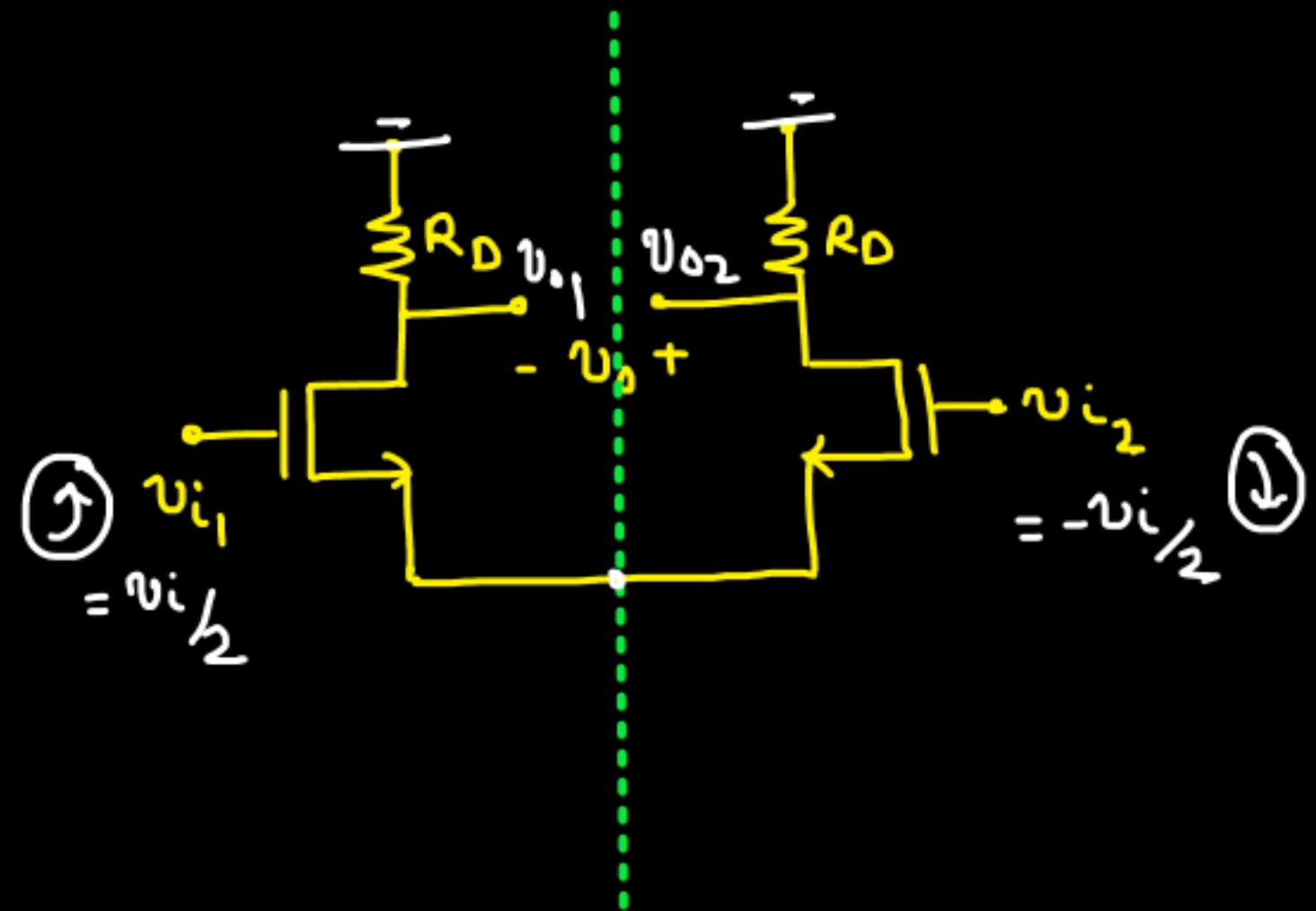


$$v_{o1} = -g_m R_D v_{i/2}$$

$$v_{o2} = g_m R_D v_{i/2}$$

$$v_o = g_m R_D v_i$$


$$(\partial v)_d = g_m R_D$$

For common Mode gain :-

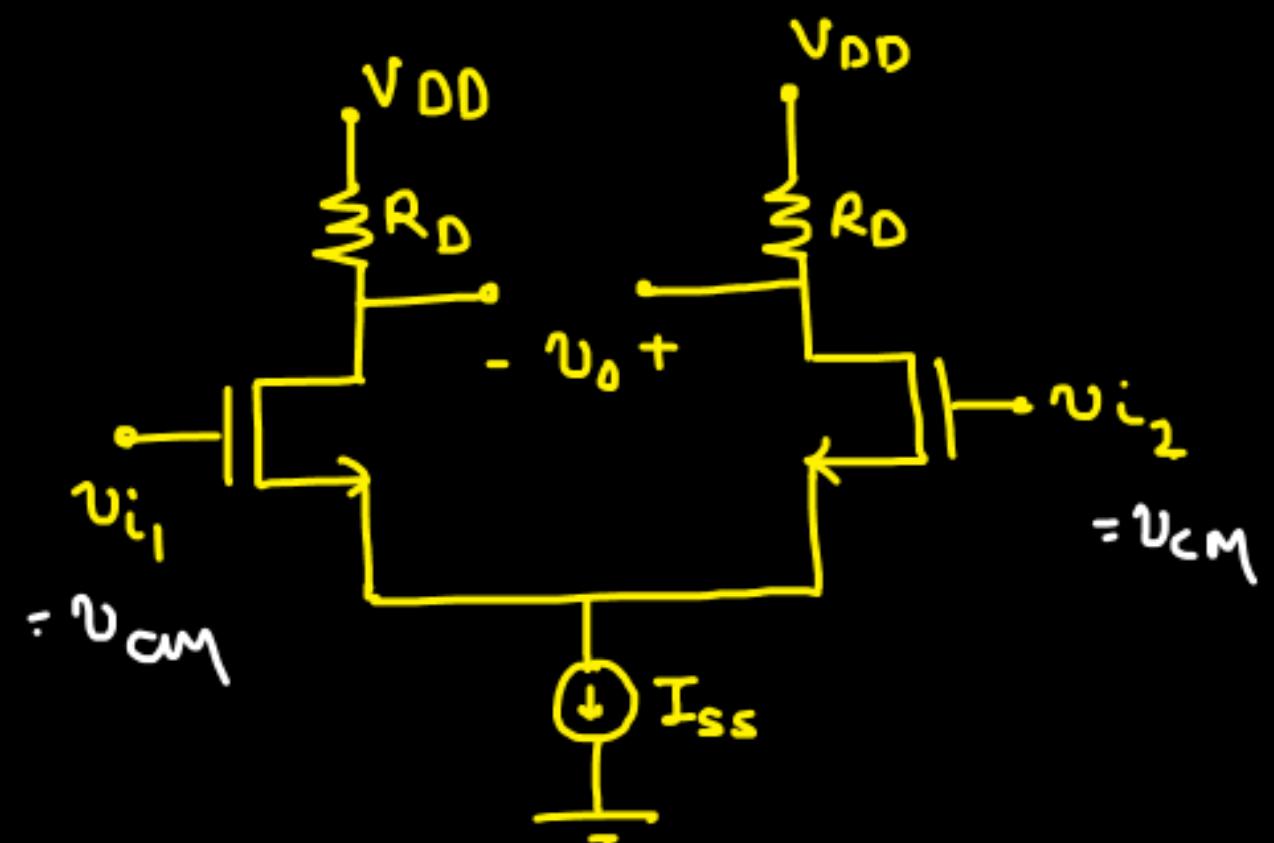

$$v_{i_1} - v_{i_2} = v_{in}$$

## Small Signal Model :-

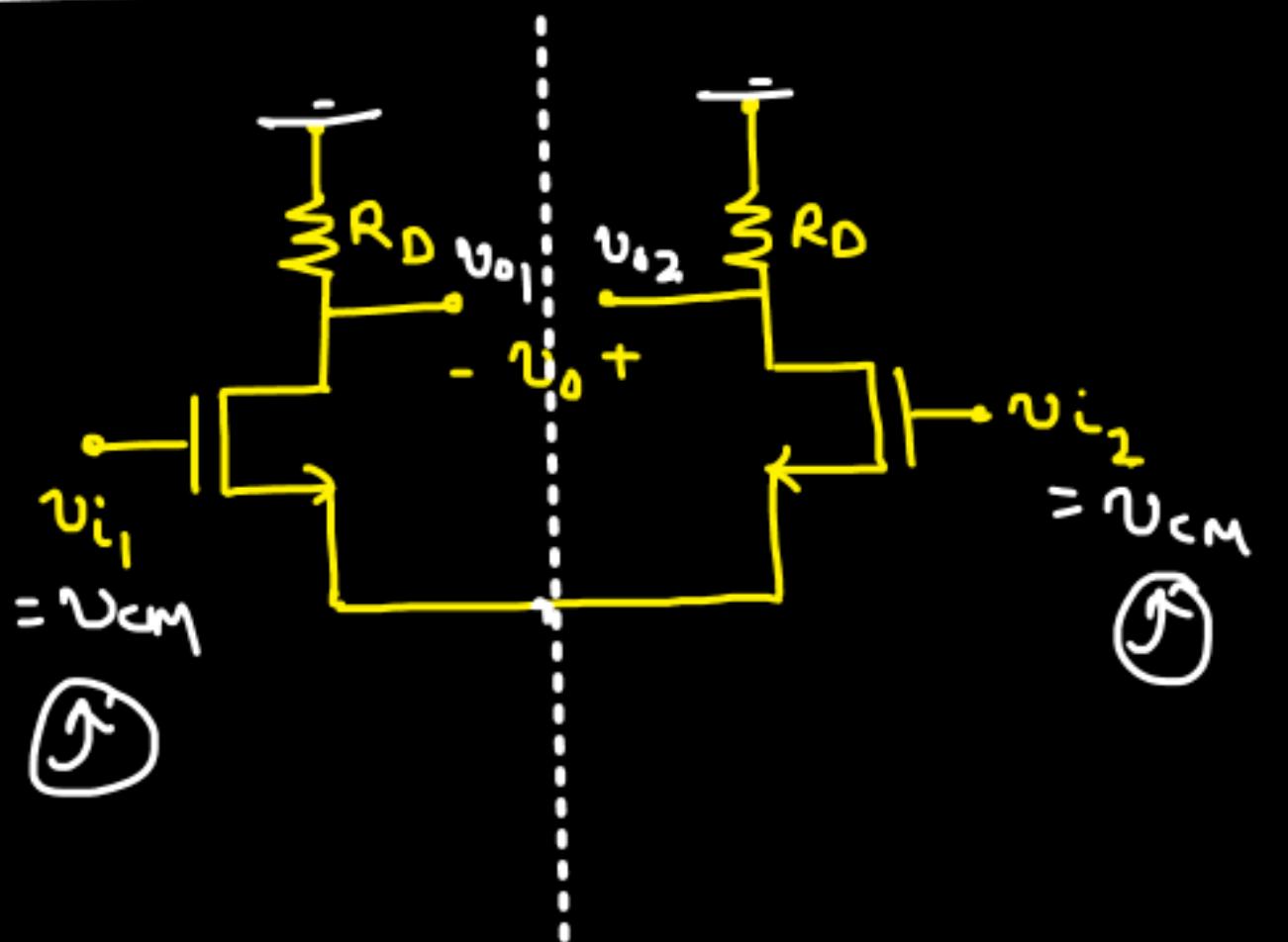


$$(v_o)_{CM} = \frac{v_{o_2} + v_{o_1}}{2}$$

$$(v_i)_{CM} = v_{CM}$$

⑤

Same Half ckt  $\leftarrow$   
for CM-DM

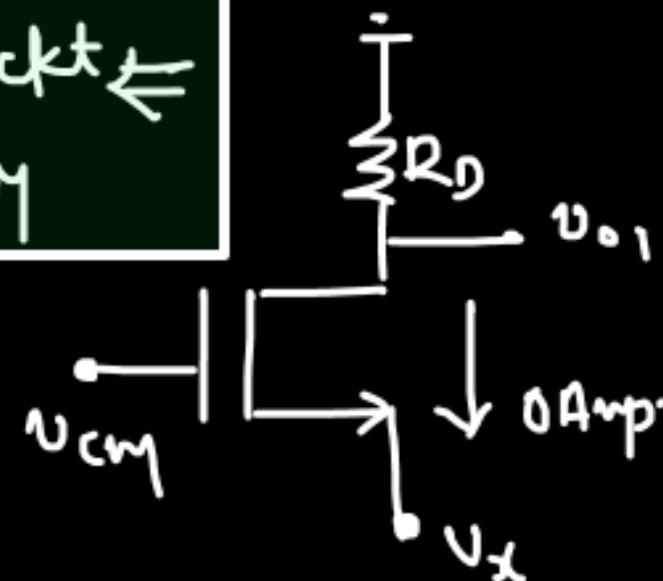

$$v_{o_1} = 0$$


$$v_{o_2} = 0$$

$$g_m(v_{CM} - v_x) = 0$$

$$v_x = v_{CM}$$

$$(Av)_{CM} = 0$$


Q.

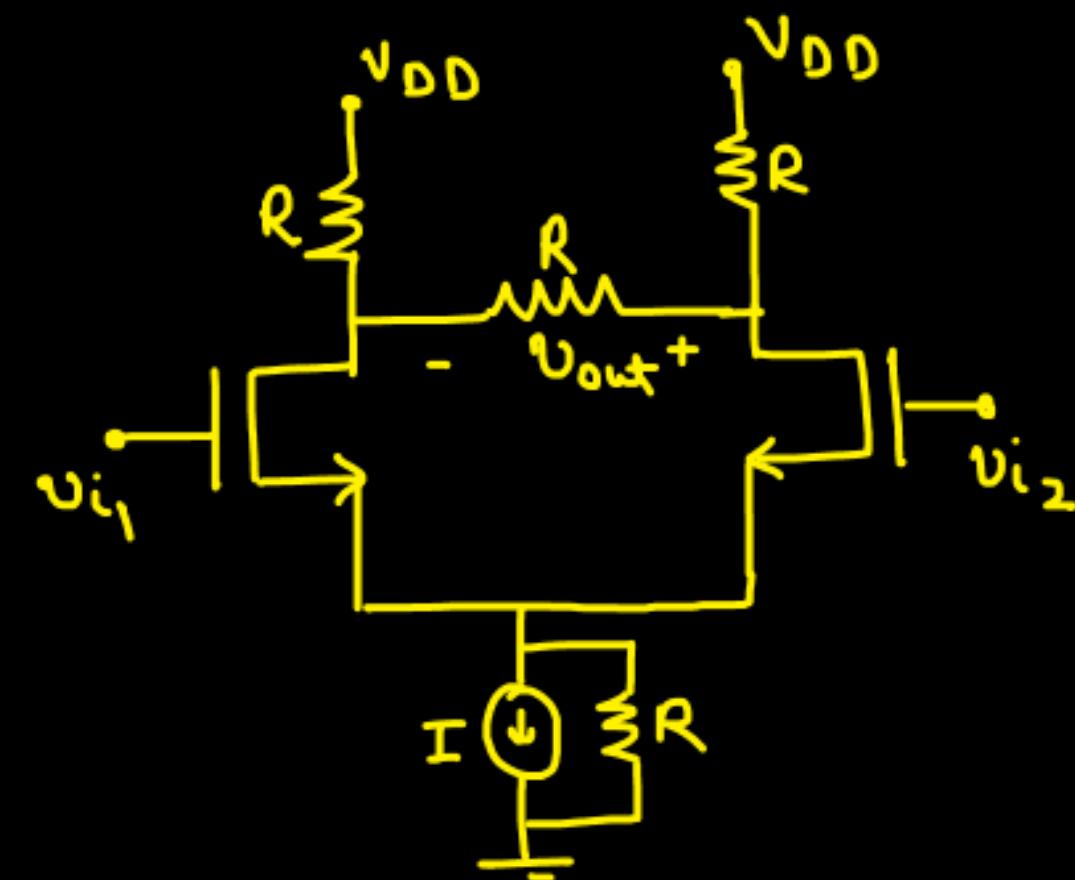

Find

- (a) Differential Gain
- (b) Common-Mode Gain
- (c) Common-Mode Differential Gain
- (d) CMRR



(q) Differential gain:-

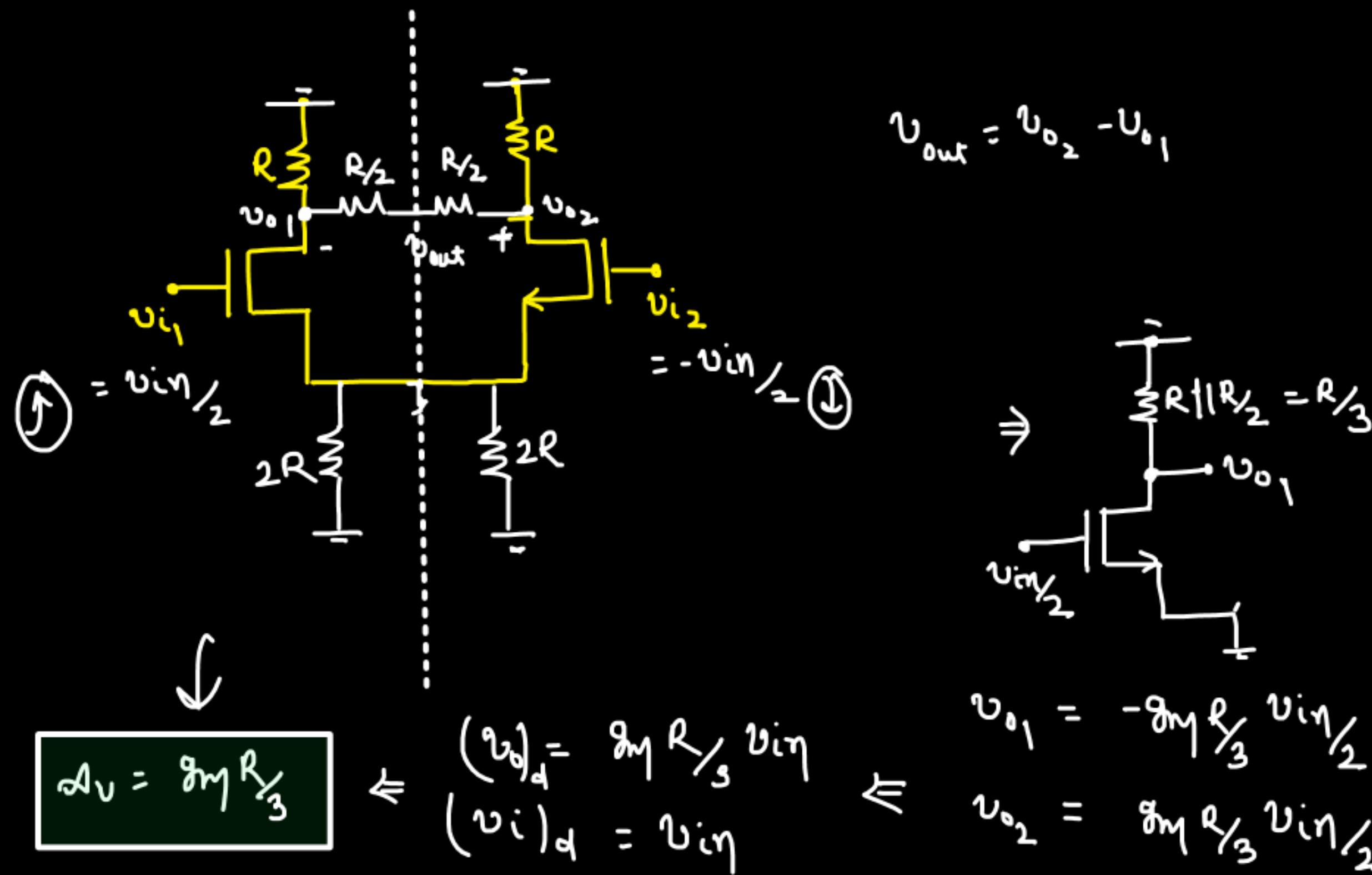

(b) Common Mode gain :-

$$(v_o)_{CM} = \frac{v_{o_1} + v_{o_2}}{2}$$

$$(v_i)_{CM} = v_{CM}$$

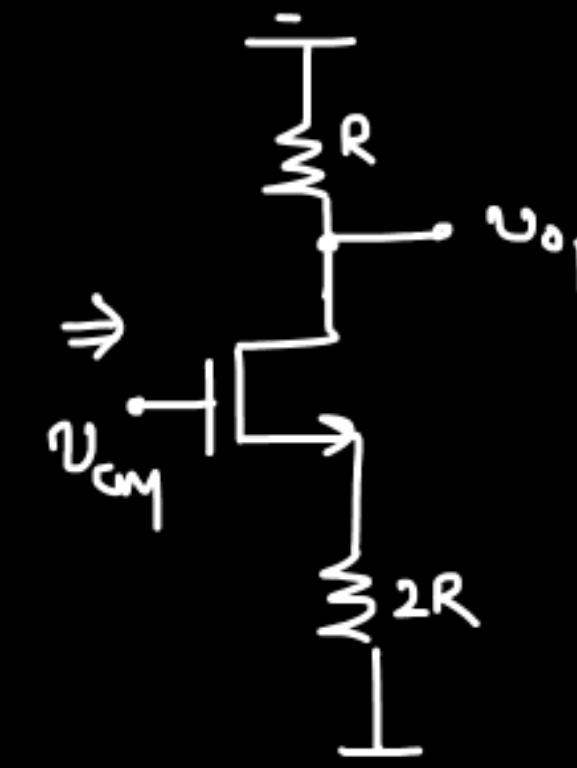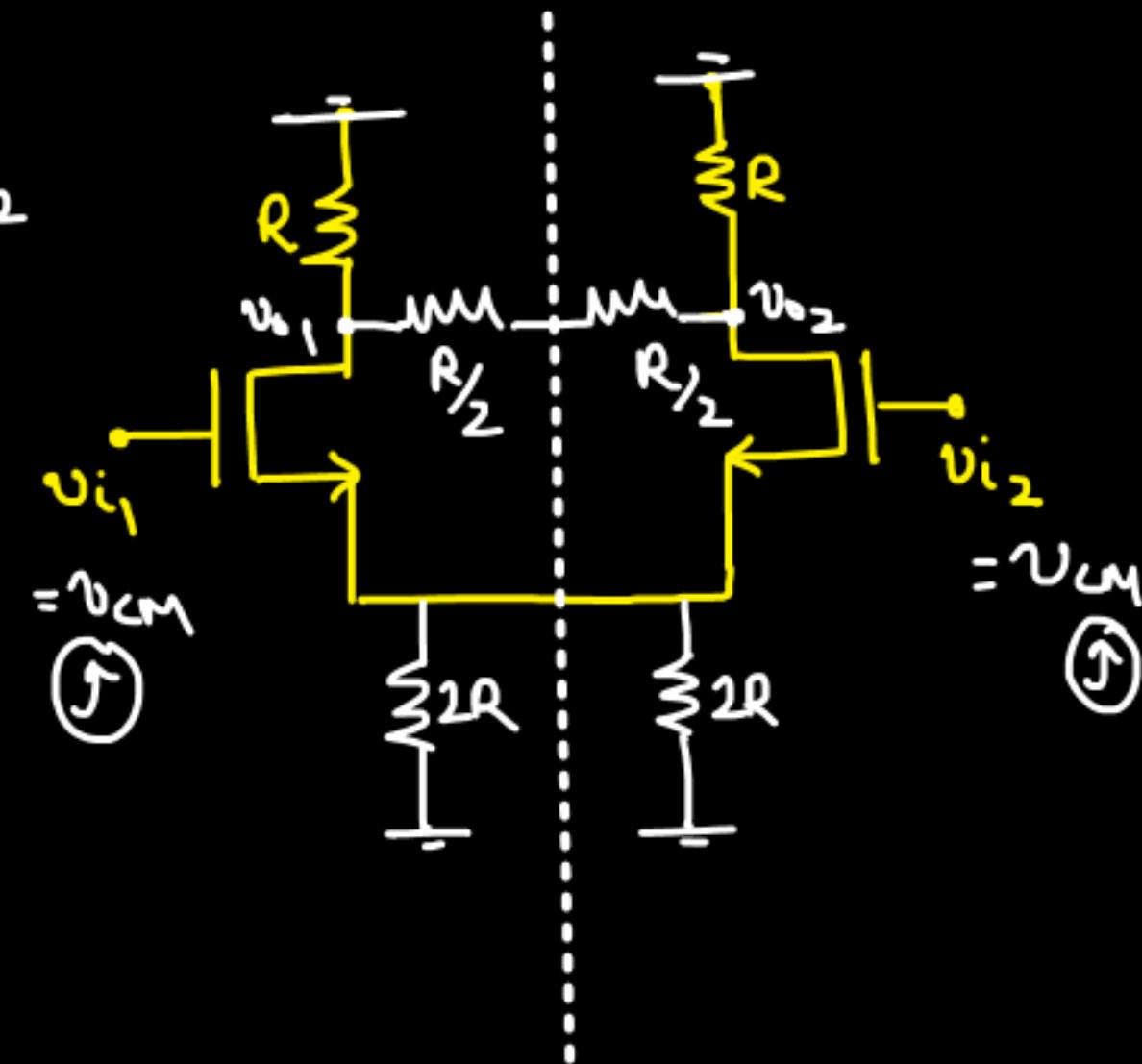

$$v_{o_1} = -\frac{g_m R}{1 + 2g_m R} v_{CM}$$

$$v_{o_2} = -\frac{g_m R}{1 + 2g_m R} v_{CM}$$

$$(A_v)_{CM} = -\frac{g_m R}{1 + 2g_m R}$$

$$(v_o)_{CM} = -\frac{g_m R}{1 + 2g_m R} v_{CM}$$


(c) Common Mode Differential Gain :-

$$(V_o)_{CM-DM} = V_{o_2} - V_{o_1}$$
$$= 0$$

$$(A_v)_{CM-DM} = 0$$

## ⇒ Large Signal Analysis of differential amplifier:-

(DC)

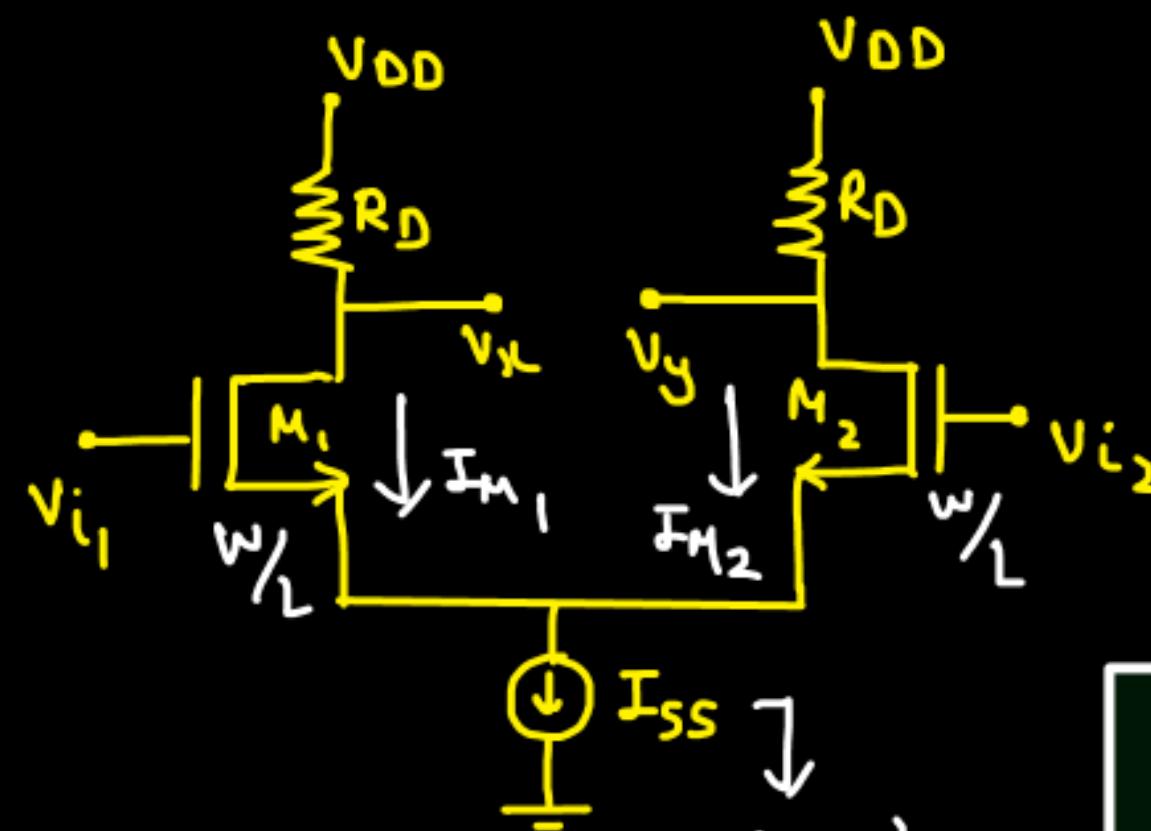

$$I_{M_1} + I_{M_2} = I_{ss}$$

$$v_x = V_{DD} - I_{M_1} R_D$$

$$v_y = V_{DD} - I_{M_2} R_D$$

Let

@ some  $v_{i_1} = v_a \Rightarrow I_{M_1} = I_{ss}, I_{M_2} = 0 \text{ A.P.}$

$$v_x = V_{DD} - I_{ss} R_D$$

$$v_y = V_{DD}$$

$$v_{xy} = - I_{ss} R_D$$

↳

if  $v_{i_1} \uparrow \Rightarrow I_{M_1} \uparrow \Rightarrow v_x \downarrow$

$\downarrow$   
 $I_{M_2} \downarrow \Rightarrow v_y \uparrow$   
 $\downarrow$

$$v_{xy} = v_x - v_y$$

if  $v_{i_2} \uparrow \Rightarrow I_{M_2} \uparrow \Rightarrow v_y \downarrow$

$\downarrow$

$I_{M_1} \uparrow \Rightarrow v_x \uparrow$

$\downarrow$

$$v_{xy} = v_x - v_y \uparrow$$

let @ some  $v_{i_2} = v_b$

$$I_{M_2} = I_{ss}$$


$\downarrow$

$$I_{M_1} = 0 \text{ Amp}$$

$$v_y = V_{DD} - I_{ss} R_D$$

$$v_x = V_{DD}$$

$$v_{xy} = I_{ss} R_D$$

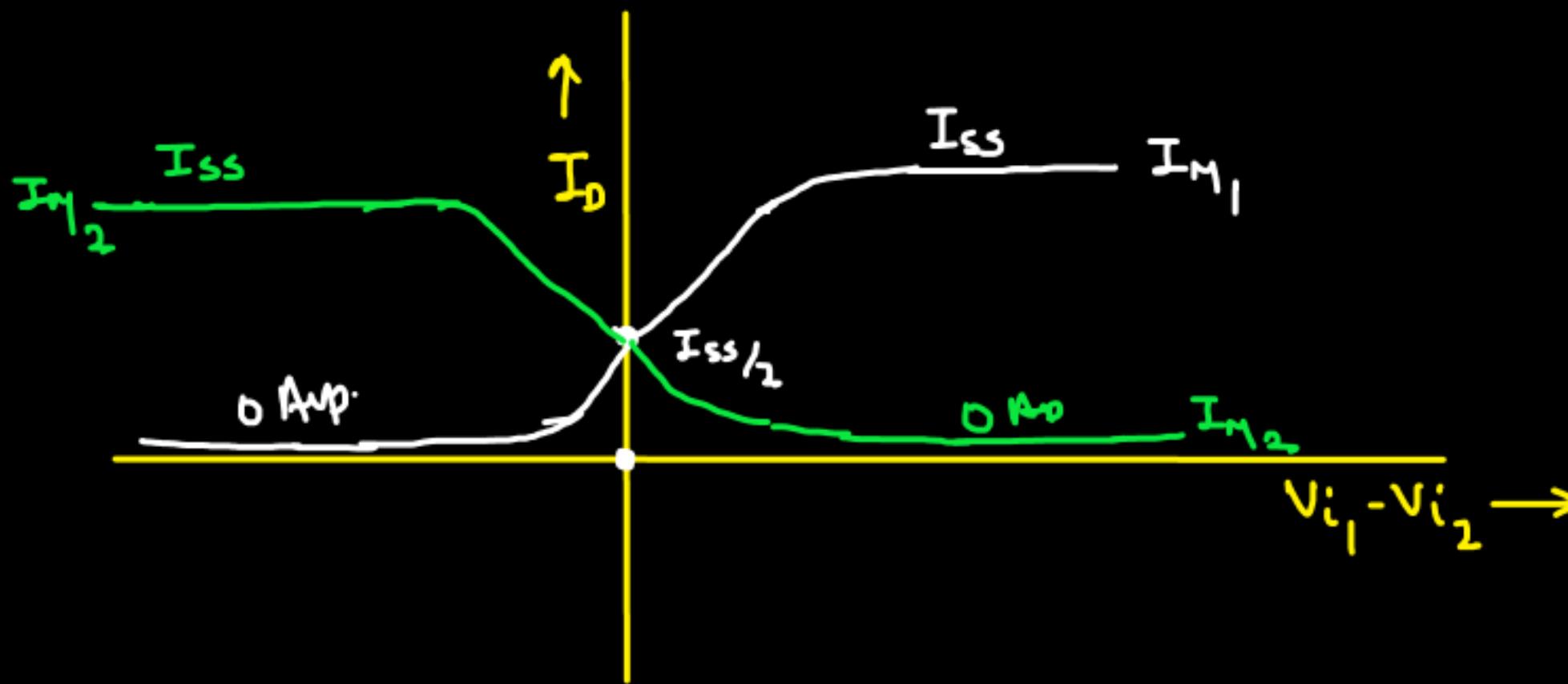


if  $v_{i_1} - v_{i_2} > 0$

$\Rightarrow v_{i_1} > v_{i_2}$

if  $v_{i_1} - v_{i_2} < 0$

$\Rightarrow v_{i_1} < v_{i_2}$

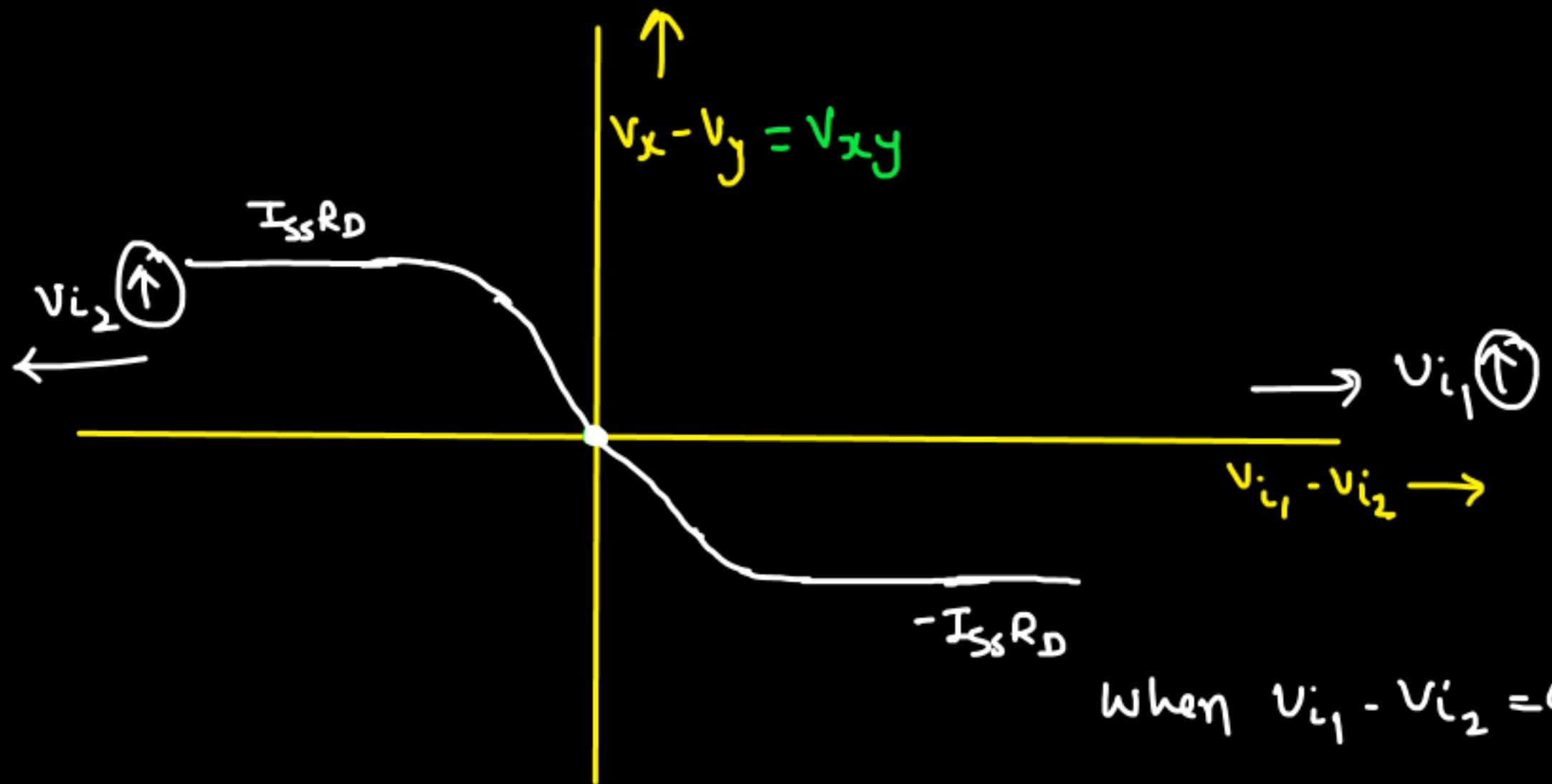

if  $V_{i_1} > V_{i_2} \Rightarrow V_x < V_y \Rightarrow V_{xy} = -ve$

if  $V_{i_2} > V_{i_1} \Rightarrow V_x > V_y \Rightarrow V_{xy} = +ve$

$$\text{when } V_{i_1} - V_{i_2} = 0$$

$$\Rightarrow V_{i_1} = V_{i_2} \Rightarrow I_{M_1} = I_{M_2} = I_M$$


$$V_x = V_{DD} - I_M R_D$$

$$V_y = V_{DG} - I_M R_D$$

$$V_{xy} = 0$$

Assignment - 11

Q.

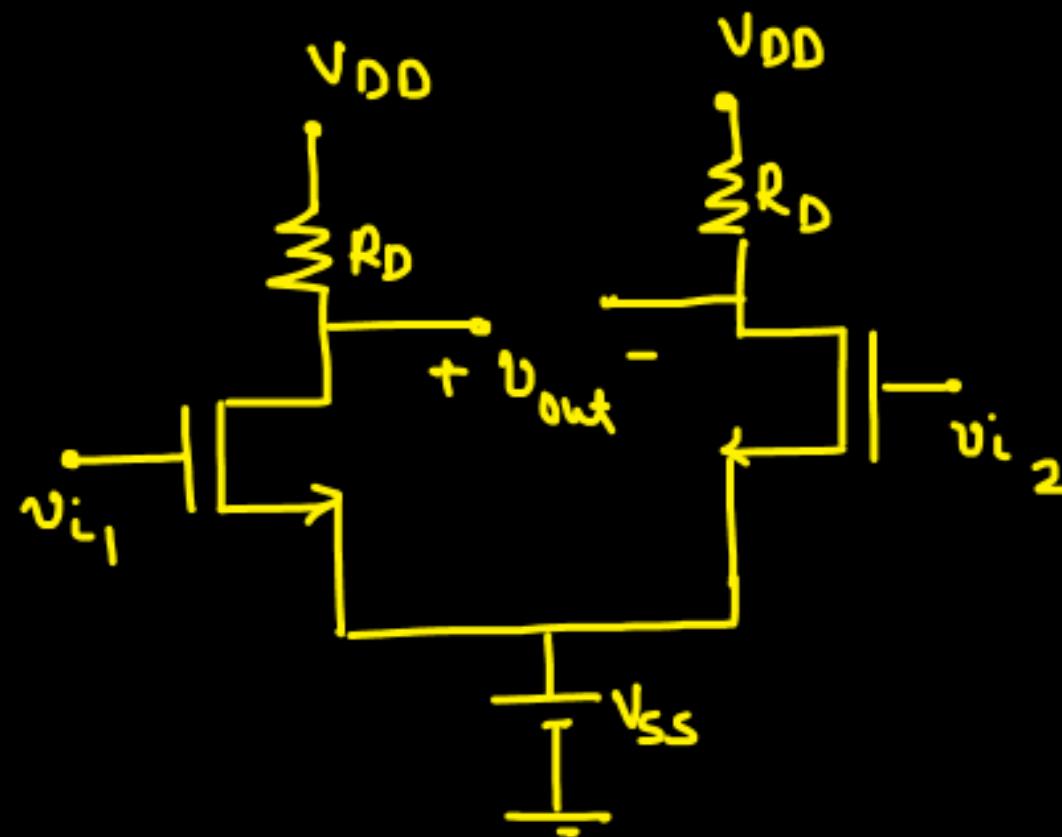


Find

(a) Differential gain

(b) Common-Mode gain

$$v_{i_1} - v_{i_2} = 2v_{in}$$

⇒ (a)

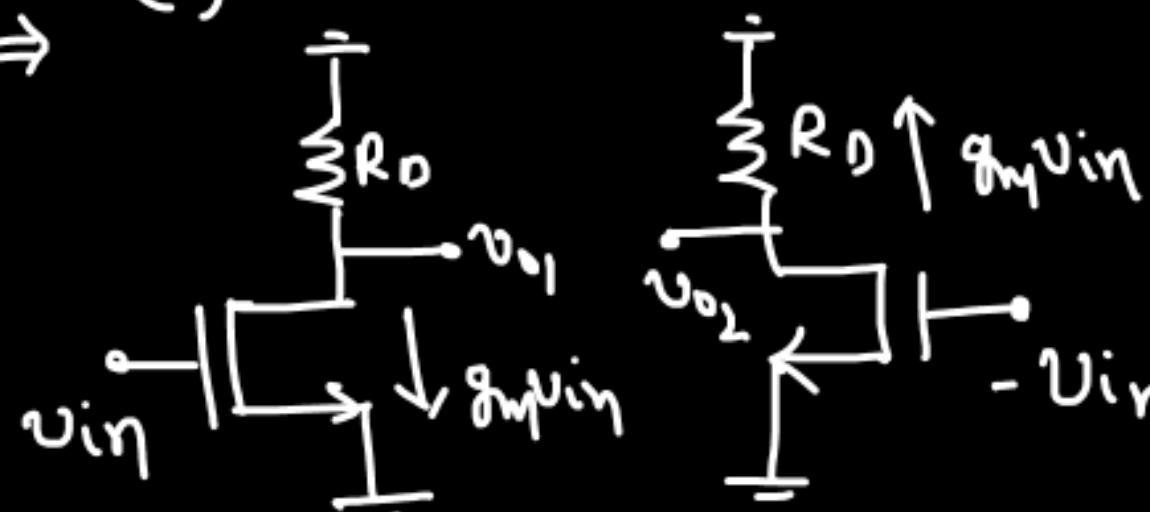

$$v_{o_1} = -g_m R_D v_{in}$$


$$v_{o_2} = g_m R_D v_{in}$$

$$(v_o)_d = v_{o_1} - v_{o_2} = -2g_m R_D v_{in}$$

$$(v_i)_d = 2v_{in}$$

$$(\partial v) = -g_m R_D$$

(b)

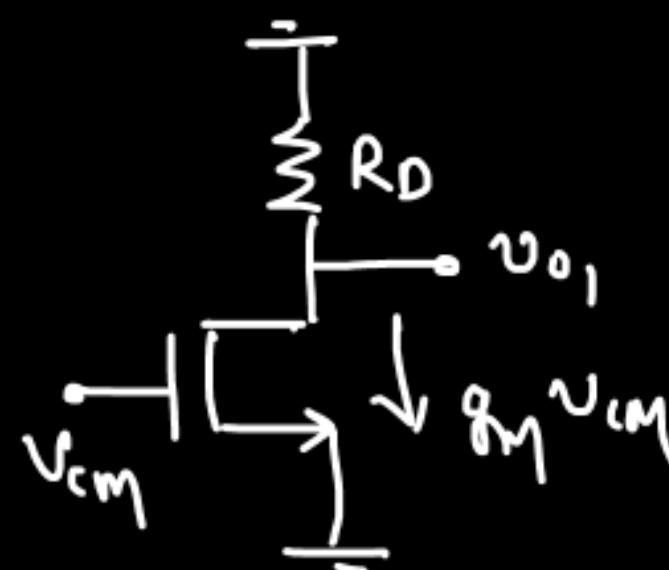


$$v_{01} = -g_M R_0 v_{cm}$$

$$v_{02} = -g_M R_D v_{cm}$$

$$(N_0)_{cm} = -g_M R_0 v_{cm}$$

$$(\Delta v)_{cm} = -g_M R_D$$


Q. 2

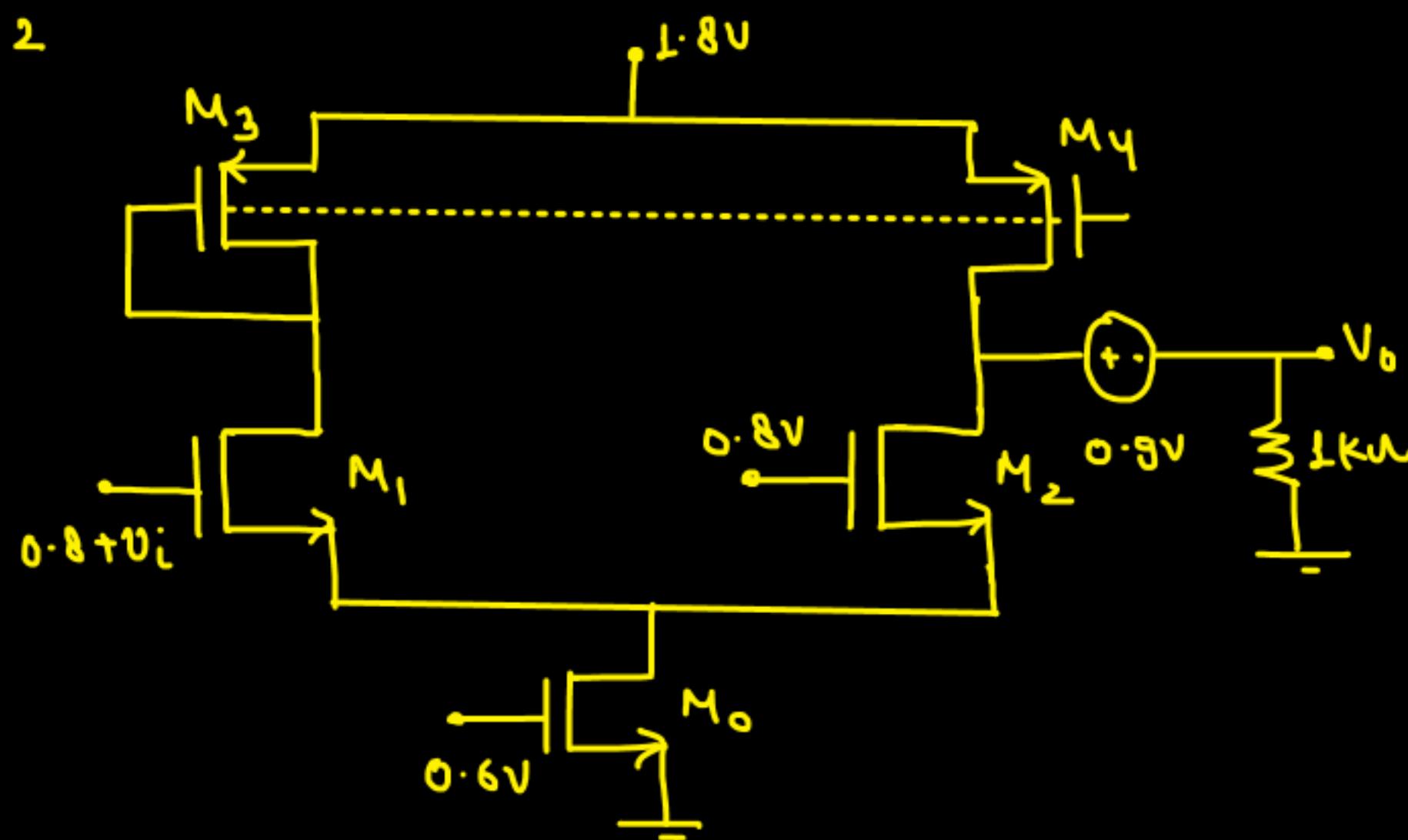

M<sub>0</sub> - M<sub>4</sub> all are biased in sat. region.

for all Transistors  $\beta_M = 25 \text{ mS}$ ,  $\lambda = 0$

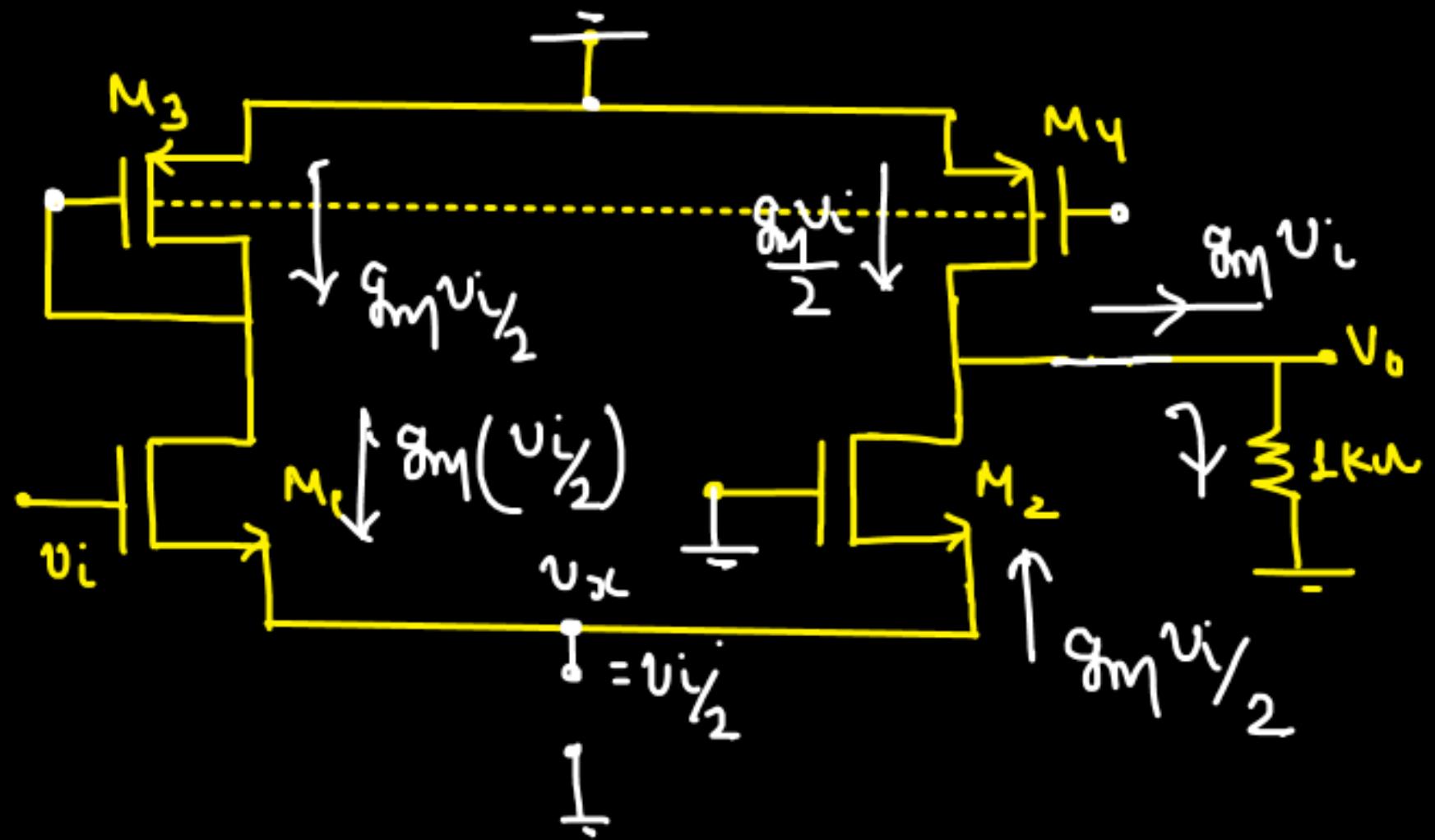Find small signal voltage gain. ( $\frac{V_o}{v_i}$ )



$$g_m(v_i - v_x) = g_m v_x$$

$v_x = v_{i/2}$

for  $M_3$  and  $M_4$   
 both  $g_m$  &  $v_{gs}$  are  
 same

$$\Rightarrow (i_a)_{M_3} = (i_a)_{M_4}$$


$$v_0 = g_m v_i (\text{Lk} \text{n})$$

$$\frac{v_0}{v_i} = 25m (\text{Lk})$$

$$\frac{v_0}{v_i} = 25 \text{ v/J}$$


Ans

Q.

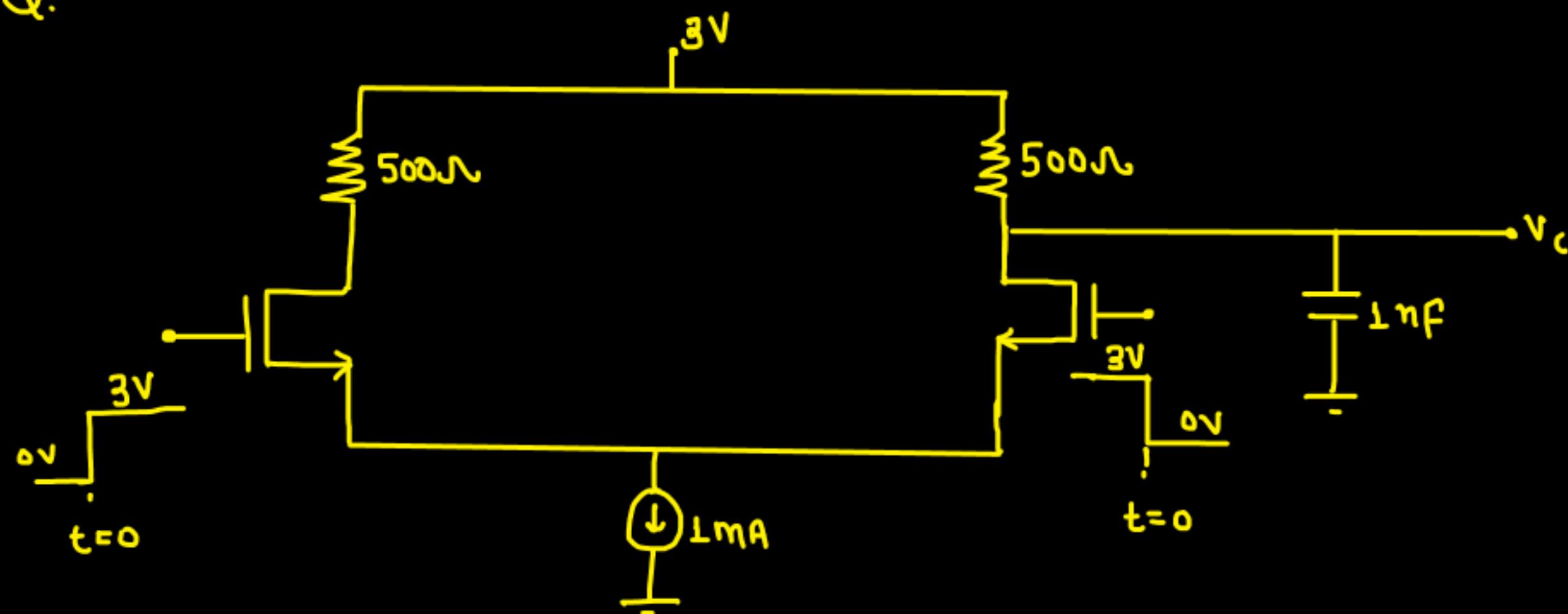


Find the time at which  $V_C$  node reaches to 2.9V

for  $t < 0$ :

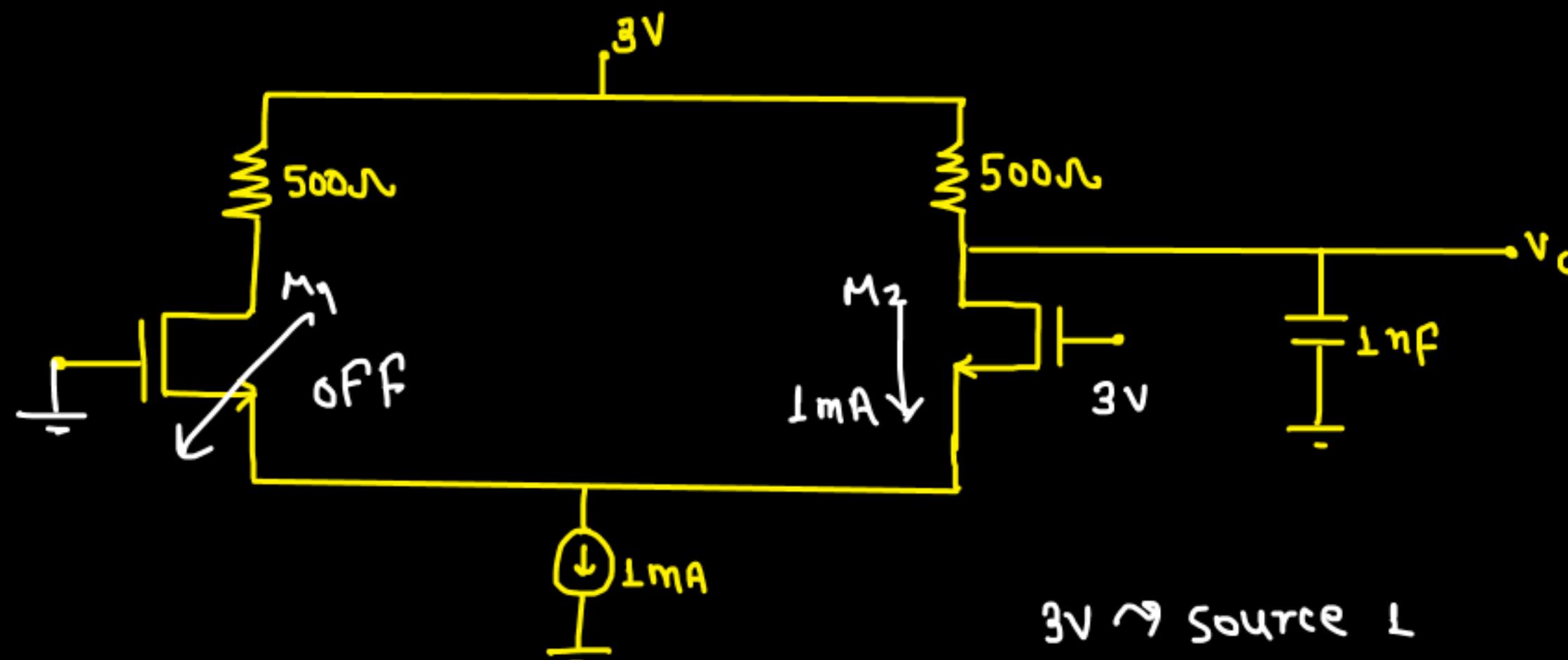


3V  $\rightsquigarrow$  SOURCE L

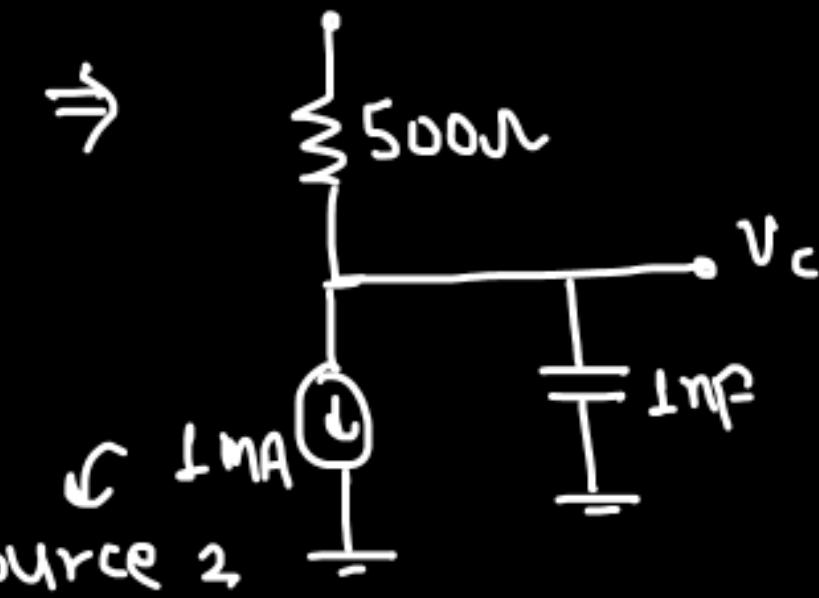


$$v_c(-\infty) = 0V$$
$$v_c(0^+) =$$

$$V_c = 0^\circ \text{ (S.S.)}$$


@ S.S.  $\Rightarrow$  Cap. O.C.

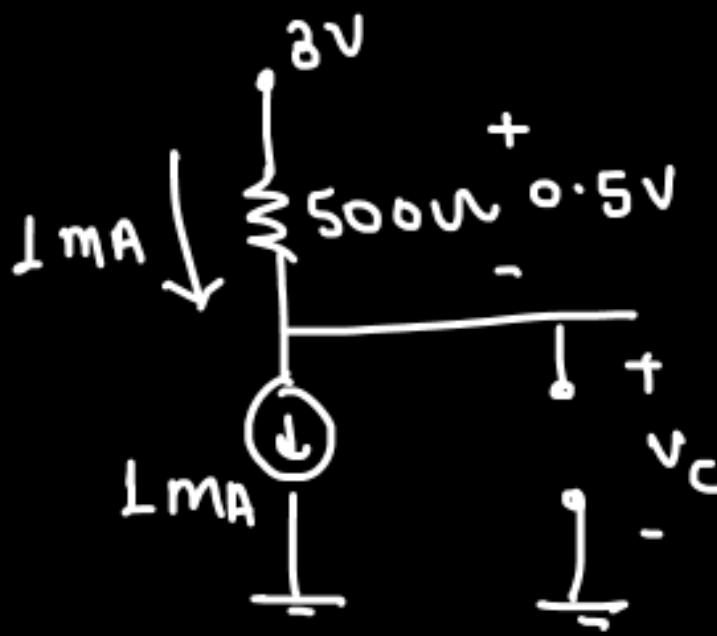


$$V_c(0^\circ) = 2.5V$$

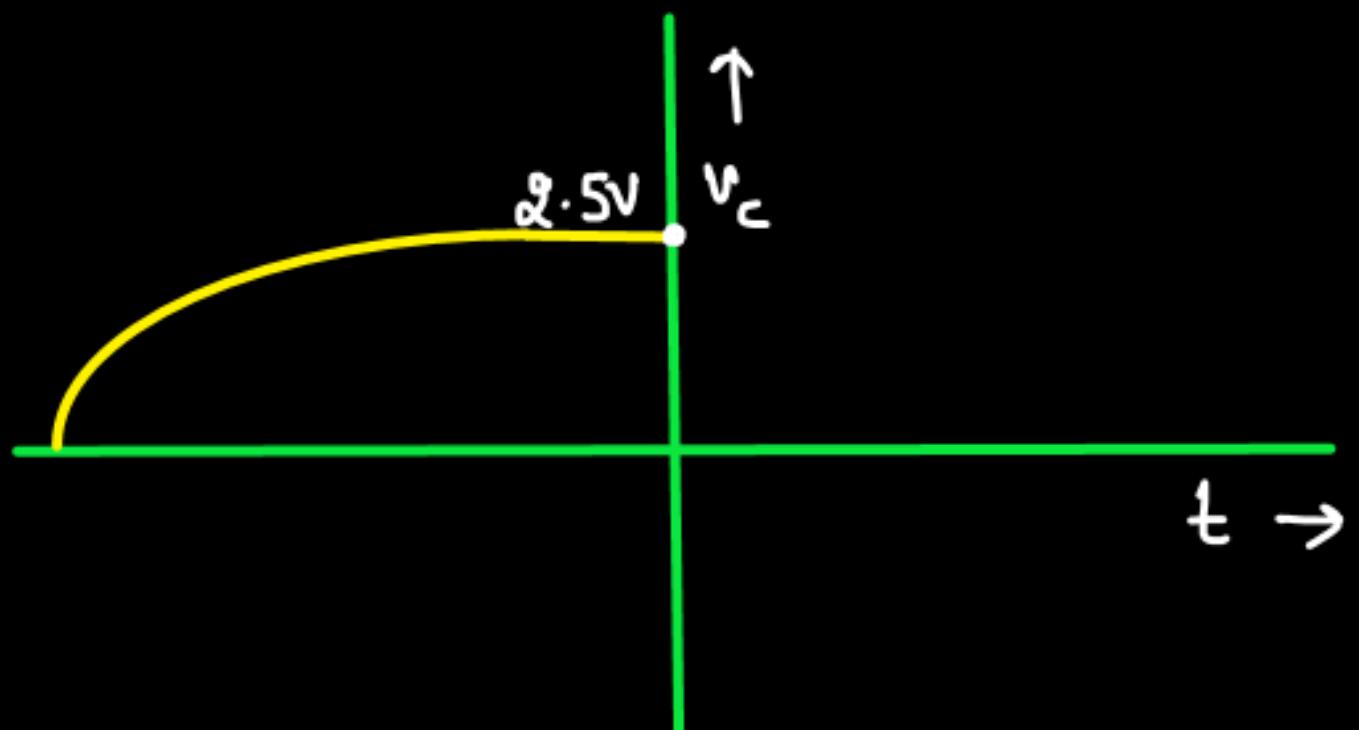


for  $t > 0$

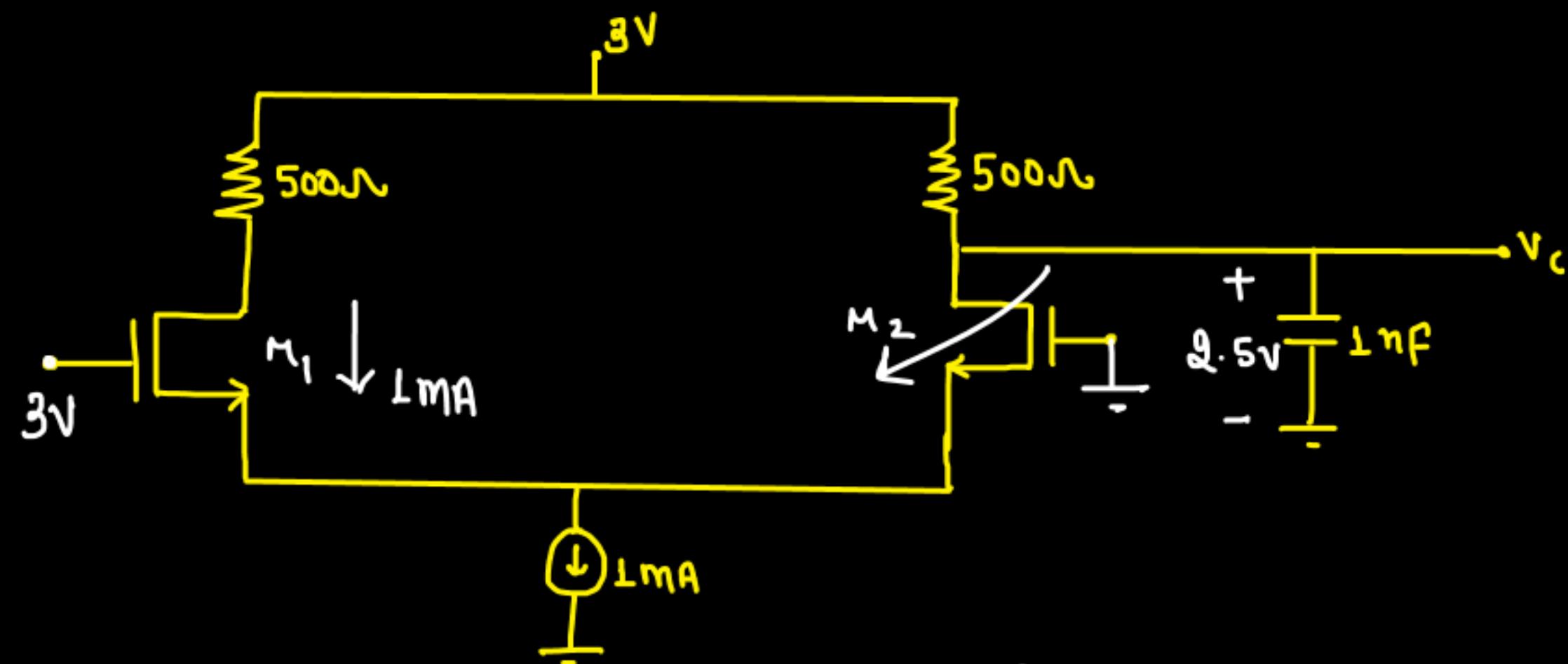

$M_2$  is off

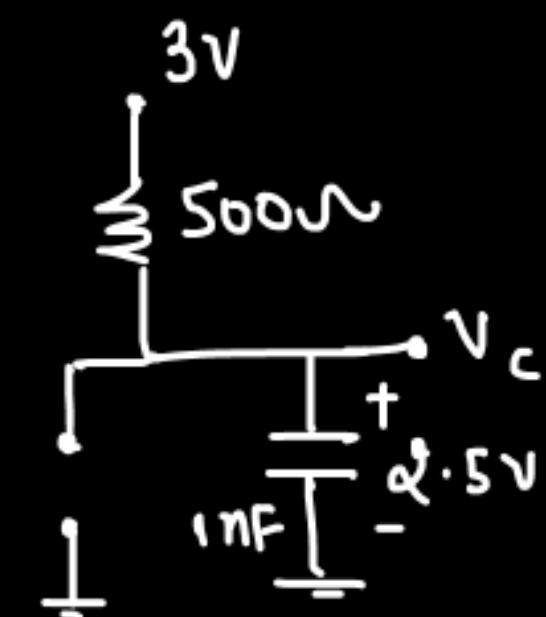

$\Rightarrow$

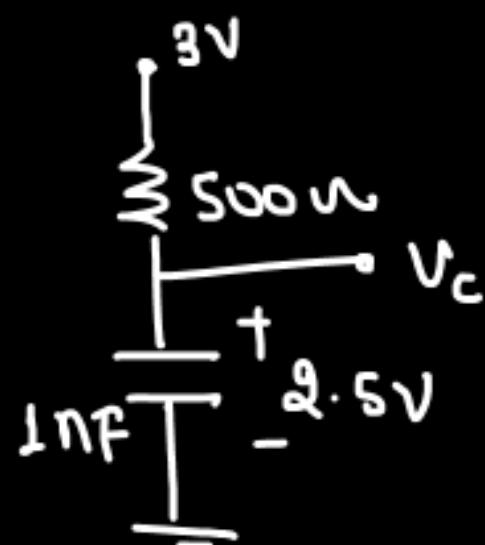


$$V_c(0^+) = 2.5V$$

$$V_c(\infty) = 3V$$

$$\tau = RC = 500 \times 1nF = 0.5\mu\text{sec.}$$

$$V_c(t) = 3 - 0.5 e^{-t/0.5\mu}$$

Let @  $t = t_1$ ,  $V_c(t_1) = 2.9V$

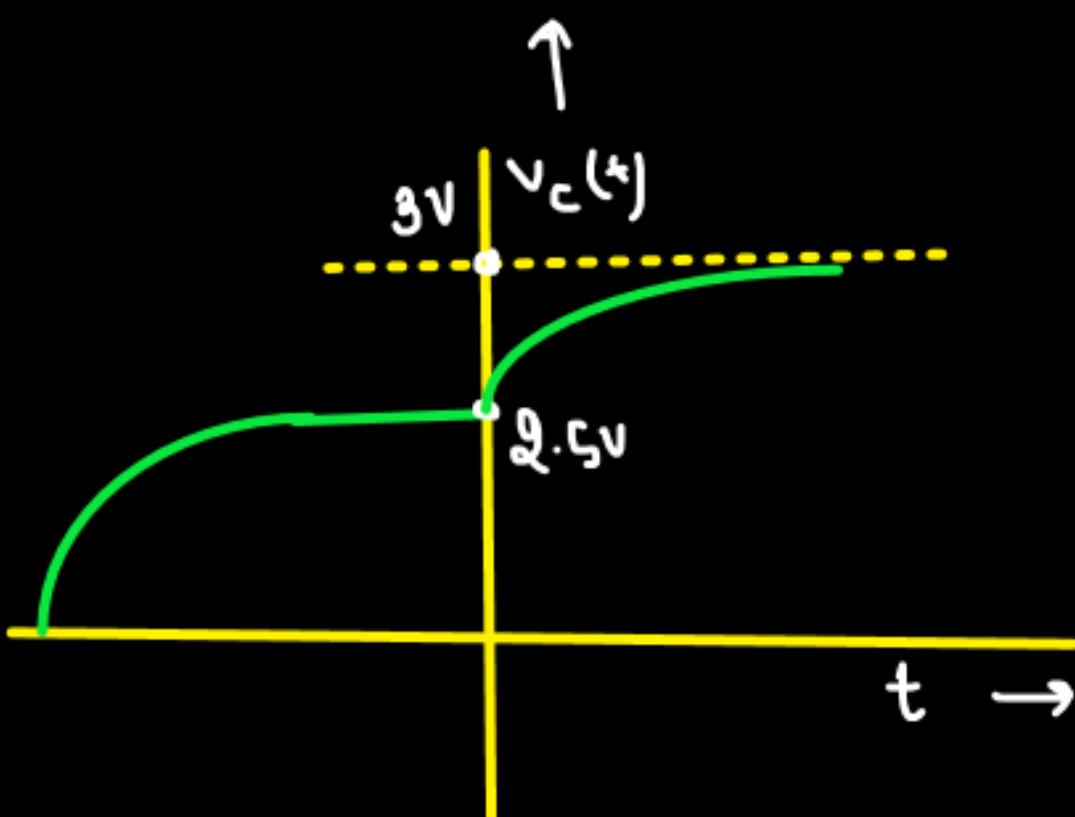

$$2.9 = 3 - 0.5 e^{-t_1/0.5\mu}$$


$$t_1 = 0.5 \ln(5) \mu\text{sec.}$$

$$t_1 = 0.8 \mu\text{sec.}$$

ANS

=

Q.

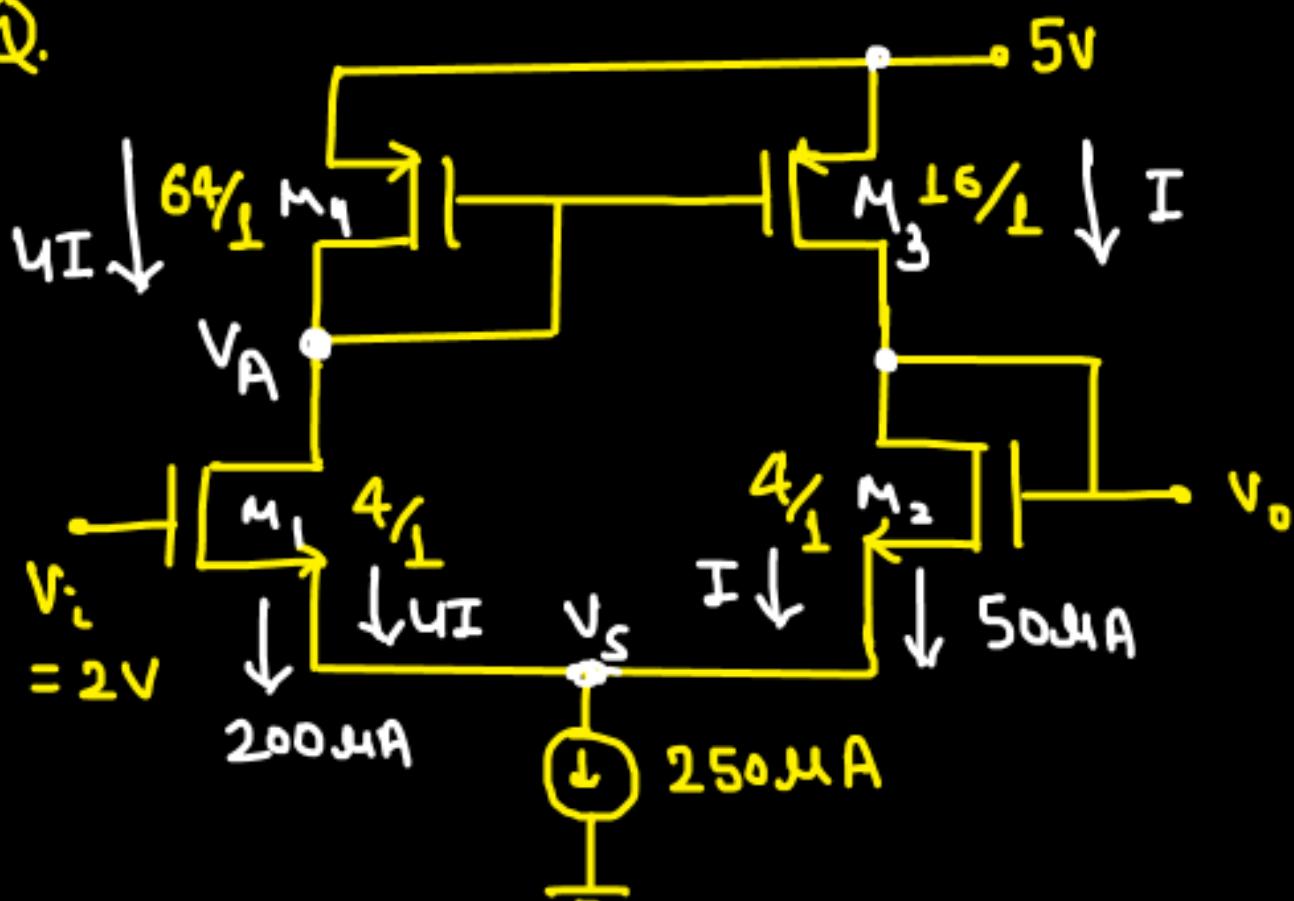

$M_4$  and  $M_3$  are in current mirror. [ $M_3$  should be in sat.]

∴

Assuming  $M_3$  to be in sat.

⇒  $M_4$  and  $M_3$  are in C.M.

$$4I + I_c < 250 \mu A$$

$$I = 50 \mu A$$

$$\mu_n C_{ox} = 400 \mu A/V^2, V_{Tn} = 0.5V$$

$$\mu_p C_{ox} = 100 \mu A/V^2, V_{Tp} = 0.5V$$

Find Output Voltage  $V_o$ .

Both  $M_1$  and  $M_2$  are having same source potential


but,  $M_1$  is in saturation

$$I_{M_1} = 200 \mu A$$

$$\Rightarrow 200 \mu A = \frac{400 \mu A \times 4}{2} \left( 2 - V_s - 0.5 \right)^2$$

$$0.5 = 1.5 - V_s$$

∴  $V_s = 1V$

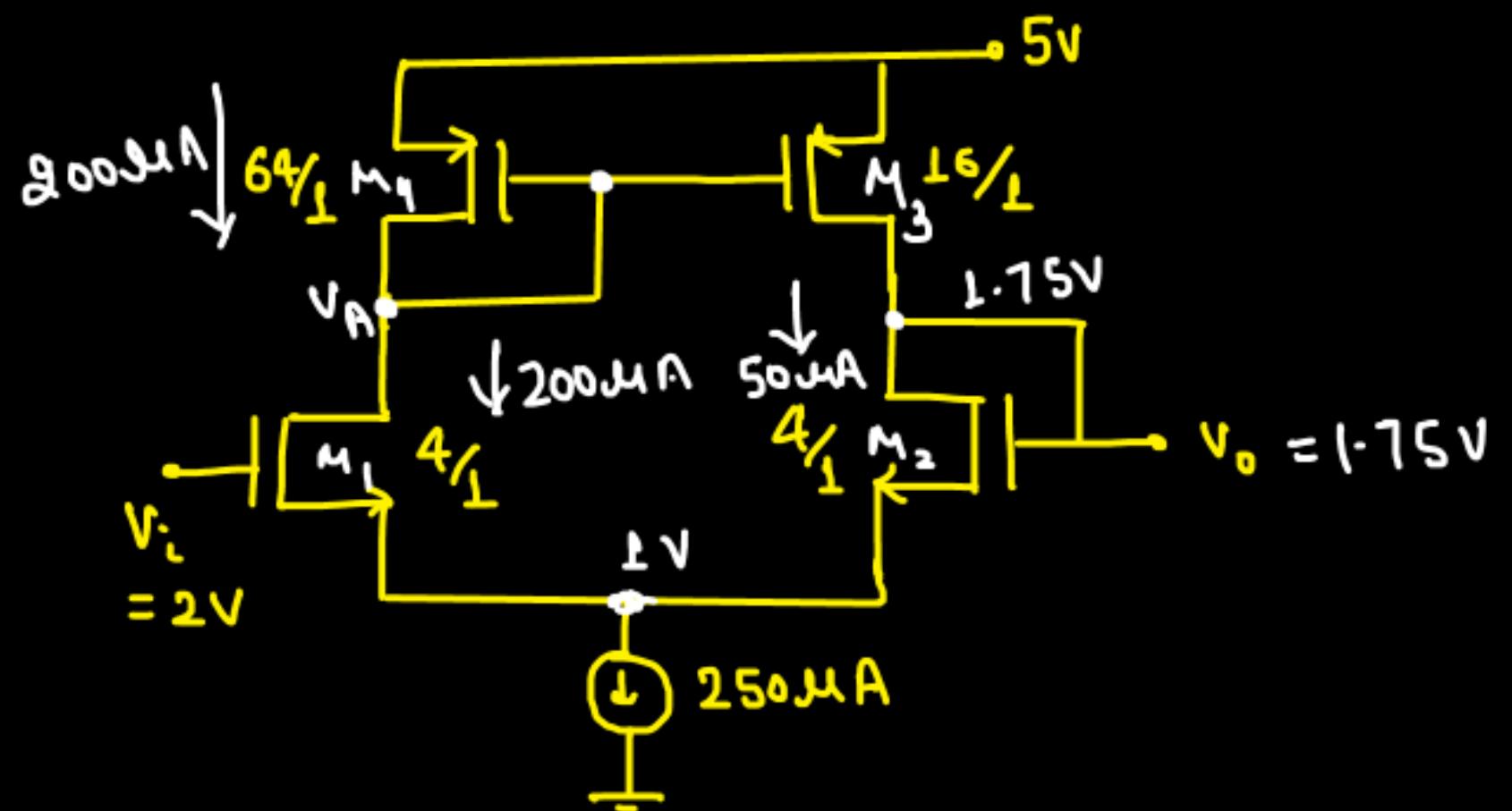

$M_2$  is in sat.

$$I_{M_2} = 50\mu A$$

$$\Rightarrow 50\mu A = \frac{400\mu A \times 4}{2} [V_o - 1 - 0.5]^2$$

$$V_o = 1.75V$$

$\Rightarrow$  correct?  $\Rightarrow$  NOT SURE  $\Rightarrow$  Take care of Assump.

check:- if  $M_1$  and  $M_3$  are in sat. or NOT.


$$I_{M_4} = 200 \mu A \quad [\text{Sat.}]$$

$$\Rightarrow 200\mu = \frac{100\mu \times 64}{2} [5 - V_A - 0.5]^2$$

$$0.25 = 4.5 - V_A$$

$$V_A = 4.25V$$

for  $M_1$  :-

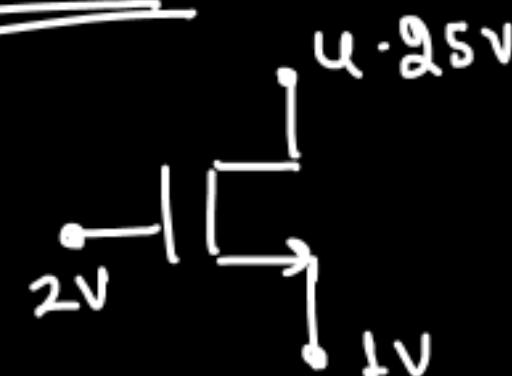

$$V_{DS} = 4.25V$$


$$V_{GS} = 1V$$

$$V_T = 0.5V$$

$$V_{OV} = 0.5V$$

$V_{DS} > V_{OV} \Rightarrow M_1$  is in sat  $\Rightarrow$  assumption correct

For  $M_3$ :

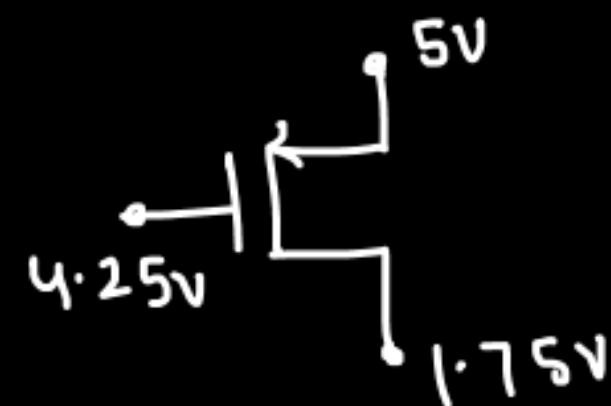

$$V_{SD} = 0.75$$

$$V_T = 0.5$$

$$V_{OV} = 0.25$$

$$V_{SD} = 3.25$$

$\Rightarrow V_{SD} > V_{OV} \Rightarrow$  sat. region



Assumption correct


$\Rightarrow$  all Tr  $M_1, M_2, M_3$  and  $M_4$  are in sat.

$$V_D = 1.75V$$

Ans.


=

Q.


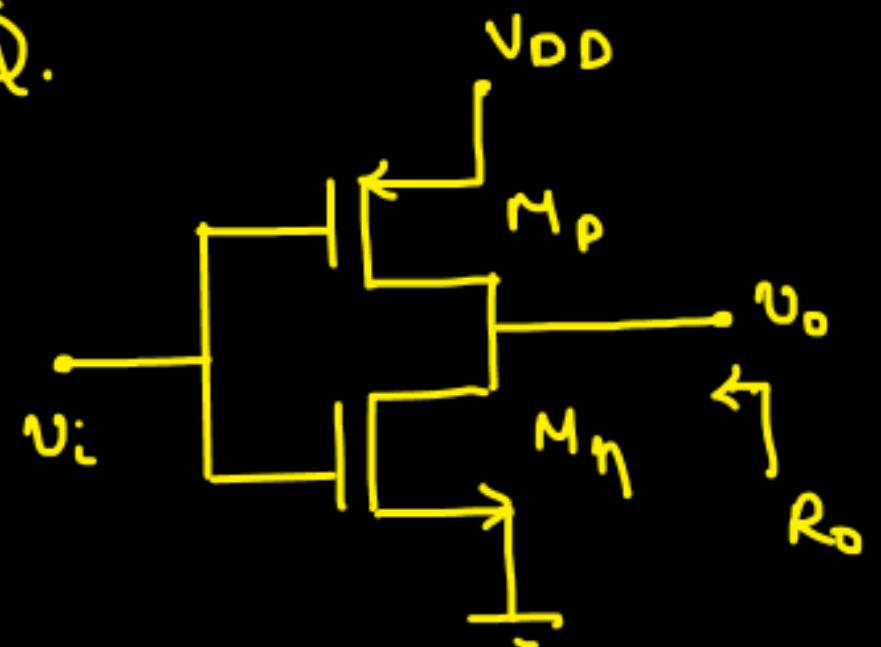


- ① find the small signal voltage gain.
- ② find Small signal o/p resistance.



$\Rightarrow$

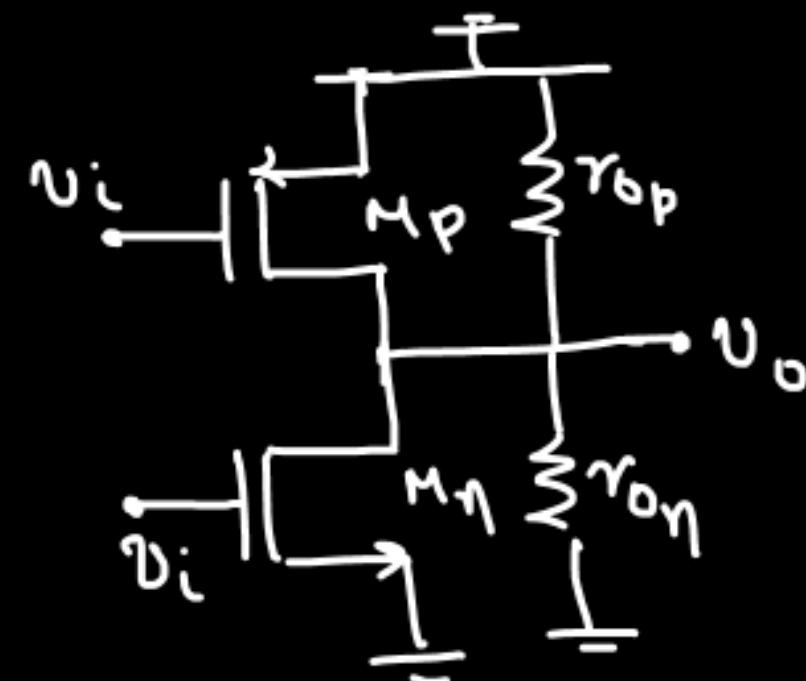

Applying super position :-

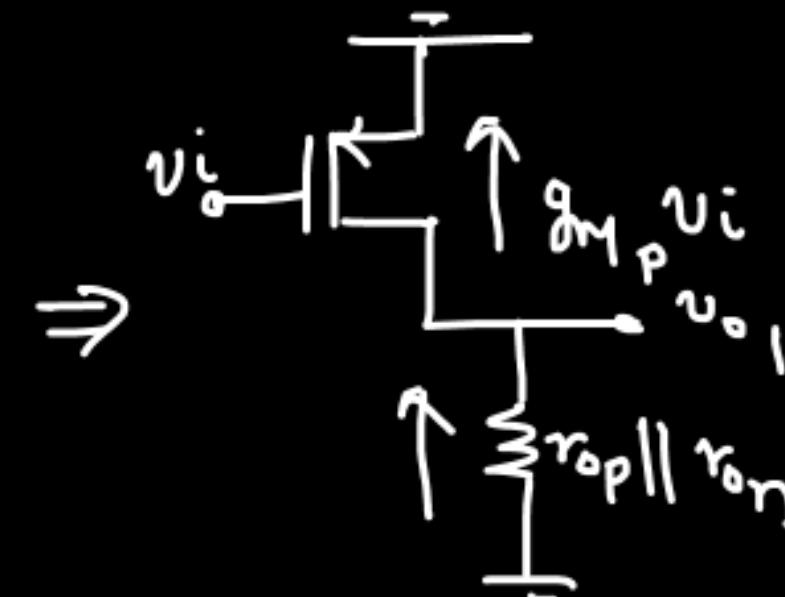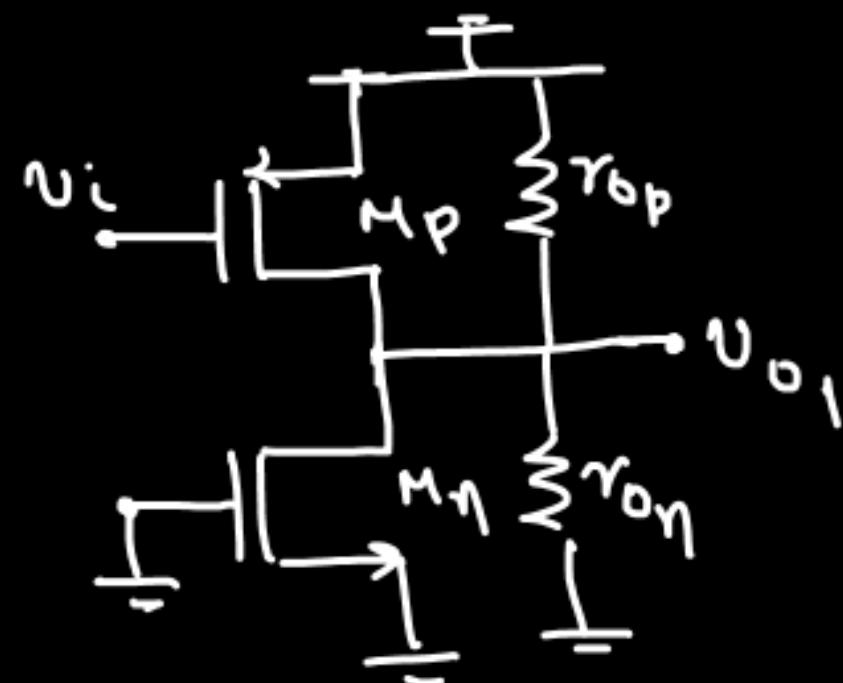

$$v_{o1} = -g_{mP} (r_{oP} || r_{o\eta}) v_i \quad \textcircled{1}$$

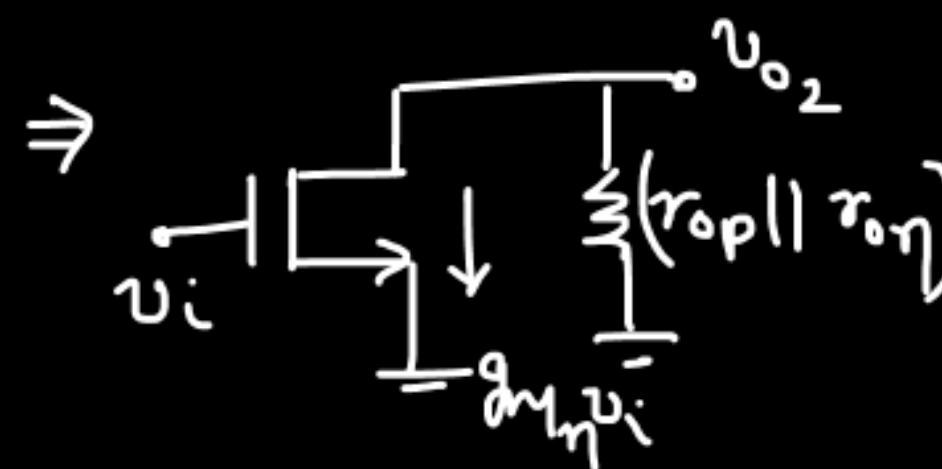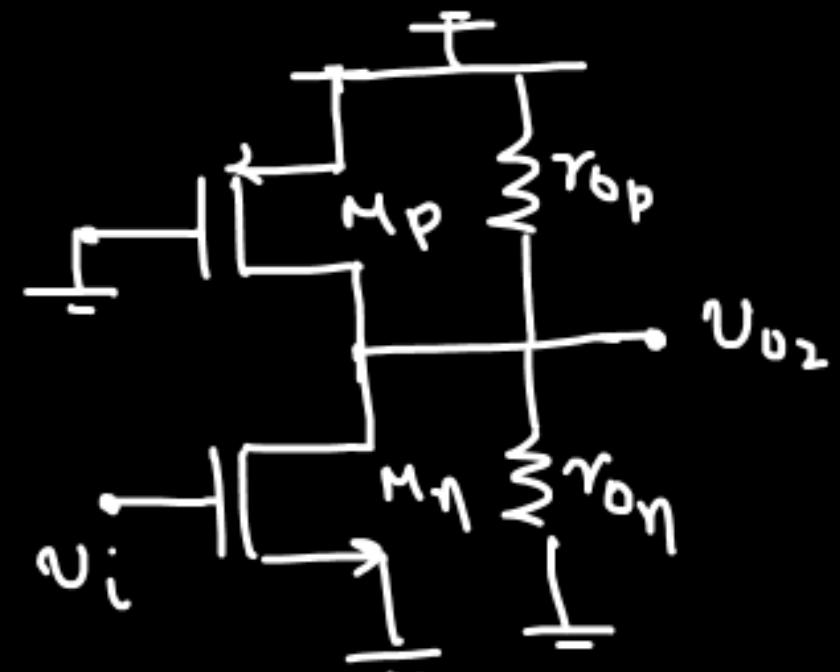

$$v_{o2} = -g_{m\eta} (r_{oP} || r_{o\eta}) v_i \quad \textcircled{2}$$


$$v_o = v_{o1} + v_{o2}$$

$$v_o = -(\text{g}_{m_p} + \text{g}_{m_n})(r_{o_p} \parallel r_{o_n}) v_{in}$$

$$\frac{v_o}{v_{in}} = -(\text{g}_{m_p} + \text{g}_{m_n})(r_{o_p} \parallel r_{o_n})$$

ANS

O/P impedance :-

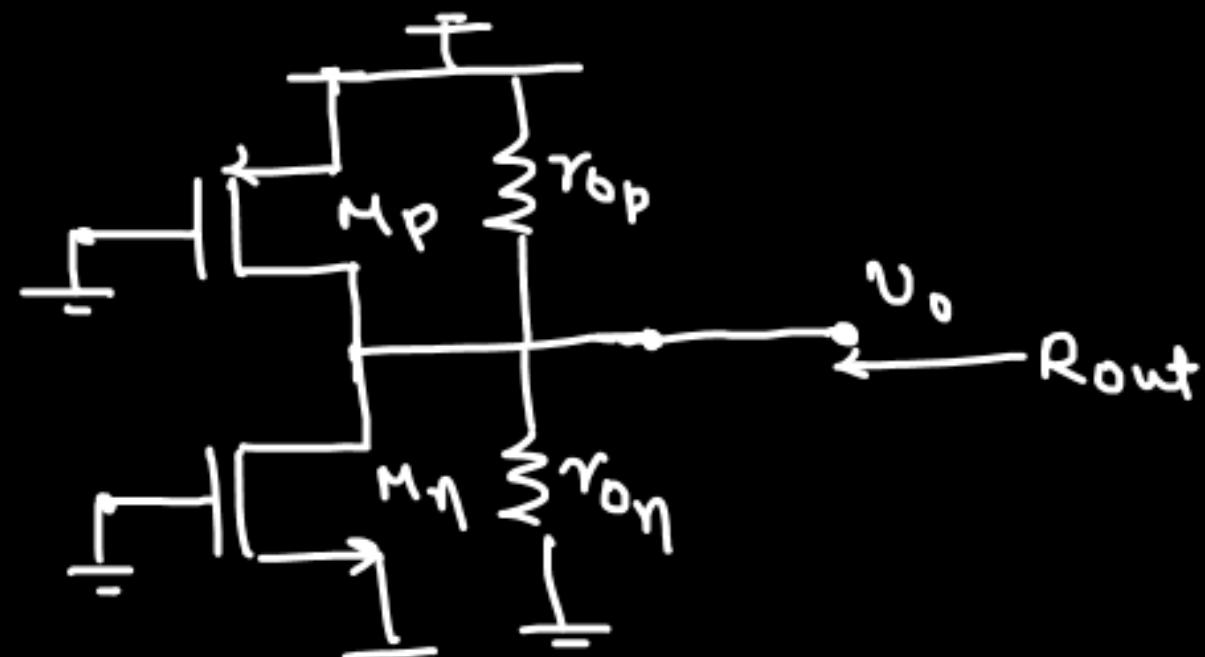

$$R_{out} = r_{o_p} \parallel r_{o_n}$$

w

Q. For a n-channel enhancement type MOS,

$$W/L = 10$$

$$\mu_n C_{ox} = 1 \text{ mA/V}^2$$

$$V_T = 1 \text{ V}$$

$$V_{GS} = 2 - \sin(2t) \text{ V}$$

$$V_{DS} = 1 \text{ V}$$

max<sup>m</sup> value of drain to source current = ?

(a) 40 mA

(b) 20 mA

(c) 15 mA

(d) 5 mA

$$\rightarrow V_{GS} = 2 - \sin(2t) \vee \{ 1 < V_{GS} < 3 \}$$

$$V_{DS} = 1V$$



more  $V_{GS}$   $\Rightarrow$  more  $I_D$

$$(I_D)_{\max} = ?$$

@  $(V_{GS})_{\max} \Rightarrow (I_D)_{\max}$

$$(V_{GS})_{\max} = 2 - (-1) = 3V$$
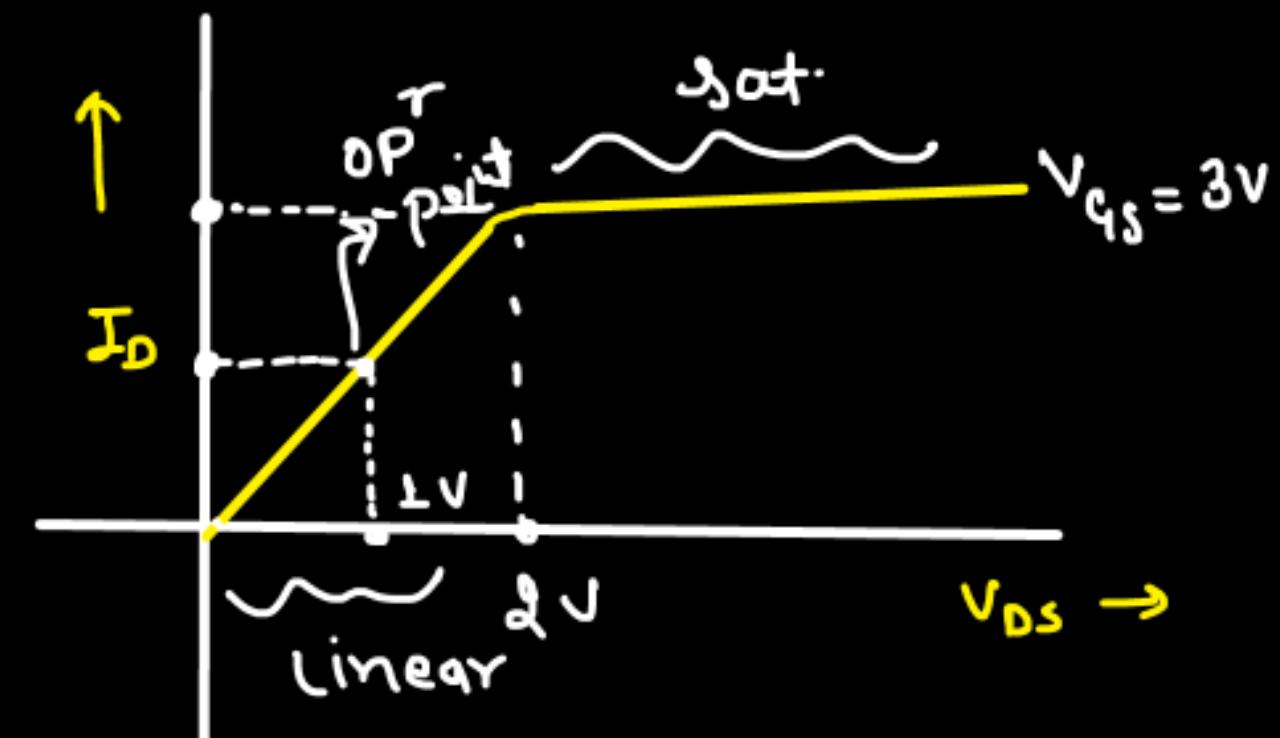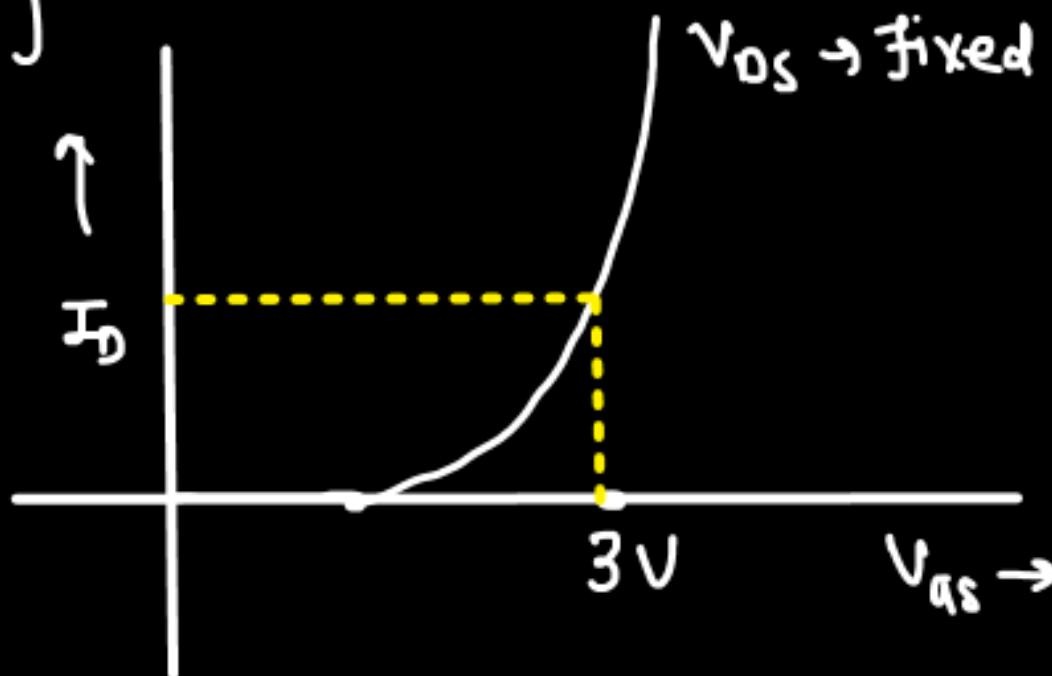
$$(I_D)_{\max} = \frac{1m \times 10}{2} (3-1)^2 = 20mA \quad \times$$



$$(V_{GS})_{max} = 3V$$

$$V_{DS} = 1V$$

$$V_T = 1V$$

$$V_{OV} = 3 - 1 = 2V$$


$V_{DS} < V_{OV} \Rightarrow$  Mos is working in linear region for  
 $\max V_{GS}$

$$(I_D)_{max} = 10m \left[ (2)(1) - \frac{1^2}{2} \right]$$


$$(I_D)_{max} = 15mA$$

Ans.

Q.

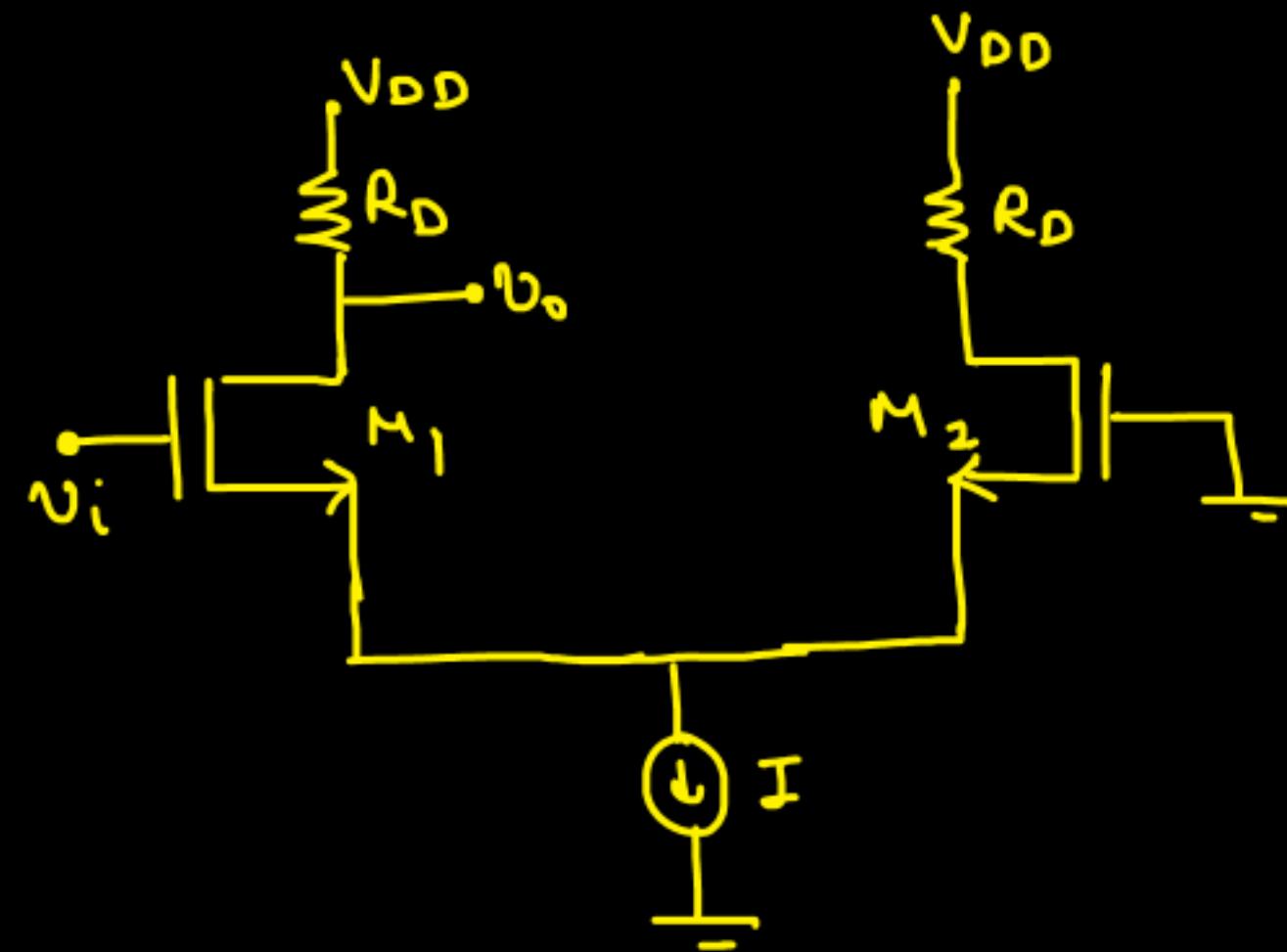

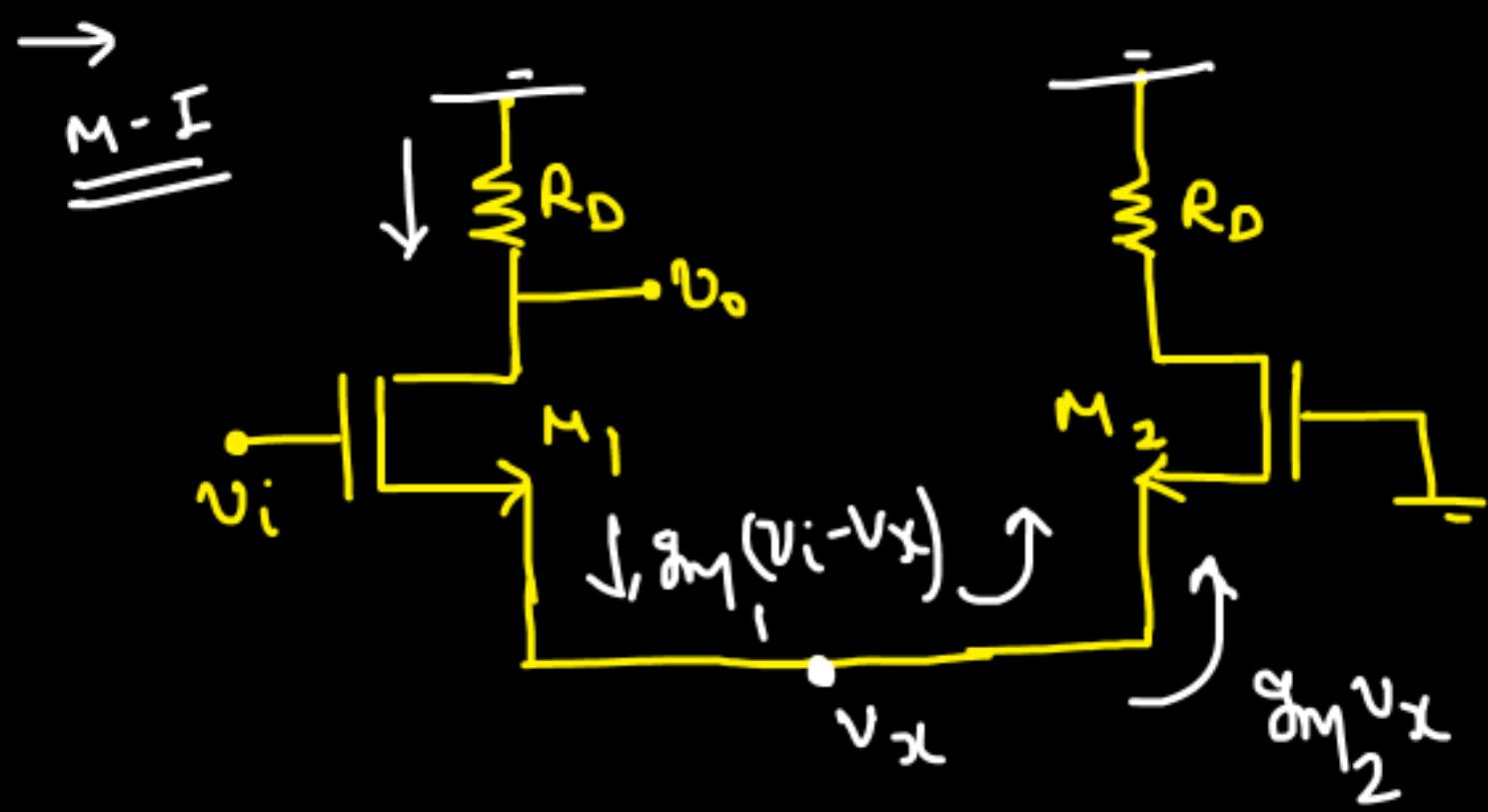Take  $\lambda = 0$   
Find small signal  
Voltage gain  $\frac{v_o}{v_i}$ .



$$g_{M_1}(v_i - v_x) = g_{M_2} v_x$$

$$v_x = \frac{g_{M_1}}{g_{M_1} + g_{M_2}} v_i$$

$$\frac{v_o}{v_i} = ?$$


$$v_o = -g_{M_1} R_D (v_i - v_x)$$

$$v_o = -g_{M_1} R_D \left( v_i - \frac{g_{M_1}}{g_{M_1} + g_{M_2}} v_i \right)$$


$$v_o = -g_{M_1} R_D \left[ \frac{g_{M_2}}{g_{M_1} + g_{M_2}} \right] v_i$$

$$\frac{v_o}{v_i} = -\frac{g_{M_1} g_{M_2}}{g_{M_1} + g_{M_2}} R_D$$

M-II

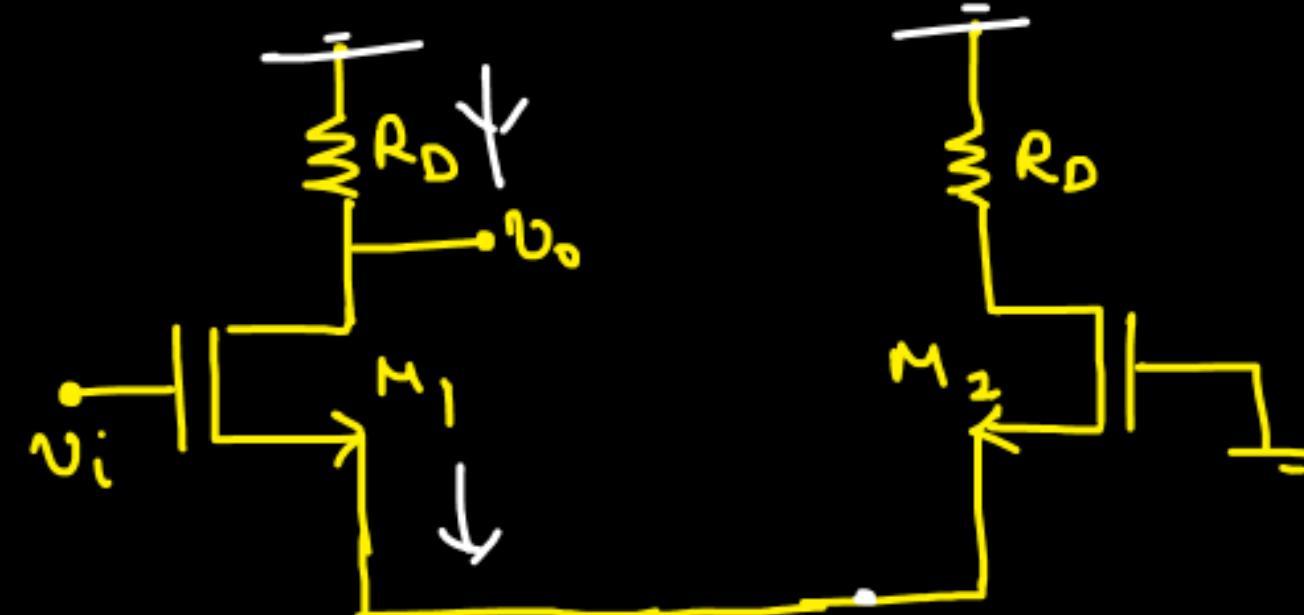

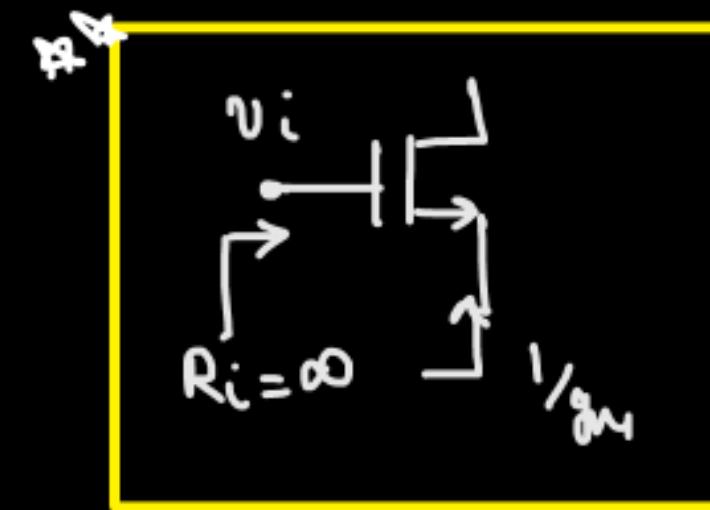
$$-\frac{v_i}{\frac{1}{g_m_1} + \frac{1}{g_m_2}} R_D = v_o$$



$$\frac{v_o}{v_i} = -\frac{g_m_2 g_m_1}{g_m_2 + g_m_1} R_D$$
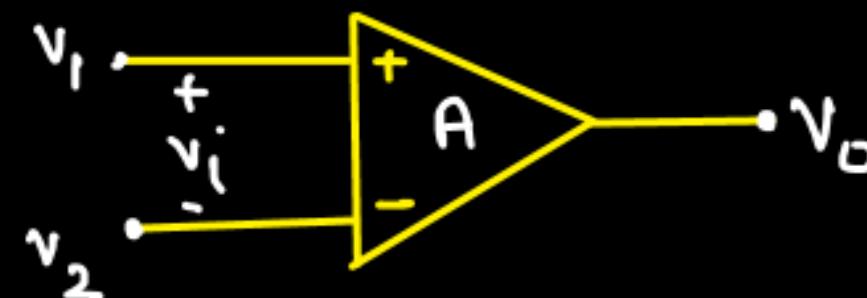
## ⇒ Building 2-stage OP-Amp:-

\* What is OP-Amp? (operational amplifier)




$$v_0 = A(v_+ - v_-)$$

$$v_0 = A(v_1 - v_2)$$


$$v_0 = A v_i$$

High

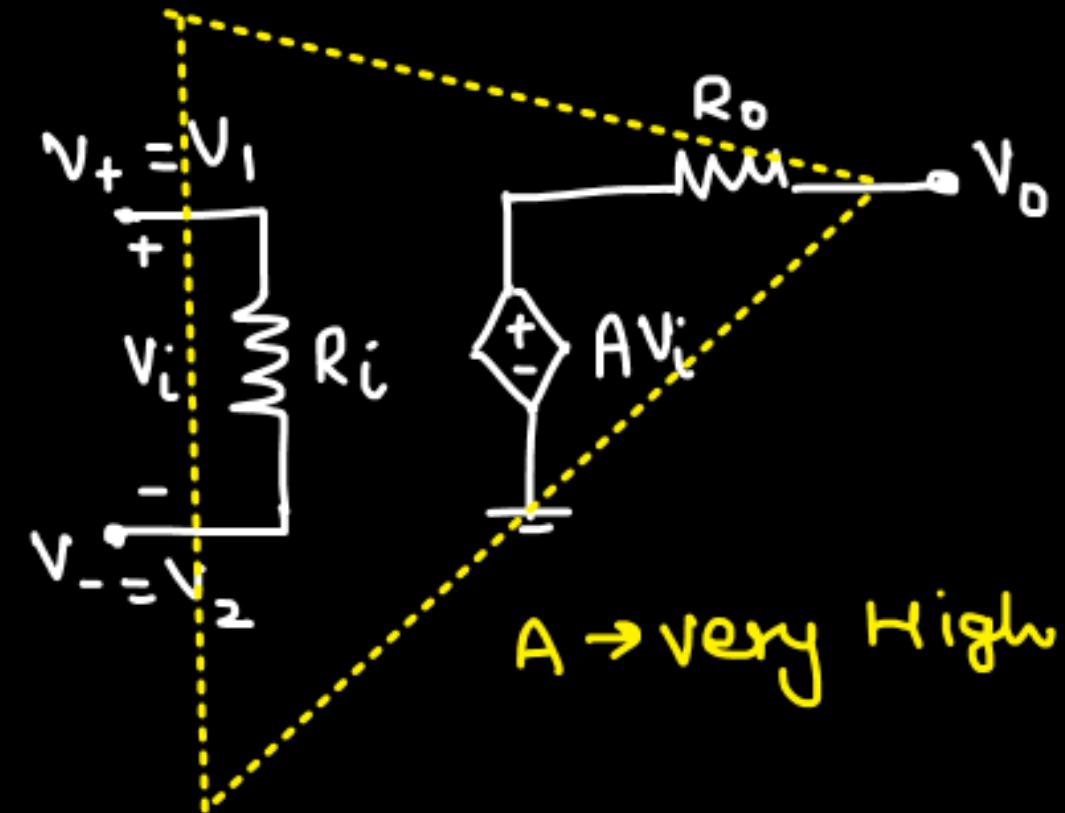

$R_i \rightarrow \text{very High } (\infty)$

$R_o \rightarrow \text{very low } (0)$

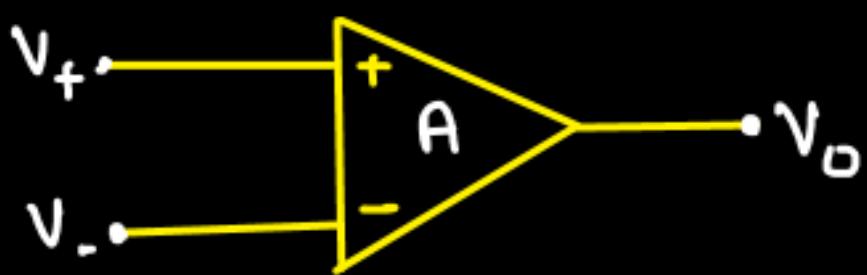

$\star \star$   $V_o = A(V_+ - V_-)$


$$\begin{array}{l} V_+ \uparrow \Rightarrow V_o \uparrow \\ V_- \uparrow \Rightarrow V_o \downarrow \end{array}$$

Target :-

Designing High input impedance, Low o/p impedance  
and a High gain amplifier.


( double ended, single ended o/p )  
i/p

⇒ What we have studied?

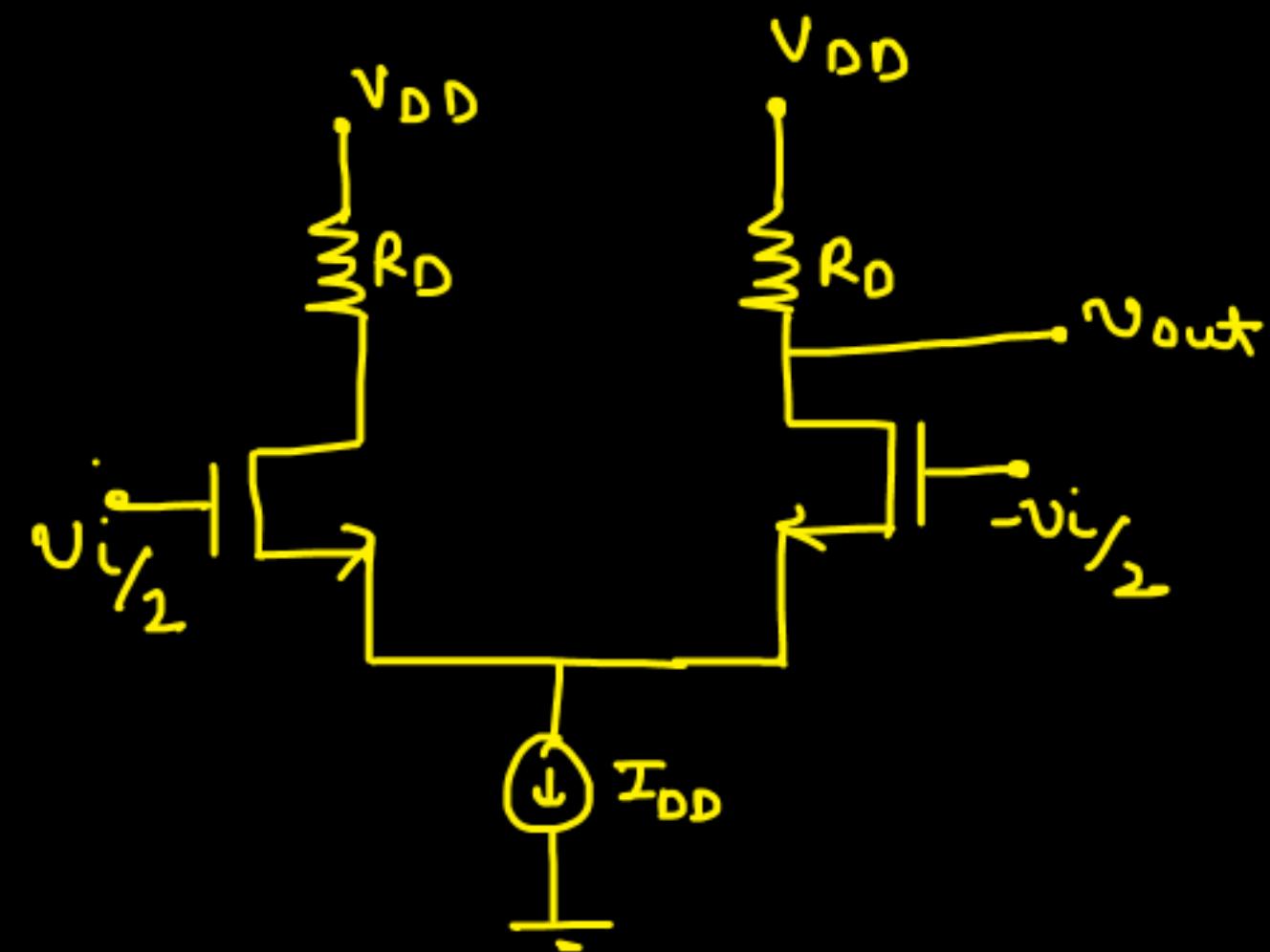

- (i) gain = ? =  $\frac{v_o}{v_i}$
- (ii) i/p impedance = ?
- (iii) o/p impedance = ?

(ii) gain:-

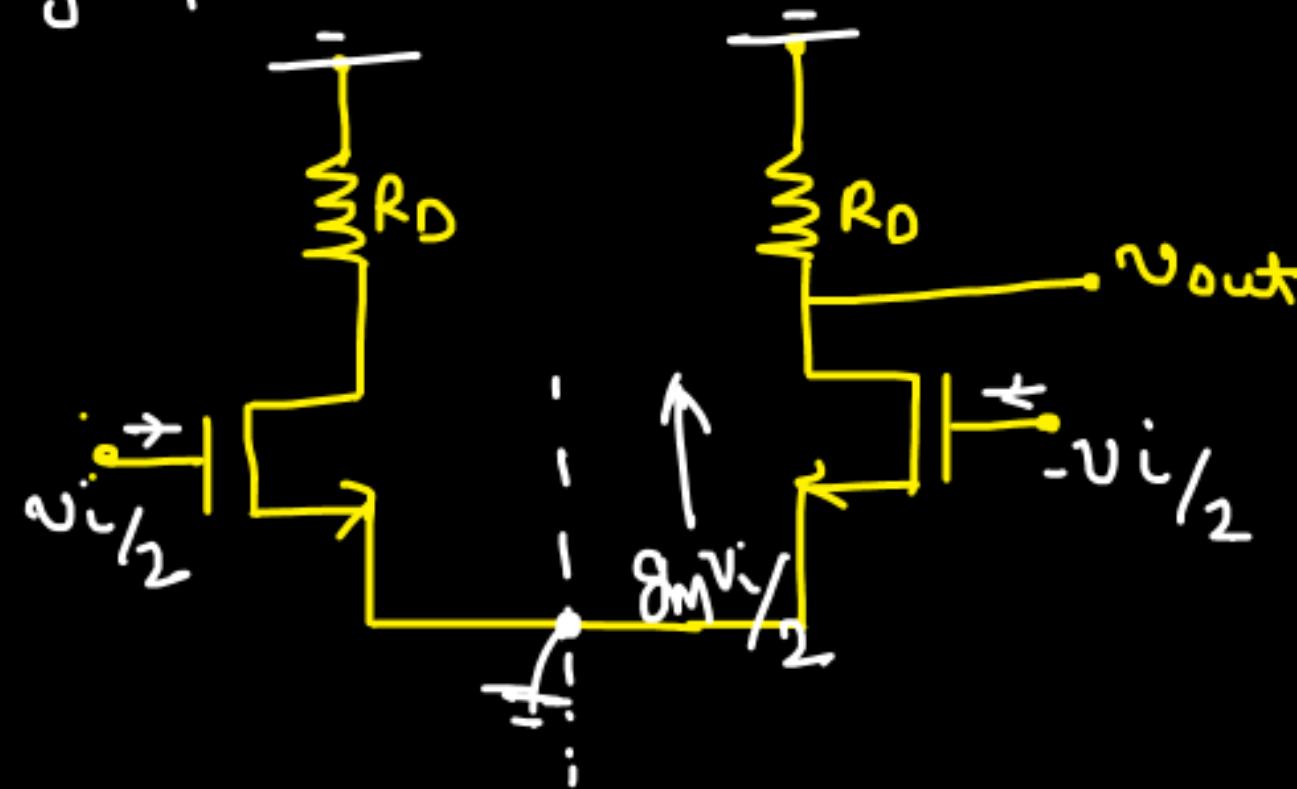

$$V_0 = \frac{g_m V_i}{2} R_D$$


$$\frac{V_0}{V_i} = \frac{g_m R_D}{2} \Rightarrow \text{NOT VERY HIGH } (x)$$

(iii) Input Impedance:-

$$\frac{V_i}{I_i} = \frac{V_i}{0} = \infty \Rightarrow \text{High Input Impedance (V)}$$

(iii) O/P impedance:-


(Let's take  $\lambda \neq 0$ )

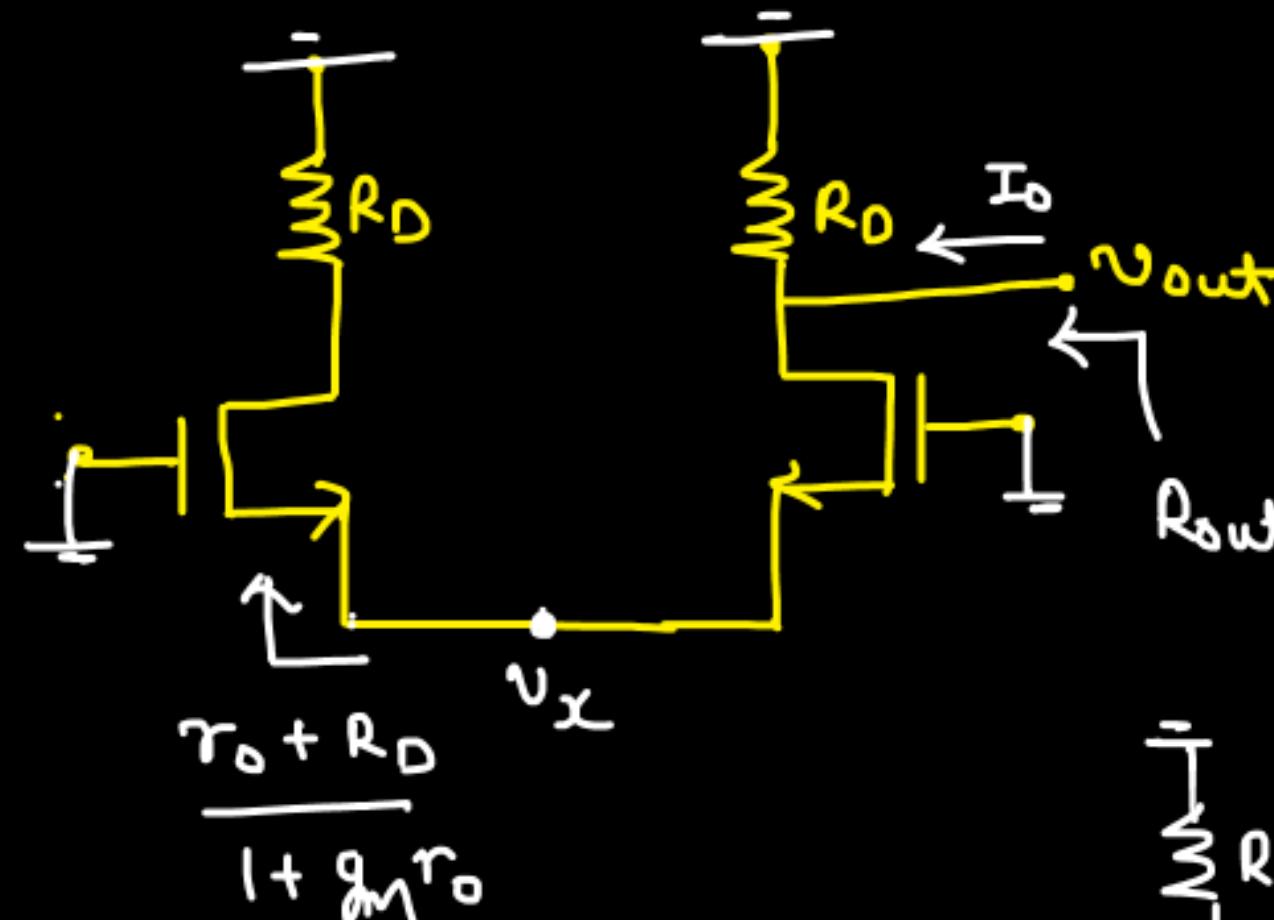

$$R_{out} = R_f || R_D$$

$$R_{out} = (2r_o + R_D) || R_D$$

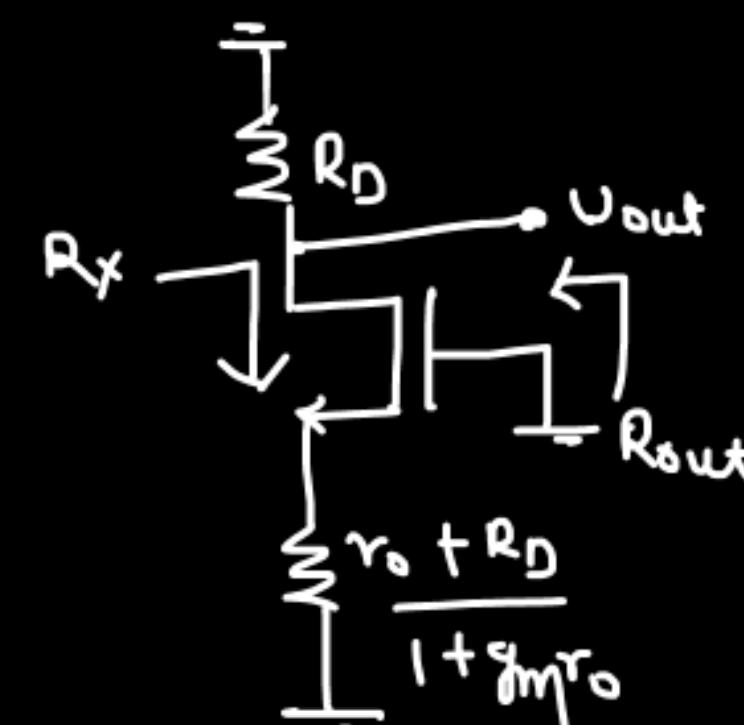
$$\approx R_D \Rightarrow \text{low} (\checkmark)$$



$$\begin{aligned}
 R_X &= g_m r_o \left( \frac{r_o + R_D}{1 + g_m r_o} \right) + r_o + \left( \frac{r_o + R_D}{1 + g_m r_o} \right) \\
 &= \frac{r_o + R_D}{1 + g_m r_o} [1 + g_m r_o] + r_o
 \end{aligned}$$

$$R_X = 2r_o + R_D$$

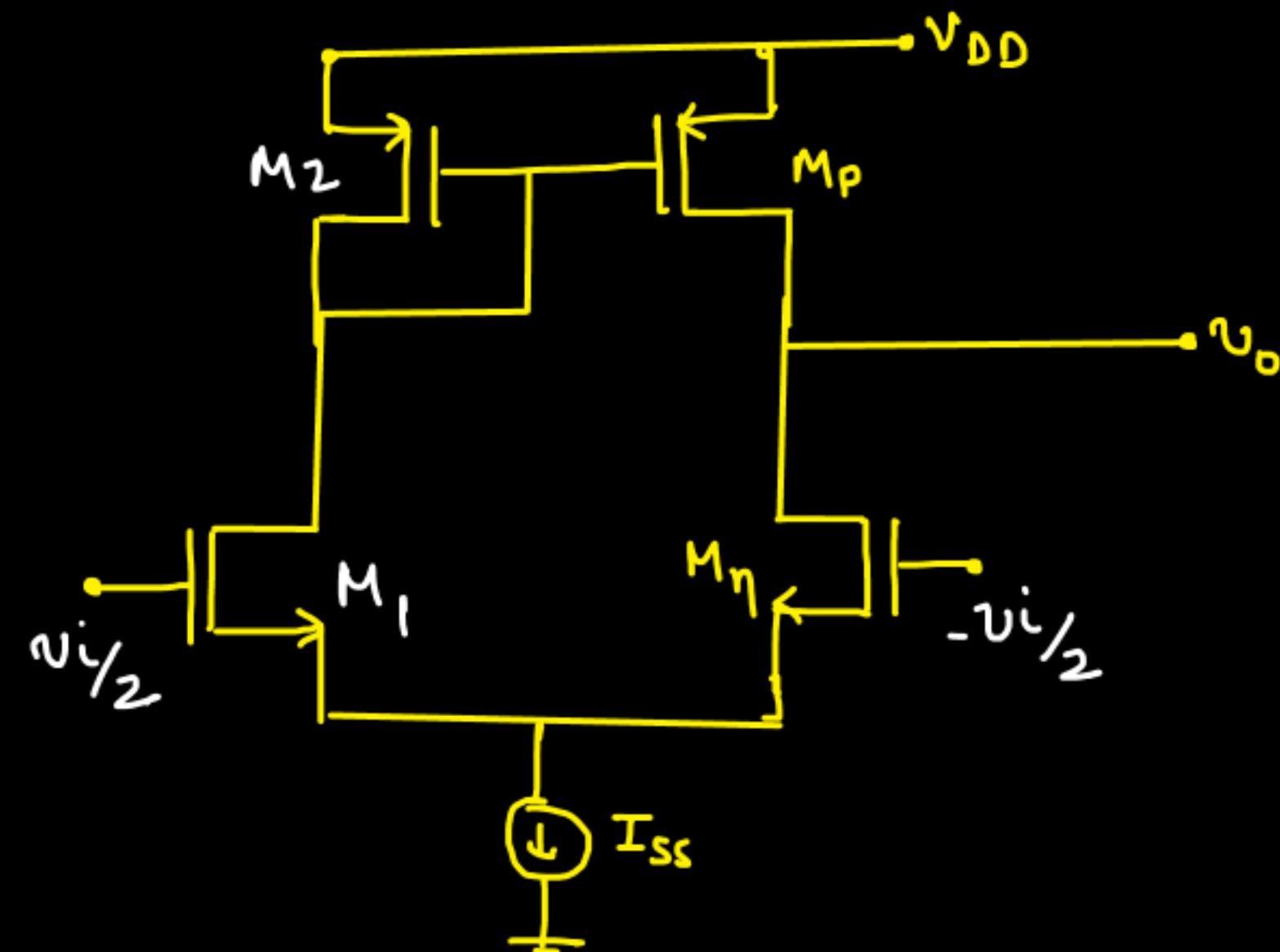
## Differential Amplifier with active load :-



For ease of calculation, we will take  $\lambda = 0$  for  $M_1$  &  $M_2$   
 $\lambda \neq 0$  for  $M_n$  &  $M_p$

Voltage Gain :-


$$\underline{g_m \rightarrow}$$

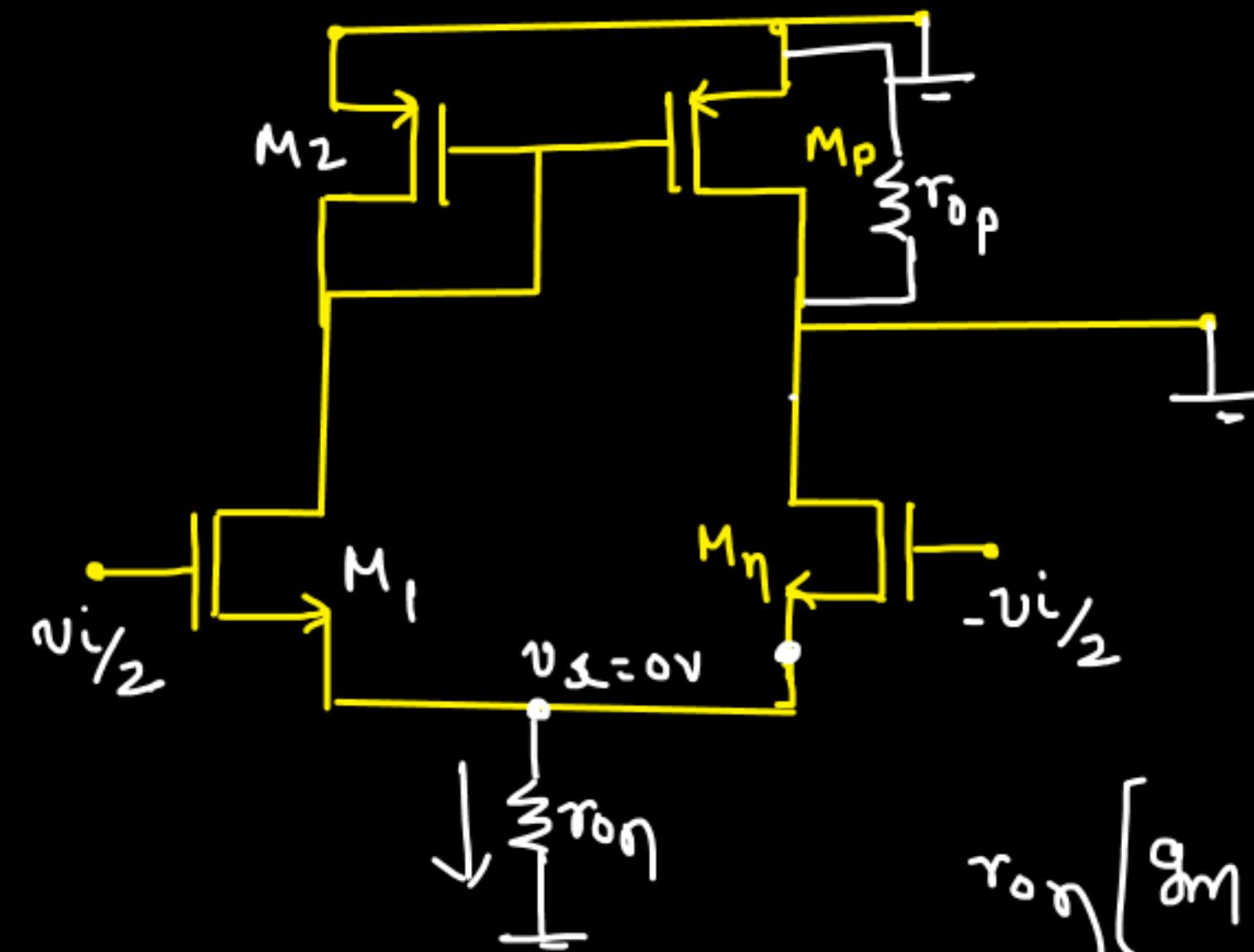

$$r_{o\eta} \left[ g_m \left( \frac{v_i}{2} - v_x \right) + g_m \left( -\frac{v_i}{2} - v_x \right) \right] = v_x$$

$$-2g_m r_{o\eta} v_x = v_x$$
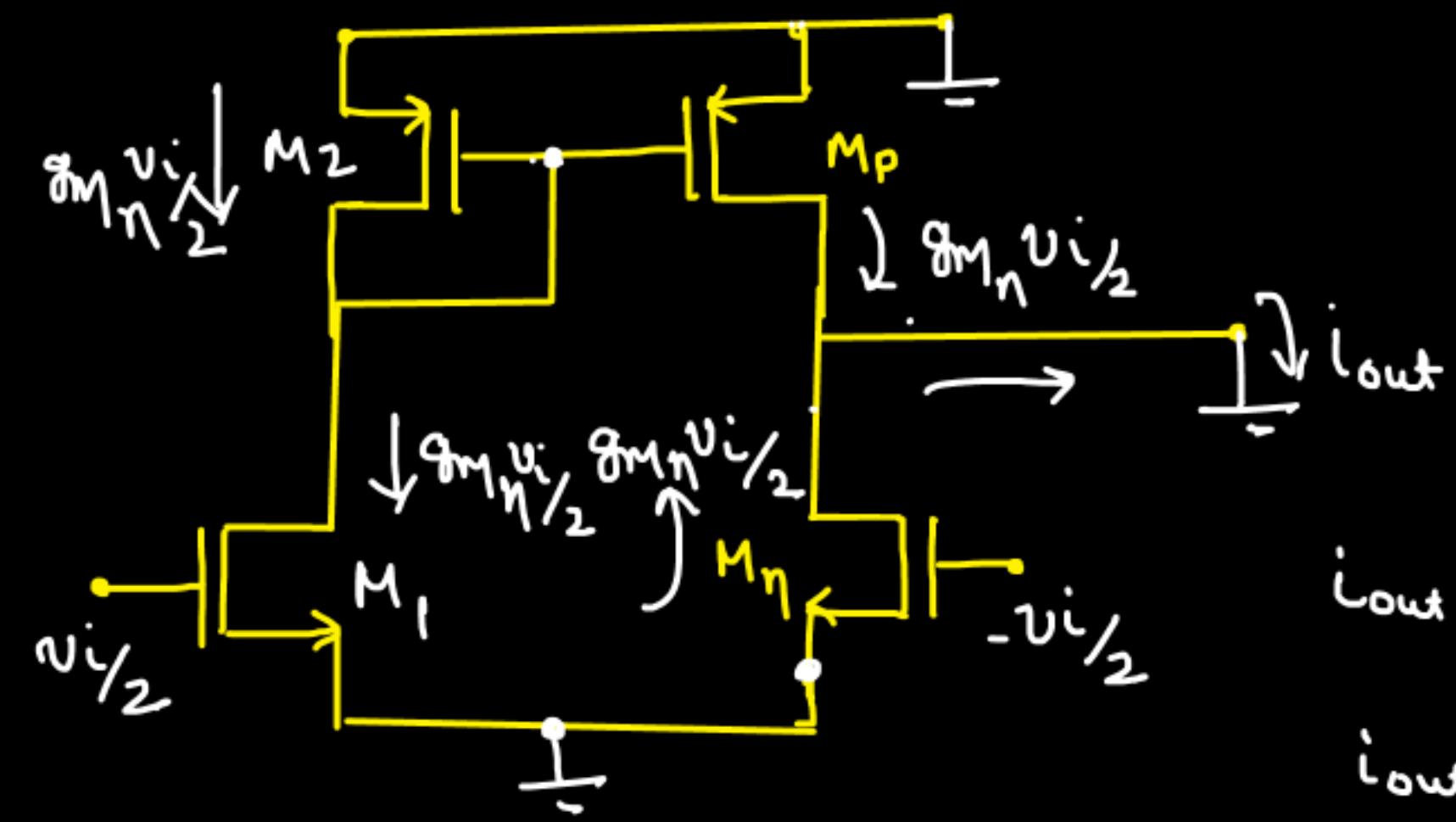
$$v_x [1 + 2g_m r_{o\eta}] = 0 \Rightarrow v_x = 0$$





$$i_{out} = g_{M_n} v_{i/2} + g_{M_p} v_{i/2}$$

$$i_{out} = g_{M_n} v_i$$


$$G_m = g_{M_n}$$

R<sub>out</sub> :-

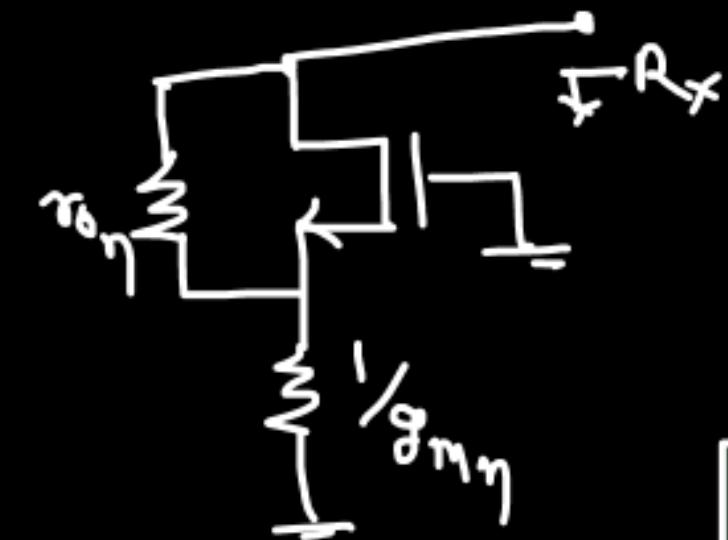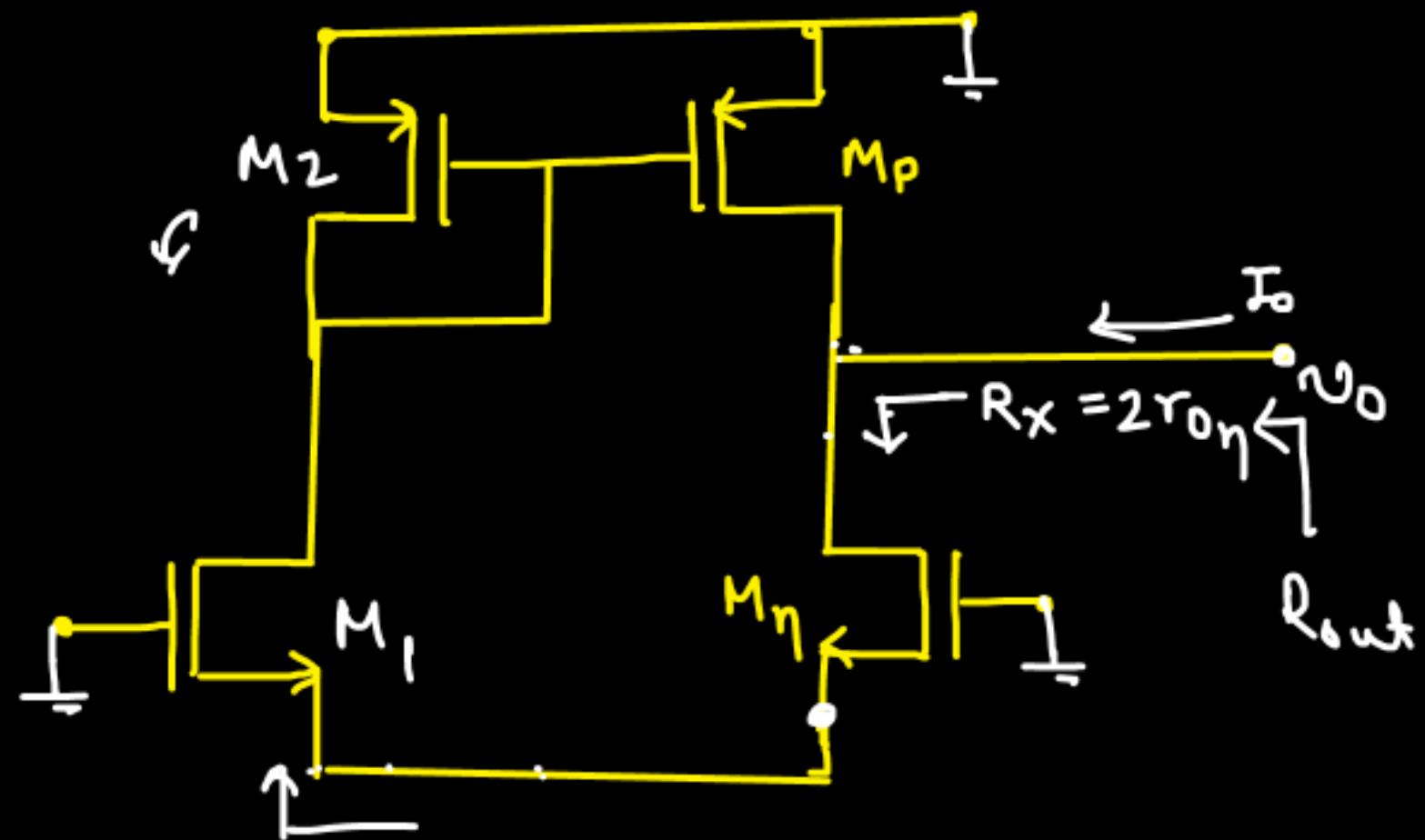

$$R_x = g_{mn\eta} r_{0\eta} \times \frac{1}{g_{mn\eta}} + r_{0\eta} + \frac{1}{g_{mn\eta}}$$
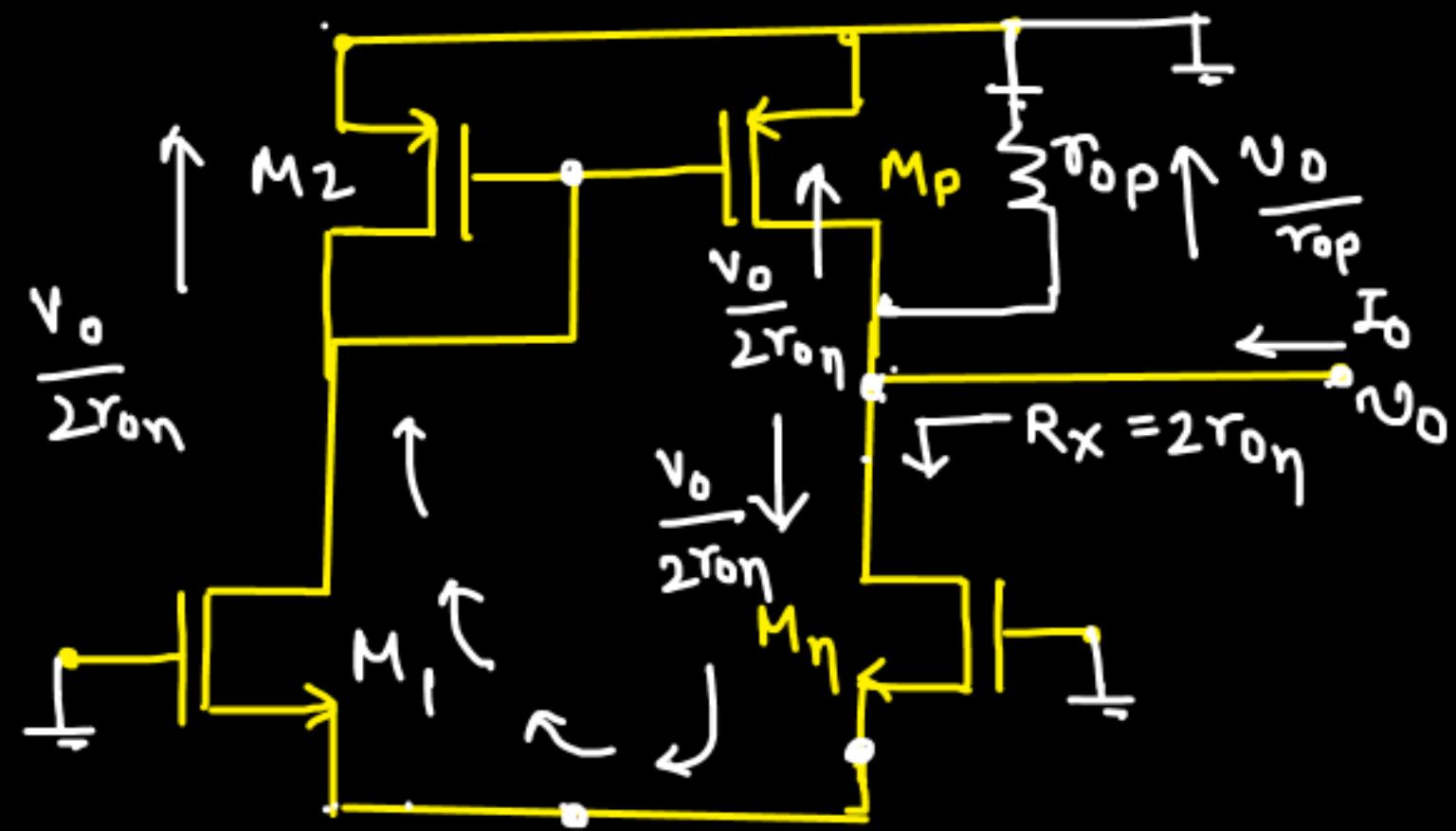
$$R_x = 2r_{0\eta} + \frac{1}{g_{m\eta}} \approx 2r_{0\eta}$$



$$\frac{V_o}{r_{0P}} + \frac{V_o}{2r_{0\eta}} + \frac{V_o}{2r_{0\eta}} = I_o \quad \Rightarrow \quad \frac{V_o}{r_{0P}} + \frac{V_o}{r_{0\eta}} = i_o$$

$$\boxed{\frac{V_o}{i_o} = R_{out} = r_{0P} \parallel r_{0\eta}}$$


$\approx$  High (Not Desired)

$$A_V = g_m n (r_{op} \parallel r_{on}) \Rightarrow \text{High}$$

(desired)


Input impedance  $R_i = \infty \Rightarrow \text{High}$   
(desired)

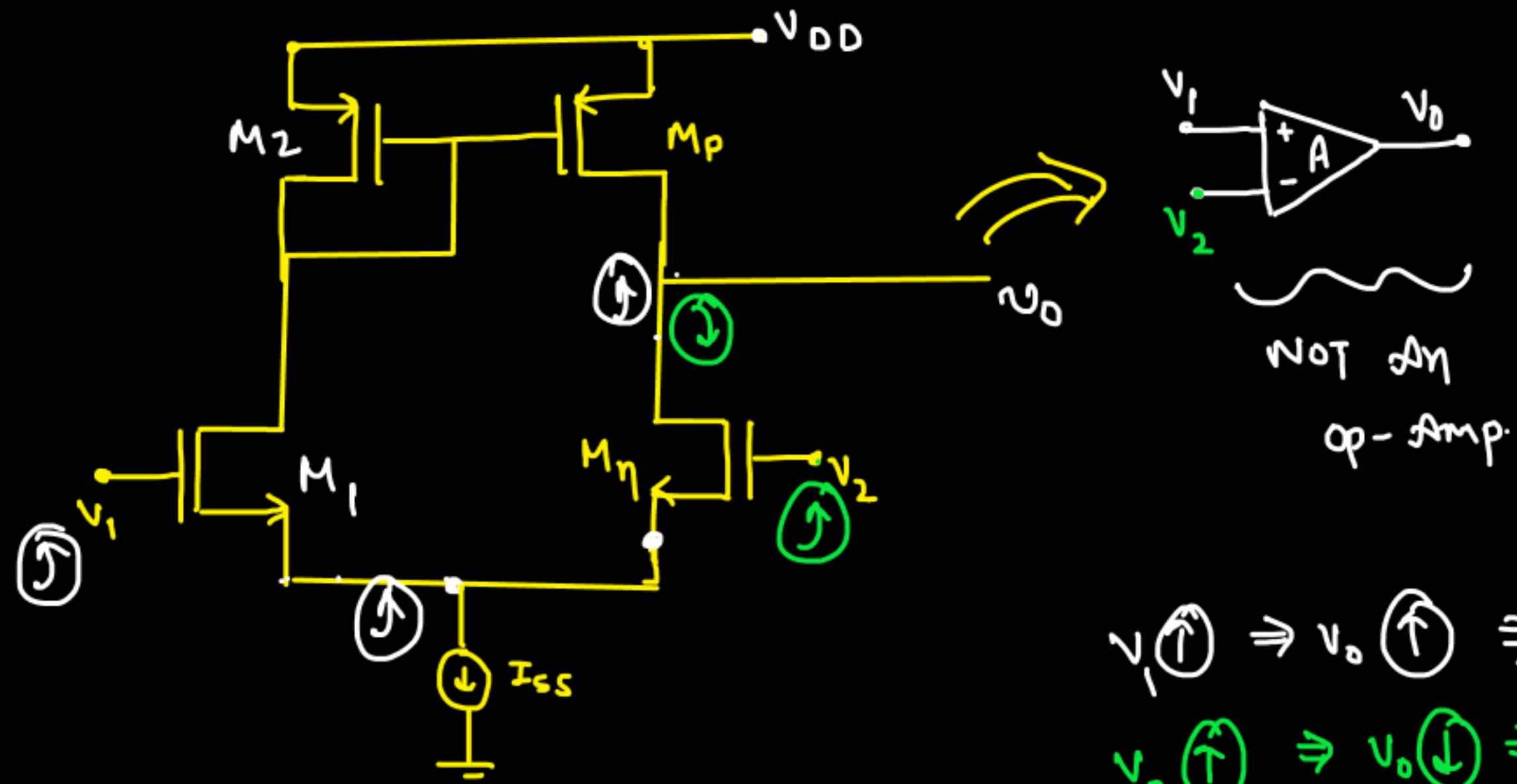Matter of concern  $\Rightarrow$  o/p impedance




$$v_1 \uparrow \Rightarrow v_0 \uparrow \Rightarrow v_1 = v_+$$
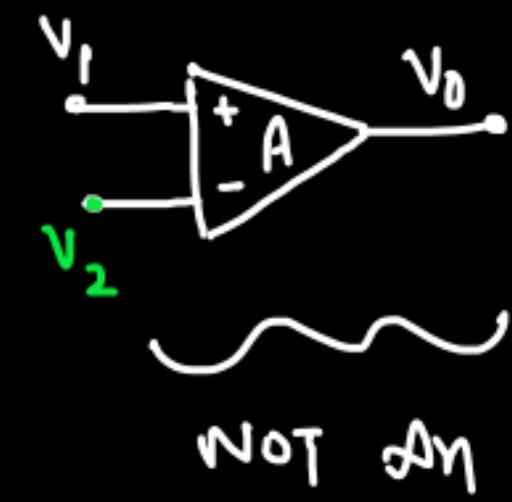
$$v_2 \uparrow \Rightarrow v_0 \downarrow \Rightarrow v_2 = v_-$$




NOT AN  
OP-AMP.

	Gain	o/p impedance
① Common Source	$-g_m r_o$	$r_o \rightarrow \text{High}$
② Common Gate	$1 + g_m r_o$	$r_o \rightarrow \text{High}$
③ Common drain	$\frac{g_m r_o}{1 + g_m r_o} \approx 1$	$r_o    \frac{1}{g_m} \approx \frac{1}{g_m} \rightarrow \text{low}$

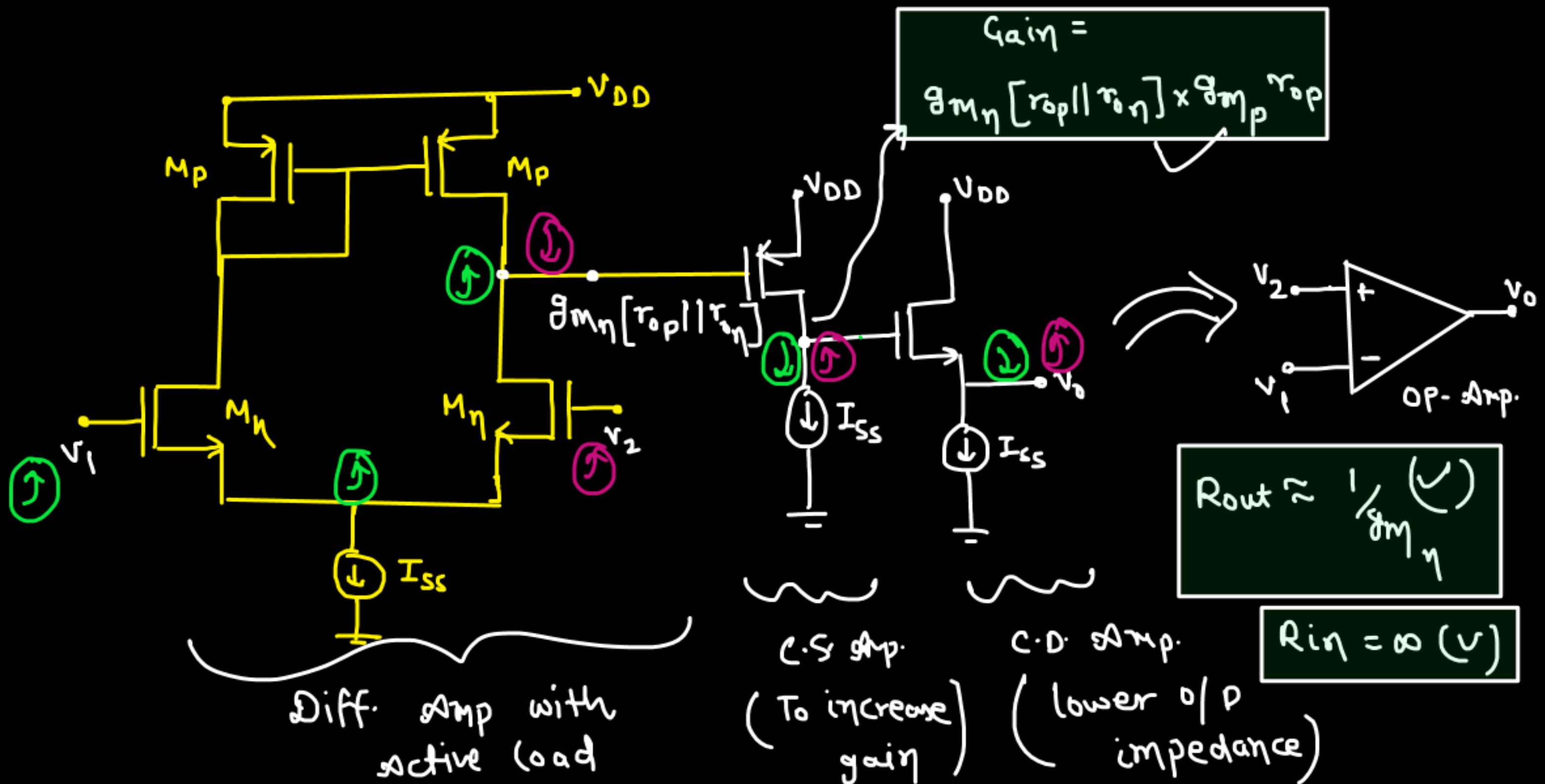

Final design :-

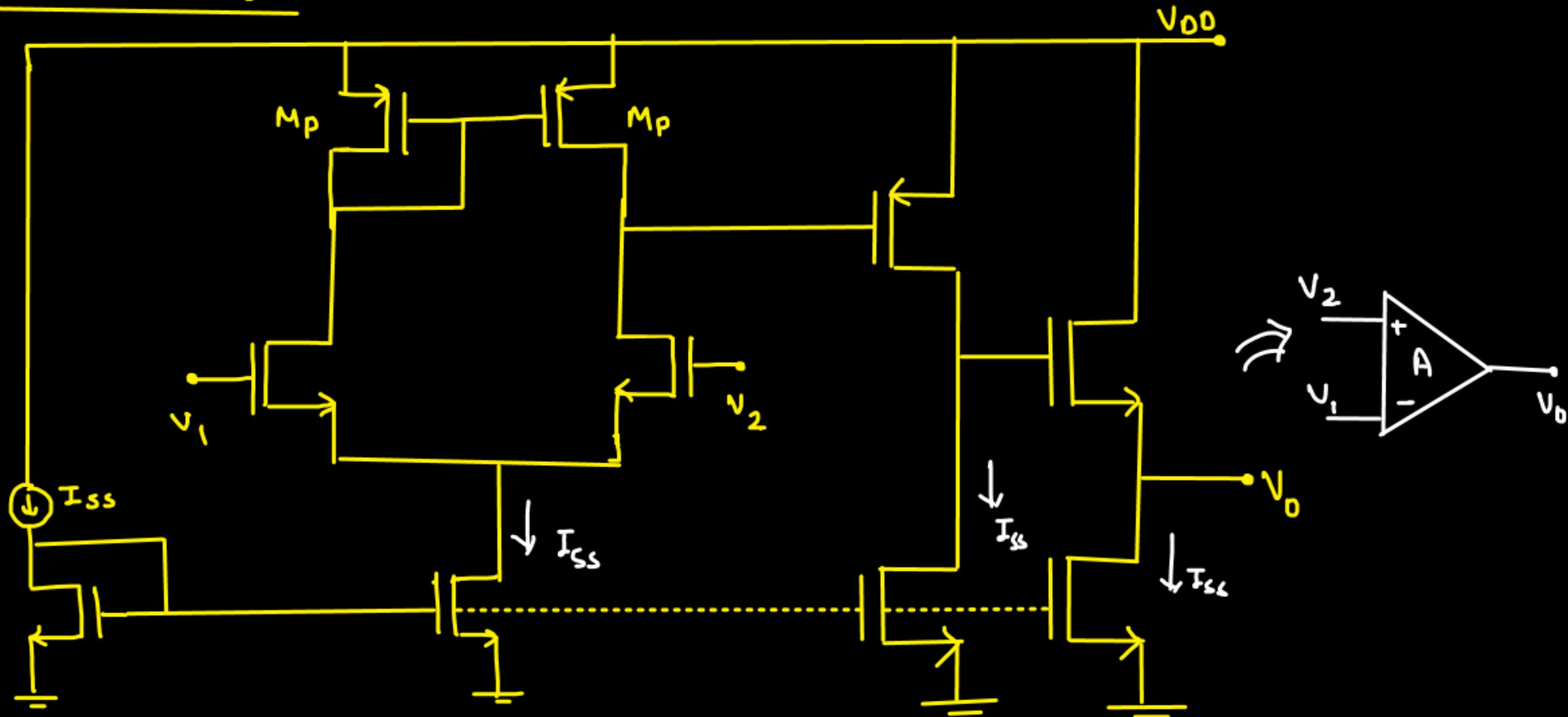



## Some Basics of OP-Amp:-

$$V_o = A V_d$$

$$-V_{sat} < V_o < +V_{sat}$$

$$-V_{sat} < A V_d < +V_{sat}$$
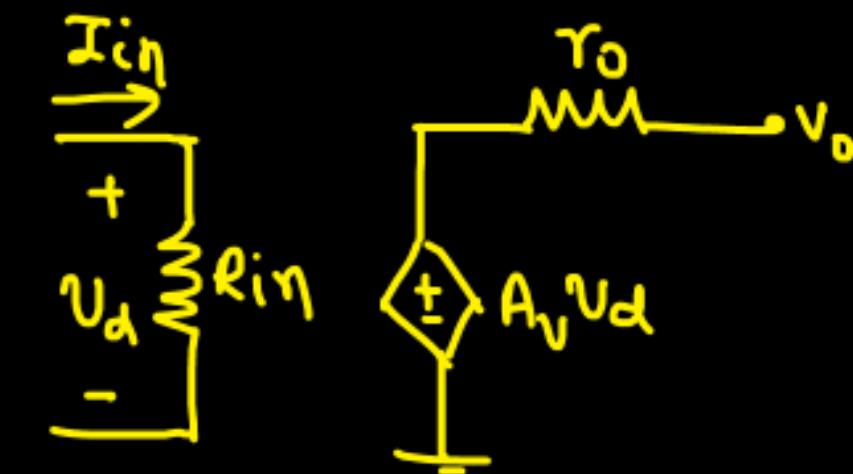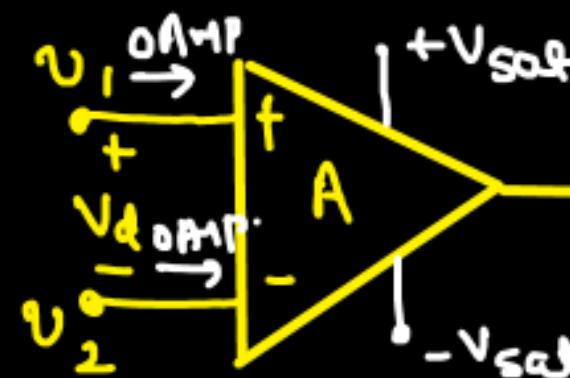
$$\frac{-V_{sat}}{A} < V_d < \frac{+V_{sat}}{A}$$



$$V_o = A (V_1 - V_2)$$

$$V_+ = V_1 \uparrow \Rightarrow V_o \uparrow$$

$$V_- = V_2 \uparrow \Rightarrow V_o \downarrow$$

\* For an OP-amp, o/p can never go above tve Sat. voltage and can never go below -ve sat. voltage

For an ideal op-amp  $\Rightarrow$

$$R_{in} = \infty$$

$$I_{in} = 0$$

$$V_o = 0$$

$$A_v = \infty$$

$$CMRR = \infty$$

$$\text{slew rate} = \infty$$

Let,  $A = 10^3 \text{ v/V}$  ;  $\pm V_{\text{sat}} = \pm 5 \text{ v}$

(i)  $V_d = 1 \text{ mV}$

$$V_o = AV_d = 10^3 \times 1 \text{ mV} = 1 \text{ V}$$

(ii)  $V_d = -3 \text{ mV}$

$$V_o = -3 \text{ mV} \times 10^3 = -3 \text{ V}$$

(v)  $V_d = -6 \text{ mV}$

(iii)  $V_d = -5 \text{ mV}$

$$V_o = -5 \text{ mV} \times 10^3 = -5 \text{ V}$$


$$\begin{aligned} V_o &= -6 \text{ mV} \times 10^3 \\ &= -6 \text{ V} \times \\ &\Rightarrow -5 \text{ V} \end{aligned}$$

(iv)  $V_d = 7 \text{ mV}$

$$V_o = 7 \text{ mV} \times 10^3 = 7 \text{ V} \times \Rightarrow 5 \text{ V}$$

$$V_o = A V_d$$


$$\frac{V_o}{V_d} = A$$

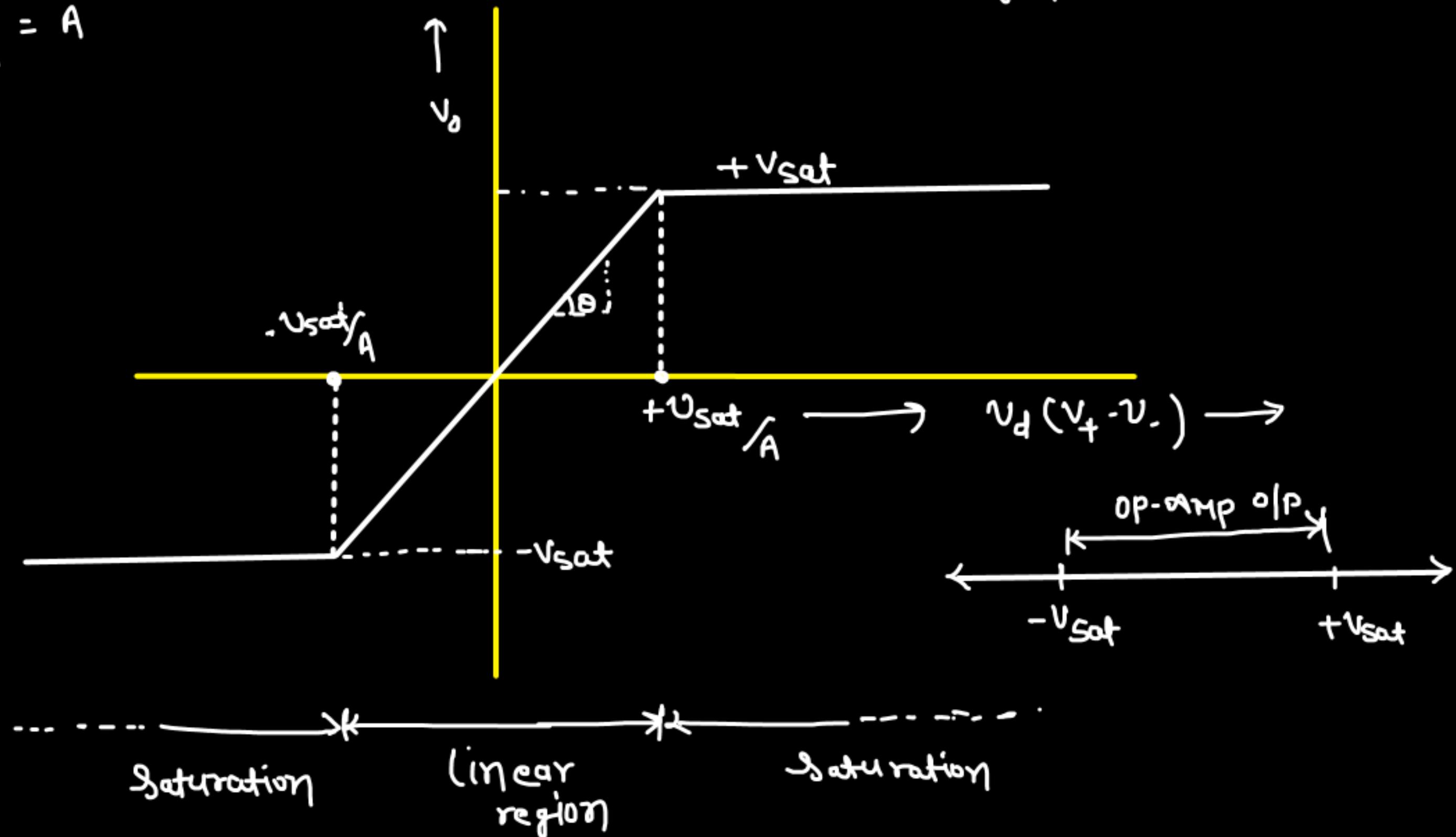

## Feedback:-

Taking a fraction of the o/p of an amplifier and connecting it back to the i/p. This fed-back signal can be connected in a way that it either adds to the normal input or subtracts from it.


## System w/o any feedback:-

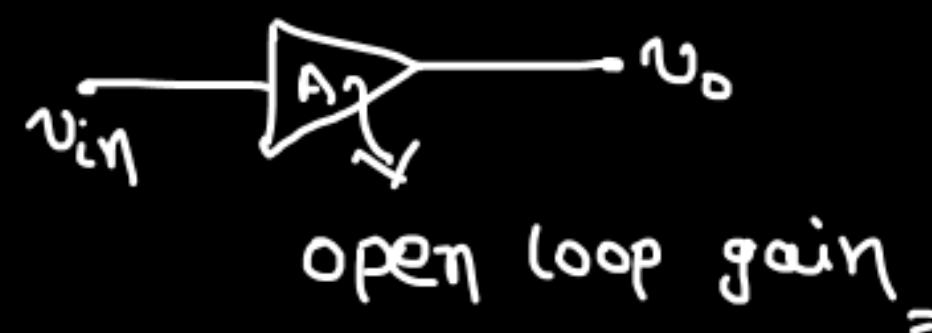

open loop gain =

$$v_o = A v_{in}$$

## ① Positive feedback :-

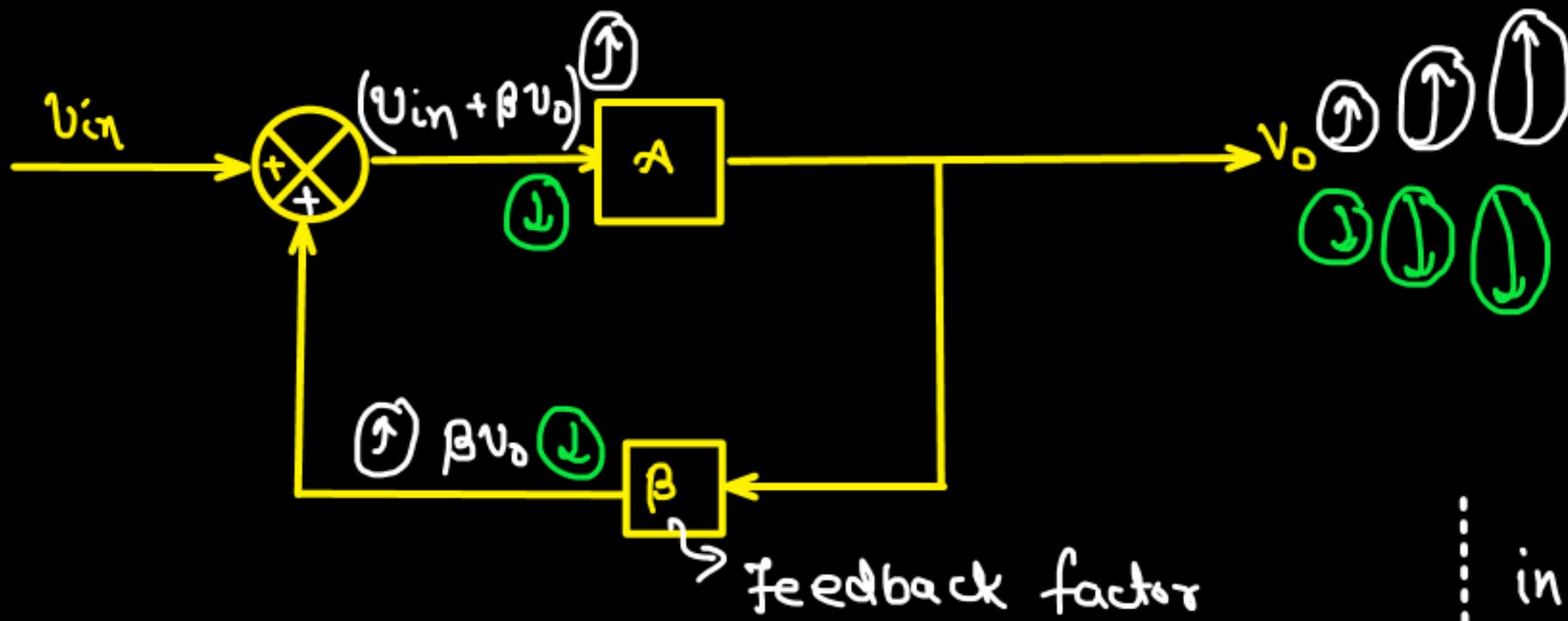

$$V_o = A(V_{in} + \beta V_o)$$

$$V_o - A\beta V_o = AV_{in}$$


$$\frac{V_o}{V_{in}} = \frac{A}{1-A\beta}$$

→ Closed loop gain

in positive f/b, if o/p increases, then it keeps on increasing and results in unstable o/p.

positive f/b s/s are unstable.



## ② Negative feedback:-

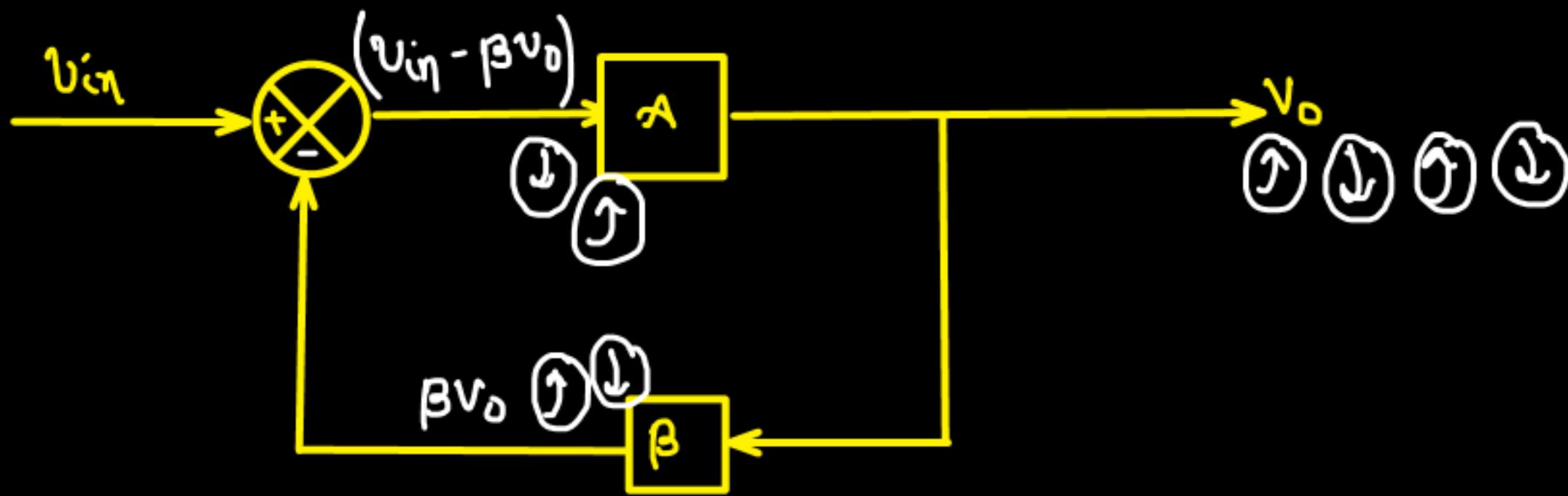

$$(V_{in} - \beta V_o)A = V_o$$

$$\frac{V_o}{V_i} = \frac{A}{1 + A\beta} \text{ closed loop gain}$$

in negative f/b, you get  
a stable o/p.

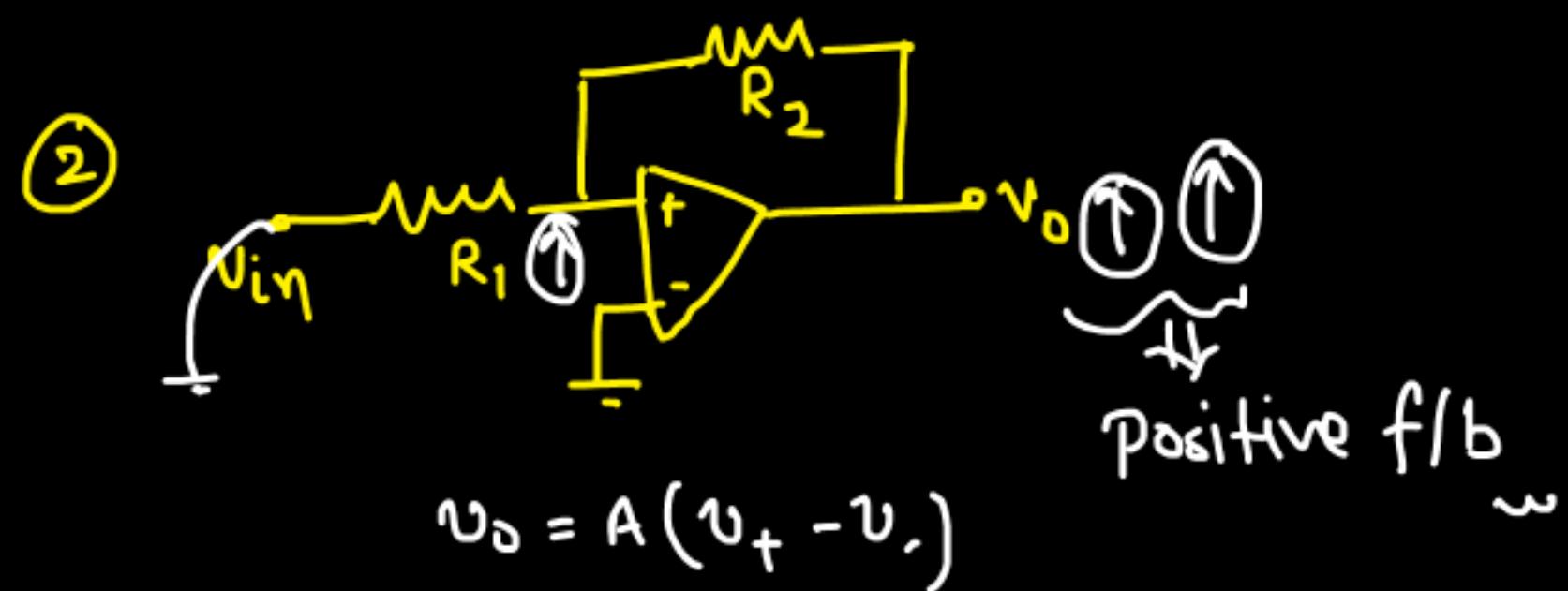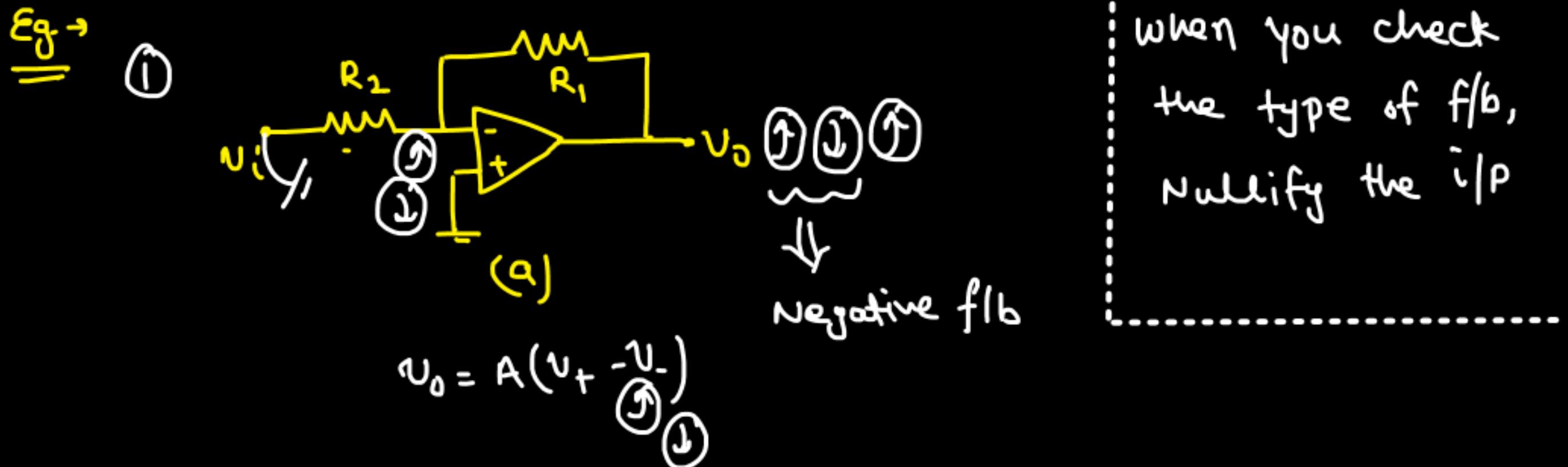

When you check  
the type of f/b,  
nullify the i/p

\* Advantages of feedback:-

1. Gain stability:-




open-loop

$$V_o = A V_{in}$$

Let's assume, your gain  $A = 10^3 \rightarrow 10^4$   
Let;  $V_{in} = 1mV$

$$\begin{aligned} V_o &= A V_{in} \\ &= 1V \rightarrow 10V \end{aligned}$$

## Introducing negative f/b :-

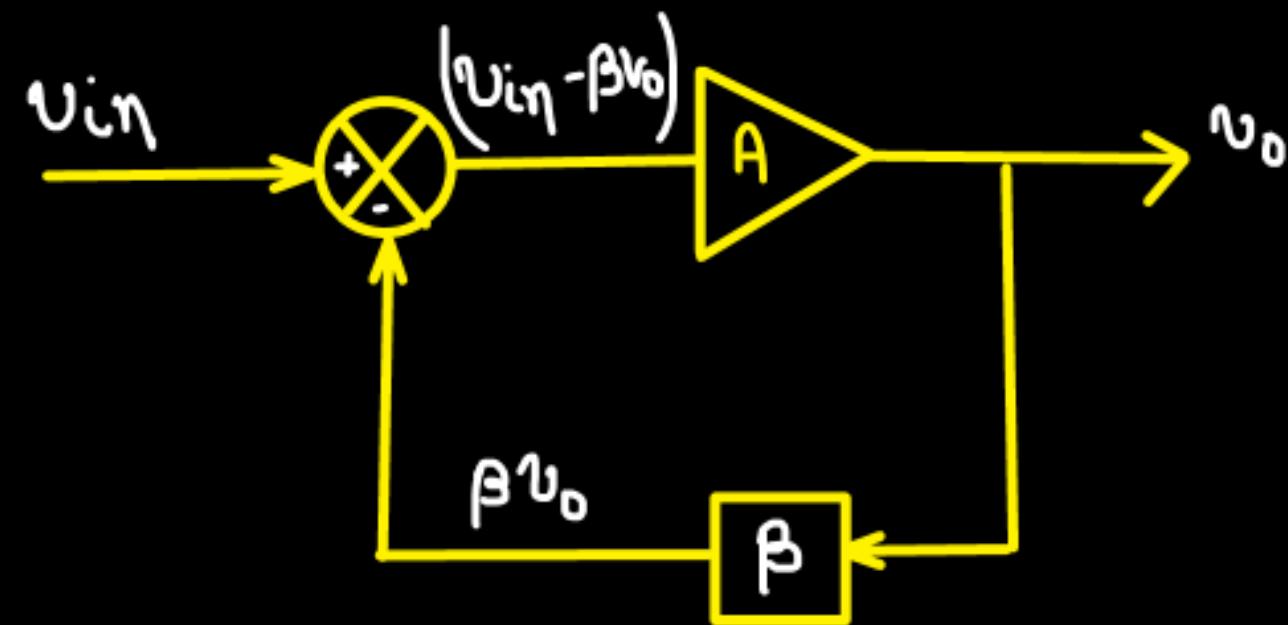

$$v_o = A(v_{in} - \beta v_o)$$

$$\frac{v_o}{v_{in}} = \frac{A}{1 + AB}$$


$\beta$  is designed such that  $A\beta \gg 1$

$$\frac{v_o}{v_{in}} \approx \frac{A}{A\beta} \approx \frac{1}{\beta} \Rightarrow \text{constant}$$

$\Rightarrow$  Here you are getting a constant gain.

Example:-


Before f/b:-

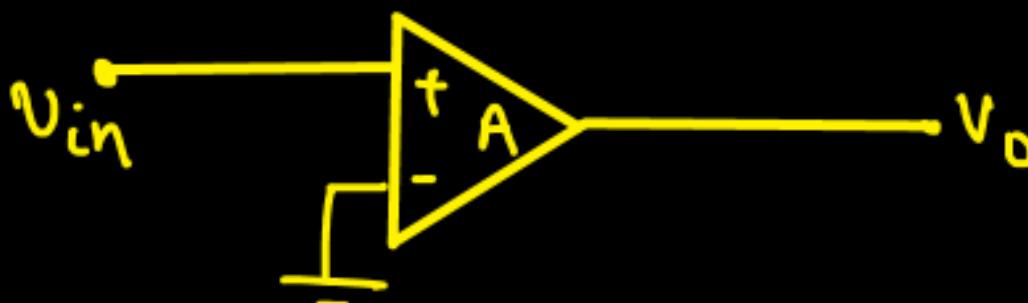

$$V_o = A V_{in}$$

if  $A \rightarrow \text{variable}$ , then  $V_o \rightarrow \text{variable}$

After f/b:-

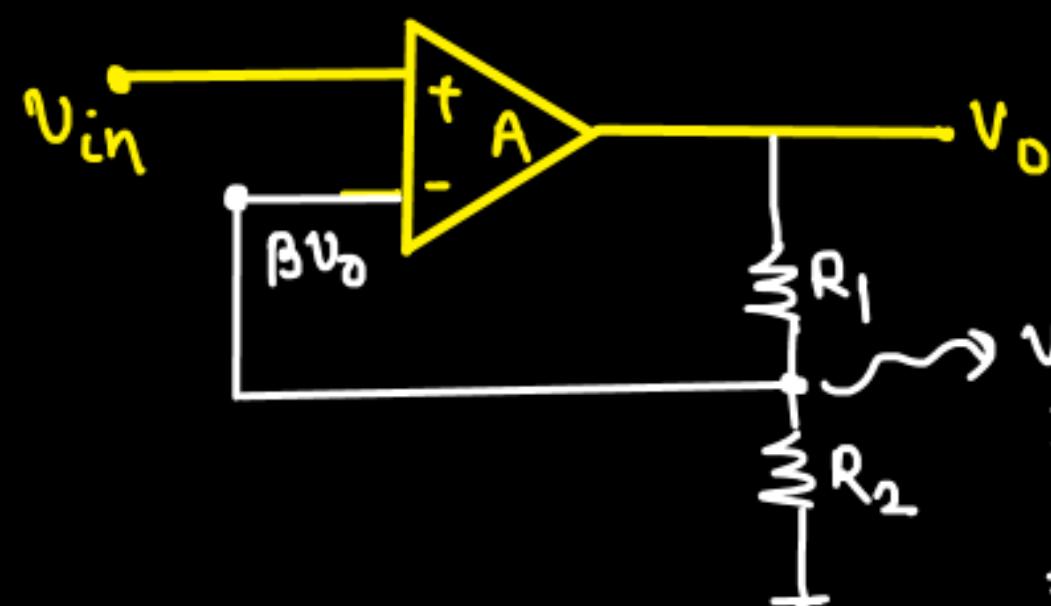

$$\begin{aligned} \frac{V_o R_2}{R_1 + R_2} &= \beta V_o \\ \Rightarrow \beta &= \frac{R_2}{R_1 + R_2} \end{aligned}$$

$$(V_{in} - \beta V_o) A = V_o$$

$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta}$$

$$\frac{V_o}{V_{in}} \approx \frac{1}{\beta} = 1 + \frac{R_1}{R_2}$$

$\Rightarrow$  Loop gain :-

$$(A_v)_{w/o \text{ f/b}} = A \rightarrow \text{open loop gain}$$

$$(A_v)_{\text{with neg f/b}} = \frac{A}{1 - A\beta} \rightarrow \text{closed loop gain}$$

$$A\beta = \text{loop gain}$$

Q. An amplifier is connected in negative f/b. if the percentage change is open loop gain is 10%. then what will be the % change in closed loop gain. Loop gain is 99.

→

$$\text{closed loop gain } A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} \quad \textcircled{1}$$

$$\frac{DA_{OL}}{A_{OL}} \times 100\% = 10\%$$

$$\frac{DA_{OL}}{A_{OL}} = 0.1$$

$$\frac{DA_{CL}}{A_{CL}} = ?$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$$

$$\Delta A_{CL} = \frac{(1 + A_{OL}\beta) \Delta A_{OL} - A_{OL}\beta \Delta A_{OL}}{(1 + A_{OL}\beta)^2}$$

$\beta \rightarrow \text{constant}$

$$\Delta A_{CL} = \frac{\Delta A_{OL}}{(1 + A_{OL}\beta)^2}$$

$$\frac{\Delta A_{CL}}{A_{CL}} = \frac{\Delta A_{OL}}{(1 + A_{OL}\beta)^2} \times A_{OL}$$

$$\left\{ A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} \right\}$$

\*\*

$$\boxed{\frac{\Delta A_{CL}}{A_{CL}} = \frac{\Delta A_{OL}/A_{OL}}{(1 + \alpha\beta)}}$$


Given  $\pi\beta = 99$

$$\frac{\Delta A_{CL} \cdot \%}{A_{CL}} = \frac{\Delta A_{DL}/A_{DL} \cdot \%}{1 + 99}$$


$$= \frac{20 \cdot \%}{100}$$

$$\boxed{\frac{\Delta A_{CL}}{A_{CL}} = 0.2 \cdot \%}$$

## 2. Increase in B.W. -

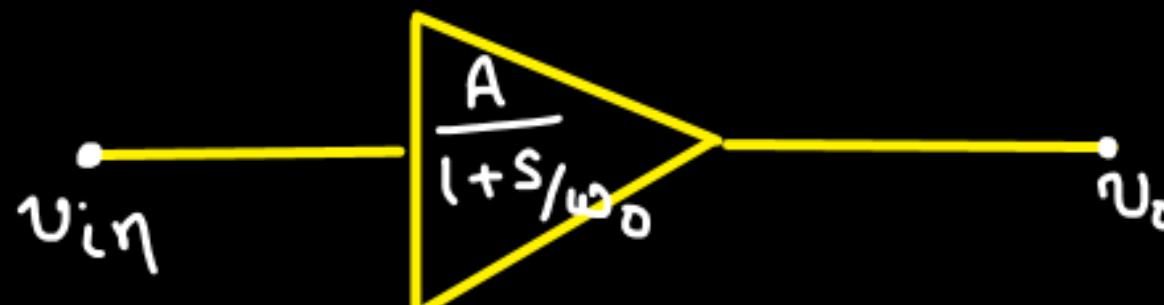

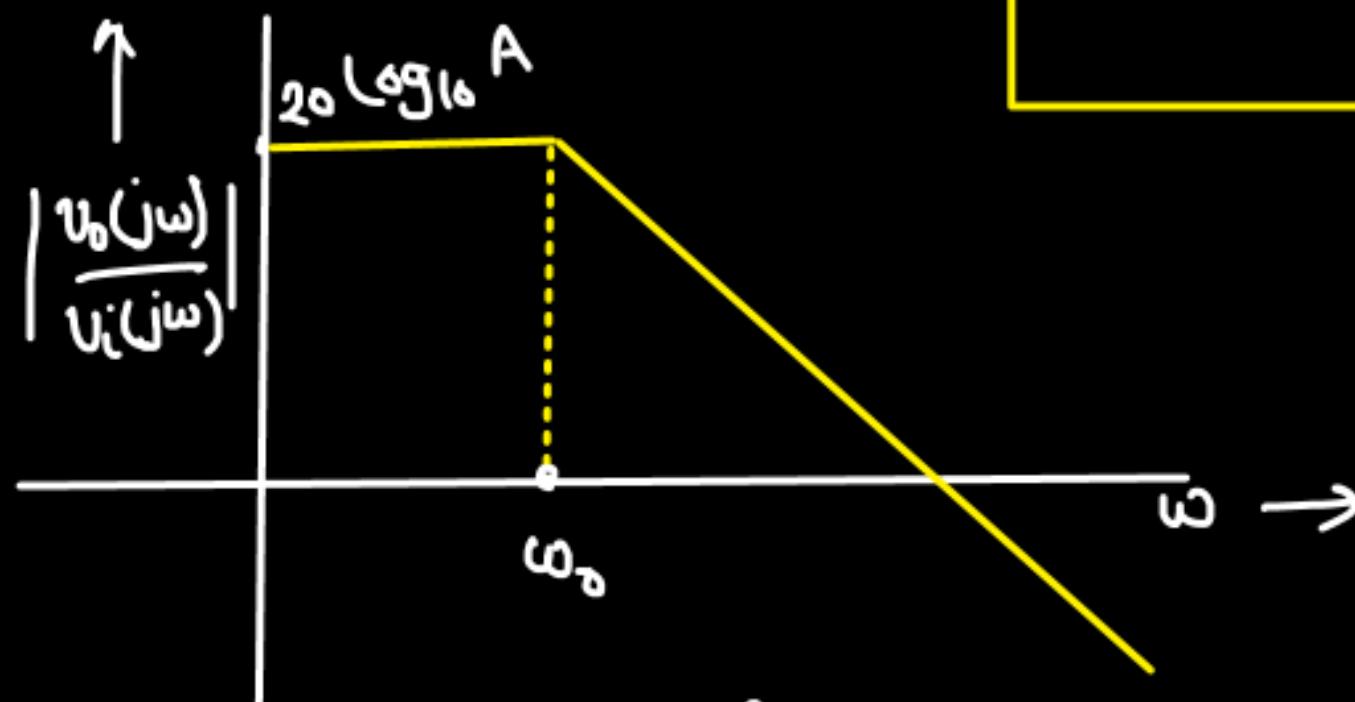
$$v_o(s) = \frac{A}{1+s/\omega_0} v_{in}(s)$$



$\theta.B.W = \omega_0 \{ \text{getting a good gain} \}$

## Introducing feedback:-

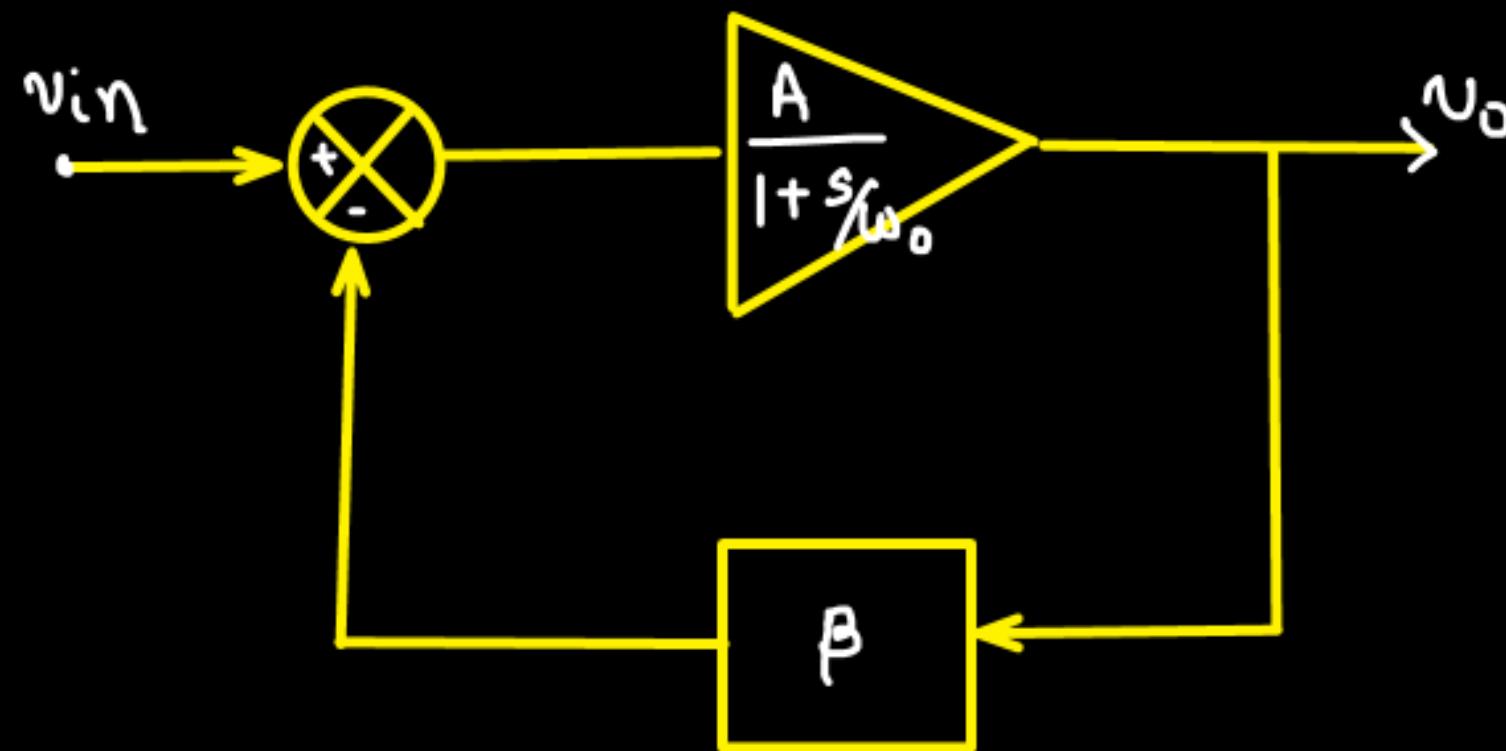

$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{A}{1+s/\omega_0}}{1 + \frac{\alpha\beta}{1+s/\omega_0}} = \frac{A}{A\beta + 1 + s/\omega_0} = \frac{A\omega_0}{s + \omega_0(1 + A\beta)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\omega_0}{s + \omega_0(1 + \alpha\beta)}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{\frac{A}{1 + \alpha\beta}}{\frac{s}{\omega_0(1 + \alpha\beta)} + L}}$$


dc gain =  $\frac{A}{1 + \alpha\beta}$

Bandwidth =  $\omega_0(1 + \alpha\beta)$

For open loop:- DC gain = A ,  $B \cdot \omega_c = \omega_0$



For closed loop:- DC gain =  $\frac{A}{1 + \alpha\beta}$  ,  $B \cdot \omega_c = \omega_0(1 + \alpha\beta)$

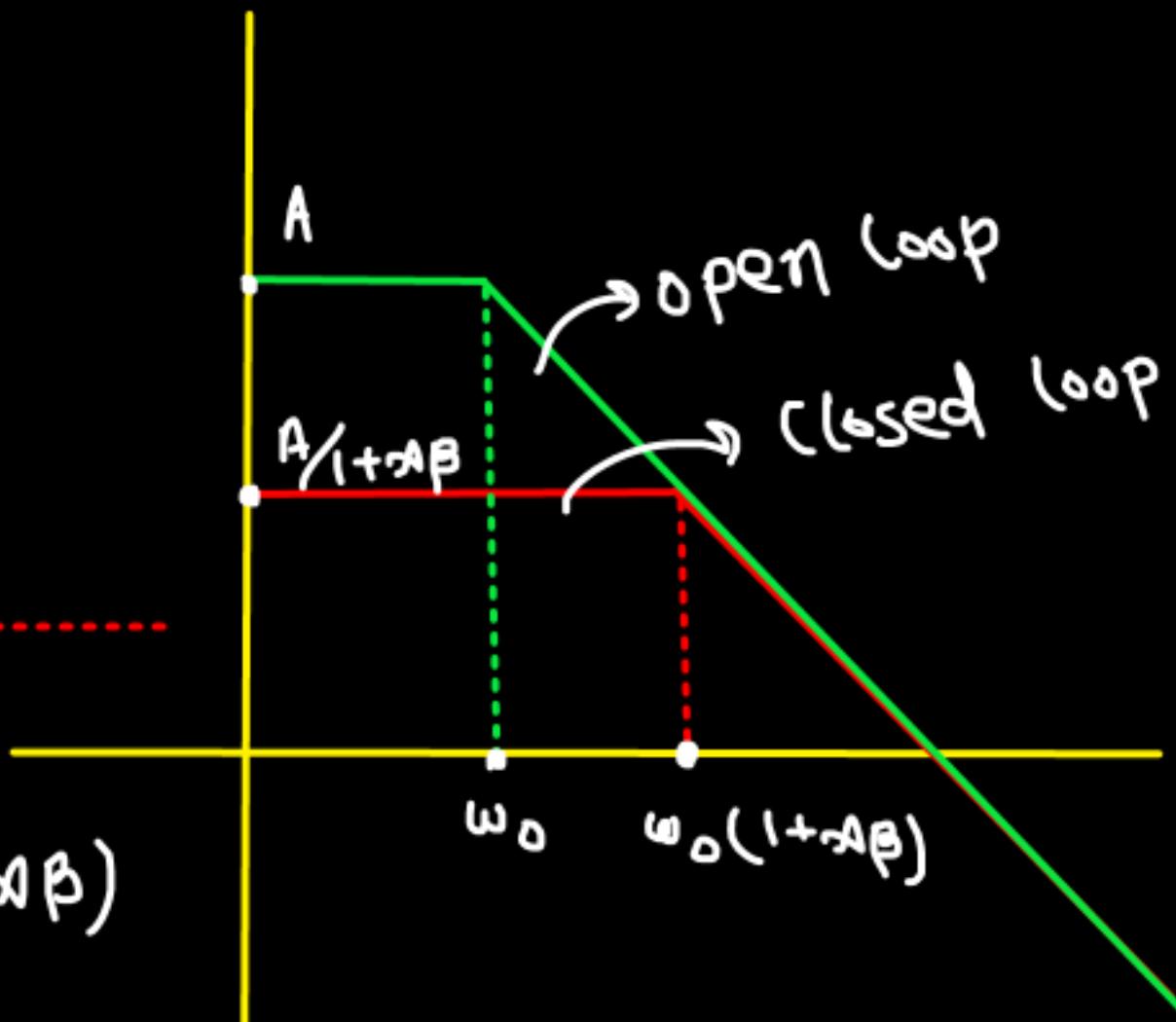in both cases  $G_B \cdot \omega_c = \alpha\omega_0$




### (iii) Increase in linearity:-

Before f/b:-

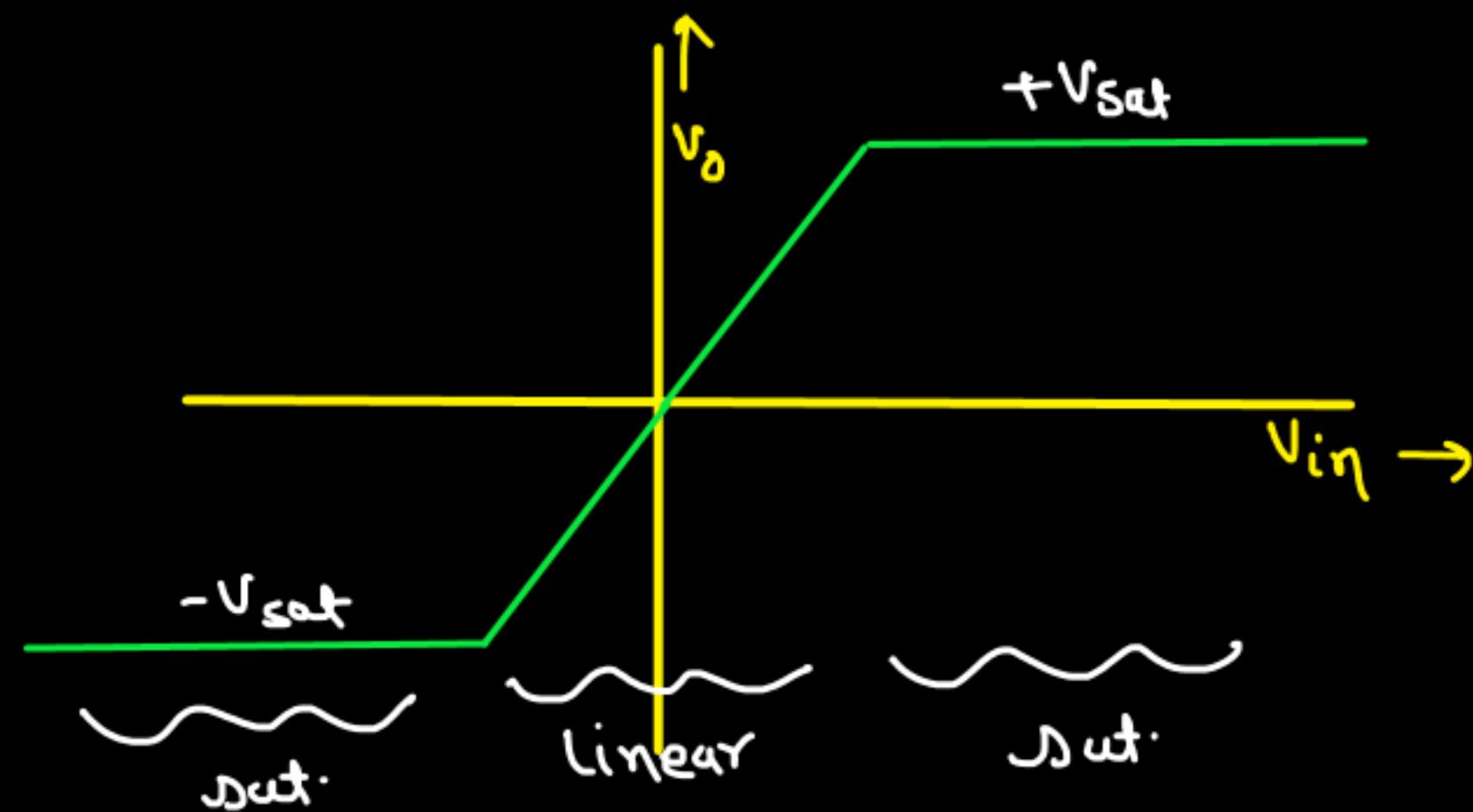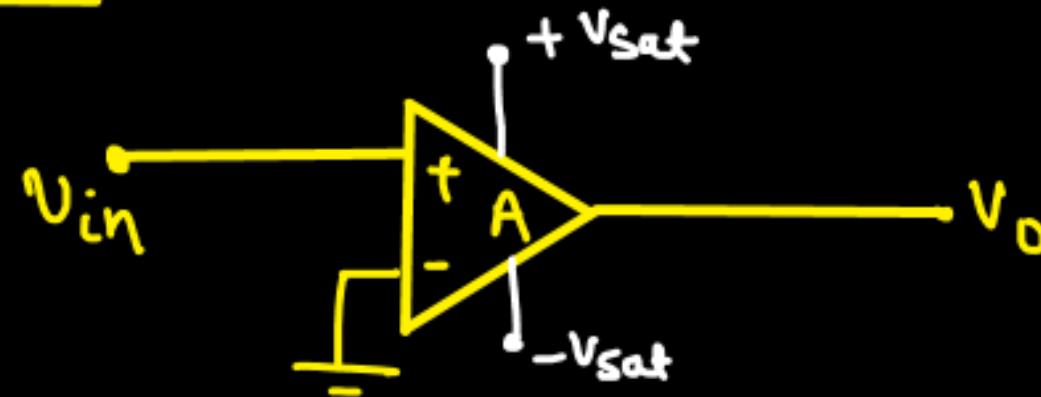


linearity  $\downarrow$

After f/b:-

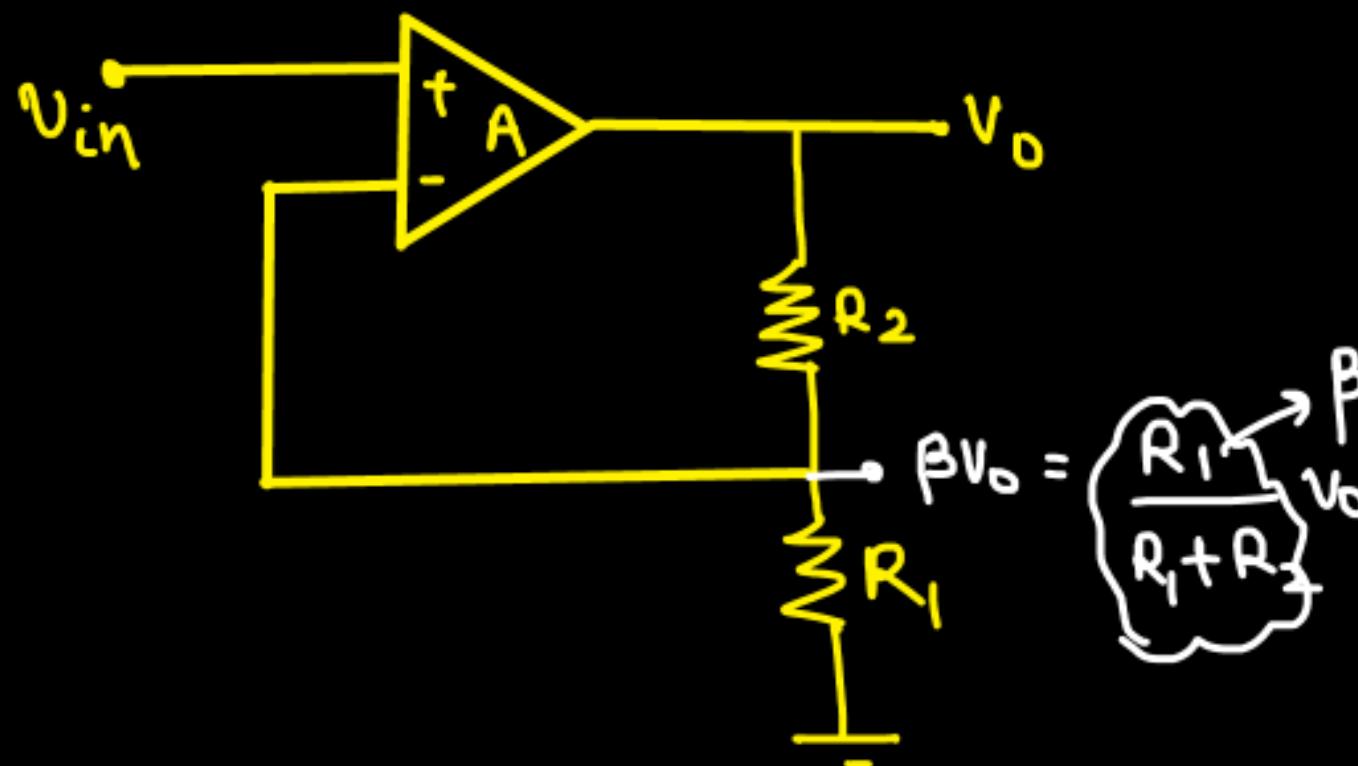

$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} = \frac{1 + R_2}{R_1}$$
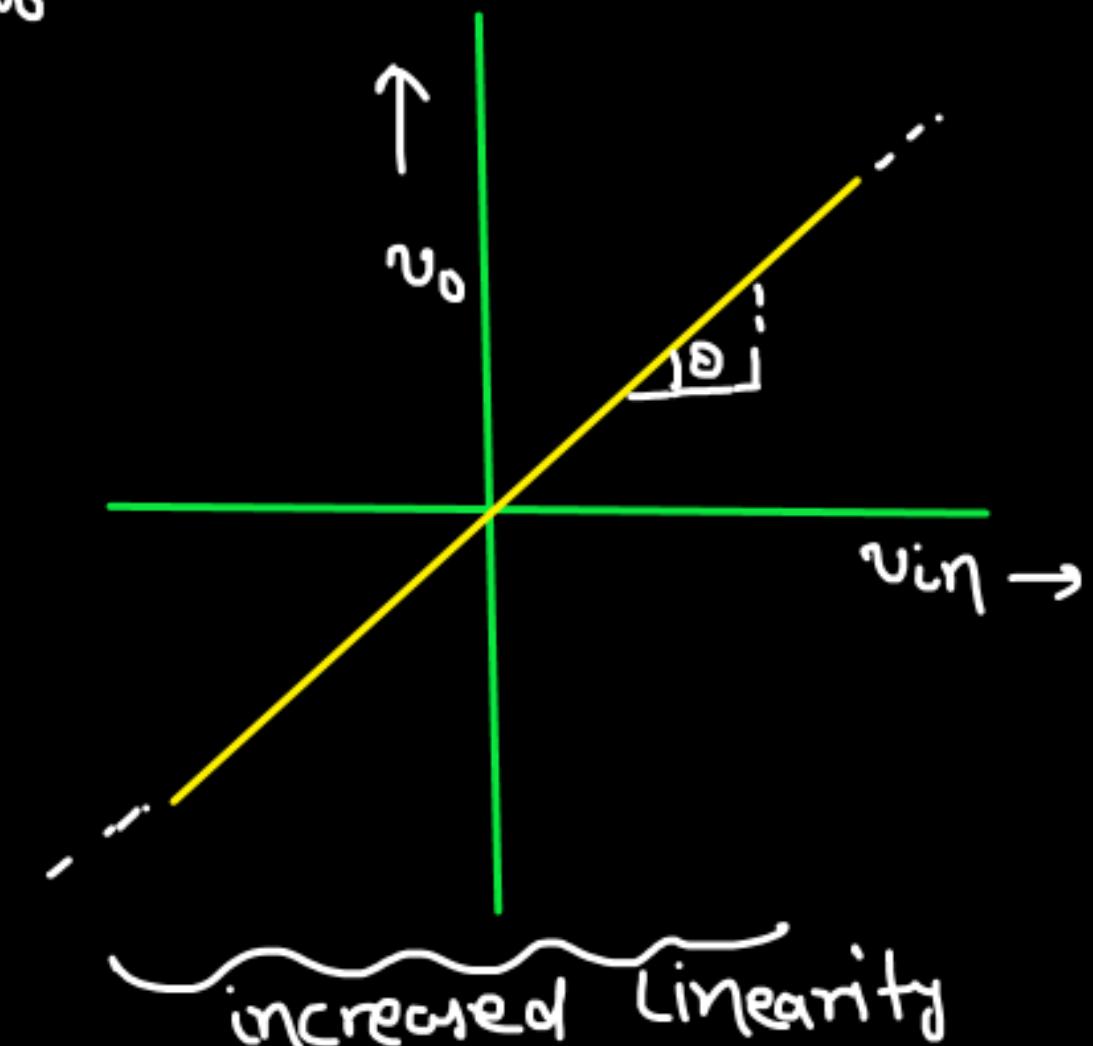
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$



$\Rightarrow$  In Negative fb:-

- ①  $S/S \rightarrow$  stable [Gain is constant]
- ② Gain  $\rightarrow$  Reduces
- ③  $B \cdot w \cdot \rightarrow$  Increases
- ④ Linearity  $\rightarrow$  Increases
- ⑤ Time constant  $\rightarrow$  decreases [ $B \cdot w \propto \frac{1}{\tau}$ ]


\* open loop gain = A

After f/b:-


(i) Closed loop gain ( Neg f/b) =  $\frac{A}{1 + A\beta} = \frac{\text{open loop gain}}{1 + \text{loop gain}}$

(ii) Closed loop gain ( pos f/b) =  $\frac{A}{1 - A\beta} = \frac{\text{open loop gain}}{1 + \text{loop gain}}$

## \* How to find loop gain?

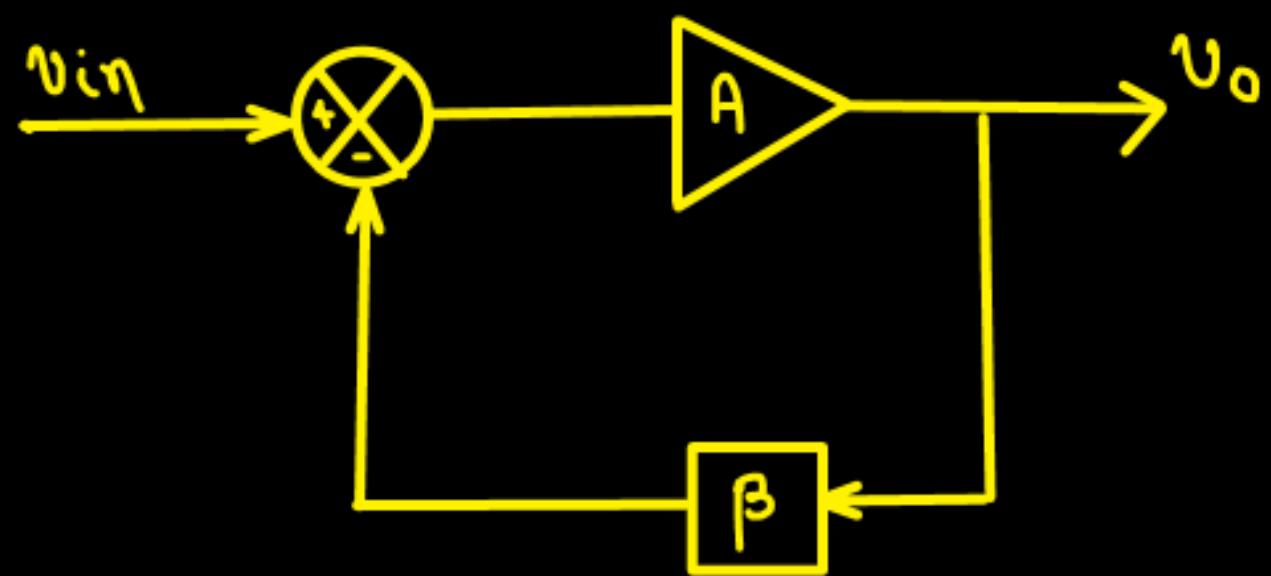

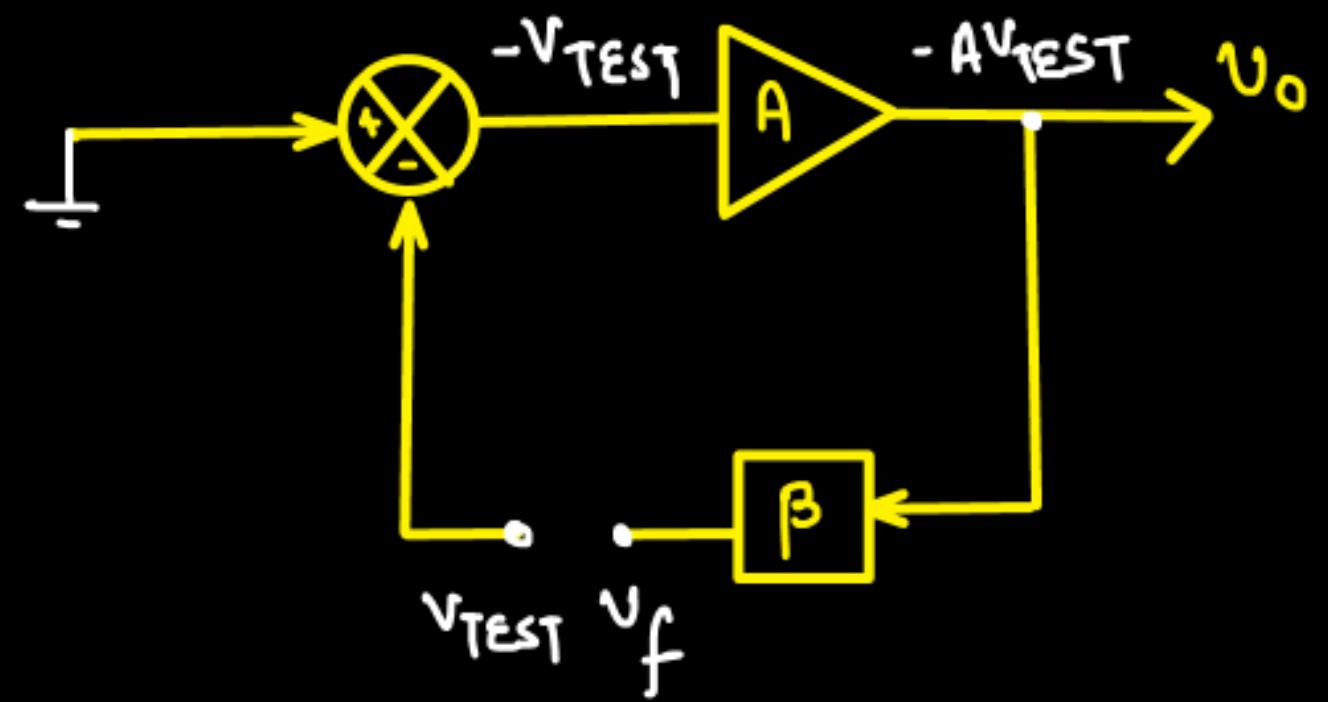
- (i) Nullify the IP.
- (ii) Break the loop in feedback path.
- (iii) Mark the open end as  $v_f$  and  $v_{TEST}$ . ( $v_{TEST}$  should go towards the input side)
- (iv) loop gain  $\alpha\beta = -\frac{v_f}{v_{TEST}}$



$$V_f = -\beta(AV_{TEST})$$


$$\frac{-V_f}{V_{TEST}} = \alpha\beta$$

Example:

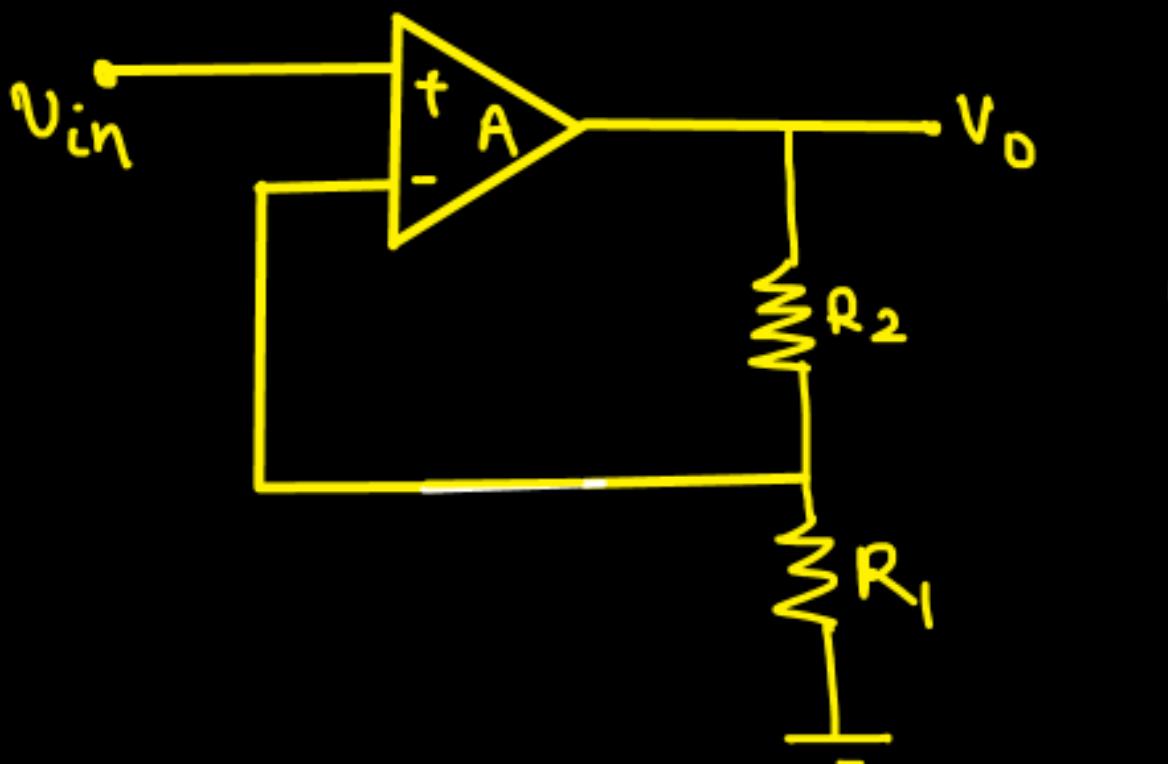

loop gain = ?

→

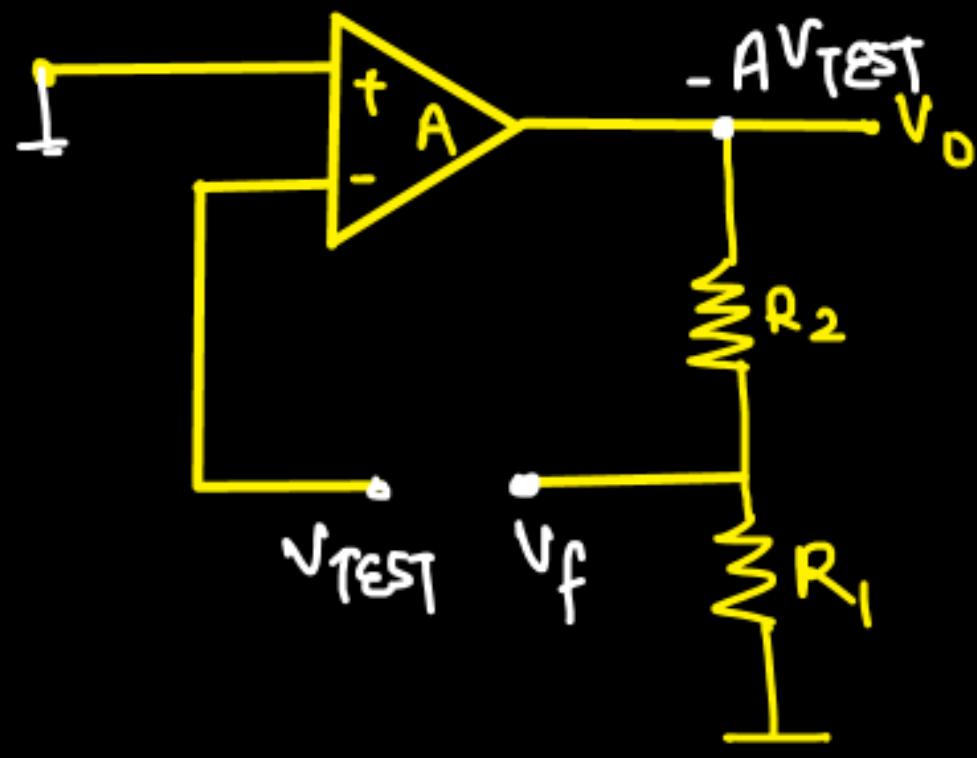



$$-AV_{TEST} \times \frac{R_1}{R_1 + R_2} = V_f$$

$$\frac{-V_f}{V_{TEST}} = \boxed{\text{loop gain} = \frac{-AR_1}{R_1 + R_2}}$$

## Types of Amplifiers:-

- (i) Voltage amplifiers :-
- (ii) Transresistance amplifiers:-
- (iii) Transconductance amplifiers:-
- (iv) Current amplifiers:-

## (ii) Voltage Amplifiers:-

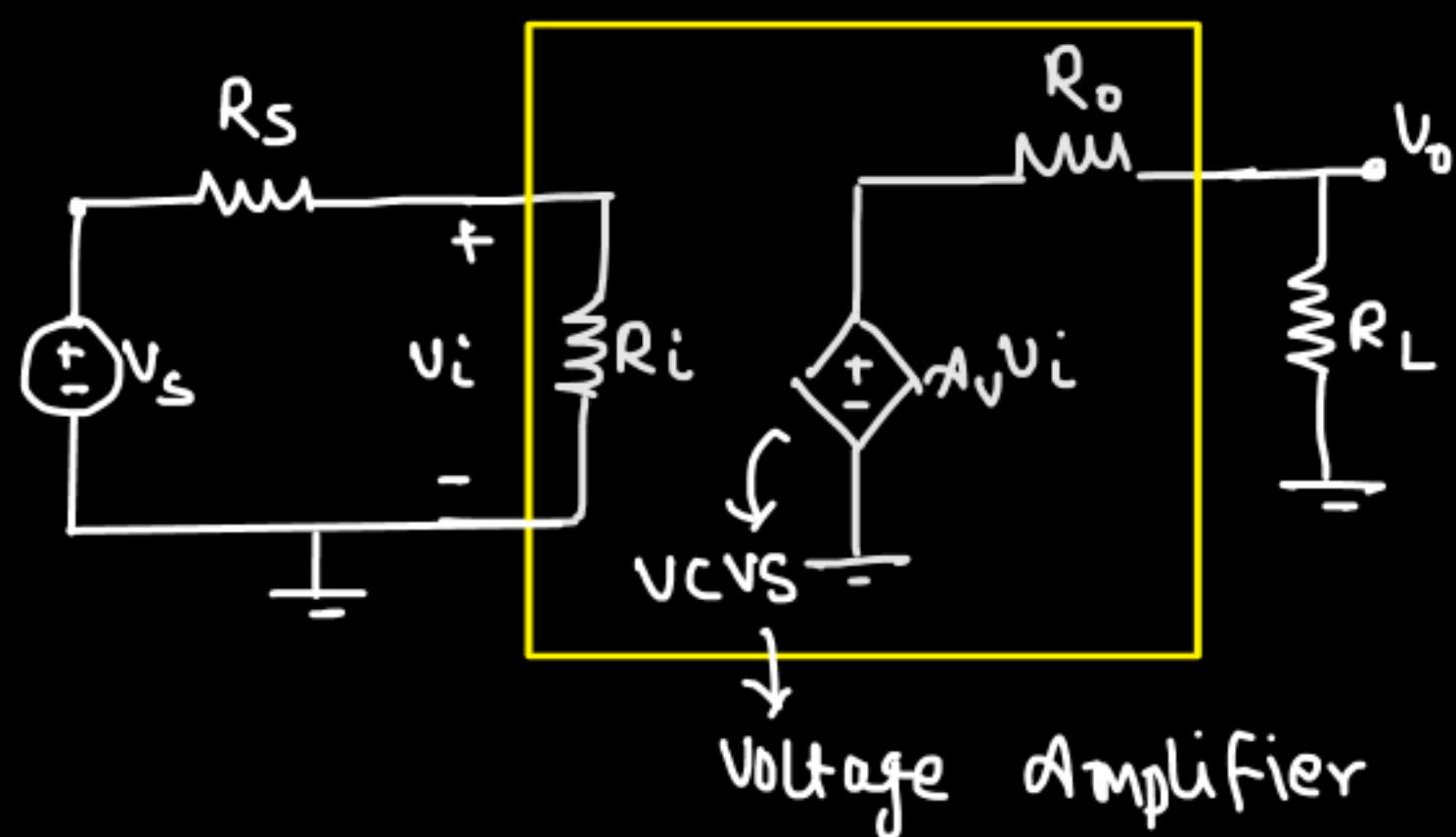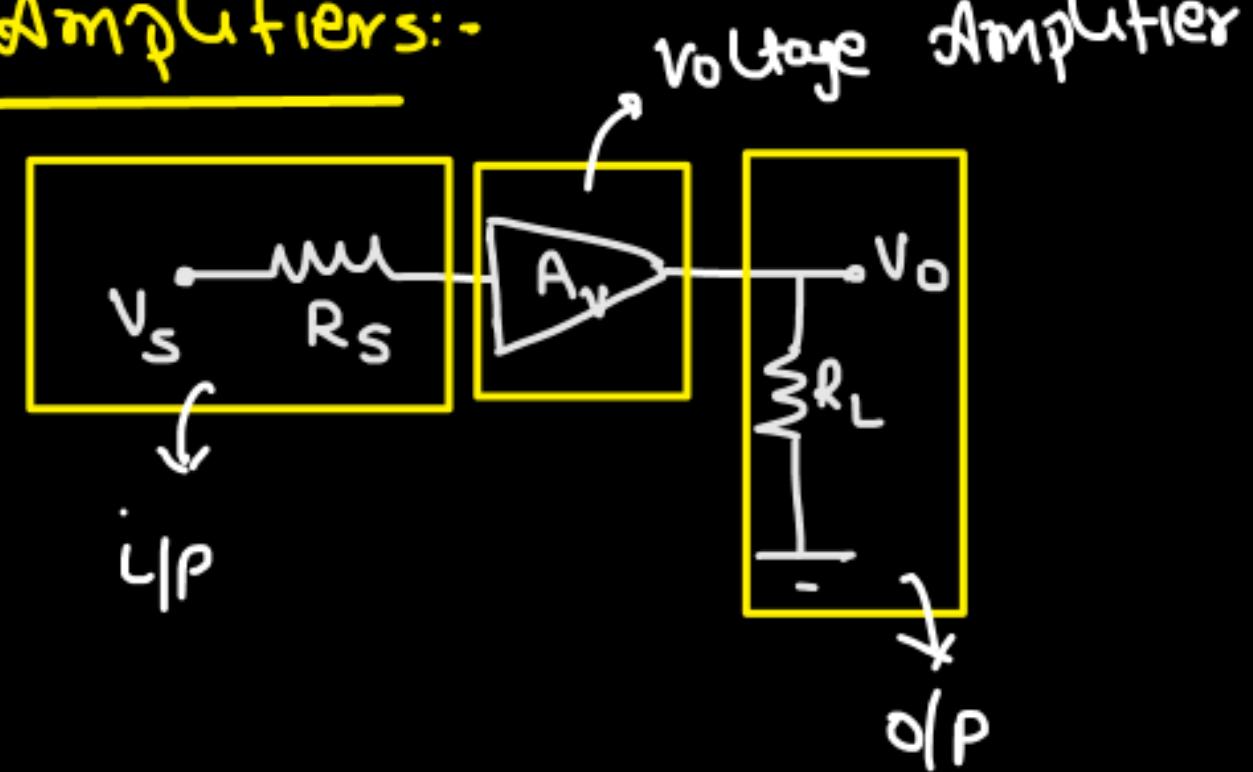

$$V_i = \frac{R_i}{R_i + R_s} V_s$$

$$V_o = \frac{A_v \times V_i \times R_L}{R_L + R_o}$$

$$V_o = A_v \left[ \frac{R_i}{R_i + R_s} \right] V_s \times \frac{R_L}{R_L + R_o}$$

$$\frac{V_o}{V_s} = A_v \left[ \frac{R_i}{R_i + R_s} \right] \left[ \frac{R_L}{R_L + R_o} \right]$$

For an ideal voltage amplifier :-


$R_i = \infty$	→ High
$R_o = 0$	→ Low

if  $R_i = \infty$ ,  $R_o = 0$

$$\frac{V_o}{V_s} = A_v$$


Unit of  $A_v = \frac{V}{V}$

### (iii) Trans-resistance amplifier:-

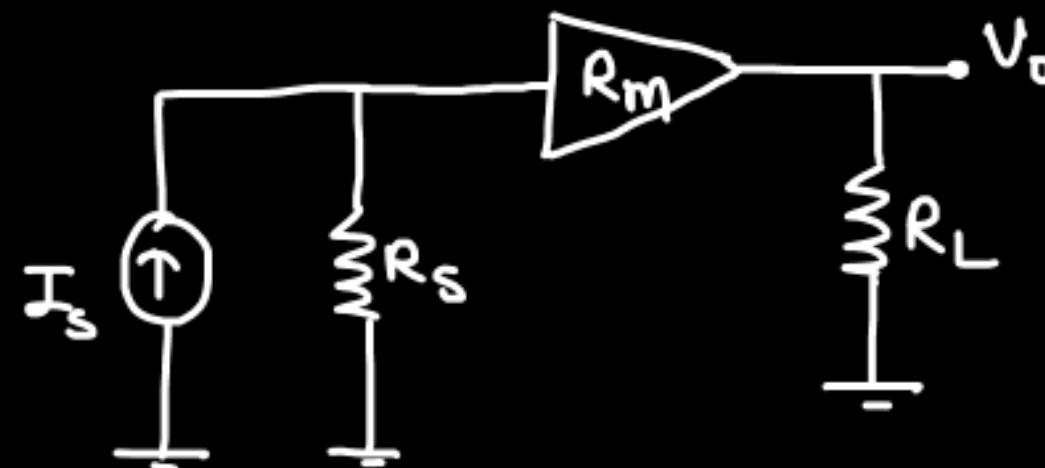

$$R_m = \frac{V_o}{I_s} = \text{ohm}$$

ampere

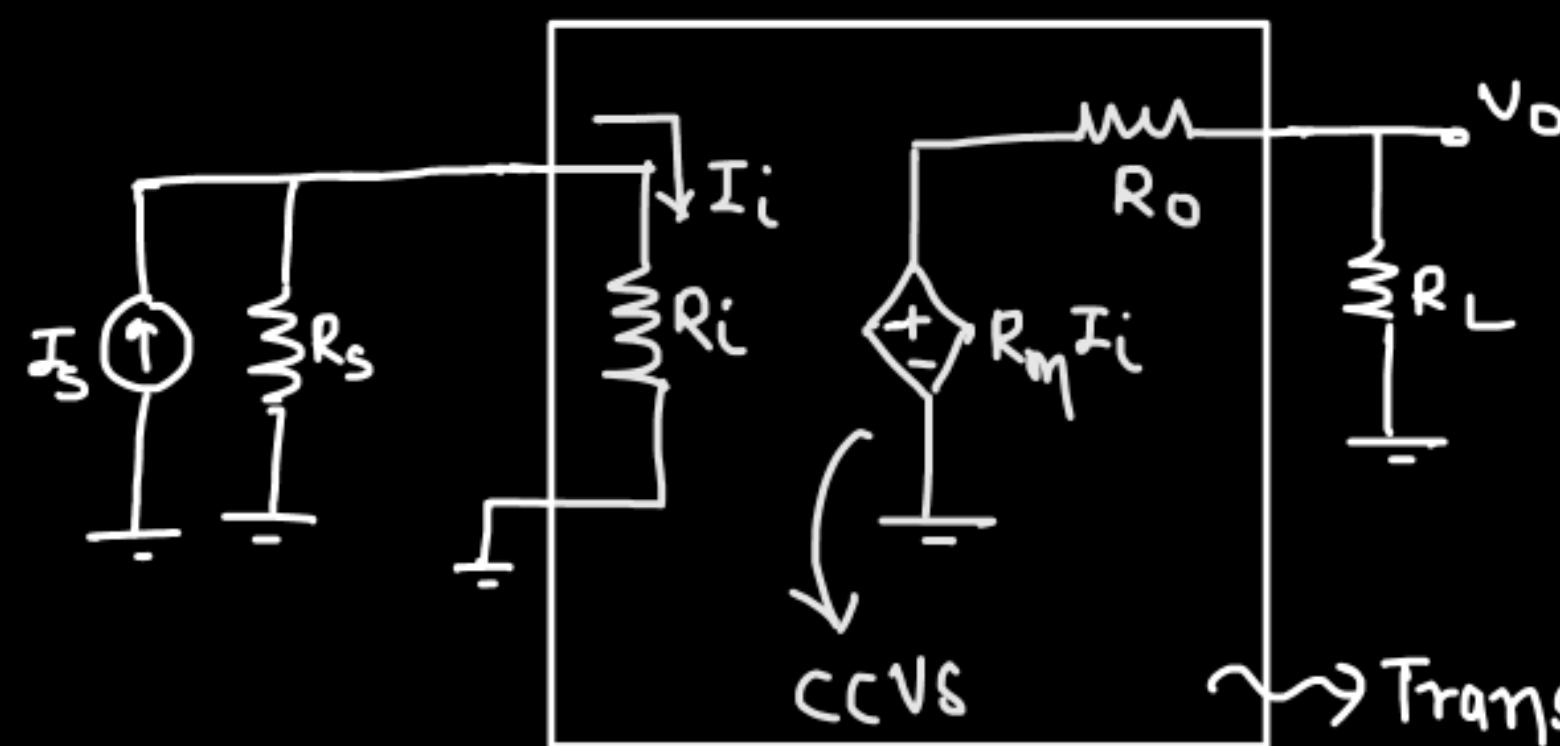

$$I_i = \frac{R_s}{R_s + R_i} I_s$$

$$V_o = \frac{R_L}{R_L + R_o} \times R_m I_i$$

Trans-resistance amplifier

$$V_o = (R_m) \left( \frac{R_L}{R_L + R_o} \right) \left( \frac{R_S}{R_S + R_i} \right) I_s$$

$$\frac{V_o}{I_s} = [R_m] \left( \frac{R_L R_S}{(R_L + R_o)(R_S + R_i)} \right)$$

For ideal Transresistance amplifier,


$R_i = 0 \Omega$	$\rightarrow$ low
$R_o = 0 \Omega$	$\rightarrow$ low

if  $R_i = 0$  and  $R_o = 0$


$$\frac{V_o}{I_s} = R_m$$

Unit of  $R_m \rightarrow$  ohm

### (iii) Transconductance Amplifier :-

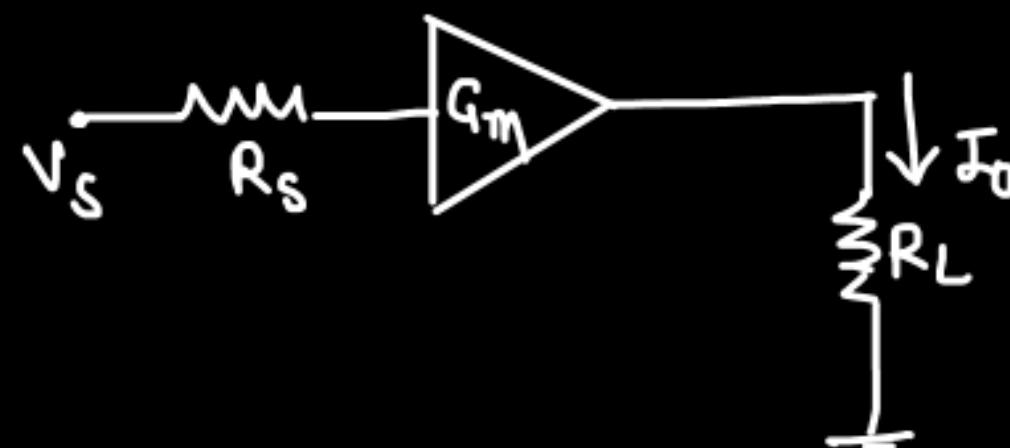
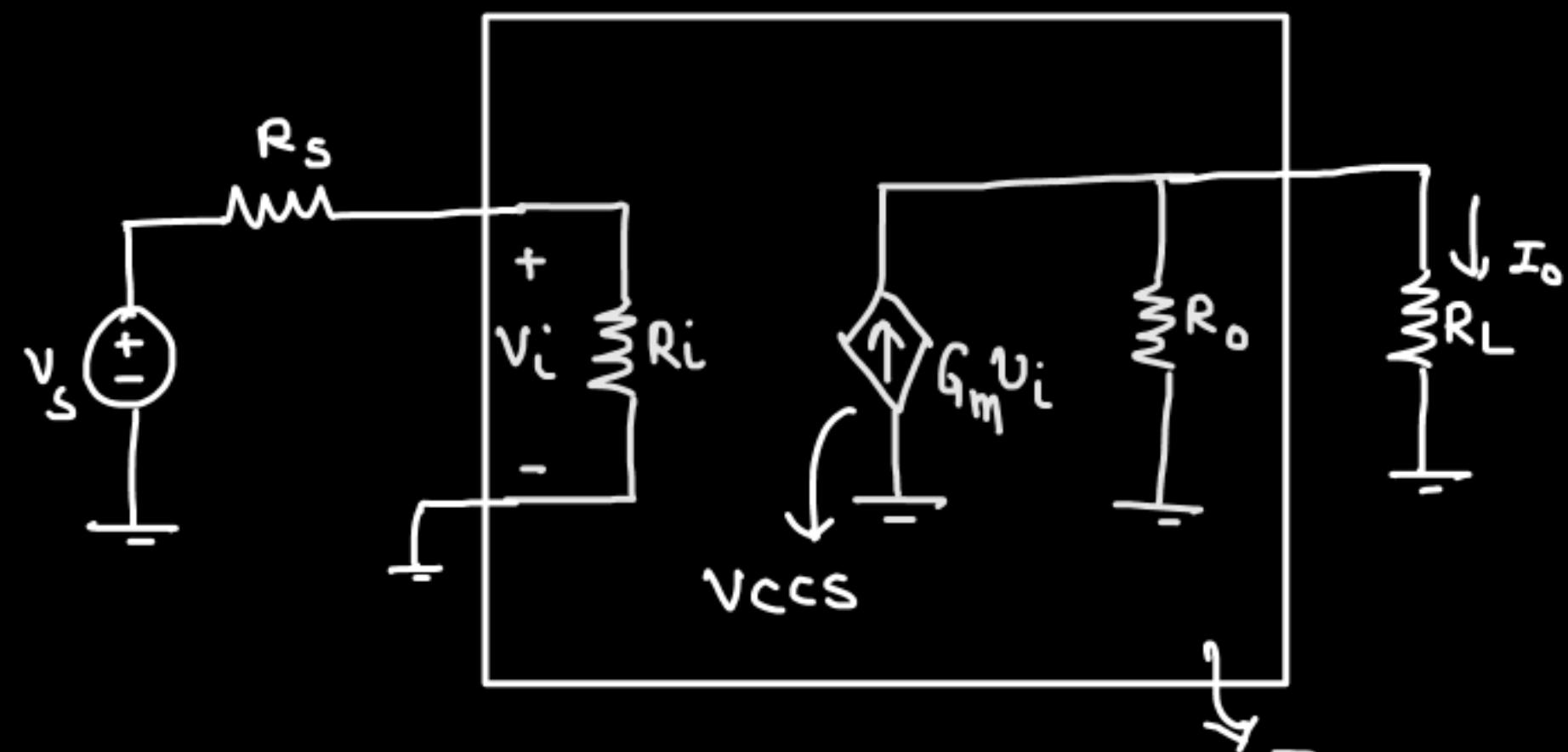
$$G_m \rightarrow \frac{\text{Current}}{\text{Voltage}} = \frac{A}{V} \\ = mho = S$$



$$V_i = \frac{R_i}{R_i + R_s} V_s$$

$$I_o = \frac{R_o}{R_i + R_L} \times G_m V_i$$

Transconductance amplifier

$$I_o = (G_m) \left( \frac{R_o}{R_o + R_L} \right) \left( \frac{R_i}{R_i + R_S} \right) v_s$$

$$\frac{I_o}{v_s} = G_m \left( \frac{R_o}{R_o + R_L} \right) \left( \frac{R_i}{R_i + R_S} \right)$$

For ideal Transconductance amplifier ;

$$R_i = \infty$$



$$R_o = \infty$$

$$R_i = \infty, R_o = \infty$$

$$\frac{I_o}{v_s} = G_m$$

Unit of  $G_m \rightarrow \text{mho/s}$

## (iv) Current Amplifier:-

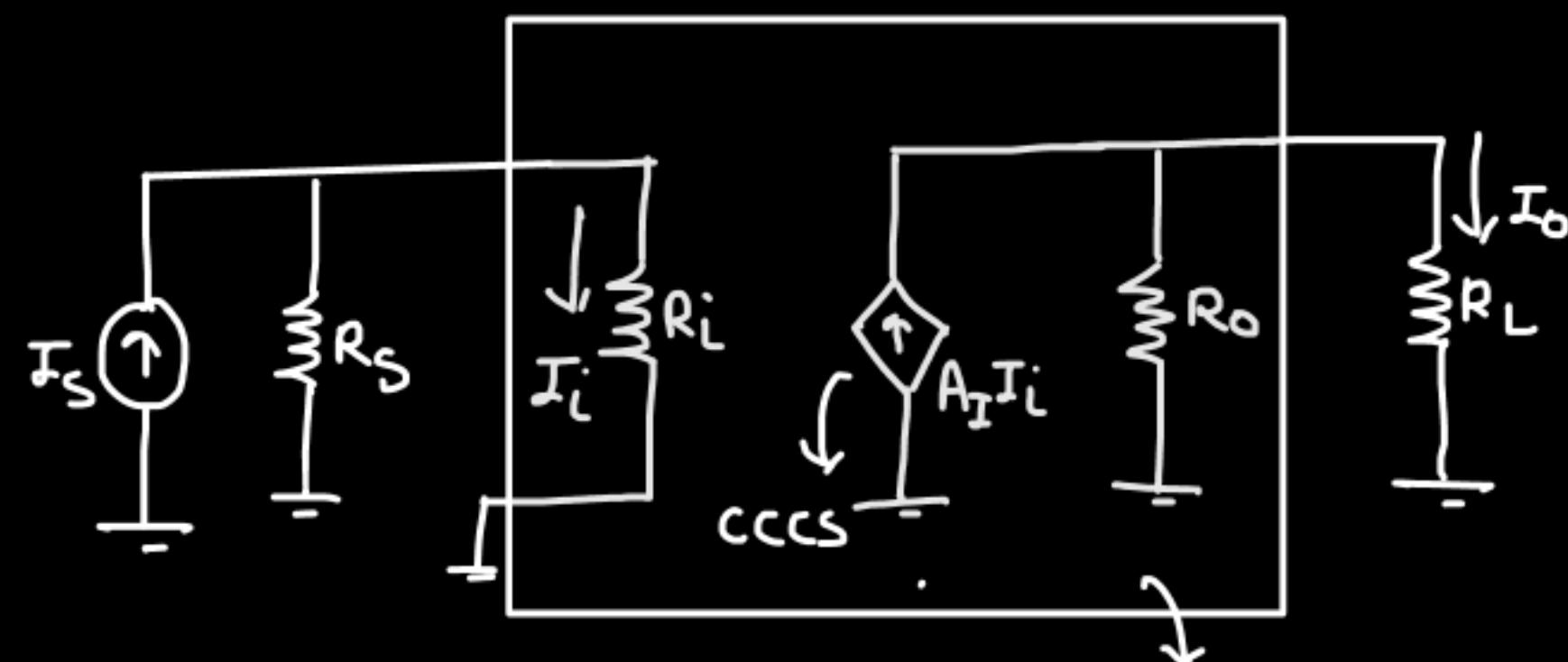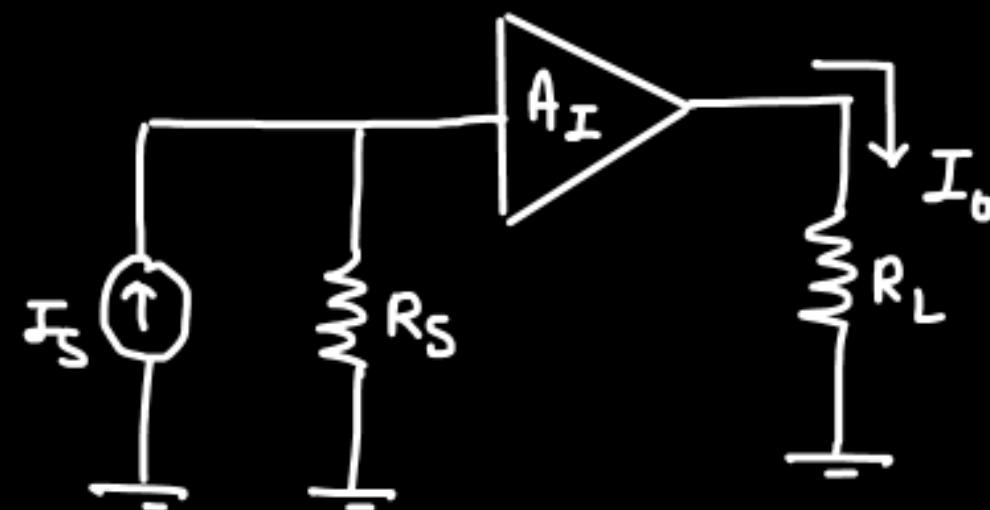

Current Amplifier

$$I_L = \frac{R_s}{R_s + R_i} I_s$$

$$I_o = \frac{R_o}{R_o + R_L} A_I I_i$$

$$I_o = A_I \left( \frac{R_o}{R_o + R_L} \right) \left( \frac{R_s}{R_s + R_i} \right) I_s$$

$$\frac{I_o}{I_s} = A_I \left( \frac{R_o}{R_o + R_L} \right) \left( \frac{R_s}{R_s + R_i} \right)$$

for ideal current amplifier,

$$R_i = 0$$



$$R_o = \infty$$

$$R_i = 0, R_o = \infty$$



$$\frac{I_o}{I_s} = A_I$$

Type of Amplifier	Input Resistance	Output Resistance
(i) Voltage Amplifier	$\infty$	0
(ii) Transresistance Amp.	0	0
(iii) Transconductance amp	$\infty$	$\infty$
(iv) Current Amplifier	0	$\infty$


## Alternative feedback Model :-

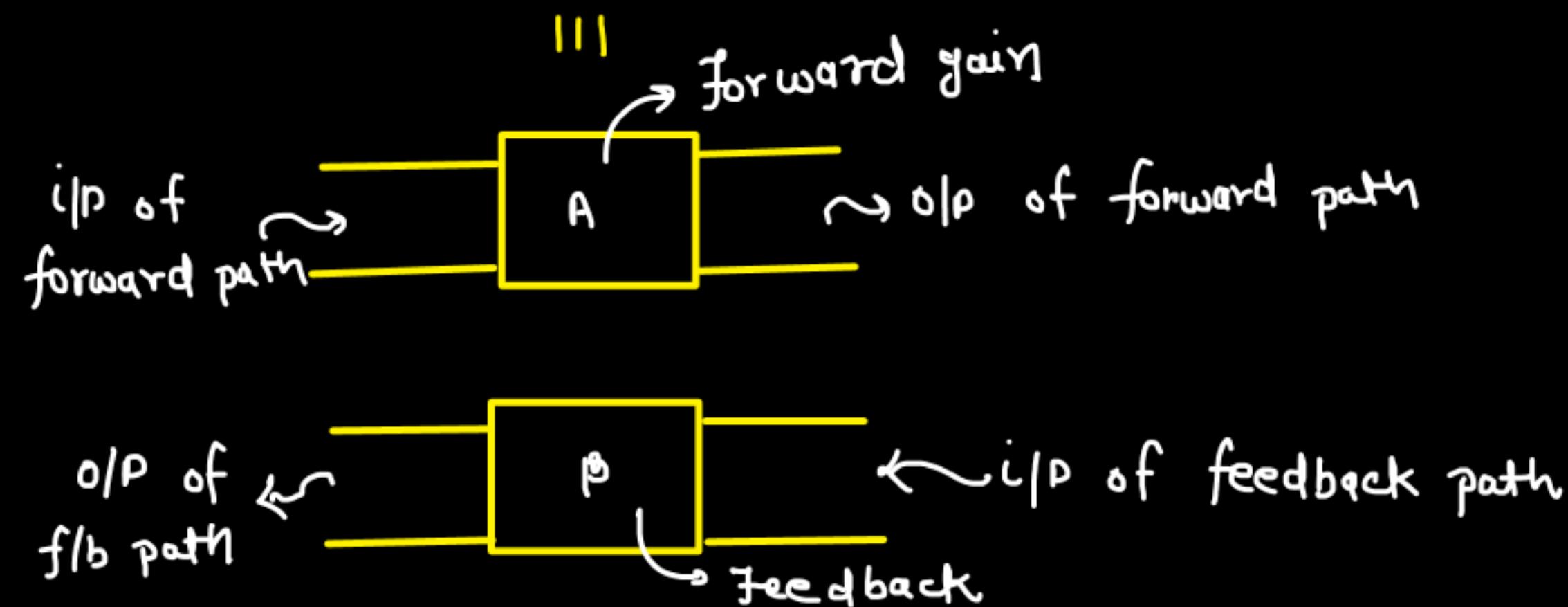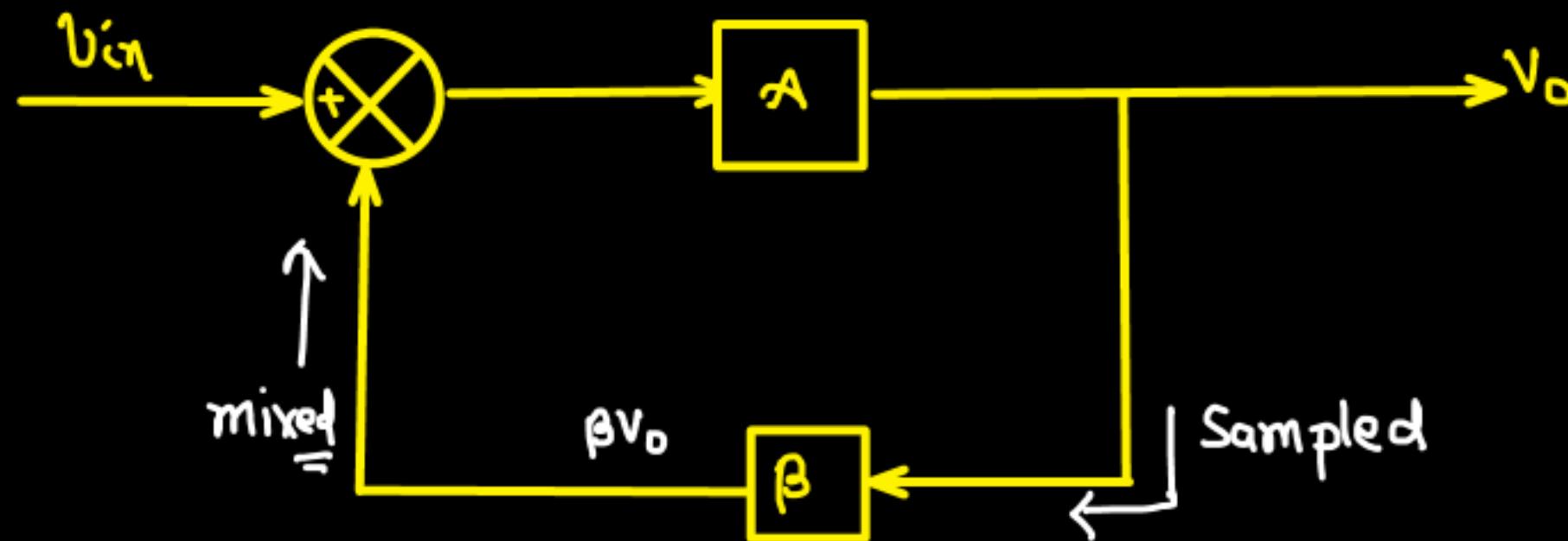
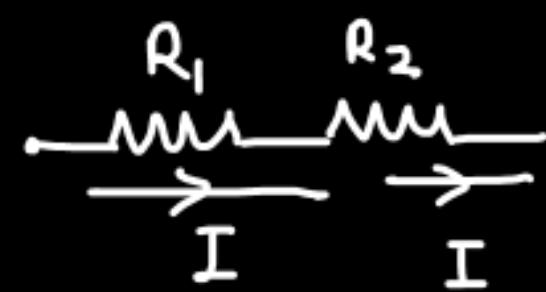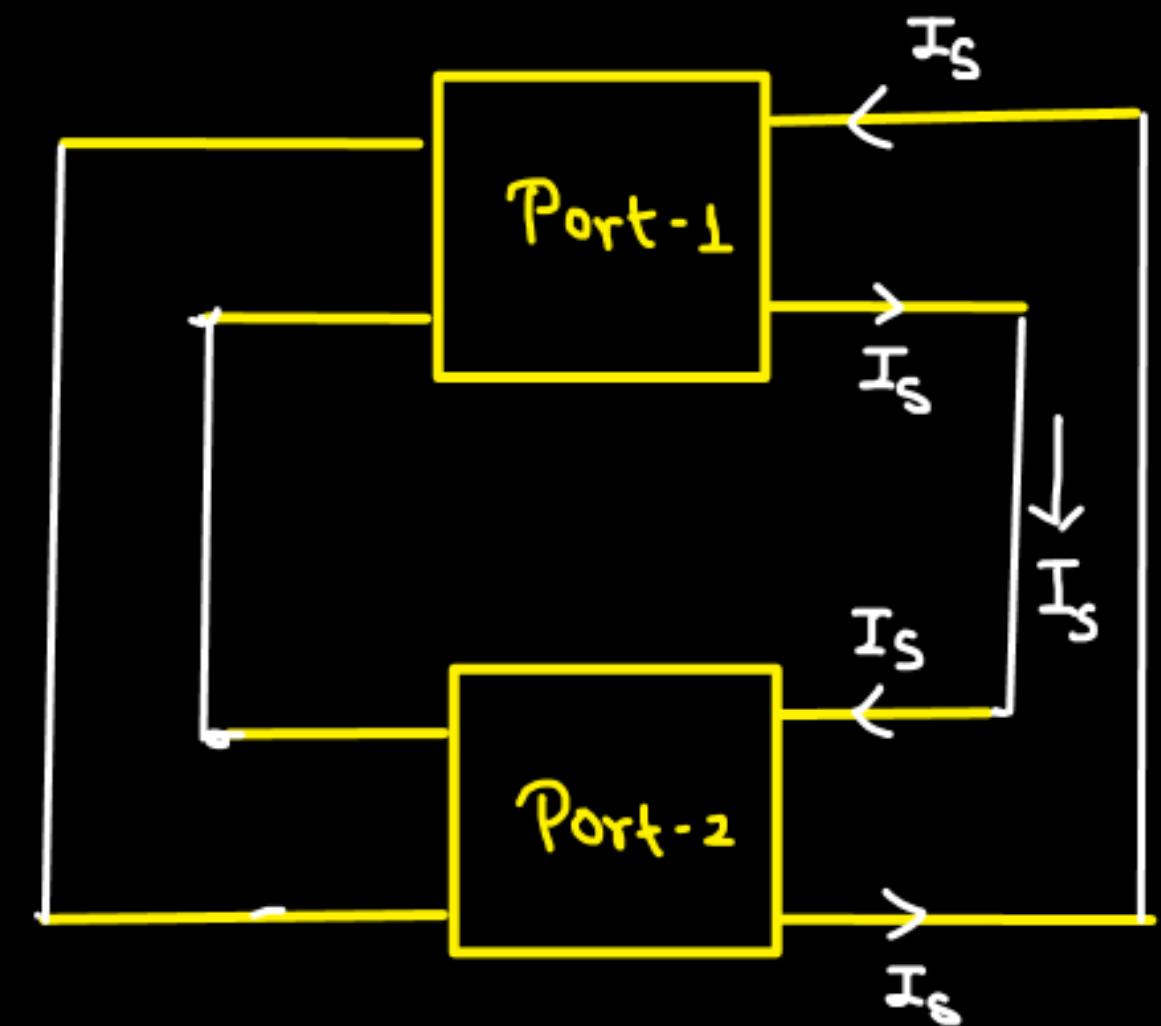
## \* Series Connection of 2-Two port N(w):-




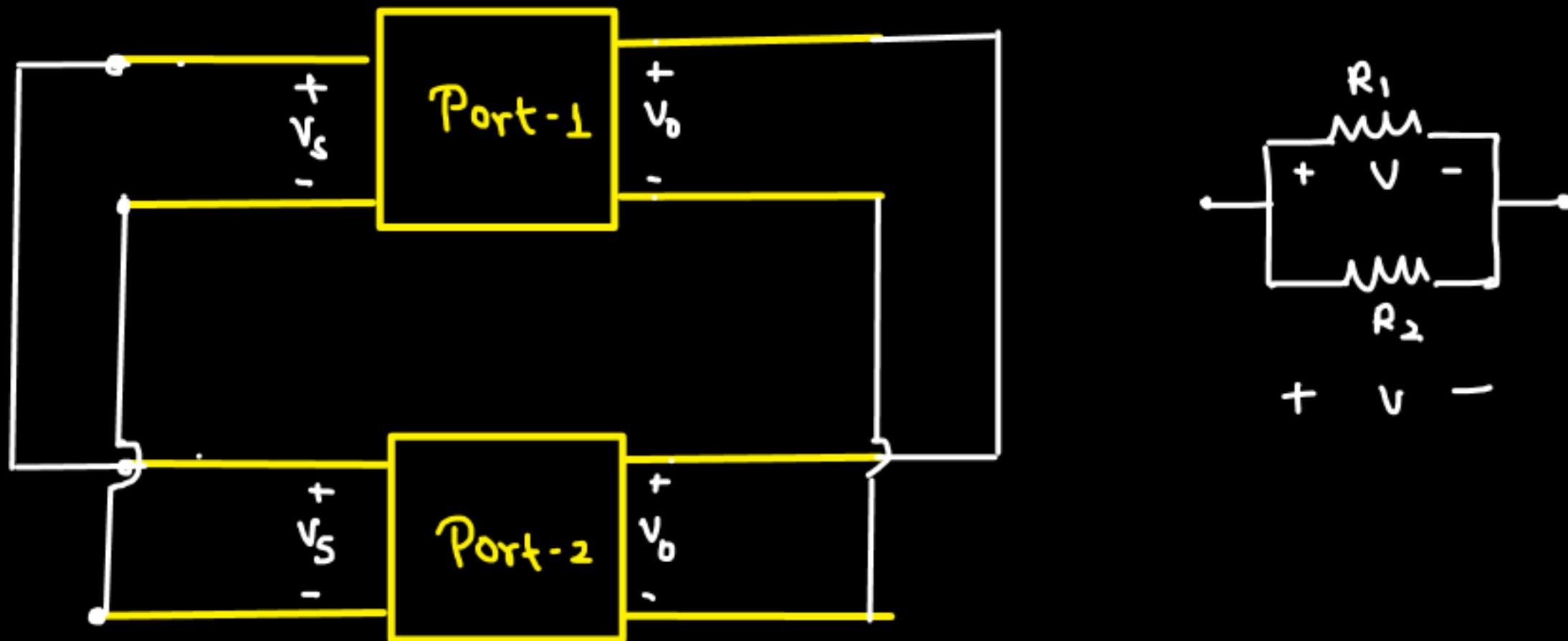\* Parallel Connection of 2 - Two Port Networks  
(Shunt)



## \* Important points to remember:-

### 1. Series Connection:-

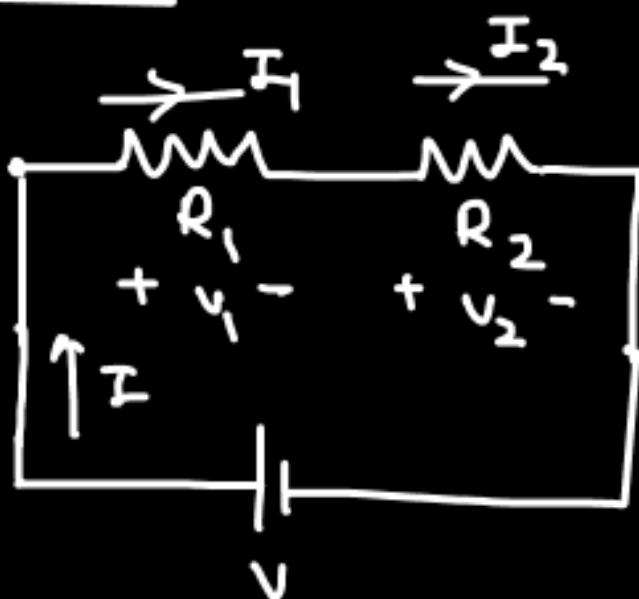


$I = I_1 = I_2 \rightarrow$  current same

$V = v_1 + v_2 \rightarrow$  voltage mixed

Series = current sampled, voltage mixed

### 2. Parallel connection:-

(Shunt)

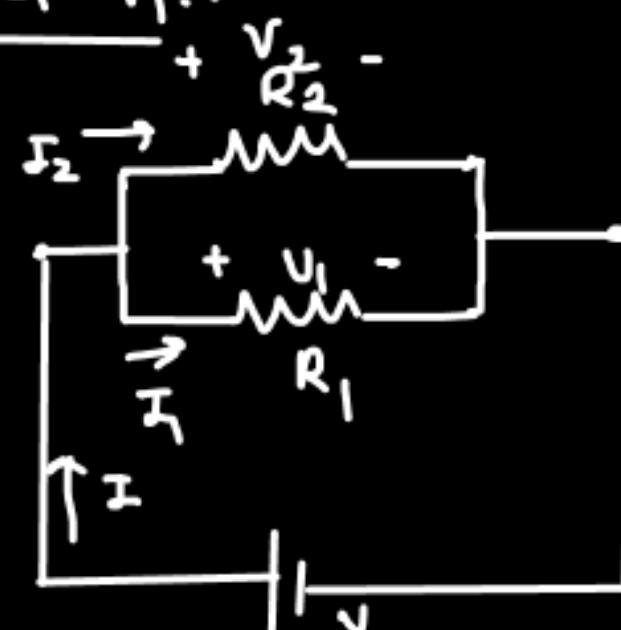


$V = V_1 = V_2 \rightarrow$  voltage same

$I = I_1 + I_2 \rightarrow$  current mixed

Parallel = voltage sampled, current mixed

For a two port N/W:-

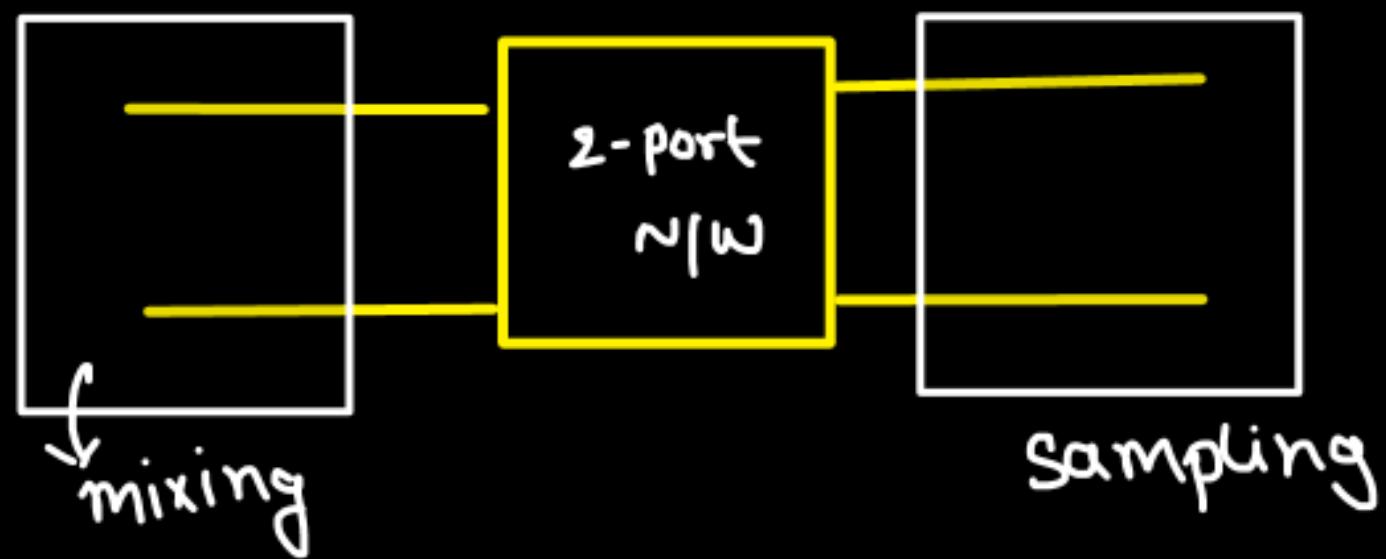

\* Decode the following:-

- ① Voltage Sampling  $\rightarrow$  Shunt connection
- ② Current Mixing  $\rightarrow$  Shunt connection
- ③ Voltage Mixing  $\rightarrow$  Series connection
- ④ Current Sampling  $\rightarrow$  Series connection

- ⑤ Series connection  $\rightarrow$  Current Sampling , Voltage mixing
- ⑥ Shunt Connection  $\rightarrow$  Voltage Sampling , Current mixing
- ⑦ Series connection at input  $\rightarrow$  Voltage mixing
- ⑧ Series connection at output  $\rightarrow$  Current Sampling
- ⑨ Shunt connection at input  $\rightarrow$  current mixing
- ⑩ Shunt connection at output  $\rightarrow$  Voltage Sampling

Conclusion:-

- ①  $i/p \rightarrow$  mixing ,  $o/p \rightarrow$  sampling
- ② Series  $\rightarrow$  Current Sampling , Voltage mixing
- ③ Shunt  $\rightarrow$  Voltage Sampling , Current mixing

⇒ Feedback Topologies :-

O/P - I/P

I/P - O/P

O/P - I/P

① Voltage - Voltage | Series - Shunt | Voltage - Series


② Voltage - Current | Shunt - Shunt | Current - Shunt

③ Current - Voltage | Series - Series | Voltage - Series

④ Current - Current | Shunt - Series | Current - Series
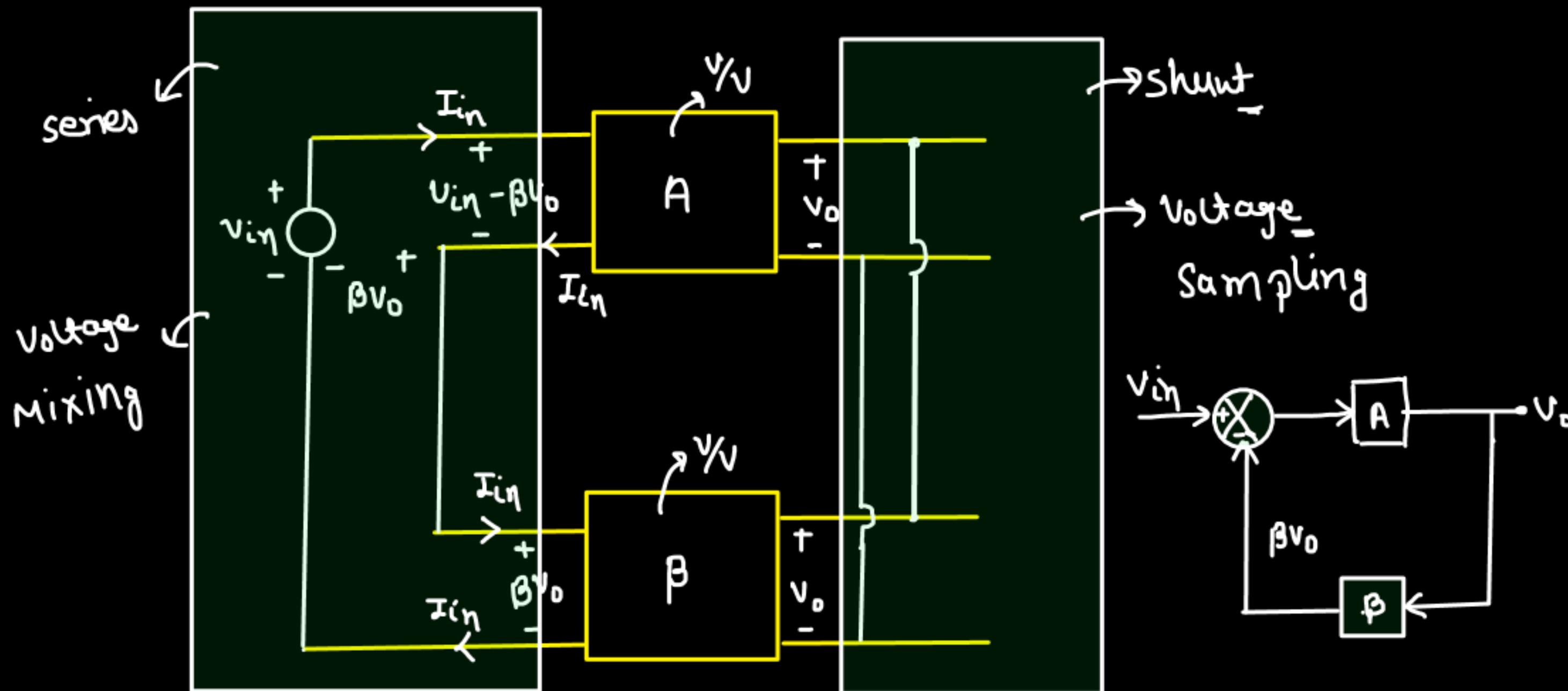
## \* Voltage - Voltage Feedback Topology :-

(Series - Shunt)  $\hookrightarrow$  from o/p voltage is sensed and fed back to the i/p




open loop gain = A

open loop input resistance =  $R_{in}$

open loop output resistance =  $R_o$

① Closed loop Gain :-

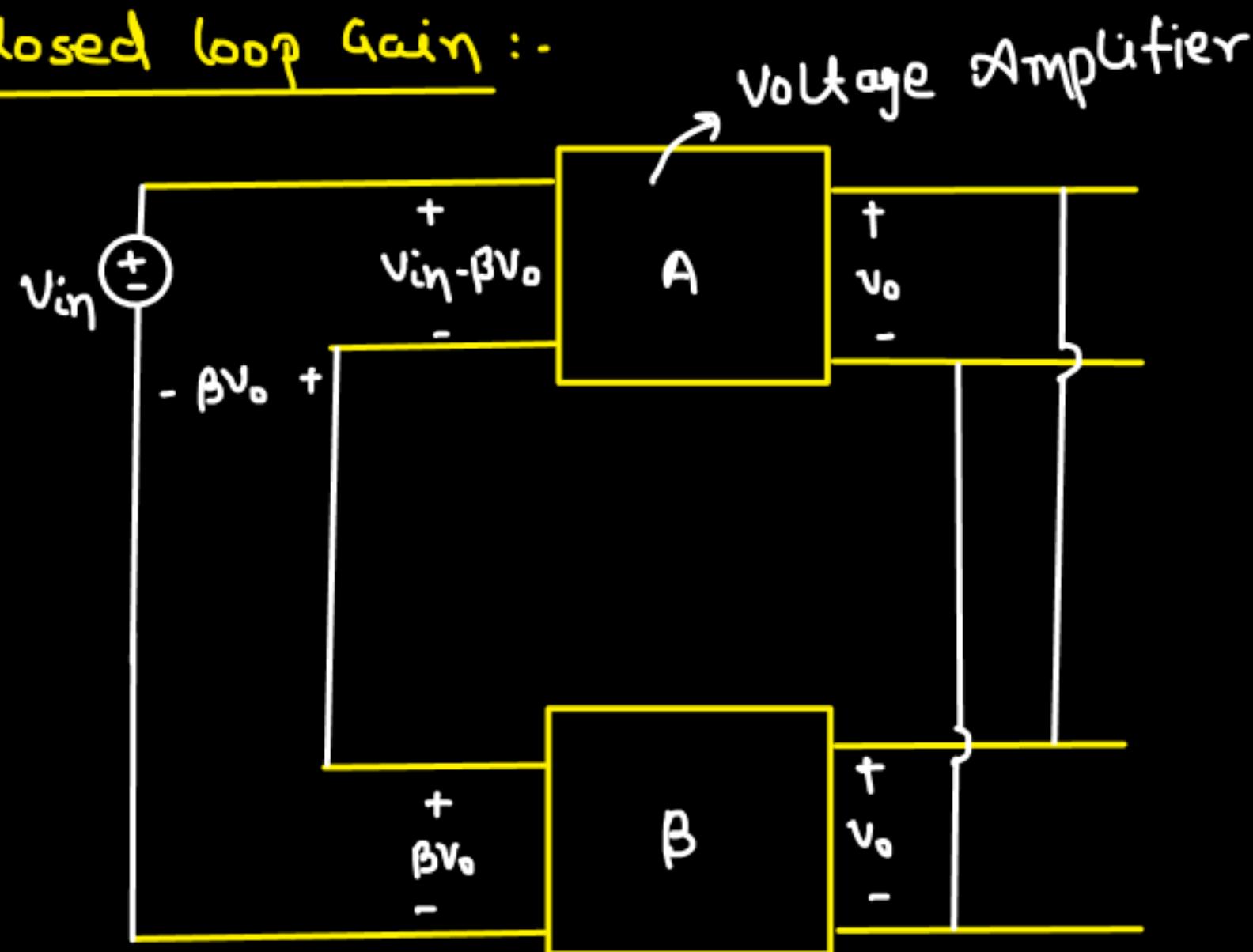


$$CLG = \frac{V_{in}}{V_o} = (AV)_f$$

$$A(V_{in} - \beta V_o) = V_o$$

$$\frac{V_o}{V_{in}} = (AV)_f = \frac{A}{1 + A\beta}$$

## ② Closed loop input impedance :-

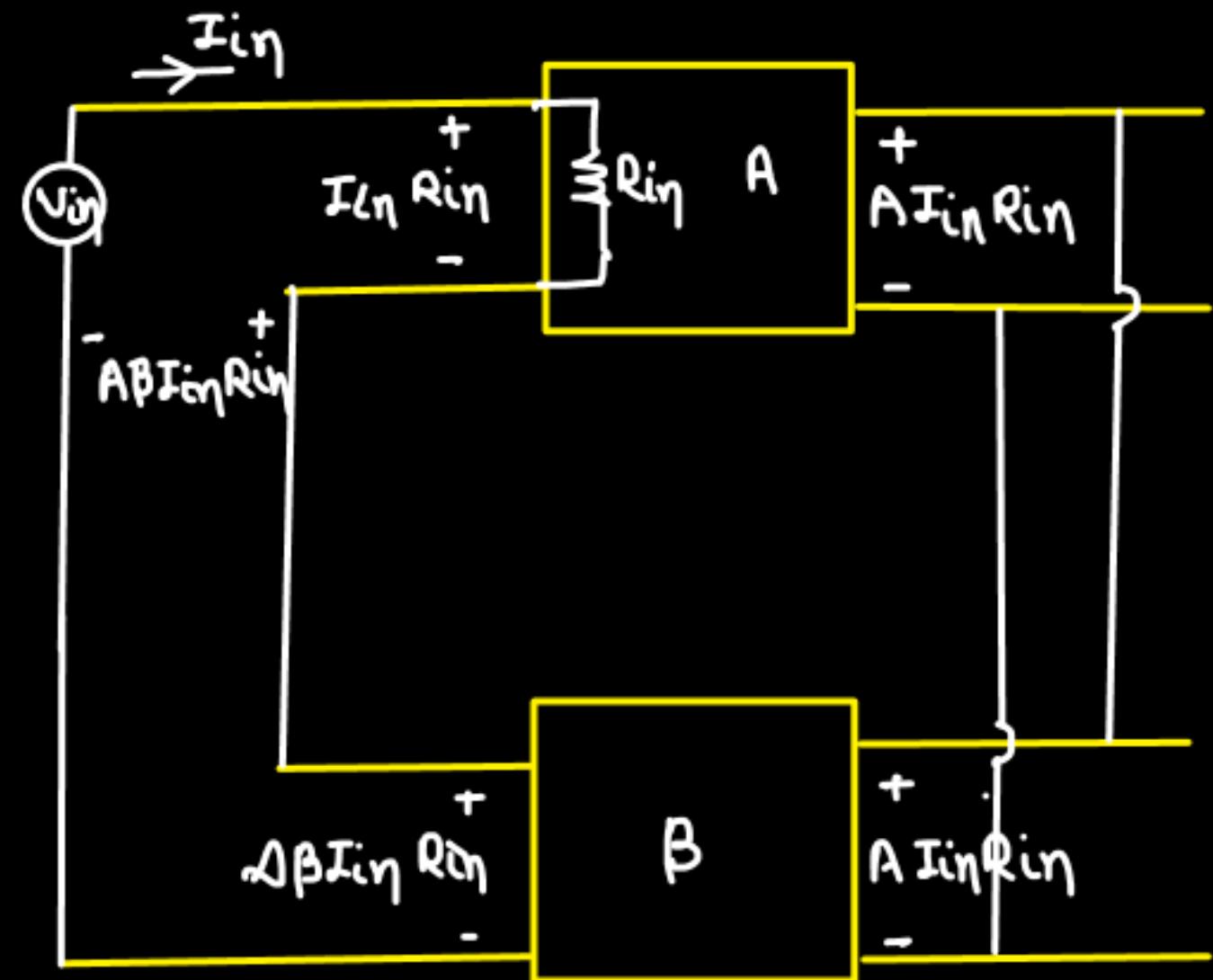


$$(R_{in})_f = \frac{V_{in}}{I_{in}}$$

$$V_{in} = I_{in} R_{in} + A \beta I_{in} R_{in}$$

$$\frac{V_{in}}{I_{in}} = (R_{in})_f = R_{in} (1 + A \beta)$$

### ③ Closed - Loop Output Impedance :-

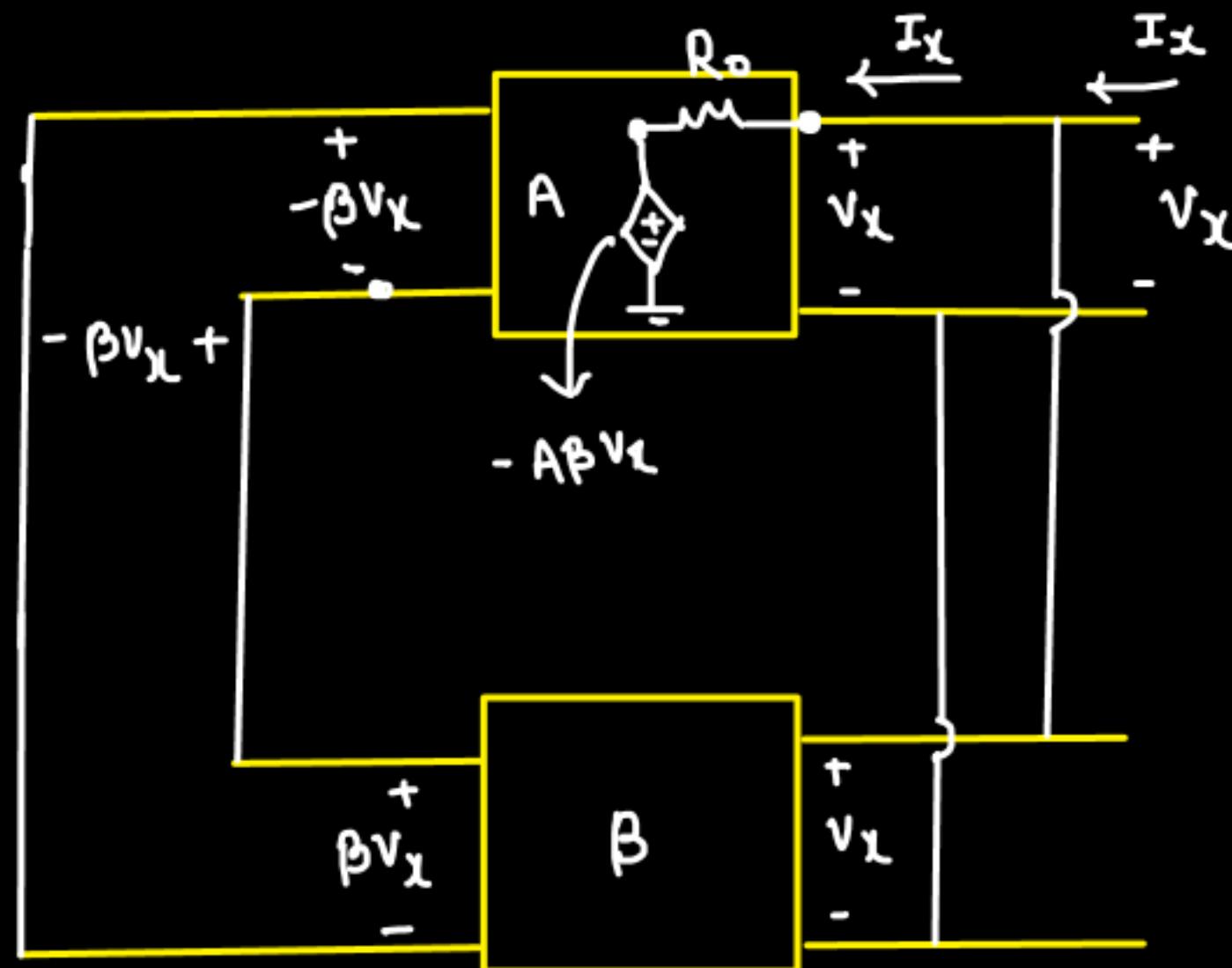

$$(R_o)_f = \frac{v_x}{I_x}$$

Assumption :-


$R_o$  is very small, so complete  $I_x$  will be flowing through  $R_o$ . (NOT in f/b path)

$$\frac{v_x - (-A\beta v_x)}{R_o} = I_x$$

$$\Rightarrow (R_o)_f = \frac{v_x}{I_x} = \frac{R_o}{1 + A\beta}$$

Example:-

Q.

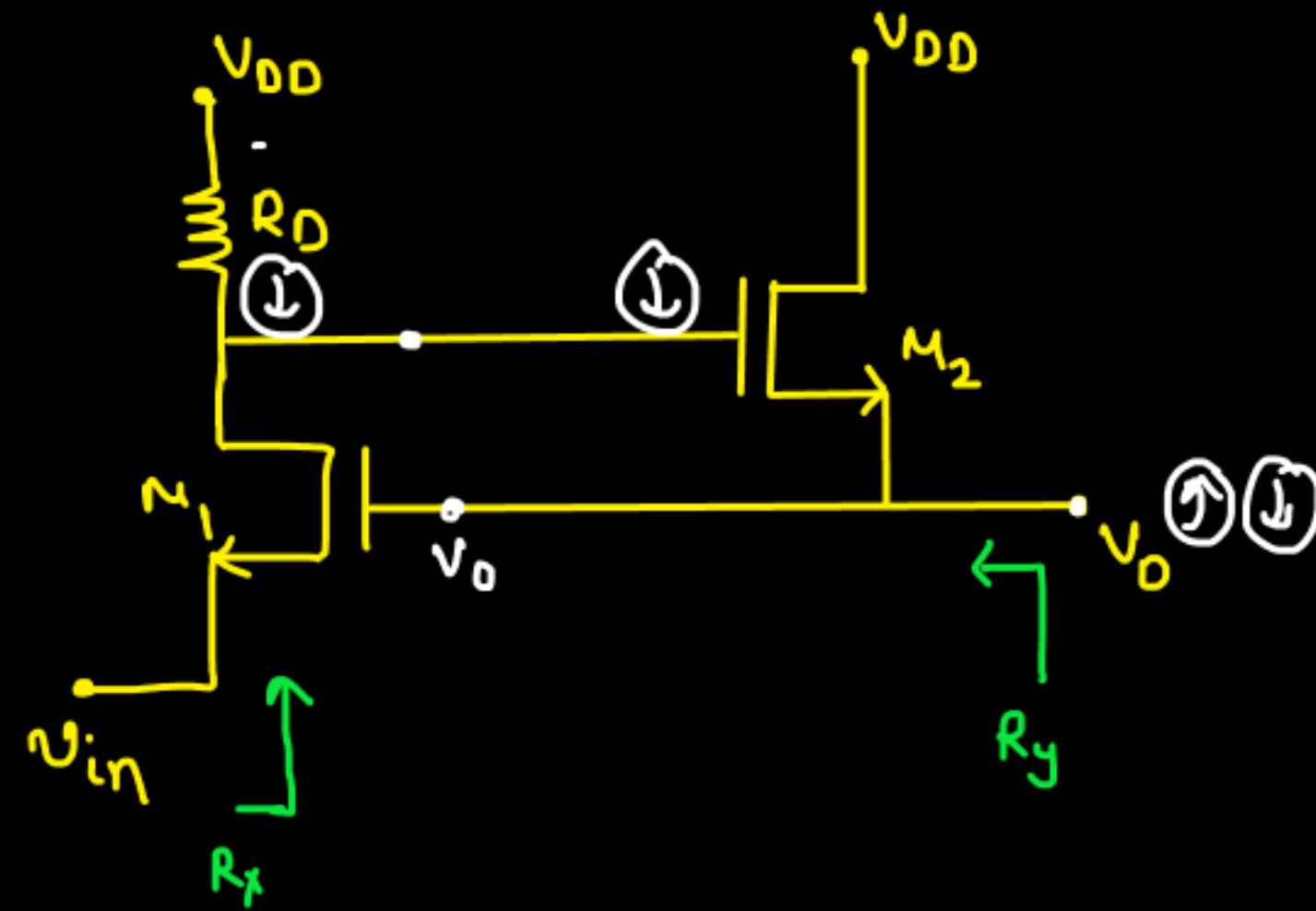

Take  $\lambda = 0$

Find  $R_x$ ,  $R_y$  and  $\frac{v_o}{v_i} = ?$

Negative f/b

Topology  $\rightarrow$  Voltage -  
Voltage  
f/b

## \* Short-cut to find f/b Topology:-

① For sampling, always look at o/p voltage

if there is voltage sampling


$$V_f = \beta V_o , I_f = G_m V_o$$

if we put  $V_o = 0V \Rightarrow$  There should be no f/b that is coming towards the i/p side.

$\Rightarrow$  if that is so, that means there is voltage sampling  
o/w current sampling

② For mixing, always check the i/p current. If current is mixed, then there is current mixing, o/w voltage mixing.

M-I w/o the concept of fib topology:-

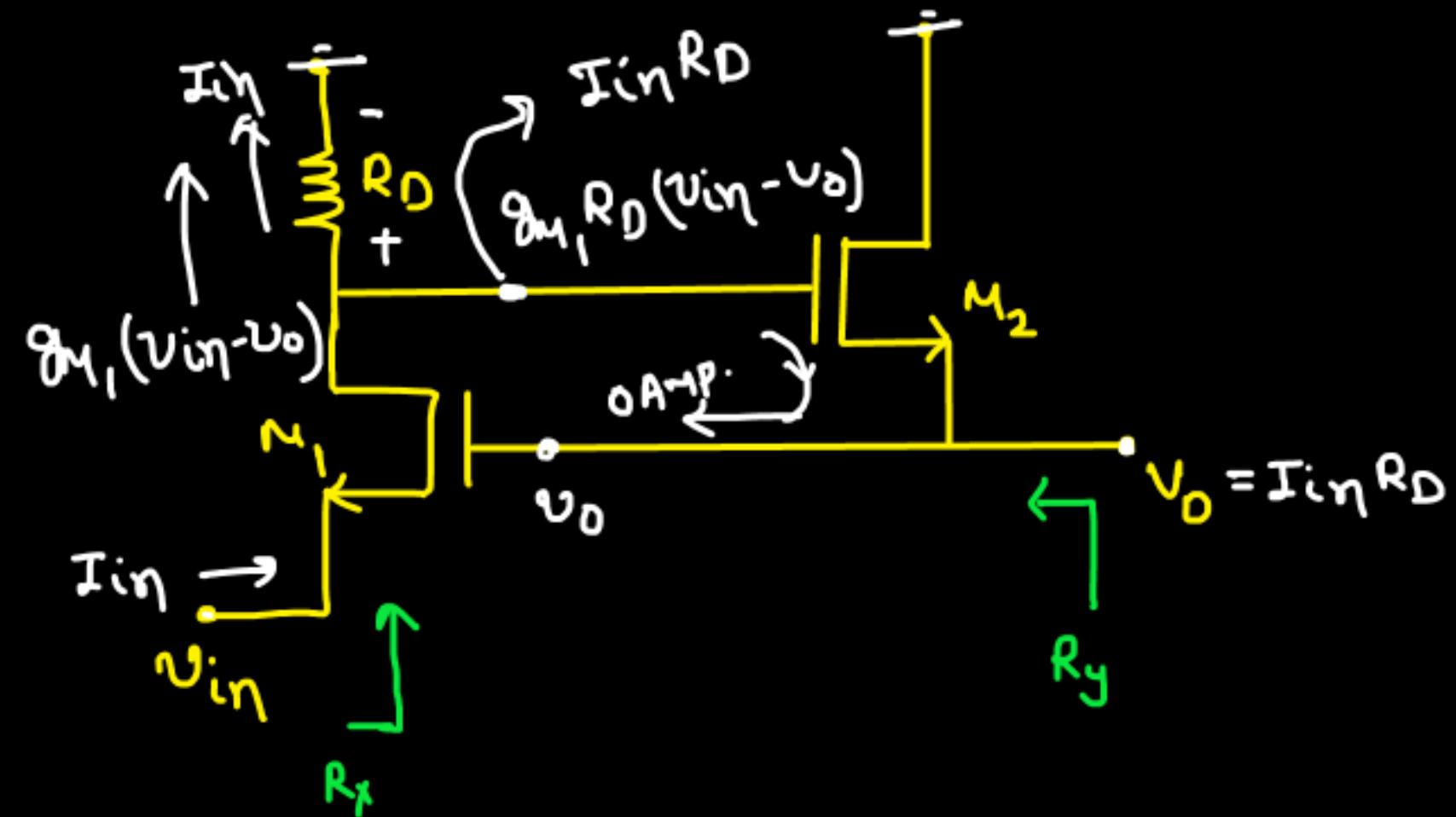

$$g_{M_1} R_D (V_{in} - V_o) = V_o$$


$$\frac{V_o}{V_{in}} = \frac{g_{M_1} R_D}{1 + g_{M_1} R_D}$$

$$R_x = \frac{V_{in}}{I_{in}}$$

$$g_{M_1} (V_{in} - I_{in} R_D) = I_{in}$$

$$g_{M_1} V_{in} = (g_{M_1} R_D + 1) I_{in}$$
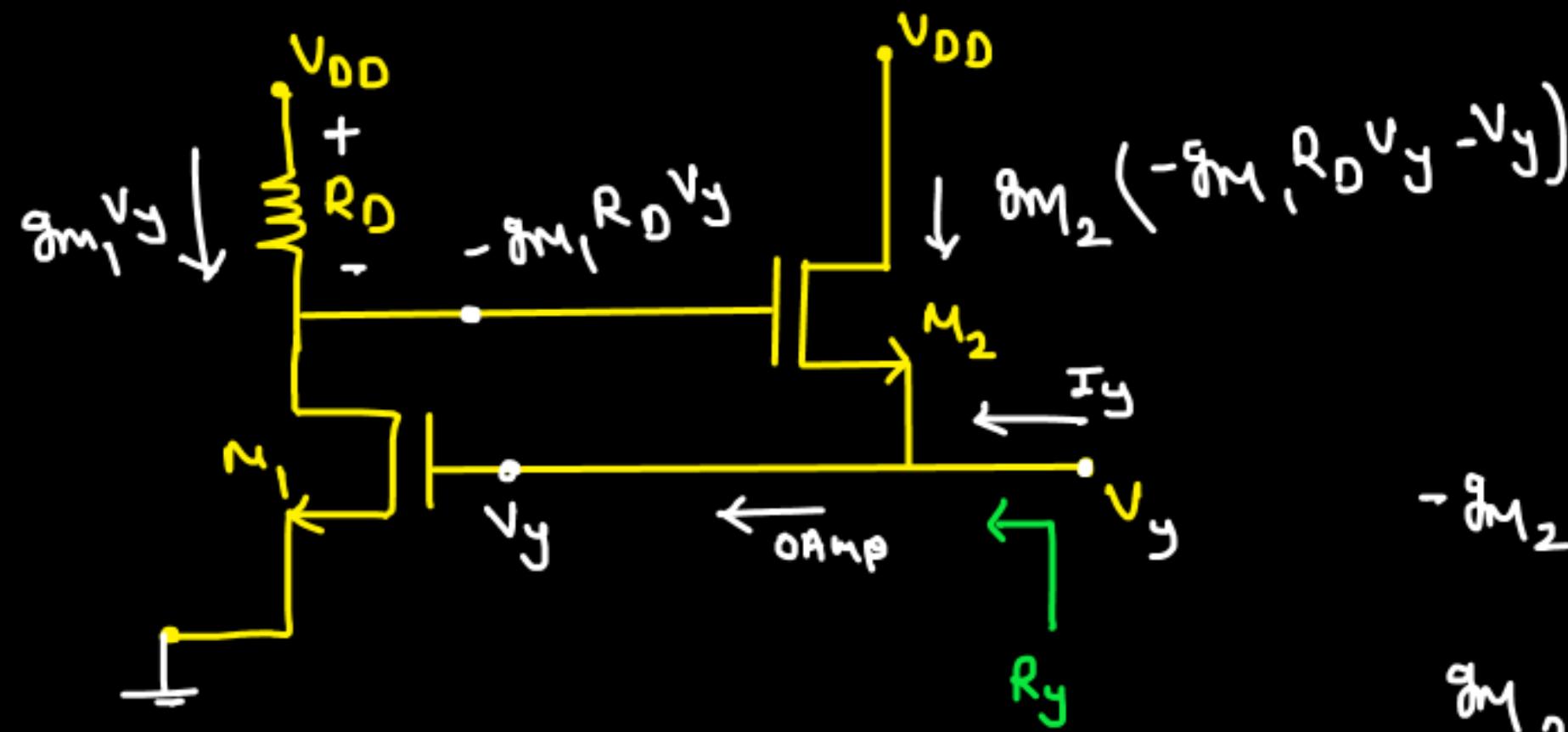
$$\frac{V_{in}}{I_{in}} = R_x = \frac{1}{g_{M_1}} (1 + g_{M_1} R_D)$$




$$-g_{m2}(-g_{m1}R_D V_y - V_y) = I_y$$

$$g_{m2}(g_{m1}R_D + 1)V_y = I_y$$



$$R_y = \frac{V_y}{I_y} = \frac{g_{m2}}{1 + g_{m1}R_D}$$

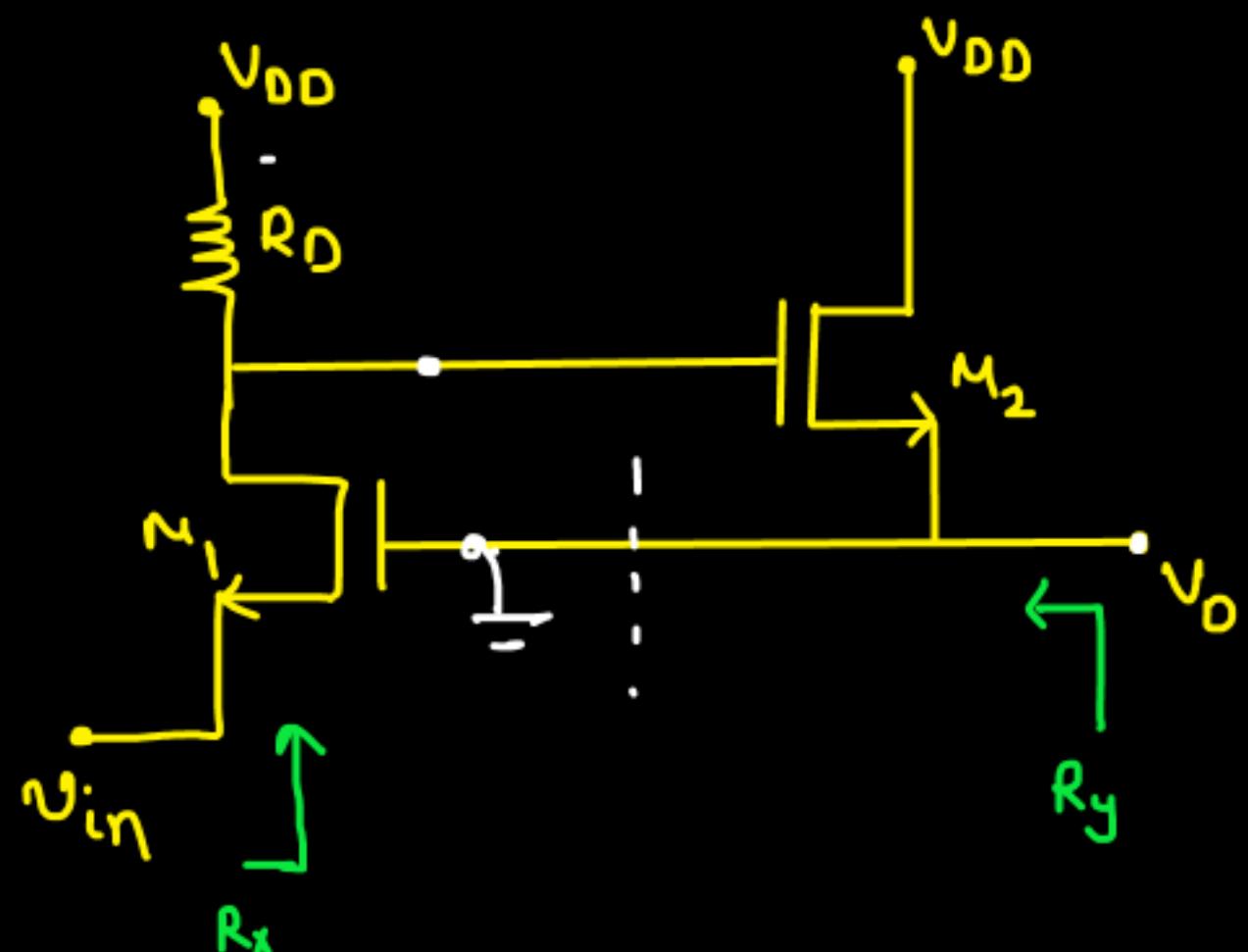\* with the concept of feedback Topology:-



→ Voltage - Voltage f/b

\* open loop gain = ? = A

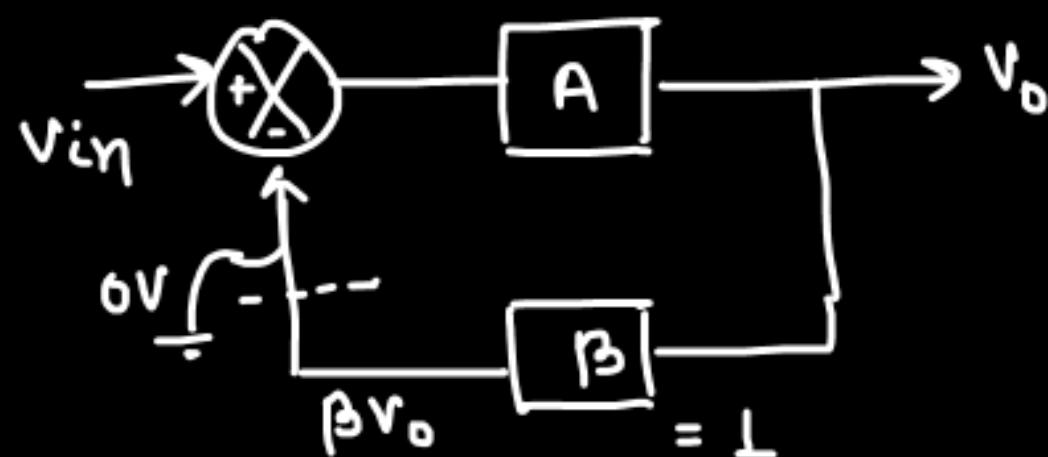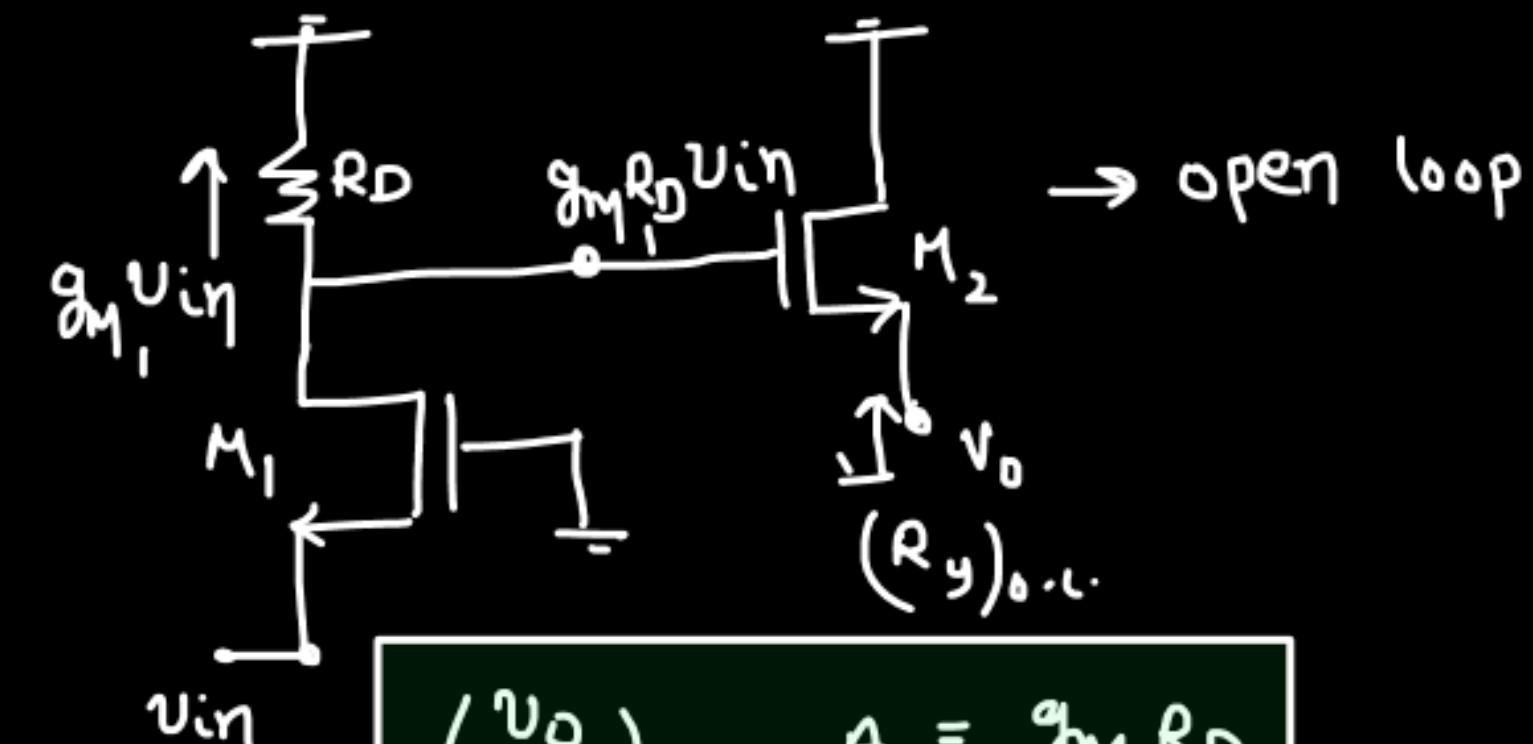

$$(R_x)_{o\cdot l\cdot} = \frac{1}{g_{m1}}$$

$$\beta = L$$

$$\left( \frac{V_o}{V_{in}} \right)_{o\cdot l\cdot} = A = g_{m1} R_D$$

$$(R_y)_{o\cdot l\cdot} = \frac{1}{g_{m2}}$$

For Voltage - Voltage f/b Topology :-

(in case of Neg. f/b)

① Close loop gain

$$(A_V)_f = \frac{A}{1 + \alpha\beta} = \frac{g_m R_D}{1 + g_m R_D}$$

② Close loop input impedance  $R_X = (R_X)_{o.l.} (1 + \alpha\beta)$


$$R_X = \frac{1}{g_m} (1 + g_m R_D)$$

③ Closed loop o/p impedance

$$R_Y = \frac{(R_Y)_{o.l.}}{1 + \alpha\beta} = \frac{1/g_m}{1 + g_m R_D}$$

\* Voltage - Current fb :-

( Shunt - Shunt )

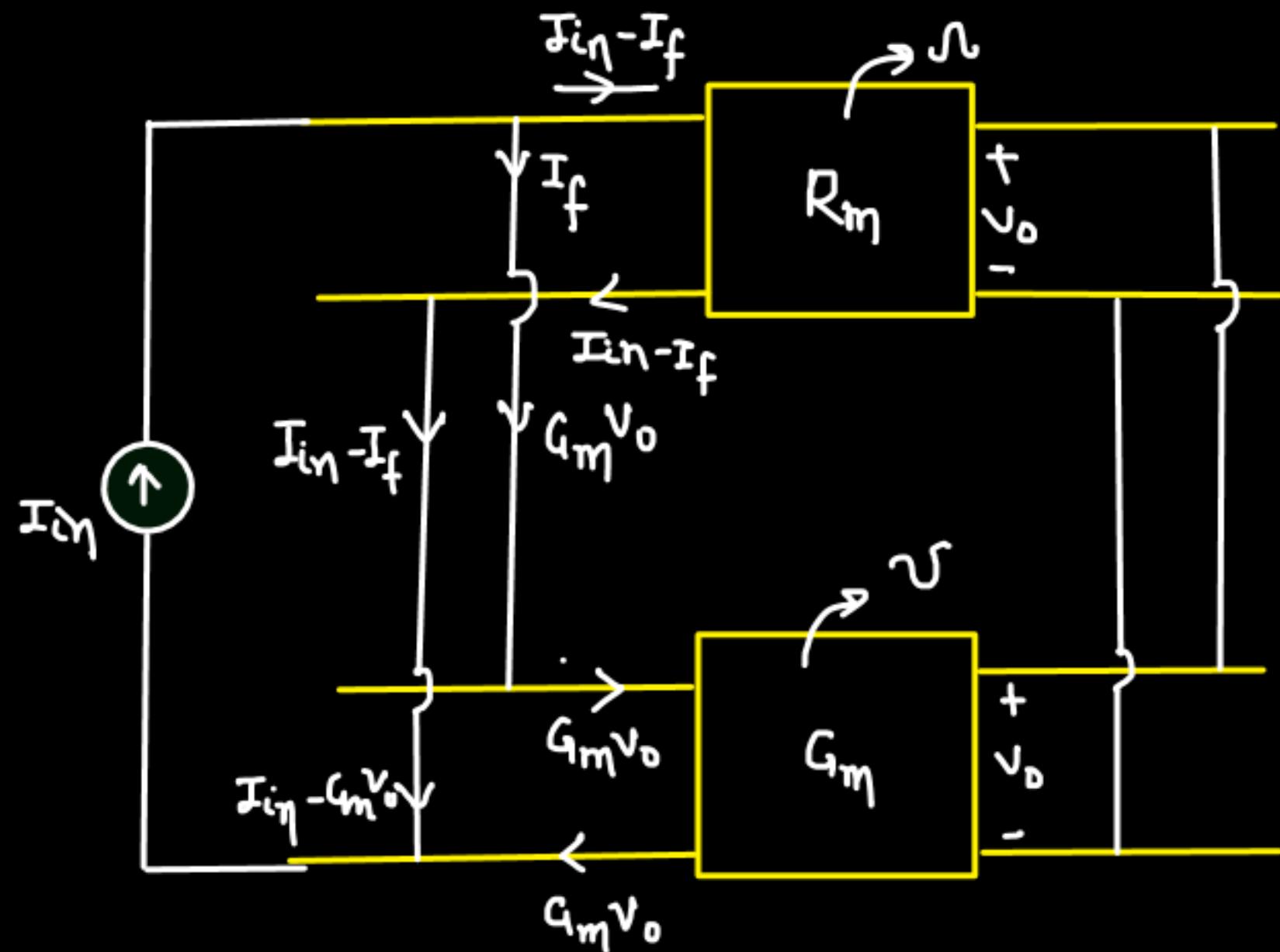


Open loop gain  $\rightarrow R_m (\infty)$

Open loop input impedance  $\rightarrow R_{in}$

Open loop output impedance  $\rightarrow R_o$

① Closed loop gain:-

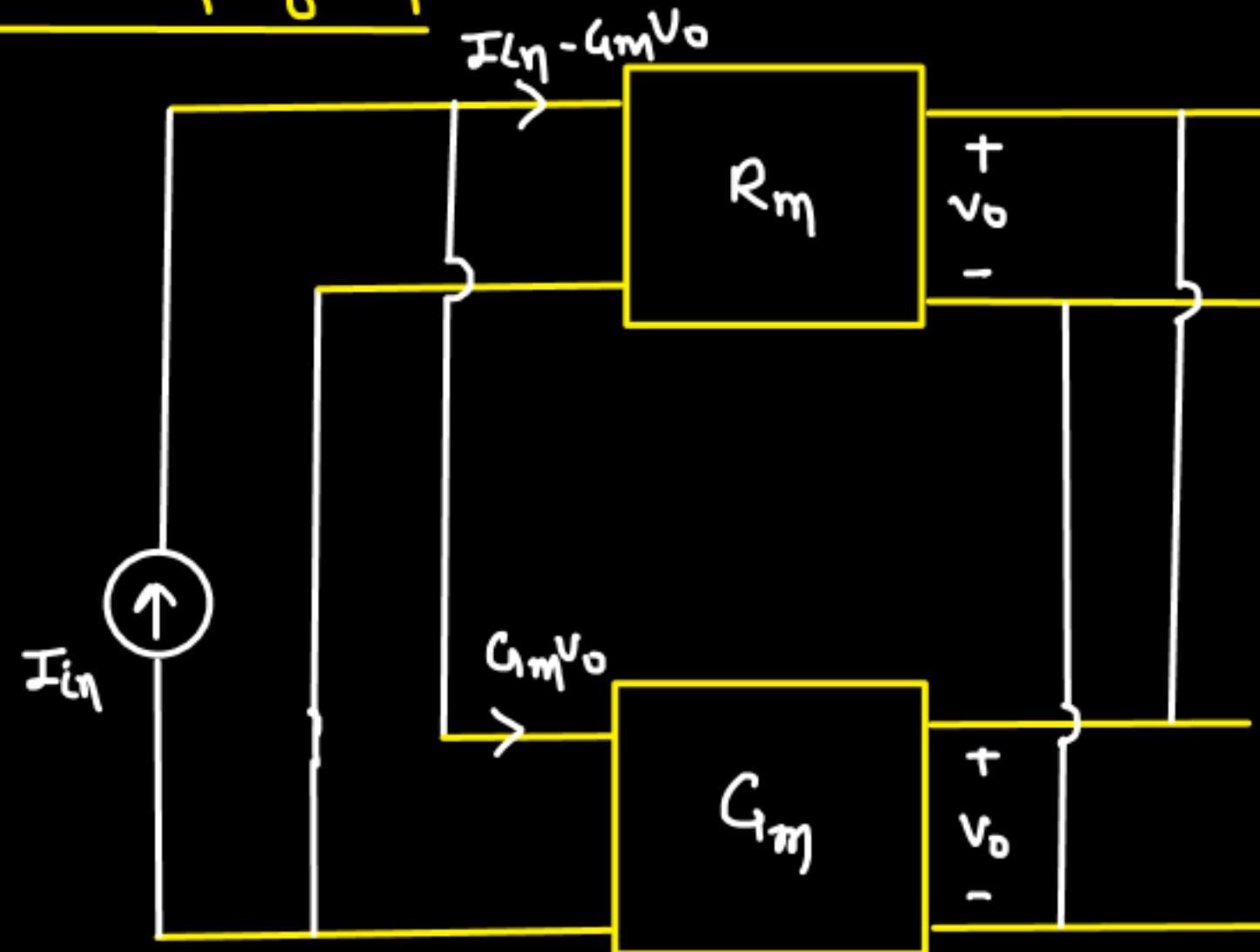


Closed loop gain

$$(\mathcal{A}_R)_f = \frac{V_o}{I_{in}}$$

$$(I_{in} - G_m V_o) R_m = V_o$$

$$\frac{V_o}{I_{in}} = (\mathcal{A}_R)_f = \frac{R_m}{1 + G_m R_m}$$

② Closed Loop Input Resistance :-

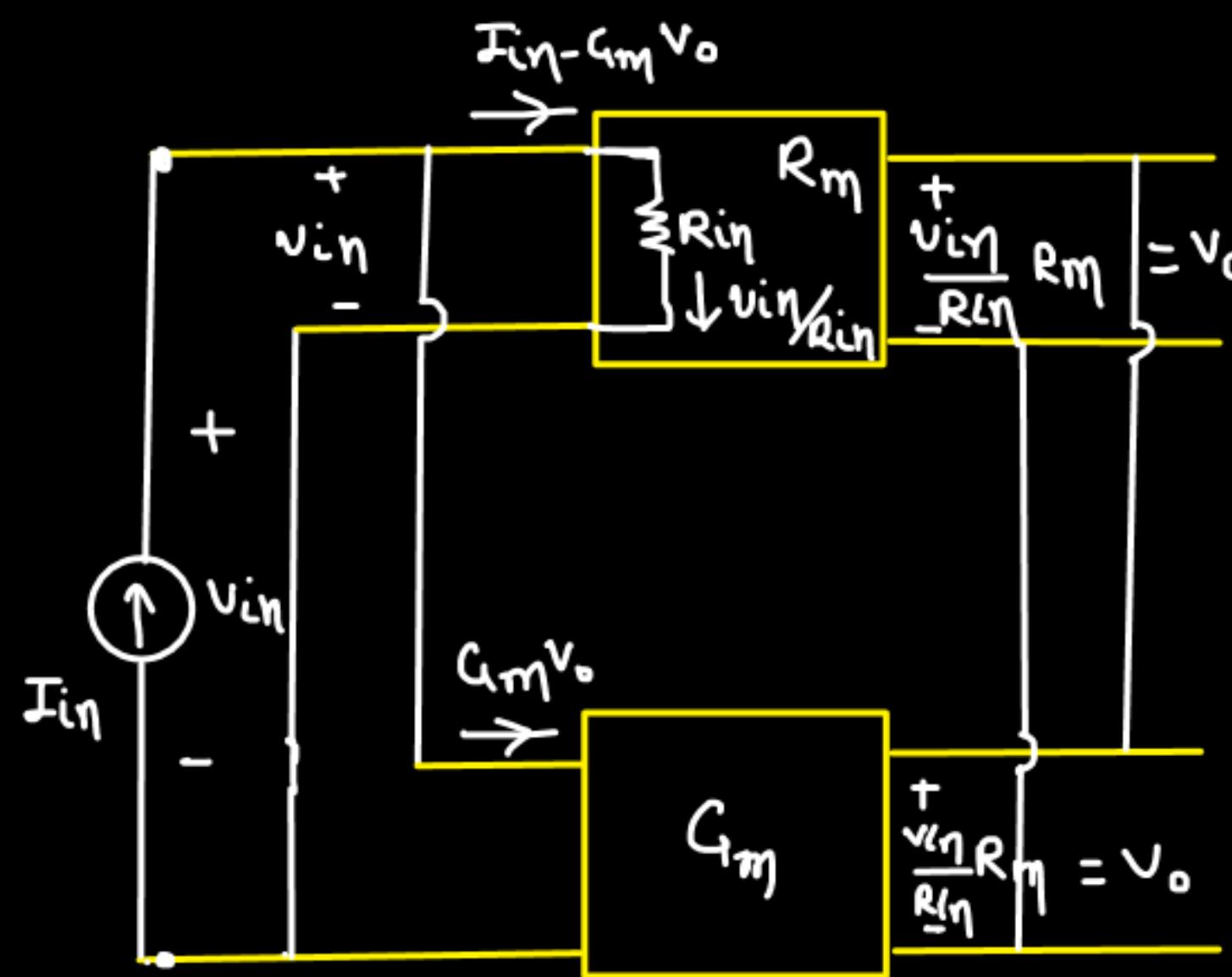

$$(R_{in})_f = \frac{v_{in}}{I_{in}}$$

$$\frac{v_{in}}{R_{in}} = I_{in} - G_m v_o$$


$$\frac{v_{in}}{R_{in}} = I_{in} - \frac{G_m v_{in}}{R_{in}} R_m$$

$$v_{in} [1 + G_m R_m] = R_{in} I_{in}$$

→

$$(R_{in})_f = \frac{R_{in}}{1 + G_m R_m}$$

### ③ Closed Loop Output Impedance:-

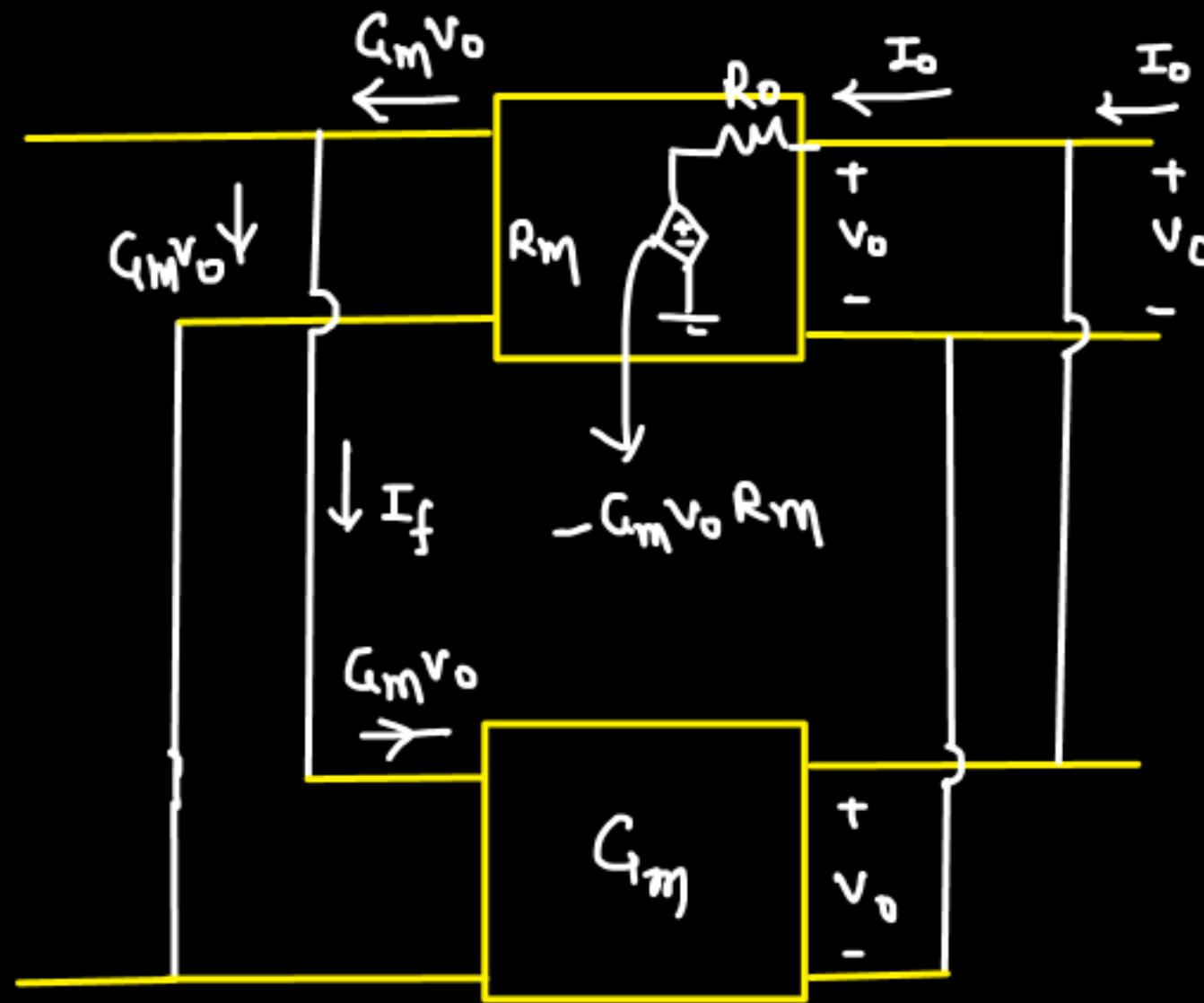

$$(R_o)_f = \frac{v_o}{I_o}$$

Assumption:-


Complete  $I_o$  is flowing through  $R_o$ .

$$\frac{v_o + G_m v_o R_m}{R_o} = I_o$$

PP

$$\frac{v_o}{I_o} = (R_o)_f = \frac{R_o}{1 + G_m R_m}$$

Eg:-

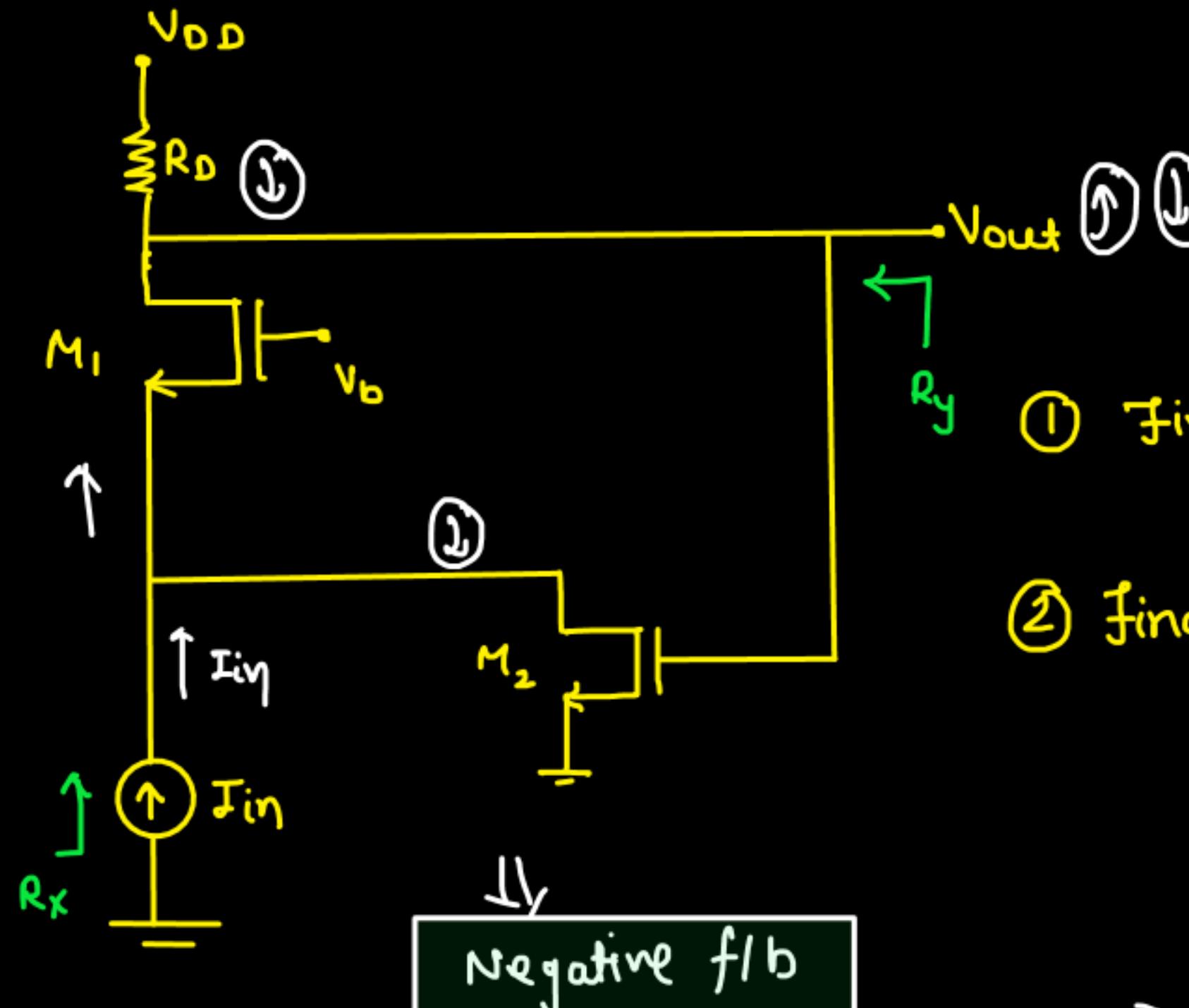

Take  $\lambda = 0$


① Find  $\frac{V_o}{I_{in}}$

② Find  $R_f$  and  $R_y$

current mixing  
voltage sampling


$\Rightarrow$  Voltage Current f/b

M-I w/o using the concept of f/b

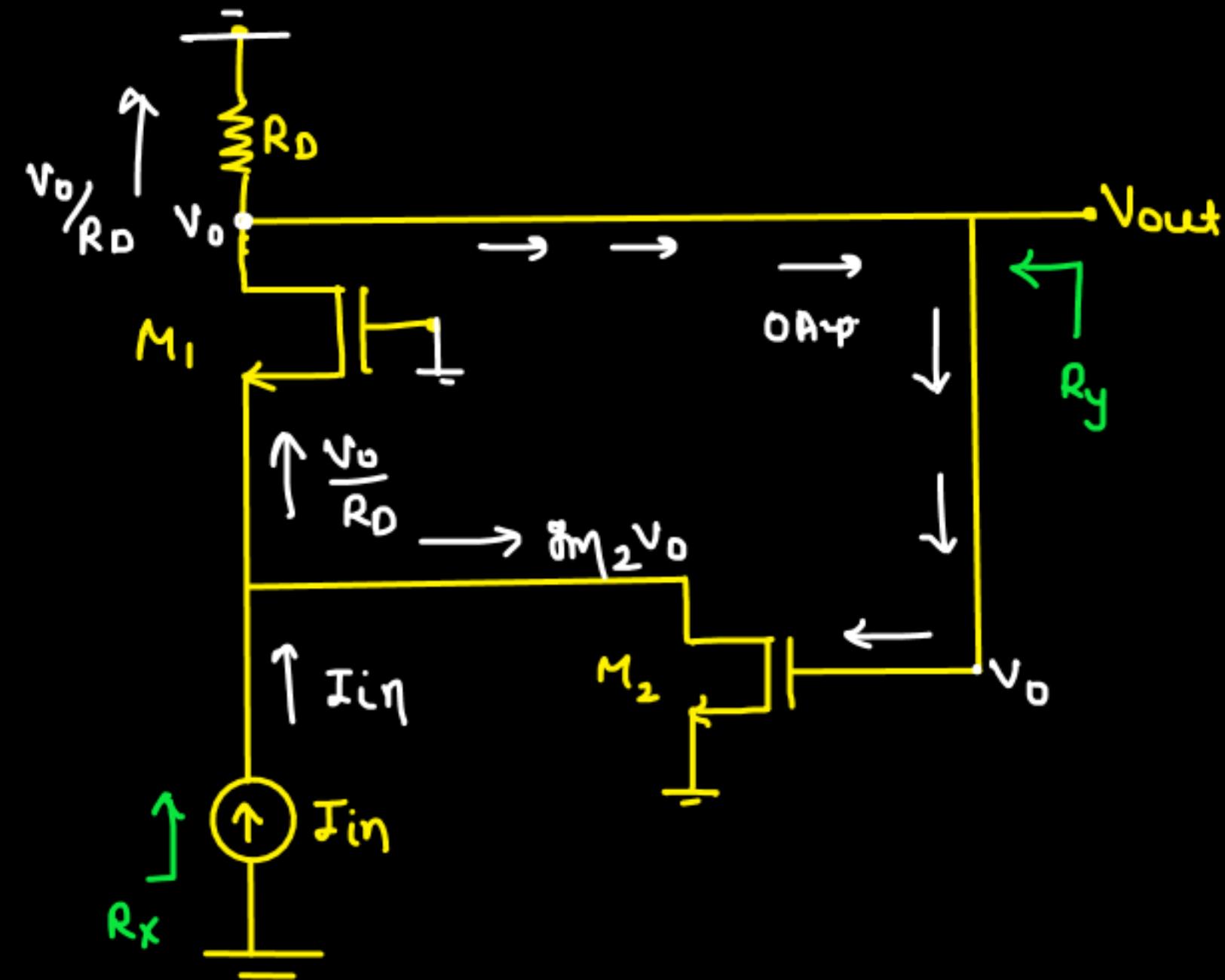

$$\textcircled{1} \quad I_{in} = g_{M_2} v_o + \frac{v_o}{R_D}$$

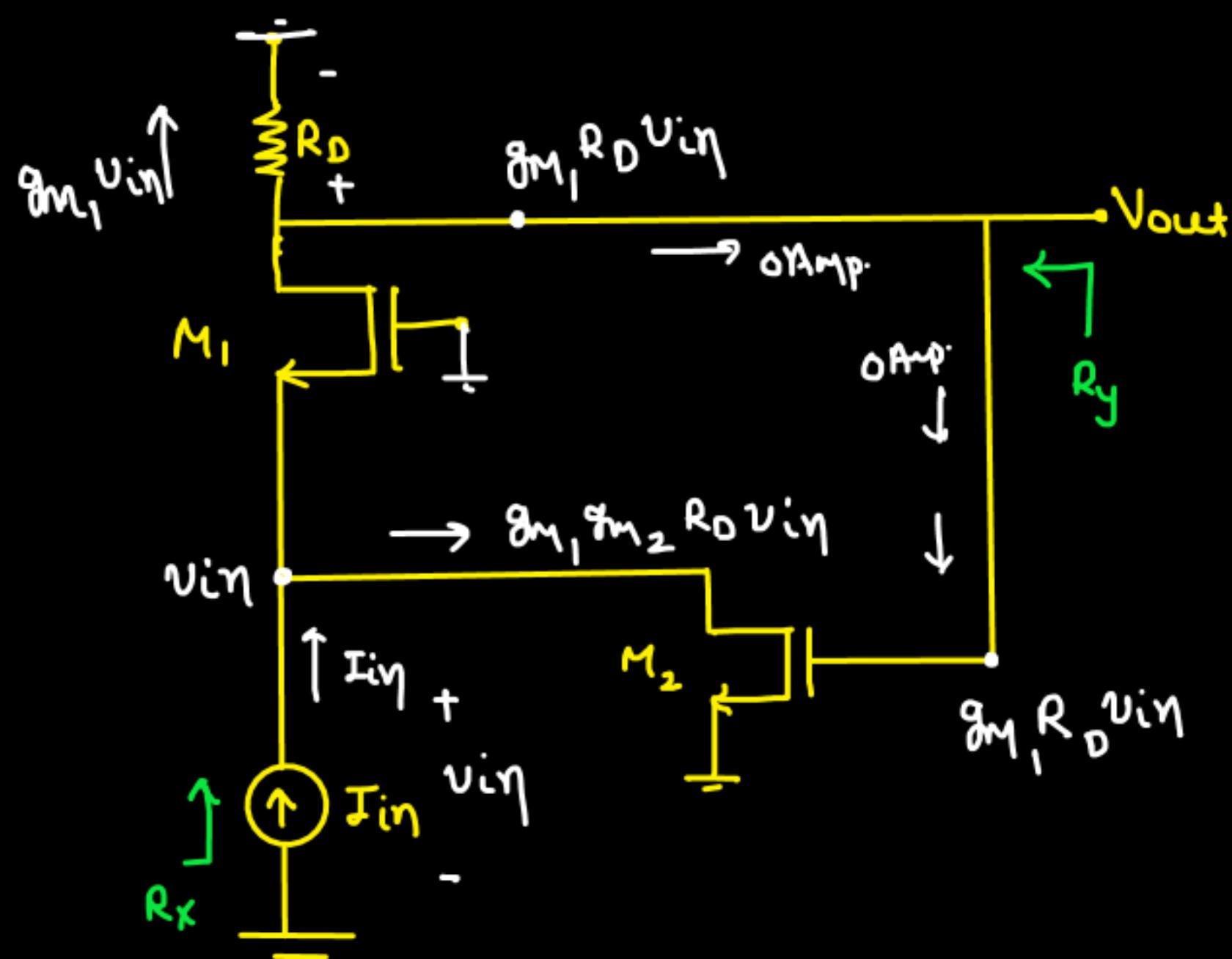
$$\frac{v_o}{I_{in}} = \frac{R_D}{g_{M_2} R_D + 1}$$



$$R_X = \frac{v_{in}}{I_{in}}$$

$$I_{in\eta} = g_m v_{in} + g_m g_m R_D v_{in}$$
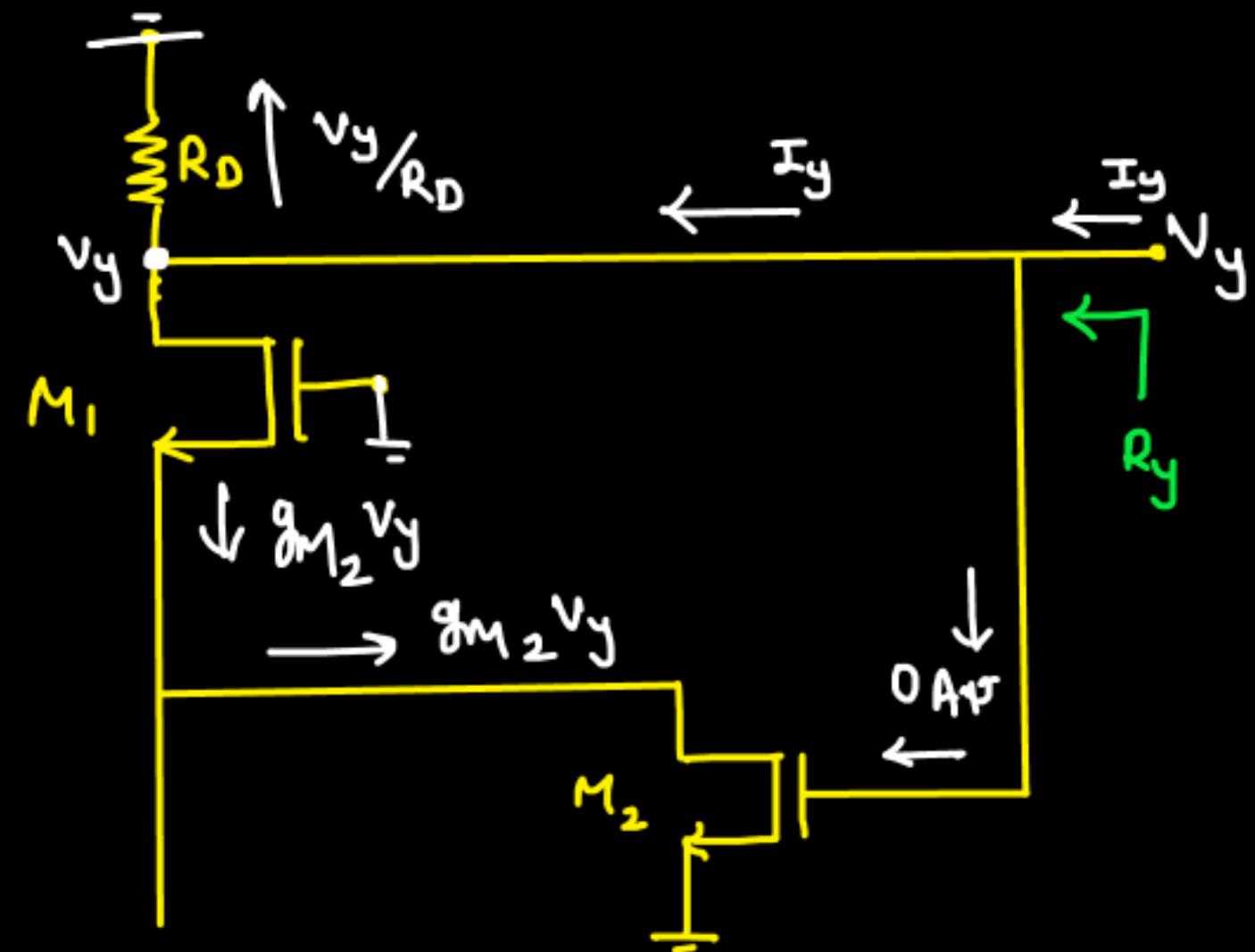
$$\boxed{\frac{v_{in}}{I_{in}} = \frac{1/g_m}{1 + g_m R_D}}$$




$$I_y = \frac{v_y}{R_D} + g_m M_2 v_y$$

$$R_y = R_D \parallel \frac{1}{g_m M_2}$$



$$R_y = \frac{R_D}{1 + g_m M_2 R_D}$$

M-II with the concept of f/b topology:-

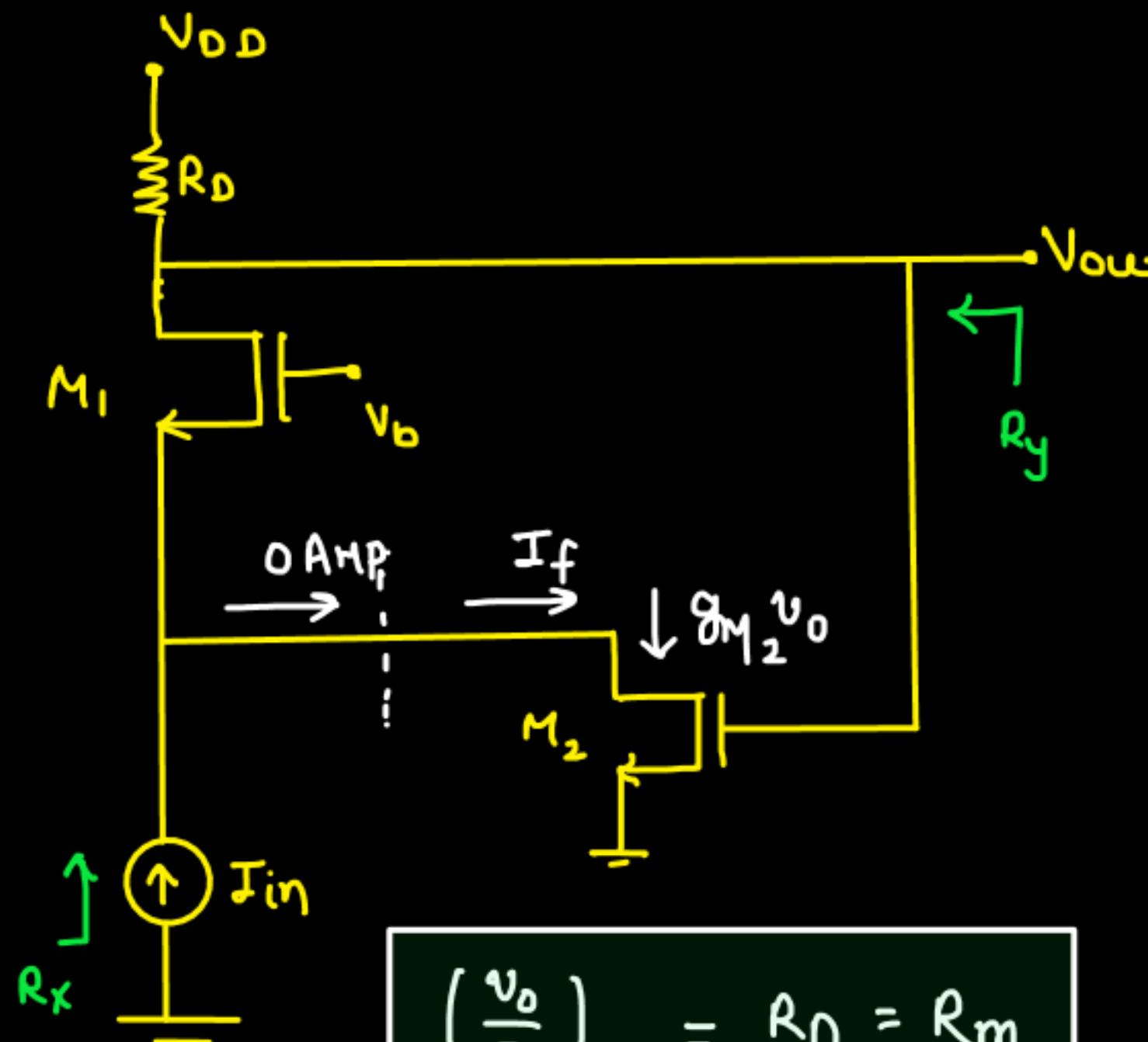

$$\left( \frac{V_o}{I_{in}} \right)_{O.L.} = R_D = R_m$$

$$(R_x)_{O.L.} = \frac{1}{g_m_1}$$

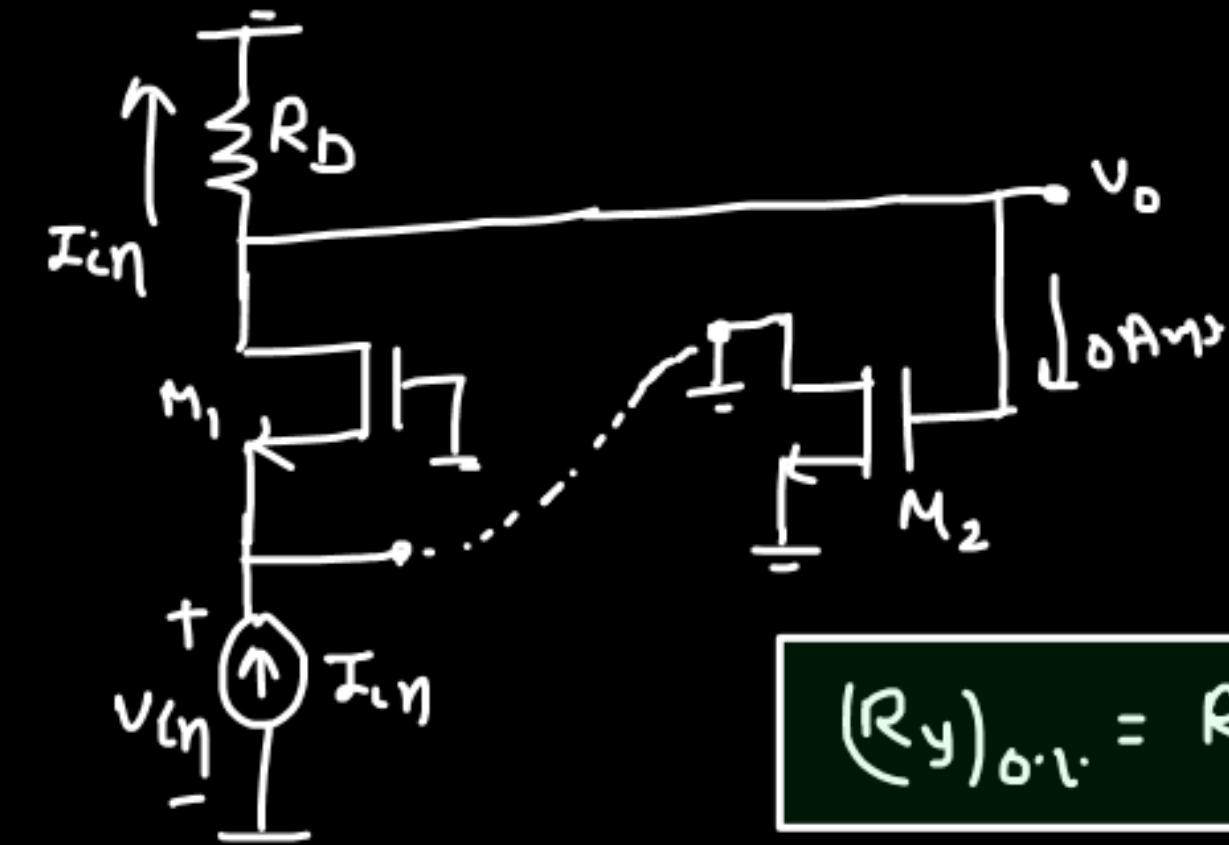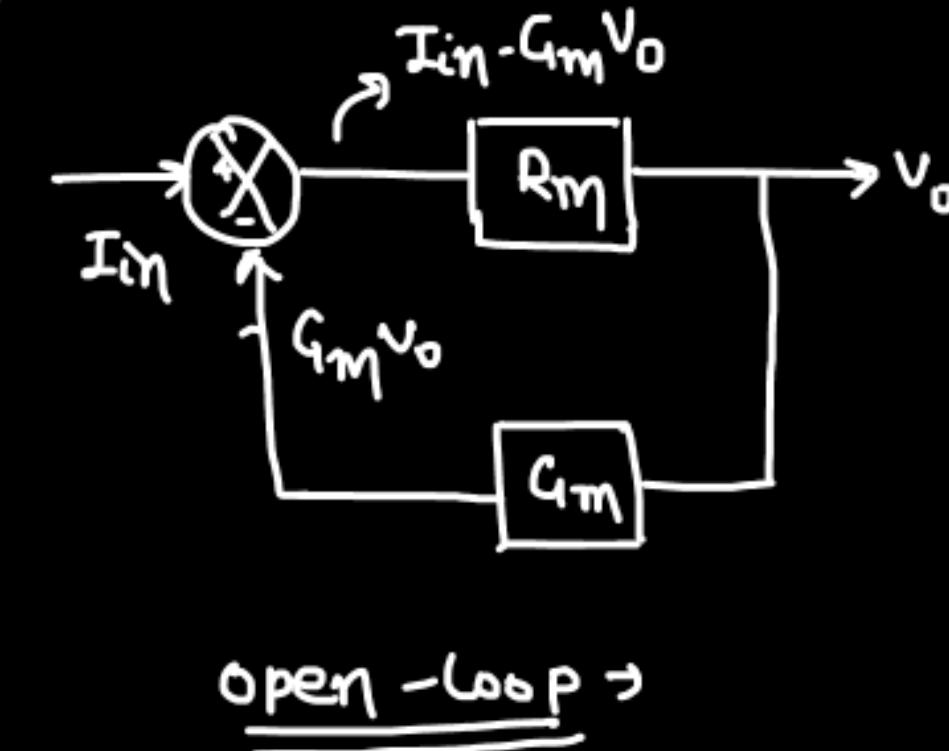

$$(R_y)_{O.L.} = R_D$$

$$I_f = g_m v_o$$

$$\frac{I_f}{v_o} = G_m = g_m$$


① Closed loop gain  $= \frac{R_D}{1 + g_m R_m} = \frac{R_D}{1 + g_m R_D}$

② Closed loop input impedance

$$(R_{in})_f = \frac{1/g_m}{1 + g_m R_D}$$

③  $(R_o)_f = \frac{R_D}{1 + g_m R_D}$
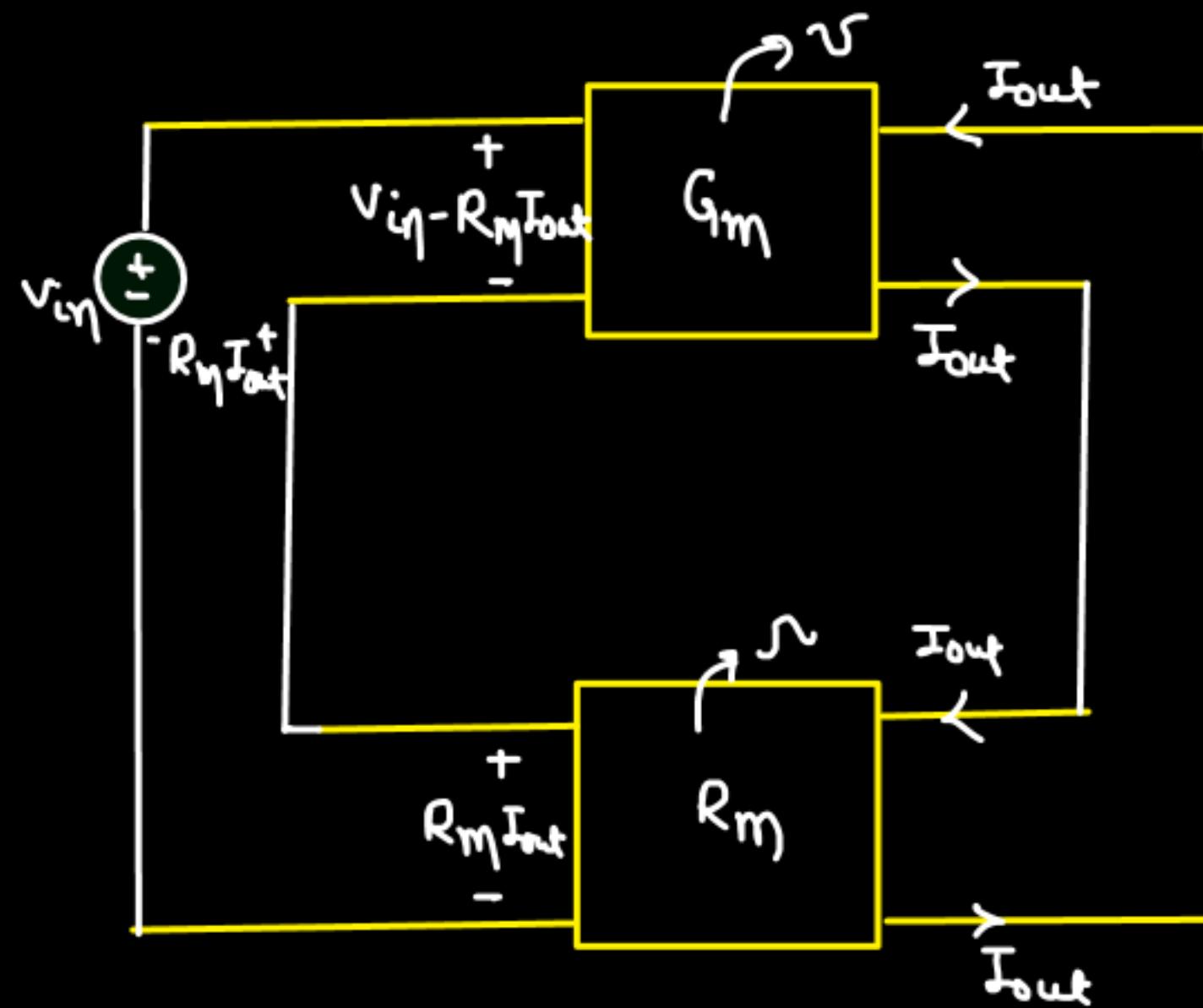
## \* Current-Voltage feedback :- (series-series)



open loop gain =  $G_m$

open loop i/p impedance =  $R_{in}$

open loop o/p impedance =  $R_o$

① Closed loop gain =  $\frac{G_m}{1 + G_m R_m}$


② Closed loop input impedance

$$(R_i)_f = R_{in} (1 + G_m R_m)$$

③ Closed loop o/p impedance :-


$$(R_o)_f = R_o (1 + G_m R_m)$$

Eg. -

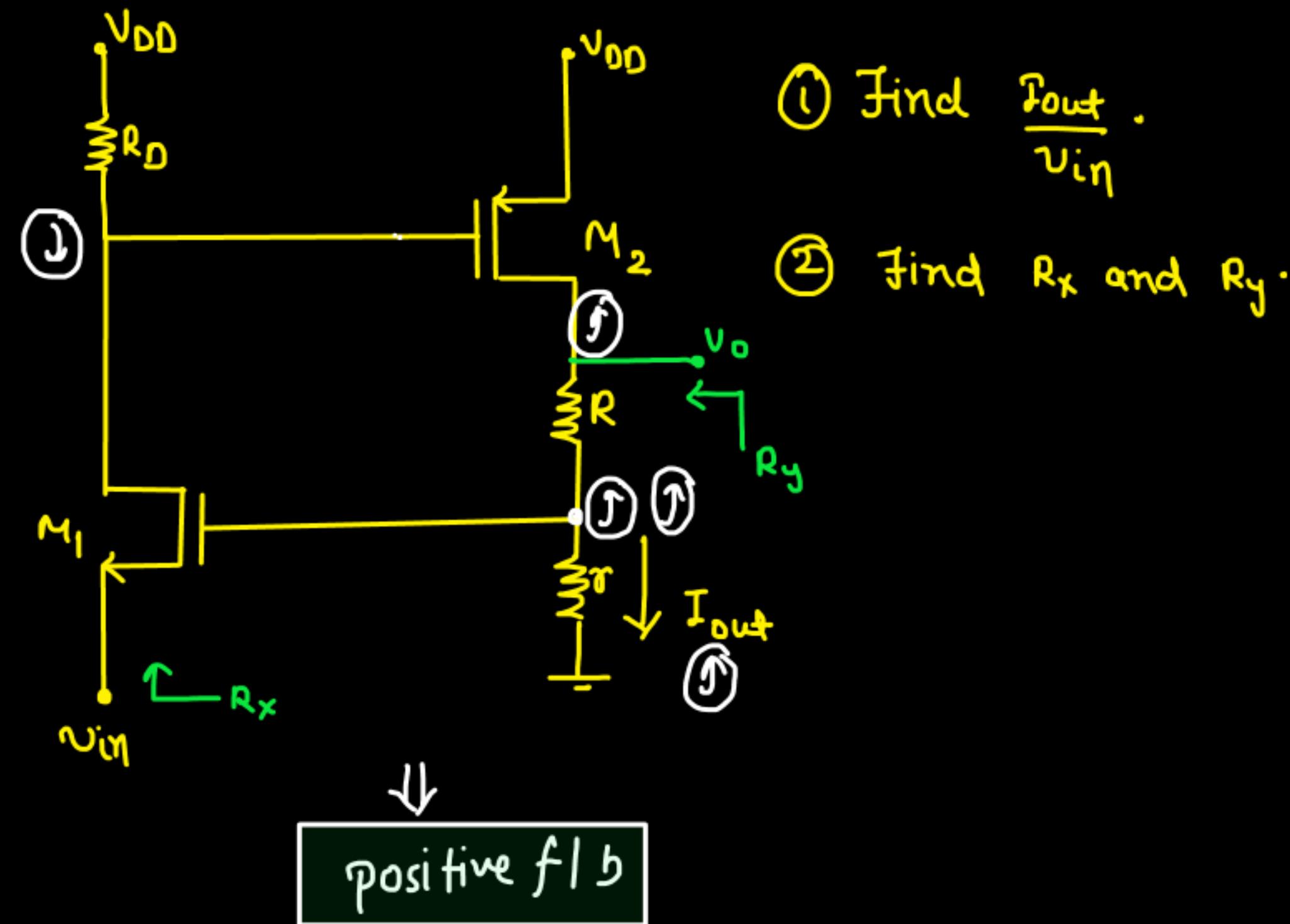


M-I

w/o the concept of feedback:-

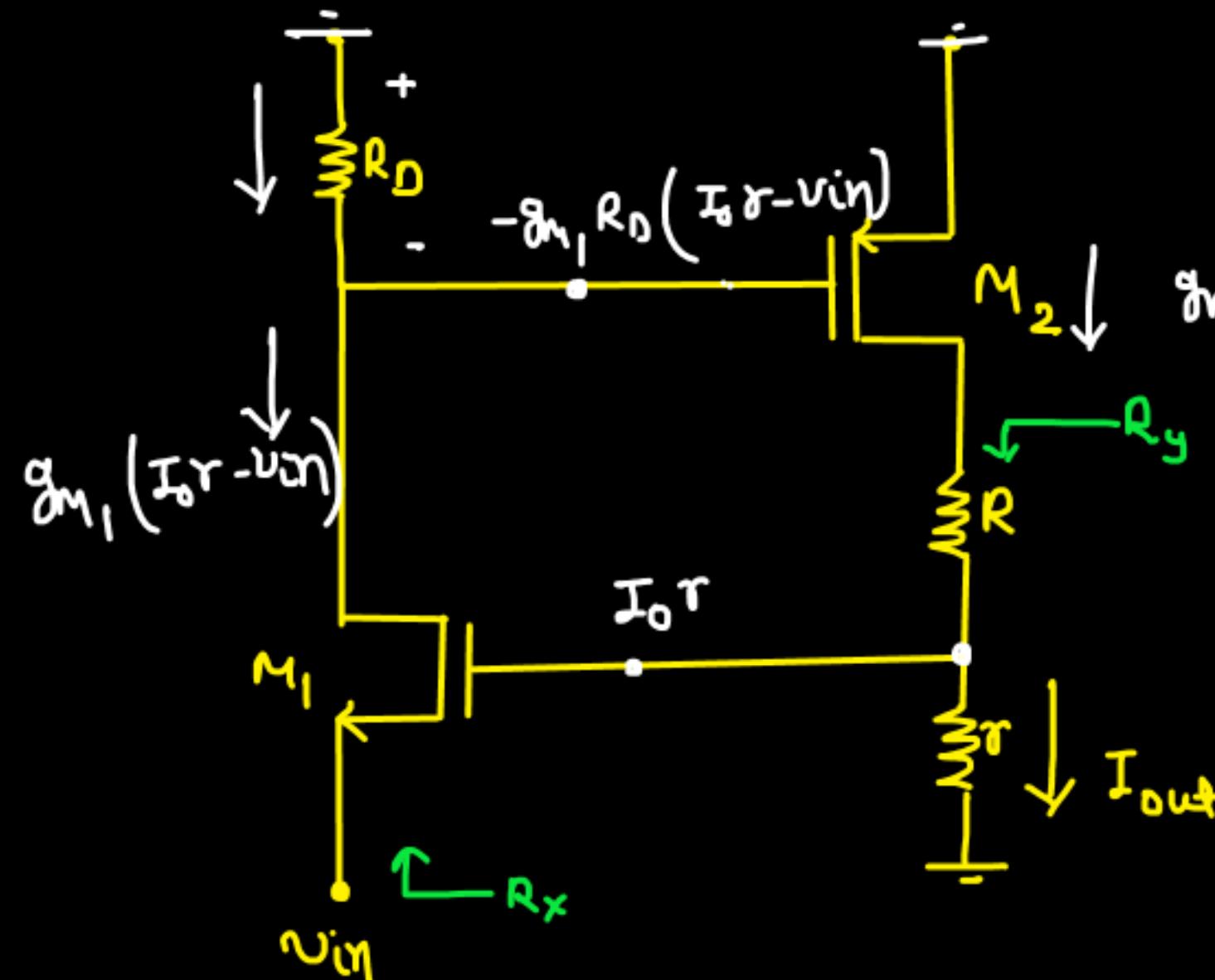

$$g_{m_2} g_{m_1} R_D r I_0 - I_0 = g_{m_1} g_{m_2} R_D v_{in}$$

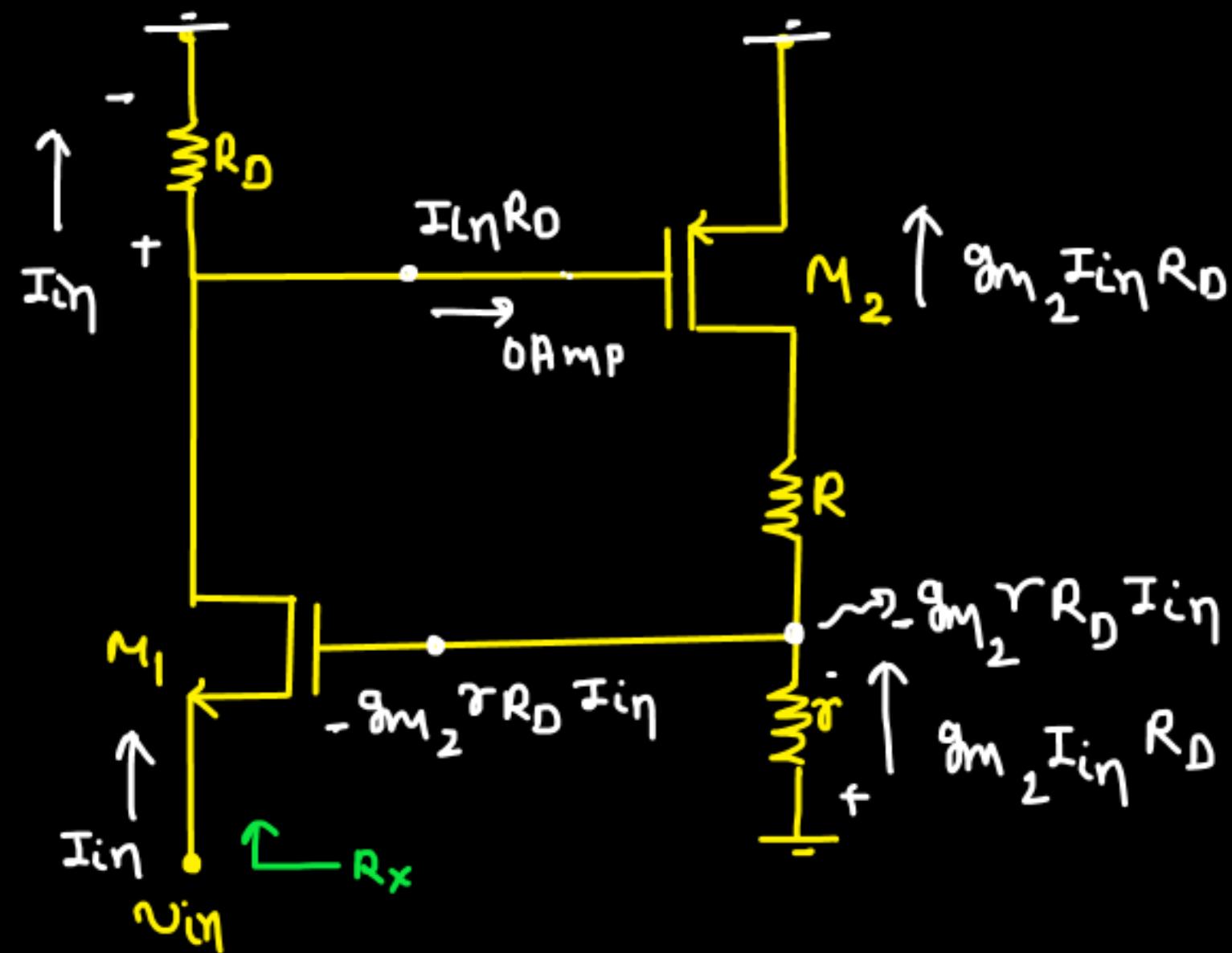
$$\frac{I_0}{v_{in}} = \frac{-g_{m_1} g_{m_2} R_D}{1 - g_{m_1} g_{m_2} R_D r}$$



$$g_m_1(v_{in} + g_m_2 r R_D I_{in}) = I_{in}$$

$$g_m_1 v_{in} = I_{in} [1 - g_m_1 g_m_2 r R_D]$$
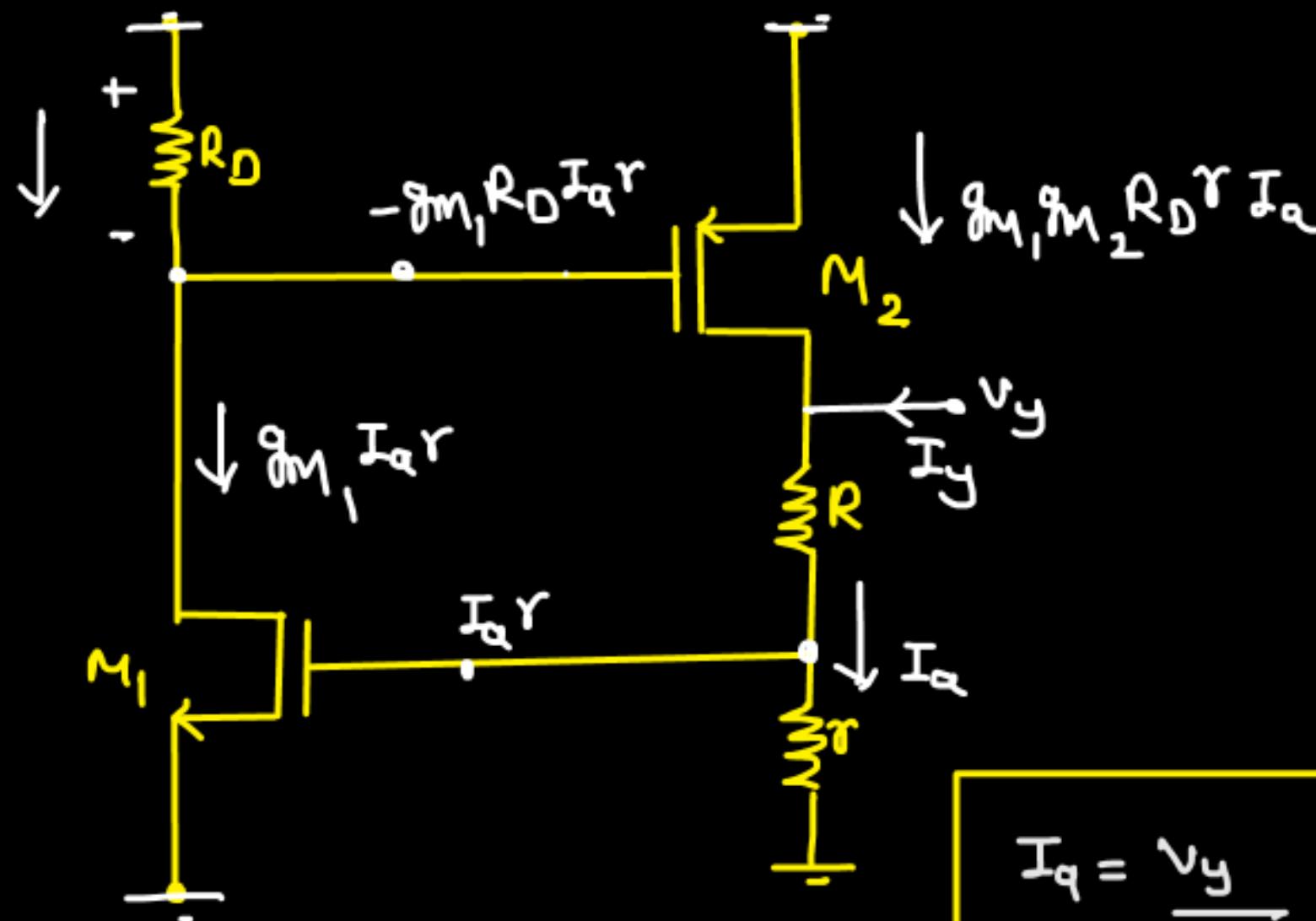
$$\frac{v_{in}}{I_{in}} = \left[ 1 - g_m_1 g_m_2 r R_D \right] \frac{1}{g_m_1}$$



$$R_y = \frac{v_y}{I_y}$$

$$I_q = \frac{v_y}{r + R}$$

$$\begin{aligned} & \downarrow g_{m_1} g_{m_2} R_D r I_q \\ & \xrightarrow{\quad I_y \quad} v_y \\ & \downarrow I_q \end{aligned}$$


$$I_y + \frac{g_{m_1} g_{m_2} R_D r v_y}{r + R} = \frac{v_y}{r + R}$$

if

$$\frac{v_y}{I_y} > R_y = \frac{r + R}{1 - g_{m_1} g_{m_2} R_D r}$$


$$I_y = \left( \frac{1 - g_{m_1} g_{m_2} R_D r}{r + R} \right) v_y$$

M-I with the concept of f/b Topology:-

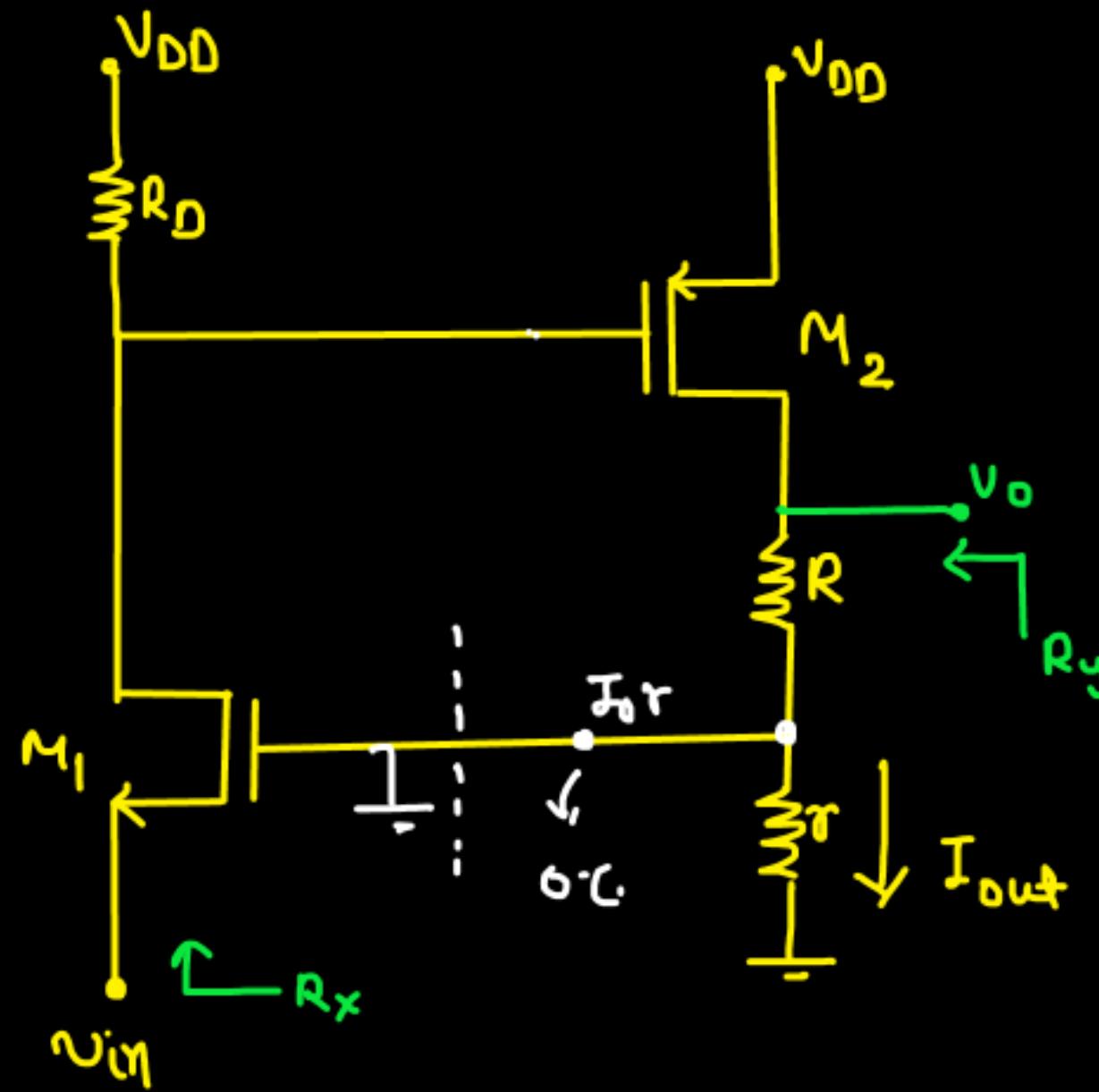

Current - Voltage f/b


Voltage mixing , Current sampling

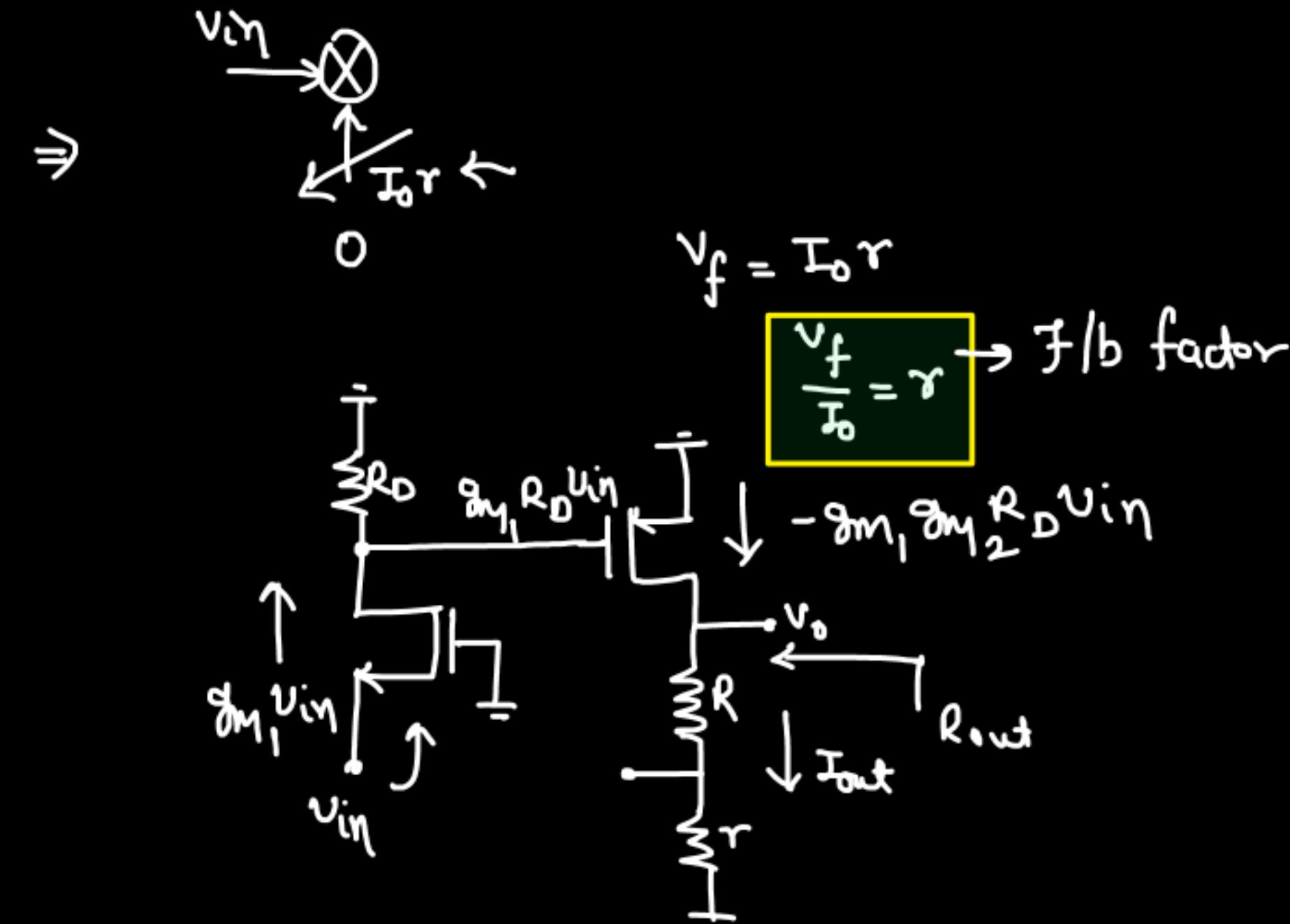

$$\left( \frac{I_{out}}{V_{in}} \right)_{o.c.} = -g_{m1} g_{m2} R_D$$

$$(R_{in})_{0-L} = \frac{1}{g_m_1}$$

$$(R_o)_{0-L} = R + r$$

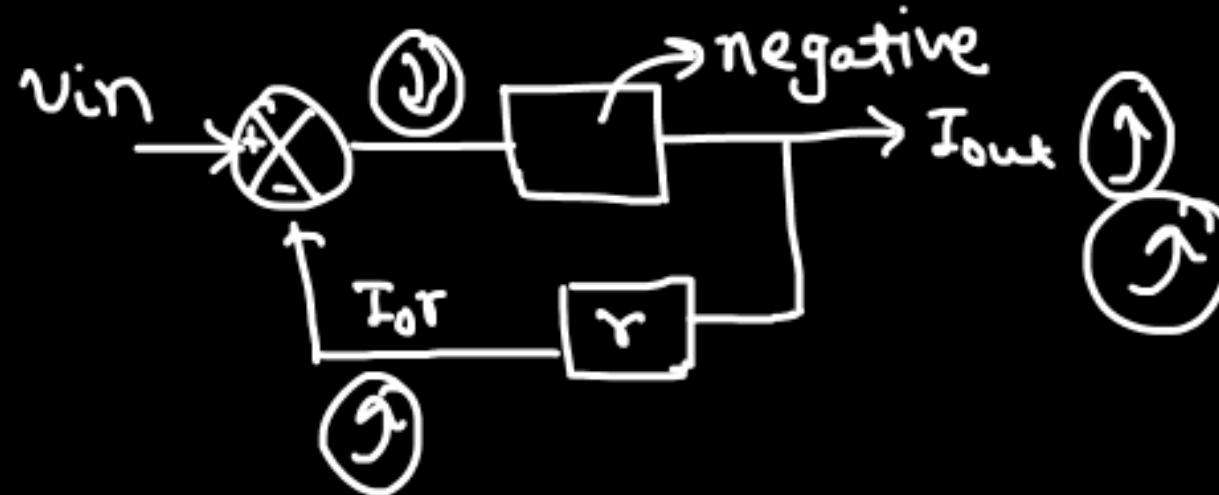


\* Closed loop gain  $= \frac{-g_m_1 g_m_2 R_D}{1 - g_m_1 g_m_2 R_D r}$

\*  $R_x = \frac{1}{g_m_1} [1 - g_m_1 g_m_2 R_D r]$

\*  $R_y = (R + r) [1 - g_m_1 g_m_2 R_D r]$
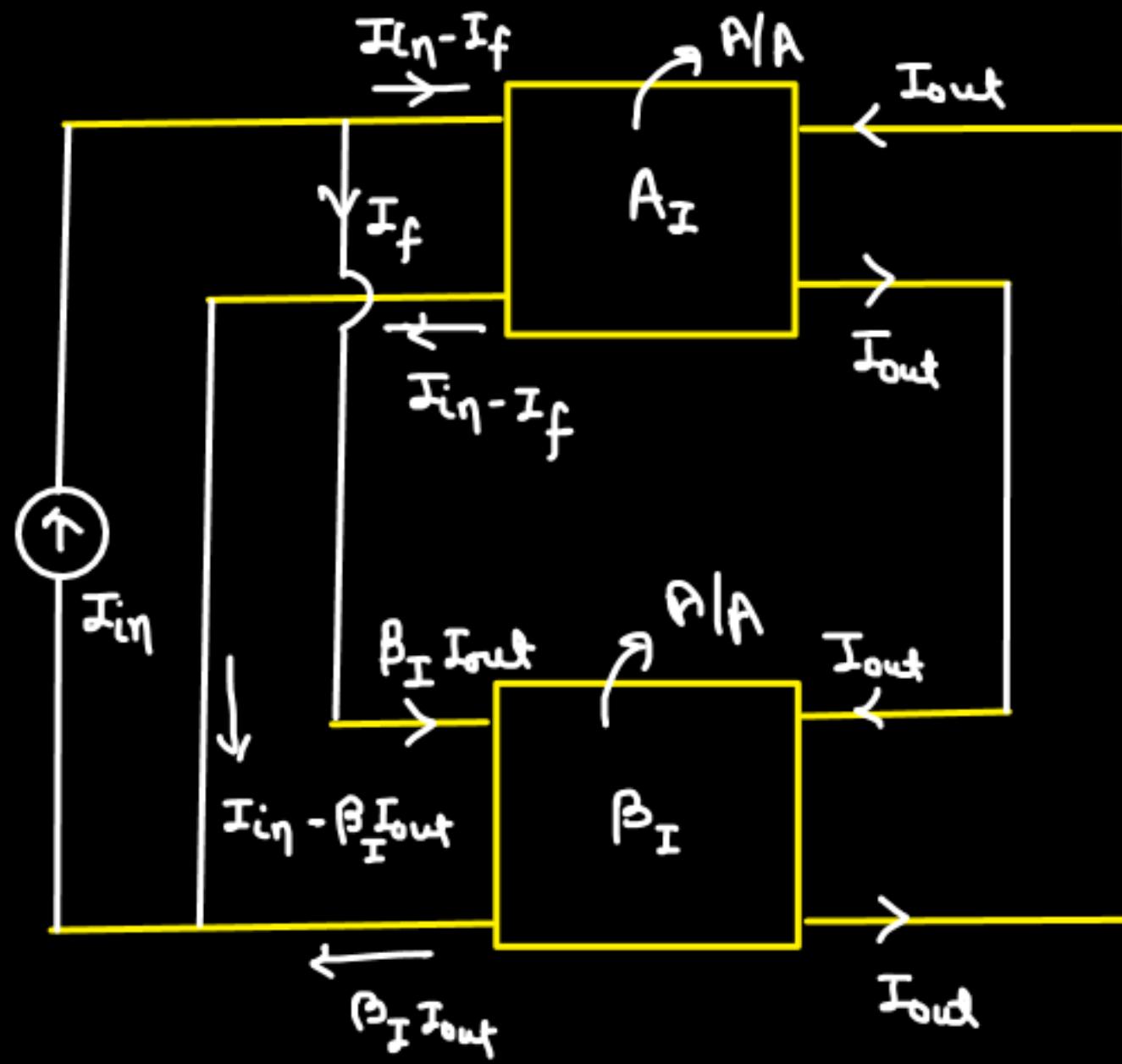
## \* Current-Current feedback :- (Shunt-Series)



open loop gain =  $A_I$

open loop i/p impedance =  $R_{in}$


open loop o/p impedance =  $R_o$

① Closed loop gain =  $\frac{A_I}{1 + A_I \beta_I}$

② Closed loop Z/p impedance  
=  $R_{in} / \frac{1 + A_I \beta_I}{1 + A_I \beta_I}$

③ Closed loop o/p impedance  
=  $R_o [1 + A_I \beta_I]$

Eg. →

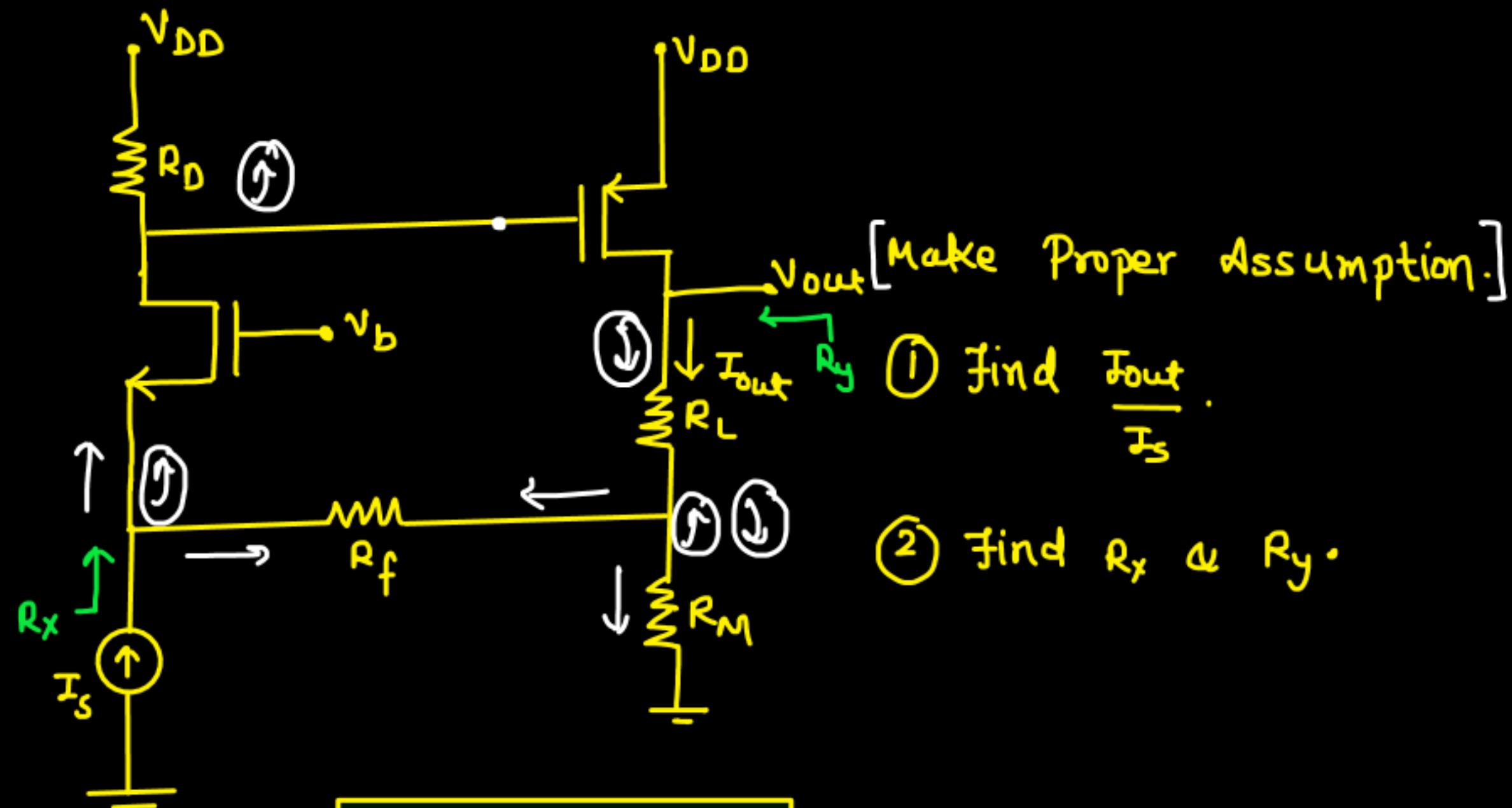


- [Make Proper Assumption.]
- ① Find  $\frac{I_{out}}{I_s}$ .
  - ② Find  $R_x$  &  $R_y$ .

⇒ negative f/b

current mixing, current - sampling ⇒

Current - Current f/b Topology

M-I w/o the concept of f/b Topology :-

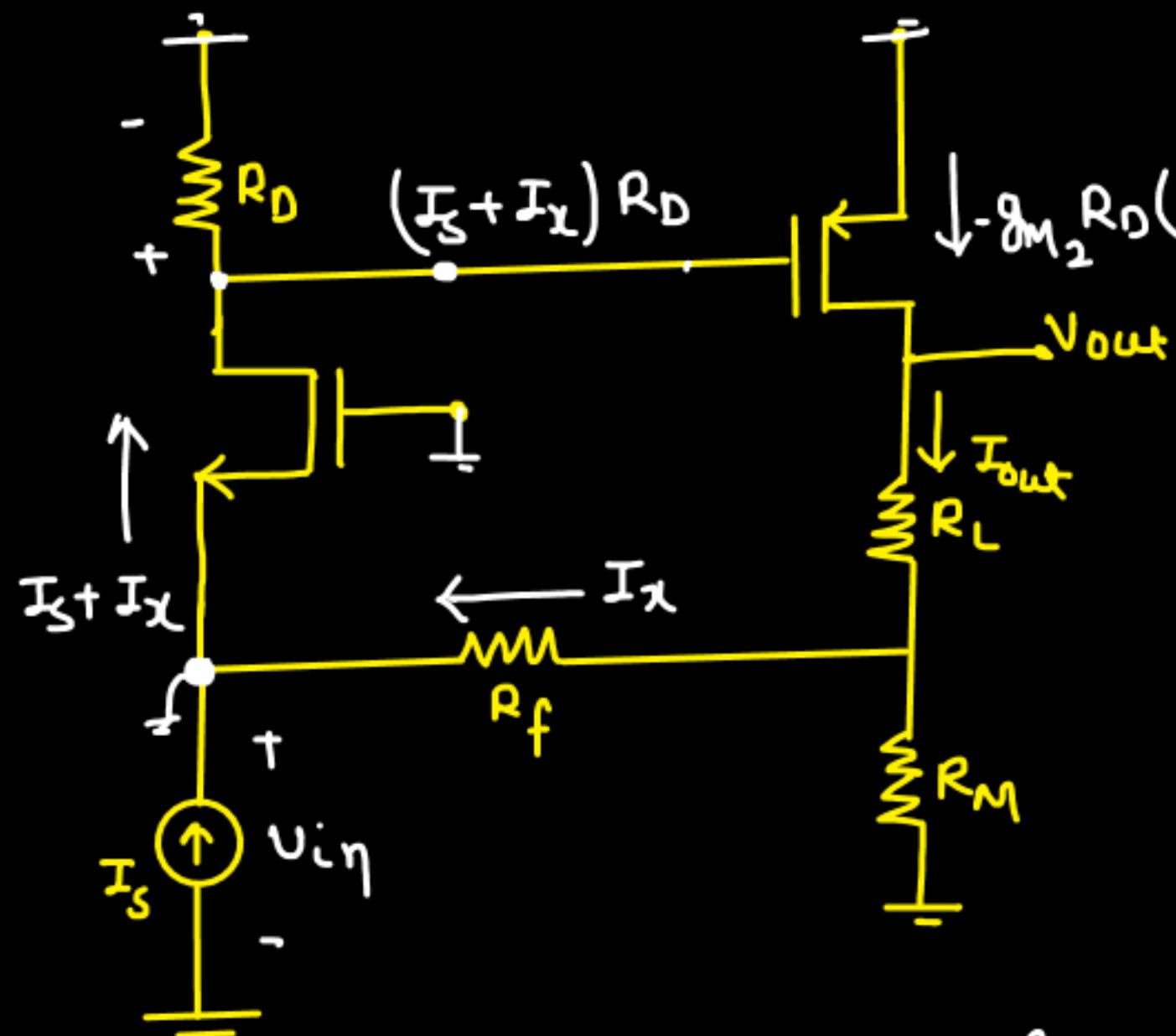

$$\frac{I_{out}}{I_s} = ?$$

CURRENT - CURRENT f/b

$R_{in} \rightarrow$  very low

$\frac{V_{in}}{I_s} \rightarrow$  very low


$I$  can take,  $V_{in} \rightarrow 0$

$$I_x = \frac{R_M}{R_M + R_f} I_{out}$$

$$- g_m R_D \left( I_S + \frac{R_M}{R_M + R_f} I_{out} \right) = I_{out}$$

$$- g_m R_D I_S = I_{out} \left[ 1 + \frac{g_m R_D R_M}{R_M + R_f} \right]$$
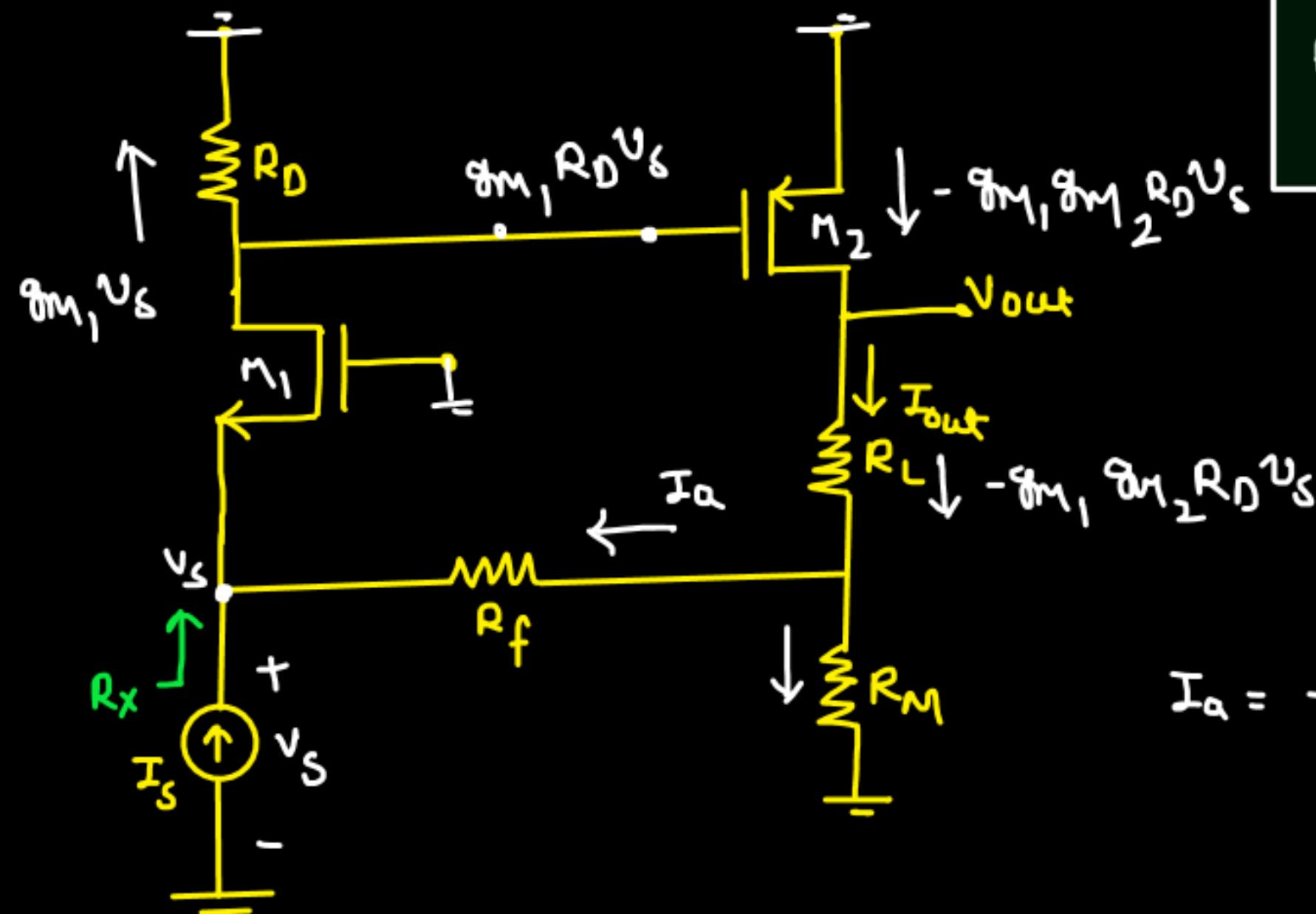
$$\frac{I_{out}}{I_S} = \frac{- g_m R_D}{1 + g_m R_D \left( \frac{R_M}{R_M + R_f} \right)}$$



$$R_X = \frac{V_S}{I_S}$$

$$I_a = -g_{m1} g_{m2} R_D V_S \times \frac{R_M}{R_M + R_f} \rightarrow 0$$


$\left\{ V_S \rightarrow \text{very small} \right\}$

$$I_s + I_a = g_{m1} V_S$$

$$I_s - g_{m1} g_{m2} R_D \left( \frac{R_M}{R_M + R_f} \right) V_S = g_{m1} V_S$$


$$I_s = \left[ g_{m_1} + g_{m_1} g_{m_2} R_D \left( \frac{R_M}{R_M + R_f} \right) \right] v_s$$
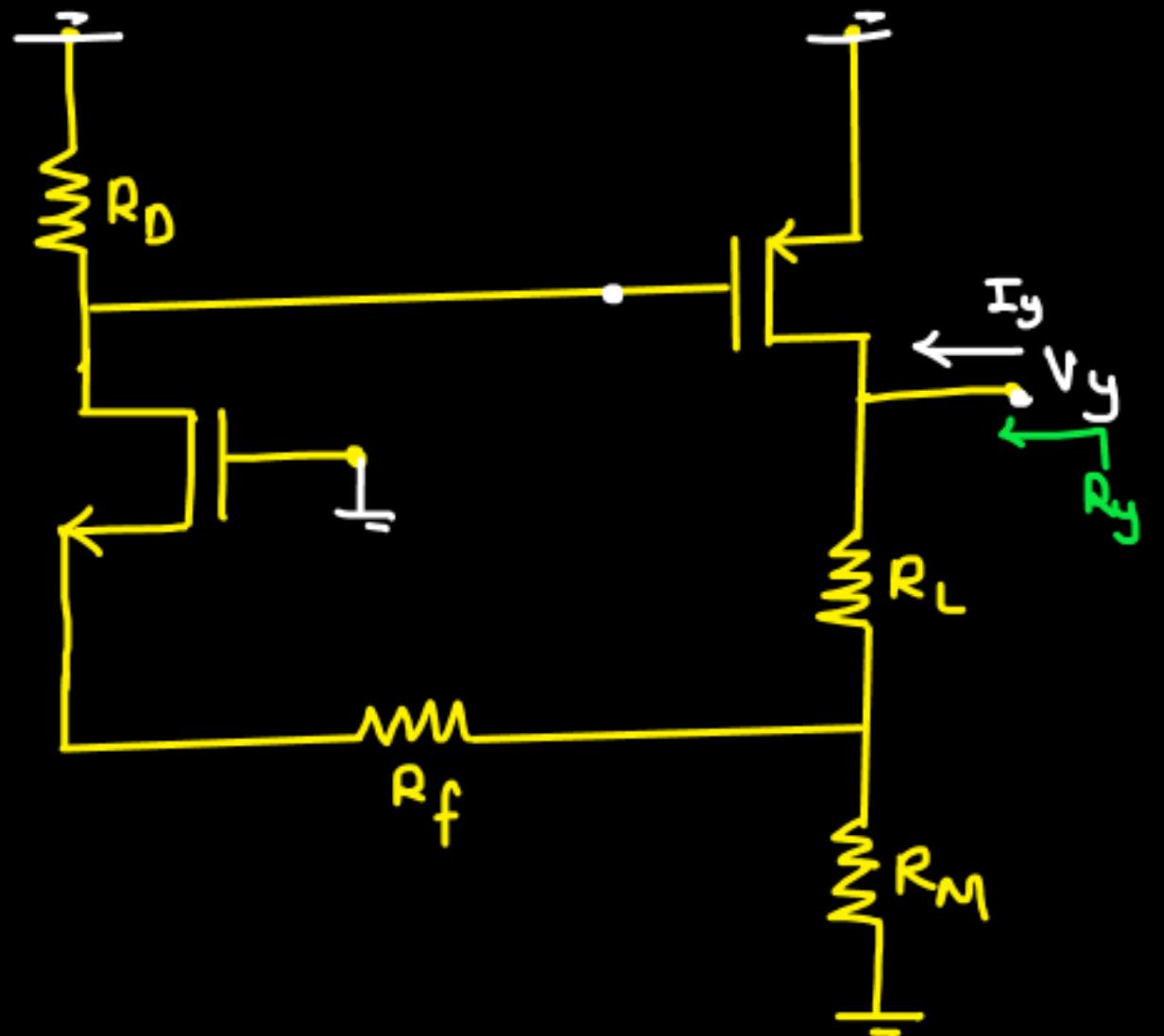
$$R_x = \frac{v_s}{I_s} = \frac{1/g_{m_1}}{1 + g_{m_2} R_D \left( \frac{R_M}{R_M + R_f} \right)}$$



$$R_y = \frac{V_y}{I_y} \rightarrow \text{complex expression} =$$

with the concept of f/b Topology:-

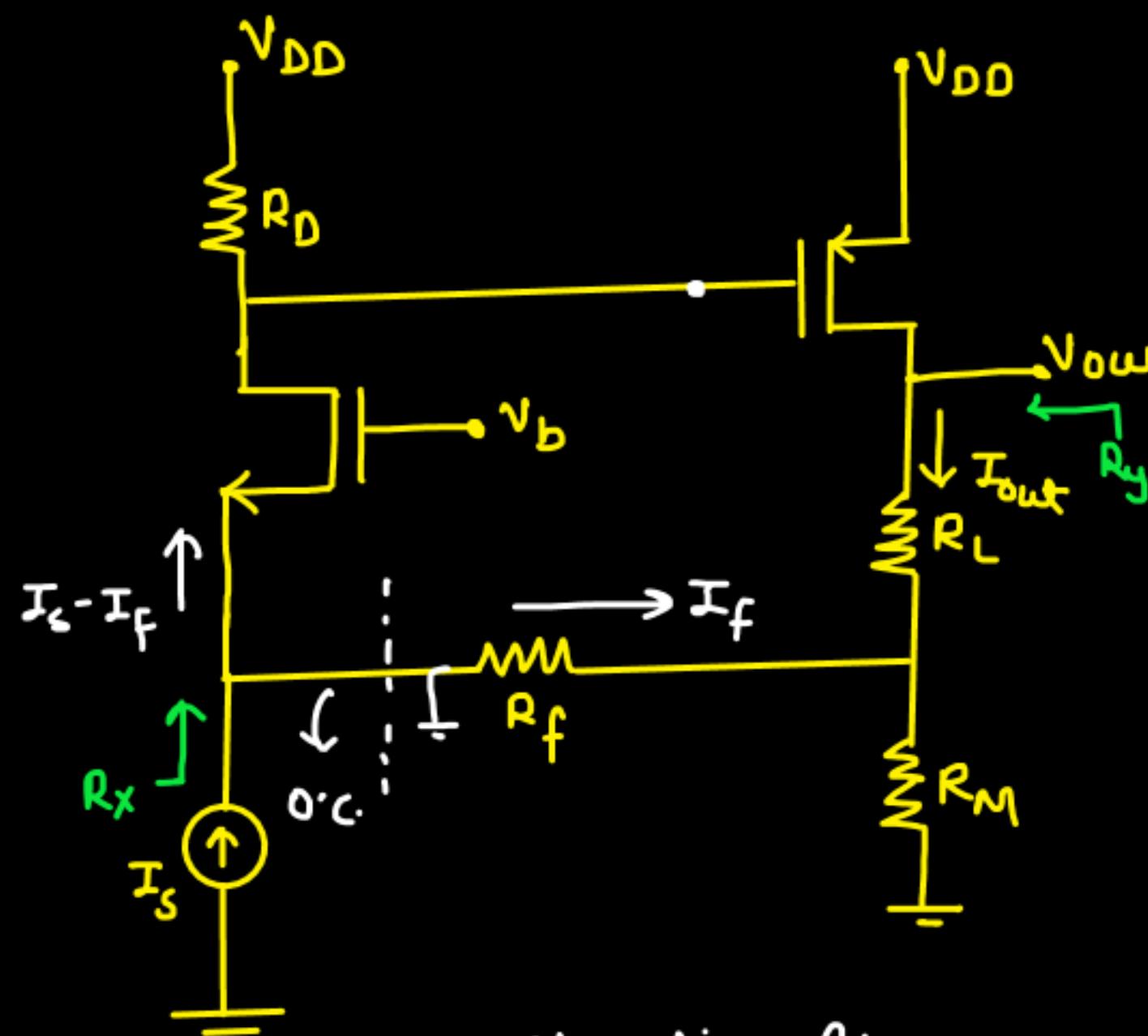


$$\left(\frac{I_{out}}{I_s}\right)_{0\text{-L}} = -g_{m_2} R_D$$




$$I_f = -\frac{R_M}{R_M + R_f} I_{out}$$

$$\beta_I = -\frac{R_M}{R_M + R_f}$$

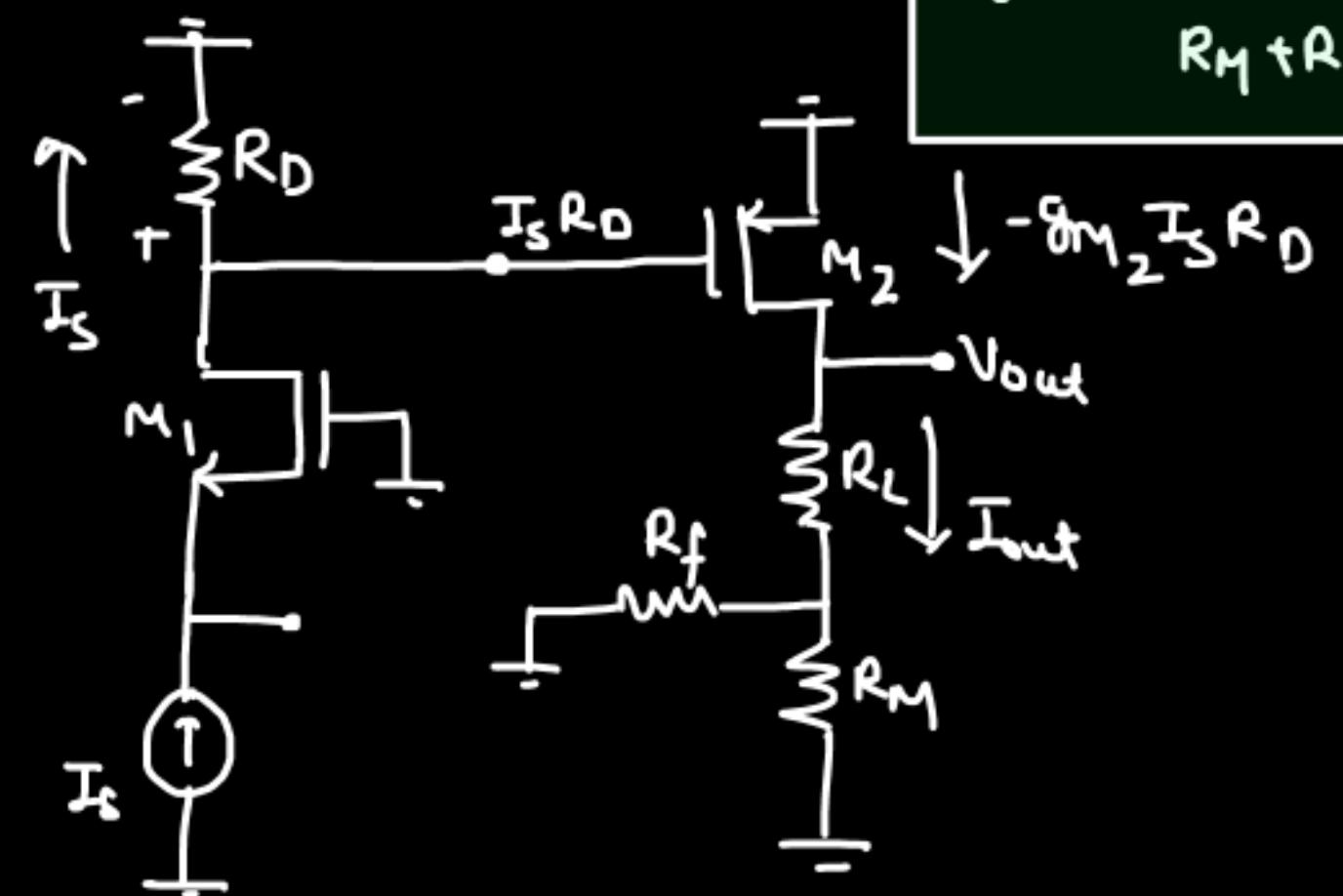


$$I_{out} = -g_{m_2} I_s R_D$$

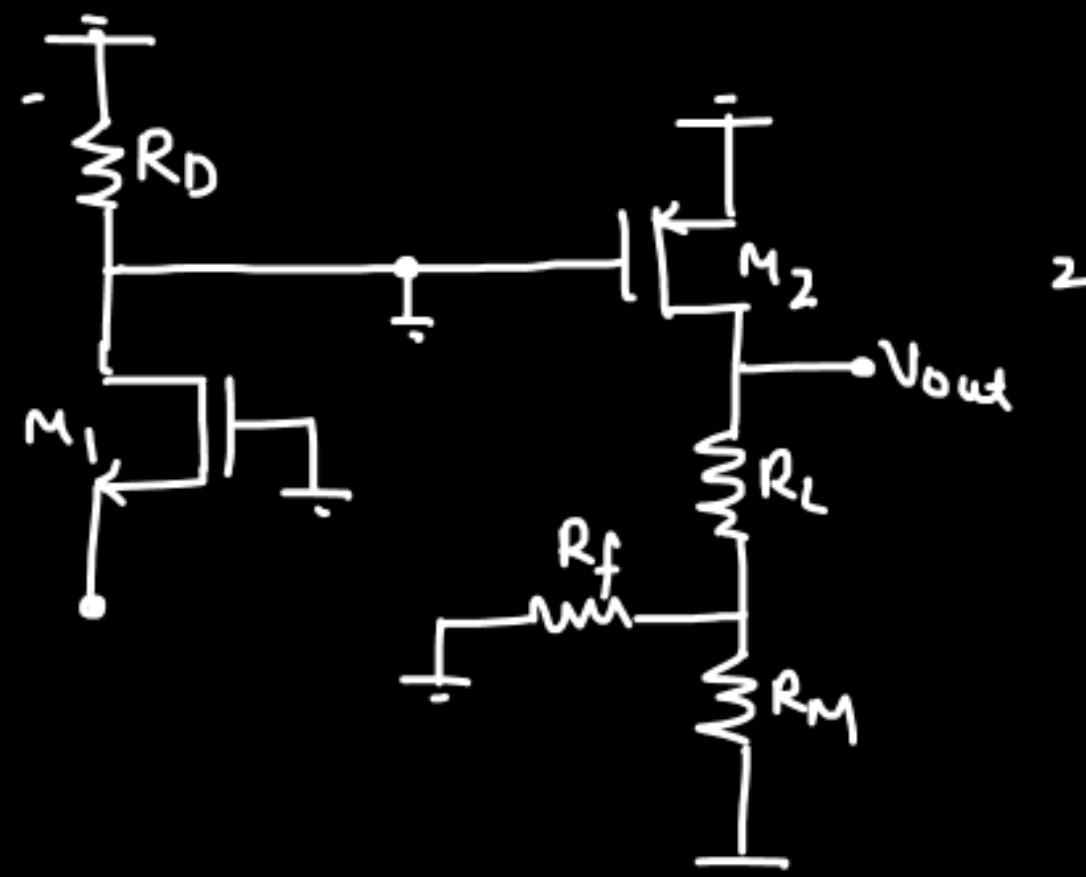

$$(R_i)_{D.L.} = \frac{1}{g_m 1}$$

$$(R_o)_{D.L.} = (R_L + R_M || R_f)$$

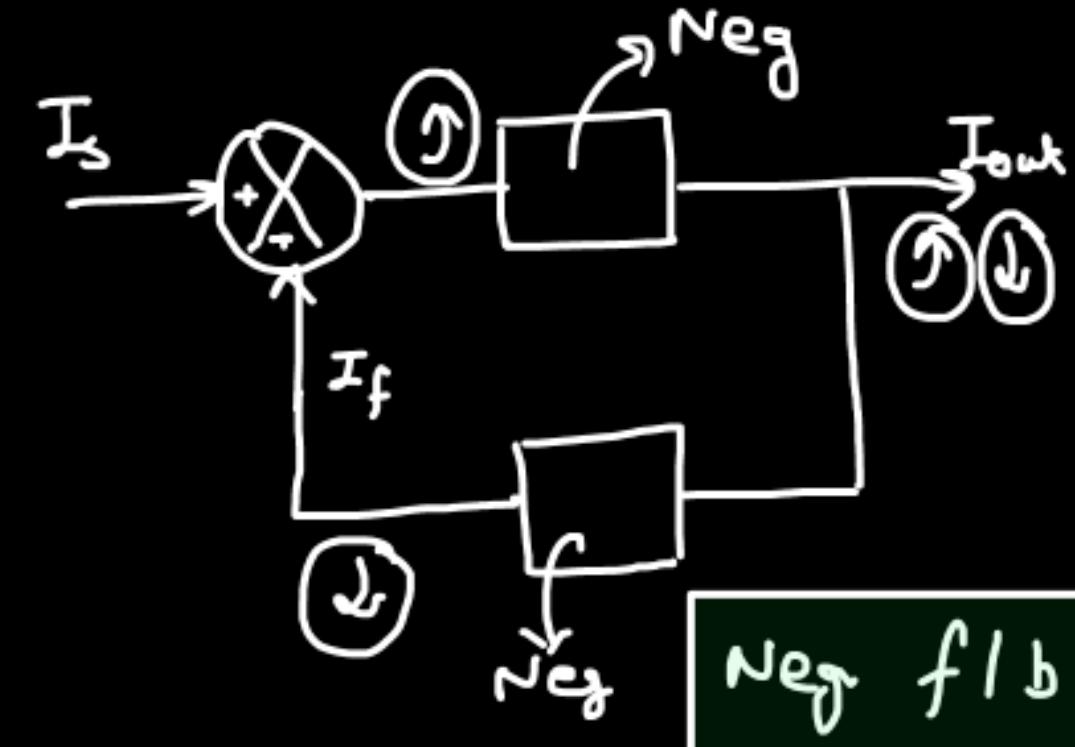① Closed loop gain =  $\frac{-g_m 2 R_D}{(1 + g_m 2 R_D) \left( \frac{R_M}{R_M + R_f} \right)}$




②  $R_x = \frac{1/g_m 1}{1 + g_m 2 R_D \left( \frac{R_M}{R_M + R_f} \right)}$

③  $R_y = (R_L + R_M || R_f) \left( 1 + g_m 2 R_D \left\{ \frac{R_M}{R_M + R_f} \right\} \right)$


4x4x4

Type of feedback Topology	Forward gain (open loop)	Feedback factor ( $\beta$ )	Closed loop Gain	Closed loop Input impedance	Closed loop O/P impedance
1. Voltage - voltage	$A_V$	$\beta_V$	$\frac{\alpha_V}{1 + \alpha_V \beta_V}$	$R_{in} (1 + \alpha_V \beta_V)$	$R_o / (1 + A_I \beta_I)$
2. Voltage - Current	$R_m$	$G_m$	$\frac{R_m}{1 + G_m R_m}$	$\frac{R_{in}}{1 + G_m R_m}$	$\frac{R_o}{1 + G_m R_m}$
3. Current - Voltage	$G_m$	$R_m$	$\frac{G_m}{1 + R_m G_m}$	$R_{in} (1 + G_m R_m)$	$R_o (1 + G_m R_m)$
4. Current - Current	$A_I$	$\beta_I$	$\frac{A_I}{1 + A_I \beta_I}$	$\frac{R_{in}}{1 + A_I \beta_I}$	$R_o (1 + A_I \beta_I)$

\*

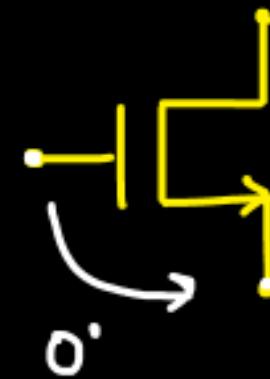


\*

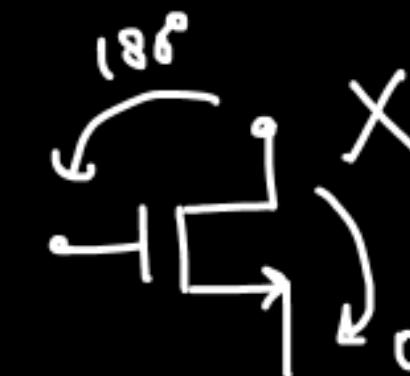


@ drain, you  
never  
apply i/p.


\*

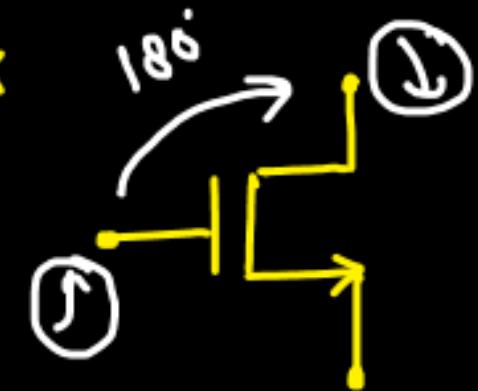

\*

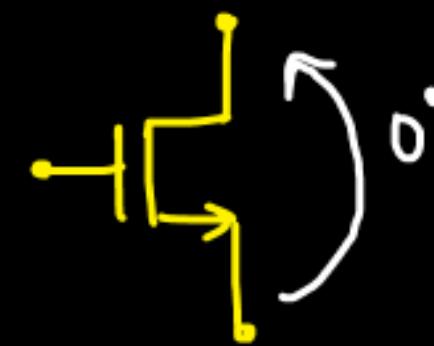

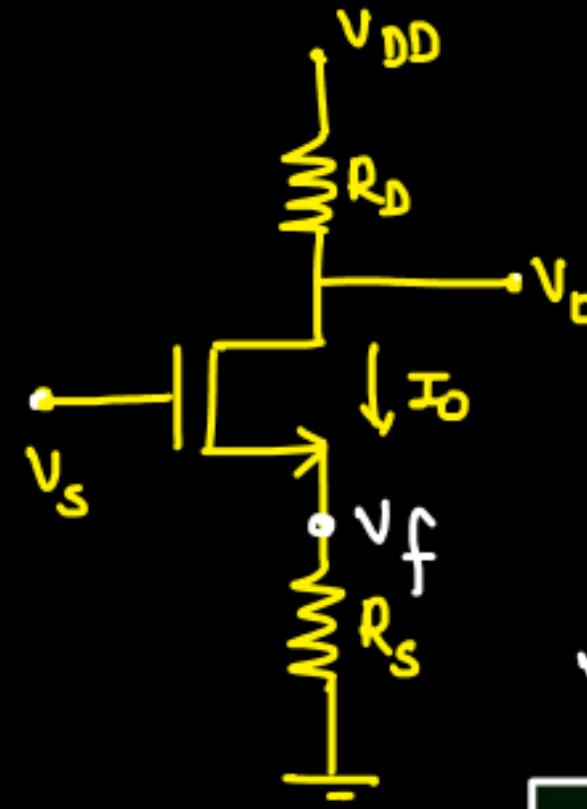Q. Determine the type of feedback and feedback factor.




(a)

$$V_f = I_o R_s$$

$$R_{in} = \frac{V_f}{I_o} = R_s$$

Current sampled  
Voltage mixing

Current - Voltage

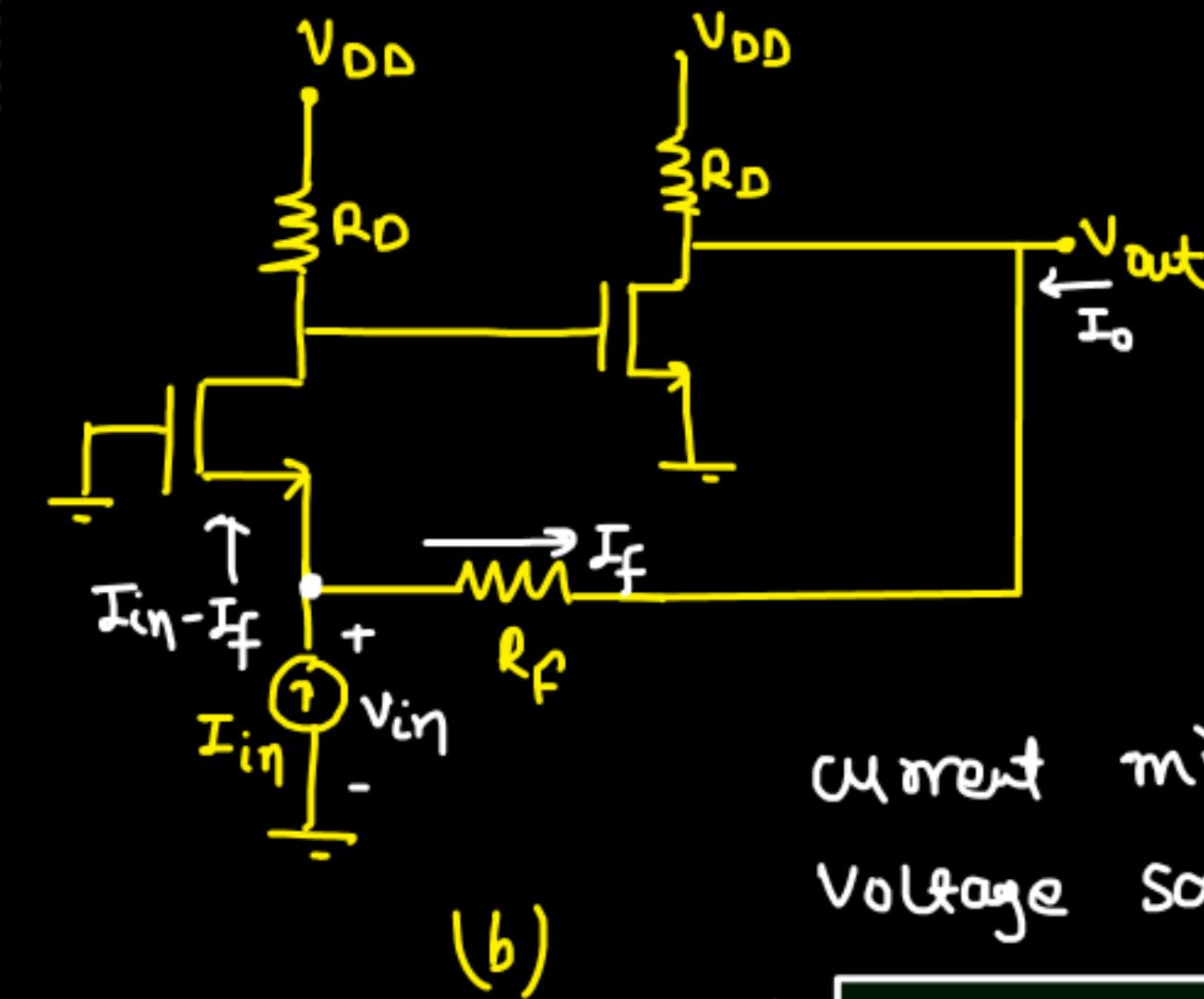

(b)


current mixing

Voltage Sampling


$$\rightarrow \text{Voltage - Current}$$

$$\leftarrow (R_{in})_f \rightarrow (\text{low} \Rightarrow V_{in} \rightarrow 0)$$

$$\frac{I_f}{V_o} = -\frac{1}{R_f}$$

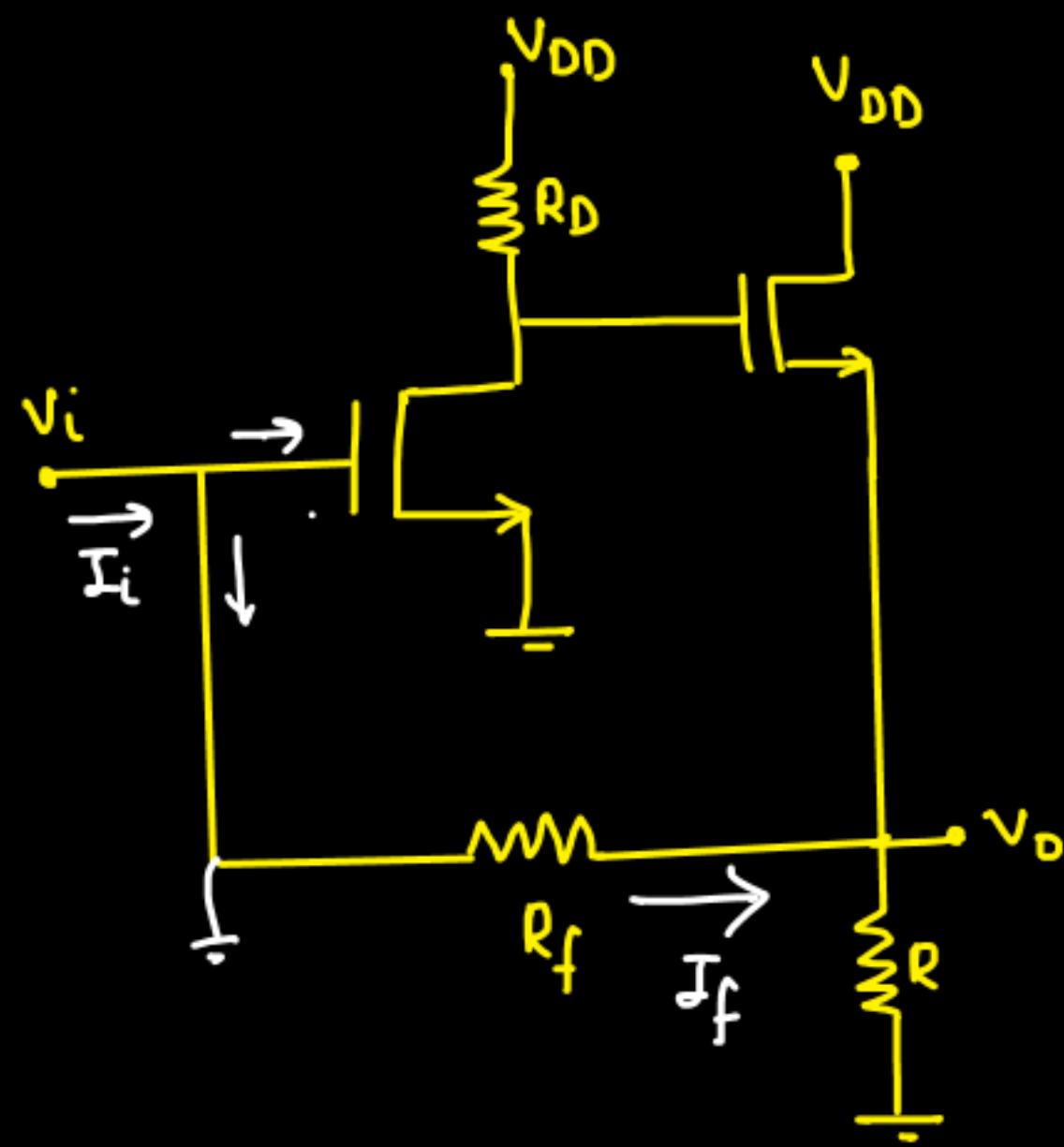


(c)  
current mixing  
Voltage Sampling

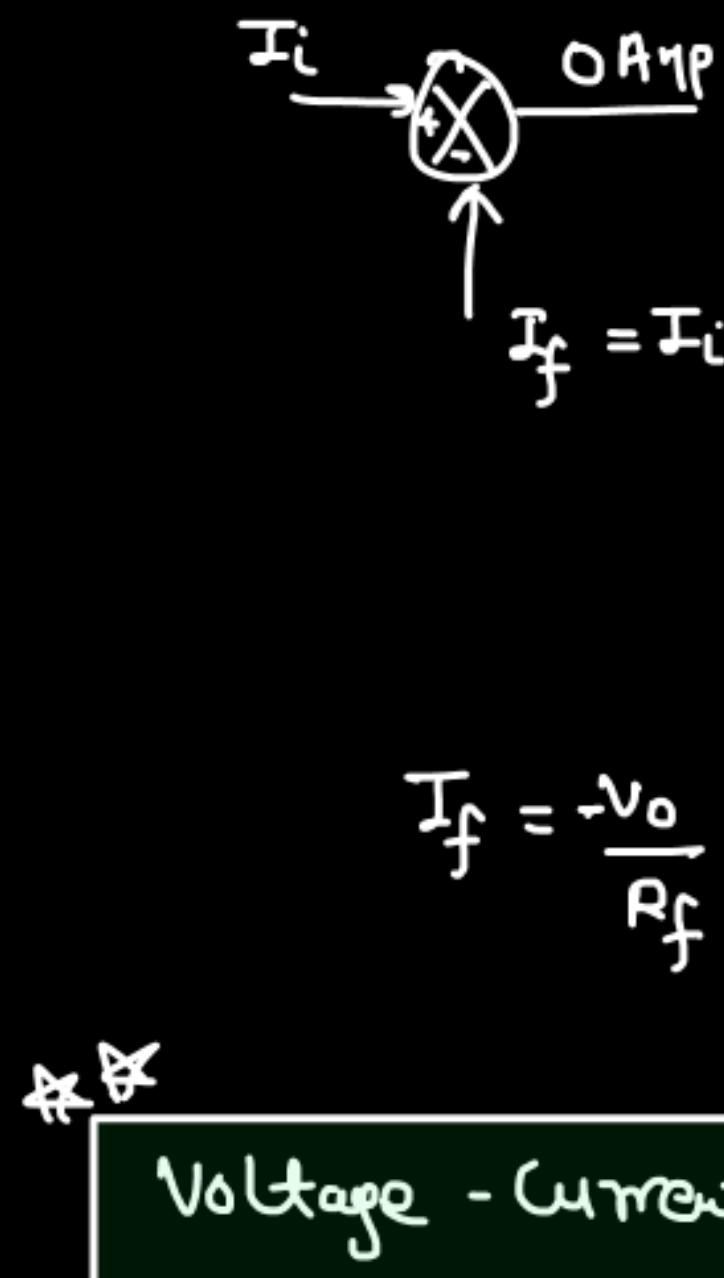

$$R_{in} \rightarrow \text{low} \Rightarrow V_{in} \rightarrow \text{low}$$


$$\frac{I_f}{V_o} = -\frac{1}{R_f}$$

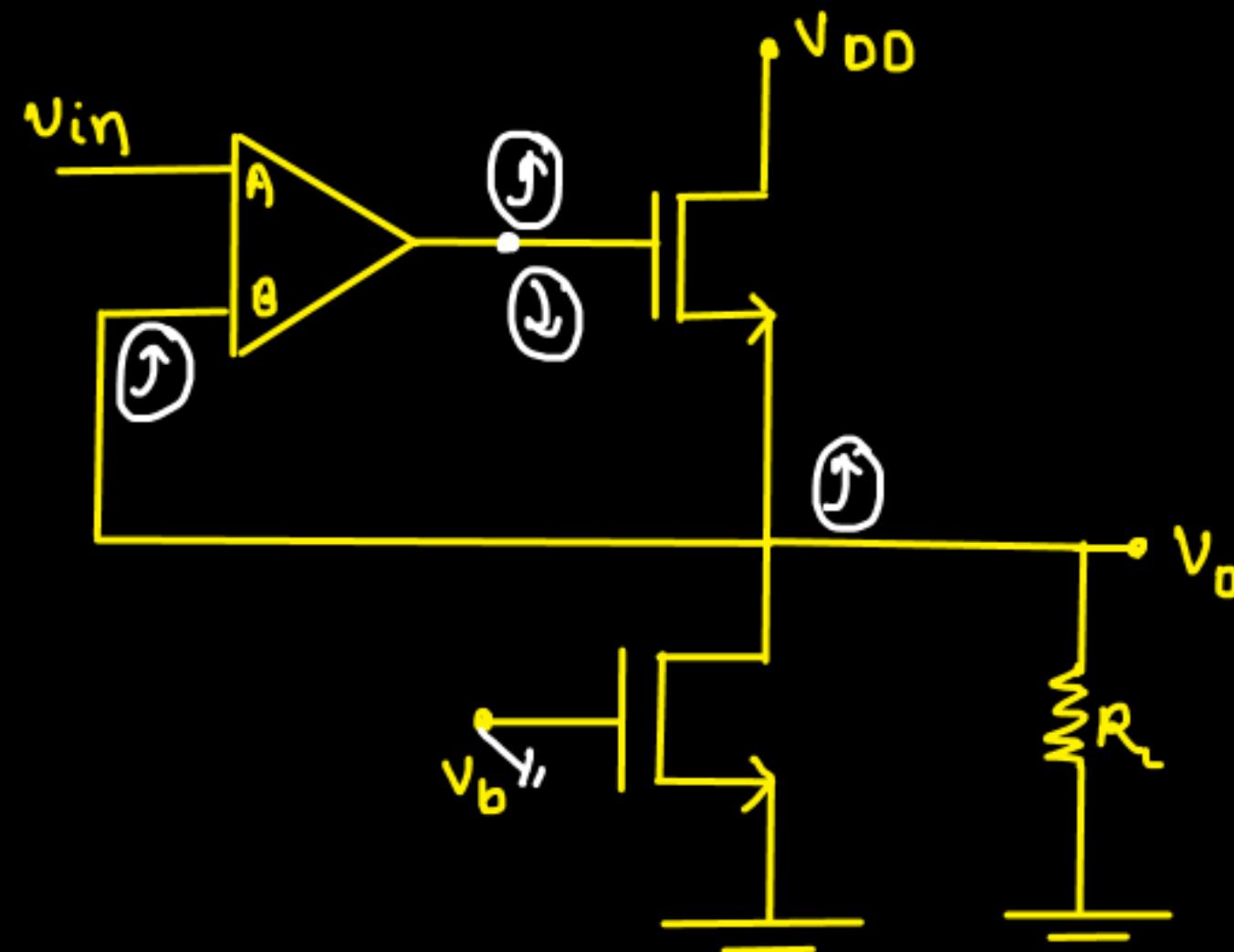Q. Determine the sign of A and B for negative f/b.



(a)

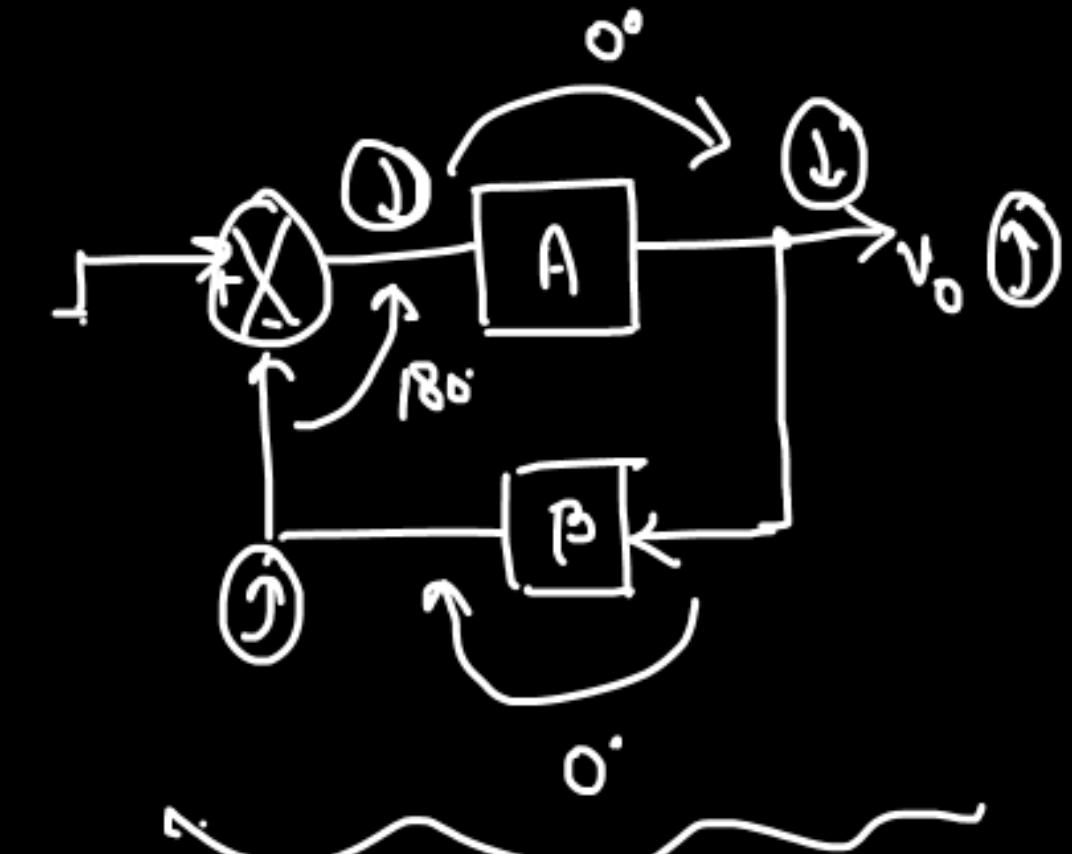
$B \rightarrow -ve$   
 $A \rightarrow +ve$



$$\text{neg f/b} \rightarrow 180^\circ, 540^\circ - \dots (2n+1)180^\circ$$


$$\text{pos f/b} \rightarrow 0^\circ, 360^\circ - \dots 360^\circ n =$$

$$\Rightarrow \underline{180^\circ}$$

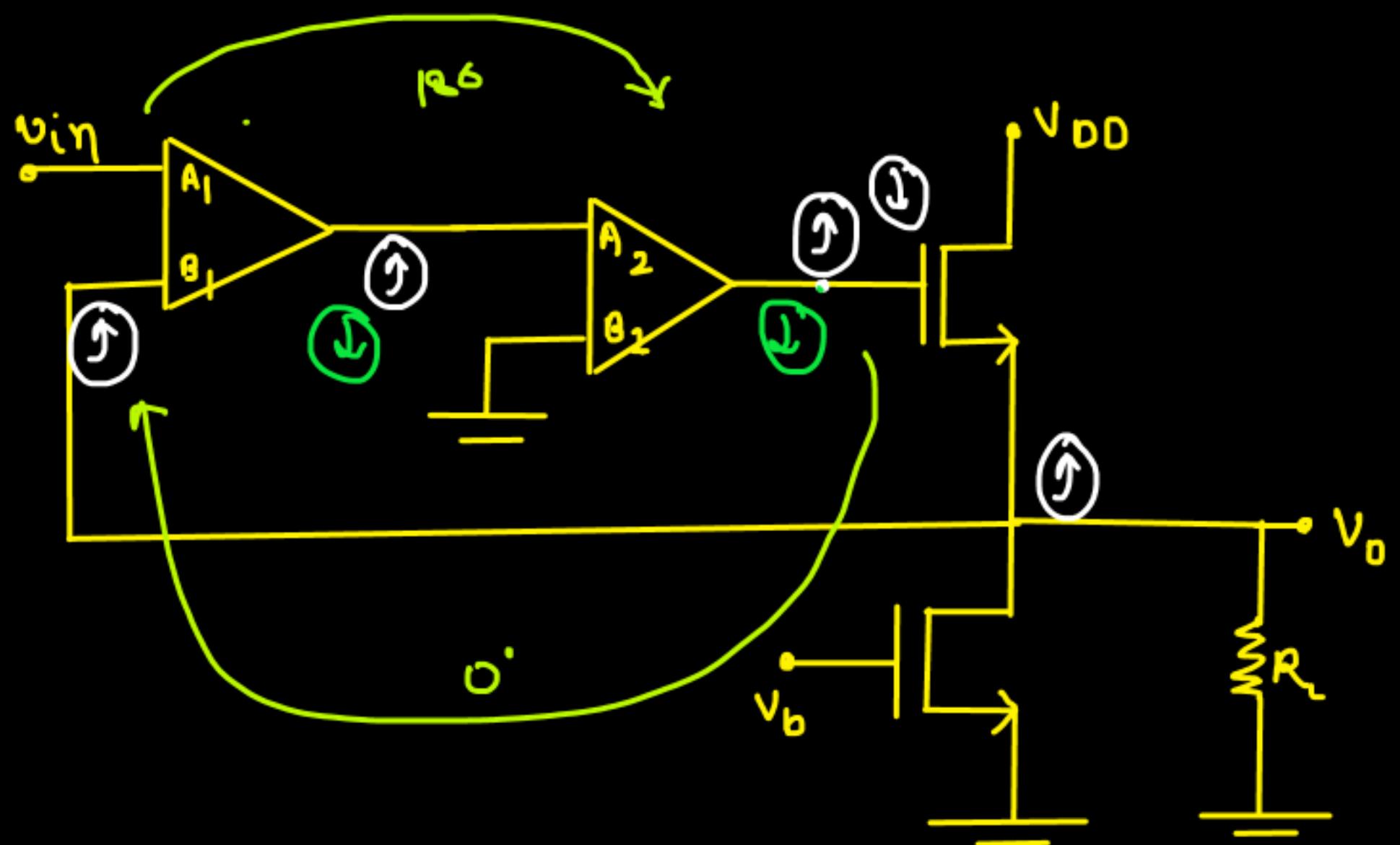


(b)

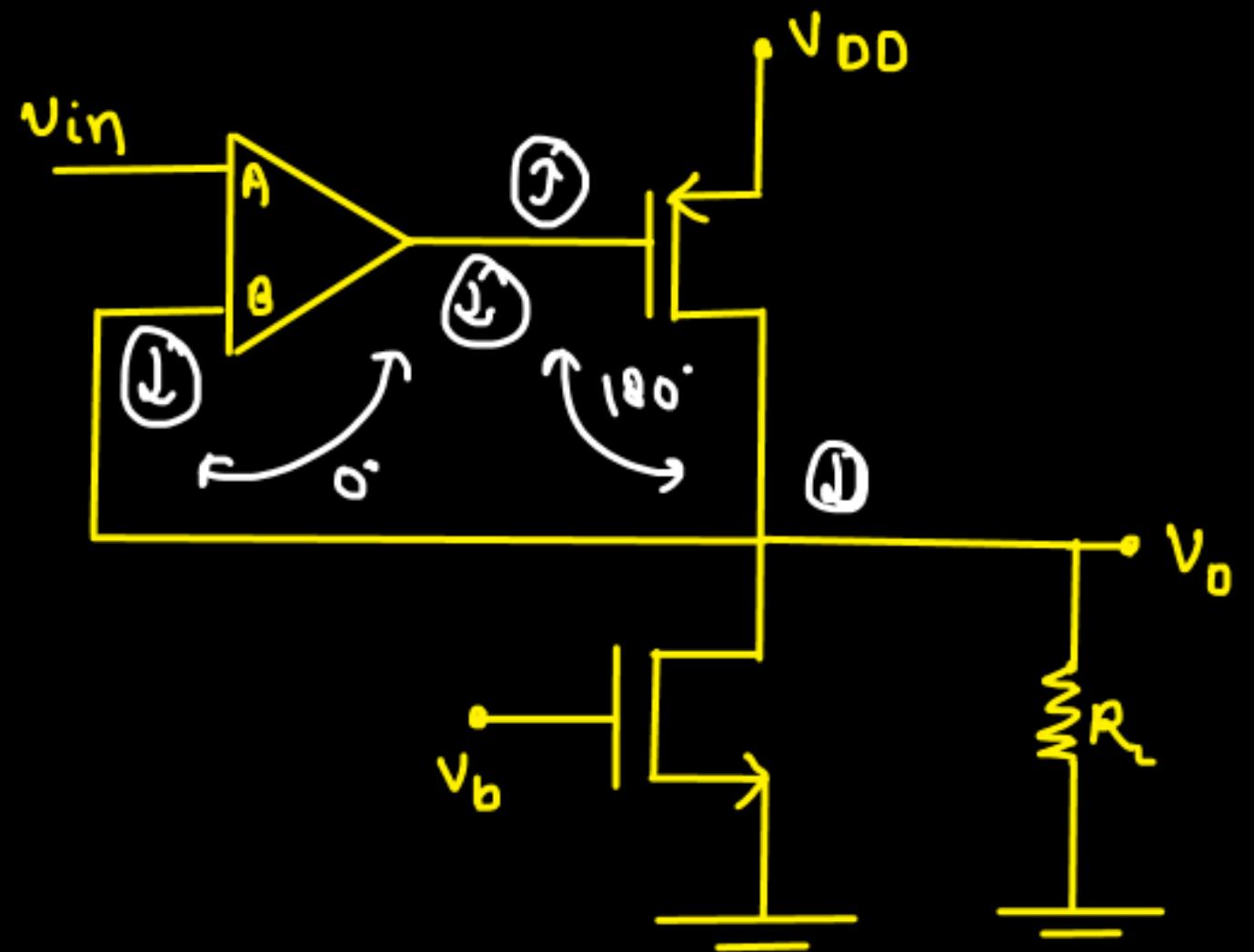- ① if  $A_1 = -ve$ ,  $B_1 = +ve \Rightarrow A_2 = -ve, B_2 = +ve$
- ② if  $A_1 = +ve, B_1 = -ve \Rightarrow A_2 = +ve, B_2 = -ve$



$$\begin{aligned} B &= +ve \\ A &= -ve \end{aligned}$$

(c)

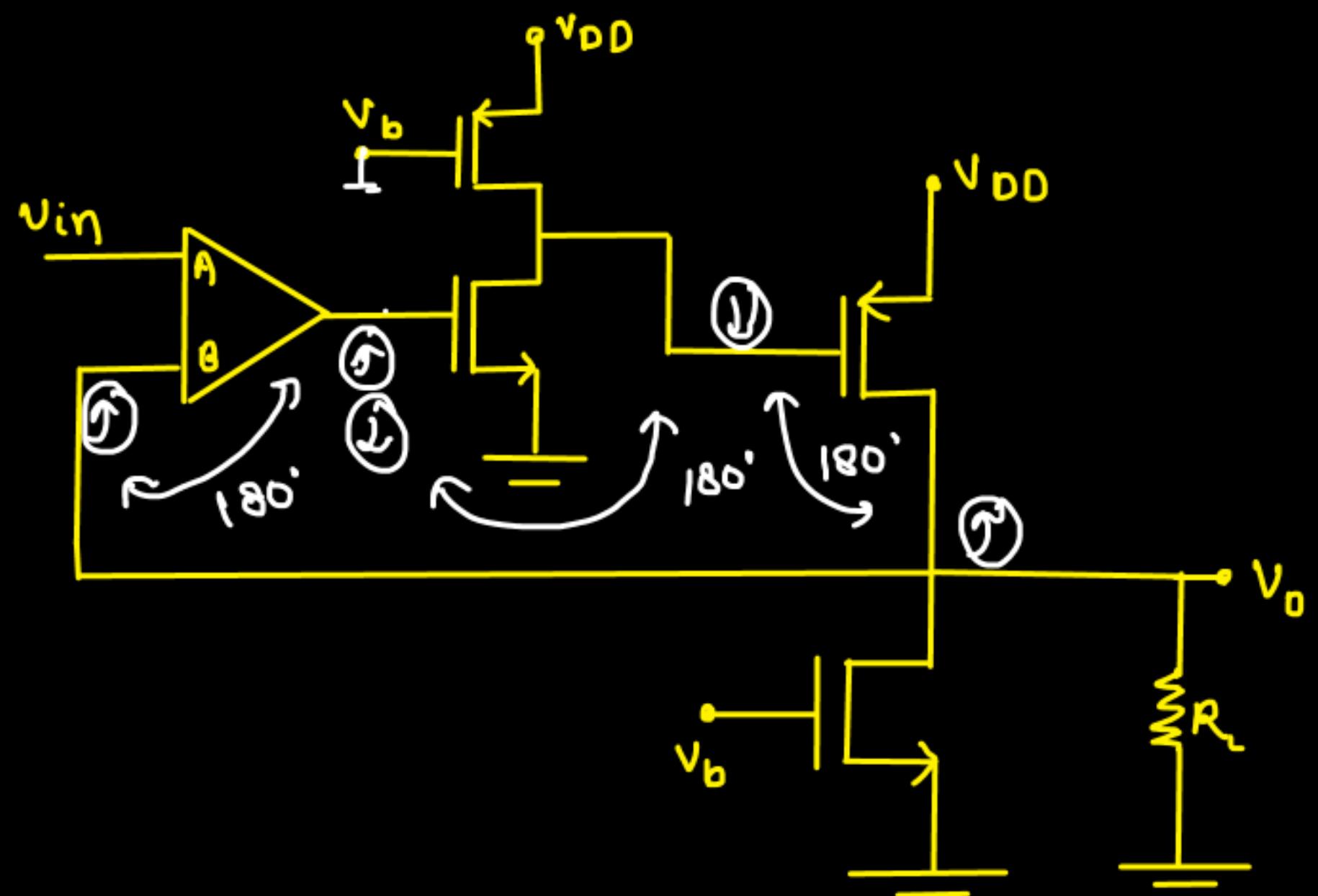

B = -ve  
A = +ve

(d)