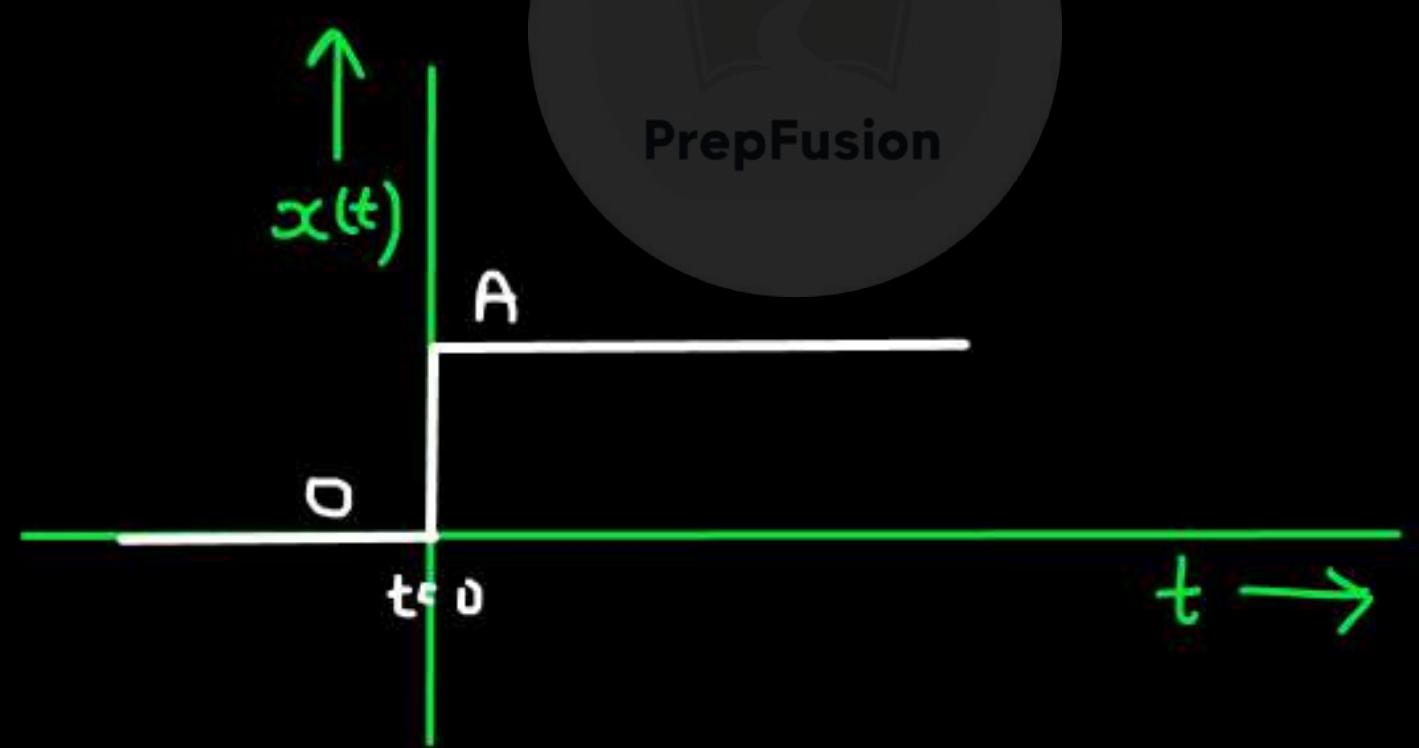


Basics of Signals :-

(a) Step Signal :-

$$x(t) = A u(t) = \begin{cases} A, & t > 0 \\ 0, & t < 0 \end{cases}$$




② Impulse Signal:-

$$x(t) = \underline{A} \delta(t) = \begin{cases} \infty, & t=0 \\ 0, & t \neq 0 \end{cases}$$

↳ Area = A

↳ Magnitude = ∞

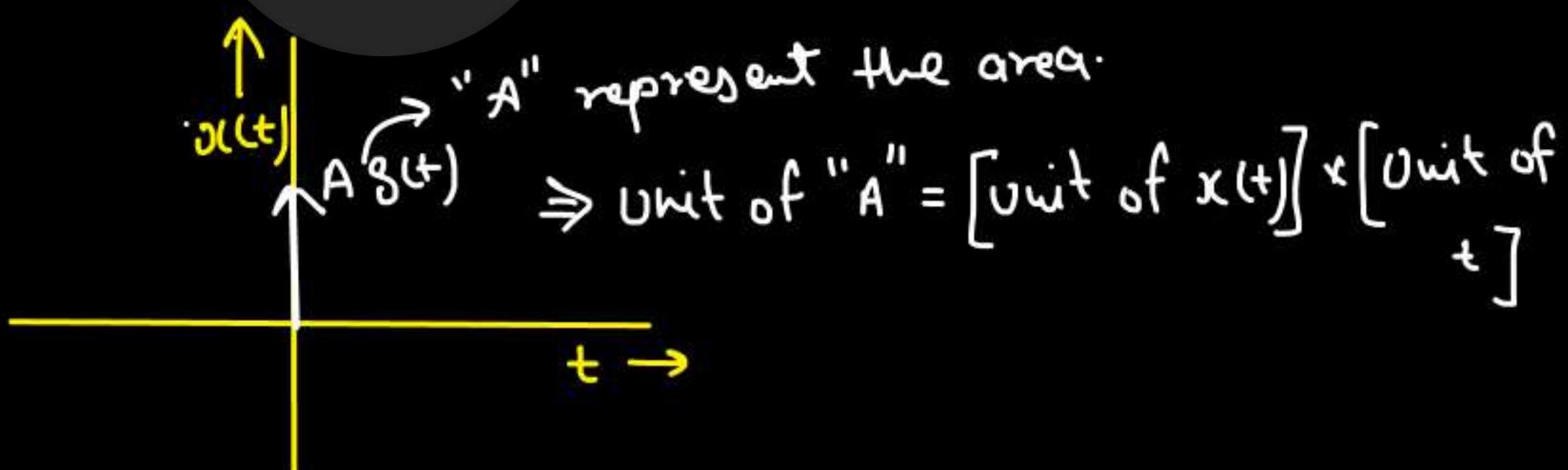





Actual meaning of impulse signal :-

Suppose in a circuit, you have to deliver $4C$ charge.

$$Q = \int_{-\infty}^{\infty} I(t) \cdot dt ; \quad I(t) = \frac{dQ(t)}{dt}$$

Way-1

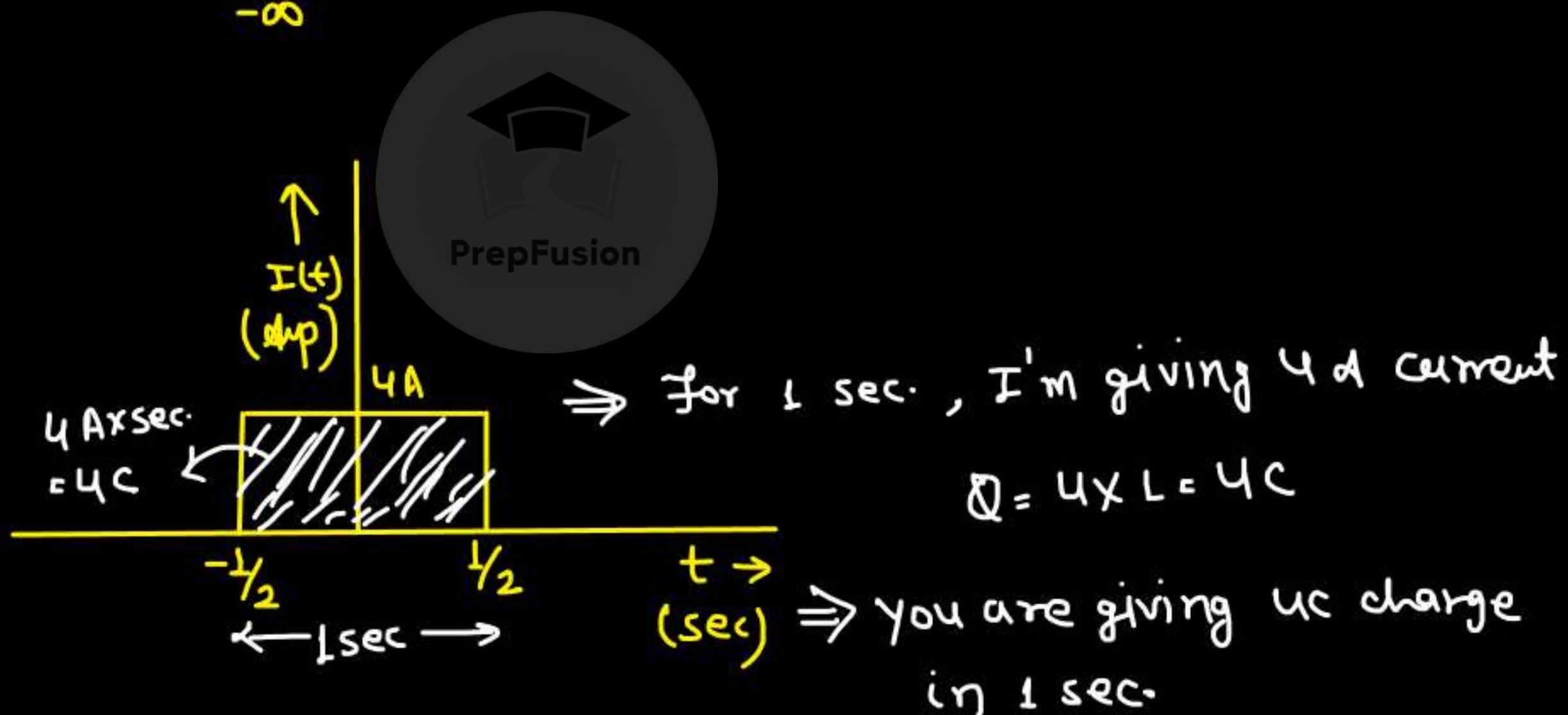


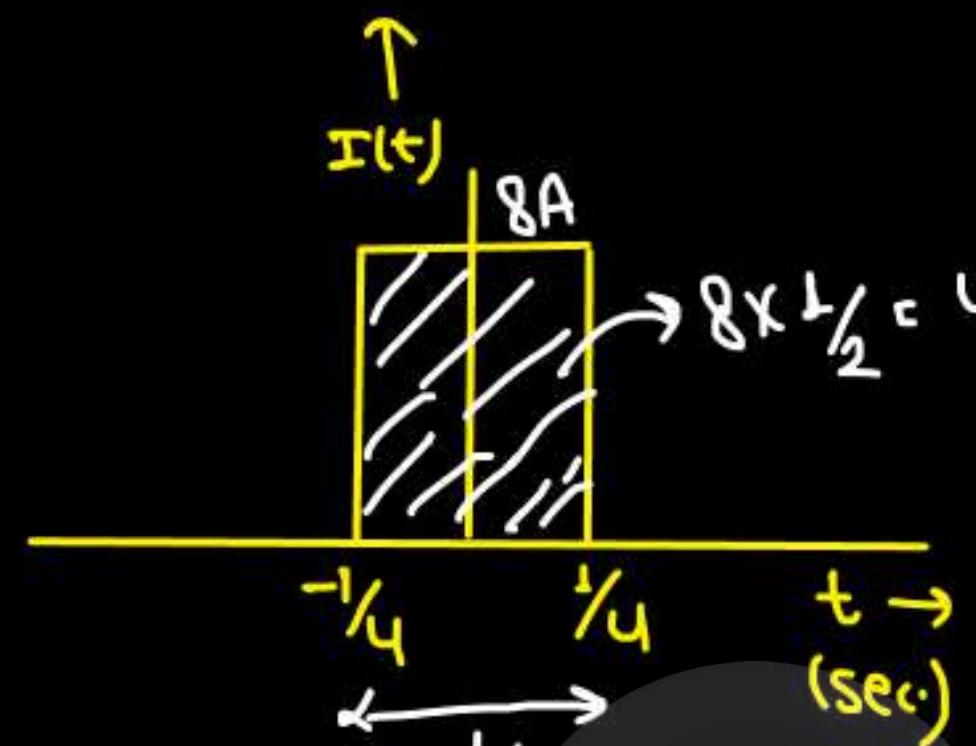Way-2

$8 \times \frac{1}{2} = 4C \Rightarrow$ decreased
the time span
 \Downarrow

Increased the value of
 $I(t)$

\Rightarrow You are giving $4C$ charge
in $\frac{1}{2}$ sec.

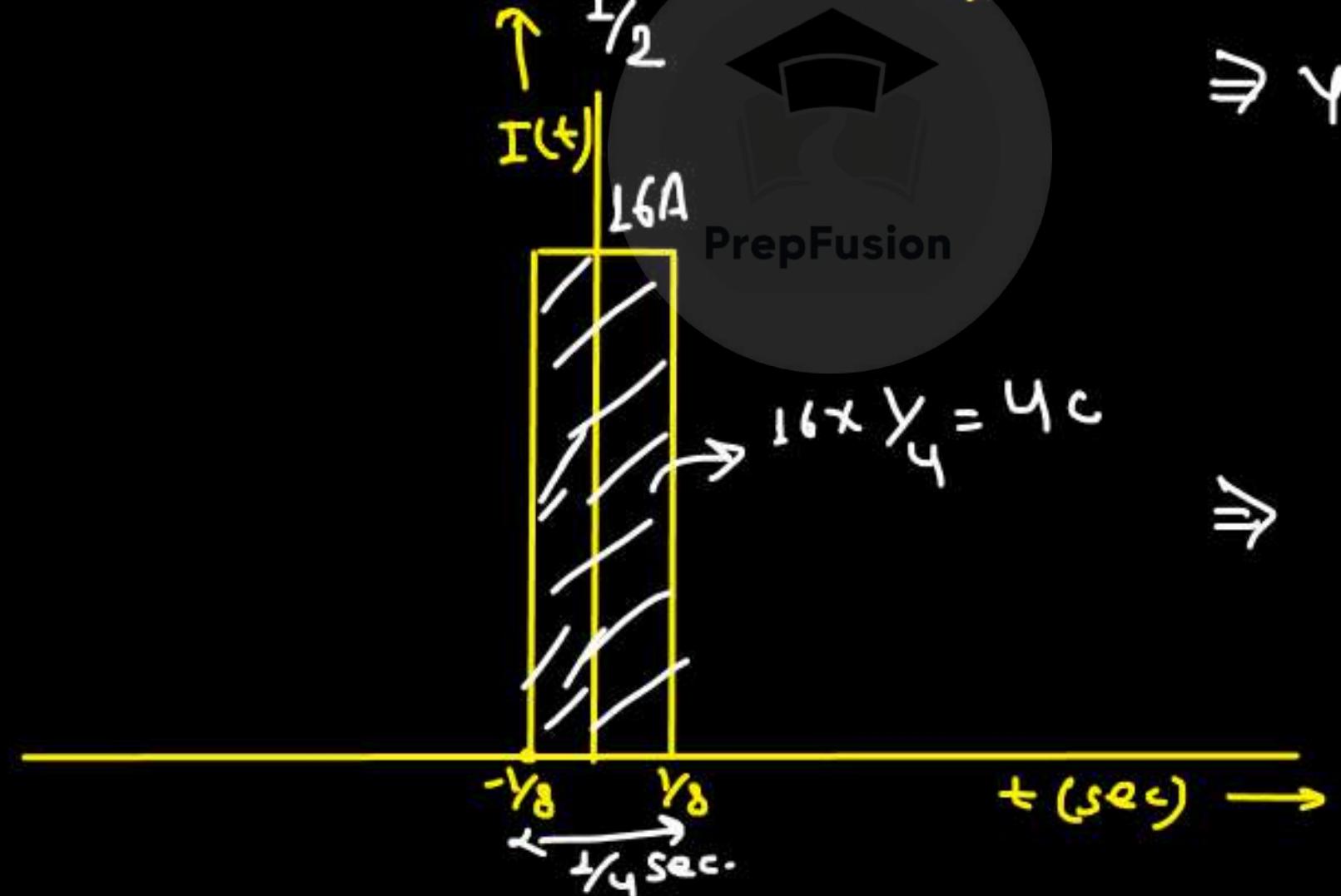
Way-3

\Rightarrow You are giving $4C$
charge in $\frac{1}{4}$ sec.

Now, what if $t \rightarrow 0$

$$\Rightarrow I(t) \rightarrow \infty$$

$$\text{But Area} = Q(t) = 4C$$

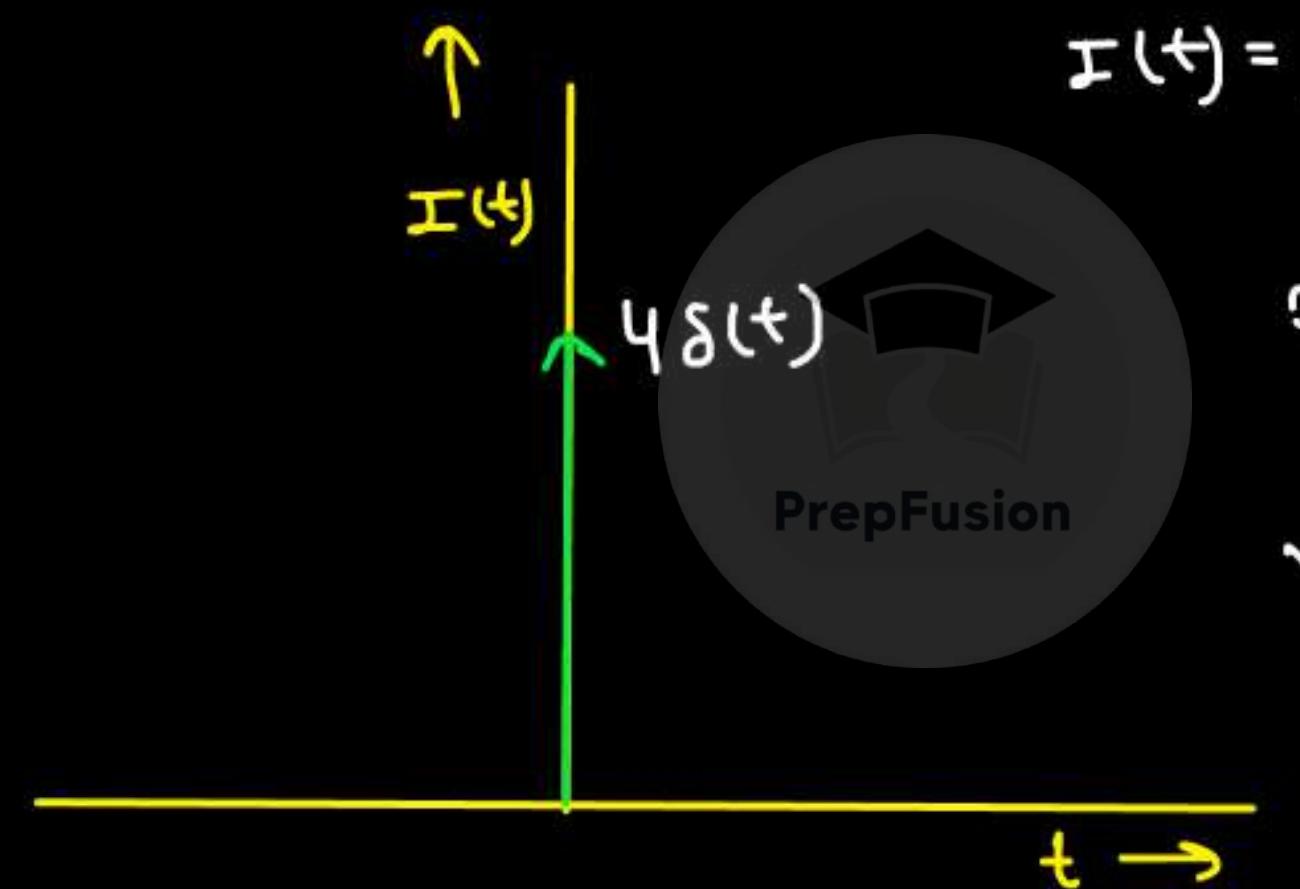


$$I(t) = \underbrace{4}_{\downarrow} \delta(t)$$

$$\text{Amp}\times \text{Sec.} = \text{coulomb} =$$

You are giving $4C$ charge
in no time


③ Ramp Signal :-
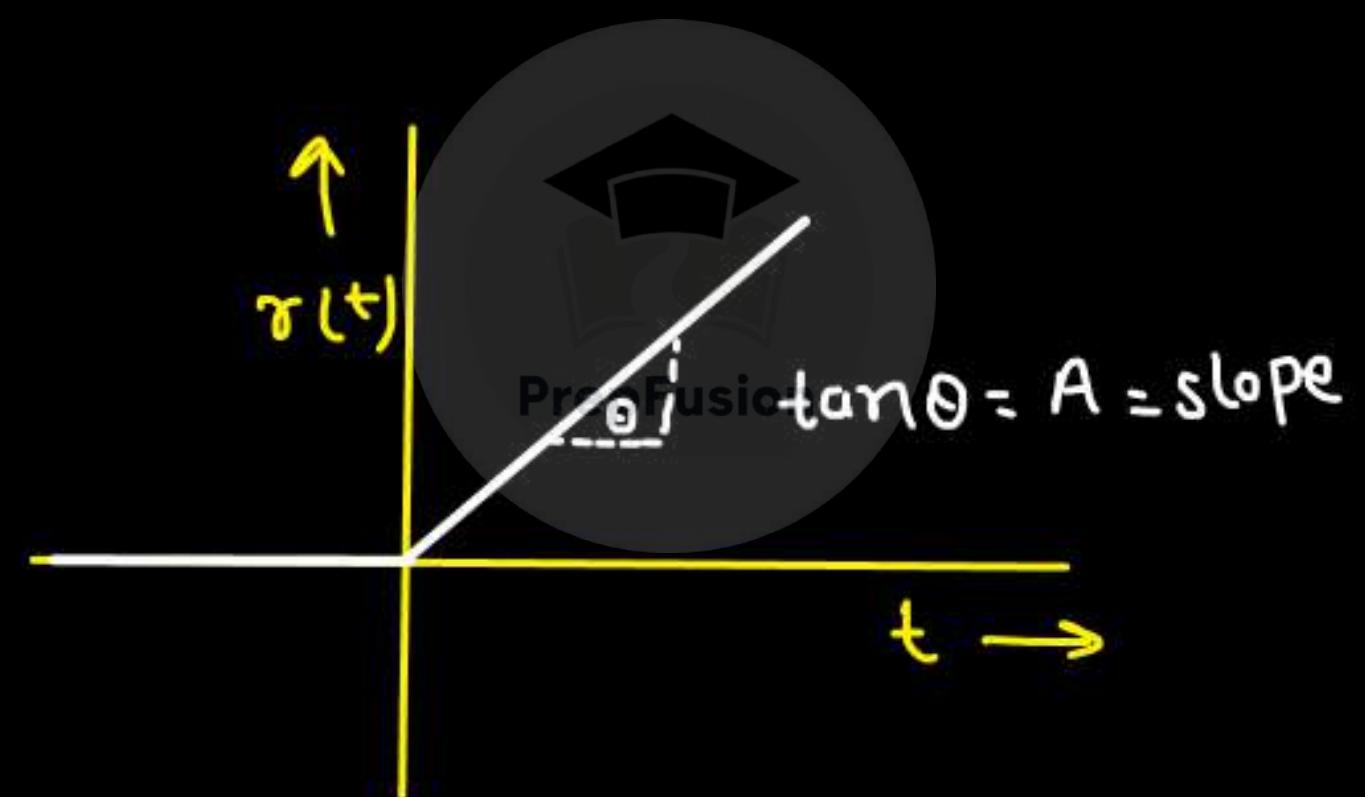
$$x(t) = A \gamma(t) = At \cdot u(t) = \begin{cases} At & , t \geq 0 \\ 0 & , t < 0 \end{cases}$$



Differentiation of a step signal:-
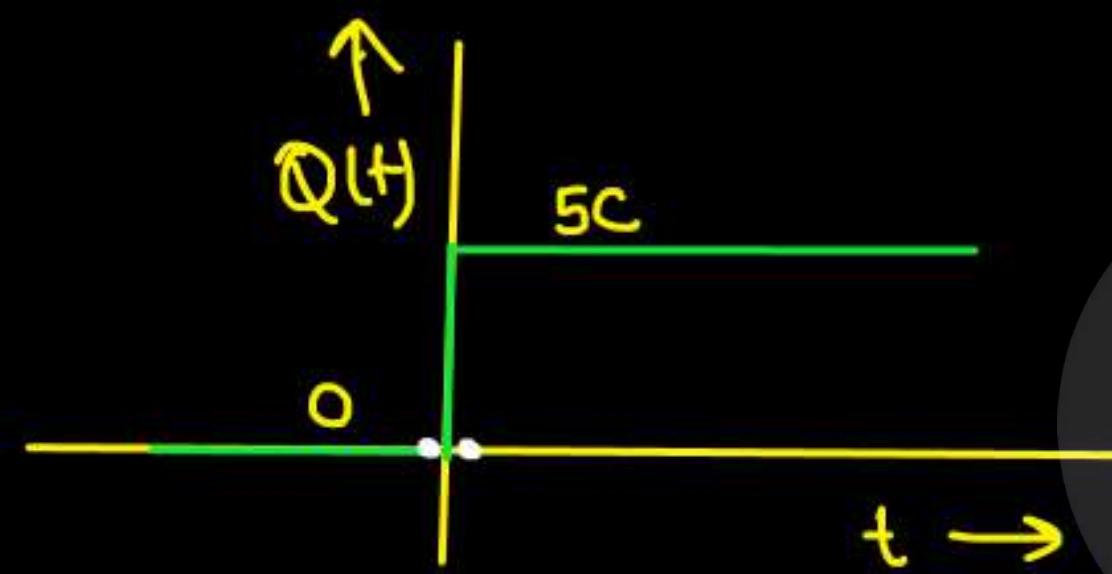
$$\frac{d}{dt} (\text{Step}) = \text{Impulse}$$



differentiation


$I(t) = \frac{dQ(t)}{dt}$

@ $t = 0^- \rightarrow 0^+$

$= \frac{5}{0} = \infty$

Differentiation of ramp signal:-
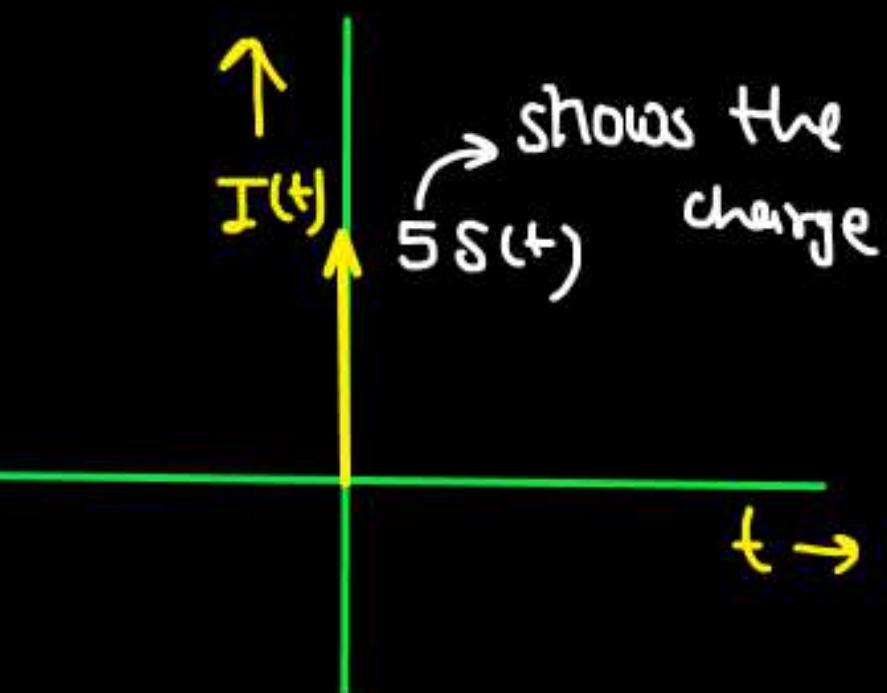
$$\frac{d}{dt} (\text{Ramp}) = \text{Step}$$




derivation :-


$$x(t) = A \tau(t) = A t \cdot u(t)$$

$$\frac{dx(t)}{dt} = A [t \cdot \delta(t) + u(t)]$$

$$\frac{dx(t)}{dt} = A u(t)$$

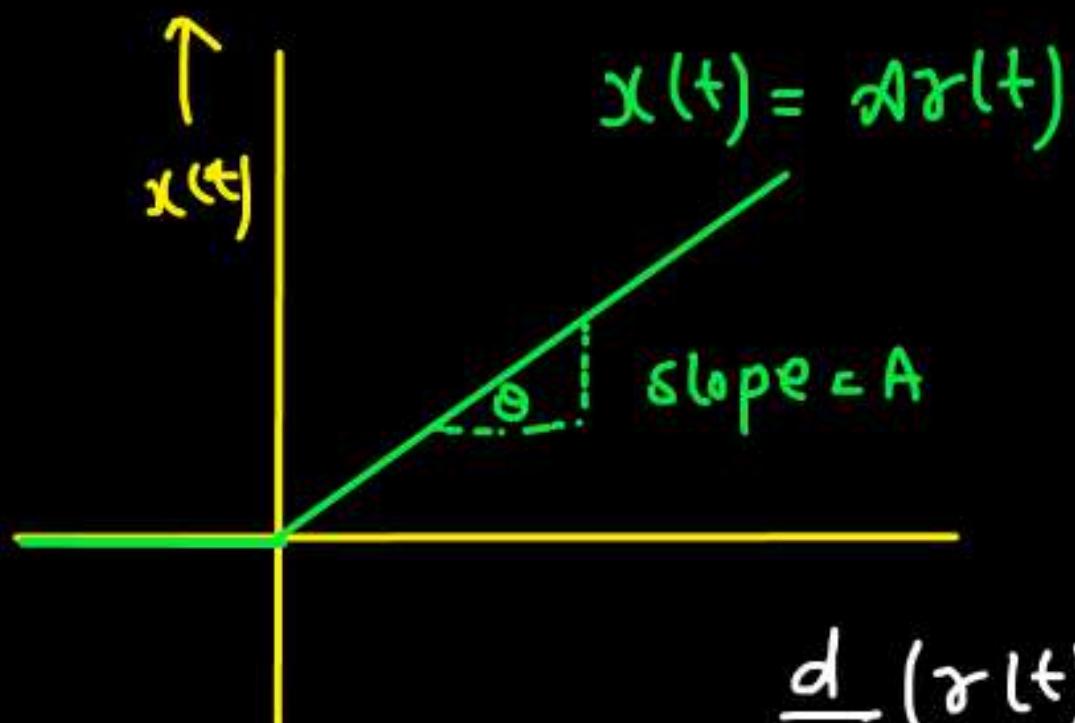

$$\frac{d}{dt}(\tau(t)) = u(t)$$

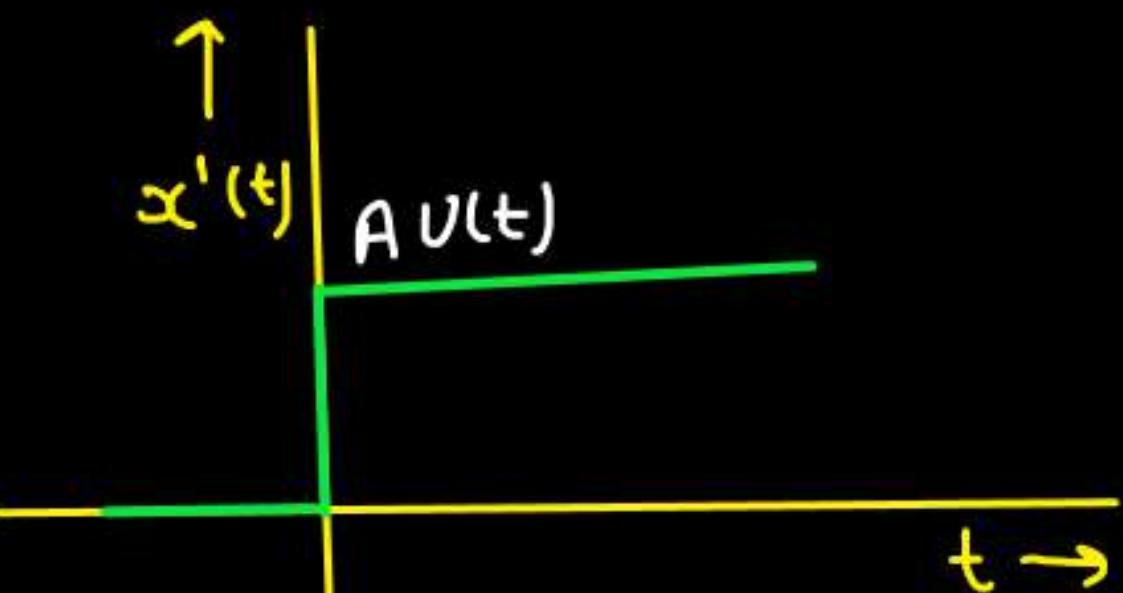


Summary :-



Generating a step signal :-



Q. Find $V_o(t)$.

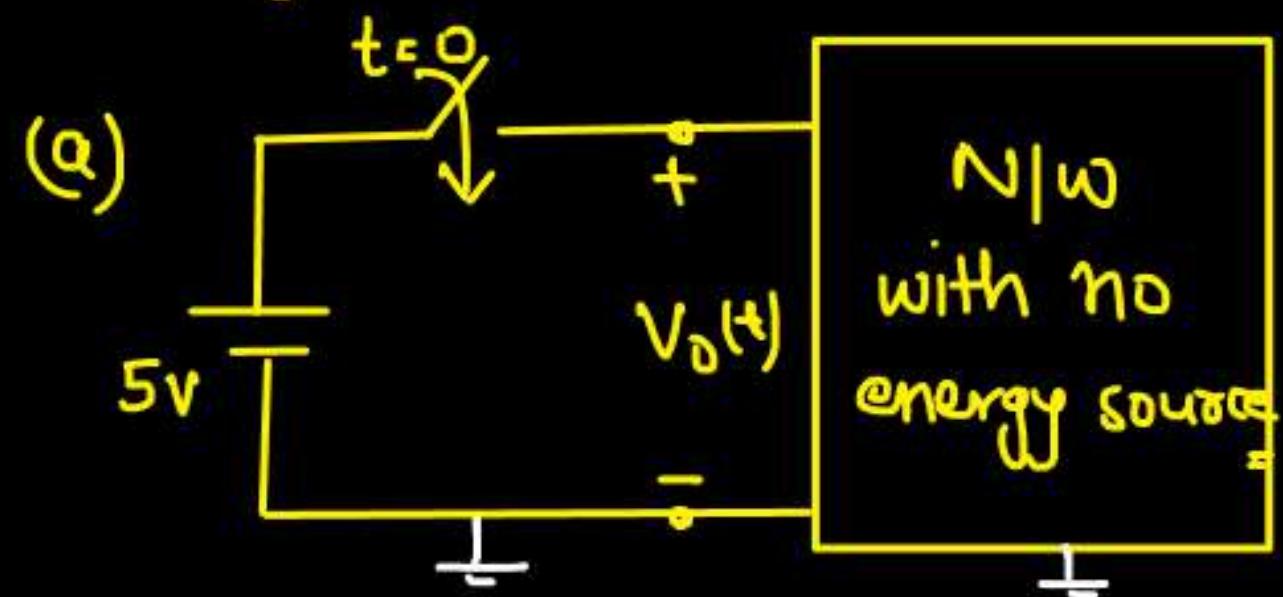


for $t < 0 \Rightarrow V_o(t) = 0V$

for $t > 0 \Rightarrow V_o(t) = 5V$


$$\Rightarrow V_o(t) = 5U(t)$$



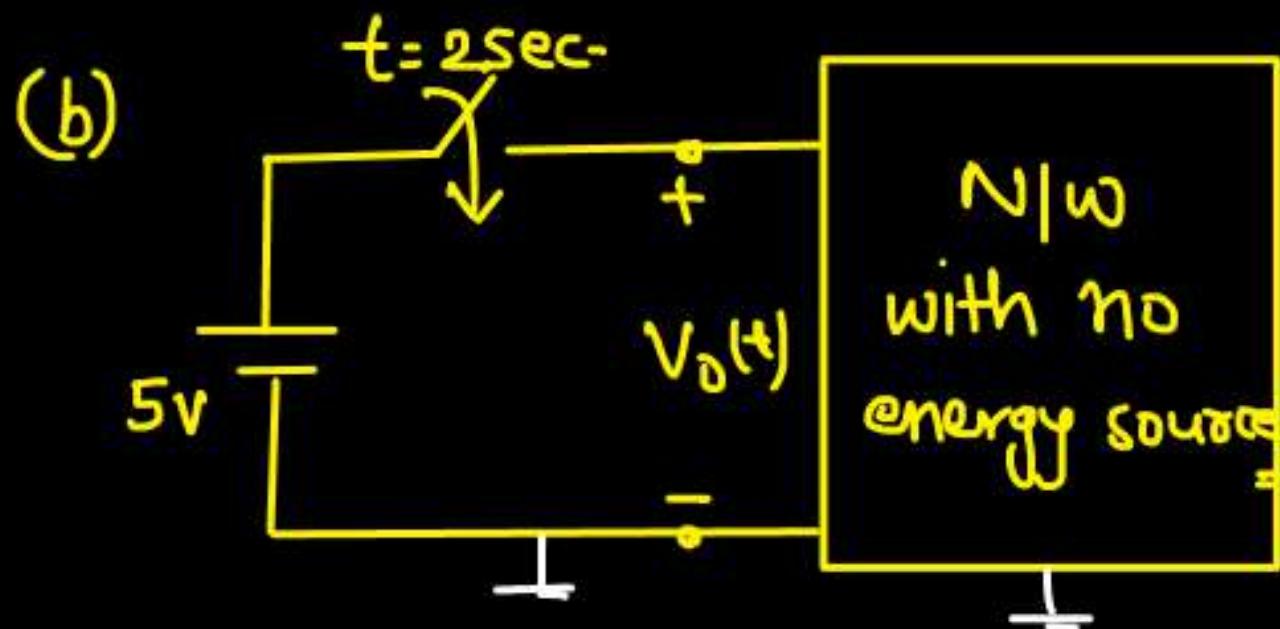

for $t < 2 \text{ sec.} \rightarrow V_o(t) = 0$

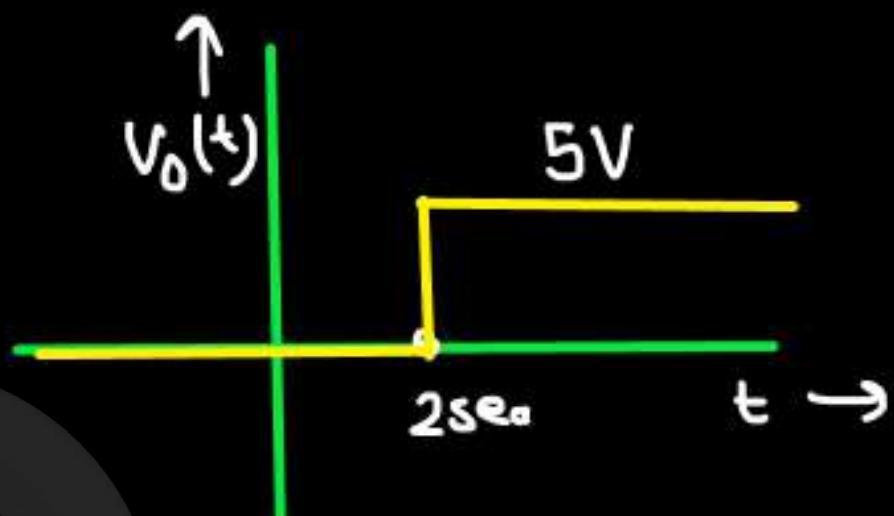$t > 2 \text{ sec.} \rightarrow V_o(t) = 5 \text{ V}$




$$V_o(t) = 5 \mathcal{U}(t - 2)$$

Right shift $\Rightarrow v(t - t_0)$


Left shift $\Rightarrow v(t + t_0)$

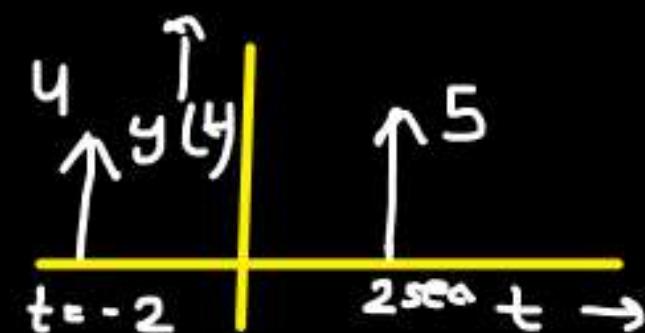Q. Write $y(t)$ in terms of
impulse signals




$$y(t) = 5 \delta(t - 2)$$

$$+ 4 \delta(t + 2)$$

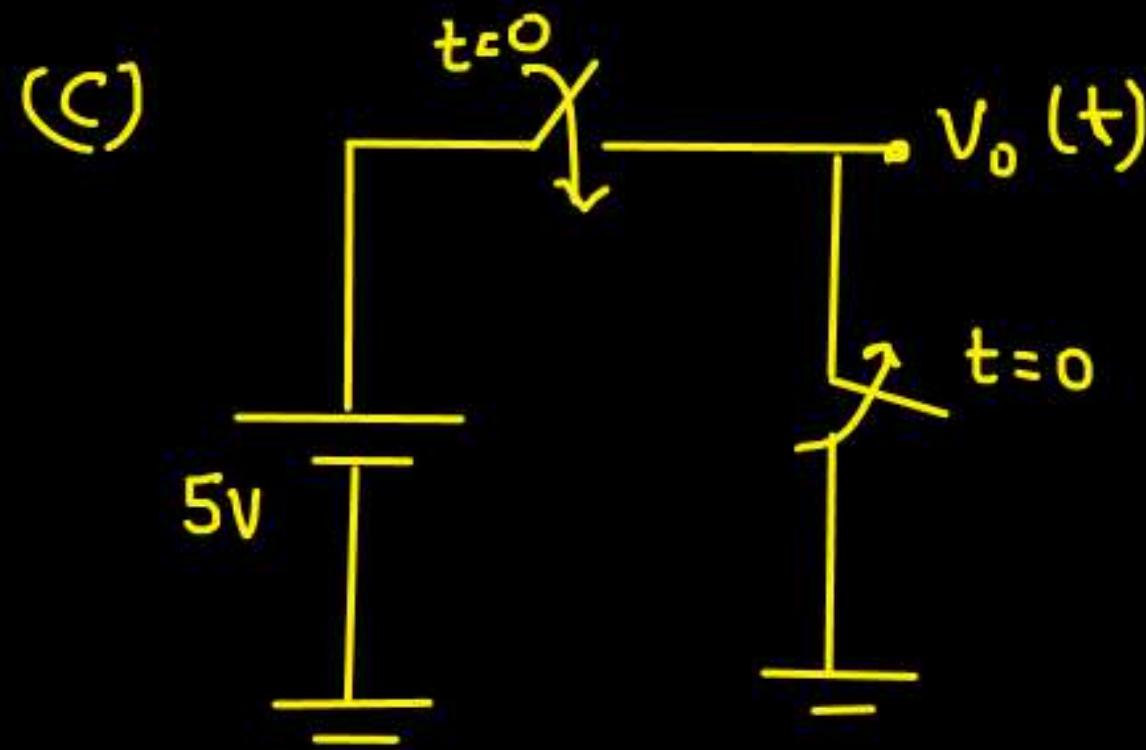


For $t < 0$

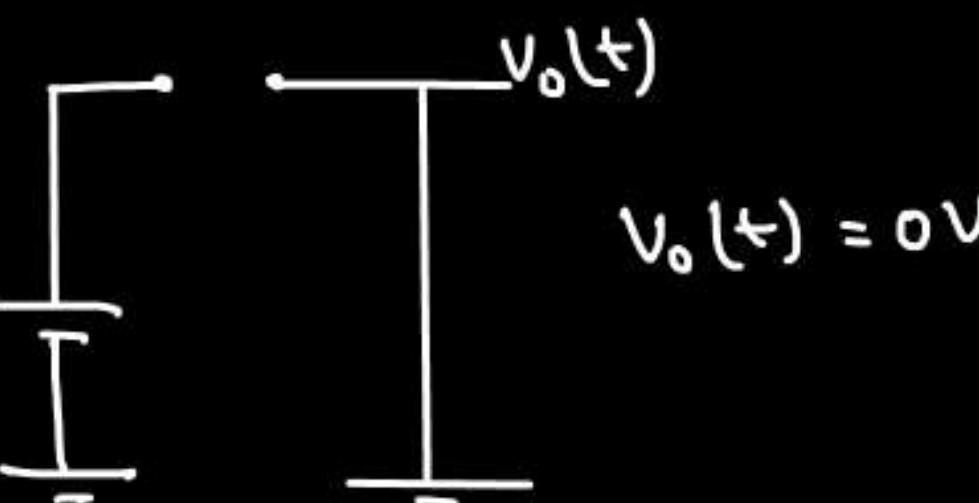

$$V_o(t) = 0 \text{ V}$$

For $t > 0$

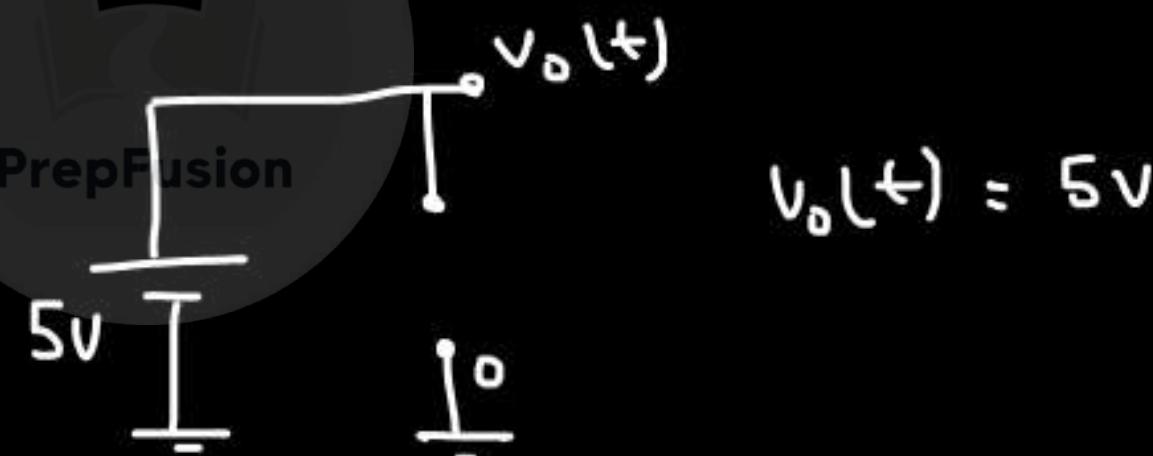



$$V_o(t) = 5 \text{ V}$$


$$\Rightarrow V_o(t+) = 5 U(t)_-$$

AIR 27 (ECE)
AIR 45 (IN)

frequency content in a step signal:-

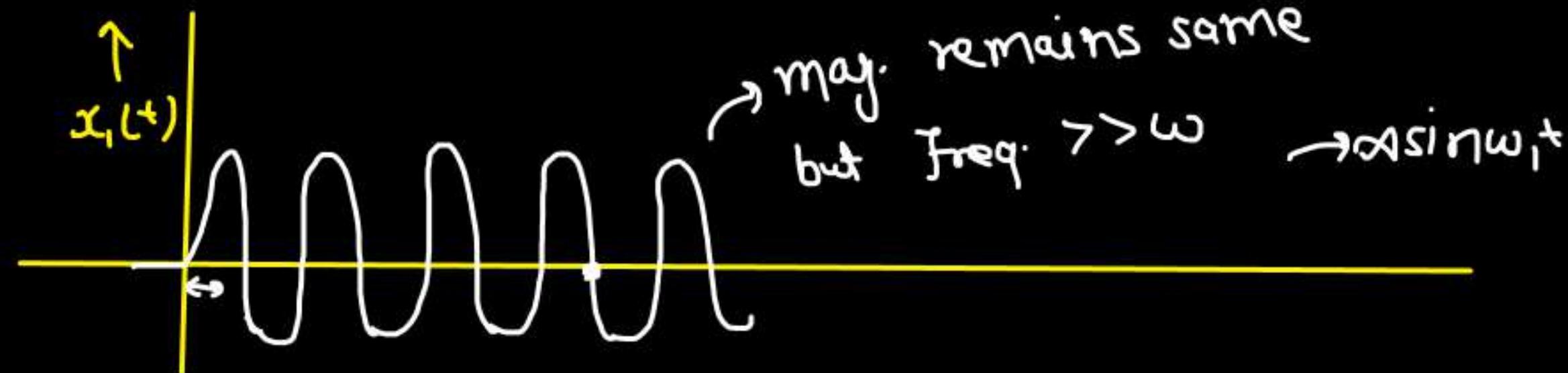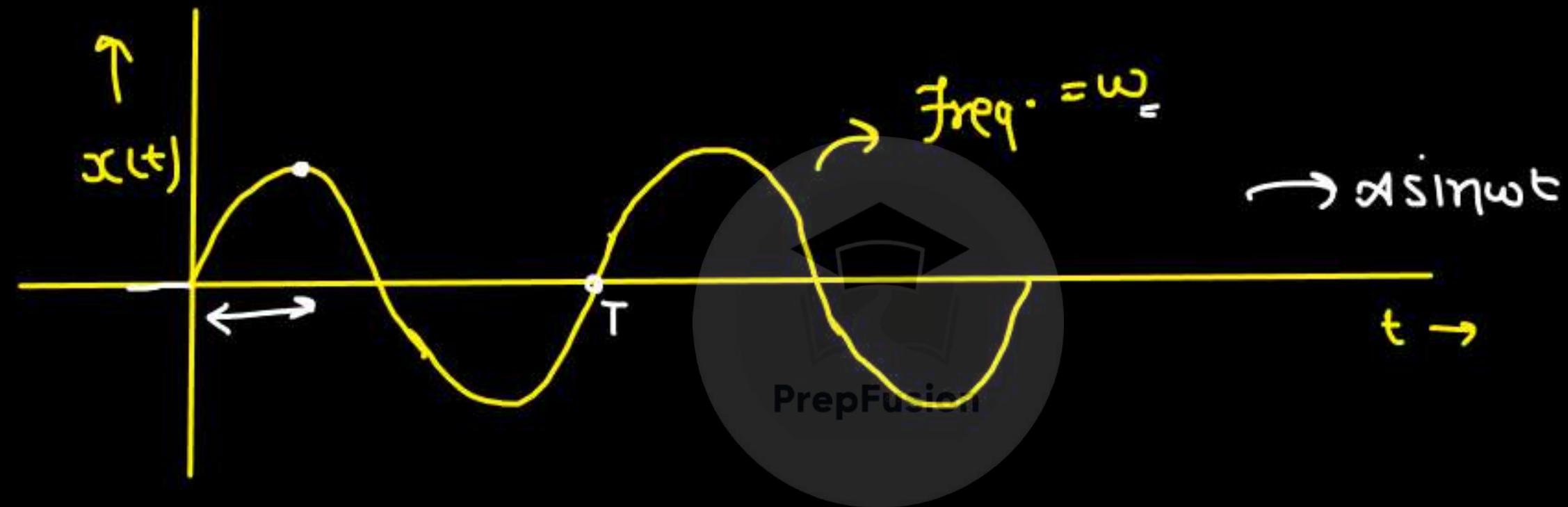↳ let's take an example of a sinusoid signal.




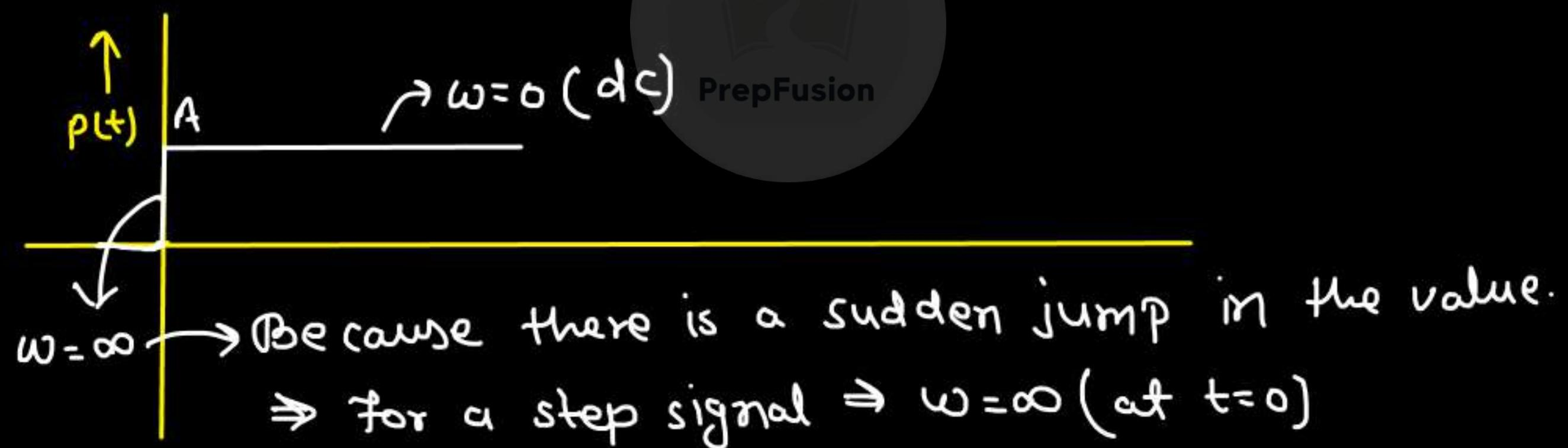

In-depth analysis of capacitors

* Capacitors :-

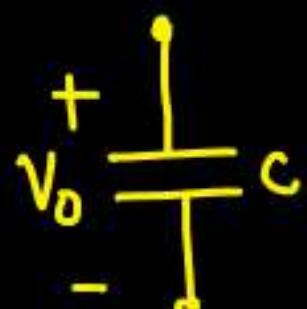
Let's assume a capacitor is initially charged to V_0 voltage.



Initial charge $Q_0 = CV_0$

Initial voltage = V_0

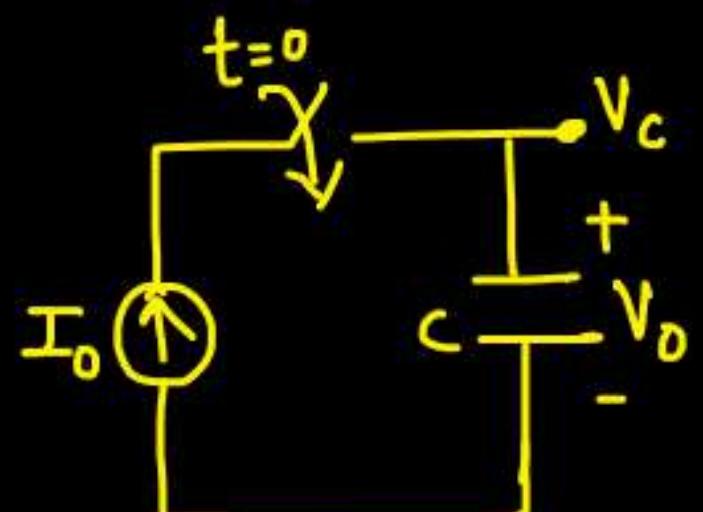Now let's assume, we are forcing some current to the capacitor.



It will charge and gain voltage

$$V_C(t) = V_0 + \frac{1}{C} \int_0^t I_0 dt$$

If you are giving some current to the capacitor,
The capacitor will charge and gain voltage.

Properties of Capacitors:-

- ① Capacitor is a charge storing element.
- ② When there is finite current (not impulse) flowing through the capacitor,

then

$$V_C(t^-) = V_C(t) = V_C(t^+)$$

But $I_C(t^-) \neq I_C(t^+)$

→ capacitor doesn't change its voltage instantaneously but it can change its current instantaneously.


$$\text{Eg. } \rightarrow V_C(0^-) = 5V \Rightarrow V_C(0^+) = 5V$$

$$I_C(0^-) = 1A \Rightarrow I_C(0^+) \neq 1A$$


Initial and final condition:-

* Initial condn of capacitor:- ($t = 0$)

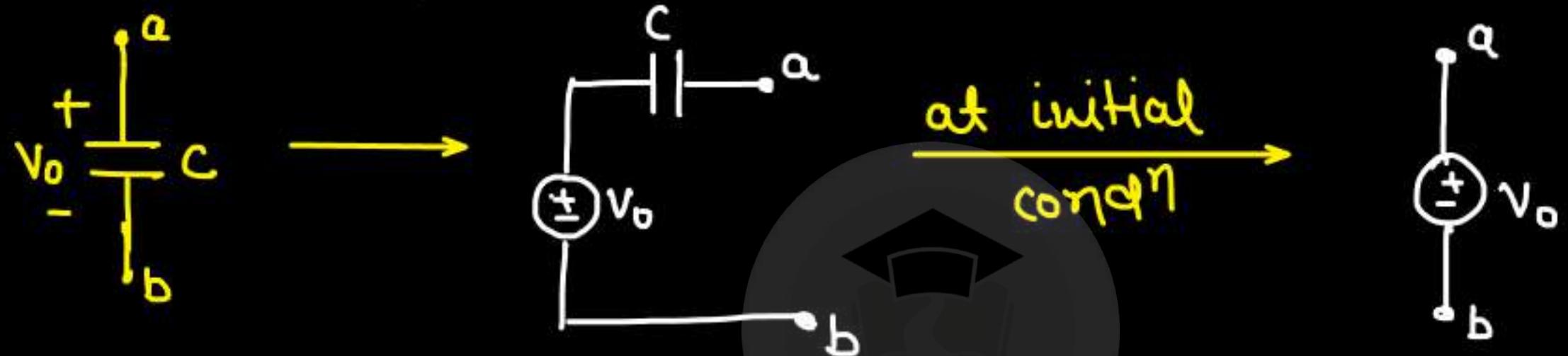Let's assume a capacitor is initially charged to V_0 voltage.



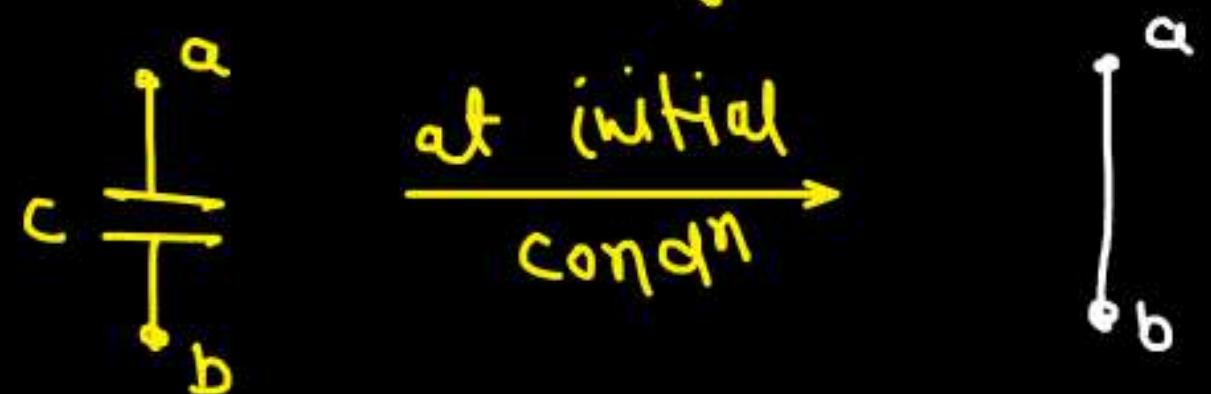- Replace the cap. with it's initial voltage.
- If there is no charge on cap.



Current zero = D.C.
Voltage zero = S.C.

Steady state of Capacitor :- ($t = \infty$)

↳ When the current flow stops in the capacitor




The capacitor will not charge further



The capacitor has reached its max voltage



Steady state

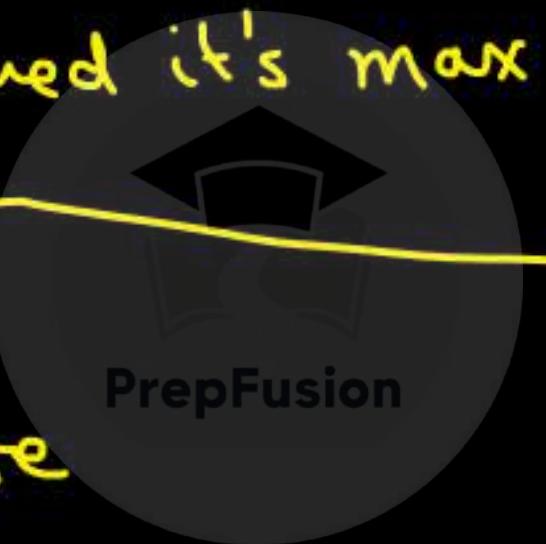

so, at steady state, The cap. will have zero current $\Rightarrow I_c = 0$
↳ D.C.

\Rightarrow at steady state, cap is replaced with D.C. $=$



2nd analogy:-

@ steady state, $V_C = \text{max value it can attain}$

$$i_C = C \frac{dV_C}{dt}$$

if $V_C = \text{max}$ $\Rightarrow \frac{dV_C}{dt} = 0$

$$\Rightarrow i_C = 0 \Rightarrow 0 \text{ A}$$


Summary :-

(t=0) Initial condn \rightarrow S.C. (if there is no initial voltage)

(t= ∞) Steady state \rightarrow D.C.



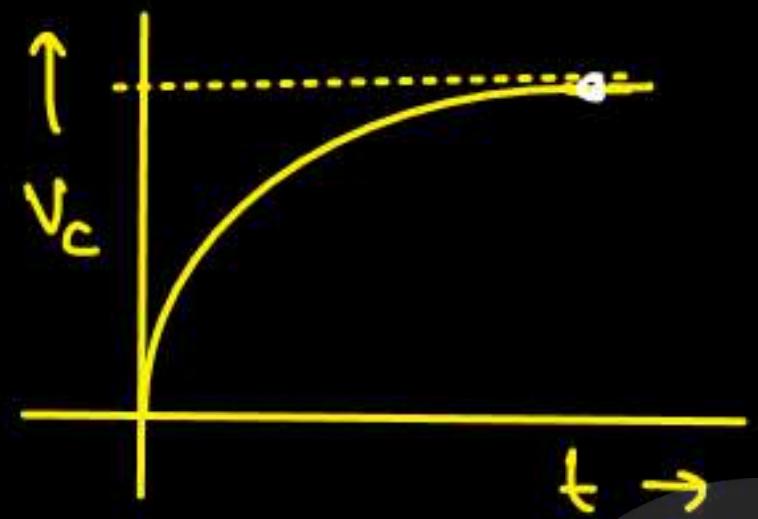
Q. The curve for "Voltage across cap. V_C " is given.



Comment on the current curve I_C across the capacitor.



$$I_C \propto C \frac{dV_C}{dt}$$

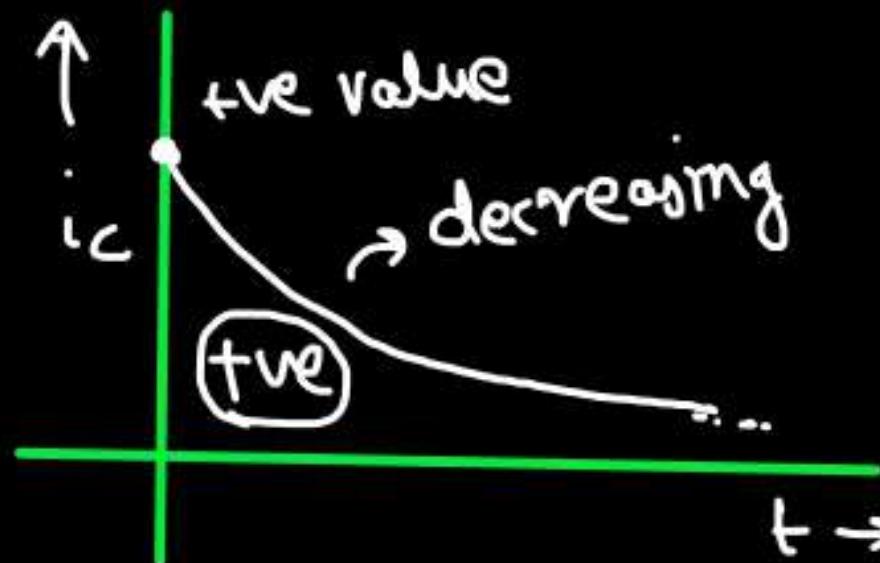

PrepFusion


↳ for the given curve ; $\frac{dV_C}{dt} = +ve \Rightarrow I_C = +ve$

↳ $\frac{dV_C}{dt}$ is always decreasing and goes down to 0.
 $\Rightarrow I_C$ always decreases and goes to 0.




Q. Write the eqn for $v_o(t)$.


(a)

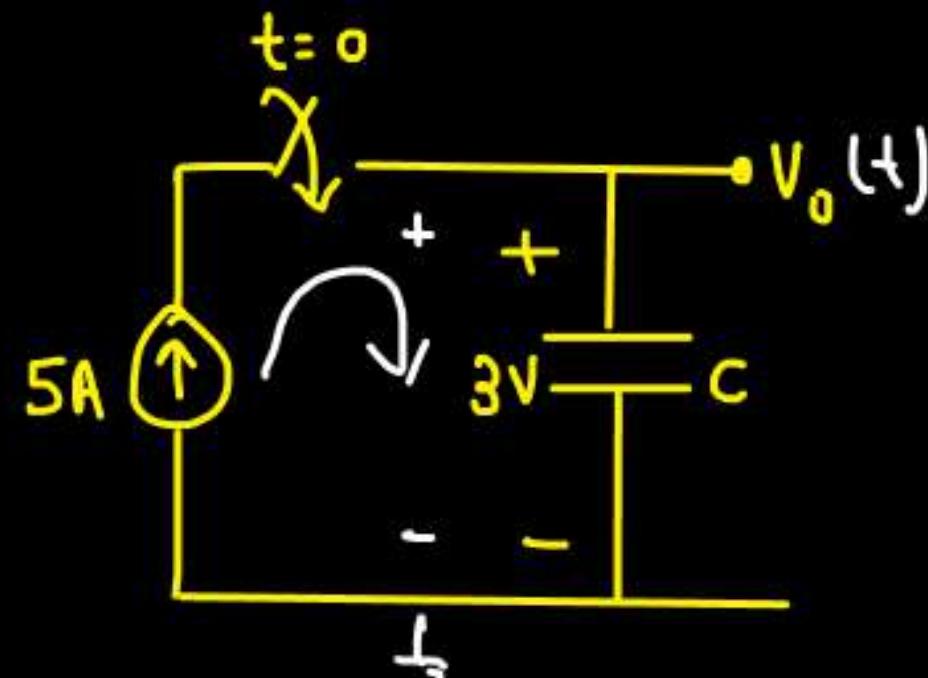

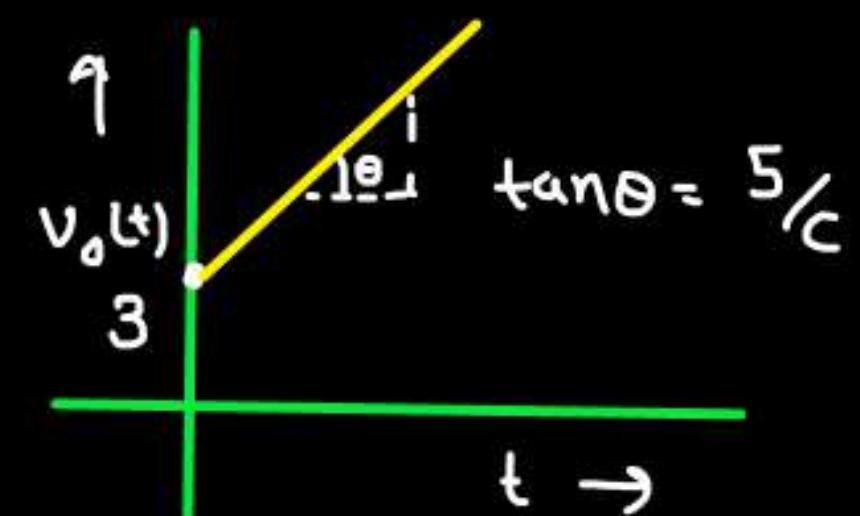
$$\begin{aligned}v_o(t) &= 3 + \frac{1}{C} \int 5 \cdot dt \\&= 3 + \frac{5t}{C}\end{aligned}$$




(b)

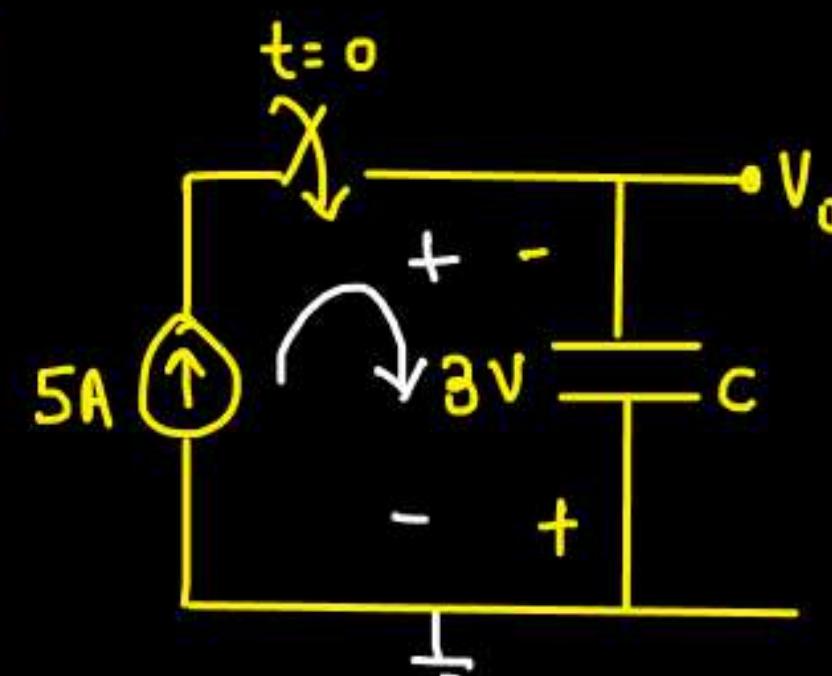


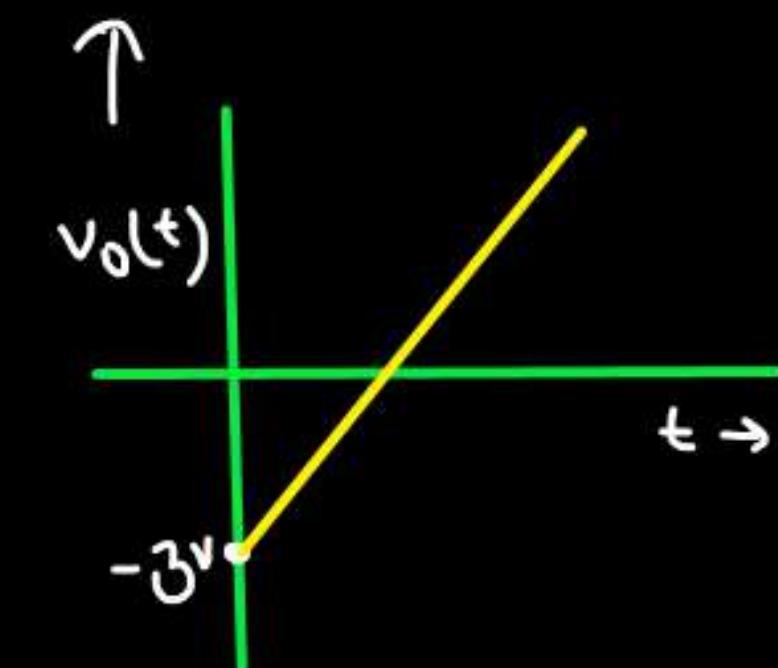
$$\begin{aligned}v_o(t) &= -3 + \frac{1}{C} \int i dt \\&= -3 + \frac{5t}{C}\end{aligned}$$



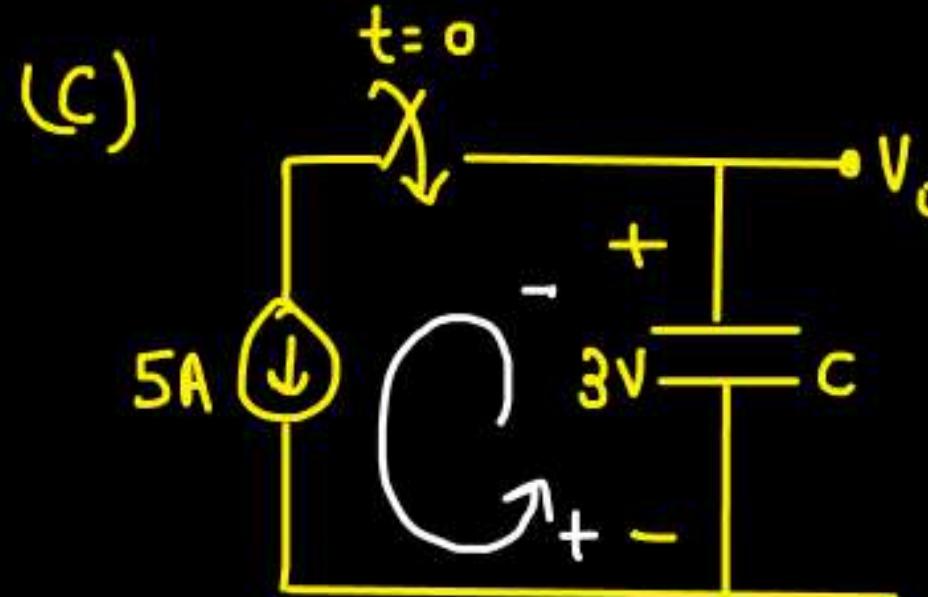


$$V_o(t) = 3 - \frac{1}{C} \int i dt$$

$$V_o(t) = 3 - \frac{5t}{C}$$

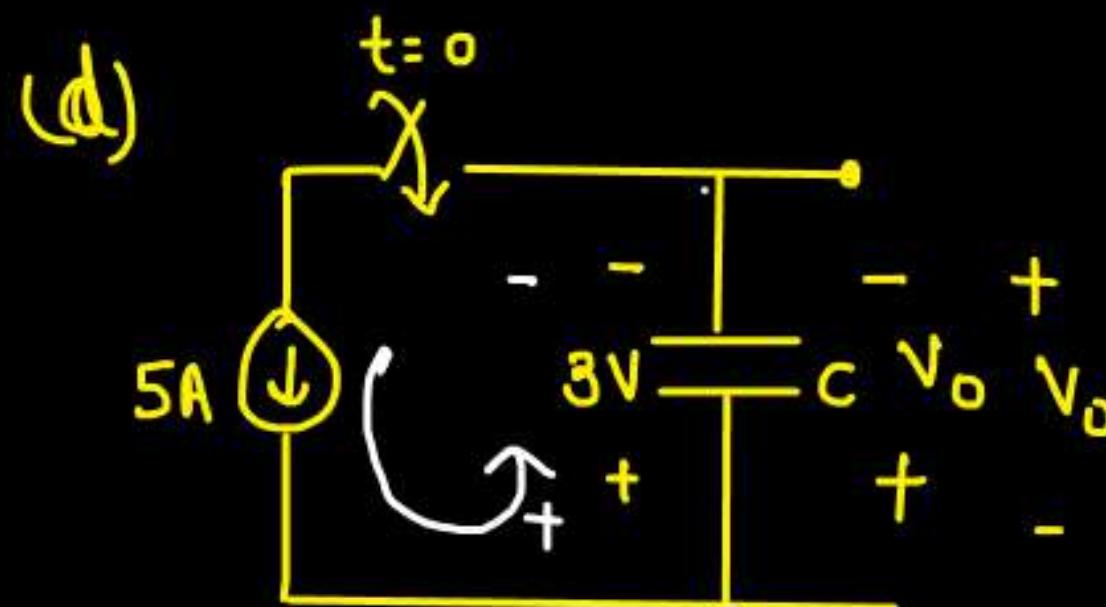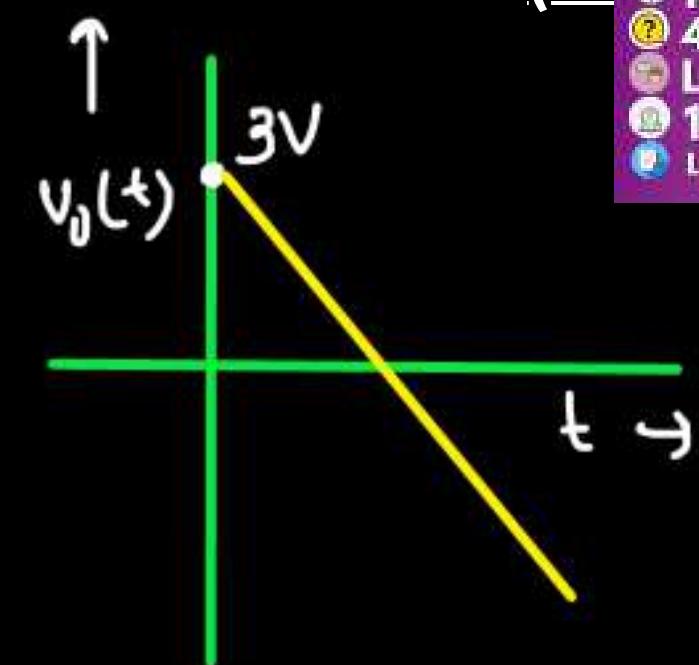

$$V_o(t) = 3 + \frac{5t}{C}$$
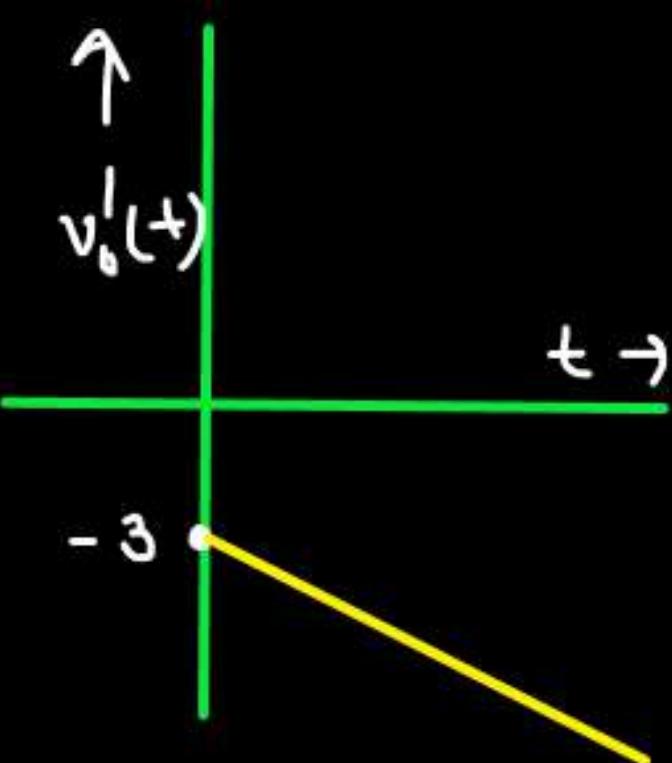
$$V_o'(t) = - \left[3 + \frac{5t}{C} \right]$$






- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

Zero order ckt:-

- ↳ ckts having no storing elements. (Cap. A Inductance & Capacitance)
- ↳ Order of differential eqⁿ is zero.

Eg. .

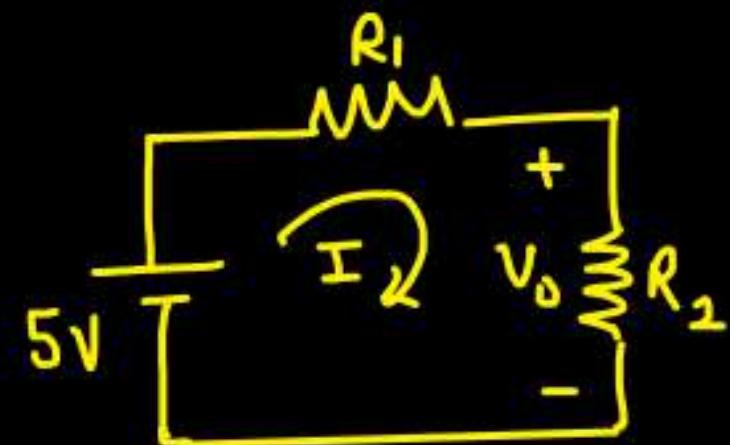

$$I = \frac{5}{R_1 + R_2}$$

$$V_o = \frac{5R_2}{R_1 + R_2}$$

→ zero order differential
eqⁿ

"



Zero order ckt =


YouTube -PrepFusion
**(CLICK HERE FOR FULL
PLAYLIST)**

First order ckt:-

- ↳ ckts having one effective storing element.
- ↳ Order of differential eqn will be one.

Eg. →

First order RC ckt :-

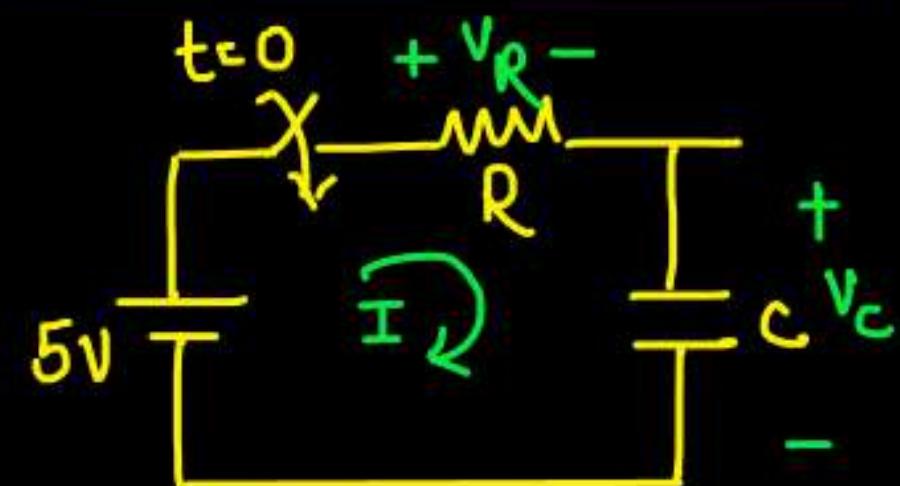


Find $V_R, V_c, I = ?$

→ Method 1 :-

By writing differential eqn :-



① for Current I :-

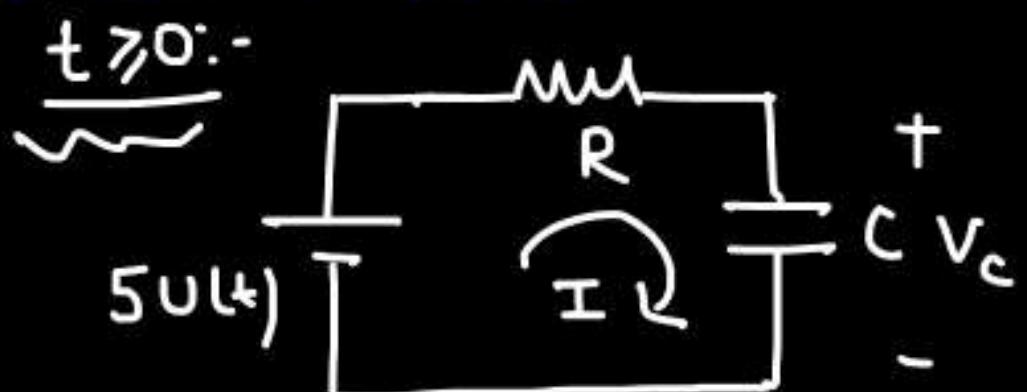

KVL :-

$$5 = IR + \frac{1}{C} \int I dt$$

differentiation on both sides

$$0 = R \frac{dI}{dt} + \frac{I}{C}$$

$$\Rightarrow R \frac{dI}{dt} + \frac{I}{C} = 0 \rightarrow \text{1st order differential eqn}$$

Solve

$$R \frac{dI}{dt} + \frac{I}{C} = 0$$

$$f(D) = RD + \frac{I}{C} = 0$$

$$D = -\frac{1}{RC}$$

$$I(t) = C_1 e^{-\frac{1}{RC} t}$$






$$I(t) = C_1 e^{-t/RC}$$

$$\text{at } t=0 \quad I(0) = C_1$$


Ckt @ t=0 :-

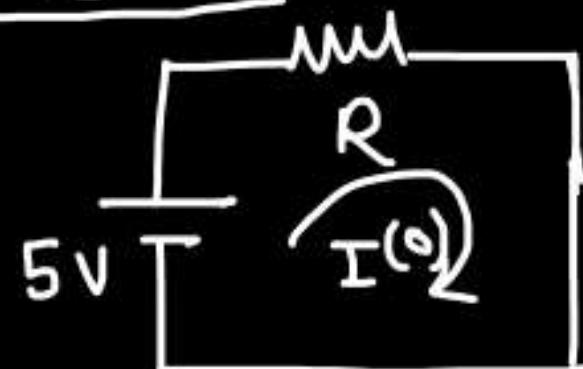

→ cap is shorted @ $t=0$


$$I(0) = \frac{5}{R} = C_1$$
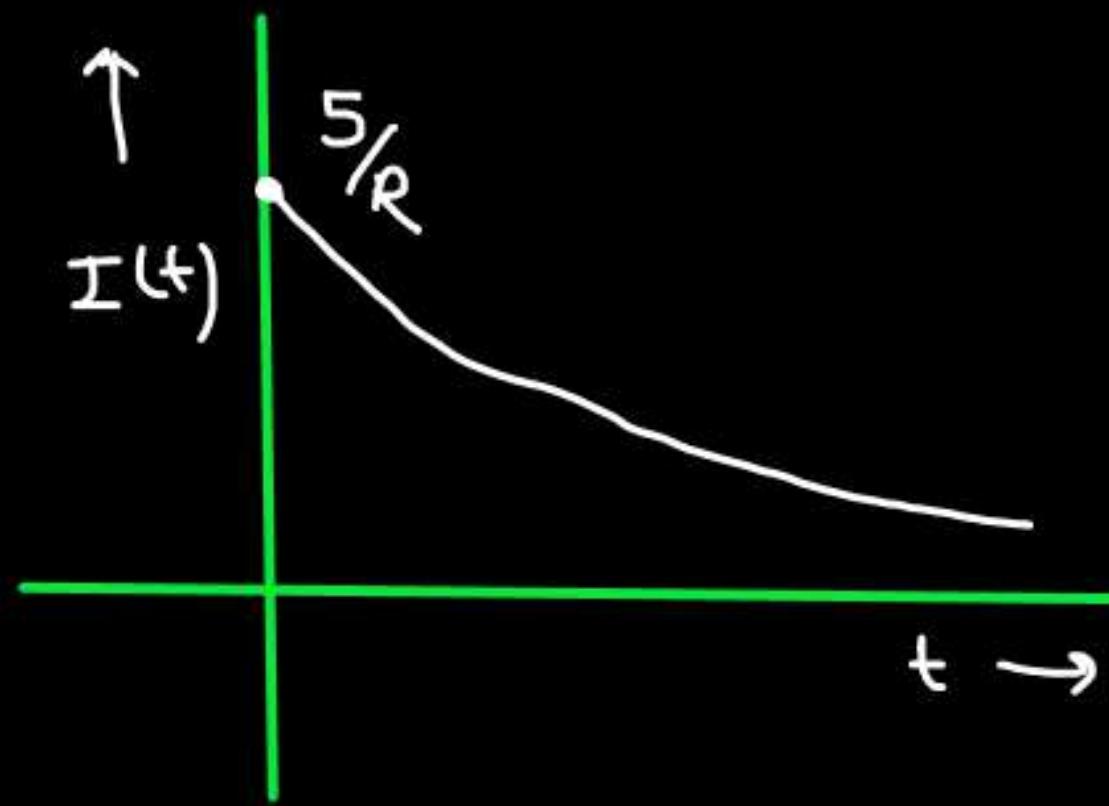
$$\Rightarrow I(t) = \frac{5}{R} e^{-t/RC}$$





② for voltage V_R

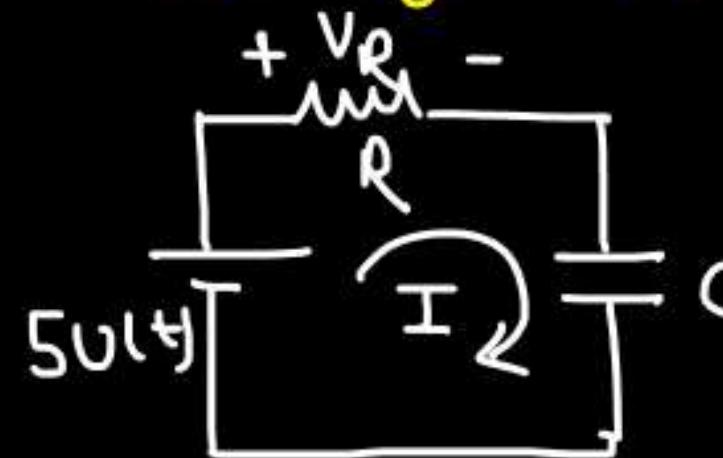

$$S = V_R(t) + \frac{1}{C} \int I(t) \cdot dt$$

$$V_R(t) = I(t) \times R$$

$$I(t) = \frac{V_R(t)}{R}$$

PrepFusion

$$\Rightarrow S = V_R(t) + \frac{1}{C} \int \frac{V_R(t)}{R} \cdot dt$$

differentiating \rightarrow

$$0 = \frac{d}{dt} V_R(t) + \frac{V_R(t)}{RC} \rightarrow \text{1st order ckt}$$

$$(D + \frac{1}{RC}) V_R(t) = 0$$


$$\Rightarrow D = -\frac{1}{RC}$$

$$V_R(t) = C_1 e^{-\frac{1}{RC}t}$$

$$V_R(t) = C_1 e^{-\frac{1}{RC}t}$$

$$@ t=0 ; V_R(0) = C_1$$


ckt @ t=0

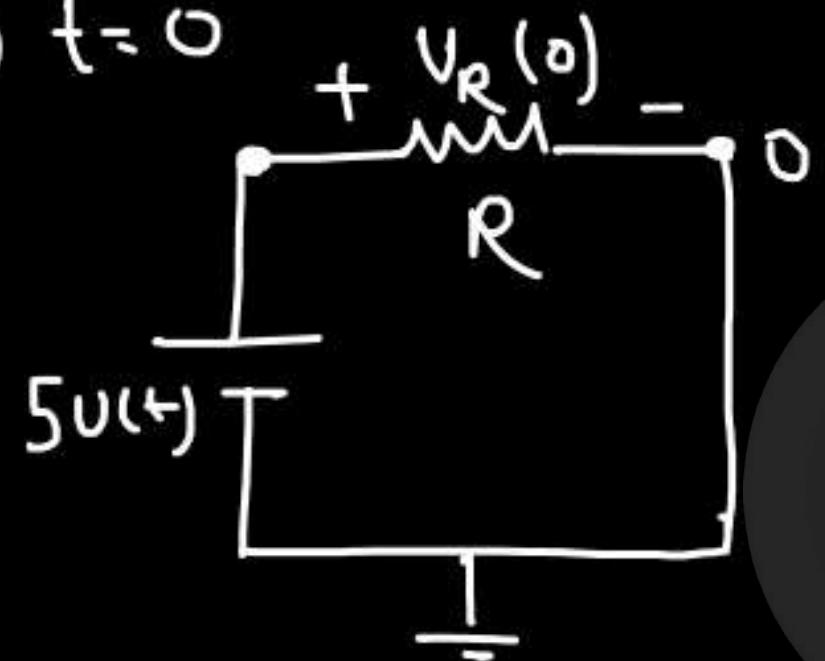


$$V_R(0) = 5V = C_1$$


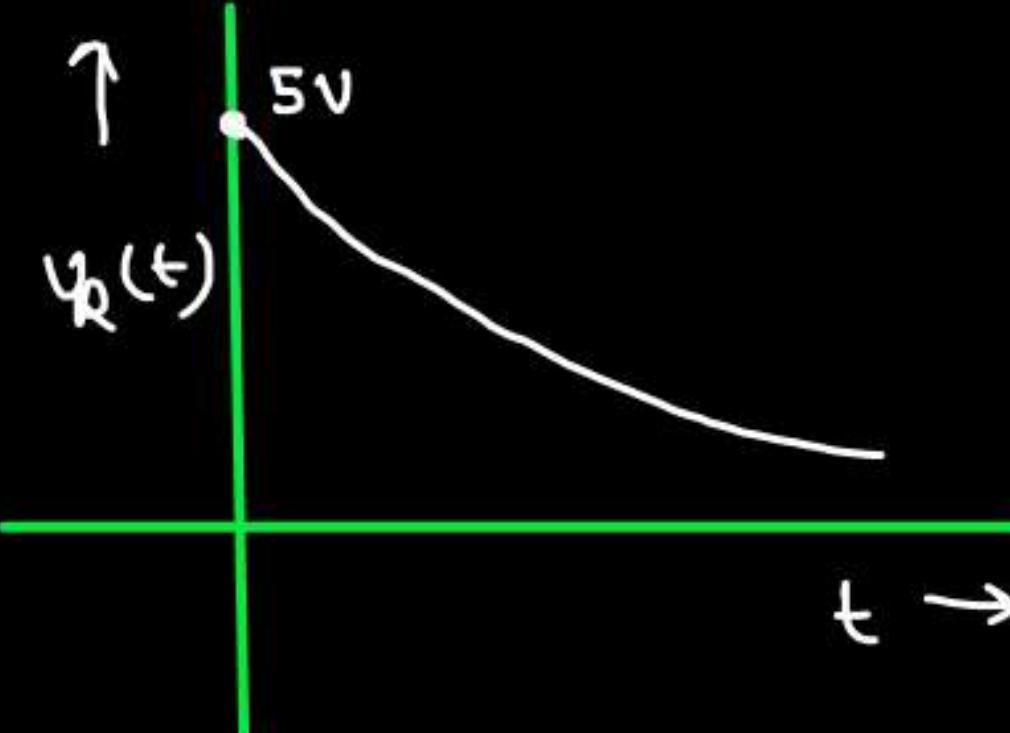
$$\Rightarrow V_R(t) = 5 e^{-\frac{t}{RC}}$$



③ For voltage V_C :-

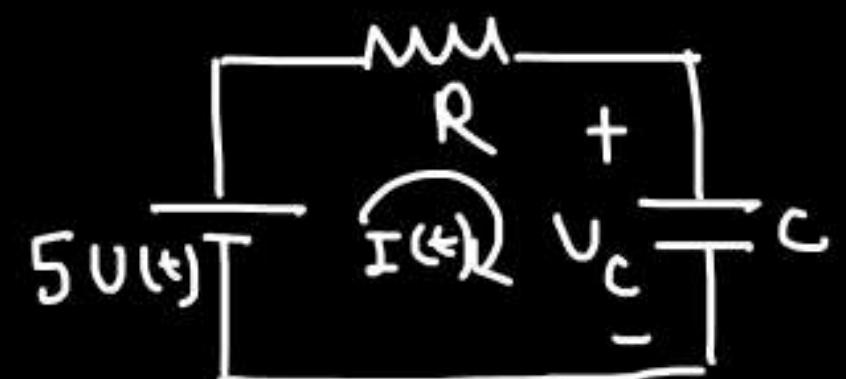

$$S = I(t) R + V_C(t)$$

By eqn ①

$$S = RC \frac{dV_C(t)}{dt} + V_C(t)$$

PrepFusion
 $\rightarrow 1^{st}$ order ckt

$$V_C(t) = Cf + PI$$

CF:-

$$DRC + I = 0$$

P.I. :-

$$V_C(t) = \frac{5}{DRC + I}$$

$$D = -\frac{1}{RC}$$


Put $D = 0$

P.I. = 5


$$CF = C_1 e^{-\frac{t}{RC}}$$

$$V_C(t) = 5 + C_1 e^{-\frac{t}{RC}} \Rightarrow @ t=0 \Rightarrow V_C(0) = 5 + C_1 =$$

PrepFusion

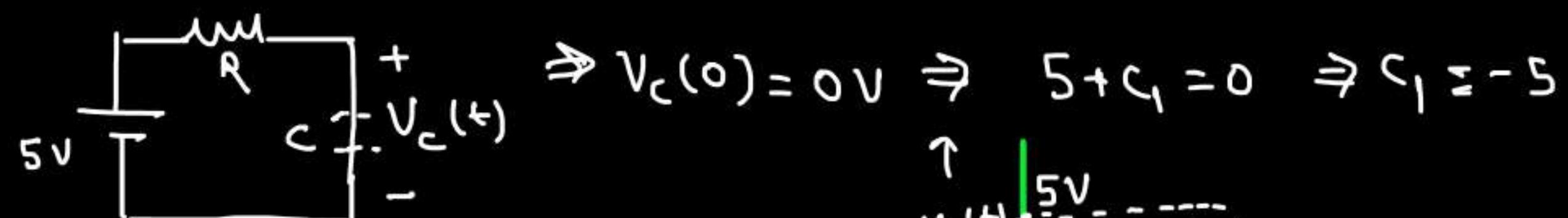ckt @ $t=0$ 
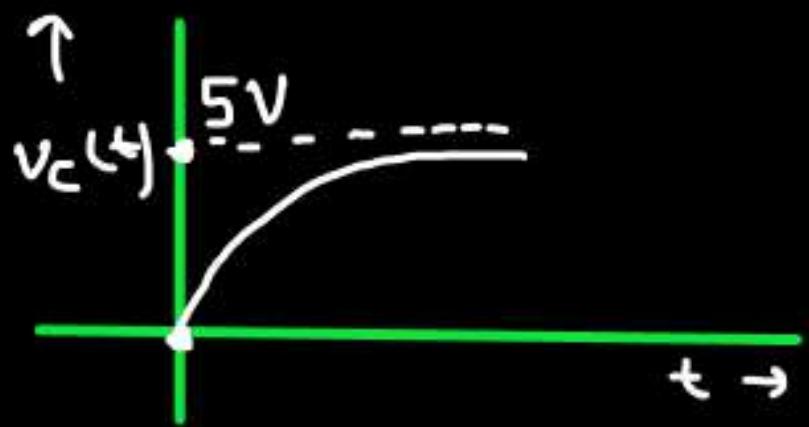
$$\Rightarrow V_C(t) = 5 - 5e^{-\frac{t}{RC}}$$



N.B. -

If there is only one effective storing element



The ckt is first order ckt



The differential eqn for all the parameters (current / voltage)
will be of 1st order only

Soln for first order eqn:-

$$y(t) = y(\infty) + \underbrace{(y(0) - y(\infty)) e^{-\frac{t}{\tau}}}_{\text{Steady state part}} \rightarrow \tau = \text{Time constant}$$

Steady state
part

Transient part

M - IIGeneral sol'n of a 1st order differential eqn


$$Y(t) = Y(\infty) + [Y(0) - Y(\infty)] e^{-t/\tau}$$

 $\tau = ?$ = Time const.

↳ How to find time const. of first order ckt.


- * Nullify the independent sources. [Voltage source \rightarrow S.C., Current source \rightarrow G.C.]
- * Find the effective Storing component.
(Effective cap. | Effective inductance)
- * Find the equivalent resistance across the effective storing element.
- * For 1st order RC ckt, Time constant $\tau = R_{eq} C_{eff}$
1st order RL ckt, Time constant $\tau = \frac{L_{eff}}{R_{eq}}$

Given ckt:-

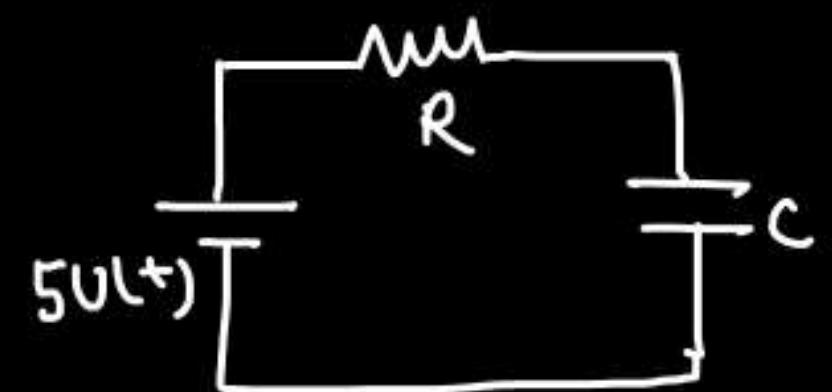


$$\tau = ?$$

\Rightarrow S. c. the voltage source

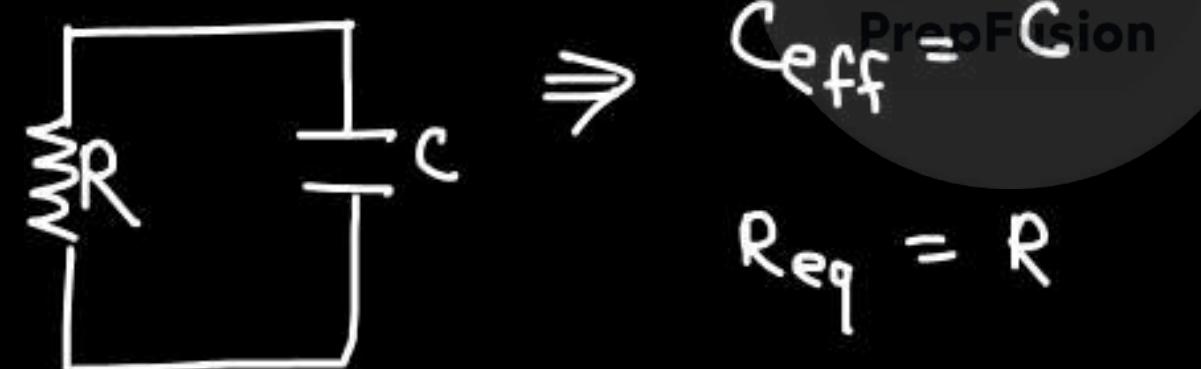


$$\tau = RC$$

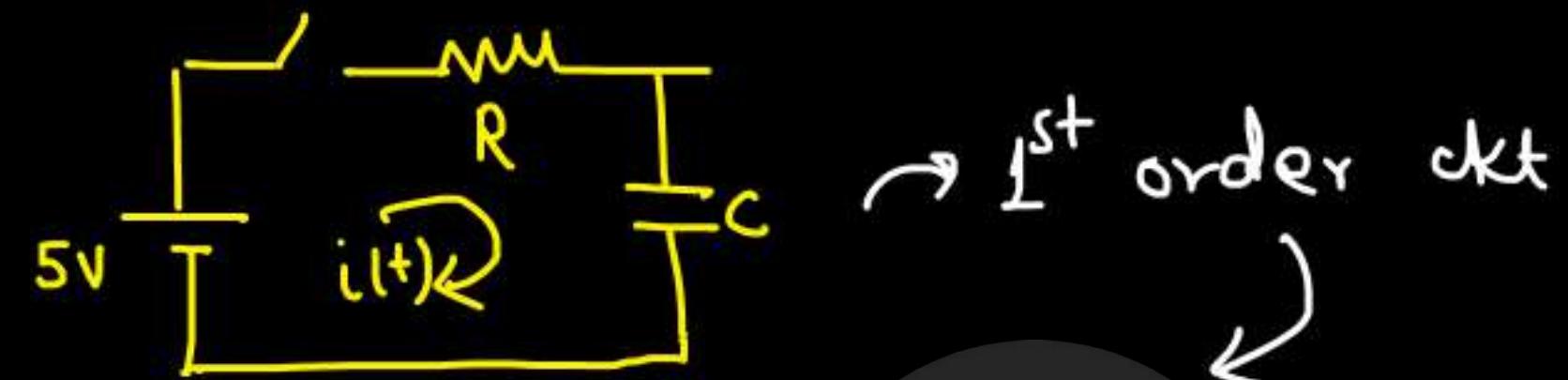Method II:-① Solving for current $i(t)$ 

$$i(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/\tau} \Rightarrow \tau = RC$$

$$i(0) = ?, \quad i(\infty) = ?$$


\Rightarrow CKT @ $t=0$

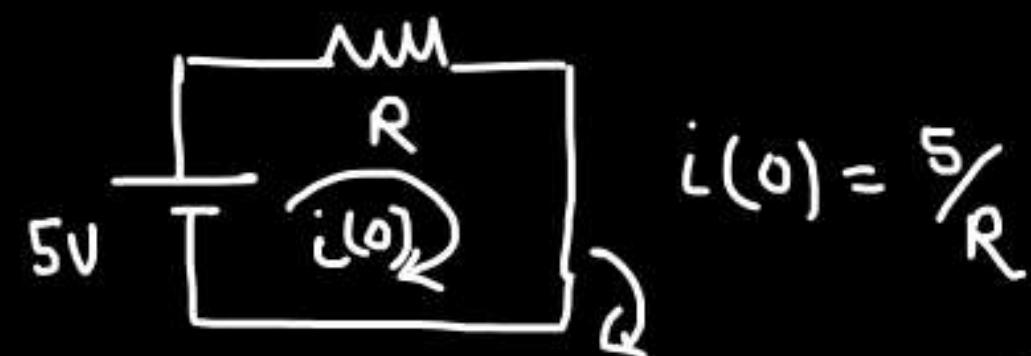

cap. shorted

PrepFusion

CKT @ $t=\infty$

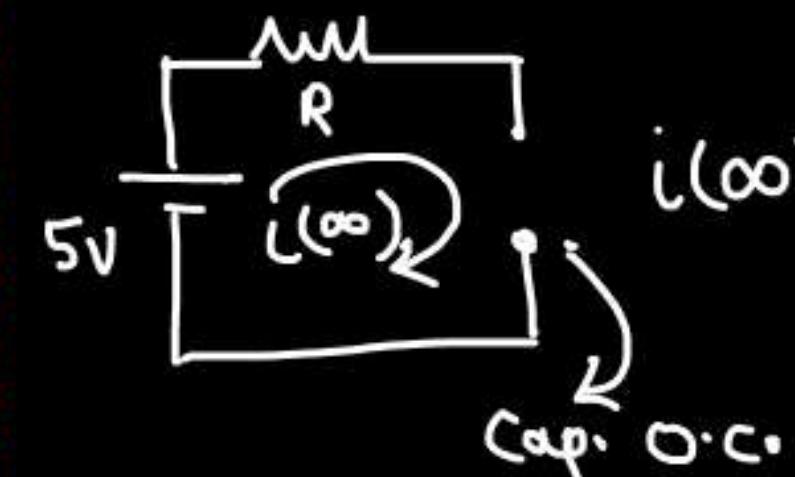

$i(\infty) = 0$ amp.


$$i(t) = 0 + \left(\frac{5}{R} - 0 \right) e^{-t/RC}$$

$$i(t) = \frac{5}{R} e^{-t/RC}$$




Solving for $V_R(t)$:-
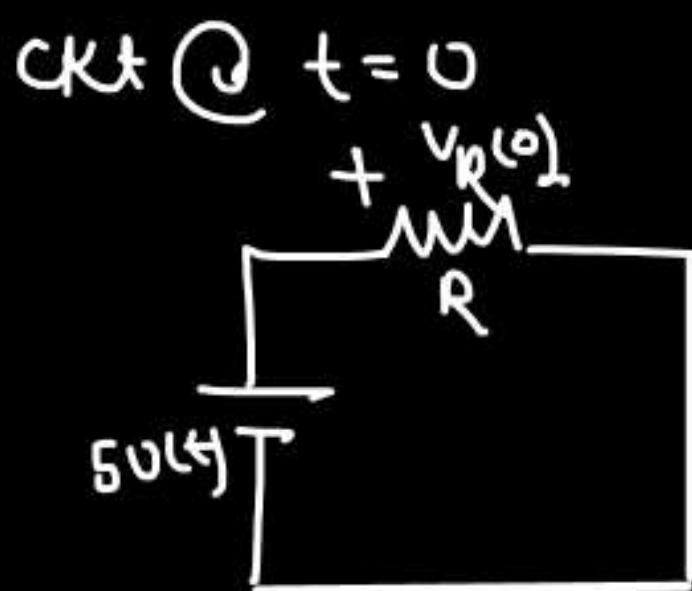
$$V_R(t) = V_R(\infty) + [V_R(0) - V_R(\infty)] e^{-\frac{t}{RC}} \quad ; \text{ Here } \tau = RC$$



$$V_R(0) = 5V$$

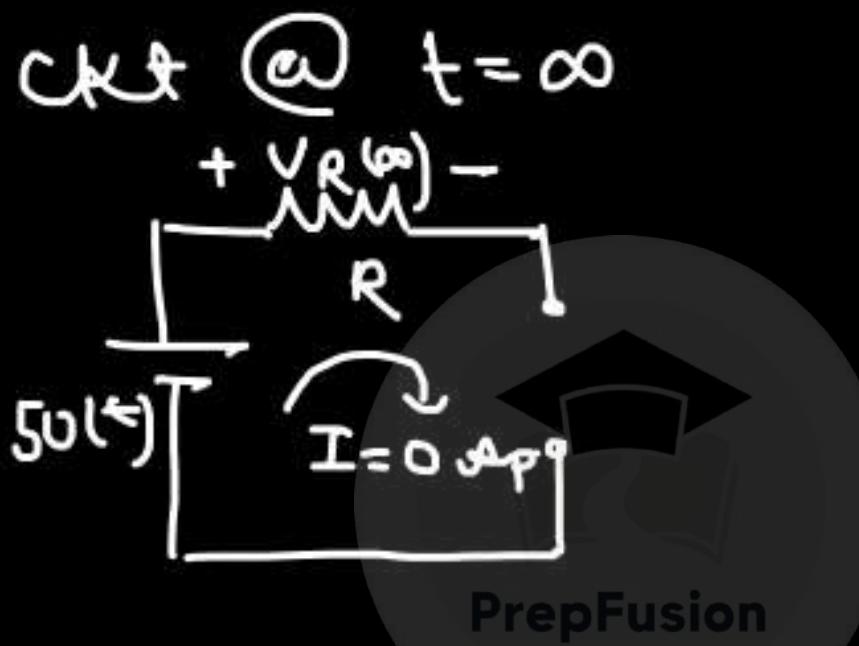

$$V_R(\infty) = 0V$$


$$V_R(t) = 5e^{-\frac{t}{RC}}$$



Solving for $V_c(t)$:-


$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau} ; \quad \tau = RC$$

Ckt @ $t=0$

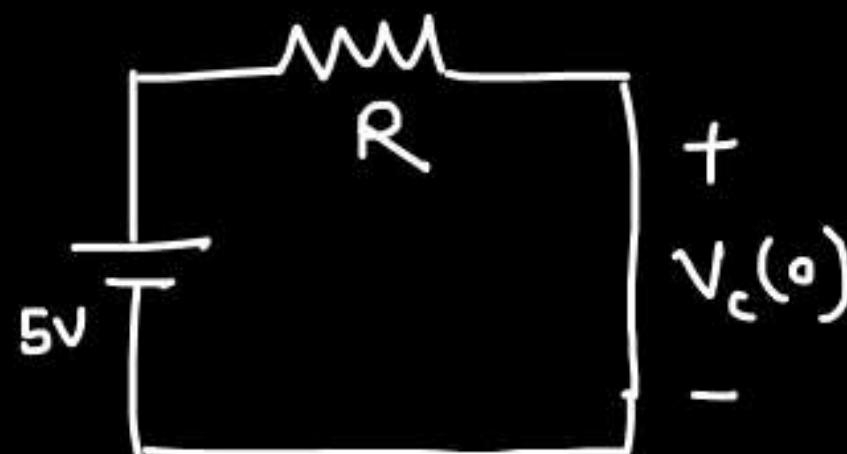

$$V_c(0) = 0 \text{ V}$$

Ckt @ $t=\infty$

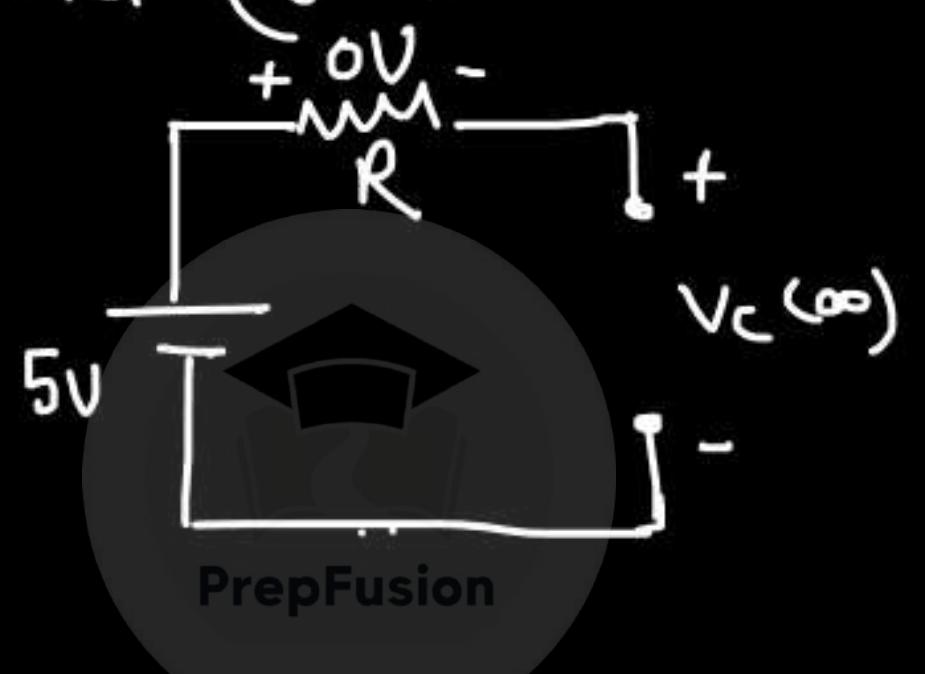


$$V_c(\infty) = 5 \text{ V}$$


$$V_c(t) = 5 + [0 - 5] e^{-t/\tau_{RC}}$$

$$V_c(t) = 5 (1 - e^{-t/\tau_{RC}})$$

* Understanding the ckt:-

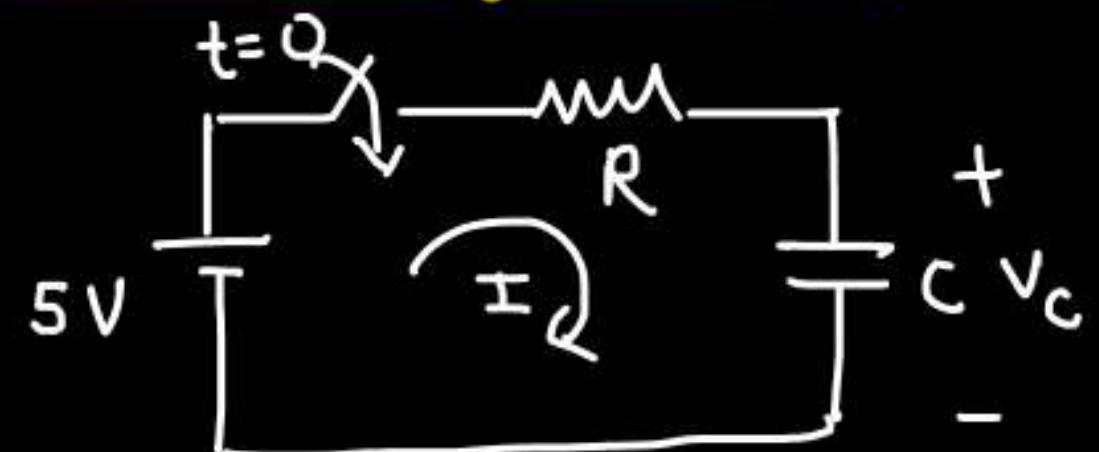

@ $t=0 \Rightarrow$ cap. acts as S.C.

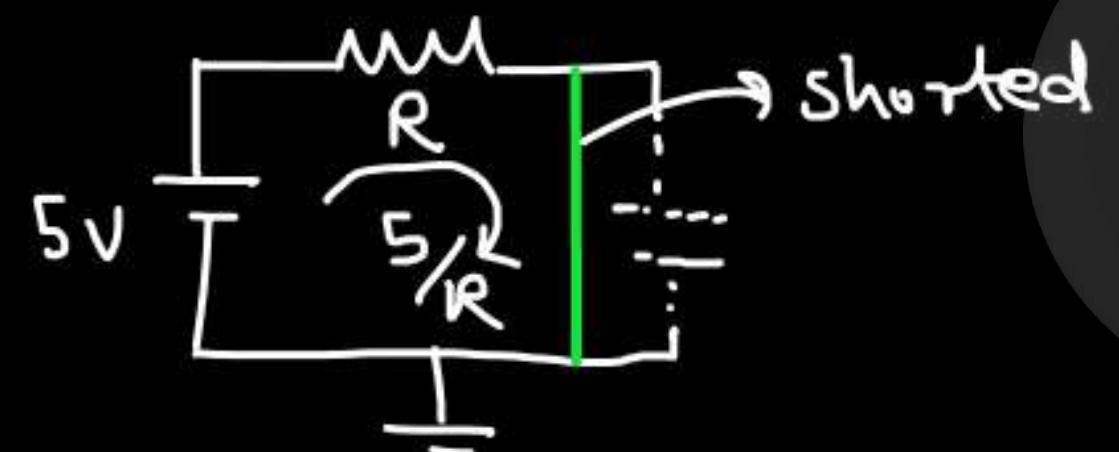

\Rightarrow This $\frac{5}{R}$ current flows through the cap \Rightarrow This charges the cap.


cap. start developing the voltage.

$I(0) = \frac{5}{R} \Rightarrow$ charging the cap.



Let's assume, after sometime the cap. is charged to
(Because of the current)

@some time t_1

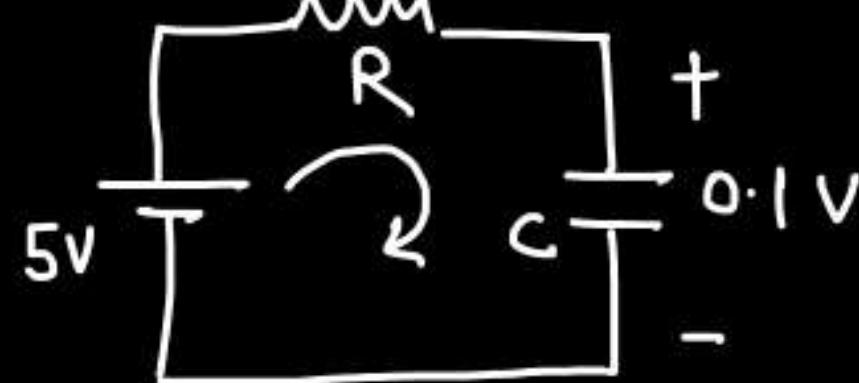


$$I(t_1) = \frac{4.9}{R} \Rightarrow \text{charges the cap. in the same dirn}$$

⇒ Although the current has reduced but still it's flowing in the same dirn that charges the cap. with more voltage.

now, let's assume, after some more time, the cap. is charged to 2V.

[YouTube -PrepFusion](#)
[\(CLICK HERE FOR FULL PLAYLIST\)](#)

@ Some time t_2

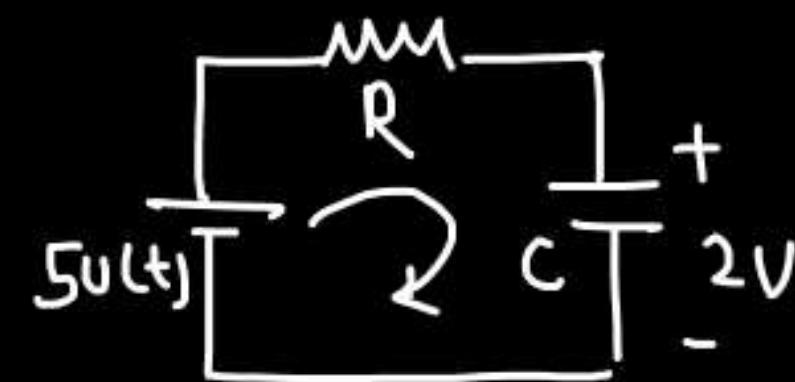

$$I(t_2) = \frac{3}{R} \text{ Amps}$$

⇒ But still it charges the cap.

$$\Rightarrow I(0) = \frac{5}{R}, \quad I(t_1) = \frac{4.9}{R}, \quad I(t_2) = \frac{3}{R}$$

$$v_c(0) = 0, \quad v_c(t_1) = 0.1, \quad v_c(t_2) = 2V$$

⇒ Slowly the current is reducing and the voltage across the cap is increasing



@ sometime t_3 , $v_c(t_3) \approx 5V \Rightarrow I_c(t_3) = 0 \text{ Amps} \Rightarrow \text{steady state} =$

Also, Here we see that the current is continuously decreasing.

more current \Rightarrow more voltage



Speed of charging \propto amount of current

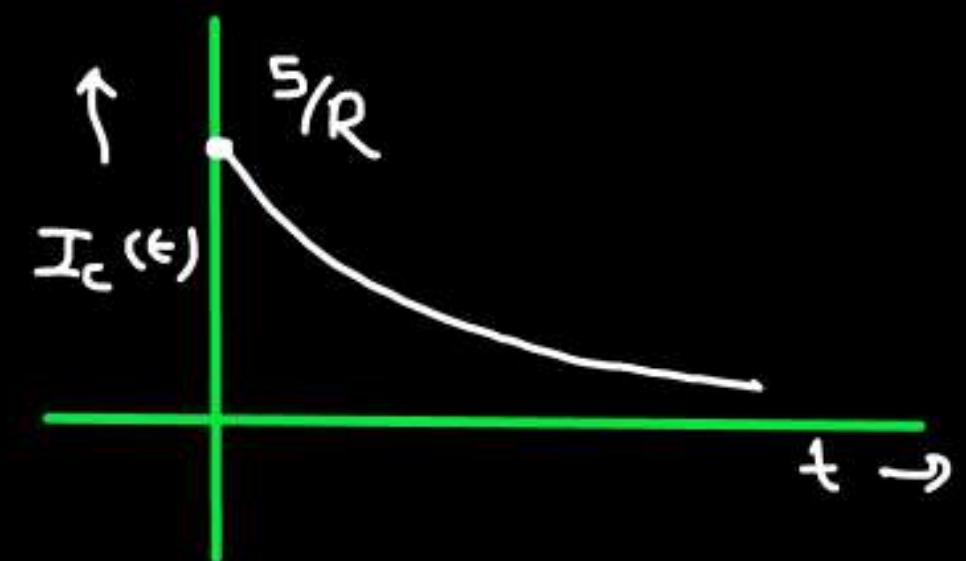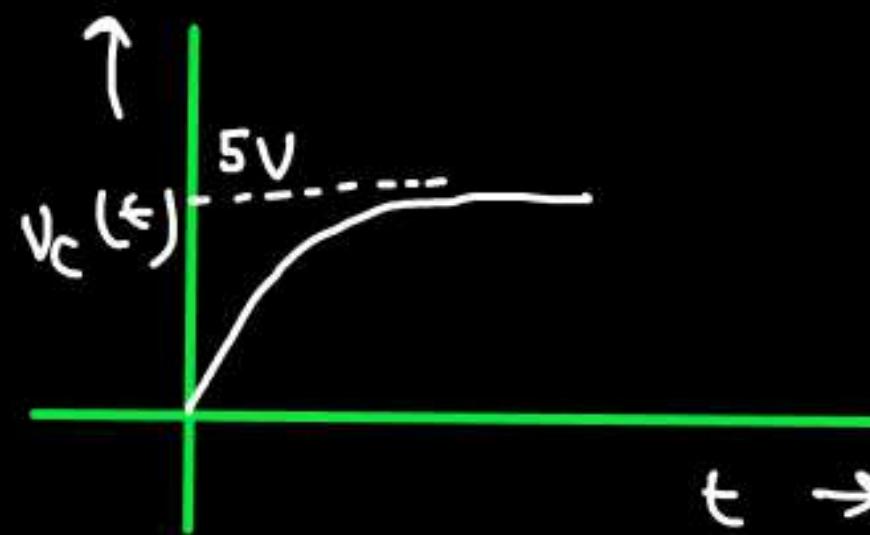\Rightarrow Since current continuously decreased, speed of charging (I), cap. will develop voltage slowly. \Rightarrow with time $\frac{dV_C(t)}{dt}$ is reducing.





Q.

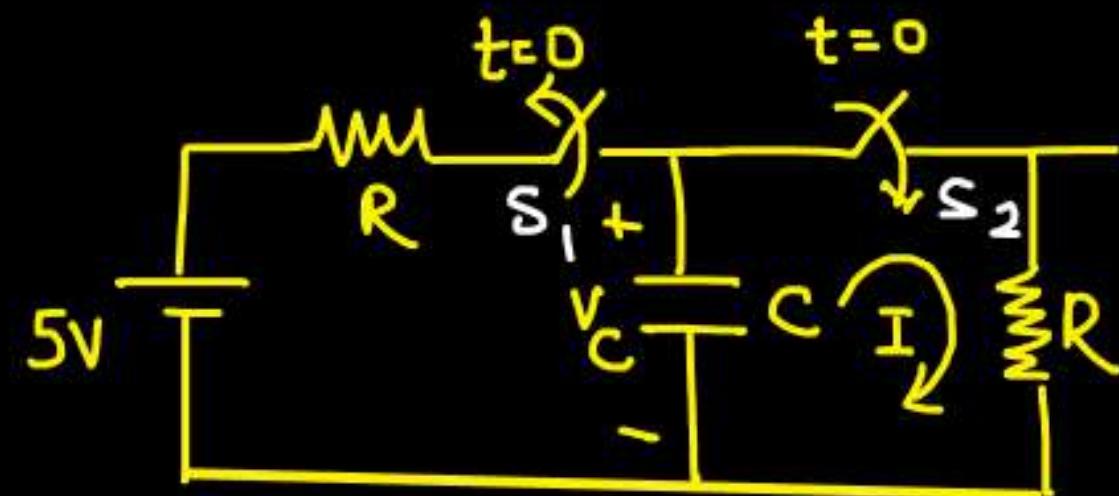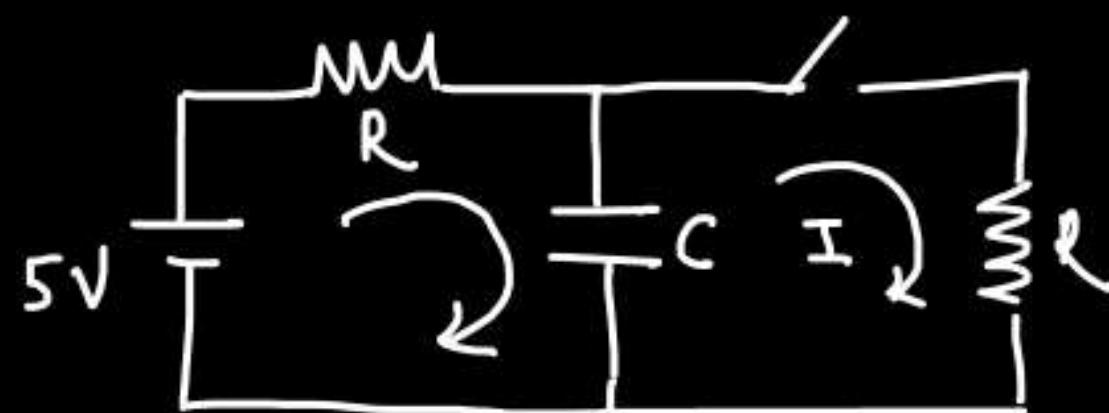
Comment on V_c & I . $\rightarrow S_1$ is closed for $t < 0$ S_1 is opened for $t > 0$ S_2 is closed for $t > 0$ S_2 is opened for $t < 0$ ckt for $t < 0 \{ -\infty < t < 0 \}$ For $t < 0$

$$I(t < 0) = 0 \text{ A}$$



$$V_c(0^-) = 5V$$

 \Rightarrow Switch S_1 is closed for long time

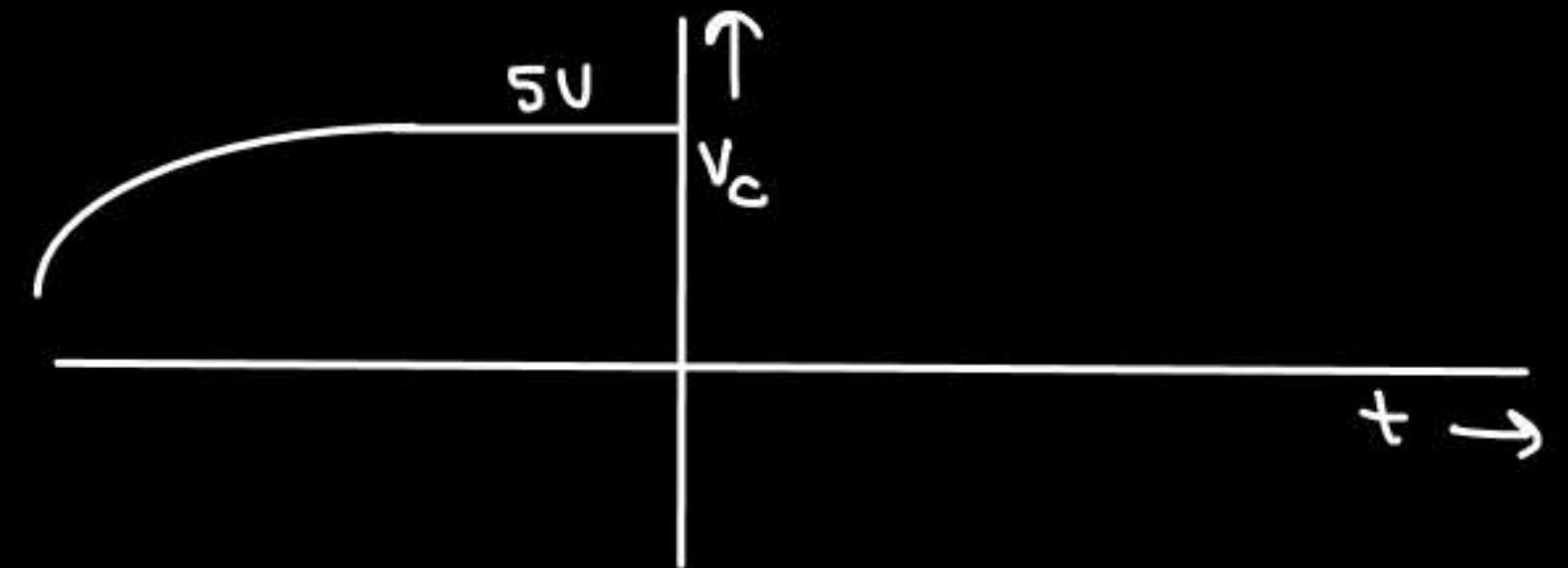$5V$ will charge the cap. \Rightarrow cap. will fully get charged to $5V$



now, ckt for $t > 0$

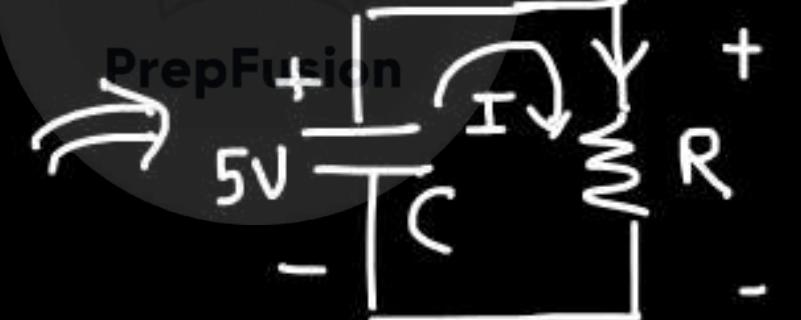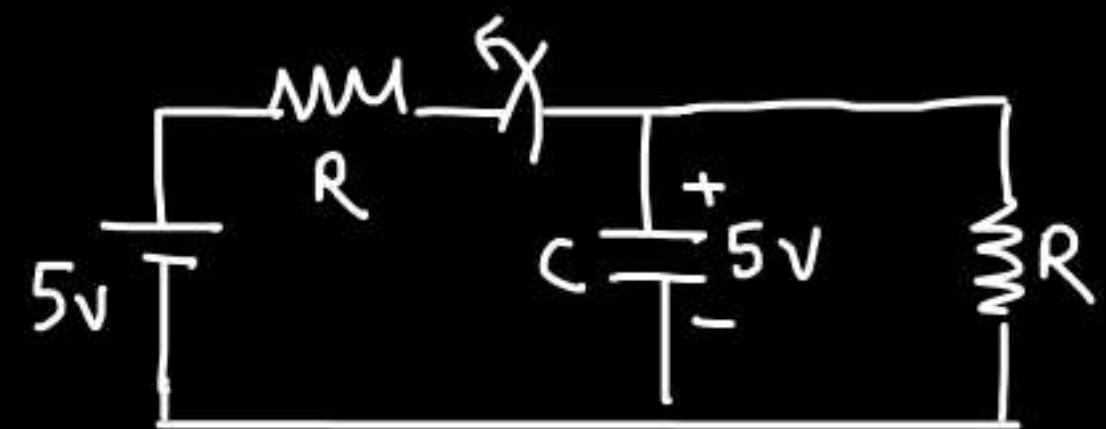

$$I(0^+) = \frac{5}{R} \rightarrow \text{finite}$$

↓
current flowing out of the cap.

$$\left. \begin{array}{l} V_c(0^-) = 5V \\ V_c(0^+) = 5V \end{array} \right\}$$

property of
cap. =



@ steady state:-

$$\overline{\overline{I}}$$

No current flow through the cap.

@ S.S. \rightarrow



$$I(\infty) = 0 \text{ Amp.}$$

$$V_C(\infty) = 0 \times R = 0V \quad \text{PrePfusion}$$




Conclusion: -

$$I(0^+) = \frac{5}{R} \quad I(\infty) = 0 \text{ Amp.}$$

$$I(t) = \frac{5}{R} e^{-t/\tau} \quad v(t) \quad \left\{ \begin{array}{l} \text{Because we are writing the eqn for} \\ t > 0 \end{array} \right\}$$

Time constant


(for $t > 0$) :-

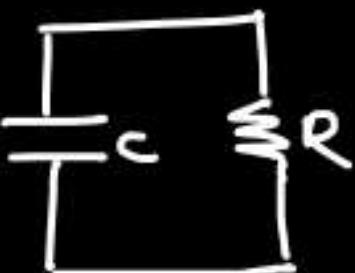

$$C_{eff} = C$$

$$R_{eq} = R$$

$$\tau = RC$$

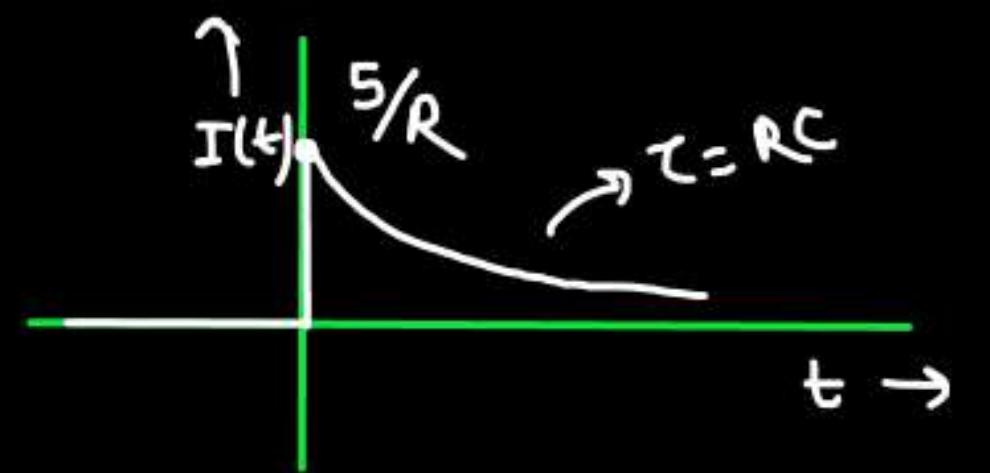


$v_c(t)$:-

$$v_c(0^+) = 5V$$

$$v_c(\infty) = 0V$$


$$v_c(t) = 5e^{-t/RC} v(t)$$

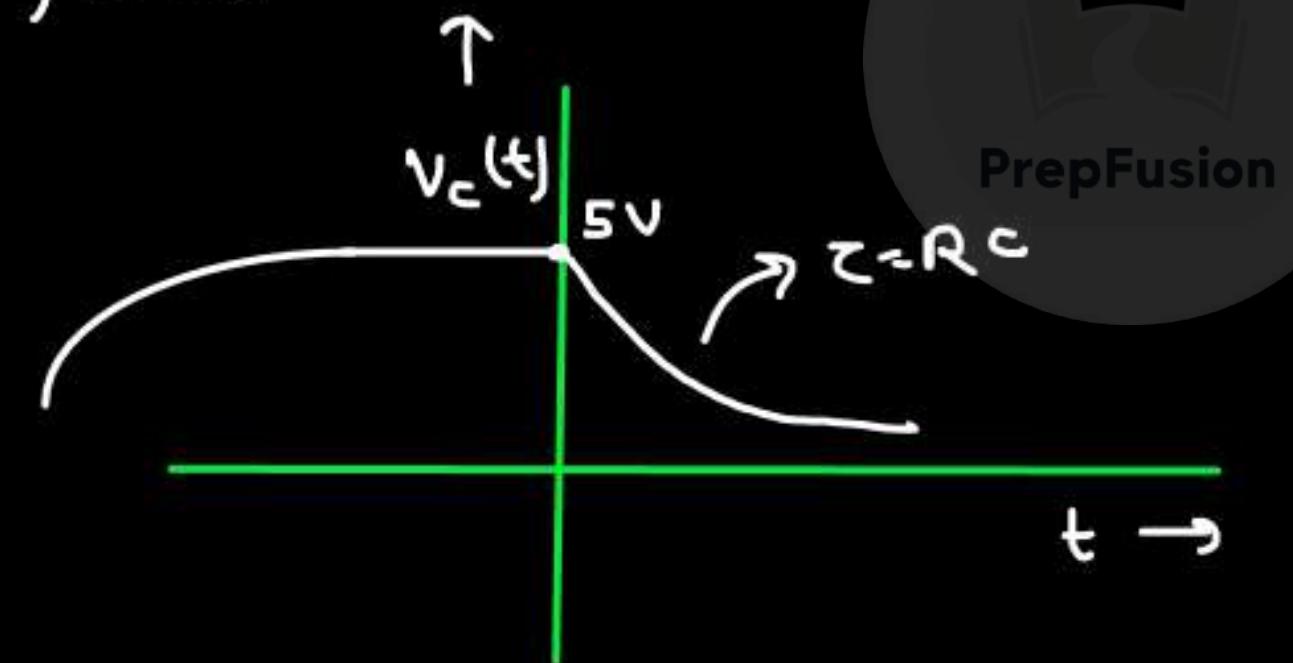

Understanding the ckt :-

from $- \infty < t < 0 \Rightarrow$ cap is being charged to 5V.


now for $t > 0$

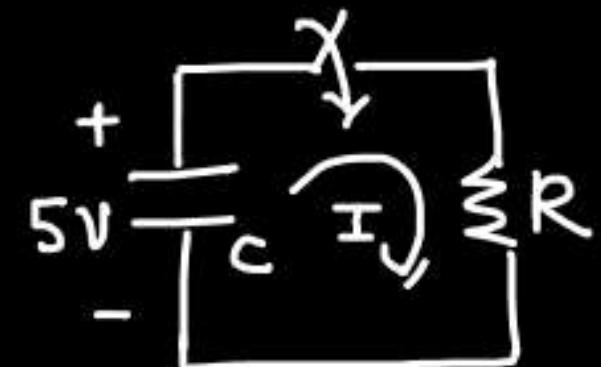

This same 5V comes across the resistor

$$\Rightarrow I = \frac{5}{R}$$

@ $t=0^+$

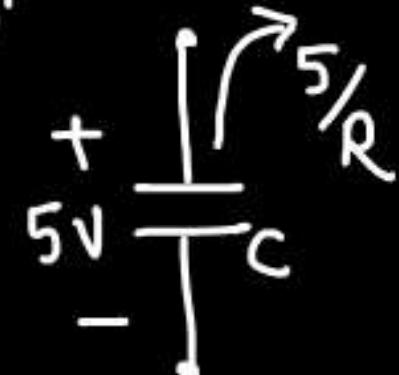


$\Rightarrow \frac{5}{R}$ current is flowing out of the cap.
cap. discharges

let's assume @ $t=t_1$, cap is discharged to 4.9V



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

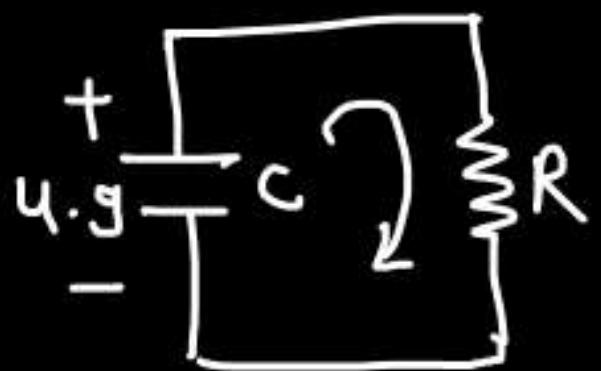AIR 27 (ECE)
AIR 45 (IN)(a) $t = t_1$ 

$$I(t_1) = \frac{4.9}{R} \Rightarrow C \frac{1}{T} - \frac{4.9V}{R}$$

now $\frac{4.9}{R}$ current flows out of the cap.
and discharges.

→ This shows that the cap will keep on discharging until the current flowing out of it becomes zero




↓

The cap will have zero voltage.

[YouTube -PrepFusion](#)
[\(CLICK HERE FOR FULL PLAYLIST\)](#)



Q.

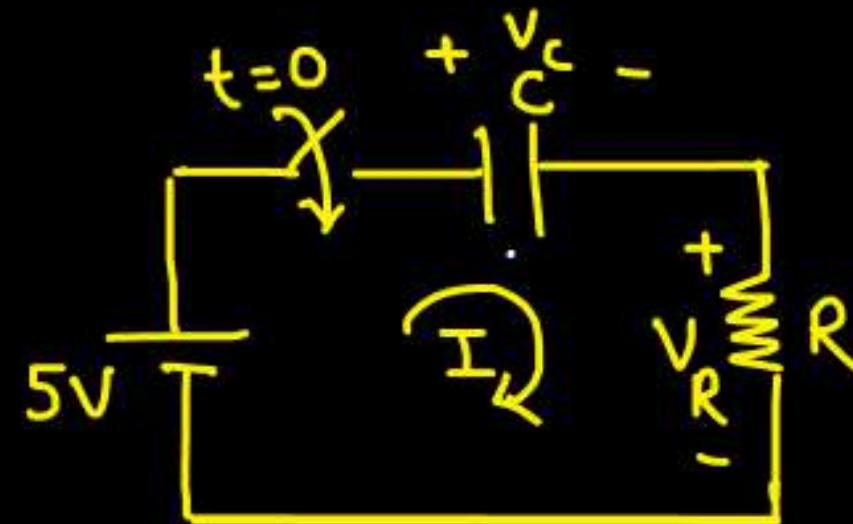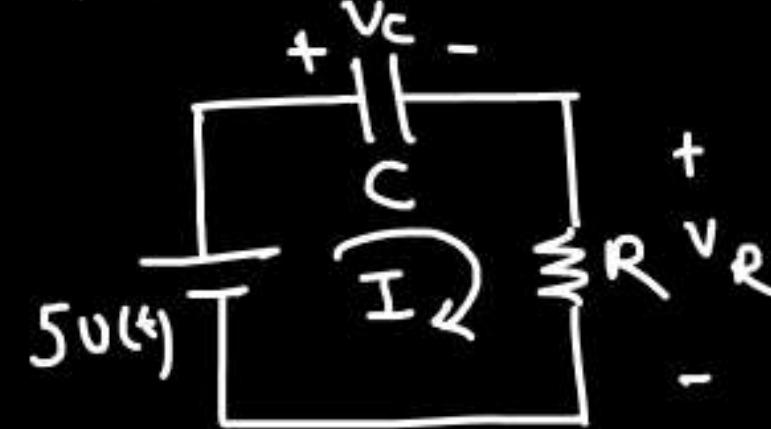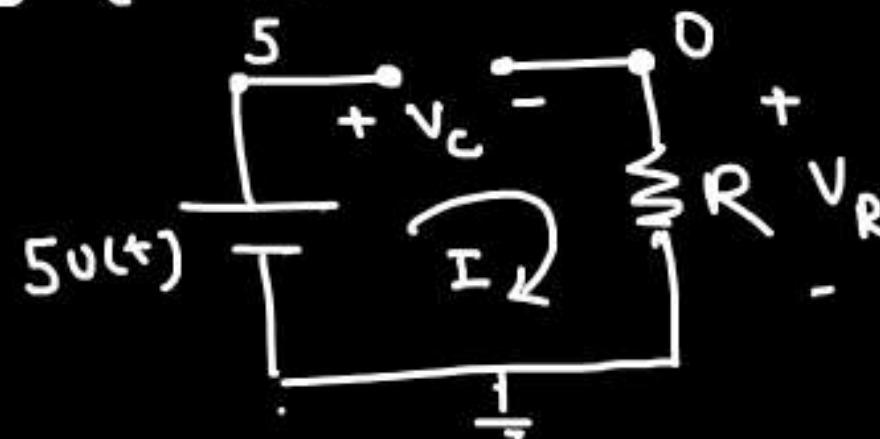 \rightarrow ckt for $t > 0$ @ $t = \infty \rightarrow C \gg 0 \cdot \infty$ Comment on V_C , V_R & I .@ $t = 0$ $\Rightarrow C \rightarrow S.C.$ 


Prepared by

$$\left. \begin{array}{l} V_C(0) = 0V \\ V_C(0^+) = 0V \\ I(0^+) = \frac{5}{R} \rightarrow \text{Finite} \\ V_R(0^+) = 5V \end{array} \right\}$$

$$I(\infty) = 0 \text{ A.P.}$$

$$V_R(\infty) = 0V$$

$$V_C(\infty) = 5V$$

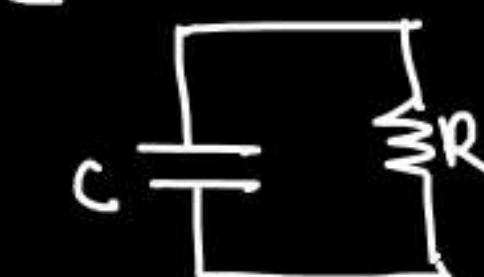 $\tau \rightarrow$ 

$$C_{eff} = C$$

$$R_{eq} = R$$

$$\tau = RC$$


- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$\underline{V_C} : \quad V_C(0^+) = 0V, \quad V_C(\infty) = 5V$$


$$V_C(t) = 5 + (0 - 5)e^{-t/\tau_{RC}}; \quad \tau = RC$$

$$= 5(1 - e^{-t/\tau}) V_L(t)$$

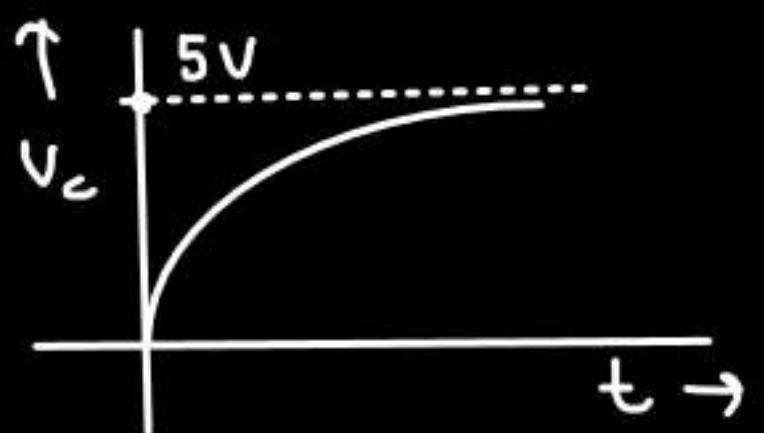


$$\underline{V_R} : \quad V_R(0^+) = 5V, \quad V_R(\infty) = 0V$$

$$V_R(t) = 5e^{-t/\tau_{RC}} V_L(t)$$

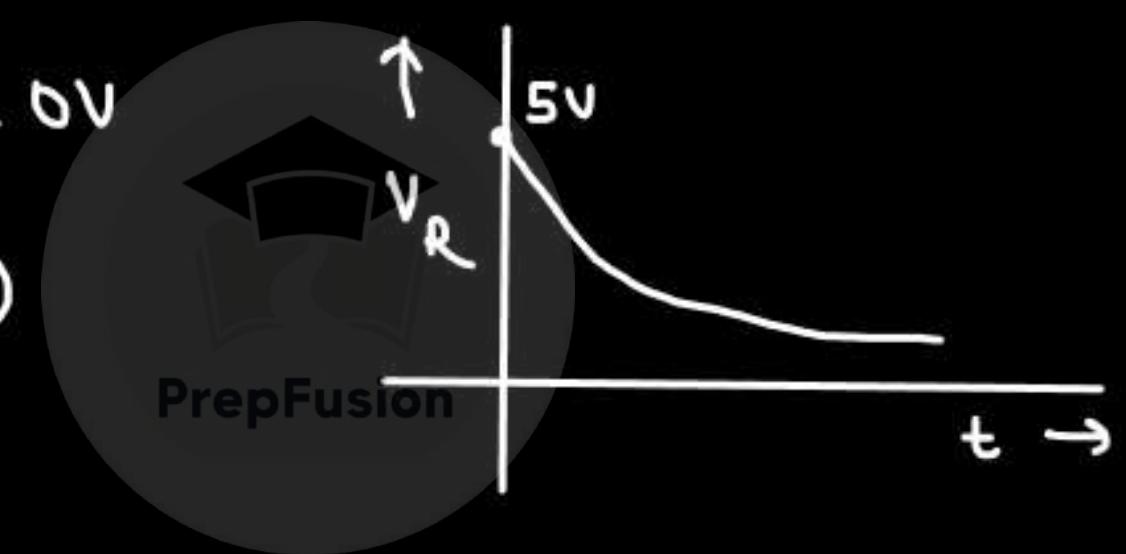


$$\underline{I} : \quad I(0^+) = \frac{5}{R}, \quad I(\infty) = 0 \text{ A.P.}$$
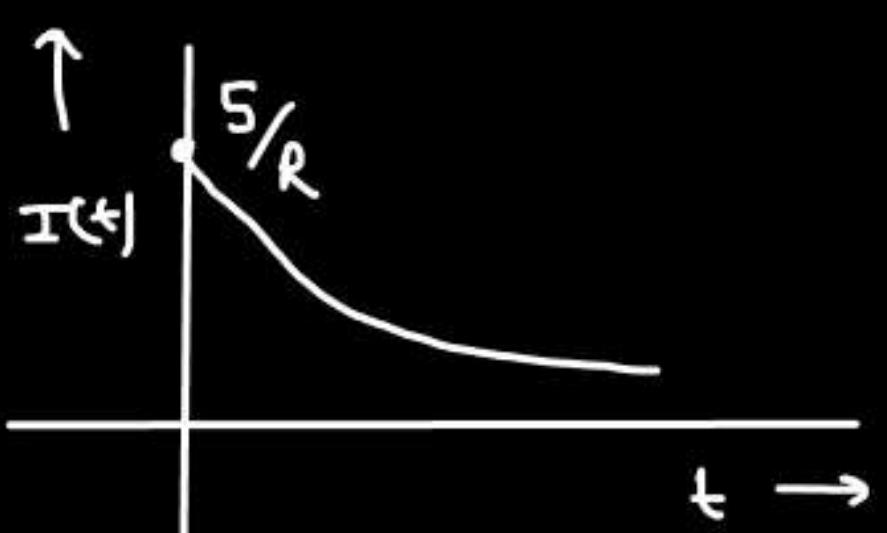
$$I(t) = \frac{5}{R} e^{-t/\tau_{RC}} V_L(t)$$






Q.

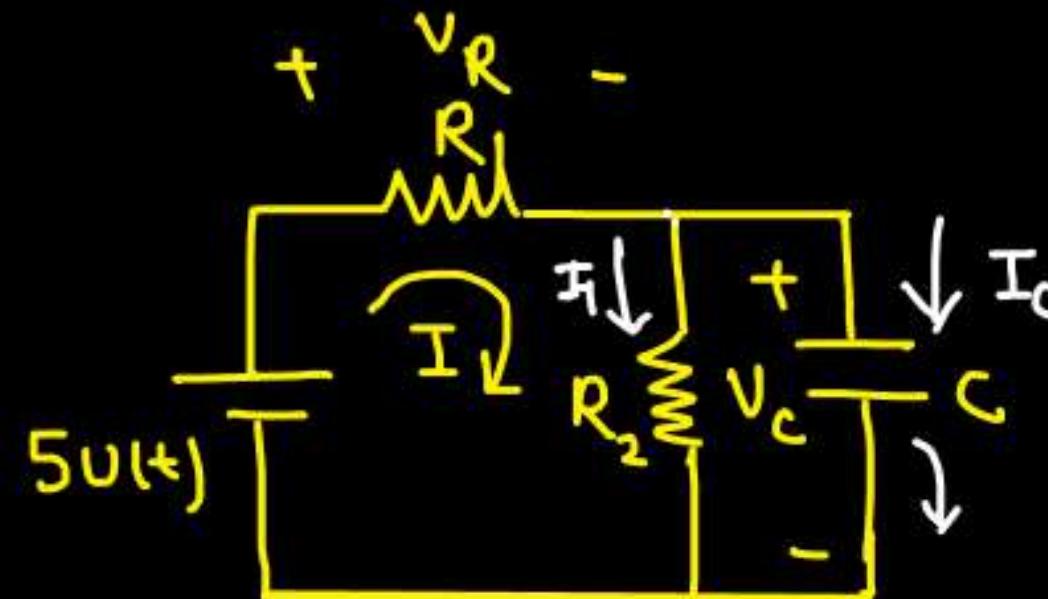
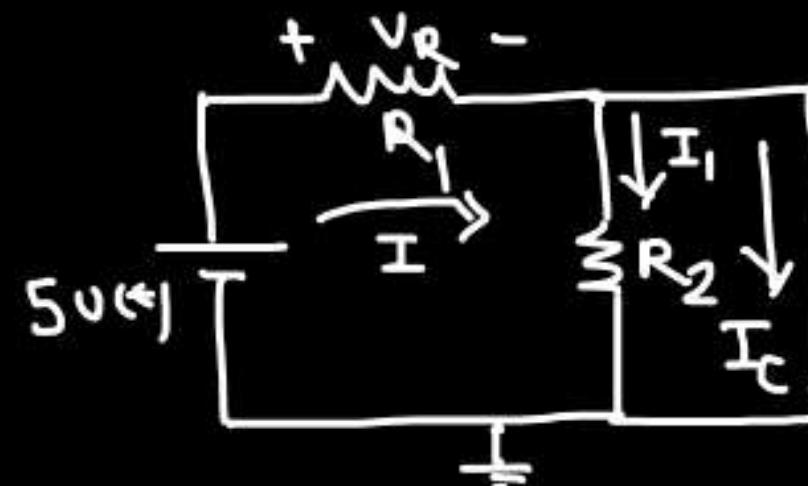
$$\rightarrow t=0 \rightarrow C \Rightarrow S.C.$$



$$R_1 = R, R_2 = 2R$$

Comment on V_C, V_R & I .

$$I_1(0) = 0 \text{ Amp.}$$


$$I(0) = \frac{5}{R_1} \text{ A}$$

$$I_C(0^+) = I(0^+) = \frac{5}{R_1} \rightarrow \text{Finite}$$

$$V_C(0) = 0V = V_C(0^+)$$

$$V_R(0^+) = 5V$$
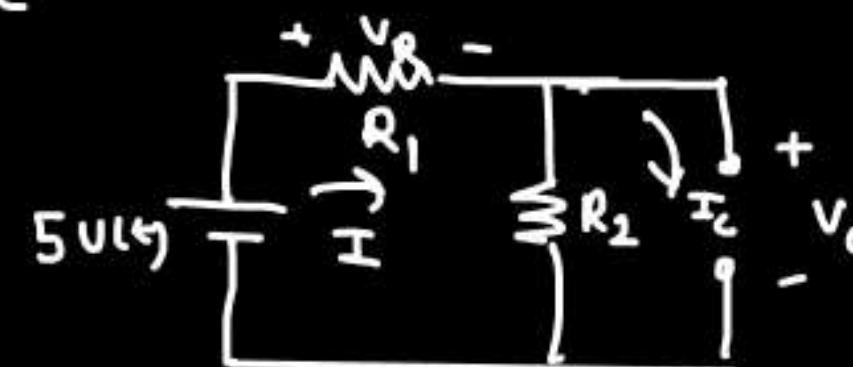
$$t=\infty \rightarrow C \Rightarrow D.C.$$



$$I(\infty) = \frac{5}{R_1 + R_2}$$

$$I_1(\infty) = \frac{5}{R_1 + R_2}$$

$$I_C(\infty) = 0 \text{ Amp.} \rightarrow \text{Steady state}$$


$$V_C(\infty) = V_{R_2}(\infty) = \frac{5R_2}{R_1 + R_2}$$

$$V_R(\infty) = \frac{5R_1}{R_1 + R_2}$$



 $\underline{\underline{V_C}} : -$

$$V_C(0^+) = 0V, \quad V_C(\infty) = \frac{5R_2}{R_1 + R_2} = \frac{5(2R)}{3R} = \frac{10}{3}V$$
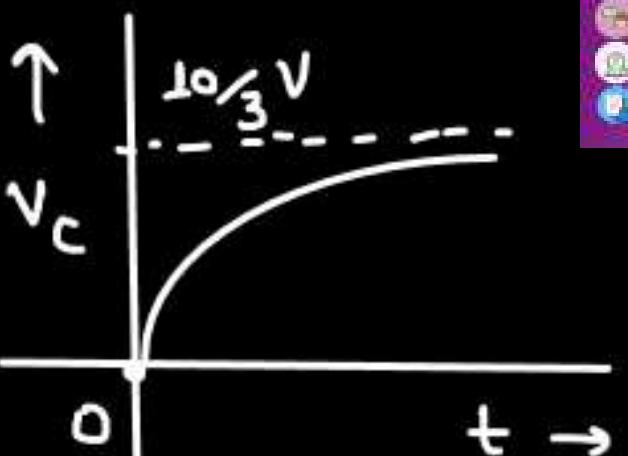
$$V_C(t) = \frac{10}{3} \left(1 - e^{-\frac{t}{\tau}} \right)$$



$\underline{\underline{\tau = ?}}$

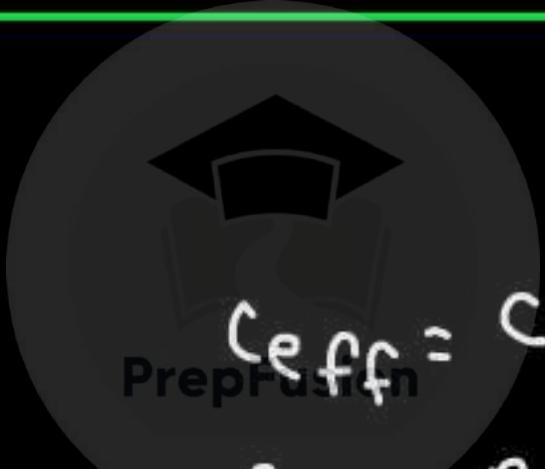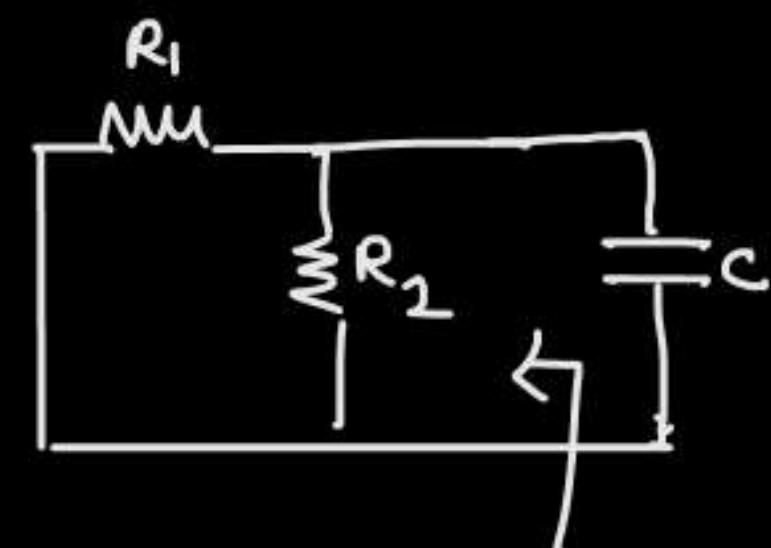

$$C_{eff} = C$$


$$R_{eq} = R_1 \parallel R_2 = R \parallel 2R = \frac{2R}{3}$$

$$\tau = \frac{2RC}{3}$$

V_R :-

$$V_R(0) = 5V \quad , \quad V_R(\infty) = \frac{5R_1}{R_1 + R_2} = \frac{5R}{3R} = \frac{5}{3}V$$

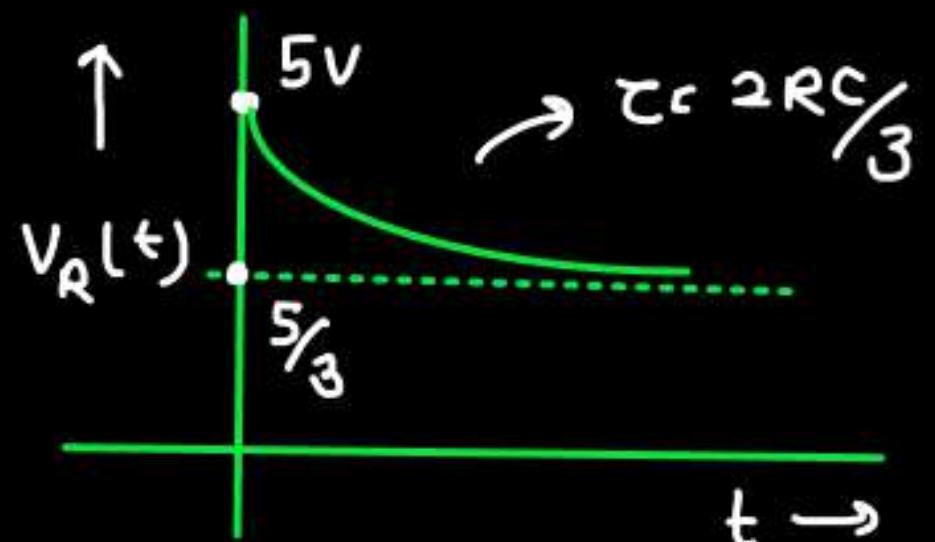
$$\begin{aligned} V_R(t) &= \frac{5}{3} + \left(5 - \frac{5}{3} \right) e^{-t/\tau} \\ &= \frac{5}{3} + \frac{10}{3} e^{-t/\tau} \end{aligned}$$



I :-

$$I_{R_1}(0) = \frac{5}{R_1} = \frac{5}{R}; \quad I_{R_1}(\infty) = \frac{5}{R_1 + R_2} = \frac{5}{3R}$$
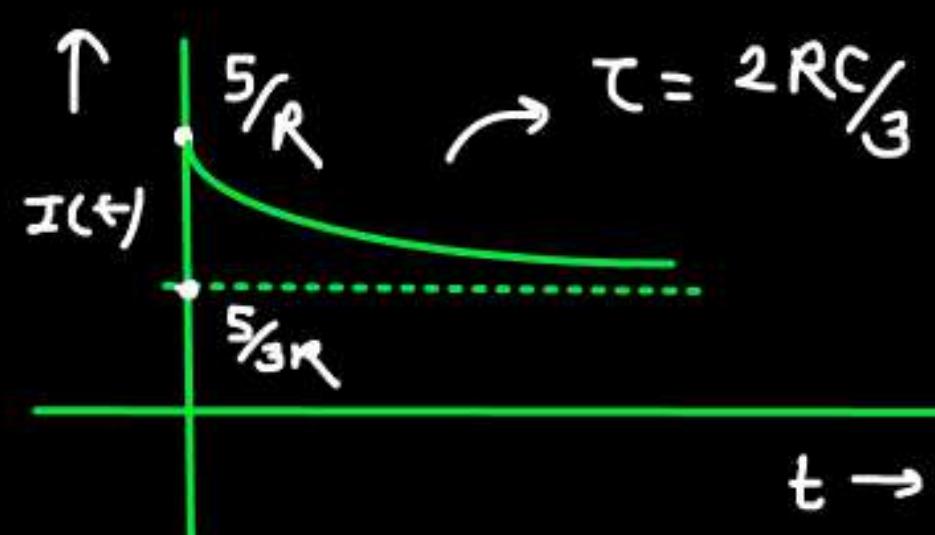
$$\begin{aligned} I_{R_1}(t) &= \frac{5}{3R} + \left(\frac{5}{R} - \frac{5}{3R} \right) e^{-t/\tau} \\ &= \frac{5}{3R} + \frac{10}{3R} e^{-t/\tau} \end{aligned}$$




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

 I_C :-

$$I_C(0) = \frac{5}{R_1} = \frac{5}{R}$$

$$I_C(\infty) = 0 \text{ A.P}$$


$$I_C(t) = \frac{5}{R} e^{-t/\tau}$$

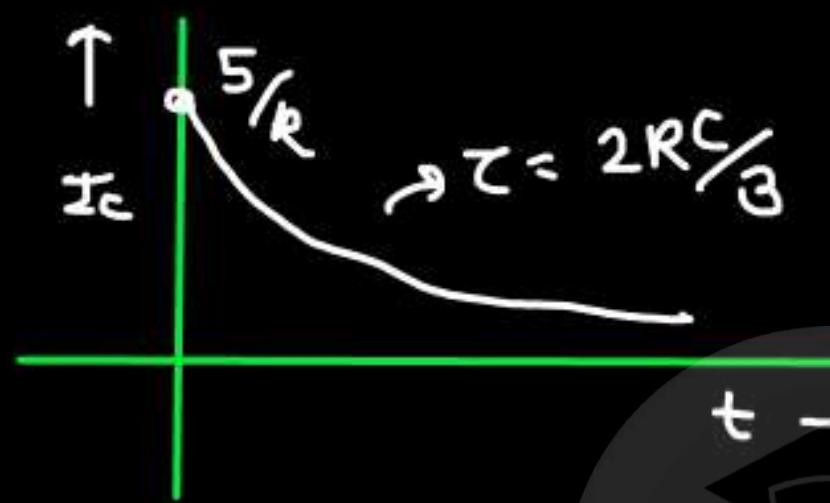 I_L :-

$$I_L(0) = 0 \text{ A.P.}$$

$$I_L(\infty) = \frac{5}{R_1 + R_2} = \frac{5}{3R}$$
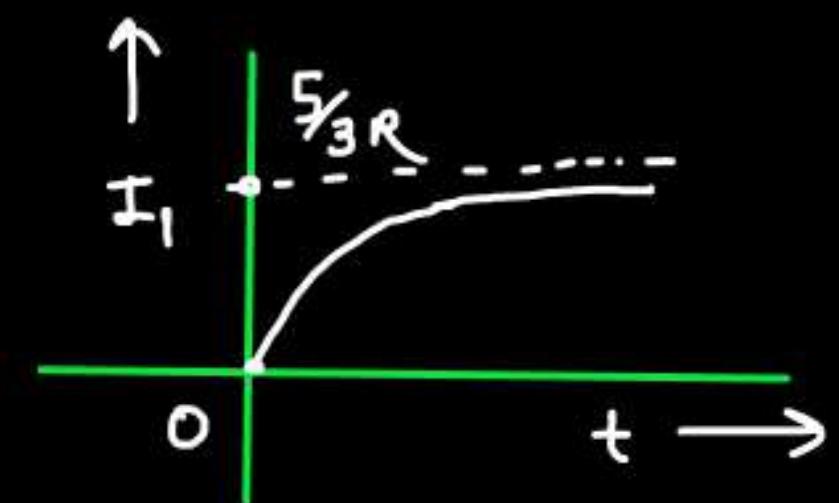
$$I_L(t) = \frac{5}{3R} (1 - e^{-t/\tau})$$





- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

Concept of ∞ current through capacitor:-

∞ current = Impulsive



$$\delta(t) = \begin{cases} \infty, & t=0 \\ 0, & t \neq 0 \end{cases}$$

Capacitor with impulse/ Infinite Current Input:-

$$I(t) = \underbrace{I_0}_{\text{charge (dx sec)}} \delta(t)$$

charge ($dx \text{ sec}$)

$$I(t) \propto I_0 \delta(t)$$

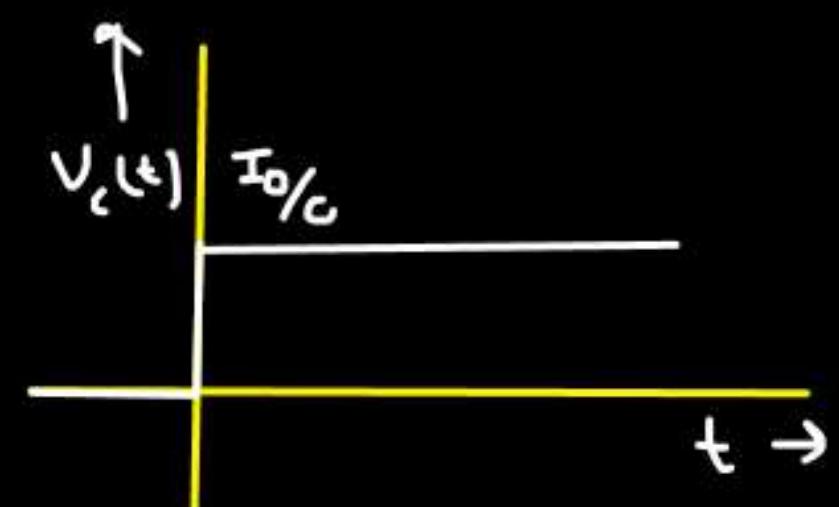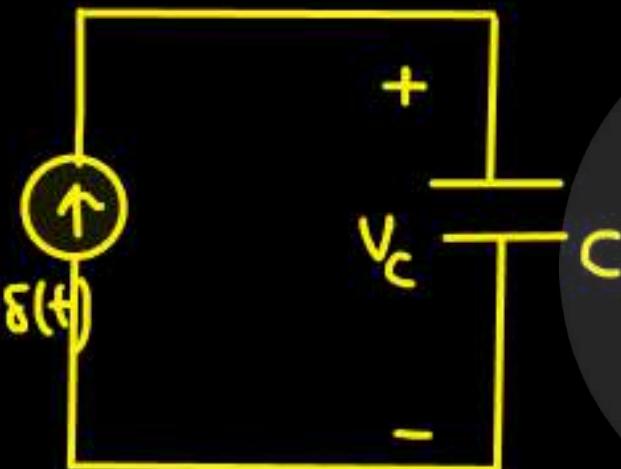

$$V_c(t) = \frac{1}{C} \int_{-\infty}^t I(t) dt$$

$$V_c(t) = \frac{1}{C} \int_{-\infty}^t I_0 \delta(t) dt$$

$$= \frac{I_0}{C} \int_{-\infty}^t \delta(t) \cdot v(t) dt$$

$$V_c(t) = \frac{I_0}{C} v(t)$$

YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)



$$I(t) = I_0 \delta(t)$$

↳ You are giving I_0 amount of charge
in no time -

M-II

$$\left\{ \begin{array}{l} \text{charge } (Q) = I_0 \\ \text{capacitor } (C) = C \end{array} \right.$$

$$\text{Voltage } (V) = Q/C = I_0/C$$


$V_C(0^-) = 0V$ } $V_C(0^+) = I_0/C$ } The cap. doesn't follow its property of
not changing the voltage immediately in
case of impulse/infinite current.

Expt-

⇒ Whenever there is an infinite current flowing through the cap.,
it will change its voltage immediately.





Q. Draw the graph of V_{C_1} & V_{C_2}

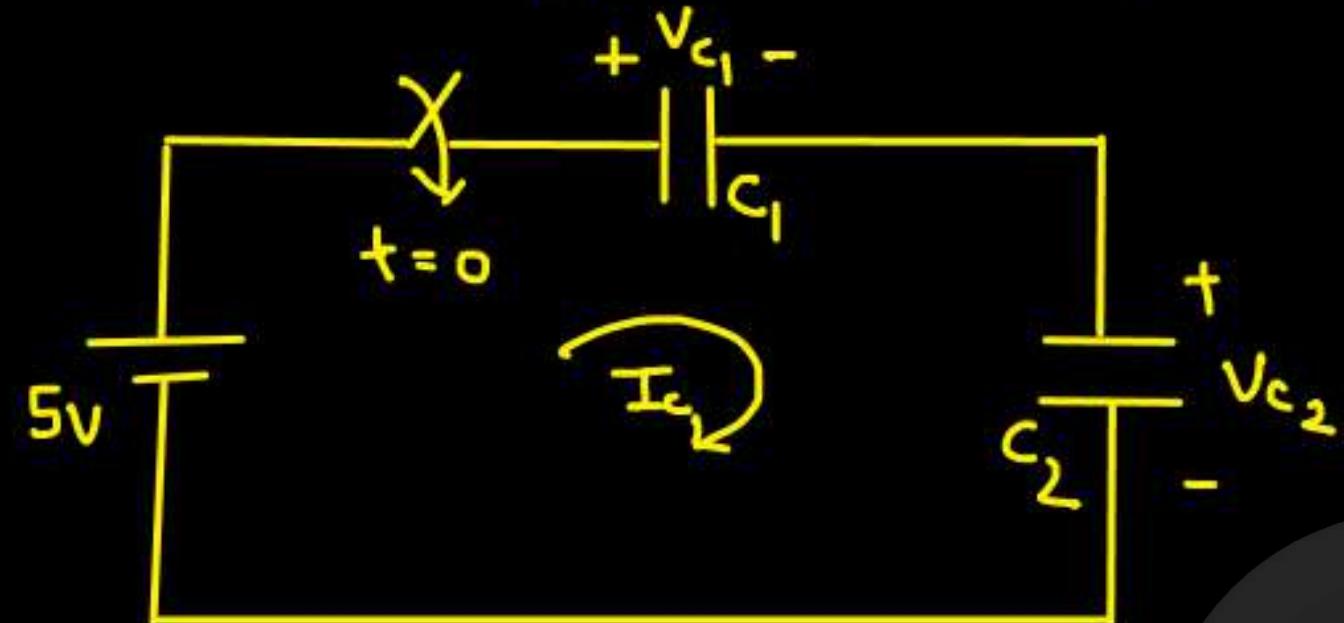

$V_{C_1}, V_{C_2}, I_c = ?$


ckt initially -- (@ $t=0$)

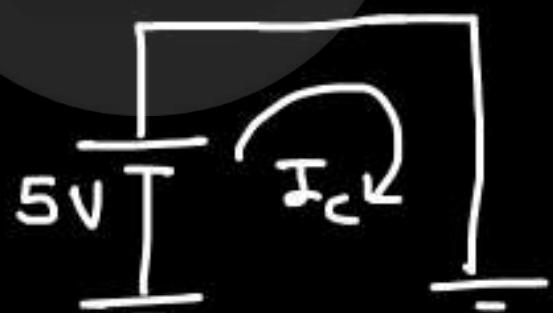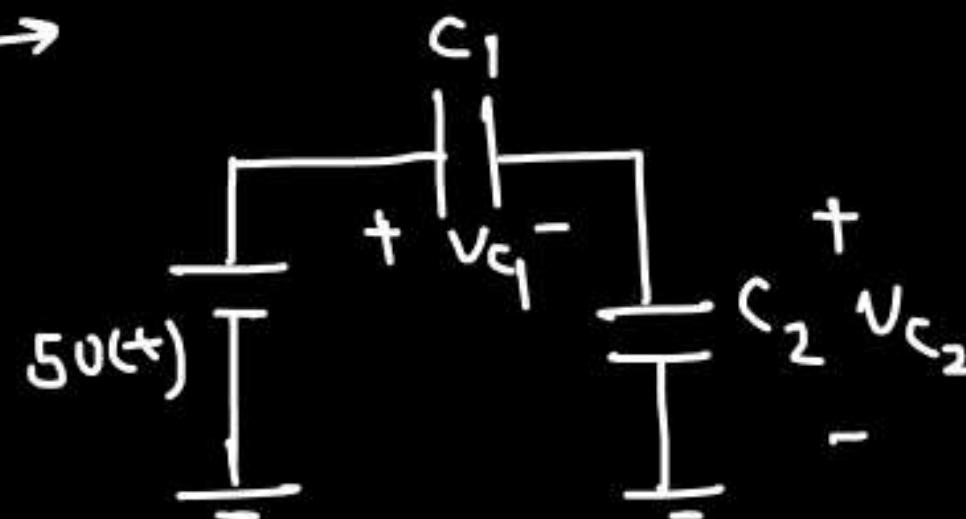

$$I_c = \frac{5}{0} = \infty \text{ current}$$

↓
cap. will change its
voltage immediately.

M-I

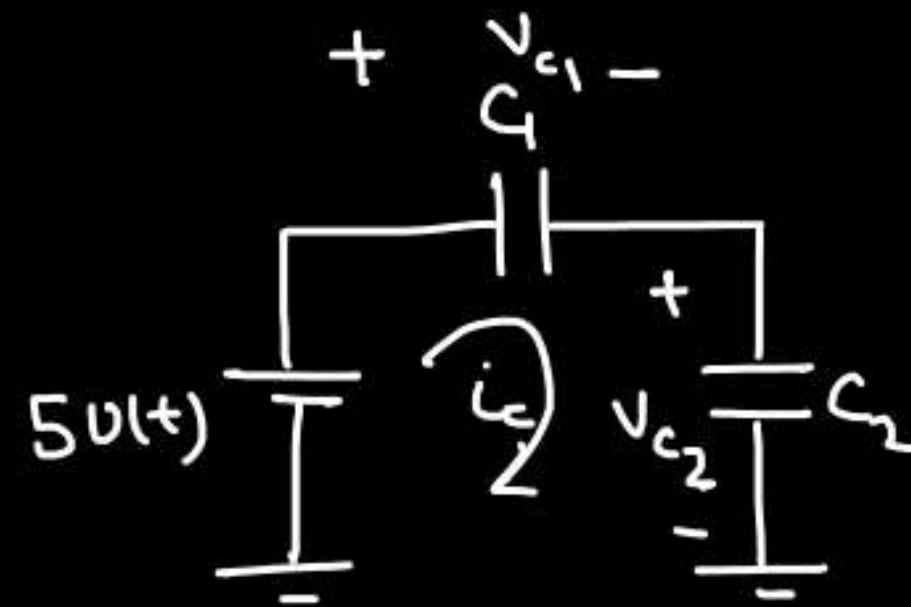

$$V_{C_2}^{(t)} = \frac{5C_1}{C_1 + C_2} v(t)$$

$$V_{C_1}^{(t)} = \frac{5C_2}{C_1 + C_2} v(t)$$







PrepFusion

$$i_C = C_1 \frac{dV_{C_1}}{dt} = C_2 \frac{dV_{C_2}}{dt}$$

$$= C_1 \times \frac{5C_2}{C_1 + C_2} \delta(t)$$
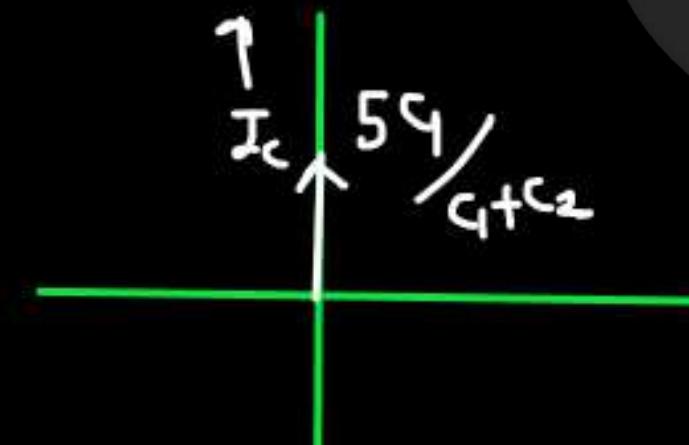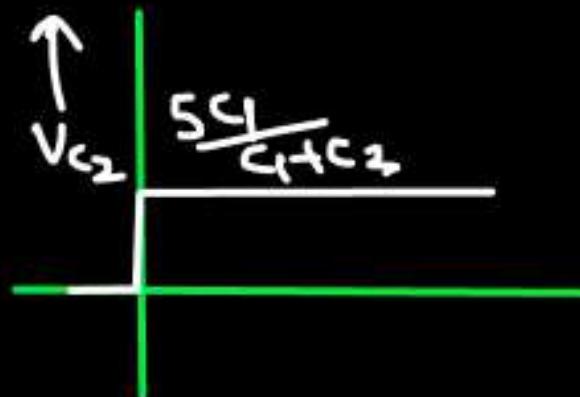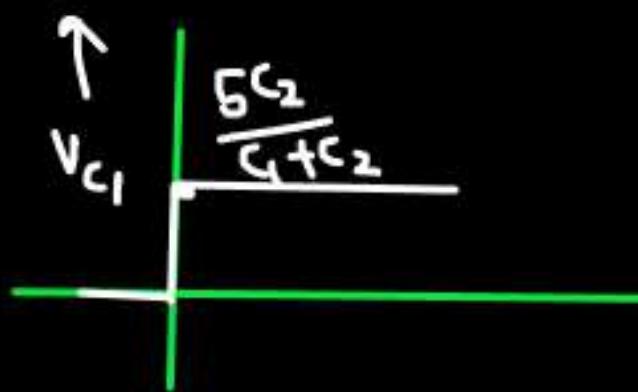
$$i_C = \frac{5C_1 C_2}{C_1 + C_2} \delta(t)$$



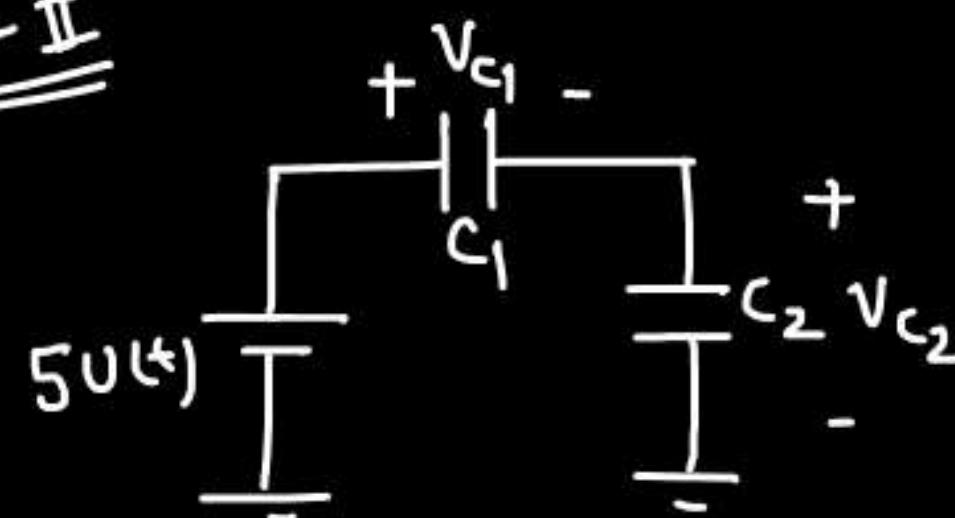M-II C_1 and C_2 is series

↓

current same \Rightarrow charge same

$$Q_1 = Q_2$$

$$C_1 V_{C_1} = C_2 V_{C_2} \quad \text{--- (1)}$$

$$5U(t) = V_{C_1} + V_{C_2}$$


$$\text{P}5U(t) = \frac{C_2 V_{C_2}}{C_1} + V_{C_2}$$

$$V_{C_2} = \frac{5C_1}{C_1 + C_2} U(t)$$

$$V_{C_1} = \frac{5C_2}{C_1 + C_2} U(t)$$




⇒ Important Concepts (for step f^n):-

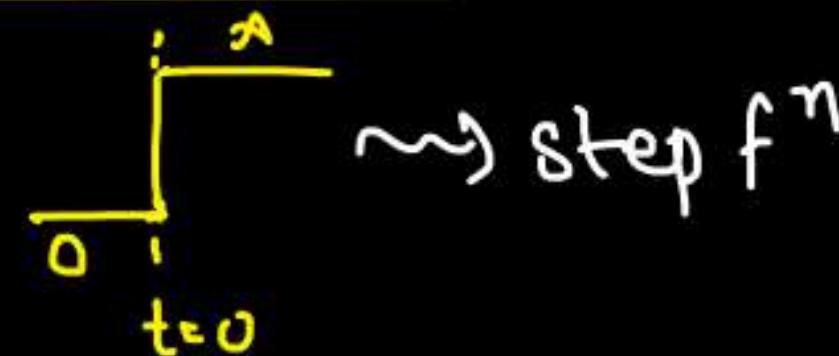

$$U(t) = \begin{cases} A, & t > 0 \\ 0, & t < 0 \end{cases}$$

→ impedance provided by the capacitance
 $\text{@ } t=0 \Rightarrow \omega=\infty \Rightarrow Z_C = \frac{1}{j\omega C} \Rightarrow Z_C = \frac{1}{j\infty C} \approx 0 \Rightarrow \text{very low}$

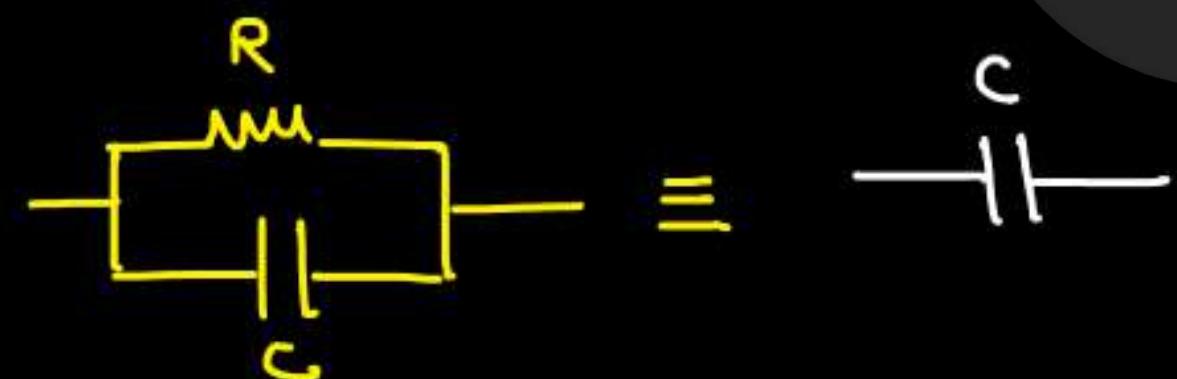N.B. - For step f^n , @ $t=0$ ($\omega=\infty$), the cap. very low impedance.







- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

@ $t = \infty$ (Steady state) $\Rightarrow \underline{\omega = 0} \Rightarrow Z_c = \frac{1}{j\omega C} \approx \infty \Rightarrow$ very high impedance
 ↳ $\omega = 0$ (steady state)

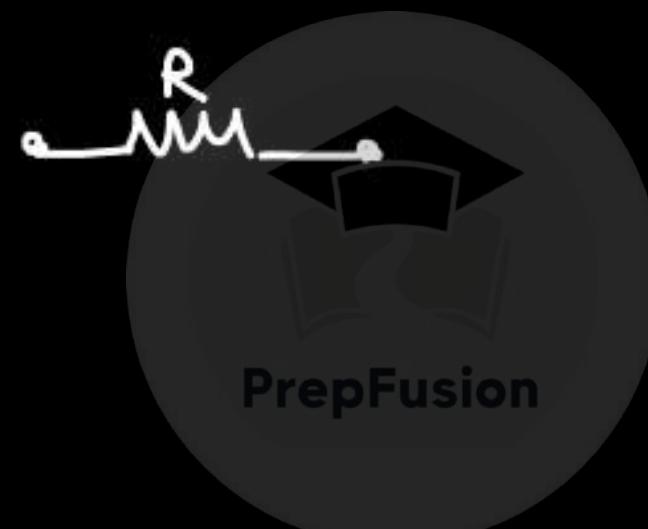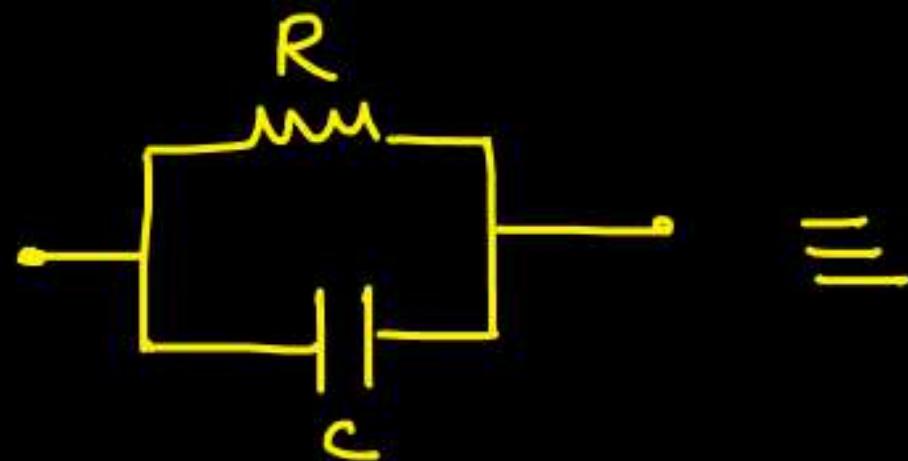\Rightarrow N.B. - Cap. provides very High impedance @ steady state



YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)

Basic Concept of Laplace Transform:-

(Only for Network Analysis)

Time domain \rightarrow Frequency domain

Laplace Transform of $x(t)$ $\xleftarrow{ }$ $X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$ $s \in j\omega$

$$L[x(t)] = X(s)$$

* $L[u(t)] = ?$

$$x(t) = u(t)$$

$$L[x(t)] = X(s)$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt$$

$$X(s) = \int_{-\infty}^{\infty} u(t) e^{-st} dt$$


$$\begin{aligned} X(s) &= \int_0^{\infty} 1 e^{-st} dt \\ &= -\frac{1}{s} [e^{-st}]_0^{\infty} \end{aligned}$$

$$= -\frac{1}{s} [e^{-\infty} - e^0]$$

$$X(s) = \frac{1}{s}$$

$$h[u(t)] = \frac{1}{s}$$

$$h[Au(t)] = \frac{A}{s}$$

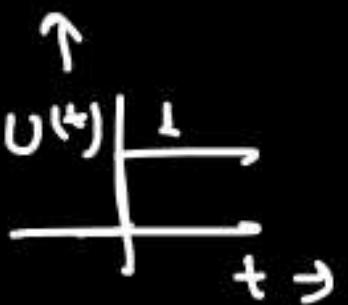



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

Some Laplace Transforms important to remember:-

$$\textcircled{1} \quad L[Au(t)] = A/s$$

$$\delta(t) \rightarrow u(t) \rightarrow r(t)$$

$$L \rightarrow 1/s \rightarrow L/s^2$$

$$\textcircled{2} \quad L[Ar(t)] = A/s^2$$

$$\textcircled{3} \quad L[A\delta(t)] = A$$

$$\textcircled{4}^* \quad L[e^{-at} u(t)] = \frac{1}{s+a}$$


$$\textcircled{5}^* \quad L[\cos at u(t)] = \frac{s}{s^2 + a^2}$$

$$\textcircled{6}^* \quad L[\sin at u(t)] = \frac{a}{s^2 + a^2}$$

$$\textcircled{7} \quad L[x_1(t) \pm x_2(t)] = X_1(s) \pm X_2(s)$$
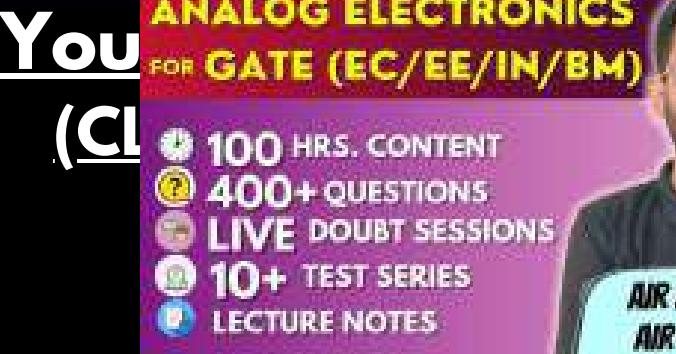
$$\textcircled{8} \quad L[x(t - t_0)] = e^{-st_0} X(s)$$





You
(CL)

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

$$\textcircled{9} \quad L \left[\int_0^t x(t) \cdot dt \right] = \frac{x(s)}{s}$$

$$\int_{-\infty}^t \rightarrow \frac{1}{s}$$

$$\textcircled{10} \quad L \left[\frac{dx(t)}{dt} \right] = s x(s) - x(0)$$

$$\frac{d}{dt} \rightarrow s$$

$$\textcircled{11} \quad L \left[\frac{d^2x(t)}{dt^2} \right] = s^2 x(s) - s x(0) - x'(0)$$

$$\left\{ \begin{array}{l} x(0) = x(t=0) \neq X(s=0) \\ x'(0) = \left[\frac{d}{dt} x(t) \right]_{t=0} \end{array} \right\}$$

$$\textcircled{12} \quad L \left[\frac{d^n x(t)}{dt^n} \right] = s^n x(s) - s^{n-1} x(0) - s^{n-2} x'(0) - \dots - s^0 x^{n-1}(0)$$

$$\textcircled{13} \quad L \left[e^{-at} x(t) \right] = X(s+a)$$

$$\mathcal{E}_j \rightarrow L[\tau(t)] = \frac{1}{s^2}$$

$$L[u(t)] = ?$$

$$\frac{d}{dt} \tau(t) = u(t)$$

$$\frac{s}{s^2} = L[u(t)]$$

$$\Rightarrow L[u(t)] = \frac{1}{s}$$





$$\text{Eg. } \rightarrow L[u(t)] = \frac{1}{s}$$

$$L[e^{-at} u(t)] = \frac{1}{s+a}$$

$$\textcircled{14} \quad L[t \cdot x(t)] = -\frac{d}{ds} \times (s)$$

$$\text{Eg. } \rightarrow L[e^{-at} u(t)] = \frac{1}{s+a}$$

$$L[t \cdot e^{-at} u(t)] = -\frac{d}{ds} \left[\frac{1}{s+a} \right]$$

$$L[t \cdot e^{-at} u(t)] = \frac{1}{(s+a)^2}$$

$$\text{Eg. } \rightarrow L[u(t)] = \frac{1}{s}$$

$$L[t u(t)] = ?$$

$$\text{or} \\ L[\tau(t)] = ?$$

$$L[t u(t)] = -\frac{d}{ds} \left[\frac{1}{s} \right]$$


$$L[\tau(t)] = \frac{1}{s^2}$$



YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)

Laplace Transforms of Circuit elements:-

① Resistor :-

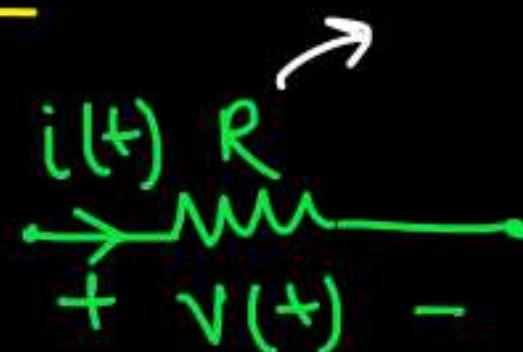


$$Z_R = R \neq f(t)$$

$$V(t) = i(t) \times R$$

$$\frac{V(t)}{i(t)} = R \Rightarrow Z(t) = R$$

$$Z(s) = R$$

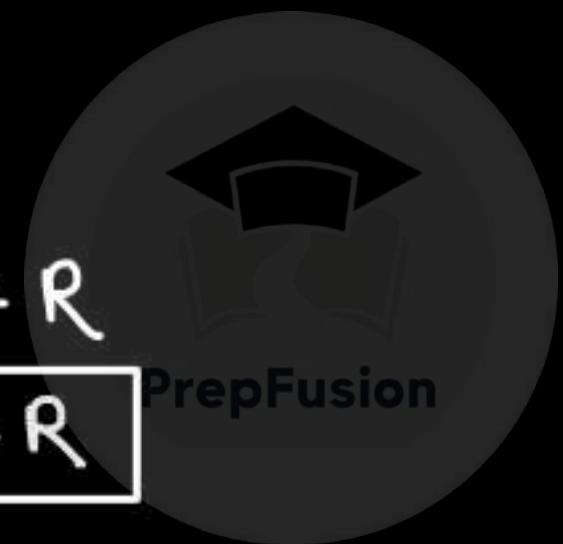




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

② Capacitor:-

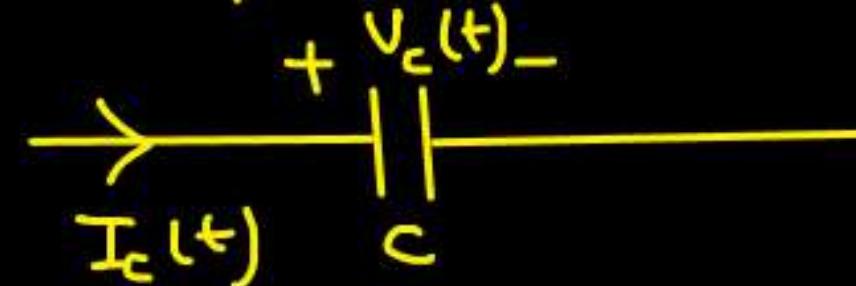* Assume Capacitor is having no initial Voltage.




$$V_c(0^-) = 0 \text{ V}$$

$$I_c(t) = C \frac{dV_c(t)}{dt}$$

$$I_c(s) = C [sV_c(s) - V_c(0^+)]$$

$$I_c(s) = CSV_c(s)$$

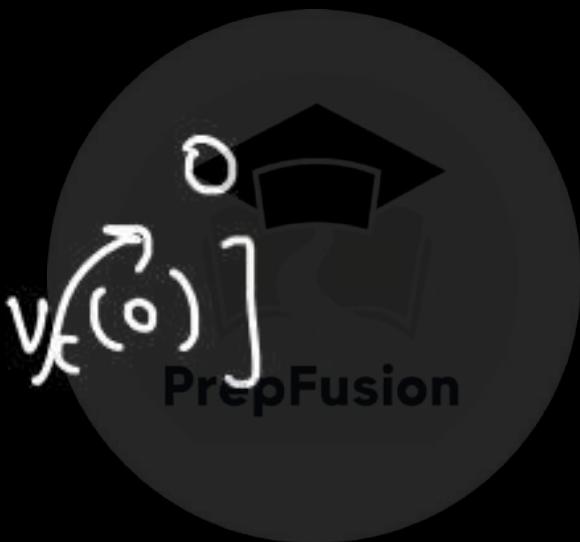
$$\frac{V_c(s)}{I_c(s)} = Z(s) = \frac{1}{CS}$$



Impedance provided by the cap.
in laplace Transform.



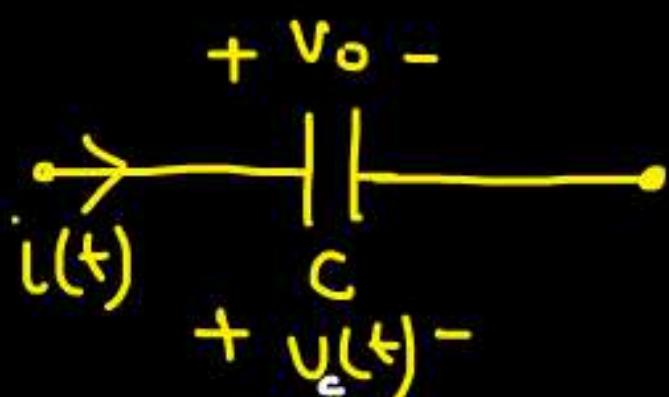* Capacitor is having some initial voltage :-



$$\Rightarrow V_c(0) = V_0$$

$$I_c(s) = C [sV_c(s) - V_c(0)]$$

$$I_c(s) = C [sV_c(s) - V_0]$$

$$I_c(s) = CSV_c(s) - CV_0$$

$$CSV_c(s) = I_c(s) + CV_0$$

$$V_c(s) = \underbrace{\frac{I_c(s)}{CS}} + \frac{V_0}{s}$$



$$\frac{V_c(s)}{I_c(s)} = 1/CS$$





- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

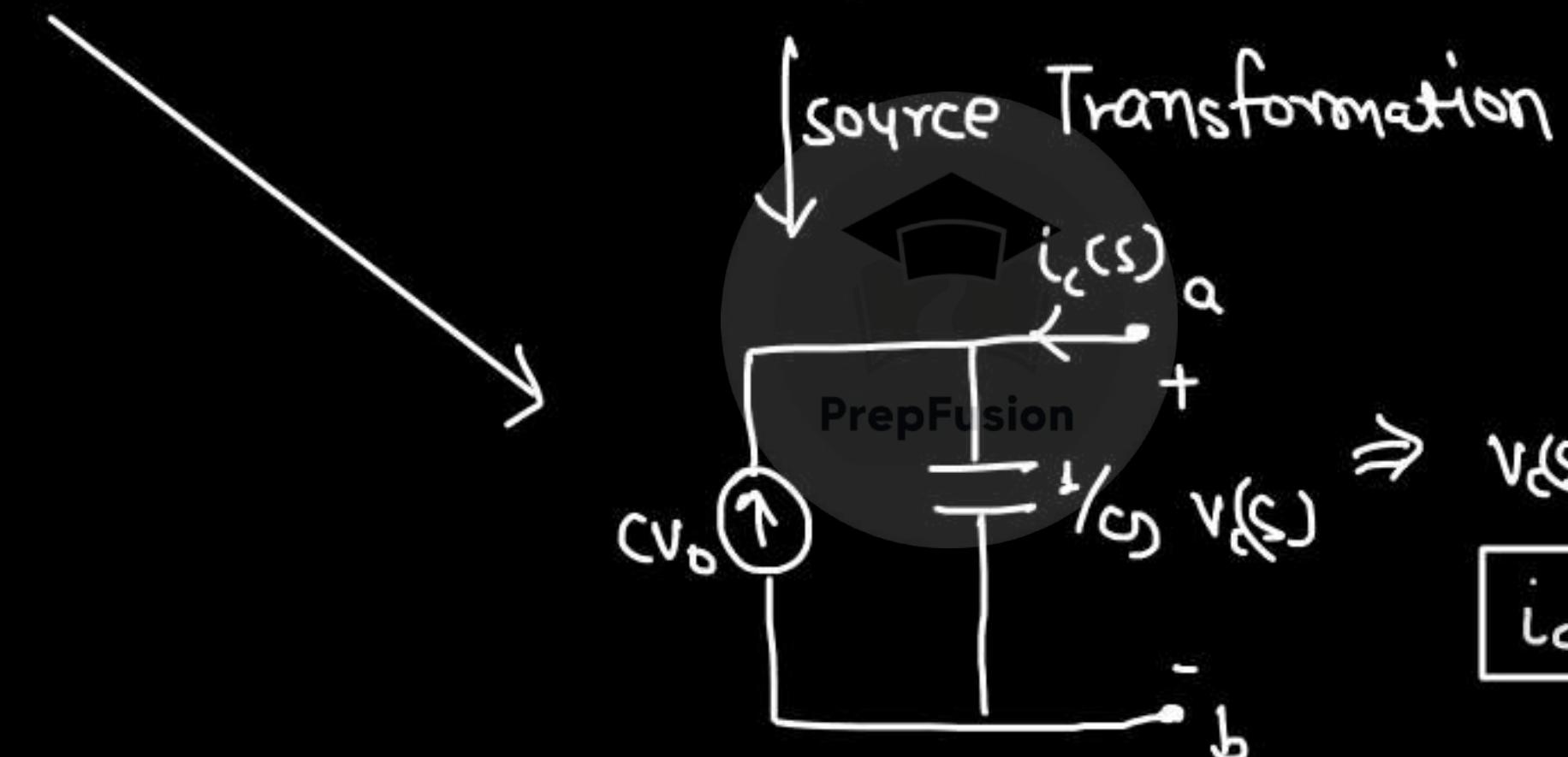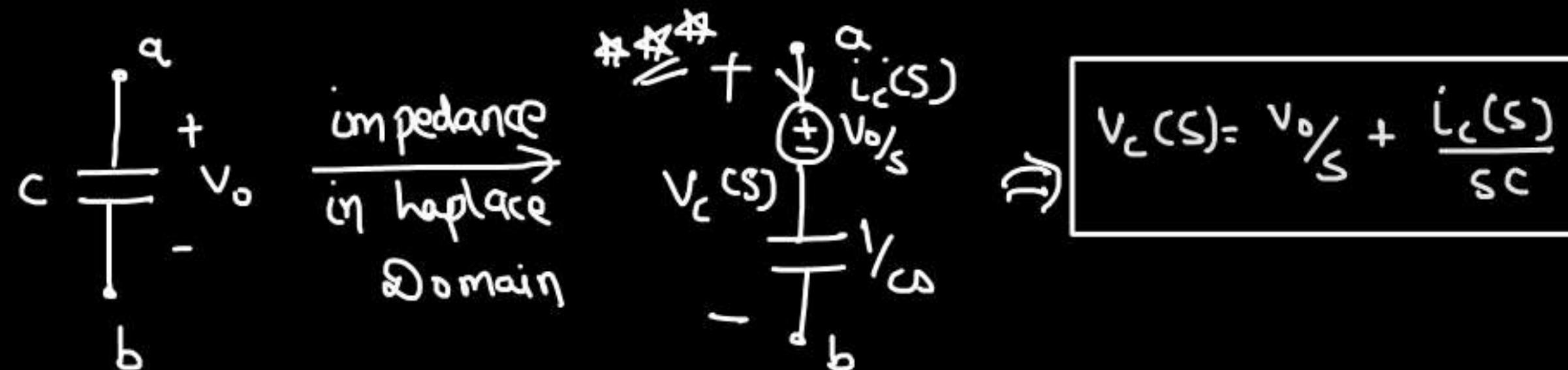


YouTube -PrepFusion
(CLICK HERE FOR FULL PLAYLIST)



③ Inductor :-

* Inductor is having no initial current.

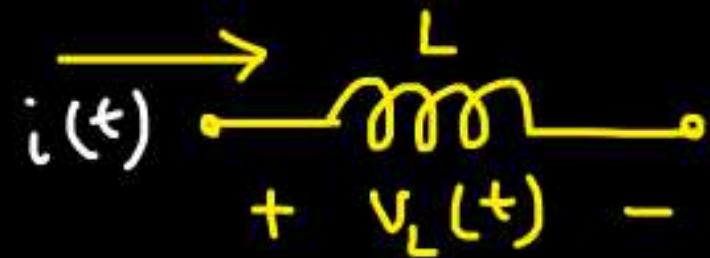


$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$v_L(s) = L [s I_L(s) - i_L(0)]$$

$$v_L(s) = LS I_L(s)$$


$$\frac{v_L(s)}{I_L(s)} = Z(s) = LS$$

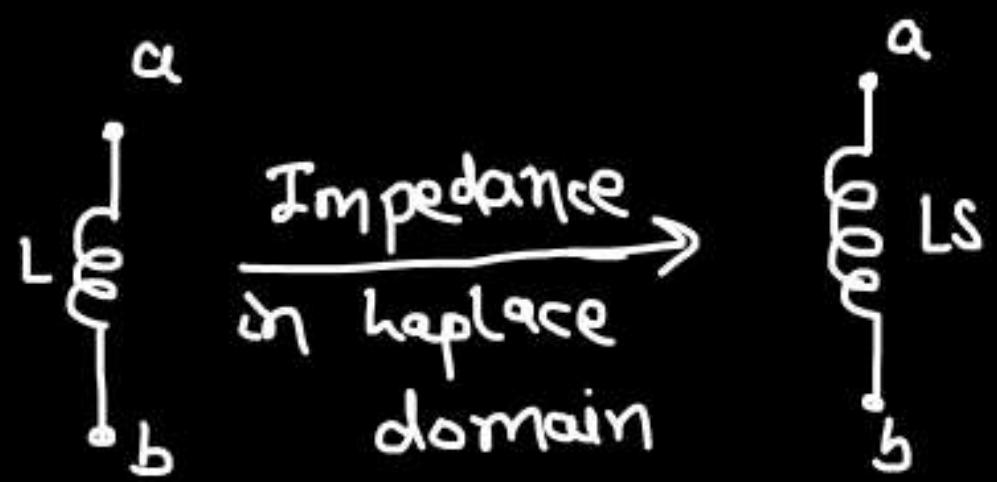→ Impedance provided by the inductor in Laplace domain.





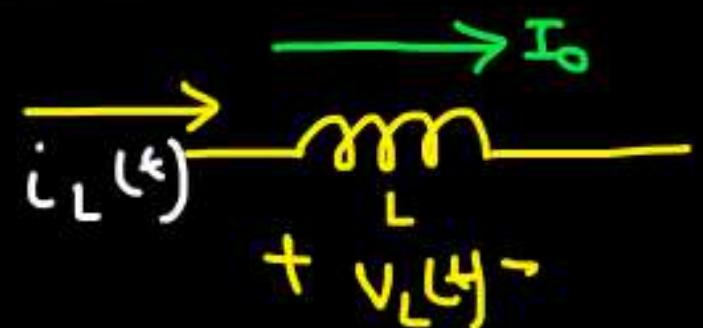* Inductor is having some initial current



$$V_L(s) = L \left[s I_L(s) - i_L(0) \right]$$

$$V_L(s) = L \left[s I_L(s) - I_0 \right]$$

$$V_L(s) = Ls I_L(s) - L I_0$$

PrepFusion



$$I_L(s) = \frac{V_L(s)}{Ls} + \frac{I_0}{s}$$



$$I_o \downarrow i_L(t) + \overset{a}{\cancel{\text{---}}} = V_L(t)$$

\int

$$I_o \quad - \quad b$$

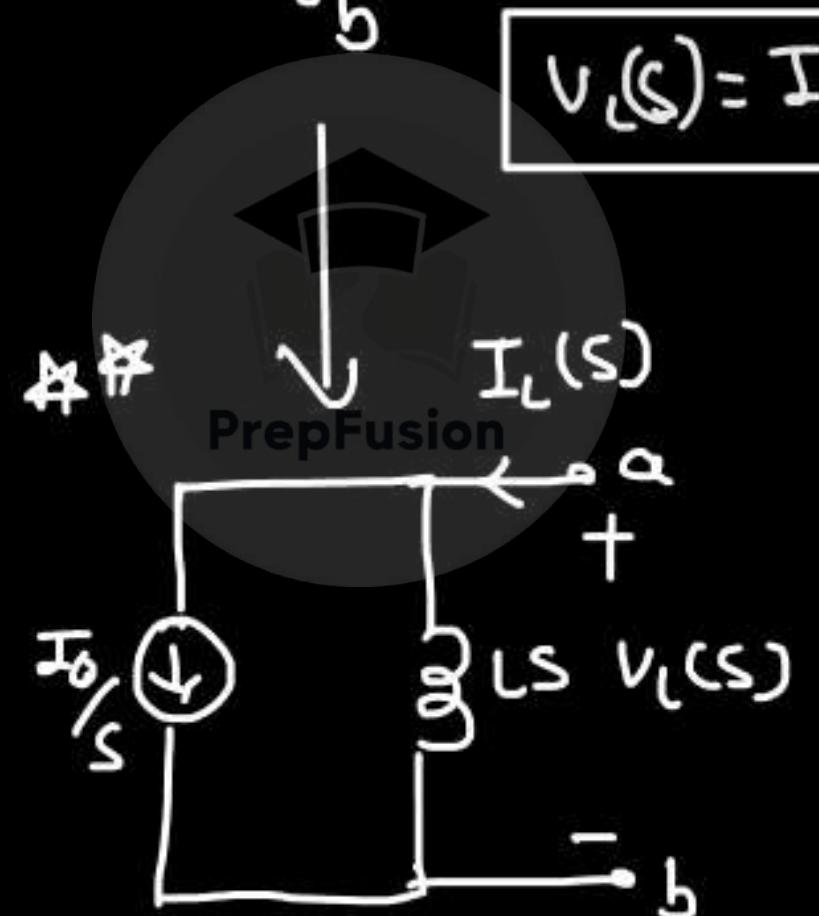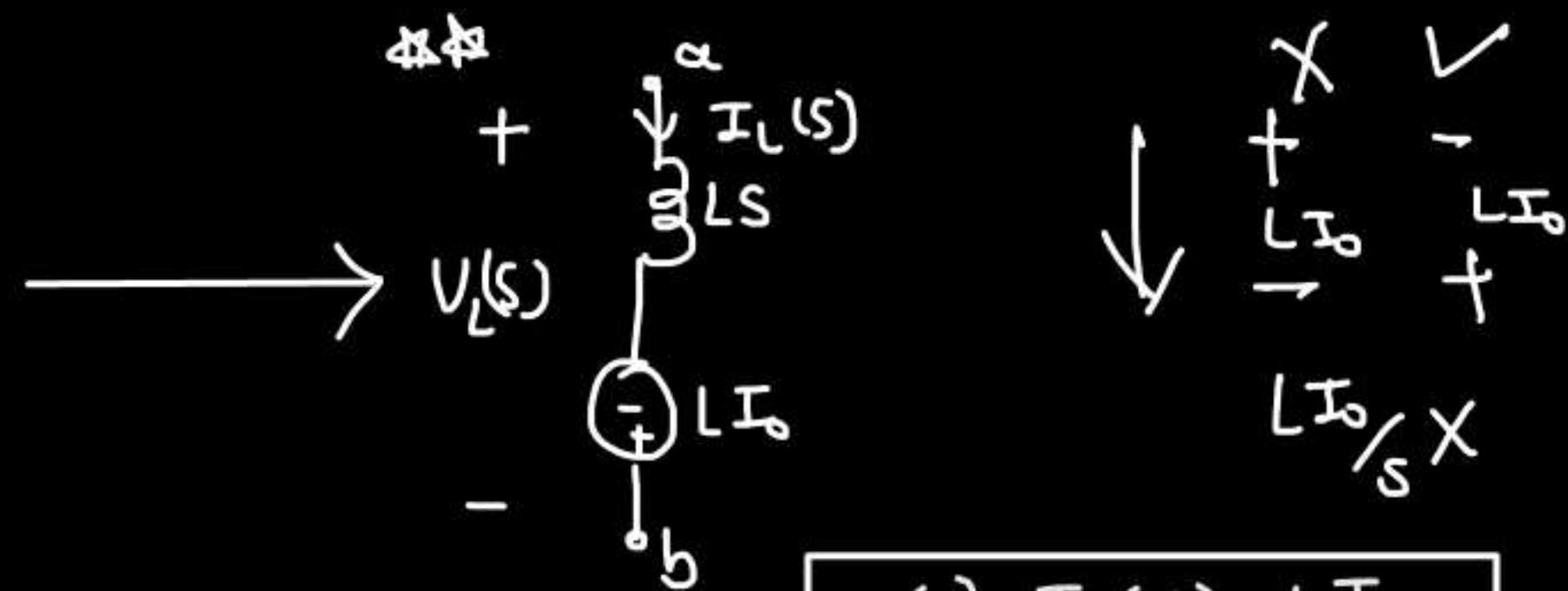


$$I_L(s) = \frac{V_L(s)}{Ls} + \frac{I_o}{s}$$

YouTube -PrepFusion
**(CLICK HERE FOR FULL
PLAYLIST)**

- (CL)
 • 100 HRS. CONTENT
 • 400+ QUESTIONS
 • LIVE DOUBT SESSIONS
 • 10+ TEST SERIES
 • LECTURE NOTES






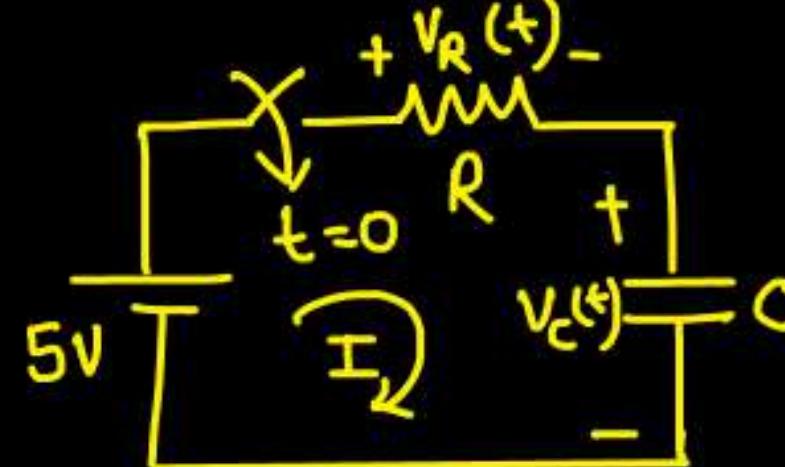Q. Solve the ckt using Laplace Transform.



Find $V_C(t)$, $V_R(t)$
or $I(t)$?

→

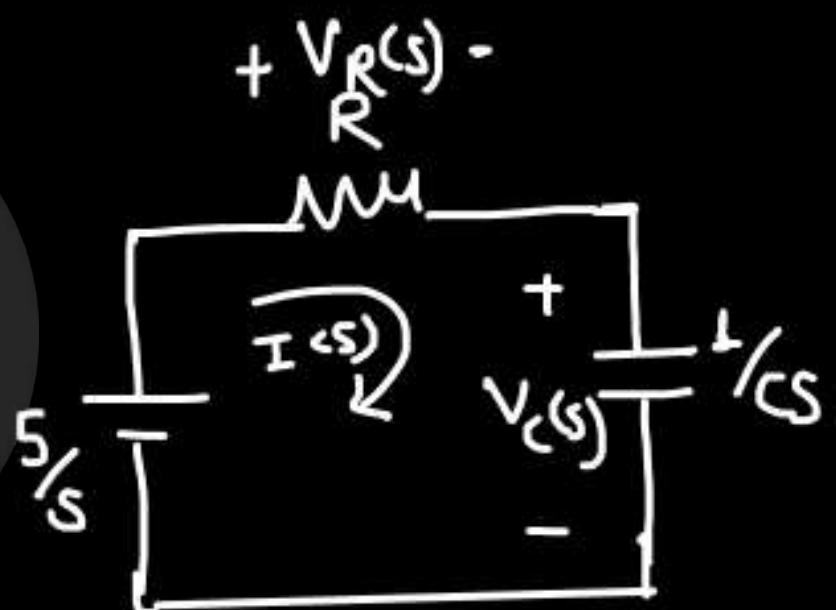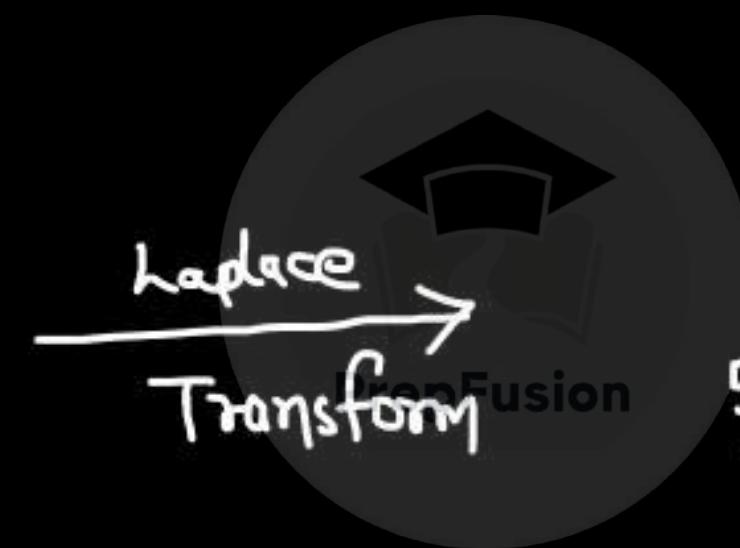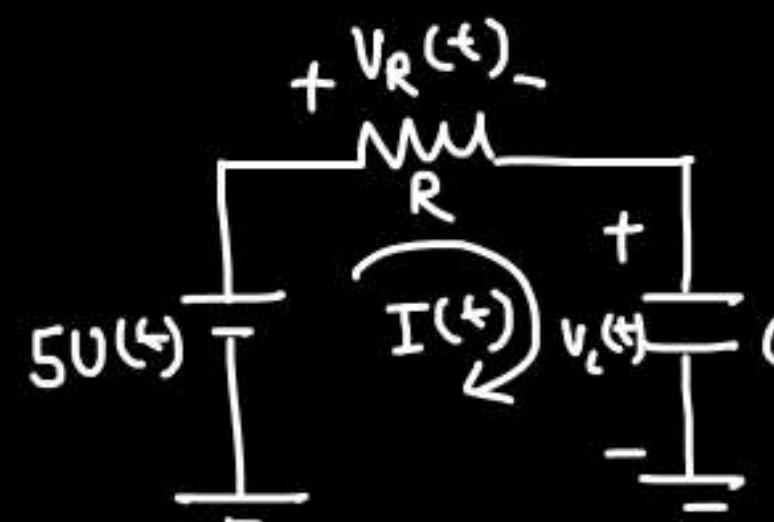

KVL: -

$$\frac{5}{s} = I(s) \times R + I(s) \times \frac{1}{Cs}$$

$$\frac{5}{s} = I(s) \left[R \frac{1}{Cs} + 1 \right]$$

$$\frac{5}{s} = I(s) \left[\frac{RC + 1}{s} \right]$$

$$I(s) = \frac{5c}{RC + sL} \quad \textcircled{1}$$

$$I(s) = \frac{\frac{5c}{RC}}{s + \frac{1}{RC}}$$

$$I(s) = \frac{5}{R} \left[\frac{\frac{1}{L}}{s + \frac{1}{RC}} \right]$$

$$i(t) = \frac{5}{R} e^{-\frac{t}{RC}} v(t)$$

$$\left\{ L^{-1} \left[\frac{1}{s+a} \right] = e^{-at} u(t) \right\}$$

② $V_R(s) :-$

$$V_R(s) = R \cdot I(s)$$

By eqn ①

$$V_R(s) = \frac{5Rc}{Rcd + 1}$$

$$V_R(s) = \frac{5}{s + \frac{1}{RC}}$$

$$v_R(t) = 5e^{-t/RC} v(t)$$



$V_C(s)$:-

$$V_C(s) = \frac{1}{Cs} I(s)$$

$$= \frac{1}{Cs} \left[\frac{5C}{RC + sL} \right]$$

$$V_C(s) = \frac{5}{s(RC + L)}$$



$$= \frac{A}{s} + \frac{B}{RC + L}$$

$$\Rightarrow A(RC + L) + BS = 5$$

$$\Rightarrow A RC + B = 0$$

$$A = 5$$

$$B = -5RC$$



$$V_C(s) = \frac{5}{s} - \frac{5RC}{RC + sL}$$


$$V_C(s) = \frac{5}{s} - \frac{s}{s + \frac{1}{RC}}$$

$$V_C(t) = 5U(t) - 5e^{-t/RC} U(t)$$

$$V_C(t) = 5 \left[1 - e^{-t/RC} \right] U(t)$$

Q. find V_{C_1} , V_{C_2} , I_{C_1} , I_{C_2} , I_R

(a)

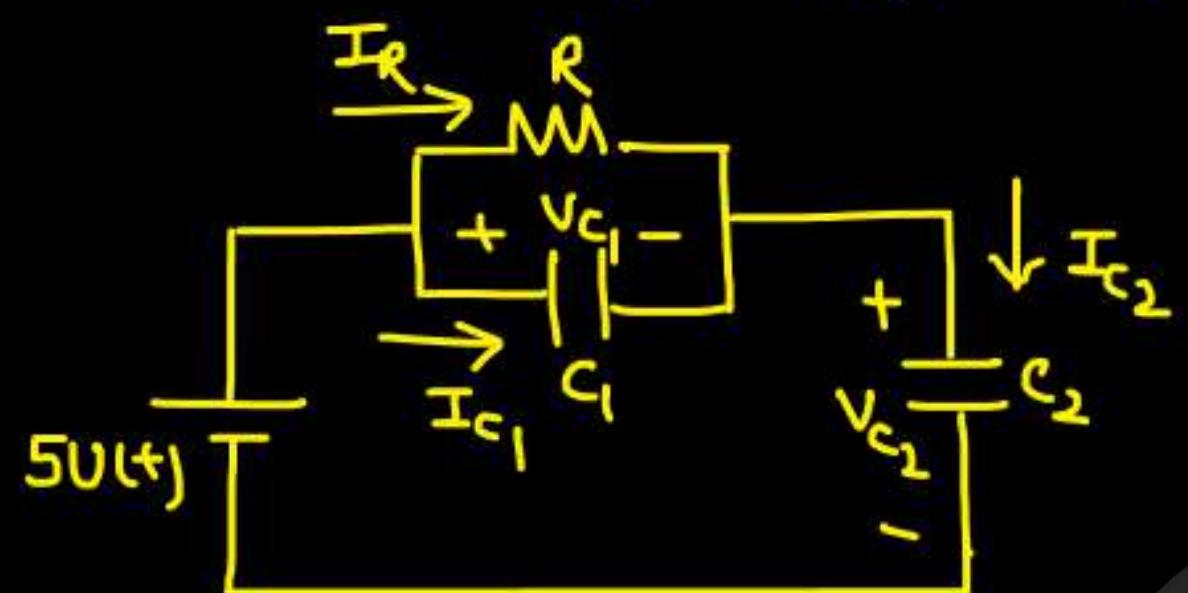


Take $C_1 = C_2 = C$

$$R = 1 \Omega$$

→ Two cap \rightarrow 2nd order ckt \rightarrow NO
 find effective storing element

PrepFusion

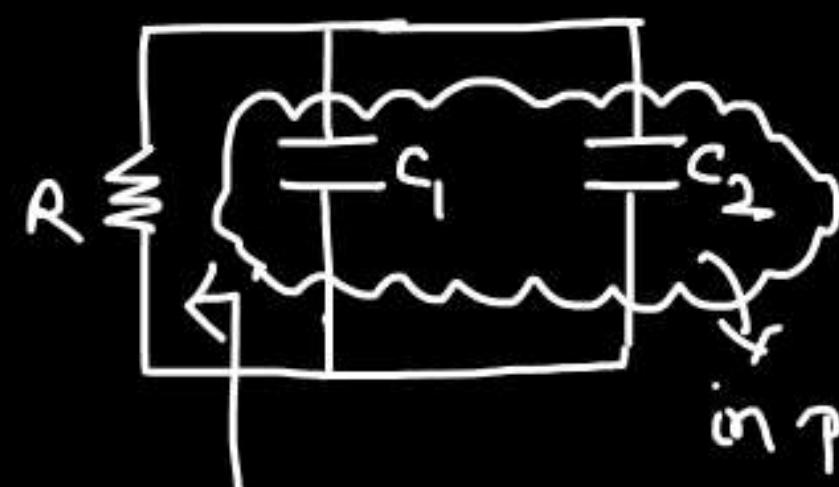

in parallel

$$C_{eff} = C_1 + C_2$$


$$R_{eq} = R$$

$$\Rightarrow \boxed{\tau = R(C_1 + C_2)}$$

1st order

→ Effective storing ele. is only one cap. ($C_1 + C_2$)


ckt @ $t=0$

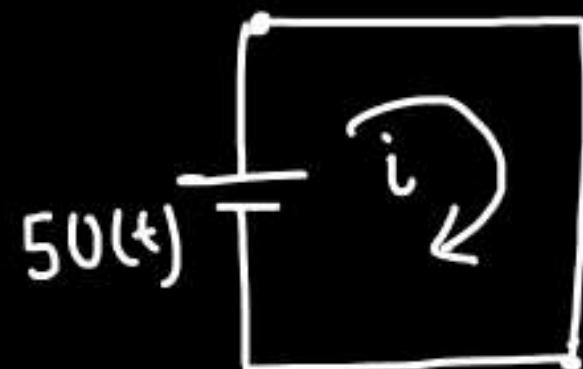

$i = \frac{5}{0} = \infty \Rightarrow$ capacitor voltage will change immediately.

For step input :- @ $t=0 \Rightarrow \omega = \infty \Rightarrow Z_C = \frac{1}{j\omega C} \rightarrow$ very low

@ $t=0$

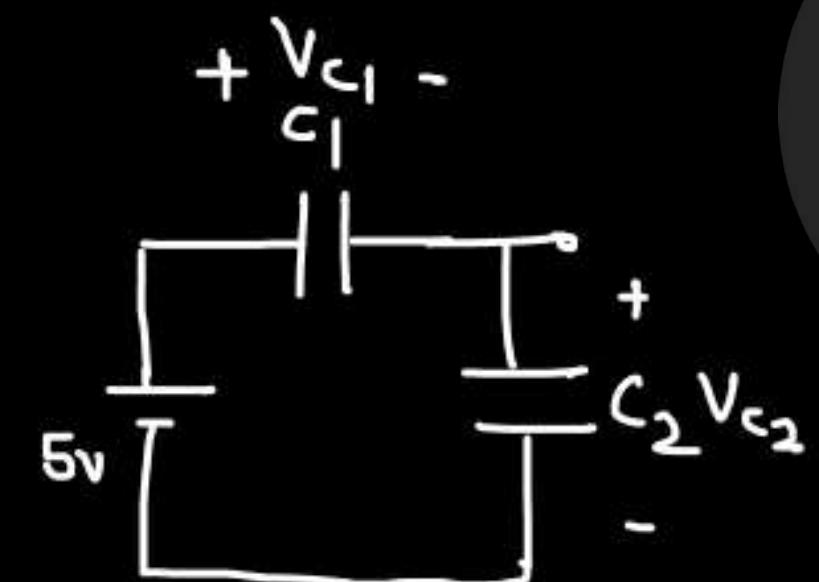

$$-\frac{R}{L} = -\frac{1}{C}$$


$$V_{C_1}(0^-) = 0V, V_{C_1}(0^+) = \frac{5C_2}{C_1 + C_2} V$$

$$V_{C_2}(0^-) = 0V, V_{C_2}(0^+) = \frac{5V}{C_1 + C_2} V$$

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



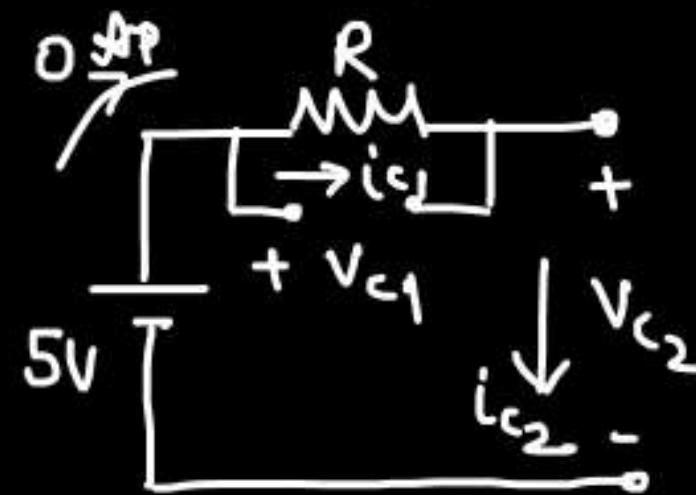@ $t = \infty \Rightarrow$ Cap. acts as O.C.



$$V_{C_1}(\infty) = 0V$$

$$V_{C_2}(\infty) = 5V$$

$$i_{C_1}(\infty) \approx i_{C_2}(\infty) = 0 \text{ A}$$

$$\Rightarrow V_{C_1}(0^+) = \frac{5C_2}{C_1 + C_2} = 2.5V \quad (\text{taking } C_1 = C_2 = C) \quad , \quad V_{C_1}(\infty) = 0V$$



$$V_{C_1}(t) = \frac{5C_2}{C_1 + C_2} e^{-\frac{t}{\tau}} \quad \boxed{\tau = R(C_1 + C_2)}$$

$$\Rightarrow V_C(0^+) = \frac{5C_1}{C_1 + C_2} = 2.5V \quad , \quad V_C(\infty) = 5V$$



$$V_{C_2}(t) = [5 + (2 \cdot 5 - 5) e^{-t/\tau}] U(t)$$
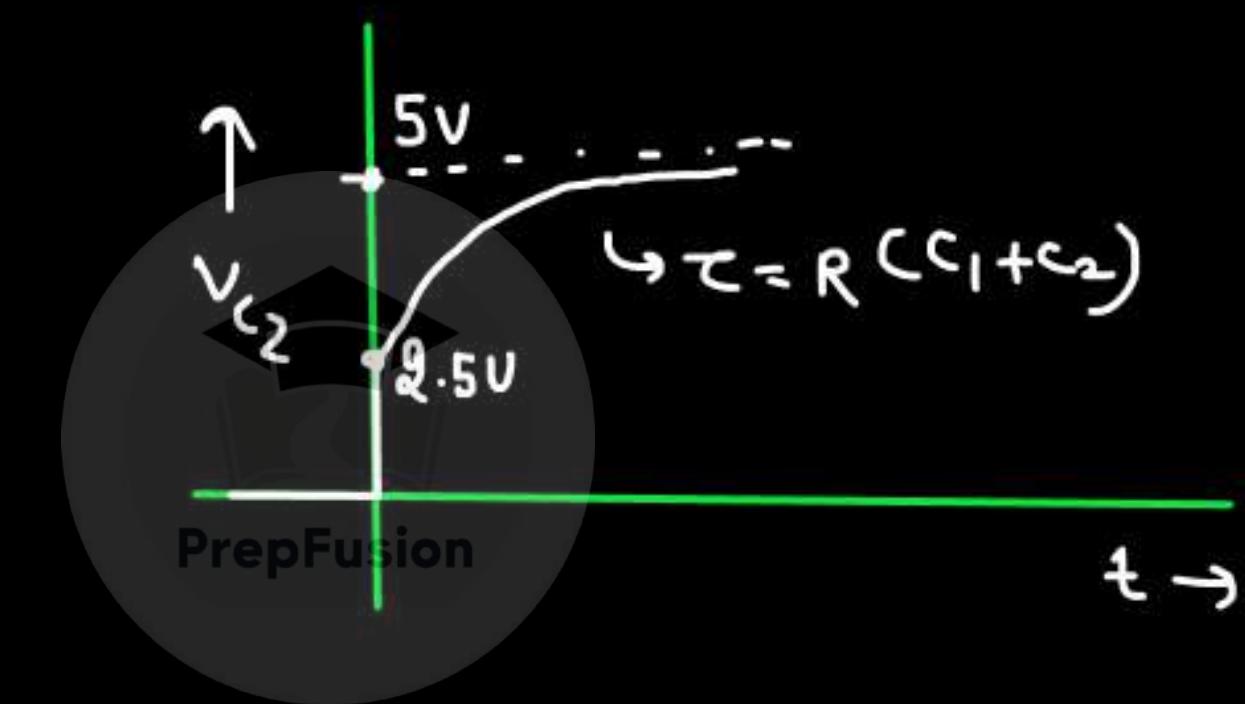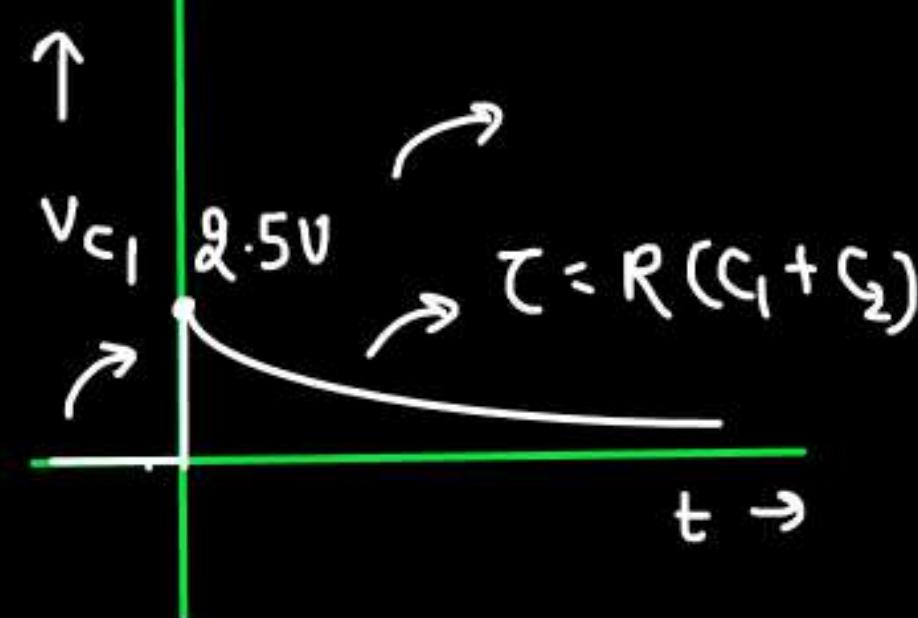
$$V_{C_2}(t) = [5 - 2 \cdot 5 e^{-t/\tau}] U(t) \quad \tau = R(C_1 + C_2)$$




↳ $I_R = \frac{\text{Voltage across resistor}}{R} = \frac{V_{C_1}}{R} = \frac{2.5}{R} e^{-t/\tau} U(t)$ $\tau = R(C_1 + C_2)$



$$x(t) \cdot \delta(t) = x(0)$$

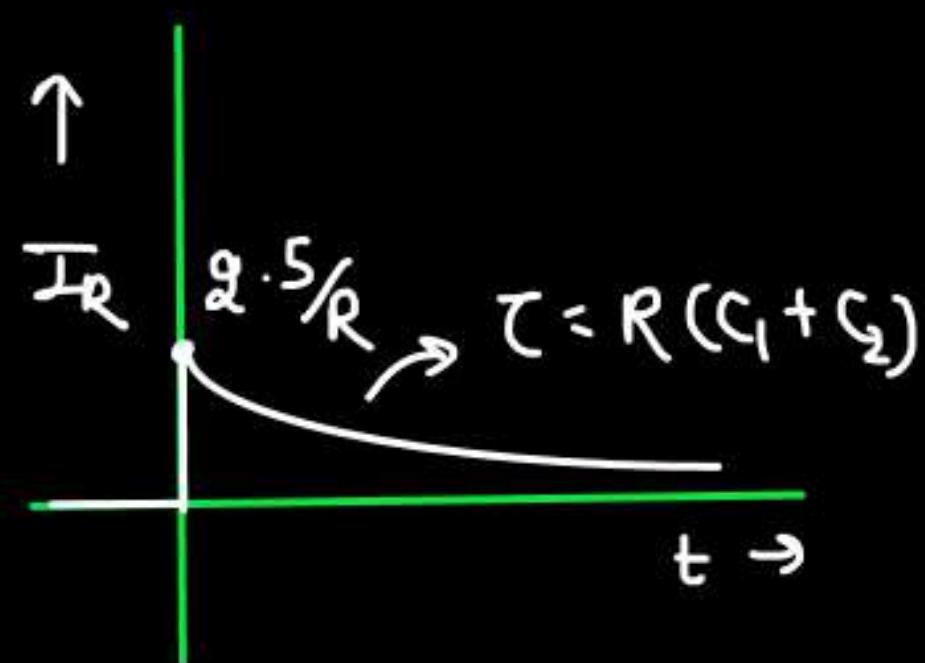- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$I_{C_1} \text{ and } I_{C_2} = ?$$

Time domain f^n

$$I_{C_1}(t) = C_1 \frac{dV_{C_1}(t)}{dt} = C_1 \frac{d}{dt} [2.5 e^{-\frac{t}{\tau}} v(t)]$$

$$= 2.5 C_1 \left[e^{-\frac{t}{\tau}} \delta(t) - \frac{e^{-\frac{t}{\tau}}}{\tau} v(t) \right]$$

$$= 2.5 C_1 \left[\delta(t) - \frac{e^{-\frac{t}{\tau}}}{\tau} v(t) \right]$$


YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)
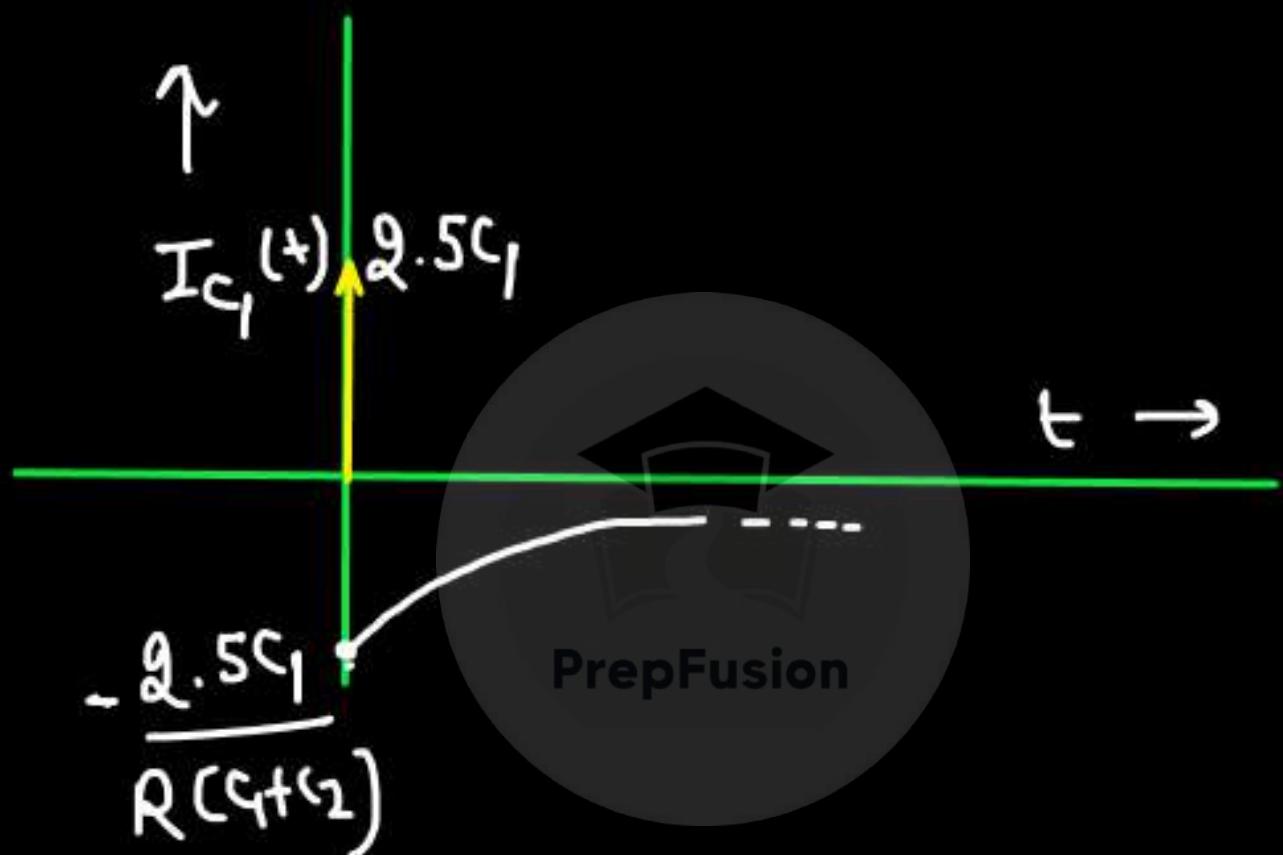
$$I_{C_1}(t) = Q \cdot 5 C_1 \delta(t) - \frac{Q \cdot 5 C_1 e^{-\frac{t}{\tau}}}{R(C_1 + C_2)} u(t)$$



$$\begin{aligned} I_{C_2}(t) &= C_2 \frac{dV_{C_2}(t)}{dt} = C_2 \frac{d}{dt} \left[5 - Q \cdot 5 e^{-\frac{t}{\tau}} \right] u(t) \\ &= C_2 \frac{d}{dt} \left[5u(t) - Q \cdot 5 e^{-\frac{t}{\tau}} u(t) \right] \end{aligned}$$

[YouTube -PrepFusion](#)
[\(CLICK HERE FOR FULL PLAYLIST\)](#)




$$I_{C_2}(t) = C_2 \left[5\delta(t) - 2.5 \left(e^{-\frac{t}{\tau}} \delta(t) - e^{-\frac{t}{\tau}} U(t) \right) \right]$$

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

$$I_{C_2}(t) = 5C_2 \delta(t) - 2.5C_2 \delta(t) + 2.5C_2 e^{-\frac{t}{\tau}} U(t)$$

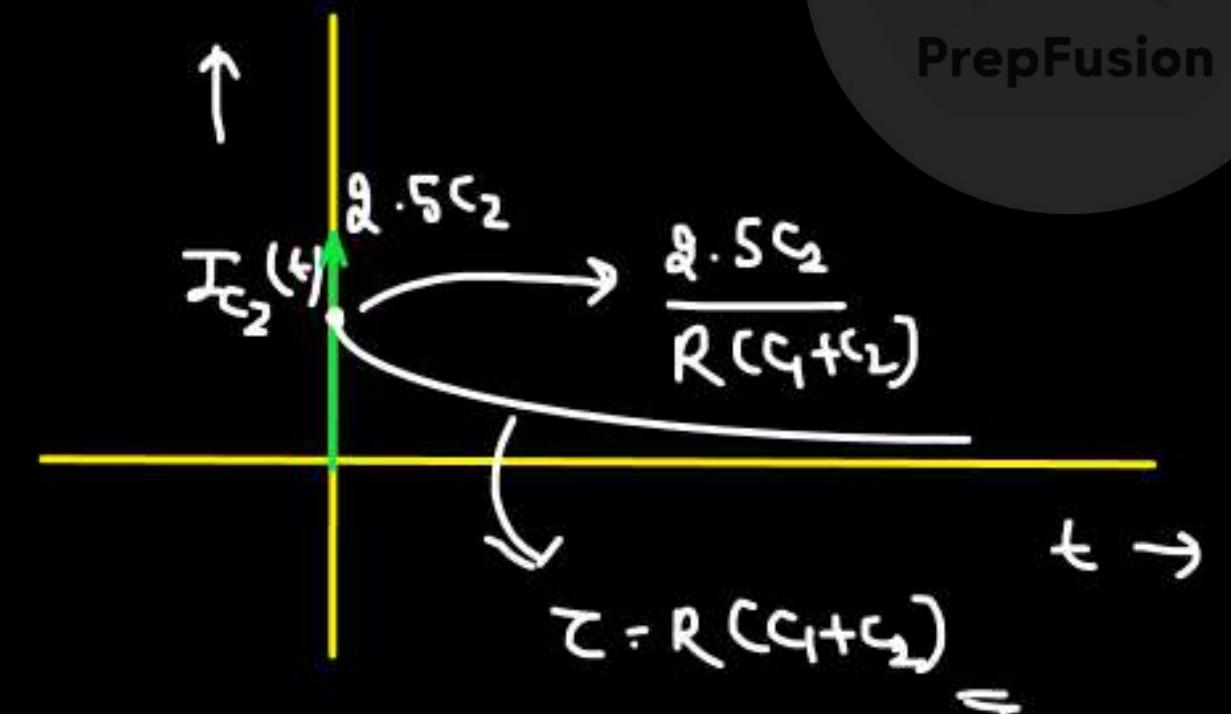
$$I_{C_2}(t) = 2.5C_2 \delta(t) + \frac{2.5C_2}{R(C_1+C_2)} e^{-\frac{t}{\tau}} U(t)$$



YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)

Q. Find V_{C_1} , V_{C_2} , I_{C_1} , I_{C_2} , I_R


(a)

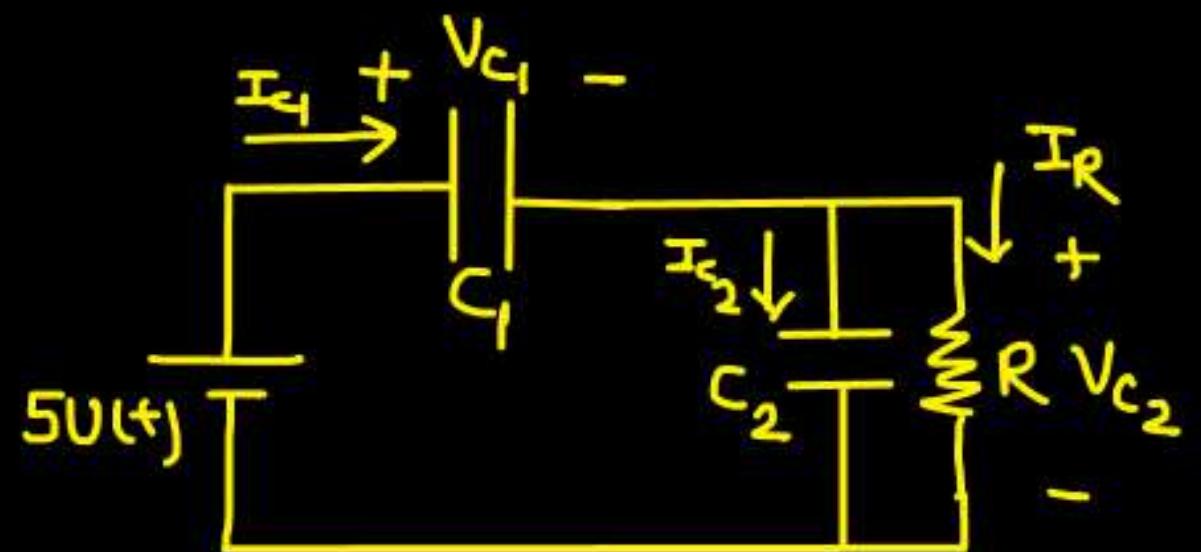

Take $C_1 = C_2 = C$


$$R = 1 \text{ S} =$$

→ Order → 2nd order? → No:-

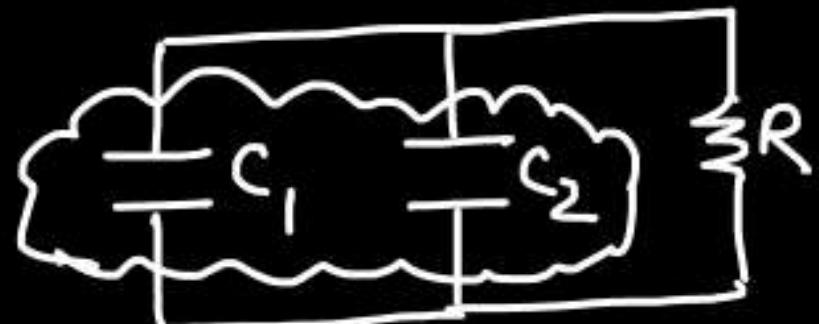

$\tau = R(C_1 + C_2)$ → 1st order


@ t=0

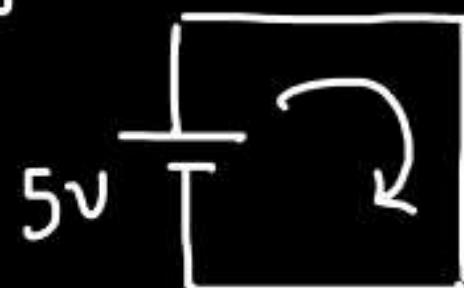

$I = \frac{5V(t)}{0} = \infty \rightarrow$ Cap. voltage will change immediately.

@ $t=0 \Rightarrow \omega = \infty$


ckt @ $t=0$

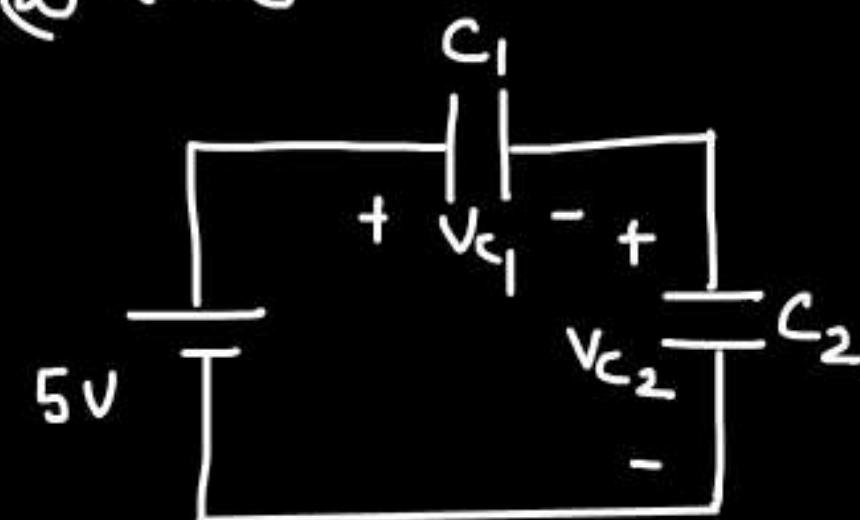

$$V_{c_1}(0^+) = \frac{5C_2}{C_1 + C_2}$$

$$V_{c_2}(0^+) = \frac{5C_1}{C_1 + C_2}$$

ckt @ $t=\infty$

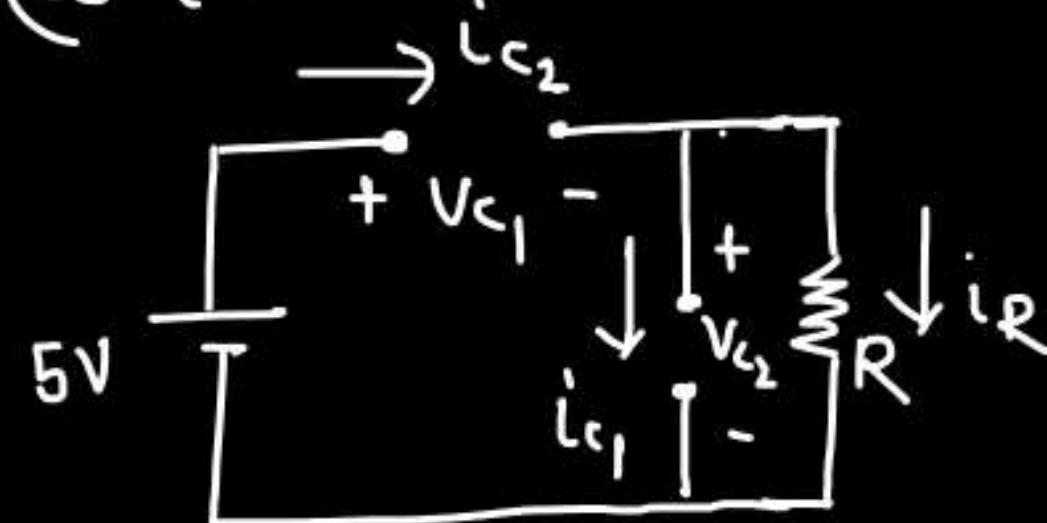

PrepFusion

$$i_R(\infty) = i_{c_1}(\infty) = i_{c_2}(\infty) = 0 \text{ A.P.}$$

$$V_{c_1}(\infty) \approx 5V$$

$$V_{c_2}(\infty) \approx 0V$$

V_{C_1} :-

$$V_{C_1}(0^+) = \frac{5C_2}{C_1+C_2} = 2.5V \quad (\text{Considering } C_1 = C_2 = C)$$

$$V_{C_1}(\infty) = 5V$$



$$V_{C_1}(t) = [5 - 2.5e^{-t/\tau}] u(t)$$

V_{C_2} :-

$$V_{C_2}(0^+) = \frac{5C_1}{C_1+C_2} = 2.5V$$

$$V_{C_2}(\infty) = 0V$$

$$V_{C_2}(t) = 2.5 e^{-t/\tau} u(t)$$

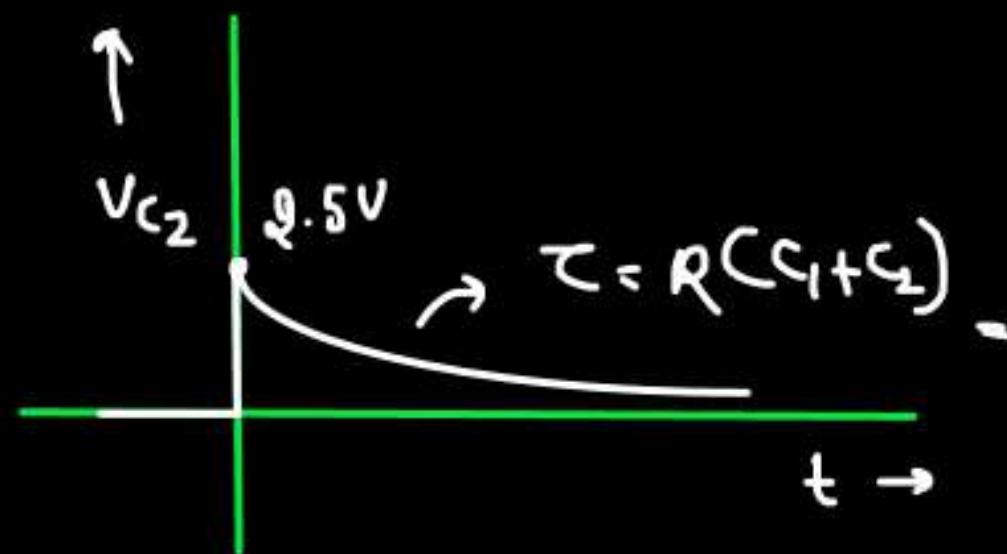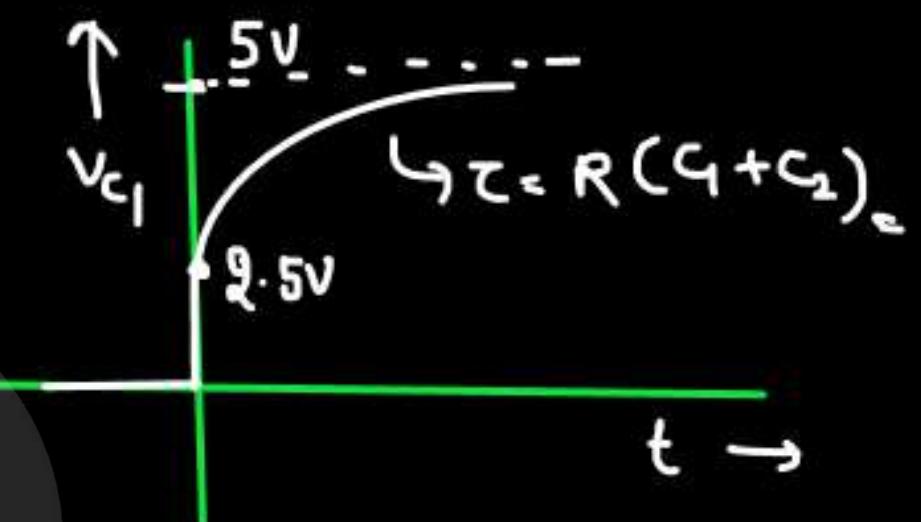


- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



I_0 :-
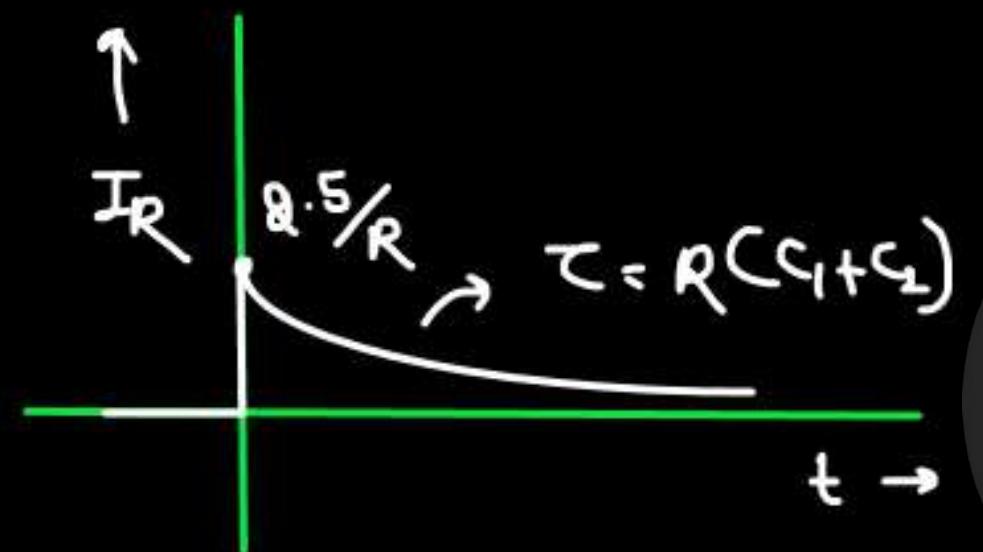
$$I_R = \frac{V_{C_2}}{R} = \frac{Q \cdot 5}{R} e^{-t/\tau} v(t)$$



$I_{C_1}, I_{C_2} \Rightarrow ?$




$$I_{C_1} = C_1 \frac{dV_{C_1}(t)}{dt}$$

$$I_{C_1}(t) \approx 2.5 C_1 \delta(t) + \frac{2.5 C_1}{R(C_1+C_2)} e^{-\frac{t}{\tau}} U(t)$$


$$I_{C_2} = C_2 \frac{dV_{C_2}(t)}{dt}$$
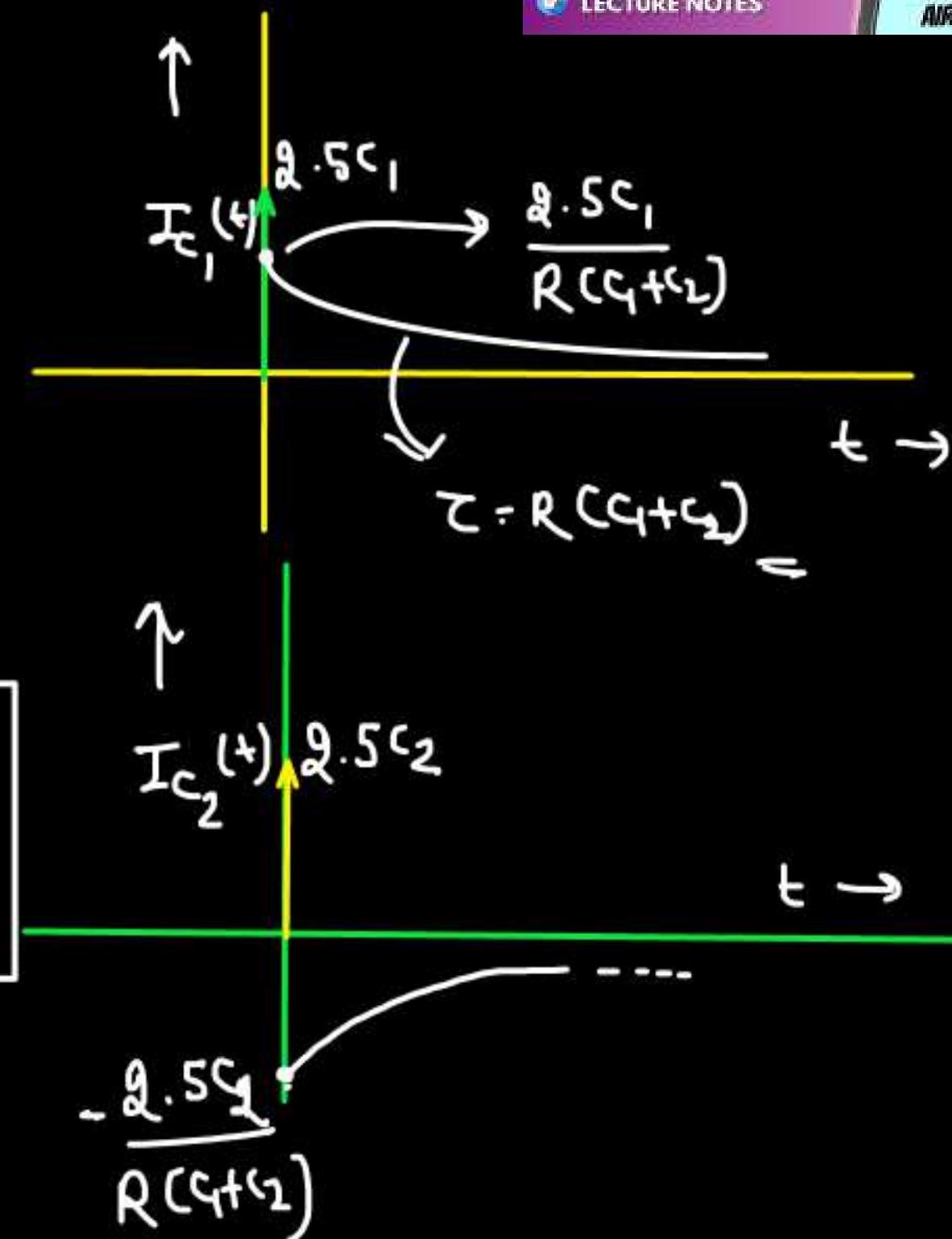
$$I_{C_2}(t) = 2.5 C_2 \delta(t) - \frac{2.5 C_2}{R(C_1+C_2)} e^{-\frac{t}{\tau}} U(t)$$




AIR 27 (ECE)
AIR 45 (IN)

Q.

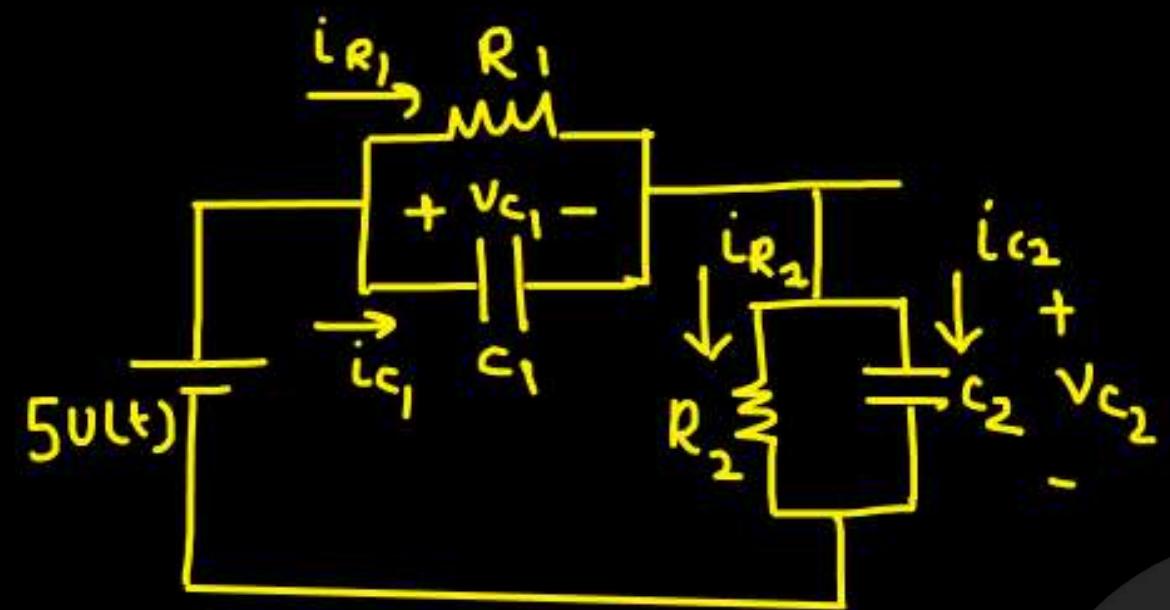

→

order = ?

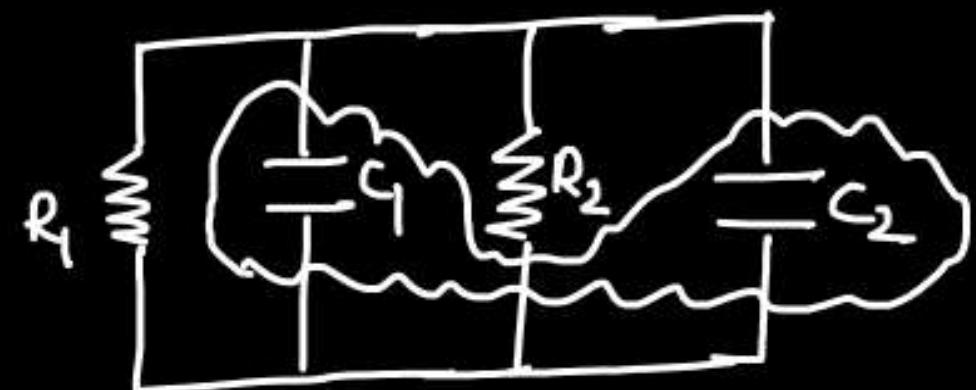

Comment on all the parameters for three cases

$$\textcircled{1} R_1 C_1 > R_2 C_2$$


$$\textcircled{2} R_1 C_1 < R_2 C_2$$

$$\textcircled{3} R_1 C_1 = R_2 C_2$$



PrepFusion

$$C_{ef} = C_1 + C_2 \rightarrow 1^{\text{st}} \text{ order}$$

$$R_{eq} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

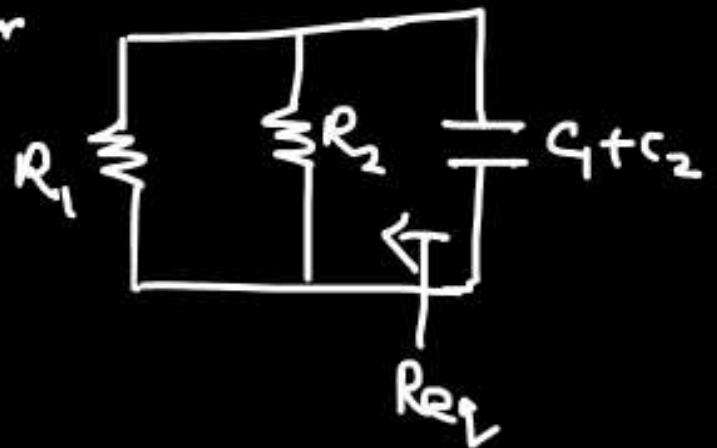

$$\tau = \frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2)$$

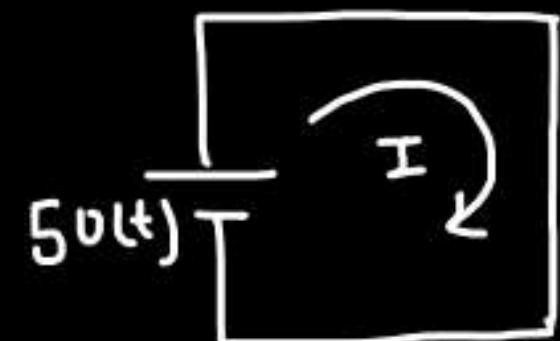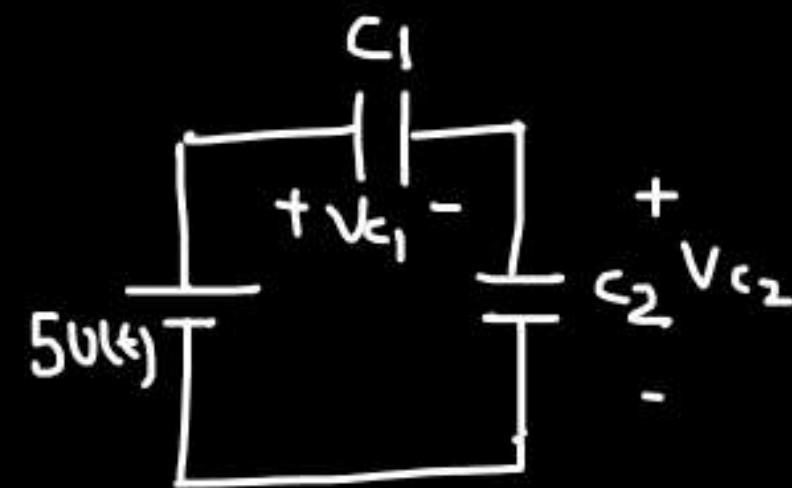(a) $t=0$:-
 $I = \frac{5}{0} = \infty \Rightarrow \text{Cap. voltage will change immediately}$


$$\boxed{V_{C_1}(0^+) = \frac{5C_2}{C_1 + C_2}}$$


$$V_{C_2}(0^+) = \frac{5C_1}{C_1 + C_2}$$

$= \frac{5}{1 + \frac{C_1}{C_2}}$

$= \frac{5}{1 + \frac{C_2}{C_1}}$



@ $t = \infty$

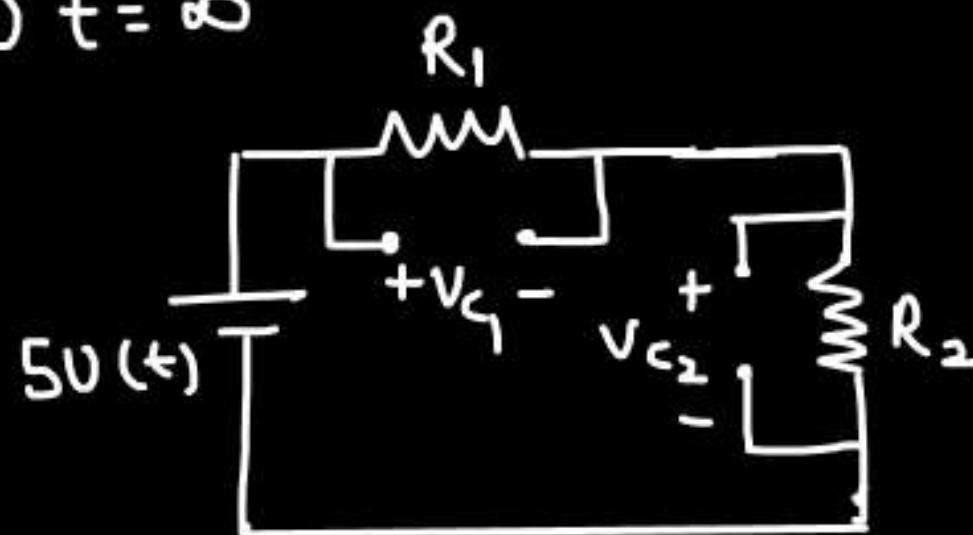

$$V_{C_1}(\infty) = \frac{5R_1}{R_1 + R_2}$$

$$V_{C_2}(\infty) = \frac{5R_2}{R_1 + R_2}$$

$$= \frac{5}{1 + \frac{R_2}{R_1}}$$

$$= \frac{5}{1 + R_1/R_2}$$

$$\textcircled{1} \quad R_1 C_1 > R_2 C_2$$

$$\Rightarrow \frac{R_1}{R_2} > \frac{C_2}{C_1} \quad \Rightarrow \quad \frac{R_2}{R_1} < \frac{C_1}{C_2}$$

$$V_{C_1}(0^+) = \frac{5}{1 + C_1/C_2}$$

$$, \quad V_C(\infty) = \frac{5}{1 + R_2/R_1}$$

$$\Rightarrow \boxed{V_{C_1}(0^+) < V_C(\infty)}$$

$$V_{C_2}(0^+) = \frac{5}{1 + C_2/C_1}$$

$$V_{C_2}(\infty) = \frac{5}{1 + R_1/R_2}$$

$$\boxed{V_{C_2}(0^+) > V_{C_2}(\infty)}$$







- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t/\tau} \quad ; \quad \tau = \frac{R_1 R_2}{R_1 + R_2} \quad (1)$$

(R_1 C_1 > R_2 C_2)

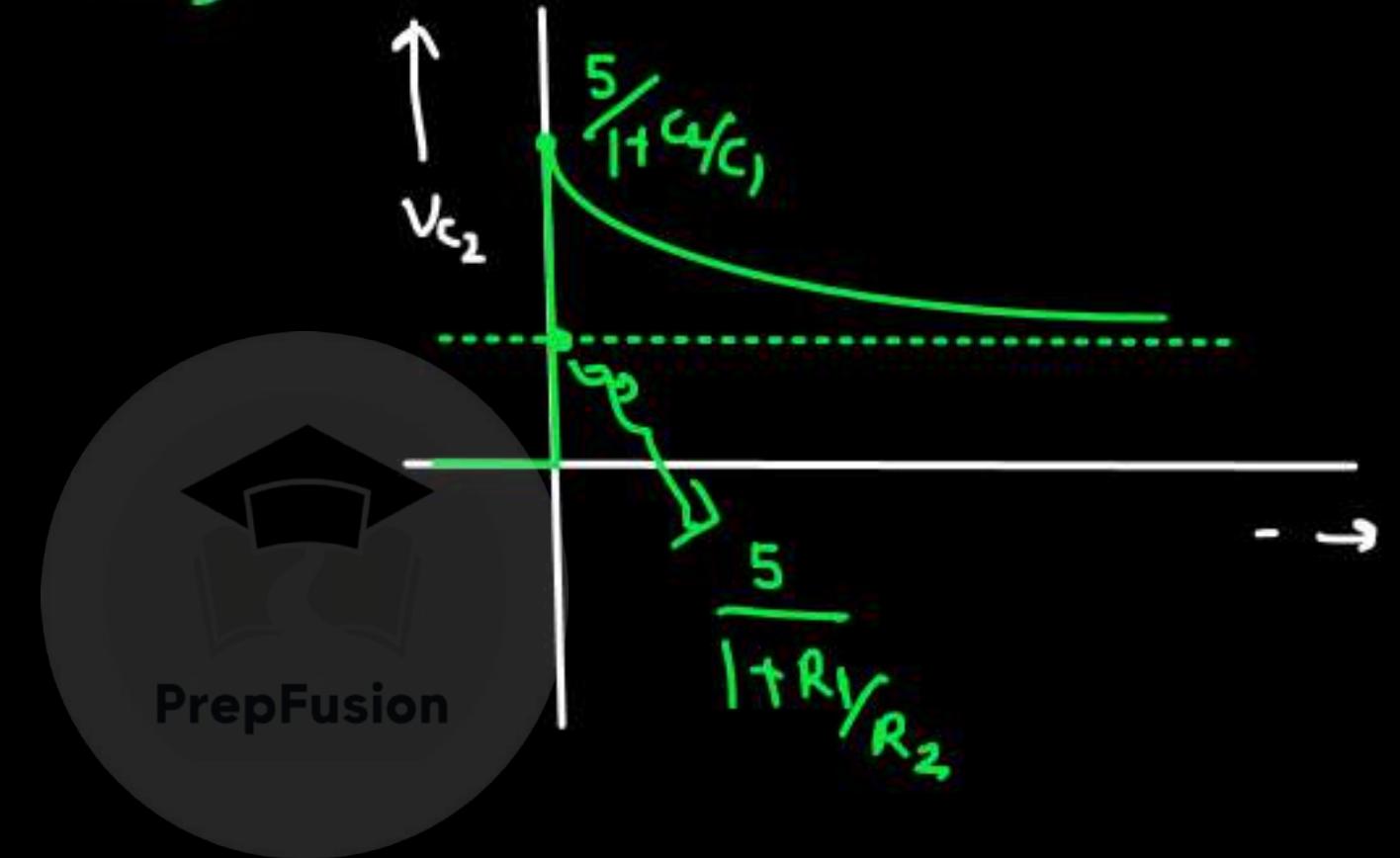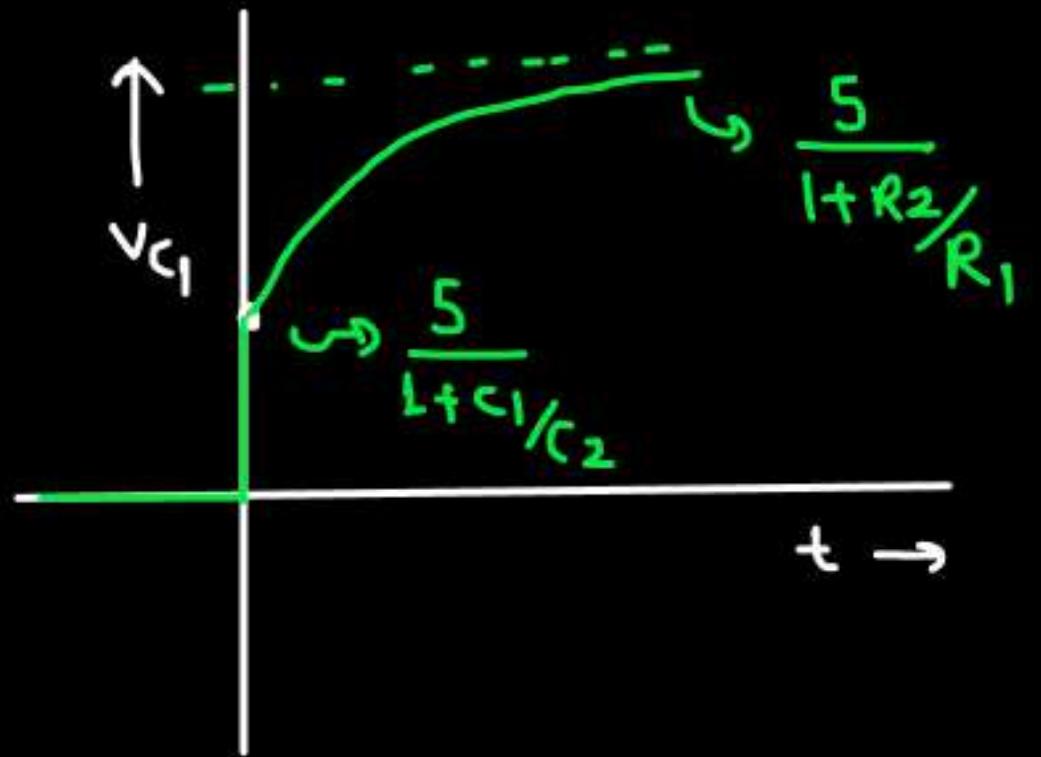



② $R_1 C_1 < R_2 C_2$

$$\Rightarrow \frac{R_1}{R_2} < \frac{C_2}{C_1} \quad \text{OR} \quad \frac{R_2}{R_1} > \frac{C_1}{C_2}$$

$$V_{C1}(0^+) > V_{C1}(\infty)$$


$$V_{C2}(0^+) < V_{C2}(\infty)$$

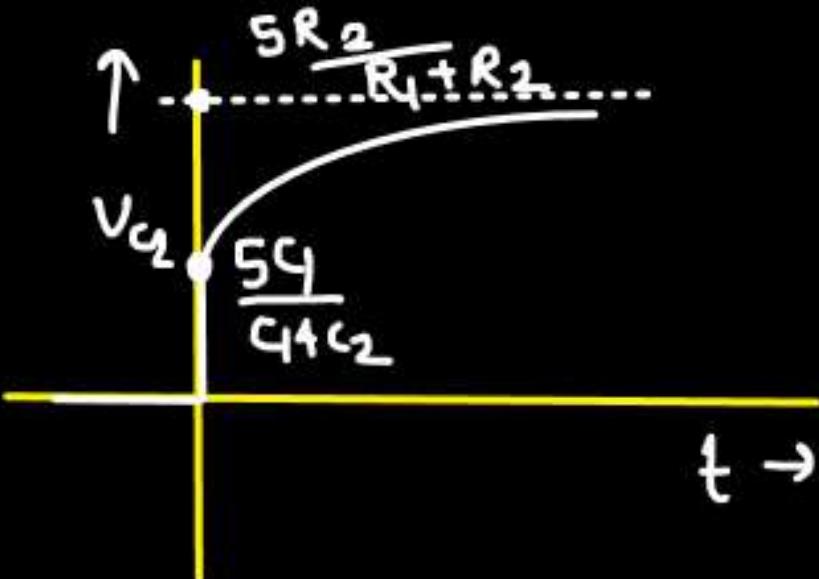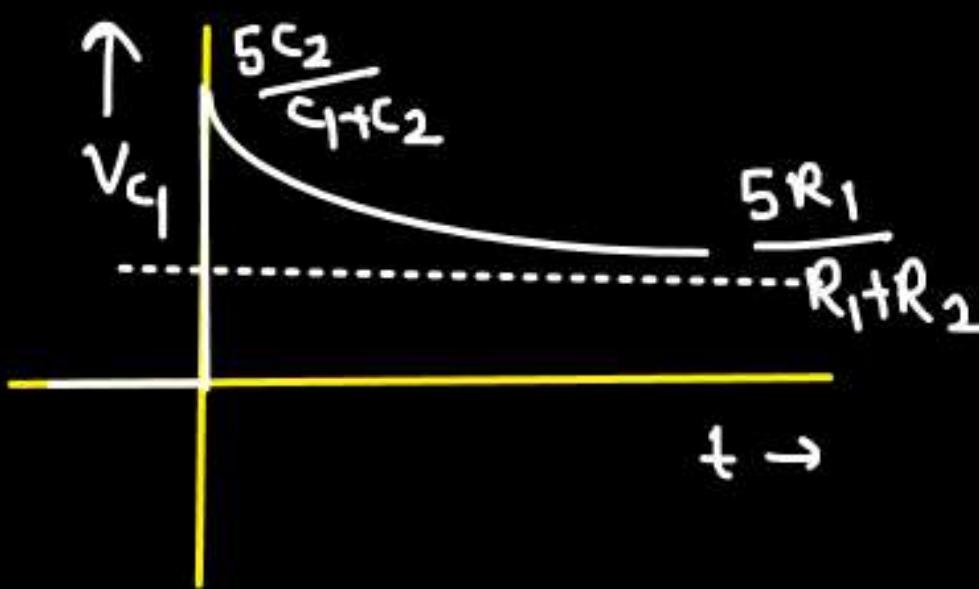YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)





$$\textcircled{3} \quad R_1 C_1 = R_2 C_2$$
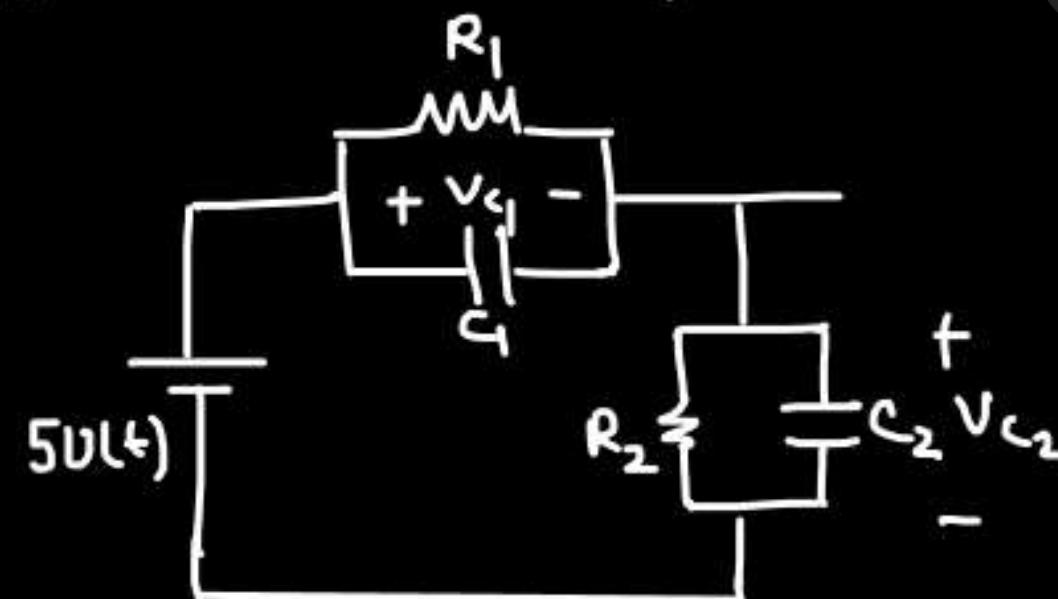
$$\Rightarrow \frac{R_1}{R_2} = \frac{C_2}{C_1} \quad \text{and} \quad \frac{R_2}{R_1} = \frac{C_1}{C_2}$$



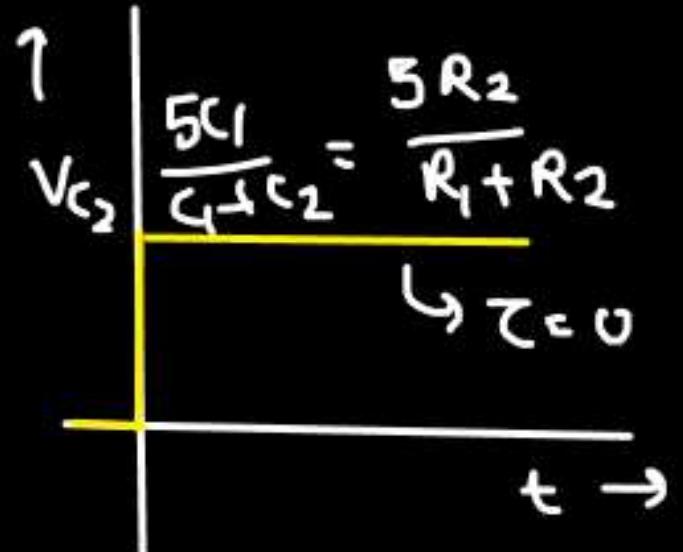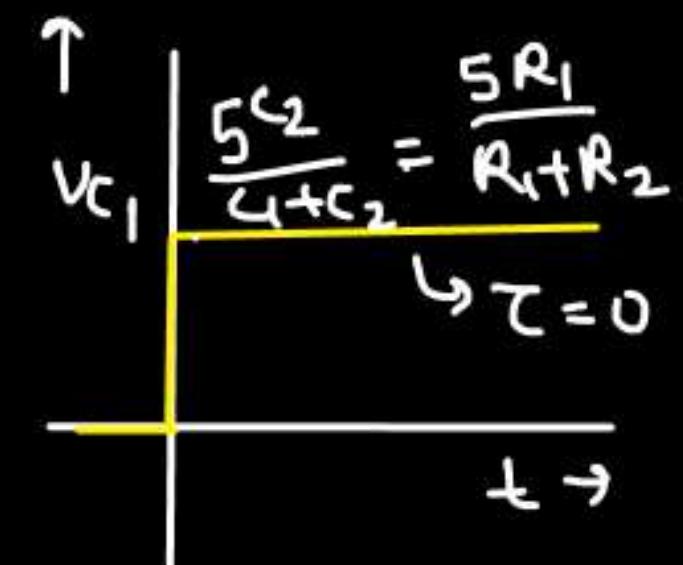PrepFusion $\Rightarrow V_{C_1}(0^+) = V_{C_1}(\infty)$
 $V_{C_2}(0^+) = V_{C_2}(\infty)$





$i_{C_1}, i_{C_2}, i_{R_1}, i_{R_2}$:-





$$i_{C_1} = C_1 \frac{dV_{C_1}}{dt}$$

$$; \quad i_{C_2} = C_2 \frac{dV_{C_2}}{dt}$$

$$i_{R_1} = \frac{V_{C_1}}{R_1}$$





$$; \quad i_{R_2} = \frac{V_{C_2}}{R_2}$$

① $R_1 C_1 > R_2 C_2$

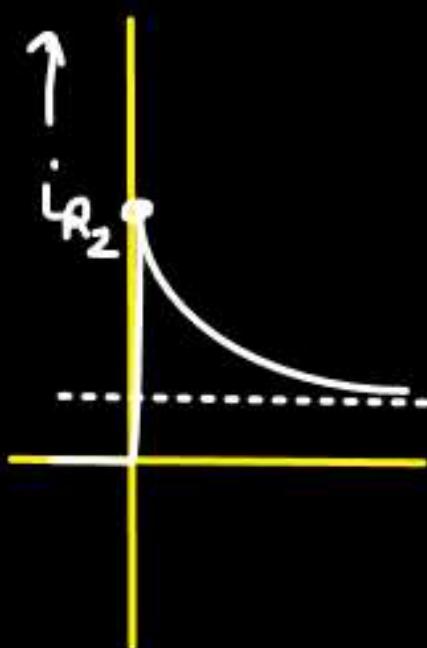
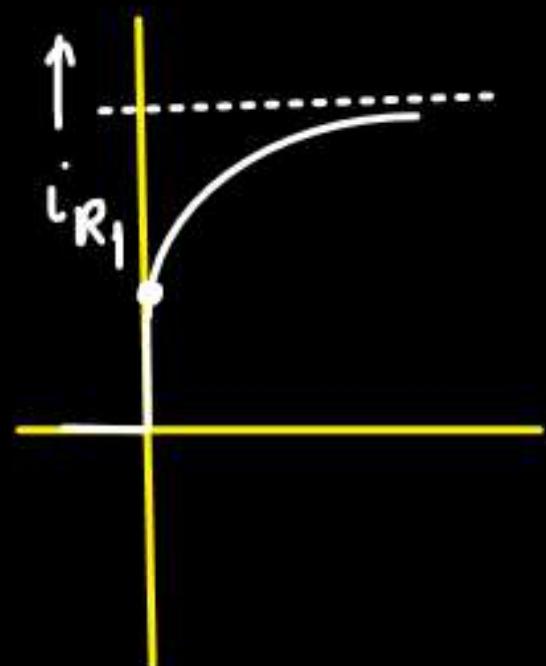
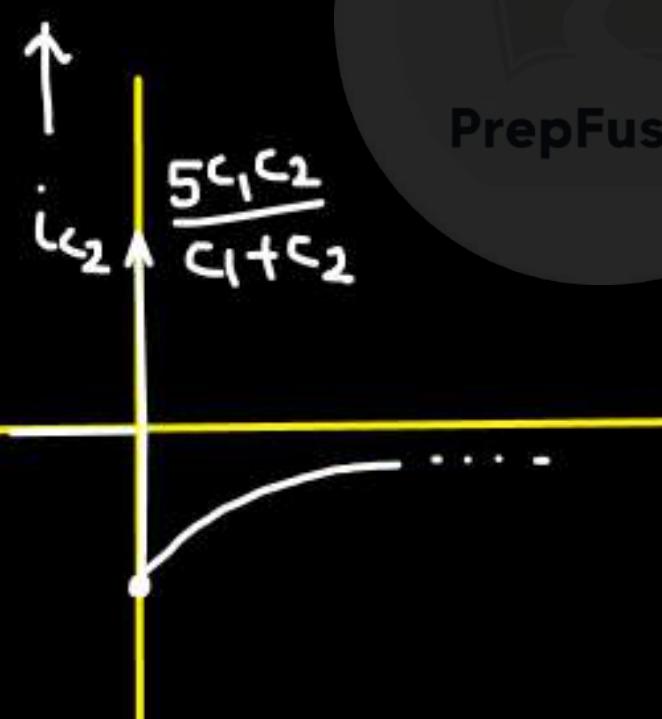
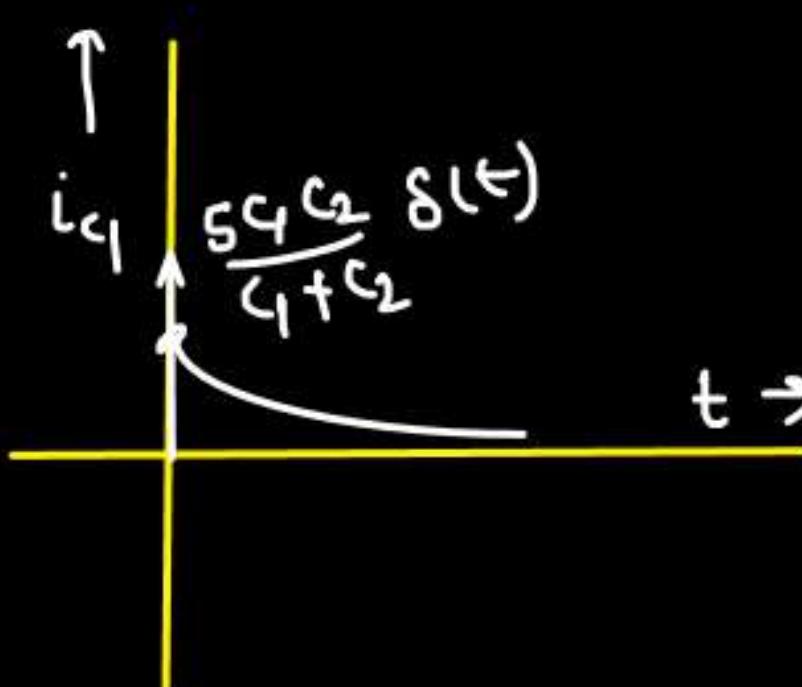



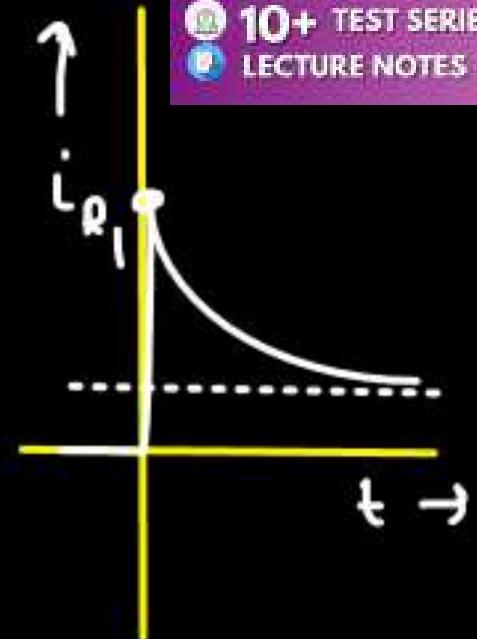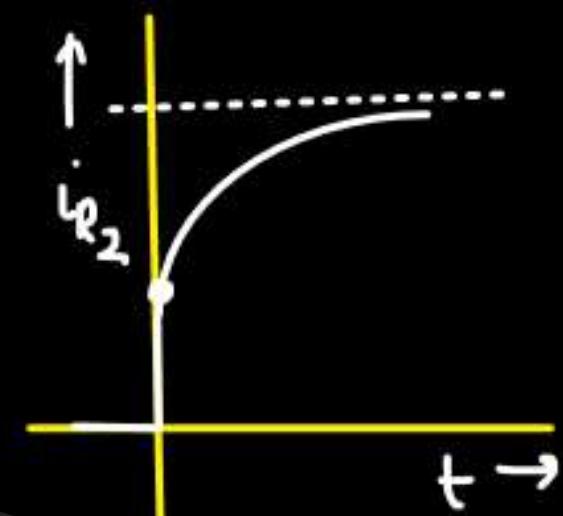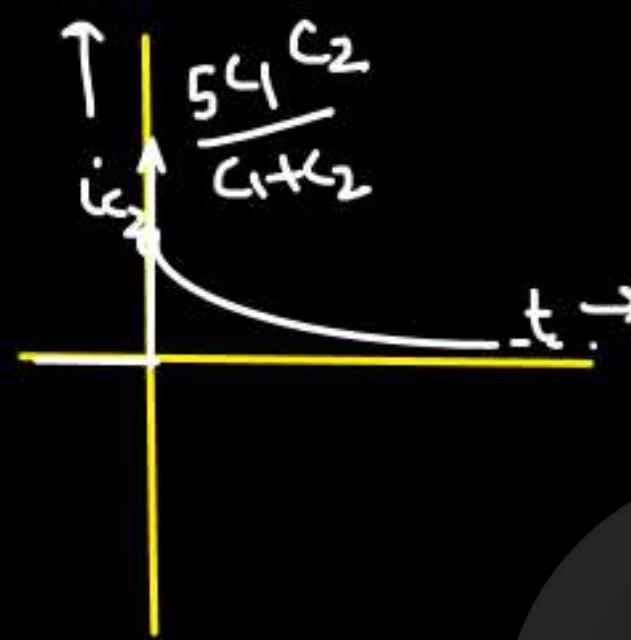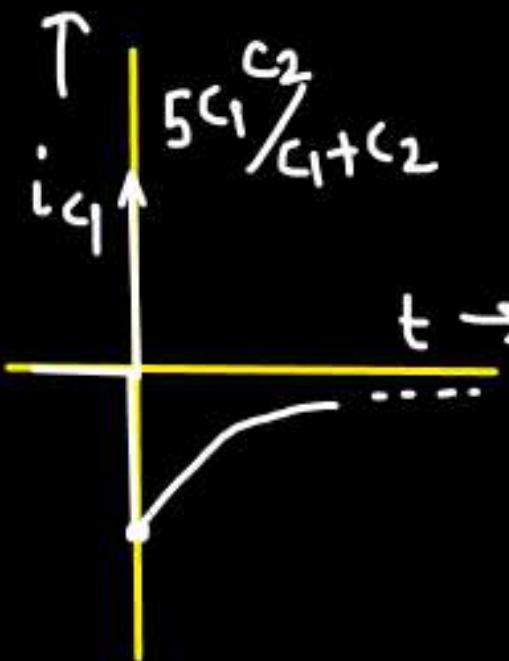
$$\textcircled{2} \quad R_1 C_1 < R_2 C_2$$


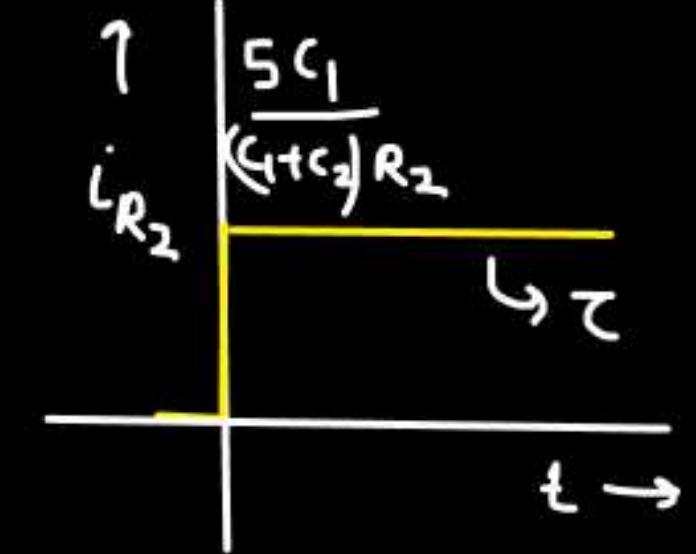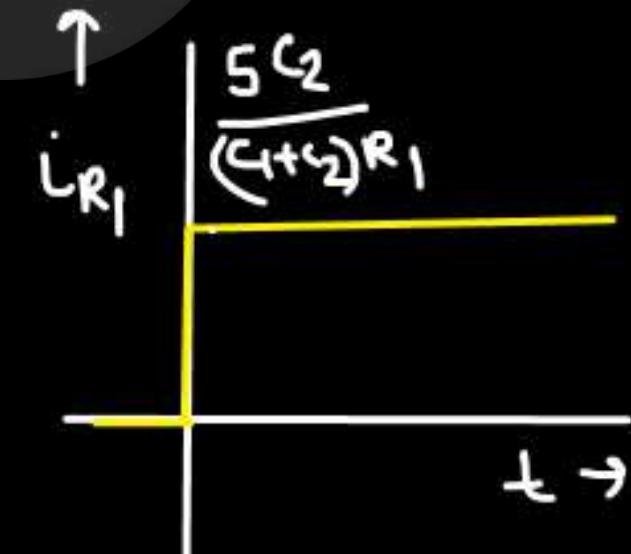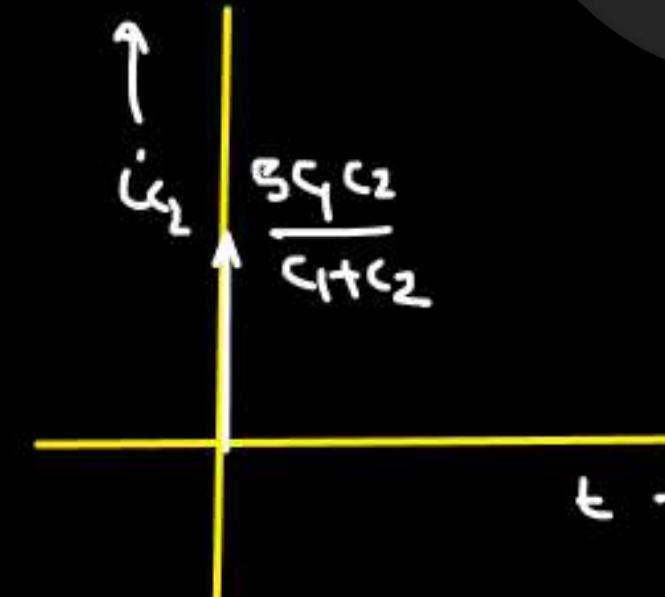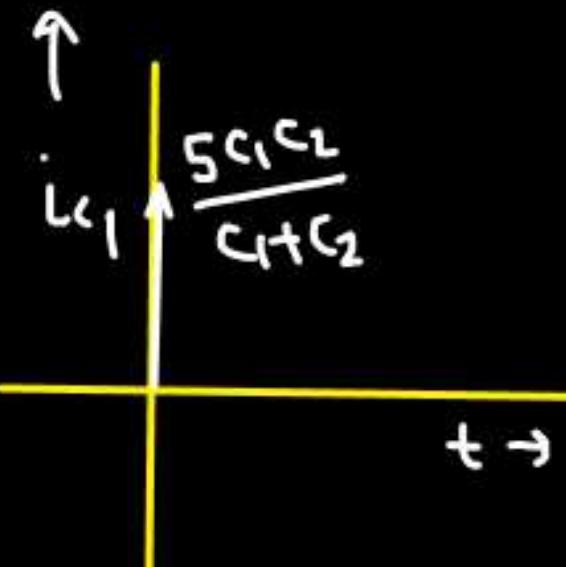
$$\textcircled{3} \quad R_1 C_1 = R_2 C_2$$







AIR 27 (ECE)
AIR 45 (IN)

* RC ckt to current i/p :-

Q.

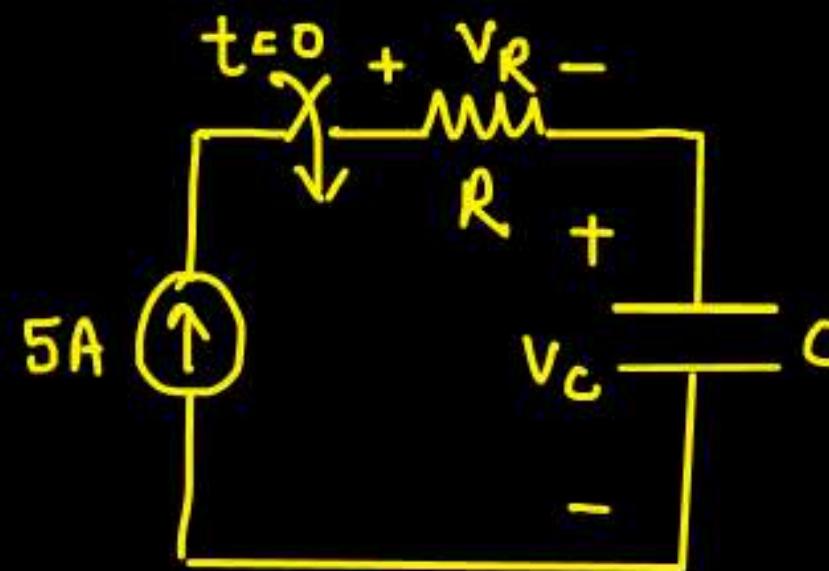

$$I(t) = 5v(t)$$

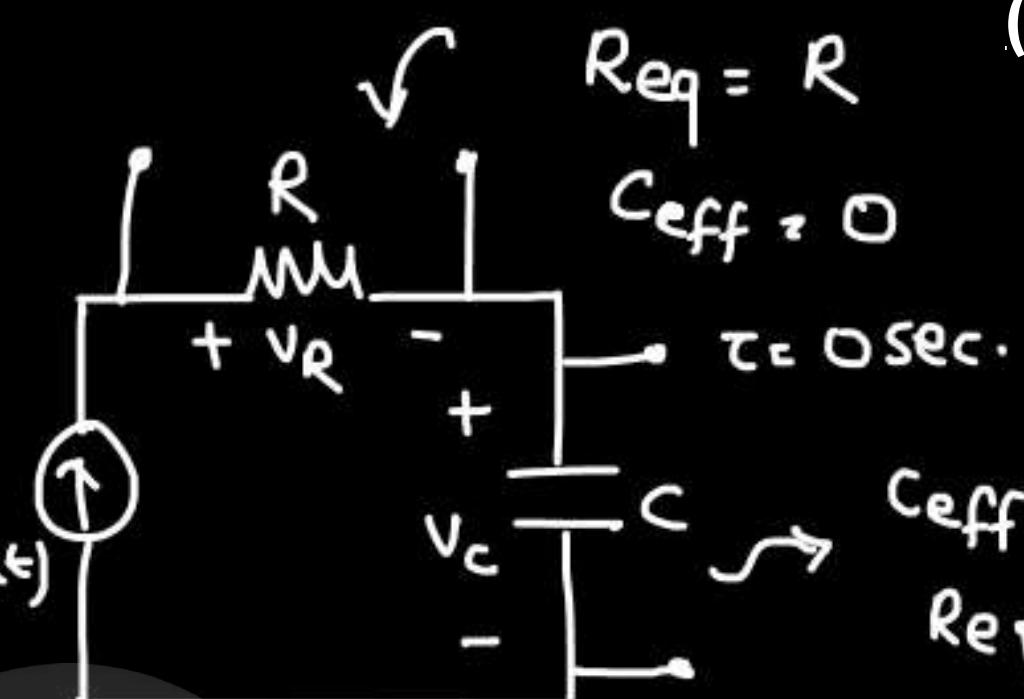

$$Req = R$$

$$C_{eff} = 0$$


$$\tau \approx 0 \text{ sec.}$$

$$C_{eff} = C \Rightarrow \tau = \infty \text{ sec.}$$

$$Req = \infty$$


$$VR(t) = I(t) \times R$$

$$\text{PrepFusion} = 5Rv(t)$$


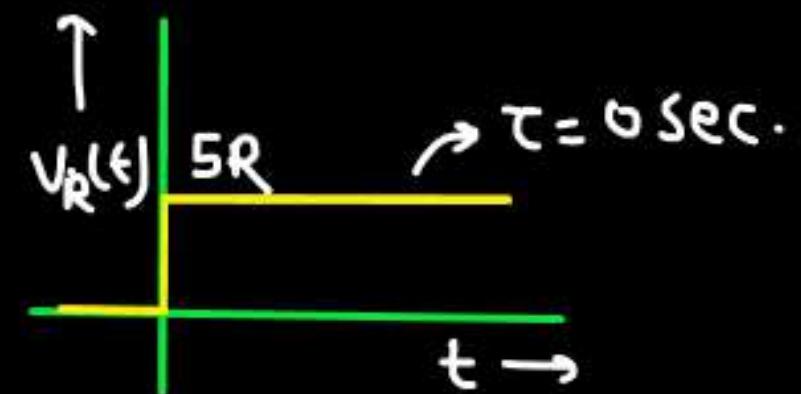


Vc(t) :- ?

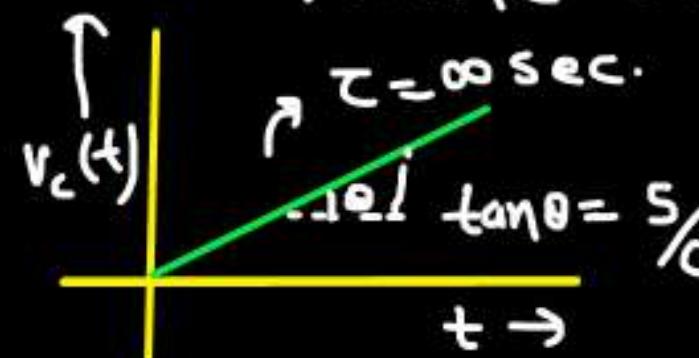↳ Same current 5v(t) always flows through the cap.




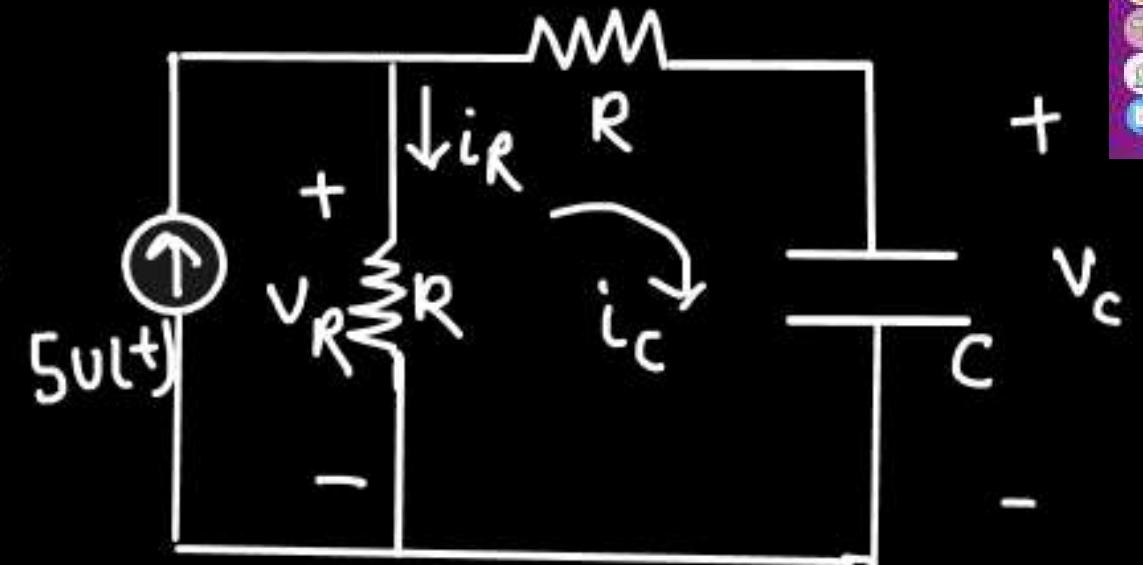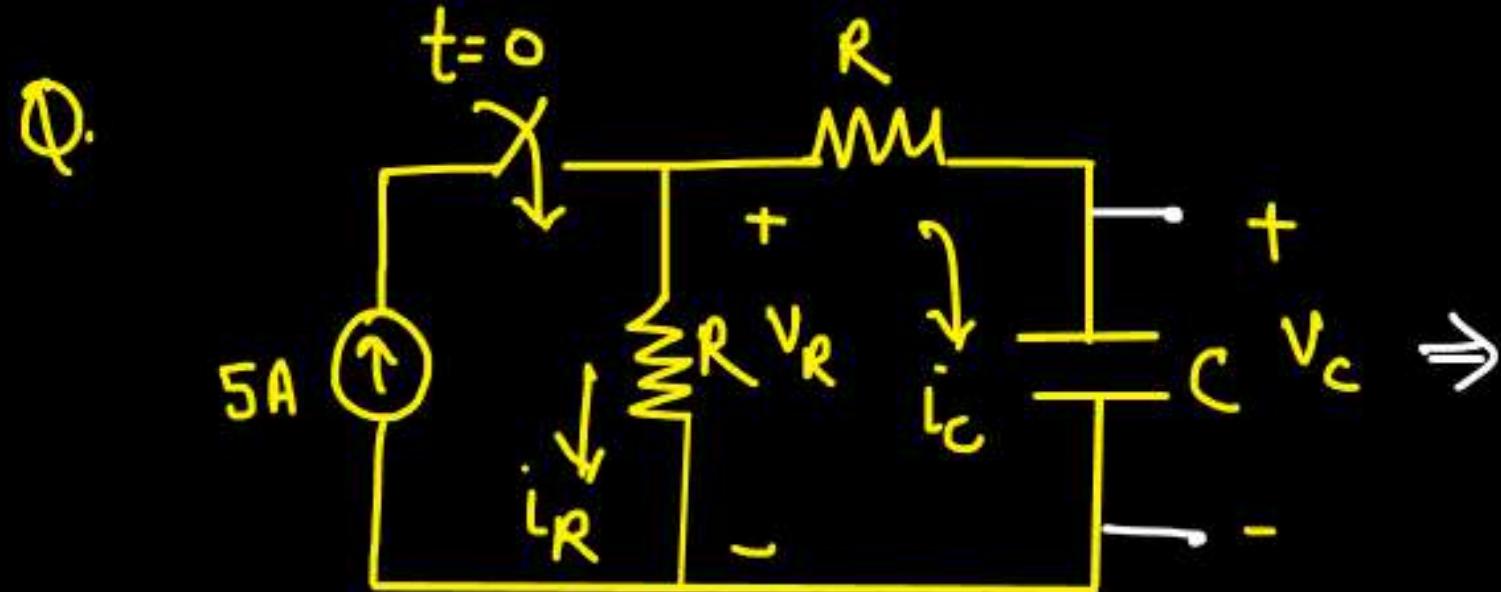
$$Vc(t) = \frac{1}{C} \int_0^t i \cdot dt = \frac{1}{C} \int_0^t 5v(t) \cdot dt = \frac{5}{C} r(t) = \frac{5t}{C} v(t)$$





$$V_c : - \\ V_c(0^+) = 0V$$

$$V_c(\infty) = 5R$$

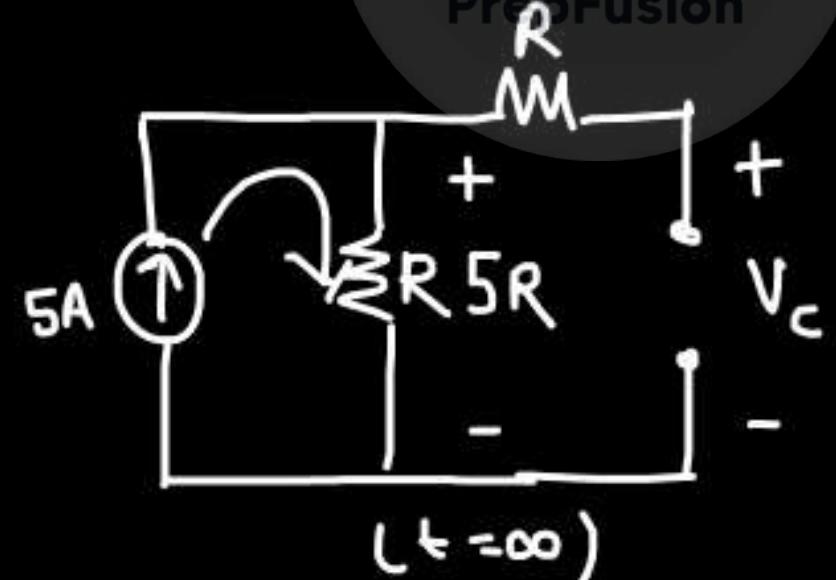
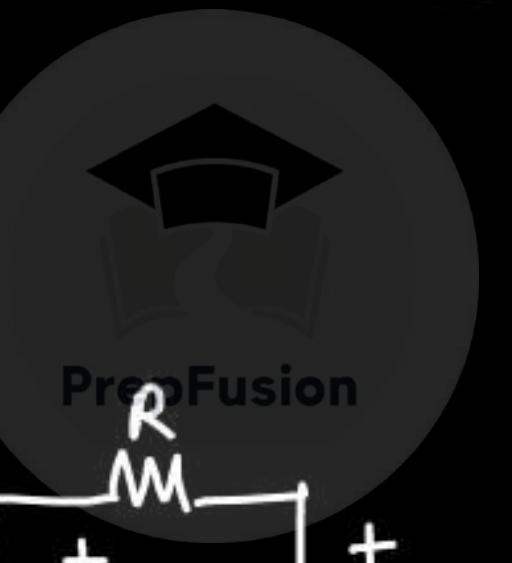


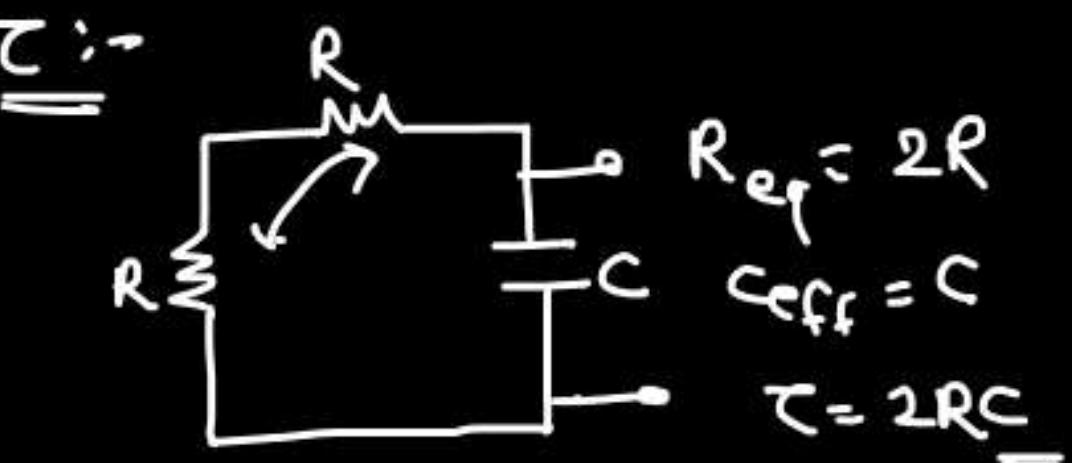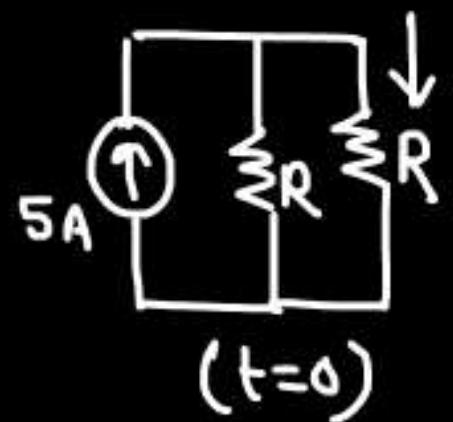
$$i_c : - \\ i_c(0^+) = 2 \cdot 5A \\ i_c(\infty) = 0 A$$



$$V_c(t) = 5R \left[1 - e^{-t/\tau} \right] v(t); \quad \tau = 2RC$$
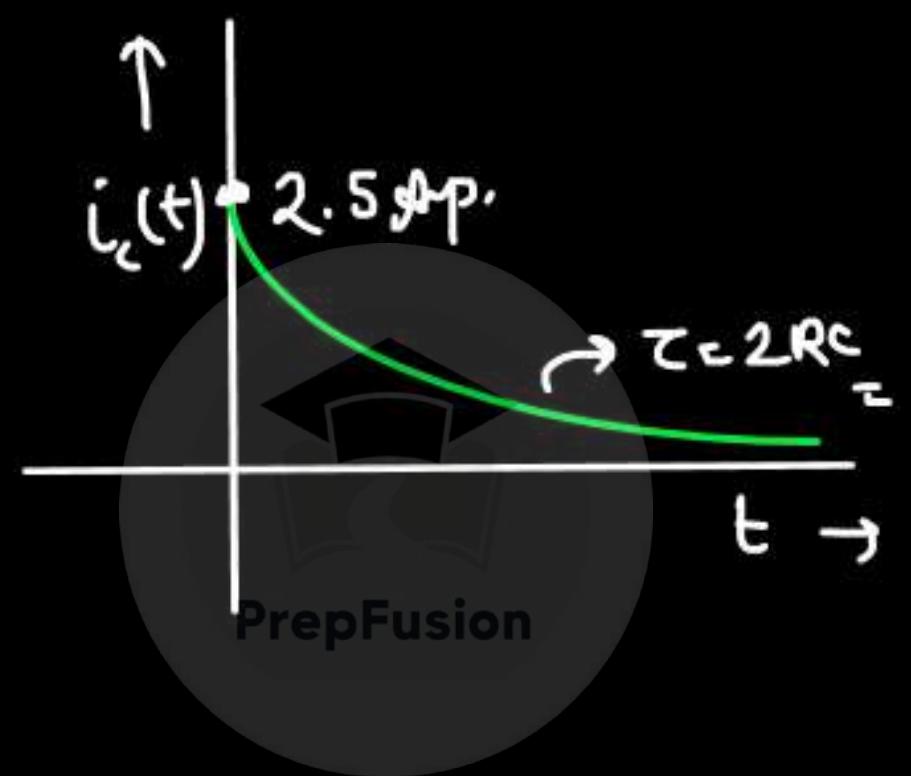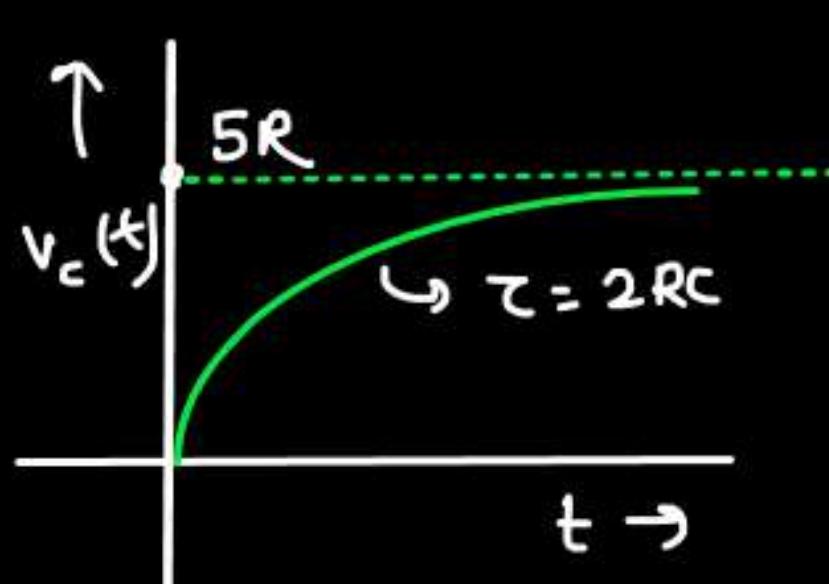
$$i_c(t) = 2.5 e^{-t/\tau} v(t); \quad \tau = 2RC$$



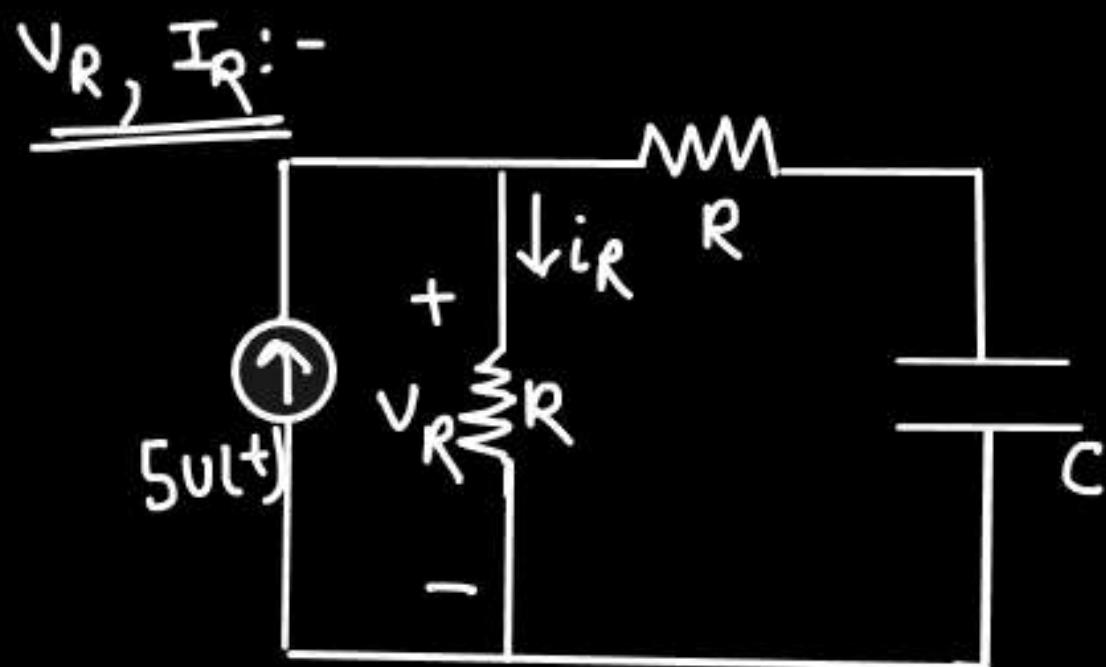

$$i_R(0^+) = 2.5 \text{ Amp}$$



$$i_R(\infty) = 5 \text{ Amp}$$

$$V_R(0^+) = 2.5R$$

$$V_R(\infty) = 5R$$

$$i_R(t) = 5 - 2.5 e^{-t/\tau_{0(t)}} ; \tau = 2RC$$
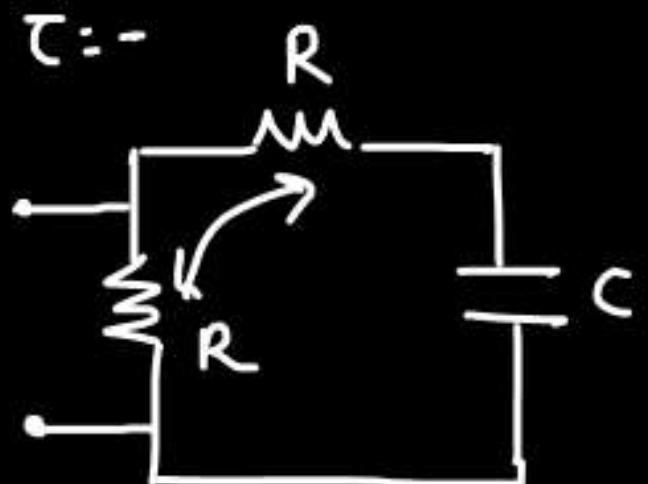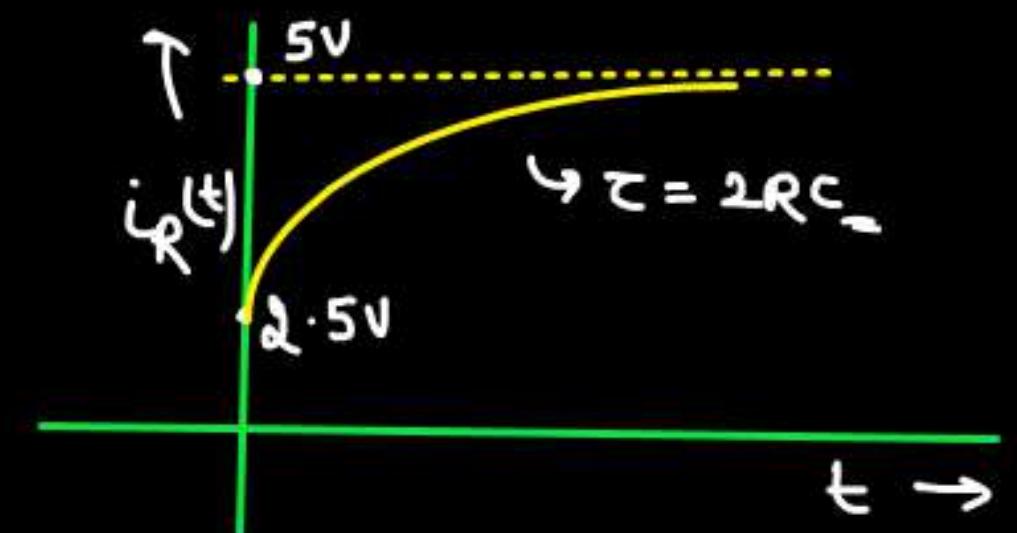
$$V_R(t) = 5R - 2.5R e^{-t/\tau_{0(t)}} ; \tau = 2RC$$





$$R_{eq} = 2R, C_{eff} = C$$

$$\tau = 2RC =$$




M-II :-

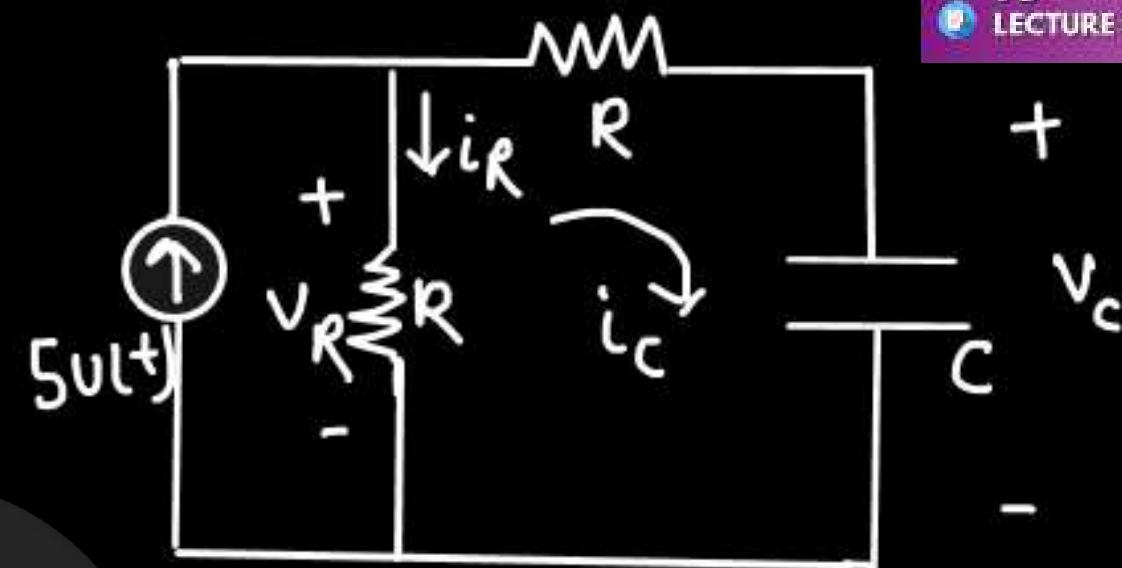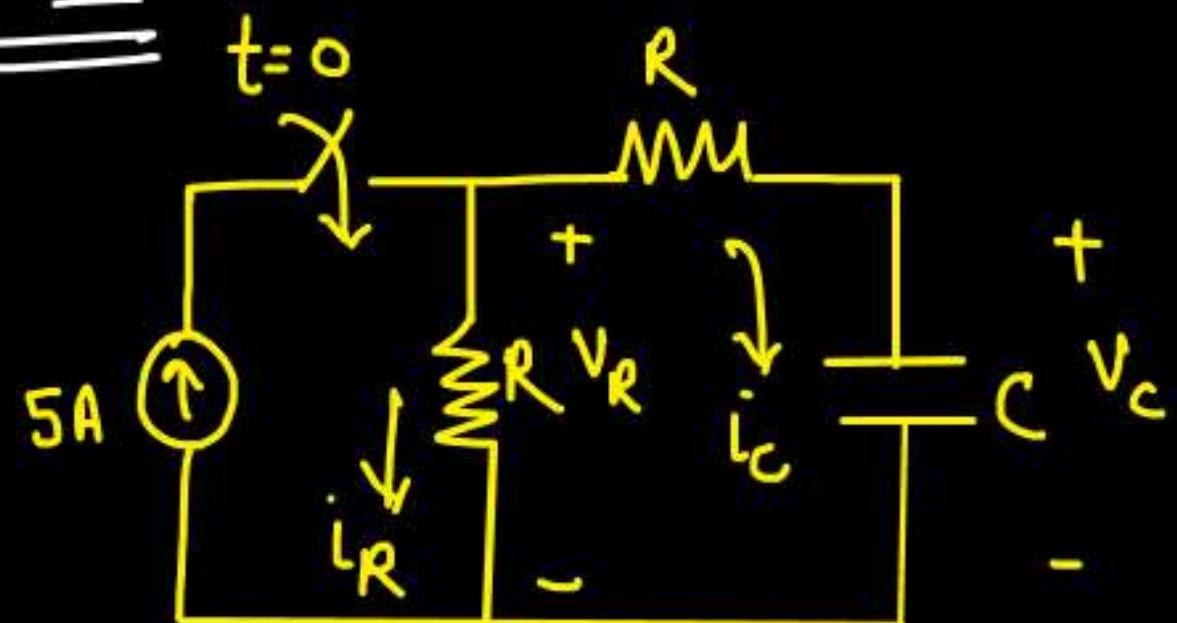

$$\begin{aligned} V_R' &= V_R \times X \\ i_R' &= i_R \times X \\ i_C' &= i_C \quad \checkmark \\ V_C' &= V_C \quad \checkmark \end{aligned}$$

Can't find V_R & i_R
from Source Transformation

↓ source Transformation


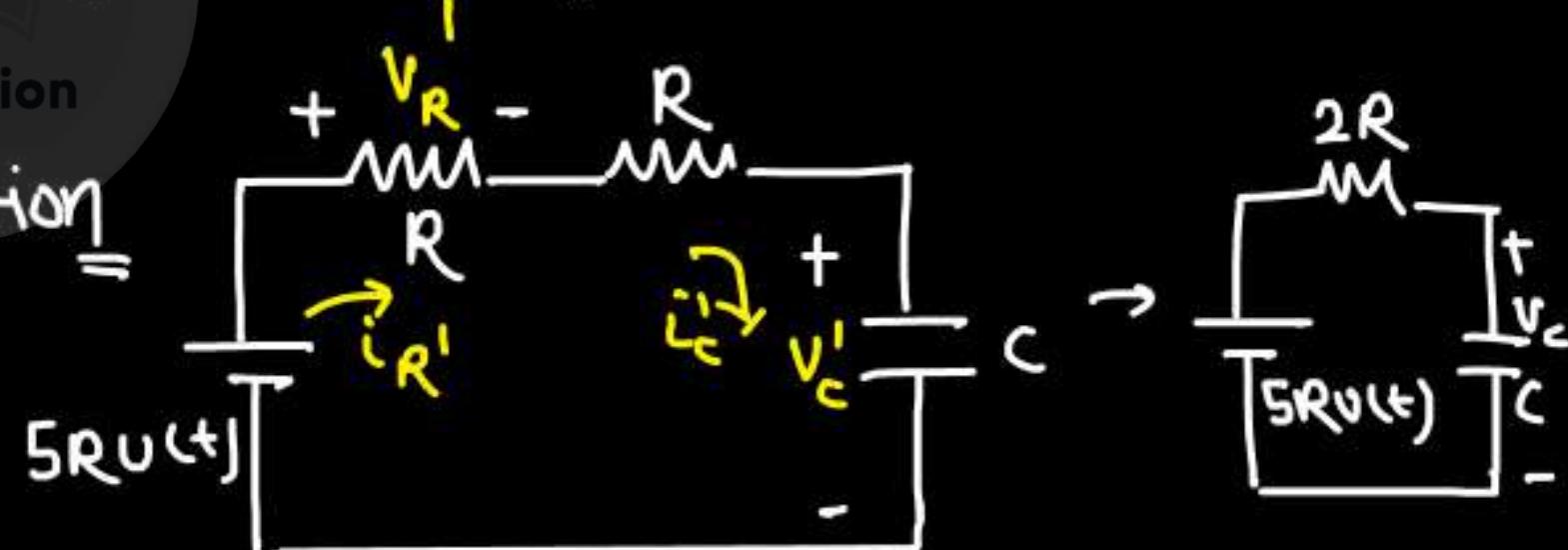


- (CL)
 • 100 HRS. CONTENT
 • 400+ QUESTIONS
 • LIVE DOUBT SESSIONS
 • 10+ TEST SERIES
 • LECTURE NOTES




AIR 27 (ECE)
AIR 45 (IN)

Q.

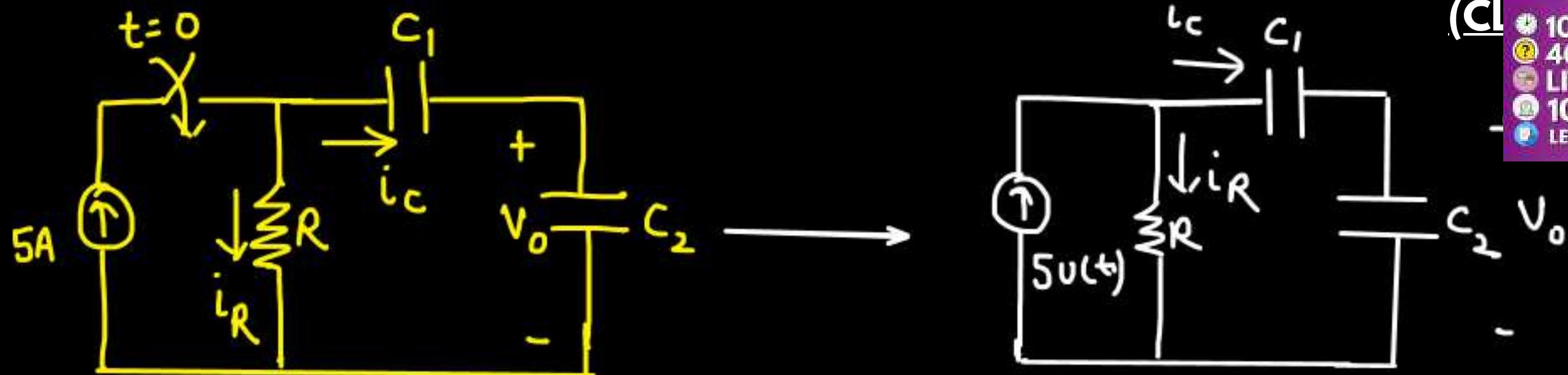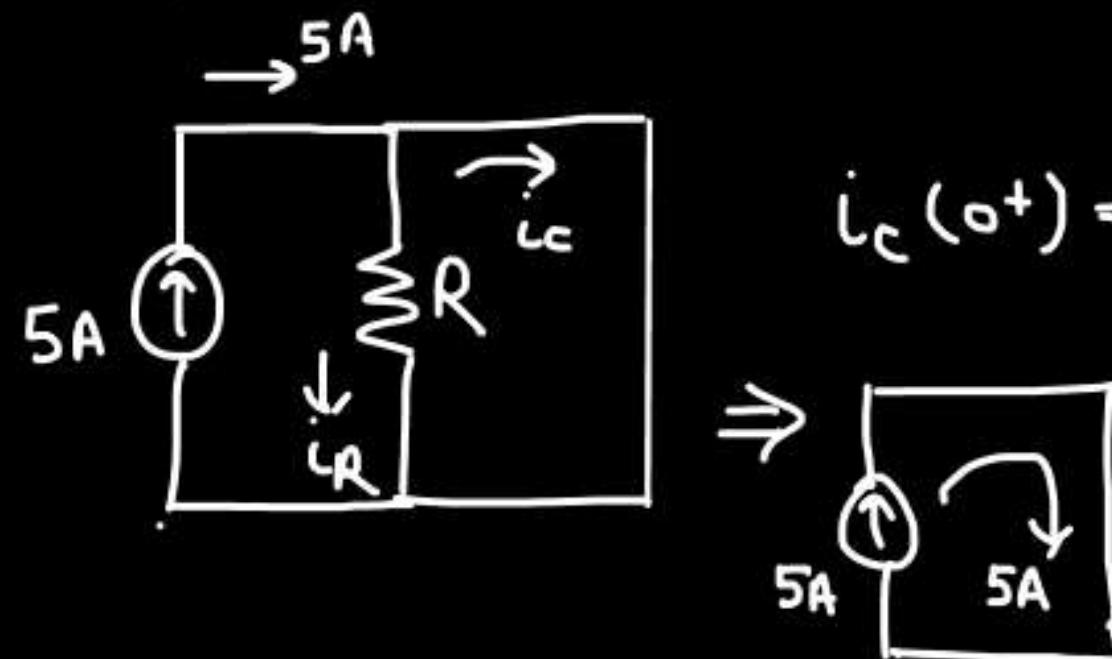CKT @ $t=0$ 

$$i_C(0^+) = 5A, \quad v_o(0^+) \approx 0V, \quad i_R(0^+) = 0 \text{ A.p.}$$

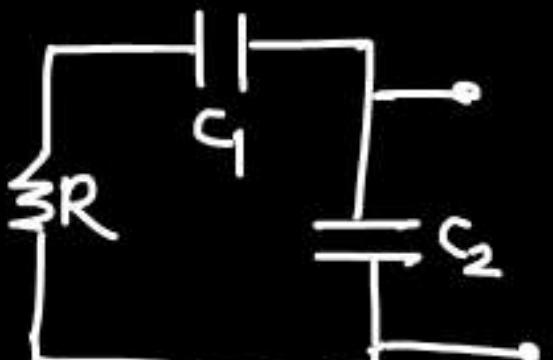 $\tau_c ?$ 

$$C_{eff} = \frac{C_1 C_2}{C_1 + C_2}$$

$$R_{eq} = R$$



$$\tau = \frac{RC_1 C_2}{C_1 + C_2}$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

ckt @ $t = \infty$

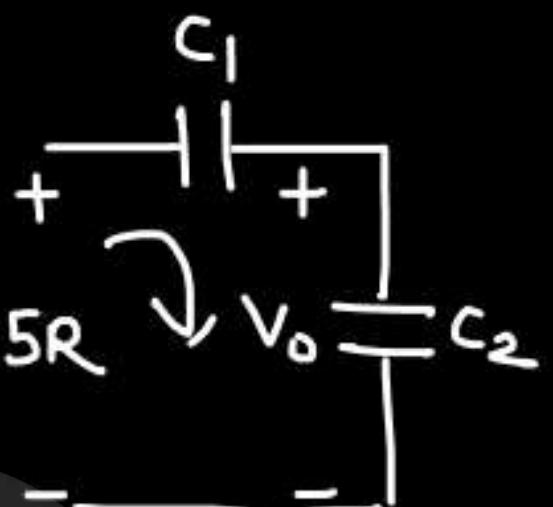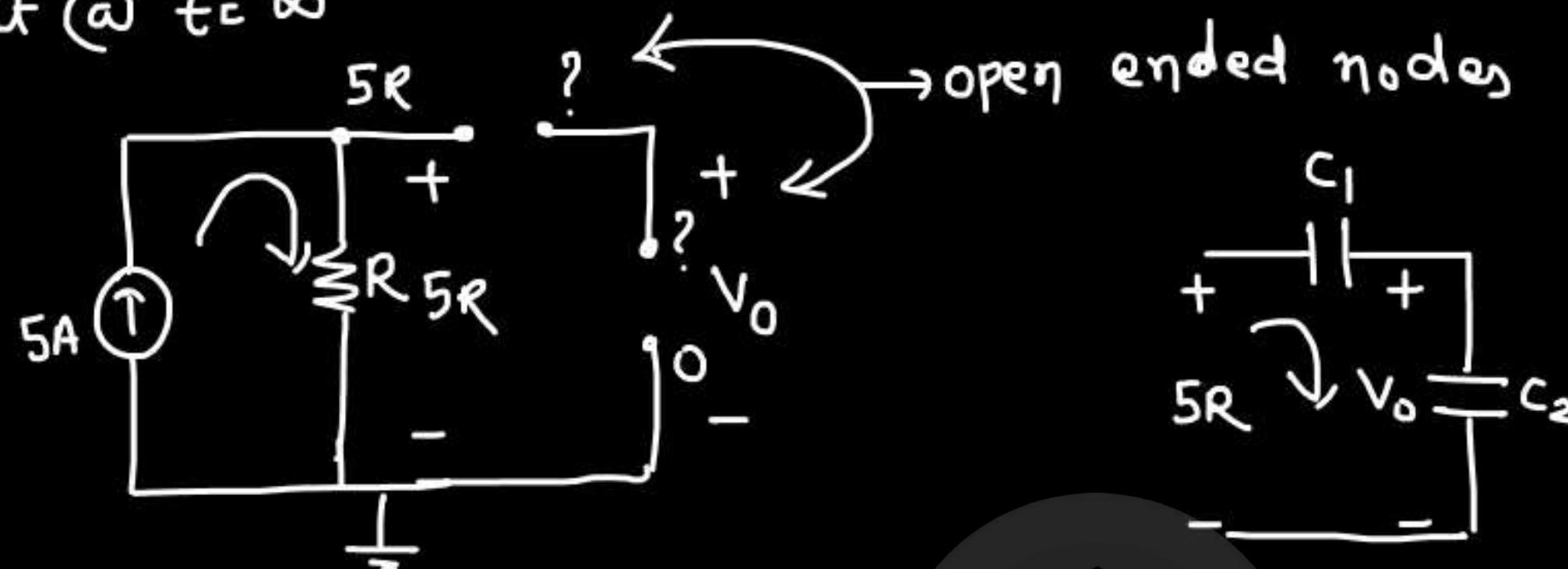




$$V_o(\infty) = \frac{5RC_1}{C_1 + C_2}, \quad i_c(\infty) = 0 \text{ A.P.}, \quad i_R(\infty) = 5 \text{ A.P.}$$

$$i_c(t) = 5e^{-t/\tau} u(t) \text{ A.P.}$$

$$V_o(t) = \frac{5RC_1}{C_1 + C_2} \left[1 - e^{-t/\tau} \right] u(t) \text{ V}$$

$$i_R(t) = 5 \left[1 - e^{-t/\tau} \right] u(t) \text{ A.P.}$$

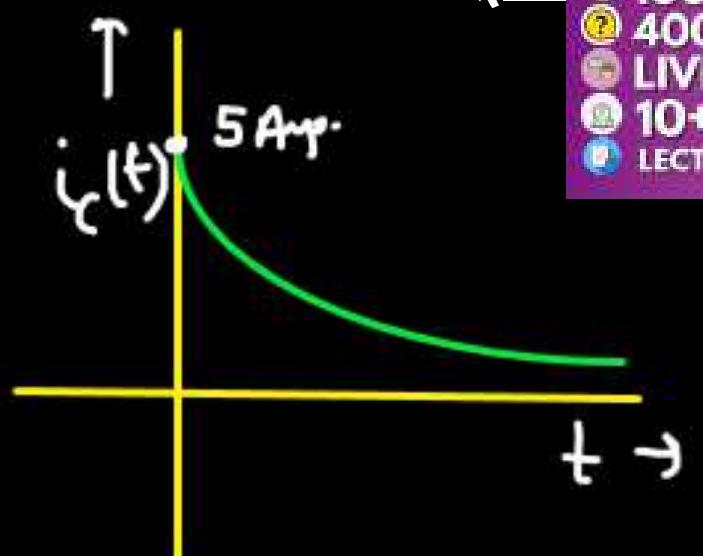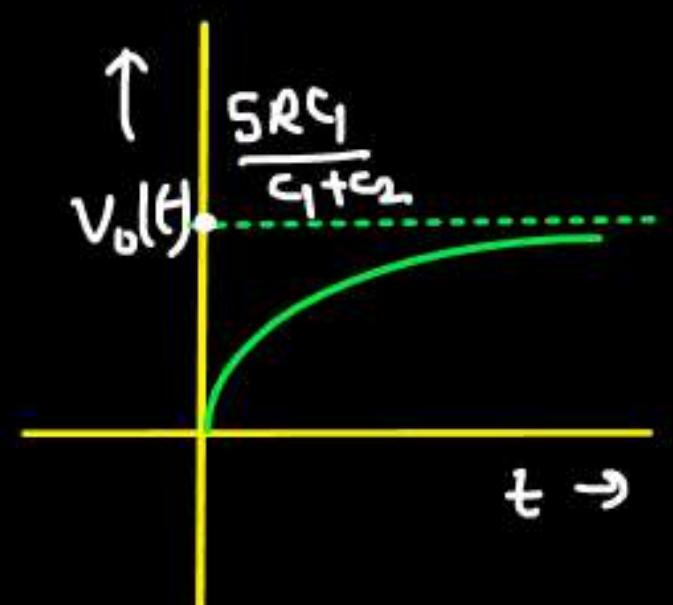
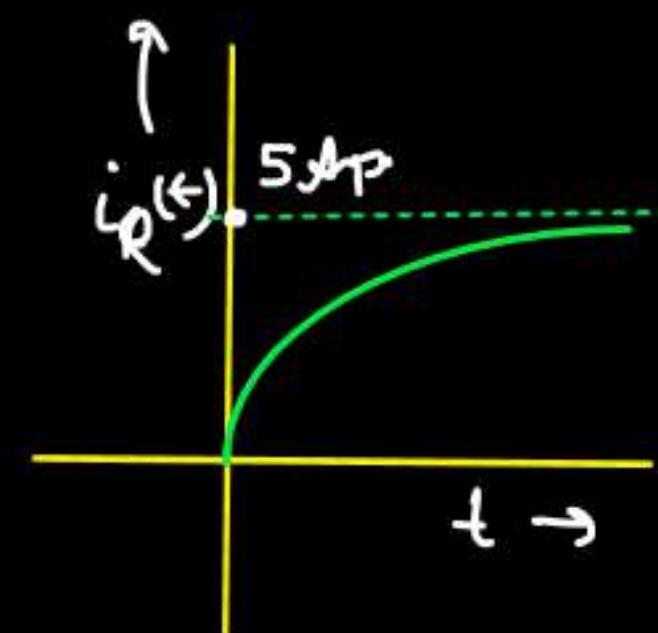
- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES






More Examples of RC ckt's :-

Q.

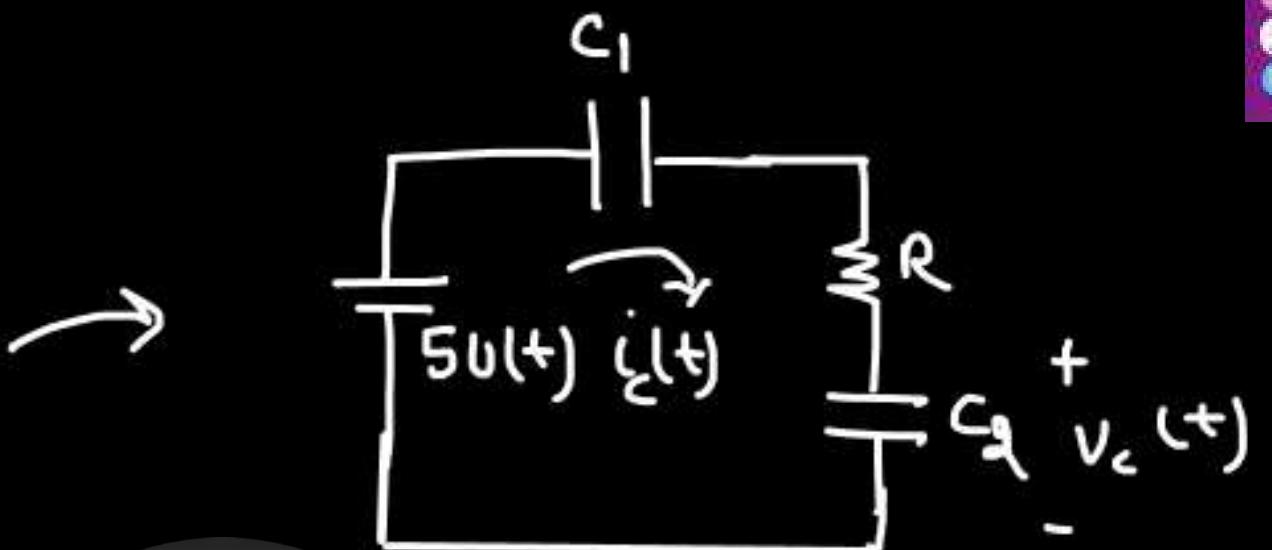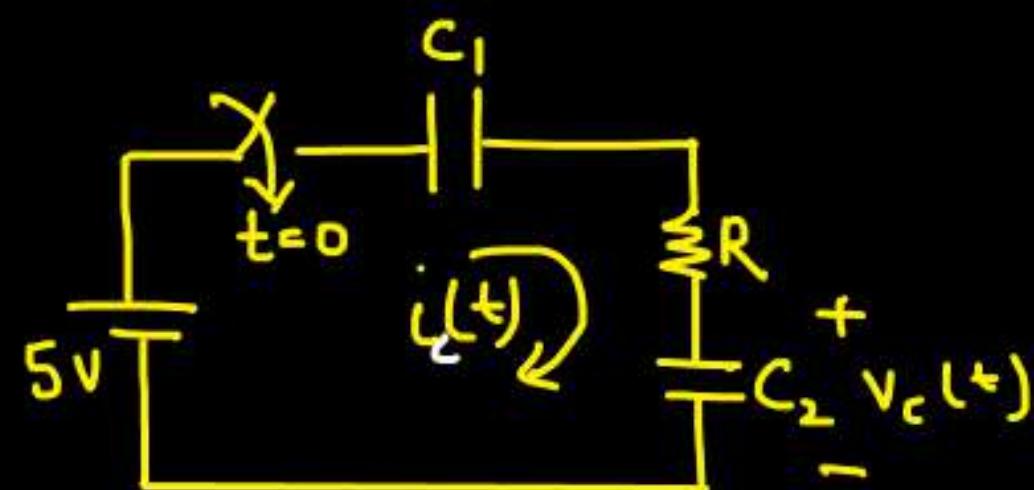

$$\rightarrow \tau = ?$$

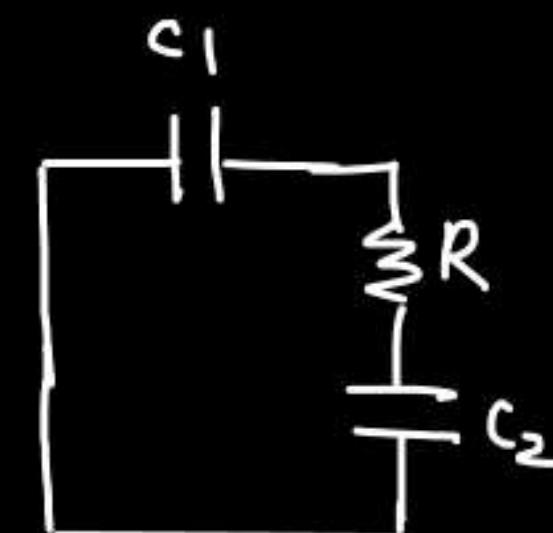


$$R_{eq} = R$$

$$C_{eff} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\tau = \frac{RC_{eq}}{C_1 + C_2}$$

$$i(0^+) = \frac{5}{R} \text{ A} ; \quad v_c(0^+) = 0 \text{ V}$$

ckt @ $t = \infty$

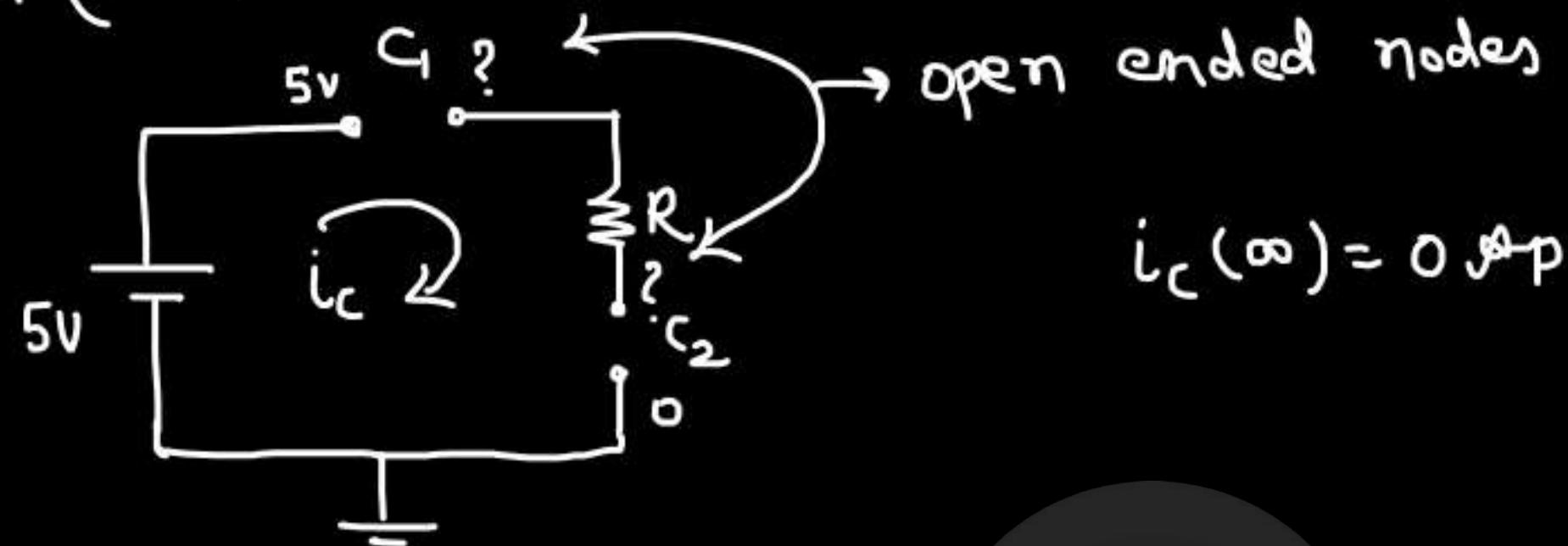


$$i_C(\infty) = 0 \text{ A.p.}$$

@ $t = \infty \Rightarrow$ steady state $\Rightarrow \omega = 0 \Rightarrow Z_C = \frac{1}{j\omega C} = \infty \Rightarrow$ impedance by capacitor is very High



equivalent ckt @ $t = \infty$

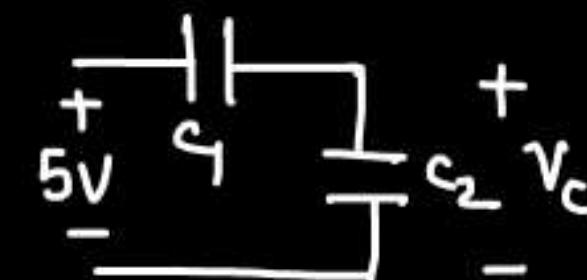

$$V_C(\infty) = \frac{5C_1}{C_1 + C_2}$$

$$V_C(0^+) = 0 \text{ V} ; \quad V_C(\infty) = \frac{5C_1}{C_1 + C_2}$$



$$I_C(0^+) = \frac{5}{R} \text{ A} ; \quad I_C(\infty) = 0 \text{ A}$$

$$V_C(t) = \frac{5C_1}{C_1 + C_2} \left(1 - e^{-t/\tau} \right) v(t)$$

$$I_C(t) = \frac{5}{R} e^{-t/\tau} v(t)$$


$$\tau = \frac{RC_2}{C_1 + C_2}$$

PrepFusion

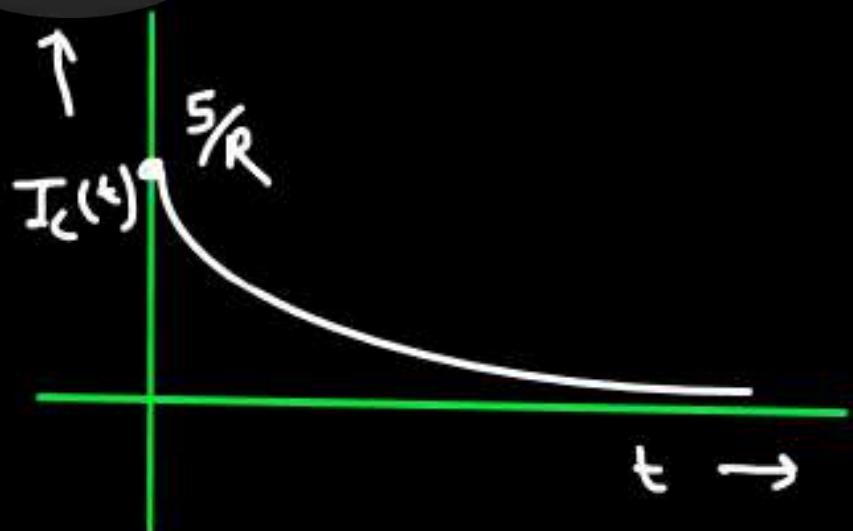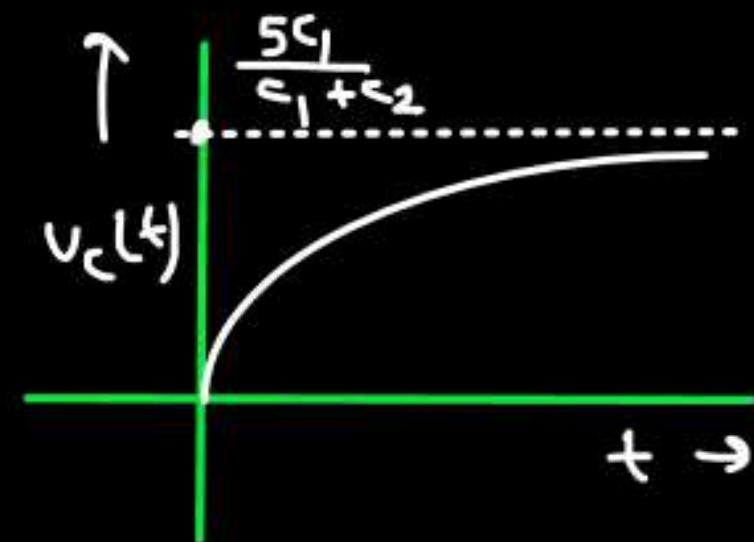



Q.

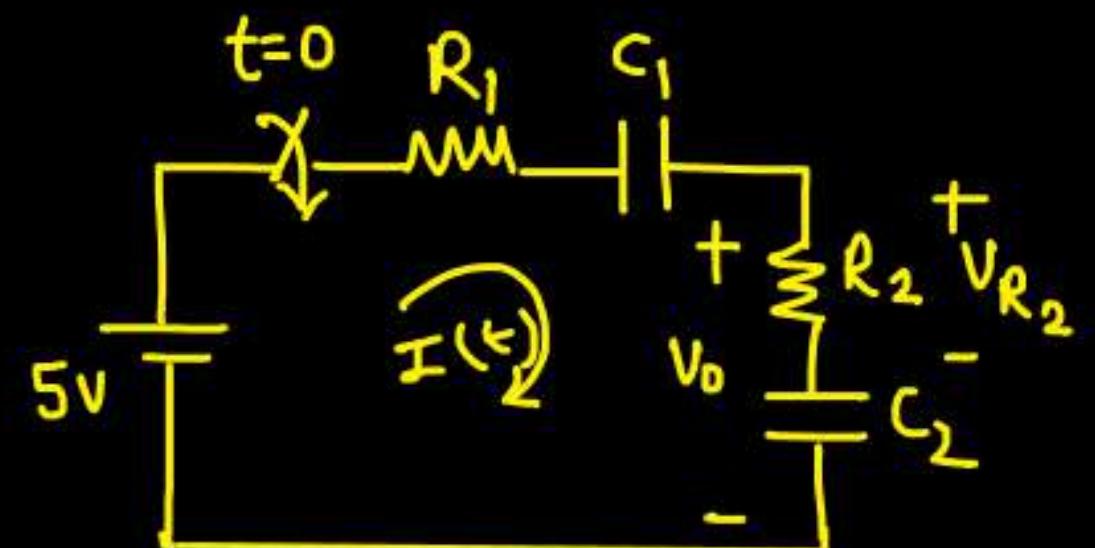

→

$$\tau = ?$$

$$R_{eq} = R_1 + R_2$$


$$C_{eff} = \frac{C_1 C_2}{C_1 + C_2}$$

$\tau = (R_1 + R_2) \frac{C_1 C_2}{C_1 + C_2}$


at $t=0$:-

$$I(0^+) = \frac{5}{R_1 + R_2} ; \quad V_0(0^+) = \frac{5R_2}{R_1 + R_2} ; \quad V_{R_2}(0^+) = \frac{5R_2}{R_1 + R_2}$$

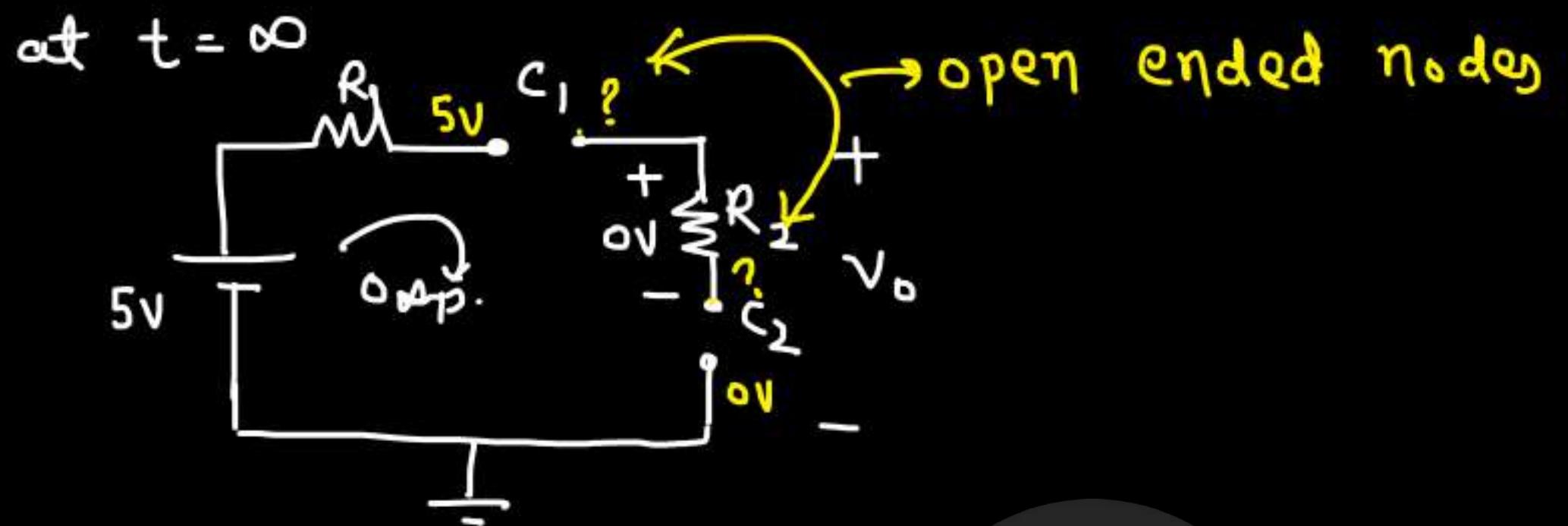- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



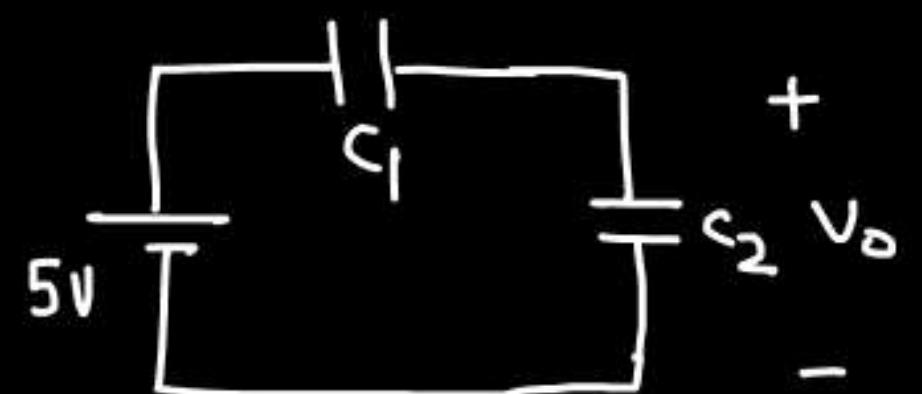@ $t = \infty \Rightarrow \omega = 0 \Rightarrow$





PrepFusion

$$V_{R_2}(\infty) = 0V$$

$$V_o(\infty) = \frac{5C_1}{C_1 + C_2}$$

$$I(\infty) \approx 0 \text{ Aamp.}$$

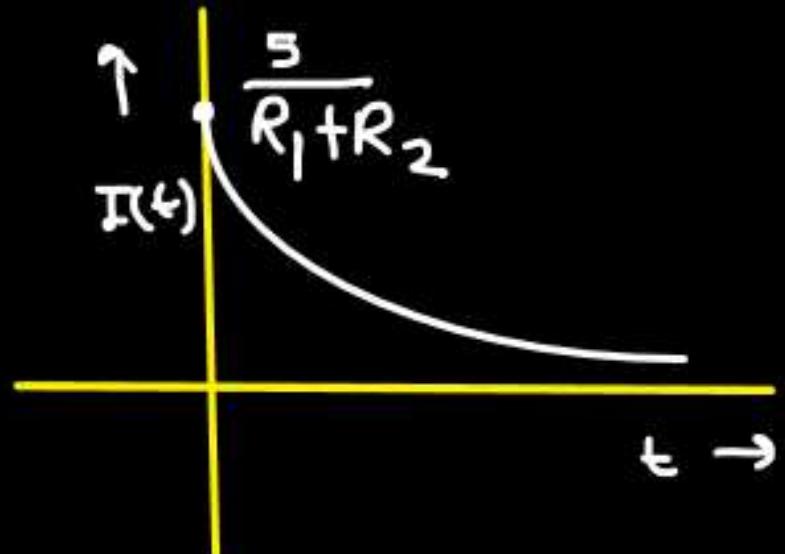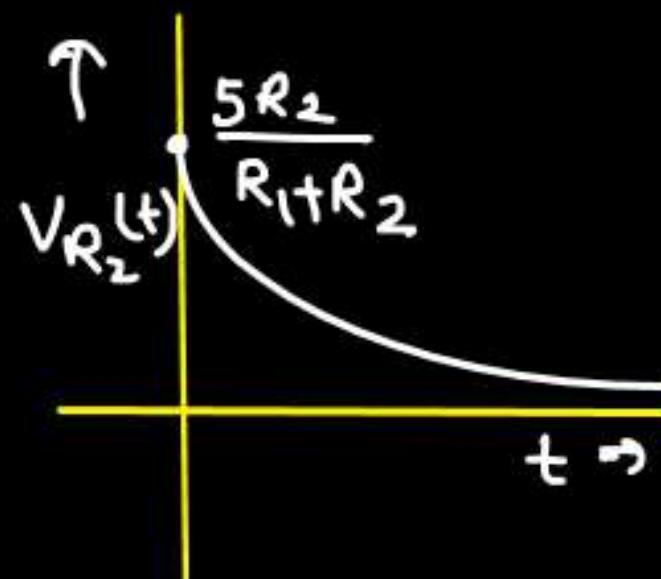




$$V_o(0^+) = \frac{5R_2}{R_1 + R_2}$$

$$= \frac{5}{1 + R_1/R_2}$$

$$V_o(\infty) = \frac{5C_1}{C_1 + C_2}$$




$$= \frac{5}{1 + C_2/C_1}$$


PrepFusion

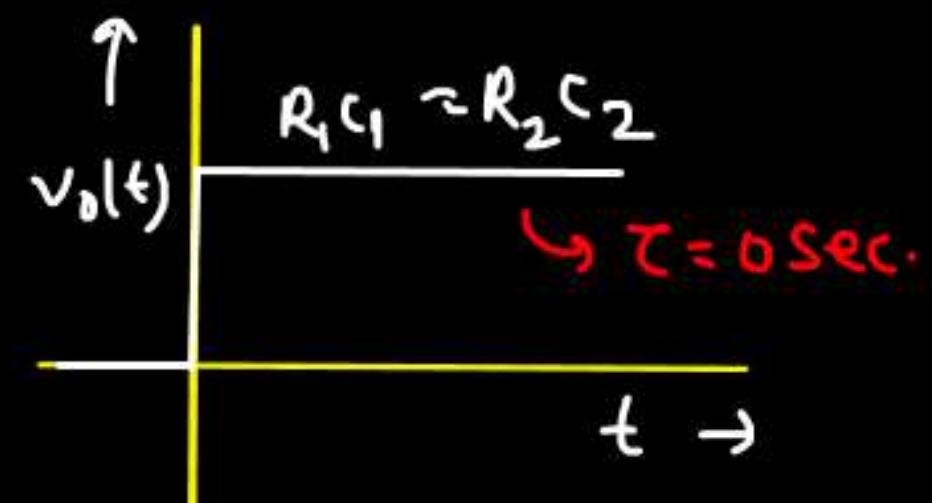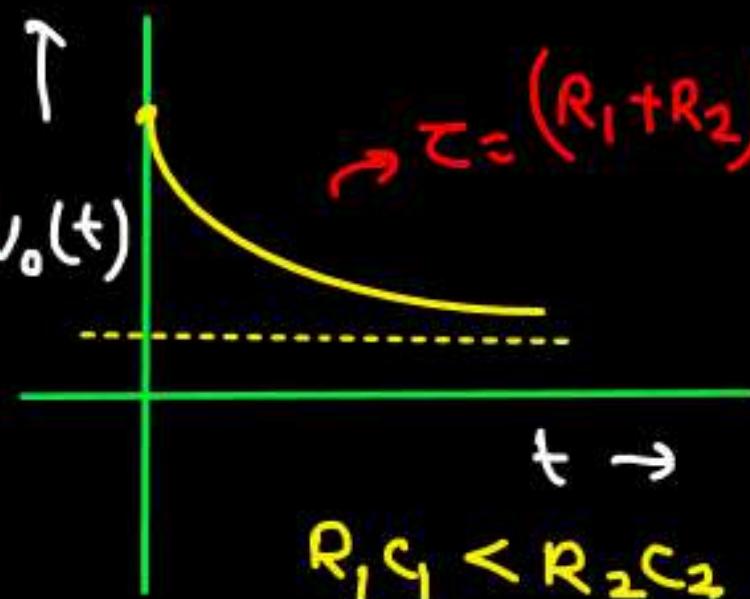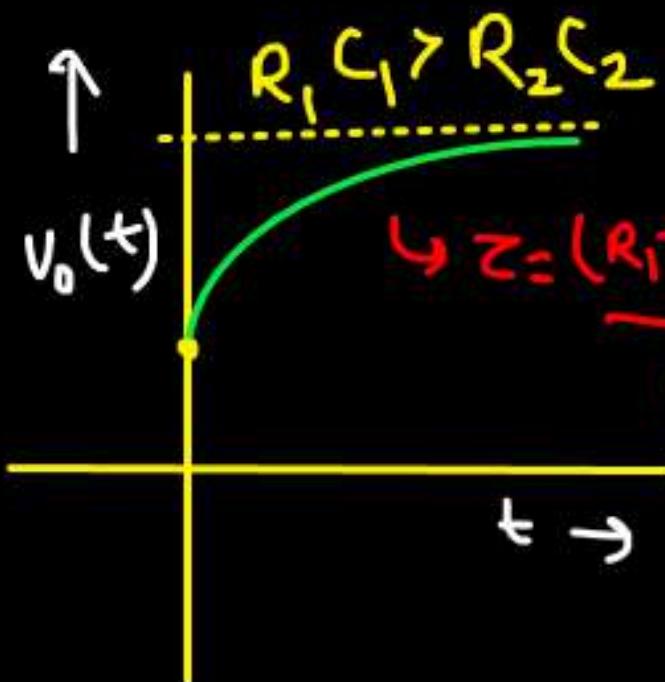


Q. In the given ckt Cap. C_1 is already charged to

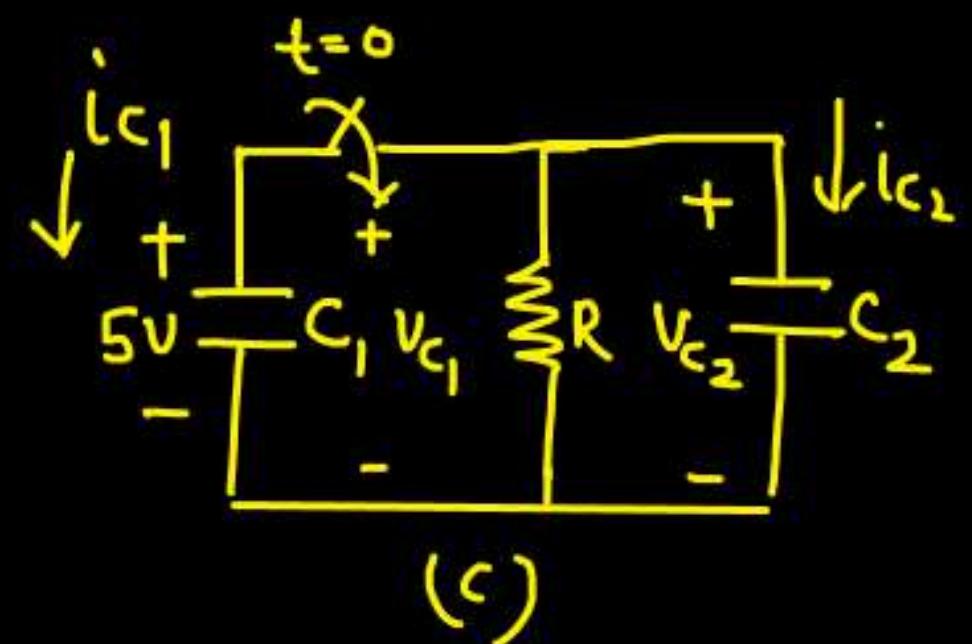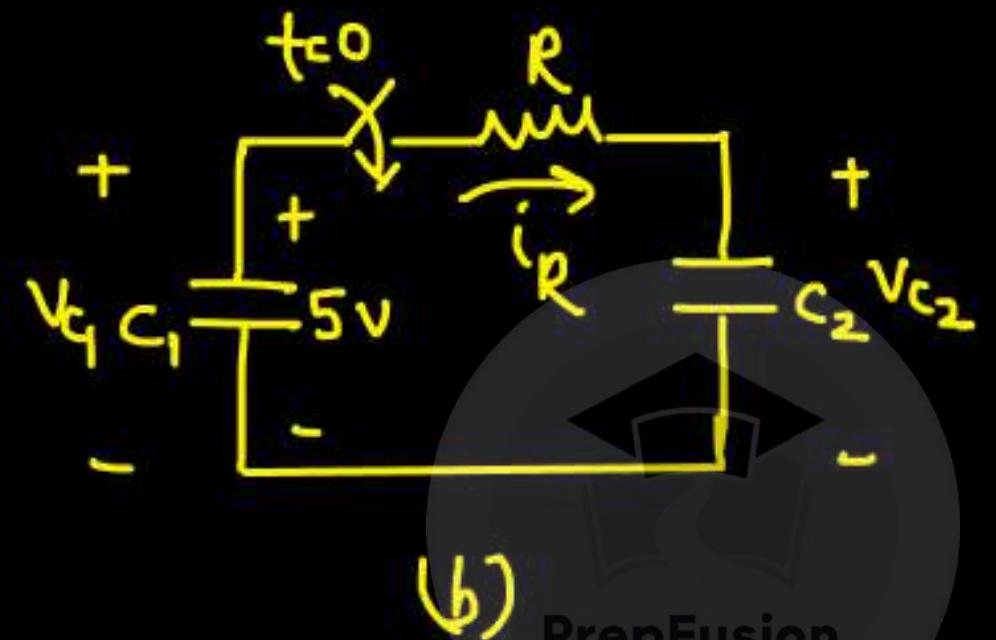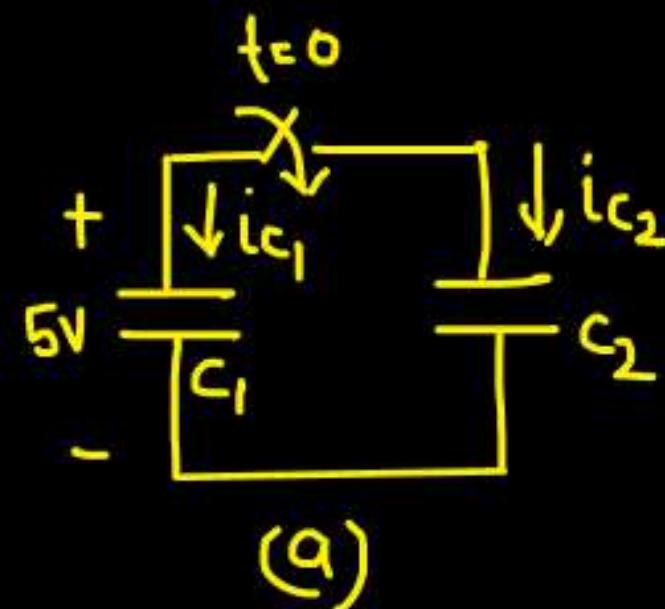5V. Find V_{C_1} , V_{C_2} , V_R , i_{C_1} , i_{C_2} and i_R .



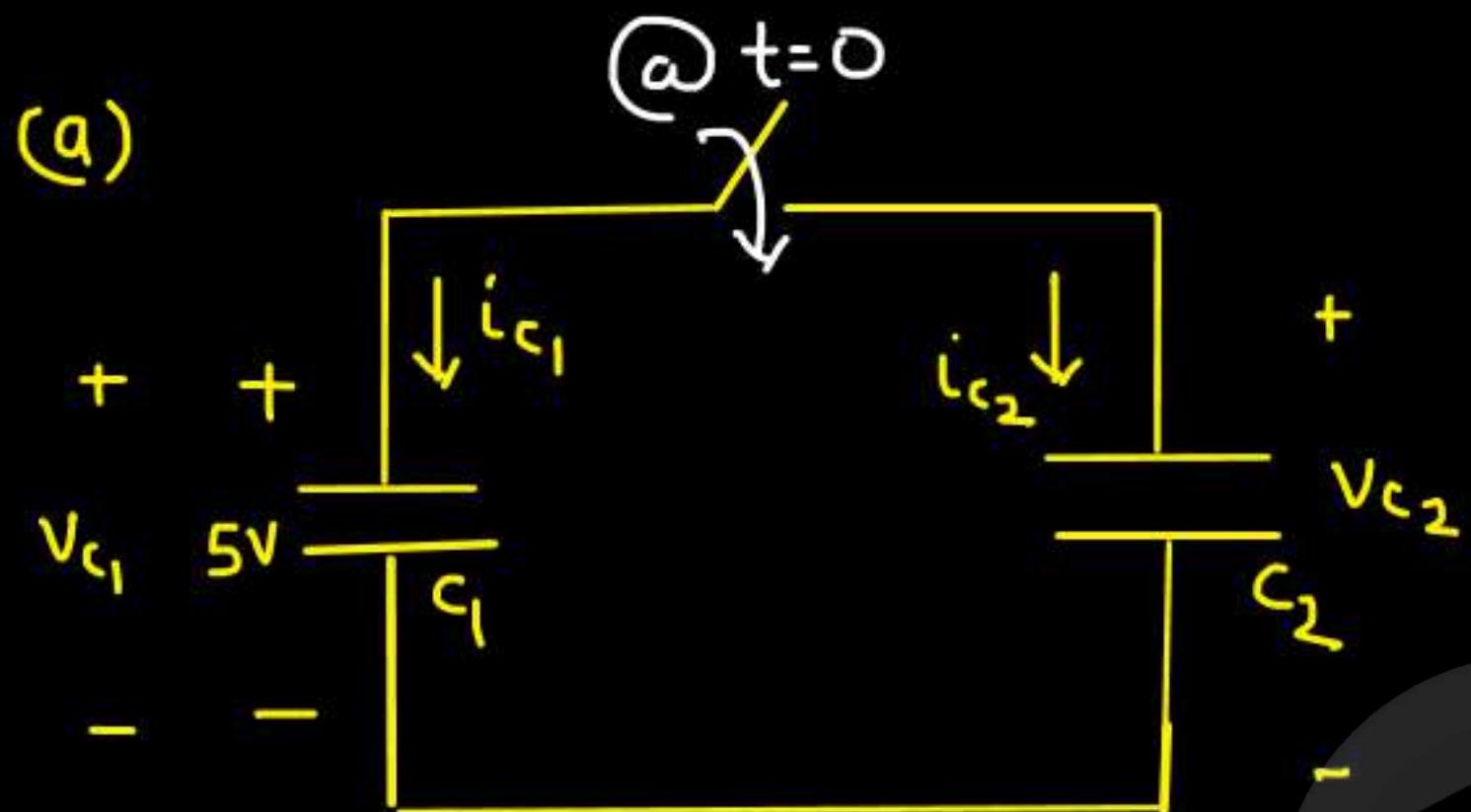


Ckt @ t=0

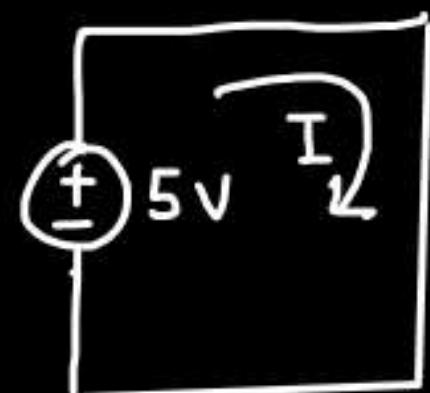

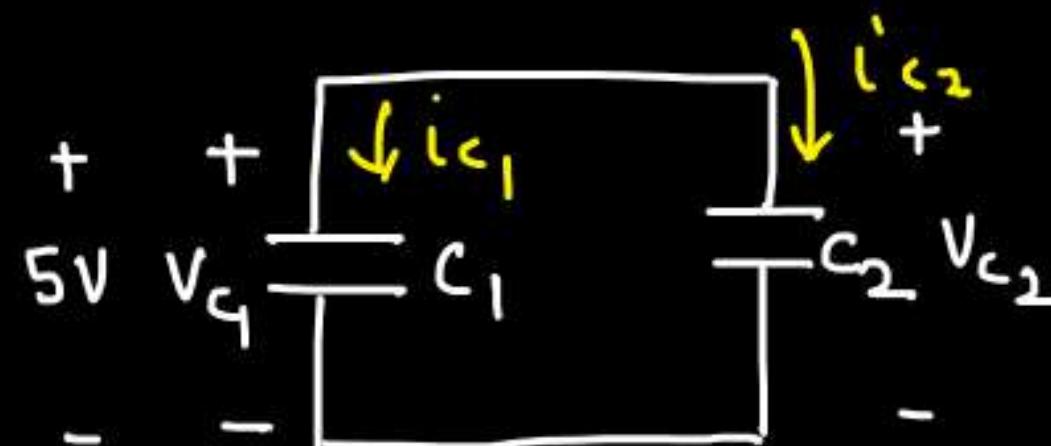$I = \frac{5}{0} = \infty \Rightarrow$ impulse current \Rightarrow sudden change in cap. voltage







charge conservation;

charge before switching = charge after switching

$$5C_1 = C_1 V_{C_1} + C_2 V_{C_2}$$

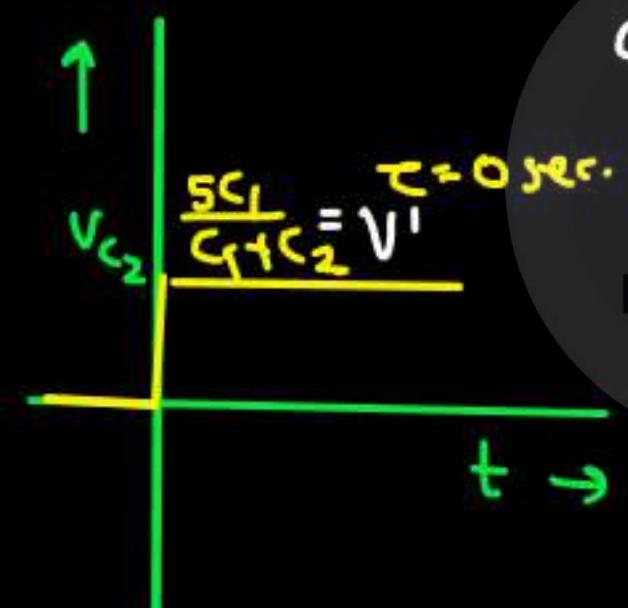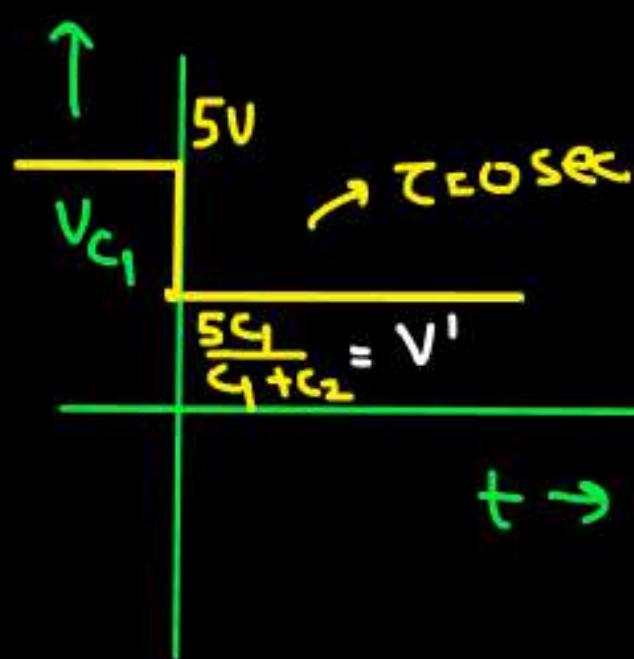


after switching, $V_{C_1} = V_{C_2} = V_C$

$$5C_1 = (C_1 + C_2) V_C$$

$$V_C = \frac{5C_1}{C_1 + C_2}$$

$$i_{C_1} = -i_{C_2}$$

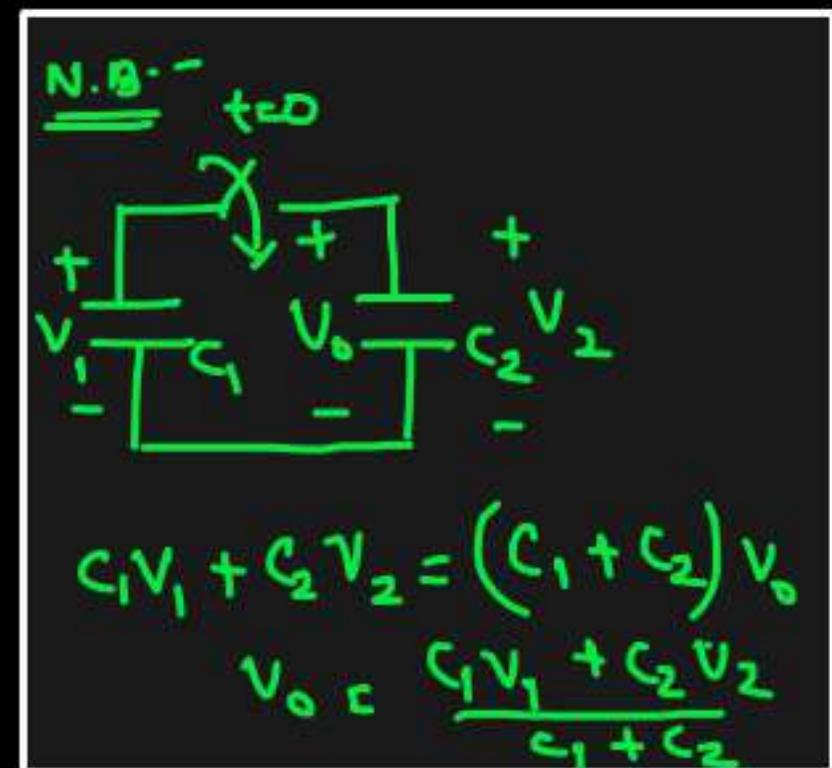



100 HRS. CONTENT
400+ QUESTIONS
LIVE DOUBT SESSIONS
10+ TEST SERIES
LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

C_1 cap. is getting discharged \Rightarrow Current flowing out of the cap. ($i_{C_1} \rightarrow$ negative)

C_2 cap. is getting charged \Rightarrow Current flowing into the cap. ($i_{C_2} \rightarrow$ positive)

$$i_{C_1}(t) = -\frac{5C_1C_2}{C_1+C_2} \delta(t)$$


$$C_1[V^I - 5] = -\frac{5C_1C_2}{C_1+C_2}$$

$$i_{C_2}(t) = \frac{5C_1}{C_1+C_2} \delta(t)$$


$$i_{C_1} = -i_{C_2}$$

$$V^I = \frac{5C_1}{C_1+C_2}$$

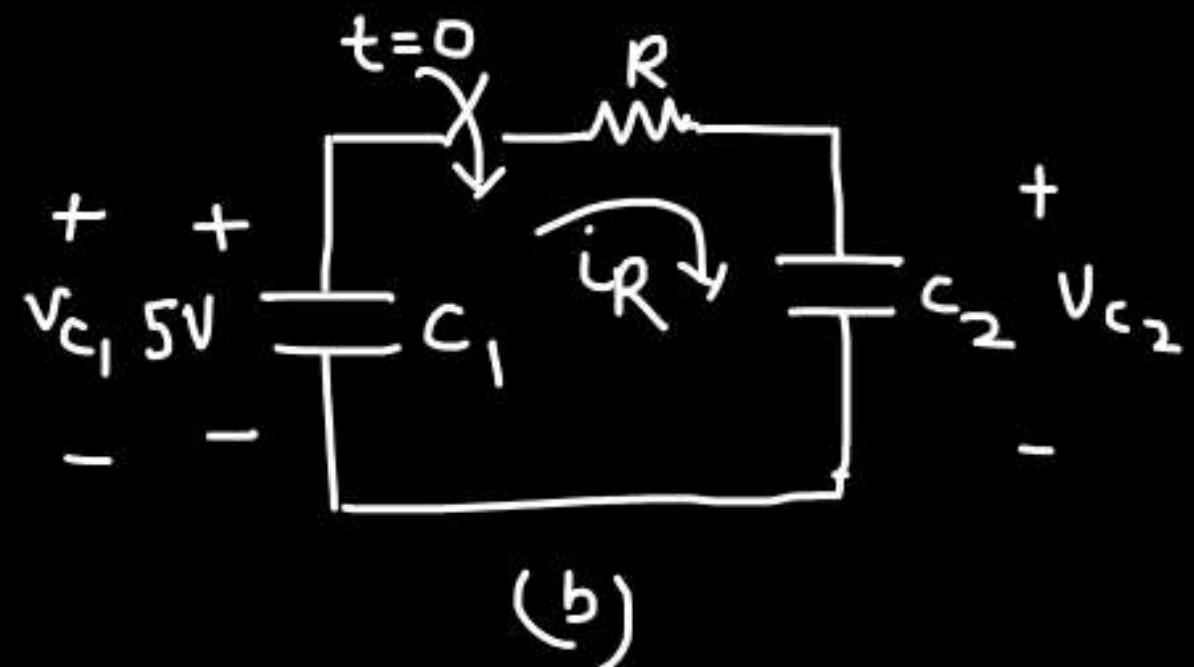YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)



Ckt @ $t=0$

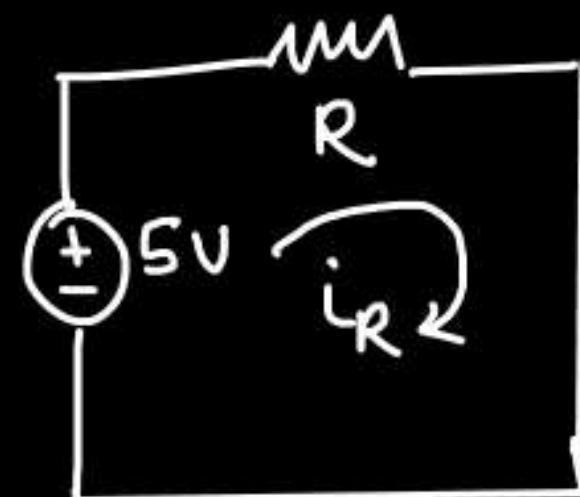


$i_R(0^+) = \frac{5}{R} \neq \infty$

$V_{c_1}(0^+) = 5V , V_{c_2}(0^+) = 0V$



after $t=0^+$

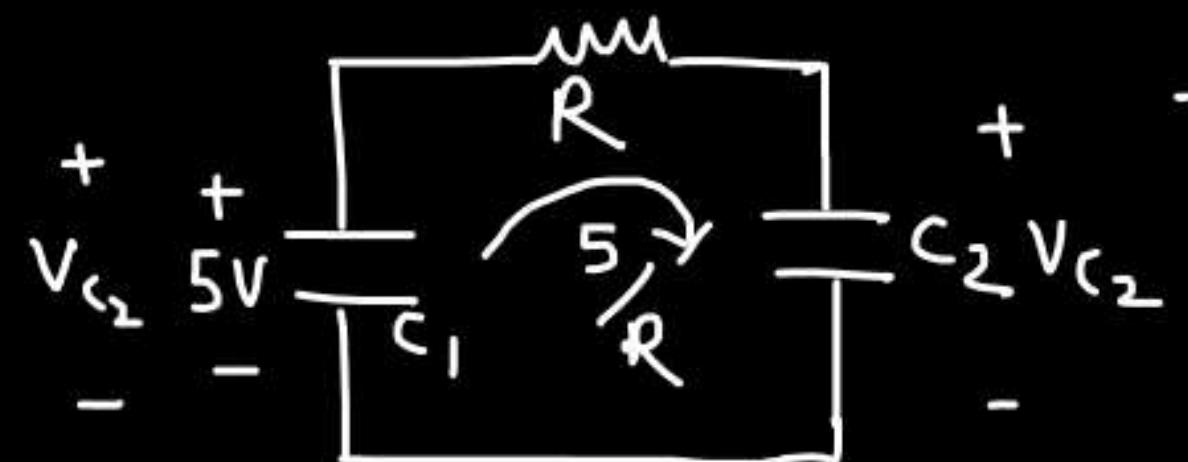

$\Rightarrow \frac{5}{R}$ current charges C_2
and discharges C_1



This charging and discharging

will go on until $i_R = 0$



PrepFusion

if $V_{C1} = V_{C2} = V_C \Rightarrow i_R = 0$ ~~App.~~



no current through
cap.

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES




$\Rightarrow @ \text{ steady state } V_{C_1}(\infty) = V_{C_2}(\infty) = V_C$

Apply charge conservation;

$$5C_1 = (C_1 + C_2) V_C$$

$$V_C = \frac{5C_1}{C_1 + C_2} = V_{C_1}(\infty) = V_{C_2}(\infty)$$

$$\tau = ?$$

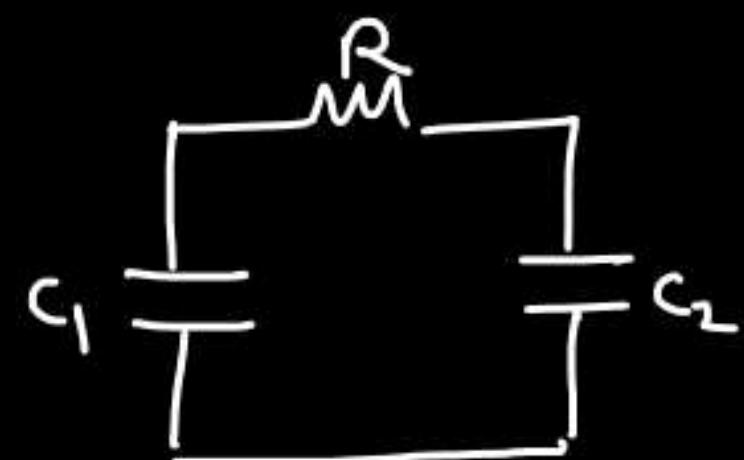




PrepFusion

$$C_{\text{eff}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$R_{\text{eq}} = R$$

$$\tau = \frac{RC_1 C_2}{C_1 + C_2}$$

$$I_R(\infty) = 0 \text{ A}$$

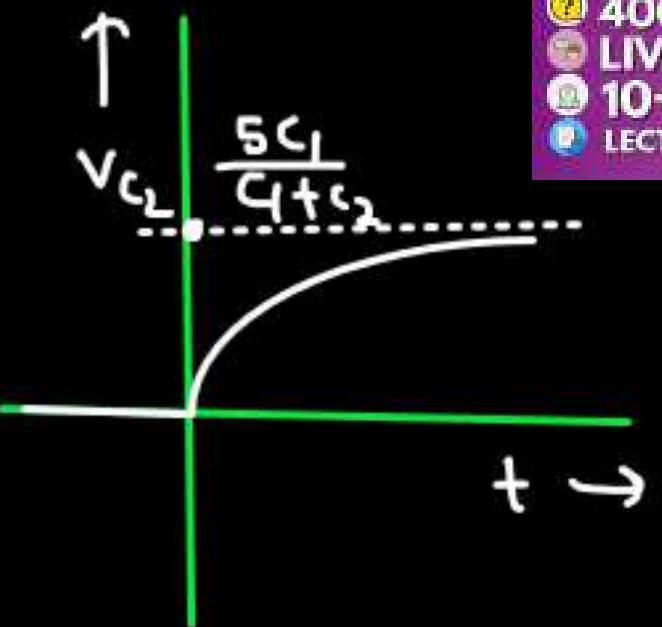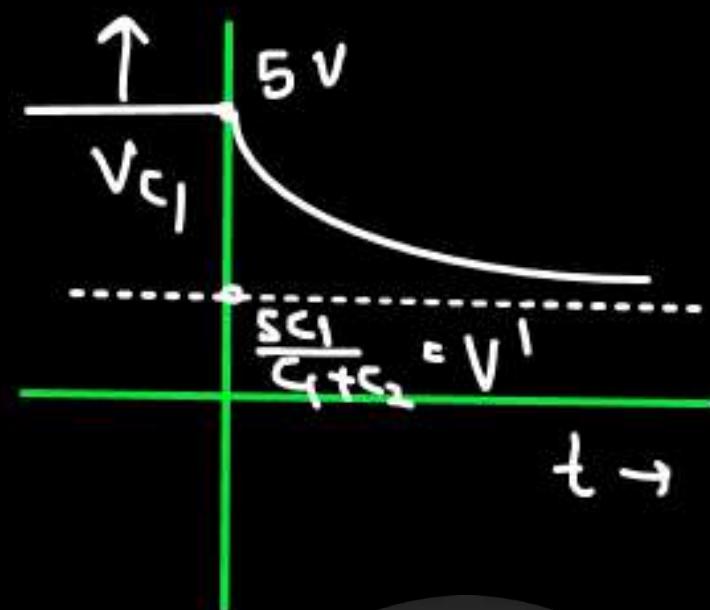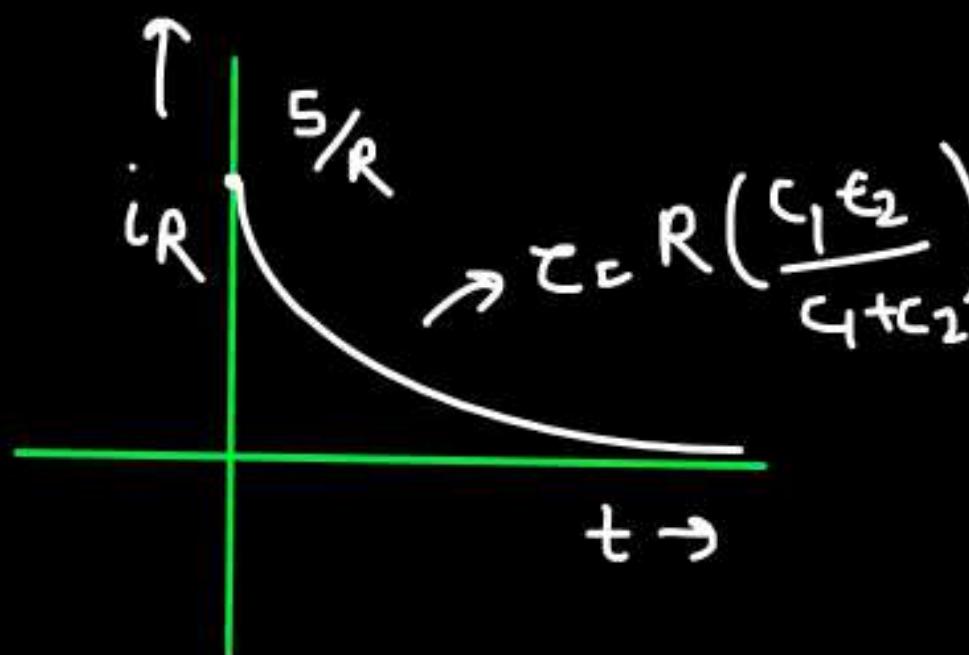


$$i_R = \frac{5}{R} e^{-t/\tau_C} u(t)$$

PrepFusion

$$V_{C1}(t) = [V' + (5 - V') e^{-t/\tau_C}] u(t), \quad V_{C2} = \frac{5V}{C_1 + C_2} (1 - e^{-t/\tau_C}) u(t)$$
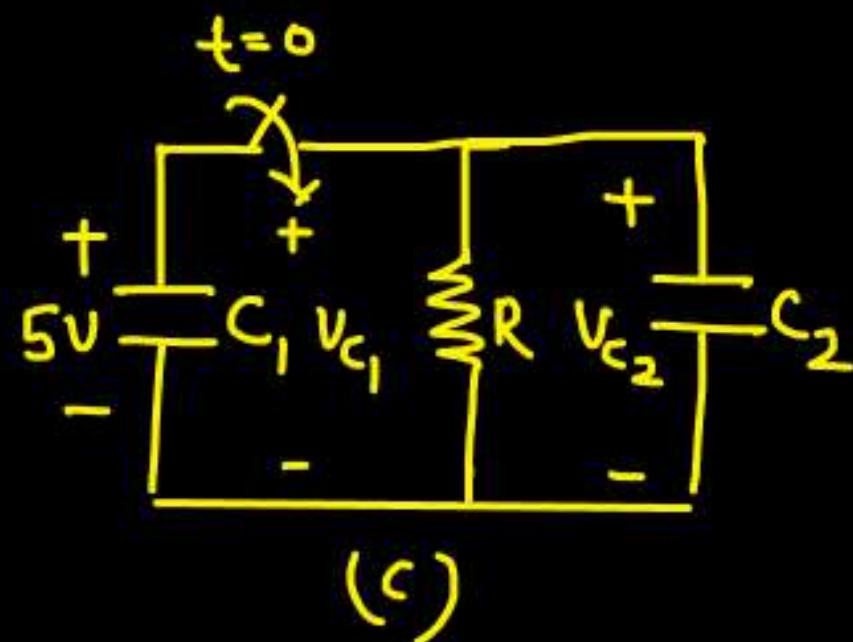
$$= \left[\frac{5C_1}{C_1 + C_2} + \frac{5C_2}{C_1 + C_2} e^{-t/\tau_C} \right] u(t)$$



ckt @ $t=0$

$5V$

i_{C_1}

R

i_{C_2}

i_R

$$i_{C_1} = -i_{C_2} = \frac{5}{R} = \infty \text{ A p.}$$


↳ impulsive current

@ $t=0^+$; $V_{C_1}(0^+) = V_{C_2}(0^+) = V_C$

$$\frac{5C_1}{C_1 + C_2} = V_C$$



after $t=0^+$

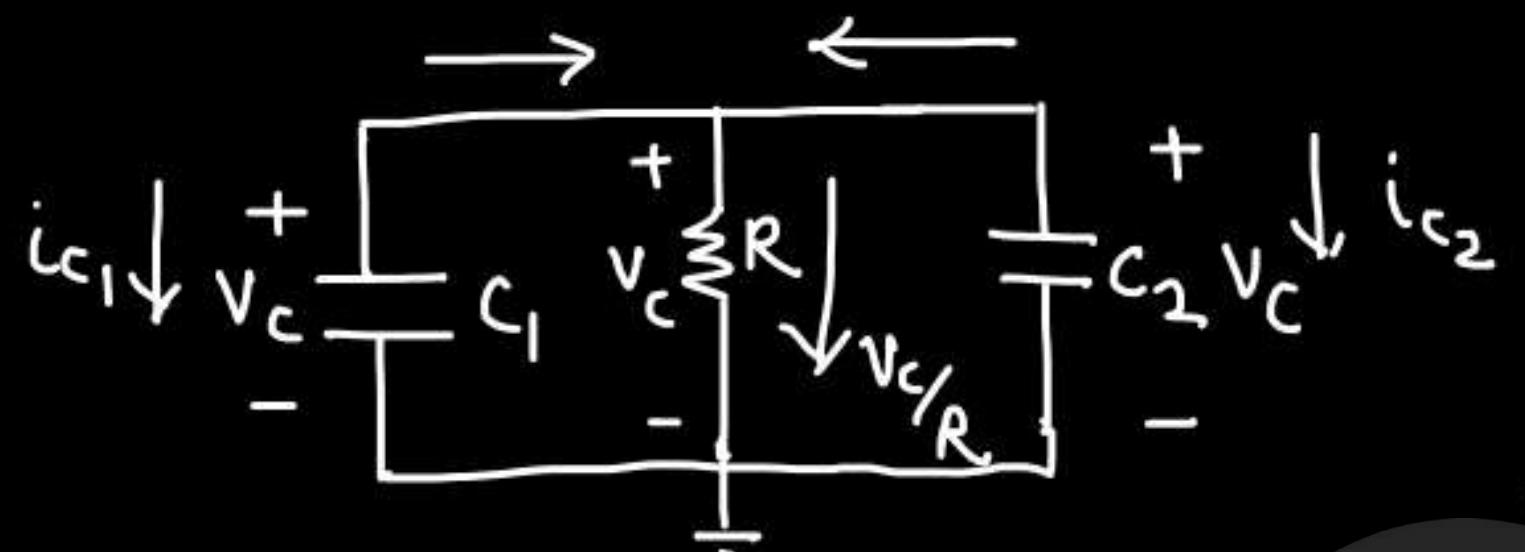

$$i_{C_1}(0^+) = -\frac{V_C}{R} \times \frac{C_1}{C_1 + C_2}$$

$$i_{C_2}(0^+) = -\frac{V_C}{R} \times \frac{C_2}{C_1 + C_2}$$

$$i_R(0^+) = \frac{V_C}{R}$$

From both of the cap., current is flowing outward




Both of the cap. are getting discharged.

The cap. will charge until i_{C_1} and i_{C_2} goes to zero

\Rightarrow if i_{C_1} and i_{C_2} goes to zero $\Rightarrow i_R$ goes to zero

@ steady state ;

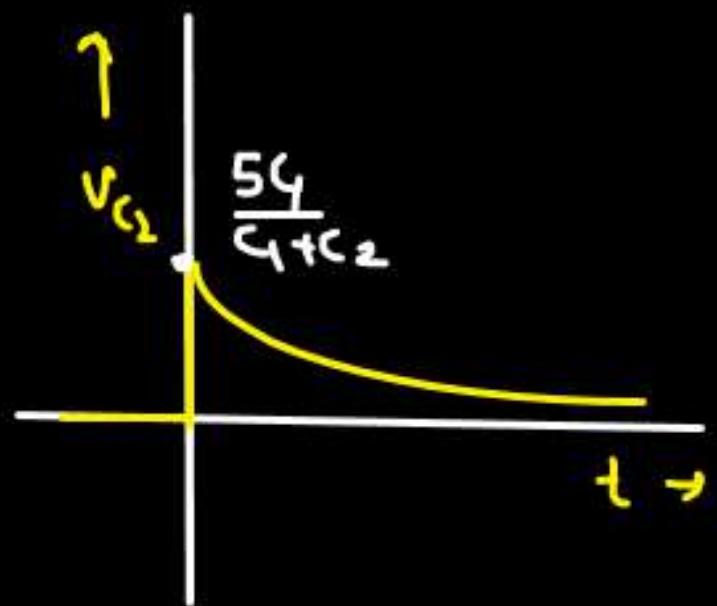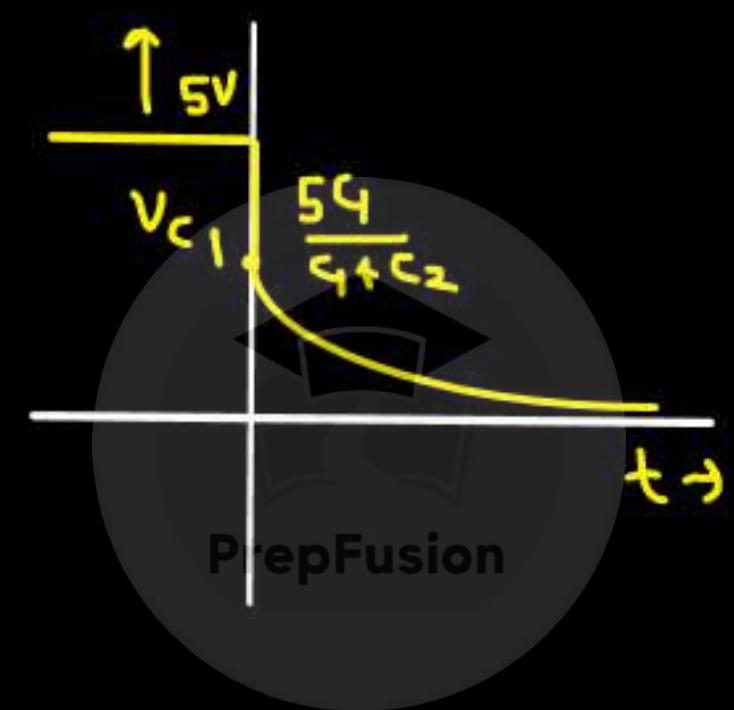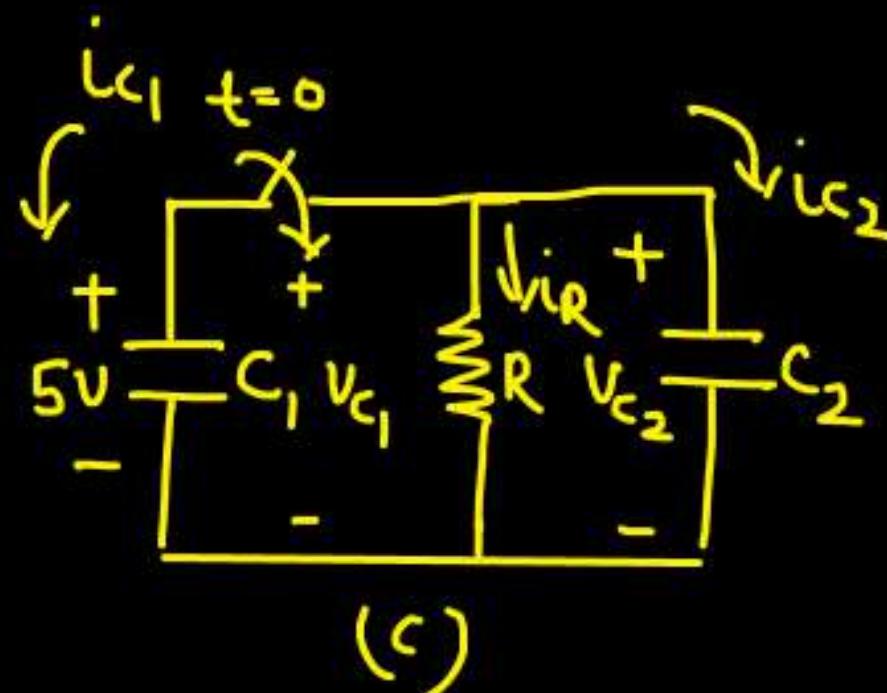
$$V_{C_1}(\infty) = V_{C_2}(\infty) = V_R(\infty) = 0V$$




$$\tau = R(C_1 + C_2)$$

$$V_{C_1}(t) = 5U(-t) + \frac{5C_1}{C_1 + C_2} e^{-\frac{t}{\tau}} U(t)$$
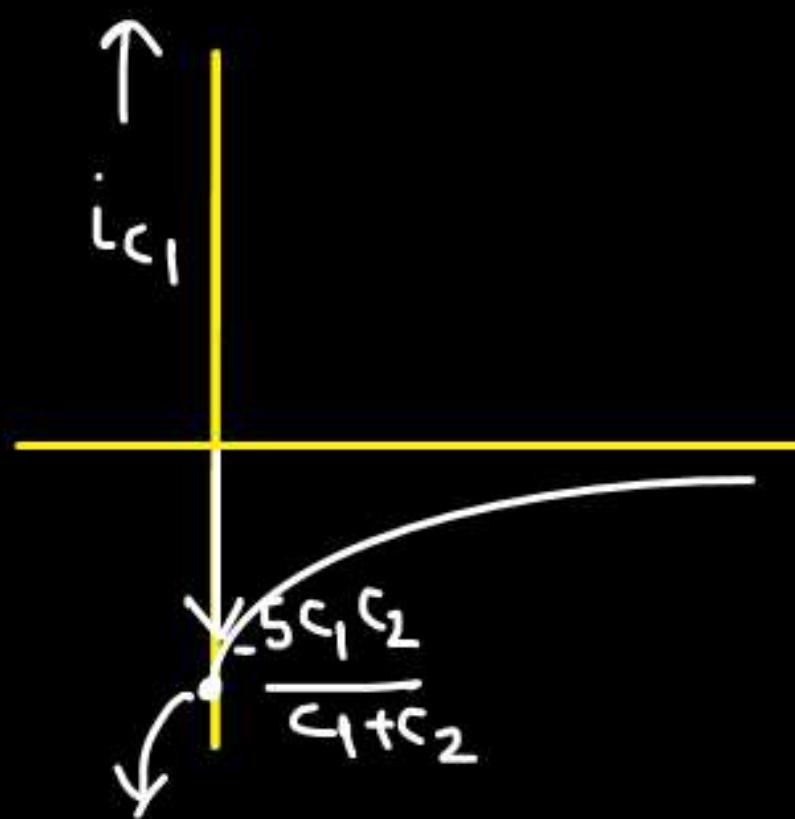
$$V_{C_2}(t) = \frac{5C_1}{C_1 + C_2} e^{-\frac{t}{\tau}} U(t)$$



$$-V_c \times \frac{C_1}{C_1 + C_2}$$

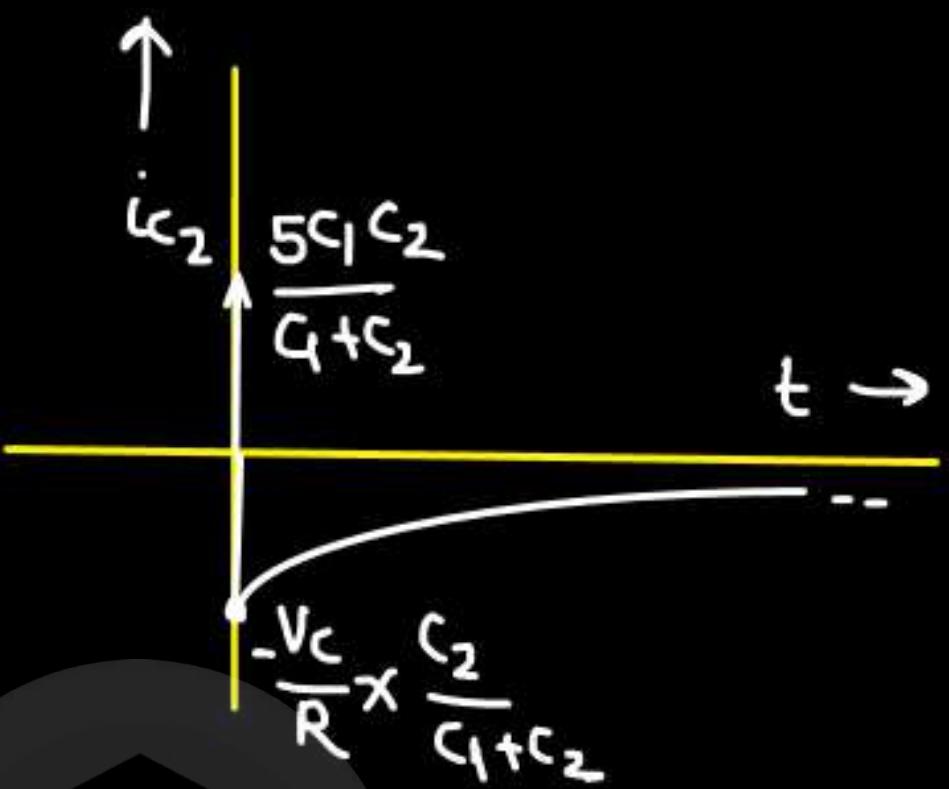

PrepFusion

$$V_c = \frac{5C_1}{C_1 + C_2}$$


$$i_{C_2}(t) = \frac{5C_1C_2}{C_1 + C_2} \delta(t) - \frac{V_c}{R} \times \frac{C_1}{C_1 + C_2} e^{-t/\tau} u(t)$$

$$i_{C_1}(t) = -\frac{5C_1C_2}{C_1 + C_2} \delta(t) - \frac{V_c}{R} \times \frac{C_1}{C_1 + C_2} e^{-t/\tau} u(t)$$

$$i_R(t) = \frac{5C_1}{R(C_1 + C_2)} e^{-t/\tau} u(t)$$



↳ Solving the ckt by Laplace Transform:-

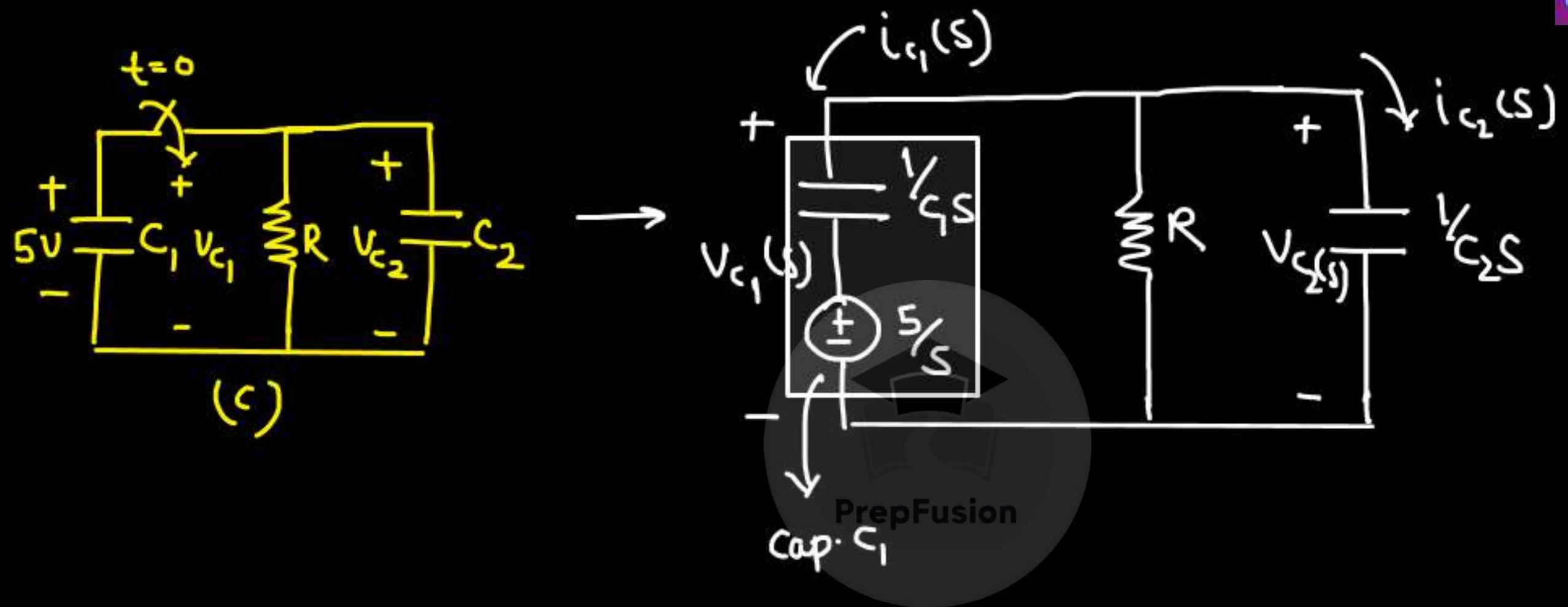

$$\frac{V_{C_1}(s) - \frac{5}{s}}{\frac{1}{C_1 s}} + \frac{V_{C_1}(s)}{R} + \frac{V_{C_1}(s)}{\frac{1}{C_2 s}} = 0$$

$$\Rightarrow V_{C_1}(s) = - - -$$



Slope @ $t=0^+$ in RC ckt's:-

Q. Given $x(t) = 6t^2 + 3t$

$$\text{find } \left[\frac{dx(t)}{dt} \right]_{t=0^+} \text{ or } \frac{dx(0^+)}{dt} \text{ or } x'(0^+).$$

→

$$x(0) = 6(0)^2 + 3(0)$$

$$= 0$$

$$\frac{dx(0)}{dt} = x'(0) = 0$$

X

wrong

PrepFusion

$$\frac{dx(t)}{dt} = 12t + 3$$

$$\left[\frac{dx(t)}{dt} \right]_{t=0^+} = 12(0) + 3 = 3$$

$$\left[\frac{dx(t)}{dt} \right]_{t=0^+} = \frac{dx(0^+)}{dt} = x'(0^+) = 3$$


N.B:- Even if $x(0) = 0$,

then $x'(0^+)$ may not be zero.


Here; $x(0) = 0$ but $x'(0^+) = 3$



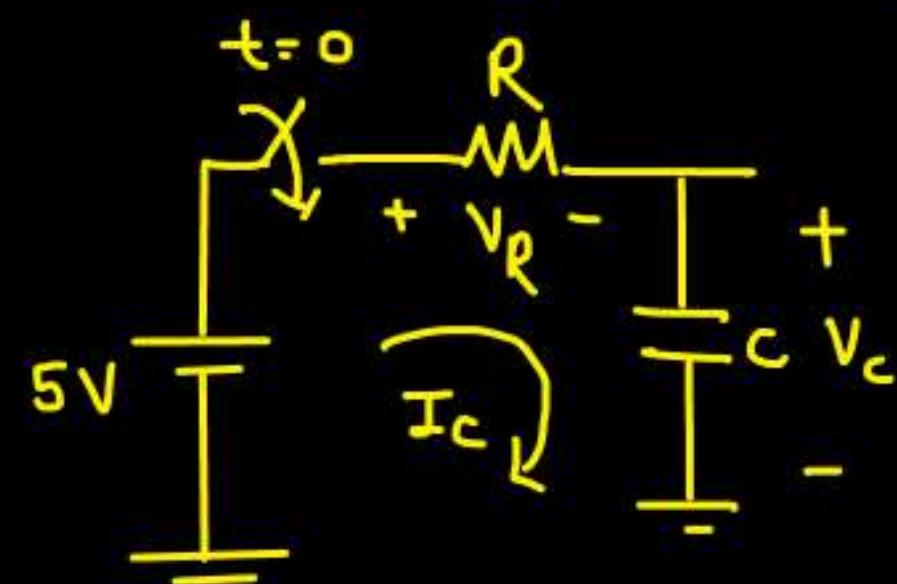Q. Find $V_R'(0^+)$, $V_c'(0^+)$, $I_c'(0^+) = ?$



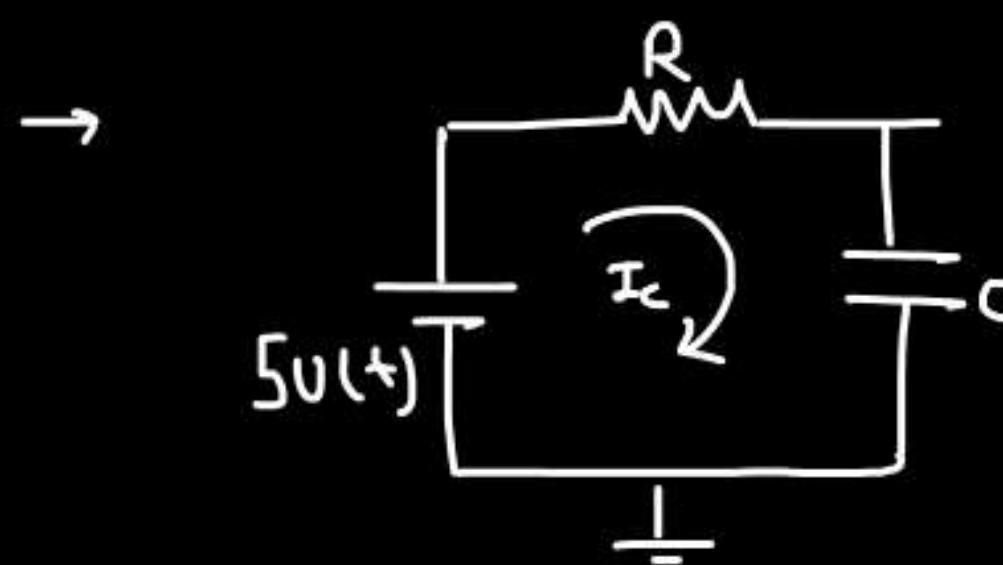where $V_R'(0^+) = \left[\frac{dV_R(t)}{dt} \right]_{t=0^+}$



$$5U(t) = I_c(t) \cdot R + \frac{1}{C} \int I_c(t) \cdot dt$$

Differentiating both sides

$$5\delta(t) = R \frac{dI_c(t)}{dt} + \frac{I_c(t)}{C}$$

at $t=0^+$,



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

$$5\delta(0^+) = R \frac{dI_c(0^+)}{dt} + \frac{I_c(0^+)}{C}$$

$$\left\{ \begin{array}{l} \delta(t) = \begin{cases} \infty, & t < 0 \\ 0, & t \geq 0 \end{cases} \\ \delta(0^+) = 0 \end{array} \right.$$

$$0 = R \frac{dI_c(0^+)}{dt} + \frac{5}{RC} \quad \left\{ I_c(0^+) = \frac{5}{R} \right\}$$

$$\frac{dI_c(0^+)}{dt} = -\frac{5}{R^2C}$$



M-II

$$I_c(t) = \frac{5}{R} e^{-t/RC} u(t)$$

$$\frac{dI_c(t)}{dt} = \frac{5}{R} \left[e^{-t/RC} \delta(t) - \frac{e^{-t/RC}}{RC} u(t) \right]$$

$$\frac{dI_c(0^+)}{dt} = \frac{5}{R} \left[0 - \frac{1}{RC} u(0^+) \right] = -\frac{5}{R^2C} u$$

$$u(t) = \begin{cases} 1, & t > 0 \\ 0, & t < 0 \end{cases}$$

$$u(0^+) = 1$$

[YouTube -PrepFusion](#)
(CLICK HERE FOR FULL PLAYLIST)



$$\frac{dV_R(0^+)}{dt} : \rightarrow$$

$$5V(t) = V_R(t) + \frac{1}{C} \int_0^t I_C(\tau) d\tau$$


Differentiating on both sides

$$5\delta(t) = \frac{dV_R(t)}{dt} + \frac{I_C(t)}{C}$$

at $t=0^+$

$$0 = \frac{dV_R(0^+)}{dt} + \frac{5}{RC}$$
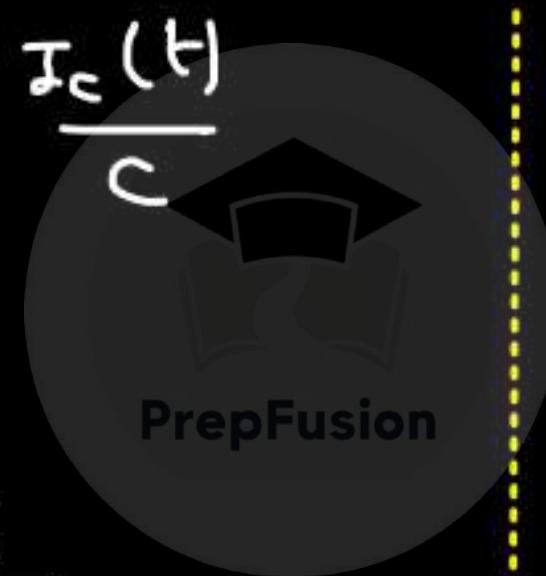
$$\boxed{\frac{dV_R(0^+)}{dt} = -\frac{5}{RC}}$$



M-II

$$V_R(t) = 5e^{-t/RC} V(t)$$

$$\frac{dV_R(t)}{dt} = 5 \left[e^{-t/RC} \delta(t) - \frac{e^{-t/RC}}{RC} V(t) \right]$$

$$\boxed{\frac{dV_R(0^+)}{dt} = -\frac{5}{RC}}$$

$$\underline{\underline{\frac{dV_C(0^+)}{dt}}} : -$$

$$5v(t) = I_C(t)R + V_C(t)$$

$$I_C(t) = C \frac{dV_C(t)}{dt}$$

$$5v(t) = RC \frac{dV_C(t)}{dt} + V_C(t)$$

for $t=0^+$

$$5v(0^+) = RC \frac{dV_C(0^+)}{dt} + V_C(0^+)$$

$$5 = RC \frac{dV_C(0^+)}{dt}$$

\therefore

$\frac{dV_C(0^+)}{dt}$	$= \frac{5}{RC}$
------------------------	------------------


$$\left\{ \begin{array}{l} V_C(0^+) \approx 0V \\ v(0^+) \approx 1 \end{array} \right.$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

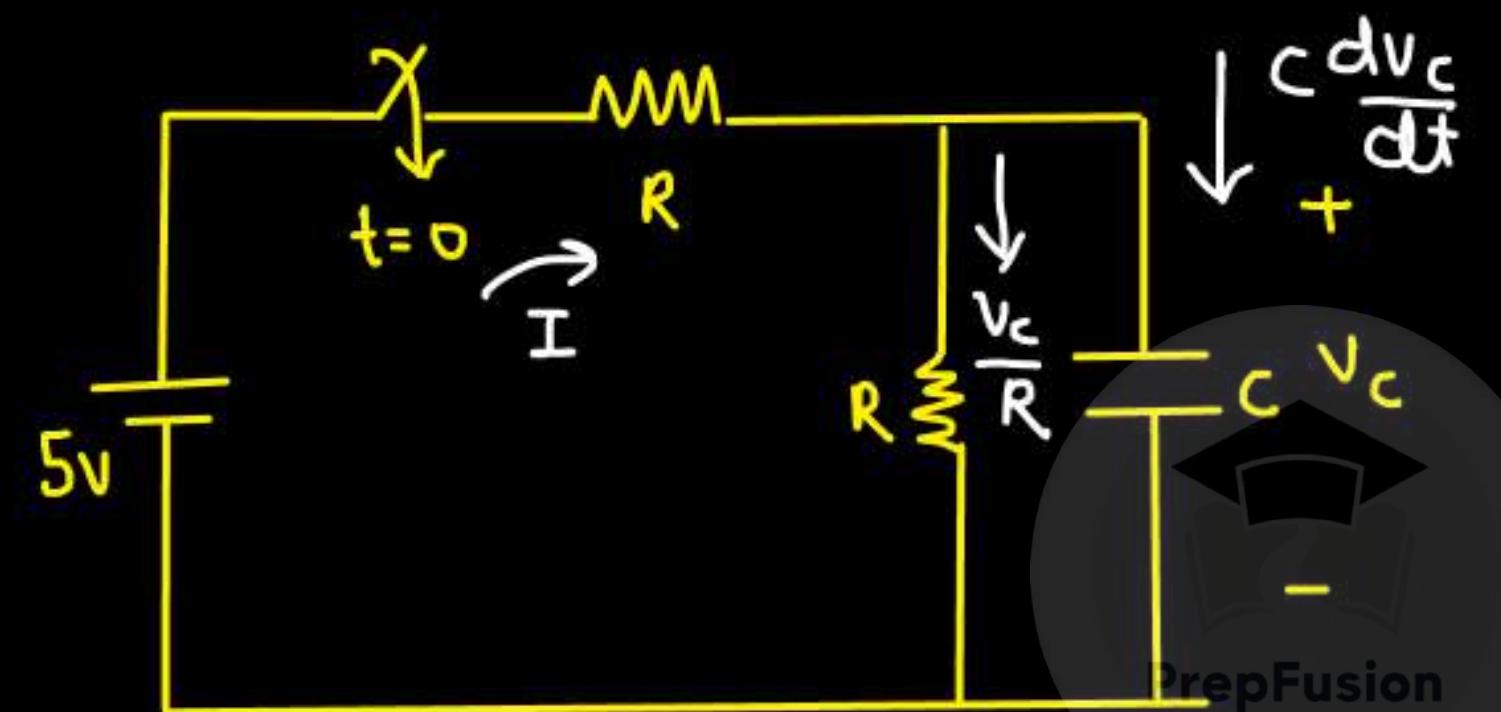Q. Find $\left[\frac{dV_C(t)}{dt} \right]_{t=0^+}$



$$\rightarrow 5V(t) = I(R + V_C(t)) \quad \textcircled{1}$$

Task:- replace 'I' in terms of 'V_C'

$$I(t) = \frac{V_C(t)}{R} + C \frac{dV_C(t)}{dt} \quad \textcircled{2}$$

By eqn ① and ②

$$5U(t) = \left[\frac{V_c(t)}{R} + C \frac{dV_c(t)}{dt} \right] R + V_c(t)$$

$$5U(t) = V_c(t) + RC \frac{dV_c(t)}{dt} + V_c(t)$$


$$5U(t) = 2V_c(t) + RC \frac{dV_c(t)}{dt}$$

at $t=0^+$

$$5U(0^+) = 2V_c(0^+) + RC \frac{dV_c(0^+)}{dt}$$

$$5 = RC \frac{dV_c(0^+)}{dt}$$
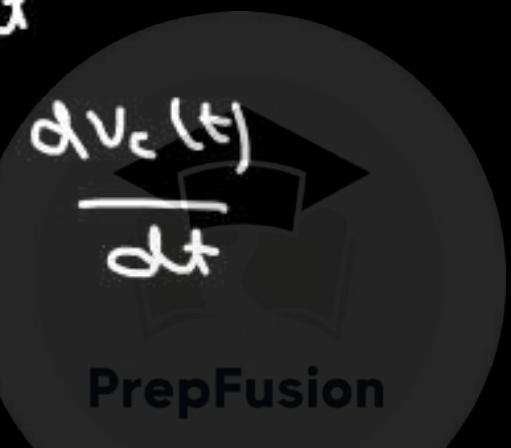
$$\therefore \boxed{\frac{dV_c(0^+)}{dt} = \frac{5}{RC}}$$



$$\begin{cases} V_c(0^+) = 0V \\ U(0^+) = 1 \end{cases}$$

M-II

$$V_C(t) = Q \cdot 5 \left(1 - e^{-t/\tau} \right) u(t) ; \quad \tau = RC/2$$

$$\frac{dV_C(t)}{dt} = Q \cdot 5 \left[(1 - e^{-t/\tau}) \delta(t) + e^{-t/\tau} \frac{1}{\tau} u(t) \right]$$

$$\begin{aligned} \frac{dV_C(0^+)}{dt} &= Q \cdot 5 \left[0 + \frac{1}{\tau} \right] \\ &= \frac{Q \cdot 5}{RC} \end{aligned}$$




$$\boxed{\frac{dV_C(0^+)}{dt} = \frac{5}{RC}}$$



Switch capacitors :-

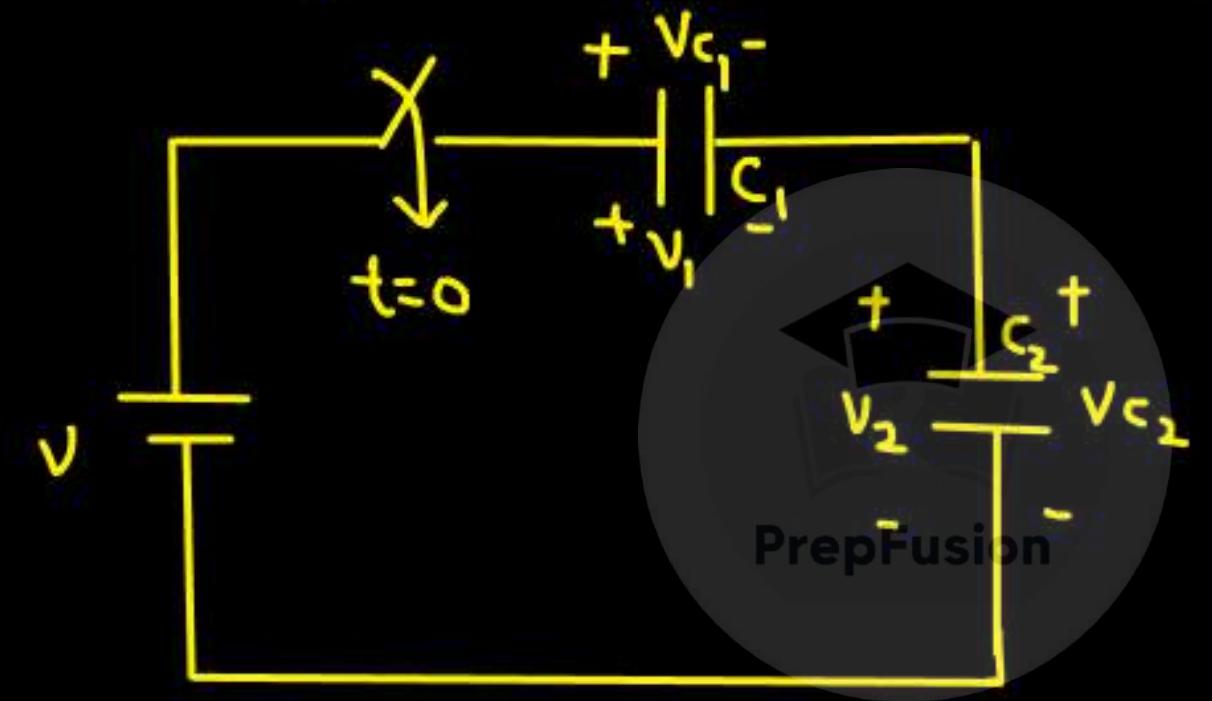* Given; initial voltage across capacitor $C_1 = V_1$
initial voltage across capacitor $C_2 = V_2$




Find steady state value of
 V_{c_1} & V_{c_2} .

$$\rightarrow V_{c_1}(0^-) = V_1$$


$$V_{c_2}(0^-) = V_2$$

ckt @ $t \geq 0^+$

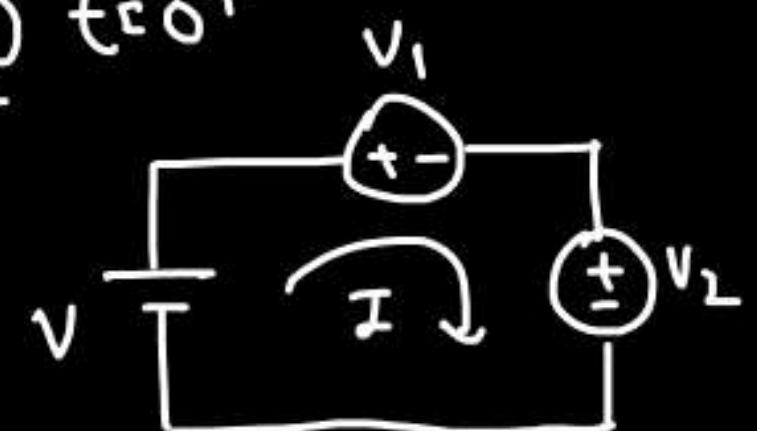

$$I_e \frac{(V - V_1 - V_2)}{0} = \infty$$

↳ impulse current

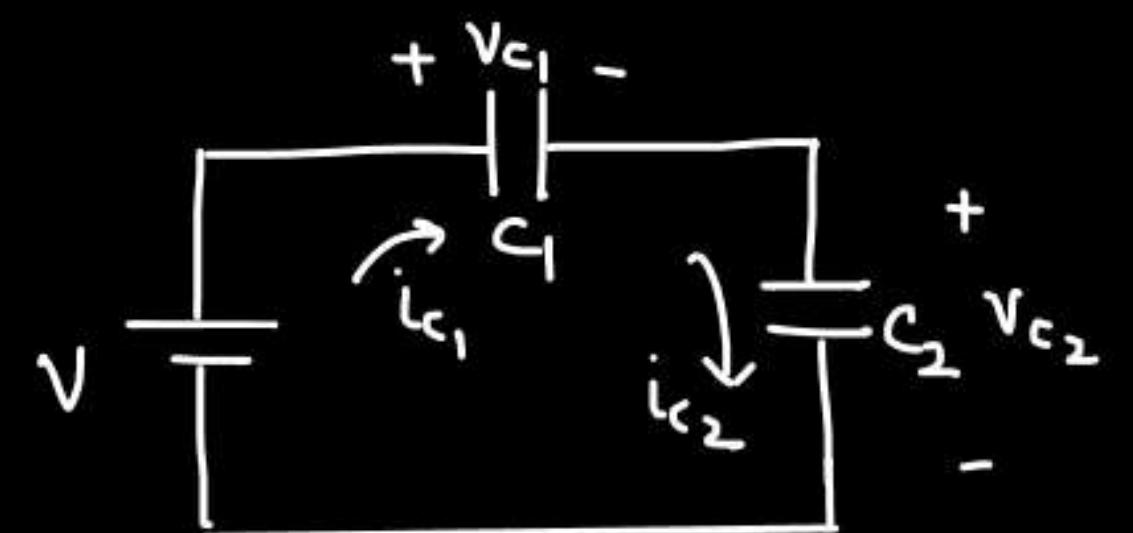

since, both cap. are connected in series

$$i_{C_1} = i_{C_2}$$


$$C_1 \frac{dV_{C_1}}{dt} = C_2 \frac{dV_{C_2}}{dt}$$

$$C_1 \Delta V_{C_1} = C_2 \Delta V_{C_2}$$

{ change in charge will be the same }

Because of voltage source V , if the change in V_{C_1} is ΔV

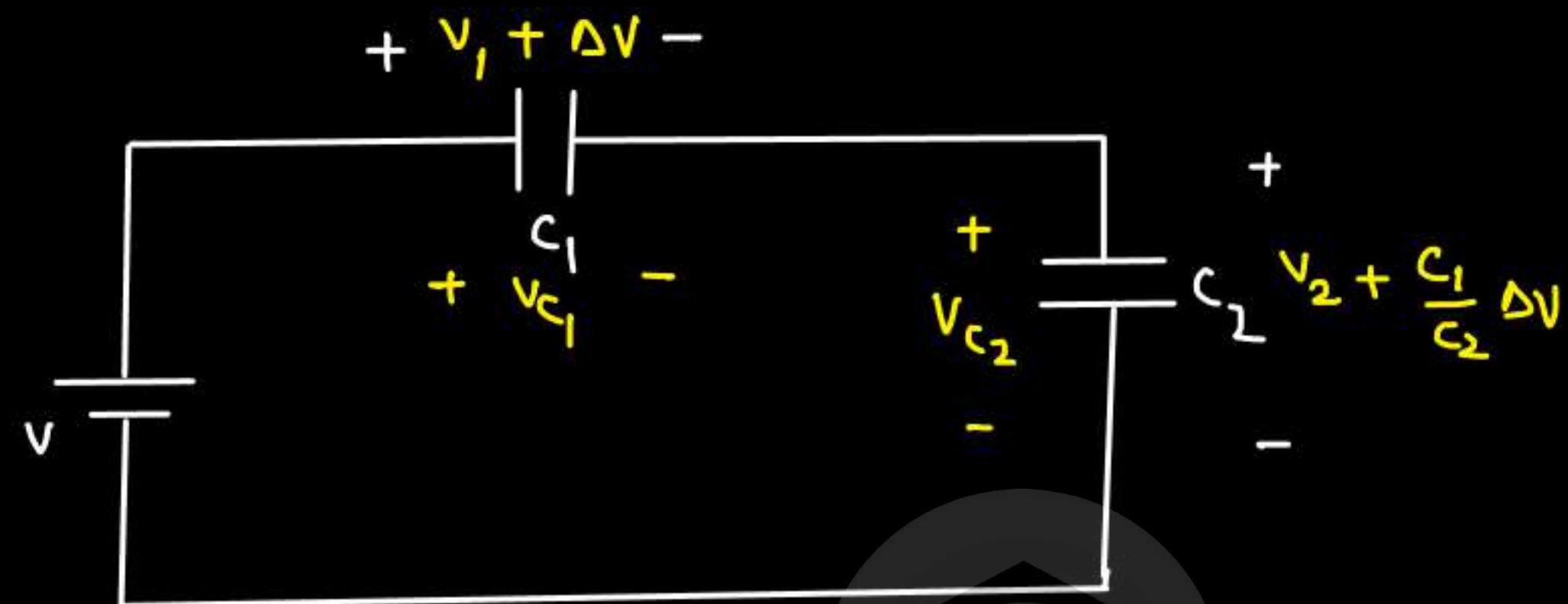the change in V_{C_2} will be $\frac{C_1}{C_2} \Delta V$



Applying KVL:-

$$V = V_{C_1} + V_{C_2}$$

$$V = V_1 + \Delta V + V_2 + \frac{C_1}{C_2} \Delta V$$

$$V - V_1 - V_2 = \left(\frac{C_1 + C_2}{C_2} \right) \Delta V$$

$$\Rightarrow \Delta V = \left(\frac{C_2}{C_1 + C_2} \right) (V - V_1 - V_2)$$

$$V_{C_1} = V_1 + \Delta V$$

$$V_{C_1} = V_1 + \left(\frac{C_2}{C_1 + C_2} \right) (V - V_1 - V_2)$$

$$V_{C_2} = V_2 + \frac{C_1}{C_2} \Delta V$$


$$V_{C_2} = V_2 + \frac{C_1}{C_2} \left(\frac{C_2}{C_1 + C_2} \right) (V - V_1 - V_2)$$

PrepFusion

$$V_{C_2} = V_2 + \frac{C_1}{C_1 + C_2} (V - V_1 - V_2)$$



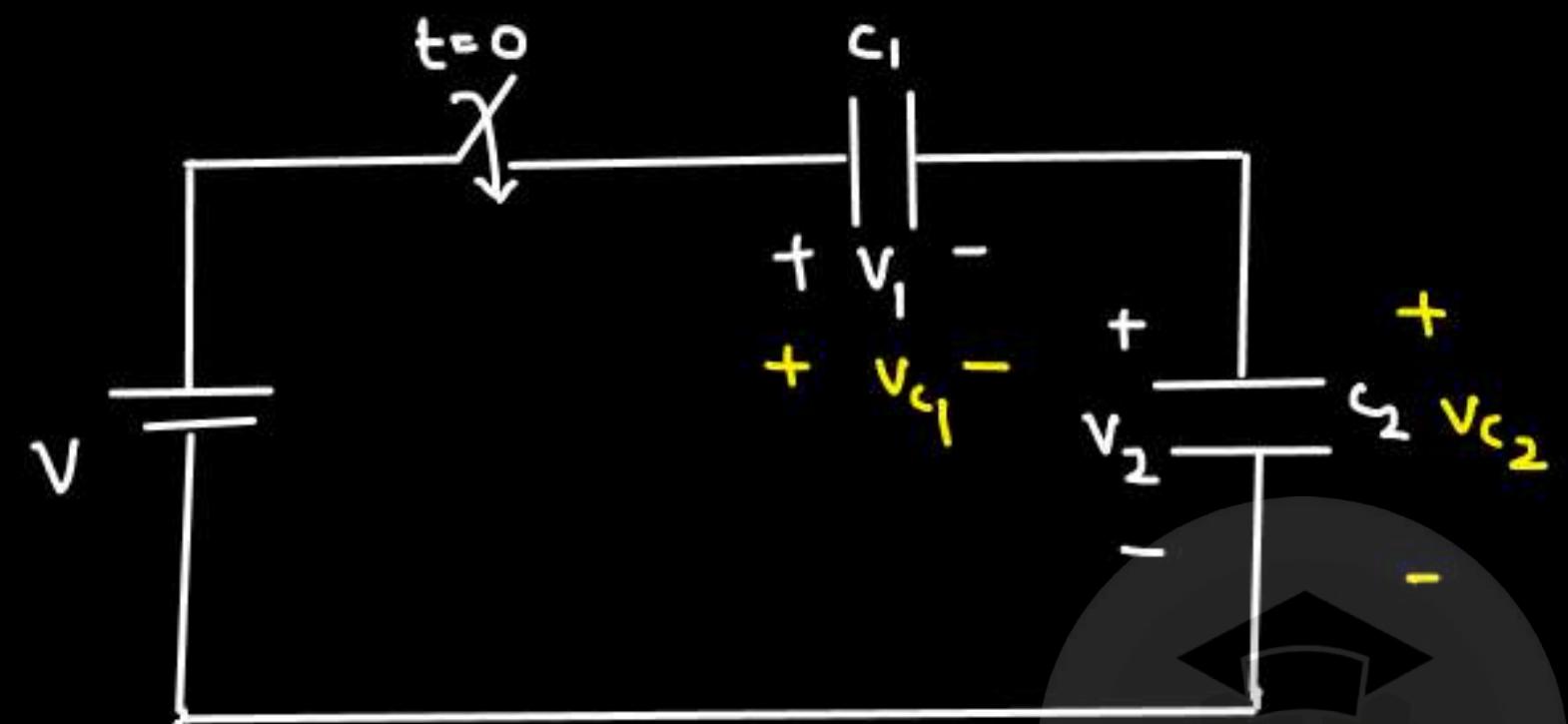How will you write steady state v_{c_1} & v_{c_2} in one step? (CL)



PrepFusion


$$v_{c_1} = v_1 + \left(V - v_1 - v_2 \right) \frac{C_2}{C_1 + C_2}$$

$$v_{c_2} = v_2 + \left(V - v_1 - v_2 \right) \frac{C_1}{C_1 + C_2}$$

Question :-

Q. Find $v_{c_1}(0^+)$ and $v_{c_2}(0^+)$.

Draw the waveform of i_c .

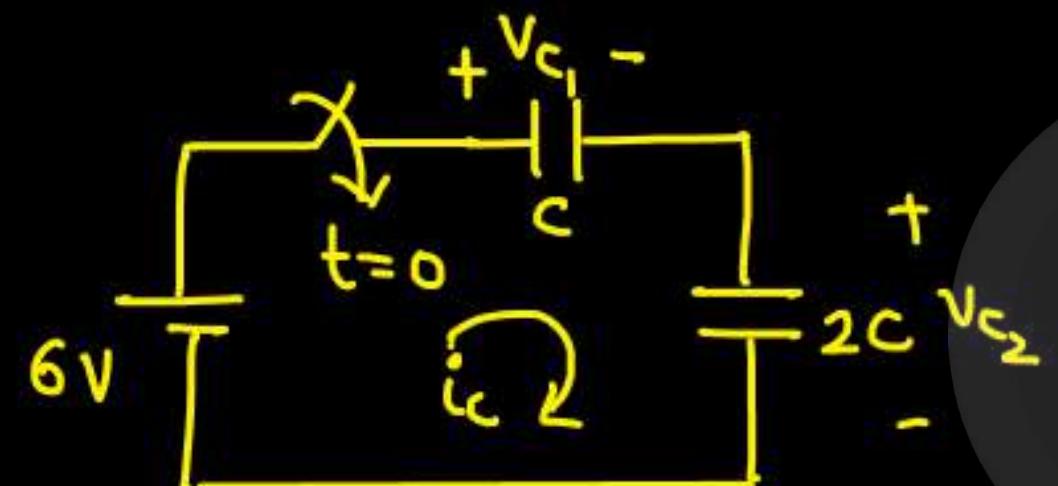



$$\rightarrow v_{c_1}(0^+) = 2 + (6 - 2 - 1) \frac{2C}{3C}$$

$$= 4V$$

$$v_{c_2}(0^+) = 1 + (6 - 2 - 1) \frac{C}{3C} = 2V$$

$$v_{c_1}(0^-) = 2V$$


$$v_{c_2}(0^-) = 1V$$

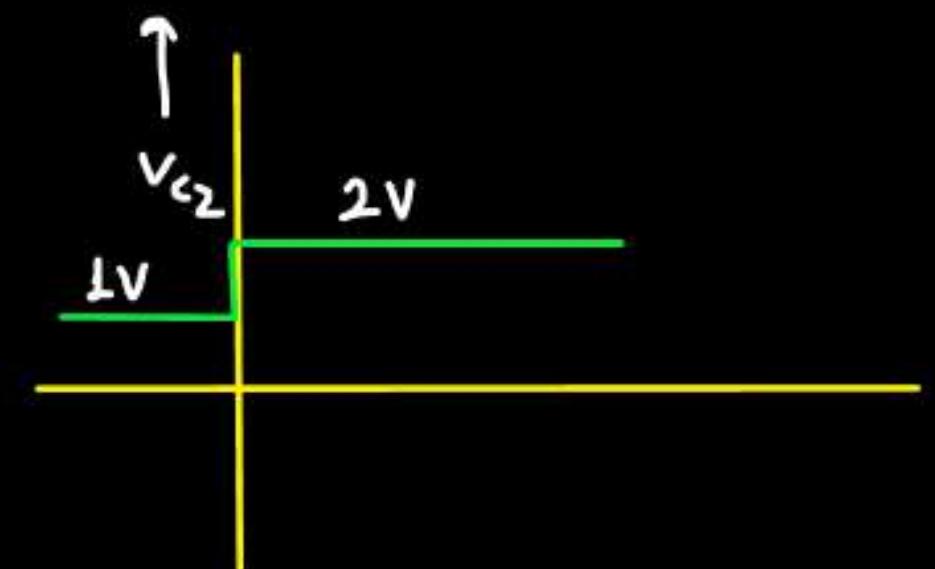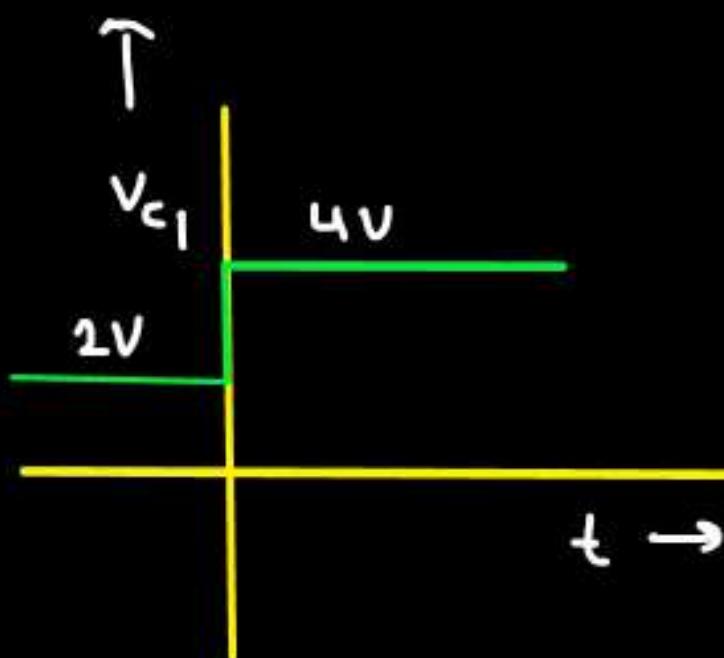

$$i_{C_1} = i_{C_2} = i_C$$


$$i_C = C_1 \frac{dV_{C_1}}{dt} = \underbrace{C \frac{dV_{C_1}}{dt}}_{\text{Pre-Resistor}} = C_2 \frac{dV_{C_2}}{dt} = \underbrace{2C \frac{dV_{C_2}}{dt}}_{\text{Post-Resistor}} = 2C \delta(t)$$

$$= 2C \delta(t)$$

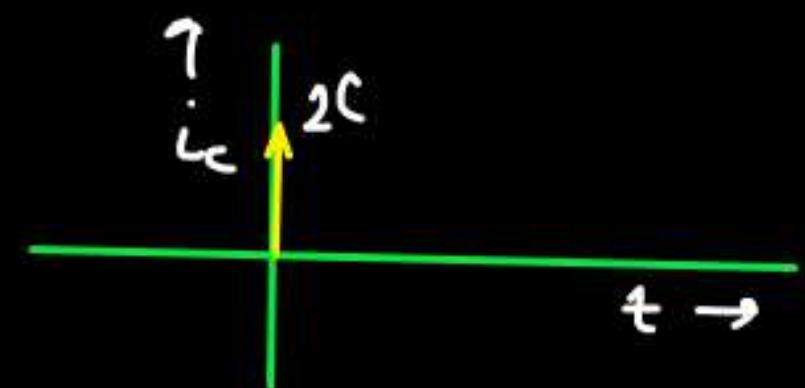

$$i_C(t) = 2C \delta(t)$$

Q.

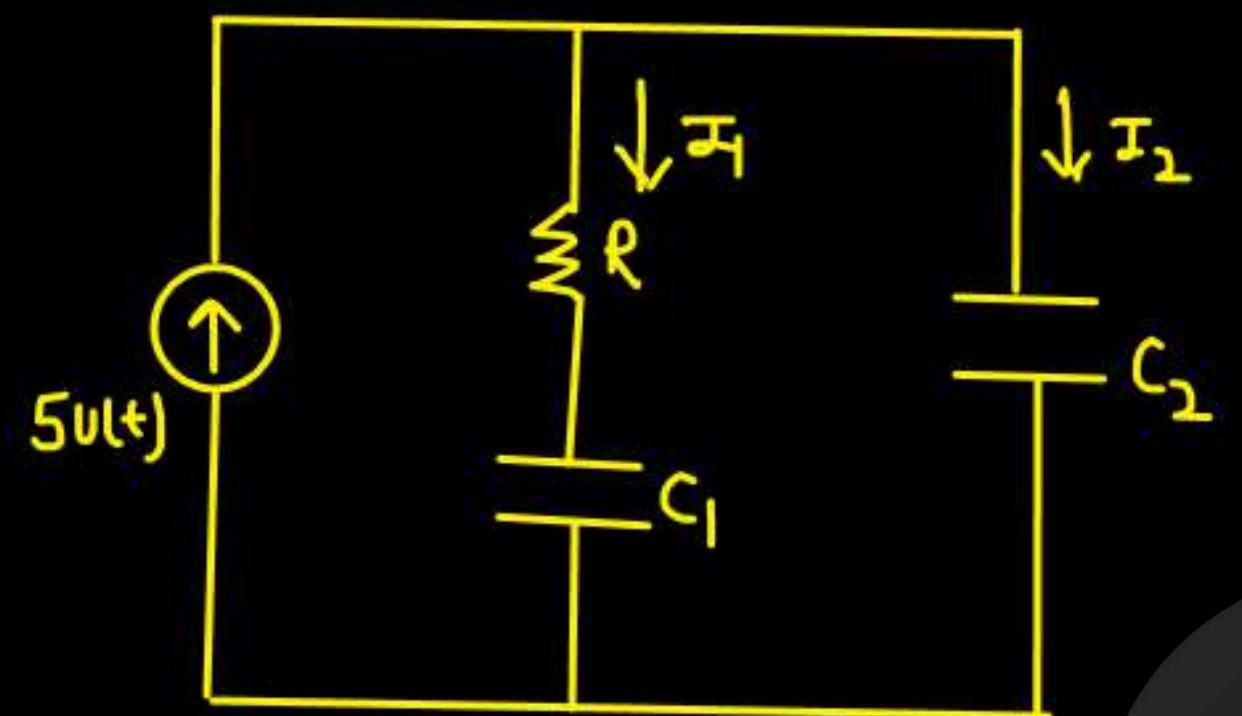

Find expression for I_1 & I_2 .

$$\rightarrow \tau = ?$$

$$\tau = \frac{R(C_1 C_2)}{C_1 + C_2}$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES




a) $t \rightarrow 0^+$

$$I_1(0^+) = 0 \text{ Amp}$$

$$I_2(0^+) \approx 5 \text{ Amp}$$

b) $t = \infty$

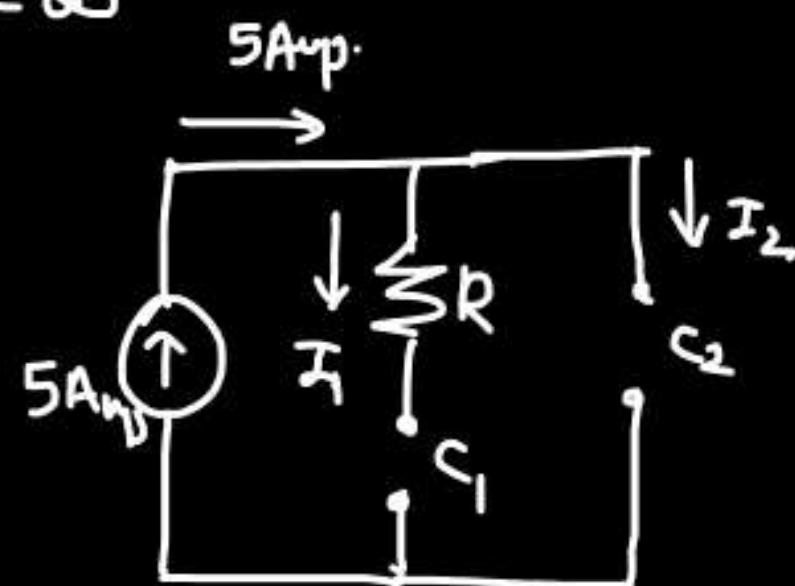


$$5 = I_1 + I_2$$

$t = \infty \Rightarrow \omega = 0 \Rightarrow Z_C \rightarrow \text{very High}$

PrepFusion

$$\frac{1}{R} - \frac{1}{C} = -\frac{1}{C}$$

$$I_1(\infty) = \frac{5C_1}{C_1 + C_2}$$

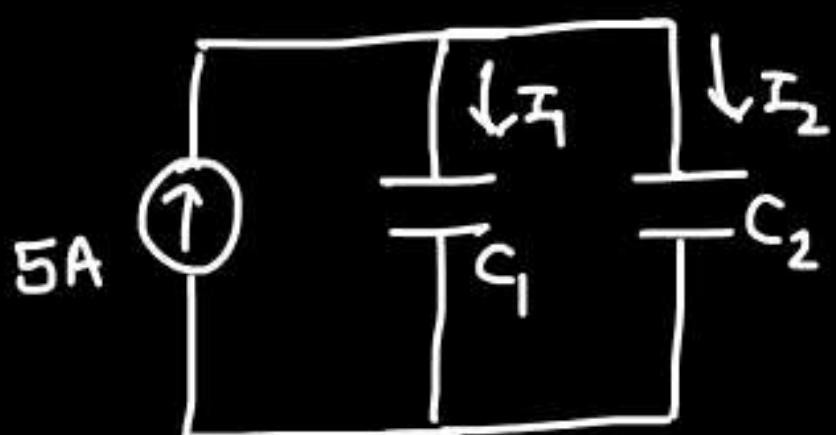

$$I_2(\infty) \approx \frac{5C_2}{C_1 + C_2}$$

AIR 27 (ECE)
AIR 45 (IN)


$$I_1(t) = \frac{5C_1}{C_1 + C_2} \left[1 - e^{-t/\tau} \right] v(t) \quad ; \quad \tau = R \left(\frac{C_1 C_2}{C_1 + C_2} \right)^{(CL)}$$

$$I_2(t) : \left[\frac{5C_2}{C_1 + C_2} + \frac{5C_1}{C_1 + C_2} e^{-t/\tau} \right] v(t)$$






RC ckt with impulse voltage i/p:-

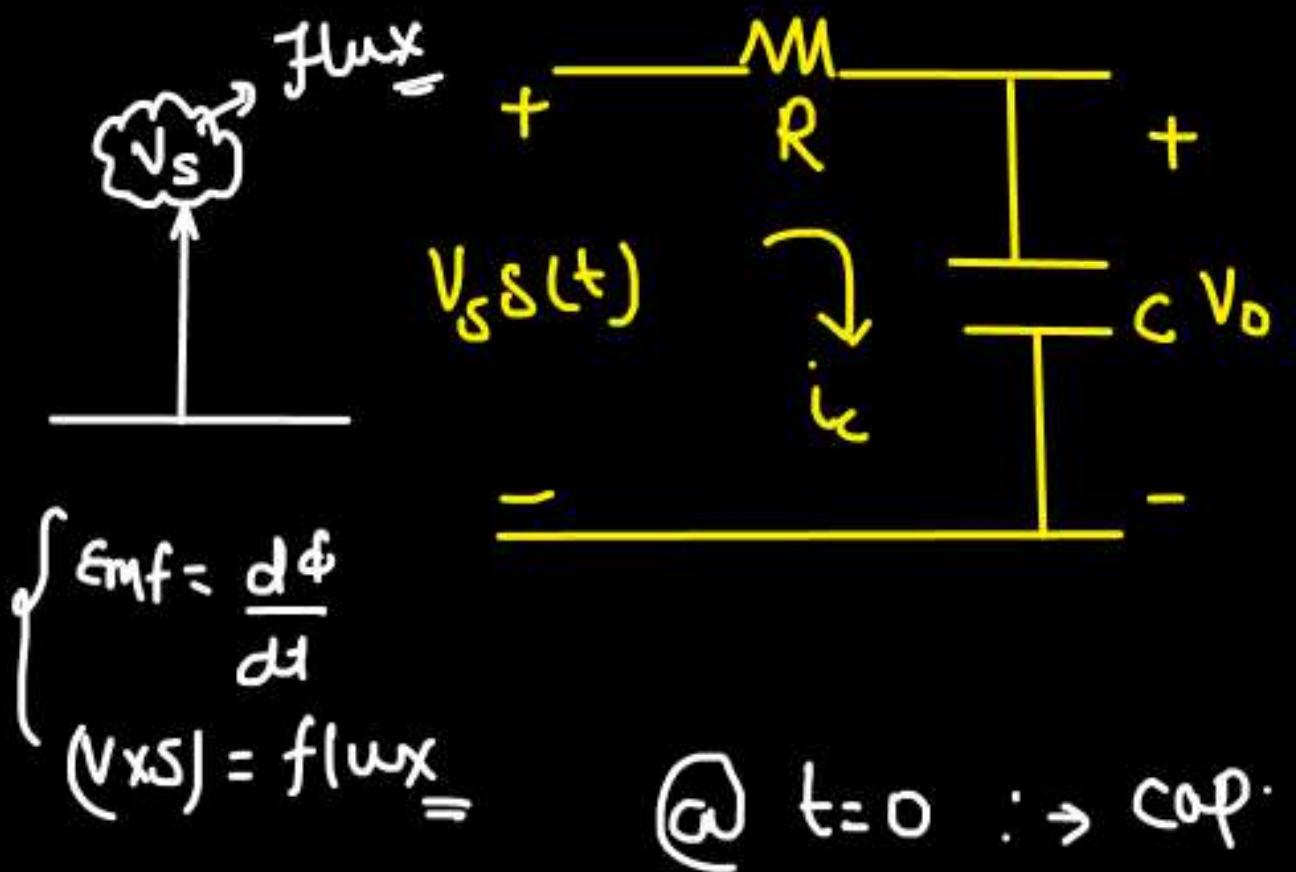

Draw V_o waveform.
Draw i_c waveform.

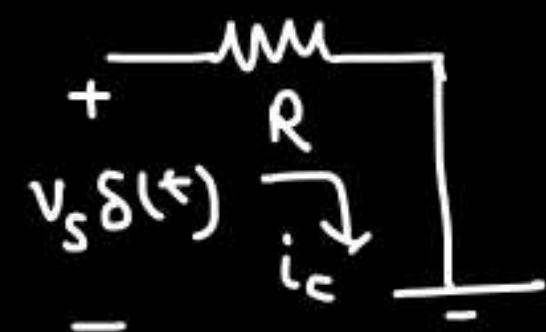

$$i_c(0) = \frac{V_s \delta(0)}{R} \rightarrow \text{impulse current}$$

$$V_c(0^- \rightarrow 0^+) = \frac{1}{C} \int_{0^-}^0 i_c(t) dt = \frac{1}{C} \int_0^0 \frac{V_s \delta(t)}{R} dt$$

$$V_c(0) = \frac{V_s}{RC} \int_{0^-}^0 \delta(t) \cdot dt$$

$$= \frac{V_s}{RC} \left[U(t) \right]_{0^-}^0$$

$$= \frac{V_s}{RC} [U(0) - U(0^-)]$$

$$V_c(0) = \frac{V_s}{RC} [1 - 0]$$


$$\boxed{V_c(0) \approx \frac{V_s}{RC}}$$



Ckt @ $t < 0^+$

$V_i(t) \approx V_s \delta(t)$ will be zero after $t=0$

$$V_i(0^+) = 0 \text{ V}$$

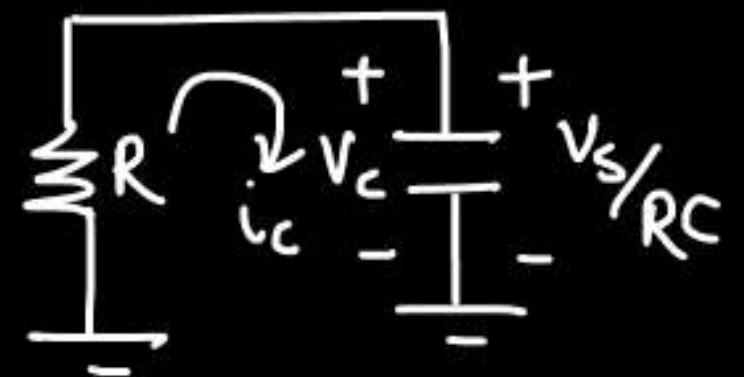

$\frac{Vs}{RC}$ voltage will be discharged with time const. RC .
 $V_c(\infty) = 0V$

$$V_c(t) = \frac{Vs}{RC} e^{-\frac{t}{RC}} ; \tau = RC$$

PrepFusion



i_c :-

$$i_c(0) = \frac{Vs}{R} \delta(t)$$

$$i_c(0^+) = -\frac{Vs}{R}$$


$$i_c(\infty) = 0$$
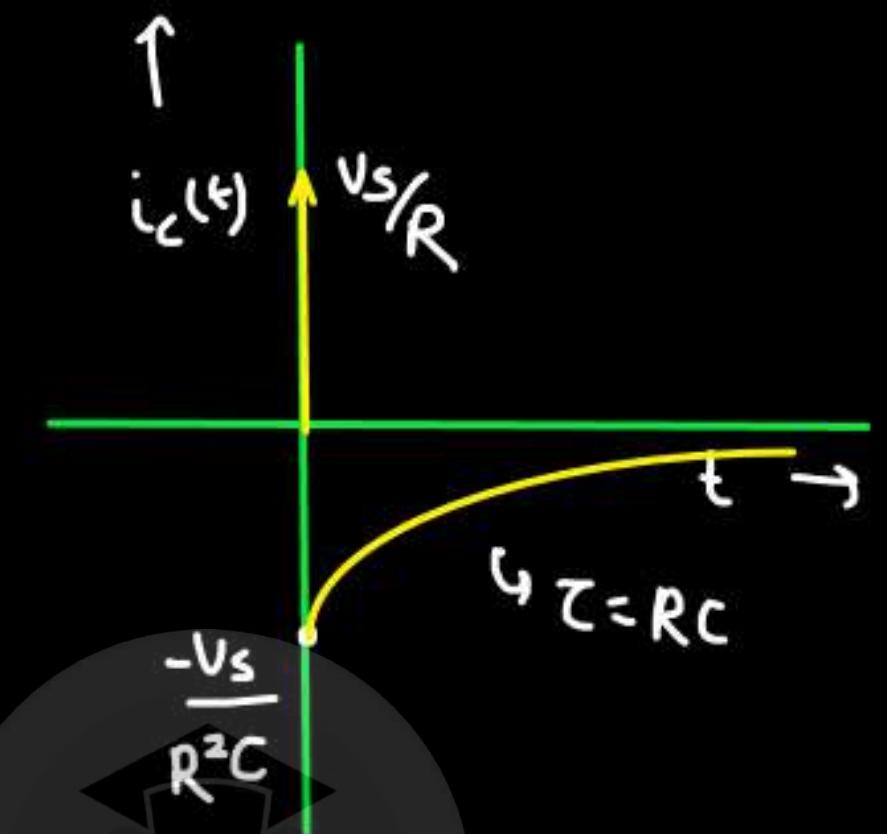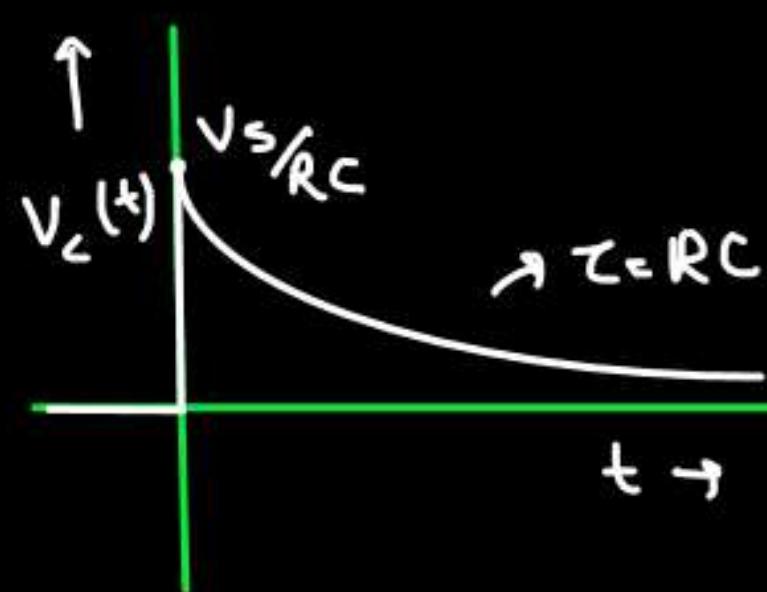
$$i(t) = \frac{Vs}{R} \delta(t) - \frac{Vs}{R^2 C} e^{-\frac{t}{RC}} ; \tau = RC$$



M-II :-

By Laplace Transform :-

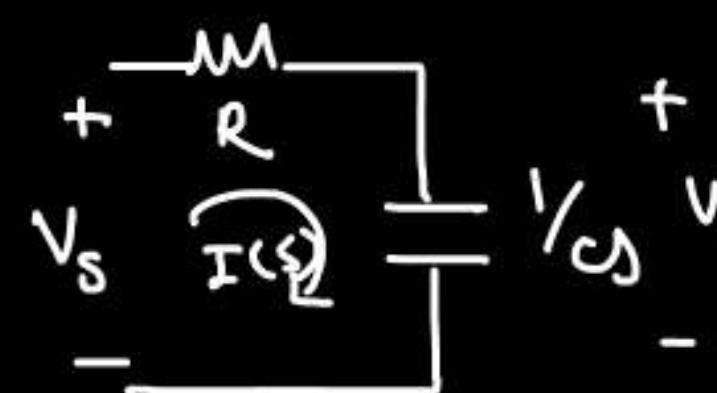

$$V_i(t) = V_s \delta(t)$$

$$V_i(s) = V_s$$

$$I(s) = \frac{V_s}{R + \frac{1}{C}}$$

$$I(s) = \frac{V_s s}{RC + 1}$$

$$= \frac{CV_s}{RC} \left(\frac{\frac{RCs+1-1}{RC+1}}{RC+1} \right)$$

$$I(s) = \frac{CV_s}{RC} \left[1 - \frac{1}{RC+1} \right]$$

$$I(s) = \frac{V_s}{R} - \frac{V_s}{R^2 C} \times \frac{1}{s + \frac{1}{RC}}$$

$$i(t) = \frac{V_s}{R} \delta(t) - \frac{V_s}{R^2 C} e^{-\frac{t}{RC}} u(t)$$

$$\left. \begin{cases} h^{-1}[A] = a \delta(t) \\ h^{-1}\left[\frac{1}{s+a}\right] = e^{-at} u(t) \end{cases} \right\}$$

$$V_c(s) = \frac{1/s}{1/s + R} \times V_s$$

$$= \frac{1}{R s + 1} \times V_s$$



$$V_c(s) = \frac{V_s}{R C} \left[\frac{1}{s + \frac{1}{R C}} \right]$$

ψ

$$v_c(t) = \frac{V_s}{R C} e^{-\frac{t}{R C}} v(t)$$

PropFusion

M-III :-

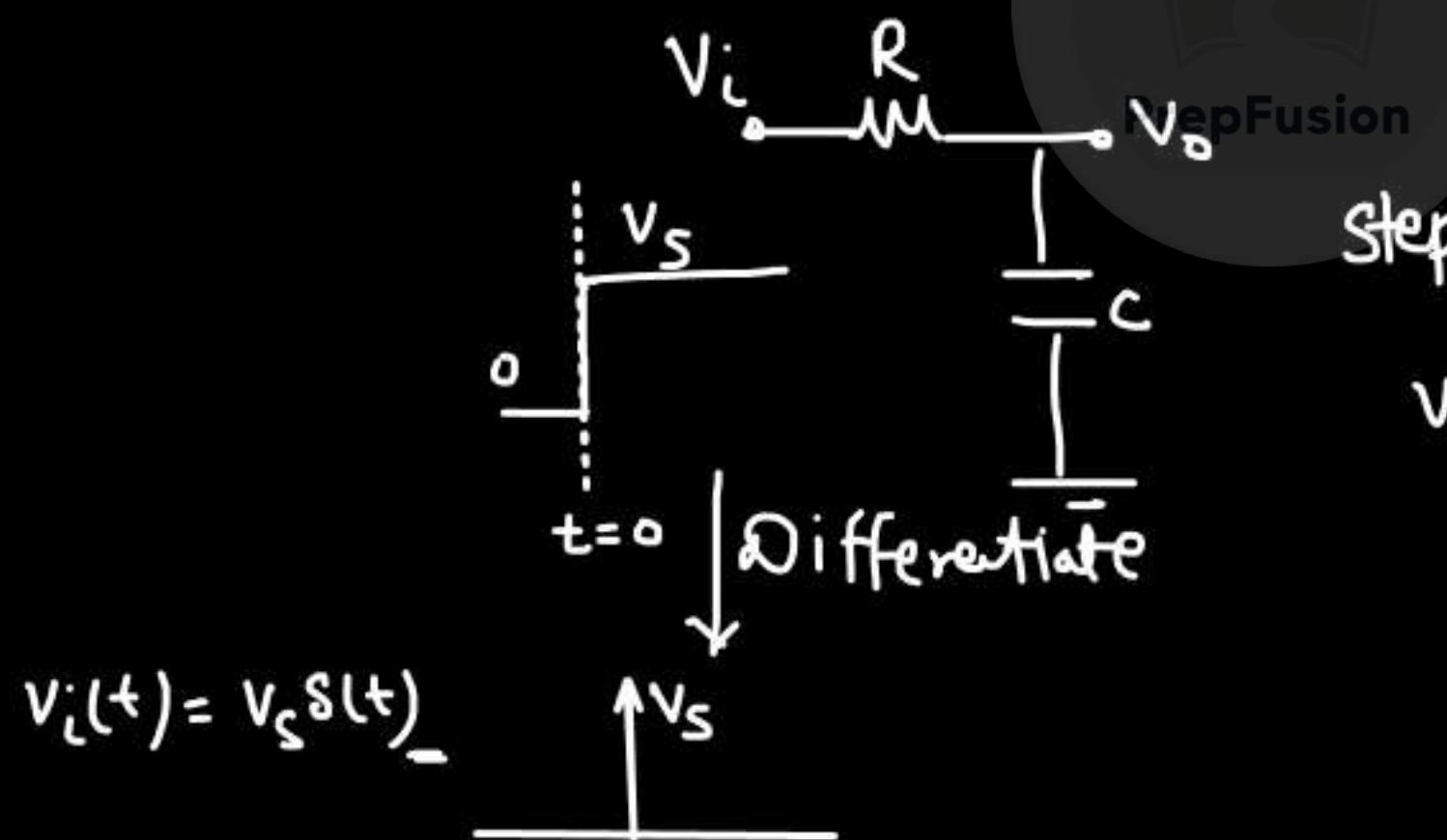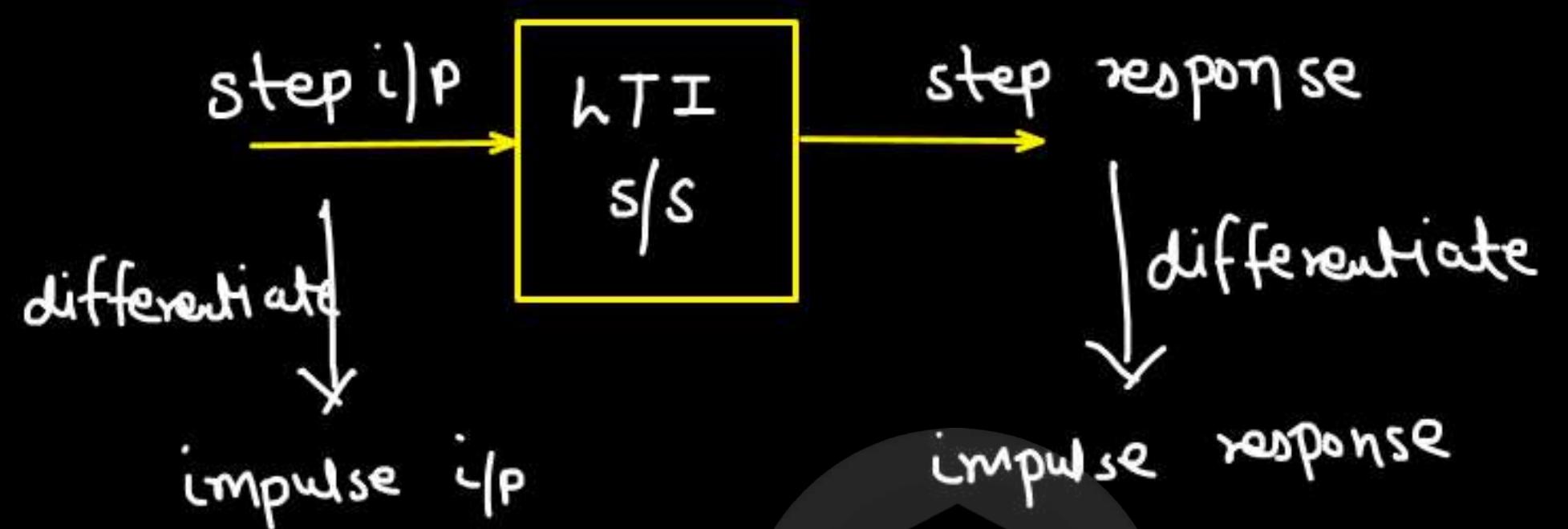



$$\text{impulse response} = \frac{d}{dt} \left[v_s (1 - e^{-t/\tau}) u(t) \right]$$

$$= v_s (1 - e^{-t/\tau}) \delta(t) + v_s \frac{e^{-t/\tau}}{\tau} u(t)$$

* * * * *

$$\text{impulse response} = \frac{v_s}{RC} e^{-t/\tau} u(t)$$

PrepFusion

$$\text{impulse response for current} = \frac{d}{dt} [\text{step response for current}]$$


$$= \frac{d}{dt} \left[\frac{v_s}{R} e^{-t/\tau} u(t) \right]$$

$$= \frac{V_s}{R} \left[e^{-t/\tau} \delta(t) - e^{-t/\tau} u(t) \right]$$

impulse current = $\frac{V_s}{R} \delta(t) - \frac{V_s}{R^2 C} e^{-t/\tau} u(t)$




★ RC CKTs with pulse-wave input:-

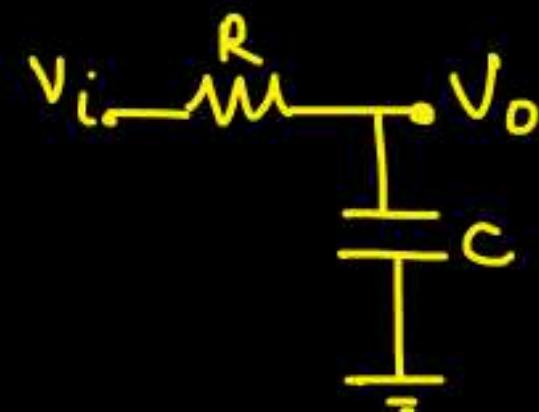

Draw V_o waveform

- ① $T \gg RC$
- ② $T \ll RC$

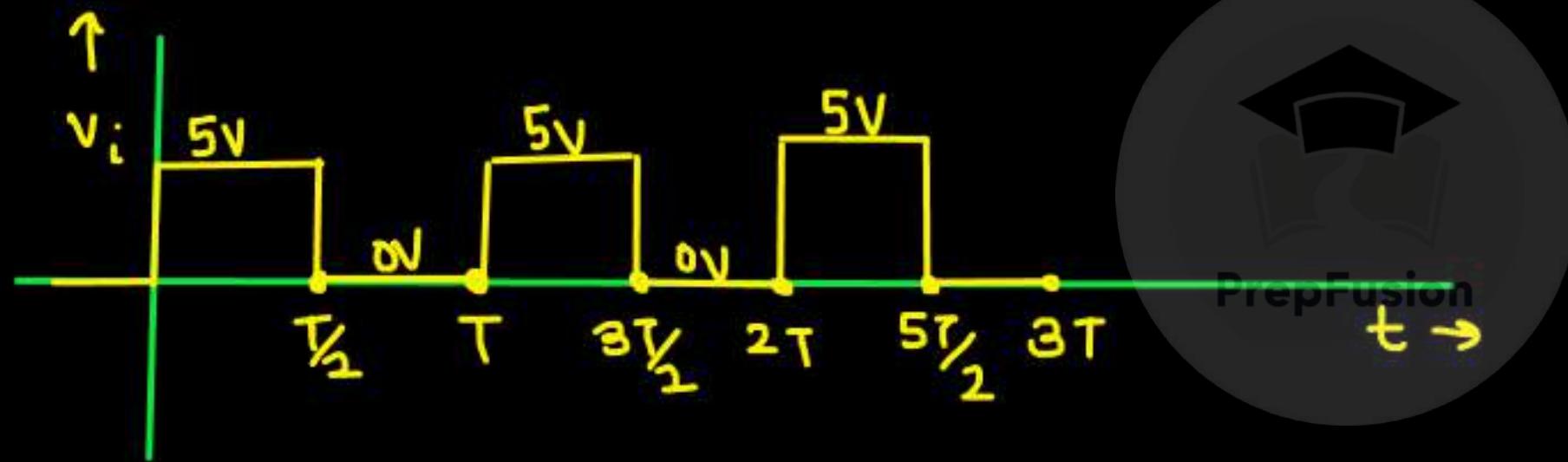




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

① $T \gg RC$:-

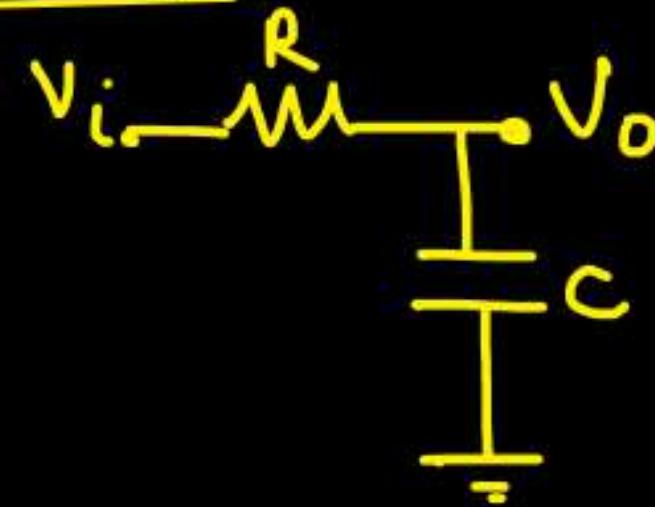

Let,


$$R = 2 \Omega, C = 1 F$$

$$RC = 2 \text{ sec}$$

$$T = 20 \text{ sec}$$

J

This would be given

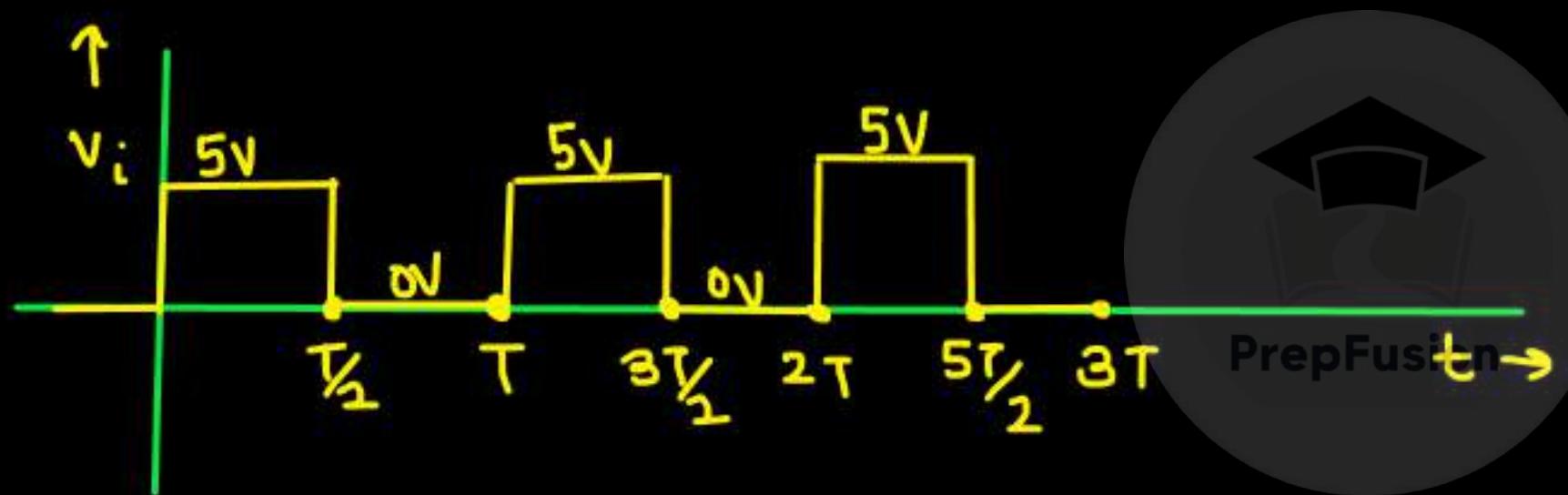


→ Given ; $T \gg RC$

Time period is very large than the time constant

YouTube -PrepFusion
(CLICK HERE FOR FULL PLAYLIST)


for $0 < t < T_{1/2}$

$$V_L = 5V$$

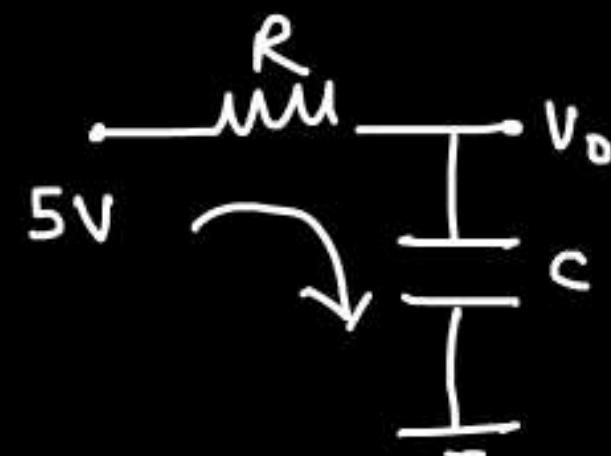

since τ is very large. The cap. will have enough time
to get charged to 5v.

$$V_c(T_{1/2}) = 5V$$

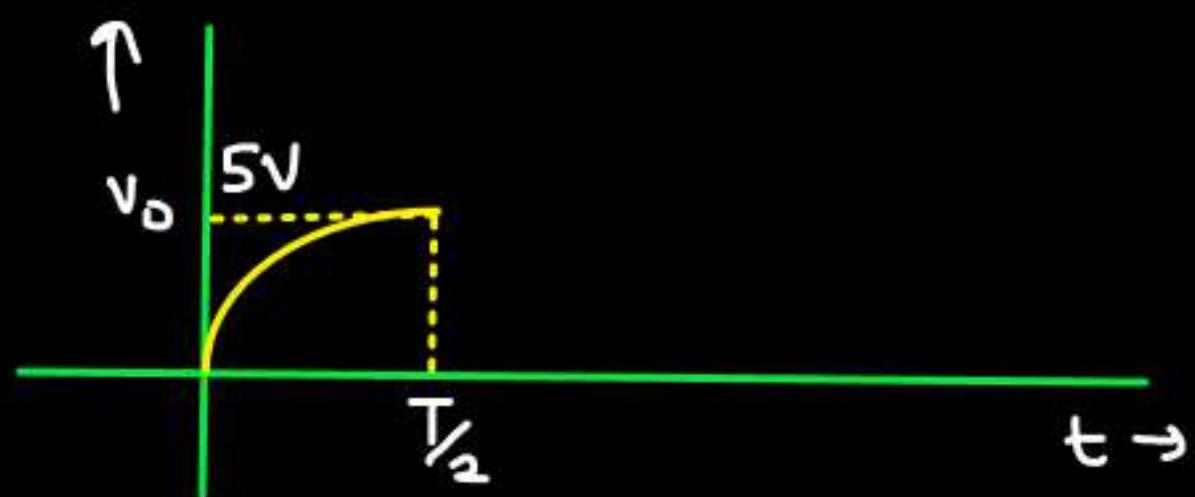


for $T_2 < t < T$


$$V_L = 0V$$

$$V_C(T_2) = V_C(T_2^+) = 5V$$

But if P is gone.

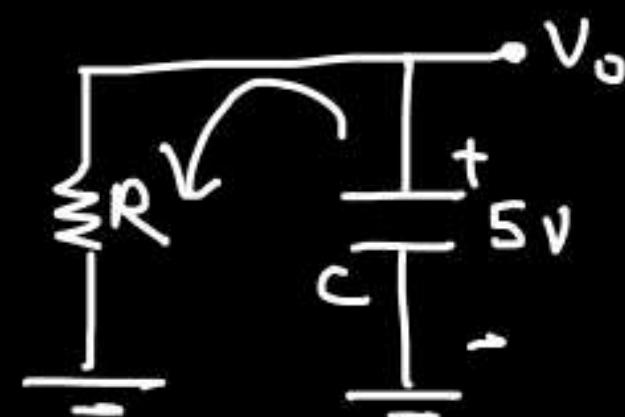

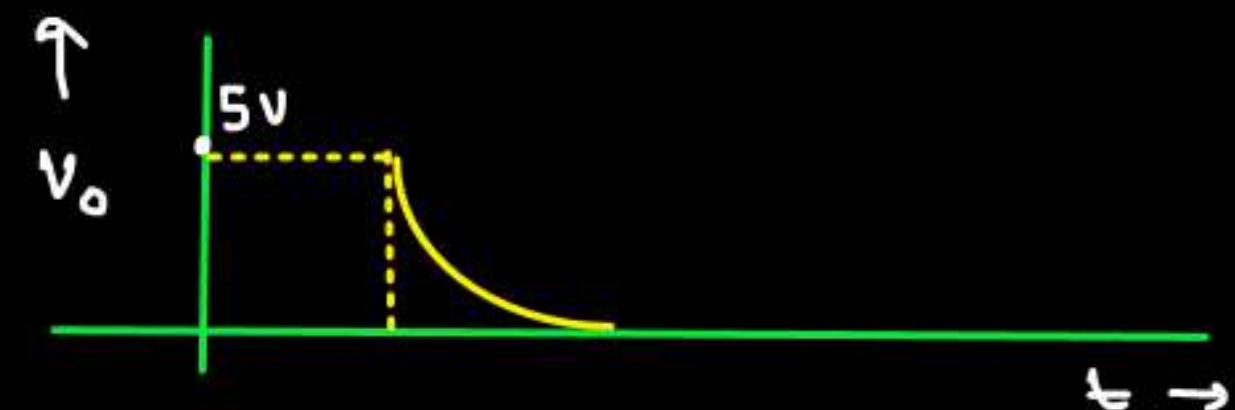⇒ Cap ^{Preassumption} will get completely discharged.
(Because T is very large)






For $T \leq t < 3T/2$

$$V_c(T) = 0 = V_c(T^+)$$

$$V_i = 5V$$

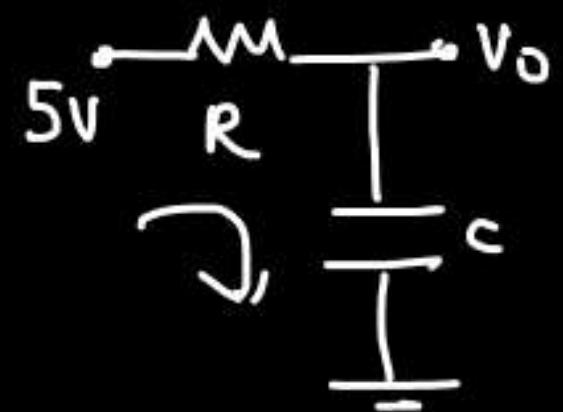


cap will again charge to 5V

$$V_c(3T/2) = 5V$$

For $3T/2 \leq t < T$


$V_i = 0V$, $V_c(3T/2) = 5V \Rightarrow$ The cap. will discharge to 0V.

This cycle goes on =

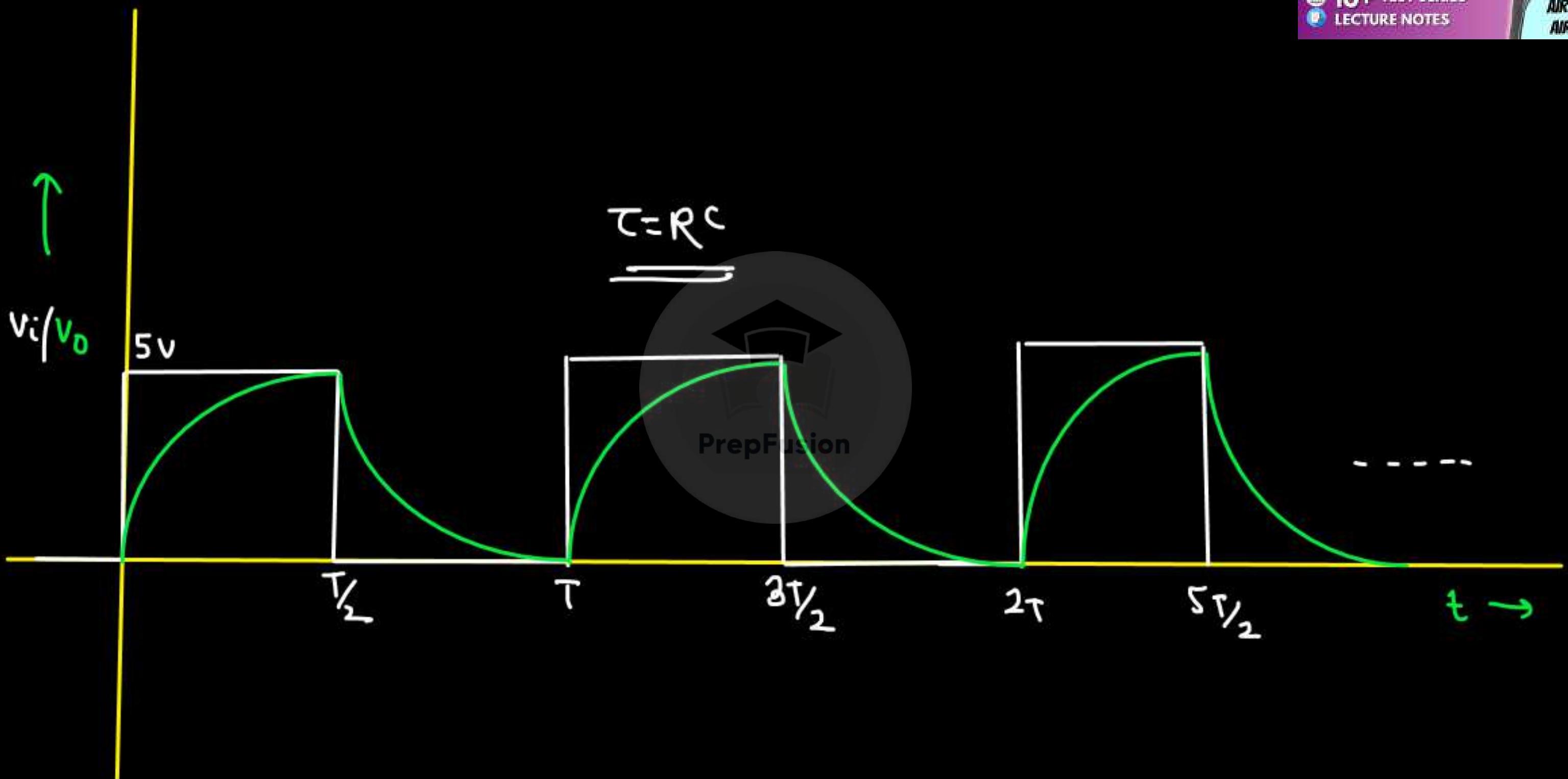



① $T \ll RC$:-

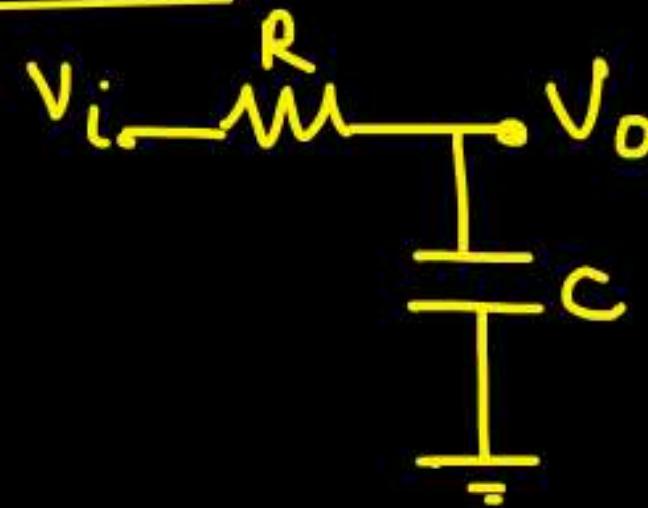


$$RC = 2 \text{ sec.}$$

$$T = L \text{ sec.}$$

$$\frac{T}{2} = 0.5 \text{ sec.}$$


would be given.

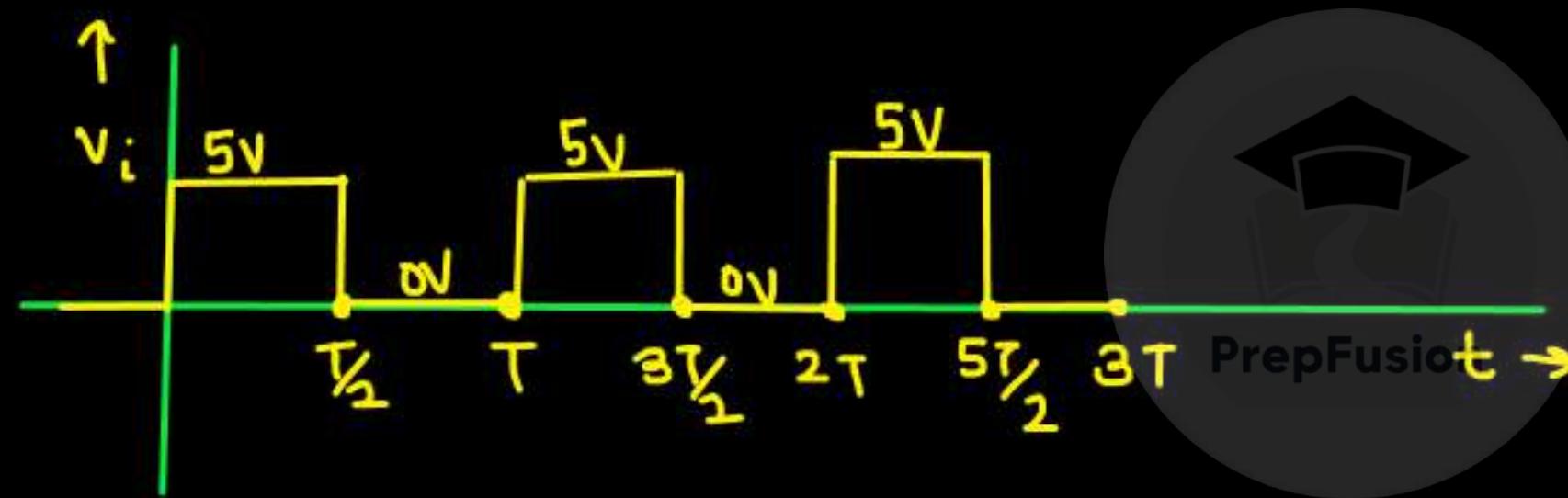

for $0 < t < \frac{T}{2}$

$$V_i = 5V$$

$$T \ll RC$$

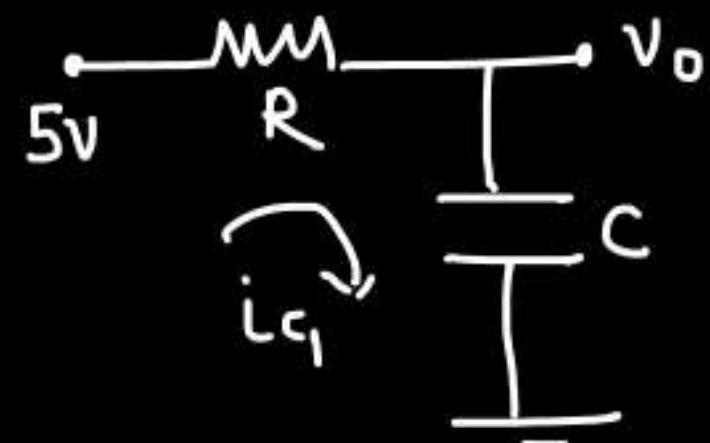


now since T is less and time constant is large.
 \Rightarrow cap will try to charge upto 5v but will not be able to reach there.

↳ depending on the values of T and RC ,

$$\text{let } V_c(T_{1/2}) = L \text{ v}$$

$$i_{c_1}(0^+) = \frac{5}{R} =$$


↳ charging current

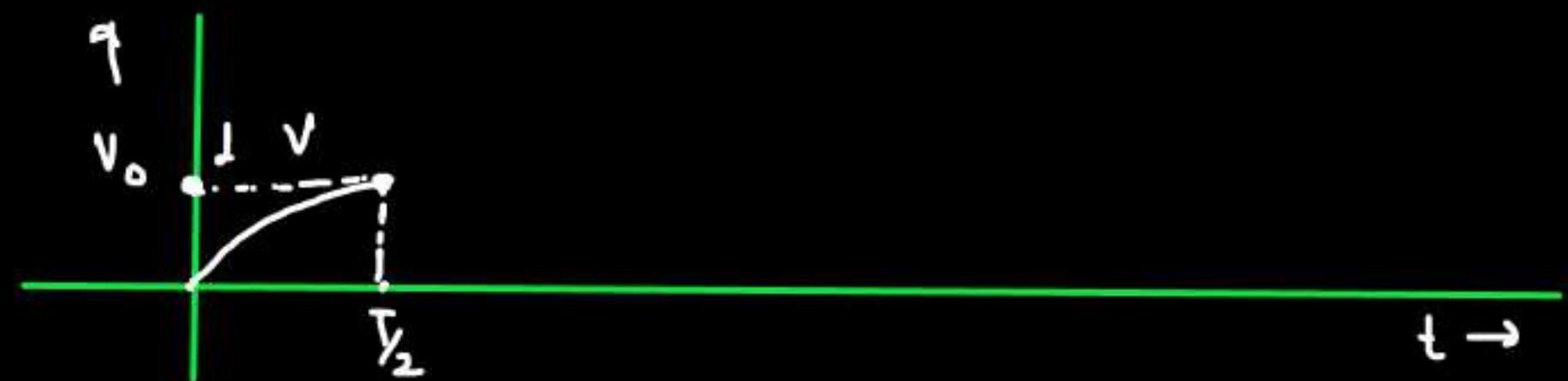

for $\frac{T}{2} < t < T$

$$V_i = 0 \text{ V}$$

$$V_c(\frac{T}{2}^+) = 1 \text{ V}$$

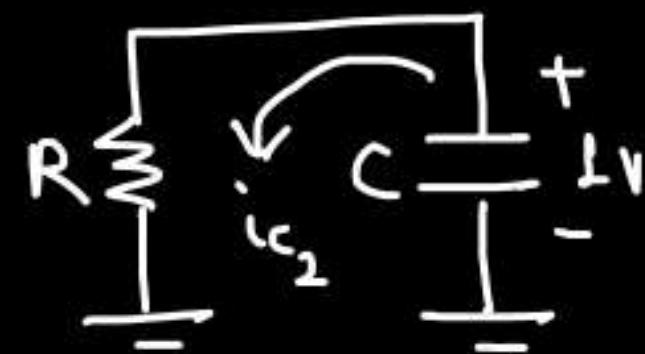


since T is very less, C will not be able to discharge to zero.

$$V_c(T) = 0.8 \text{ V}$$

$$i_{C2}(\frac{T}{2}^+) = \frac{L}{R} \Psi$$


↳ discharging current

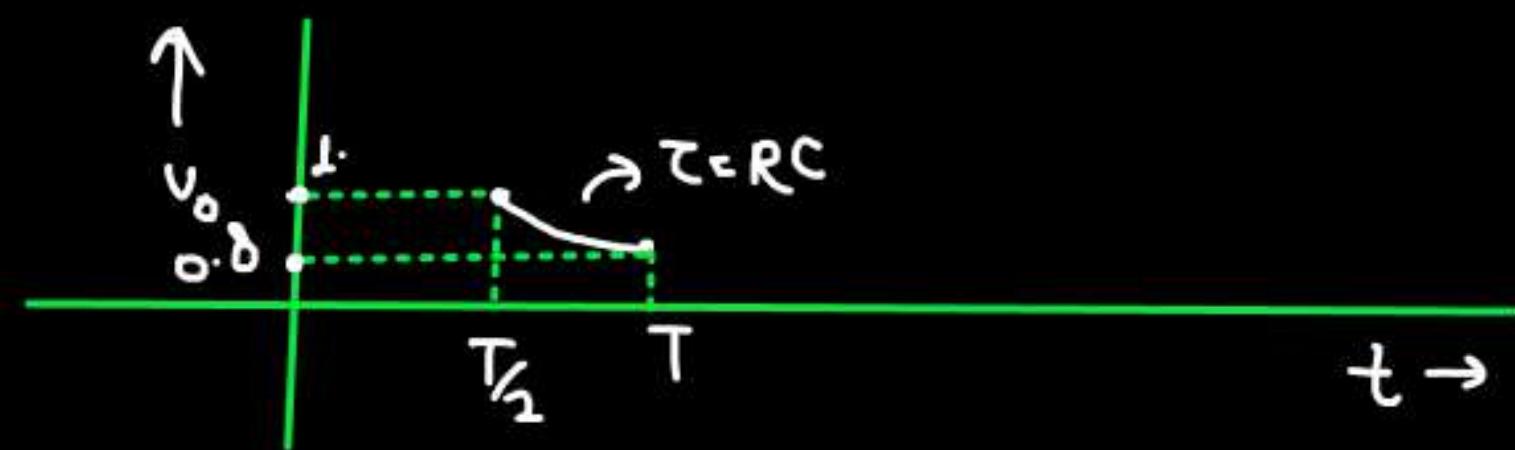

for $T \leq t < 3T/2$


$$V_L = 5V$$

$$v_c(T^+) = 0.8V$$

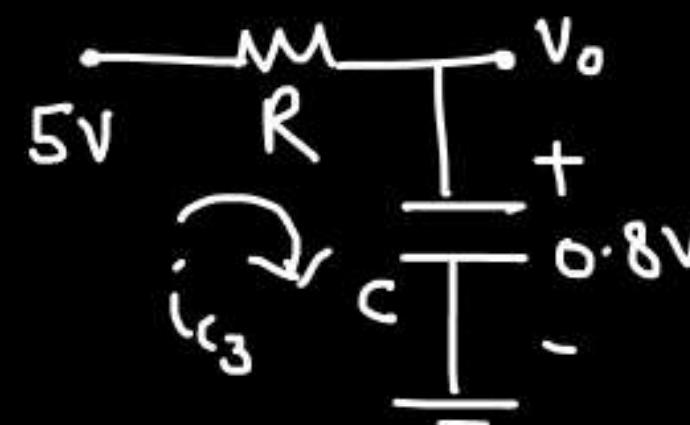

The cap will try to charge but can't reach upto 5V.

$$\text{net;} v_c(3T/2^+) = 1.5V$$

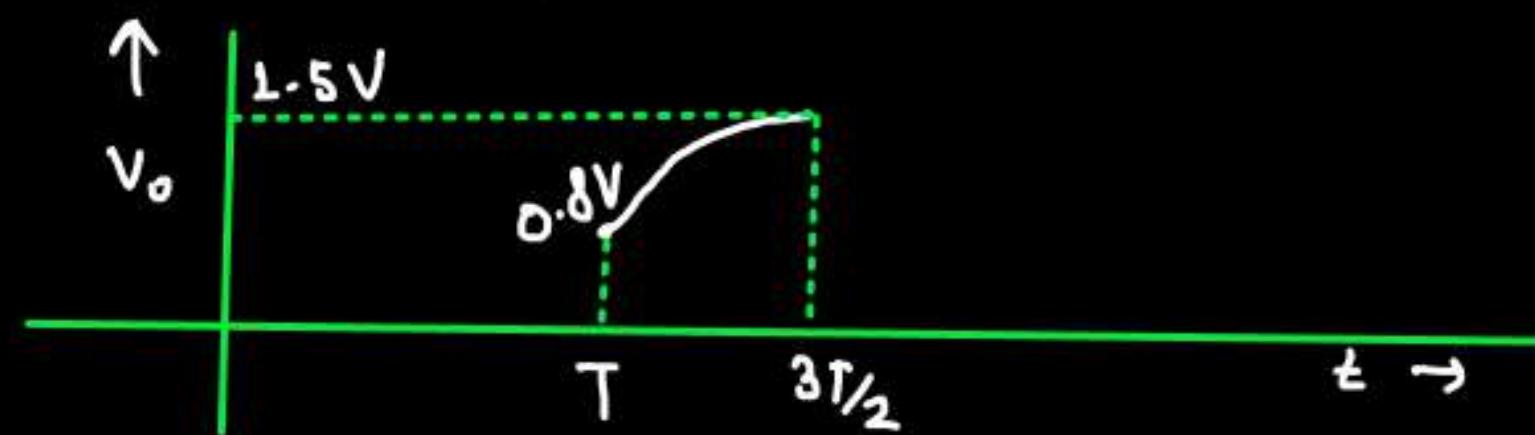


$$i_{c_3}(T^+) = \frac{4.2}{R} \rightarrow \text{charging current}$$



for $3T/2 \leq t < 2T$


$$V_{i=0} ; V_c(3T/2^+) = 1.5V$$

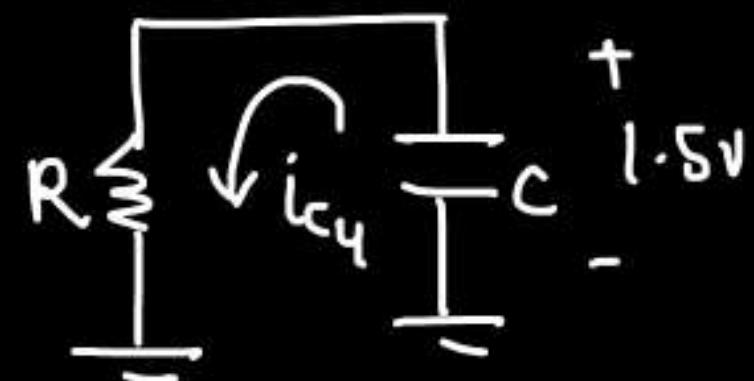

V_c will try to go till zero voltage but can't reach there.

$$V_c(T) = 1.1V$$
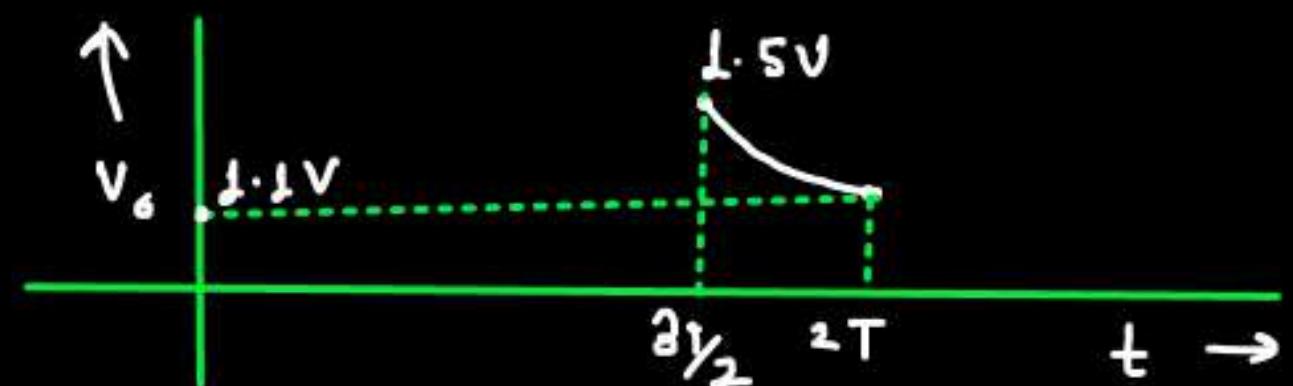
$$i_{C4}(3T/2) = 1.5/R \rightarrow \text{discharging}$$



for $2T < t \leq 5T/2$

$$i_{C5}(2T) = \frac{5 - 1.1}{R} = \frac{3.9}{R} \rightarrow \text{charging current}$$

Net cap. charges from 1.1V to 1.6V

for $5T/2 < t \leq 3T$

$$i_{C6}(5T/2) = \frac{1.6}{R} \rightarrow \text{discharging current}$$

PrepFusion

charging current $\Rightarrow \frac{5}{R} \rightarrow \frac{4.2}{R} \rightarrow \frac{3.9}{R}$


discharging current $\Rightarrow \frac{1}{R} \rightarrow \frac{1.5}{R} \rightarrow \frac{1.6}{R}$

with continuous cycle,
charging current \textcircled{J}

discharging current \textcircled{P}

at some time;

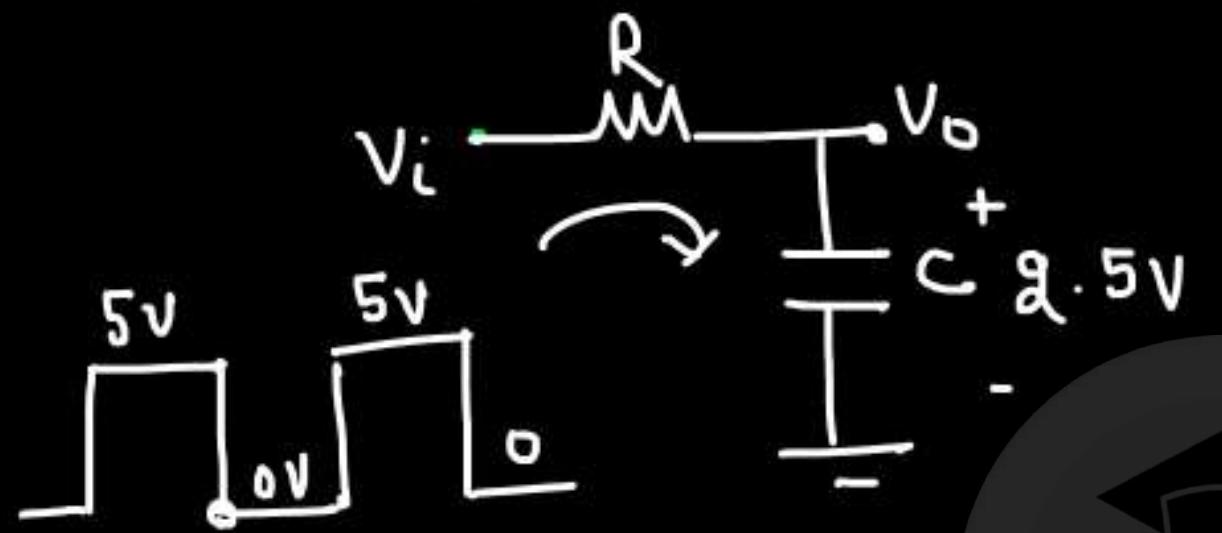charging current = discharging current = $2.5/R$




when $V_i = 5V \Rightarrow i_c = 2.5/R \rightarrow$ charging current

when $V_i = 0V \Rightarrow i_c = -2.5/R \rightarrow$ discharging current



steady state
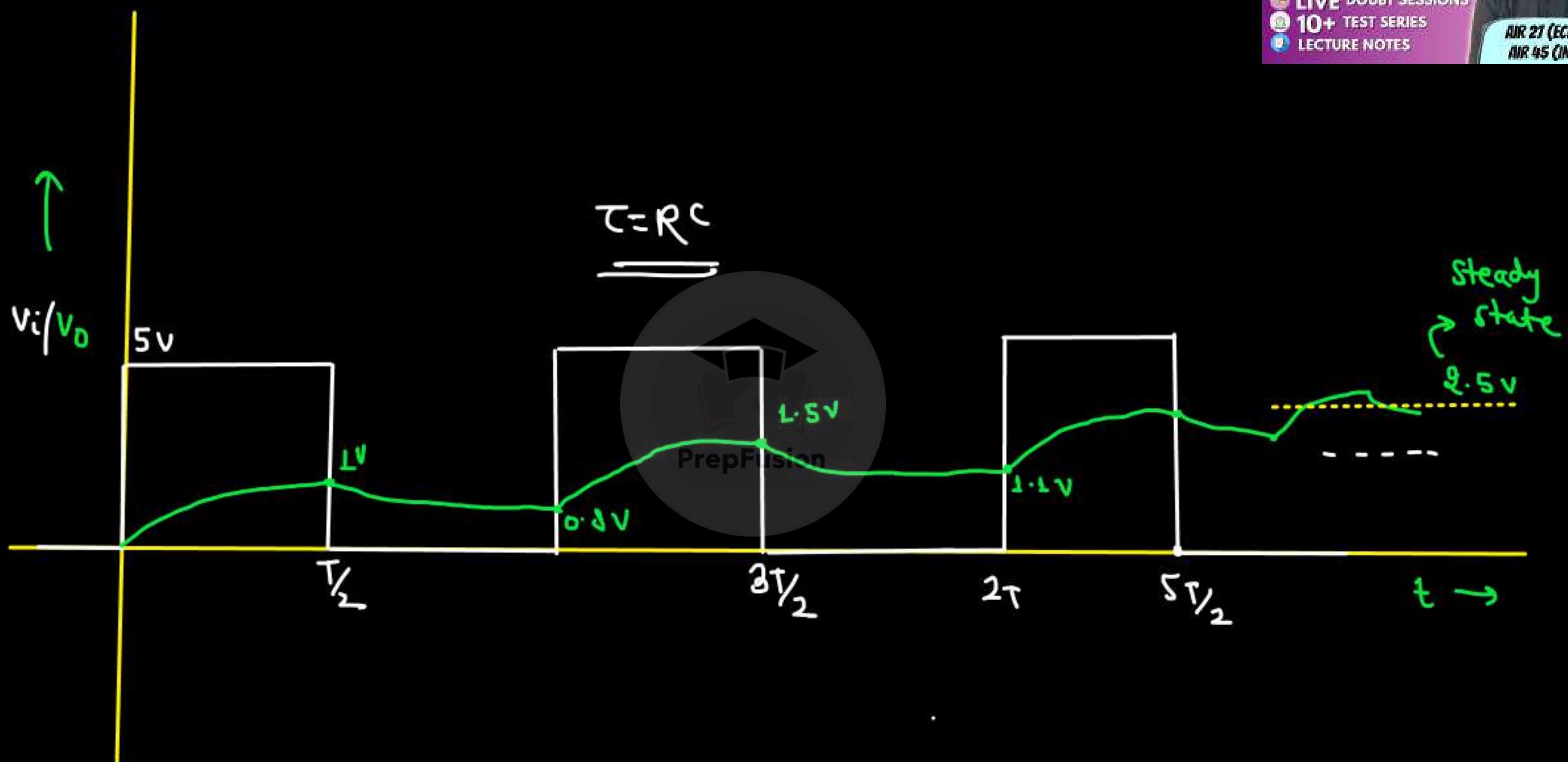
$$V_c (\text{ steady state}) \approx 2.5V$$





conclusion

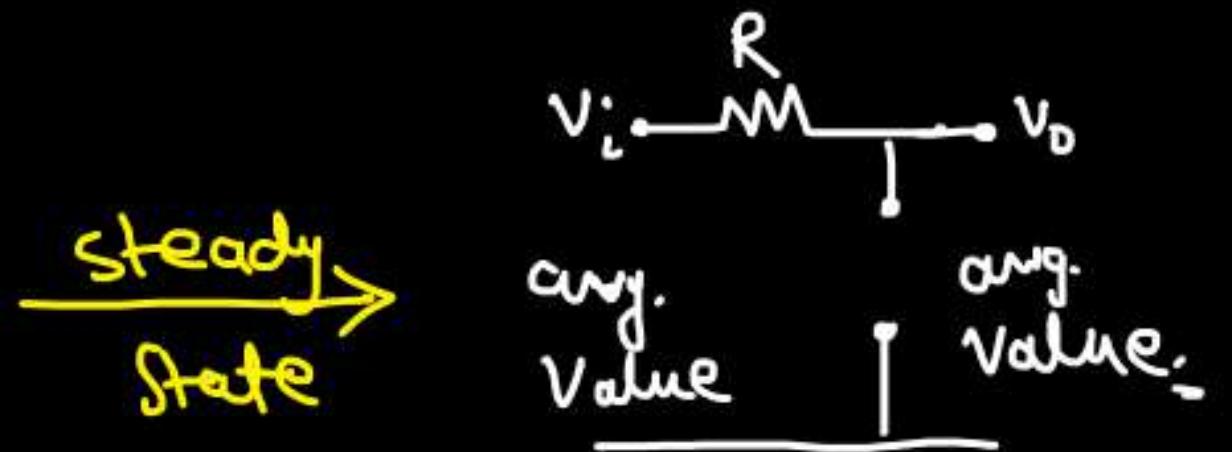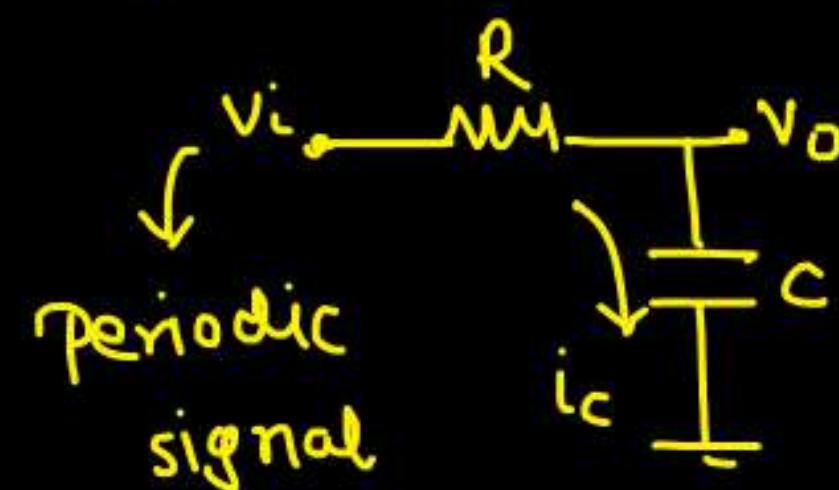


$$\rightarrow [V_o]_{\text{avg.}}|_{\text{S.S.}} = [V_i]_{\text{avg.}}$$

$$[(i_c)_{\text{avg.}}]_{\text{S.S.}} = 0 \text{ Amp}$$


$$[(V_R)_{\text{avg.}}]_{\text{S.S.}} = DV = \left\{ (V_R)_{\text{avg.}} = (i_c)_{\text{avg.}} \times R \right\}$$



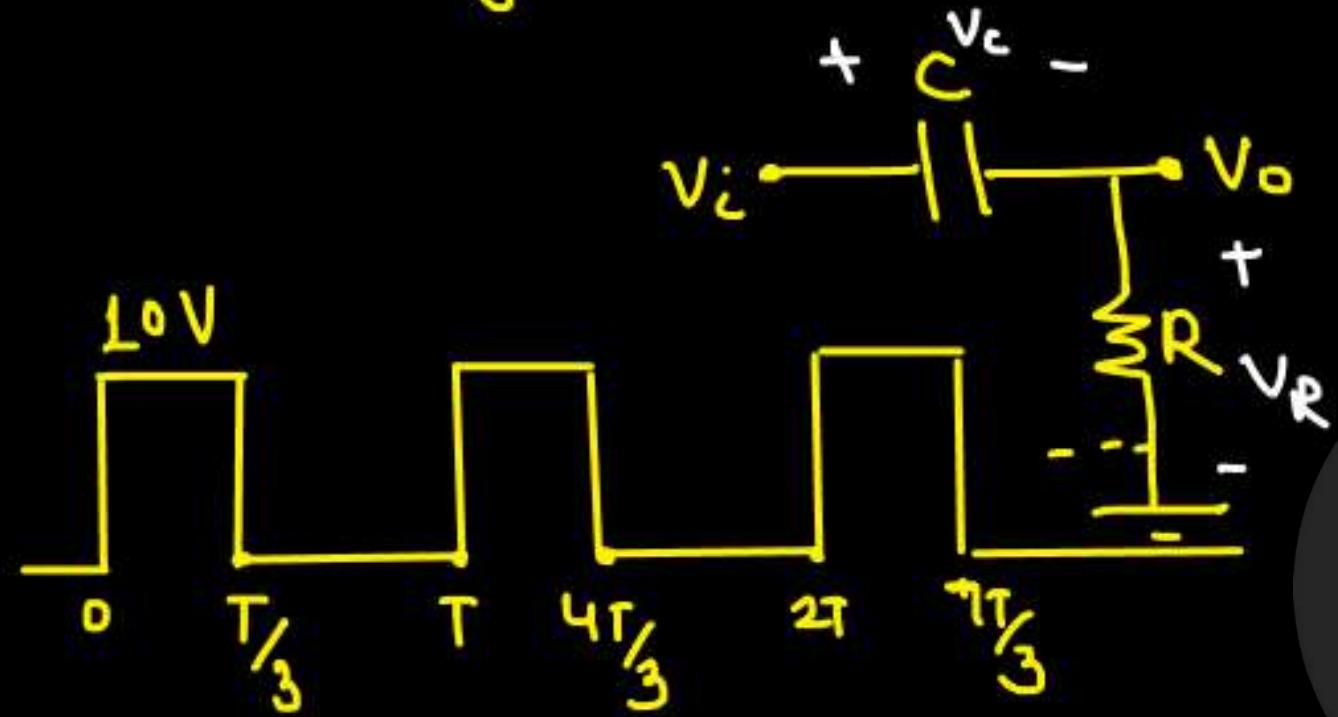Q. Find steady state avg. value of cap. voltage and voltage across resistor.




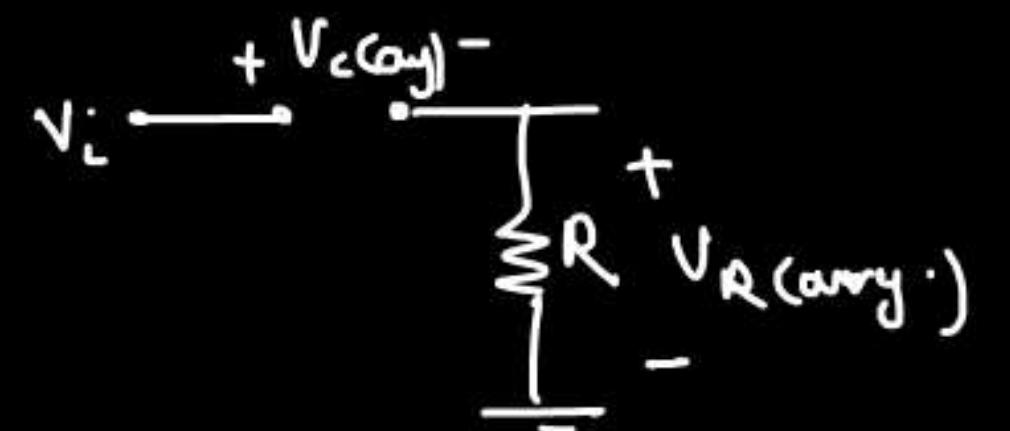→ @ steady state; $(i_c)_{avg} = 0 \text{ A}$; $(V_R)_{avg} = 0 \text{ V}$




$$\begin{aligned}
 (V_c)_{avg.} &= (V_i)_{avg.} \\
 &= \frac{(10 \times T/3) + (0 \times 2T/3)}{T} = \frac{10}{3} \text{ V}
 \end{aligned}$$

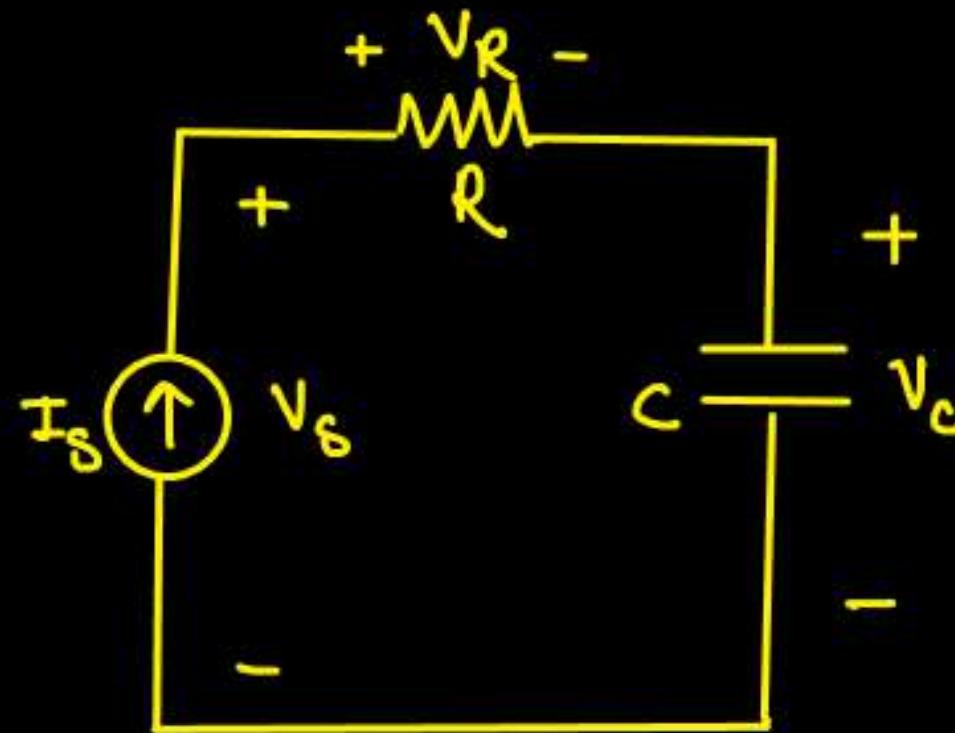- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES




Take $T = RC =$

V_C and $V_R = ?$

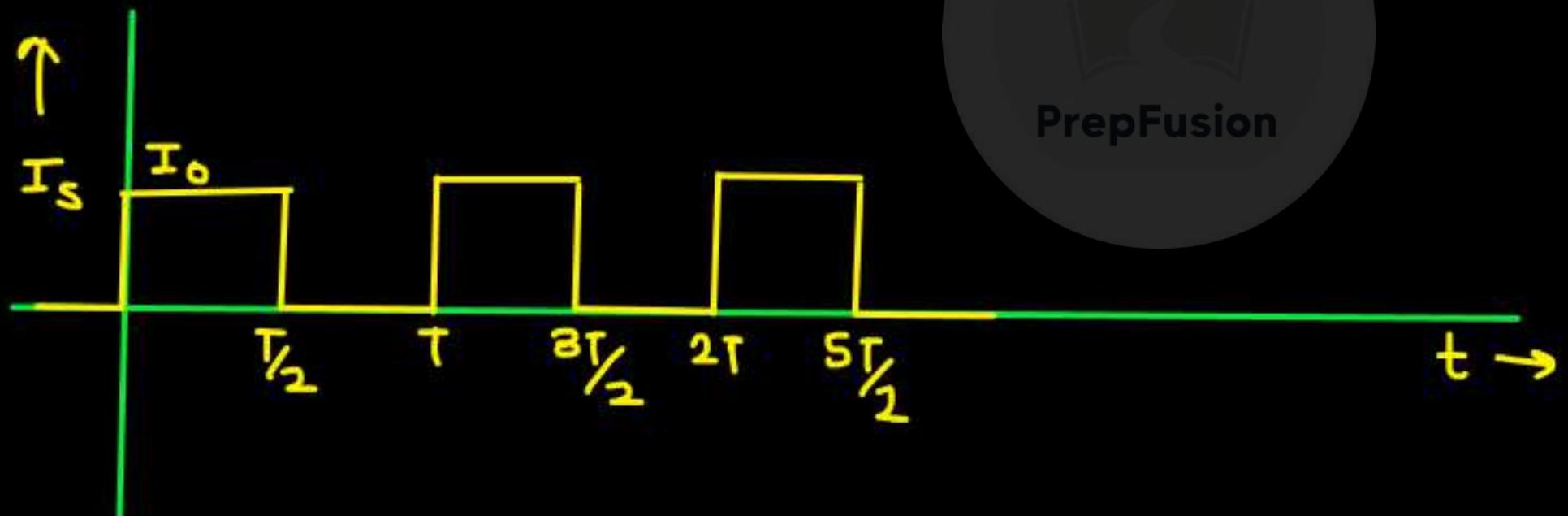




→

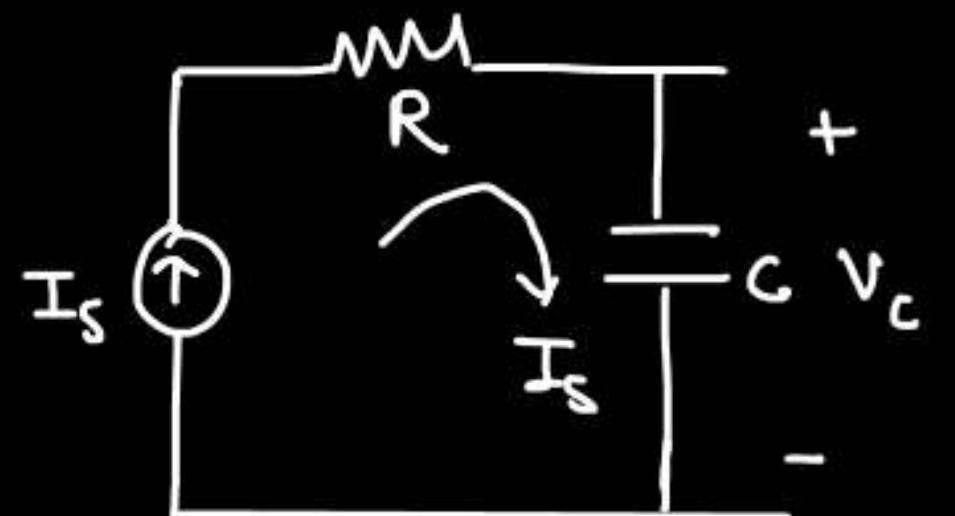

→ I_s current flows through the cap. and resistor forever

↳ constant current is flowing through the cap.

$$V_c(t) = \frac{1}{C} \int_0^t I_s dt$$

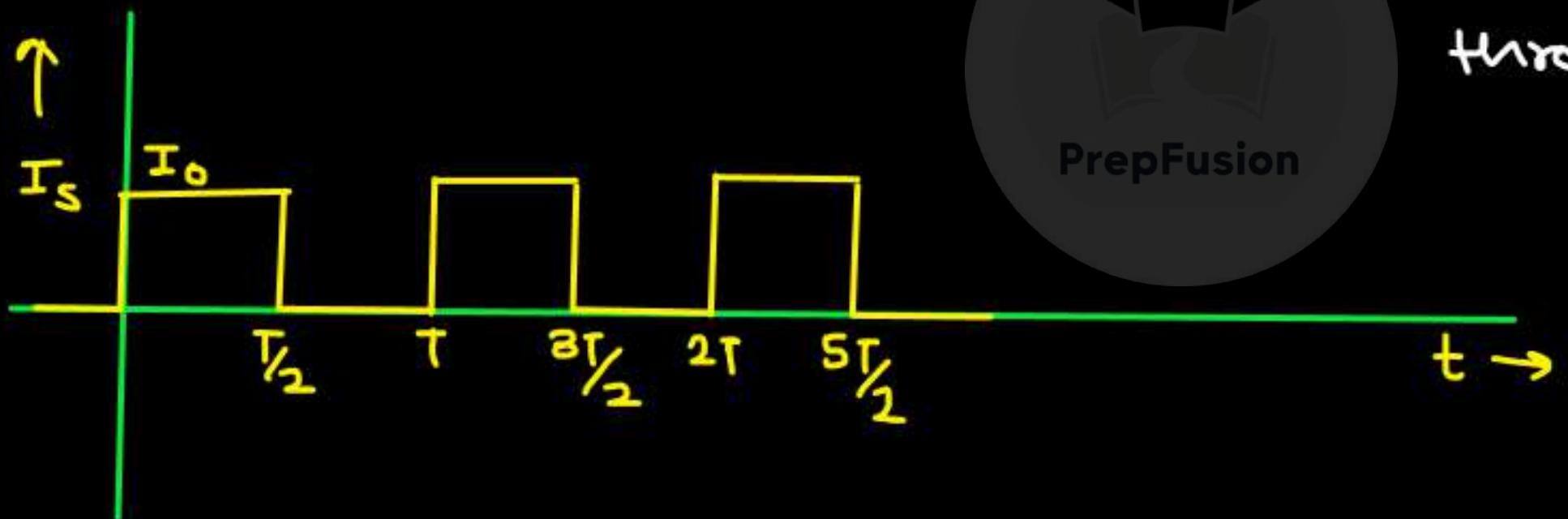

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



For $0 < t < T/2$


$$V_C(t) = \frac{1}{C} \int_0^t I_S dt$$

$$= \frac{1}{C} \int_0^t I_0 dt$$

$$V_C(t) = \frac{I_0 t}{C}$$


Given $T = RC$
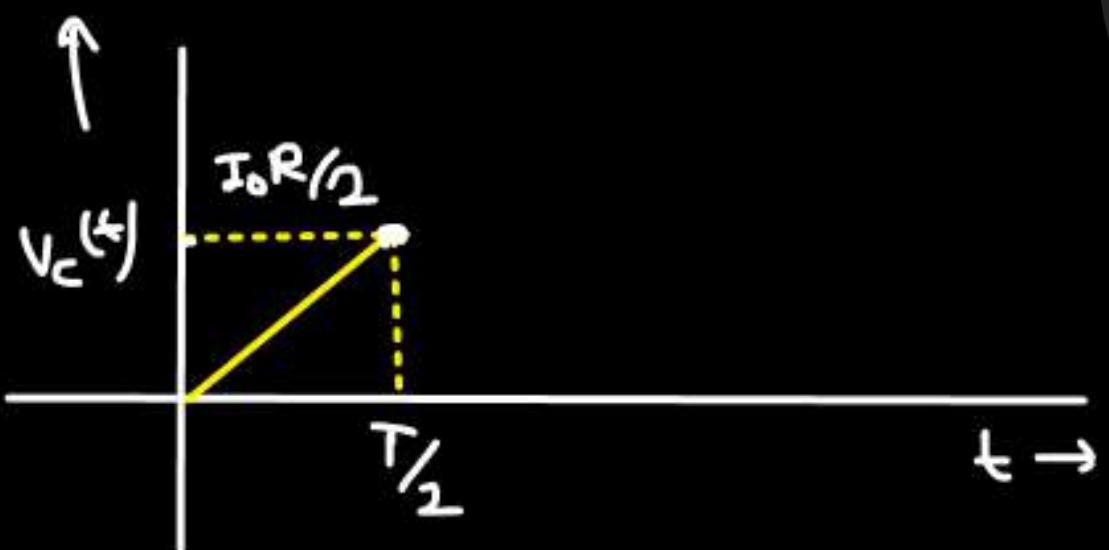
$$V_C(T/2) = \frac{I_0 T}{2C} = \frac{\frac{I_0 (RC)}{2}}{2C} = \frac{I_0 R}{2}$$




for $T/2 \leq t < T$

$$I_S = 0 \text{ A}$$

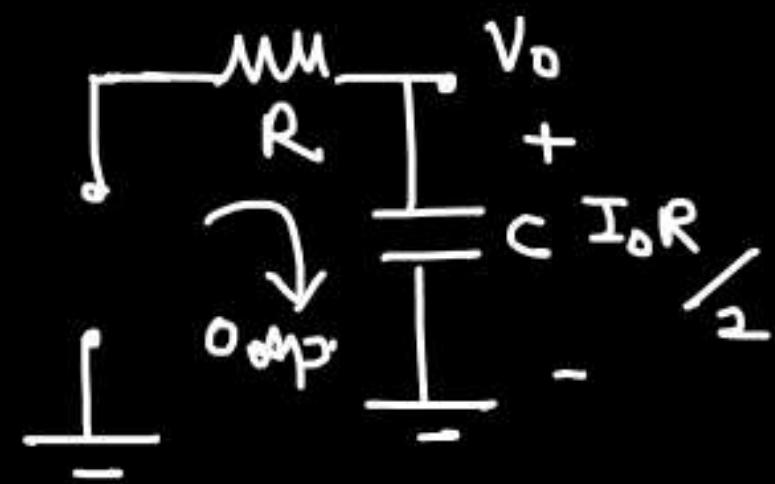

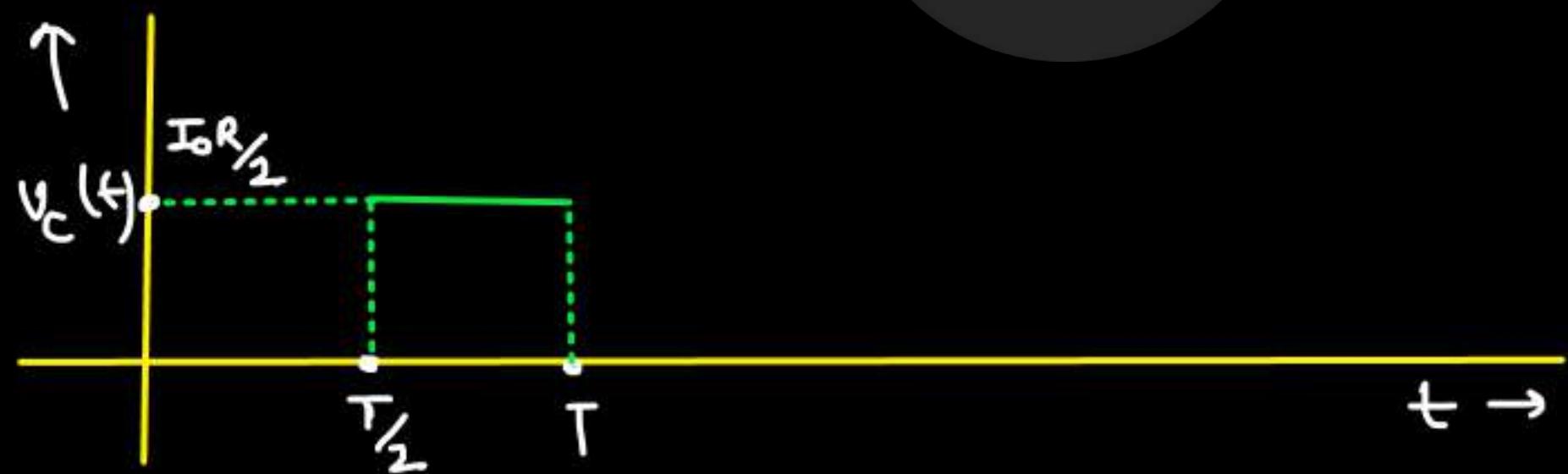\Rightarrow Cap. will neither discharge ; nor charge.







For $T \leq t < 3T_{1/2}$

$$V_C(T) = I_0 R / 2$$

$$I_S = I_0 \text{ A.P.}$$

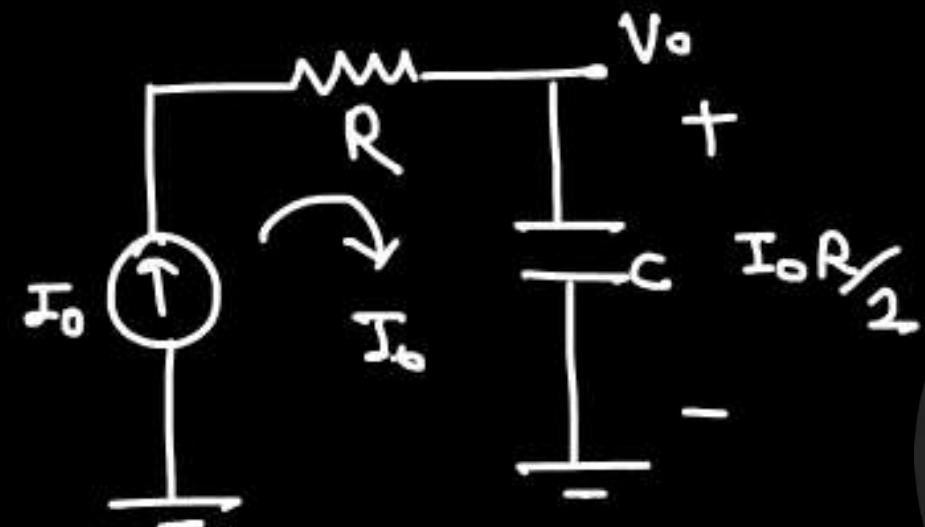

⇒ Cap. will charge.

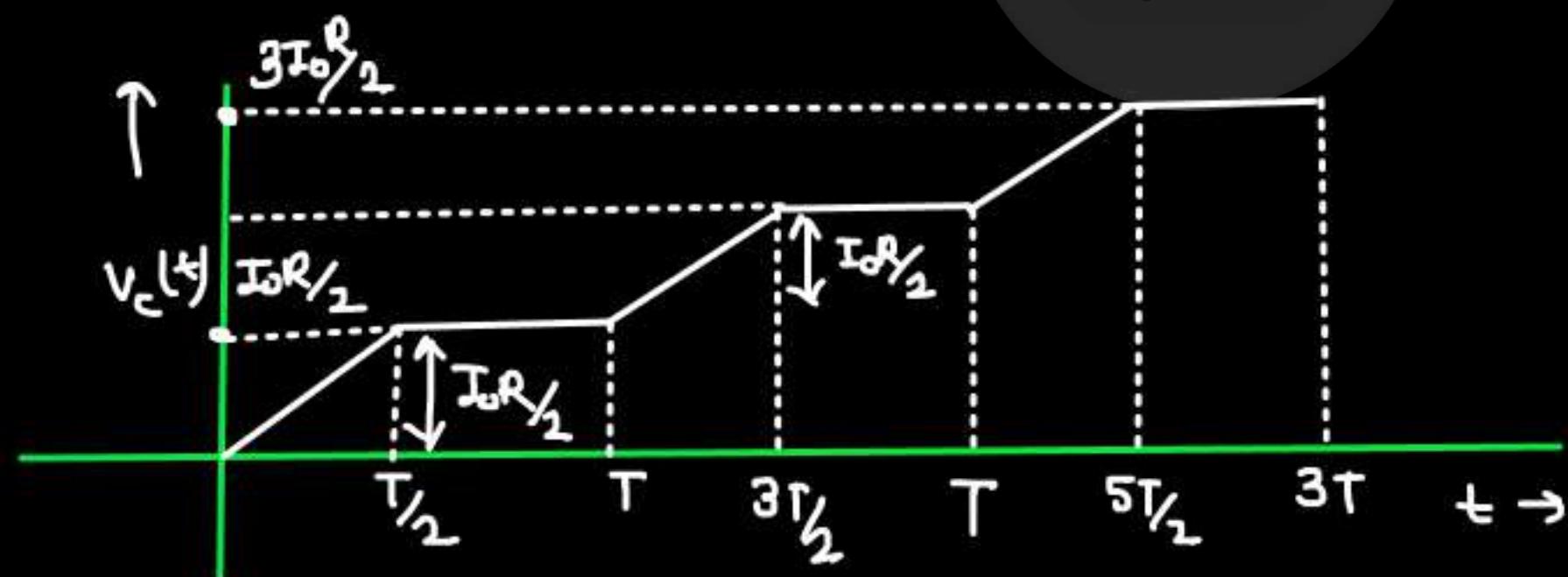

$$\begin{aligned} V_C(t) &= \frac{I_0 R}{2} + \frac{1}{C} \int_T^t I_0 \cdot dt \\ &= \frac{I_0 R}{2} + \frac{I_0}{C} [t - T] \end{aligned}$$

$$\begin{aligned} V_C(3T_{1/2}) &= \frac{I_0 R}{2} + \frac{I_0}{C} [T_{1/2}] \\ &= I_0 R \end{aligned}$$





- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

In every cycle, capacitor is developing $\frac{I_0 R}{2}$ Voltage.


capacitor voltage after n cycles of i/p = $n \frac{I_0 R}{2}$

V_R :-

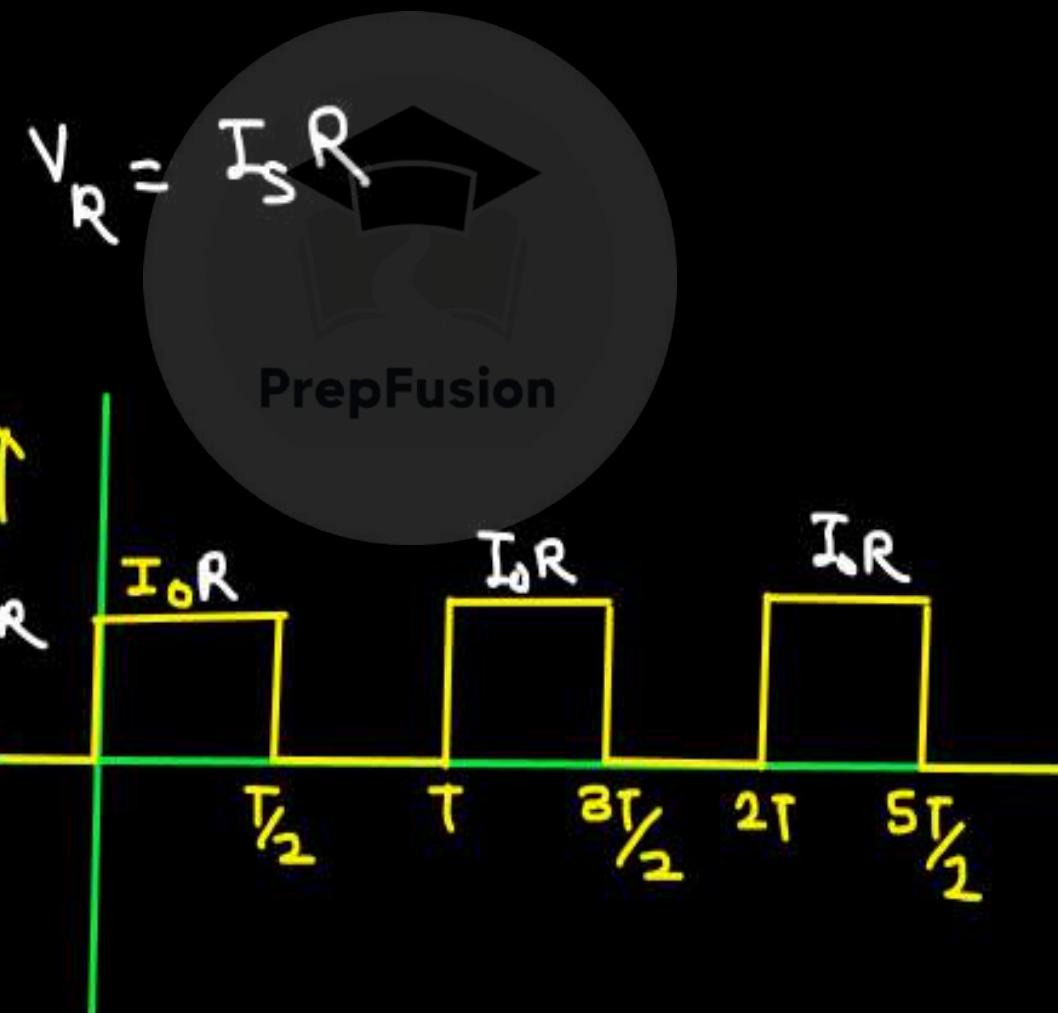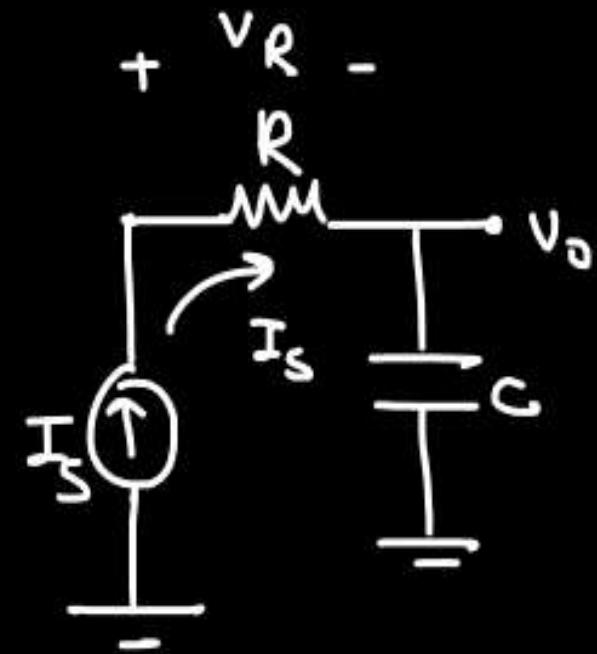

YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)

V_S :-

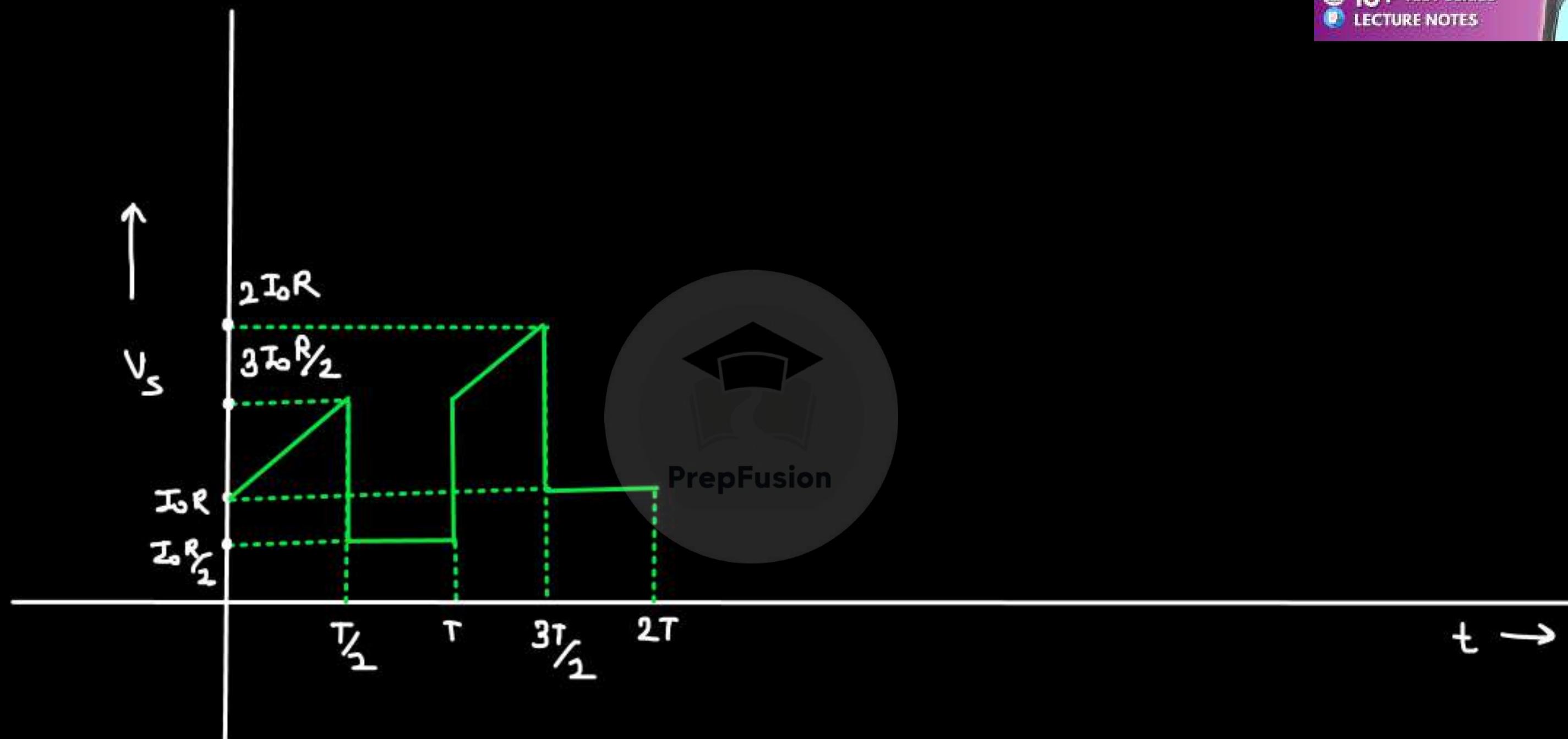

* Initial Value and Final Value Theorem :-

Q. Find the initial and final value of the

given $f(t) :- f(t) = [1 - e^{-at}] u(t)$

→ initial value ($t=0^+$) :-

$$f(0^+) = [1 - e^{-a(0)}] u(0^+)$$

$$= 0$$

Final value / steady state value / DC value ($t=\infty$) :-

$$f(\infty) = [1 - e^{-a(\infty)}] u(\infty)$$

$$= 1$$

* Initial Value Theorem:-

- i) Applicable only when $f(t) = 0 ; t < 0 \Rightarrow f(t) = f(0^+) \cdot u(t)$
- ii) $f(t)$ should not contain any impulse or discontinuity at $t=0^+$

↳ Let $\mathcal{L}[f(t)] = F(s)$

then initial value $\lim_{t \rightarrow 0^+} f(t) = f(0^+) = \lim_{s \rightarrow \infty} s \cdot F(s)$

Eg. → ① Find initial value for $f(t) = e^{-2t} u(t)$.

$$\rightarrow f(0^+) = e^{-2(0)} u(0^+) = 1$$

$$F(s) = \frac{1}{s+2}$$

$$\lim_{t \rightarrow 0^+} f(t) = f(0^+) = \lim_{s \rightarrow \infty} s \cdot F(s) = \lim_{s \rightarrow \infty} \frac{s}{s+2} = 1$$



Q. $f(s) = \frac{s^2 + 12s + 36}{s+6}$

initial value ?

$$\rightarrow f(s) = \frac{(s+6)^2}{s+6} = s+6$$

$$\hookrightarrow f(t) = s'(t) + 6\delta(t)$$

\hookrightarrow impulse @ $t=0$

Q. $f(s) = \frac{s^2 + 7s + 12}{s+2}$

$$\rightarrow f(s) = \frac{(s+4)(s+3)}{s+2}$$

$$= \frac{(s+2+2)}{s+2} (s+3) = \left(1 + \frac{2}{s+2}\right) (s+3) = (s+3) + 2 \frac{(s+2+1)}{s+2}$$



$$= S + 3 + 2 \left[1 + \frac{1}{S + 2} \right]$$

$$= S + 5 + \frac{2}{S + 2}$$

$$f(t) = g'(t) + 5\delta(t) + 2e^{-2t} u(t)$$

↳ impulse @ $t=0$

⇒ initial value theorem is not applicable.

N.B.- In Laplace transform f^H :- when

Degree of Num > Degree of den

↓
Time domain f^H will always have an impulse / differentiation of impulse
(discontinuity @ $t=0$)



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

$$F(s) = \frac{N(s)}{D(s)}$$

Degree (N(s)) < Degree (D(s))

→ For initial value Theorem
to be applicable

Eg → $F(s) = \frac{s+c}{s^2 + 7s + 12}$ Find $\lim_{t \rightarrow 0^+} f(t)$ or initial value.

$$\rightarrow f(0^+) = \lim_{s \rightarrow \infty} s F(s) = \lim_{s \rightarrow \infty} \frac{s^2 + cs}{s^3 + 7s^2 + 12s}$$

$$= \lim_{s \rightarrow \infty} \frac{s^2}{s^3}$$

$$f(0^+) = \lim_{s \rightarrow \infty} \frac{1}{s} = 0$$


YouTube -PrepFusion
(CLICK HERE FOR FULL PLAYLIST)

Final value Theorem :-

- i) Signal should not be unbounded or periodic.
- ii) Pole of $f(s)$ should lie in left Half of S-plane.
- (iii) $f(s)$ should have max one pole at the origin.


$$f(s) = \frac{1}{s(s+2)(s-3)}$$

Poles: $\rightarrow -2, 3, 0$

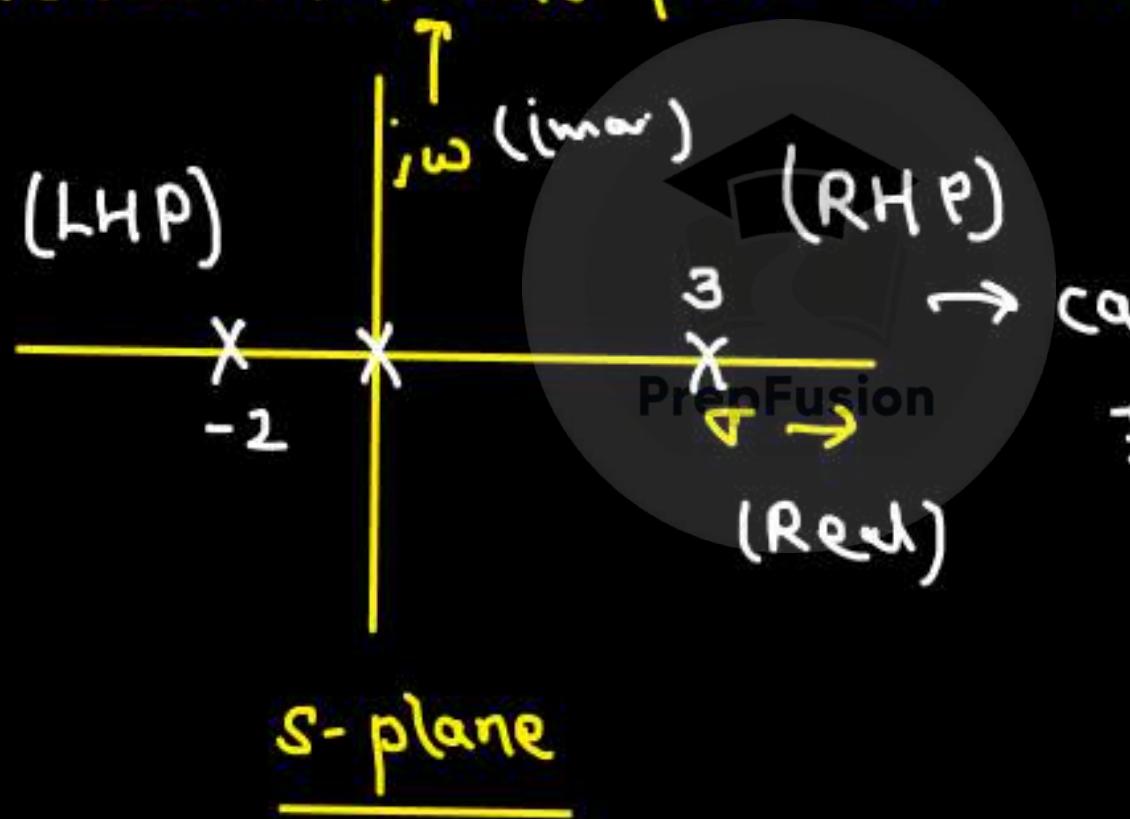

↳ Final value $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$

can't apply
final value
Theorem

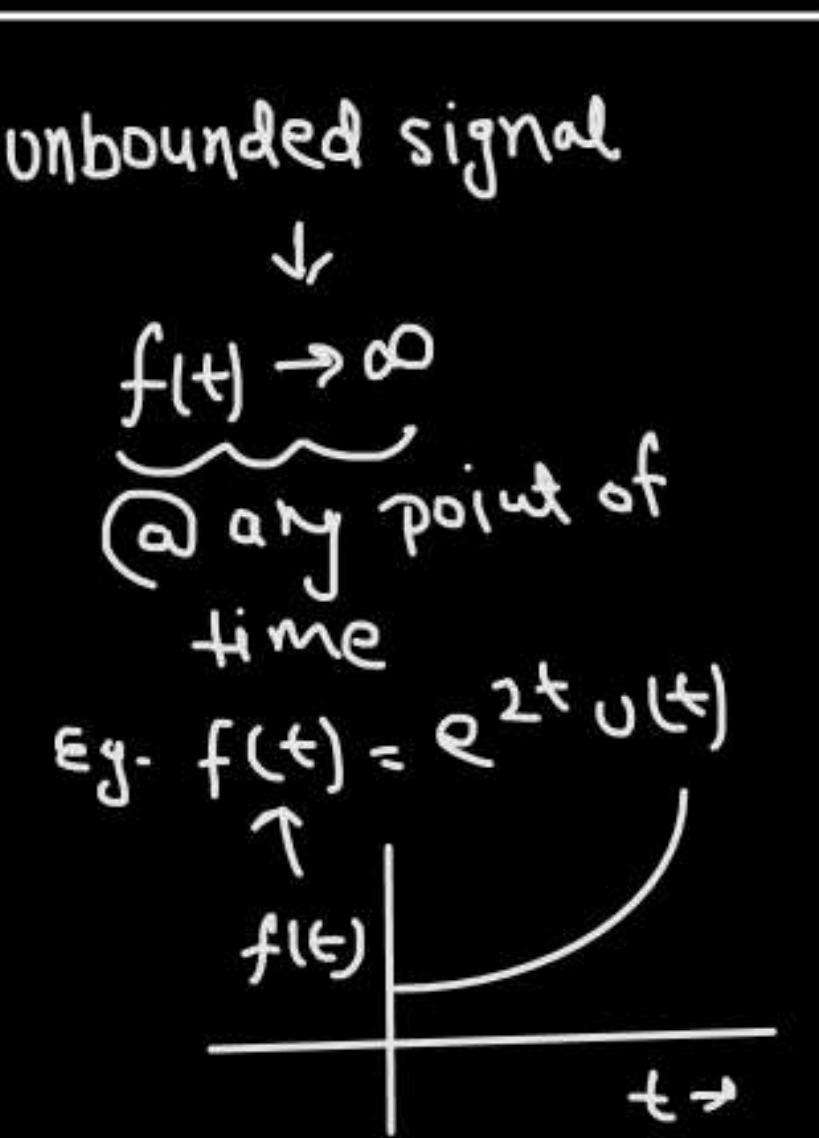



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

Q. $f(t) = e^{-2t} u(t)$. Find steady state value.

$$f(\infty) = e^{-\infty} u(\infty) \approx 0$$

$$F(s) = \frac{1}{s+2}$$

$$f(0) = \lim_{s \rightarrow 0} s \cdot F(s) = \lim_{s \rightarrow 0} \frac{s}{s+2} = 0 =$$

Q. $\mathcal{F}(s) = \frac{a}{s^2 + \omega^2}$. Find $f(\infty)$

\rightarrow

$$\mathcal{F}(s) = \frac{a}{s^2 + \omega^2}$$

$$f(t) = \sin \omega t u(t)$$

\uparrow periodic
~~final~~ $\sin \omega t$ \rightarrow



PrepFusion

$$\text{poles} \rightarrow s^2 + \omega^2 = 0$$

$$s = \pm j\omega$$

\hookrightarrow poles are not in L.H.P.

\Downarrow
Final value theorem not applicable



Eg →
$$\mathcal{F}(s) = \frac{s^2 + 6}{s(s^2 + 7s + 12)}$$


$$= \frac{s^2 + 6}{s(s+3)(s+4)}$$

→ $f(\infty) = \lim_{s \rightarrow 0} s \mathcal{F}(s) = \lim_{s \rightarrow 0} \frac{s^2 + 6}{(s+3)(s+4)}$

repulsion

$$= \frac{6}{12} = \frac{1}{2}$$

*
$$f(\infty) = \frac{1}{2}$$

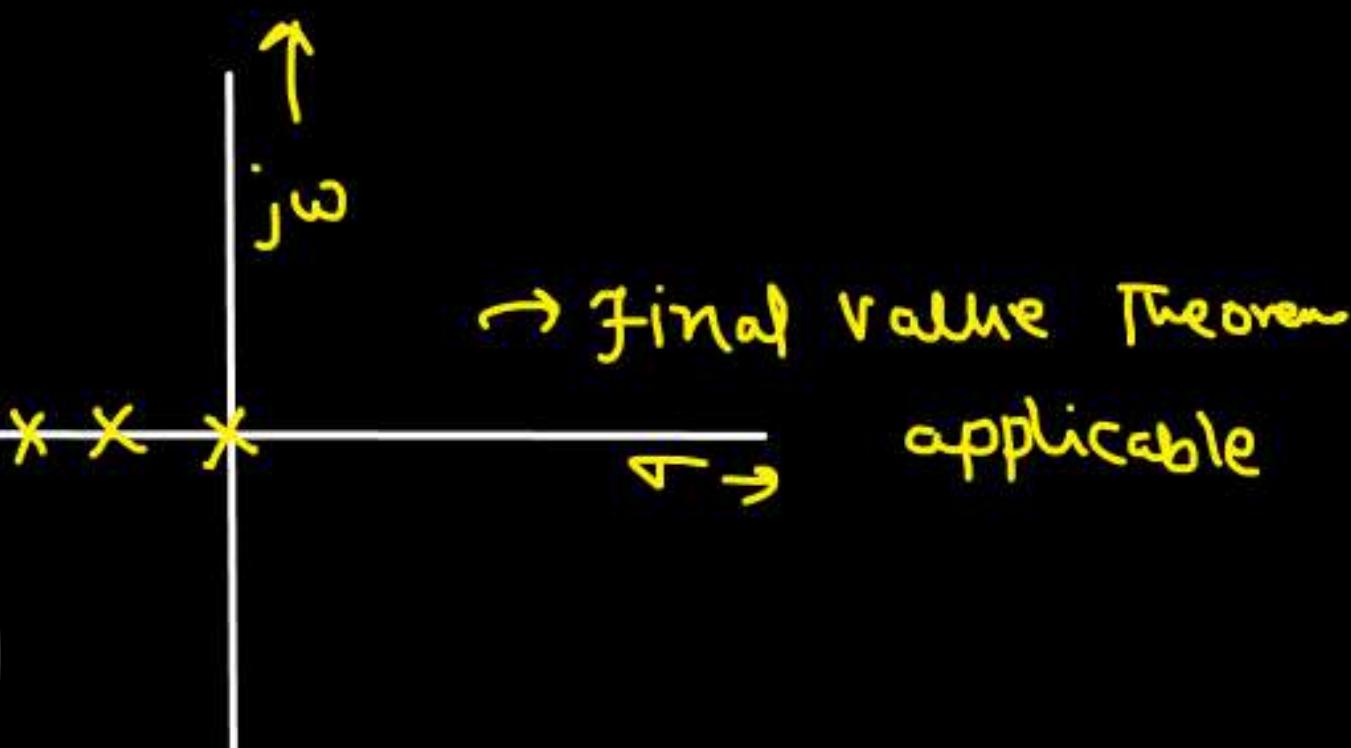


- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



AIR 27 (ECE)
AIR 45 (IN)

Q. Draw the waveforms.

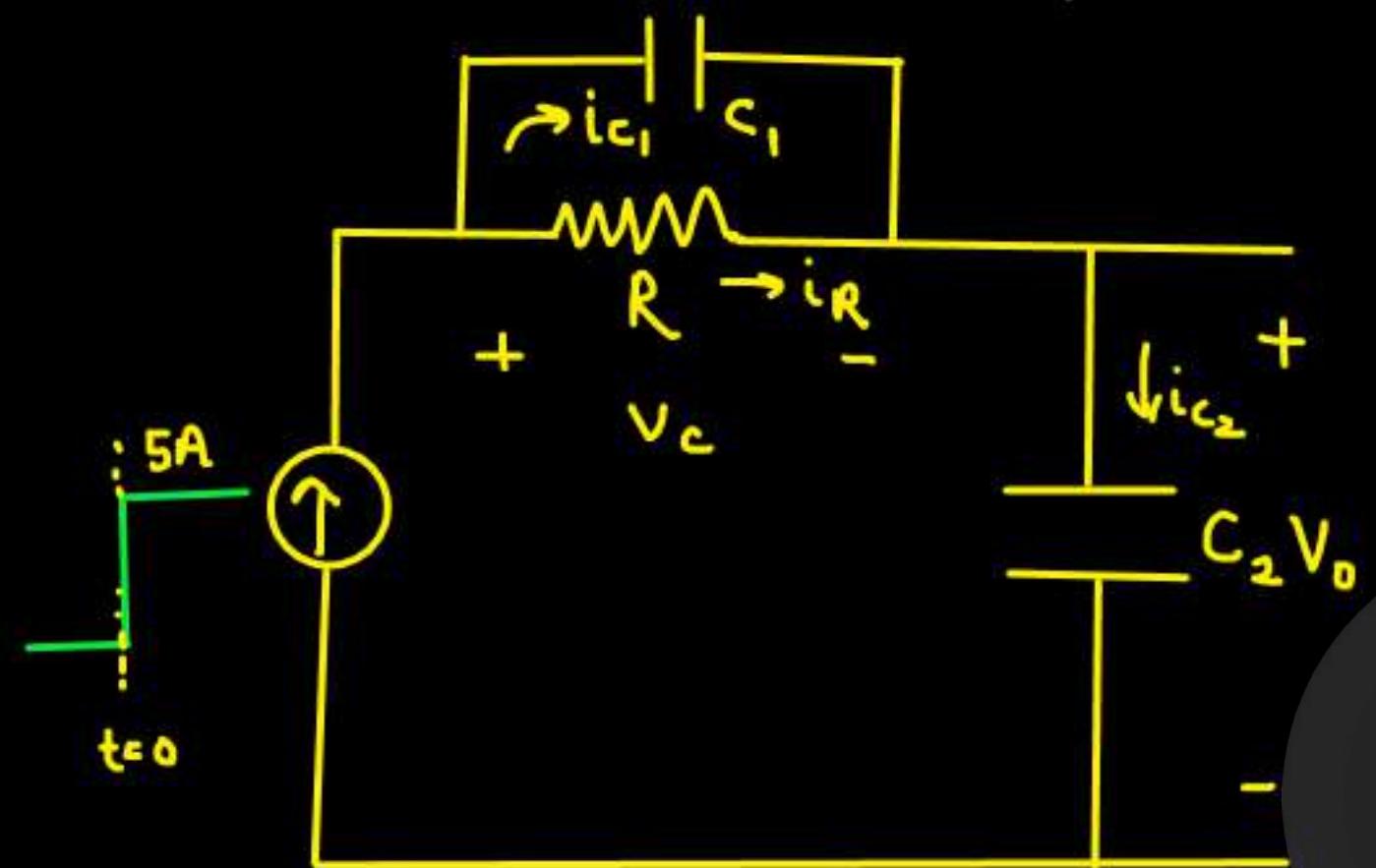

In-depth analysis of Inductors:-


Inductors :-

let's assume inductor is having I_0 current initially.



initial flux = μI_0
initial current = I_0

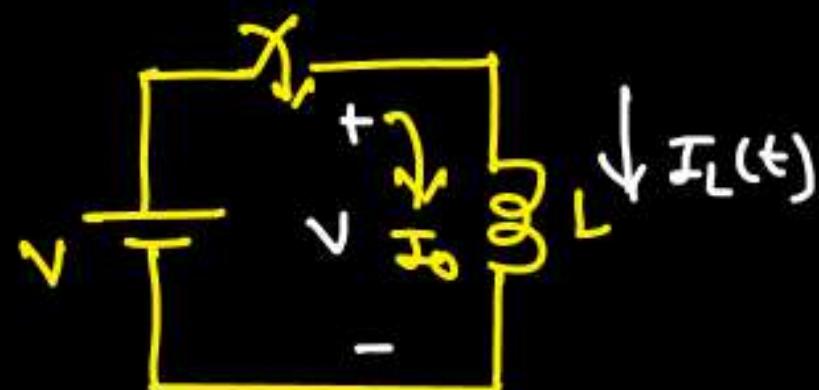now let's assume, we are forcing some voltage to the inductor.



$$I_L(t) = I_0 + \frac{1}{L} \int_{-\infty}^{\infty} v \cdot dt$$

when you force some voltage across inductor, it will develop current.

Properties of inductors:-

- ① Inductor is a flux storing element.
- ② When there is a finite voltage across the inductor-
(not impulse)

then,

$$I_L(t^-) = I_L(t) = I_L(t^+)$$

$$\text{But } V_L(t^-) \neq V_L(t^+)$$

PrepFusion

{ not necessarily equal}



The current across the inductor doesn't change instantaneously
but the voltage across the inductor can change instantaneously.



* Initial and Final Cond'n of an Inductor :-

* Initial Cond'n :-

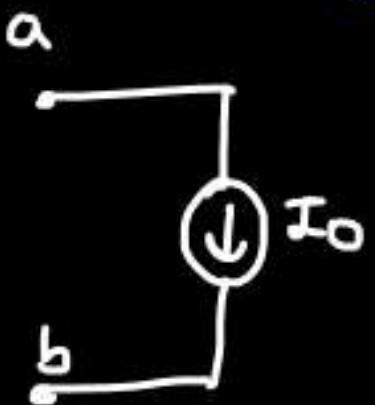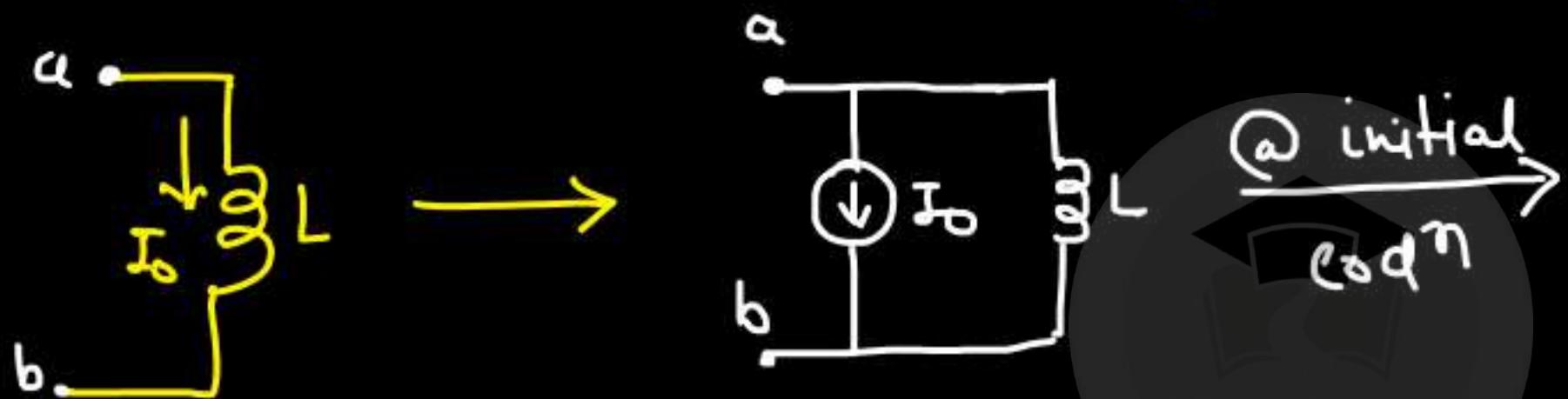Let's assume 'inductor' is having I_0 current initially:



So, initially an inductor is replaced with

↳ if there was no initial current.



Steady state of Inductor ($t = \infty$) :-

When there is zero voltage across the inductor

$$\downarrow I_r$$

The inductor will not develop further current.

$$\downarrow$$

The inductor has reached it's maximum current.

Steady state

So, @ Steady state, the current across the inductor will be constant and the voltage across the inductor will be zero.

↳ @ Steady state, inductor will be replaced by short ckt.



2nd Analogy:-

@ steady state, $I_L = \text{max value it can attain.}$

$$V_L = L \frac{dI_L(t)}{dt} \text{Fusion}$$

$$I_L = \text{max} \Rightarrow \frac{dI_L(t)}{dt} = 0$$



$$\Rightarrow V_L = 0 \text{ V}$$

summary:-

- @ $t=0 \Rightarrow$ inductor will be o.c.
 - @ $t=\infty \Rightarrow$ inductor will be s.c.
- } opposite to that of capacitor



Q. Write eqn for $I_L(t)$.

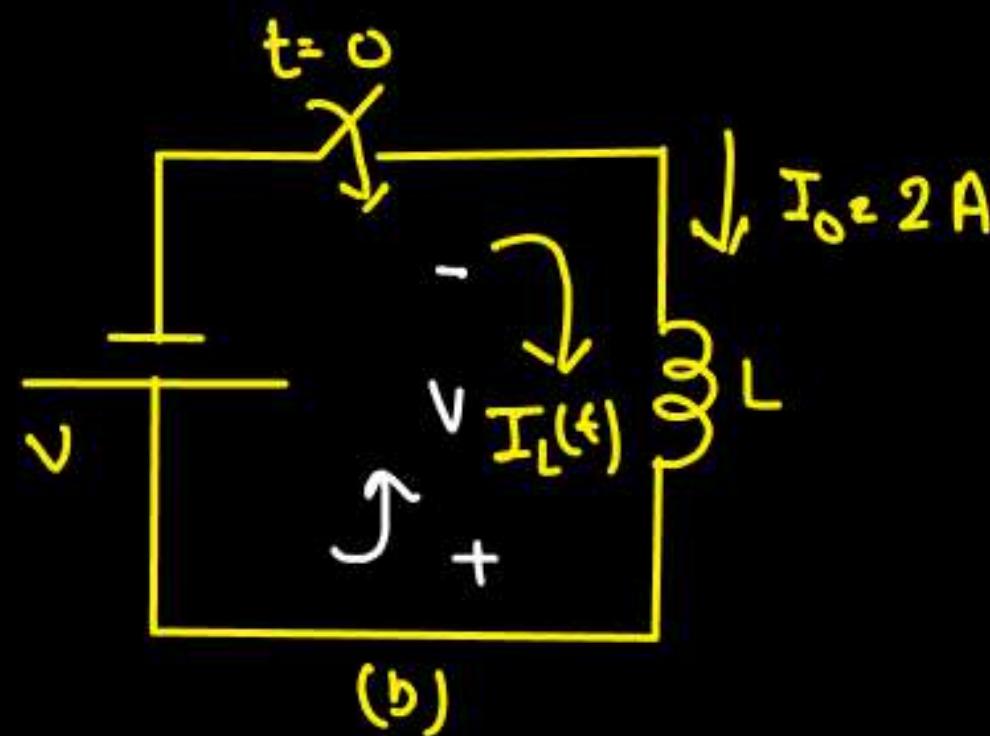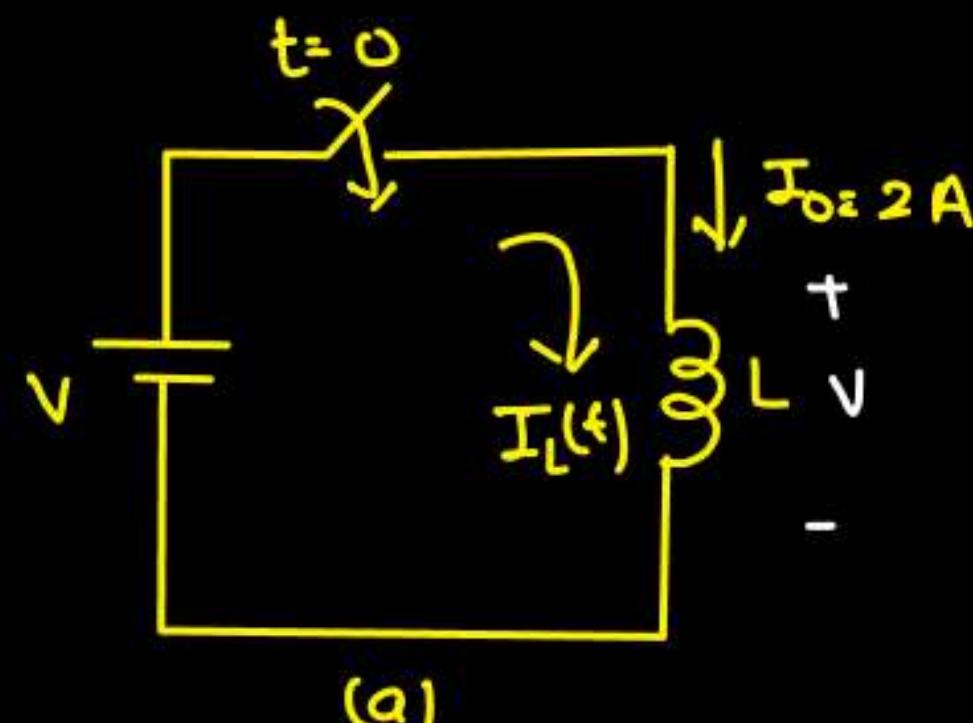



$$I_L(t) = I_0 + \frac{1}{L} \int_0^t V \cdot dt$$

$$= I_0 + \frac{Vt}{L} \quad \text{Ans.}$$




$$I_L(t) = 2 - \frac{1}{L} \int_0^t V \cdot dt$$


$$= 2 - \frac{Vt}{L} \quad \text{Ans.}$$

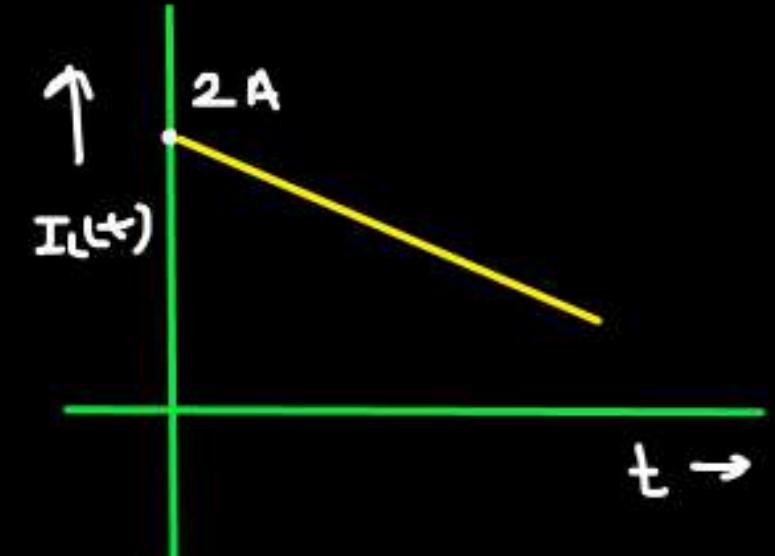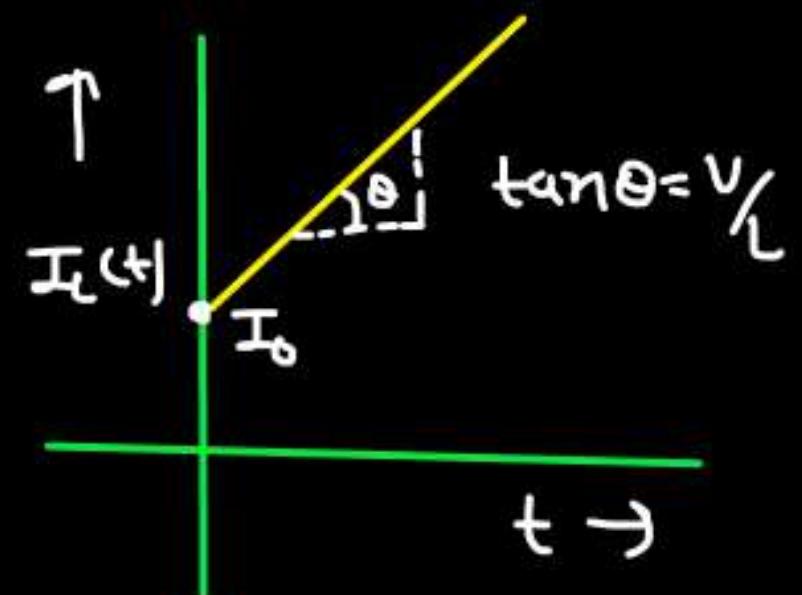

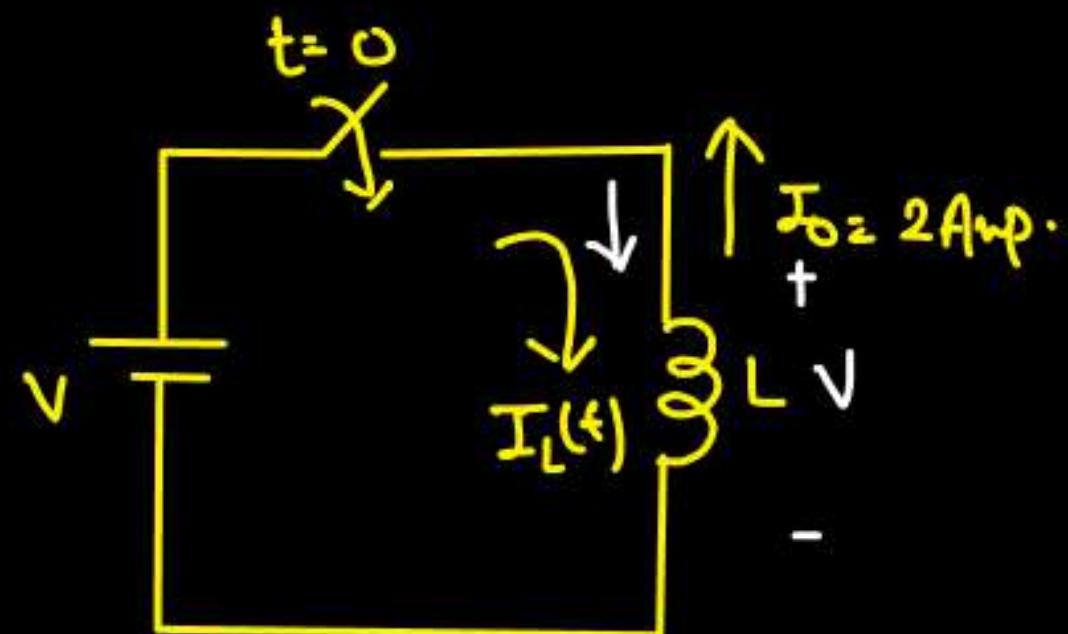- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES


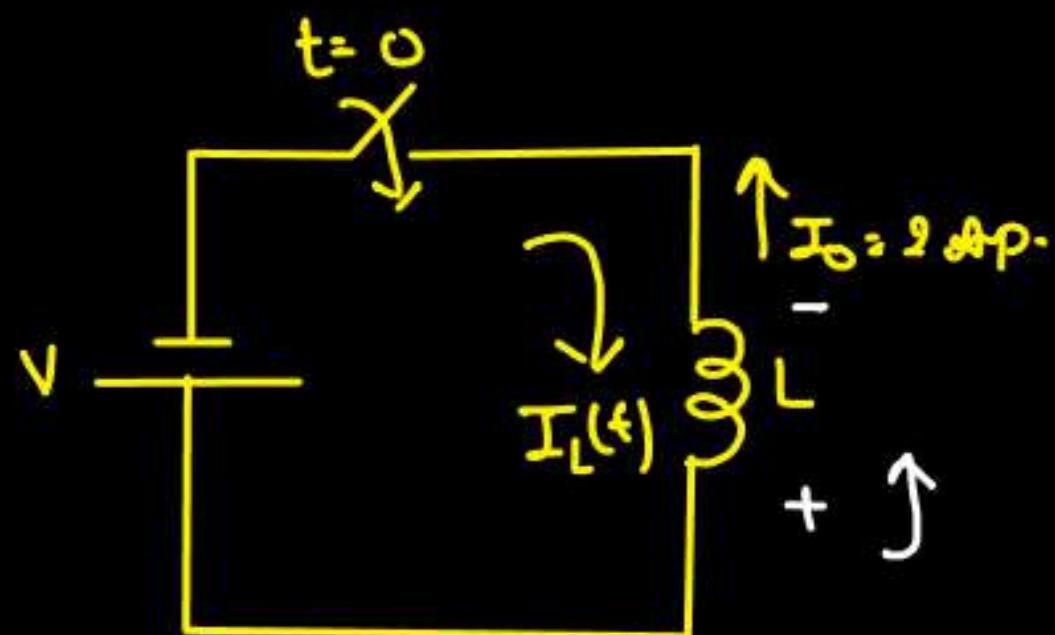
$$I_L(t) = -2 + \frac{\sqrt{t}}{L} \text{ Amp.}$$




PrepFusion

$$I_L(t) = -2 - \frac{\sqrt{t}}{L}$$

$$= -\left[2 + \frac{\sqrt{t}}{L} \right] \text{ Amp.}$$

First order RL ckt:-

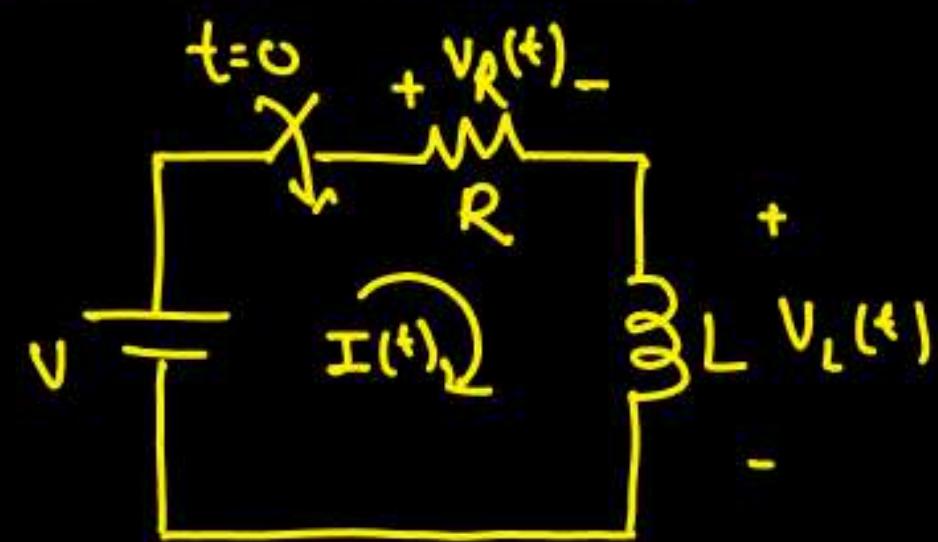

$V_R(t)$, $V_L(t)$, $I(t) = ?$

Differential eqn :-

$I(t)$:-

$$V = I(t) \cdot R + L \frac{dI(t)}{dt}$$

PrepFusion

$$\left\{ V_L(t) = L \frac{dI(t)}{dt} \right\}$$

$V_R(t)$:-

$$V = V_R(t) + L \frac{d}{dt} [V_R(t)]$$

$$\left\{ V_L(t) = L \frac{dI(t)}{dt} = L \frac{d}{dt} \left[\frac{V_R(t)}{R} \right] \right.$$

 $V_L(t)$:-

$$V = \frac{R}{L} \int_0^t V_L(t) \cdot dt + V_L(t)$$

$$\left\{ V_L(t) = \frac{L}{R} \frac{d[V_R(t)]}{dt} \right.$$

$$\Rightarrow V_R(t) = \frac{R}{L} \int_0^t V_L(t) \cdot dt \Big\}$$


$$0 = \frac{R}{L} V_L(t) + \frac{dV_L(t)}{dt} \leftarrow \text{differential eqn}$$

\Rightarrow So, solve these differential eqn to get $V_R(t)$, $I(t)$ and $V_L(t)$.

Time constant :-

$$\tau = \frac{L_{eff}}{R_{eq}}$$


$$\boxed{\tau = \frac{L}{R}}$$

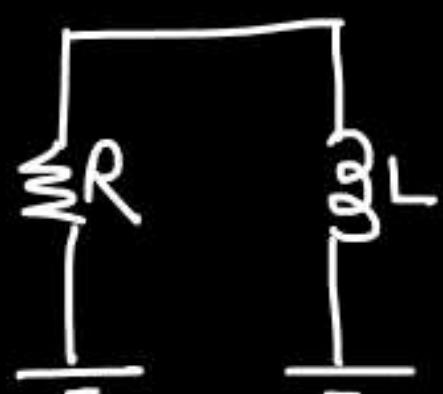


M-II

$$y(t) = y(\infty) + [y(0^+) - y(\infty)] e^{-t/\tau} \quad u(t)$$

given ckt: $+ \frac{v_R(t)}{R} -$

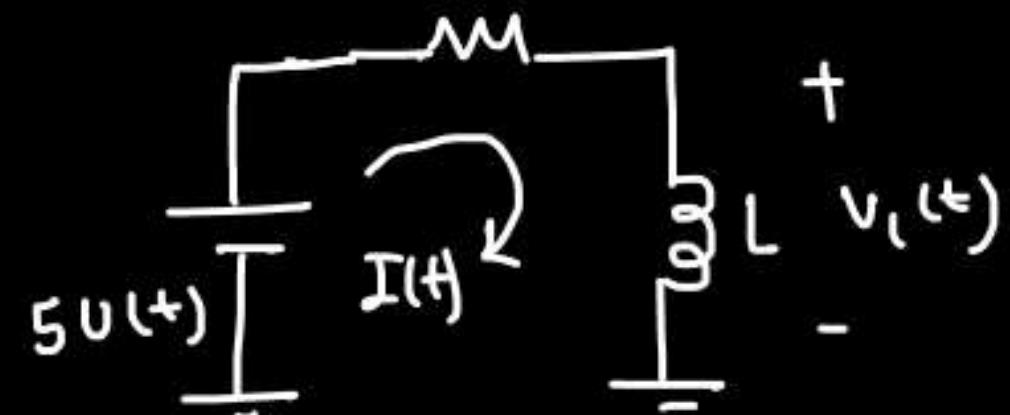

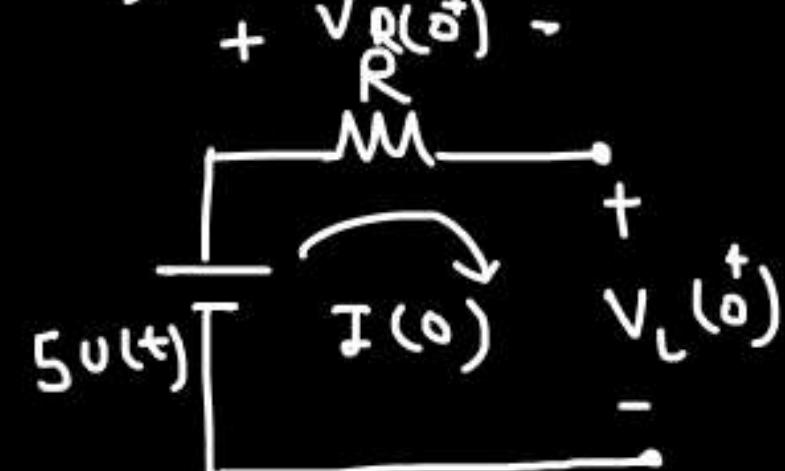① $t=0$; inductor $\rightarrow 0 \cdot C$



$$v_R(0^+) = 0V$$


$$I(0^+) = 0 \text{ A}$$

$$v_L(0^+) = 5V$$



@ $t = \infty$:-

inductor will be shorted.

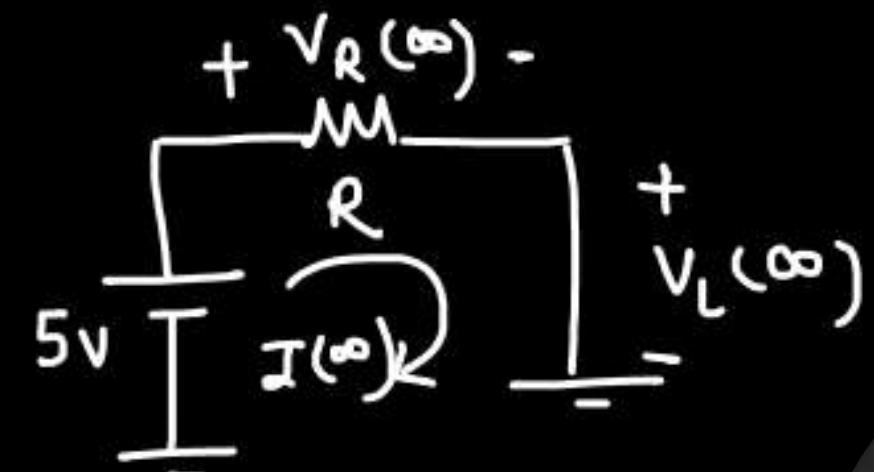

$$I(\infty) = \frac{5}{R}$$




$$V_R(\infty) = 5V$$

$$V_L(\infty) = 0V$$

↳ $I(t) = \frac{5}{R} [1 - e^{-t/\tau}] u(t) ; \tau = \frac{L}{R}$


$$V_R(t) = 5 [1 - e^{-t/\tau}] u(t) ; \tau = \frac{L}{R}$$
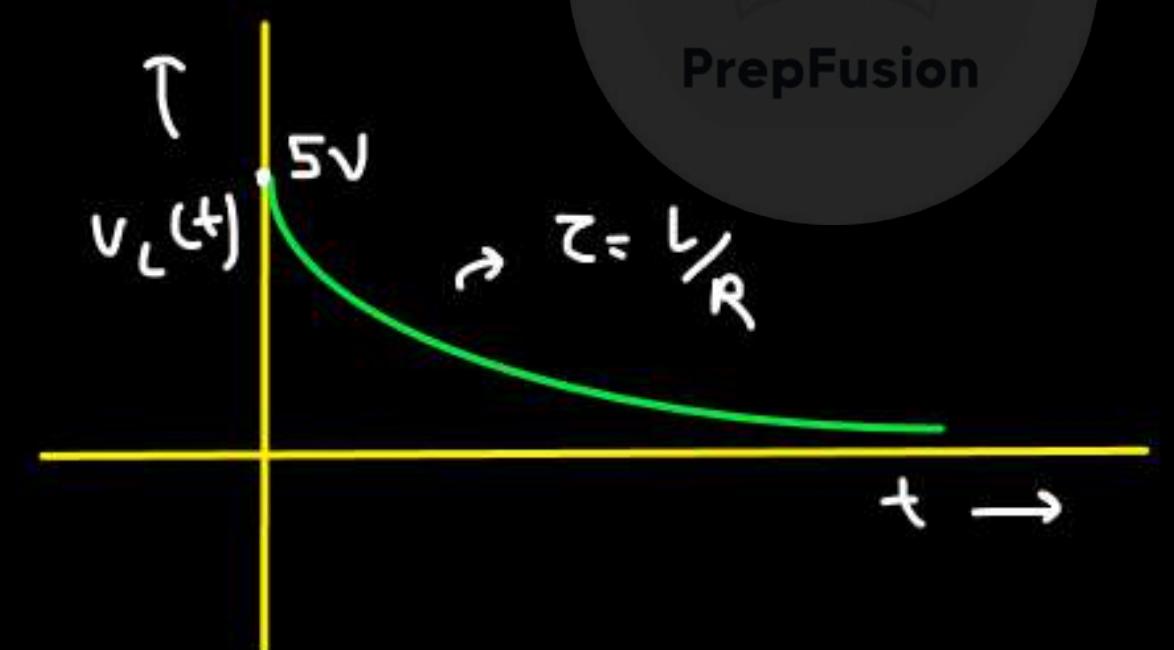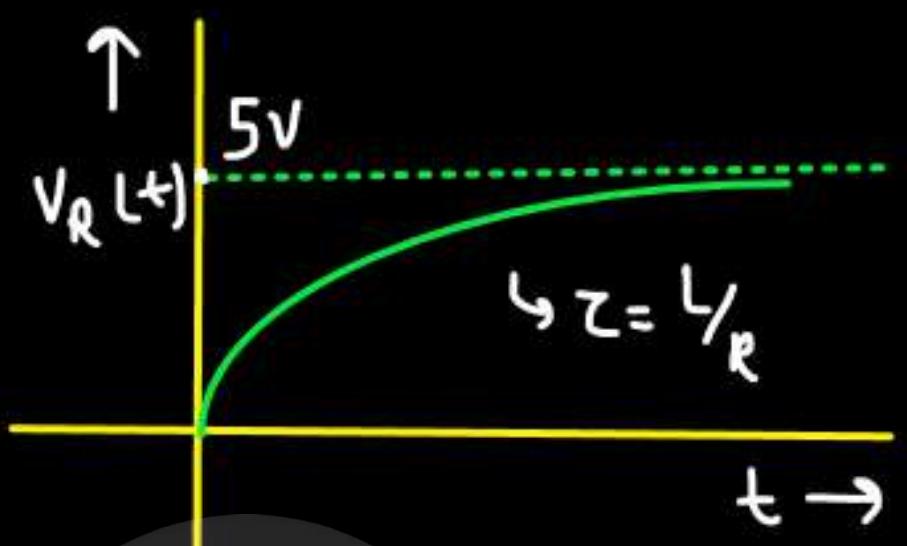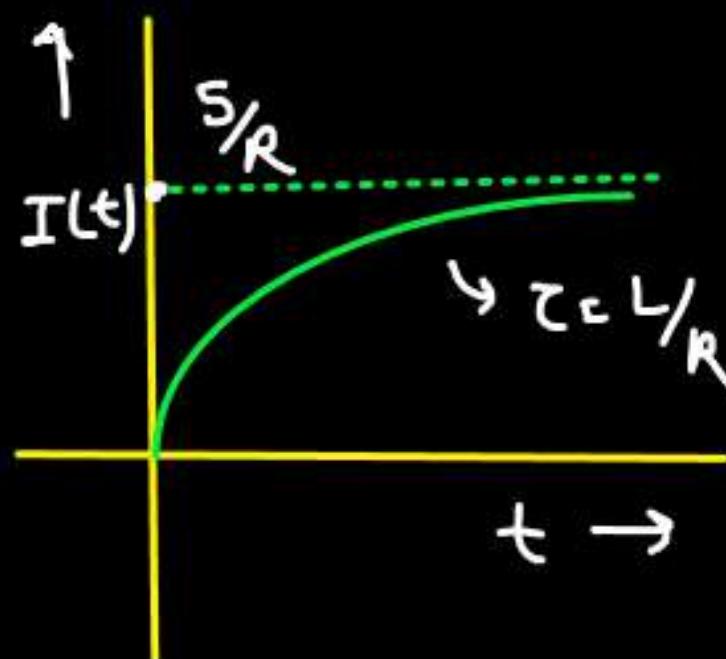
$$V_L(t) = 5e^{-t/\tau} u(t) ; \tau = \frac{L}{R}$$



What is happening in the ckt:-

@ $t=0^+$

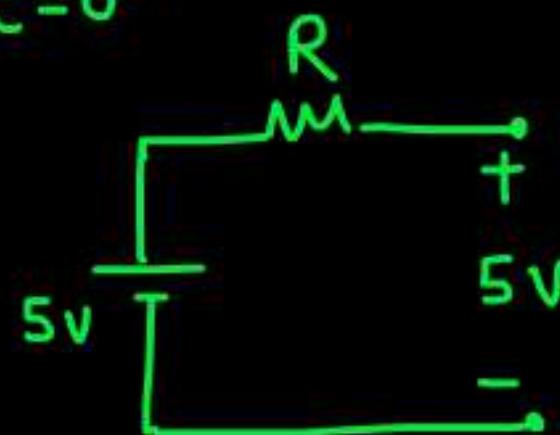


\Rightarrow 5V will come across inductor

\Downarrow
it will generate current in inductor


let's assume @ $t=t_1$, the current through inductor is 1A.

@ $t=t_1$; take $R = 1\Omega$

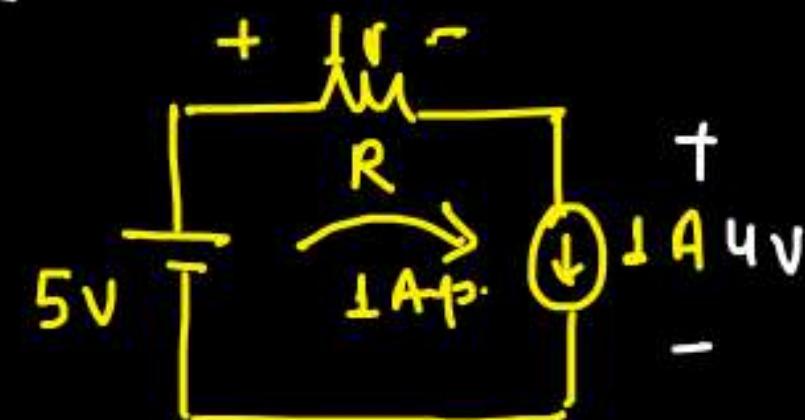

\Rightarrow now the drop across the inductor has reduced to 4V.

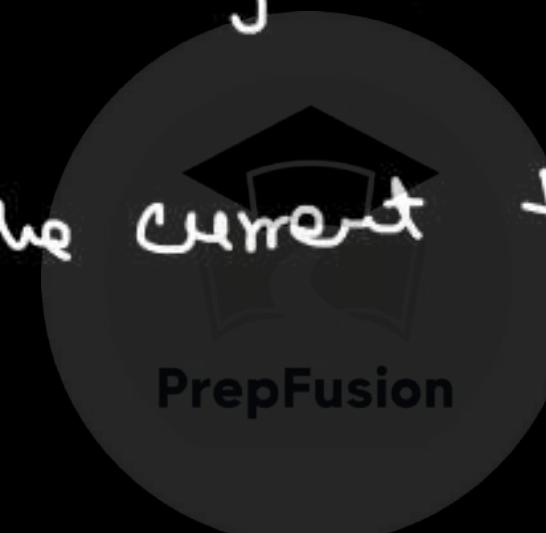\Downarrow
This 4V will also generate some current and the current will increase.





⇒ Slowly the voltage across the inductor is decreasing and the current through the inductor is increasing.


⇒ when $V_L = 0V \Rightarrow$ The current doesn't increase further.

↓
That's the steady state.

PrepFusion




Q.

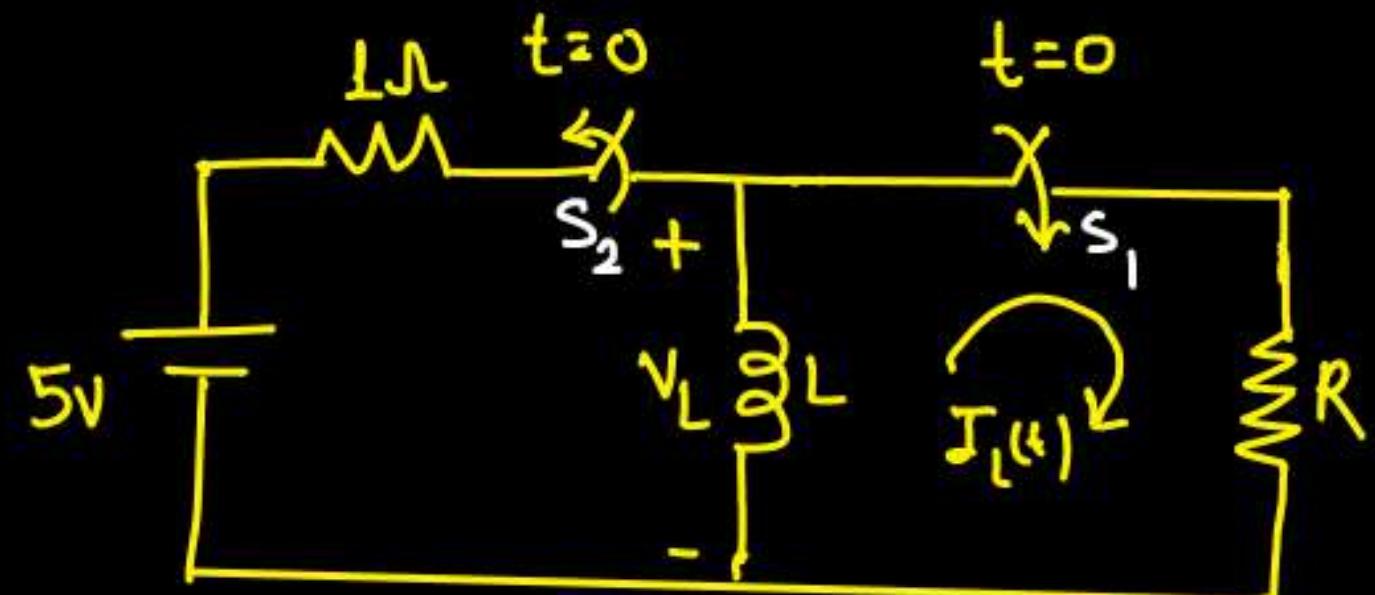comment of $I_L(t)$.

→ For $t < 0 \{ -\infty < t < 0 \}$

S_1 is open. S_2 is closed.

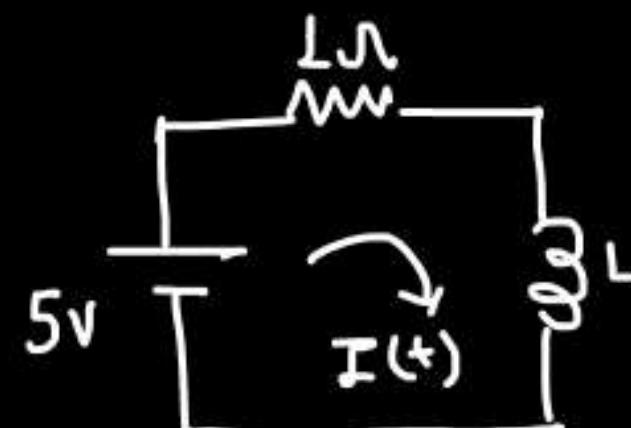

⇒ switch is closed for $-\infty < t < 0$ (very long time)




Steady state would have reached.

$$I(0^+) = 5 \text{ amp.}$$


For $t > 0$:-

$$I_L(0^-) = I_L(0) = I_L(0^+) = 5 \text{ Amp.}$$

S_2 is open and S_1 is closed.

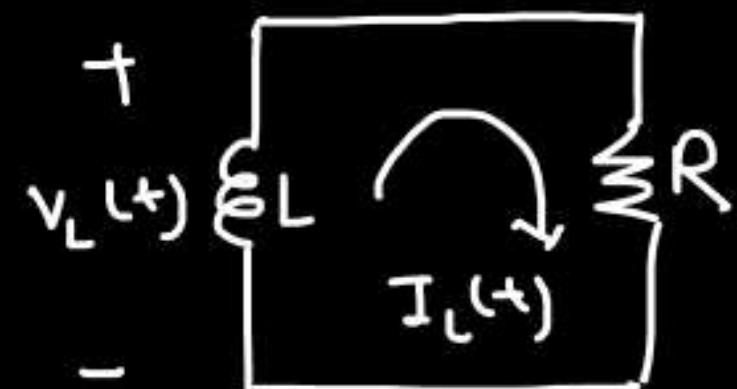

@ $t=0^+$

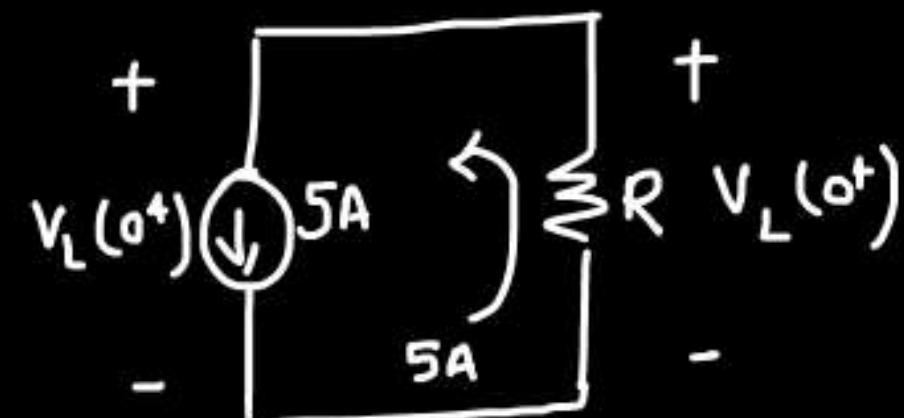


PrepFusion

$$V_L(0^+) = -5R$$

$$I_L(0^+) = -5 \text{ Amp.} =$$

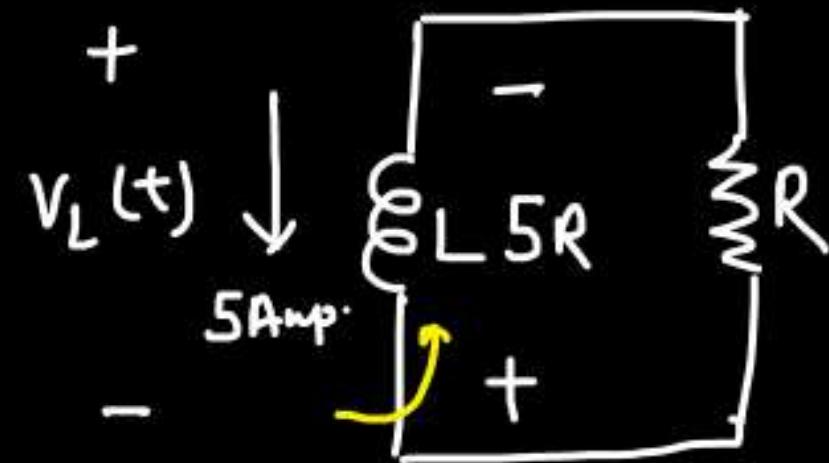This $-5R$ voltage will come across the inductor.



⇒ This $5R$ voltage will reduce the current.
 ↓

current will keep on reducing until $V_L = 0V$

so, @ steady state; $V_L = 0V$



$$V_L(\infty) \approx 0V$$

$$I_L(\infty) = 0 \text{ Amp.}$$







$$V_L(0^+) = -5R ; \quad I_L(0^+) = -5 \text{ Amp}$$

$$V_L(\infty) = 0 \text{ V} ; \quad I_L(\infty) = 0 \text{ Amp}$$


$$V_L(t) = -5R e^{-t/\tau} u(t) ; \quad \tau = L/R$$
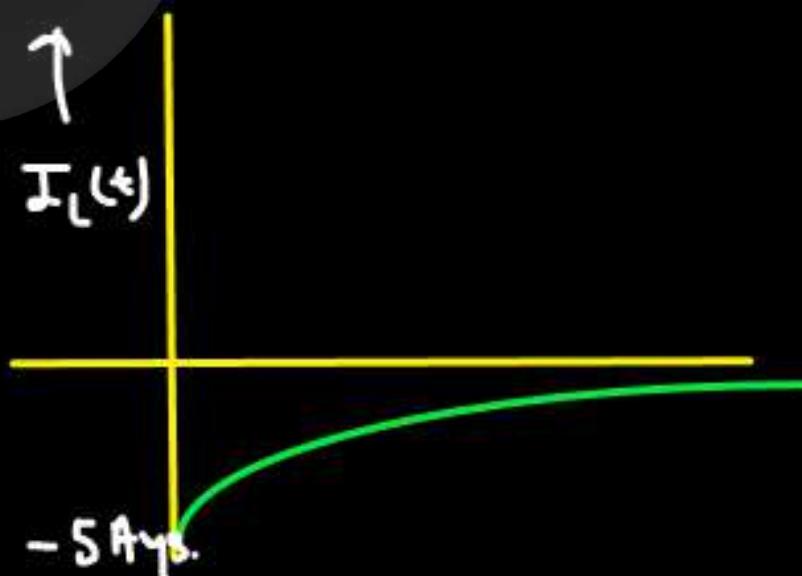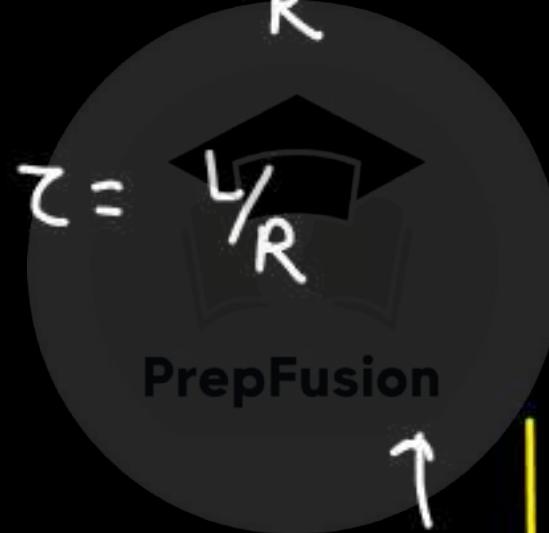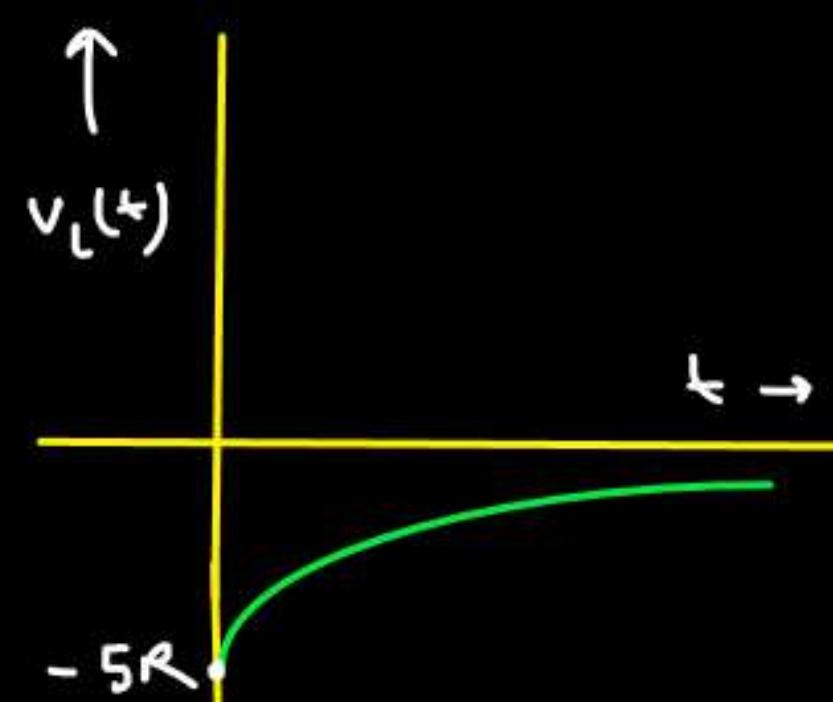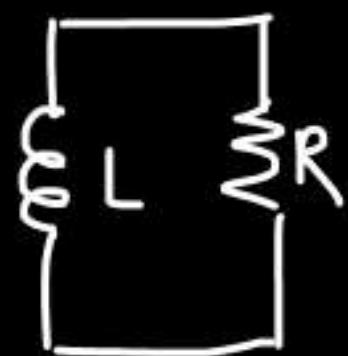
$$I_L(t) = -5 e^{-t/\tau} u(t) ; \quad \tau = L/R$$






Let's solve by Laplace Transform:-

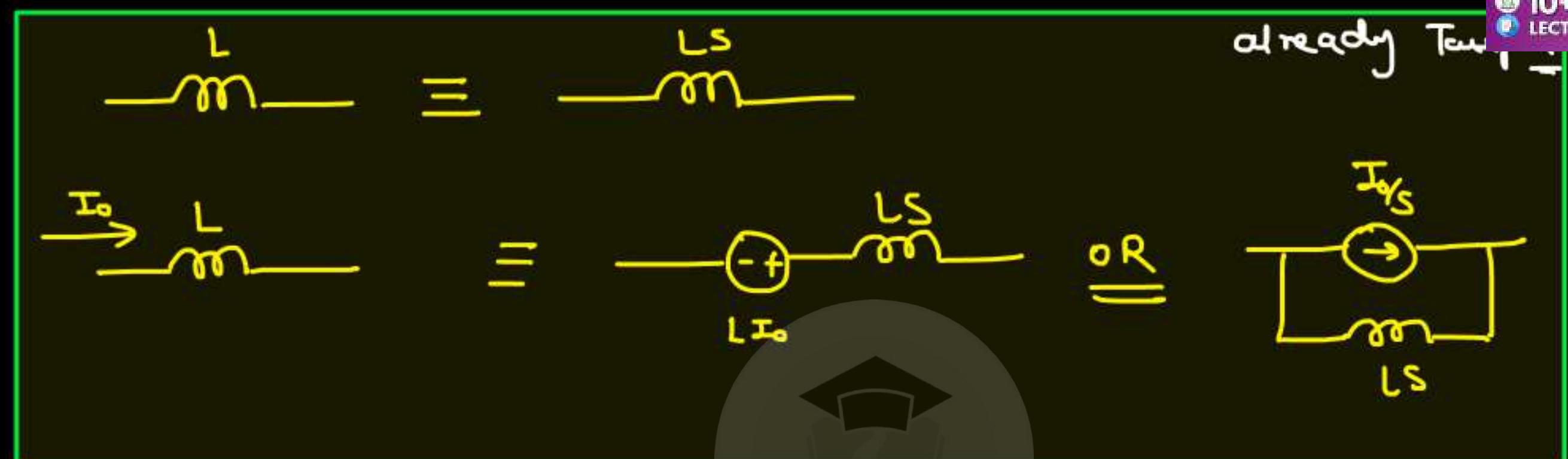

for $t > 0$

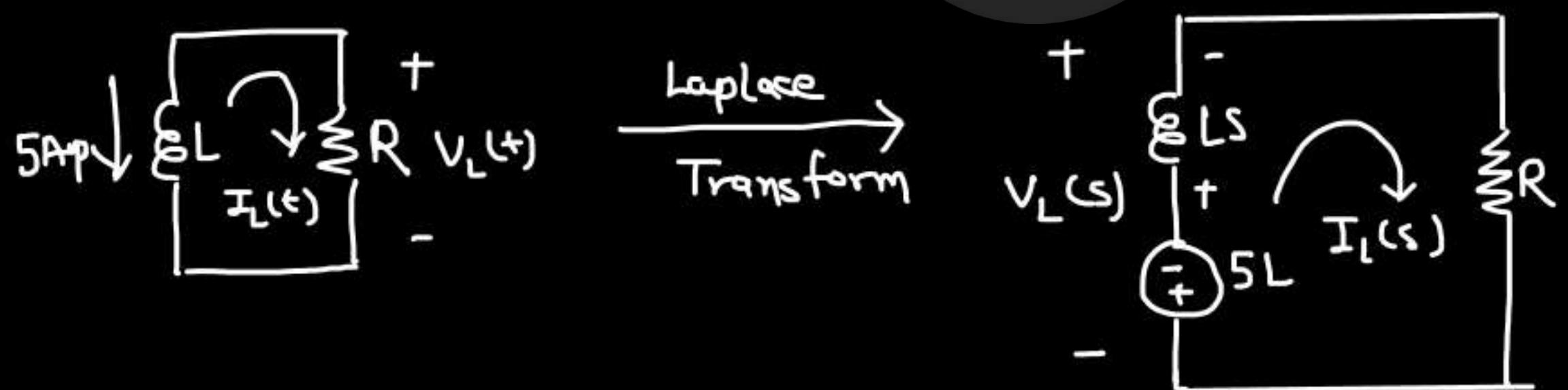

KVL :-

$$(i) -5L = I_L(s) [sL + R]$$

$$I_L(s) = -\frac{sL}{sL + R}$$

$$I_L(s) = \frac{-s}{s + R/L}$$

$$i_L(t) = -5 e^{-R/L t} v(t)$$


$$(ii) V_L(s) = I_L(s) R$$

$$= -\frac{5R}{s + R/L}$$

$$v_L(t) = -5R e^{-R/L t} v(t)$$



Q.

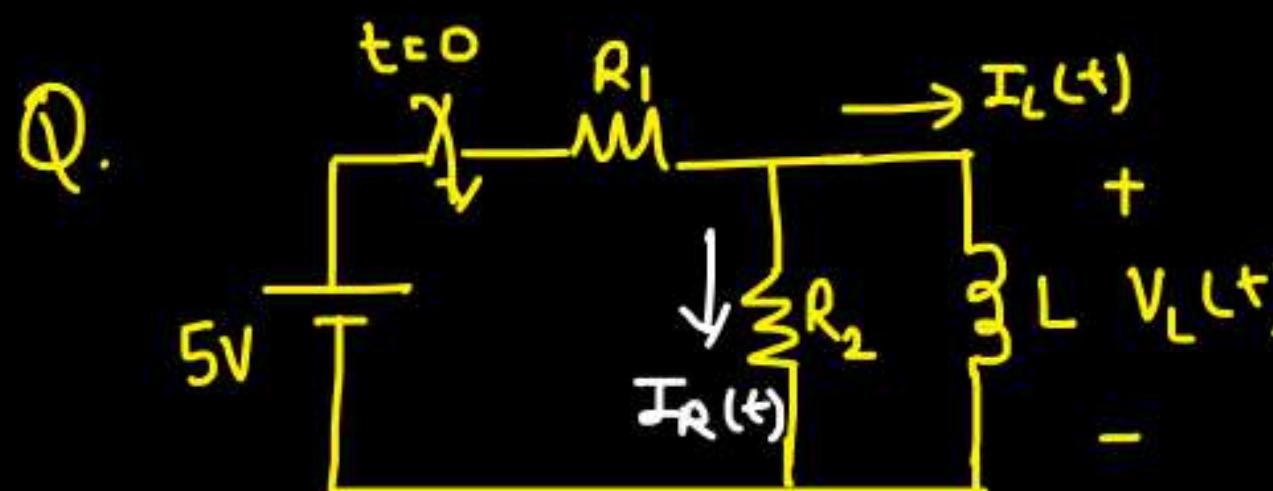Comment on $v_L(t)$ & $I_L(t)$ 

$$\tau_c = \frac{L}{\left(\frac{R_1 R_2}{R_1 + R_2}\right)}$$

→ initially; inductor $\rightarrow 0\text{-c.}$

$$v_L(0) = \frac{5R_2}{R_1 + R_2} ;$$

PrepFusion
 $I_L(0) = 0 \text{ A}$




$$, I_R(0) = \frac{5}{R_1 + R_2} \text{ A}$$

@ steady state; inductor $\rightarrow \infty\text{-c.}$


$$v_L(\infty) = 0V ,$$

$$I_L(\infty) = \frac{5}{R_1} ;$$

$$I_R(\infty) = 0 \text{ A}$$

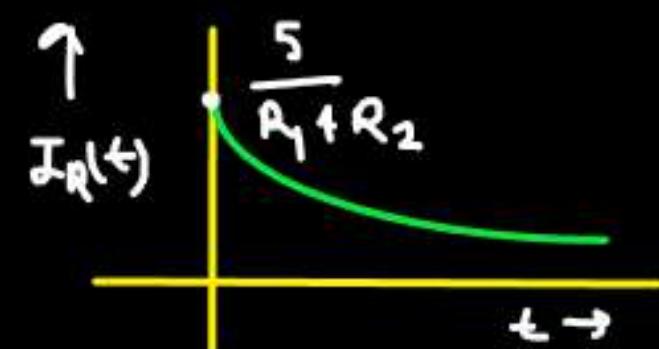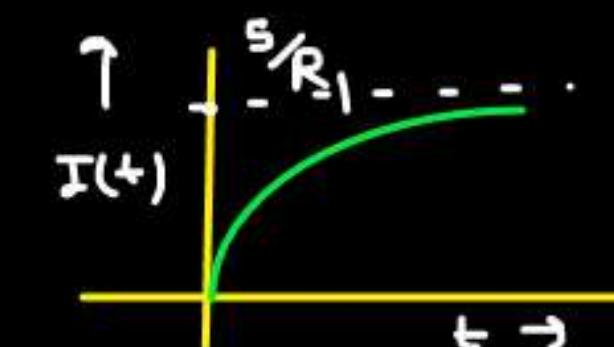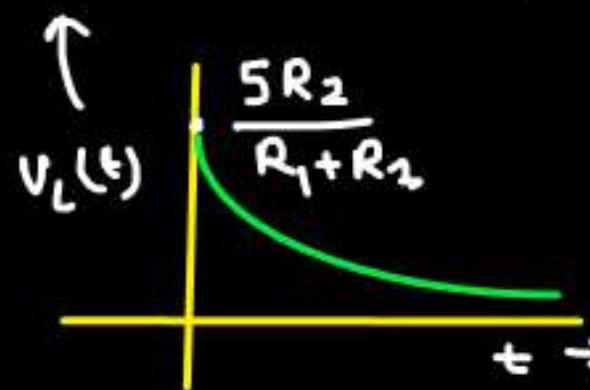

Q. Find I_L .

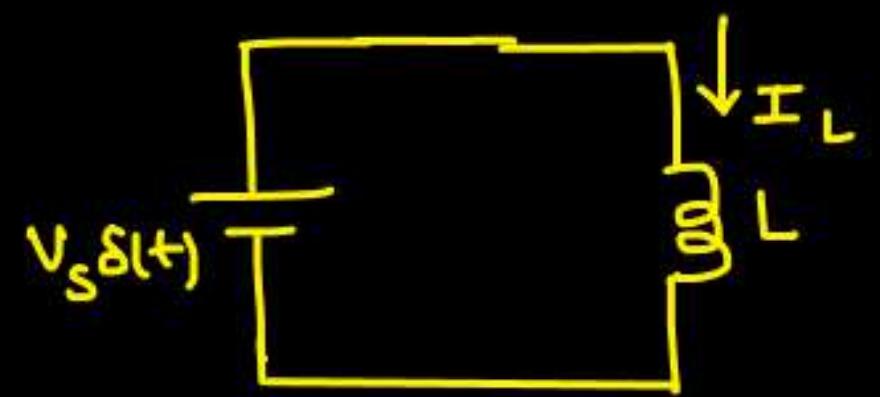


Here inductor is connected
across infinite voltage
(impulse voltage)

$$I_L(t) = \frac{1}{L} \int_0^t V(t) \cdot dt$$

$$= \frac{1}{L} \int_0^t V_s \delta(t) \cdot dt$$

$$I_L(t) = \frac{V_s}{L} U(t)$$

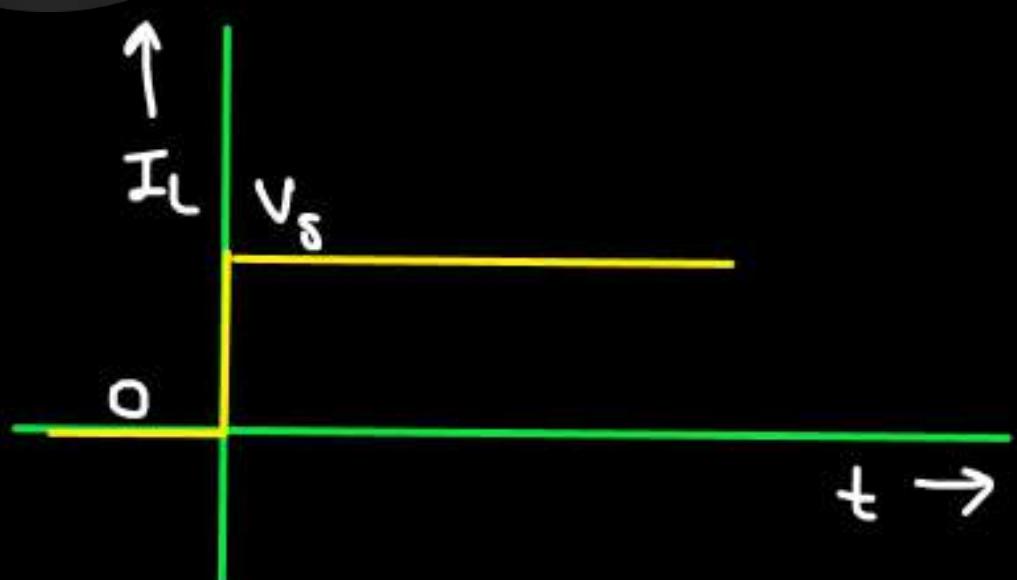↓
current can change instantaneously
 $I_L(0^-) = 0 \text{ Amp} \neq I_L(0^+)$



AIR 27 (ECE)
AIR 45 (IN)

V_s is the flux Here.

You are giving V_s amount of flux to the inductor

$$\phi = LI$$


$$V_s = L I_L$$

$$I_L = V_s / L$$






Q. Find $V_L(t)$ and $I_L(t)$

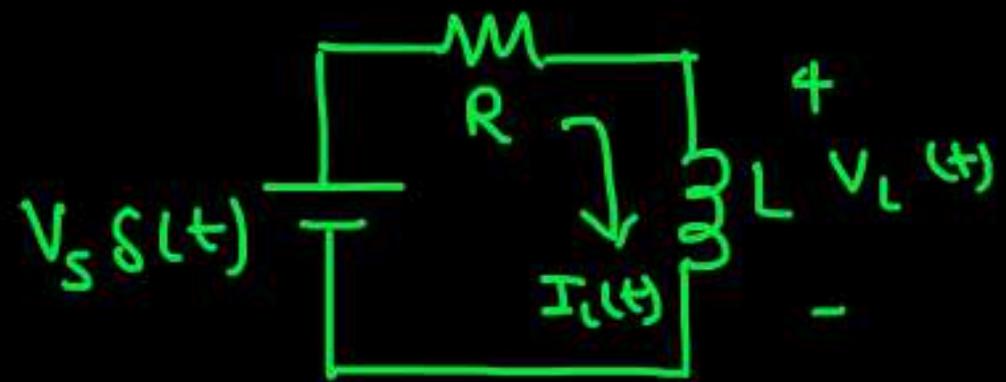

→ @ $t=0 \Rightarrow$ inductor o.c.

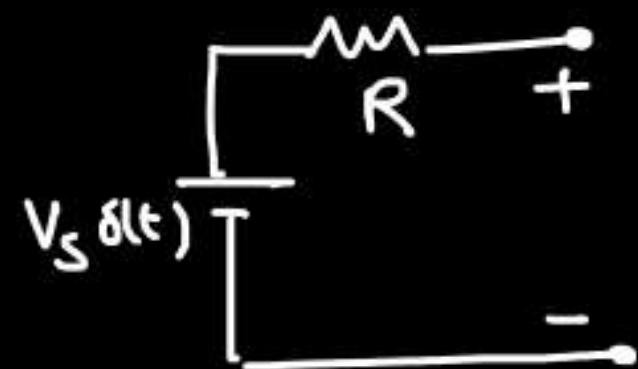


$$V_L(0) \underset{\Downarrow}{\approx} V_s \delta(t)$$

impulsive voltage is coming across inductor.

\Downarrow
sudden jump in current will be there.

@ $t=0^+$

$$V_L = 0$$

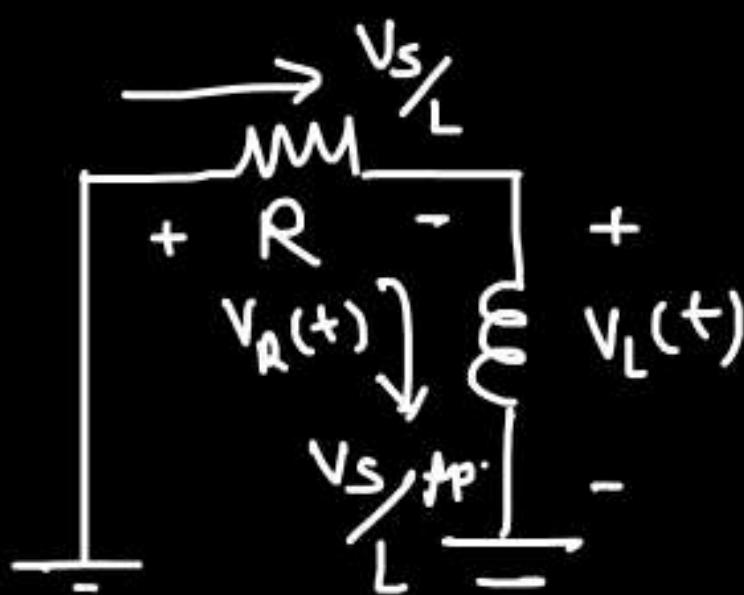


$$I_L(0^+) = \frac{V_s}{L} \text{ A}$$

{ previously derived }

$$V_L(0^+) = -\frac{V_s}{L} R \quad \left\{ V_R(t) = -V_L(t) \right\}$$

PrepFusion

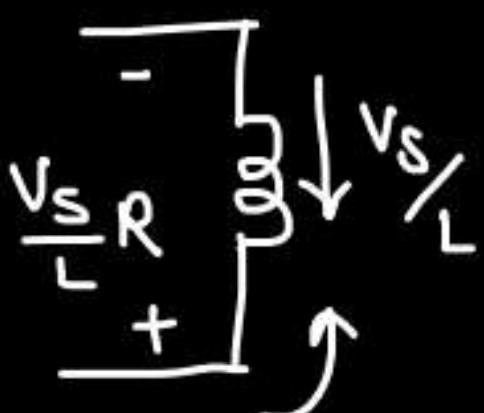Now this negative voltage will
oppose the current and reduce it




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES




@ steady state { $t = \infty$ }

$$V_L(\infty) = 0 \text{ V}$$

$$I_L(\infty) = 0 \text{ A}$$

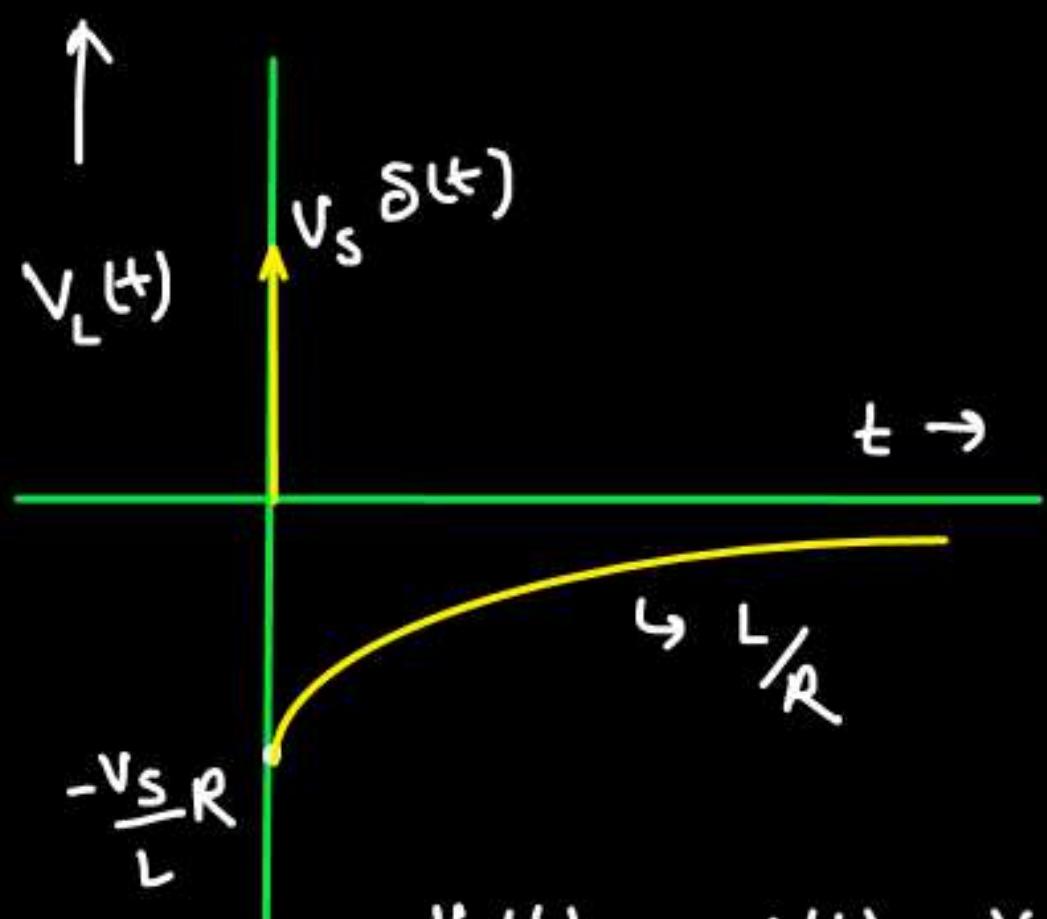
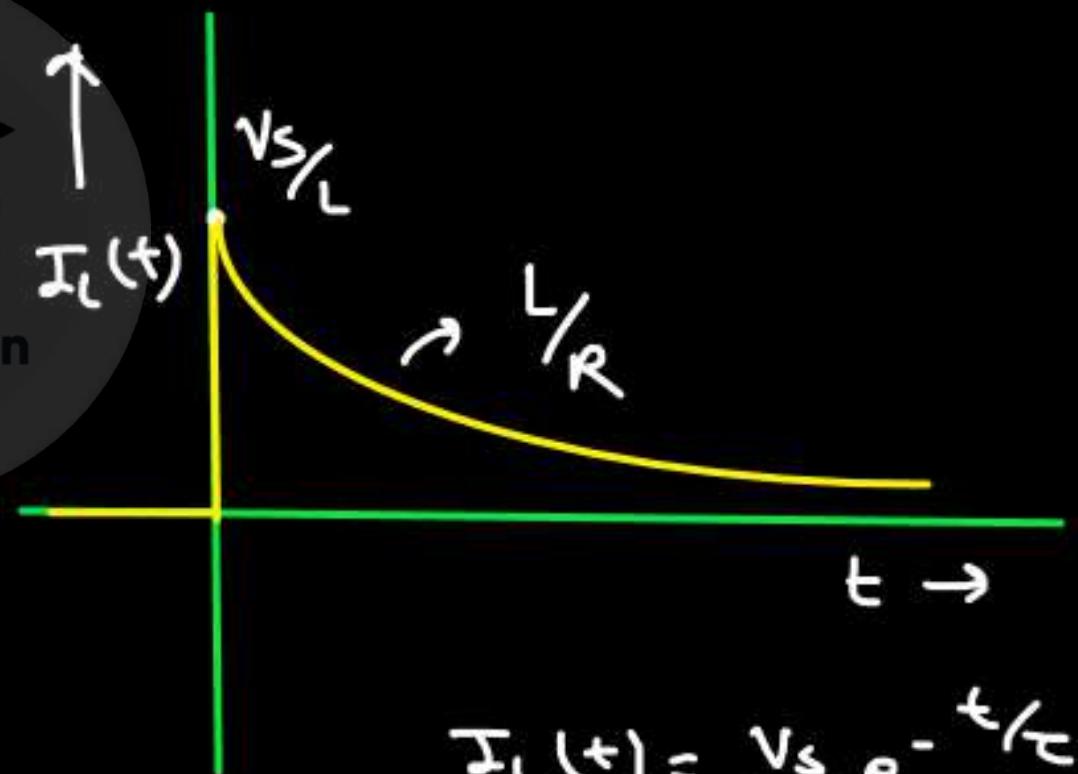
$$V_L(t) = V_s \delta(t) - \frac{V_s}{L} R e^{-t/\tau} u(t)$$




$$I_L(t) = \frac{V_s}{L} e^{-t/\tau} u(t)$$



Solving by Laplace:-
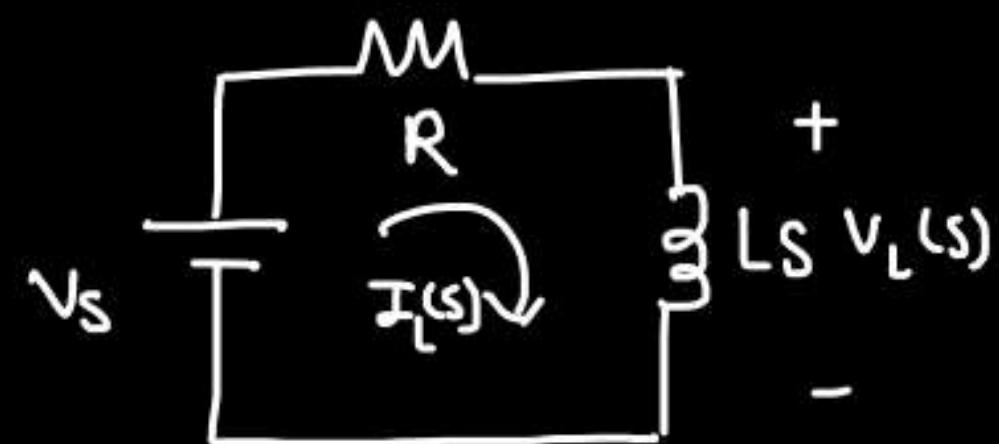
$$V_s \delta(t) \xrightarrow{\text{Laplace}} V_s$$



$$V_s = I_L(s) [R + Ls]$$

$$I_L(s) = \frac{V_s}{R + Ls}$$

$$V_L(s) = I_L(s) \times Ls$$

$$= V_s \times \frac{Ls}{R + Ls}$$

$$= V_s \left[\frac{R + Ls - R}{R + Ls} \right]$$

$$= V_s \left[1 - \frac{R/L}{s + R/L} \right] \Rightarrow$$




$$I_L(t) = \frac{V_s}{L} \frac{1}{s + R/L}$$

$$I_L(t) = \frac{V_s}{L} e^{-R/L t} u(t)$$


$$V_L(t) = V_s \delta(t) - \frac{V_s R}{L} e^{-R/L t} u(t)$$

Q. Find I_{L_1} , I_{L_2} and I_R .

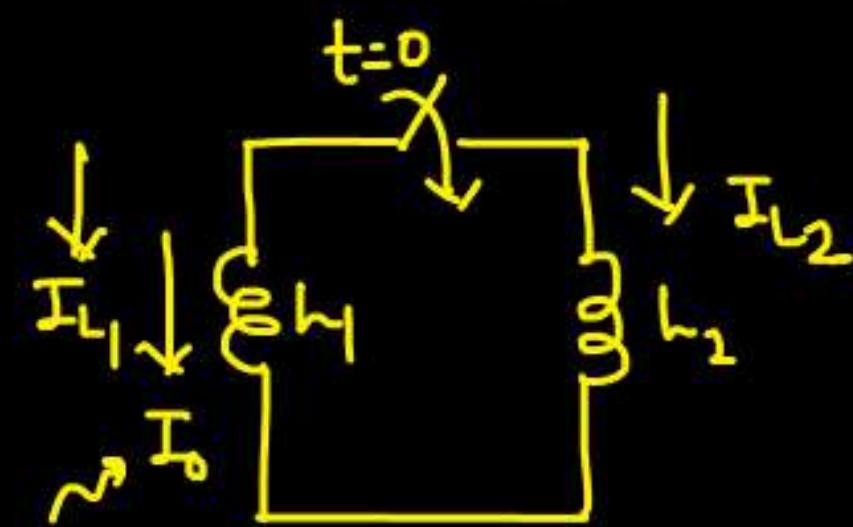



initial
current

(a)

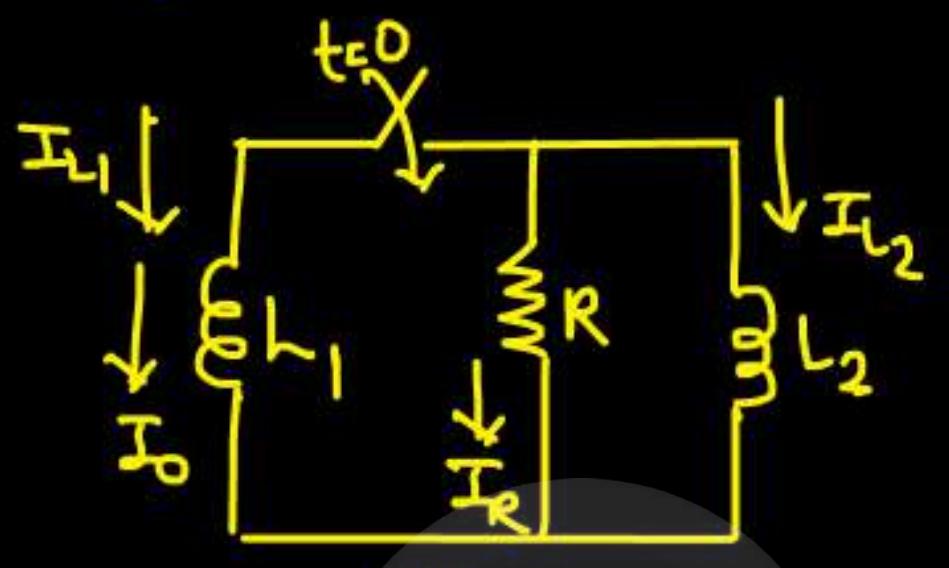


(b)

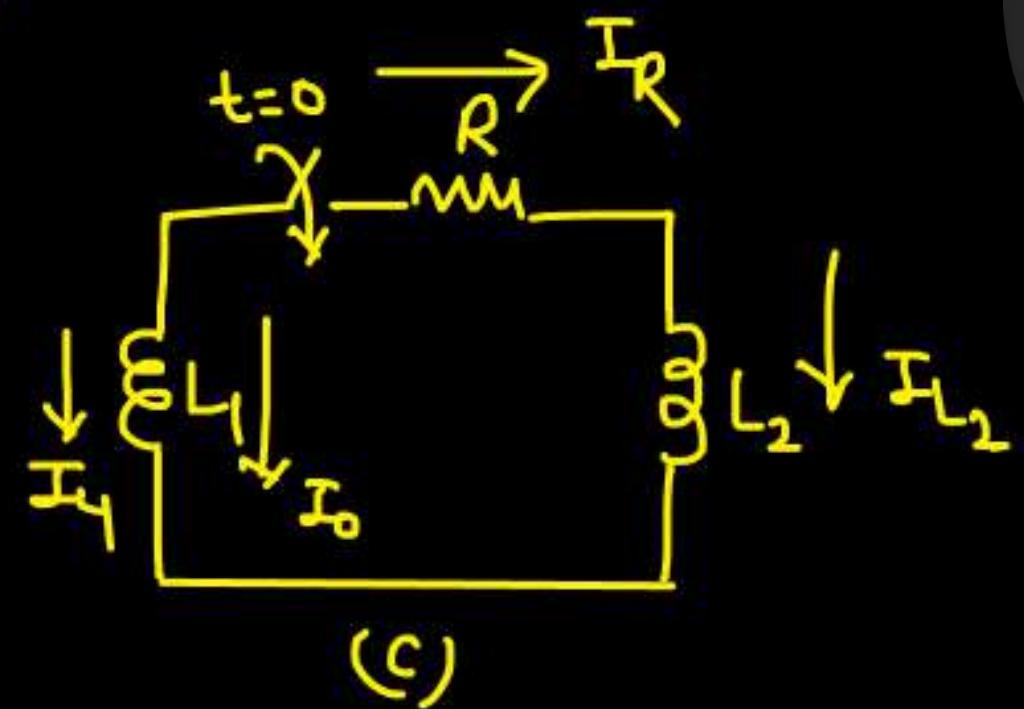


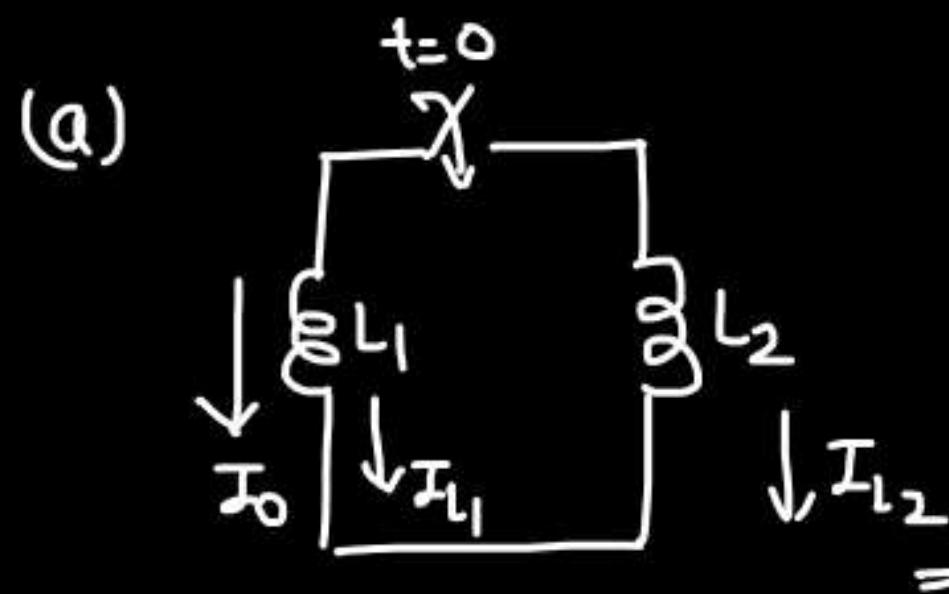

→ By Laplace Transform :-

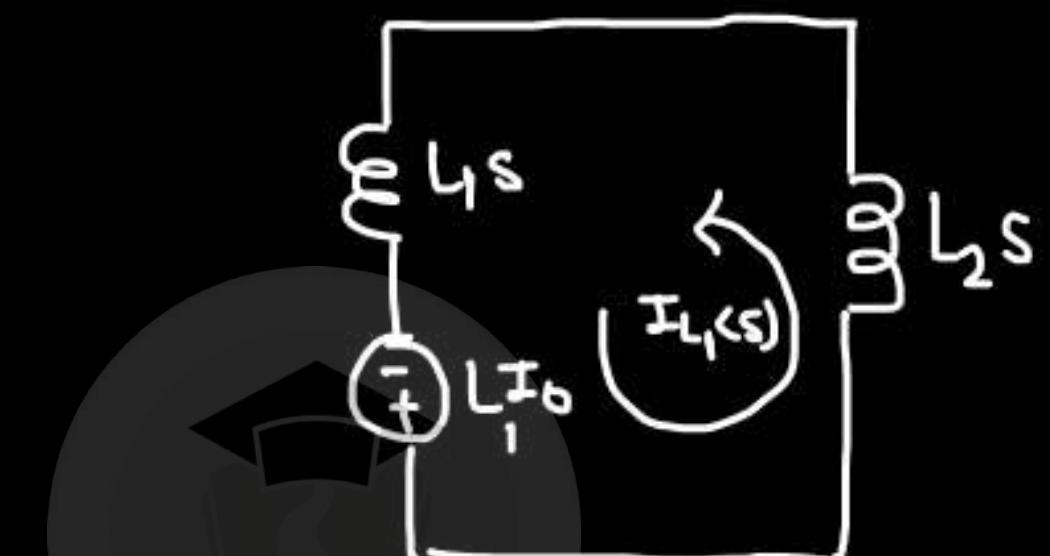


$$i_{L_1}(t) = -i_{L_2}(t)$$

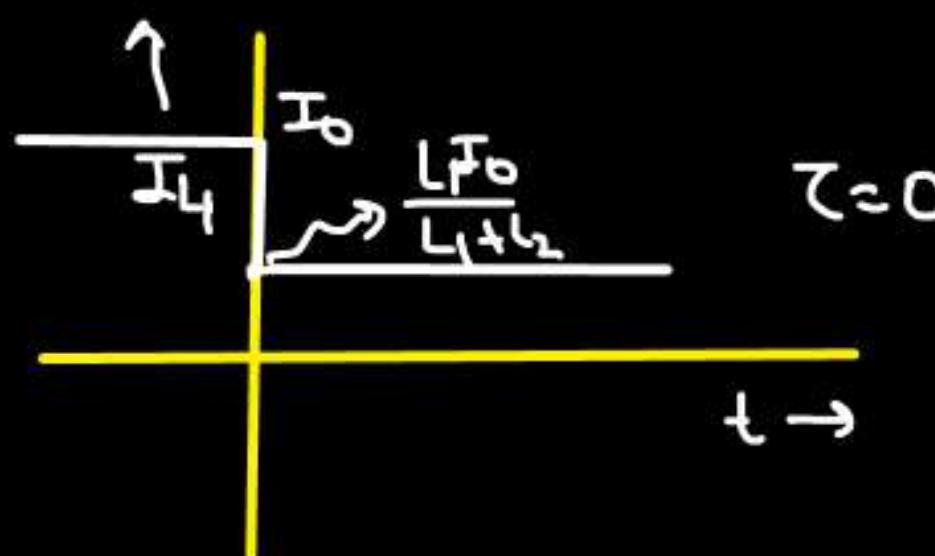

$$L_I_0 = \frac{I_0(s)}{L_1 + L_2}$$


$$I_4(s) = \frac{L_1 I_0}{(L_1 + L_2)s}$$
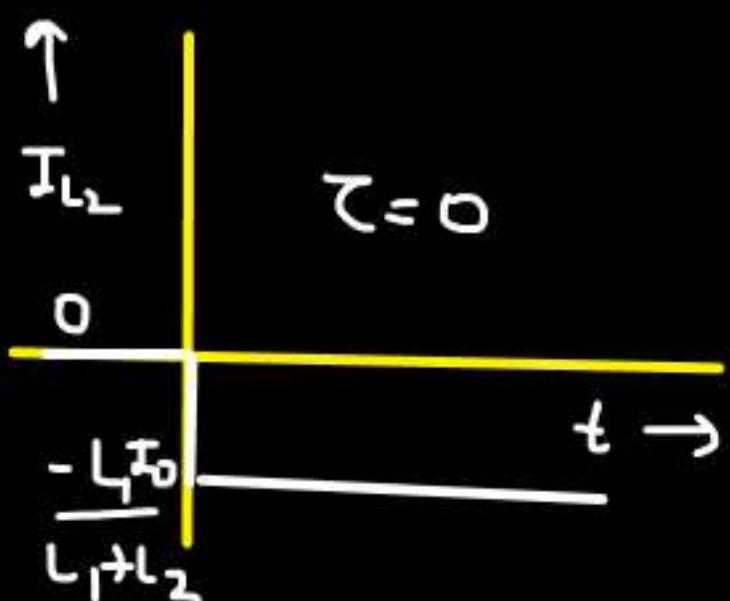
$$i_4(t) = \frac{L_1}{L_1 + L_2} I_0 u(t)$$



M-II

@ t=0

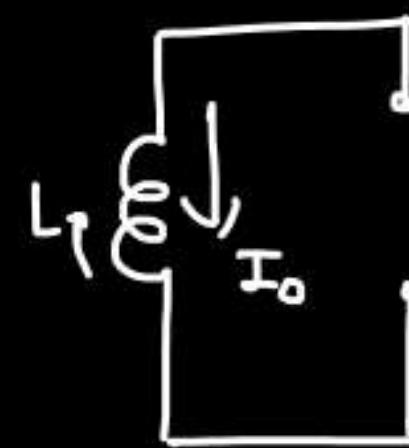

$L_2 \uparrow 0 \text{ A}$ → KCL invalid

⇒ flux conservation →

$$L_1 I_0 = (L_1 + L_2) I_L$$

$$I_L = \frac{L_1 I_0}{L_1 + L_2}$$




PrepFusion

$$V_{L_2} = I \times \infty$$

$$V_{L_2} = \infty = V_{L_1}$$


$$I_{L_1} = \frac{L_1 I_0}{L_1 + L_2}$$

$$I_{L_2} = -\frac{L_1 I_0}{L_1 + L_2}$$

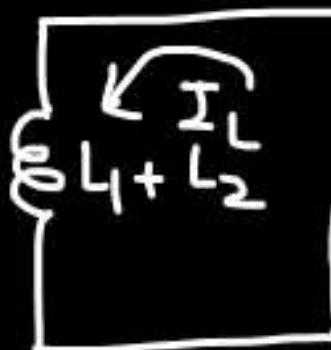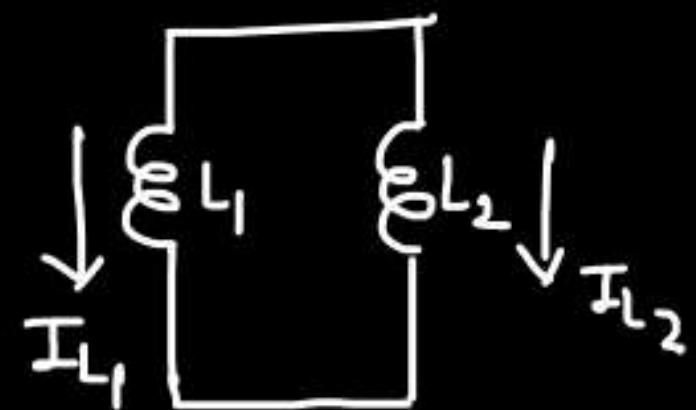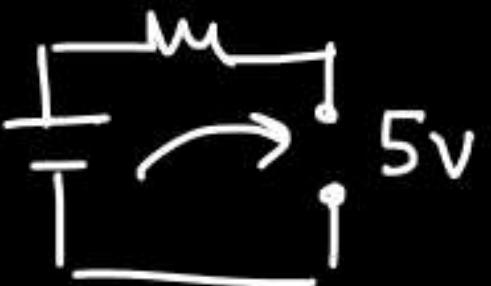


$$I_L = I_{L_1} = -I_{L_2}$$

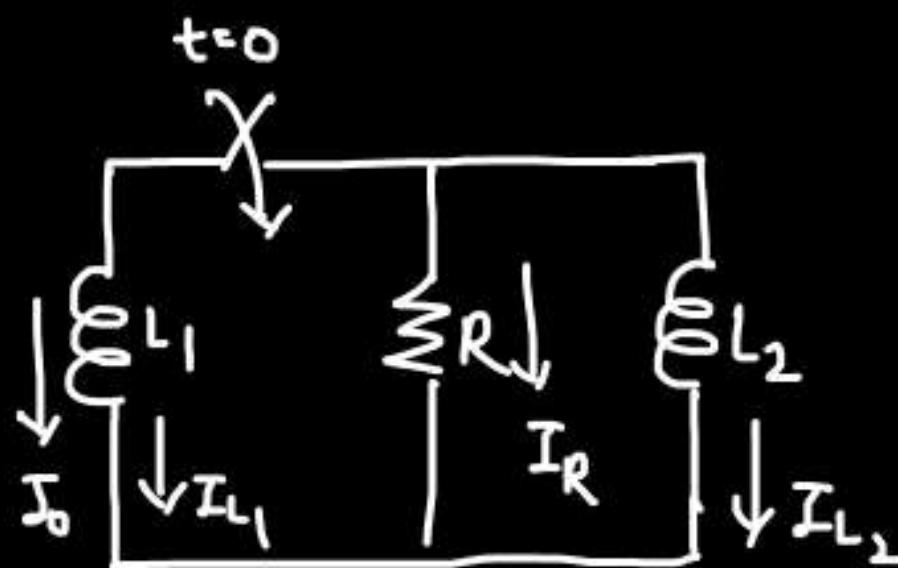- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



→ By Laplace Transform

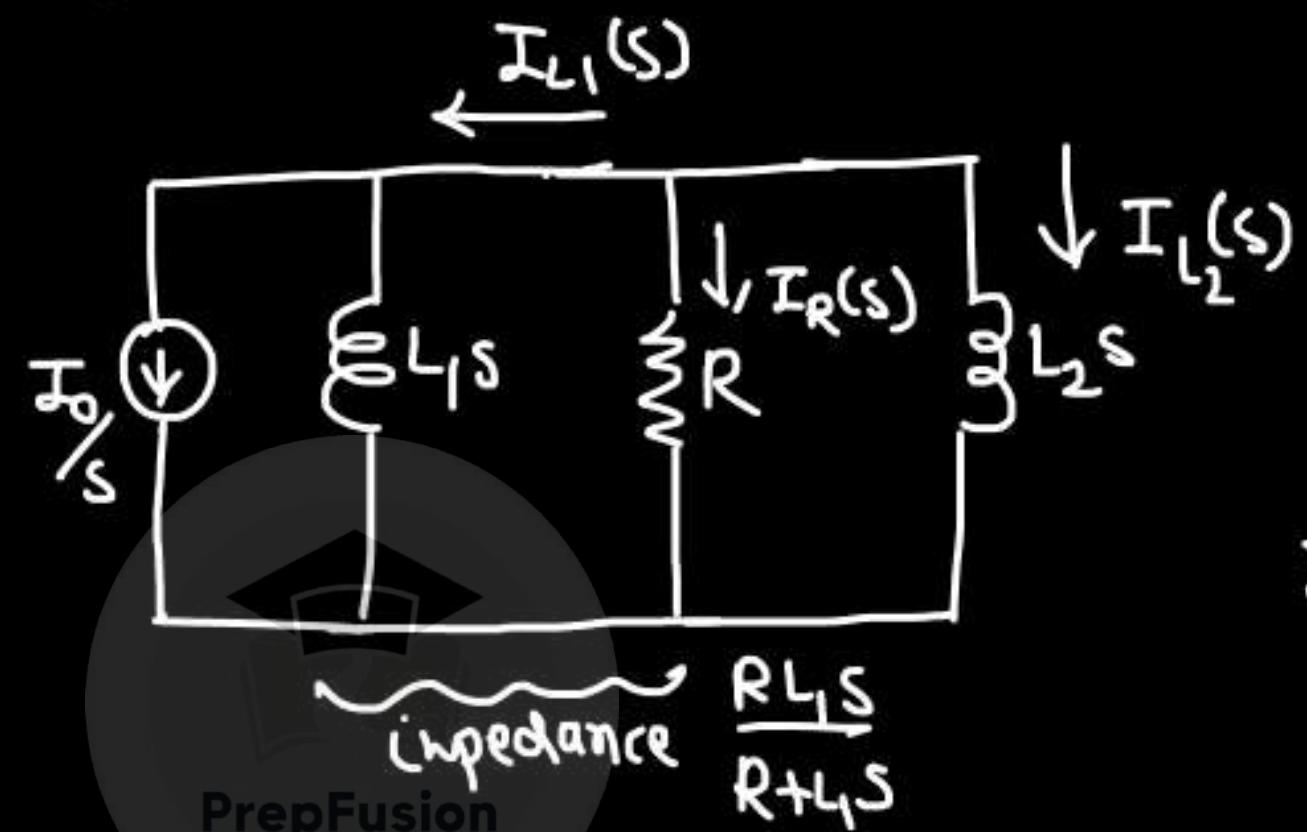

$$I_{L1}(s) = -[I_R(s) + I_L(s)]$$

$$I_{L2}(s) = \frac{-\frac{RL_1s}{R+L_1s} \times \frac{I_0}{s}}{\frac{RL_1s}{R+L_1s} + L_2s} = \frac{-RL_1s}{RL_1s + R(L_1 + L_2)} \times \frac{I_0}{s}$$




$$i_{L_2}(t) = \frac{L_1 I_0}{L_1 + L_2} \left[1 - e^{-\frac{t}{\tau}} \right] u(t); \quad \tau = \frac{L_1 L_2}{R(L_1 + L_2)}$$


Solve similarly for $I_R(s)$ and $I_{L_1}(s)$ using current division.

M-II :-

@ $t=0$

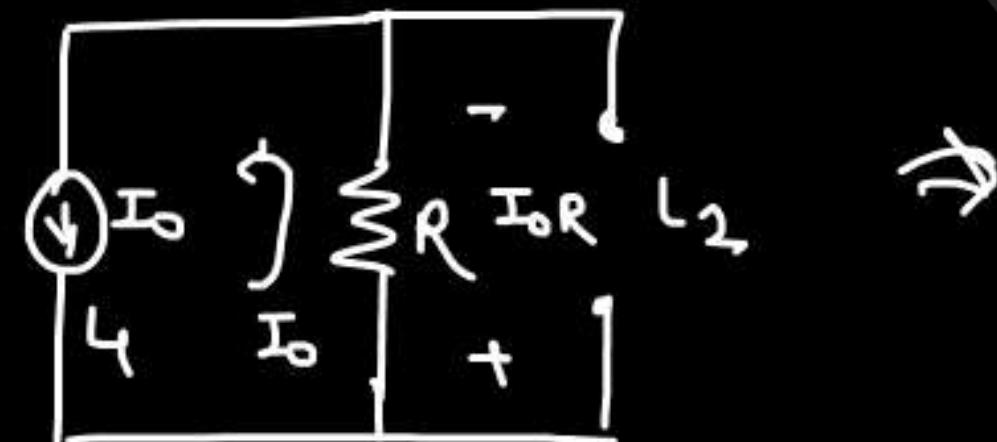

@ $t=0^+$

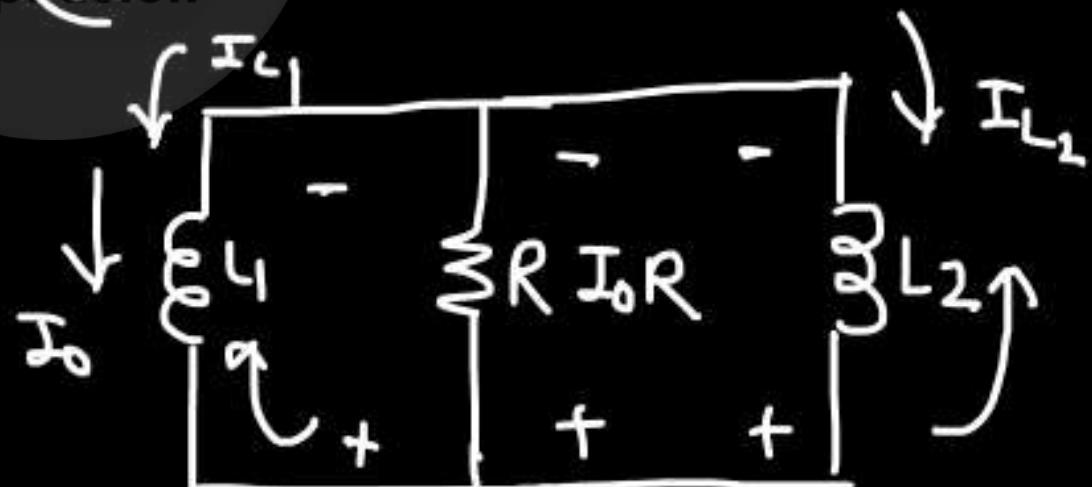

I_{L_1} will be reducing from I_0 to some value.
and I_{L_2} will be increasing (but in negative dirⁿ)

I_{L_1} and I_{L_2} will be constant when the drop across them becomes zero \Rightarrow when there is no current in resistance

$\hookrightarrow I_{L_1} \downarrow$ and $-I_{L_2} \uparrow$

@ steady state $I_{L_1} = -I_{L_2}^{PrepFusion}$ and $I_R = 0$

steady state I_{L_1} and I_{L_2} ?


Hux conservation,

$$I_0 = (L_1 + L_2) I_L$$

$$I_L = \frac{L_1 I_0}{L_1 + L_2}$$

where;
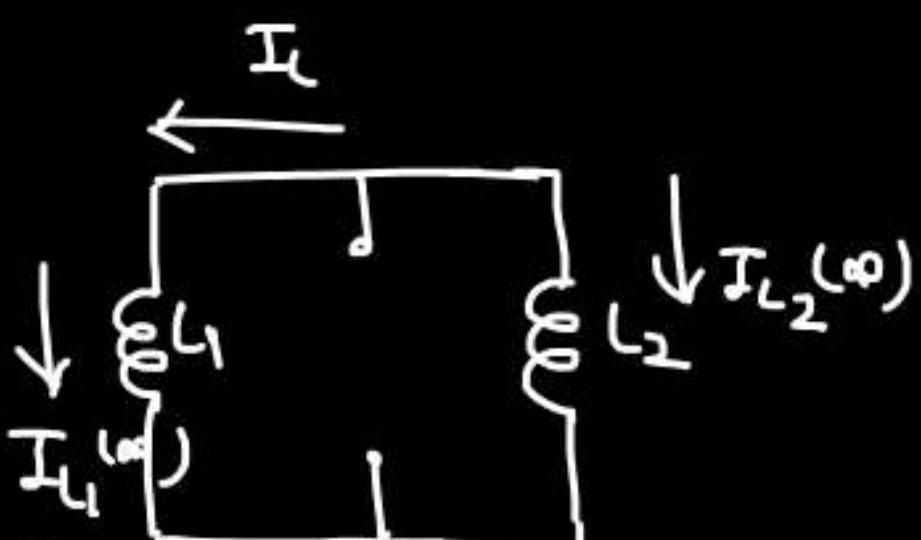
$$I_L = I_{L_1}^{(\infty)} = -I_{L_2}^{(\infty)}$$





$$I_{L_1}(\infty) = \frac{L_1 I_0}{L_1 + L_2}$$

$$I_{L_2}(\infty) = -\frac{L_1 I_0}{L_1 + L_2}$$

$$\Rightarrow I_R(0^+) = I_0$$

$$I_R(\infty) = 0$$

$$I_{L_1}(0^+) = I_0$$


$$I_{L_1}(\infty) = \frac{L_1 I_0}{L_1 + L_2}$$

$$I_{L_2}(0^+) = 0$$

$$I_{L_2}(\infty) = -\frac{L_1 I_0}{L_1 + L_2}$$



$\tau \rightarrow$

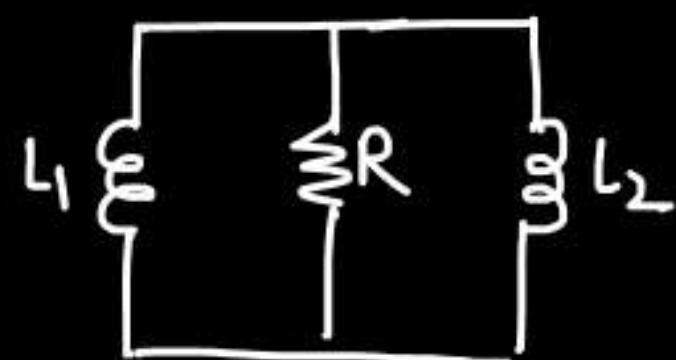

$$I_{eff} = \frac{L_1 L_2}{L_1 + L_2}$$

$$R_{eq} = R$$

$$\tau = \frac{L_1 L_2}{R(L_1 + L_2)}$$




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$I_R(t) = I_0 e^{-t/\tau} u(t)$$

$$I_{L_1}(t) = \frac{L_1 I_0}{L_1 + L_2} + \frac{L_2 I_0}{L_1 + L_2} e^{-t/\tau} u(t)$$
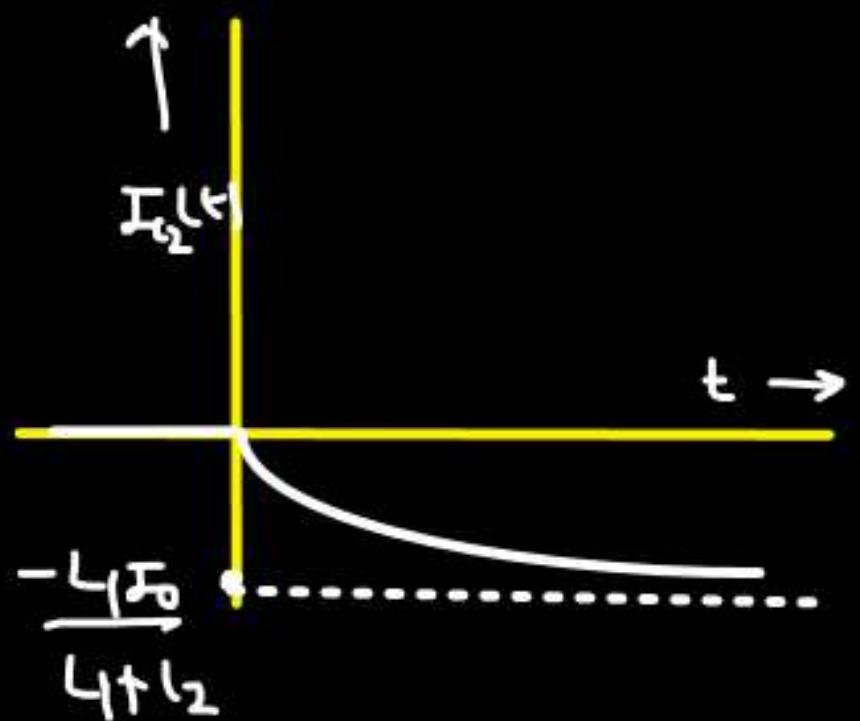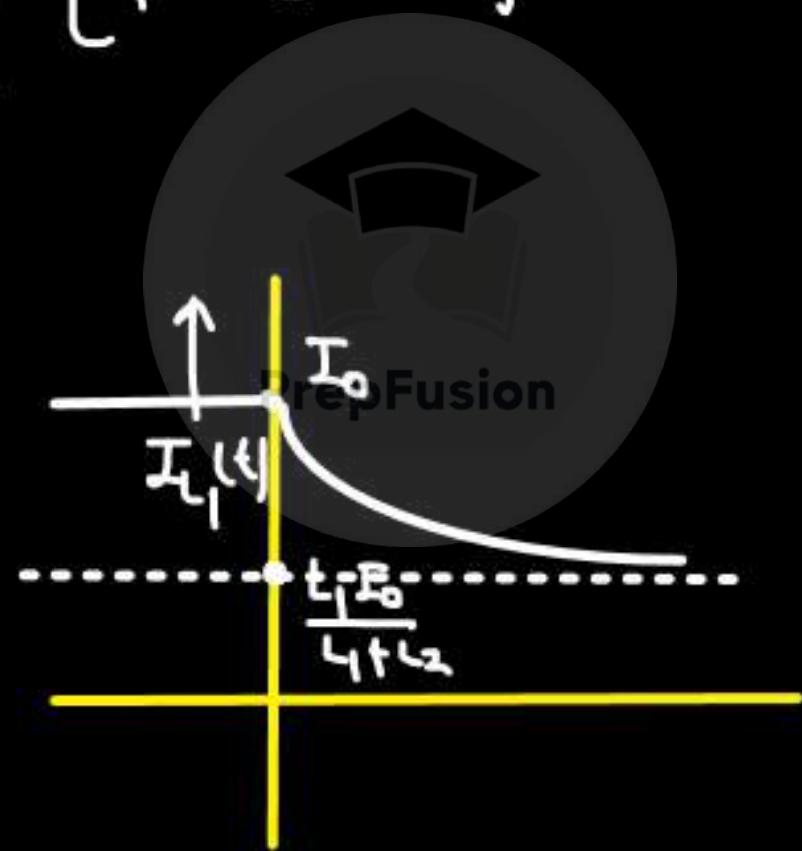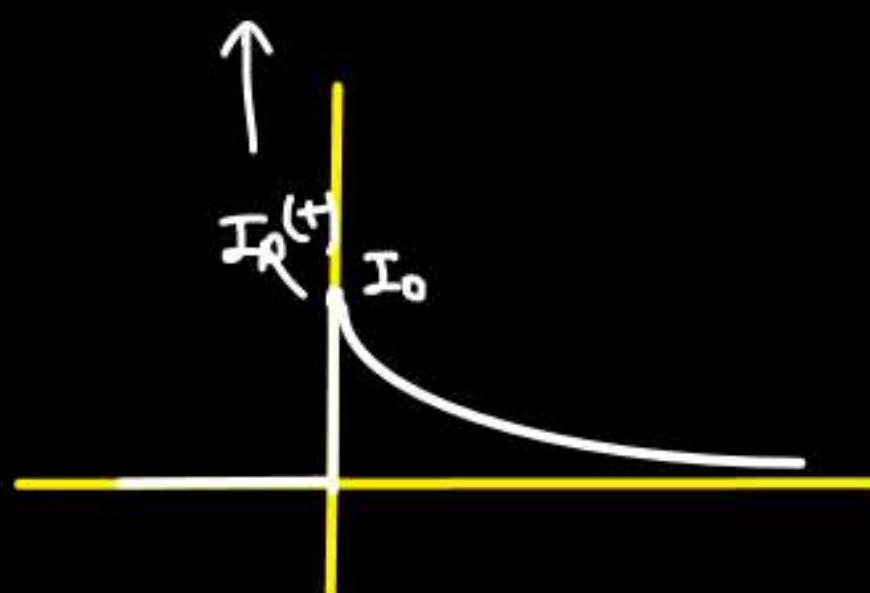
$$I_{L_2}(t) = -\frac{L_1 I_0}{L_1 + L_2} \left[1 - e^{-t/\tau} \right] u(t)$$




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES




$$V = V_{L_1}(t) = V_{L_2}(t) = V_R(t)$$

$$v(0^+) = -I_0 R$$


$$v(\infty) = 0$$

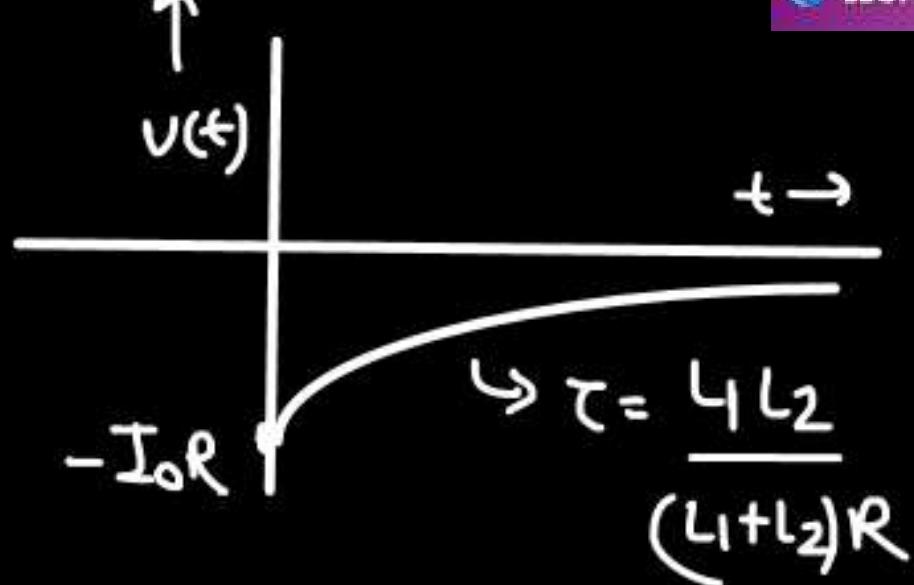

(c)

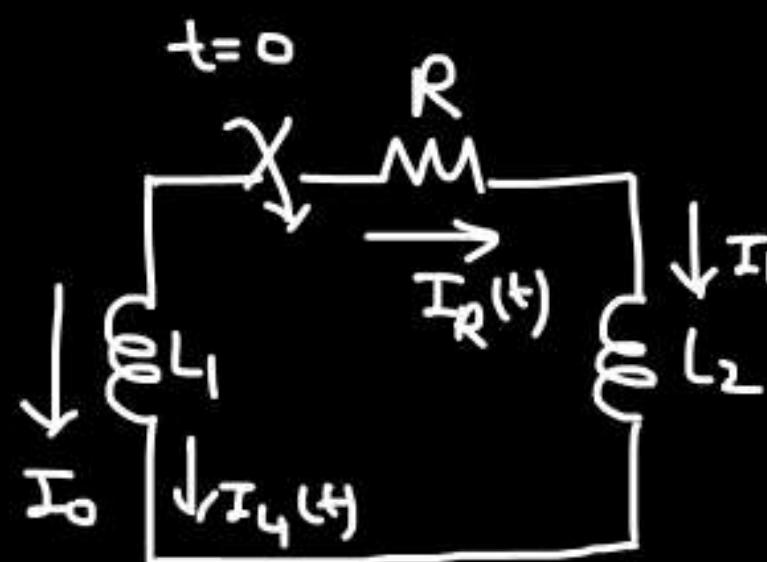

@ t=0


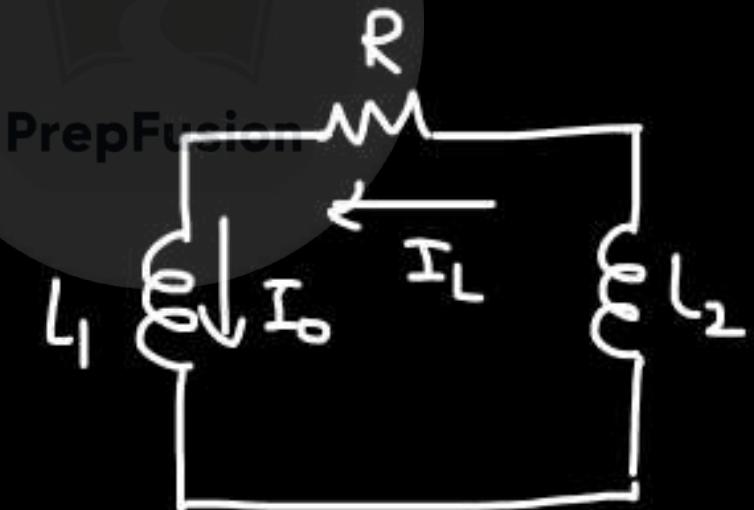


PrepFusion

$$L_1 I_0 = (L_1 + L_2) I_L$$

$$I_L = \frac{L_1 I_0}{L_1 + L_2}$$

$$I_L = I_{L_1}(0^+) = -I_{L_2}(0^+)$$

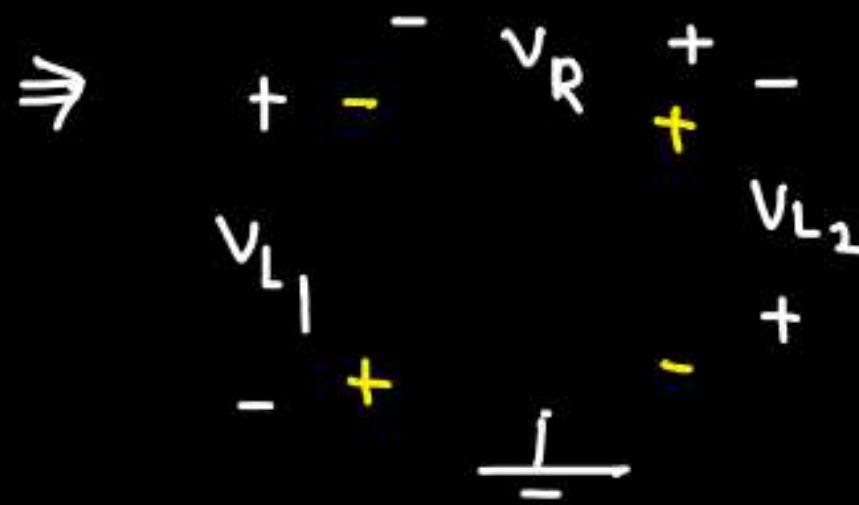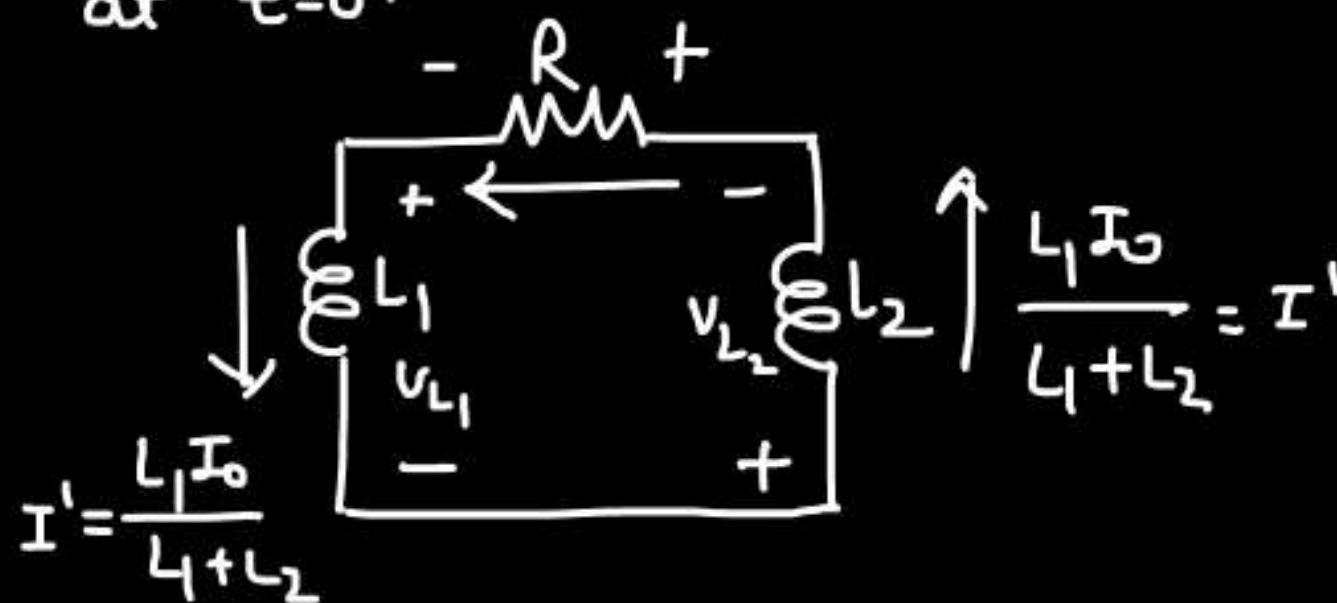at $t=0^+$ 

$$\tau = \frac{L_1 + L_2}{R}$$

$V_{L_1} = -[V_R + V_{L_2}]$
Prev $V_{L_2} = V_R + V_{L_2}$

Because of the opposite voltage drop, the current in both L_1 and L_2 will be decreasing and goes to zero @ steady state

@ S.S. $V_{L_2}(\infty) = V_{L_1}(\infty) = 0V$

or $\boxed{-\frac{V}{R}}$ $\Rightarrow I_{L_1}(\infty) = I_{L_2}(\infty) = I_R(\infty) = 0A$



$$I_{L_1}(0^+) = \frac{L_1 I_0}{L_1 + L_2}$$


$$I_{L_1}(\infty) = 0 \text{ A.p.}$$

$$I_R(0^+) = -\frac{L_1 I_0}{L_1 + L_2}$$


$$I_R(\infty) = 0 \text{ A.p.}$$

$$I_{L_2}(0^+) = -\frac{L_1 I_0}{L_1 + L_2}$$


$$I_{L_2}(\infty) = 0 \text{ A.p.}$$

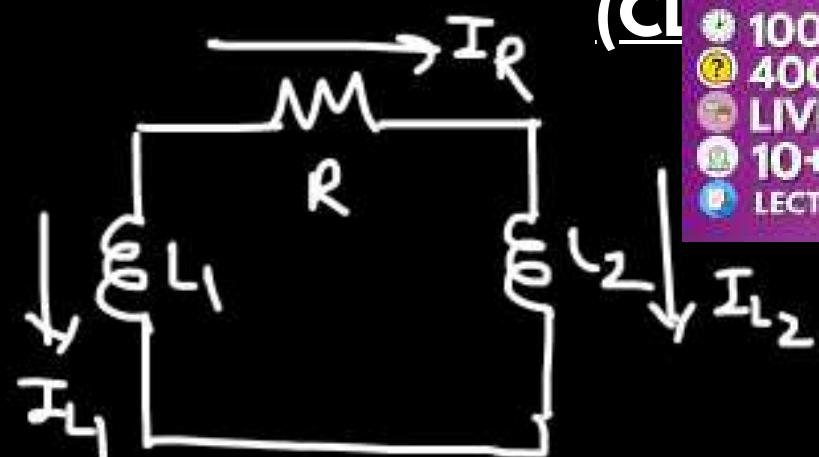


$$I_{L_1} = -I_R < -I_{L_2}$$

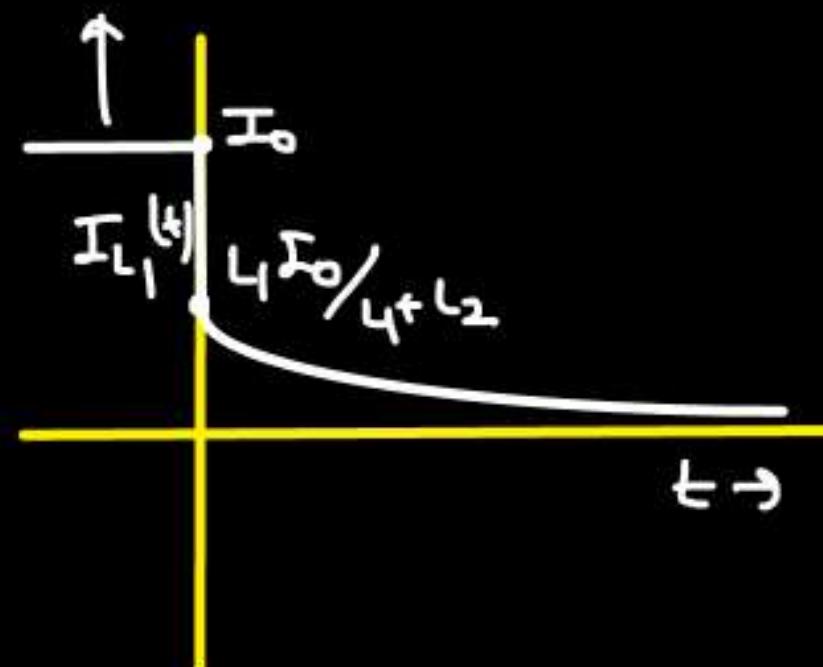
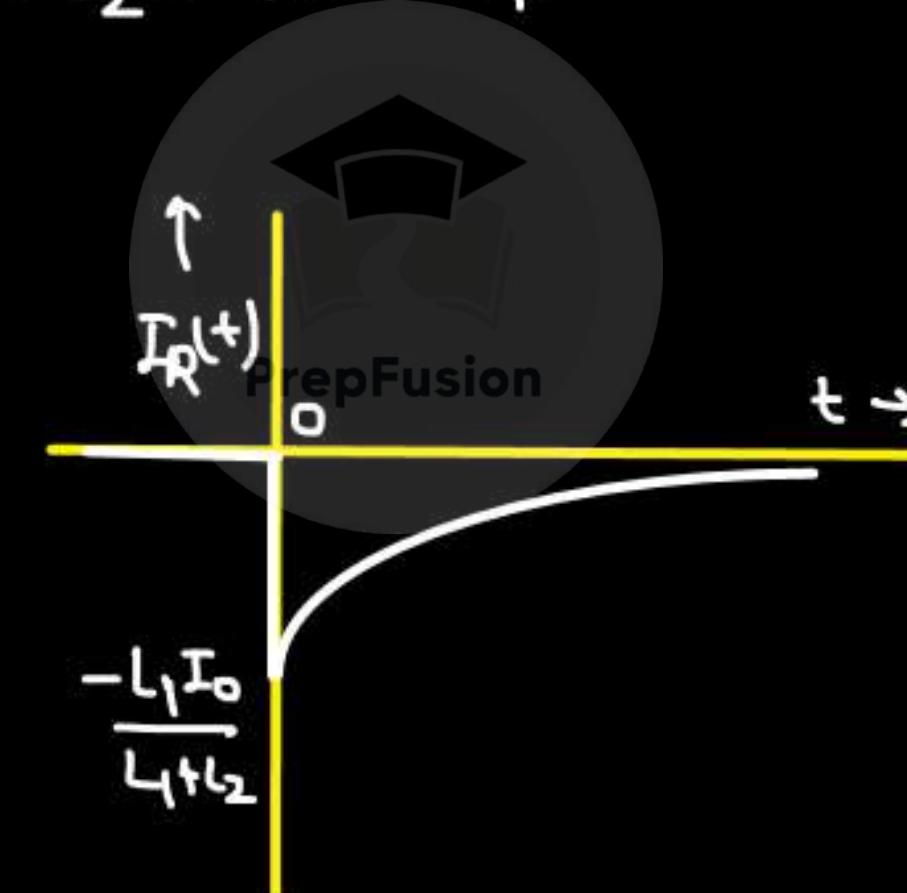
$$I_{L_1}(t) = I_0 u(-t) + \frac{L_1 I_0}{L_1 + L_2} e^{-t/\tau_{ult}} ;$$



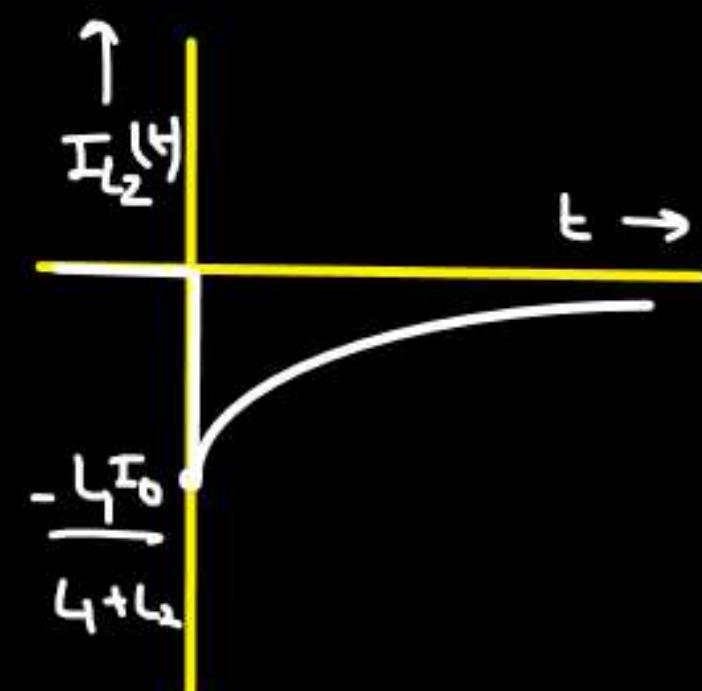
$$I_R(t) = \frac{L_1 I_0}{L_1 + L_2} e^{-t/\tau_{ult}} ;$$



$$I_{L_2}(t) = -\frac{L_1 I_0}{L_1 + L_2} e^{-t/\tau_{ult}} ;$$



Q. Draw V_o waveform.

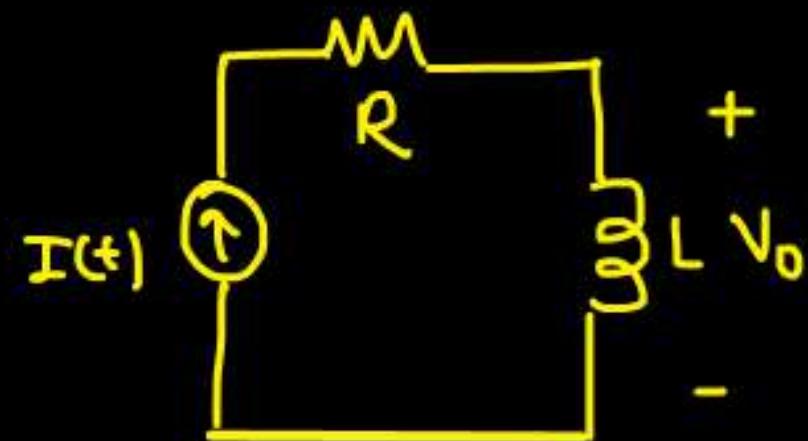

$$V_o(t) = L \frac{dI(t)}{dt}$$

$$= L \left[\frac{I_0 - 0}{0} \right] = L I_0 \delta(t) \quad \{ t=0 \}$$
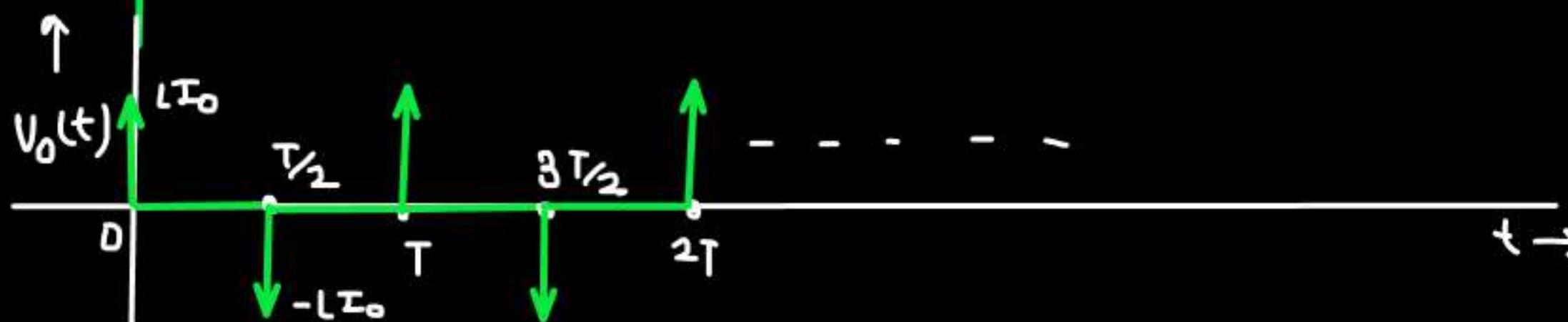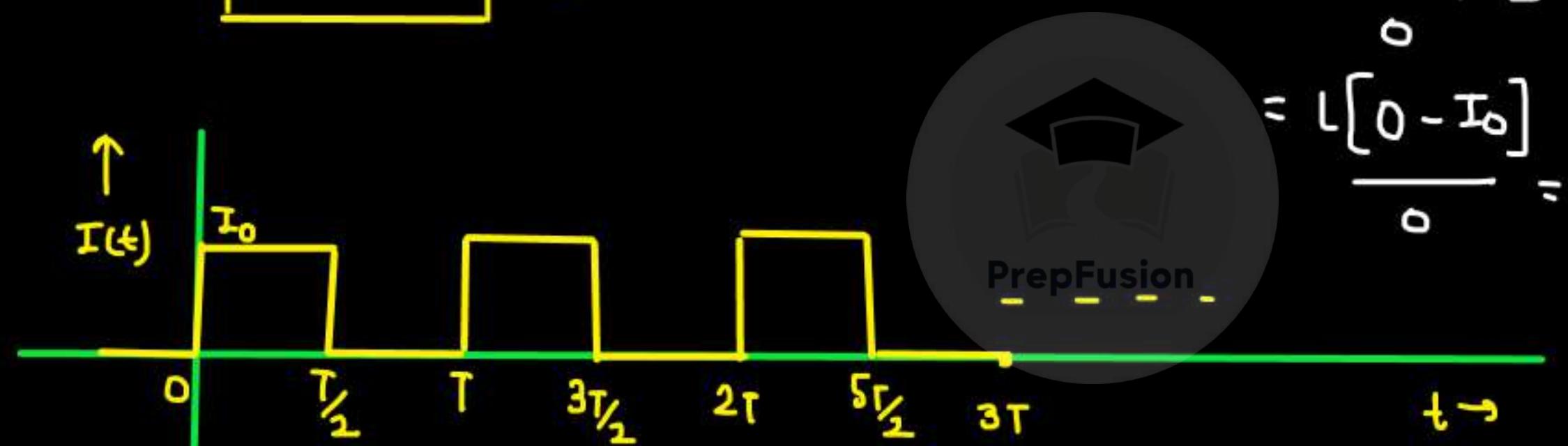
$$= L \left[\frac{0 - I_0}{0} \right] = -L I_0 \delta(t - T/2) \quad \{ t=T/2 \}$$






- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)



$$V_o(t) = \begin{cases} L I_0 \delta(t - n\tau) \\ -L I_0 \delta\left(t - \frac{(2n+1)\tau}{2}\right) \end{cases} ; n = 0, 1, 2, \dots =$$



Q. Draw the graph for V_o .

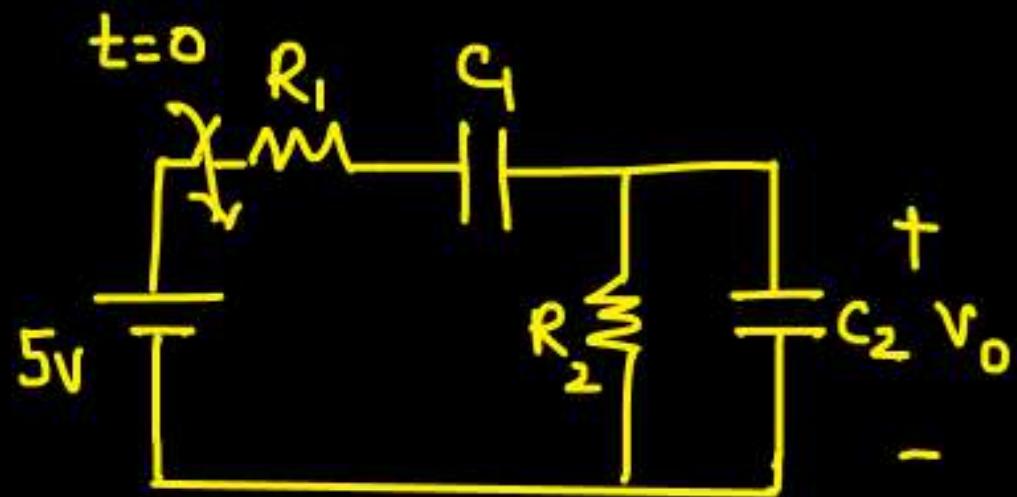

→ @ $t=0$

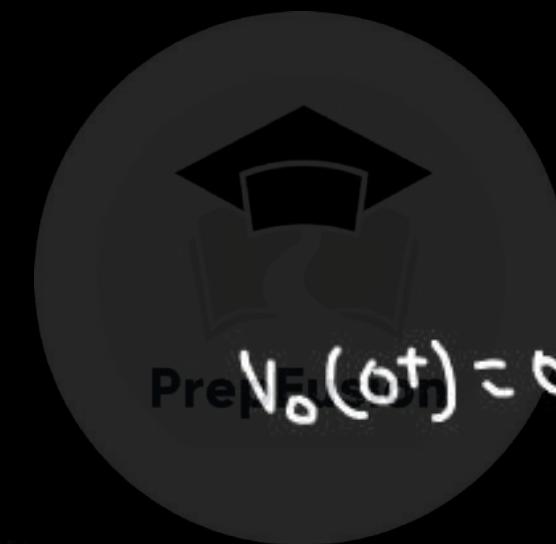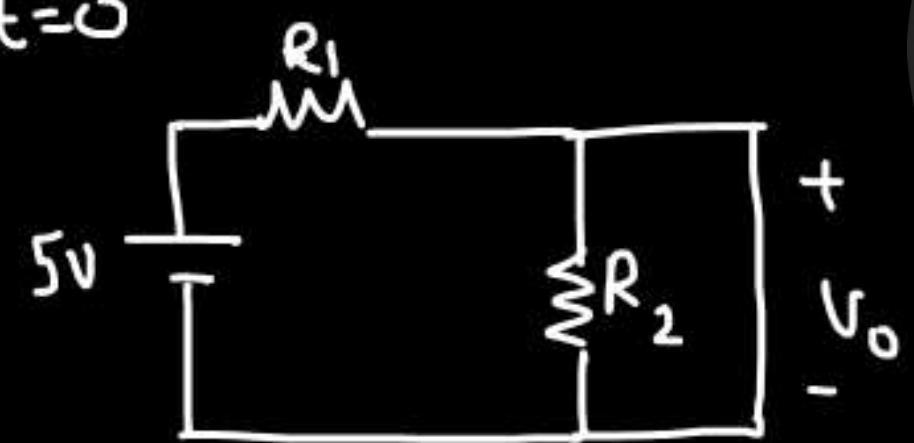

$$V_o(0^+) = 5V \quad \checkmark$$

ckt



you can't apply

$$V(\infty) \uparrow [V(0) - V(\infty)] e^{-t/\tau}$$


@ $t=0$



$$V_o(\infty) = 0V \quad \checkmark$$


{Applicable for
first order ckt}

Order ?

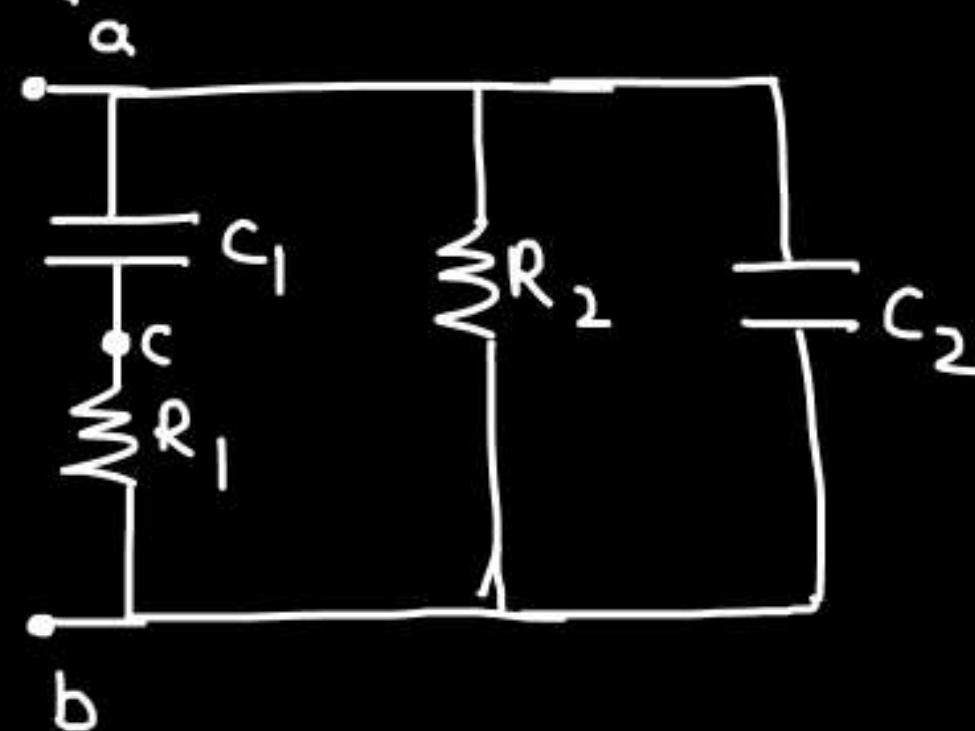

→ Two effective storing
element

↳
This is second order ckt

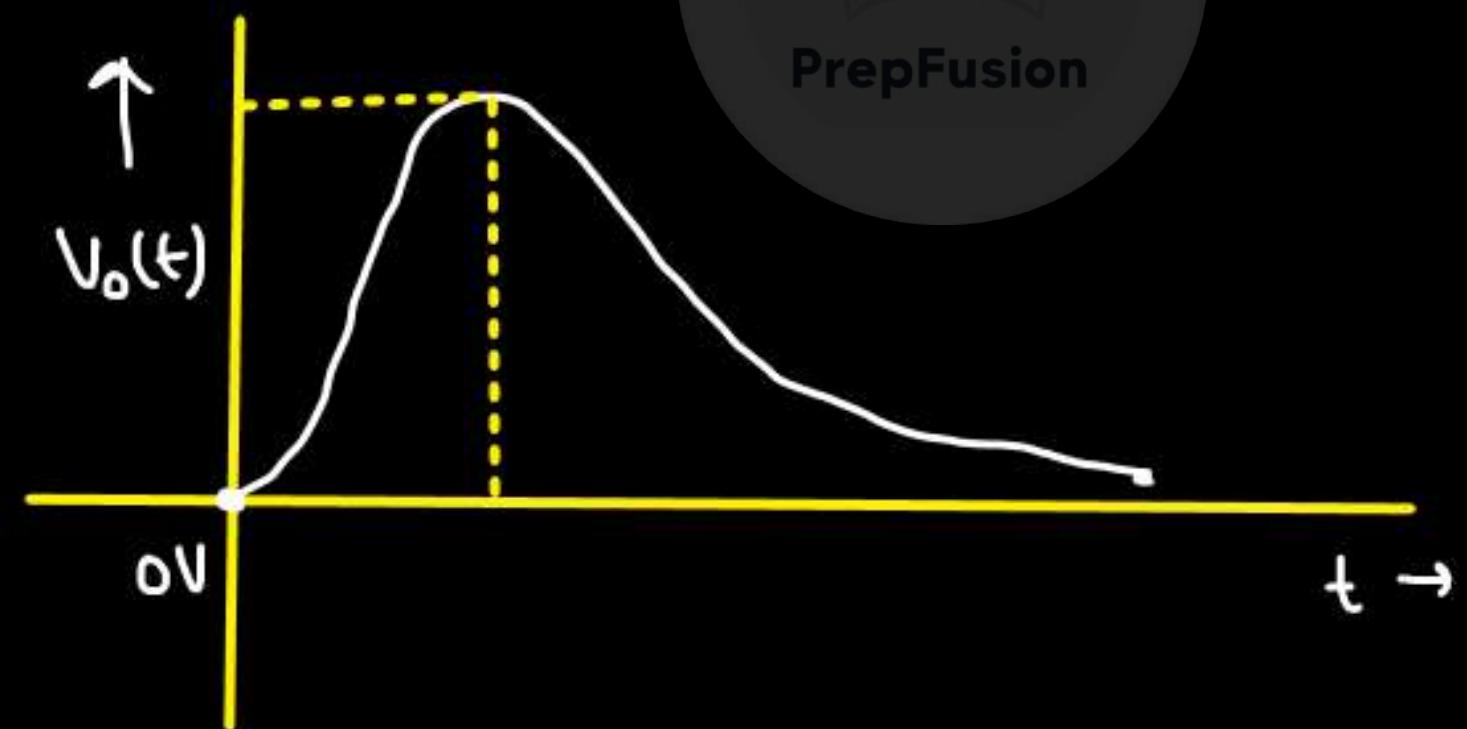

initial and final val
doesn't depend on the
order of the ckt

$$\left\{ \begin{array}{l} V_o(0^+) = 0V \\ V_o(\infty) = 0V \end{array} \right.$$

* Transfer function:-

in Laplace domain →

$$T.F. = \frac{O/P}{I/P} \mid \text{with no initial cond'n}$$

* Poles and Zeros:-

Transfer f'n $T(s) = \frac{N(s)}{D(s)}$

When $N(s) = 0 \Rightarrow s = s_{z_1}, s_{z_2}, \dots \rightarrow \text{zeros}$



when $D(s) = 0 \Rightarrow s = s_{p_1}, s_{p_2}, \dots \rightarrow \text{poles}$

Eg. $\rightarrow T(s) = \frac{(s+3)(s+2)}{(s+5)(s+1)}$

Zeros $\rightarrow -3, -2$

Poles $\rightarrow -5, -1$

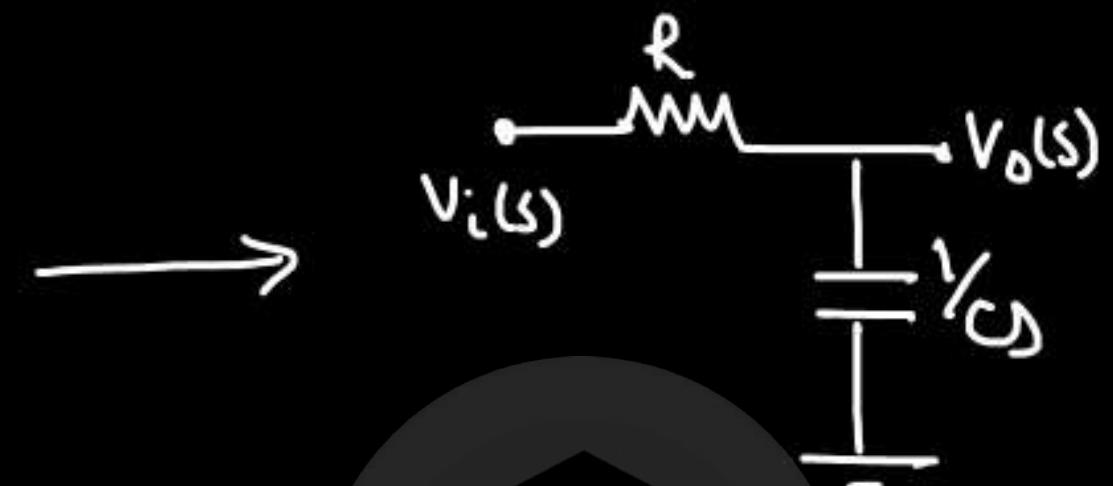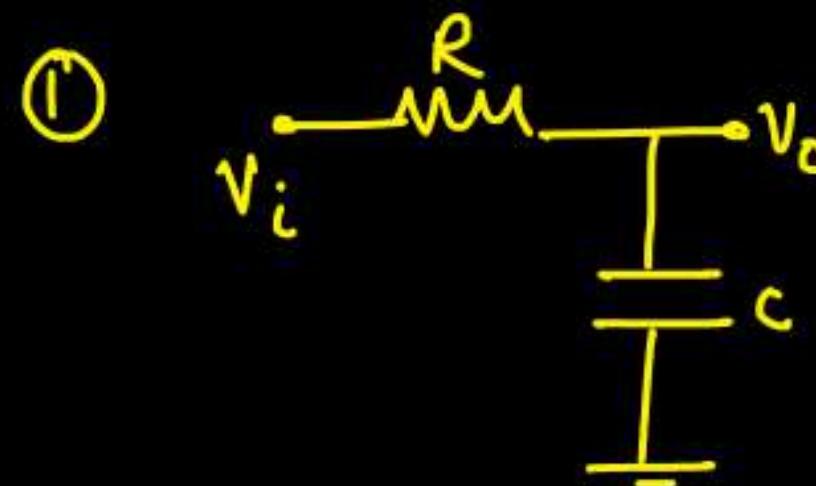Q. Find T.F. for the given ckt and then find poles &



N.B. → For a T.F., no. of zeros and no. of poles are always equal.

In this example, there is a pole at $-1/\text{RC}$ and a zero at $s=\infty$.

$\frac{V_o(s)}{V_i(s)} = \frac{1/s}{1/s + R} = \frac{1}{R\omega + 1}$

$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{R\omega + 1}$

Zeros → No zero/zero at $s=\infty \rightarrow$ No zero
 Poles → $s_p = -1/\text{RC} \rightarrow 1$ pole

N.B. → Order of the ckt is defined by the no. of poles / by the degree of $T(s)$. { ∵ $T(s) = \frac{N(s)}{D(s)}$ }

⇒ Order of the ckt has nothing to do with the no. of zeros.

* For a first order ckt;

Time constant = negative reciprocal of the pole

$$\tau = -\frac{1}{s_p}$$

PrepFusion

Eg. → For a 1st order ckt, the pole is at $-1/RC$

$$\rightarrow \text{Time constant} = \frac{-1}{-\frac{1}{RC}} = RC =$$

Eg. → Find the order of the ckt whose Transfer f'n is given such as | Also tell the time const.

(a) $\frac{V_o(s)}{V_i(s)} = \frac{L}{sRC + L} \rightarrow 1^{\text{st}} \text{ order}; \omega_p = -\frac{1}{RC}; \tau = RC$


(b) $\frac{V_o(s)}{V_i(s)} = \frac{LS}{Ls + R} \rightarrow 1^{\text{st}} \text{ order}; \omega_p = -\frac{R}{L}; \tau = \frac{L}{R}$

(c) $\frac{I_o(s)}{V_i(s)} = \frac{2}{s(s+5)} \rightarrow 2^{\text{nd}} \text{ order}; \omega_{p_1} = 0, \omega_{p_2} = -5;$

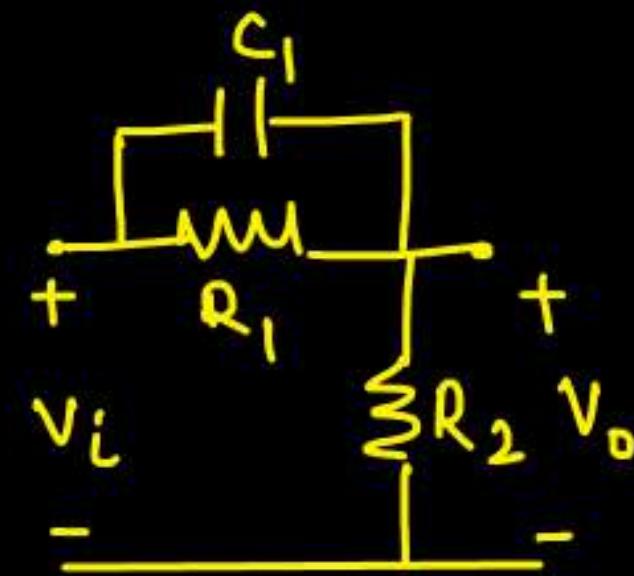
(d) $\frac{Y(s)}{X(s)^2} = \frac{s^2 + 2s + 3}{s^2 + 5s + 13} \rightarrow 2^{\text{nd}} \text{ order}; \omega_{p_1}, \omega_{p_2} \checkmark; \omega_{z_1}, \omega_{z_2}$

Q. Write down the transfer f'n for the given ckt.


- ↳ Tell the location of poles and zeros.
- ↳ Tell the time constant.
- ↳ Define the order of the ckt.



(a)

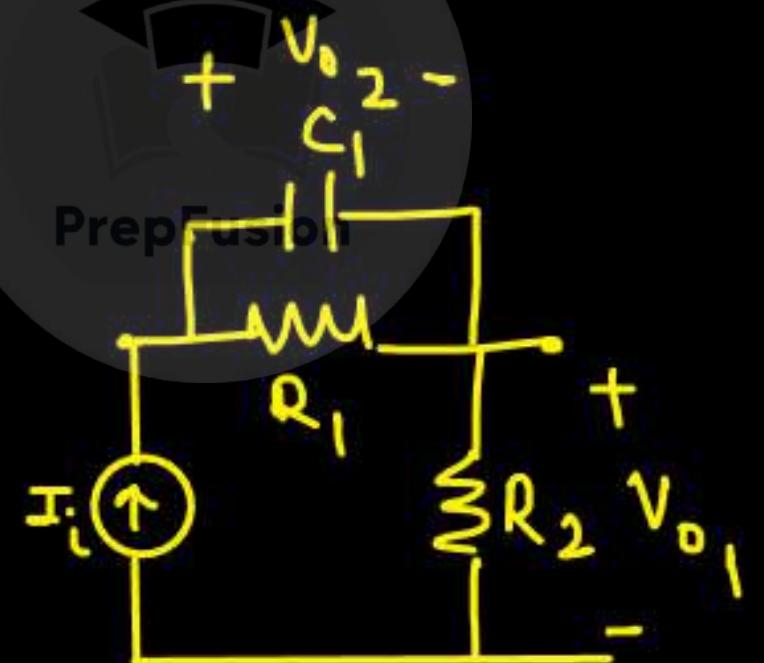

(b)

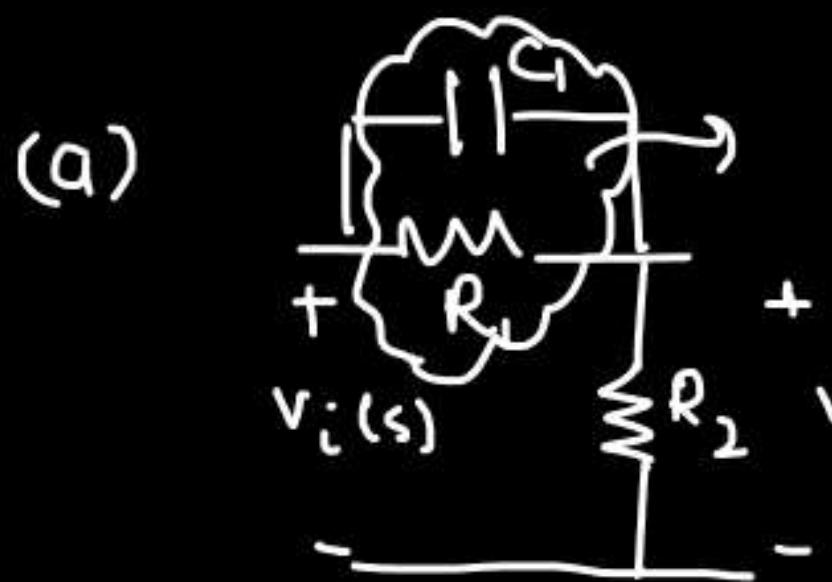AIR 27 (ECE)
AIR 45 (IN)

$$\frac{R_1/C_s}{R_1 + 1/C_s s^2} + \frac{R_1}{R_1 C_1 s + 1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_2 + \frac{R_1}{R_1 C_1 s + 1}}$$

PrepFull

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 (R_1 C_1 s + 1)}{R_1 R_2 C_1 s + (R_1 + R_2)}$$

→ Transfer
 f^n

$$\tau = \frac{1}{\omega_p}$$


$$\tau = \left(\frac{R_1 R_2}{R_1 + R_2} \right) C$$

Only one pole
↓
1st order

$$\omega_z = -\frac{1}{R_1 C_1}$$

$$\omega_p = -\frac{(R_1 + R_2)}{R_1 R_2 \cdot C_1}$$

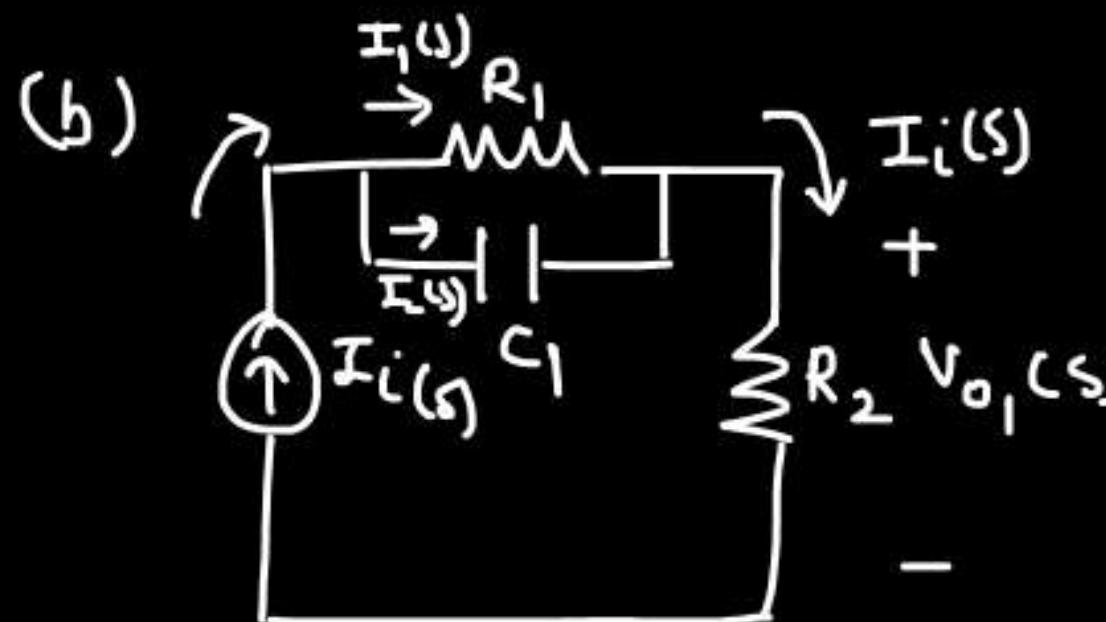- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$I_i(s) = I_1(s) + I_2(s)$$

$$V_{01}(s) = I_i(s) \times R$$

$$\frac{V_{01}(s)}{I_i(s)} = R$$


→ Transfer f^n



no poles, no zero



Zero order

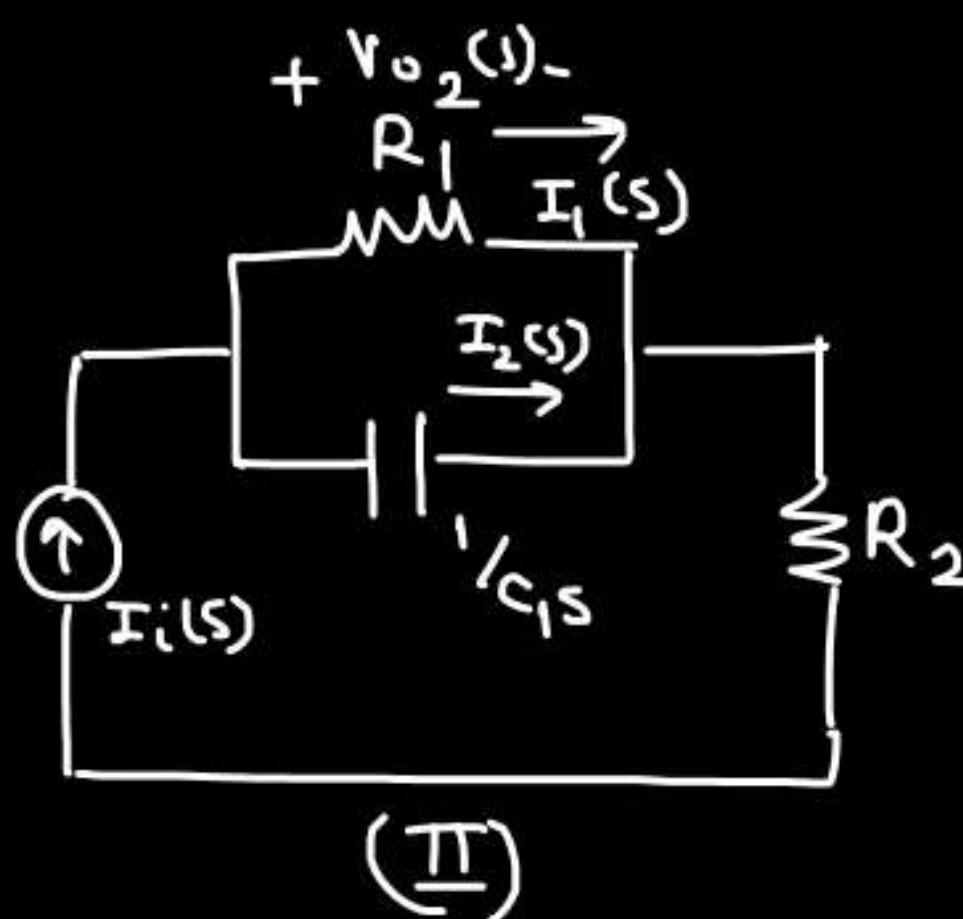

$$V_{02}(s) = I_1(s) R_1 = I_2(s) \times \frac{1}{C_1 s}$$

$$V_o(s) = I_i(s) \times \frac{\frac{1}{C_1 s}}{\frac{1}{C_1 s} + R_1} \times R_1 = \frac{I_i(s) R_1}{R_1 C_1 s + 1}$$



$$\frac{V_o(s)}{I_i(s)} = \frac{R_1}{R_1 C_1 s + L}$$

$$\downarrow \\ \omega_p = -\frac{1}{R_1 C_1} ; \quad \tau = R_1 C_1$$

Order = 1st order








N.B. → The order of a ckt is defined w.r.t a particular o/p


For (I) $\frac{V_{o_1}(s)}{I_i(s)}$ → zero order

For (II) $\frac{V_{o_2}(s)}{I_i(s)}$ → 1st order



Q. Find the order of the ckt.

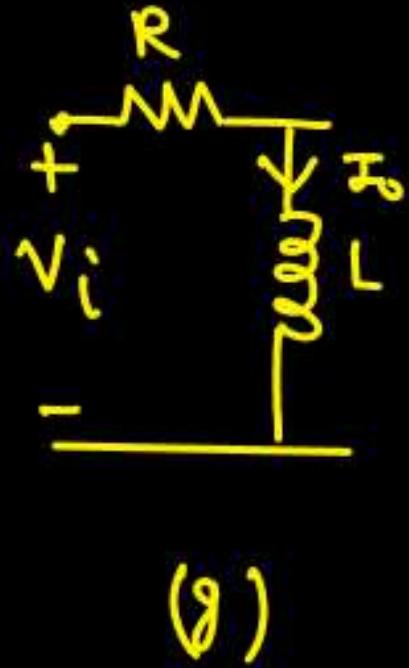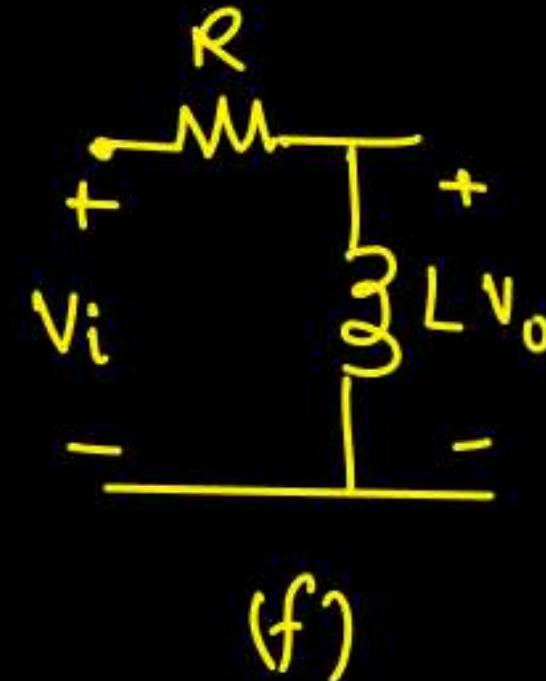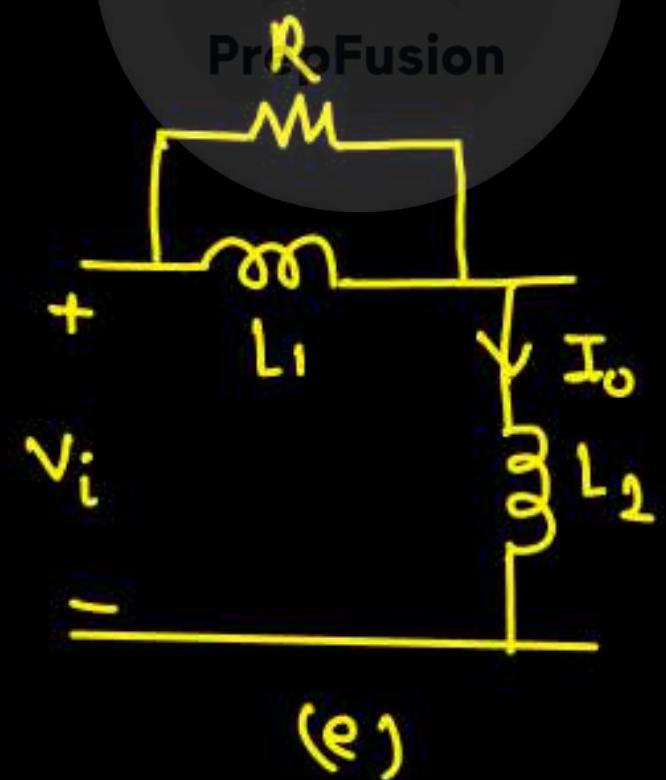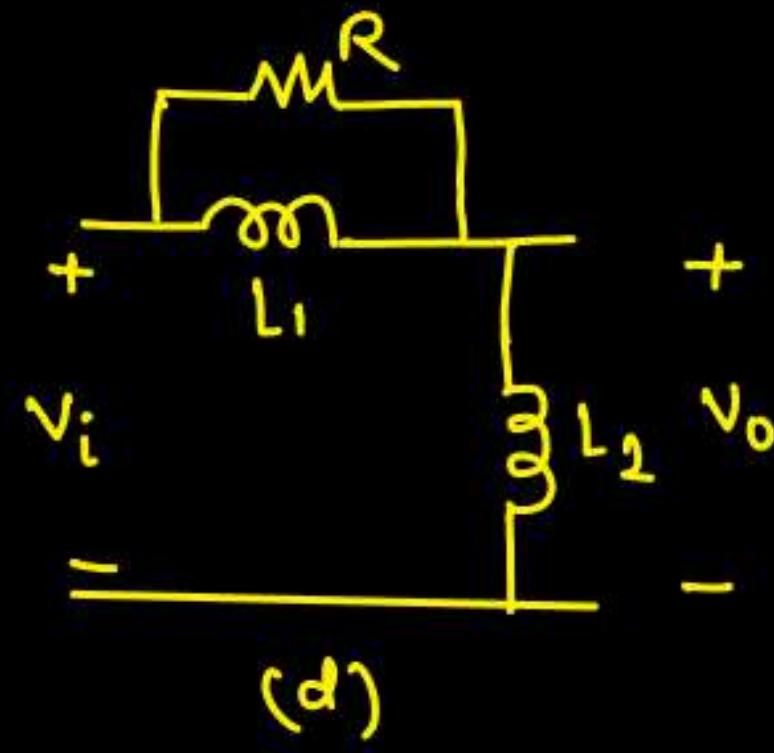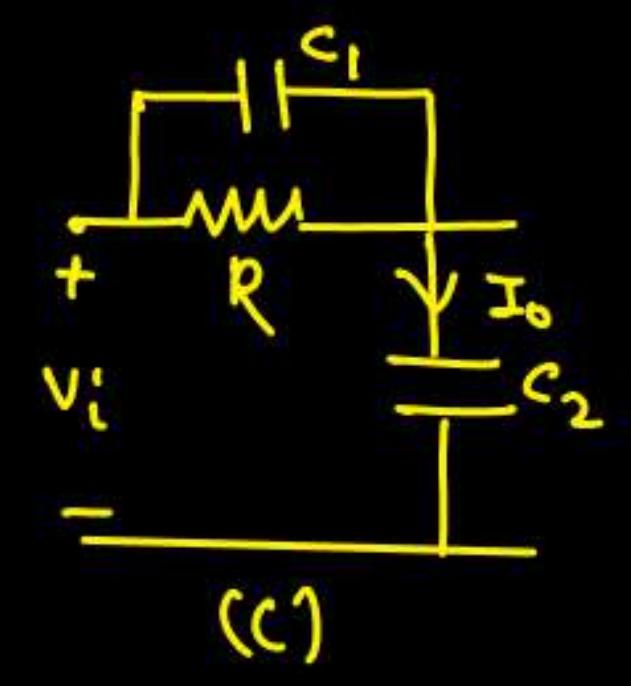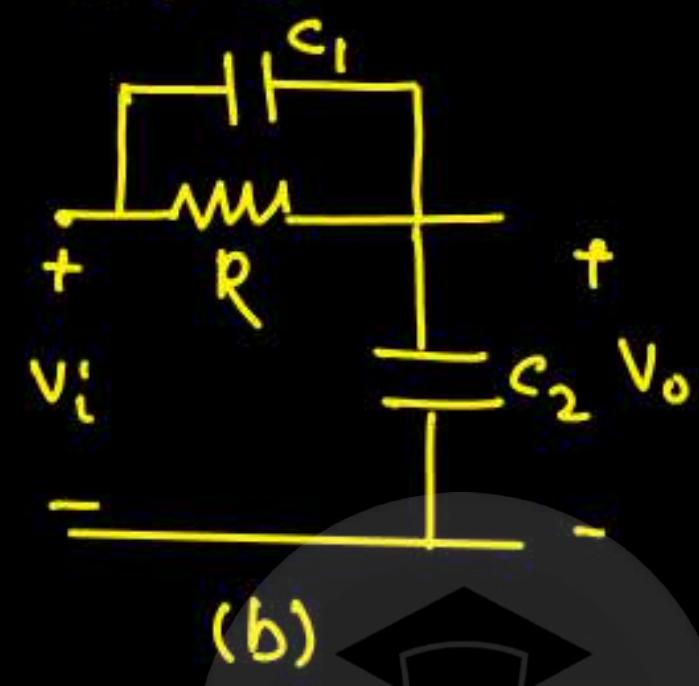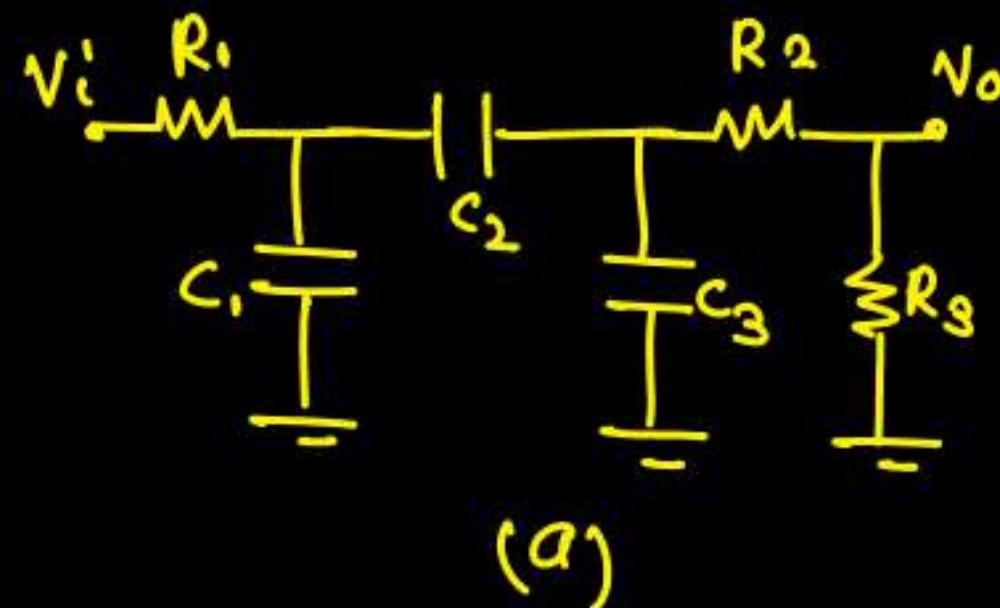

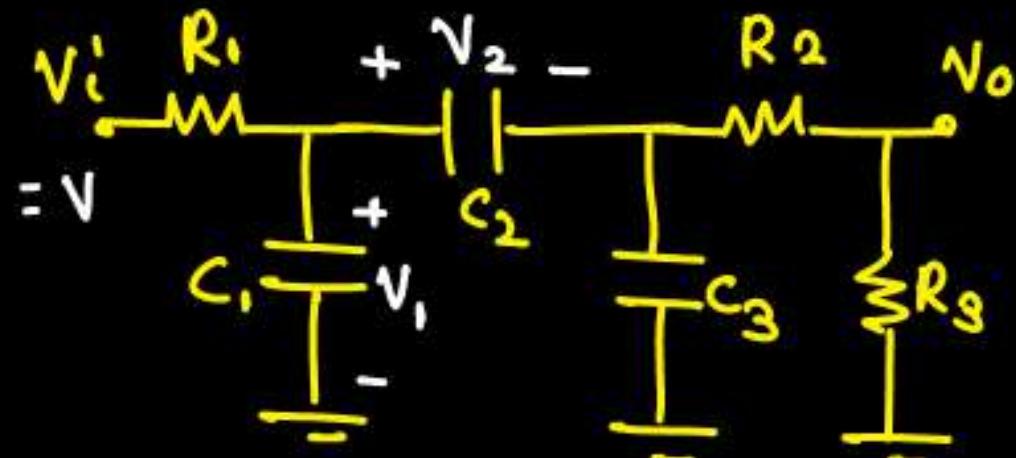



(a)

$$\rightarrow \begin{cases} V_{c_1} = V_1 \\ V_{c_2} = V_2 \end{cases} \rightarrow \text{independent Voltage} \Rightarrow \text{Effective two storing elements}$$

$V_{c_3} = V_1 - V_2 \rightarrow \text{dependent Voltage}$

J_1
2nd order ckt

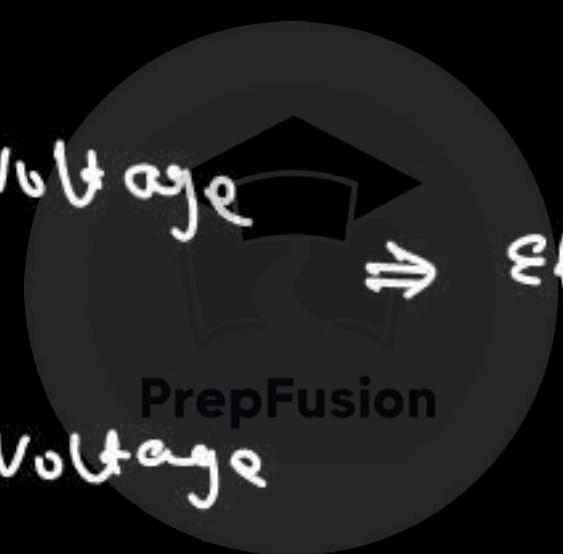

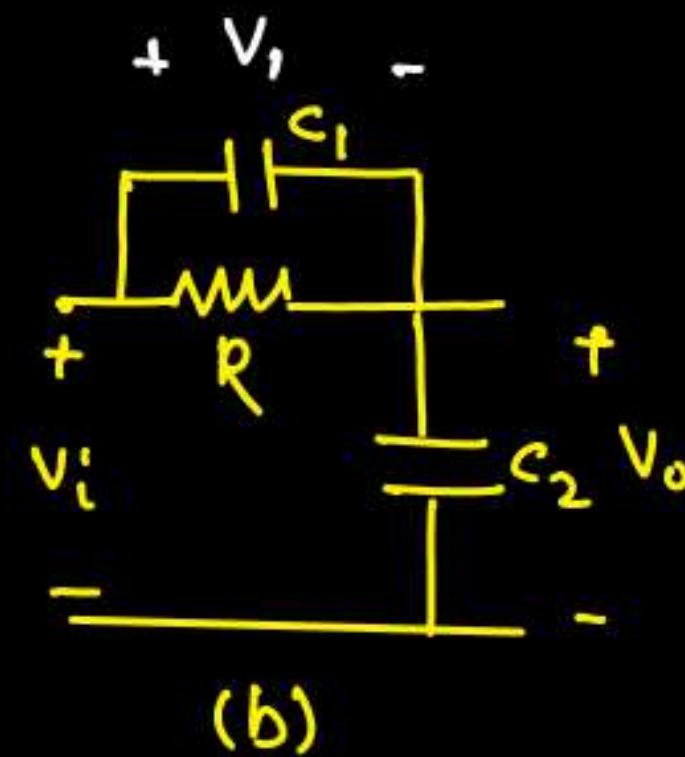


$V_{C_1} = V_1 \leftarrow$ independent

$V_{C_2} = V_i - V_1 \leftarrow$ dependent
 ↓
 4h

Only one storing element

↳ First order ckt



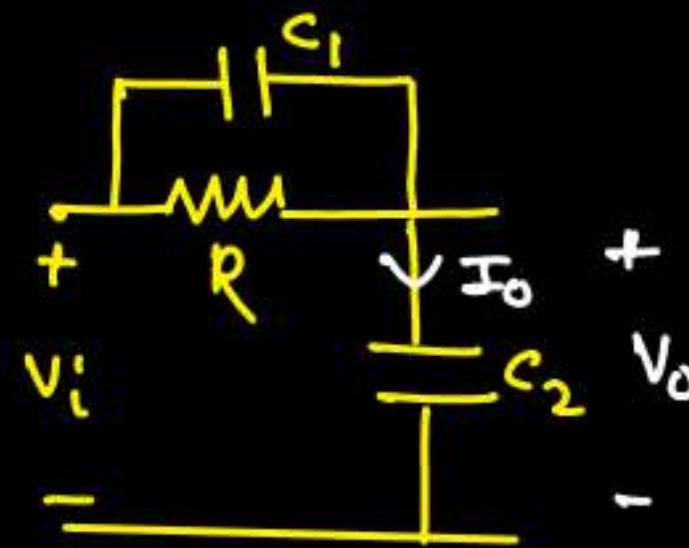

$\rightarrow \frac{I_o(s)}{\frac{1}{jC}V_o(s)}$ (b)

$$V_o(s) = \frac{A(sZ_1 + j)}{s(SP_1 + j)} V_i(s)$$

\downarrow
2nd order

$$I_o(s) = \frac{A(sZ_1 + j)}{s(SP_1 + j)} V_i(s)$$

\downarrow
2nd order

For V_o , it was first order ckt

$$V_o(s) = \frac{A(sZ_1 + j)}{(SP_1 + j)} V_i(s)$$

$$I_o(s) = CSV_i(s)$$

↳ in case of Cap., the current adds up

are zero at $\omega_x = 0$, not a pole




The order remain the same as
voltage of P

$$\frac{I_o(s)}{V_i(s)} = \frac{AC(sZ_1 + j)}{(SP_1 + j)}$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

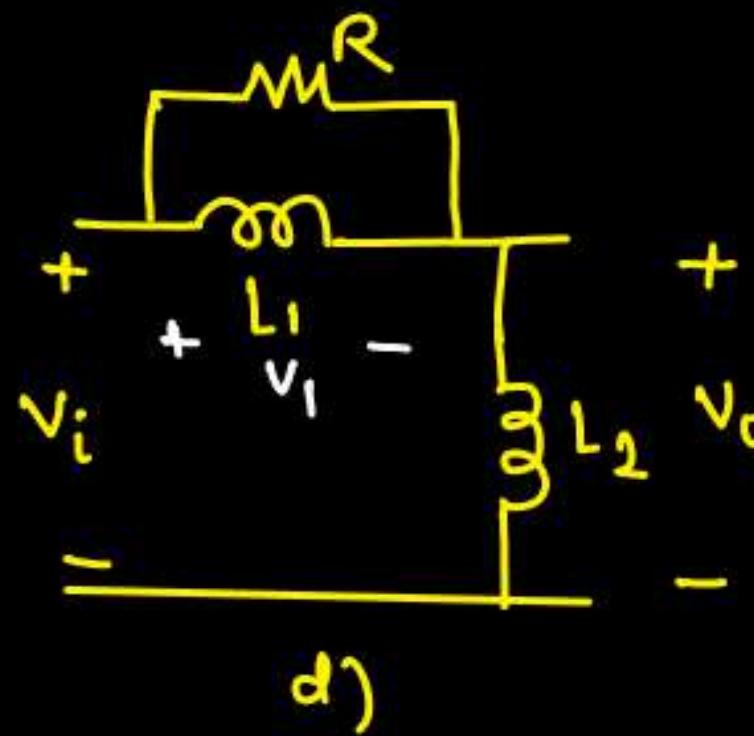
AIR 27 (ECE)
AIR 45 (IN)

$$V_{L_1} = V_i \quad \leftarrow \text{independent}$$
$$V_{L_2} = V_i - V_1 \quad \leftarrow \text{dependent}$$

$\downarrow h$

Only one effective storing element
 $\Rightarrow 1^{\text{st}}$ order


PrepFusion

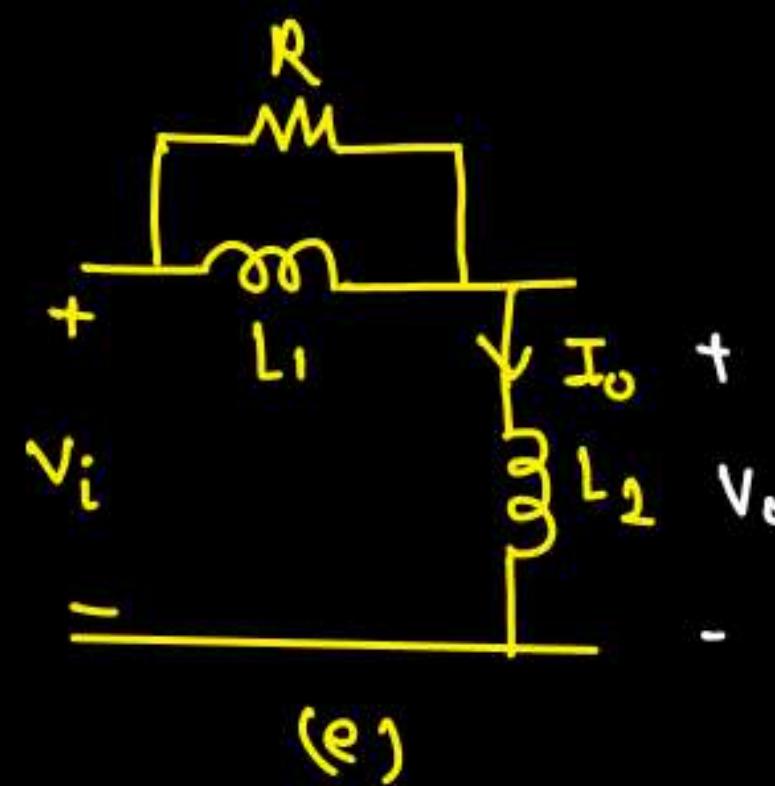

$\left\{ \begin{array}{l} \\ \end{array} \right.$
 2nd order


$$\frac{V_o(s)}{V_i(s)} = \frac{A (sZ_1 + 1)}{(sP_1 + L)}$$

$$V_o(s) = \frac{A (sZ_1 + 1)}{(sP_1 + L)} V_i(s)$$

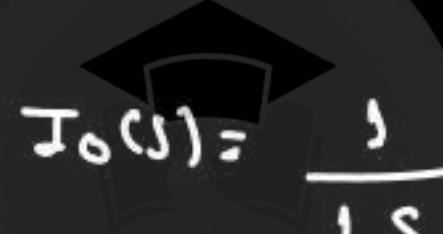
 $I_o(s) = \frac{1}{Ls} V_o(s)$
 PrepFusion

current adds up a pole @ $\omega = 0$
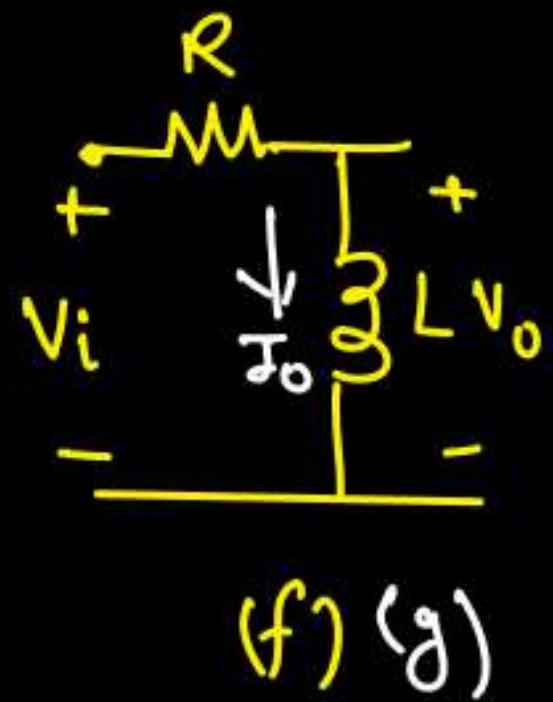
$$I_o(s) = \frac{A (sZ_1 + 1)}{Ls (sP_1 + L)} \rightsquigarrow 2^{\text{nd}} \text{ order}$$



$$\frac{V_o(s)}{V_i(s)} = \frac{LS}{R+LS} \Rightarrow \text{Zero @ } \omega=0$$

→ 1st order

$$V_o(s) = \frac{LS}{R+LS} V_i(s)$$

$$I_o(s) = \frac{1}{LS} \times \underbrace{V_o(s)}_{\substack{\hookrightarrow 1^{\text{st}} \text{ order ch} \\ \downarrow \text{PrepFusion}}} \quad \text{adding up another pole @ } \omega=0$$

$\frac{1}{s}$
2nd order $\mathcal{Z}X =$

→ $V_o(s)$ is having a zero at $\omega=0 \Rightarrow s_0$, there is pole - zero cancellation

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$I_o(s) = \frac{1}{Ls} V_o(s)$$

$$\approx \frac{1}{Ls} \times \frac{Ls}{R + Ls} V_i(s)$$

$$I_o(s) \approx \frac{1}{R + Ls} V_i(s)$$

PrepFusion



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)


Analysis of 2nd order ckt's:-

- Two effective storing element.
- Order of differential eqn is two
- no. of poles = 2

[N.B. → for a stable S/S, poles will always be in the left half of s-plane]

* nature of poles of a second order S/S:-

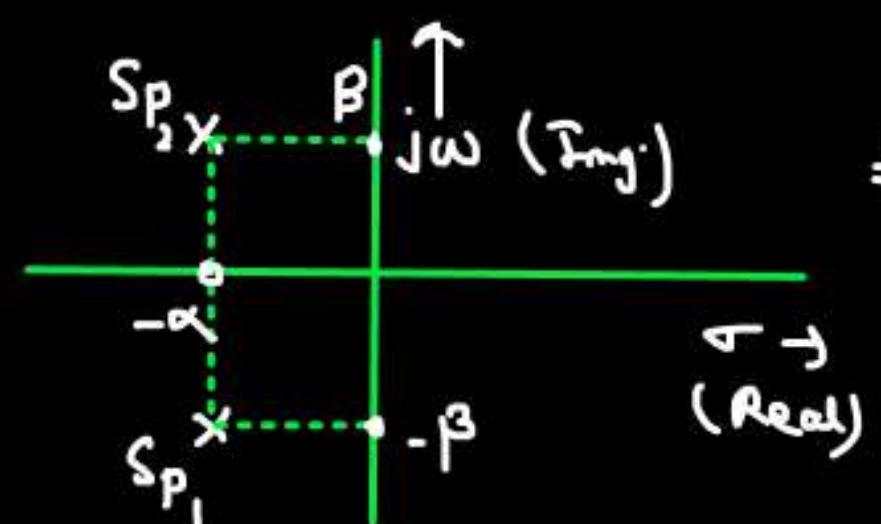(a) Both roots are complex and conjugate:-



$$s_p = -\alpha \pm j\beta$$

$\Rightarrow s_{p_1} = -\alpha - j\beta$ v \Rightarrow Underdamped S/S

$$s_{p_2} = -\alpha + j\beta$$



considering both initial and final values to be zero.


$$\text{damping} \propto \frac{1}{\text{oscillation}}$$

\Rightarrow Zero damping = infinite oscillation




N.B. - in underdamped response, damping is not enough to kill the oscillation but eventually the oscillation will die out.

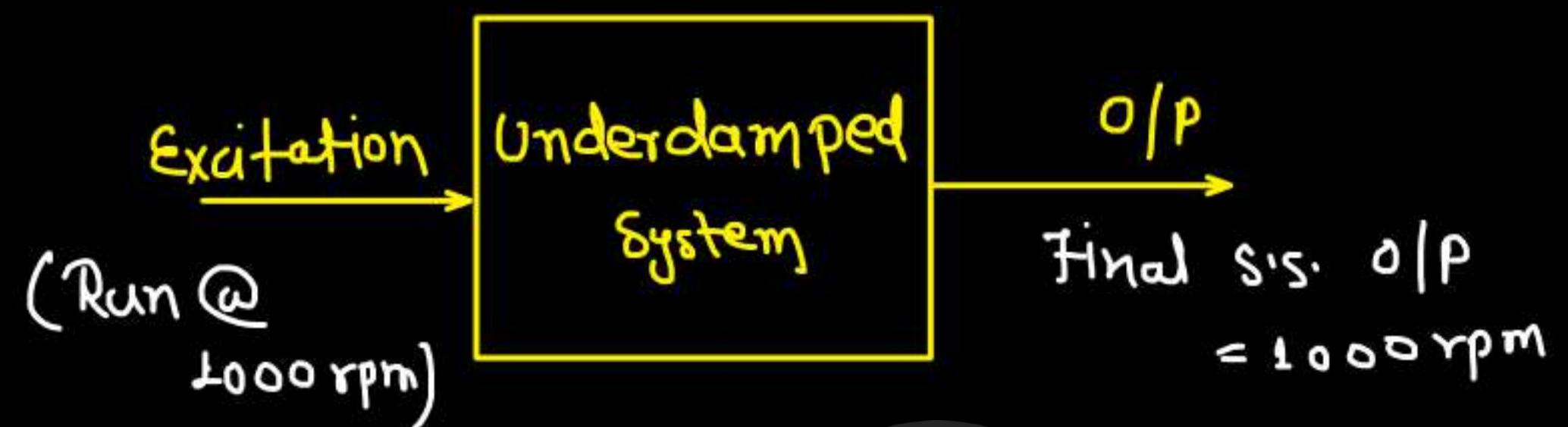Eg → let's assume I give an excitation to my motor to run @ 1000 rpm. The system is underdamped. How should the response look like?



→ since the S/S is underdamped, the response will oscillate around 1000 rpm and will reach steady state after some time.

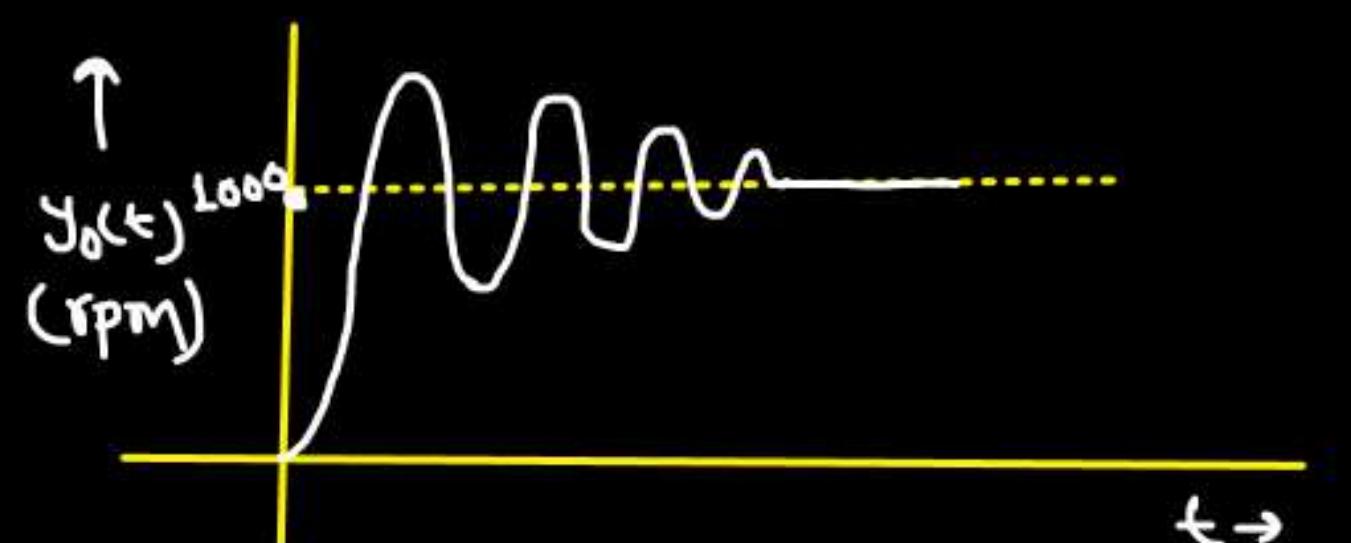
considering initial speed of motor to be zero. $\Rightarrow y_o(0^+) = 0$



(b) Both real but same roots:-


$$s_{p_1} = -\alpha$$

$$s_{p_2} = -\alpha$$

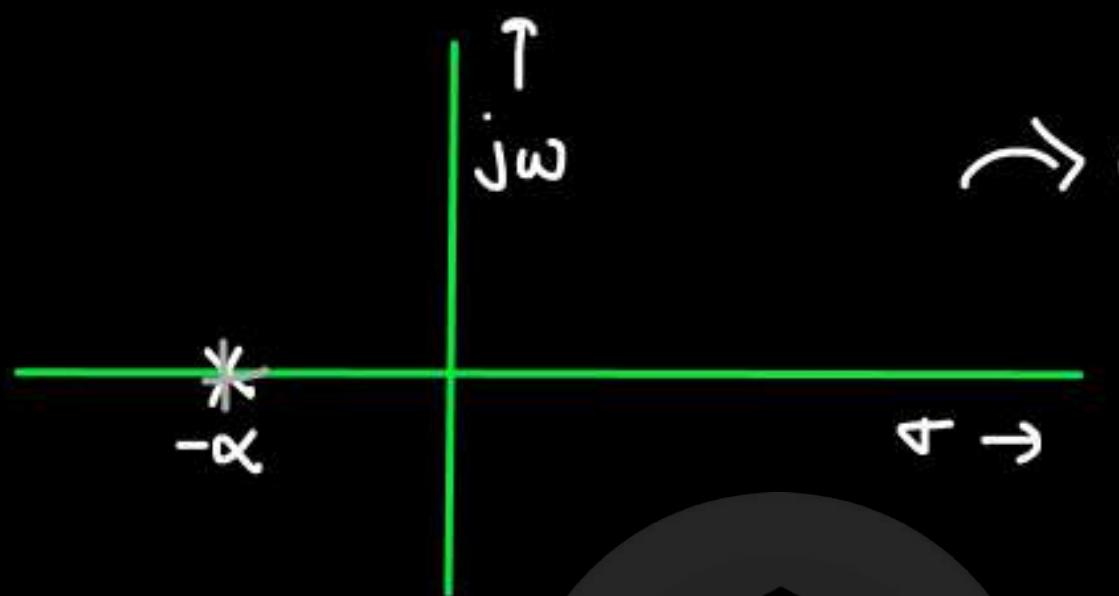

→ critically damped


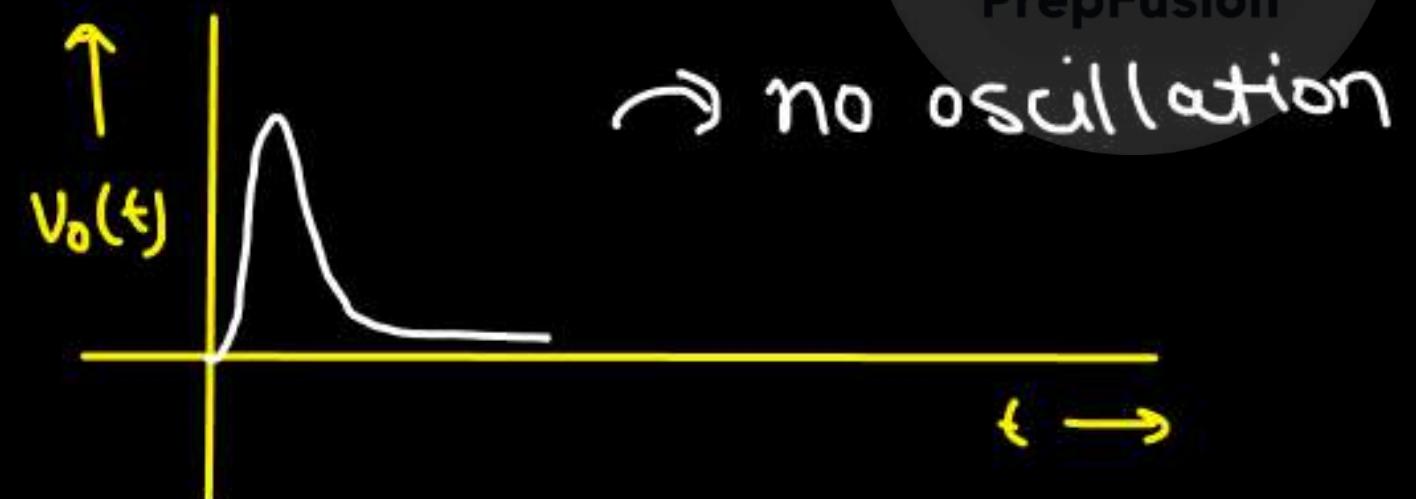
Considering both initial and final value to be zero.



→ no oscillation

N.B. - in critically damped sys, there are no oscillation and the response is faster.

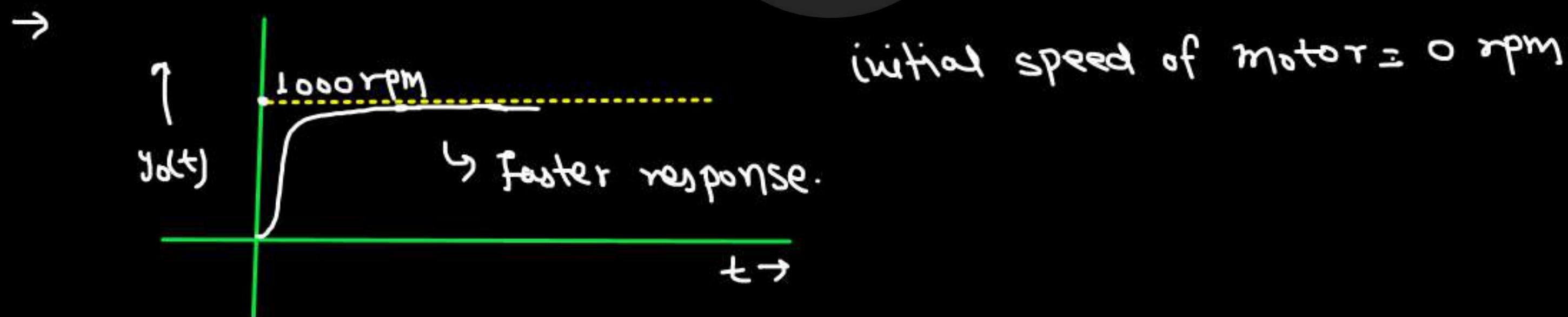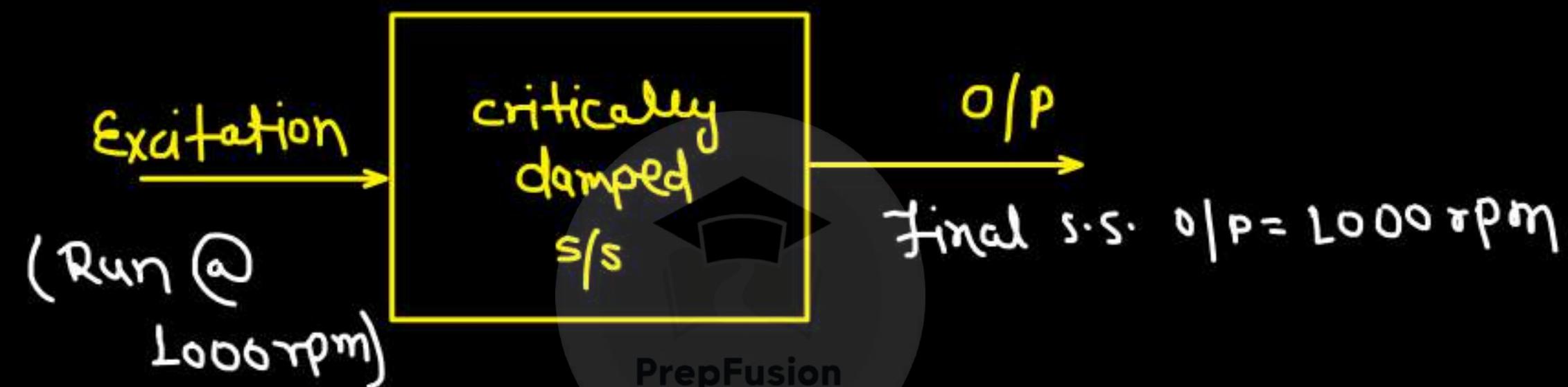
Eg → let's assume I give an excitation to my motor to run @ 1000 rpm and the system is critically damped. Then How should the response look like?




(c) Both roots are real but different.

$$s_{p_1} = -\alpha_1$$

$$s_{p_2} = -\alpha_2$$


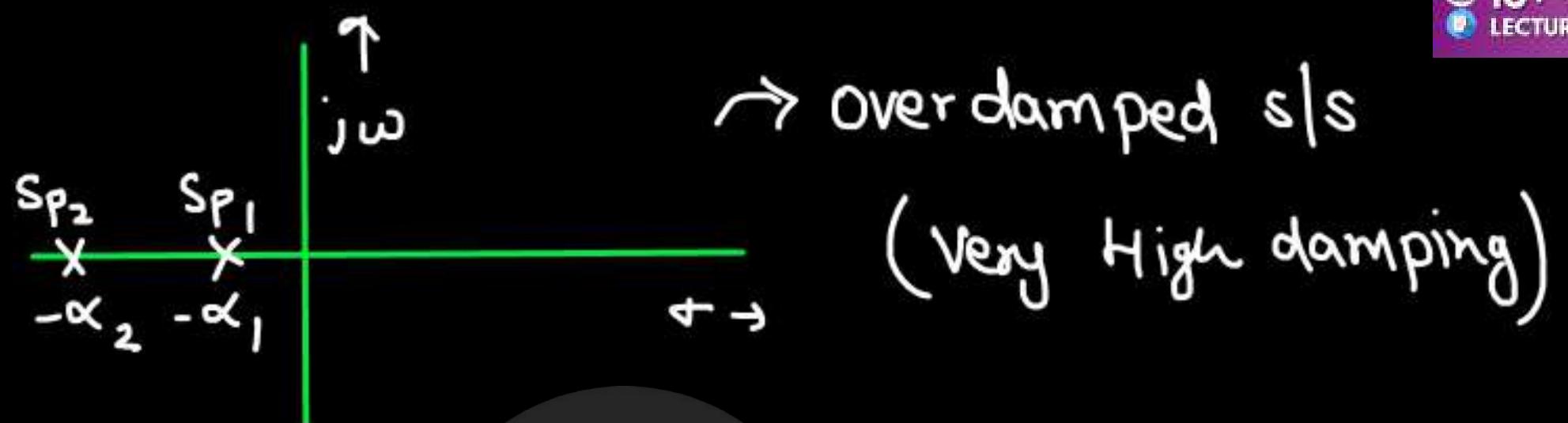


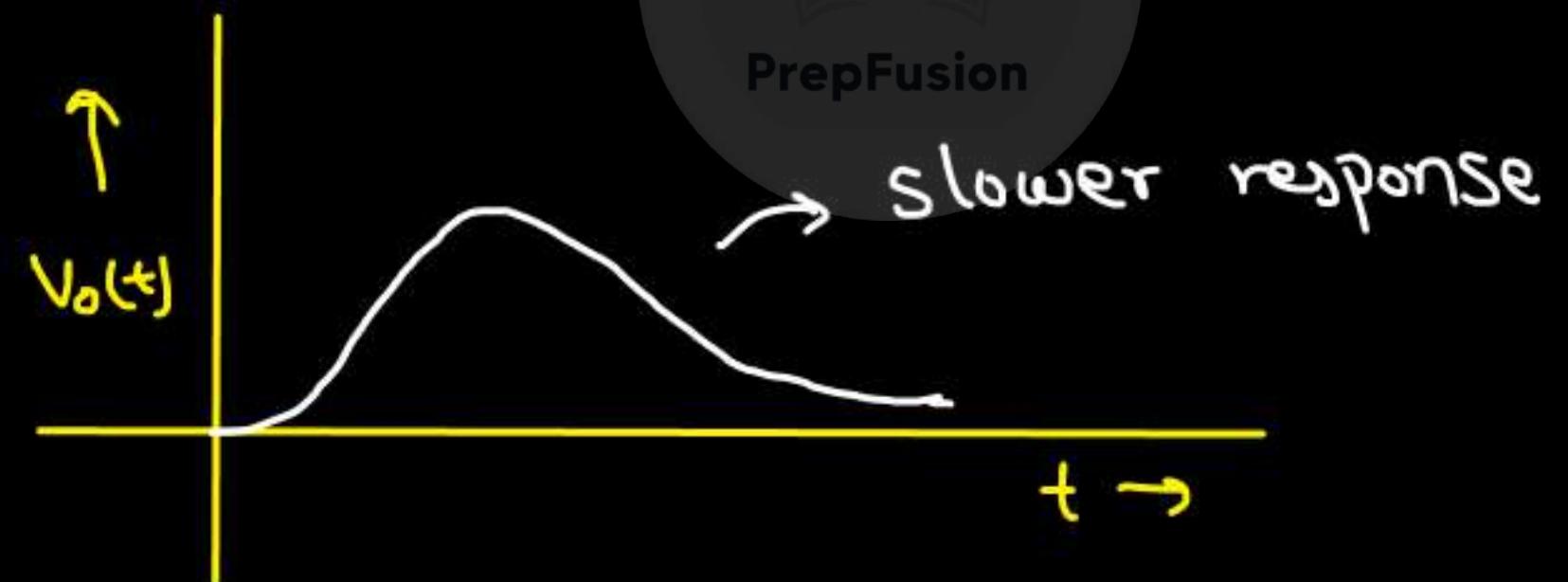Considering both initial and final value to be zero.



N.B. Here there are absolutely no oscillation but the response is slower.

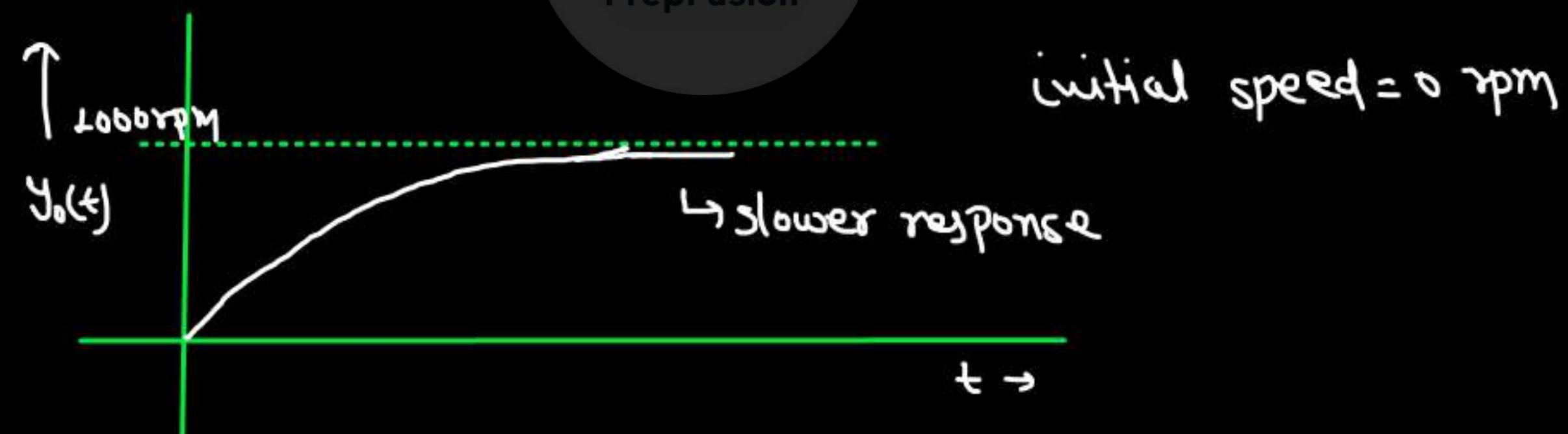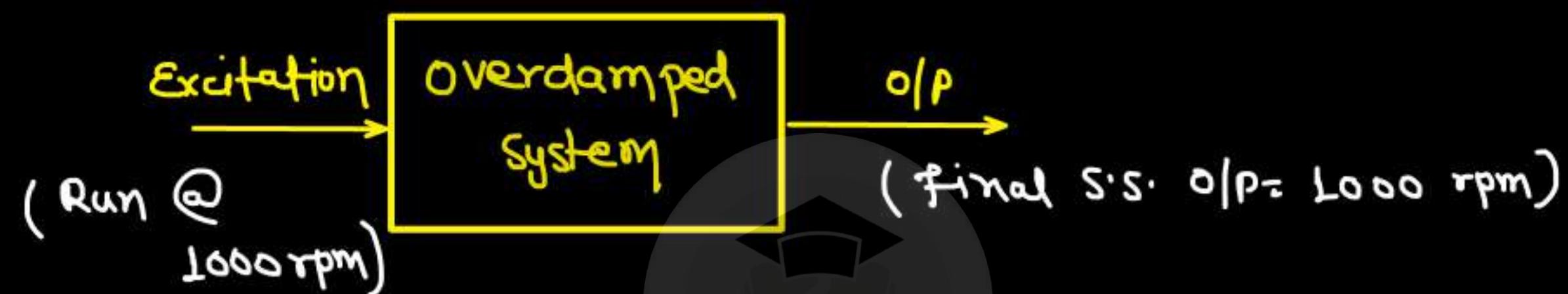Eg. → let's assume I given an excitation to my motor to run @ 1000 rpm and the system is over-damped. Then How should the o/p look like?



Speed of response:-

critical damped > Under damped > Over damped

↓ ↓ ↓

→ fastest	→ faster than overdamped	→ slowest
→ no oscillation	→ oscillation ✓	→ no oscillation
→ very tough to design		






(d) Both roots completely imaginary and conjugate :-

$$s_{P_1} = -j\beta$$

$$s_{P_2} = j\beta$$



considering initial value to be zero.

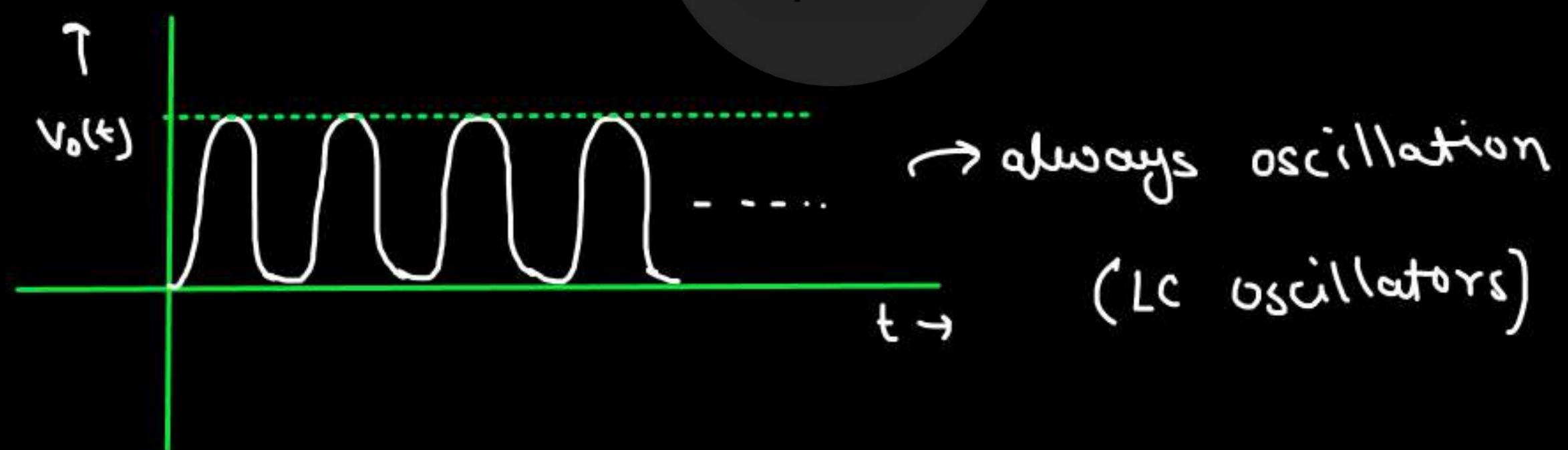


* Source free Series RLC Ckt:-

let's assume;

inductor is having initial current of I_0 .

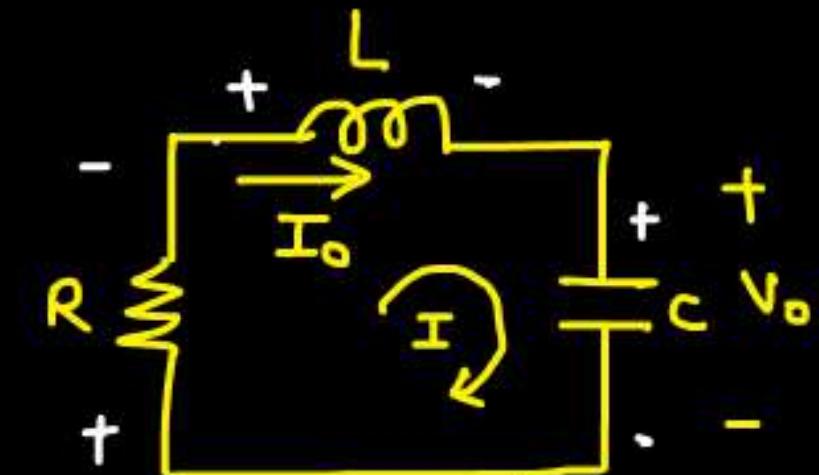capacitor is having initial voltage of V_0 .



let's write the expression for current

apply KVL

$$I(t)R + L \frac{dI(t)}{dt} + V_0 + \frac{1}{C} \int I(t) \cdot dt = 0$$

$$R \frac{dI(t)}{dt} + L \frac{d^2 I(t)}{dt^2} + \frac{I(t)}{C} = 0$$

$$\frac{d^2 I(t)}{dt^2} + \frac{R}{L} \frac{dI(t)}{dt} + \frac{1}{LC} I(t) = 0$$

$$\underbrace{\left[D^2 + \frac{R}{L}D + \frac{1}{LC} \right]}_{f(D)} I(t) = 0$$

$$\Rightarrow D^2 + \frac{R}{L}D + \frac{1}{LC} = 0$$

$$D = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2} = \frac{-\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}}{2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} ; \quad \omega_0 = \frac{1}{\sqrt{LC}}$$





Remember

$$\text{Roots} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} ; \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$; [s_{p_1} = -\alpha + \sqrt{\alpha^2 - \omega_0^2}]$$

$$s_{p_2} = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Case - I →

Underdamped system: - [poles must be complex conjugate]

$$(\alpha < \omega_0)$$

$$\text{Roots} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

$$\left\{ \begin{array}{l} \text{PrepFusion} \\ \omega_0 > \alpha \end{array} \right\}$$

$$\text{Roots} = -\alpha \pm j\omega_d ; \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

for a differential eqn, your roots are $-\alpha - j\omega_d$ and $-\alpha + j\omega_d$.

Soln of differential eqn $y(t) = e^{-\alpha t} [c_1 \cos \omega_d t + c_2 \sin \omega_d t]$

So, for a underdamped response.

$$\textcircled{1} \quad \alpha < \omega_0$$

$$\frac{R}{2L} < \frac{1}{\sqrt{LC}}$$

$$\textcircled{2} \quad Y(t) = e^{-\alpha t} [C_1 \cos \omega_0 t + C_2 \sin \omega_0 t]$$

Now for $I(t)$

$$I(t) = e^{-\alpha t} [C_1 \cos \omega_0 t + C_2 \sin \omega_0 t]$$


in the given ckt ; $I(0^+) = I_0$

$$\rightarrow I(0^+) = C_1 = I_0 \quad \text{--- } \textcircled{1}$$

⇒ similarly , by the other cond'n you can find the value of C_2 as well .
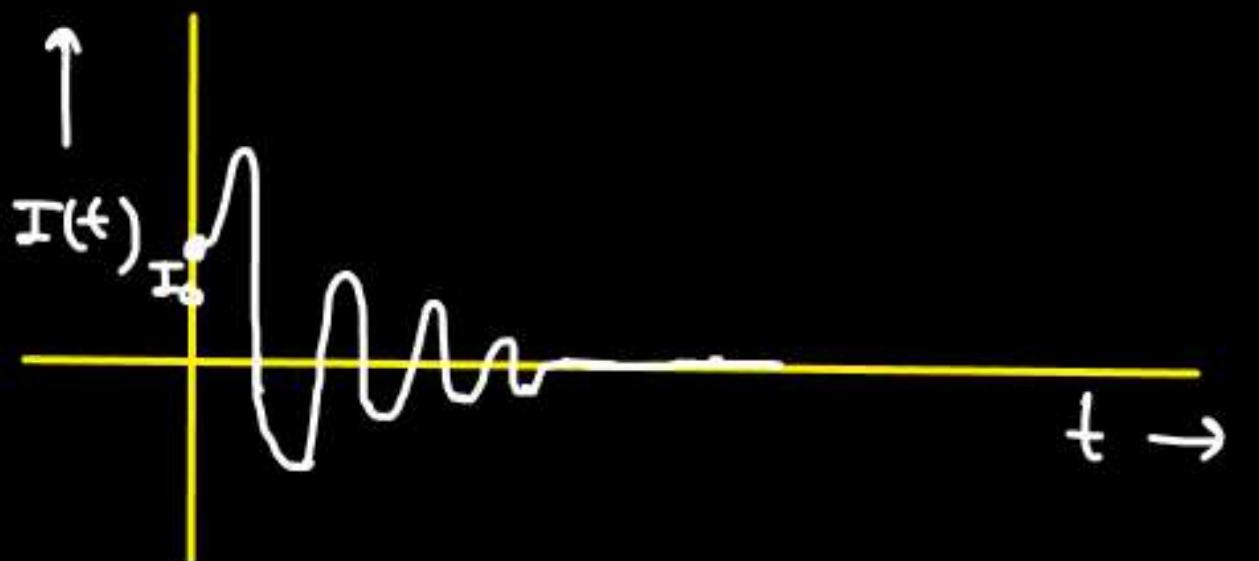
$$I(\infty) = 0 \quad \text{--- } \textcircled{2}$$





since, all the expression will follow 2nd order eqⁿ only.

Voltage across the capacitor $V_c(t) = e^{-\alpha t} [C_1 \cos \omega t + C_2 \sin \omega t]$

at $t=0^+$ $V_c(0^+) = V_0$ Preplusion

$$C_1 = V_0$$

You can find C_2 in similar way

$$V_c(\infty) = 0$$







$$\hookrightarrow V_L(t) = e^{-\alpha t} [C_1 \cos \omega_d t + C_2 \sin \omega_d t]$$

$$@ t=0^+ \quad V_L(0^+) = - I_o R - V_0$$

$$C_1 = - I_o R - V_0$$

similarly you can find C_2

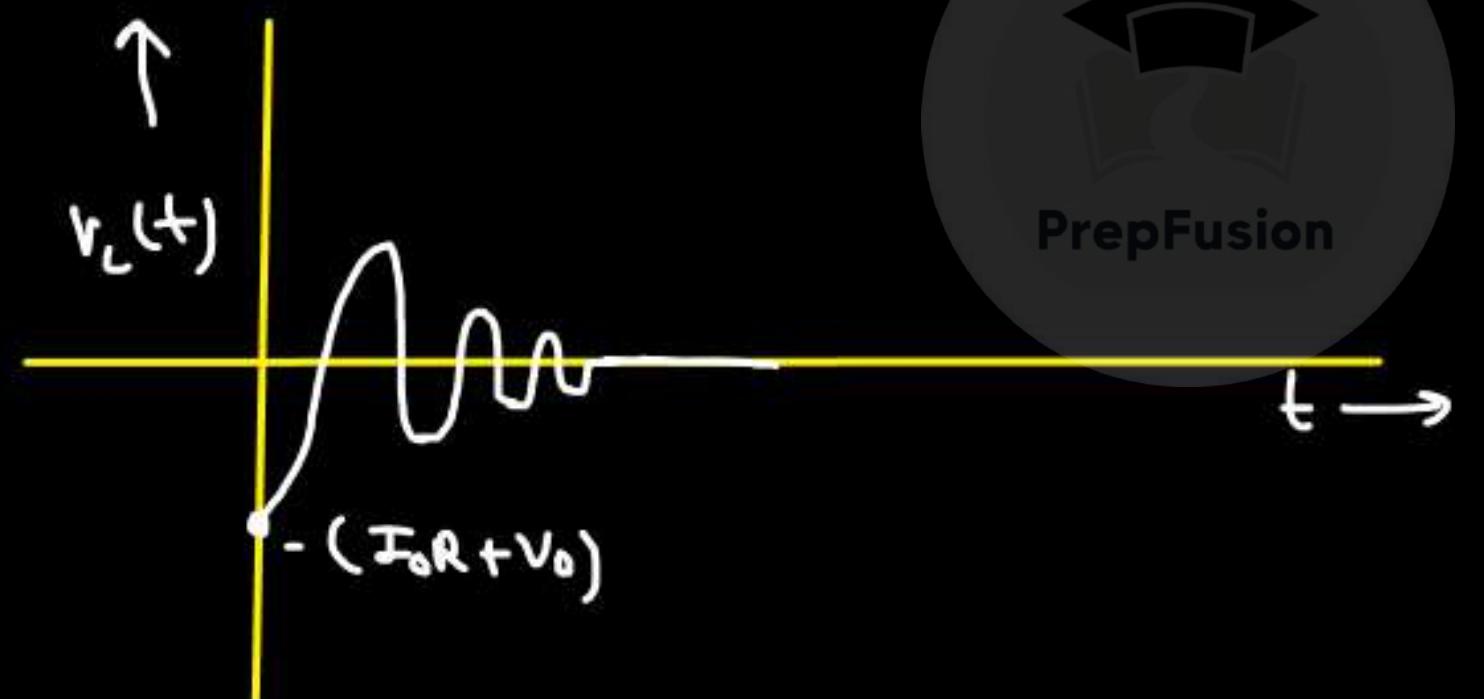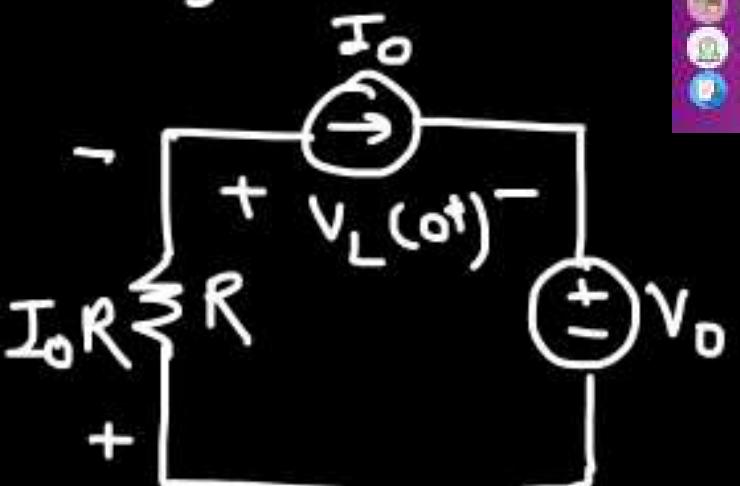



Case - 2 →

Critically damped [Both roots should equal]

$$(\alpha = \omega_0)$$

$$\text{roots} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

For critically damped ; roots = $-\alpha, -\alpha$

Solⁿ of differential equation = $[c_1 + c_2 t] e^{-\alpha t}$

For critical damped response :-

$$\alpha = \omega_0$$

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$


↳ $I(t)$:-

$$I(t) = [C_1 + C_2 t] e^{-\alpha t}$$

@ $I(0^+) = I_0 = C_1$

Similarly you can find C_2

$$I(\infty) = 0$$

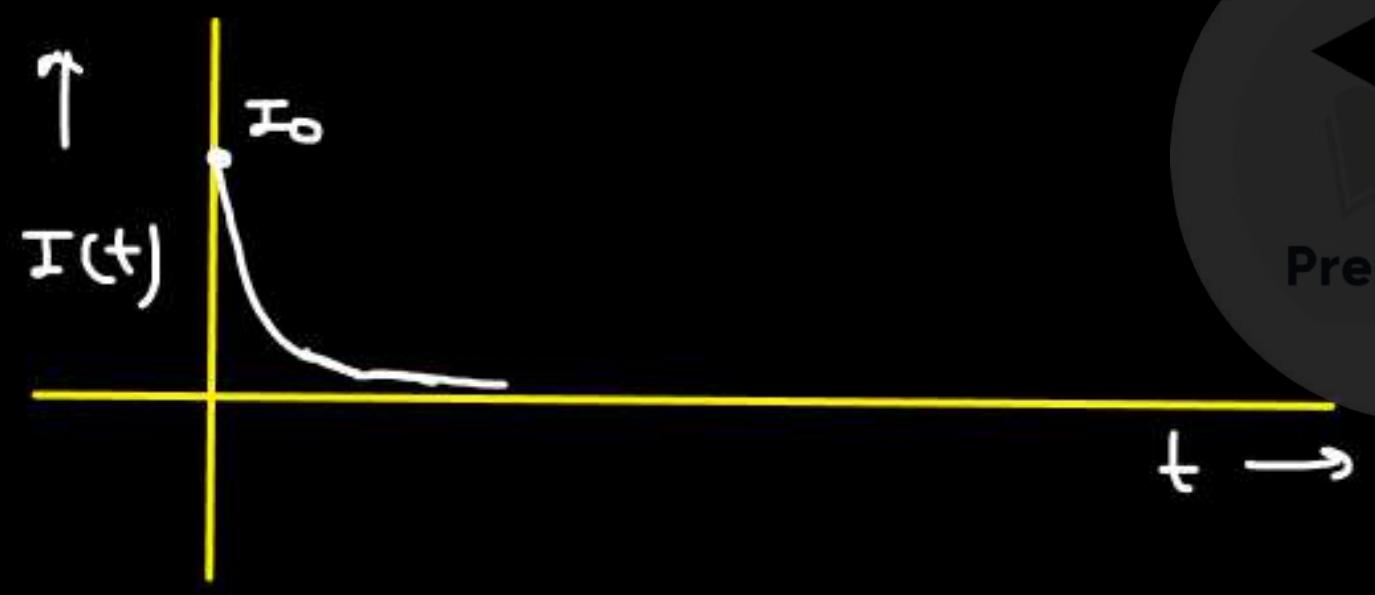

↳ $V_C(t) = [C_1 + C_2 t] e^{-\alpha t}$



$$V_C(0^+) = C_1 = V_0$$

$$V_C(\infty) = 0$$

↳ $V_R(t) = [C_1 + C_2 t] e^{-\alpha t}$

$$V_R(0^+) = C_1 = -I_0 R$$

$$V_R(\infty) = 0$$

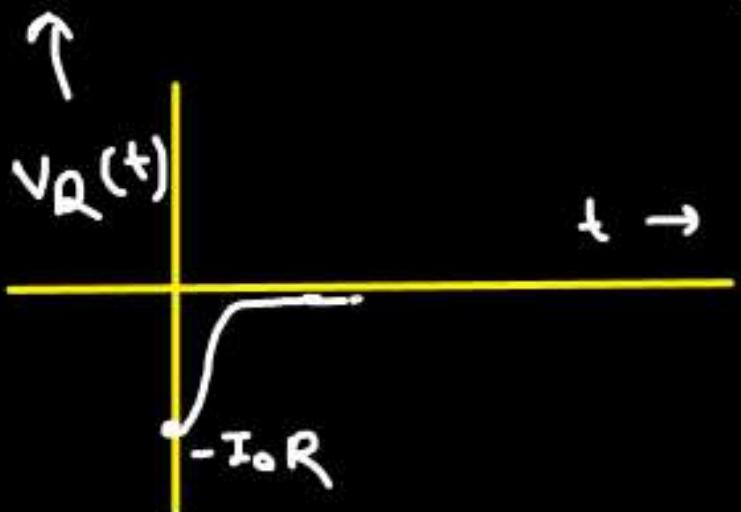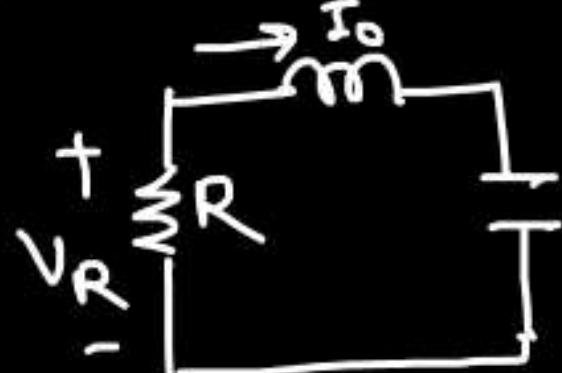

Case -3:-

Overdamped [Both roots will be different]
 $(\alpha > \omega_0)$ (Real)

$$\text{roots} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$s_{p_1} = -\alpha + \underbrace{\sqrt{\alpha^2 - \omega_0^2}}_{= \lambda_1} \\ (\text{negative})$$

$$s_{p_2} = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \\ = \lambda_2 \\ (\text{negative})$$

Solⁿ of differential eqⁿ = $c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t}$
 $y(t)$

For overdamped response ; $\alpha > \omega_0$

$$\frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

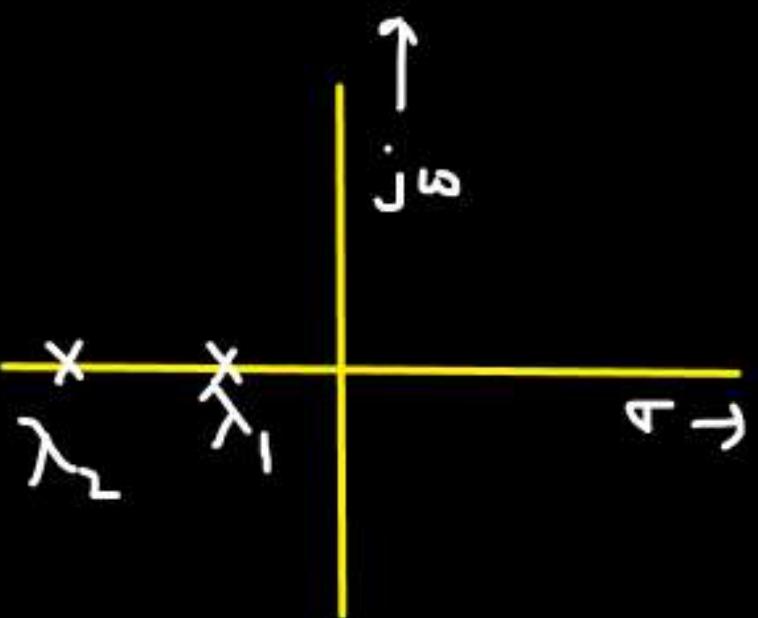


$I(t)$:-

$$I(t) = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t}$$


$$I(0^+) = c_1 + c_2 = I_0$$

$$I(\infty) = 0$$

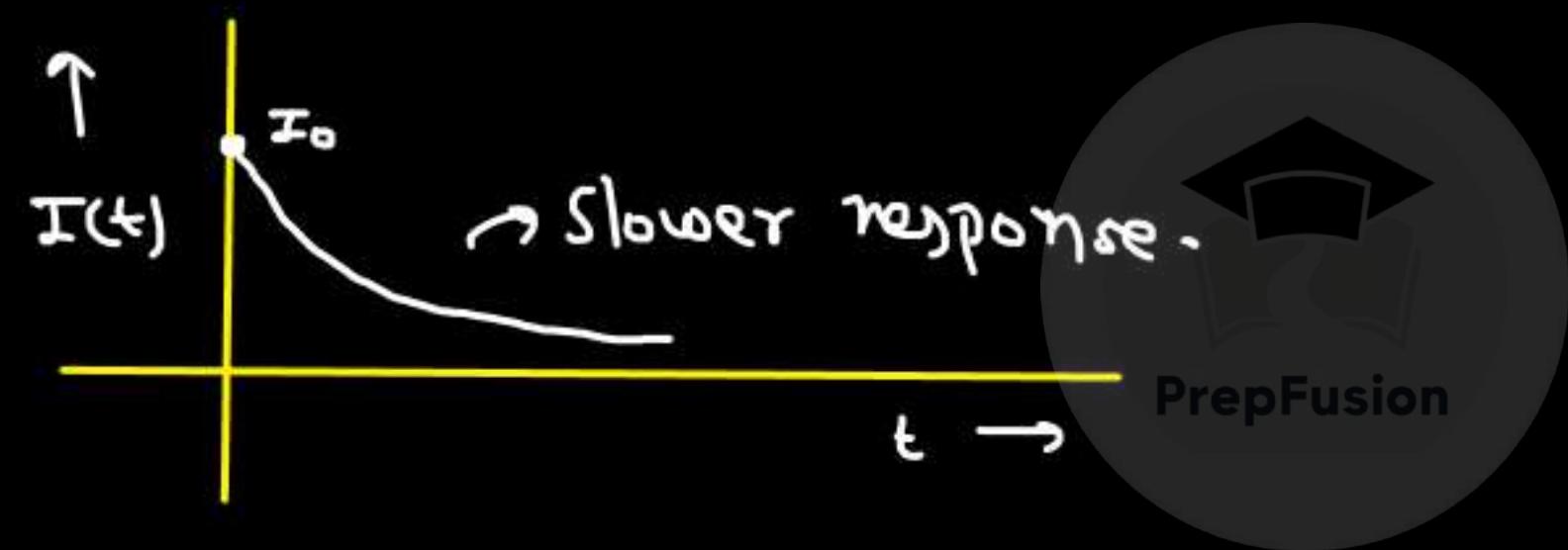

Similarly for all other expressions.

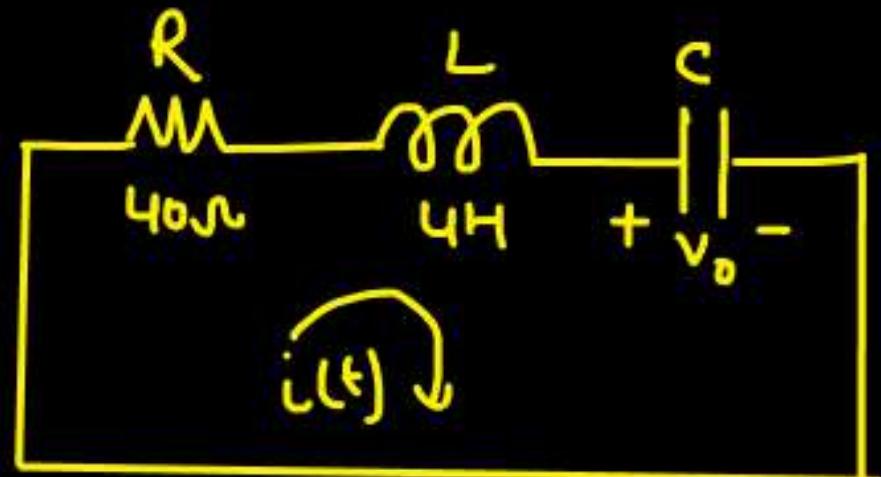Q. find the value of capacitor C to have critically damped response.



→ For critically damped

$$\alpha = \omega_0$$

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$

$$\frac{40}{8} = \frac{1}{\sqrt{4C}}$$

$$C = 10 \text{ mF}$$




* Source - Free parallel RLC ckt :-

Let's assume,

inductor is having initial current of I_0 .

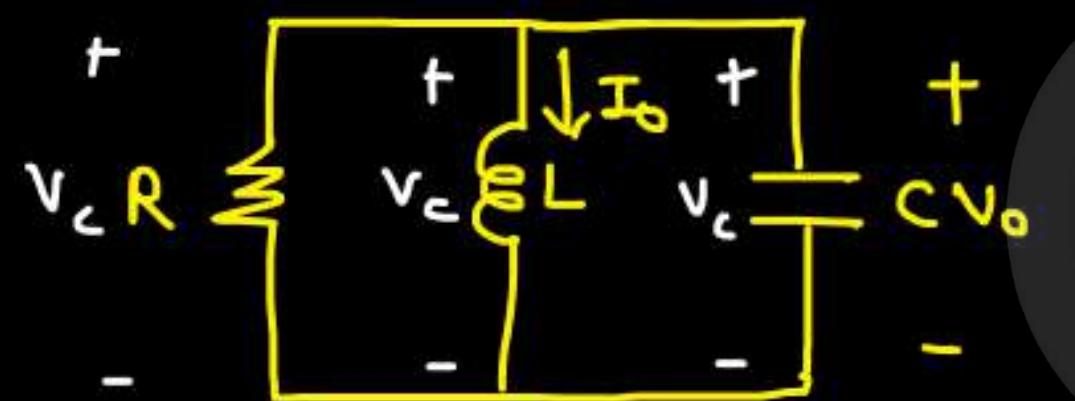capacitor is having initial voltage of V_0 .



Applying KCL

$$C \frac{dV_c}{dt} + I_0 + \frac{1}{L} \int_{-\infty}^t V_c dt + \frac{V_c}{R} = 0$$

Differentiate \rightarrow

$$C \frac{d^2 V_c(t)}{dt^2} + \frac{V_c(t)}{L} + \frac{1}{R} \frac{dV_c(t)}{dt} = 0$$

$$\frac{d^2 V_c(t)}{dt^2} + \frac{1}{RC} \frac{dV_c(t)}{dt} + \frac{V_c(t)}{LC} = 0$$

$$\left[D^2 + \frac{1}{RC} D + \frac{1}{LC} \right] V_c(t) = 0$$

$f(\omega)$

$$D^2 + \frac{1}{RC} D + \frac{1}{LC} = 0$$

$$D = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$$



$$\text{roots} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} ; \quad \omega_0 = \frac{1}{\sqrt{LC}}$$



$$\text{Roots} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

* Underdamped response:-

$$\alpha < \omega_0 \Rightarrow \frac{1}{2RC} < \frac{1}{\sqrt{LC}}$$

* Critically damped response:-

$$\alpha = \omega_0 \Rightarrow \frac{1}{2RC} = \frac{1}{\sqrt{LC}}$$

* Overdamped response:-

$$\alpha > \omega_0 \Rightarrow \frac{1}{2RC} > \frac{1}{\sqrt{LC}}$$

$$Y(t) = e^{-\alpha t} [c_1 \cos \omega_0 t + c_2 \sin \omega_0 t]$$

$$Y(t) = [c_1 + c_2 t] e^{-\alpha t}$$

$$Y(t) = c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t}$$


$$\left. \begin{array}{l} \lambda_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ \lambda_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{array} \right\} \rightarrow \begin{array}{l} \text{negative} \\ \text{values} \end{array}$$

Sinusoidal Steady State analysis:-

* Draw waveforms:-


$$(a) V_i(t) = V_m \sin \omega t$$
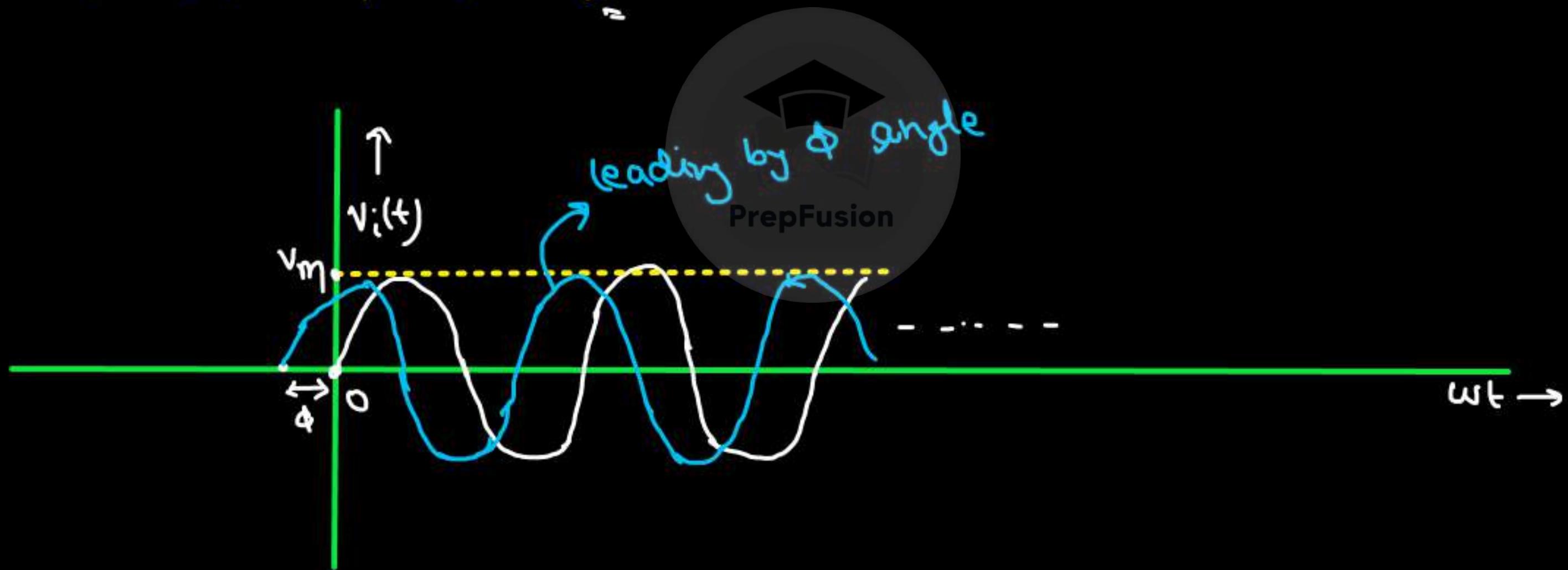
$$(b) V_i(t) = V_m \sin(\omega t + \phi)$$






Q. Find $H(j\omega)$.

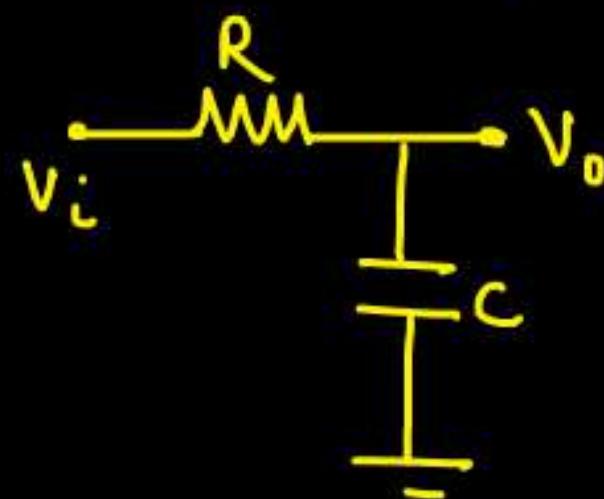

\Rightarrow

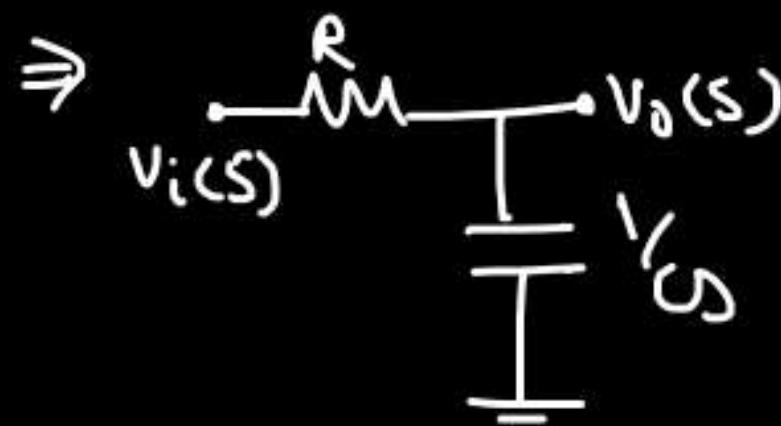

\Rightarrow

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{RCs + 1}$$

$$H(s) = \frac{1}{1 + RCs}$$



Impulse response of a system =


$s = j\omega$
PrepFusion

$$H(j\omega) = \frac{1}{j\omega RC + 1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2 R^2 C^2 + 1}}$$




$$\angle H(j\omega) = -\tan^{-1}(\omega RC)$$

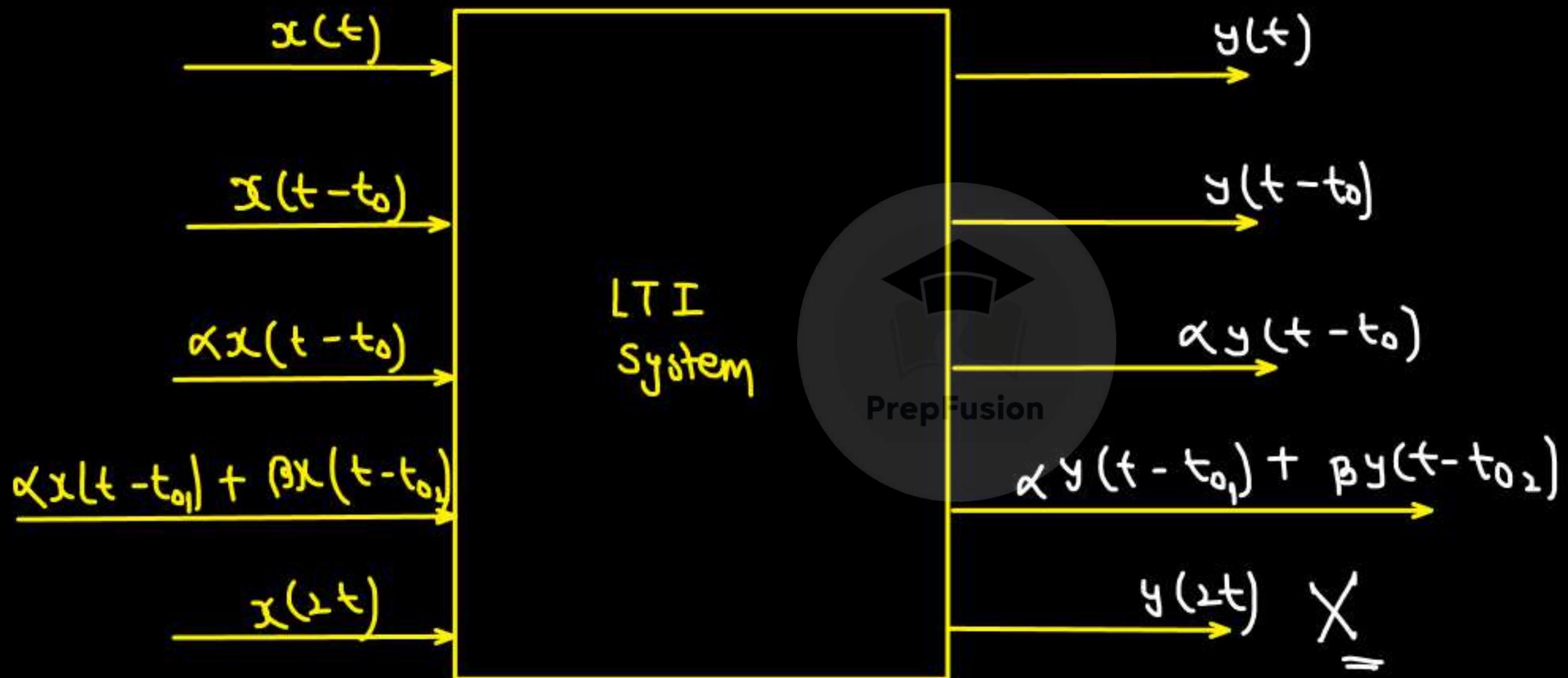For a LTI (Linear Time Invariant) System :-



N.B. - Scaling in time domain will not result similarly in the o/p.

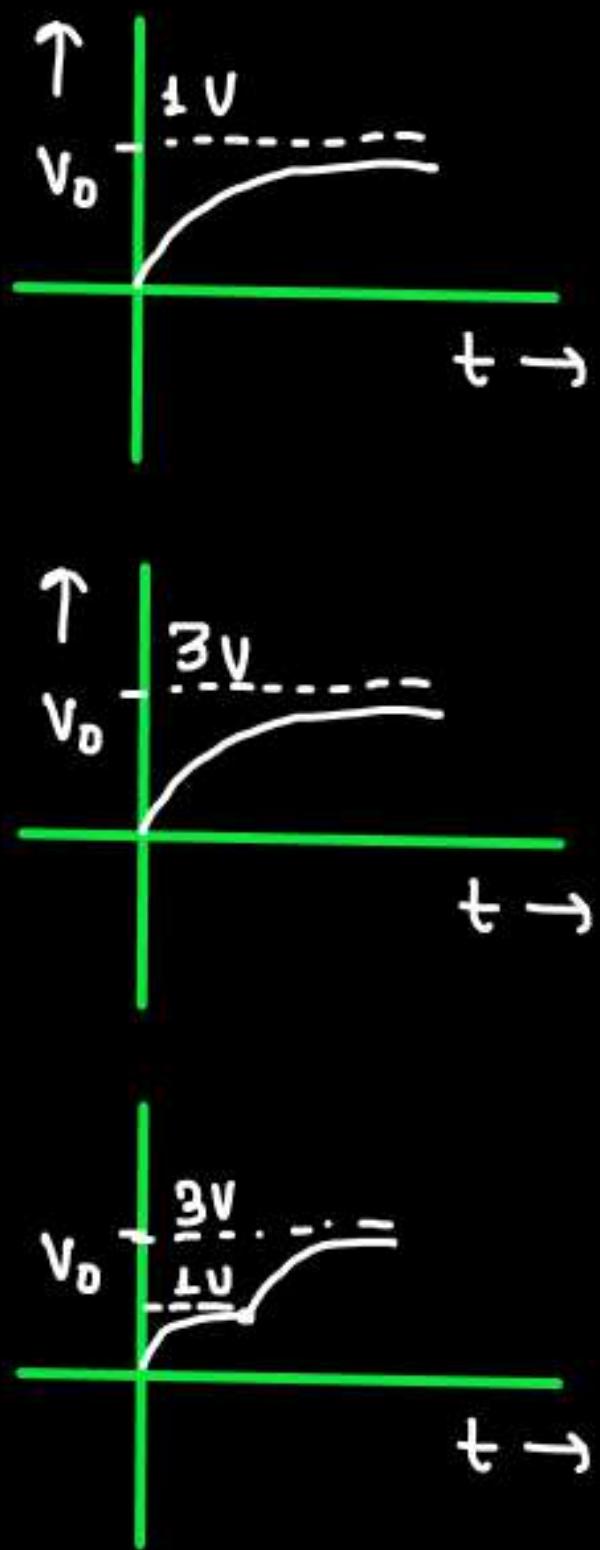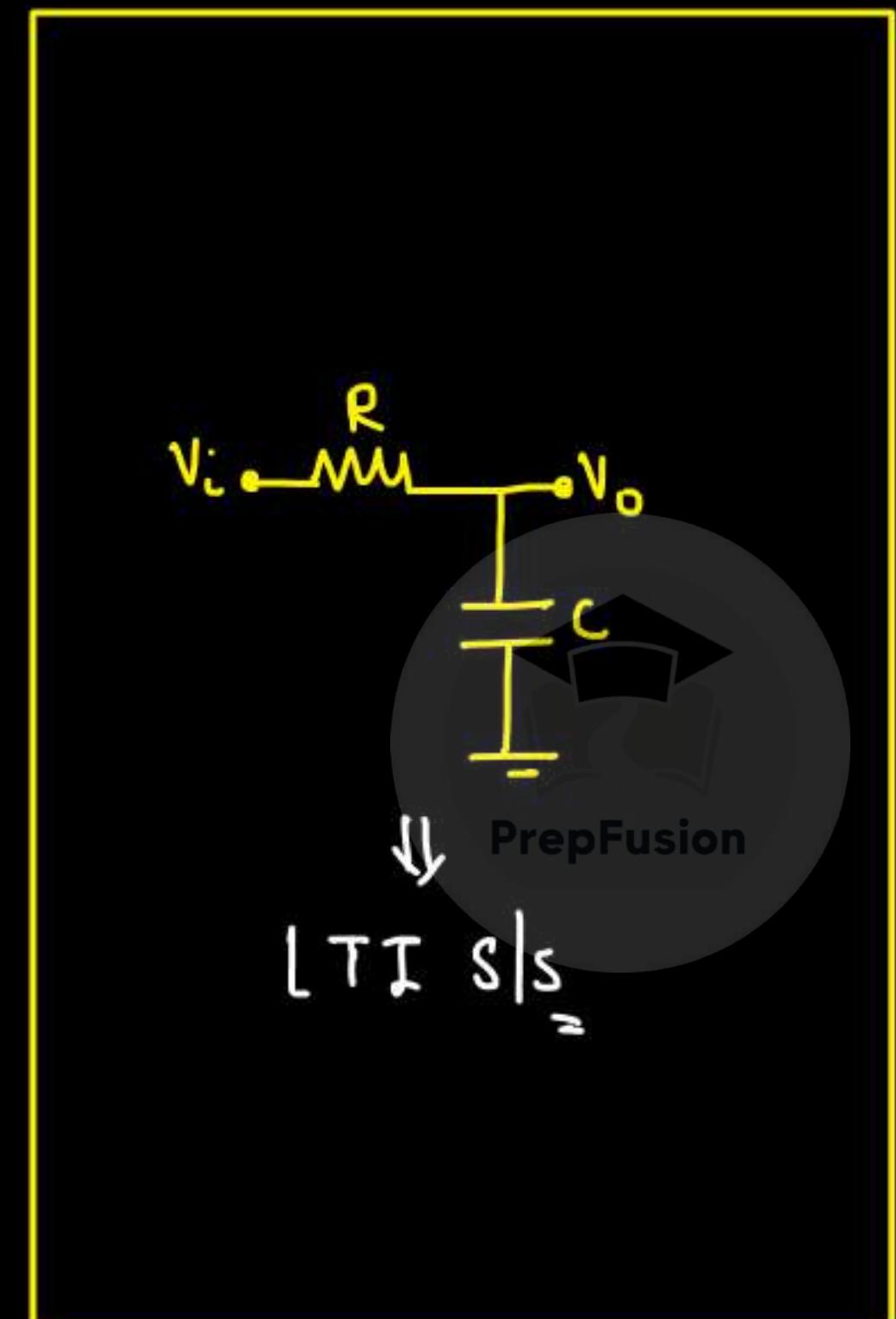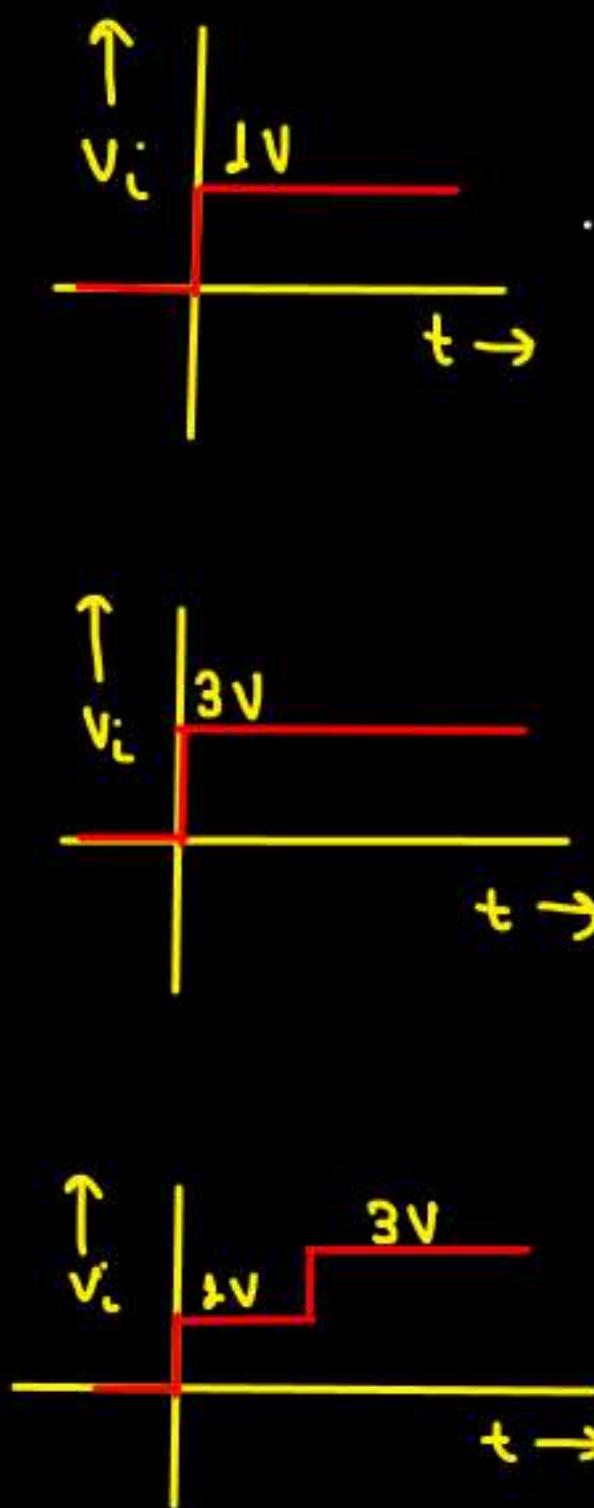
- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES





Sinusoid steady state response :-
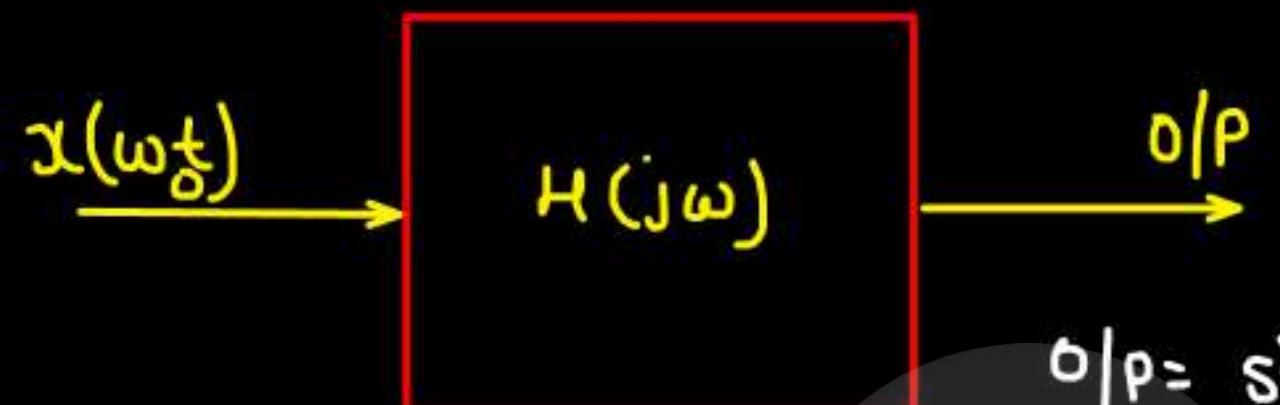
$$\begin{aligned}x(\omega_0 t) &= A \sin(\omega_0 t) \\&= B \cos(\omega_0 t) \\&= C e^{j\omega_0 t}\end{aligned}$$




O/P = steady state + Transient response
response

Here, I will be only talking about steady state response.

$$(O/P)_{\text{steady o/p}} = |H(j\omega_0)| \times [e^{j\omega_0 t + \angle H(j\omega_0)}]$$

Q.

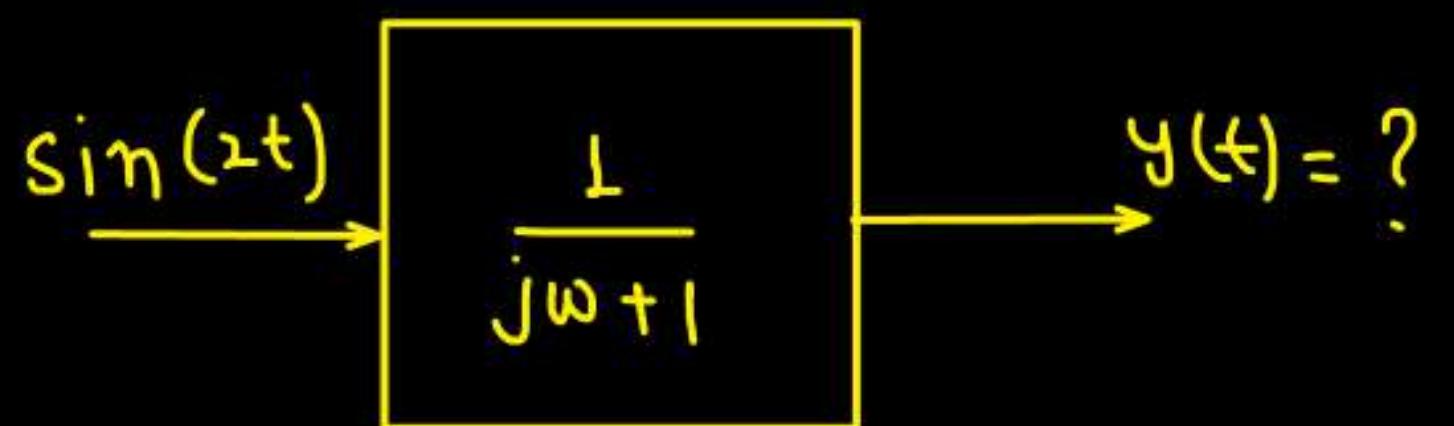

Find $y(t)$ @ steady state



$$H(j\omega) = \frac{1}{j\omega + 1}$$

$$|H(j\omega)| = \frac{1}{\sqrt{\omega^2 + 1}}$$

$$\angle H(j\omega) = -\tan^{-1}(\omega)$$



$$\Rightarrow H(j\omega) = \frac{1}{\sqrt{\omega^2 + 1}} e^{-j\tan^{-1}(\omega)}$$

$$i/p = \sin(2t)$$

$$\omega_0 = 2$$

$$H(j2) = \frac{1}{\sqrt{5}} e^{-j\tan^{-1}(2)} =$$

- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES




$$y(t) = \frac{1}{\sqrt{5}} \sin(2t - \tan^{-1} 2) \Rightarrow \text{steady state O/P}$$





Q.

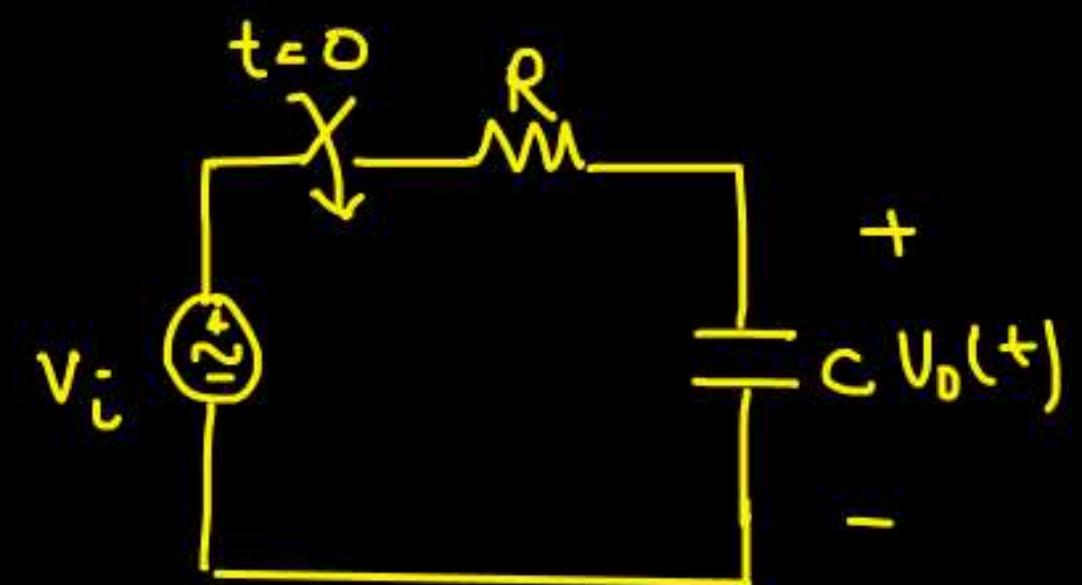

$$V_i(t) = 5 \sin(t) ; RC = 1 \text{ sec}$$

Find $V_o(t)$.

$$\rightarrow V_i(t) = 5 \sin(t)$$

$$V_o(s) = \frac{1}{1 + RC} V_i(s)$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega}$$

$$V_i(j\omega) \xrightarrow{\frac{1}{1 + j\omega}} V_o(j\omega)$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES



$$V_o(j\omega) = \underbrace{\frac{1}{1+j\omega}}_{H(\omega)} V_i(j\omega) \Rightarrow \text{freq. domain}$$

$$V_i(t) = 5 \sin t$$

$$\text{Here } \omega_0 = 1$$

$$H(\omega) = \frac{1}{1+j}$$

$$\Rightarrow H(\omega) = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_o(t) = \frac{5}{\sqrt{2}} \sin(t - 45^\circ)$$



X

@ t=0; cap. will have zero voltage. $\Rightarrow V_o(0^+) = 0V$

now, our

$$V_o(t) = \frac{5}{\sqrt{2}} \sin(t - 45^\circ)$$

$$\text{@ } t=0^+ \quad V_o(0^+) = \frac{5}{\sqrt{2}} \sin(-45^\circ) = -\frac{5}{2}V \\ = -2.5V$$

so $V_o(t) = \frac{5}{\sqrt{2}} \sin(t - 45^\circ)$ is not your final o/p but steady state response

$$[V_o(t)]_{S.S.} = \frac{5}{\sqrt{2}} \sin(t - 45^\circ)$$

$$[V_o(t)]_{t_r} = ?$$

From S.S. response, @ $t=0$ you are getting $-2.5V$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

But conceptually $V_o(0^+)$ should be zero voltage
 \Downarrow

So, there has to be some transient response


that kills out $-2.5V$

$$[V_o(t)]_{tr} = 2.5e^{-t/\tau}; \tau = RC = 1\text{sec.}$$


$$V_o(t) = \left[\frac{5}{\sqrt{2}} \sin(t - 45^\circ) + 2.5e^{-t/\tau} \right] u(t)$$

\Downarrow

S.S o/p Transient o/p

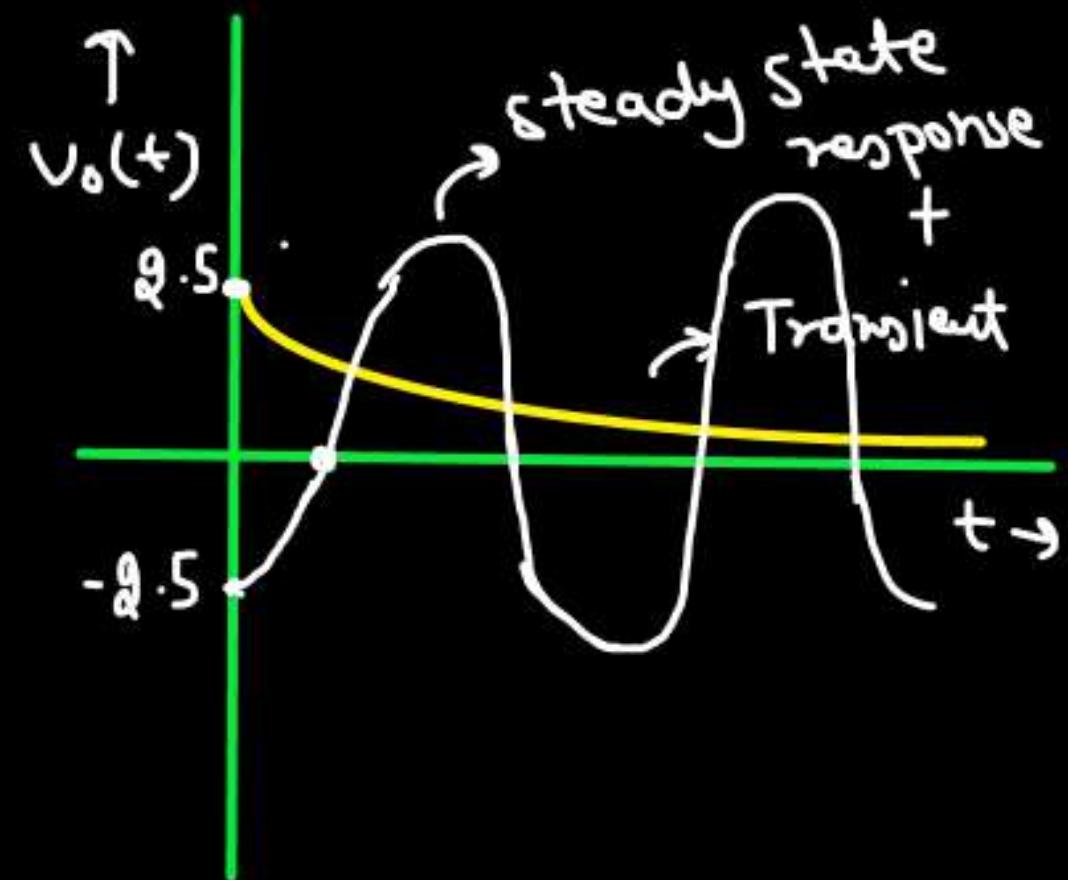

Q.

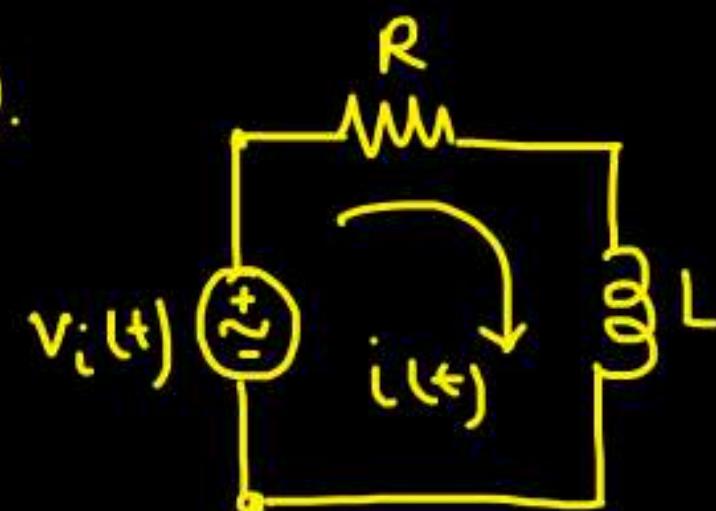

$$V_i(t) = [5 \sin(\omega t)] v(t)$$

$$R = 1\Omega, L = 1H$$

Find $i(t)$

$$\rightarrow V_i(s) = (R + Ls) I(s)$$

$$\frac{I(s)}{V_i(s)} = H(s) = \frac{1}{R + Ls}$$

$$H(j\omega) = \frac{1}{R + j\omega L}$$

$$V_i(j\omega) \xrightarrow{\frac{1}{R + j\omega L}} I(j\omega)$$

$$= \frac{1}{1 + j\omega}$$



$$H(j\omega) = \frac{1}{1+j\omega}$$

$$V_i(t) = 5 \sin t$$

$$\omega_0 = 1 \text{ rad/sec.}$$

$$H(j1) = \frac{1}{1+j}$$

$$= \frac{1}{\sqrt{2}} \angle -45^\circ$$

PrepFusion

$$[I(t)]_{ss} = \frac{5}{\sqrt{2}} \sin(t - 45^\circ)$$

At $t=0^+$ $[I(t)]_{ss} = -\frac{5}{\sqrt{2}} = -2.5 \text{ Amp.}$

But conceptually $I(0^+) = 0 \text{ Amp.}$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES


AIR 27 (ECE)
AIR 45 (IN)

$$[i(t)]_{tr} = 2 \cdot 5 e^{-t/\tau} u(t) \quad \tau = L/R \approx 1.5 \text{ sec.}$$

$$i(t) = \left[\frac{5}{\sqrt{2}} \sin(t - 45^\circ) + 2 \cdot 5 e^{-t/\tau} \right] u(t)$$



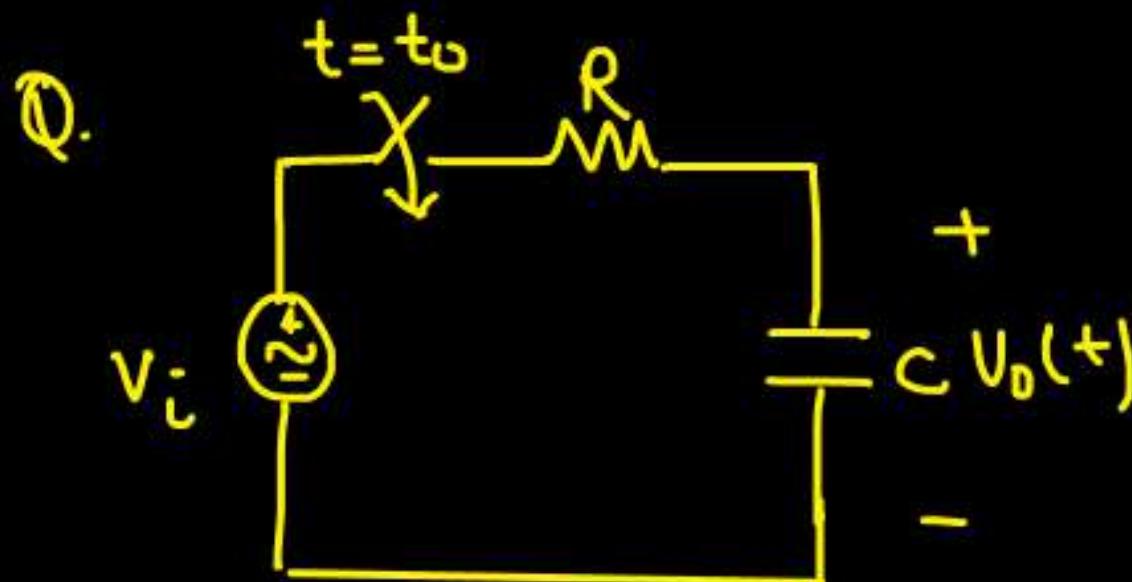YouTube -PrepFusion
(CLICK HERE FOR FULL
PLAYLIST)



$$V_i(t) = 5 \sin(t)$$

$$RC = 1 \text{ sec}$$

Find time t_0 such that $V_o(t)$ doesn't have any transient component.

$$\rightarrow V_o(j\omega) = \frac{1}{1 + j\omega RC} V_i(j\omega)$$

$$\omega_0 = 1, \quad RC = 1 \text{ sec.}$$



$$V_o(t) = \frac{5}{\sqrt{2}} \sin(t - 45^\circ) \rightarrow \text{steady state}$$




when you turn on the switch, Cap. will want zero voltage across it

$$V_o(t_0^-) = V_o(t_0^+) = 0 \text{ V}$$

$$\frac{5}{\sqrt{2}} \sin (t_0 - 45^\circ) = 0 \text{ V}$$

$$t_0 = 45 \times \frac{\pi}{180}$$

$$t_0 = 0.78 \text{ sec.}$$

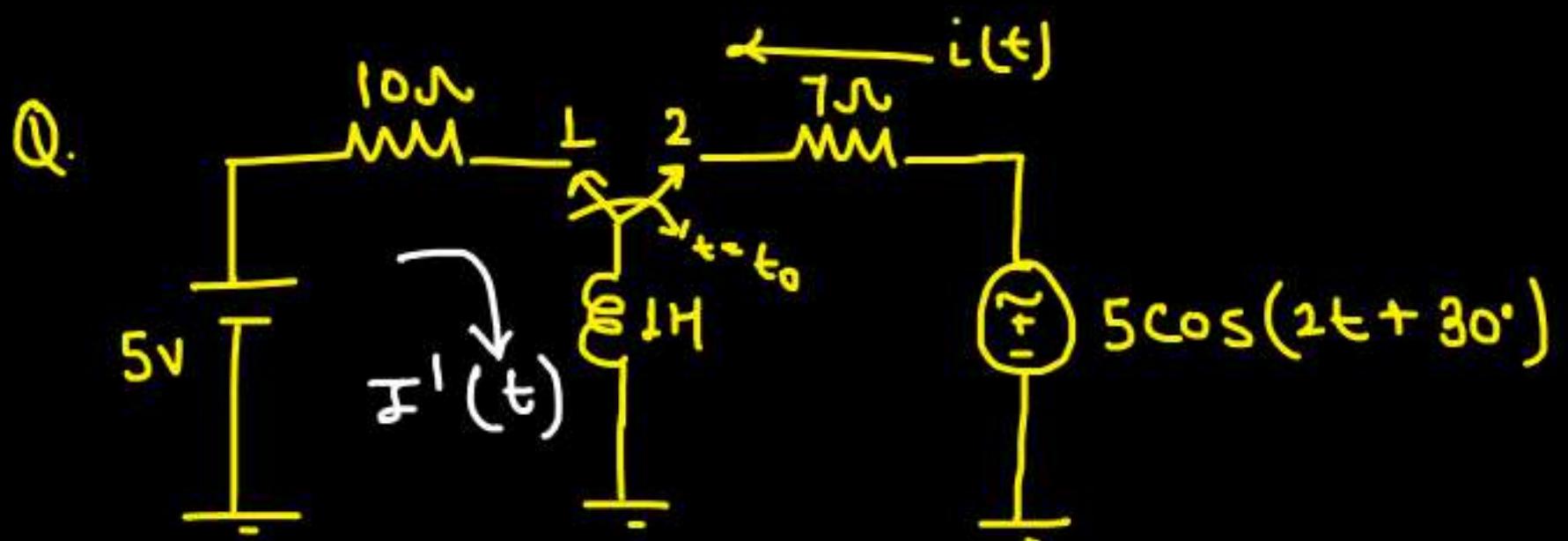


The switch is at position 1 for a long time.

It's moved to position 2 @ $t = t_0$.

Find the value of t_0 such that current $i(t)$ is transient-free.


→ for $t < t_0$

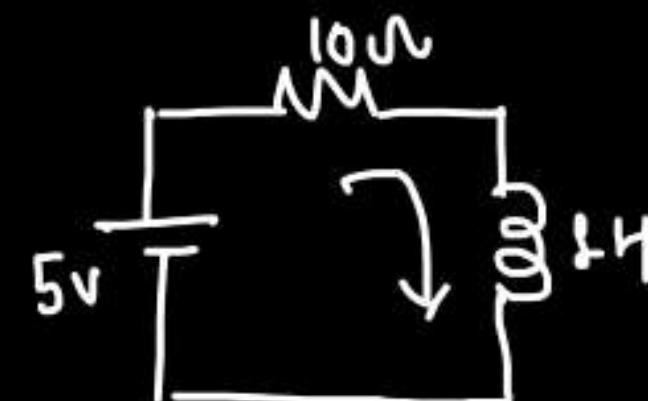

Steady state would have been reached.

$$i'(t_0^-) = \frac{5}{10} = 0.5 \text{ A}$$

For $t > t_0$

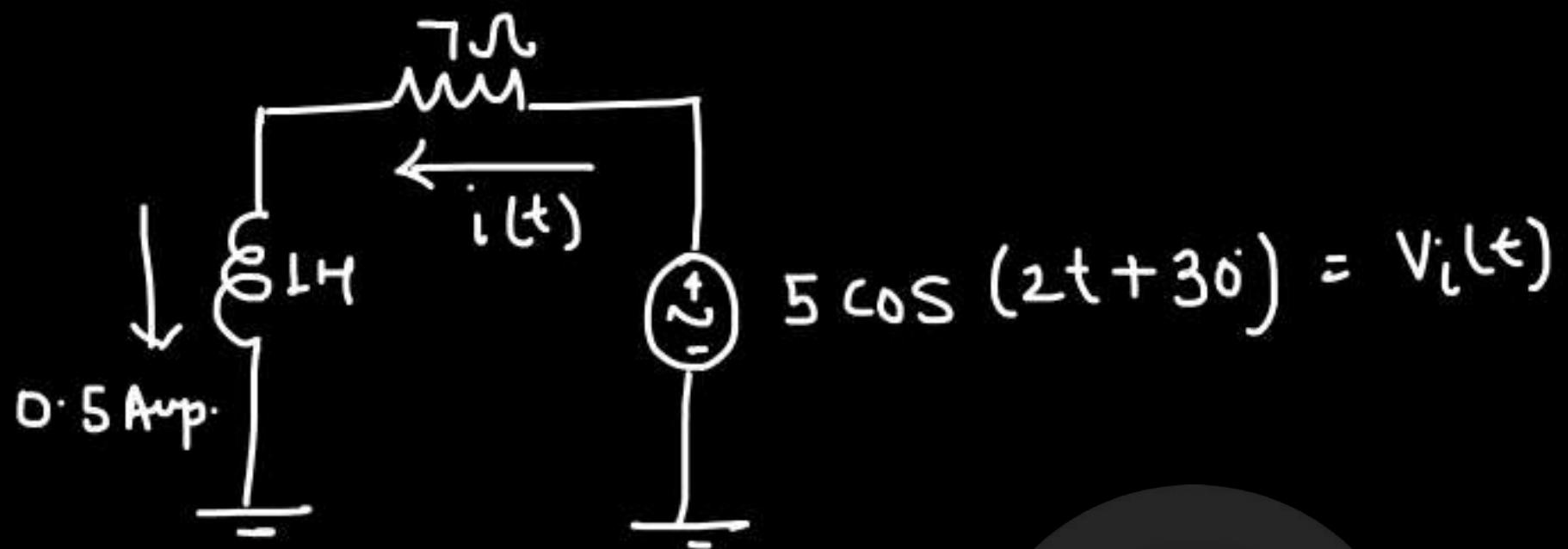

$$5 \cos(2t + 30^\circ) = V_i(t)$$

@ $t=t_0$; thus RL ckt sees an input: $5 \cos(2t + 30^\circ)$

$$[i(t)]_{S.S.} = ?$$

$$V_i(j\omega) = I(j\omega)[\tau + j\omega] \quad \{L=1H\}$$

$$I(j\omega) = \frac{V_i(j\omega)}{\tau + j\omega} \quad \omega_0 = 2 \text{ rad/sec}$$

$$i(t) = \frac{5}{\sqrt{53}} \cos \left[2t + 30^\circ - \tan^{-1}(2/\gamma) \right]$$

\Rightarrow steady state



To get a transient free response.


$$I(t_0) = 0.5 \text{ Amp} \quad \left\{ I(t_0^-) = 0.5 \text{ Amp} \right\}$$

$$\frac{5}{2\sqrt{53}} \cos \left[2t_0 + \frac{\pi}{6} - \tan^{-1} \left(\frac{2}{7} \right) \right] = 0.5$$

$$t_0 = 0.26 \text{ sec.}$$




Q.

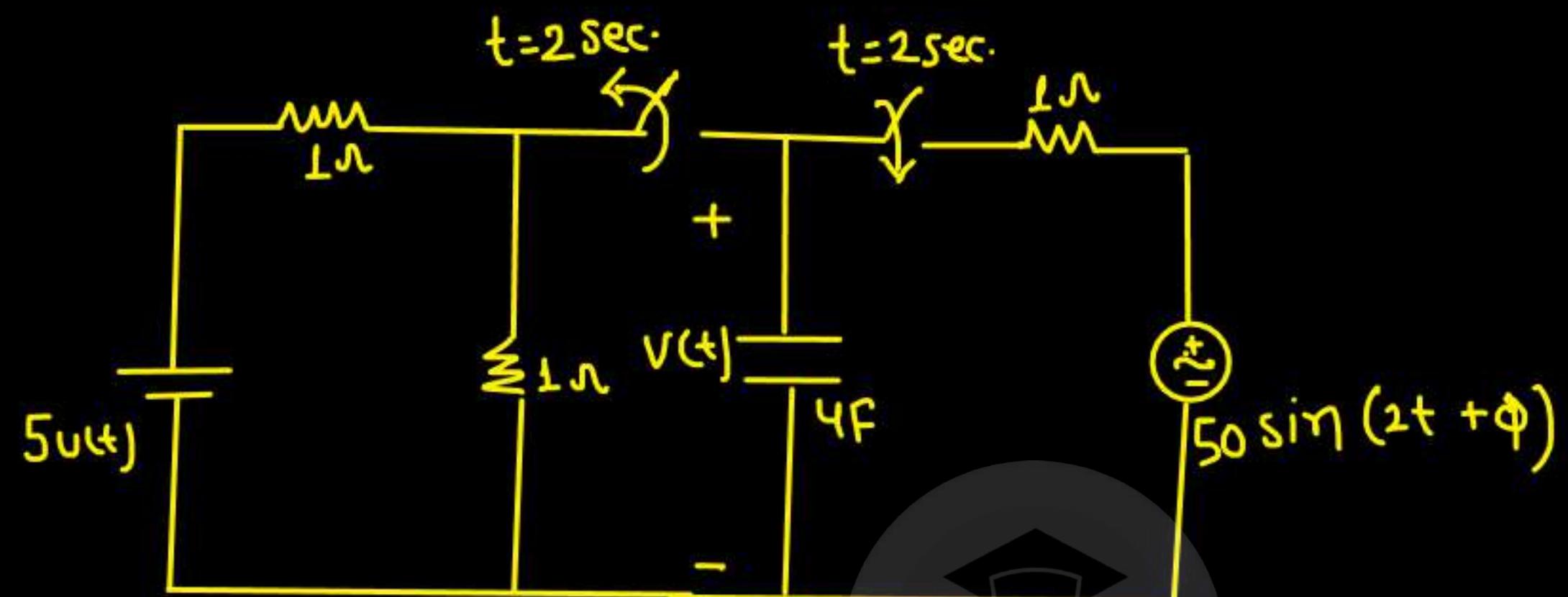

Find the value of ϕ such that $V(t)$ has a transient component of maximum amplitude of $0.5V$.

→ for $0 \leq t < 2 \text{ sec}$.

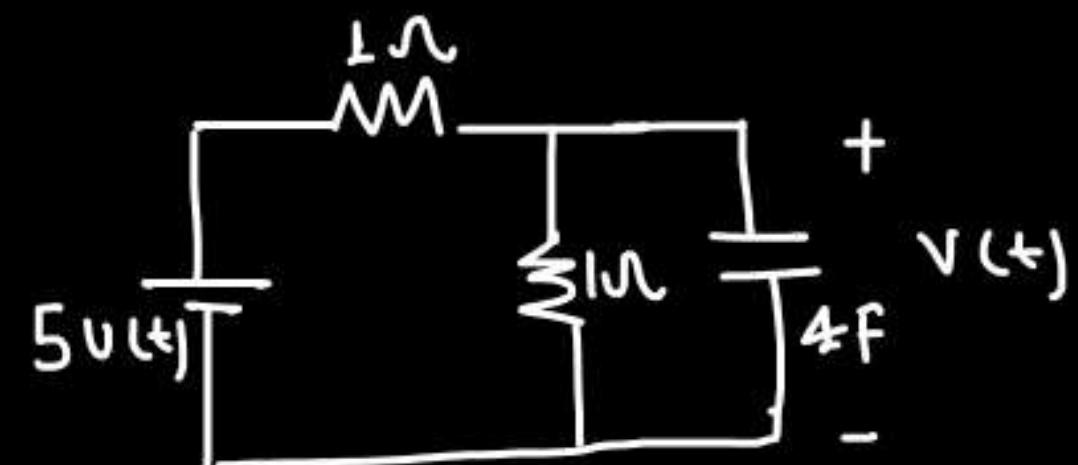

$$v(t) = Q \cdot 5 \left[1 - e^{-\frac{t}{\tau}} \right] u(t)$$


$$\tau = \frac{L}{C} = \frac{1}{2} \times 4 = 2 \text{ sec.}$$

$$v(2 \text{ sec.}) = Q \cdot 5 \left[1 - e^{-\frac{2}{2}} \right]$$

$$v(2 \text{ sec.}) = 1.58 \text{ V}$$

PrepFusion

for $t > 2 \text{ sec.}$

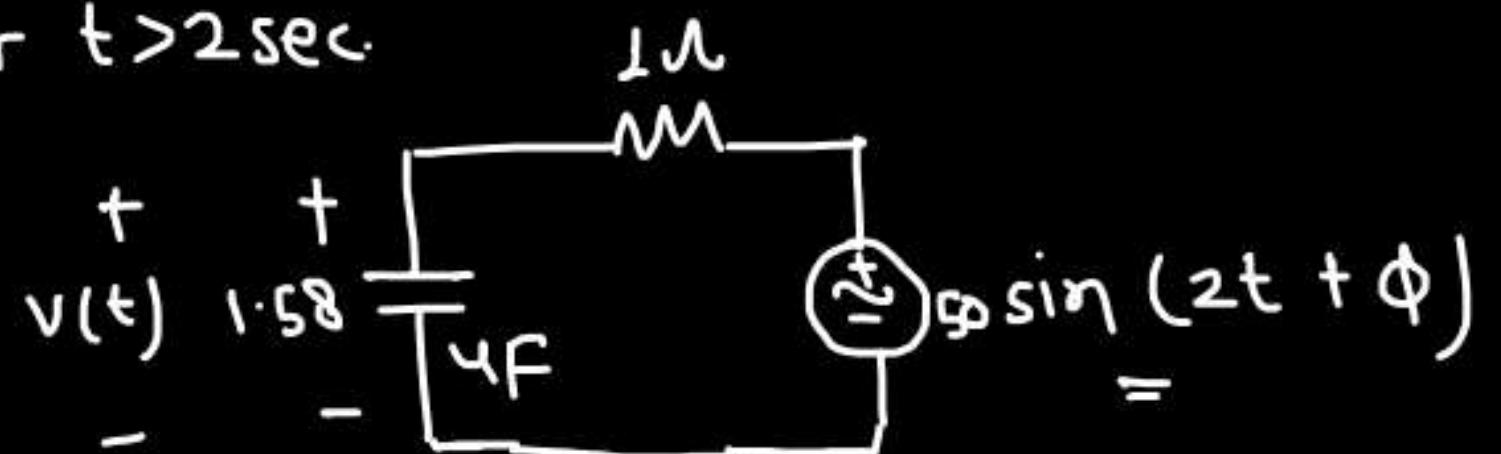

$$V(j\omega) = \frac{V_i(j\omega)}{1 + j\omega RC}$$

$$\omega_0 = 2, \quad RC = 4 \text{ sec.}$$

$$V(j\omega) = \frac{1}{1 + 8j} V_i(j\omega)$$

$$V(t) = \frac{1}{\sqrt{65}} \times 50 \sin \left(2t + \phi - \tan^{-1}(8) \right) u(t-2) \rightarrow \text{steady state response}$$

actual o/p required

$$v(t) = \left[\frac{50}{\sqrt{65}} \sin \left(2t + \phi - \tan^{-1}(8) \right) + 0.5 e^{-\frac{(t-2)}{\tau}} \right] u(t-2)$$

@ $t=2 \text{ sec}$, $V(2 \text{ sec}) = 1.58 \text{ V}$

$$\frac{50}{\sqrt{65}} \sin[\psi + \phi - \tan^{-1}(8)] + 0.5 = 1.58$$

$$\frac{50}{\sqrt{65}} \sin[\psi + \phi - \tan^{-1}(8)] = 1.08$$

$$\phi = -136.27^\circ$$

PrepFusion

ANALOG ELECTRONICS

CHAPTER 1 : DIODE CIRCUITS



↳ Basic Semiconductor Physics :-

Material
(Based on conductivity)

Conductor

↳ Allows flow of charge.

Eg → Copper, Brass, Steel, Gold etc.

PreFusion

* Semiconductor

↳ Moderately allows flow of charge

[conductivity can change by adding impurity]

Eg. → Si, Ge, GaAs

Insulator

↳ Hardly allows flow of charge


Eg. → Glass, air, wood

 **EE ELECTRONICS**
Basic Semiconductor
BASIC SEMICONDUCTOR PHYSICS 
LECTURE-1
Watch on  YouTube

AIR 27 (ECE)
AIR 45 (IN)

Semiconductor :-

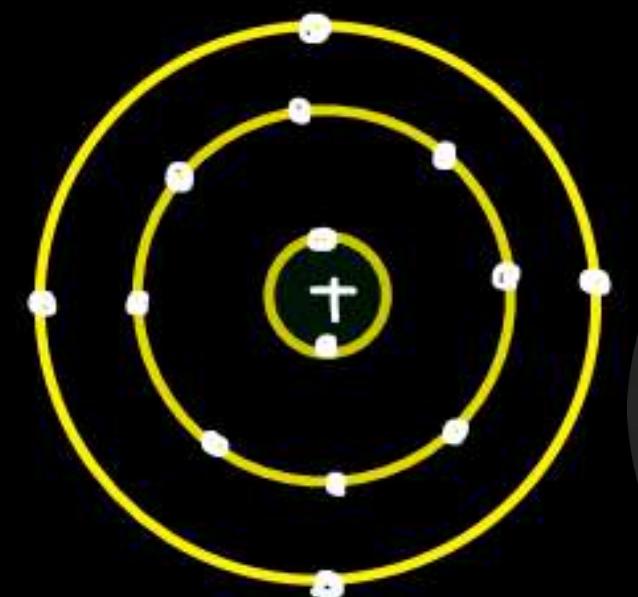
Eg. \rightarrow Si $\Rightarrow 1s^2 \ 2s^2 \ 2p^6 \ 3s^2 \ 3p^2$
(Electronic configuration)



Outermost orbit has 4 valence electrons.



Crystal of silicon:-

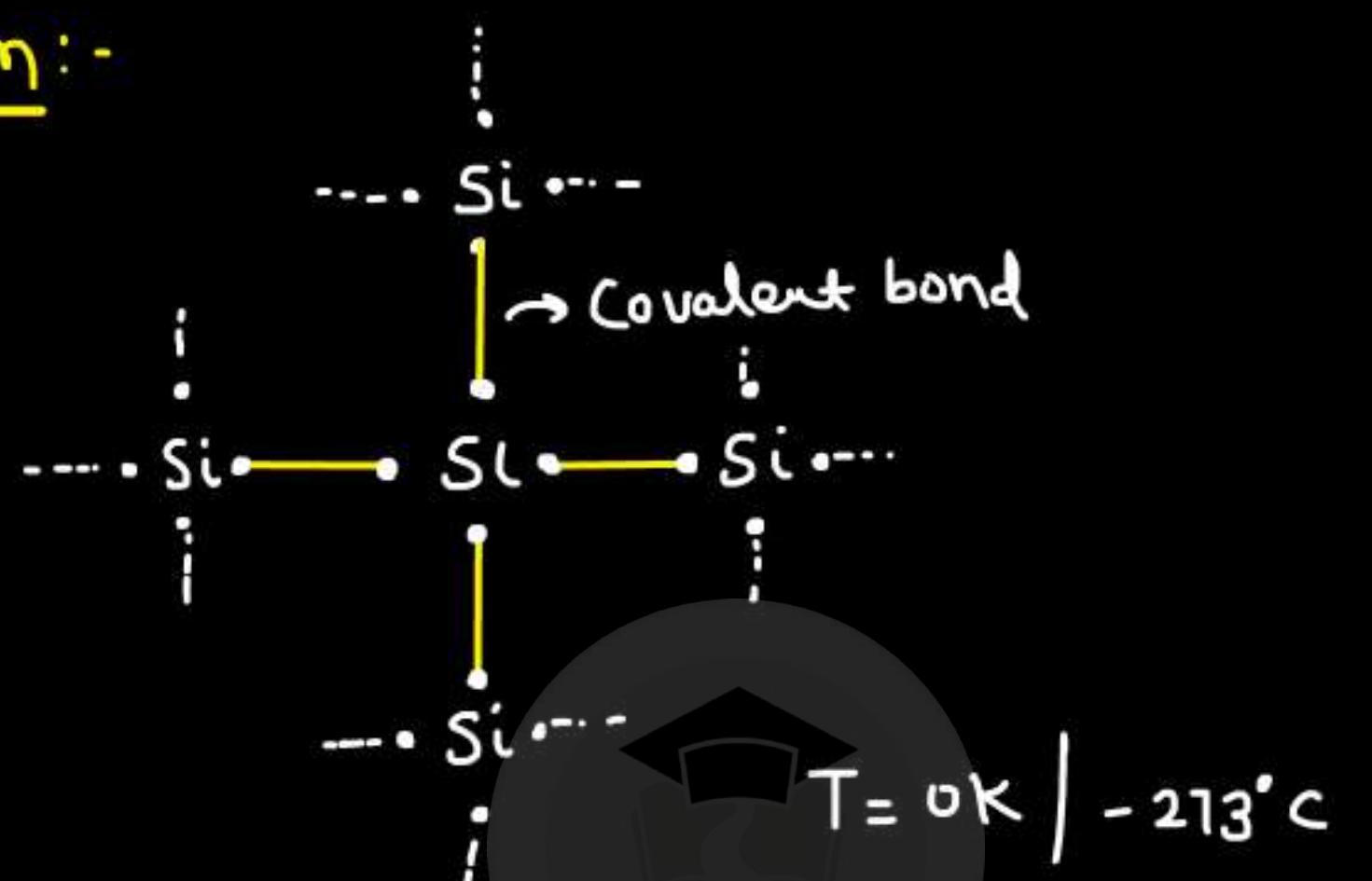

$T = 0K \mid -273^{\circ}\text{C}$


For $T > 0K \Rightarrow$ (@ room's temp.)

Due to thermal energy, some e^- gets enough energy to break this covalent bond.





Semiconductors

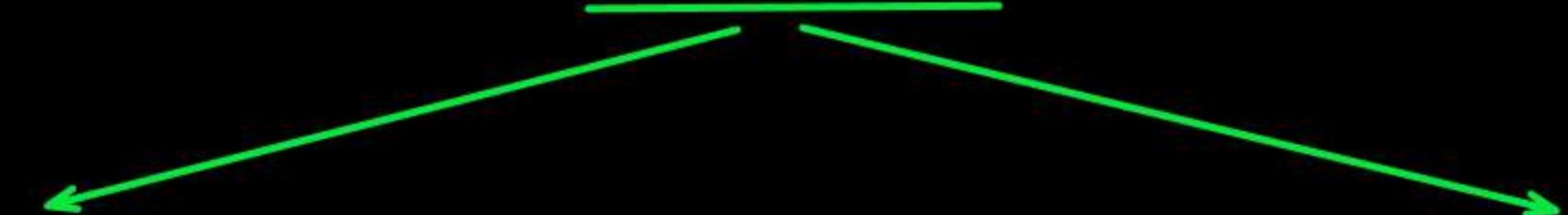

Intrinsic

Pure semiconductor

Extrinsic

(Semiconductor with
impurities)



 P-type
 n-type

P-type Semiconductors:-

Trivalent atoms are added in the Si.

Acceptor atom $\in \{B, Al, Ga\}$


\rightarrow outermost orbit having 3 free e⁻.

• B •

•

•

• Al •

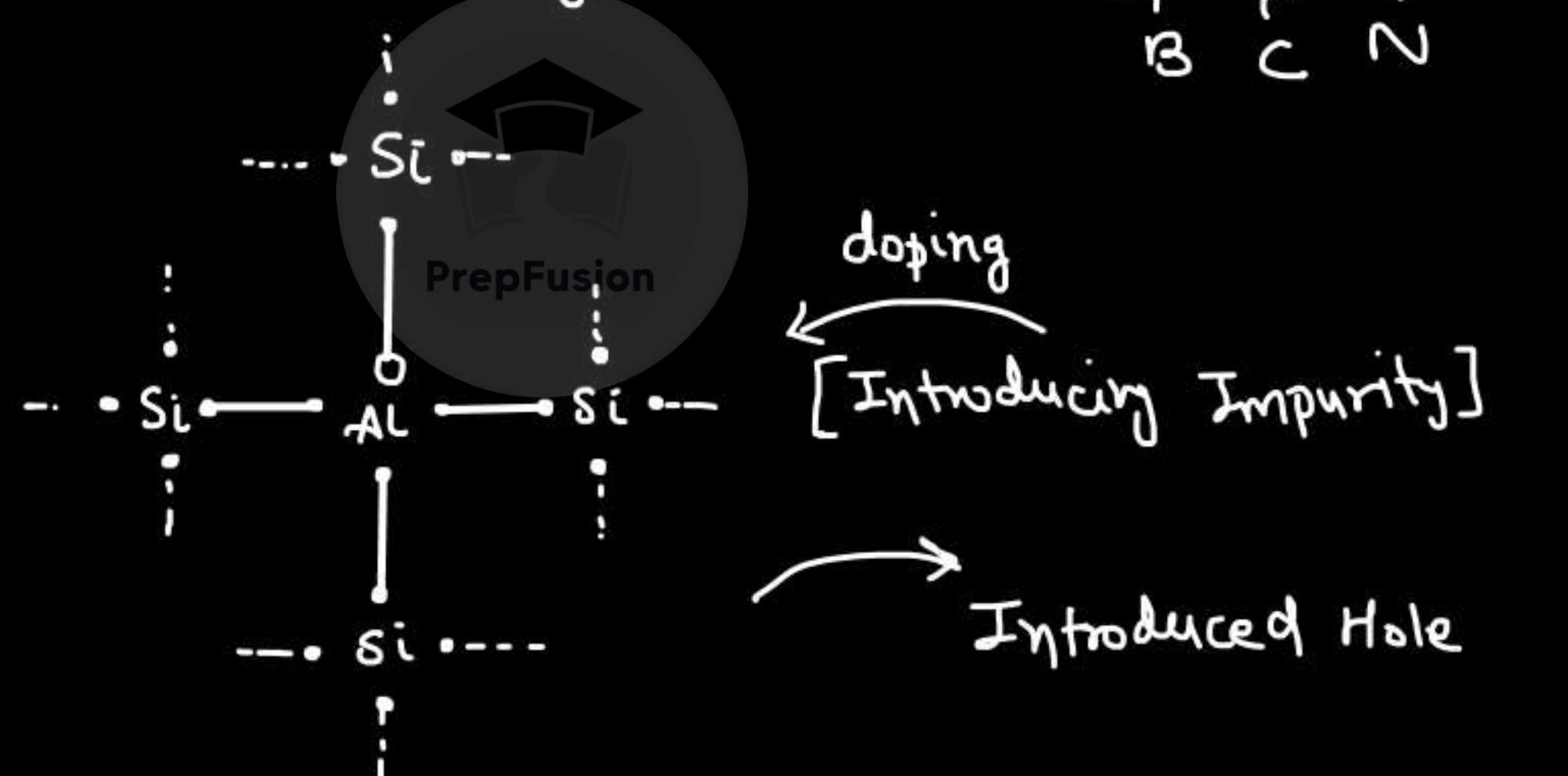




Here, "Al" can accept electrons.

→ It will create negative ion.

P-type $\rightarrow \Theta^\circ$

P-type semiconductor:-

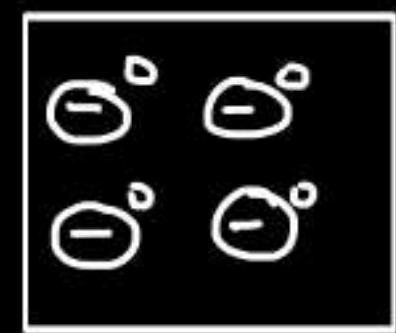

→ Electrical neutral

PrepFusion

(Majority charge carrier \rightarrow Holes)


minority charge carrier \rightarrow electron)

n-type Semiconductor :-

Pentavalent atoms are added in the s/c.

Donor $\leftarrow (N, P, As) \rightarrow$ Nitrogen, Phosphorus, Arsenic atoms

∇ outermost orbit have 5 free electrons.

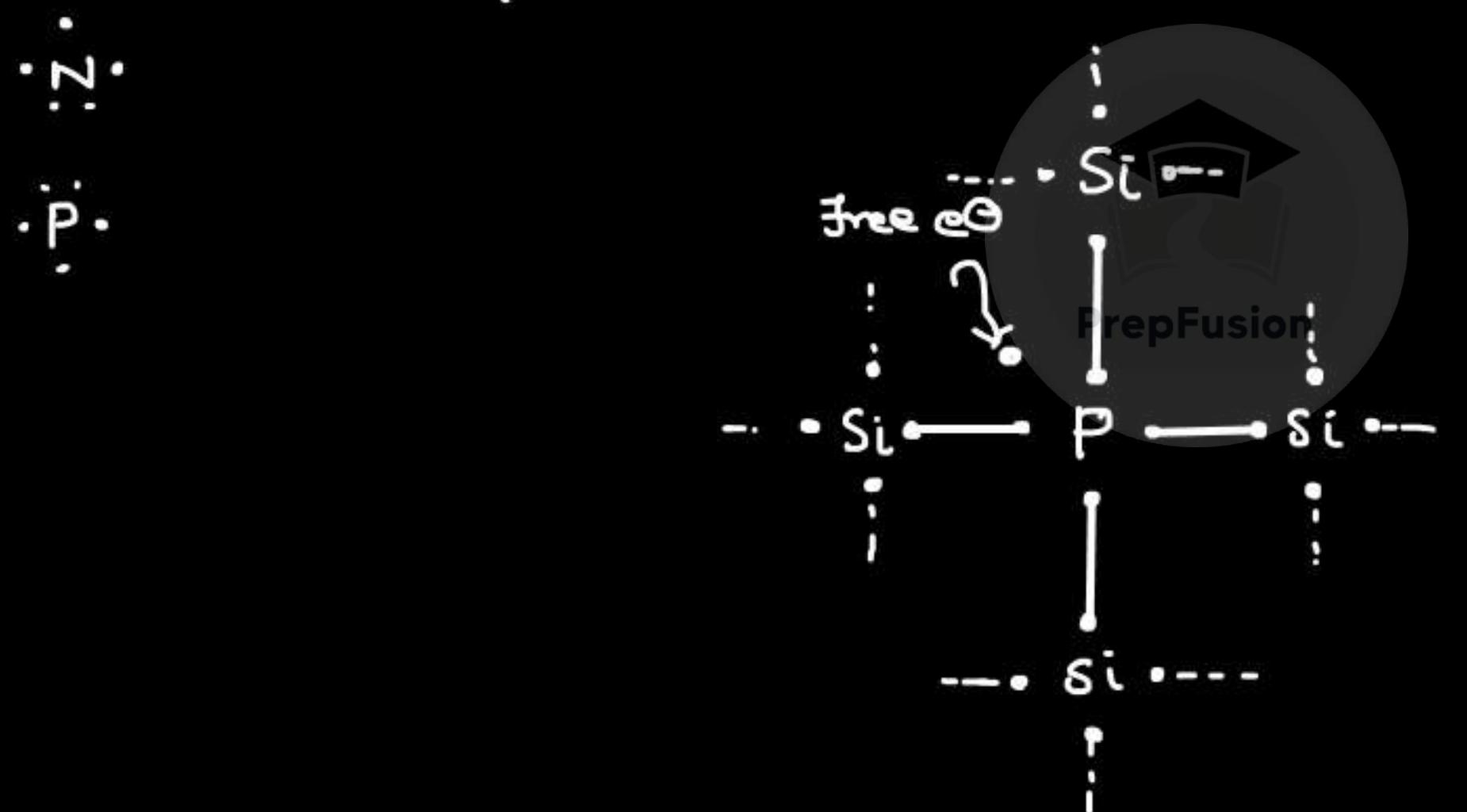


Here, "p" provides electrons.

→ It will create +ve ion

n-type → H_3^+

n-type semiconductor →

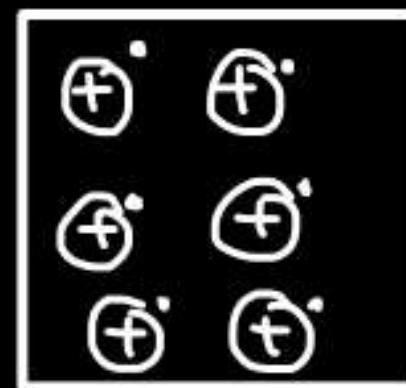


ions = H_3^+ charge carrier

→ Electrically neutral
 (Majority charge carrier → electrons)
Pre-fusion
 minority charge carrier → Holes

N.B. → When there is no external force applied across the sic, it will not generate any current.


PN- Junction

Formation:-

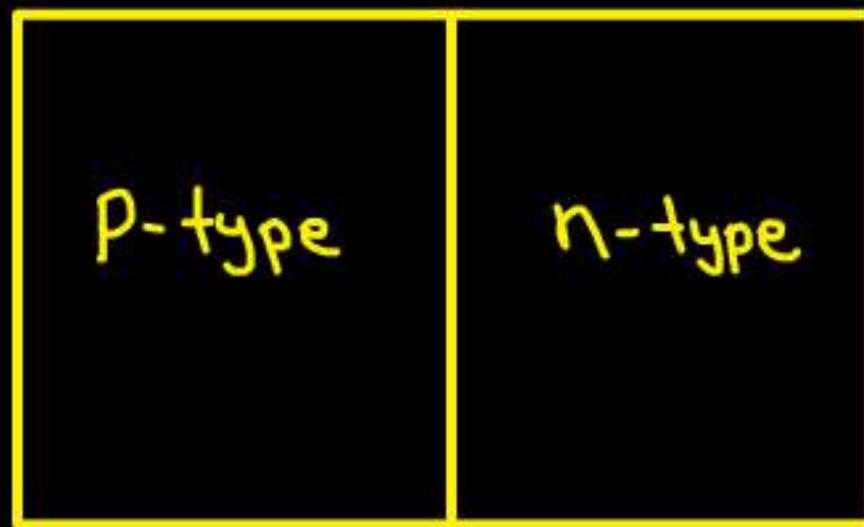

Biasing \Rightarrow Giving supply

Unbiased

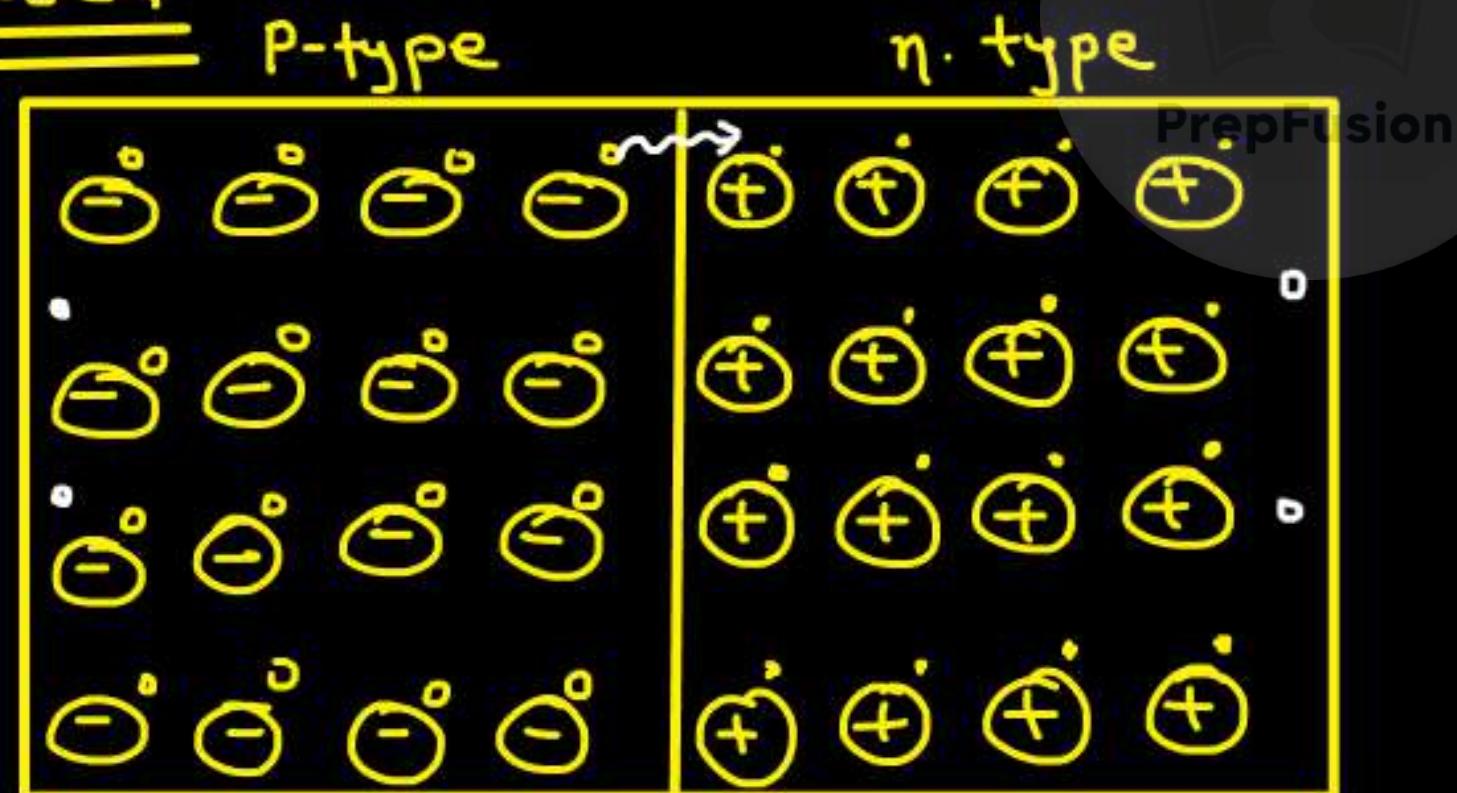


\Rightarrow Due to potential gradient,
Holes are diffusing towards
electrons and electrons are
diffusing toward Holes.


Electrons moves towards p-type region and recombines with the holes.

Holes moves towards n-type region and recombine with the electrons.

⇒ forms a depletion region

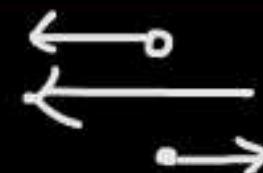

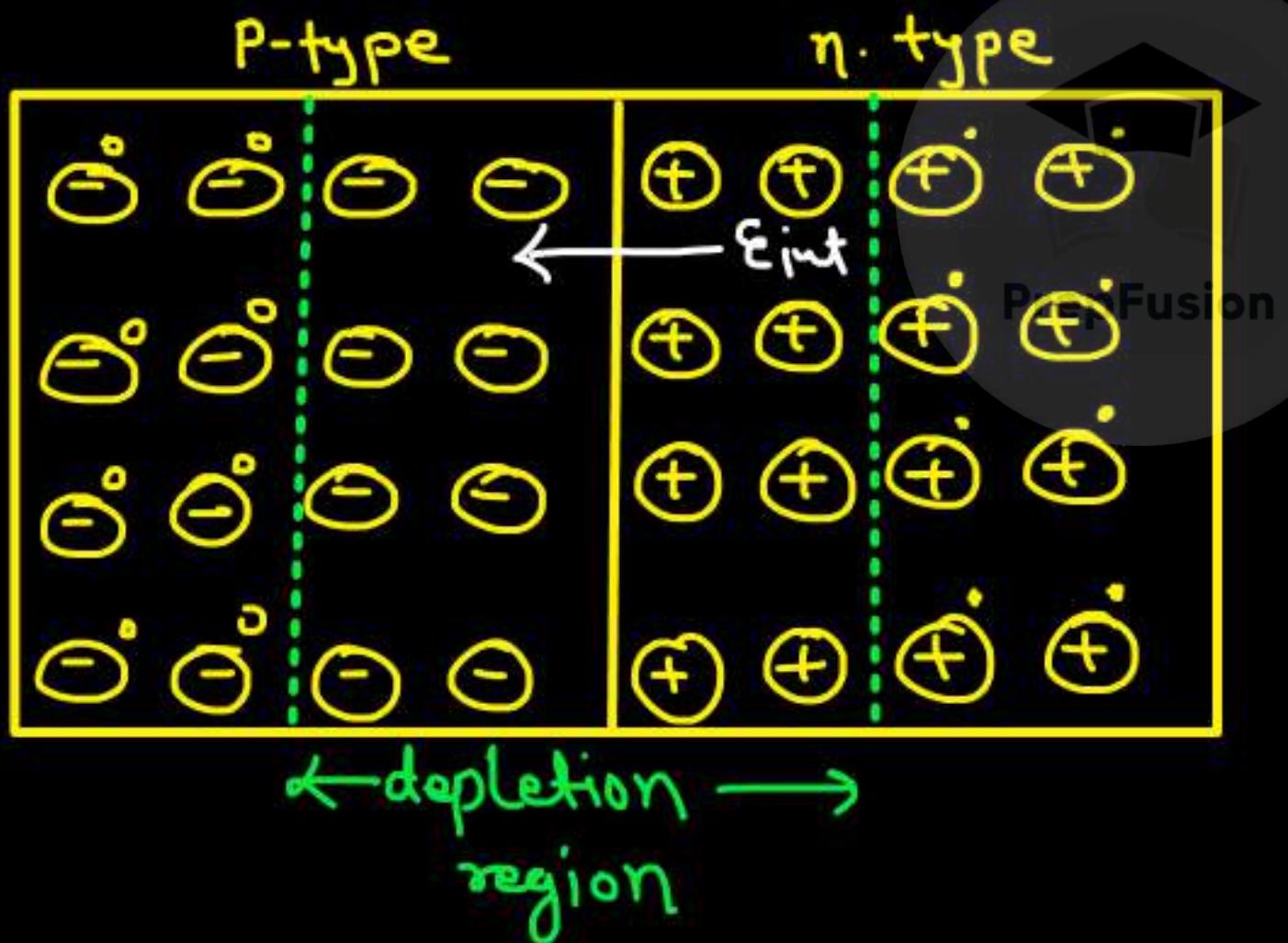↳ Electrons feel force in the opposite dirⁿ of electric field while Holes feel the force in the same dirⁿ.



- ⇒ In depletion region, only immobile ions are present, there are no charge carriers.
- ⇒ these ion generate E_{int} (internal electric field) from n-type to p-type. this E_{int} keep the equilibrium.



↳ In a P-n Junction, without an external applied Voltage, an equilibrium condition is reached in which potential difference forms across the junction. This potential difference is called built-in potential (V_{bi}).


$$\hookrightarrow (V_{bi})_{Si} = 0.7V$$

$$(V_{bi})_{Ge} = 0.3V$$


↳ So, basically these majority carrier has to cross this barrier potential to generate some current.
⇒ Unbiased P-N J^N doesn't generate any current.



Unbiased P-N Junction:-

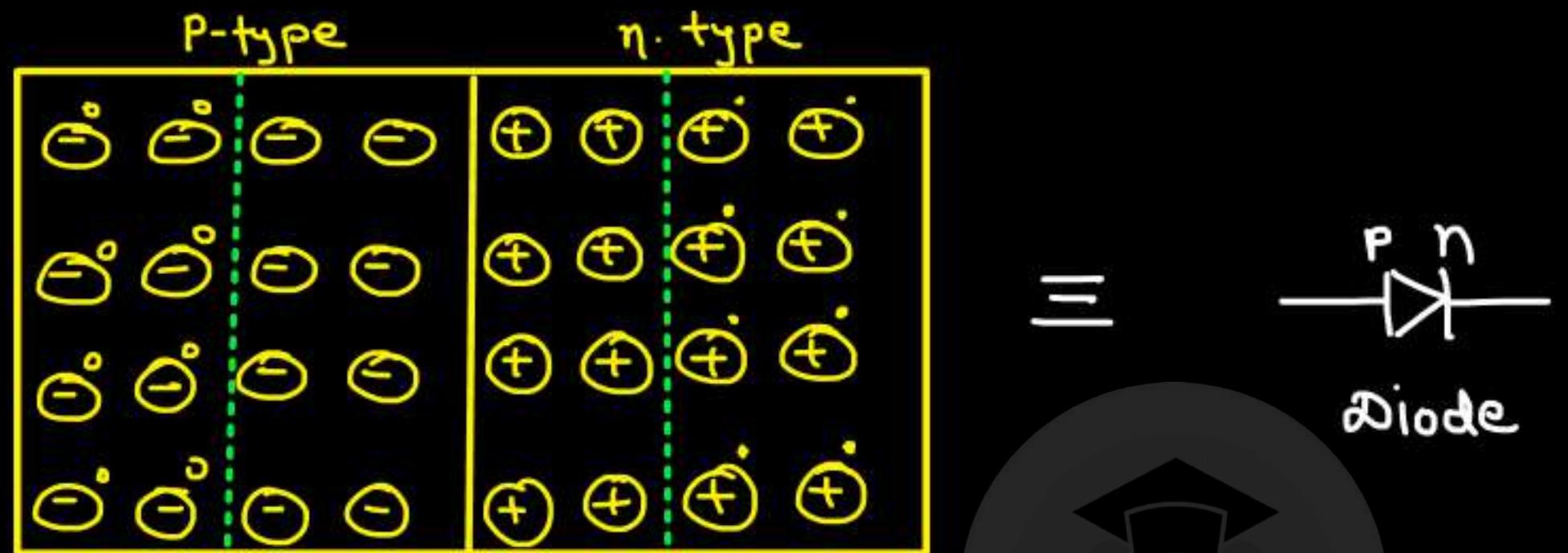


Biasing P-N J^M:-

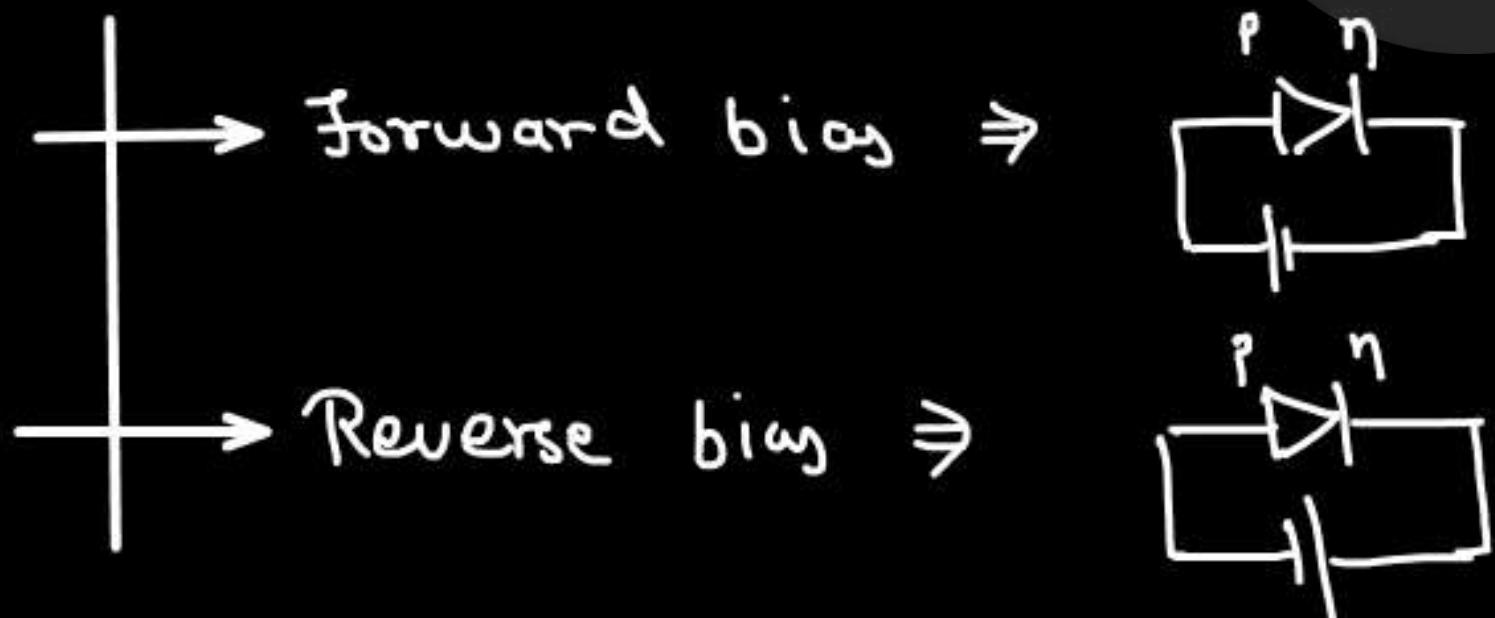


⇒ forward bias P-N Jⁿ :-

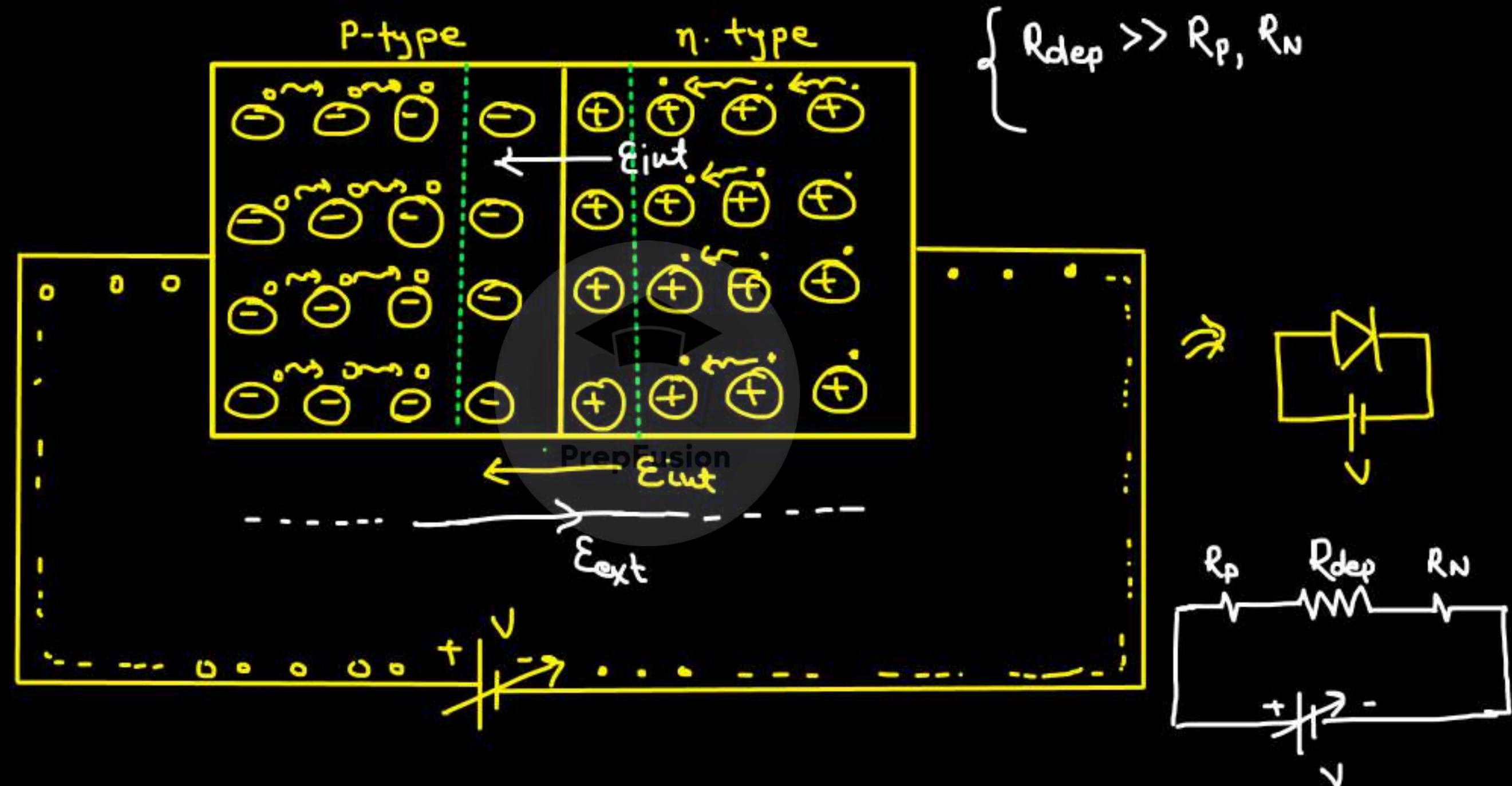⇒ depletion region provides
High impedance



Because of the applied voltage,

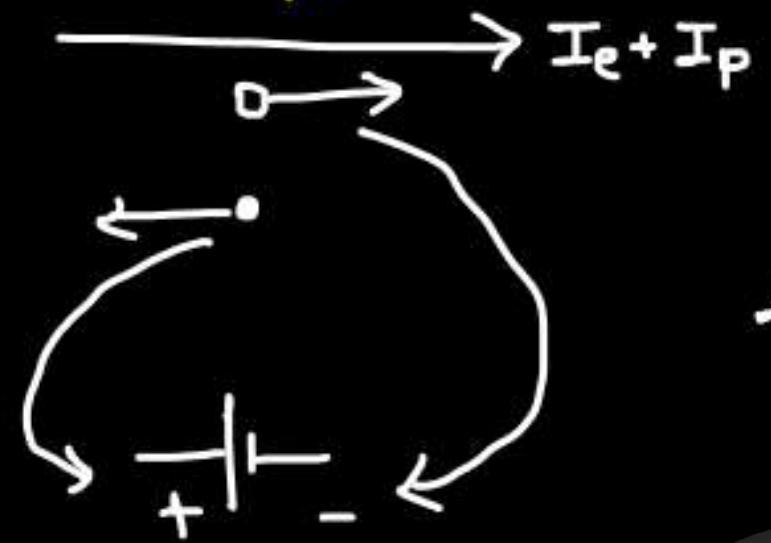


The current flows in the same dirⁿ as the flow of holes and in the opposite dirⁿ as the flow of e⁻

Because of the motion of holes and e⁻ in a certain dirⁿ, the current will flow from p to n side in forward bias.

When $V > V_{bi}$ \Rightarrow current flows

$$I_D = I_S [e^{V_D/nV_T} - 1]$$

$$\approx I_S e^{V_D/nV_T}$$

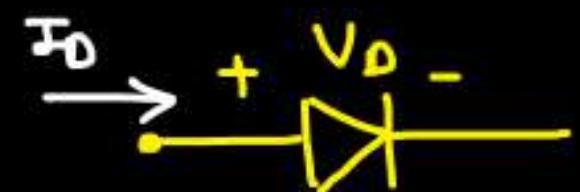


Here $I_S \rightarrow$ Reverse saturation current
 $V_D \rightarrow$ Voltage across diode

$V_T \rightarrow$ Thermal voltage

PrepFusion
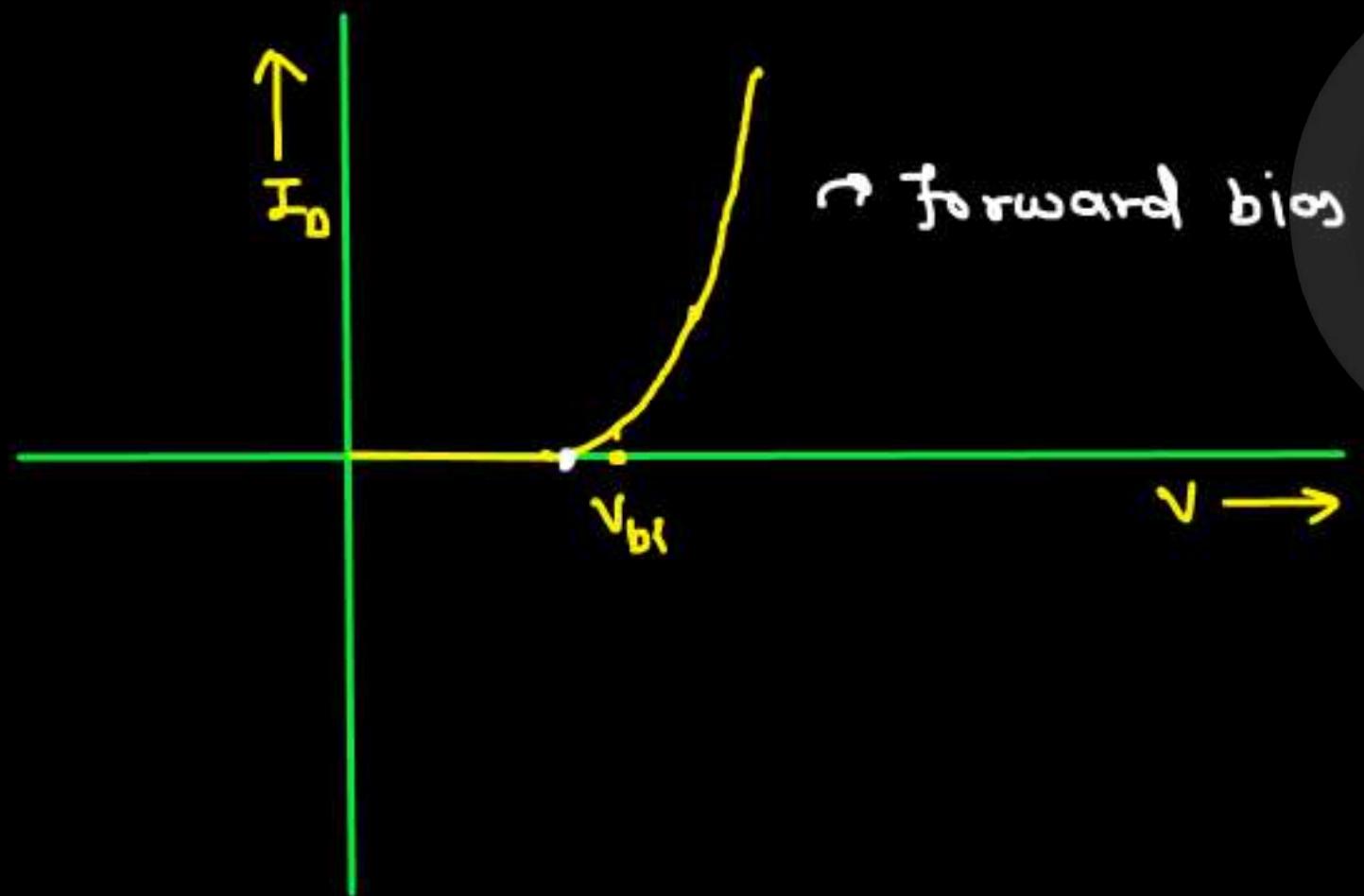
$$\left\{ \begin{array}{l} V_T = 25.9 \text{ mV} @ T = 300 \text{ K} \\ V_T \propto \frac{1}{T (\text{K})} \end{array} \right.$$




$n \rightarrow$ non-ideality co-efficient

$n=1 \rightarrow$ for Ge

$n=2 \rightarrow$ for Si


take $n=1$ when nothing mentioned

→ Reverse bias P-N Junction :-

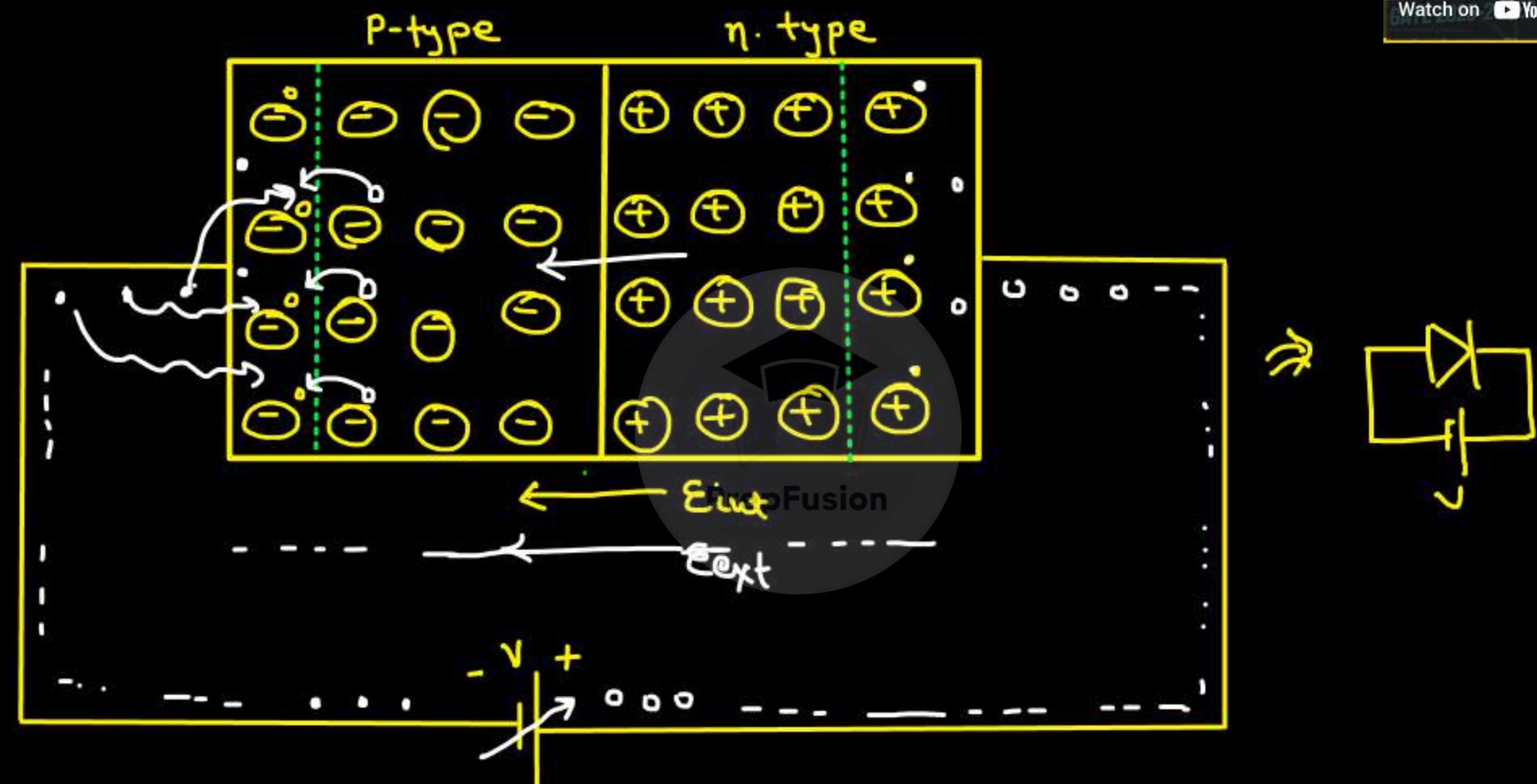




$$I_S \propto \text{Temp}$$

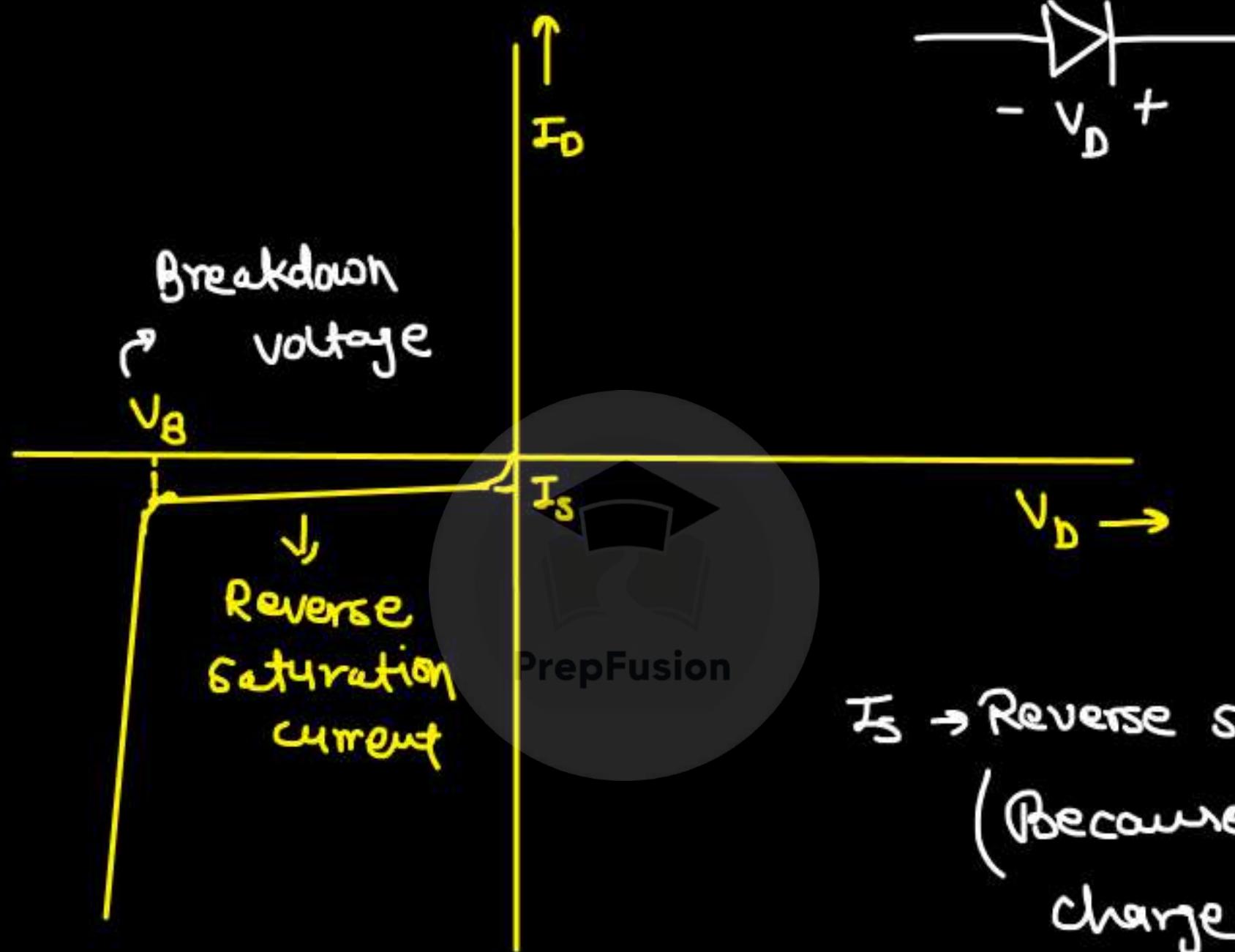


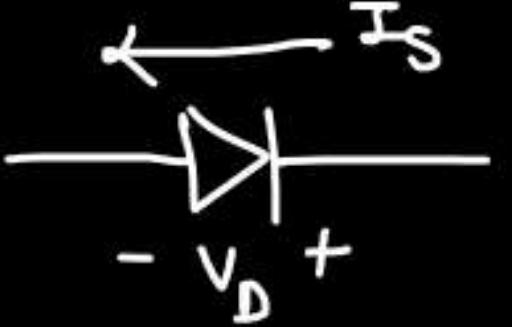$I_S \rightarrow$ Reverse saturation current
 (Because of the minority charge carriers)



Summary:-

① p-type s/c

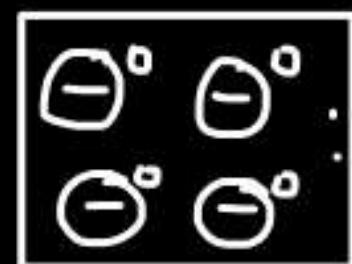

majority charge carriers \Rightarrow Holes

minority charge carriers \Rightarrow electrons


② n-type s/c



majority charge carrier \Rightarrow electrons


minority charge carrier \Rightarrow Holes

↳ Unbiased P-N J^N :-

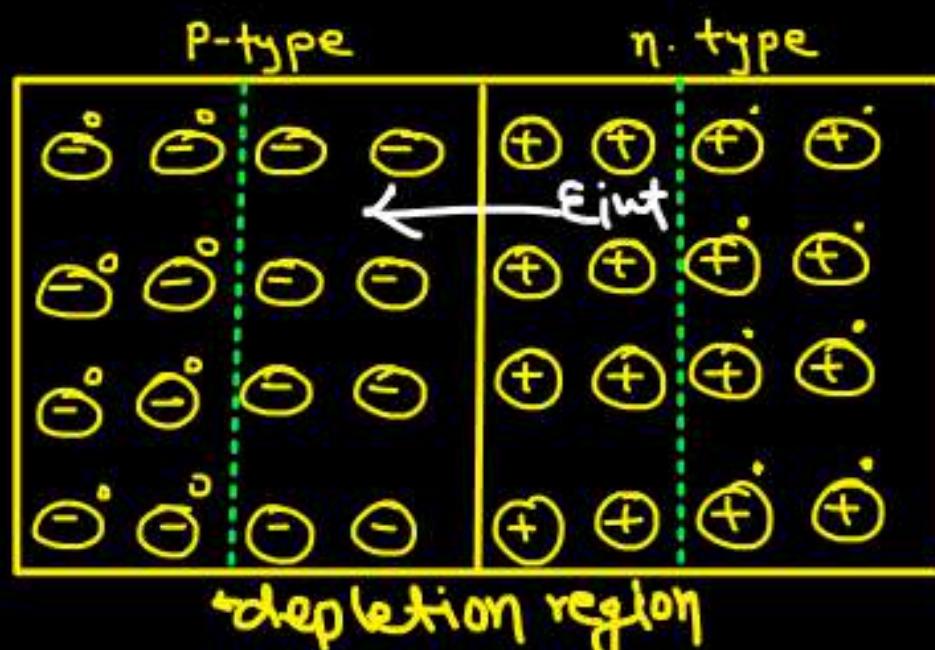

↳ Biased P-N J^N :-


① Forward :-

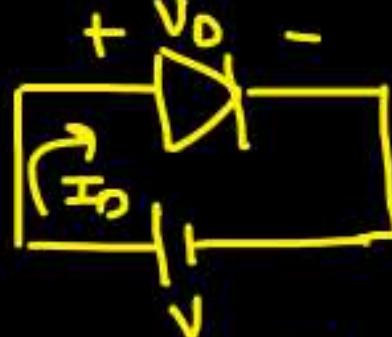


⇒ Depletion width w_D reduced

$$I_D \approx I_s e^{V_D n V_T}$$

Biased Diode:-

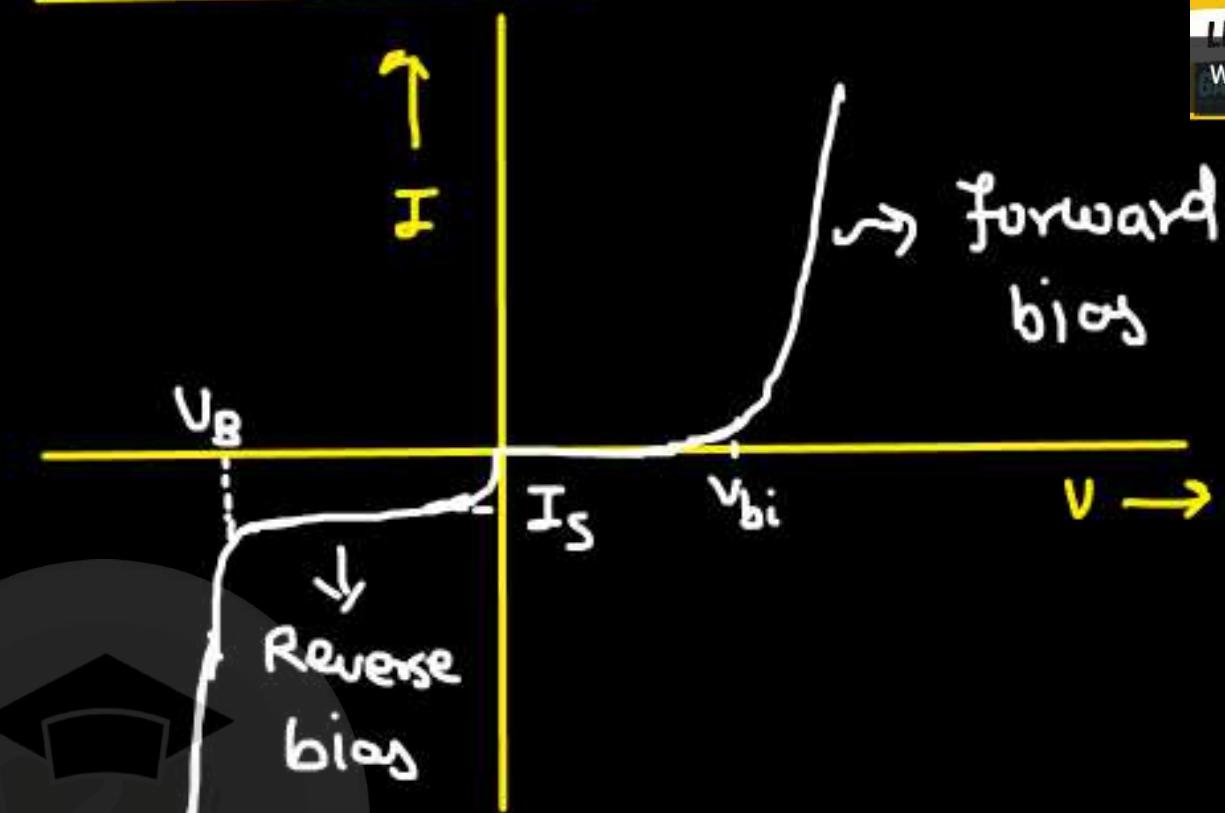


② Reverse bias:-

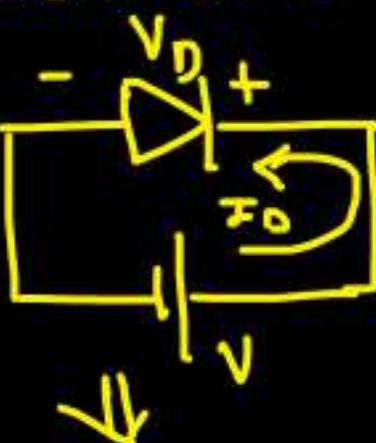

$$I_D = I_s \begin{cases} \text{Before breakdown} \\ \downarrow \\ \{ \mu A, \eta A \} \end{cases}$$

Depletion width w_D increased

Diode as a device:-

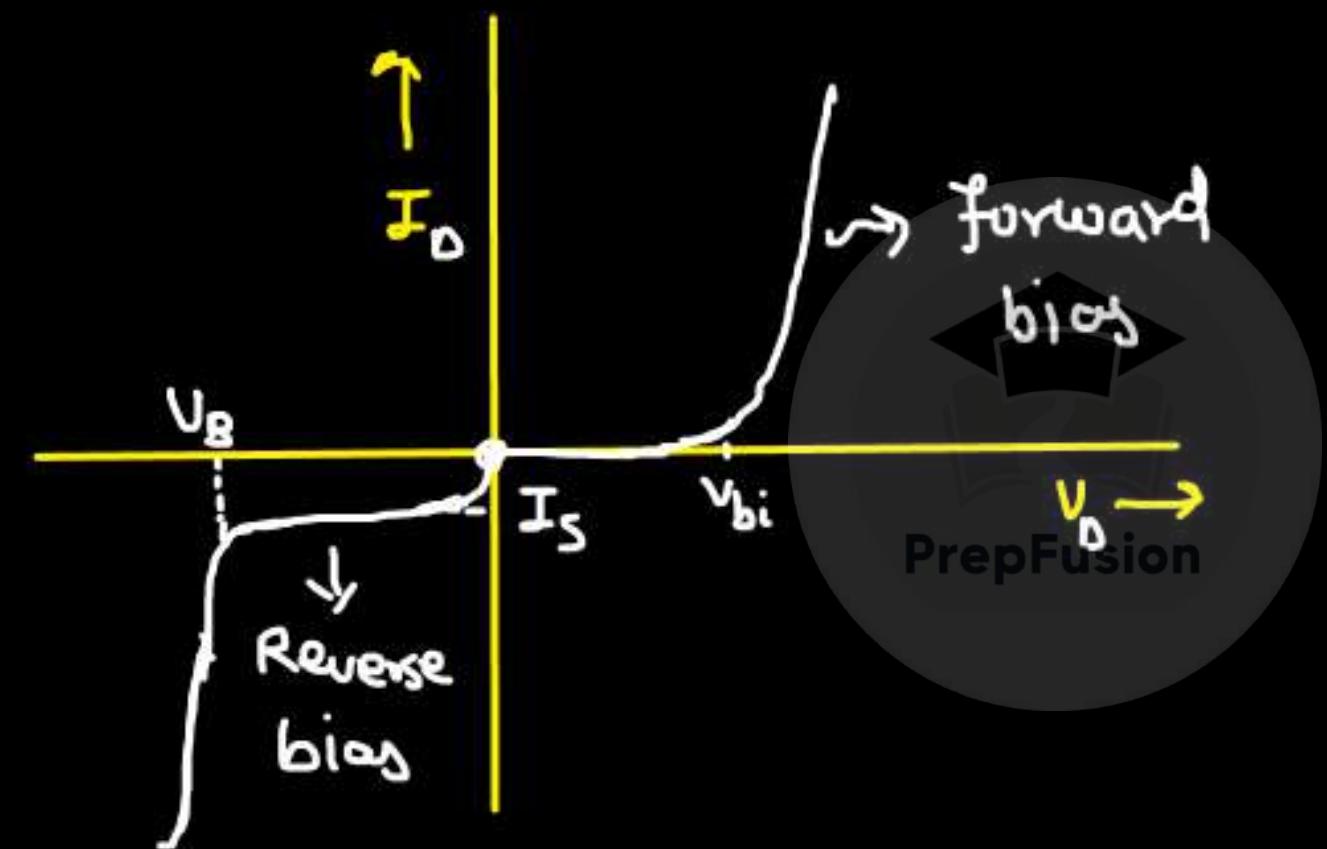

$$I_D = I_S e^{\frac{V_D}{nV_T}} \quad \leftarrow \text{forward}$$

$$I_D = I_S \quad \leftarrow \text{reverse}$$

- ↳ Non-linear
- ↳ Unilateral

↳ Diode Turning on or off:-

→ For diode to turn ON (considering ideal diode)

↳ Potential of p > Potential of n

↳ (Potential of p - Potential of n) > 0



Q. Tell if the diode is on or off



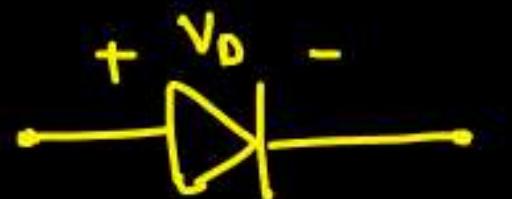

LECTURE-1

Watch on YouTube

 AIR 27 (ECE)
 AIR 45 (IN)

→ Different models of diodes :-

① Ideal diode :-


when ON


$$\rightarrow I_D$$

$$\Rightarrow \{ V_D > 0 \}$$


when off

$$\rightarrow I_D = 0$$


$$\Rightarrow \{ V_D < 0 \}$$

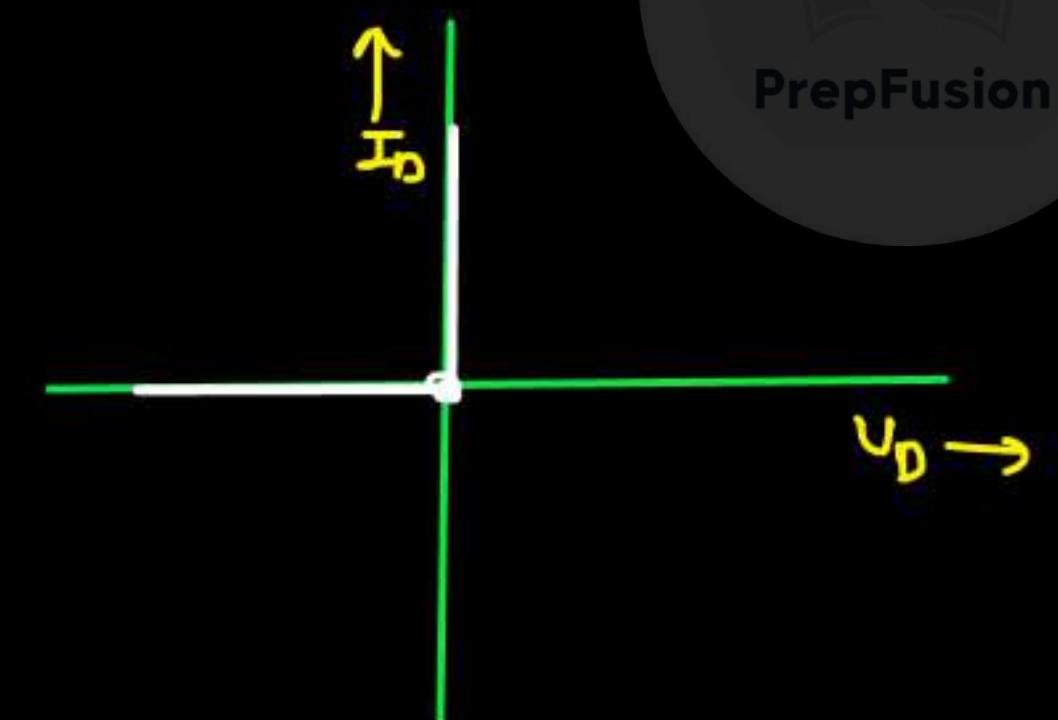

② Piecewise Linear Model:-



when ON

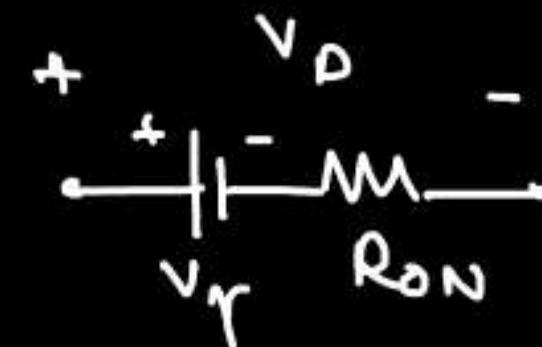


$$\left\{ V_D > V_T \right\}$$






when OFF

$$I_D = 0$$

$$\left\{ V_D < V_T \right\}$$

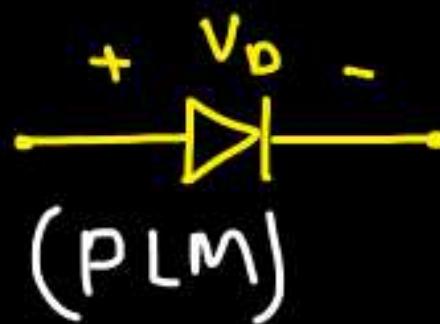


=

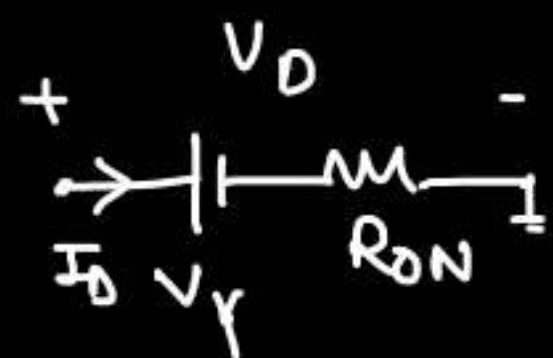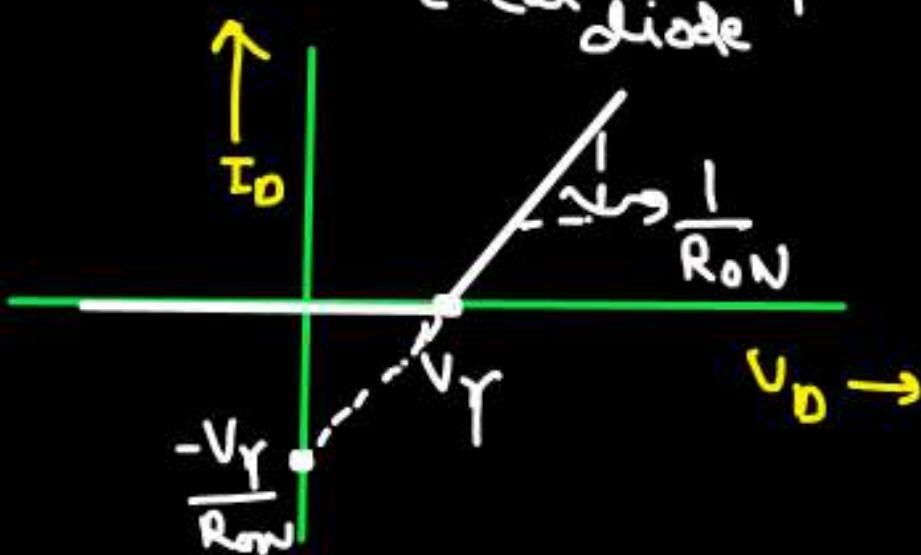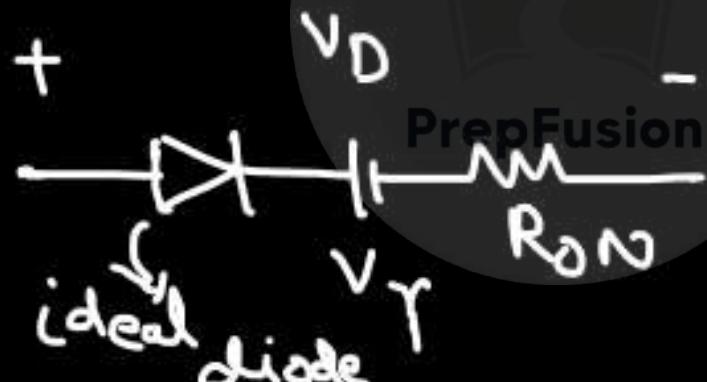


$$\frac{V_D - V_T}{R_{ON}} = I_D$$

$$\Rightarrow V_D = V_T + I_D R_{ON}$$


Constant Voltage drop model:-

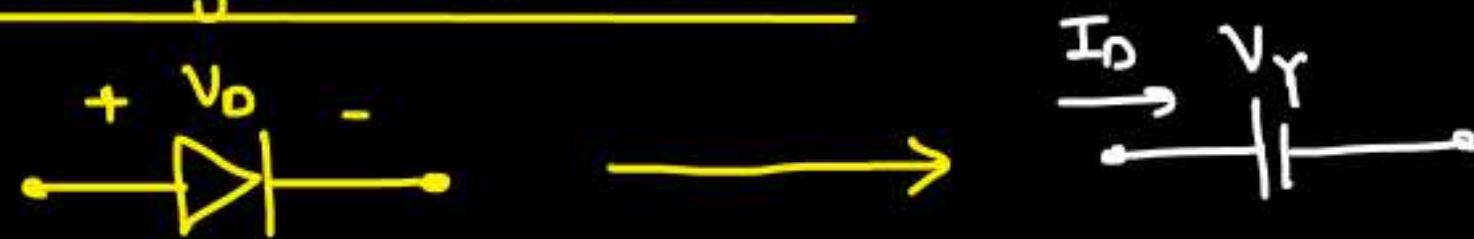

$$\left\{ V_D > V_T \right\}$$

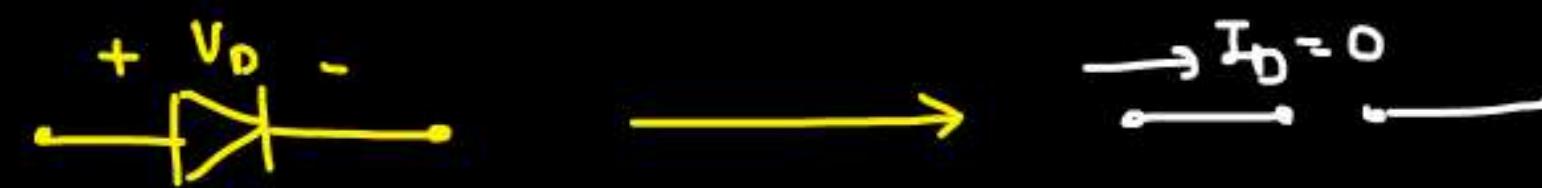

$$\left\{ V_D < V_T \right\}$$

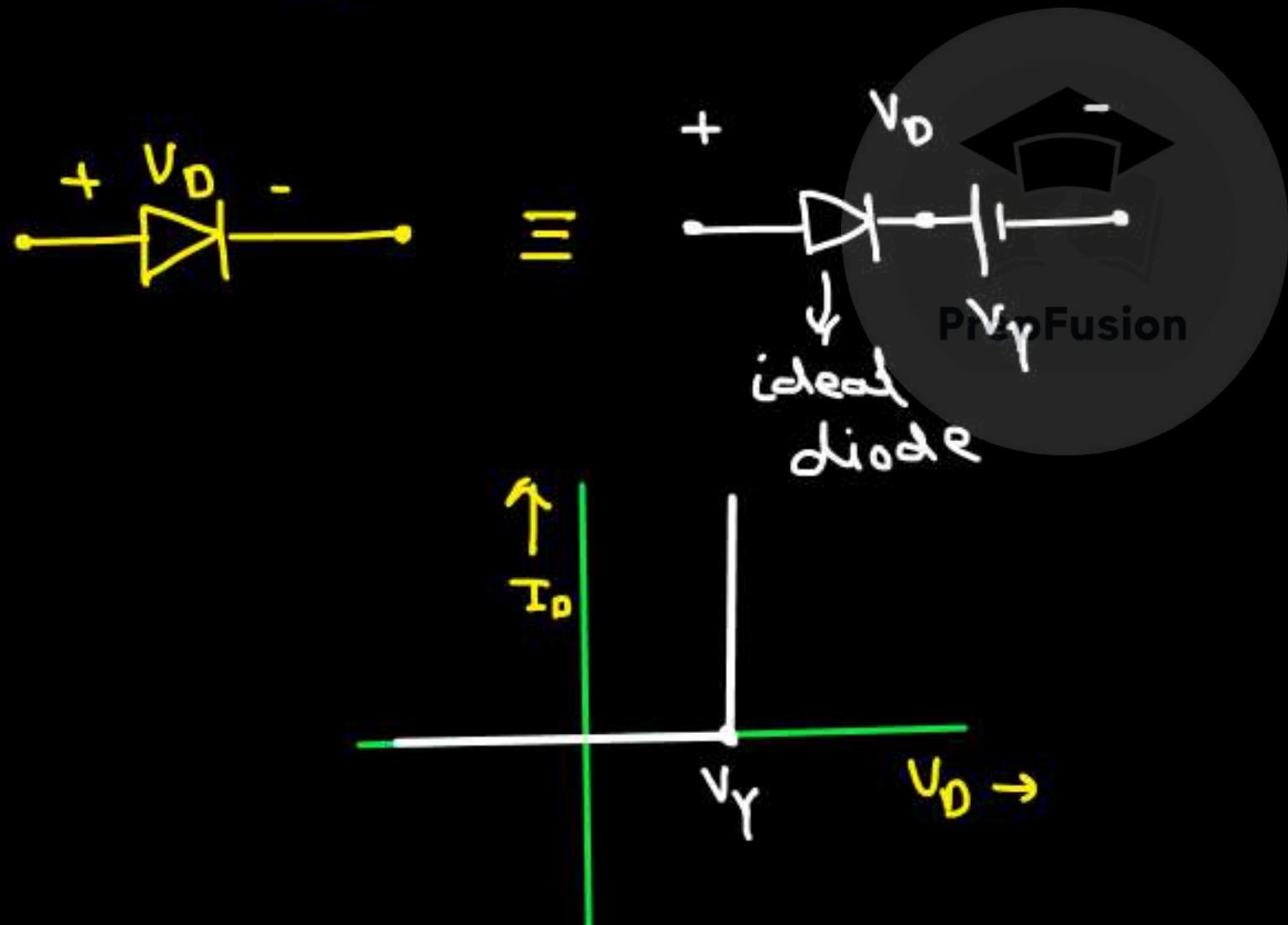

$$\left. \begin{array}{l} \text{For Si, } V_T = 0.7V \\ \text{For Ge, } V_T = 0.3V \end{array} \right\}$$


↳ Solving diode ckts:-

- Short-circuit Test (S.C. Test)
- Open-circuit Test (O.C. Test)

① Short-Circuit Test (S.C. Test) :-

- (i) Consider diode to be ON.
(Short-circuit it or replace with its equivalent model)
 - (ii) Find current direction in the diode.
- If p to n \Rightarrow  \Rightarrow Assumption correct \Rightarrow Diode ON
- If n to p \Rightarrow  \Rightarrow Assumption wrong \Rightarrow Diode OFF

Q.

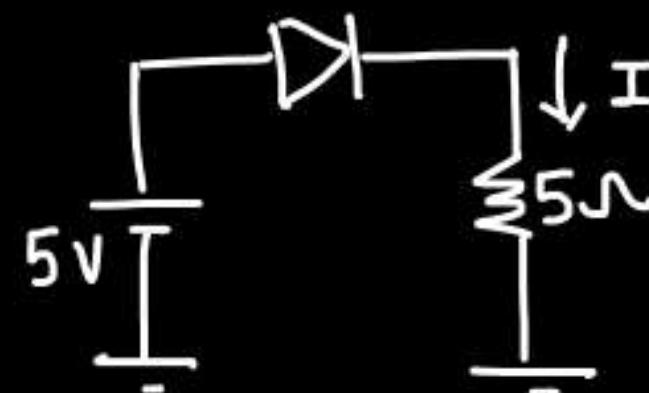

Find current I .

- (i) Diode is ideal
- (ii) Diode has $V_f = 1V$ (Cut-in voltage)
- (iii) Diode has $V_f = 1V, R_{on} = 3\Omega$

→ (i) Diode is ideal


↳ S.C. Test




$$I = 1 \text{ Amp.}$$



(ii) $V_f = 1V$

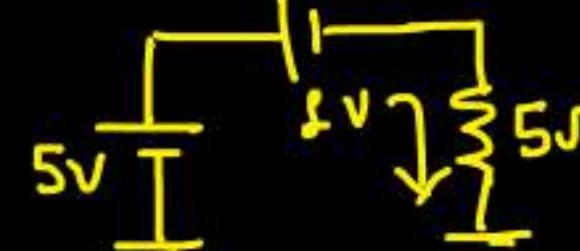

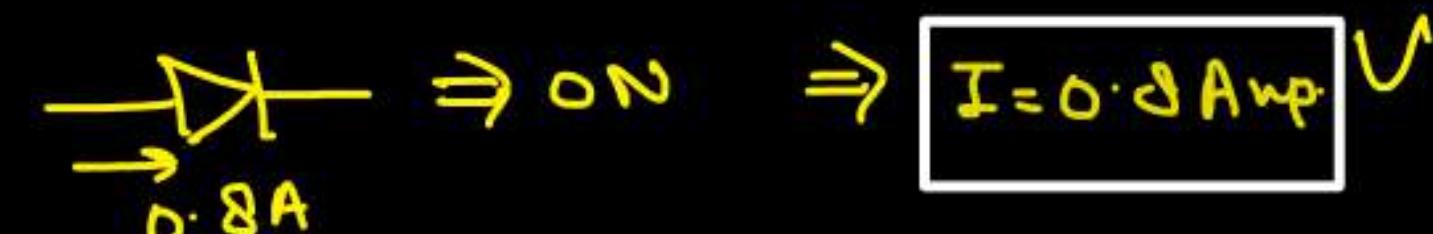
$$I = \frac{U}{R} = \frac{4}{5} = 0.8 \text{ A}$$




$$I = 0.8 \text{ Amp}$$



(iii) $V_f = 1V$, $R_{ON} = 3\Omega$

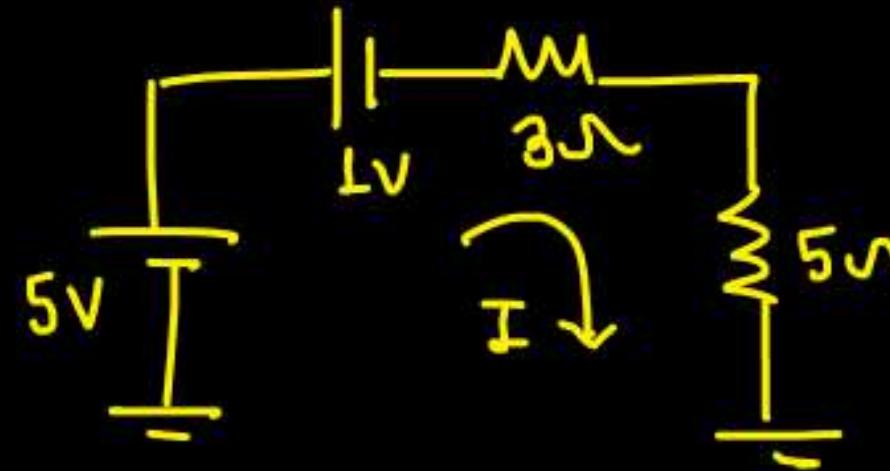


$$I = 0.5 \text{ Amp.}$$

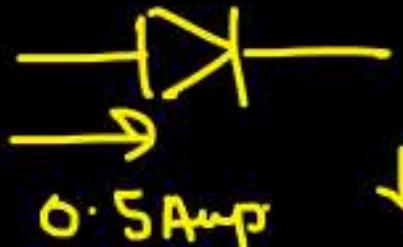

Diode ON



$$I = 0.5 \text{ Amp}$$



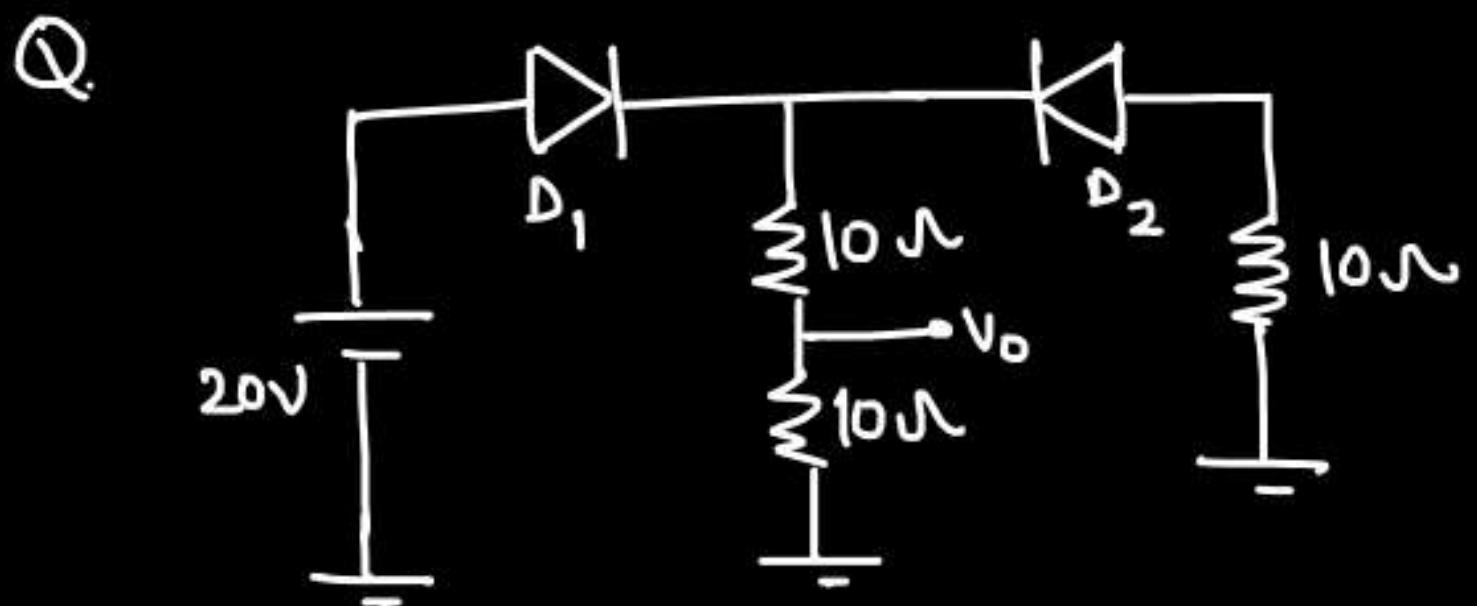


considering D_1 and D_2 to be ideal. Find V_o .

→ Applying S.C. Test

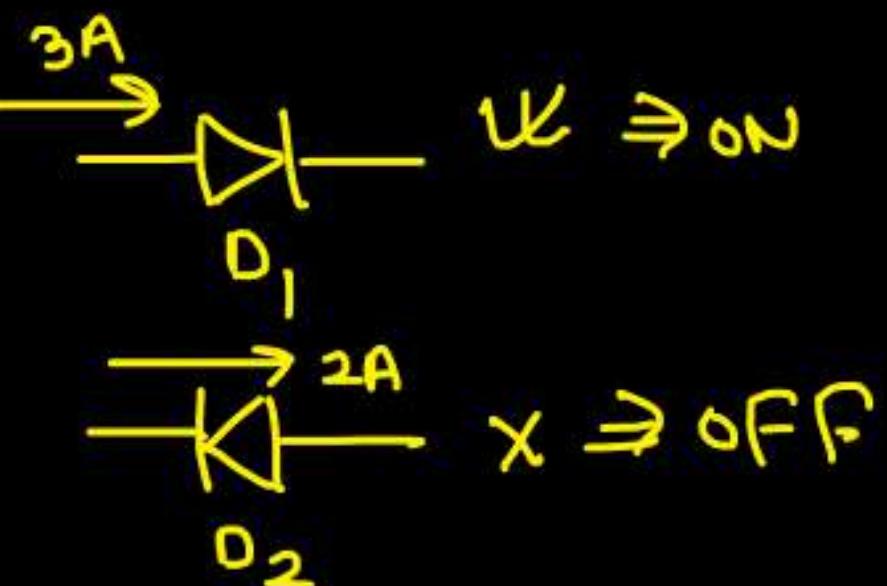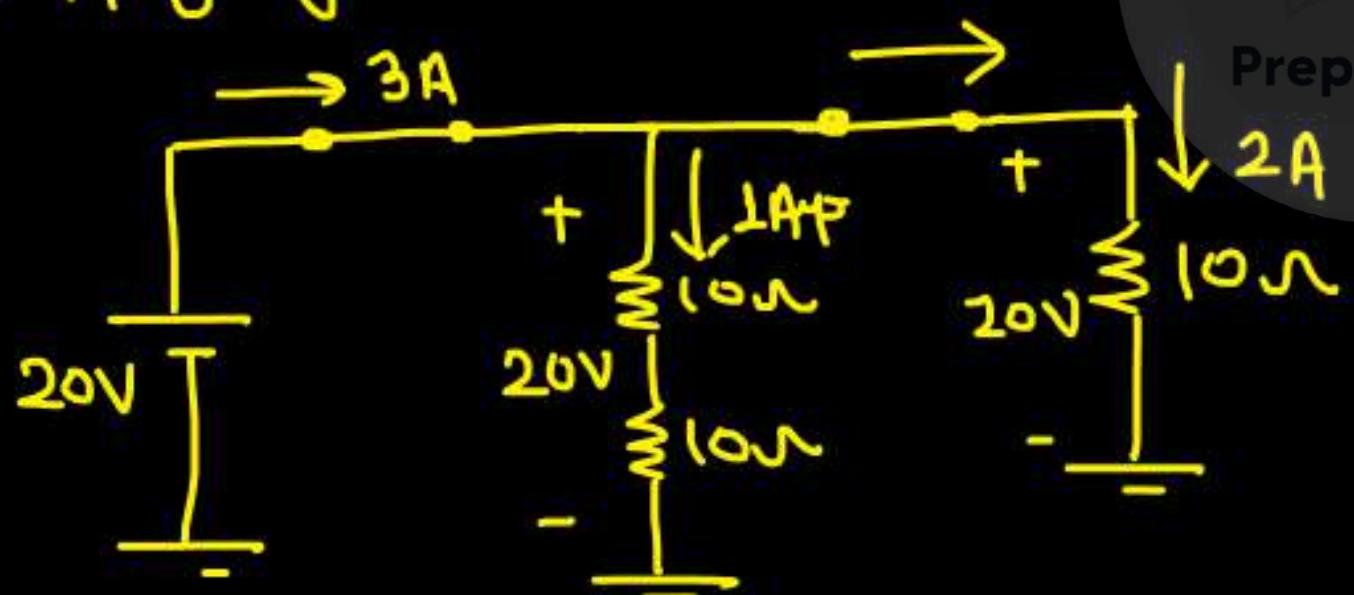

Final ckt: →

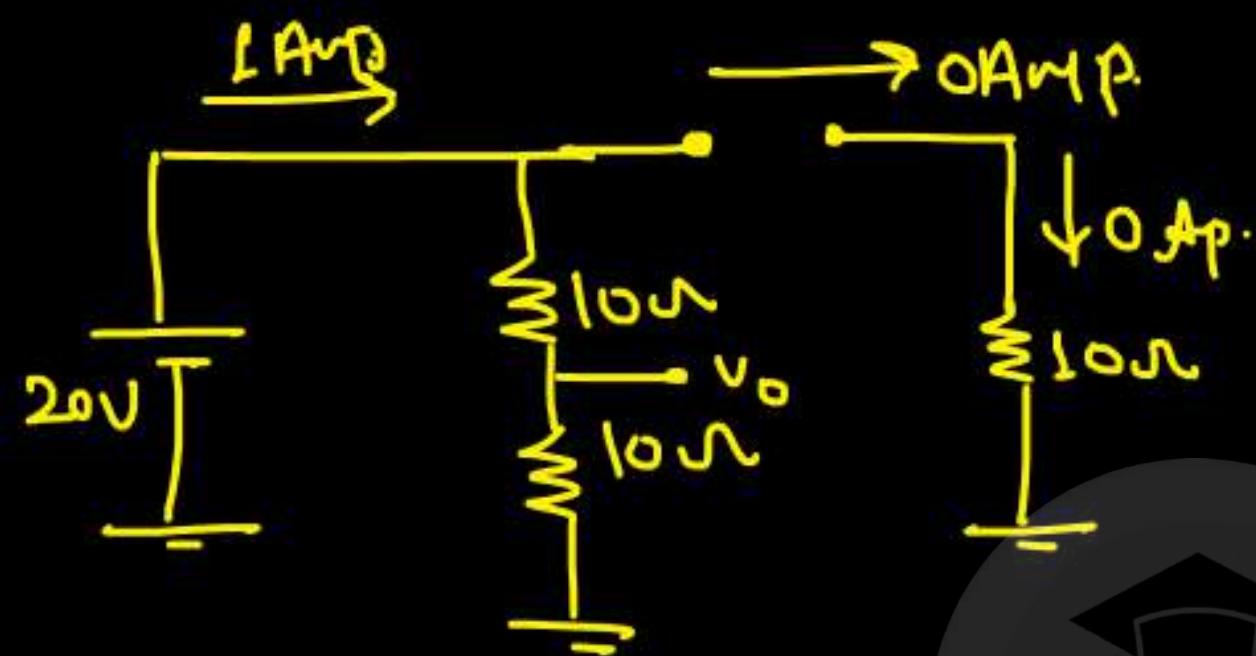$D_1 \rightarrow \text{ON}$, $D_2 \rightarrow \text{OFF}$




$$I_{D_2} = 0 \text{ A.p.}$$

$$I_{D_1} = 1 \text{ A.p.}$$


$$V_o = 20 \times \frac{1}{2} = 10V$$



Q. Apply S.C. Test to find V_o .

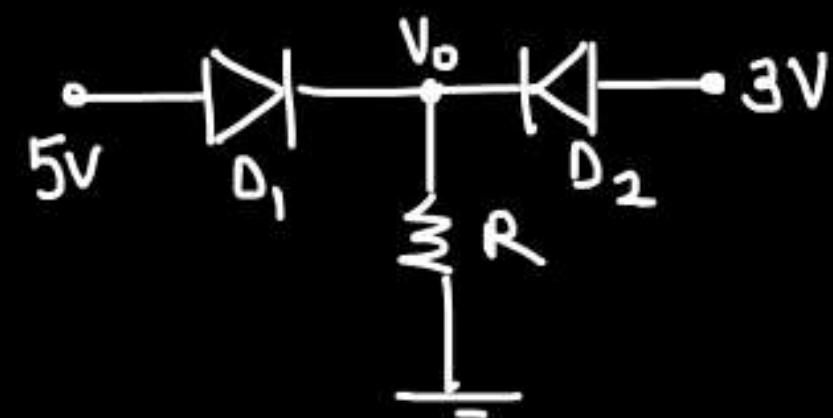

→ Applying S.C.

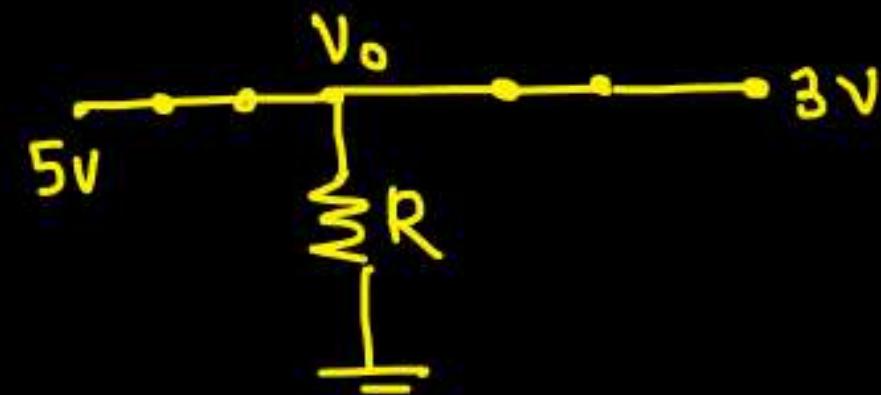

$$V_o = 5V \text{ or } 3V$$



KVL Invalid



Can't apply S.C. Test




↳ Open circuit Test:-

- ① Consider diode to be off.
(open circuit it)
- ② Find the potential across diode and check if it's ON or OFF.

N.B. -


In case of multiple diodes; the diode which has the maximum forward voltage drop, consider that to be ON first.

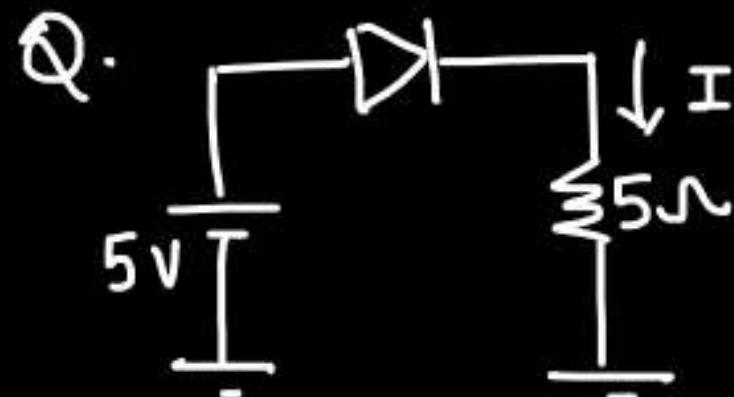Now compute voltage across rest of the diode and repeat the same process.




- (i) Diode is ideal
- (ii) Diode has $V_f = 1V$
- (iii) Diode has $V_f = 1V, R_{on} = 3\Omega$

→ (i) ideal diode

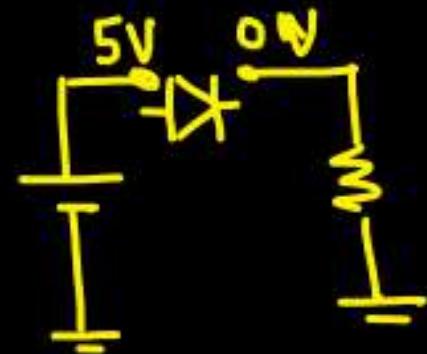


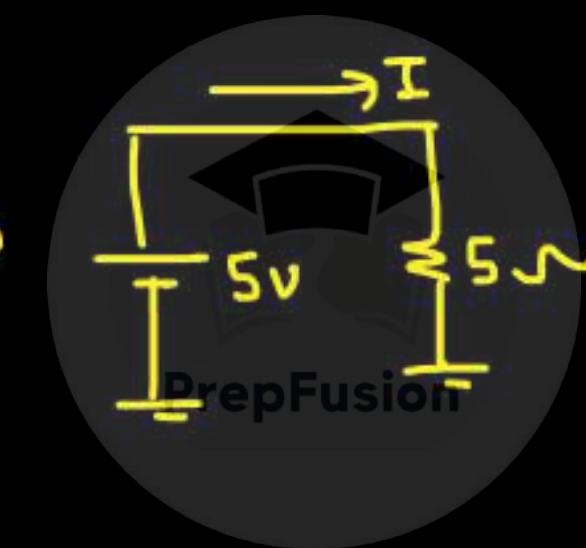\Rightarrow Diode ON \Rightarrow (5V > 0V)




$$I = 1 \text{ Amp.}$$

(ii) $V_f = 1V$

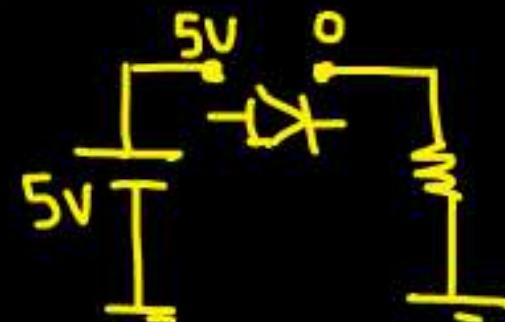


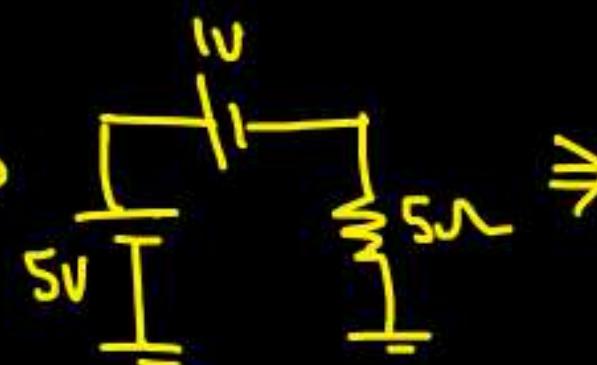$\Rightarrow 5V > 1V \Rightarrow$ diode ON \Rightarrow




$$I = 0.8 \text{ Amp}$$


(iii) $V_T = 1V$, $R_{ON} = 3\Omega$

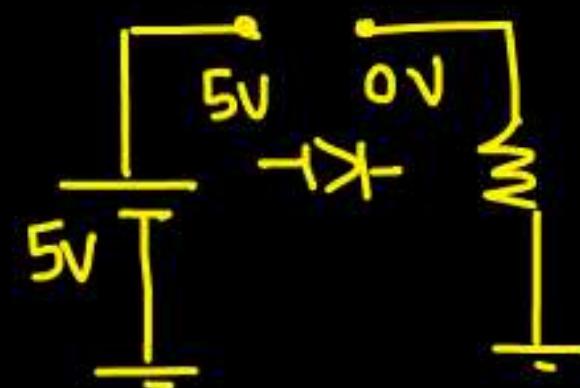

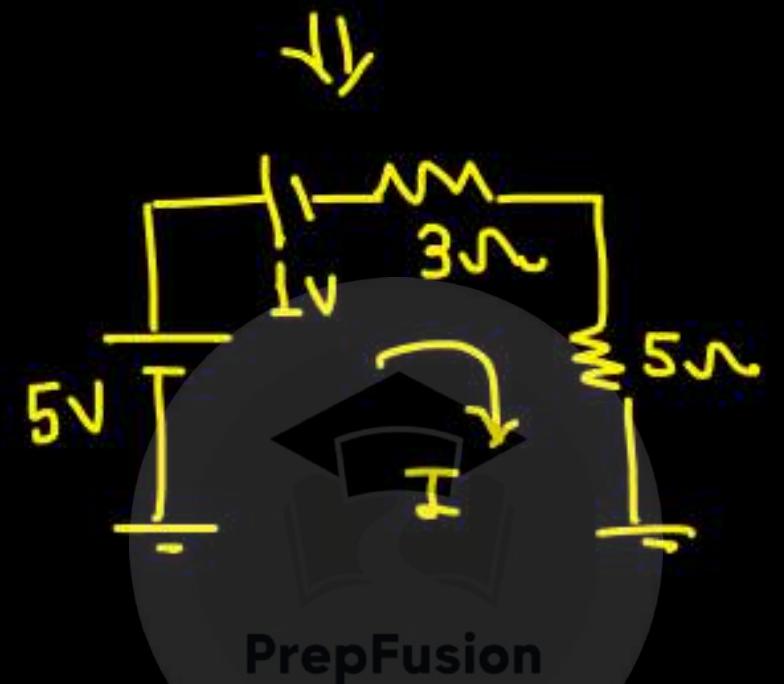$\Rightarrow 5V > 1V \Rightarrow \text{Diode ON}$



$\Rightarrow I = 0.5 \text{ Amp.}$

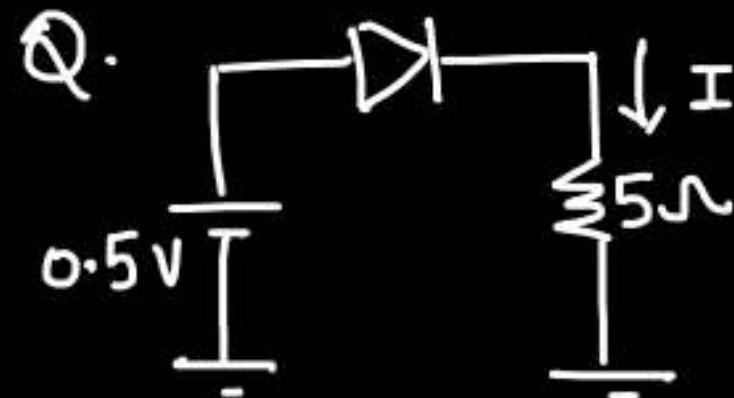


Find current I .

- (i) Diode is ideal
- (ii) Diode has $V_T = 1V$
- (iii) Diode has $V_T = 1V, R_{ON} = 3\Omega$

→ open ckt Test:-

(i) ideal diode

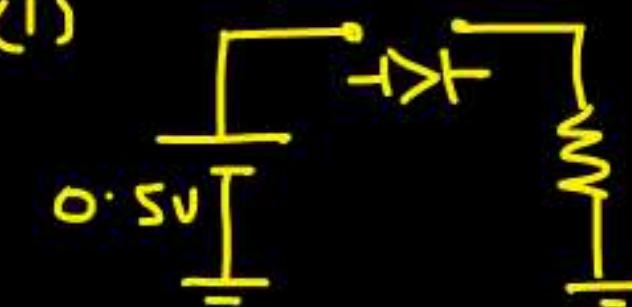


$\Rightarrow 0.5 > 0 \Rightarrow$ diode ON

PrepFusion

$$I = \frac{0.5}{5} = 0.1 \text{ Amp.}$$

(ii) $V_T = 1V$

(iii) $V_T = 1V, R_{ON} = 3\Omega$

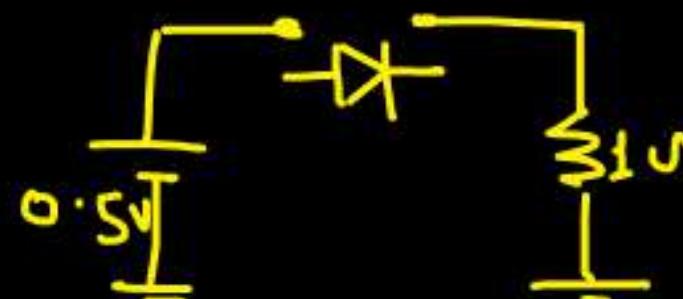


$\Rightarrow 0.5 < 1 \Rightarrow$ diode OFF




$$I = 0 \text{ Amp}$$

Q.

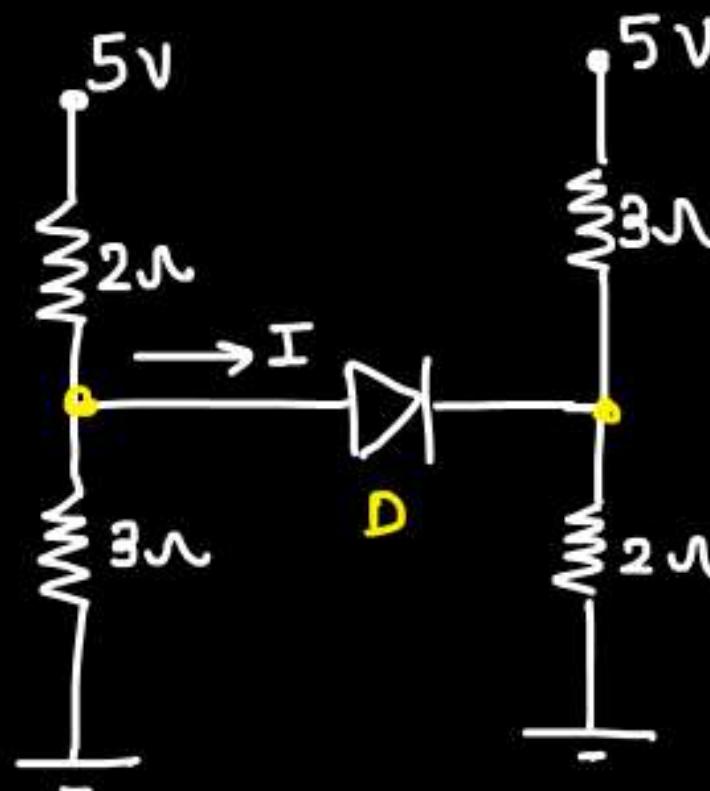

Considering ideal diode.
find current I.

→ open-ckt Test:-

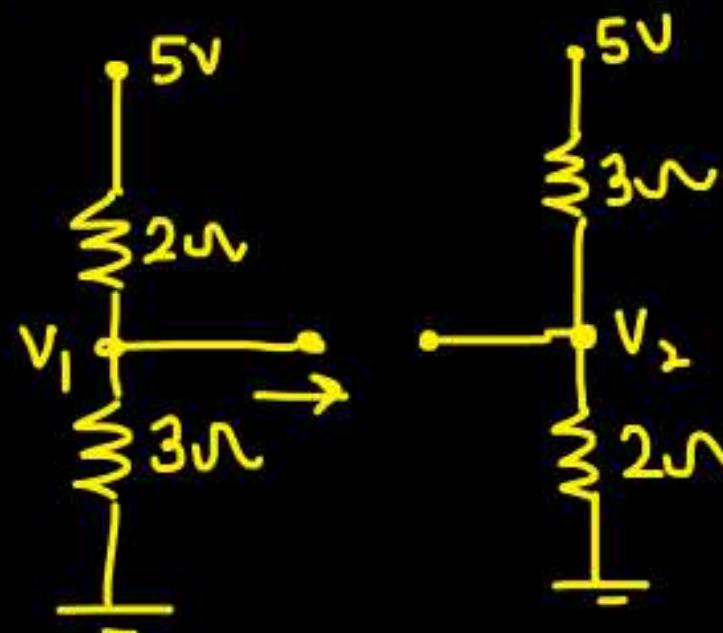


$$V_1 = \frac{5 \times 3}{5} = 3V$$

$$V_2 = \frac{5 \times 2}{5} = 2V$$

$3V \rightarrow 2V \Rightarrow ON$

Final ckt :-

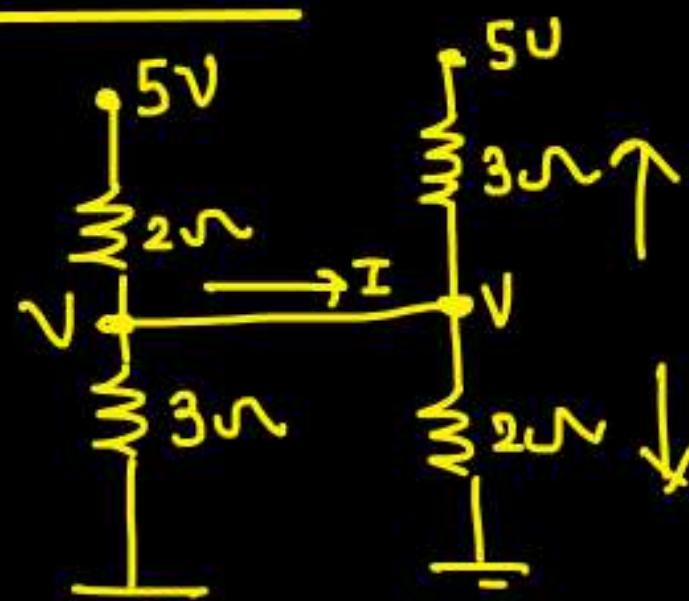

$$\frac{V-5}{2} + \frac{V}{3} + I = 0 \quad \text{--- (1)}$$

$$\frac{V-5}{3} + \frac{V}{2} = I \quad \text{--- (2)}$$



$$\Rightarrow \frac{V-5}{2} + \frac{V}{3} + \frac{V-5}{3} + \frac{V}{2} = 0$$

$$\Rightarrow V = 2.5V$$

$$I = 1.25 - 0.833$$



$$I = 0.416 \text{ Amp.}$$

Q.

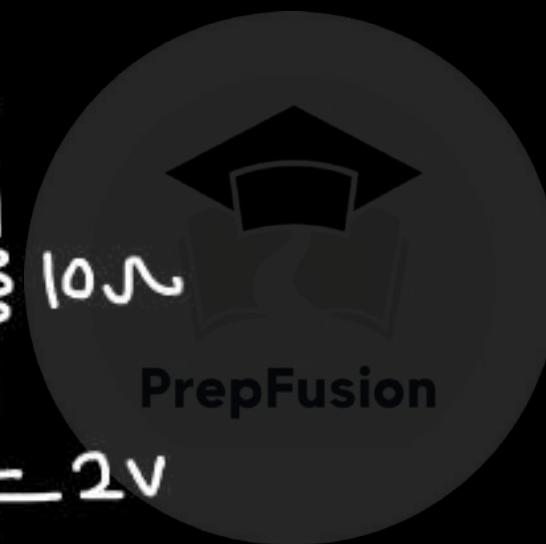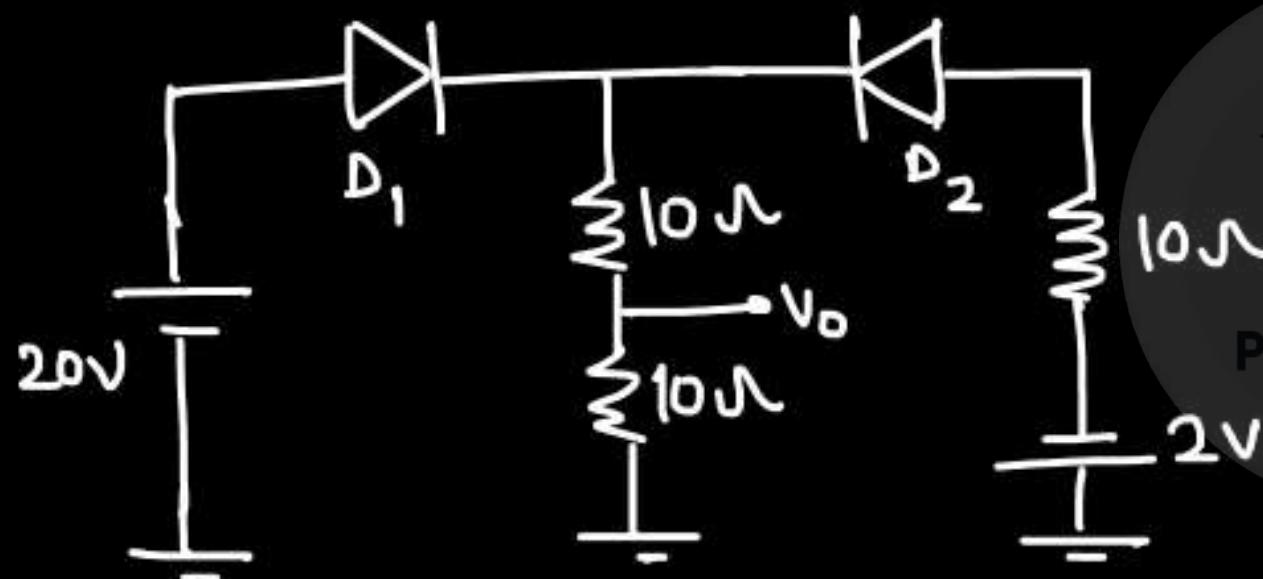



considering D_1 and D_2 to be ideal. Find V_o .

Applying O.C. Test -

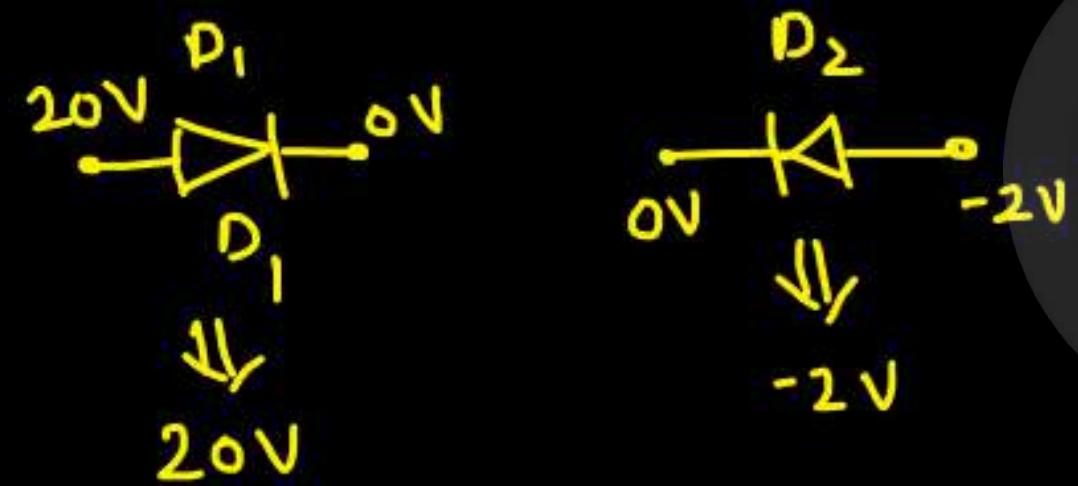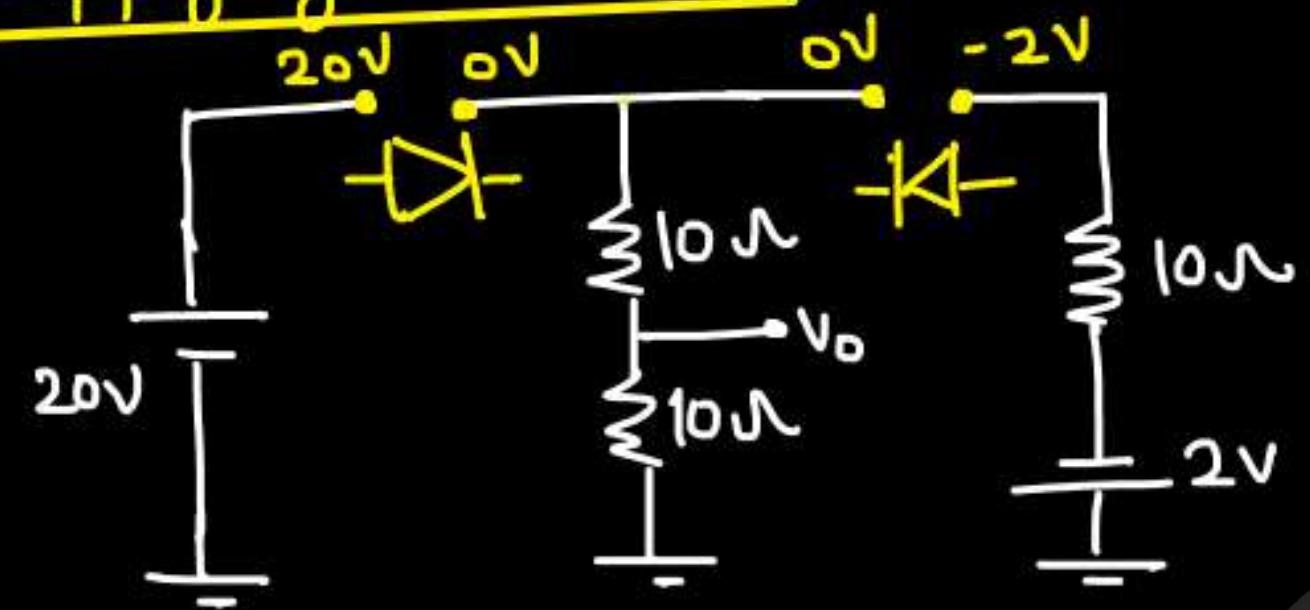




$$\Rightarrow D_1 \rightarrow 0\text{V}$$

$$D_2 \rightarrow 0\text{FF}$$

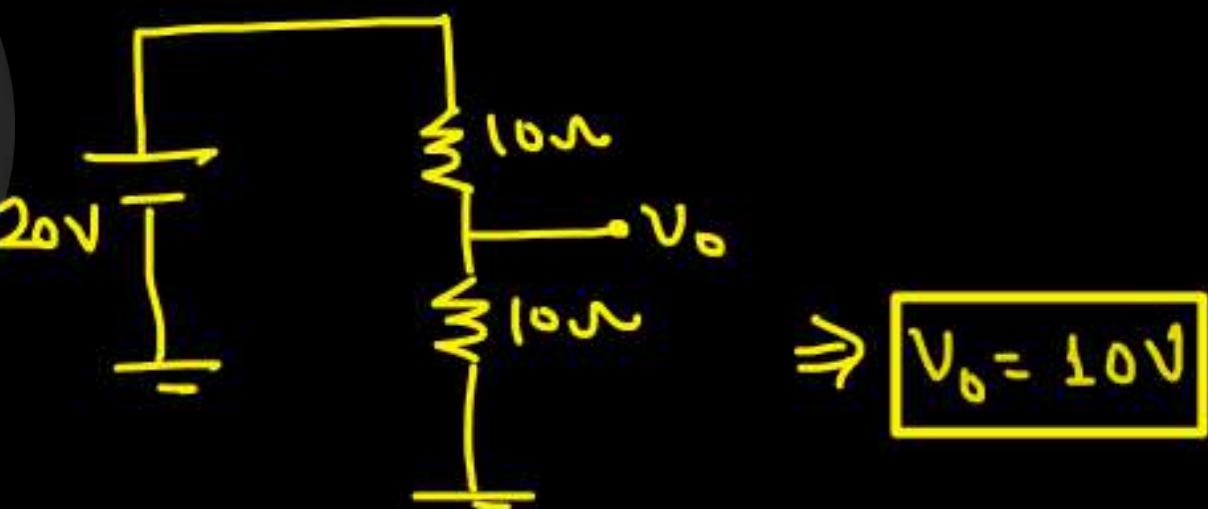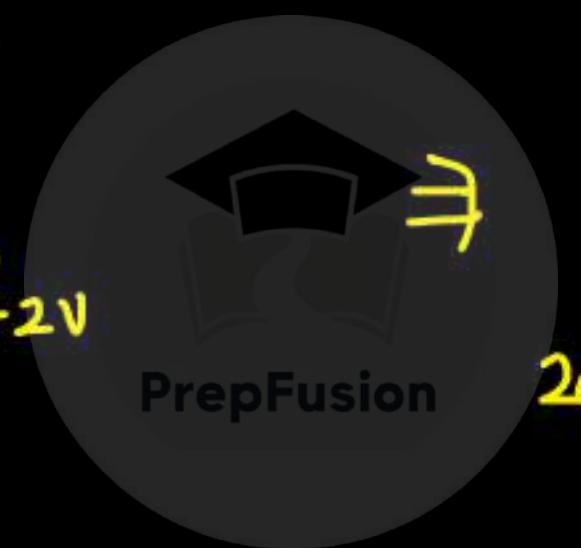


$$\Rightarrow V_o = 10\text{V}$$

Q. Apply O.C. Test to find V_o .

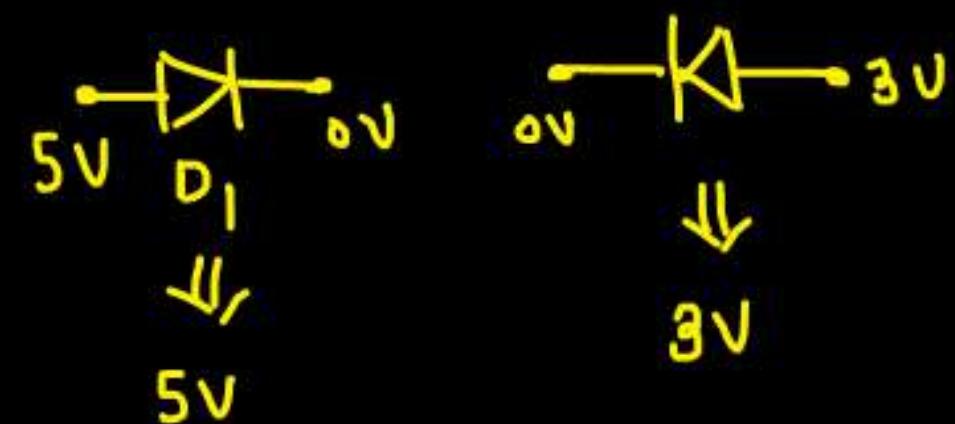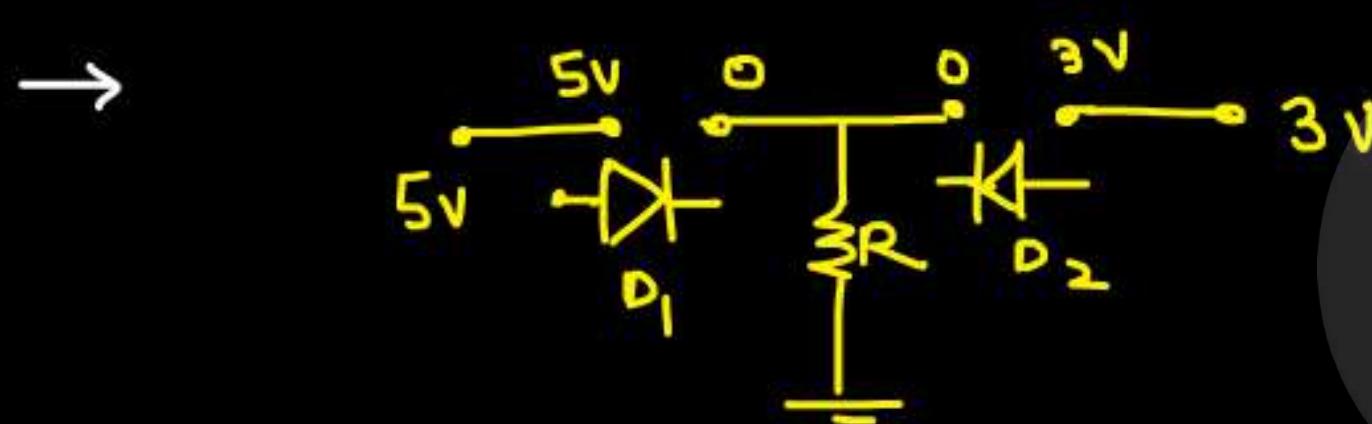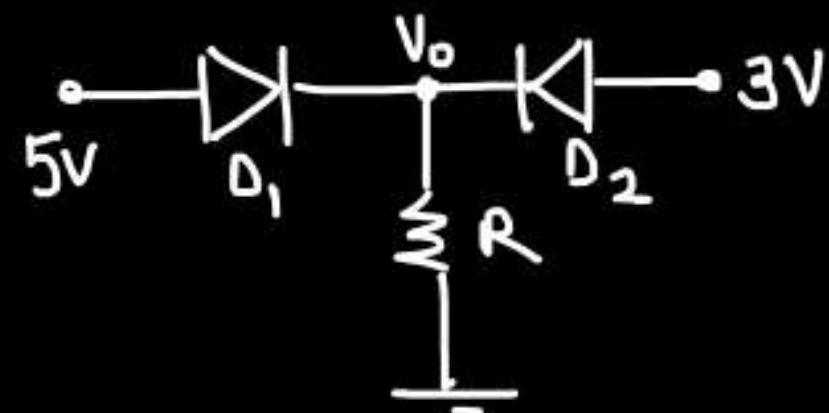


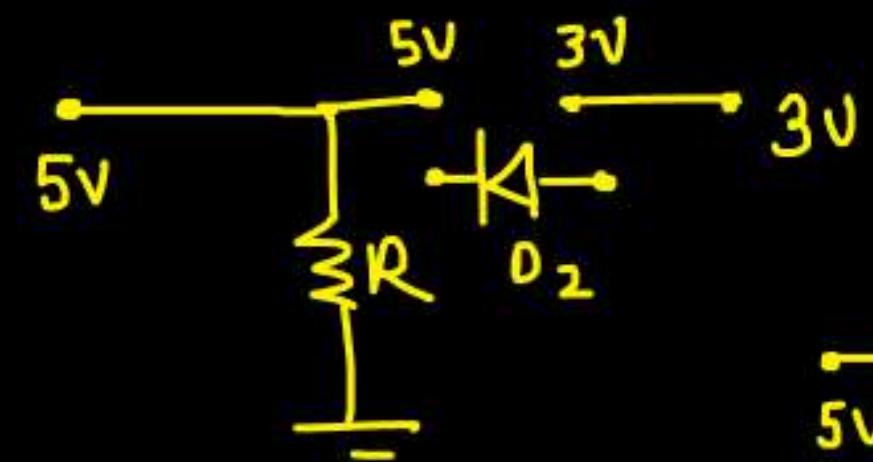⇒ Both diode can be ON. since diode D_1 is having more potential in forward dirn (from P to n) ⇒ I will turn on diode D_1 first






\Rightarrow diode D_2 is off

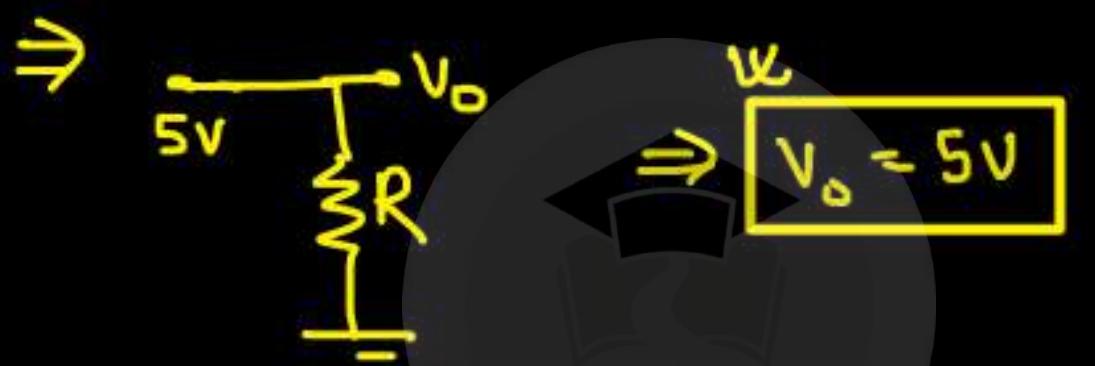


PrepFusion

$$\boxed{V_o = 5V}$$

Q. find V_o .

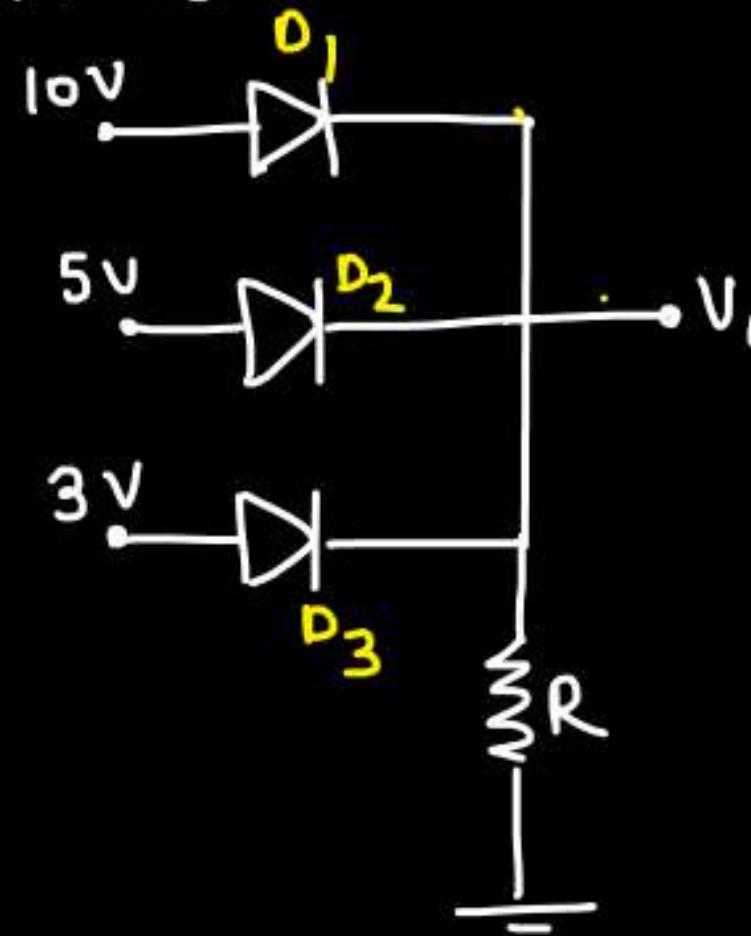

⇒ O.C. Test

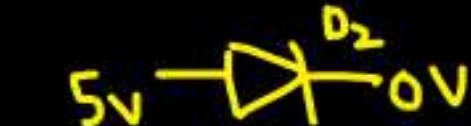


⇒ D_1 will turn on first

PrepFusion



\leftarrow $5V \xrightarrow{D_2} 10V \Rightarrow \text{off}$

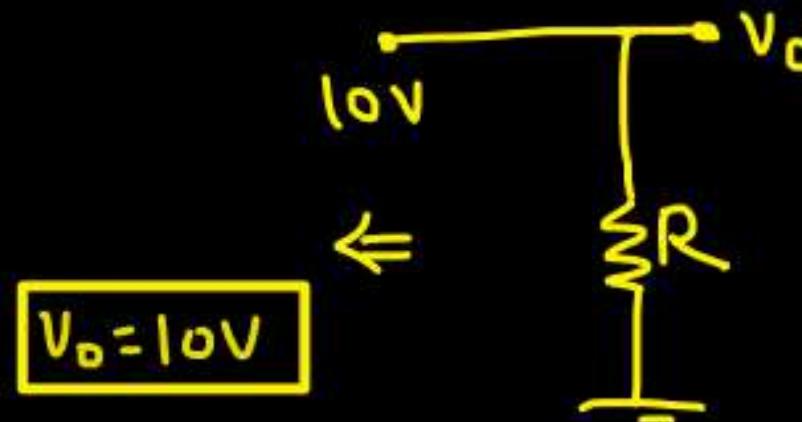$3V \xrightarrow{D_3} 10V \ni \text{off}$



Operating Point:-

Q. Solve the following eqn.


$$y = x + 5$$

$$y = -x + 1$$




$$y = 3$$

$$x = -2$$

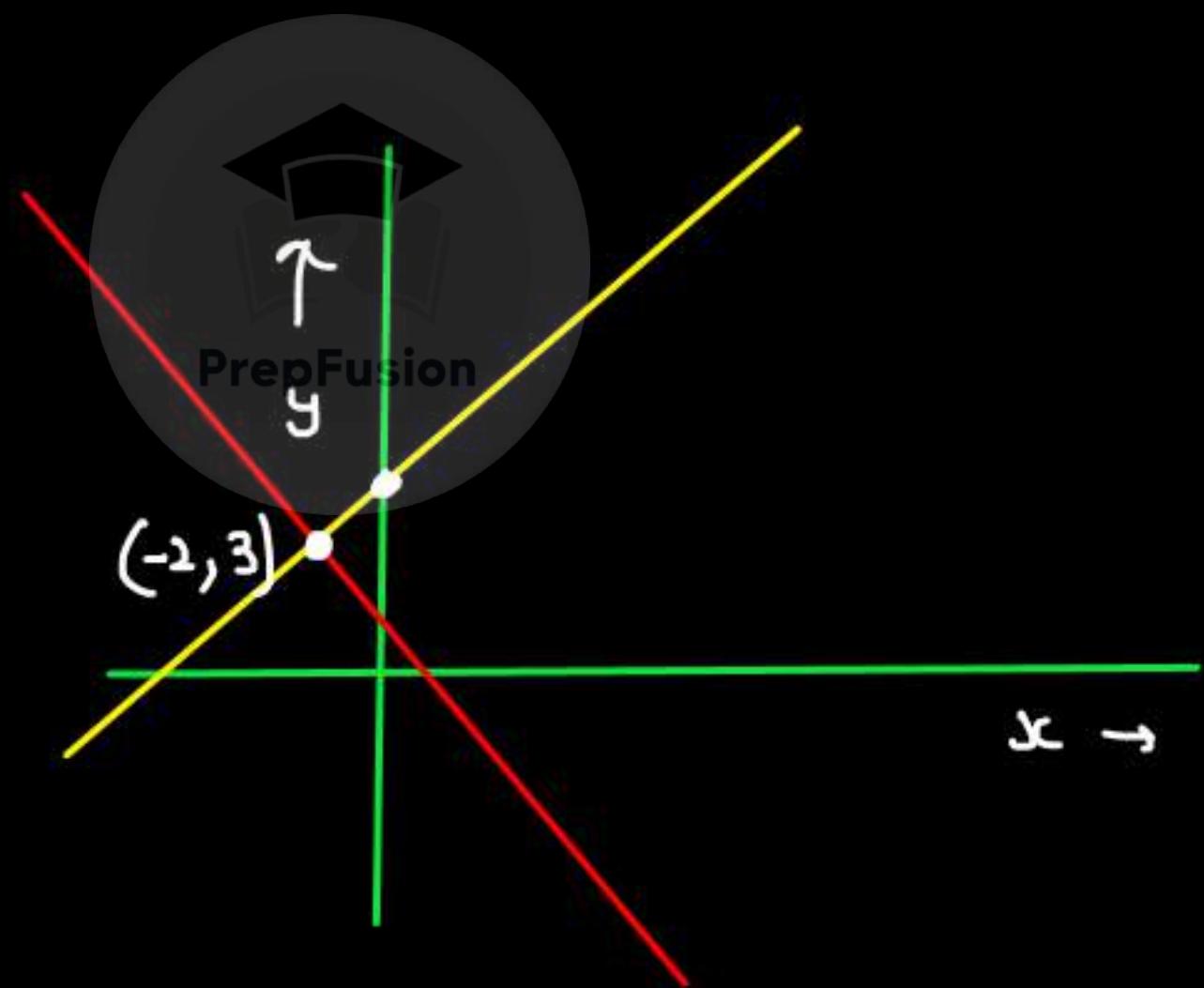

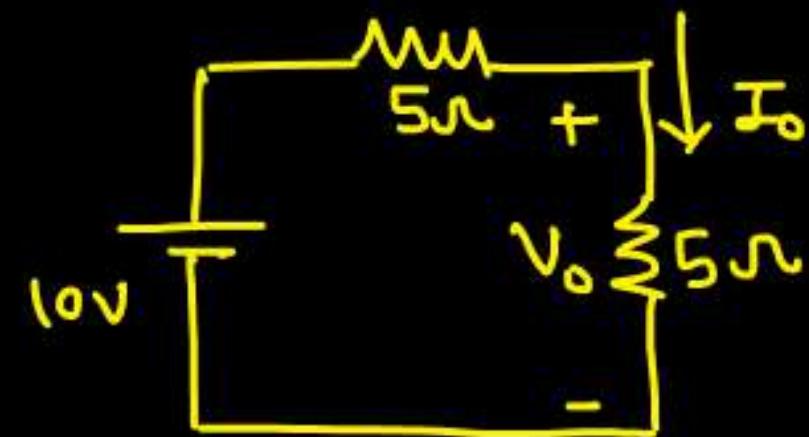Q. Find the operating point V_o and I_o .




$$\rightarrow V_o = 5I_o - \textcircled{1} \quad \text{v}$$

$$10 - V_o = 5I_o$$


$$V_o = -5I_o + 10 - \textcircled{2} \quad \text{v}$$

$$\Rightarrow \boxed{V_o = 5V \\ I_o = 1 \text{ Amp.}}$$

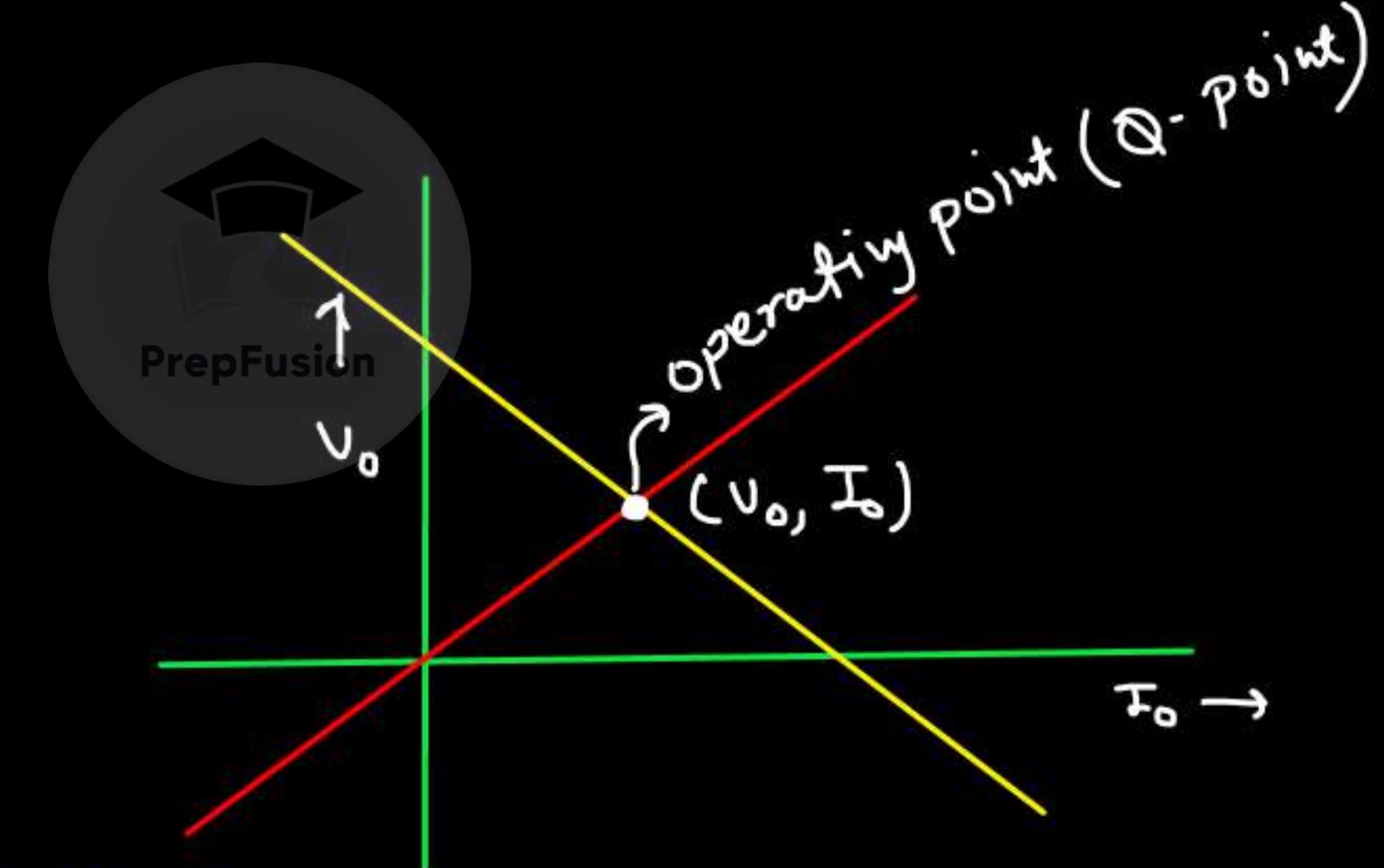↳ Your ckt is running @ $V_o = 5V$, $I_o = 1 \text{ Amp.}$



→ Operating point of a diode :-


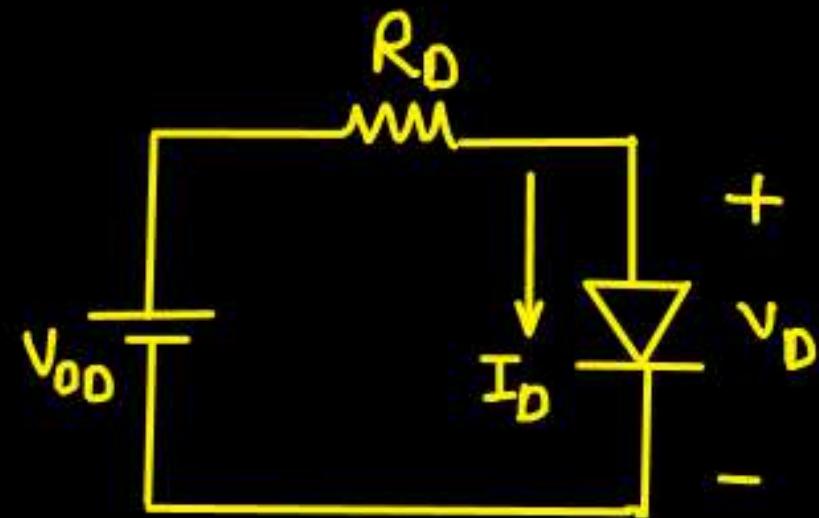


$$I_D = I_S e^{V_D/nV_T} \quad \text{--- (1)}$$

$$V_{DD} - V_D = I_D R_D$$

$$I_D = \left(-\frac{1}{R_D}\right)V_D + \frac{V_{DD}}{R_D} \quad \text{--- (2)}$$



↳ Load line

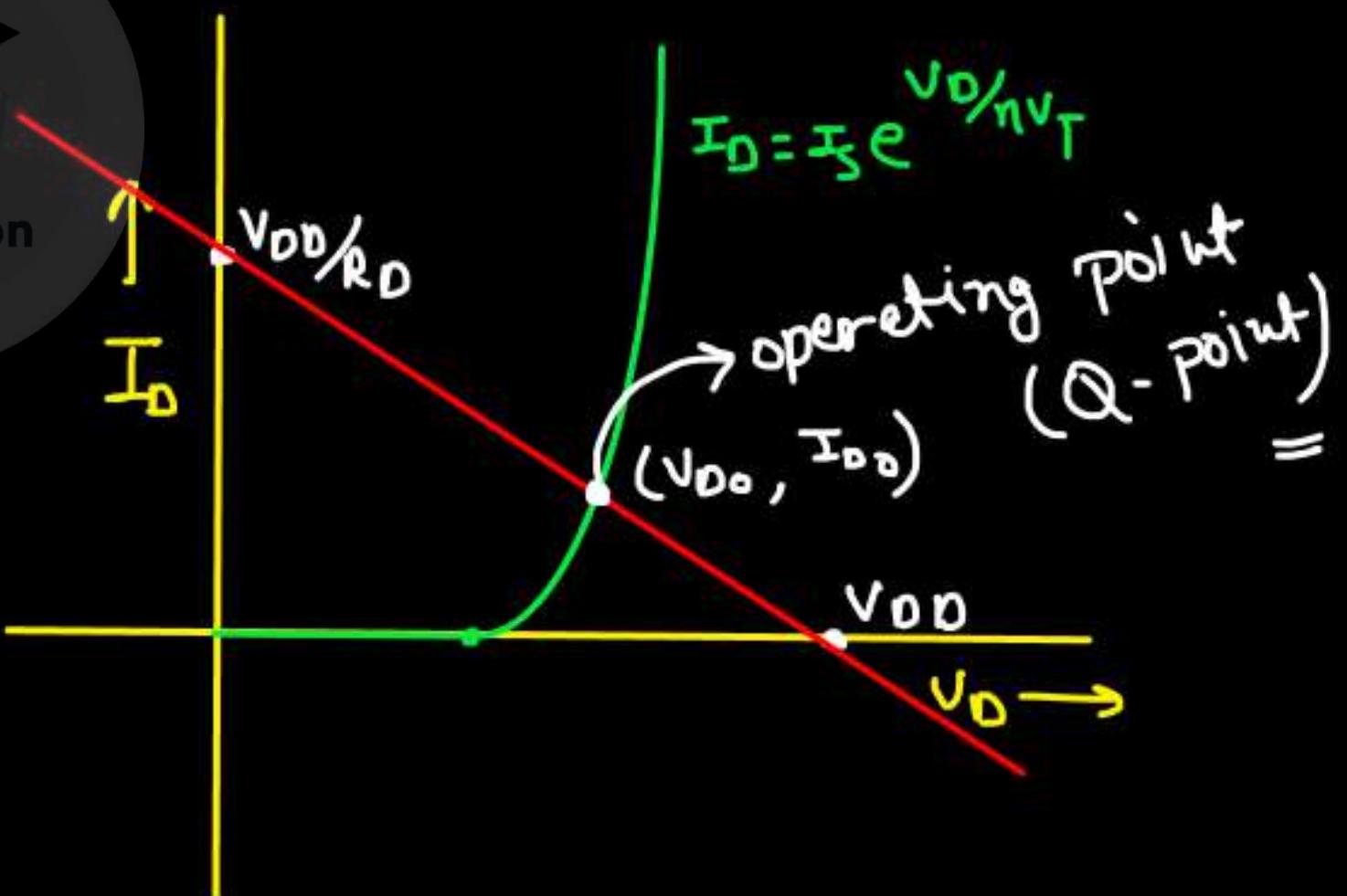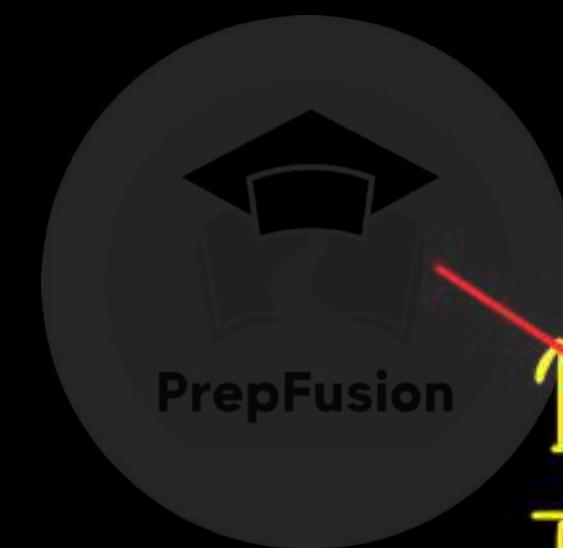

Solving exponential eqⁿ is a tough task.

To make the calculation easy, we came up with the different models of diode



① Ideal

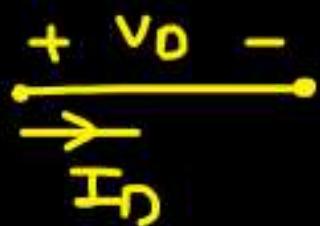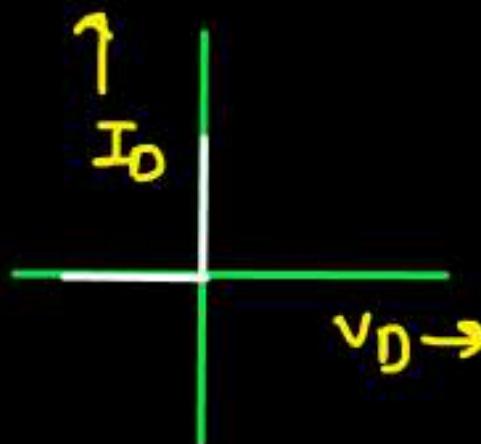

$$V_D = 0$$

I_D = any value


② Constant voltage drop

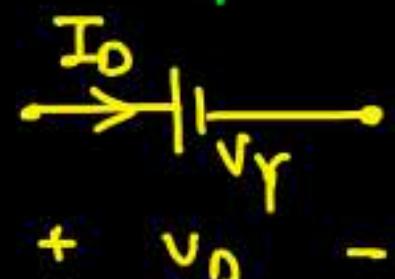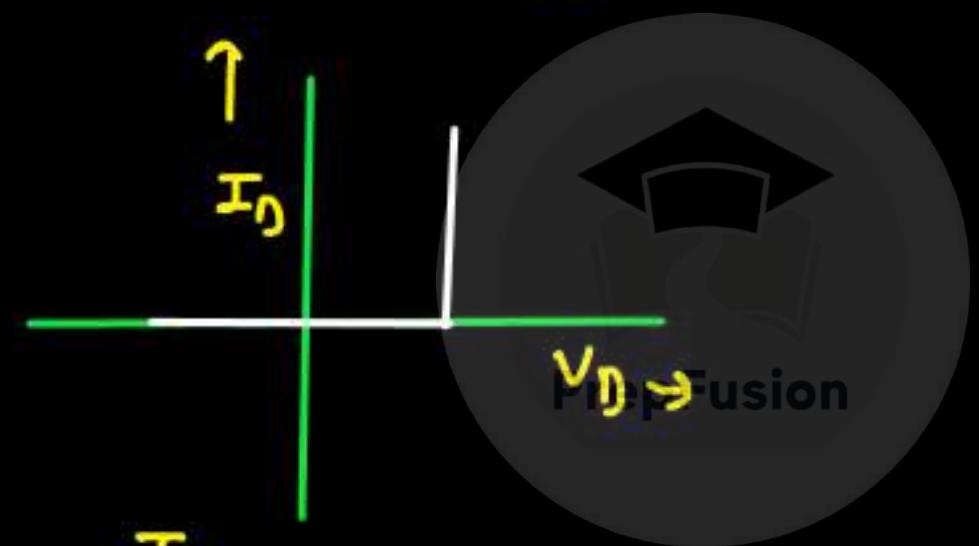

$$V_D = V_Y$$

I_D = any value


③ Piecewise Linear

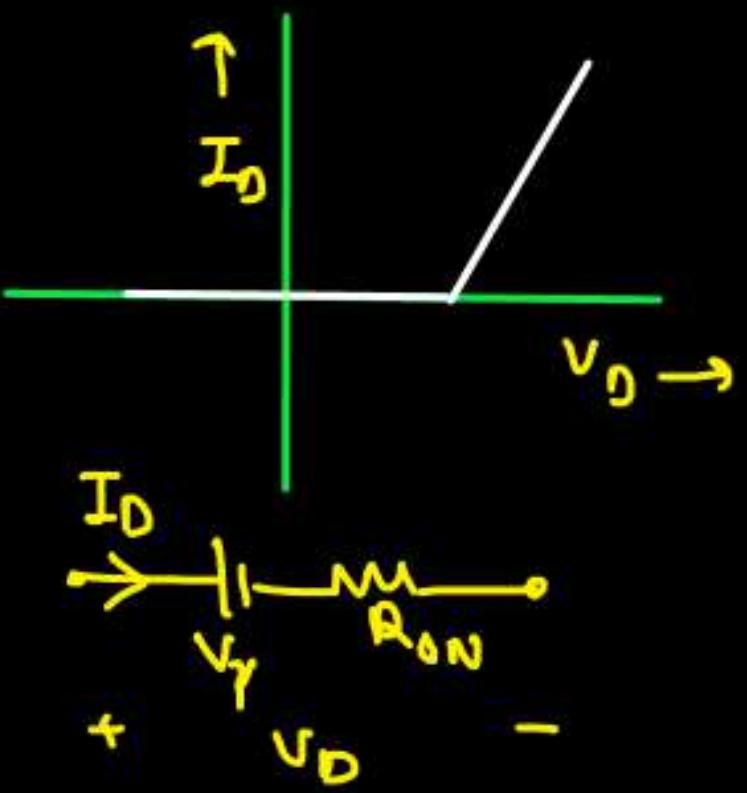

$$\Rightarrow V_D = V_Y + I_D R_{DON}$$


↳ Linear relation

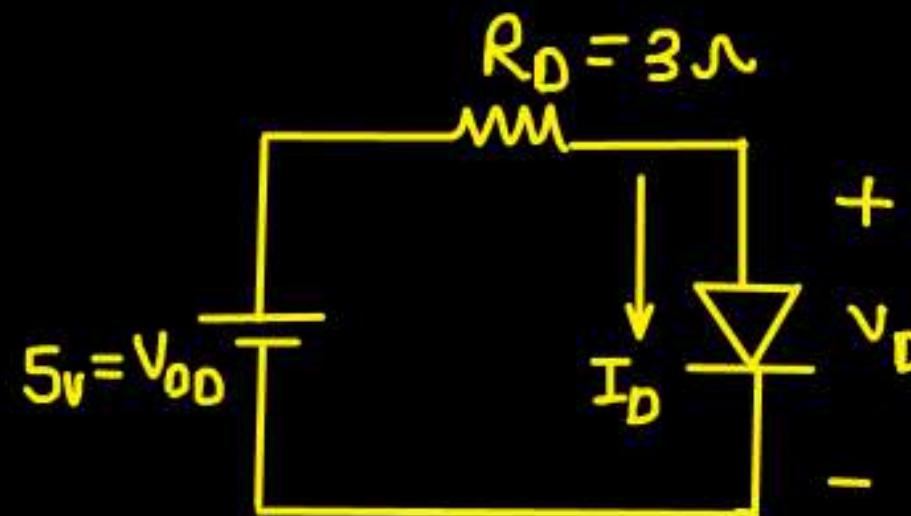* Let's solve this ckt with piecewise linear model :-



Find V_D and I_D ?

→ Solving by ckt

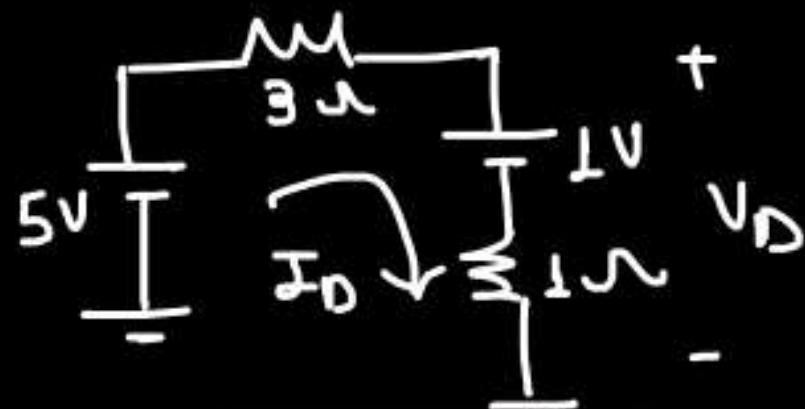

$$I_D \approx 1 \text{ Amp}$$

$$V_D = 2V$$

Take $V_{DD} = 5V$

$$R_D = 3\Omega$$

$$V_\gamma = 1V$$

$$R_{DN} = 1\Omega$$

PrepFusion $\Rightarrow V_D = V_\gamma + I_D R_{DN}$

$$V_D = 1 + I_D$$


$$I_D = V_D - 1$$

$$5 - V_D = 3 I_D$$

$$I_D = -\frac{V_D}{3} + \frac{5}{3}$$


solve these eqn

$V_D = 2V$
$I_D = 1A$

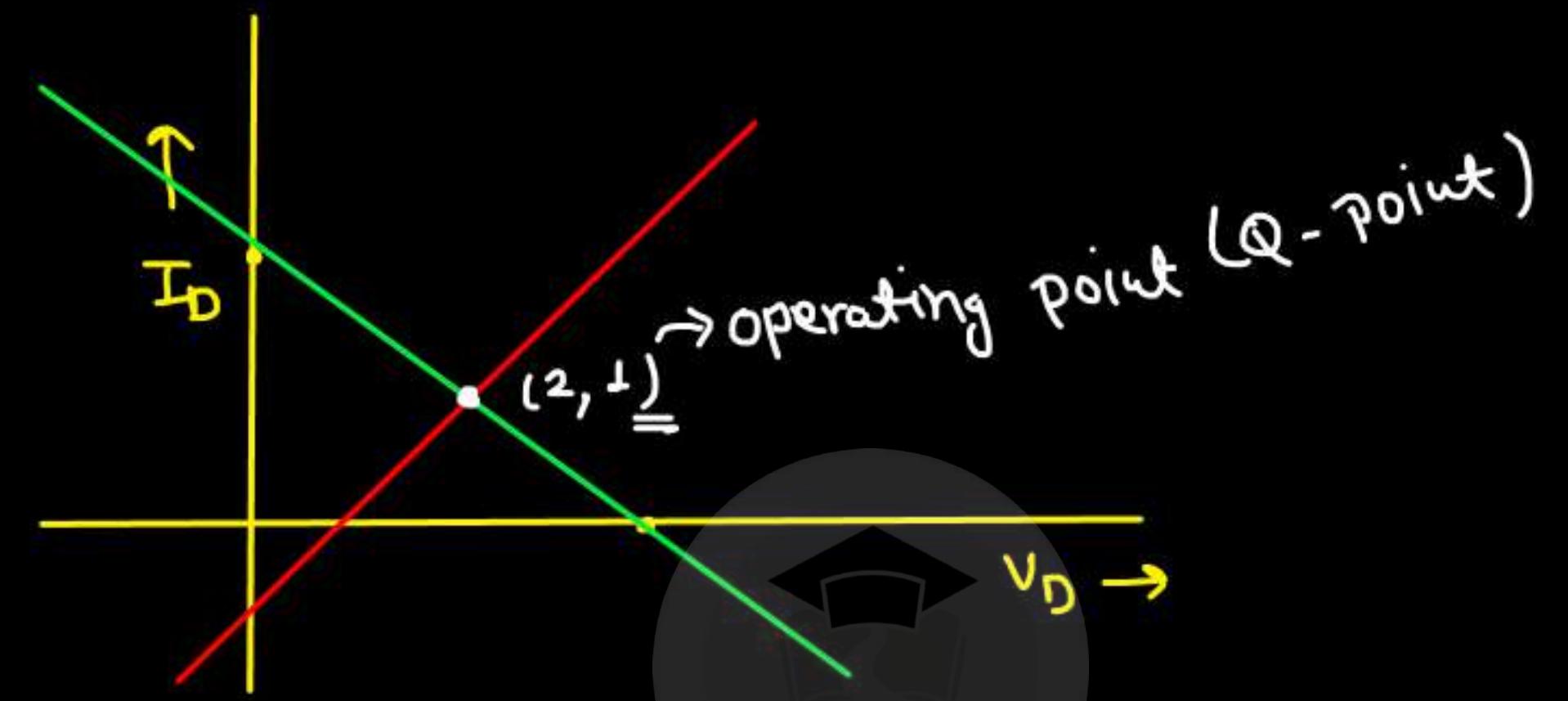


⇒ Small Signal Analysis of Diode:-

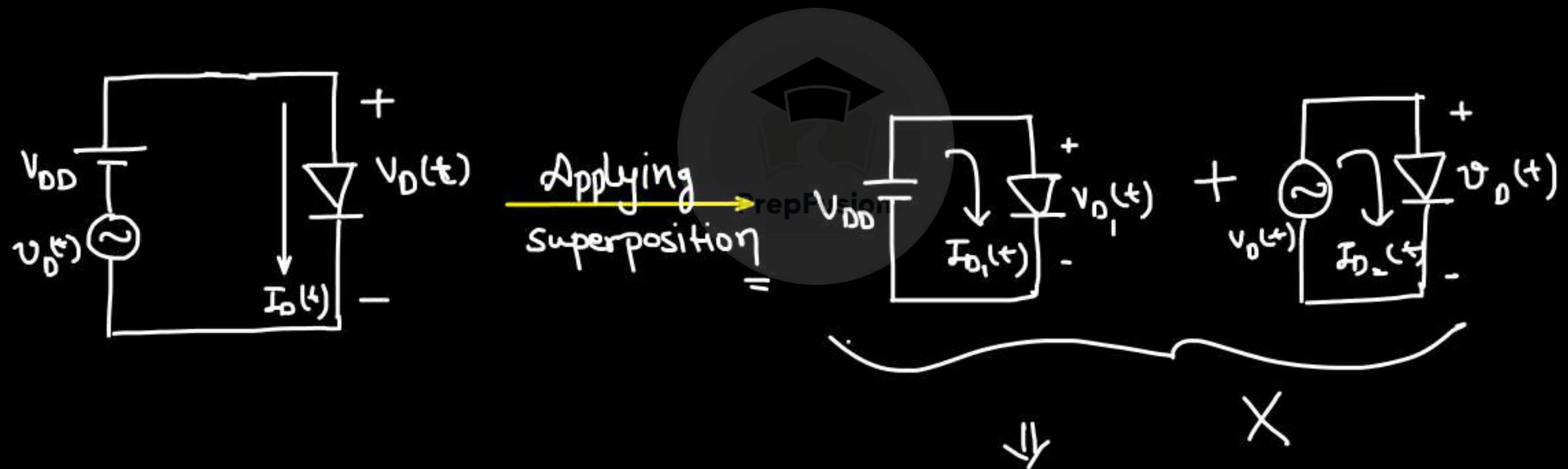↳ Small Signal :- Input signal with very small amplitude. (Typically in mV)



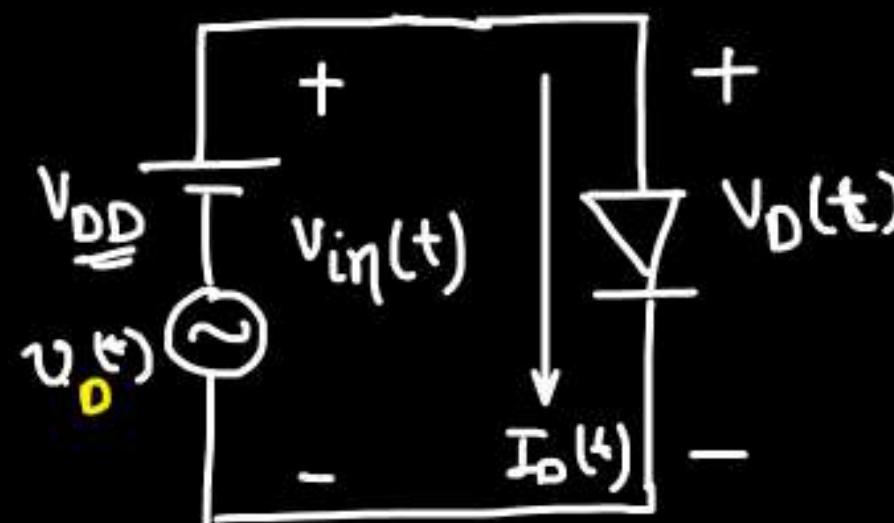
Superposition is only applicable for linear bilateral elements.



$$\Rightarrow V_{in}(t) = V_{DD} + V_D(t)$$

$\left\{ \begin{array}{l} V_{DD} \text{ is chosen such that} \\ \text{the diode is ON.} \end{array} \right\}$
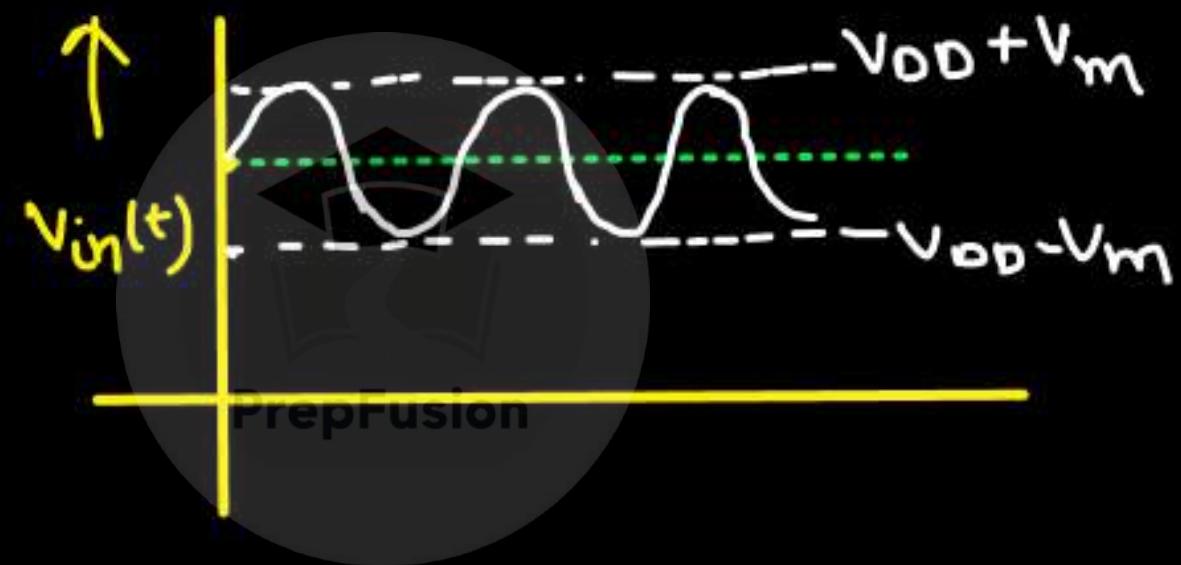
$$\text{let } V_D(t) = V_m \sin \omega t$$



Now let's find $I_D(t)$:-

$$I_D(t) = I_S e^{\frac{V_D(t)}{nV_T}}$$

$$= I_S e^{\frac{V_{DD} + V_D(t)}{nV_T}}$$

$$= I_S e^{\frac{V_{DD}}{nV_T}} \cdot e^{\frac{V_D(t)}{nV_T}}$$

$$= I_S e^{\frac{V_{DD}}{nV_T}} \left[1 + \frac{V_D(t)}{nV_T} \right] \left\{ \begin{array}{l} \frac{V_D(t)}{nV_T} \ll 1 \\ \text{Because } V_D(t) \text{ is small} \end{array} \right\}$$

$$= \underbrace{I_{DC}}_{\downarrow} \left[1 + \frac{V_D(t)}{nV_T} \right]$$

dc current of diode

$$I_D(t) = I_{DC} + \frac{I_{DC}}{nV_T} V_D(t)$$

$$I_D(t) = I_{DC} + i_a(t)$$

↓ ↓
 dc current ac current

$$i_{ac}(t) = \frac{I_{DC}}{nV_T} \times u_D(t)$$


↓ ↓
 small signal small signal
 ac current ac voltage

$$\frac{u_D(t)}{i_{ac}(t)} = r_d = \frac{\text{PrepFusion small signal}}{\text{ac resistance}} = \frac{nV_T}{I_{DC}}$$


(dynamic resistance)

$$r_d = \frac{nV_T}{I_{DC}}$$

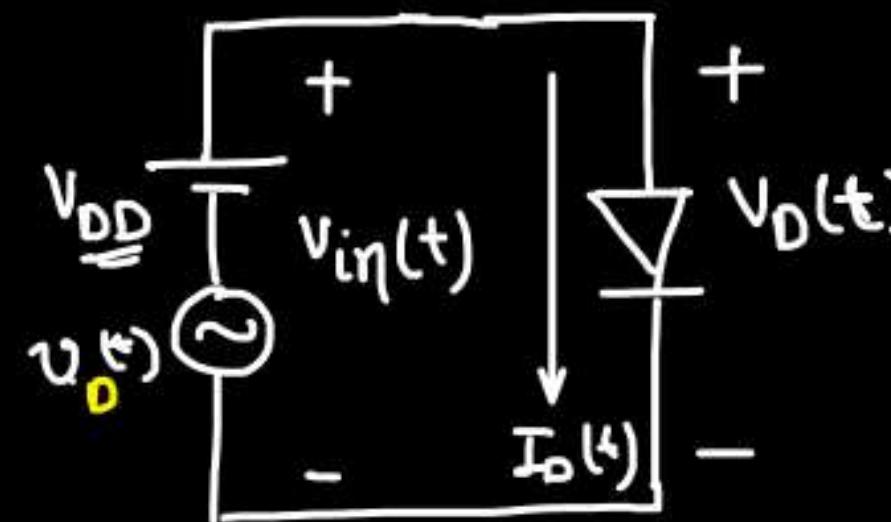$\Rightarrow n$ = non-ideality factor
 V_T = Thermal Voltage
 I_{DC} = DC current of diode




\rightarrow DC analysis

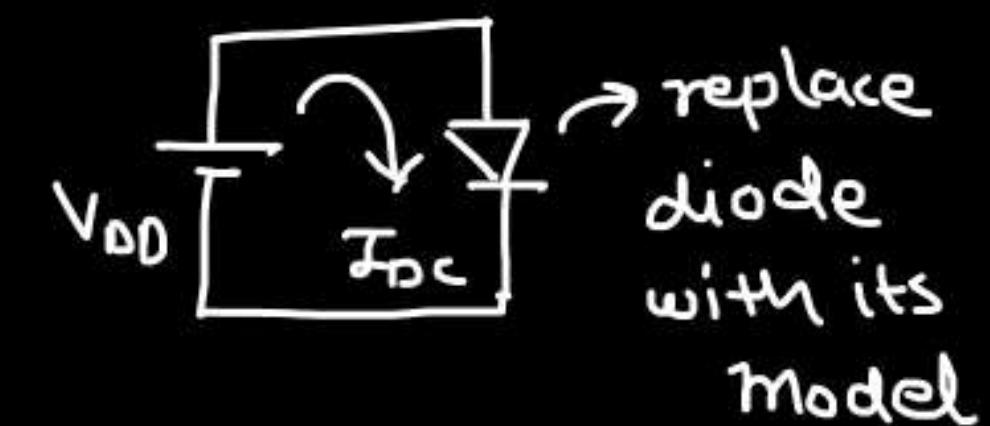

→ replace
diode
with its
model



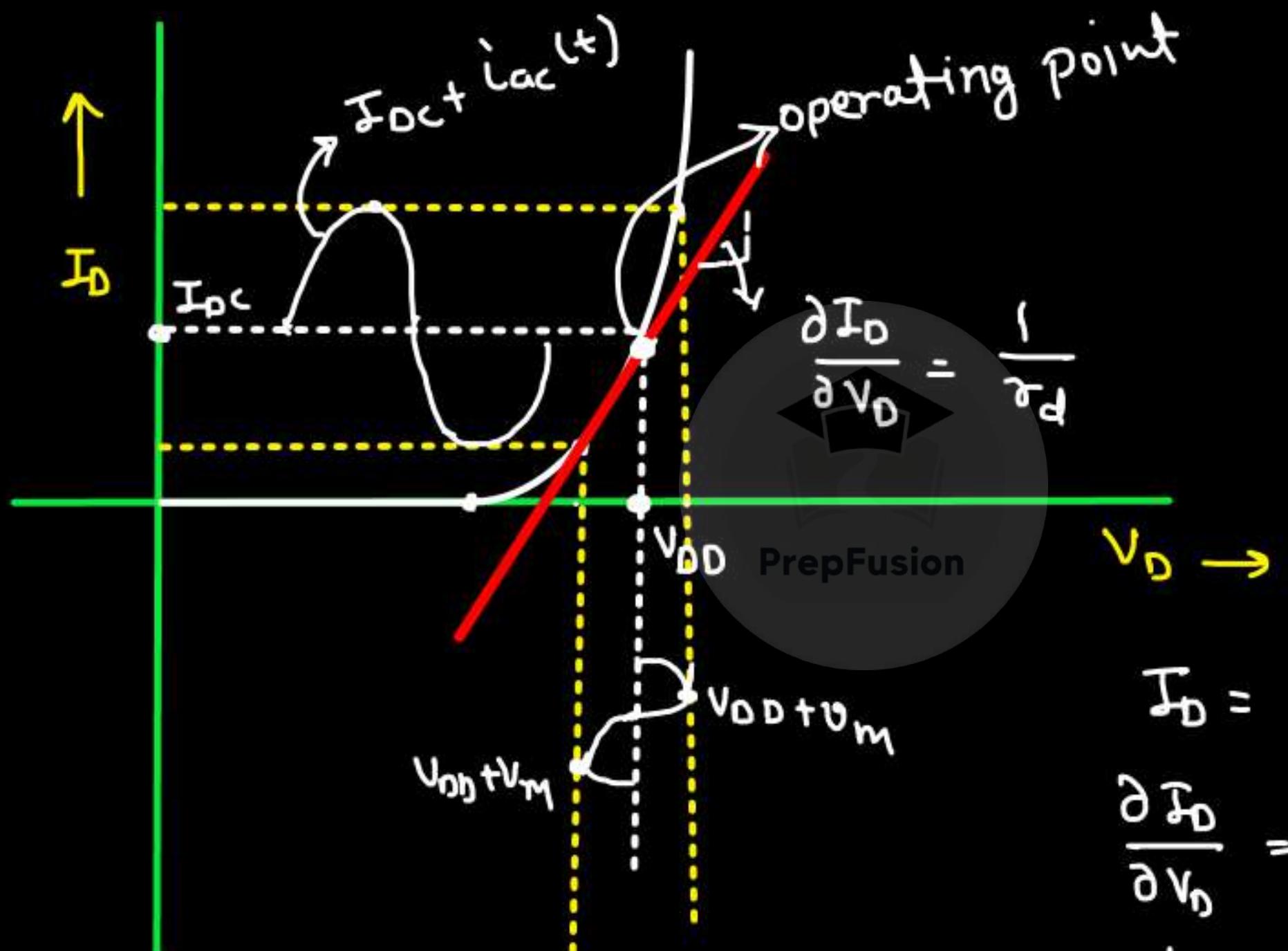Let's understand this with graphical presentation:-



$$v_q(t) = \gamma_q i_{q_c}(t)$$

$$V_{in}(t) = V_{DD} + v_q(t)$$

$$v_D(t) = V_{DD} + v_m \sin \omega t$$


$$I_D = I_s e^{\frac{V_D}{nV_T}}$$

$$\frac{\partial I_D}{\partial V_D} = \frac{I_s e^{\frac{V_D}{nV_T}}}{nV_T} = \frac{I_{DC}}{nV_T}$$

$$\frac{1}{\tau_d} = \frac{I_{DC}}{nV_T} \Rightarrow \gamma_d = \frac{nV_T}{I_{DC}}$$

Conclusion :-

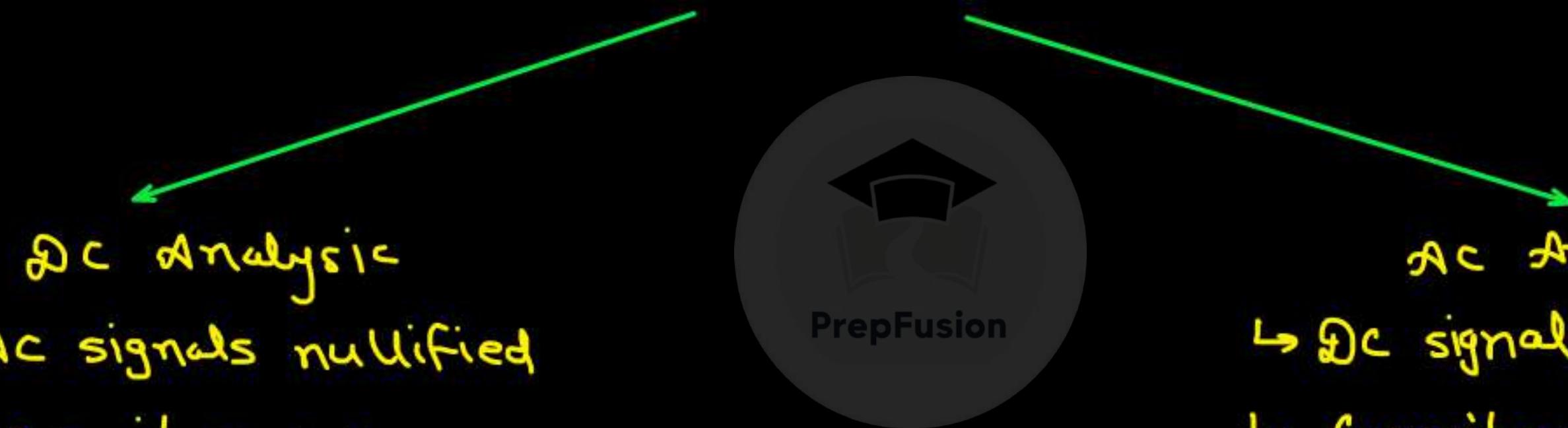
↳ Applied input $V_{in}(t) = \underbrace{V_{DD}}_{\text{DC signal}} + \underbrace{V_{in}(t)}_{\text{AC signal}}$




- ↳ DC analysis
- ↳ AC signals nullified
- ↳ Capacitor o.c.
- ↳ Diode replaced with its dc equivalent

- ↳ AC analysis
- ↳ DC signals nullified.
- ↳ Capacitor s.c.
- ↳ Diode replaced with dynamic resistance (r_d)

DC Equivalent of diode :-

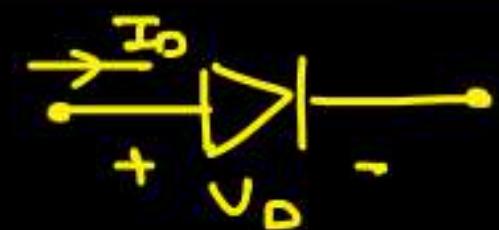


when
ON

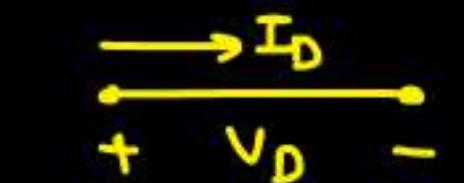



$\frac{I_D}{V_D}$

OR

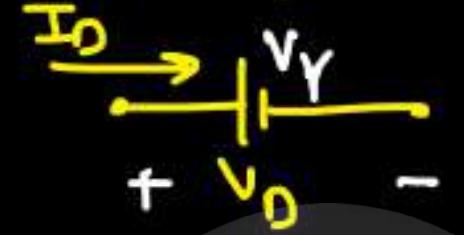

$\frac{I_D}{V_D}$

OR

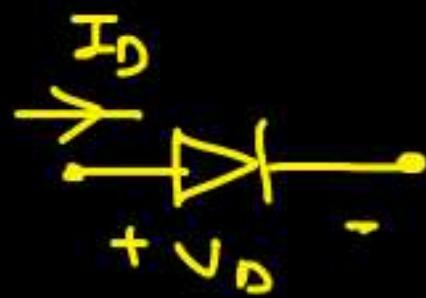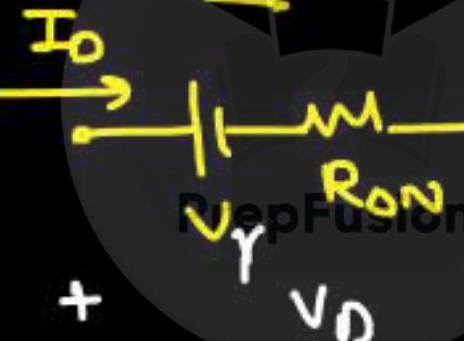

when
OFF



AC Equivalent of diode :-

$$\text{Dynamic resistance } (r_d) = \frac{nV_T}{I_{DC}}$$

↳ When diode is ON (in dc analysis) :-



↳ When diode is OFF (in dc analysis) :-




$$r_d = \frac{nV_T}{I_{DC}} = \frac{nV_T}{0} = \infty$$

$r_d \in [0, \infty)$

Question :-

Q. L

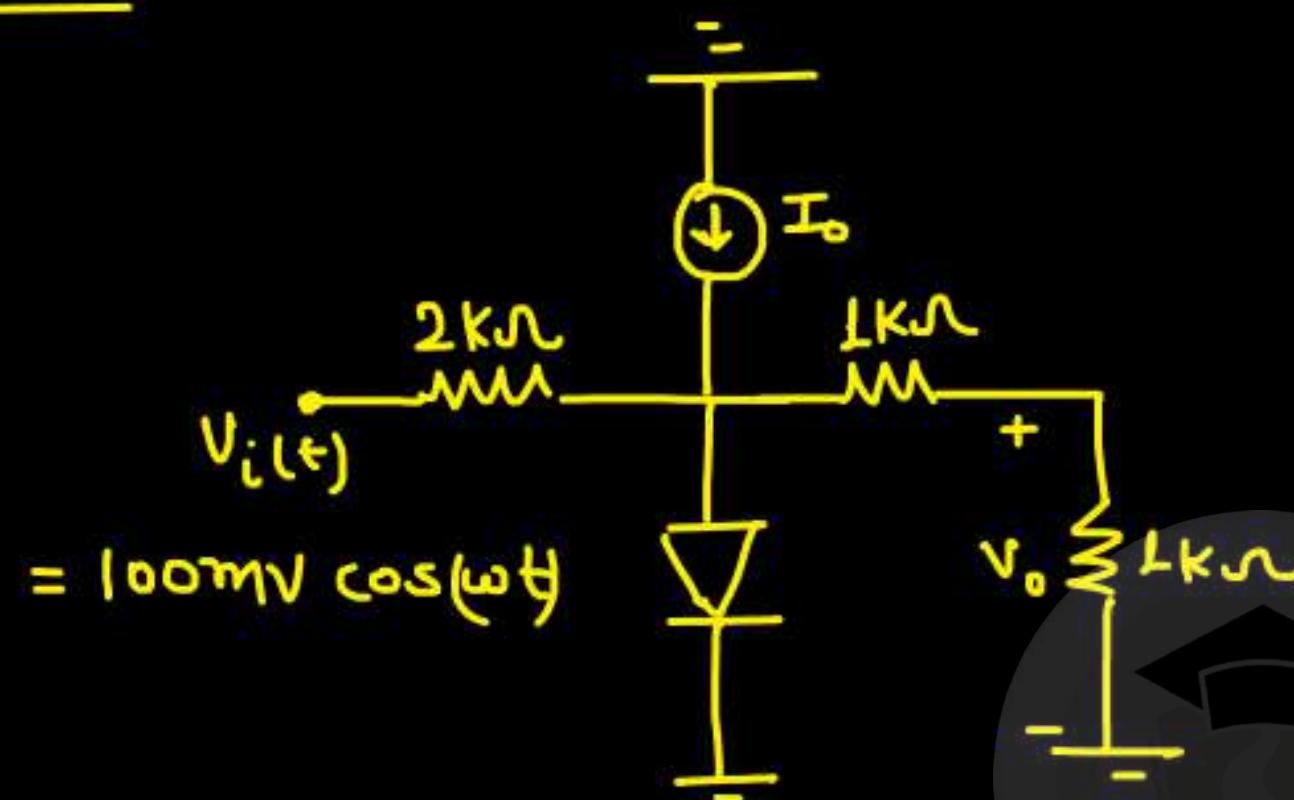

Voltage source \rightarrow S.C.

Current source \rightarrow D.C.

determine the amplitude of sinusoid component of v_o if

- (i) $I_o = 2.7 \text{ mA}$
- (ii) $I_o = -2.7 \text{ mA}$


Cut-in voltage of diode is 0.7 V .

Take $V_T = 25 \text{ mV}$



$$(i) I_D = 2.7 \text{ mA}$$

dc analysis:-

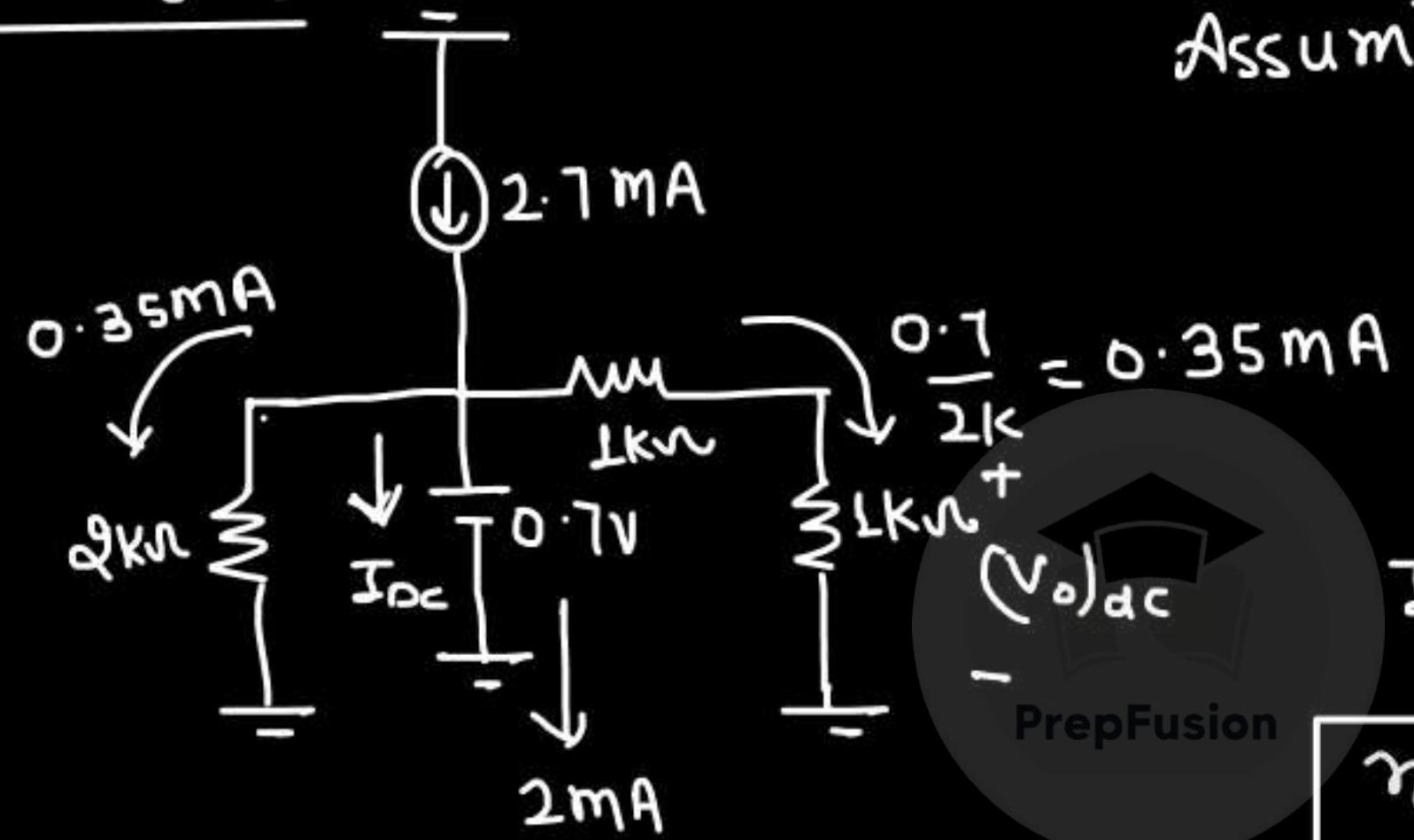


$$I_{DC} = 2 \text{ mA}$$

$$\gamma_q = \frac{\eta V_T}{I_{DC}} = \frac{25 \text{ mV}}{2 \text{ mA}} = 12.5 \text{ n}$$

$$(V_o)_{DC} = 0.35 \text{ V}$$

ac analysis:-

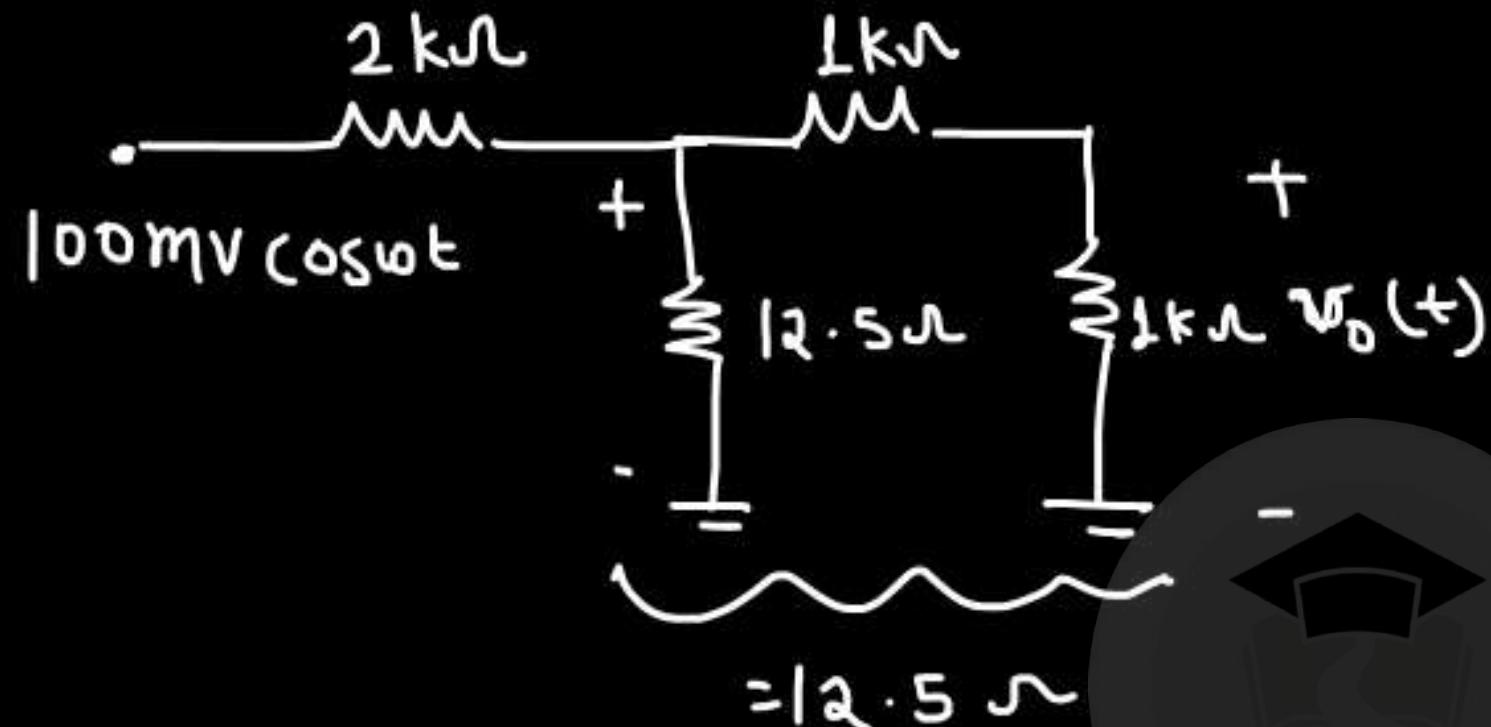


$$V_o(t) = \frac{12.5}{2012.5} \times \frac{1}{2} \times 100mV \cos\omega t$$

$$V_o(t) = 0.31mV \cos\omega t$$

$$V_o = 0.35V + 0.31mV \cos\omega t \quad \{ dc + ac \}$$



$$(ii) I_0 = -2.7 \text{ mA}$$

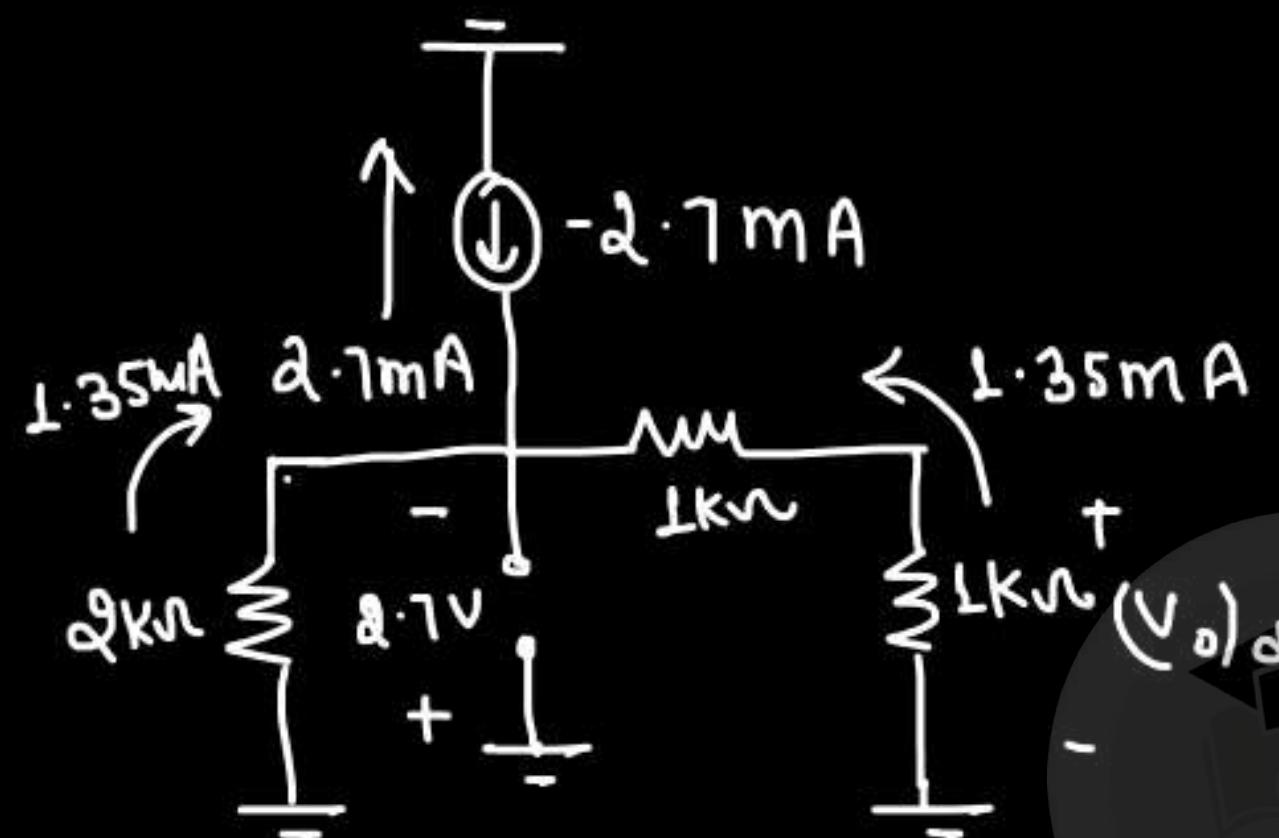

Diode is off


$$I_{DC} = 0 \text{ A.P.}$$

$$r_d = \frac{nV_T}{0} = \infty$$

$$(V_o)_{DC} = -1.35 \text{ V}$$



ac analysis:-

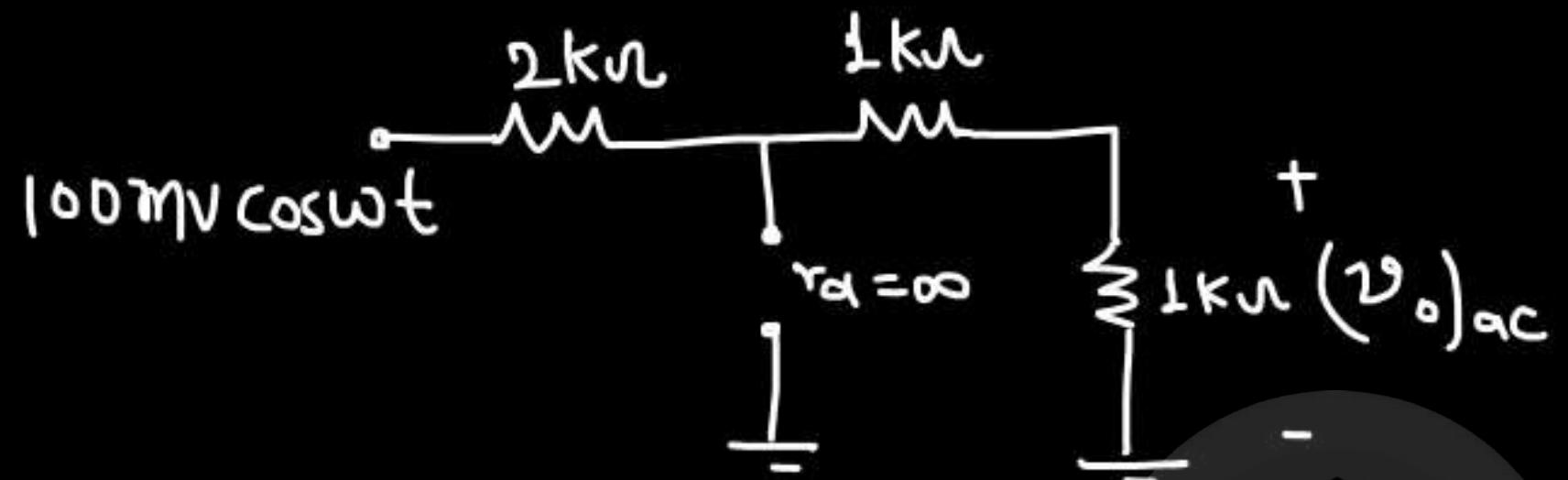


$$(V_o)_{ac} = \frac{1}{4} \times 100mV \cos \omega t$$

$$(V_o)_{ac} = 25 \cos \omega t \text{ mV}$$


$$V_o = -1.35vt + 25 \cos(\omega t) \text{ mV}$$

Q. 'I' is the dc current and v_s is the small signal ac voltage. Cap. C_1 and C_2 are very large. Find V_o if $I = 1 \text{ mA}$

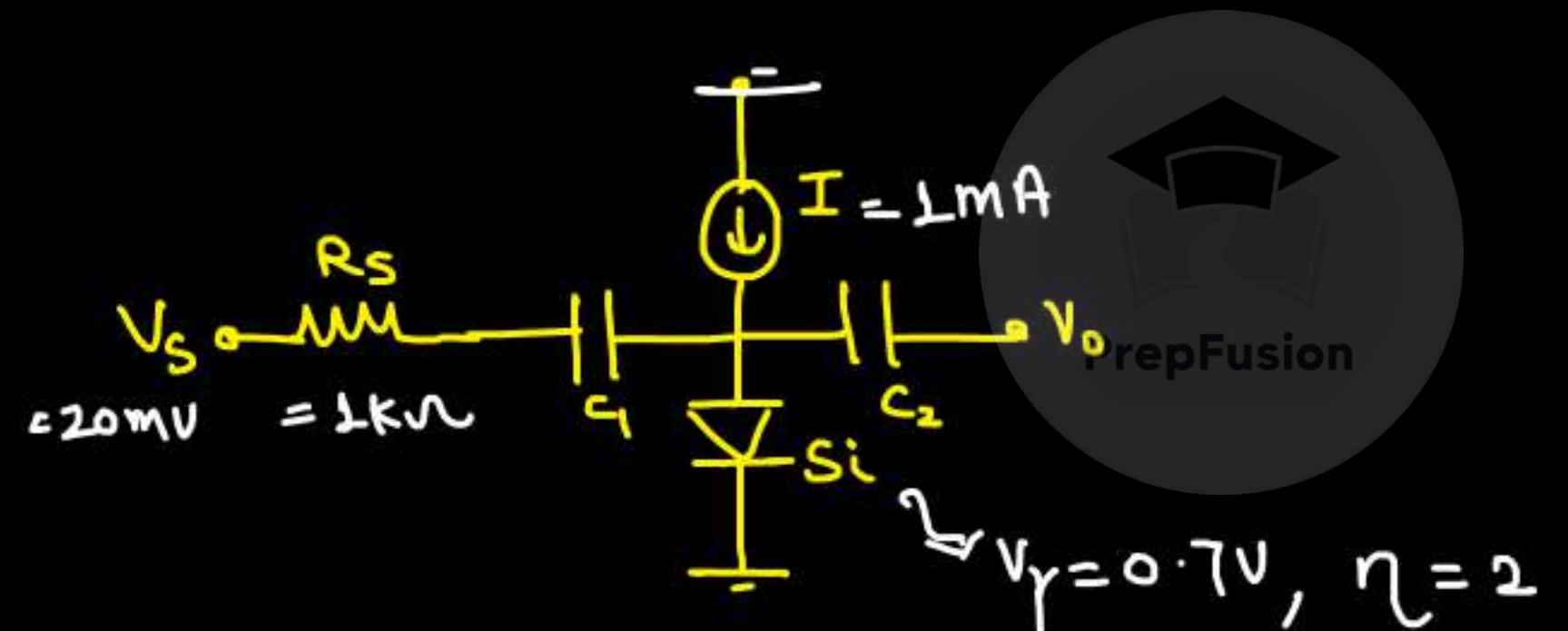Take $V_T = 25 \text{ mV}$, $V_s = 20 \text{ mV}$, $R_s = 1 \text{ k}\Omega$



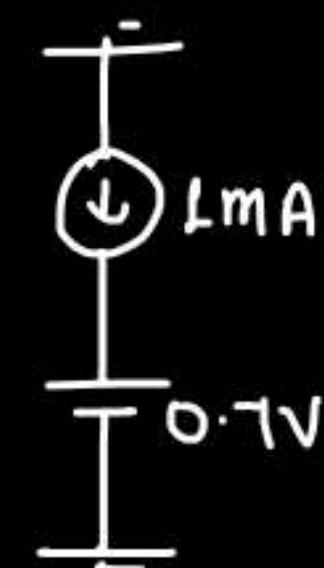→ dc analysis $\Rightarrow C \rightarrow 0 \cdot C$, $V_s \rightarrow 0 \cdot C$




$$I_{DC} = 1 \text{ mA}$$

$$r_d = \frac{nV_T}{I_{DC}}$$

$$= \frac{2(25) \text{ mV}}{1 \text{ mA}} = 50 \Omega$$

$$r_d = 50 \Omega$$

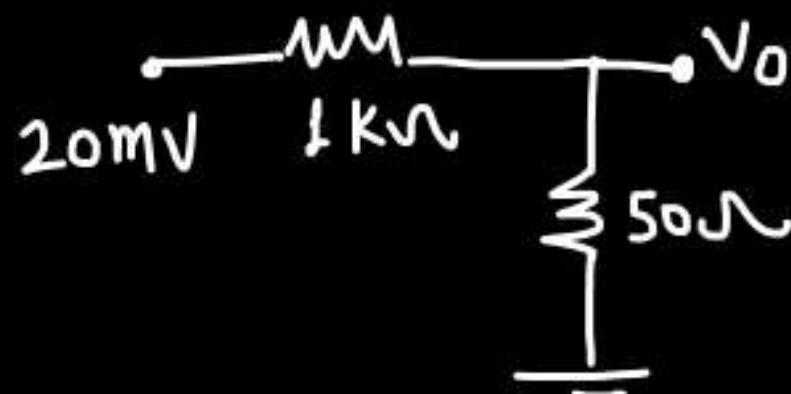
ac analysis: - C \rightarrow S.C., I_o \rightarrow O.C.



$$V_o = \frac{50}{1050} \times 20 \text{ mV}$$


$$V_o = 0.95 \text{ mV} = V_o$$

Q.

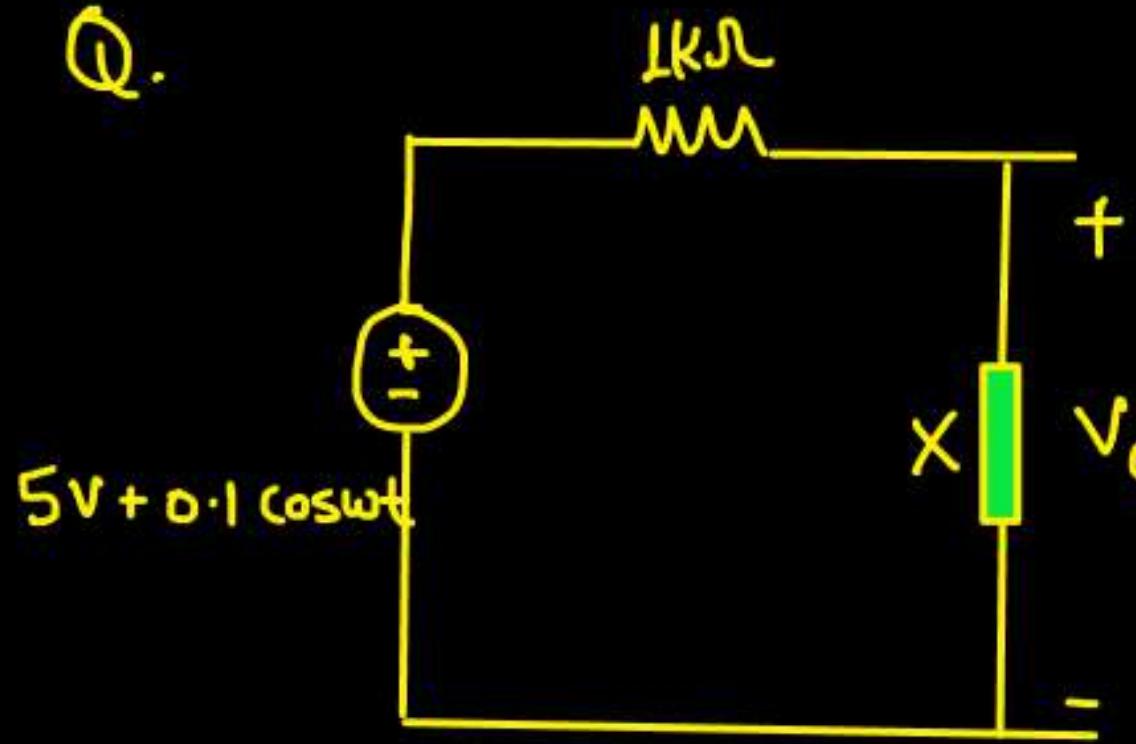


In the circuit, there is a non-linear element X is connected. The $I-V'$ characteristic of the element is shown. Determine

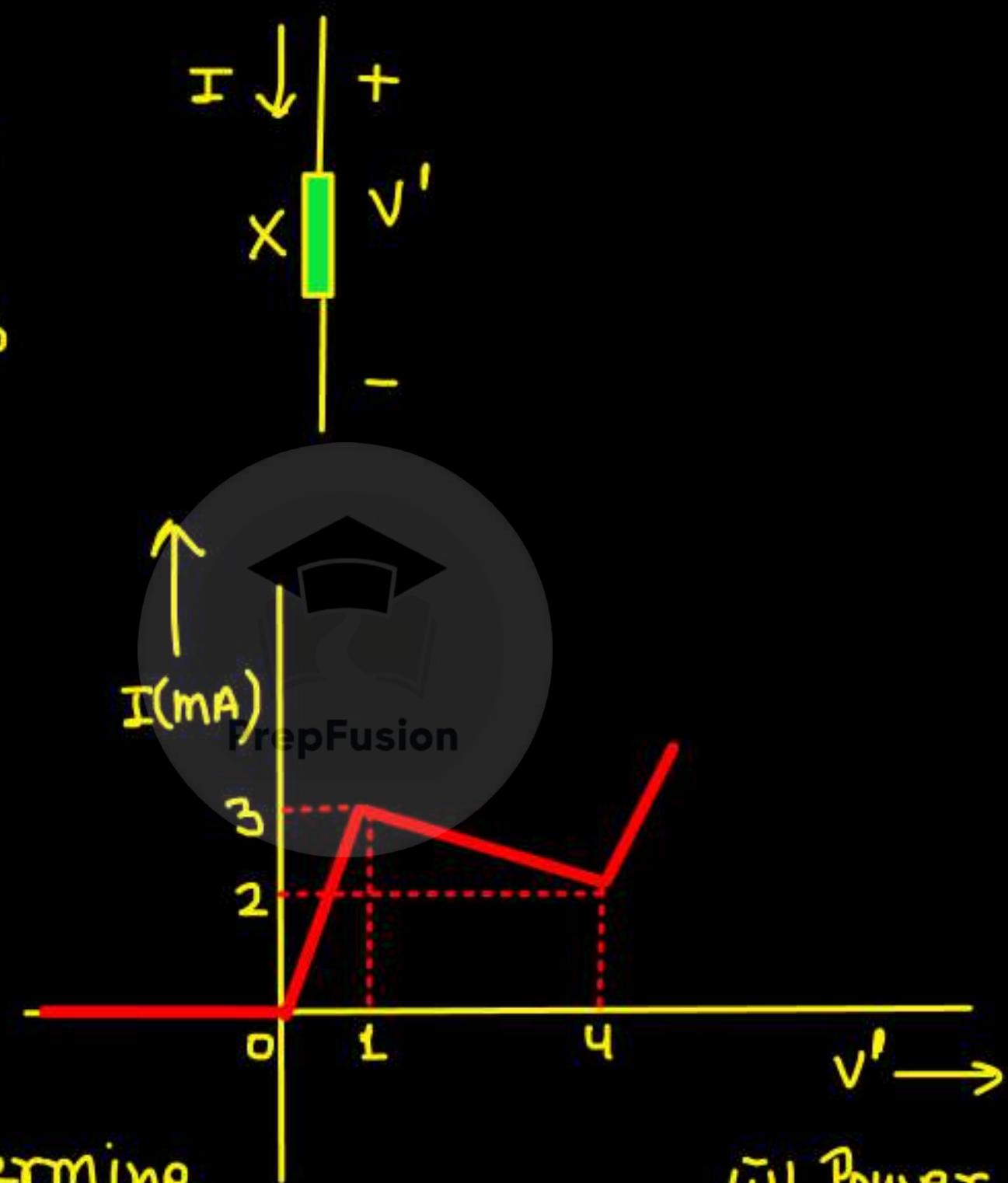(i) The amplitude of sinusoidal component of V_o .






- (ii) Power dissipated in the non-linear element @ the operation point.

(ii) op^r point → dc analysis

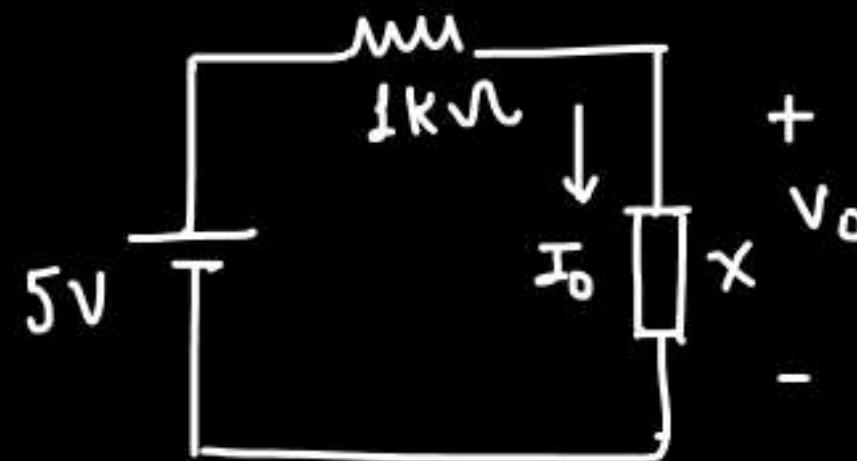

$$5 - V_o = 1k(I_o)$$

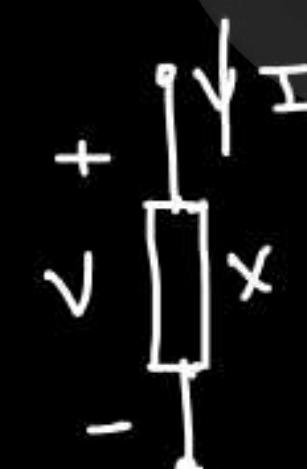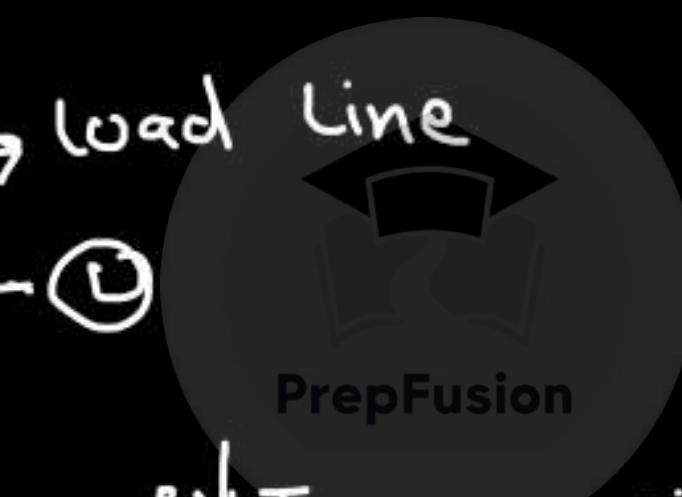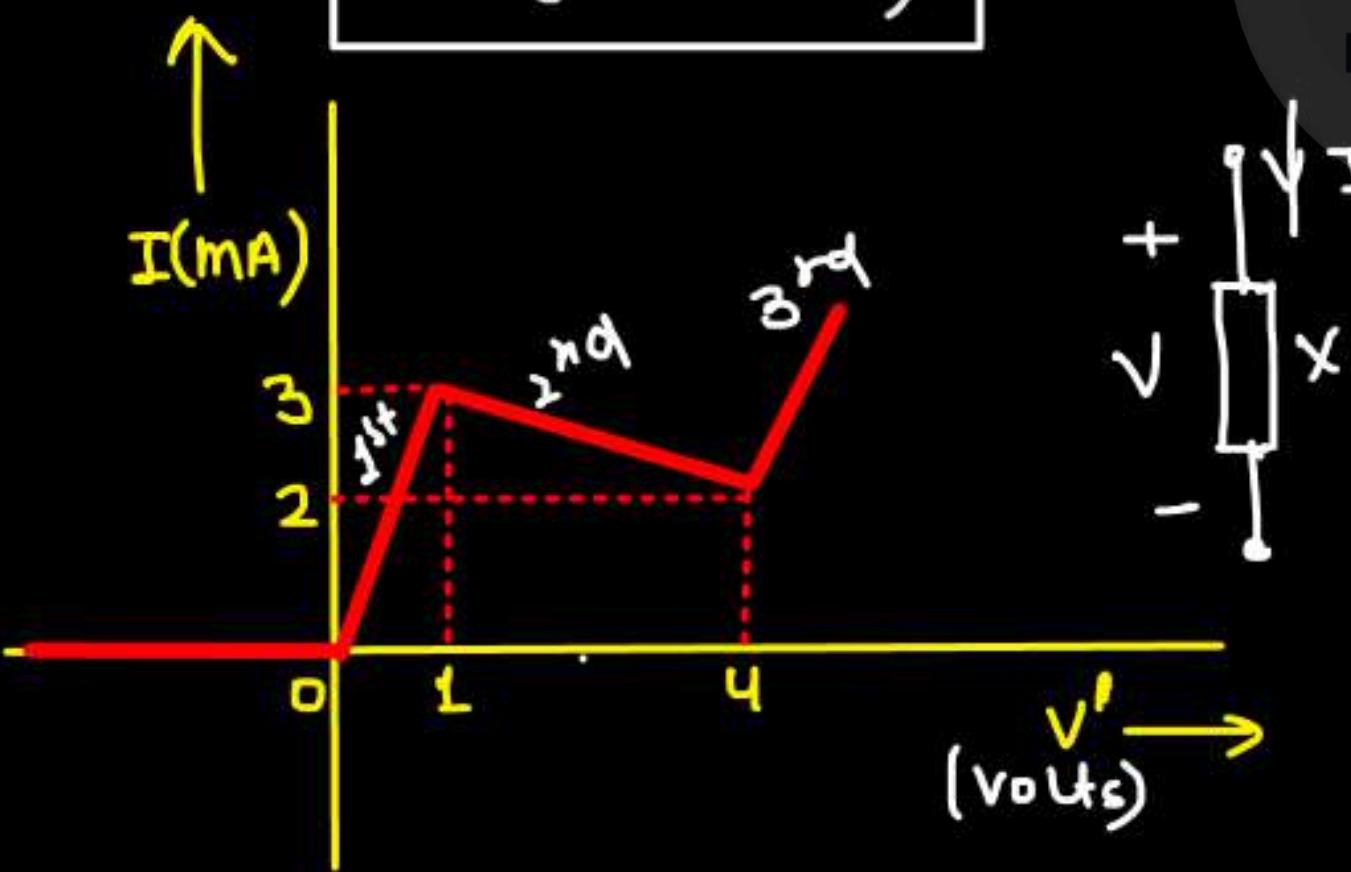

region 1st : →

$$I = 3mV' \quad \text{--- (2)}$$

region 2nd : →

$$I = -\frac{1m}{3}V' + \frac{10m}{3} \quad \text{--- (3)}$$

LECTURE-1

Watch on YouTube

AIR 27 (ECE)
AIR 45 (IN)

⇒ Device is either operating in region 1st or 2nd or 3rd.

↳ Assuming device is operating in region 1st

$$5 - V_o = 1k(I_o) \quad \text{--- (1)}$$

$$I_o = 3mV_o \quad \text{--- (2)}$$

$$5 - V_o = 3V_o$$

$$V_o = 1.25V$$

$$I_o = 3.75mA$$

→ This point doesn't lie in region 1st

PrepFusion

↳ Assuming device is working in region 2nd

$$5 - V_o = 1k(I_o) \quad \text{--- (1)} \Rightarrow I_o = 5m - 1mV_o$$

$$I_o = -\frac{1m}{3}V_o + \frac{10m}{3} \quad \text{--- (3)} \quad \checkmark \Rightarrow$$

$$5m - LmV_o = -\frac{Lm}{3}V_o + \frac{10m}{3}$$


$$\frac{5m}{3} = \frac{2m}{3}V_o$$

$$V_o = 2.5V$$

→ This point lies in region 2

$$I_o = 2.5mA$$

$$[5 - V_o = LK(I_o)]$$

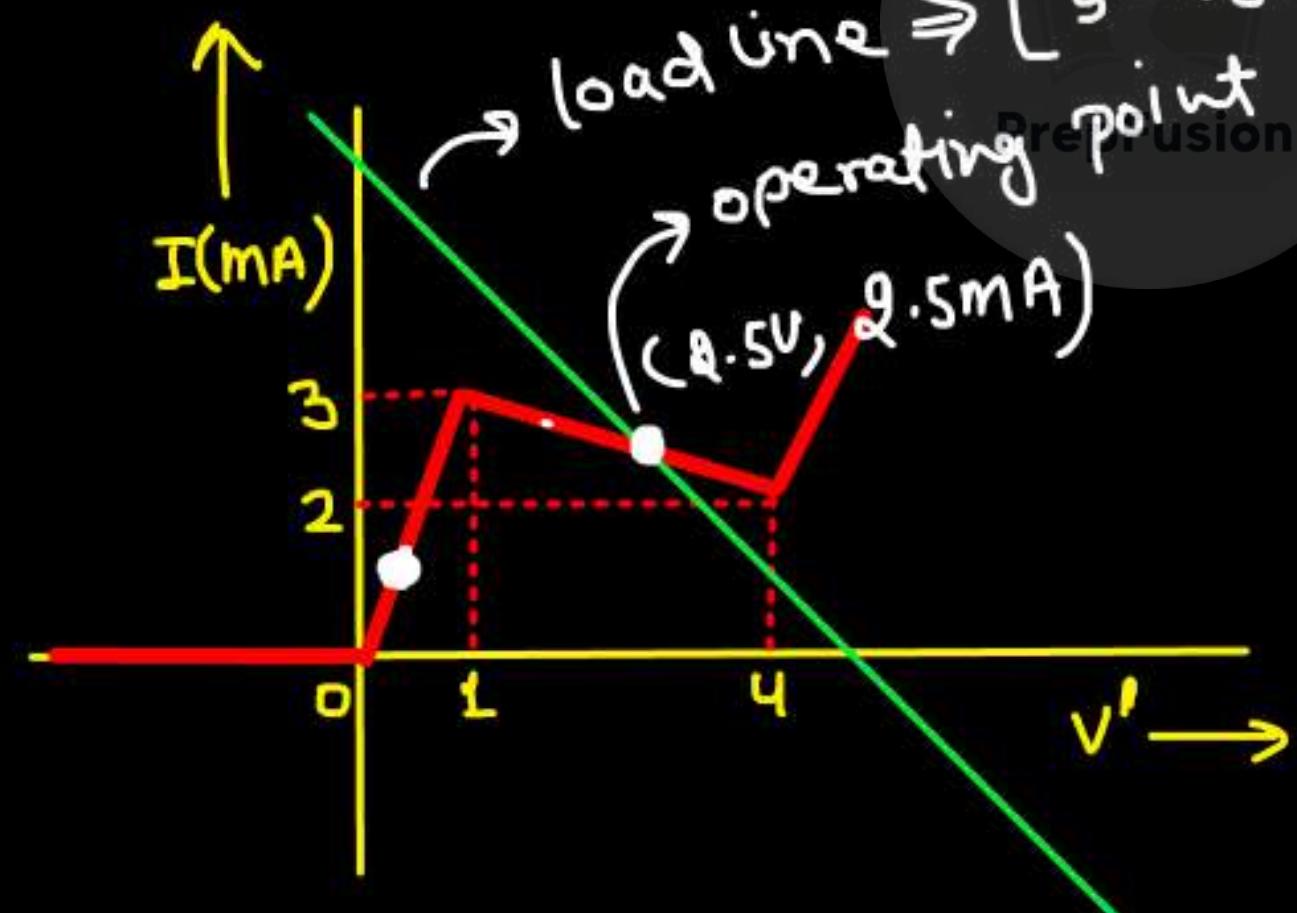

Power dissipated @
operating point

$$P = V_o I_o$$


$$\approx 2.5 \times 2.5mA$$

$$P = 6.25mW$$

(ii)

$$r_{ac} = \left(\frac{\frac{1}{L}}{\frac{\partial I}{\partial V}} \right)_{\text{operating point}} = -\frac{1}{1.5} = -3 \text{ k}\Omega$$

ac analysis :-

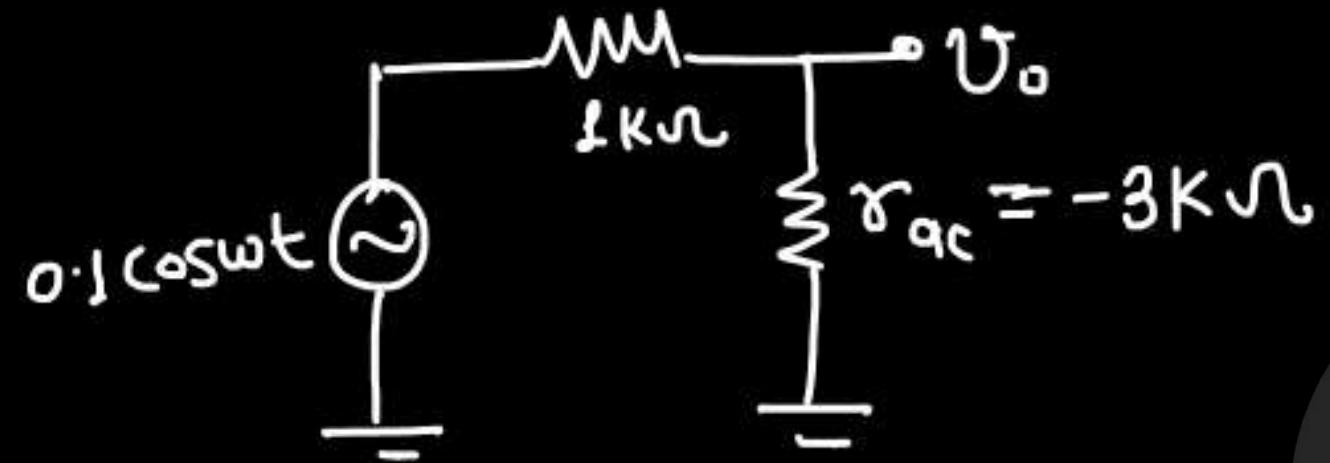


$$V_o = \frac{-3K}{1-3K} \times 0.1 \cos \omega t$$

$$V_o = 0.15 \cos \omega t \text{ mV}$$




Assignment - L

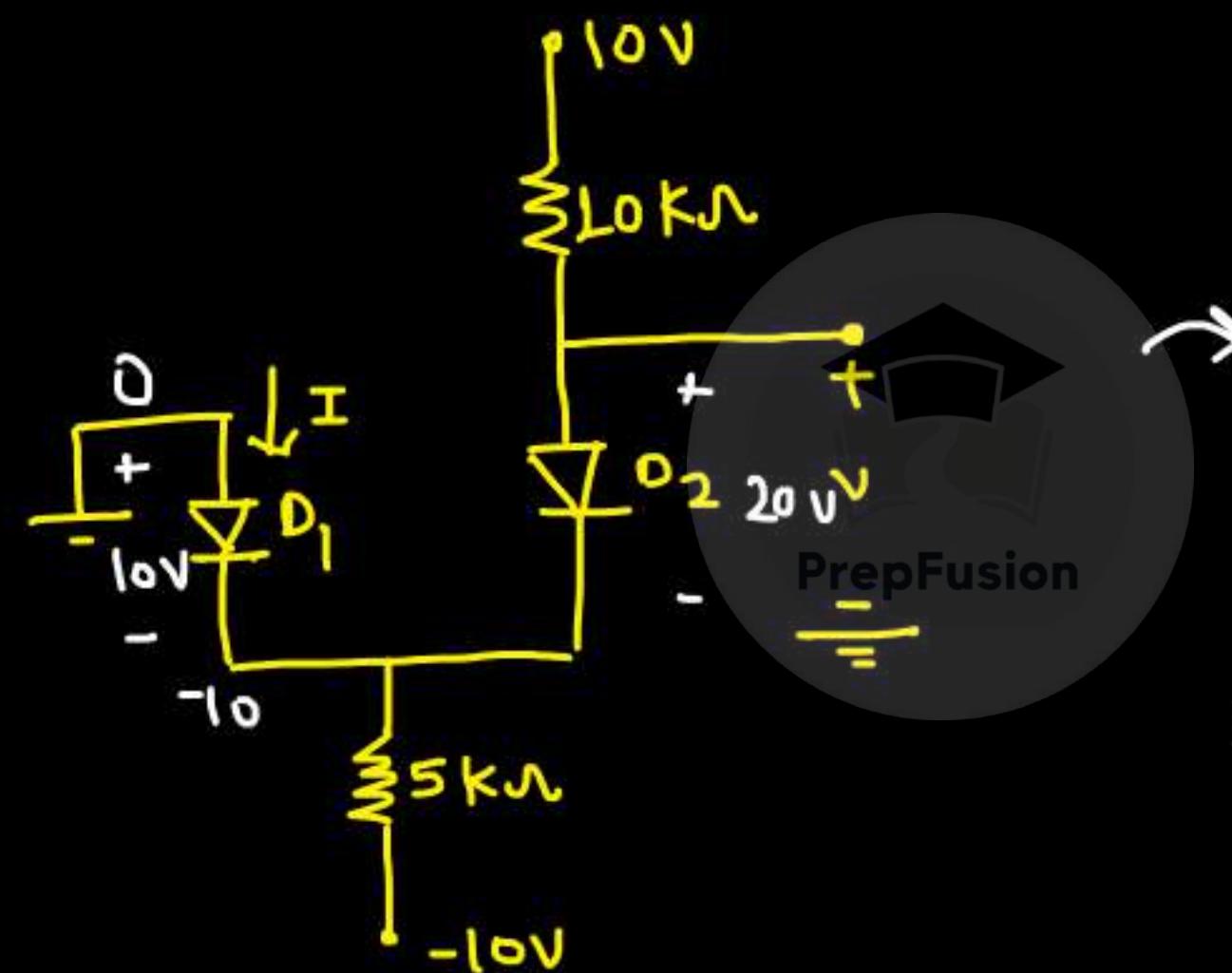
Q. Assuming diodes to be ideal. Find $I \& V$.


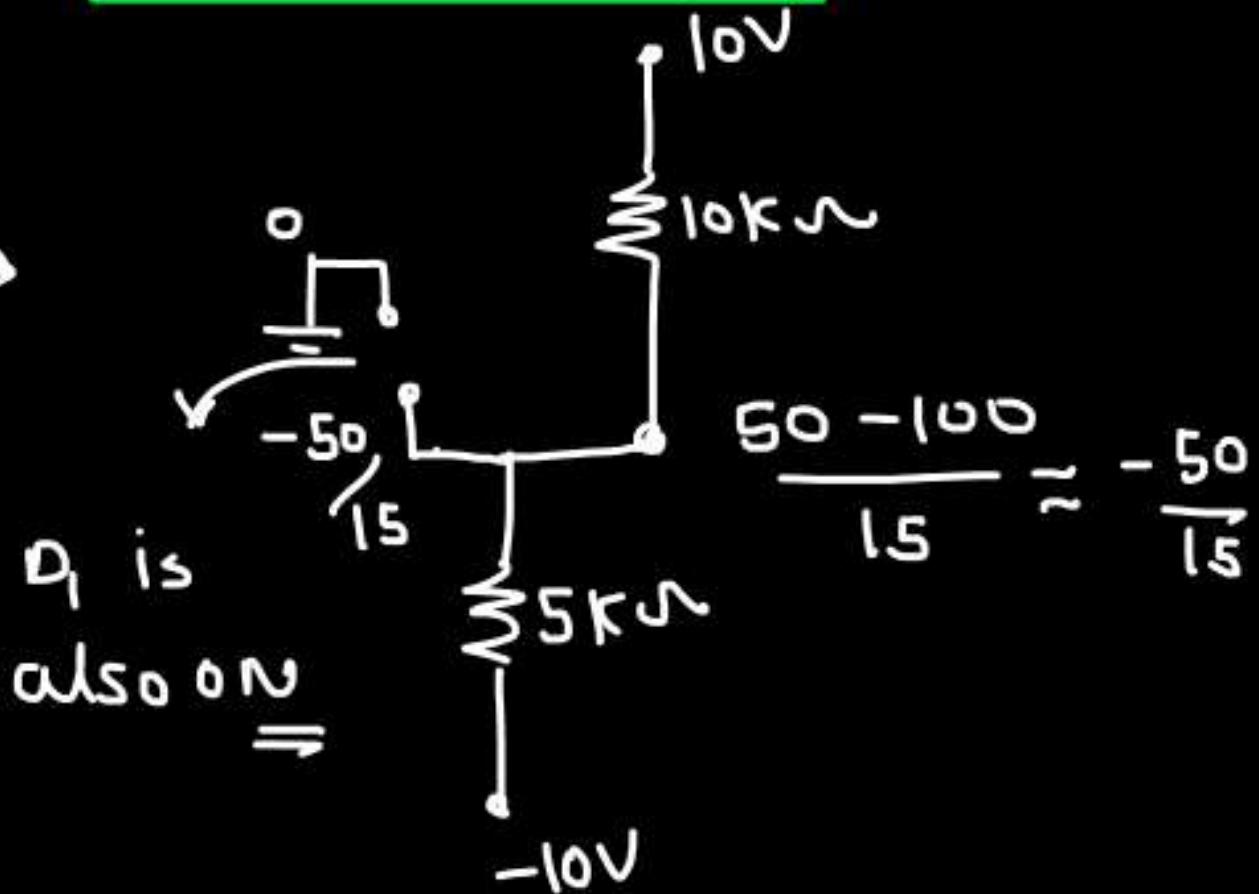
$$V = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$



D_1 is
also ON \Rightarrow

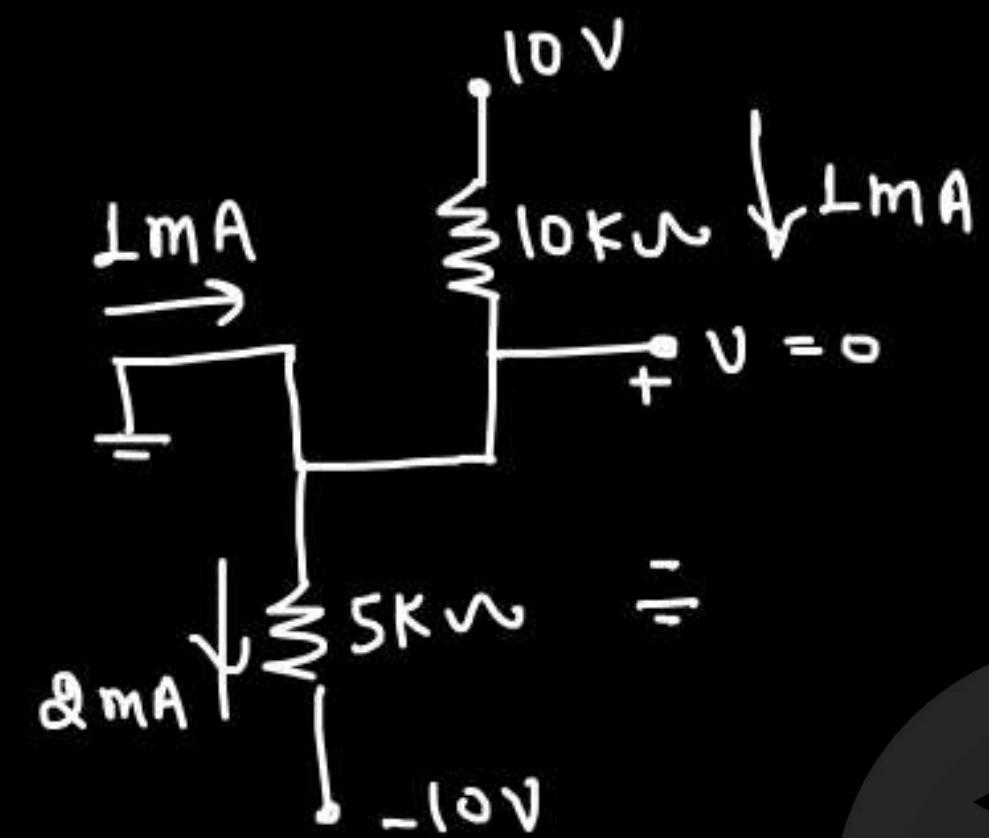


$$V = 0V$$

$$I = 1mA$$

PrepFusion


Q.

(i)

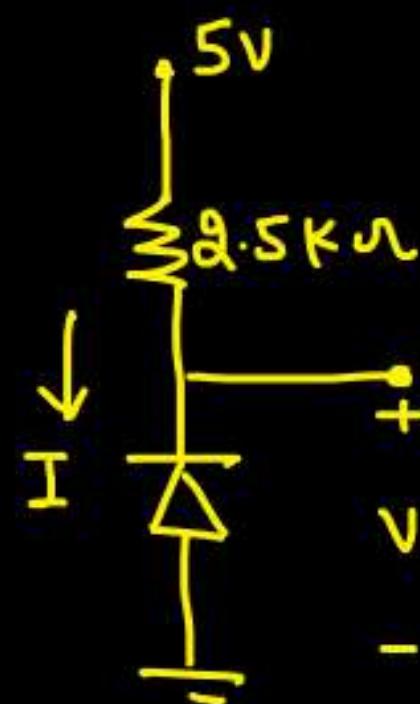


find V & I .

→ Diode off

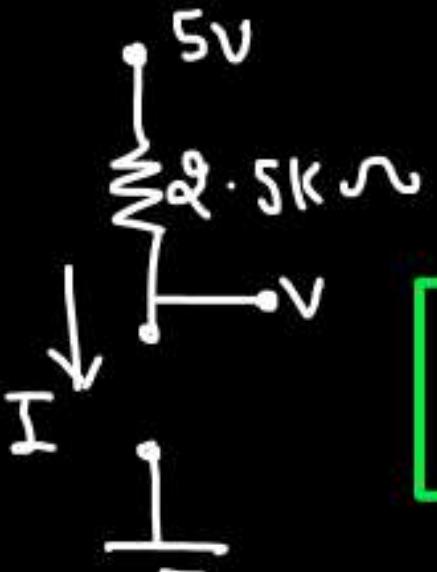


$$I = 0 \\ V = 5V$$

(ii)

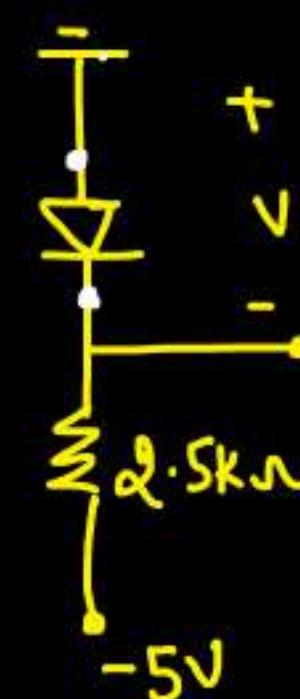

Diode → ON


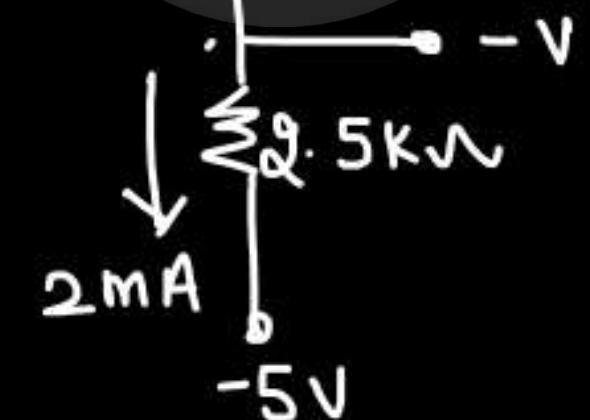


$$V = 0V$$



Q. $V_Y = 0.7V$



find V and I

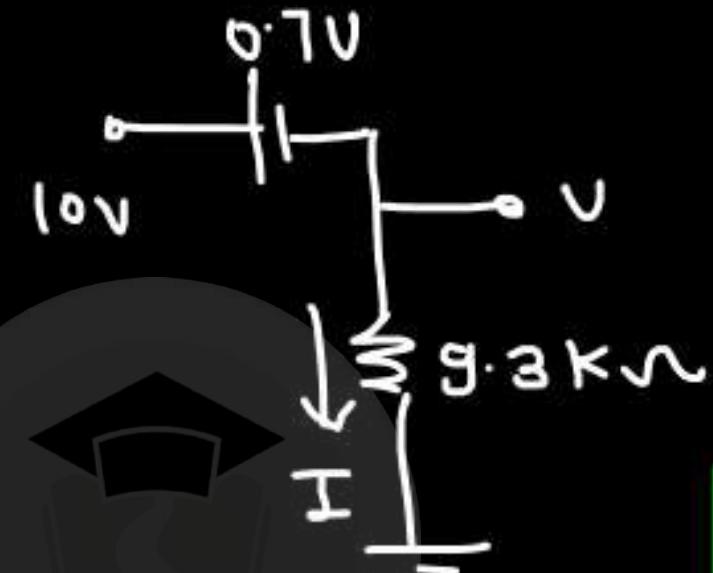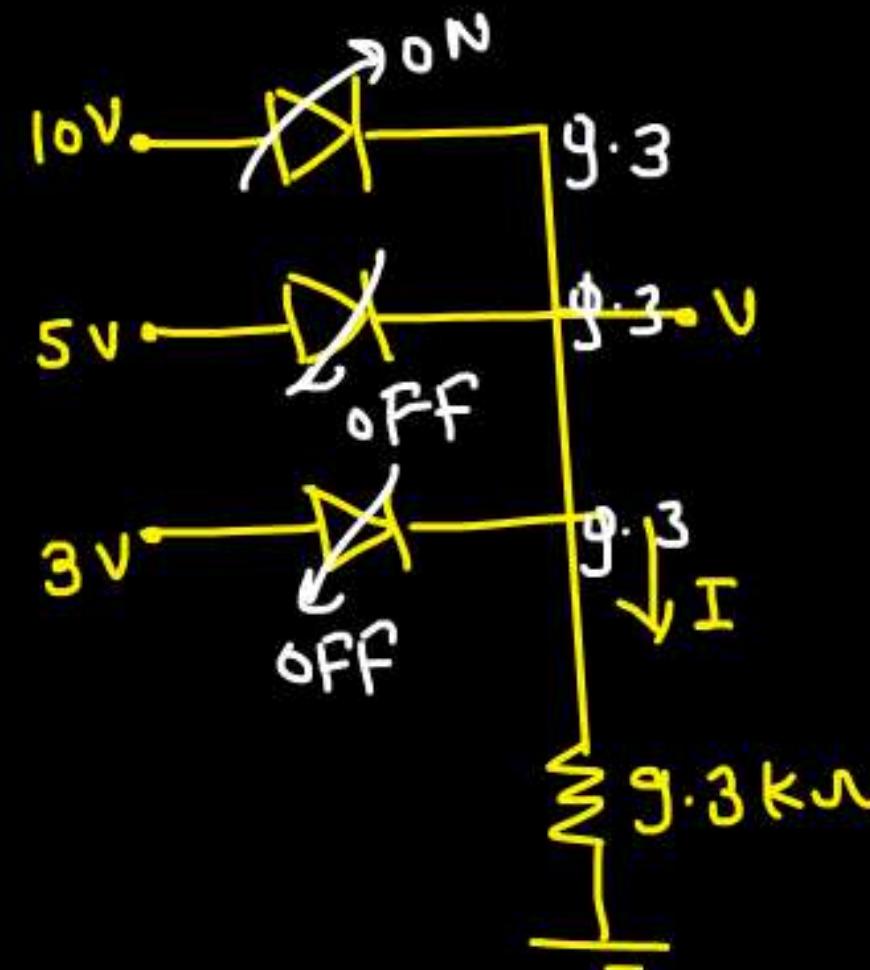

PrepFusion

$V = 9.3V$
 $I = 1mA$

Q. Find V and I

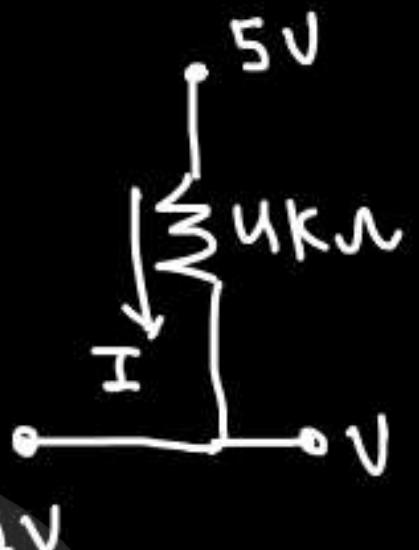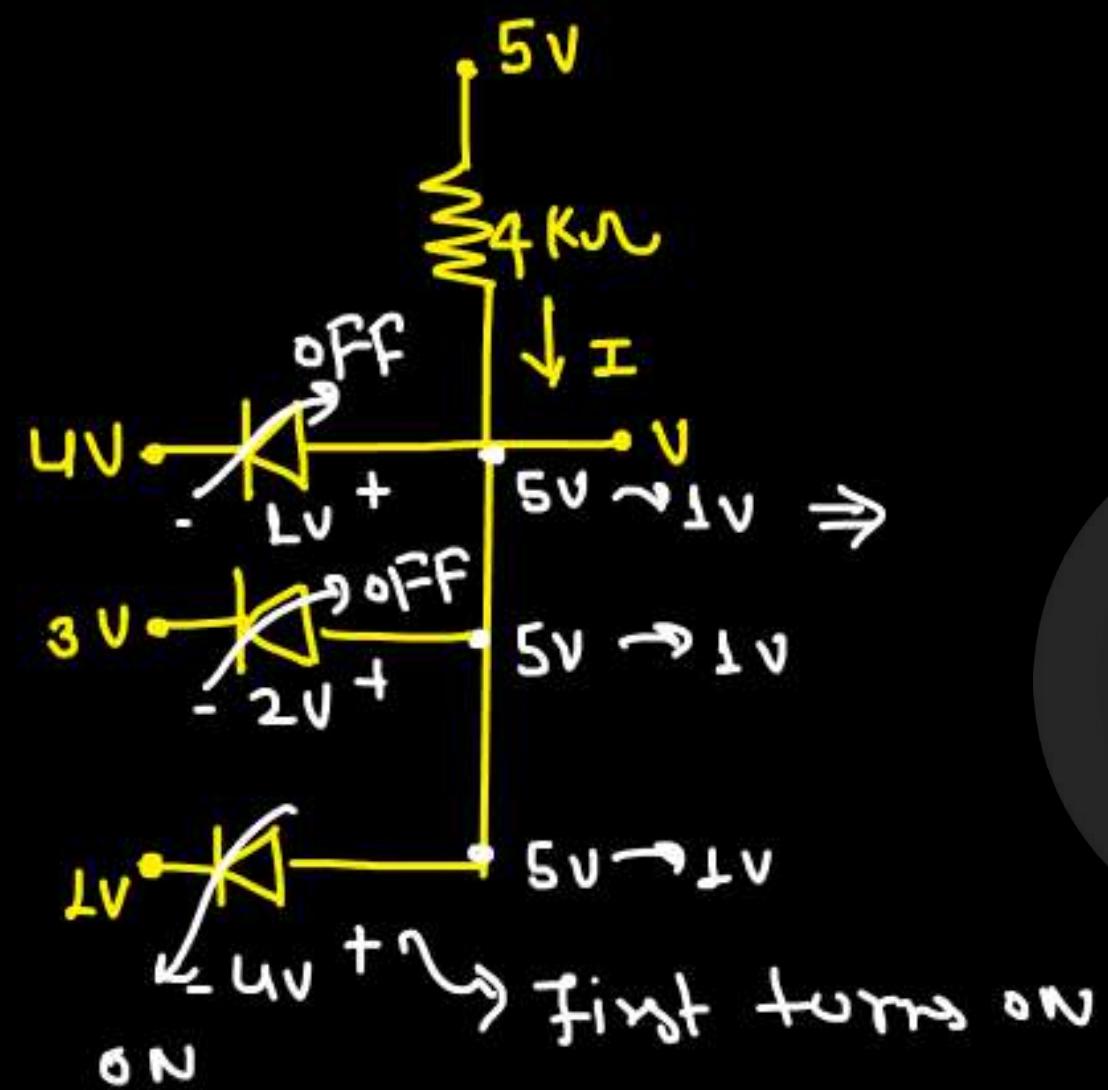


1V


$V = 1V$
 $I = 1mA$




Q.

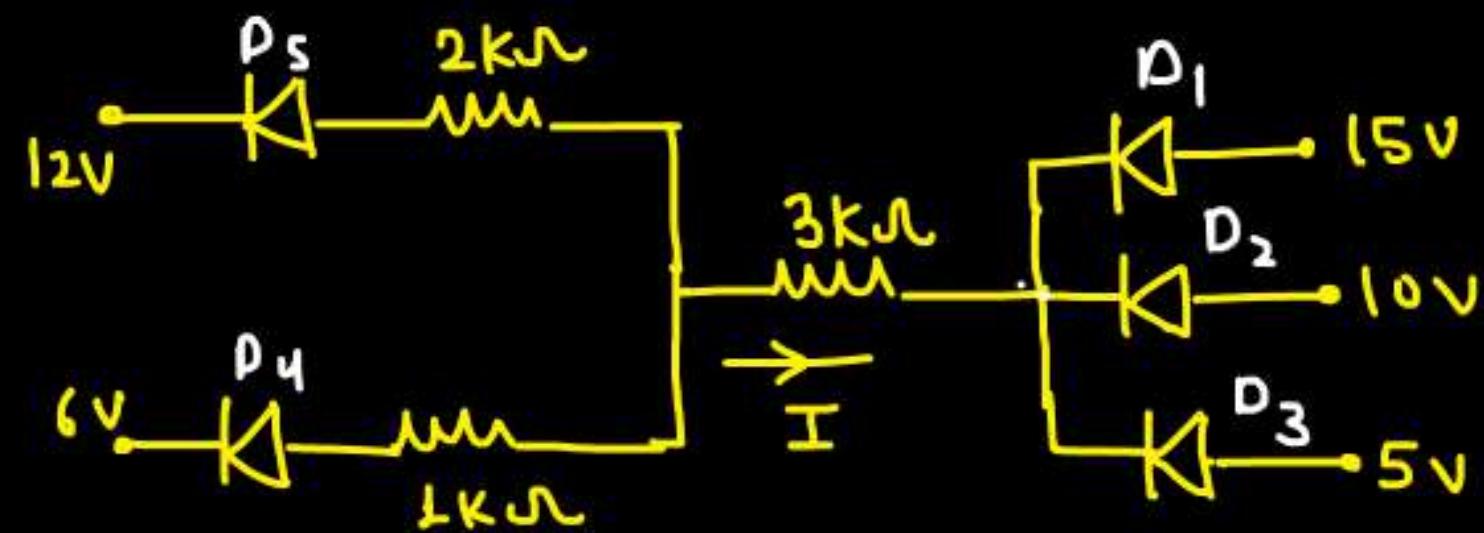

Find current I.

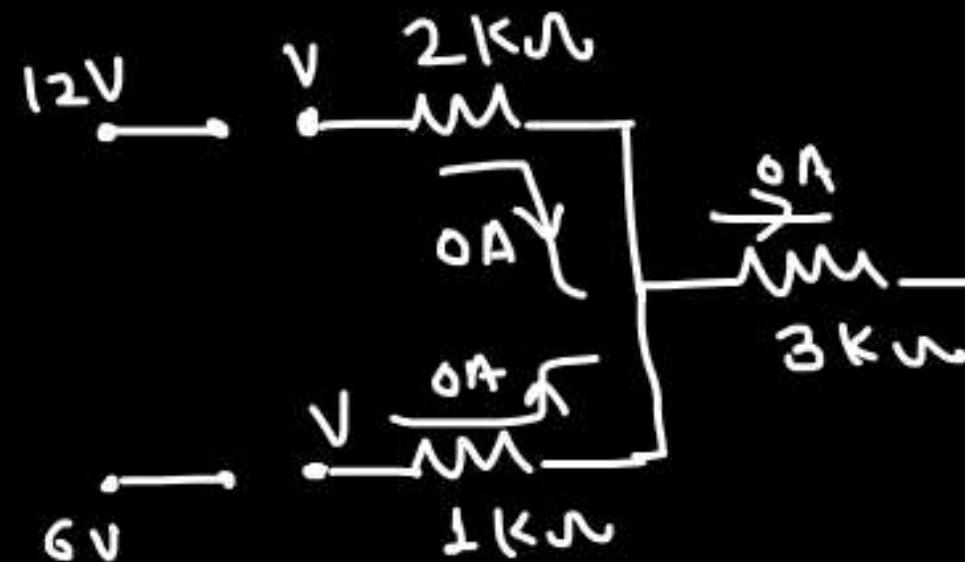


$$\text{net } V = 18V$$

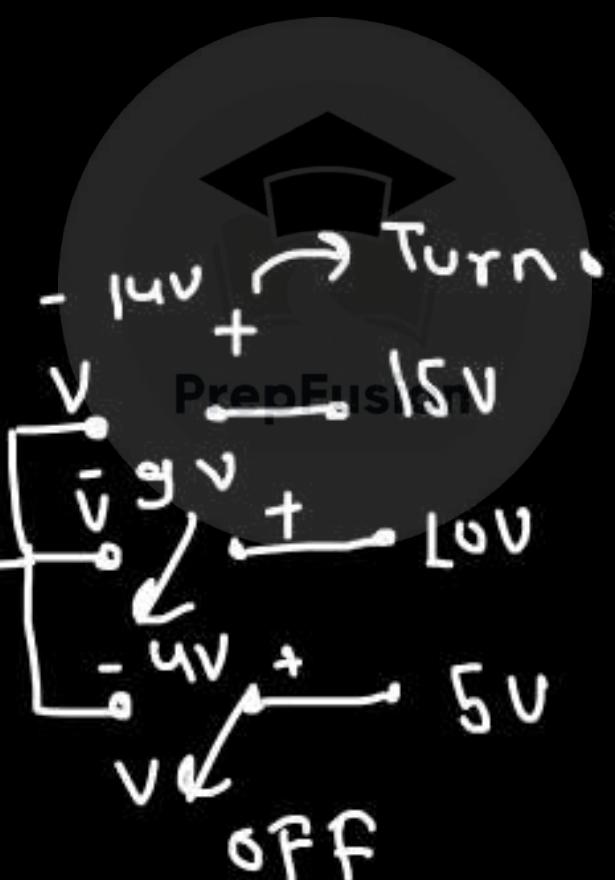

$D_1 \rightarrow ON$

$D_2, D_3 \rightarrow OFF$

$D_4 \rightarrow ON$

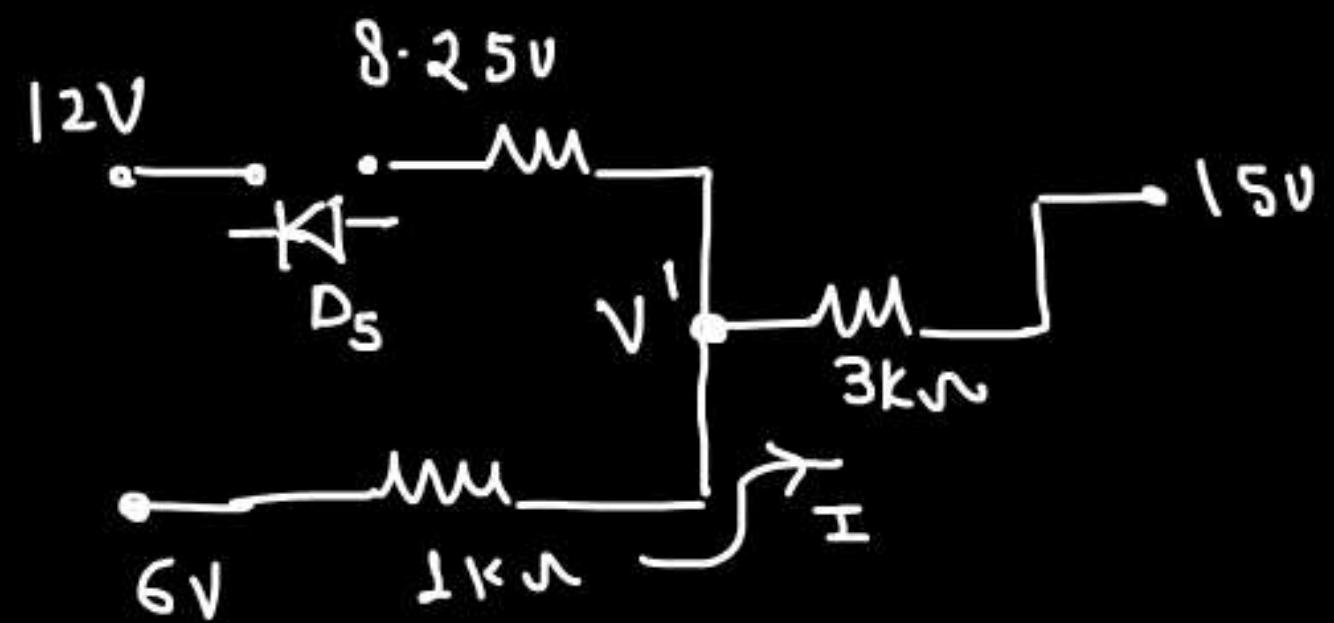



$$V' = \frac{(15 \times 1) + (6 \times 3)}{4} = \frac{33}{4} = 8.25 \text{ V}$$

PrepFusion

$\Rightarrow D_5$ is off

$I = \frac{6 - 15}{4k} = -\frac{9}{4} = -2.25 \text{ mA}$


Q. find the states of diodes.

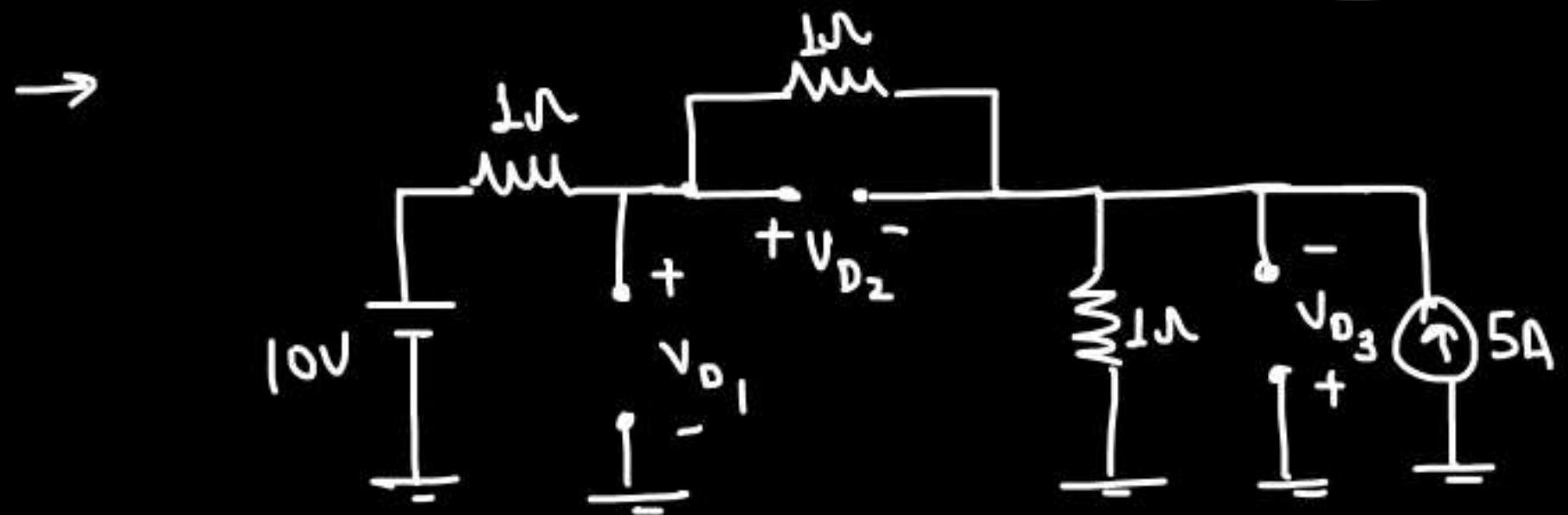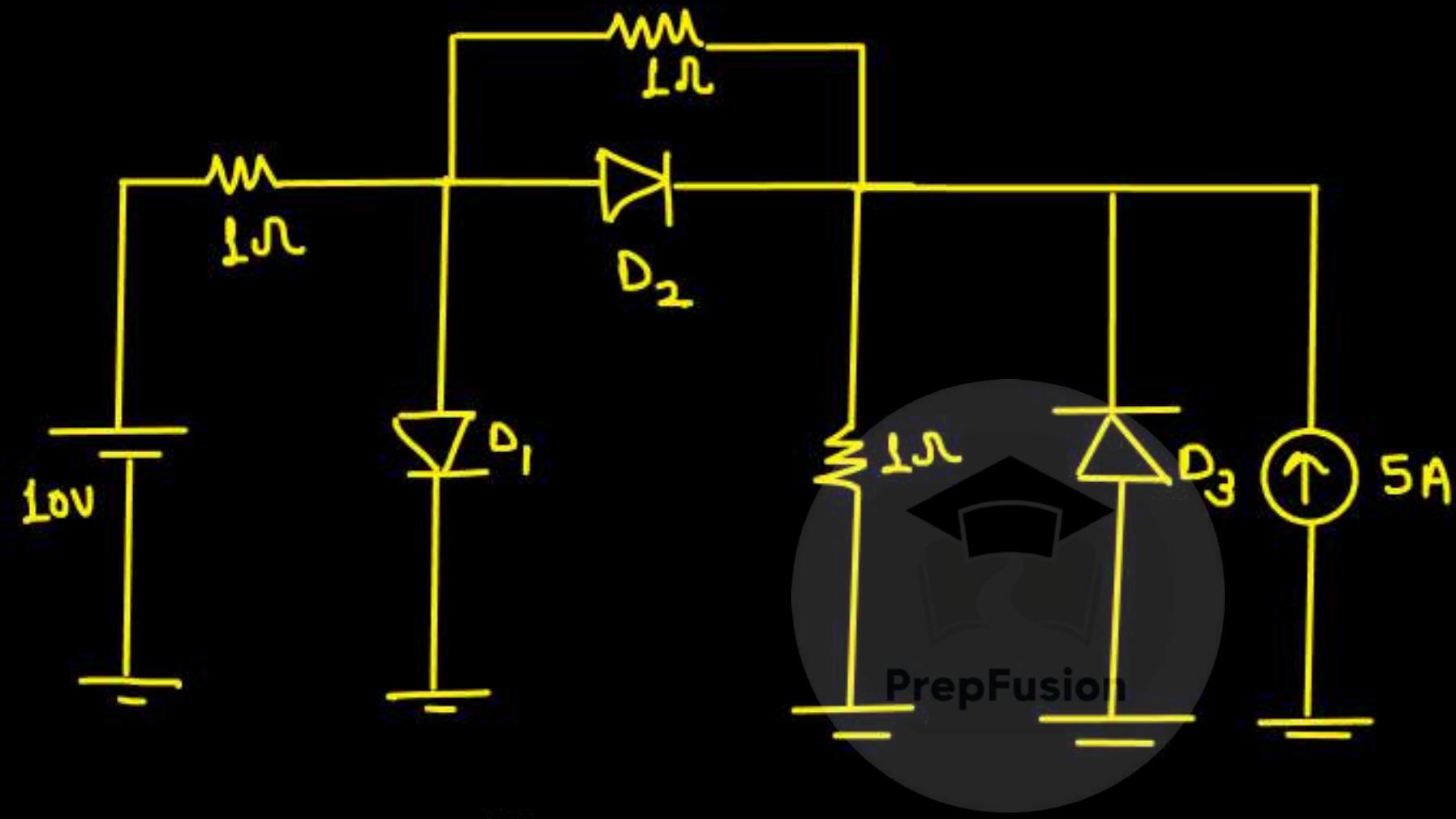

$$V_{D1} = \frac{20}{3} + \frac{5}{3} = \frac{25}{3} \rightarrow \text{ON}$$

$$V_{D2} = \frac{10}{3} - \frac{5}{3} = \frac{5}{3} \rightarrow ?$$
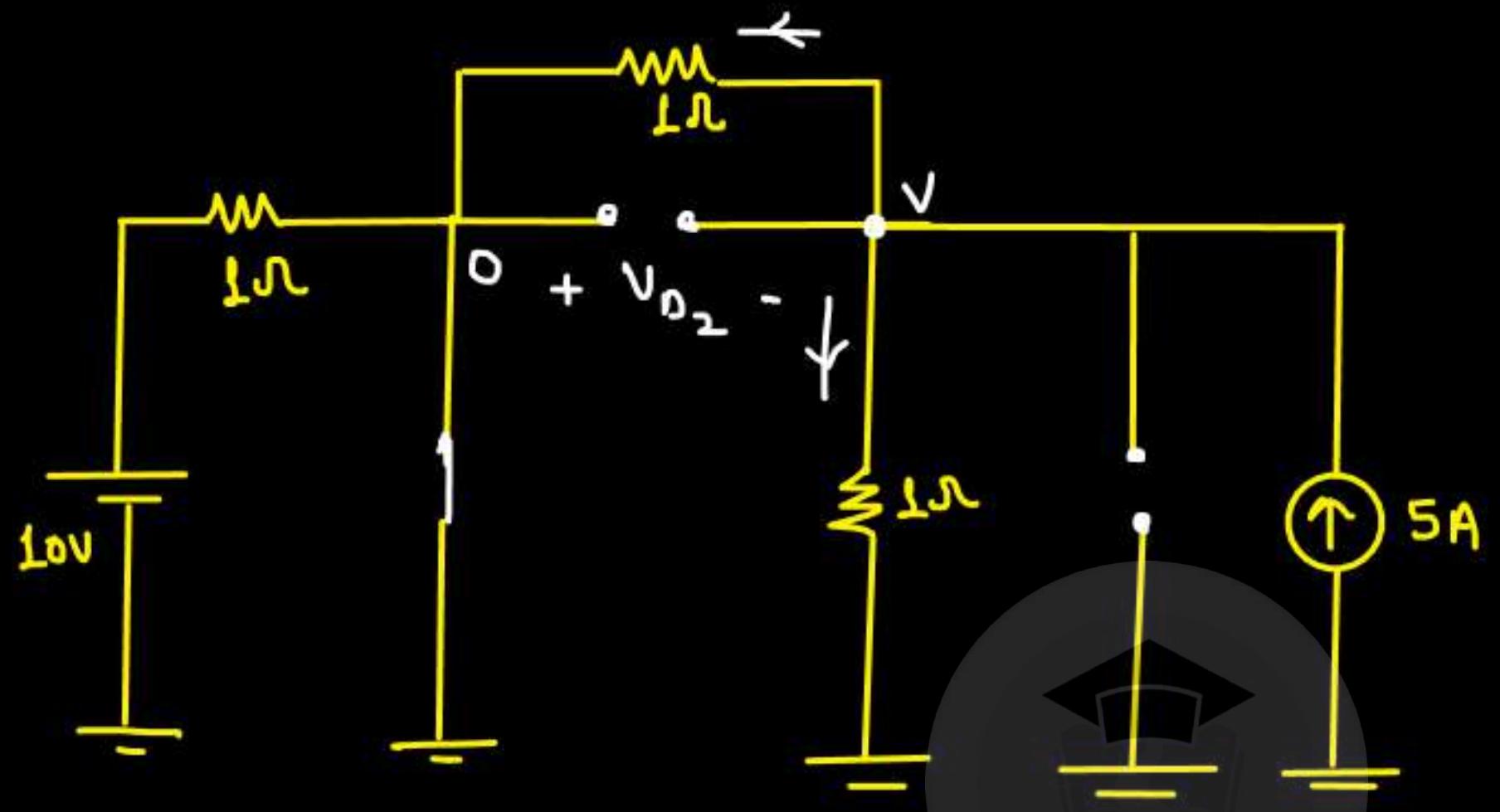
$$V_{D3} = -\frac{10}{3} - \frac{10}{3} = -\frac{20}{3} \rightarrow \text{OFF}$$



$$V + V = 5$$


$$V = 2.5V$$

$$V_{D2} = -2.5V$$

∴ D_2 is off




⇒ D₁ = ON
D₂ = OFF
D₃ = OFF

Q. Find the logic level @ z

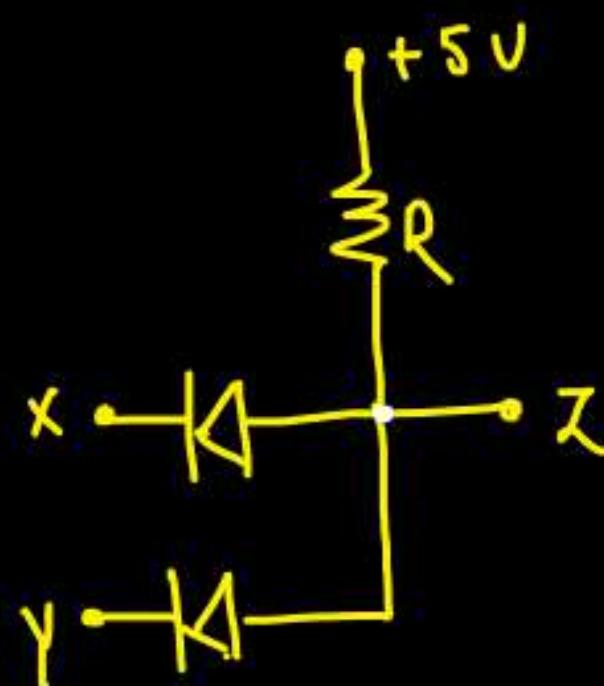


X	Y	Z
0	0	0
0	1	0
0	1	0
1	0	0
1	0	0
1	1	0
1	1	1

1 → +5V
0 → gnd / -5V

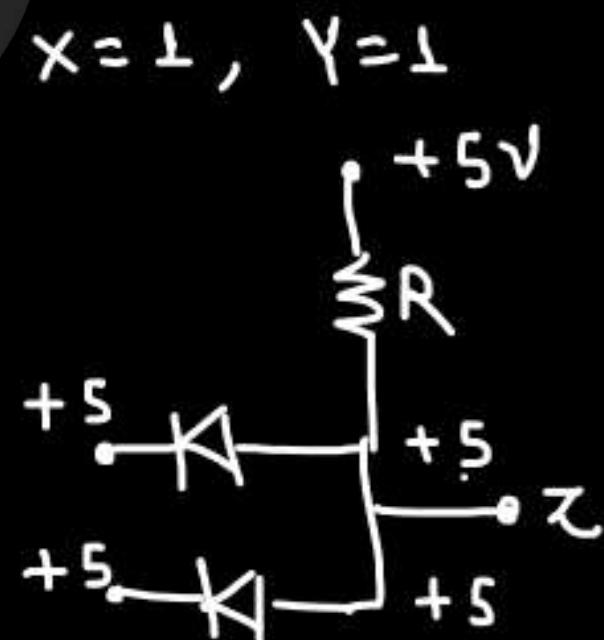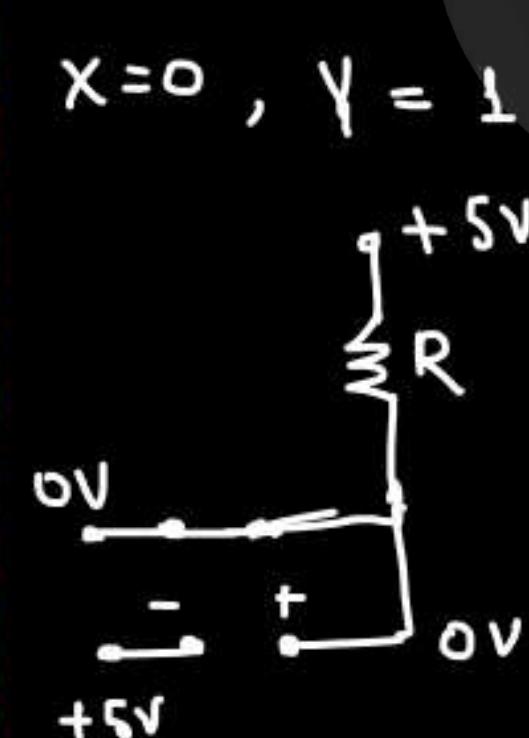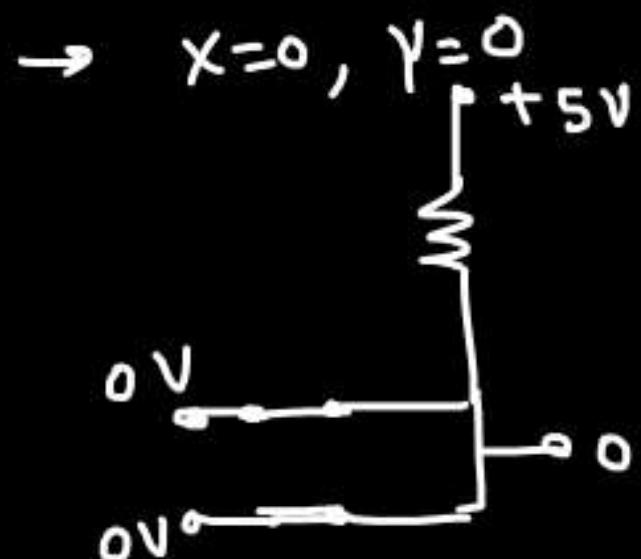

$z = xy$

Q.

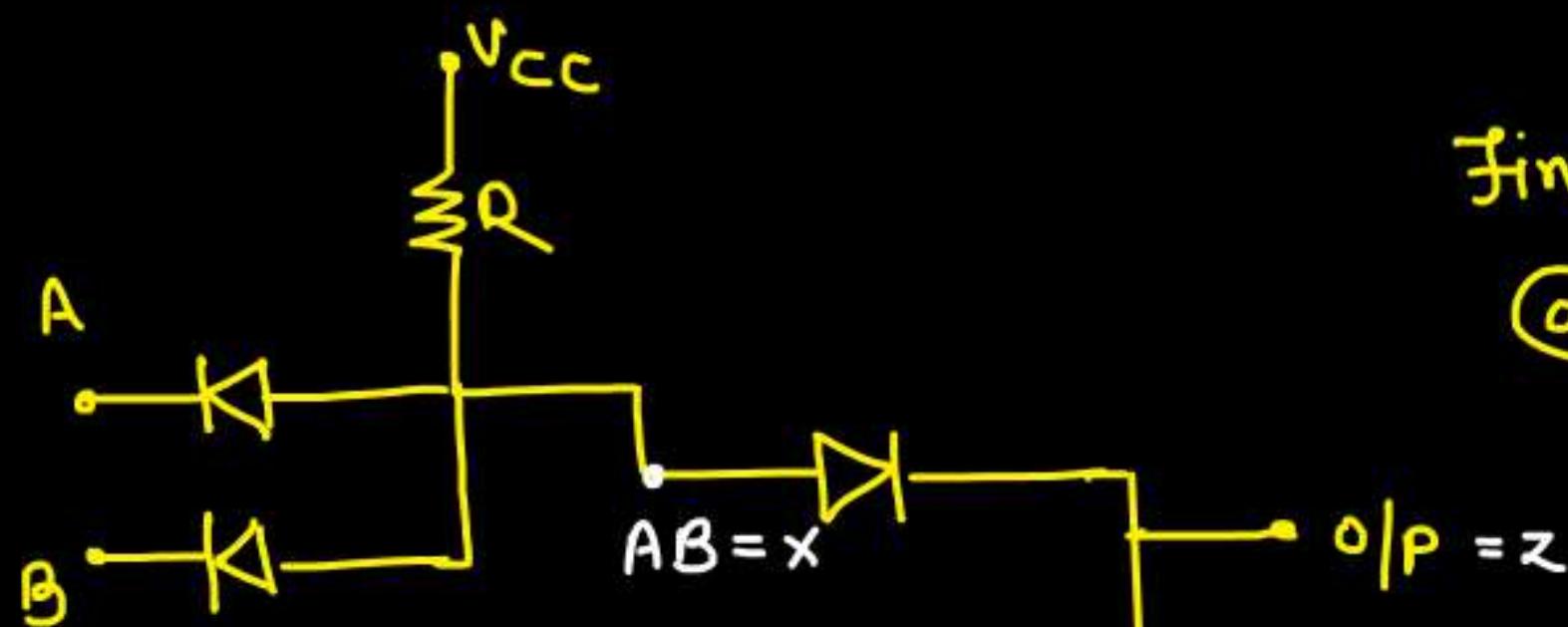

find logic level
@ O/P .








logic $0 \rightarrow -V_{CC}$

logic $1 \rightarrow +V_{CC}$

$AB = X$	$CD = Y$	$O/P = Z$
0	0	0
0	1	1
1	0	1
1	1	1

$Z = O/P = AB + CD$

Q. $V_T = 0.1V$, Find $V_o = ?$

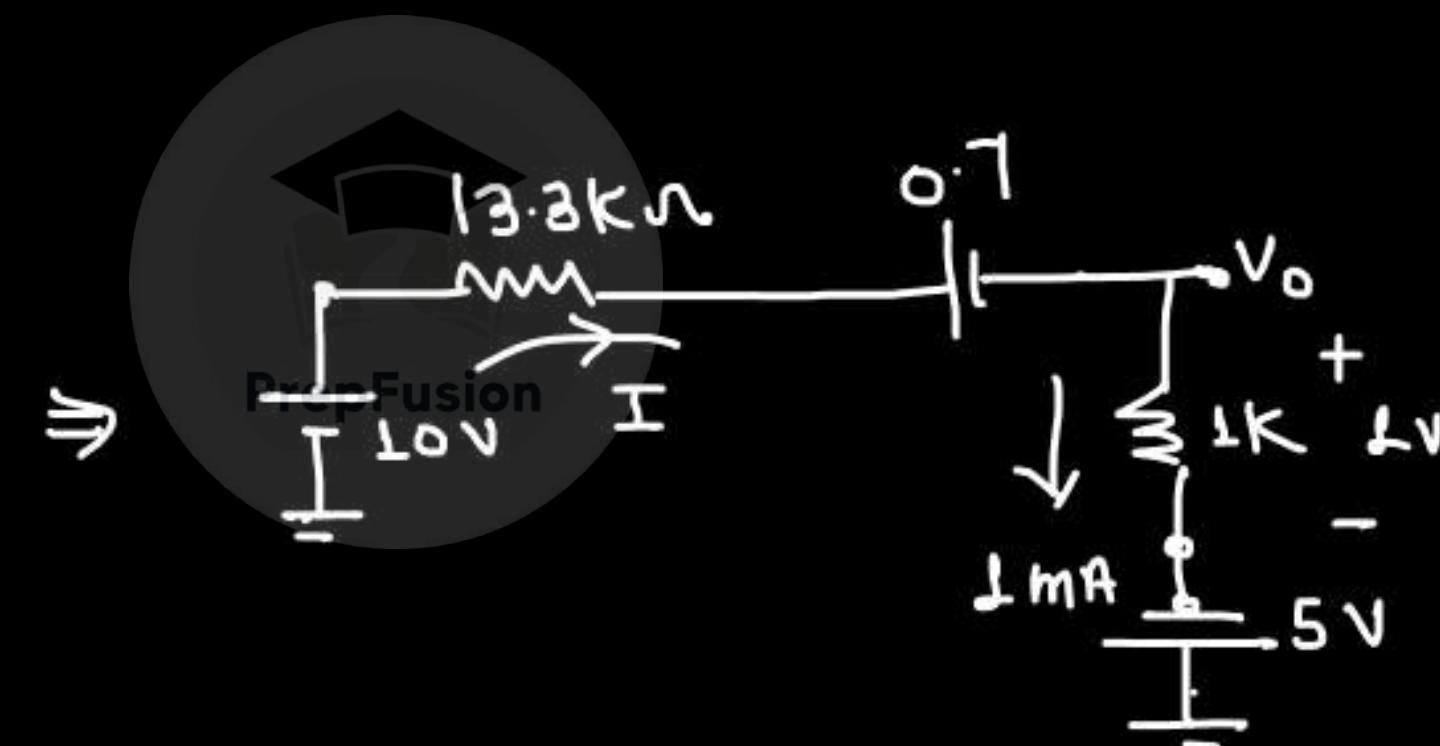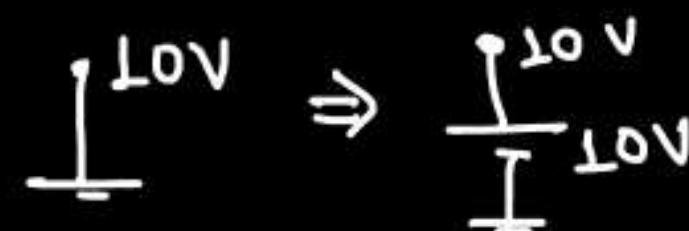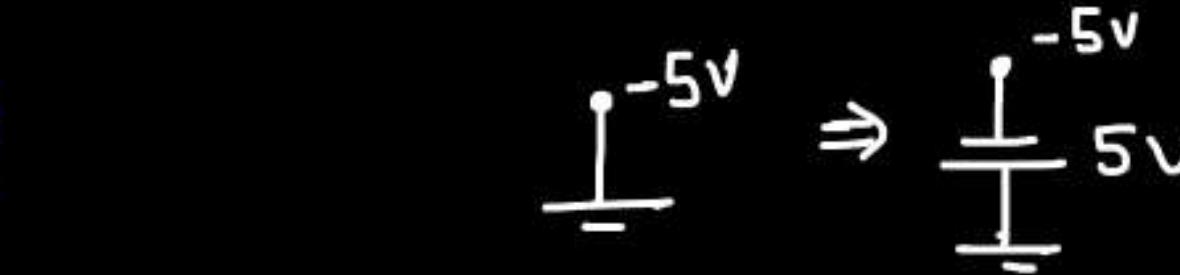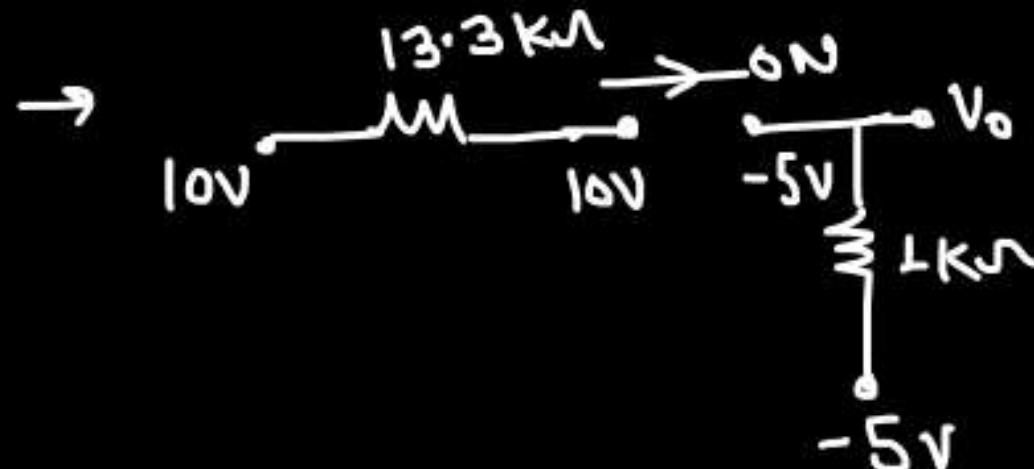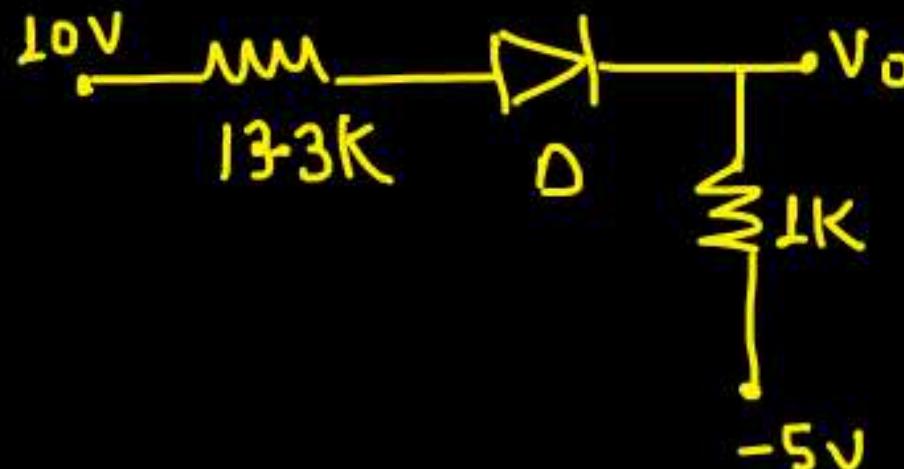


$$10 - 0.1 + 5 = (14.3k) I$$

I = 1mA

$V_o = -5 + 1$
 $V_o = -4V$

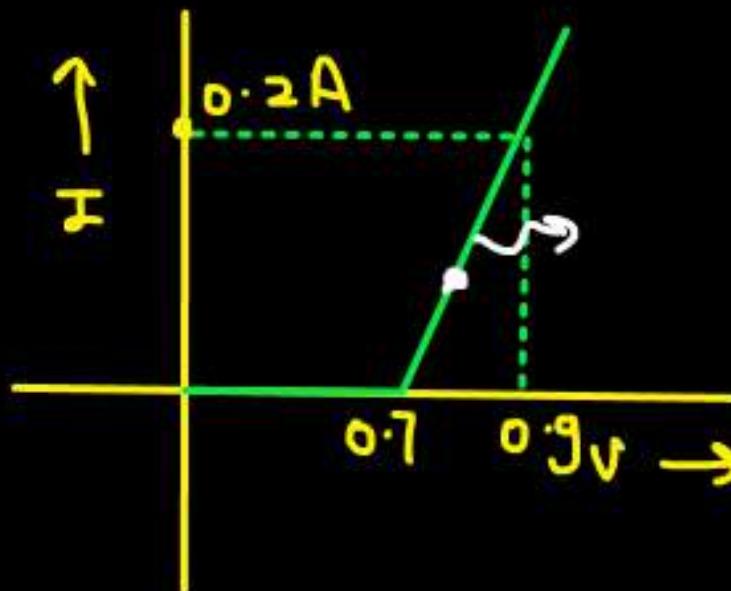Q. V-I characteristics of the diode is shown.
find current I_0 .




M-I

$$I = V - 0.7 \rightarrow \text{characteristic eqn}$$


$$10 - V = 92 I \rightarrow \text{load line}$$

$$10 - I - 0.7 = 92 I$$

$$I = 100 \text{ mA}$$

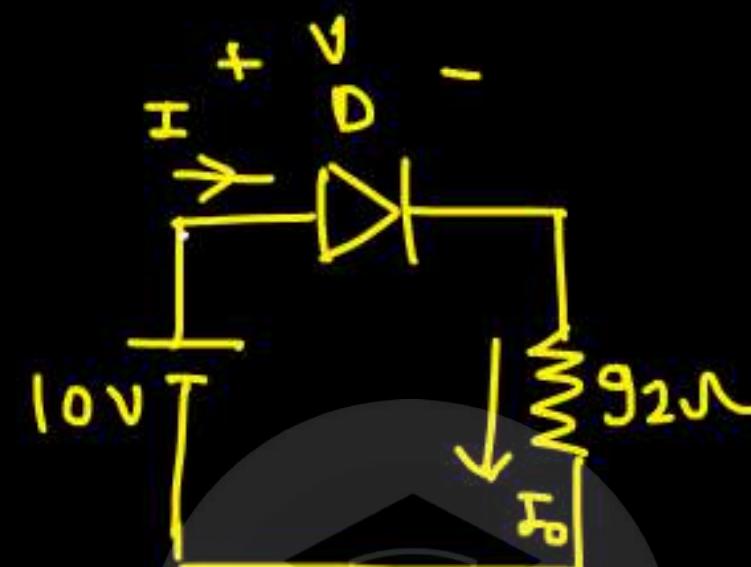
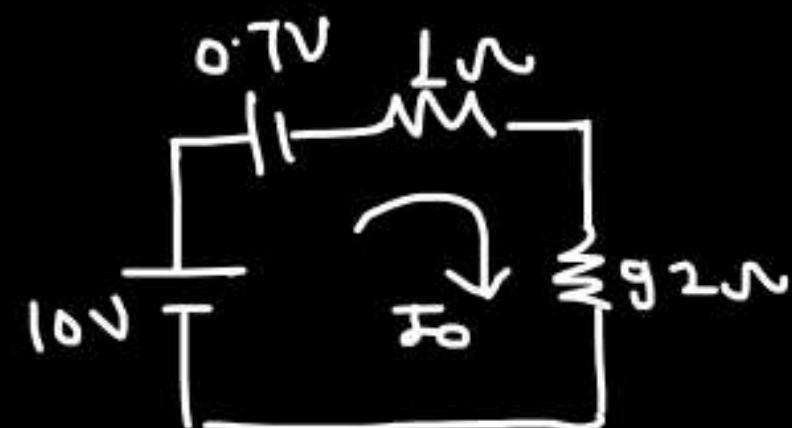
$$V_T = 0.7 \text{ V}, R_{ON} = 1 \Omega$$




$$I_0 = 100 \text{ mA}$$

Q. I-V characteristics are given.

Find current I_0 .
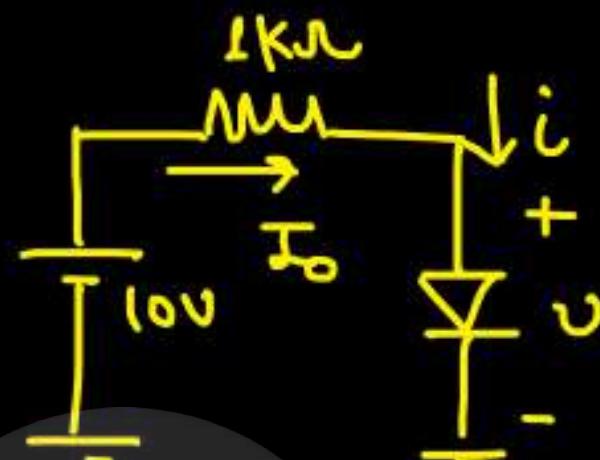
$$i = \begin{cases} \frac{v - 0.7}{500}, & v > 0.7 \\ 0, & v < 0.7 \end{cases}$$



$$\frac{1}{500\Omega} \parallel \frac{1}{0.7V}$$

→ M-I

$$i = \frac{v - 0.7}{500} \quad \left\{ \text{Considering } v > 0.7 \right\} \text{ PrepFusion} - 0$$

↳ characteristic eqn

$$10 - v = 1000i \quad - ②$$

$$10 - 500i - 0.7 = 1000i$$

$$\frac{9.3}{500} = i \Rightarrow i = 6.2 \text{ mA}$$

$$V = 3.8V$$

$$\left\{ v > 0.7 \right\}$$

M-II

$$I_D = V_D - V_T \parallel R_{on}$$

$$V_D - V_T = I_D R_D$$



$$I_D = \frac{V_D - V_T}{R_D}$$

$$i = \frac{v - 0.7}{500}$$

Q.

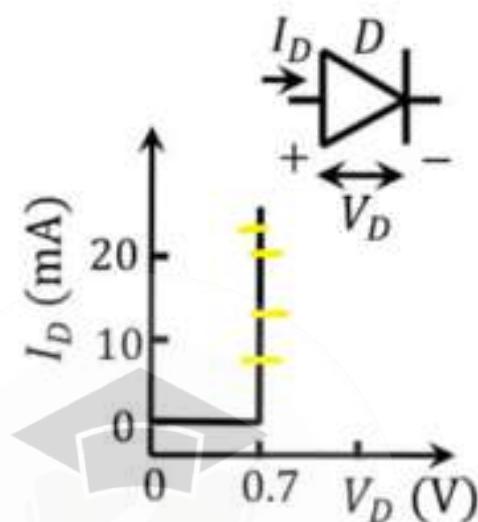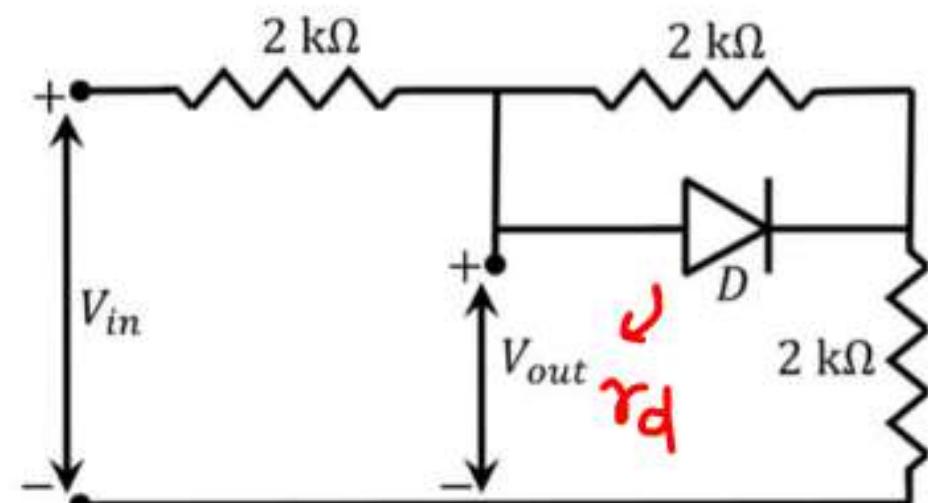Q.57

A circuit and the characteristics of the diode (D) in it are shown. The ratio of the minimum to the maximum small signal voltage gain $\frac{\partial V_{out}}{\partial V_{in}}$ is _____ (rounded off to two decimal places).



$$r_d = \frac{n v_T}{I_{DC}}$$

when $I_{DC} = 0 \Rightarrow r_d = \infty$

when $I_{DC} = \infty \Rightarrow r_d = 0$

when $r_d = 0 \Rightarrow \frac{V_o}{V_{in}} = \frac{1}{2}$

PrepFusion

$$r_d = \infty$$

$$r_d = 0$$


, when $r_d = \infty \Rightarrow \frac{V_o}{V_{in}} = \frac{2}{3}$

Ans. = $\frac{1/2}{2/3}$

ratio = 0.75

Q.

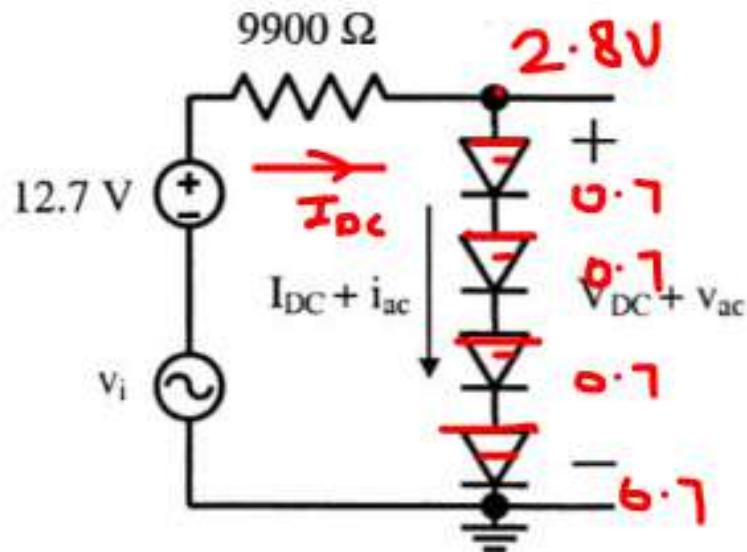In the circuit shown below, assume that the voltage drop across a forward biased diode is 0.7 V. The thermal voltage $V_T = kT/q = 25\text{mV}$. The small signal input $v_i = V_p \cos(\omega t)$ where $V_p = 100\text{ mV}$.



Q.54 The bias current I_{DC} through the diodes is

- (A) 1 mA (B) 1.28 mA (C) 1.5 mA (D) 2 mA

Q.55 The ac output voltage v_{ac} is

- (A) $0.25\cos(\omega t)\text{ mV}$ (B) $1\cos(\omega t)\text{ mV}$
 (C) $2\cos(\omega t)\text{ mV}$ (D) $22\cos(\omega t)\text{ mV}$

→

$$(i) I_{DC} = \frac{12.7 - 2.8}{9900} = \frac{9.9}{9900} = 1\text{ mA}$$

$$(ii) r_d = \frac{\eta V_T}{I_{DC}} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

ANALOG ELECTRONICS
BASIC SEMICONDUCTOR PHYSICS

LECTURE-1
GATE 2025-26 (EC/EE/IN)
 Watch on YouTube

AIR 27 (ECE)
 AIR 45 (IN)

Basic Semiconductor Physics | Analog Electro... Share 1/4

ANALOG ELECTRONICS


BASIC SEMICONDUCTOR PHYSICS

LECTURE-1

GATE 2025-26 (EC/EE/IN) Watch on YouTube

AIR 27 (ECE)
AIR 45 (IN)

ac model

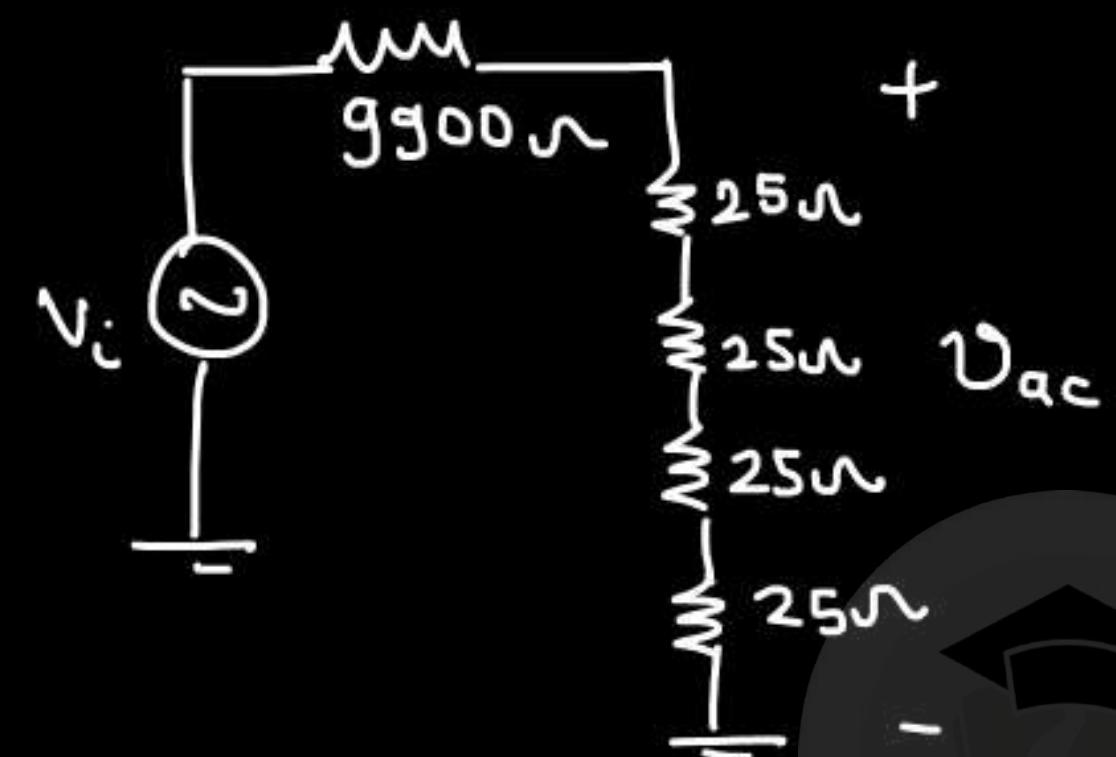

$$V_{ac} = \frac{100}{10000} \times V_i$$

$$V_{ac} = \frac{V_i}{100}$$


$$V_{ac} = 1 \text{ mV} \cos \omega t$$





Q.

A dc current of $26 \mu\text{A}$ flows through the circuit shown. The diode in the circuit is forward biased and it has an ideality factor of one. At the quiescent point, the diode has a junction capacitance of 0.5 nF . Its neutral region resistances can be neglected. Assume that the room temperature thermal equivalent voltage is 26 mV .

$$R_{ON} = 0 \Omega$$

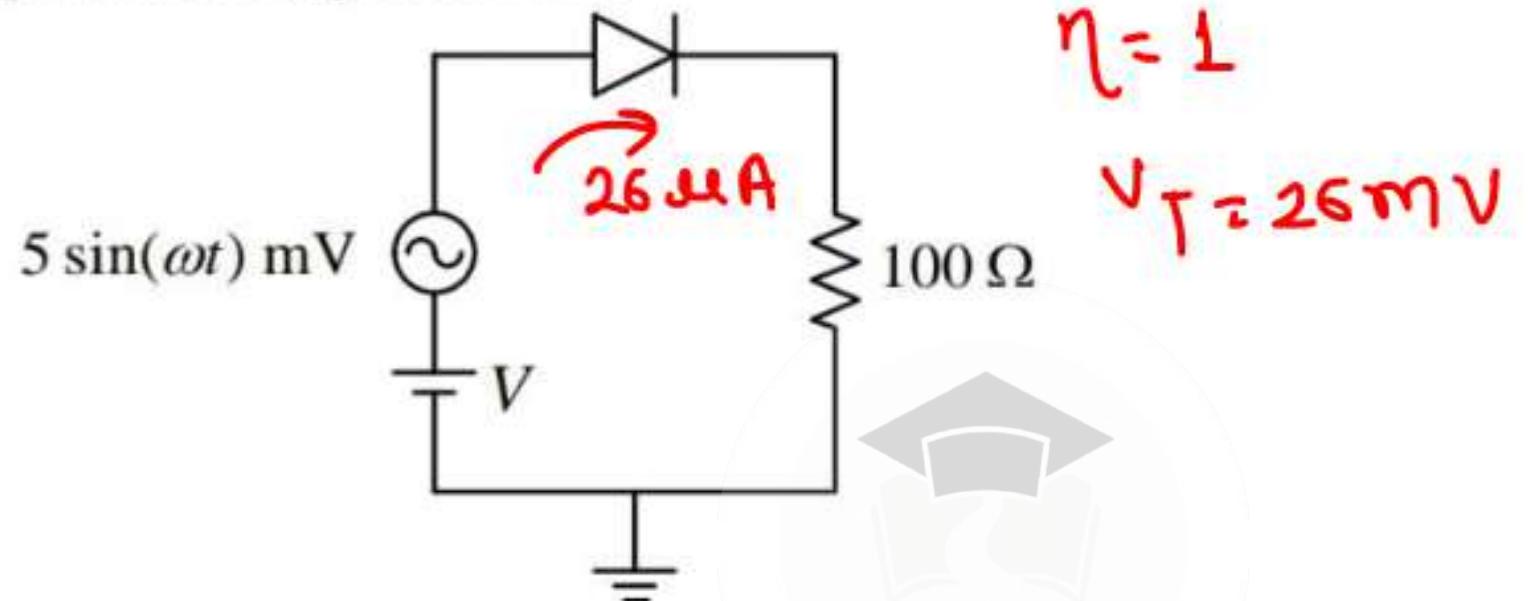


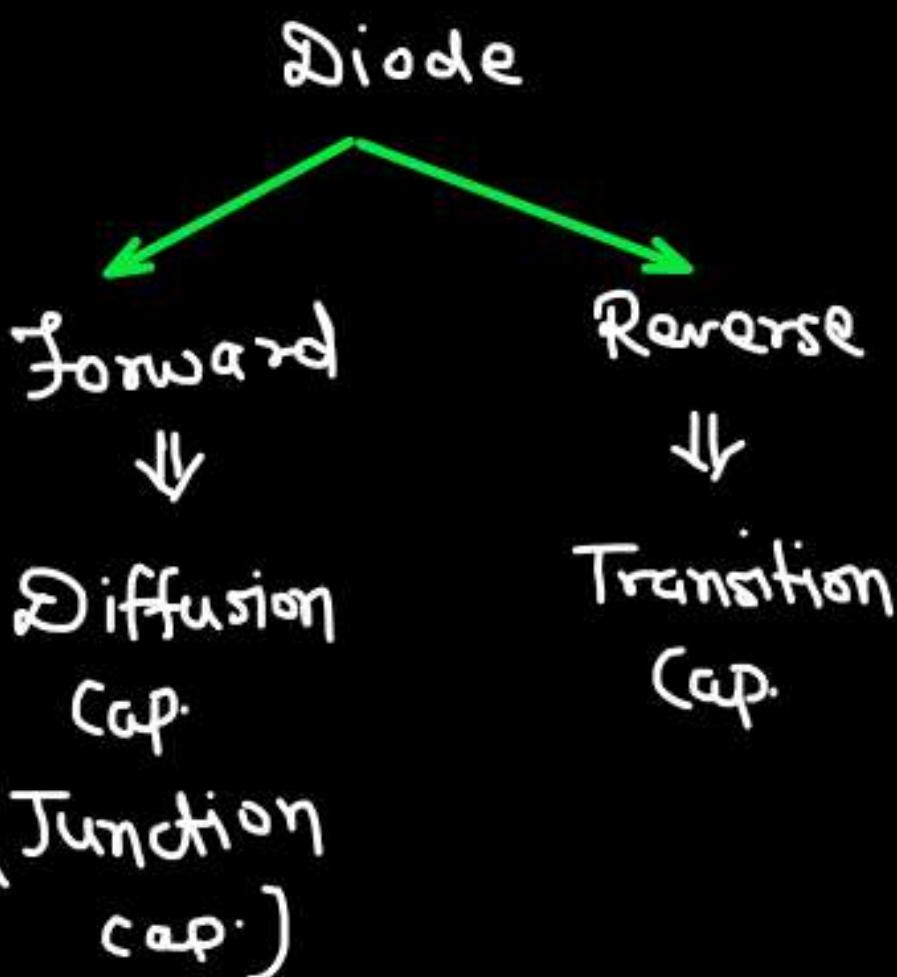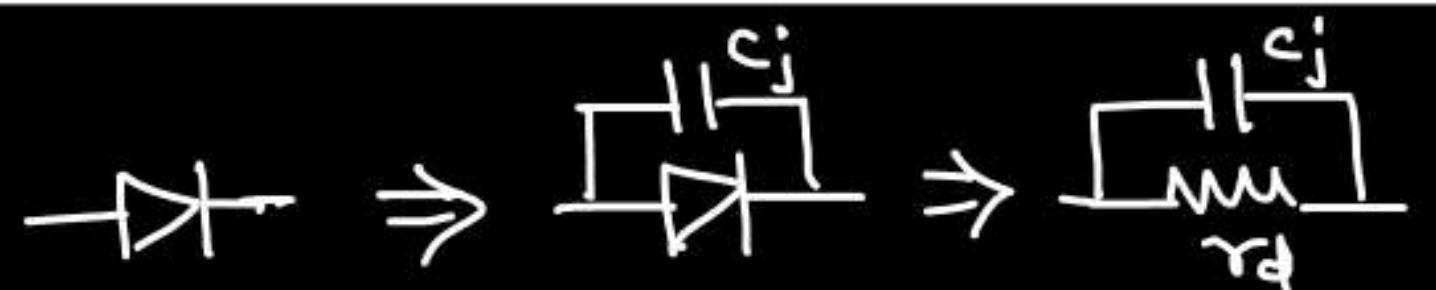For $\omega = 2 \times 10^6 \text{ rad/s}$, the amplitude of the small-signal component of diode current (in μA , correct to one decimal place) is _____.



$$\gamma_d = \frac{\eta V_T}{I_{DC}} = \frac{26mV}{26\mu A} = 1000\Omega = 1k\Omega$$

$$C_J = 0.5nF$$

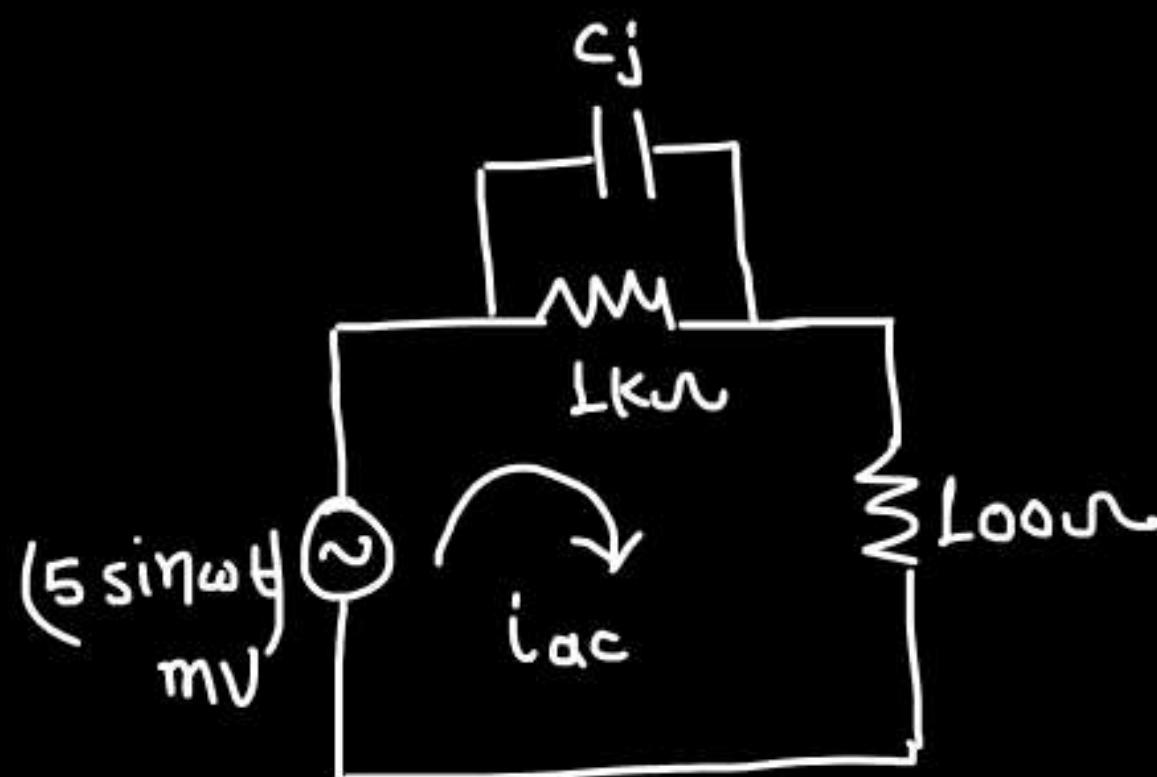

$$\hookrightarrow Z_C = -j \frac{1}{\omega C} = -j \frac{1}{2 \times 10^6 \times 0.5 \times 10^{-9}}$$

$$Z_C = -j 1000\Omega$$

Pre Fusion

$$Z_C \parallel 1K\Omega = \frac{-j 1K\Omega \times 1K\Omega}{-j 1K\Omega + 1K\Omega} = \frac{-j 1K\Omega}{-j + 1}$$

$$i_{ac} = \frac{5mV}{100 + j 1K} \times \sin \omega t$$



$$i_{ac} = \frac{5mv(j-L)}{100j - 100 + j1000} \times \sin \omega t$$


$$= \frac{5mv (j-L)}{1100j - 100} \times \sin \omega t$$

$$= \frac{5\sqrt{2}}{\sqrt{(1100)^2 + (100)^2}} mv \times \sin \omega t$$


$$i_{ac} = 6.4 \mu A \sin \omega t$$

PrepFusion

⇒ Diode in Reverse bias:-

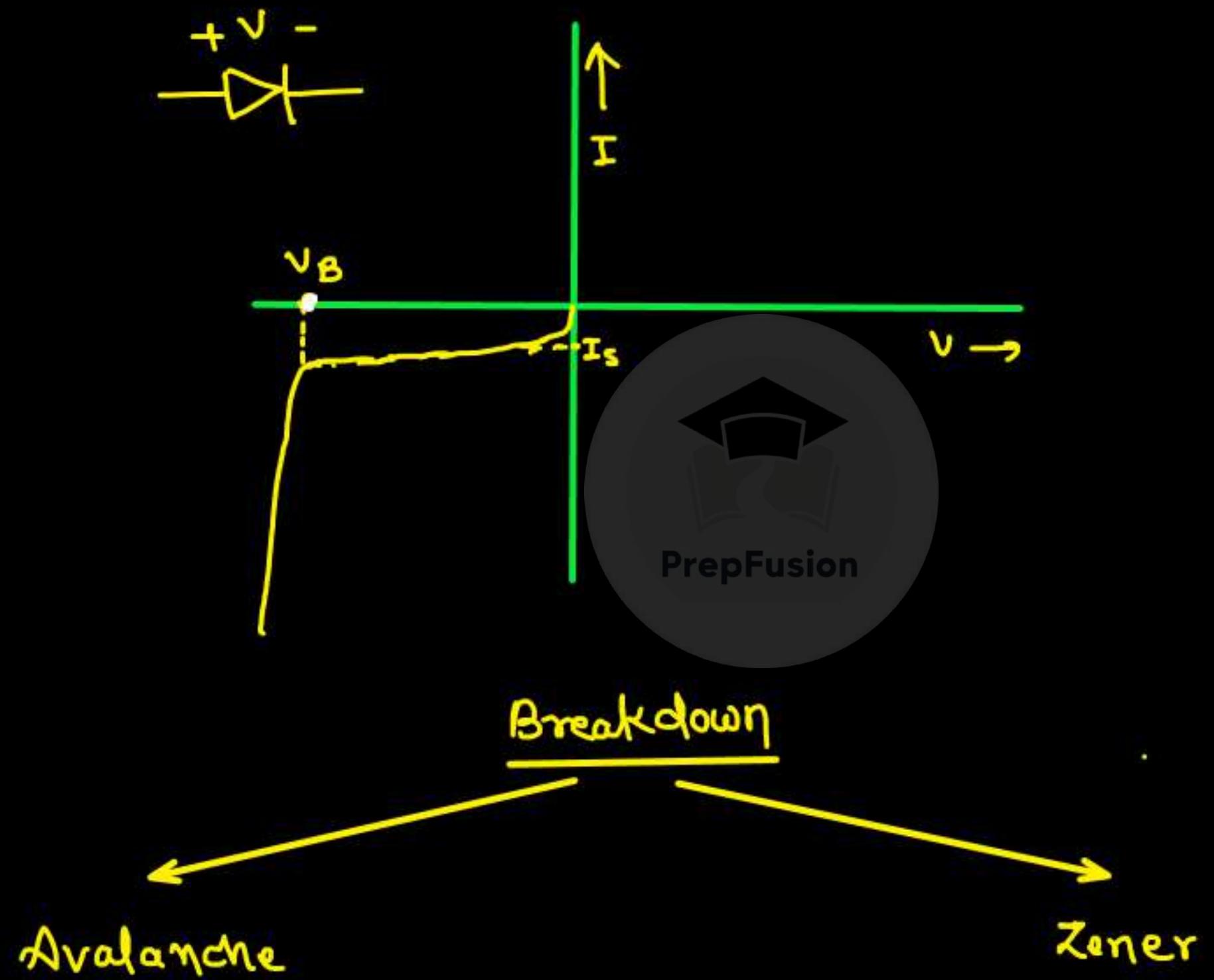

Avalanche Breakdown:-

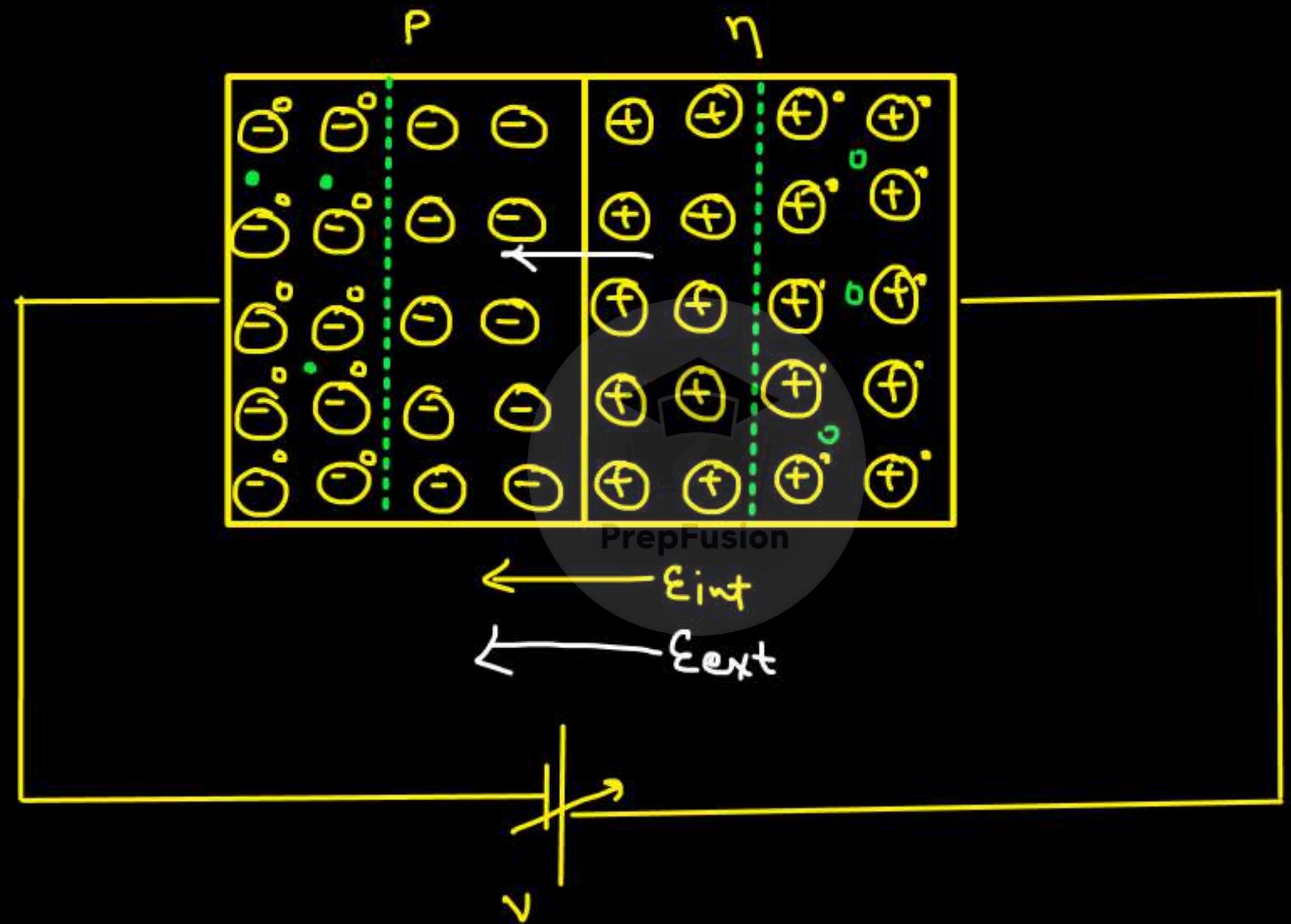



@ a particular reverse bias voltage, (Breakdown voltage)

⇒ $E_{int} \uparrow$ ⇒ free e^- gets High kinetic energy
 (minority) ↓

more e^- ← High e^- knocks out bound e^- from Si

↓

more current

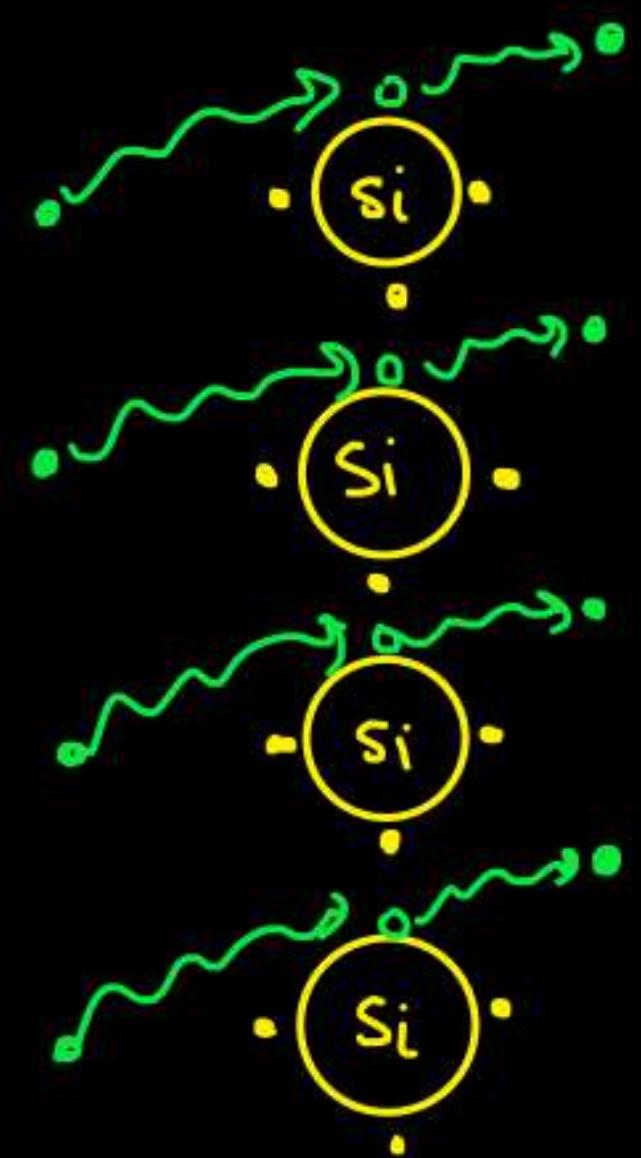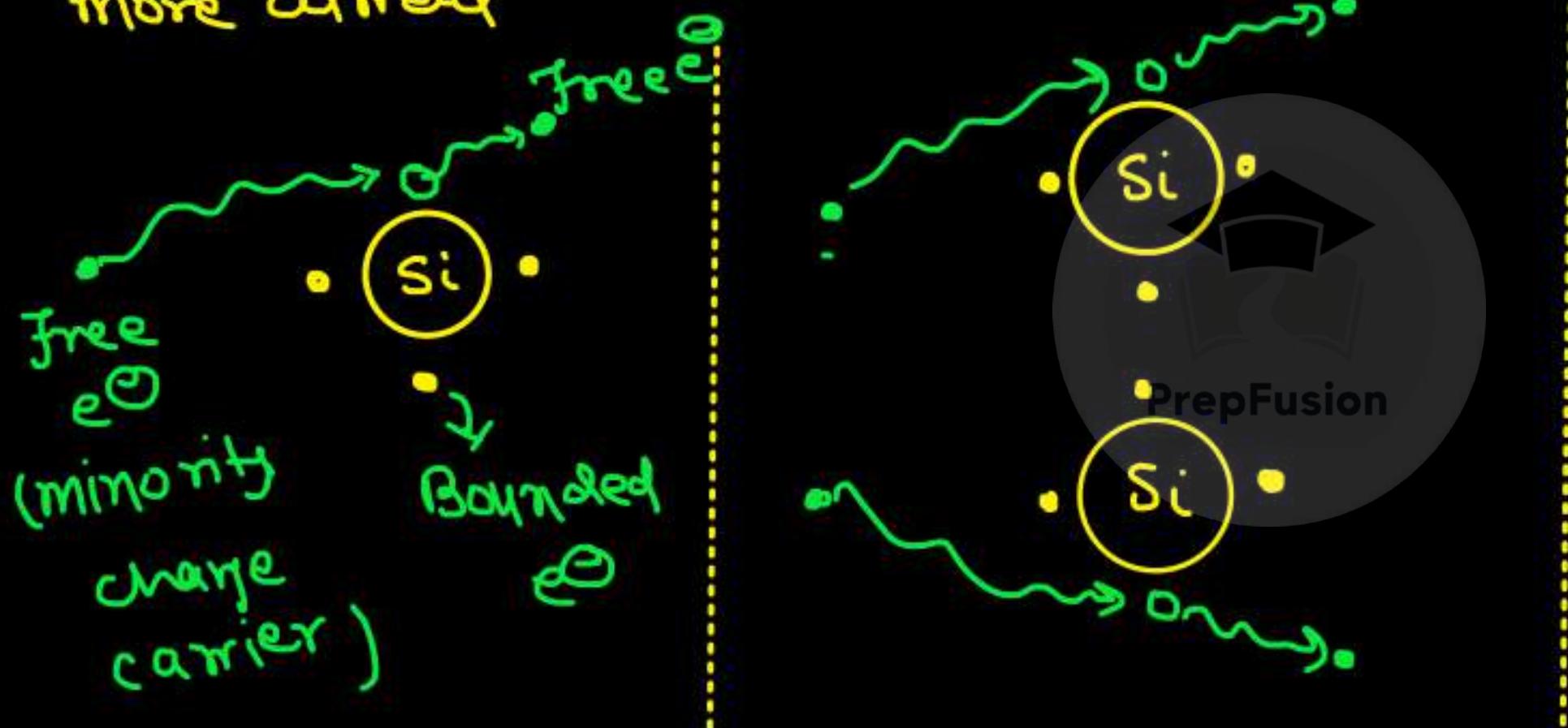




* High energy charge particle knocks out the bounded e^- from silicon atom and thus creating electron-hole pairs and the current increases. This phenomena is known as avalanche breakdown.

- * If there is no limiting resistance, the device may burn out in breakdown region.
- * There are some diodes which is meant to be operated in breakdown region.


↓
Zener diode

[Symbol →


Zener breakdown:-

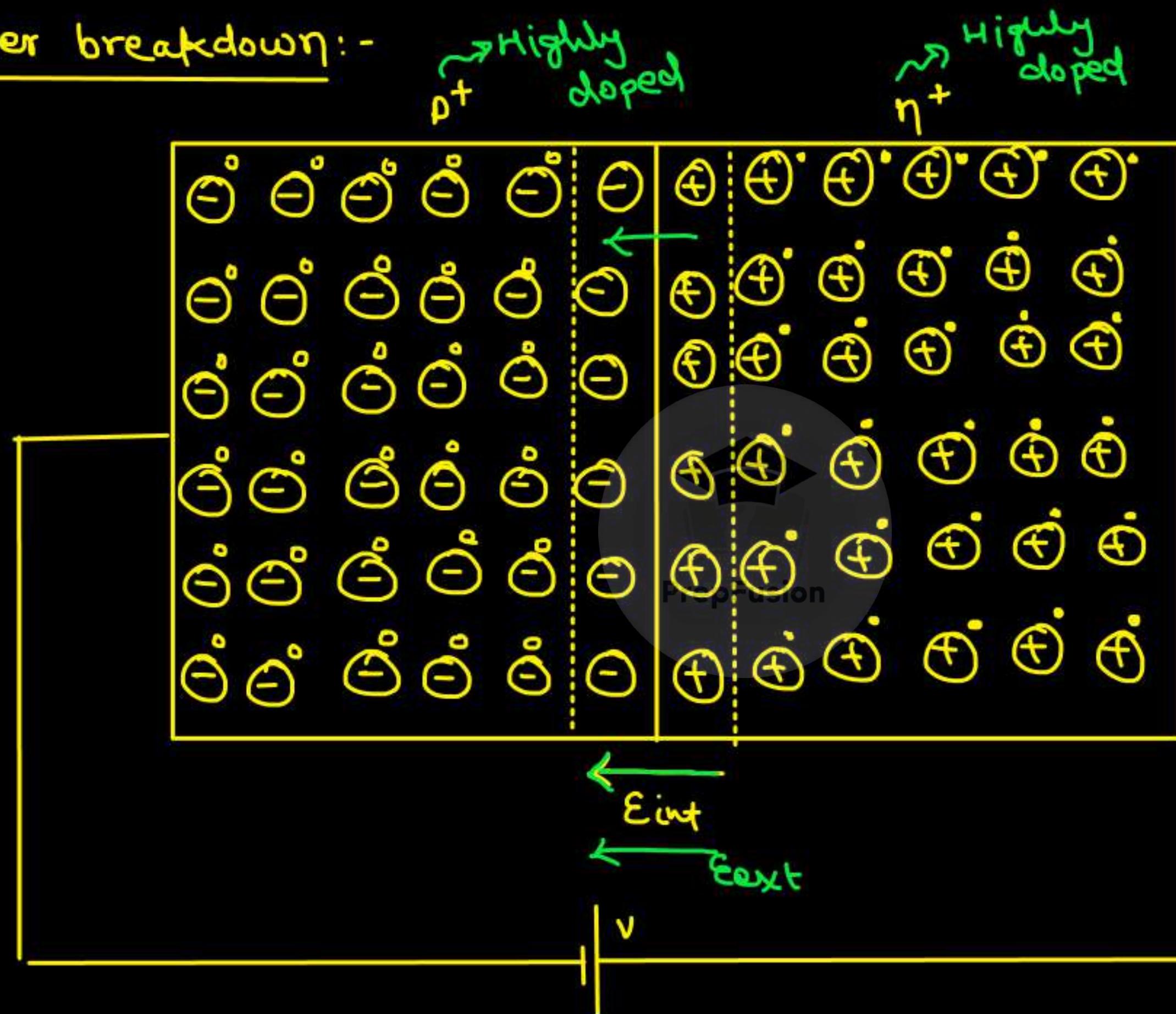

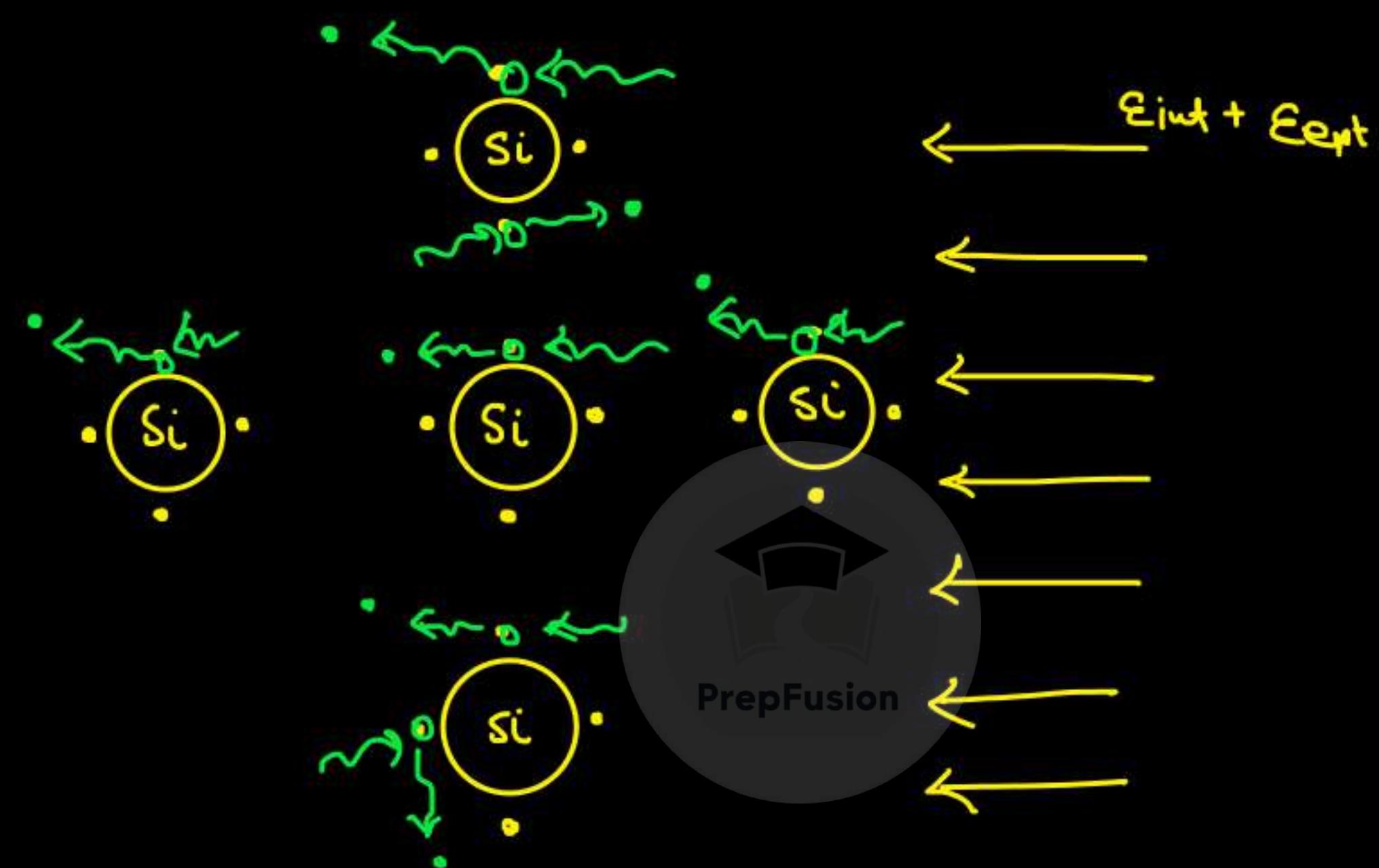Here, because
of more doping
 $\Rightarrow E_{int}$ is
very strong





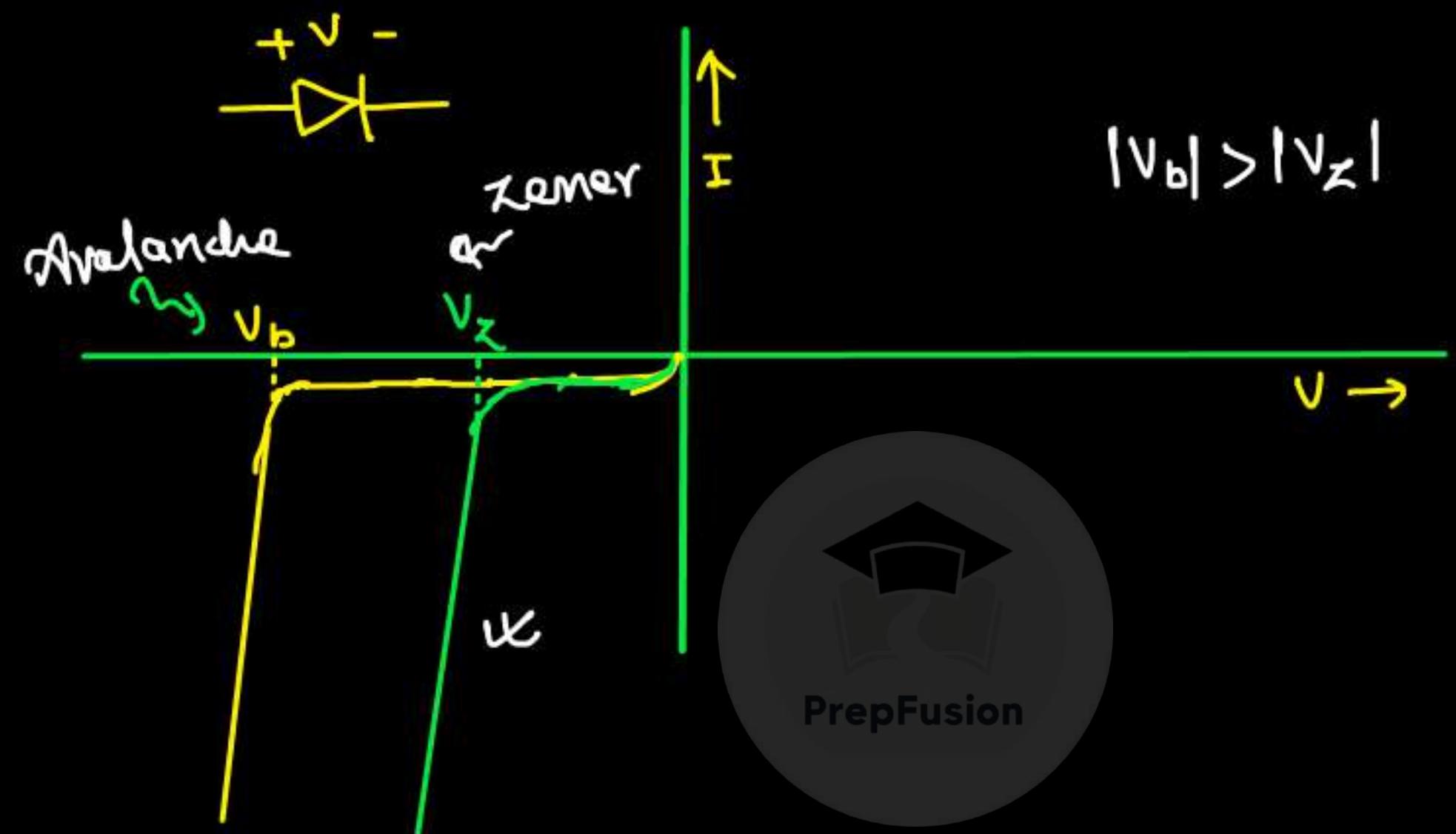$E_{int} + E_{ext}$ knocks out e^- from silicon atoms \rightarrow free $e^- \uparrow$
 \Downarrow
 current I



Zener breakdown occurs @ a lower breakdown voltage than the avalanche breakdown.

Characteristics of Zener diode :-

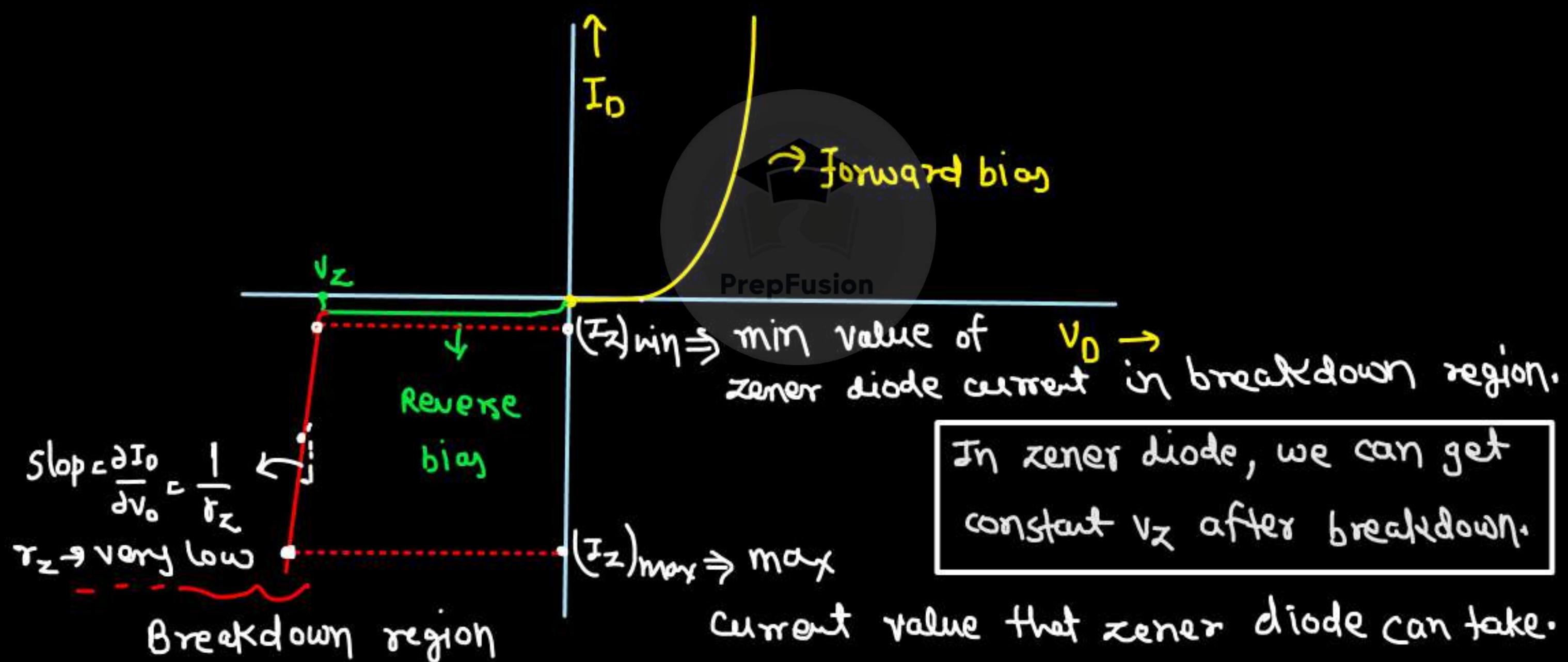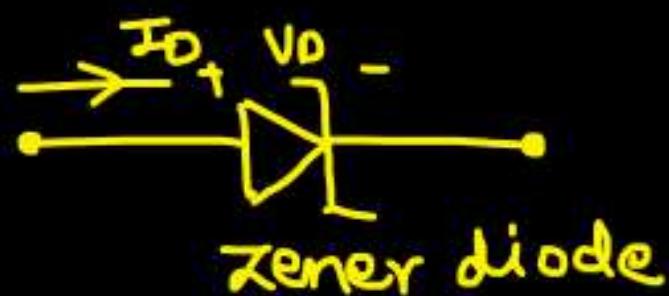

$(I_z)_{\min} \Rightarrow$ when zener is in Breakdown, the min-current it will have.

$(I_z)_{\max} \Rightarrow$ when zener is in Breakdown, the max-current it can have.

if $I_z > (I_z)_{\max} \Rightarrow$ device will burn out.

$r_z \Rightarrow$ when zener is in breakdown, the resistance it provides.

$V_z \Rightarrow$ Breakdown voltage of zener diode.



→ Power rating of zener diode:-

Power rating = $V_z \cdot (I_z)_{\max}$ = Maximum power a zener diode can handle in breakdown region.

Eg. → If a zener diode has $V_z = 5V$

$$(I_z)_{\min} = 5mA, (I_z)_{\max} = 40mA.$$


What is the min power rating of zener diode?

$$\rightarrow 5 \times 40m = 200mw =$$


② A zener diode has $V_z = 5V$ and power rating of $100mw$. What is the max^M current it can take?

$$\rightarrow \frac{100m}{5} = 20mA \leftarrow \text{max}^M 2mA \text{ current should flow through zener diode.}$$


→ Zener diode in forward bias:-

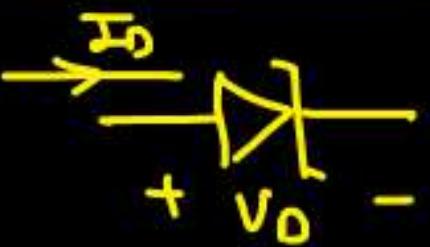

→ Acts as normal forward bias diode.

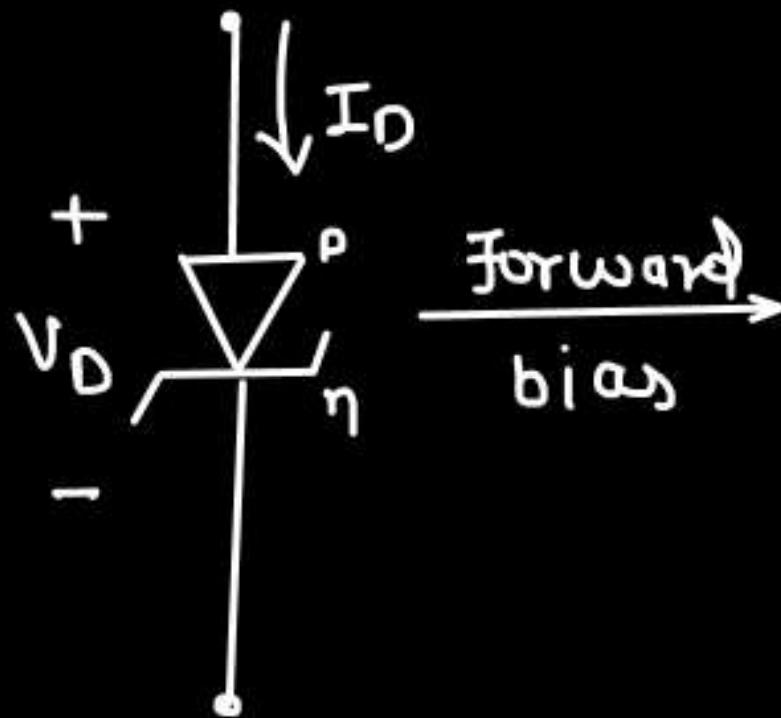


Ideal

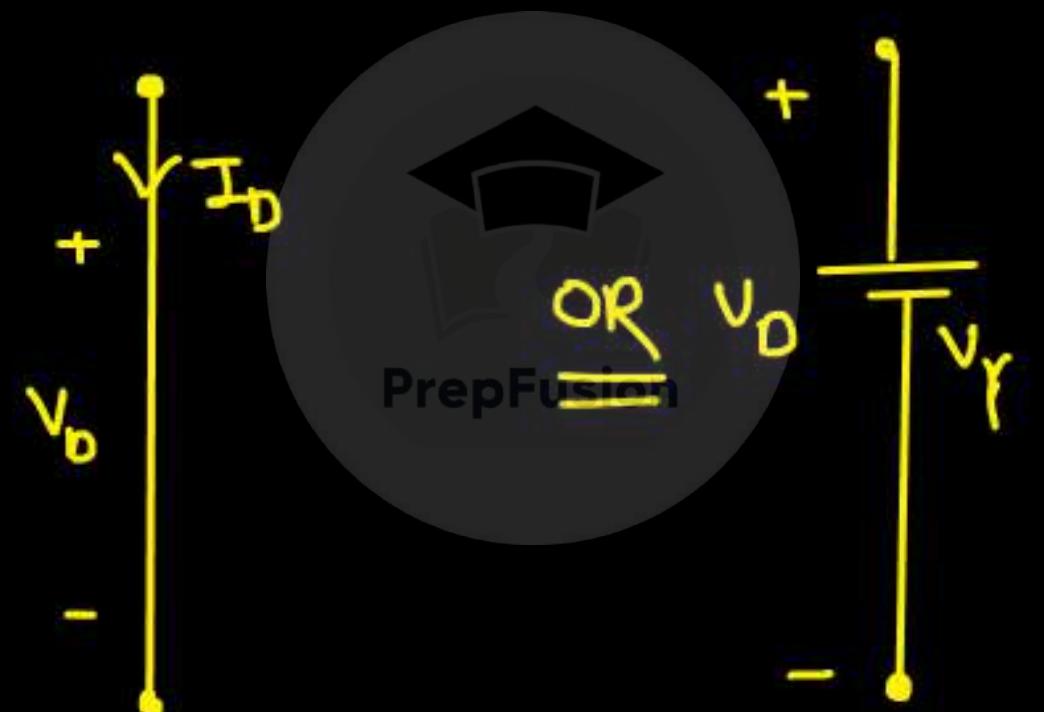

Constant
voltage drop

OR



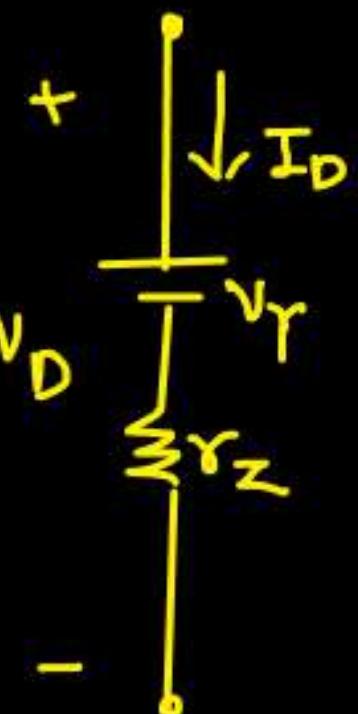


Piecewise
Linear Model






⇒ Zener diode in reverse bias :-
(Before Breakdown)

=====

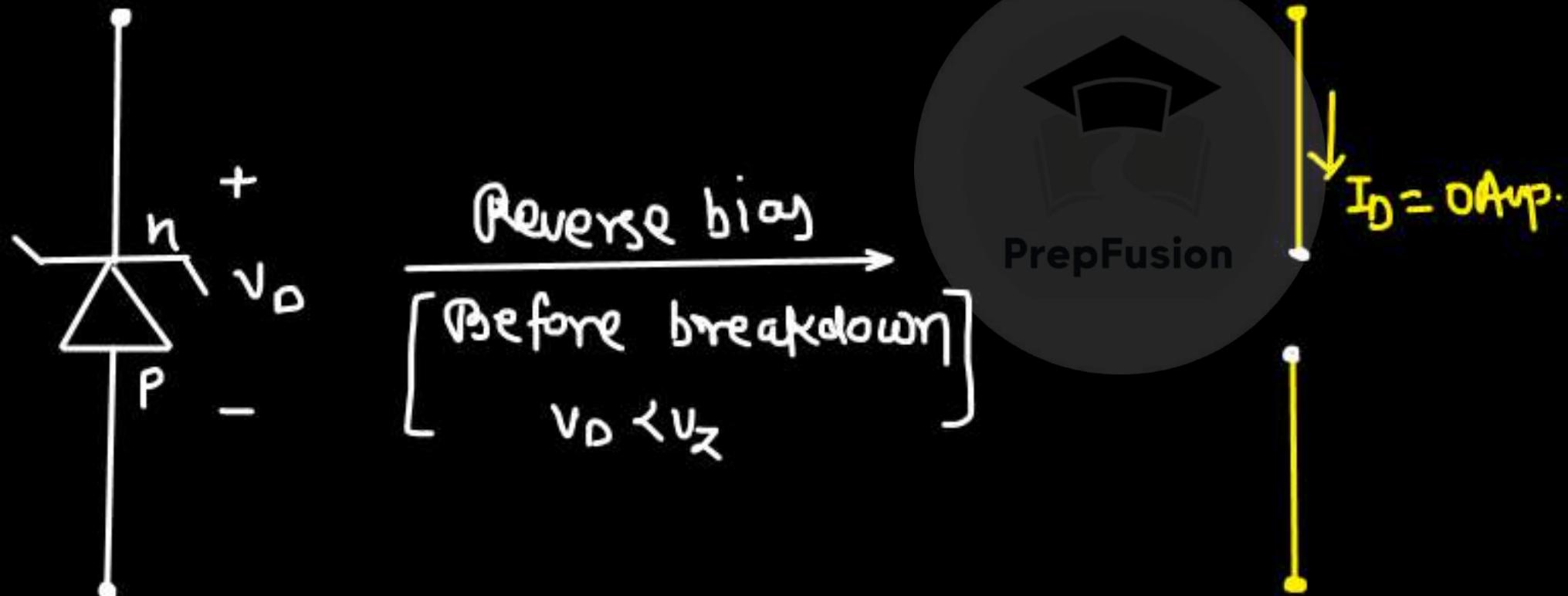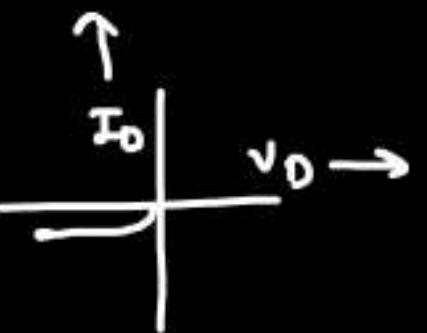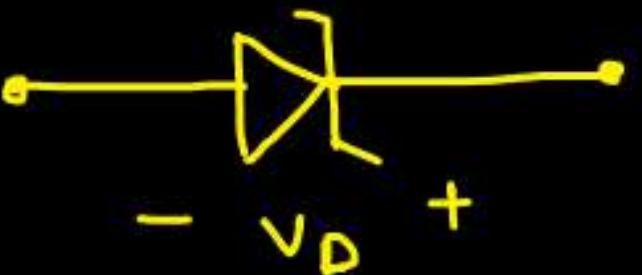





⇒ Zener diode in Breakdown :-

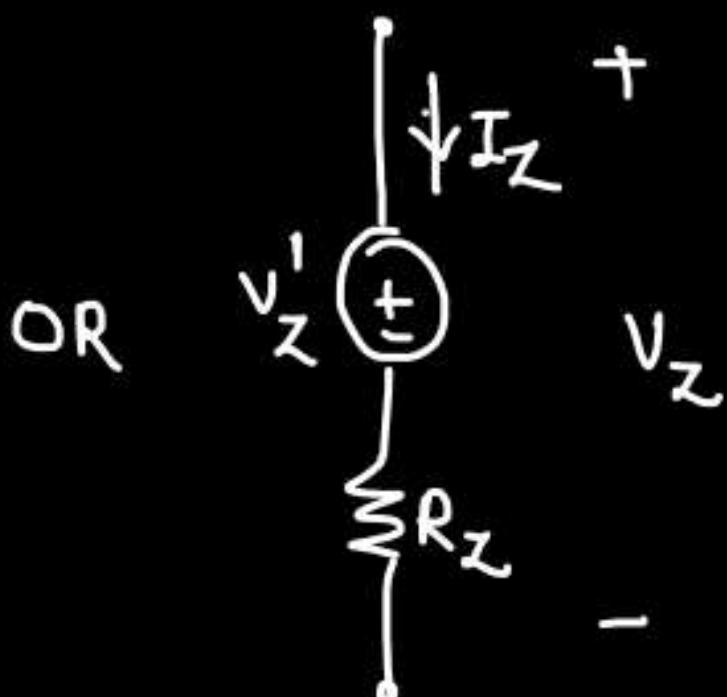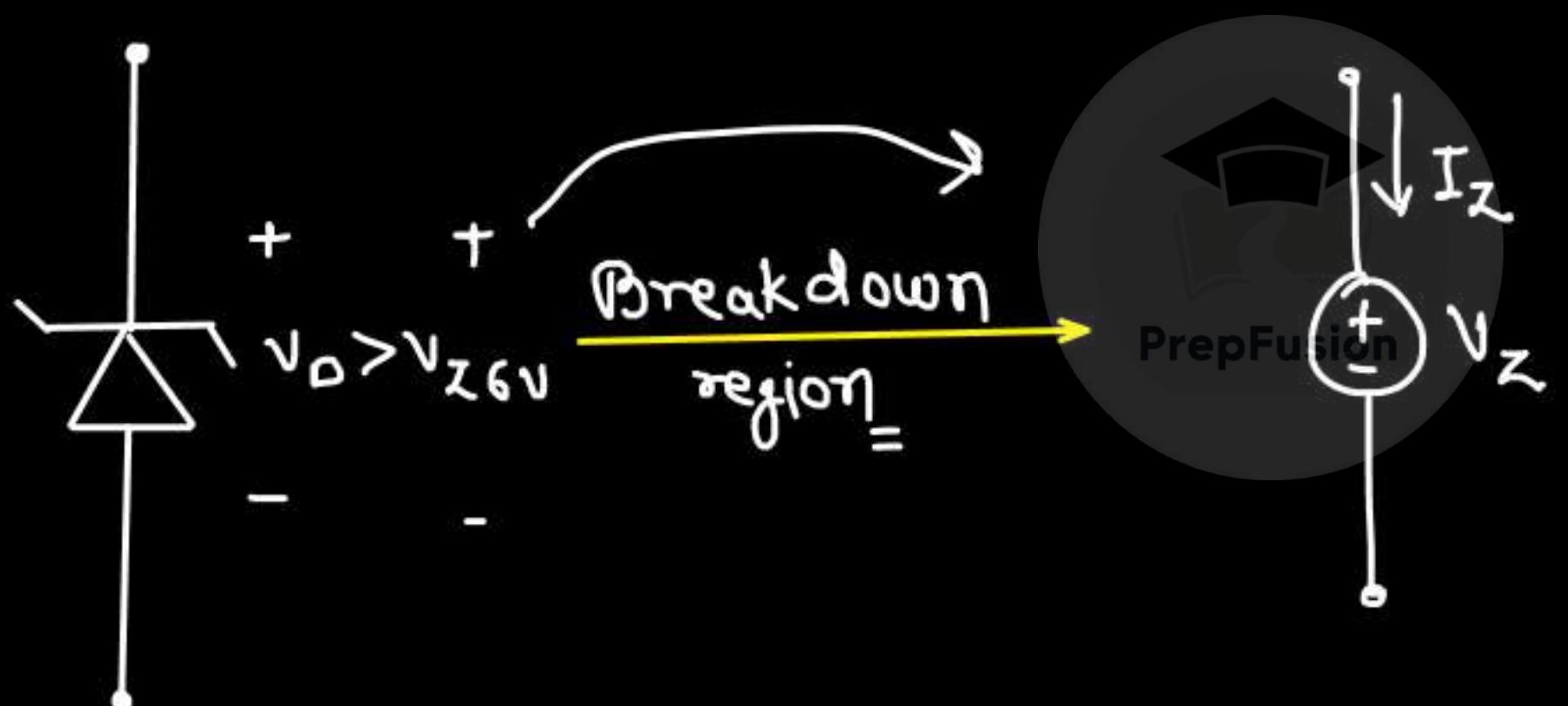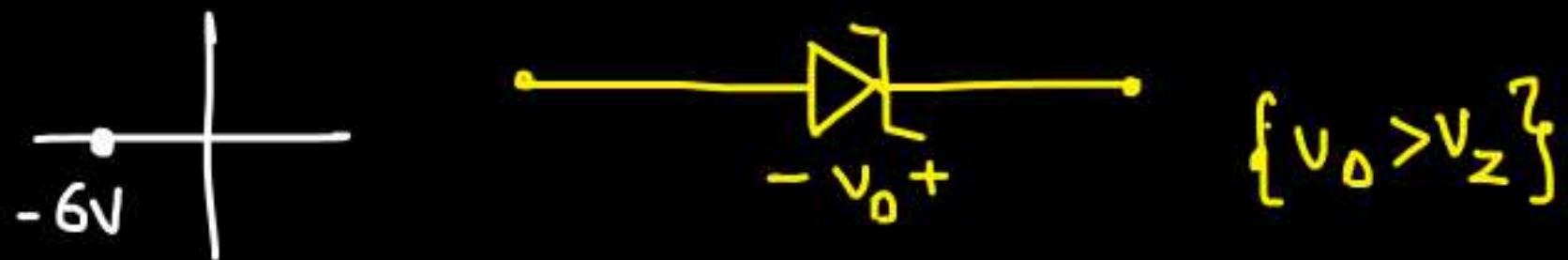


$$v_z = v_z' + I_z R_z$$

Q. The zener diode has breakdown voltage of 5V.

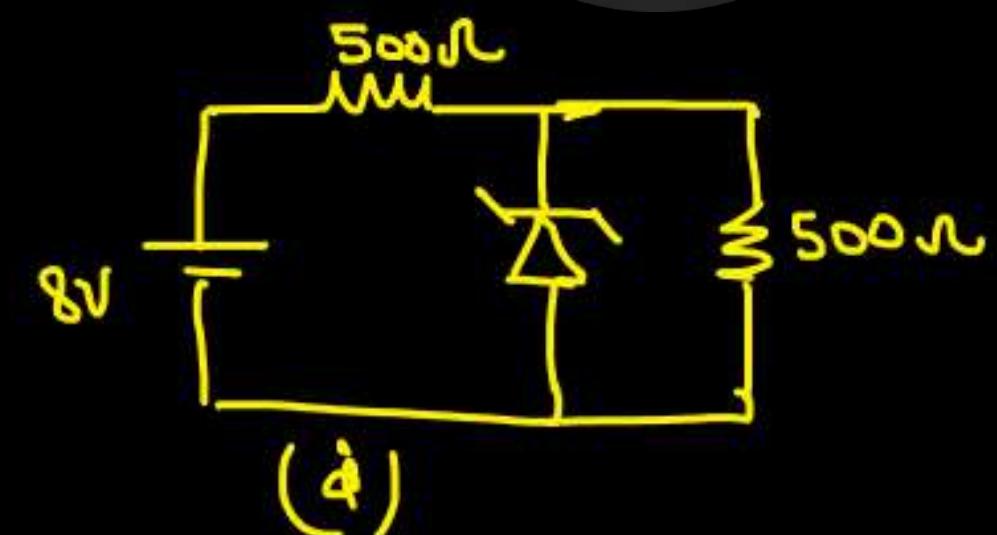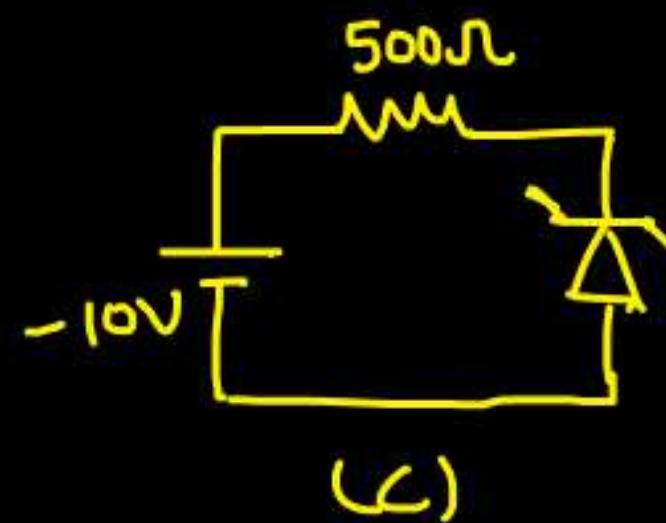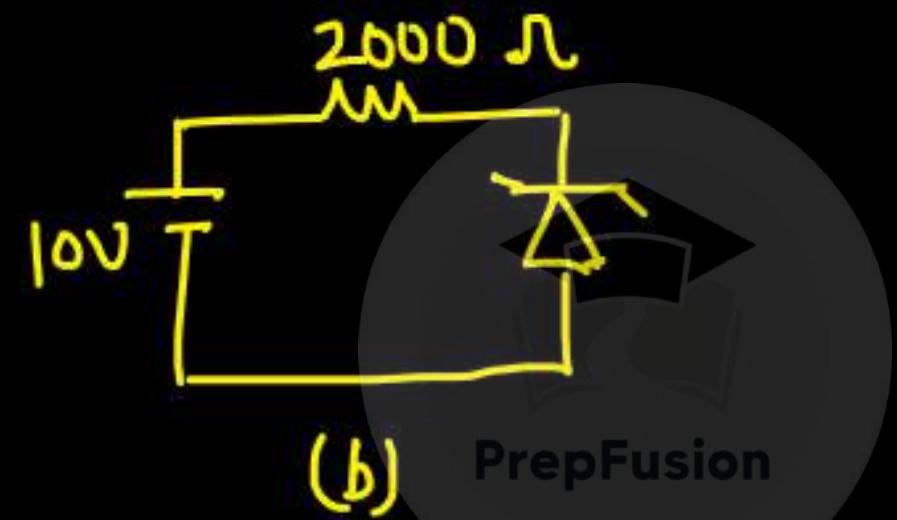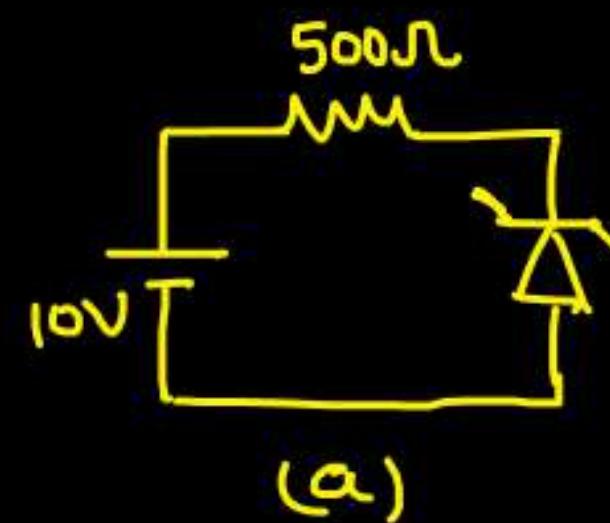
$(I_z)_{min} = \underline{\underline{5mA}}$ • check if zener goes in breakdown region or not.



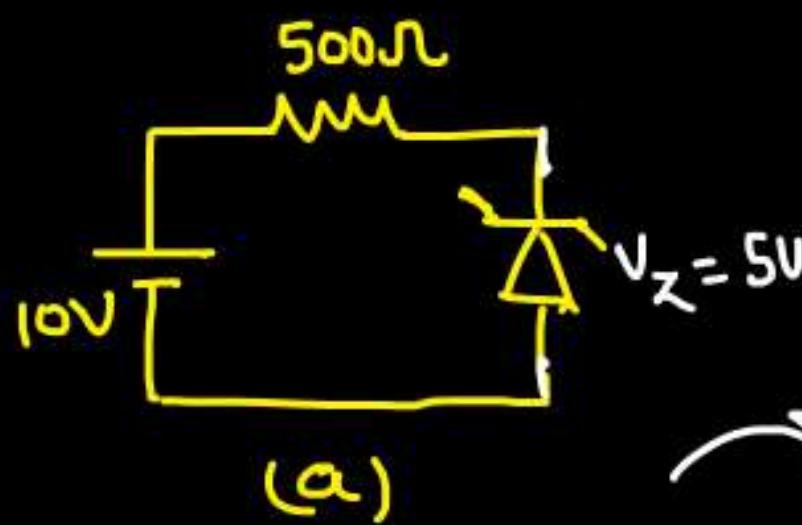


(a)

$$V_Z = 5V, (I_Z)_{\min} = 5mA$$

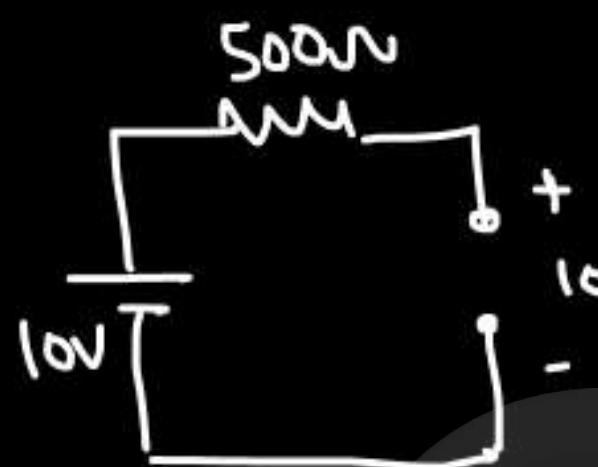


Zener can go into breakdown region

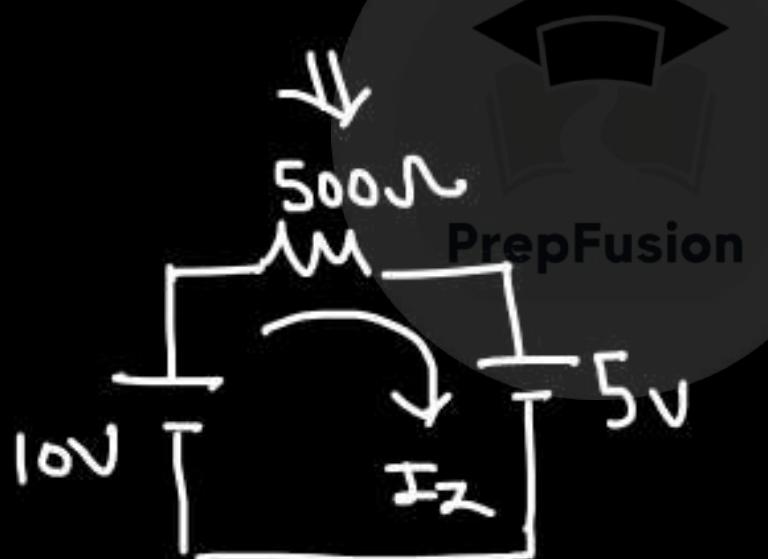

$$I_Z = \frac{5}{500} = 10mA > I_{Z\min}$$

⇒ Zener goes into breakdown

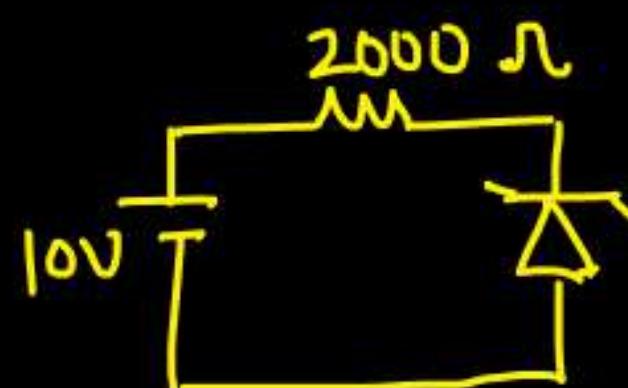

$$V_Z = 5V, (I_Z)_{min} = 5mA$$

→ it may go into breakdown

(b)




$$I_Z = \frac{5}{2000} = 2.5mA < (I_Z)_{min}$$


no, zener doesn't go into breakdown.



Zener is in reverse bias only.

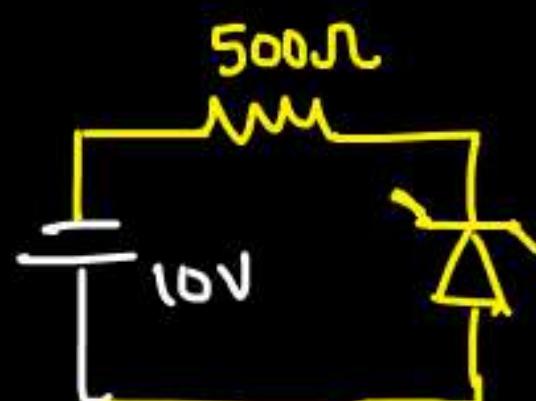
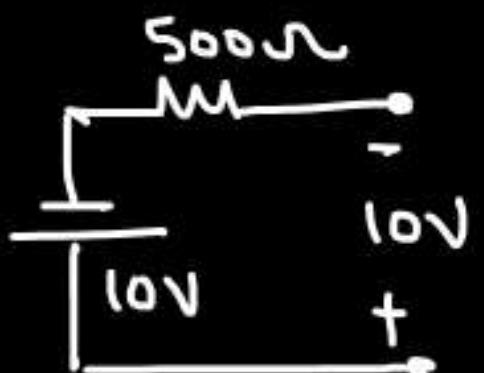
$$V_Z = 5V, (I_Z)_{\min} = 5 \text{ mA}$$



forward biased

↳ Zener is forward biased.




$$V_{\text{Zener}} = 4V < V_Z$$

↳ Zener is in reverse bias (not in breakdown)


⇒ Zener diode as a voltage regulator:-

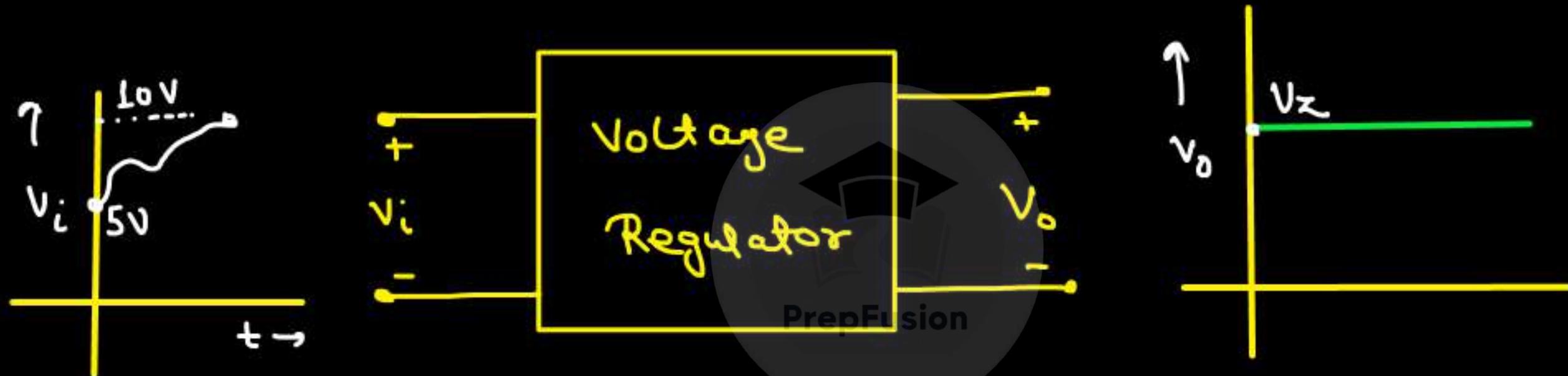voltage regulator:- Having a constant / regulated voltage o/p.



Voltage regulation is required in these cond'n.

① Line (Supply) variation

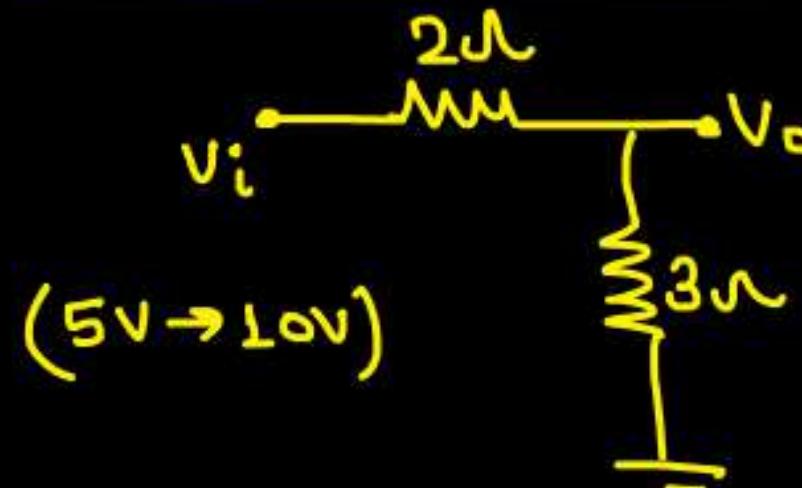


when $V_i = 5V \Rightarrow V_o = \frac{3}{5} \times 5 = 3V$

when $V_i = 10V \Rightarrow V_o = 6V$

$\Rightarrow V_o = 3V \rightarrow 6V$

② Load variation :-

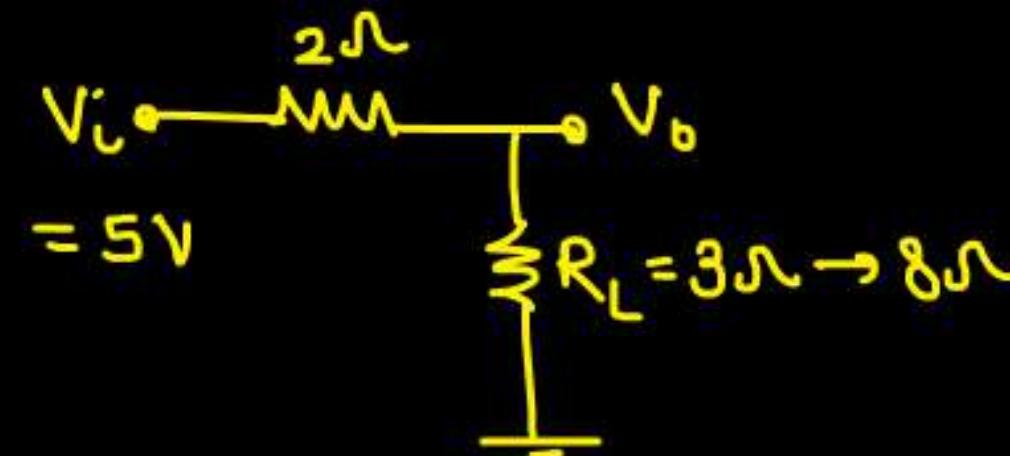

when $R_L = 3\Omega, V_o = 3V$

$R_L = 8\Omega, V_o = 4V$

$V_o = 3V \rightarrow 4V$


You want constant o/p voltage.

Here, your o/p is varying, but you want a regulated o/p (fixed o/p).



Use Zener diode

(i) When supply varies:-

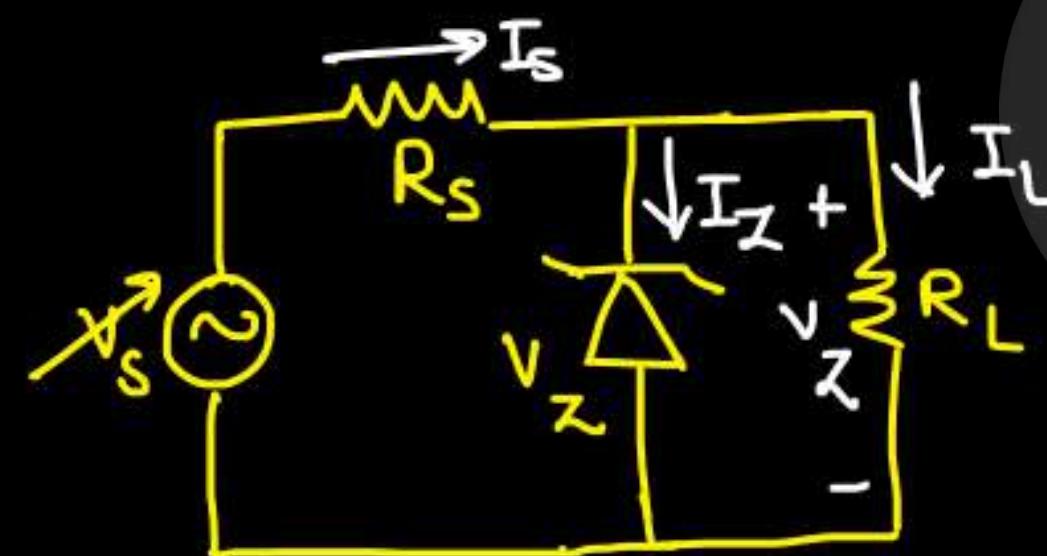

Considering zener in breakdown.

$$I_L = \frac{V_z}{R_L} \Rightarrow \text{fixed} - \odot$$





$$I_S = I_Z + I_L \quad \text{--- ②}$$

$$I_S = \frac{V_S - V_Z}{R_S} \quad \text{--- ③}$$

if $V_S \rightarrow \min \Rightarrow I_S \rightarrow \min \Rightarrow I_Z \rightarrow \min =$

4*4*

if zener is having minimum current \Rightarrow supply is also @ minimum

if zener is having maximum current \Rightarrow supply is also @ maximum

PrepFusion


Zener current \propto Supply voltage (Analogy)

LECTURE - 1

 Watch on  YouTube

 AIR 27 (ECE)
 AIR 45 (IN)

When load varies :-

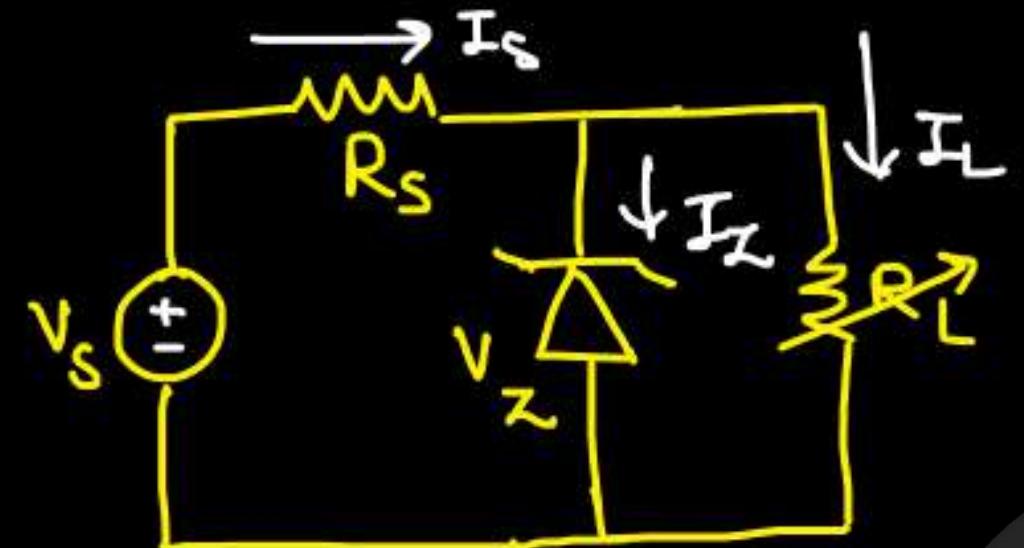

Considering Zener in breakdown

$$I_s = \frac{V_s - V_z}{R_s} \rightarrow \text{PreFusion} \quad \text{--- ①}$$

$$I_L = \frac{V_z}{R_L} \quad \text{--- ②}$$

$$I_s = I_z + I_L \quad \text{--- ③}$$



If $R_L \rightarrow \text{max} \Rightarrow I_L \rightarrow \text{min} \Rightarrow I_Z \rightarrow \text{max}$

if $R_L \rightarrow \text{min} \Rightarrow I_L \rightarrow \text{max} \Rightarrow I_Z \rightarrow \text{min}$


if load current is min , Zener current would be maximum.

if load current is max, Zener current would be minimum.

$$I_L \propto \frac{1}{I_Z} \text{ (Analogy)}$$

PreFusion

Q. Find the current through zener diode.

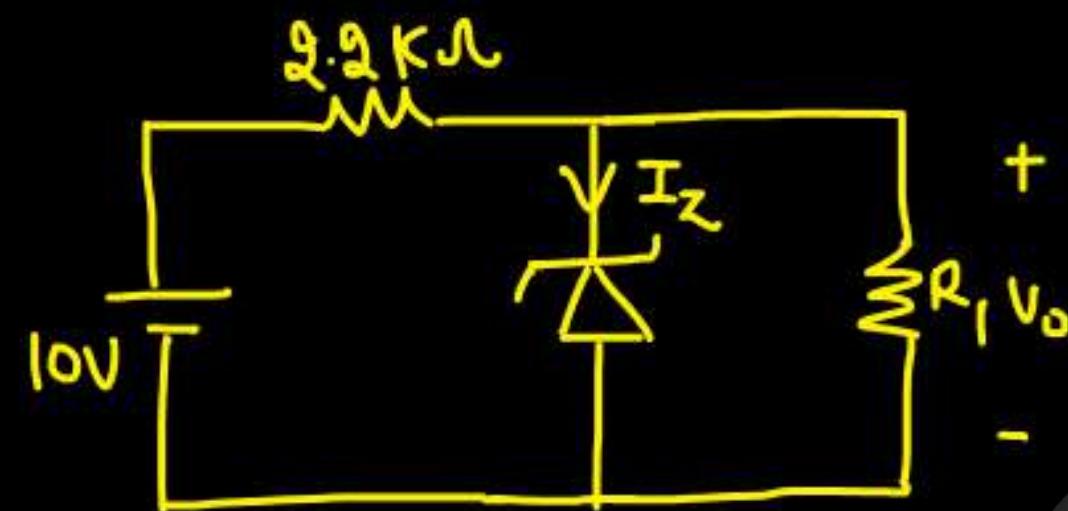


$$(i) V_o = 3.5V$$

$$(ii) V_o = 3V$$


$$V_Z = 3.3V, R_Z = 0.1k\Omega$$

→ (i) $V_o = 3.5V$

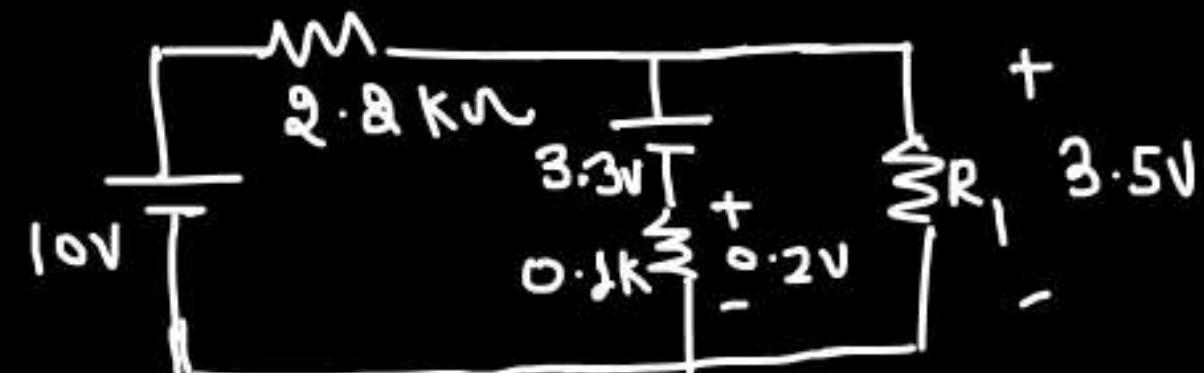

$$I_Z = \frac{0.2}{0.1k} = 2mA$$

(ii)

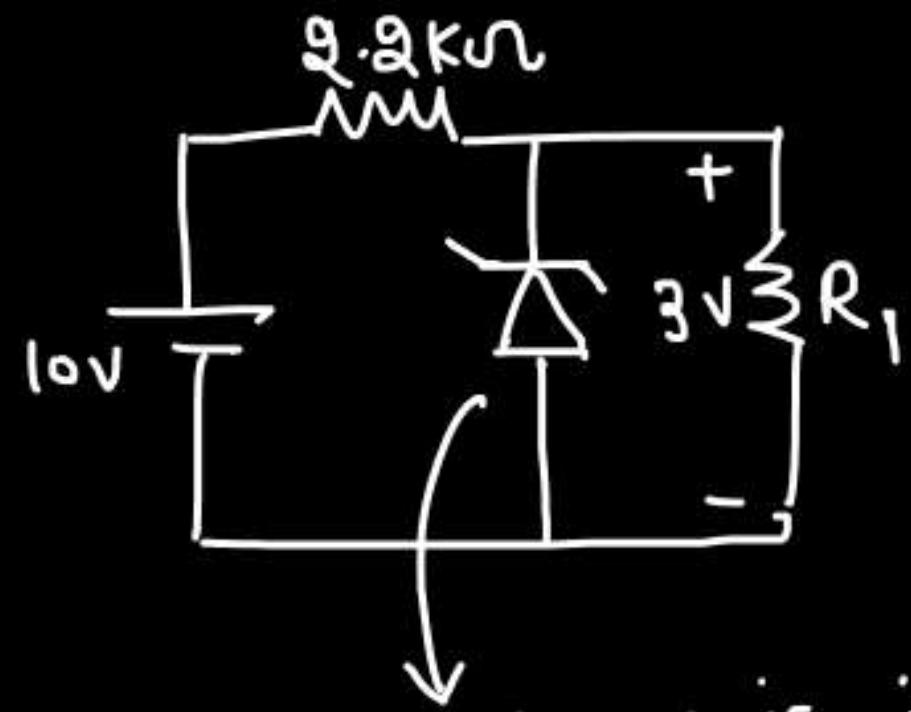


Zener is in reverse bias not in breakdown.

$$I_z = 0 \text{ A}$$

I_z = 0 A
PrepFusion

Q.

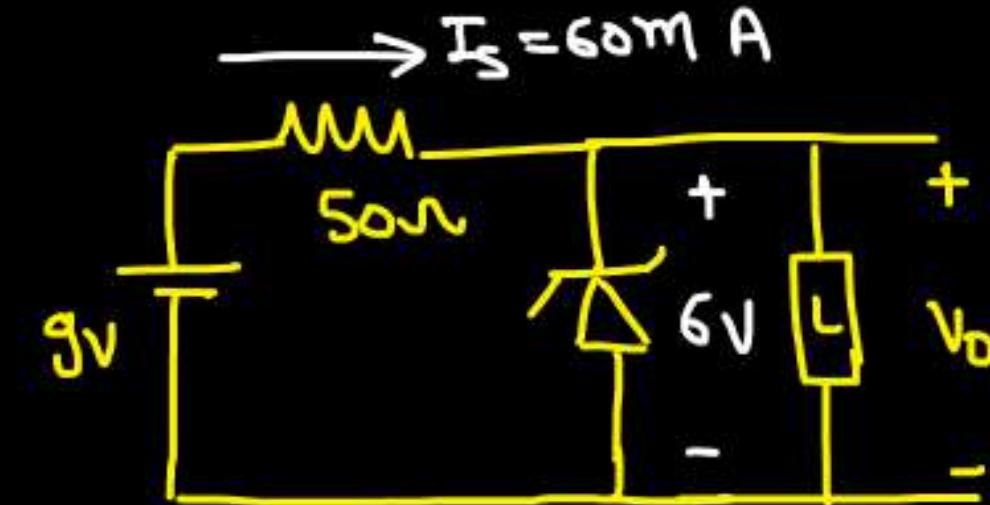

→ Load Variation

min current

The Zener diode in the circuit shown in the figure has a knee current of 5 mA, and a maximum allowed power dissipation of 300 mW. What are the minimum and maximum load currents that can be drawn safely from the circuit, keeping the output voltage V_0 constant at 6 V?

$$\rightarrow (I_Z)_{\min} = 5 \text{ mA}$$

$$V_Z = 6 \text{ V}$$

$$P_{\max} = 300 \text{ mW}$$

$$6 \times (I_L)_{\max} = 300 \text{ mW}$$

$$I_S = I_Z + I_L$$

$$60 \text{ mA} = (I_Z)_{\min} + (I_L)_{\max}$$

$$(I_L)_{\max} = 55 \text{ mA}$$

$$I_S = \frac{3}{50} = 60 \text{ mA}$$

(i) if I_Z is min $\Rightarrow I_L$ will be max


$$(I_L)_{\min} = 10 \text{ mA}$$

$$60 \text{ mA} = (I_Z)_{\max} + (I_L)_{\min}$$


Q. $(I_Z)_{\min} = 25\text{mA}$, $(I_Z)_{\max} = 50\text{mA}$

The value of R required for satisfactory voltage regulation of the ckt is →

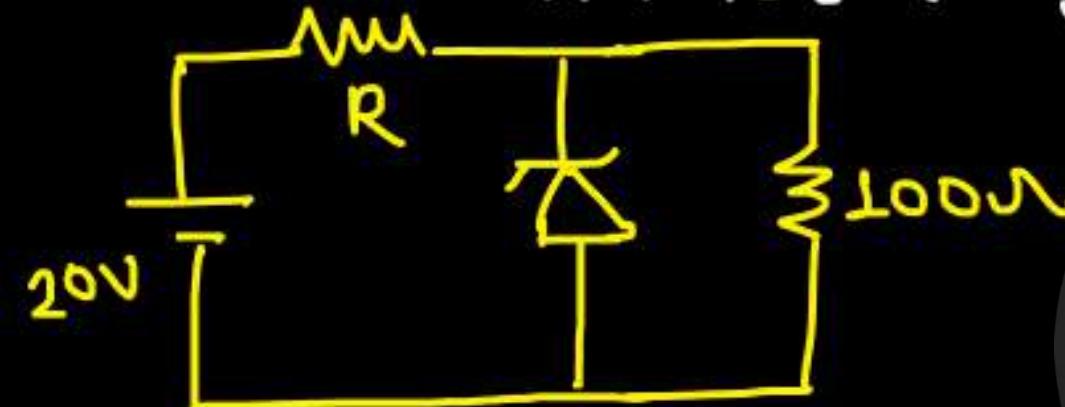↳ minimum cond'n
↳ Zener has to go into B.D.




$$V_Z = 10\text{V}$$

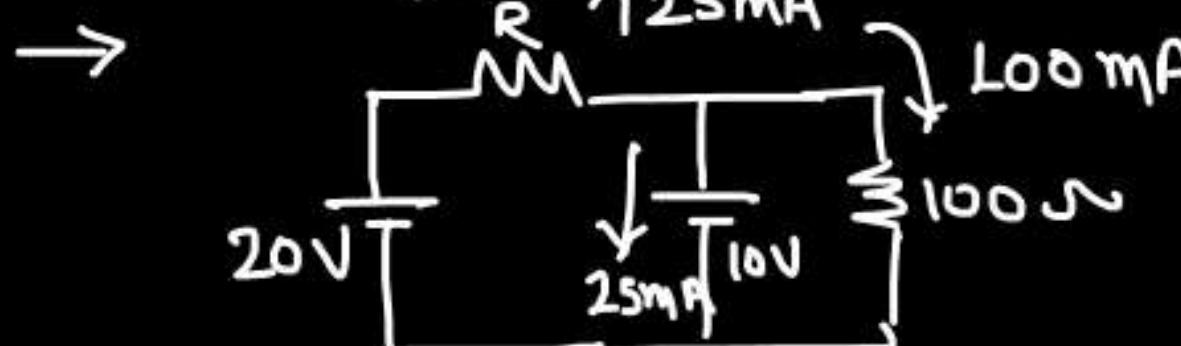



$$\frac{20 - 10}{R} \geq 125 \text{ mA}$$

R = 80Ω

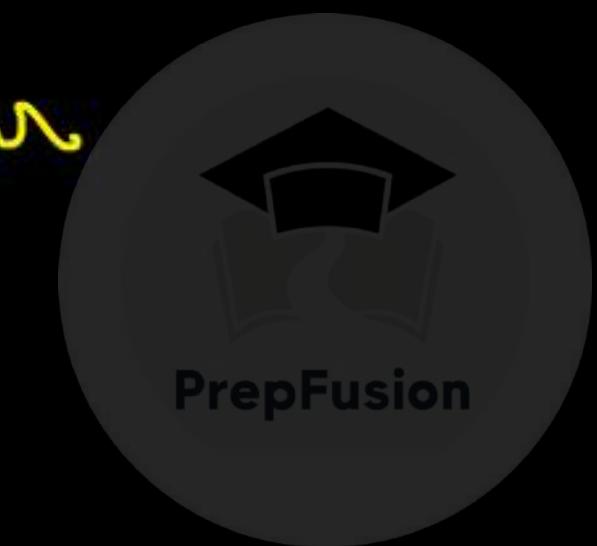

Q. Find the range of V_i for the zener to remain in "ON & Safe" state.
 min cond \leftarrow \rightarrow max cond


$$V_z = 20V, (I_z)_{\max} = 50mA$$

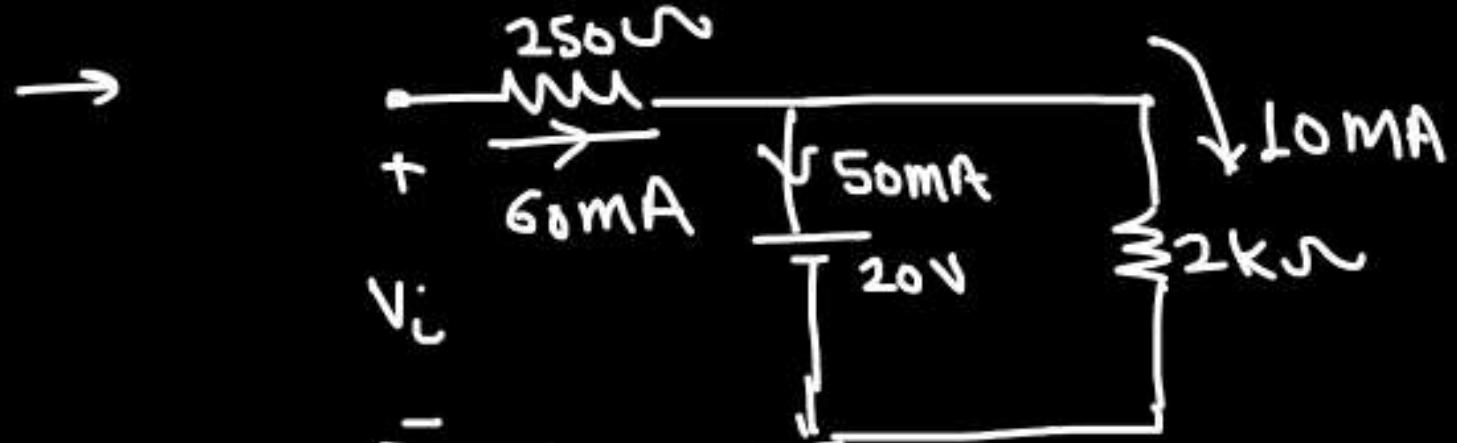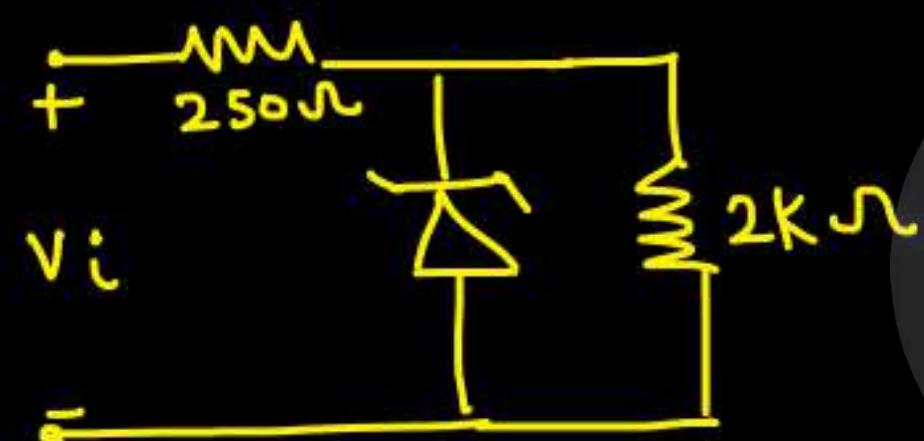

if $I_z \rightarrow \text{max} \Rightarrow V_i \rightarrow \text{max}$

$$\frac{V_i - 20}{250} = 60mA$$

$$(V_i)_{\max} = 35V$$

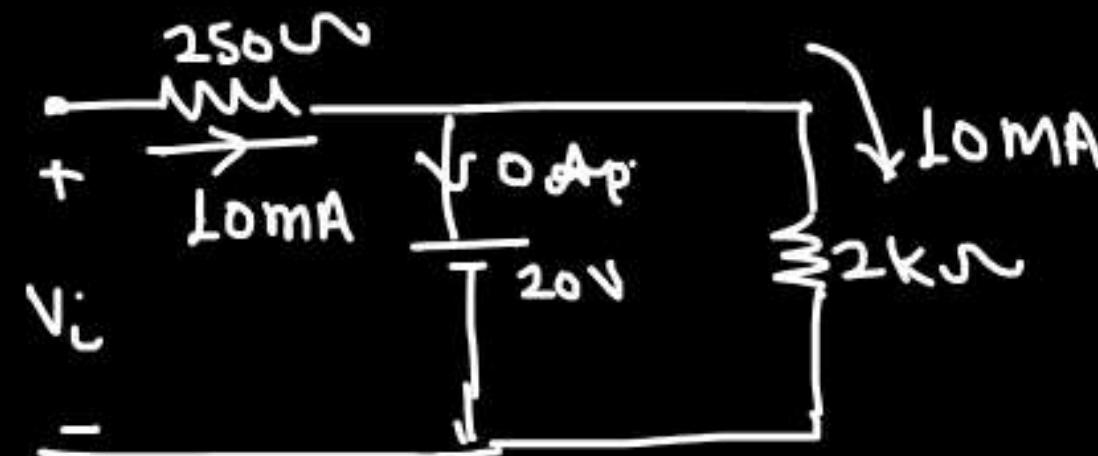

$(I_Z)_{min} \rightarrow$ not mentioned

$(I_Z)_{min} = 0 \text{ Amp.}$

$I_Z \rightarrow \min \Rightarrow V_i \rightarrow \min$

$$\frac{(V_i)_{min} - 20}{250} = 10 \text{ mA}$$

$(V_i)_{min} = 22.5 \text{ V}$


PrepFusion



Q. $V_Z = 5.8V$, $(I_Z)_{min} = 0.5mA$, $(I_Z)_{max} = 20mA$

Find the max and min current drawn by the load.


Input voltage ranges from 20V to 30V.

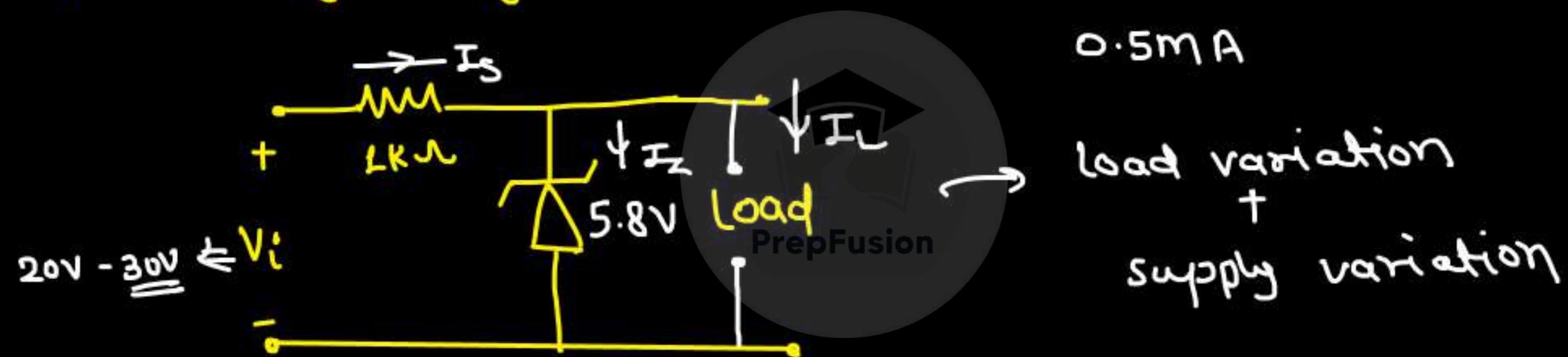

Ans

⇒ Load current min \Rightarrow Zener current max \Rightarrow Supply voltage max
 Load current max \Rightarrow Zener current min \Rightarrow Supply voltage min

(i) max load current

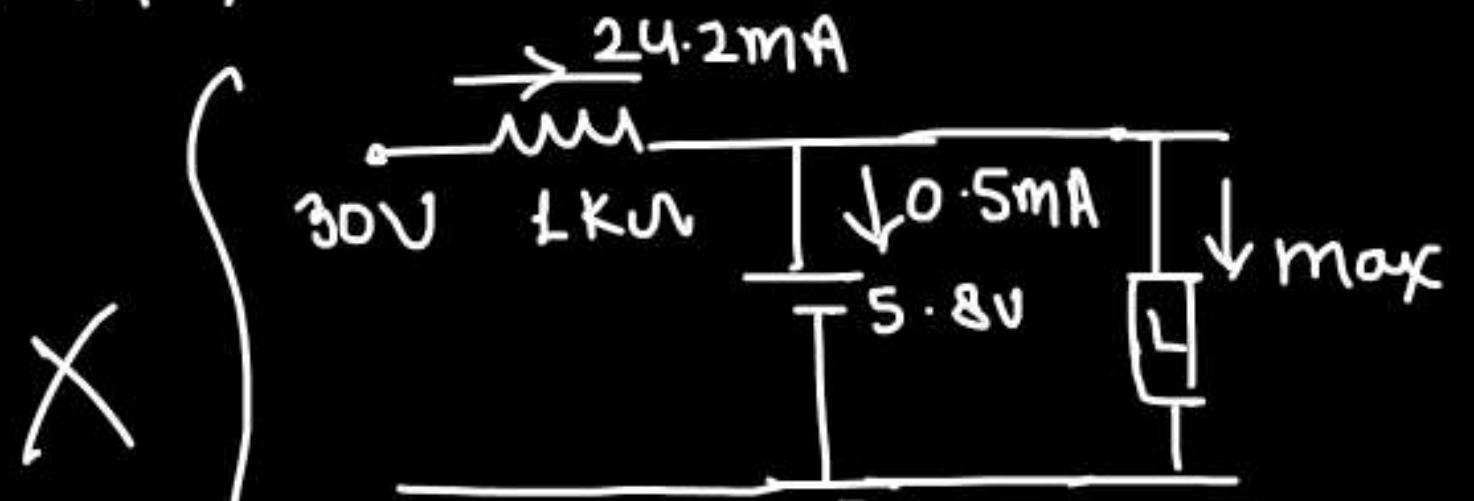


For max current, I will take supply to be max

$$(I_U)_{\text{max}} = 23.7 \text{ mA}$$

Preprusion


When your supply is max, then zener current will certainly be max \Rightarrow if zener current is max^m, the load current would be min

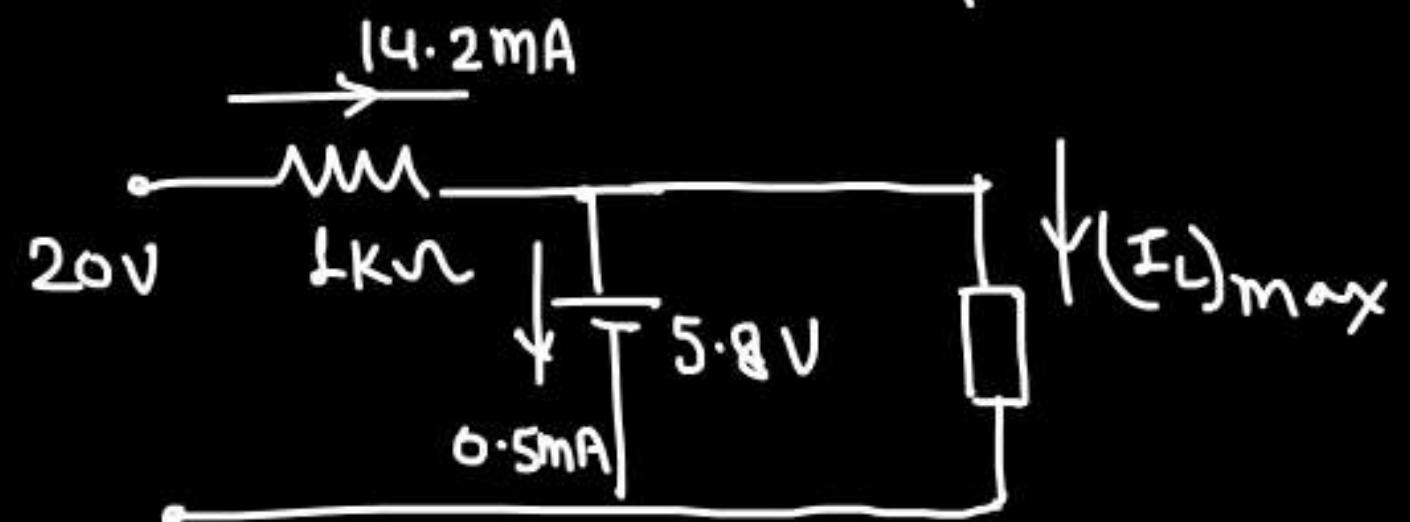(i) Max load current \Rightarrow min zener current \Rightarrow min supply



$$(I_L)_{\max} = 13.7 \text{ mA}$$

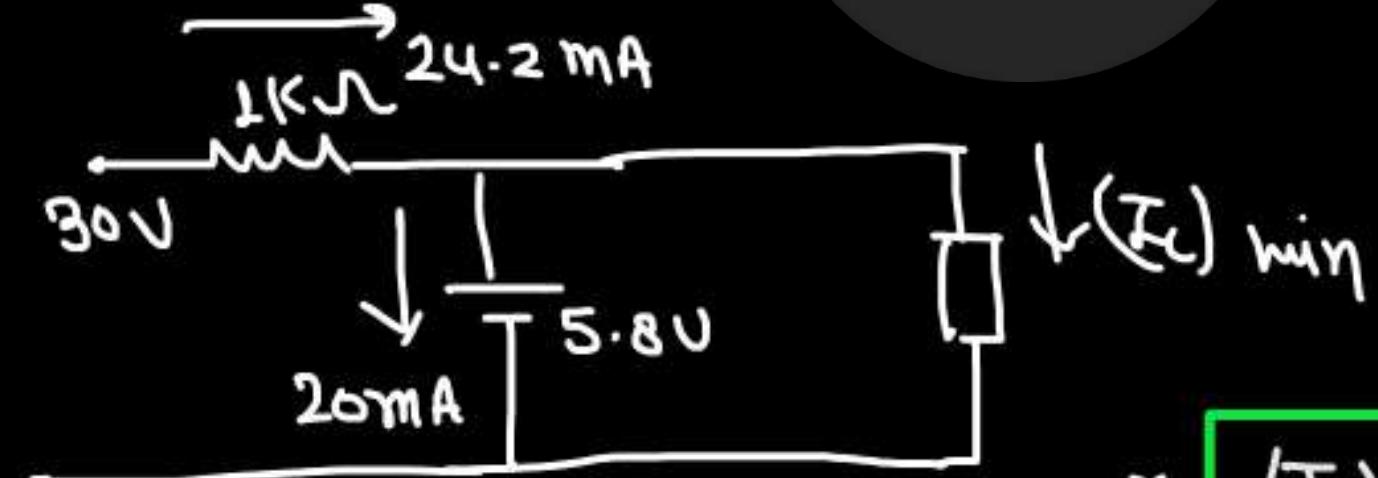(ii) min load current \Rightarrow max zener current \Rightarrow max supply



$$(I_L)_{\min} = 4.2 \text{ mA}$$



Clipper Circuits

What is clipper Circuits?


- ↳ diode clks can be used to clip a certain portion of input signal without distorting the remaining part of the signal.

Any application?


- ↳ To remove noise from a signal

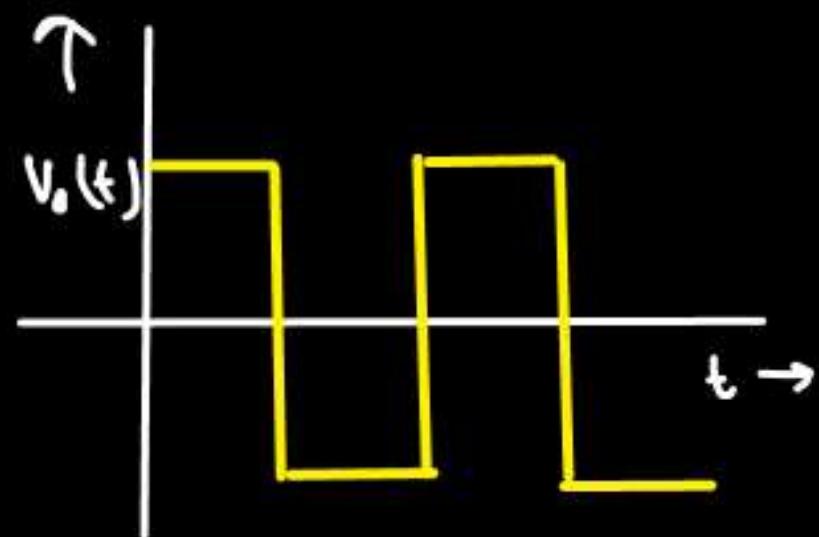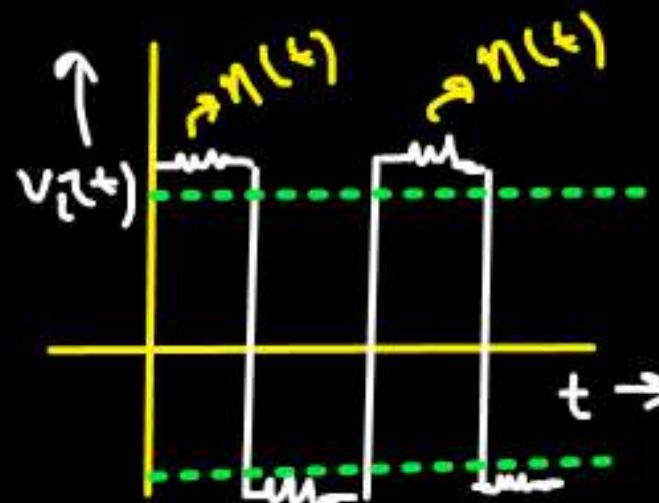



Types of Clipper Ckt (Single level)

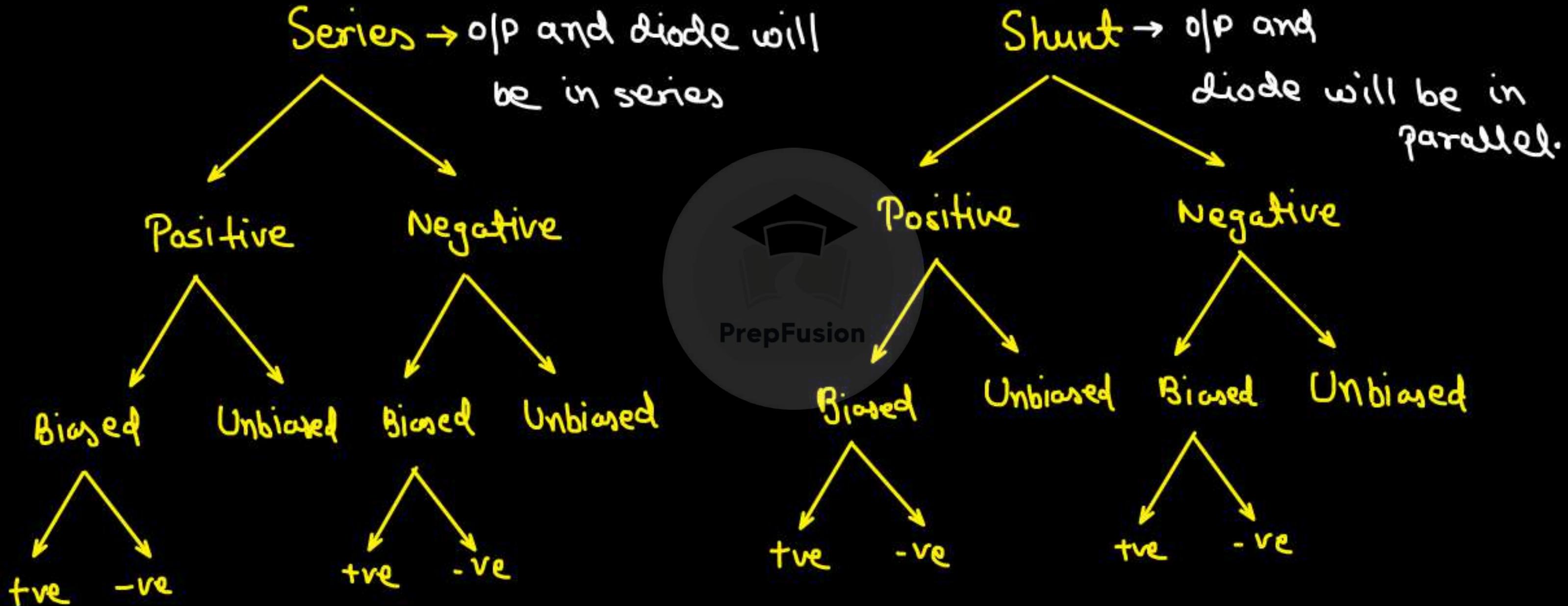

1. Positive series Clipper (Unbiased) :-

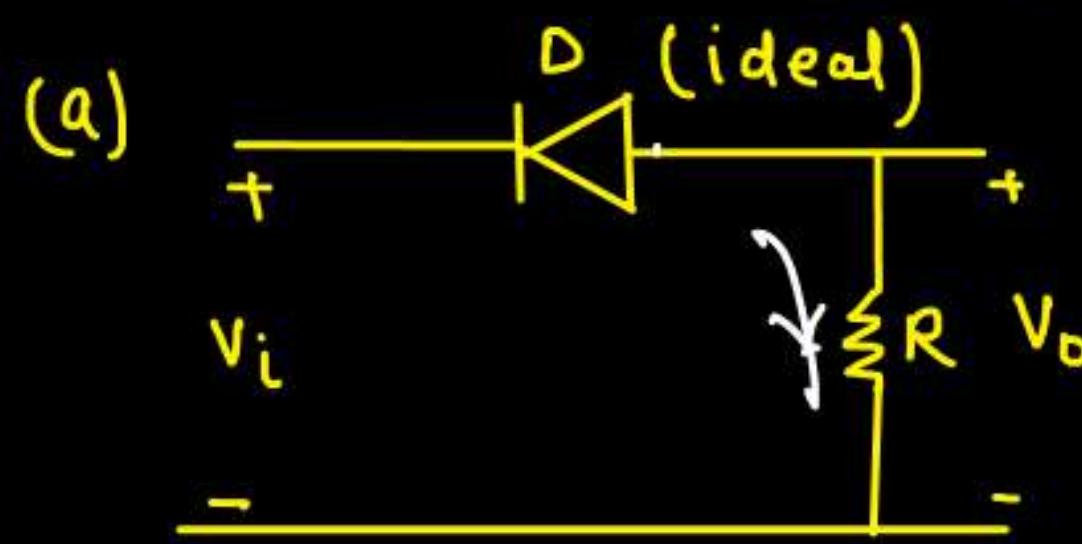


Voltage Transfer Characteristics
(VTC)

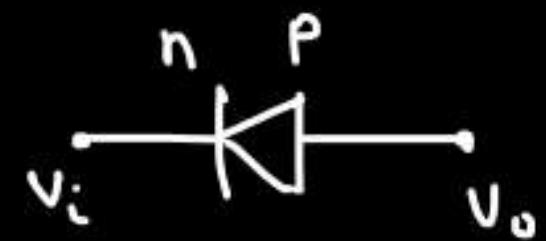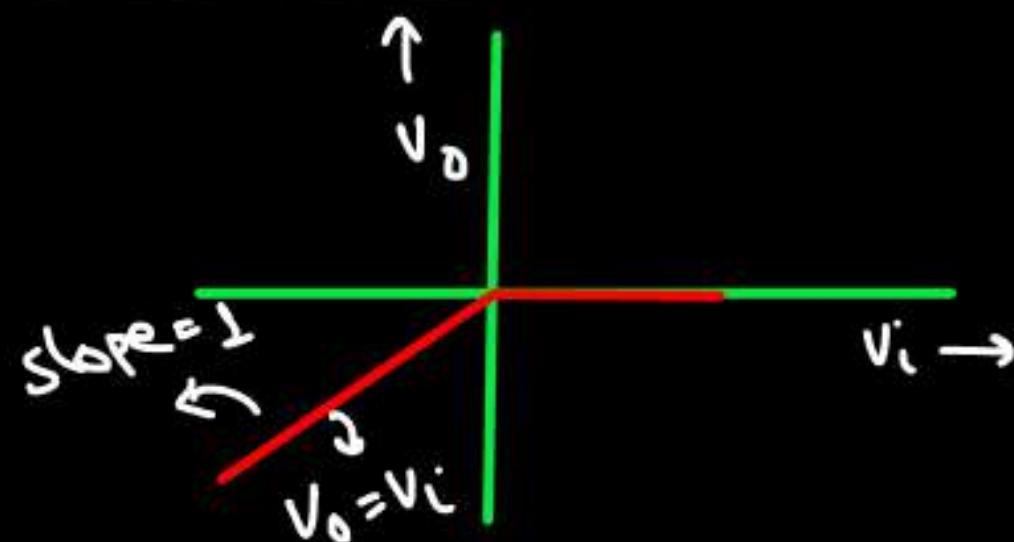

(i) $V_i > 0$




\Rightarrow diode off
 $V_o = 0V$

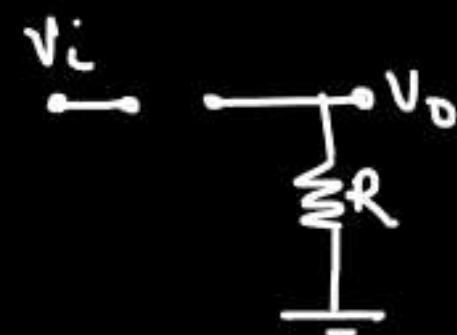


(ii) $V_i < 0$




\Rightarrow diode on
 $V_o = V_i$



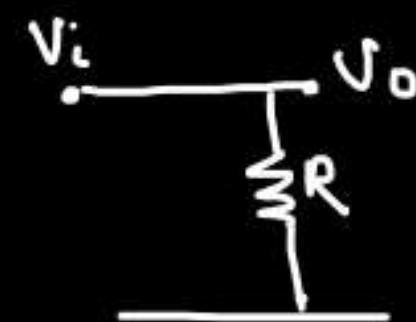


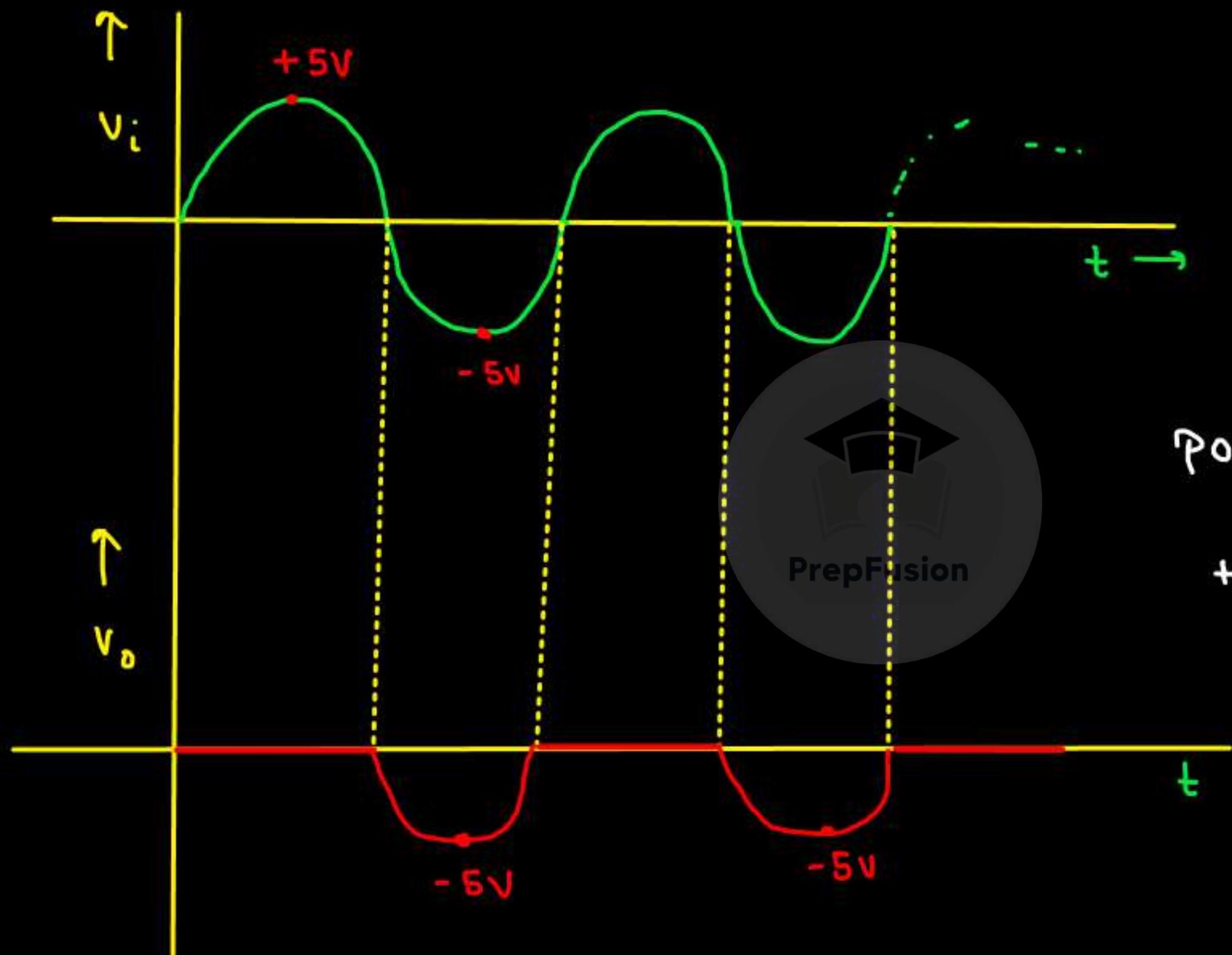

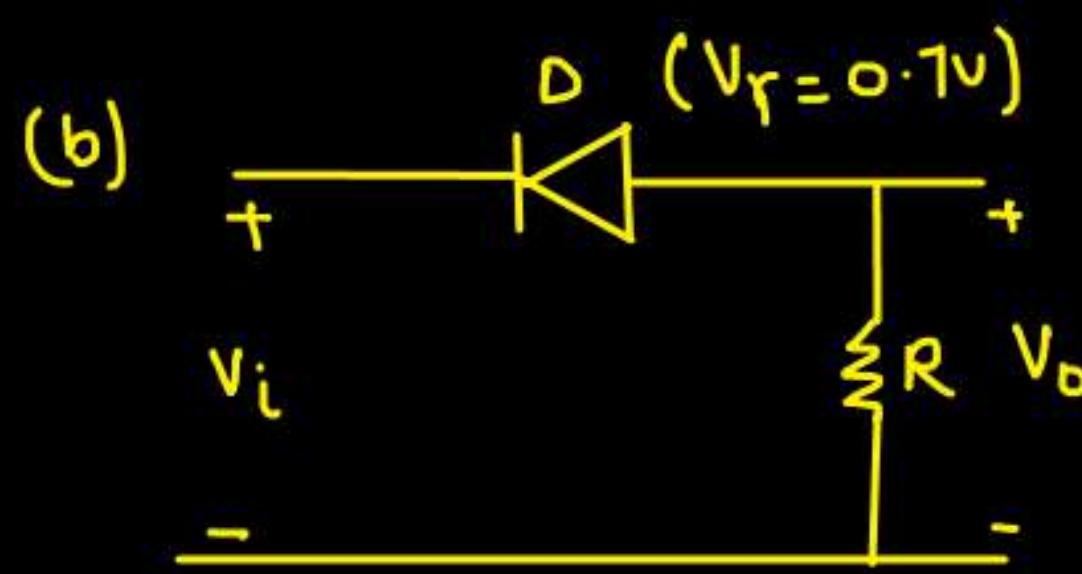Positive clipper
 ↴
 +ve part of i/p signal
 is clipped off in the
 o/p.



Draw VTC

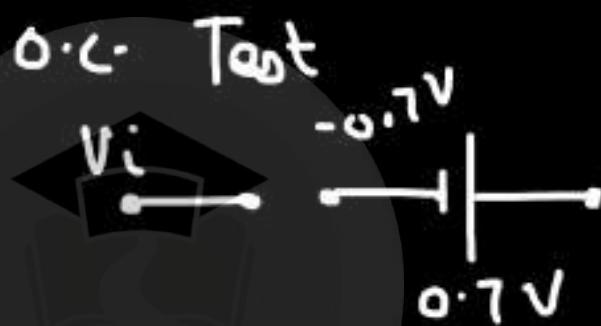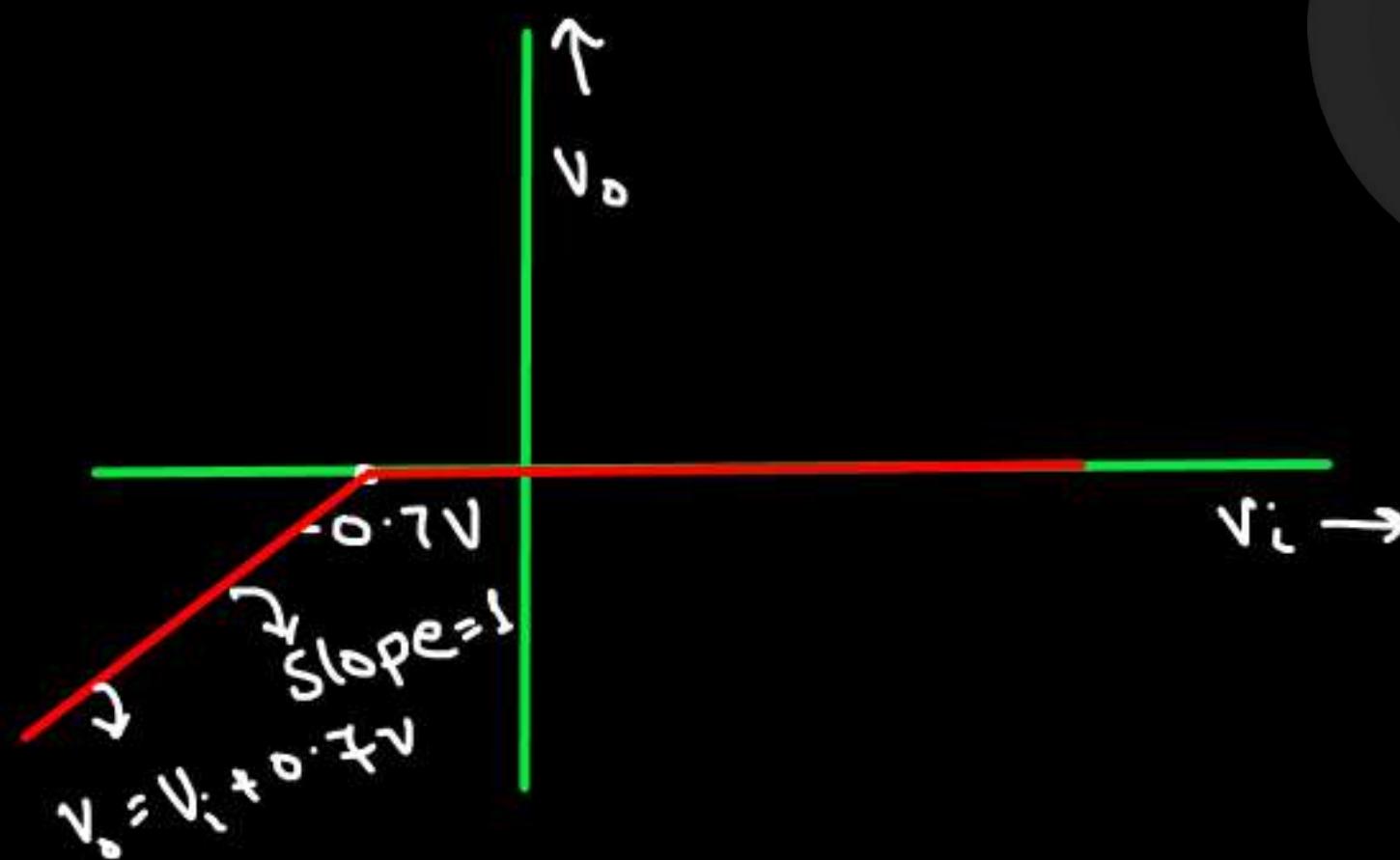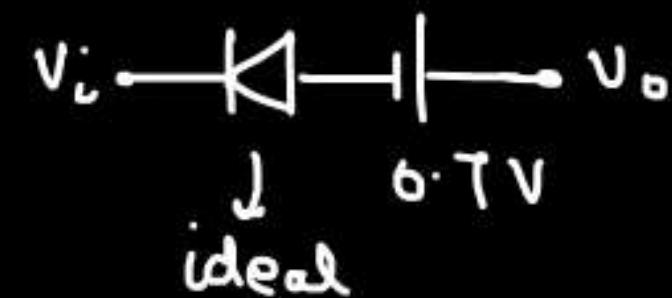

PrepFusion

(i) $V_i > -0.1V$

⇒ diode off


⇒ $V_d = 0V$

(ii) $V_i < -0.1V$


⇒ diode on



$V_d = V_i + 0.1V$

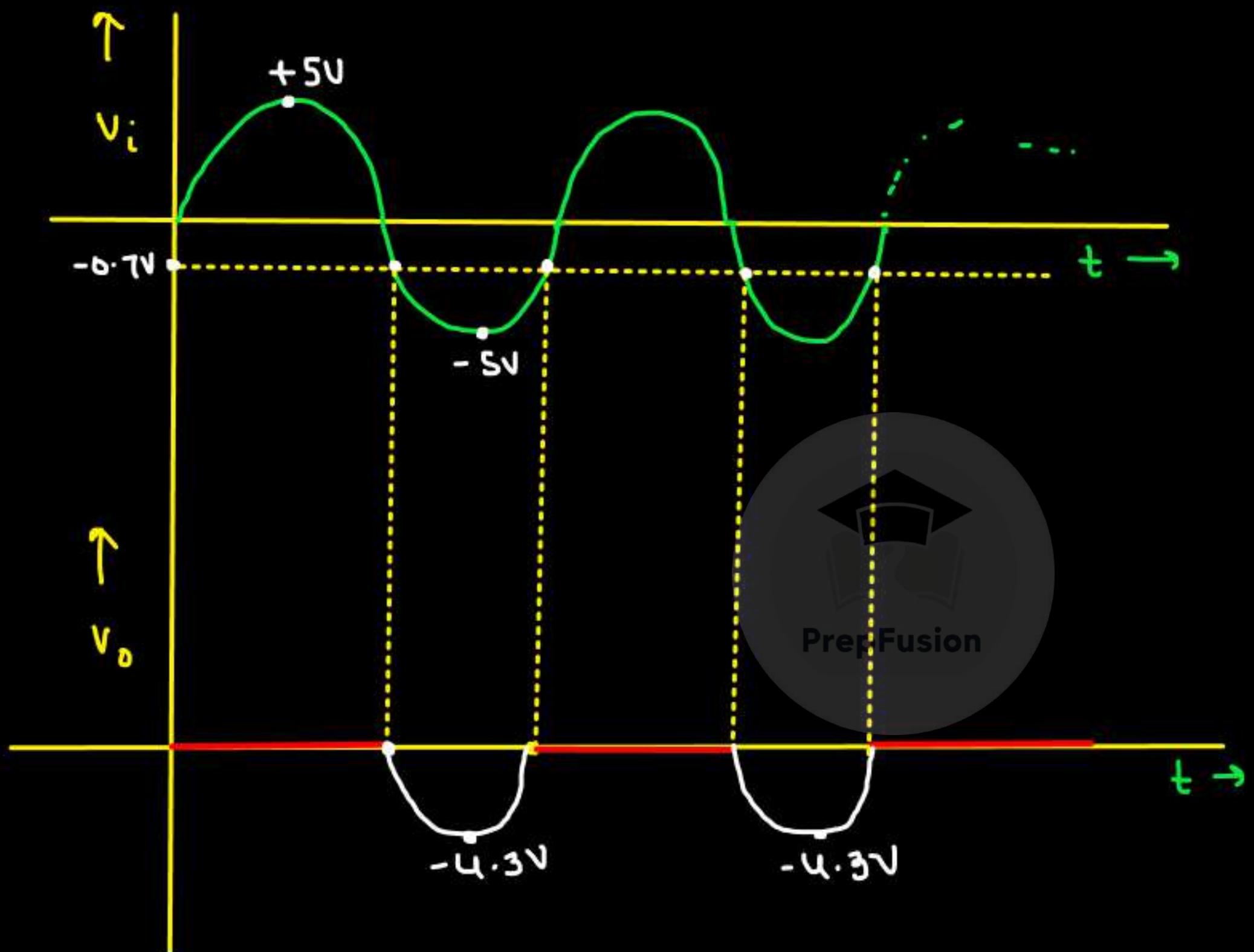

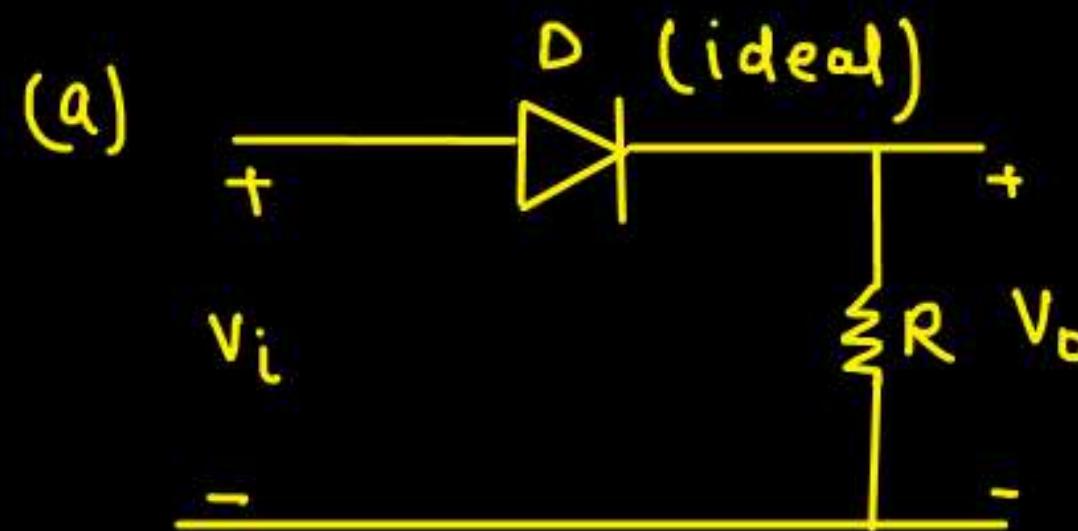2. Negative ^{Series} clipper circuit (Unbiased) :-




(i) $V_i > 0 \Rightarrow$ diode on


$$V_o = V_i$$


(ii) $V_i < 0 \Rightarrow$ diode off

$$V_o = 0$$

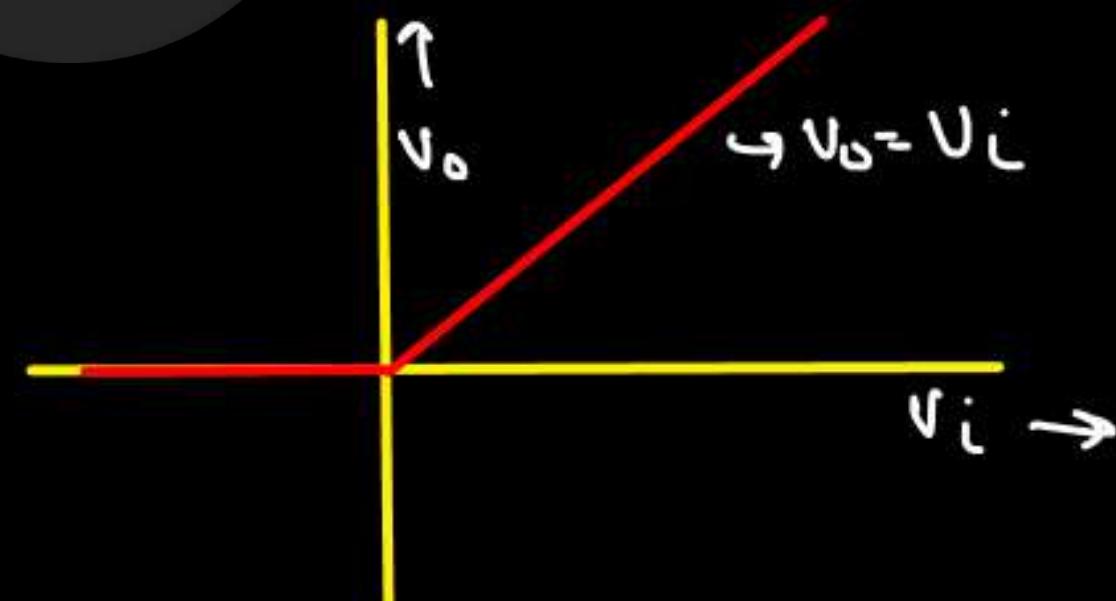


PrepFusion

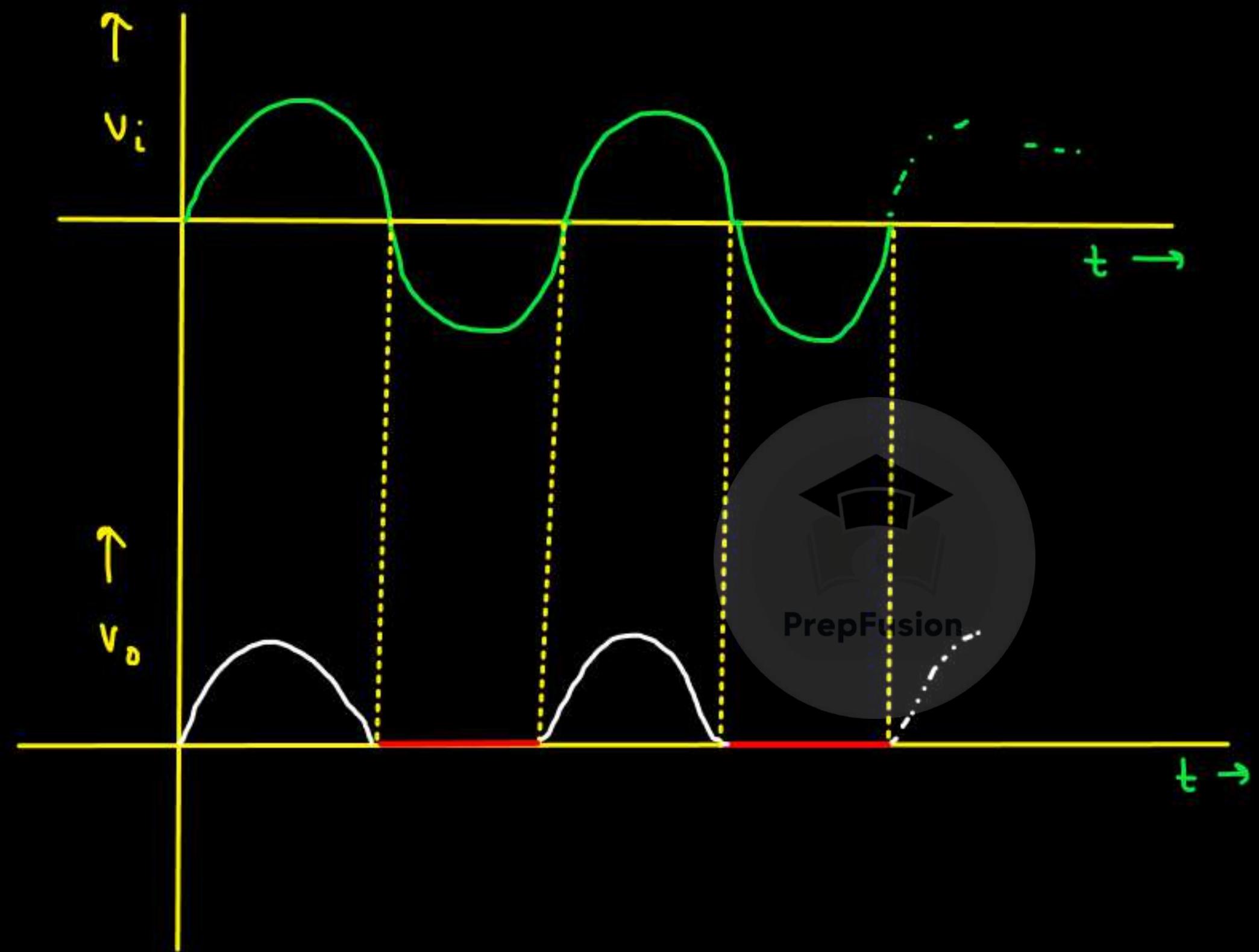


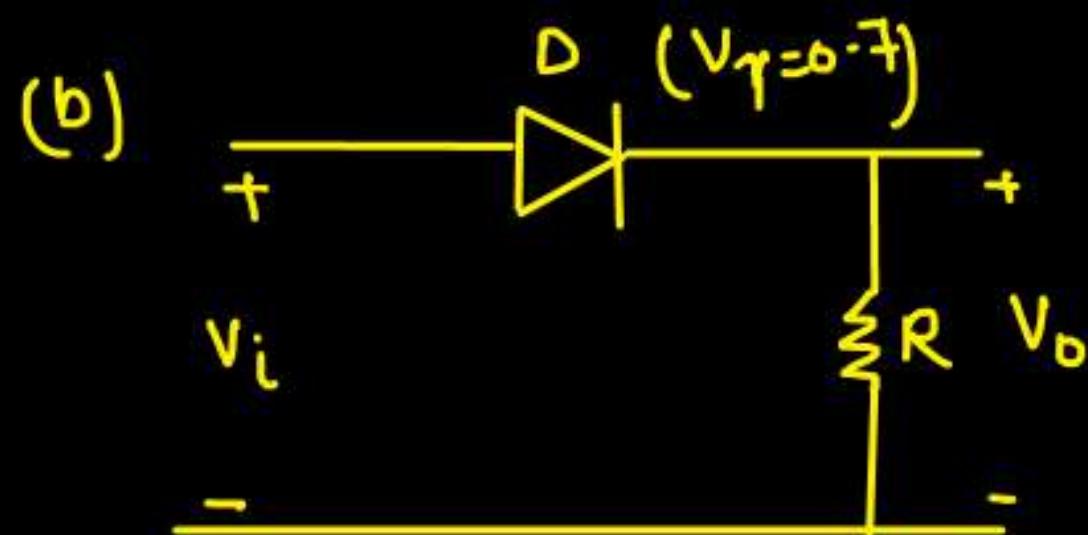

Draw VTC

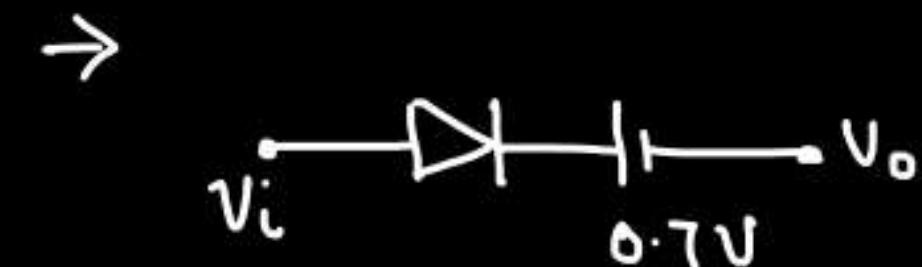

Applying O.C. Test

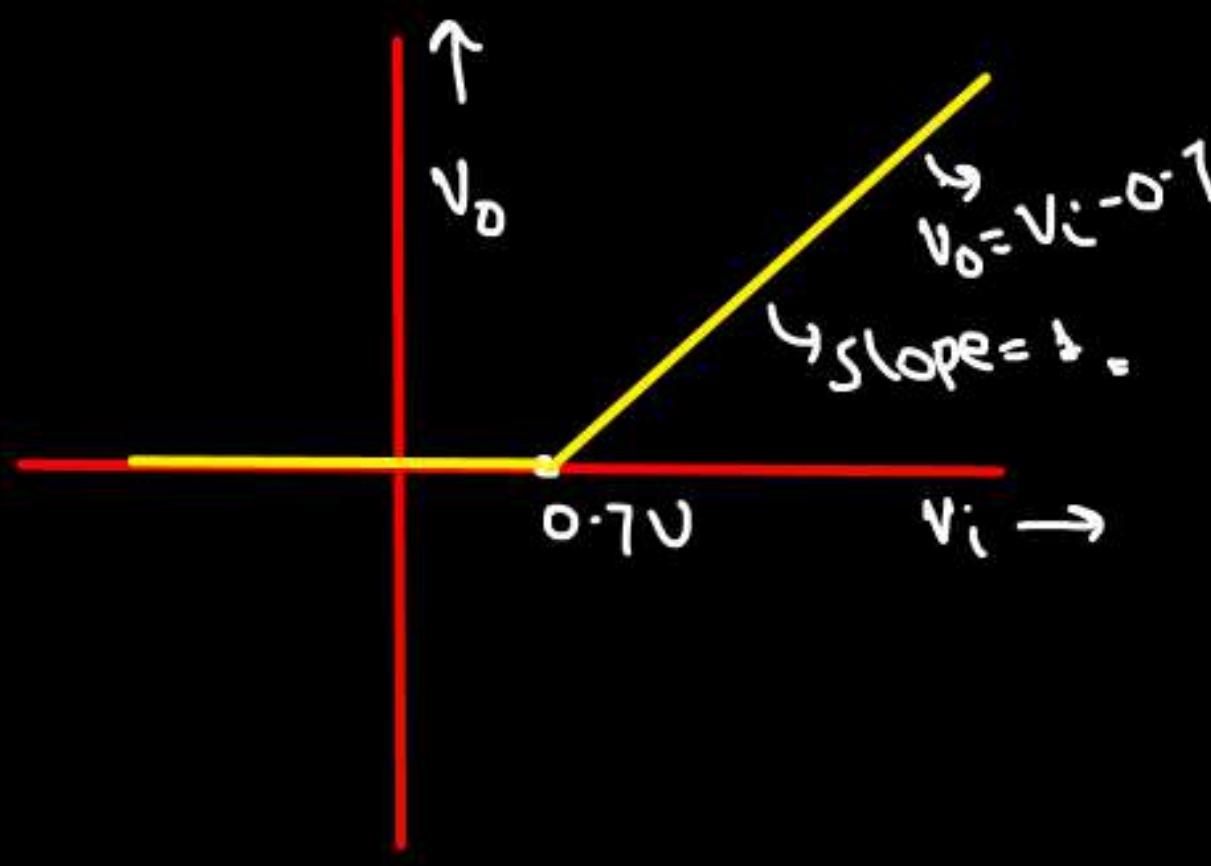


(i) $V_i > 0.7V$

→ diode ON


$$\Rightarrow V_o = V_i - 0.7$$

(ii) $V_i < 0.7V$


→ diode off

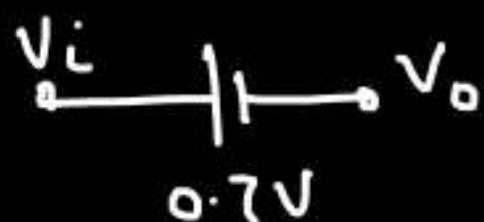

$$V_o = 0V$$

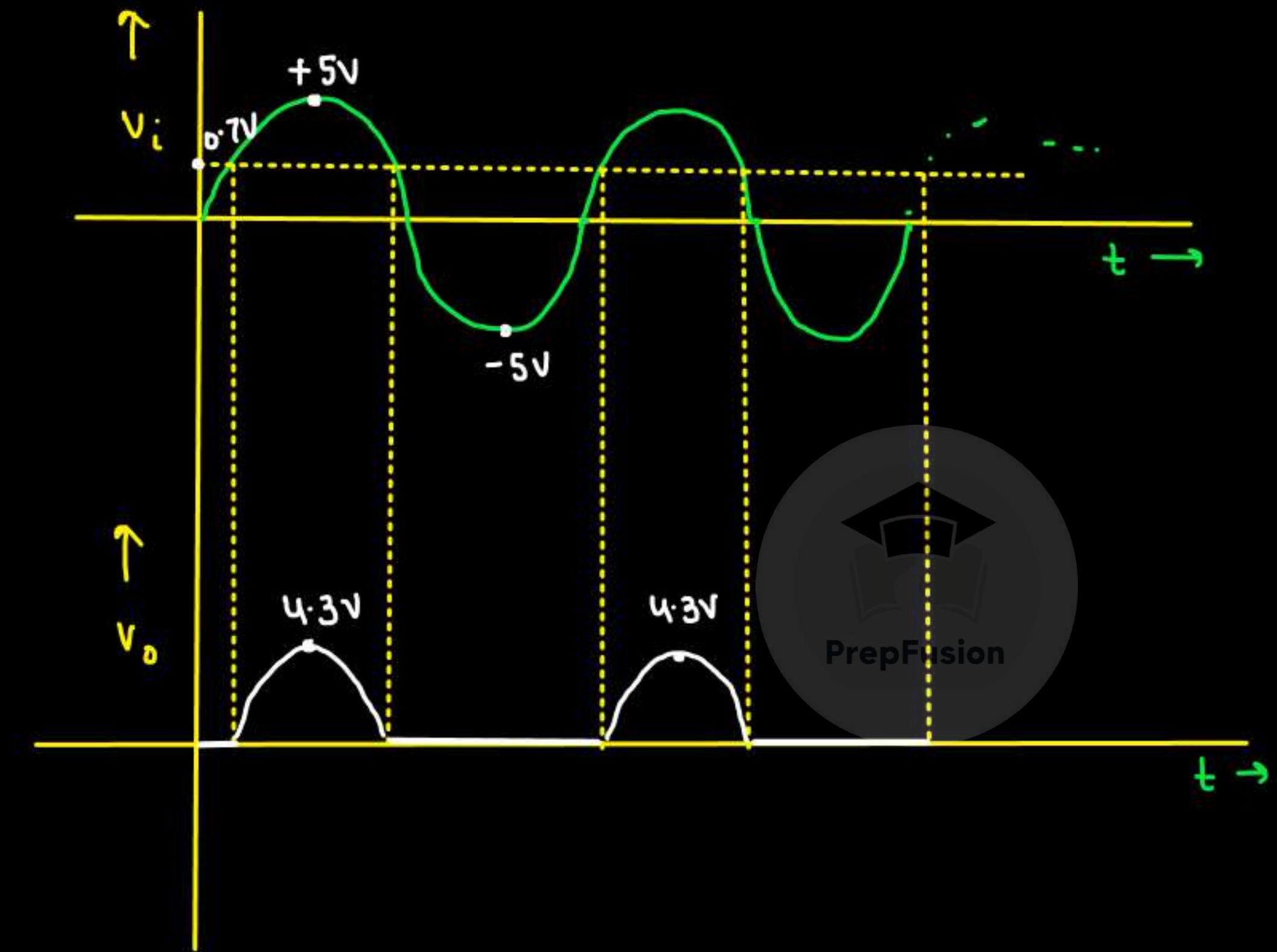

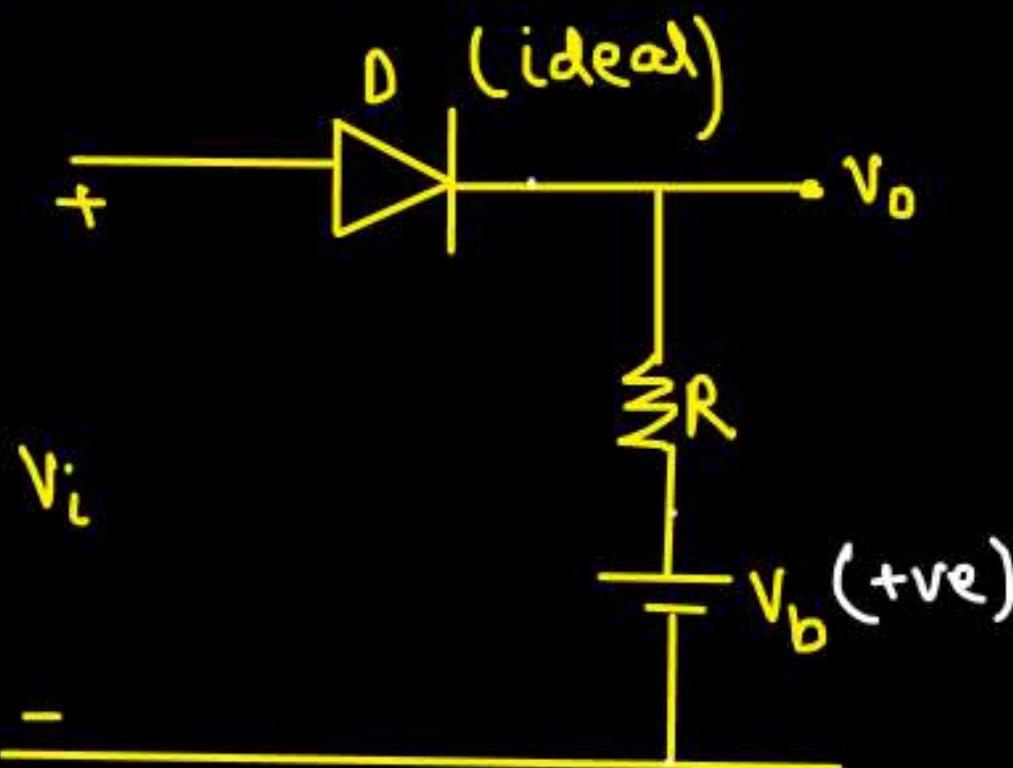3. Negative^{Series} Clipper Circuit (Positive bias) :-




Apply O.C. Test



(i) $V_i > V_b \Rightarrow$ diode ON



Prep Fusion


$$V_o = V_i$$

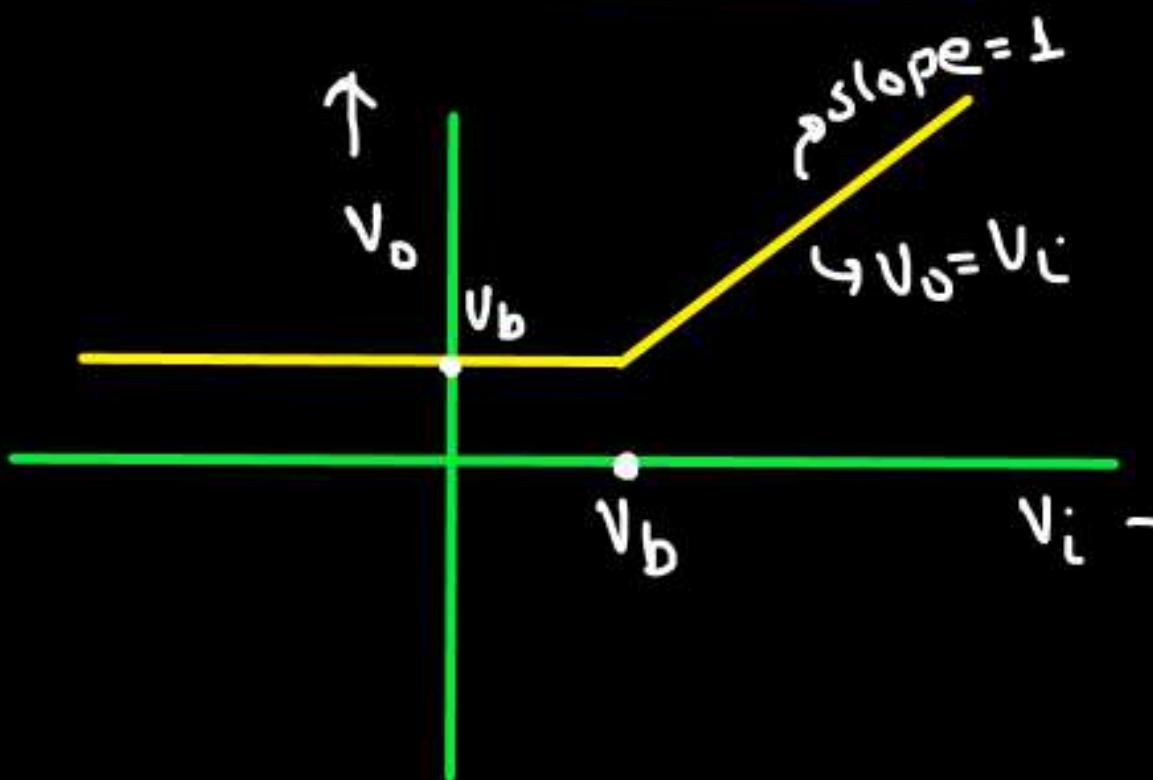


(ii) $V_i < V_b \Rightarrow$ diode OFF

$$V_o = V_b$$

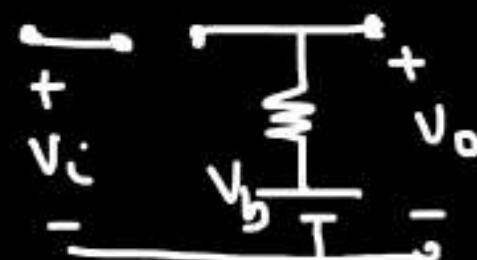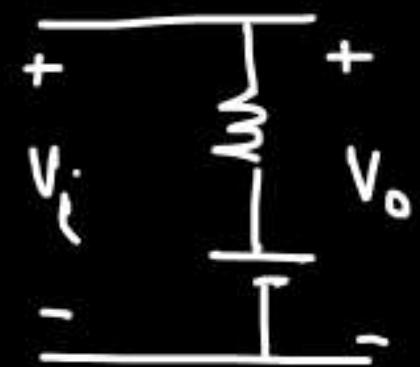

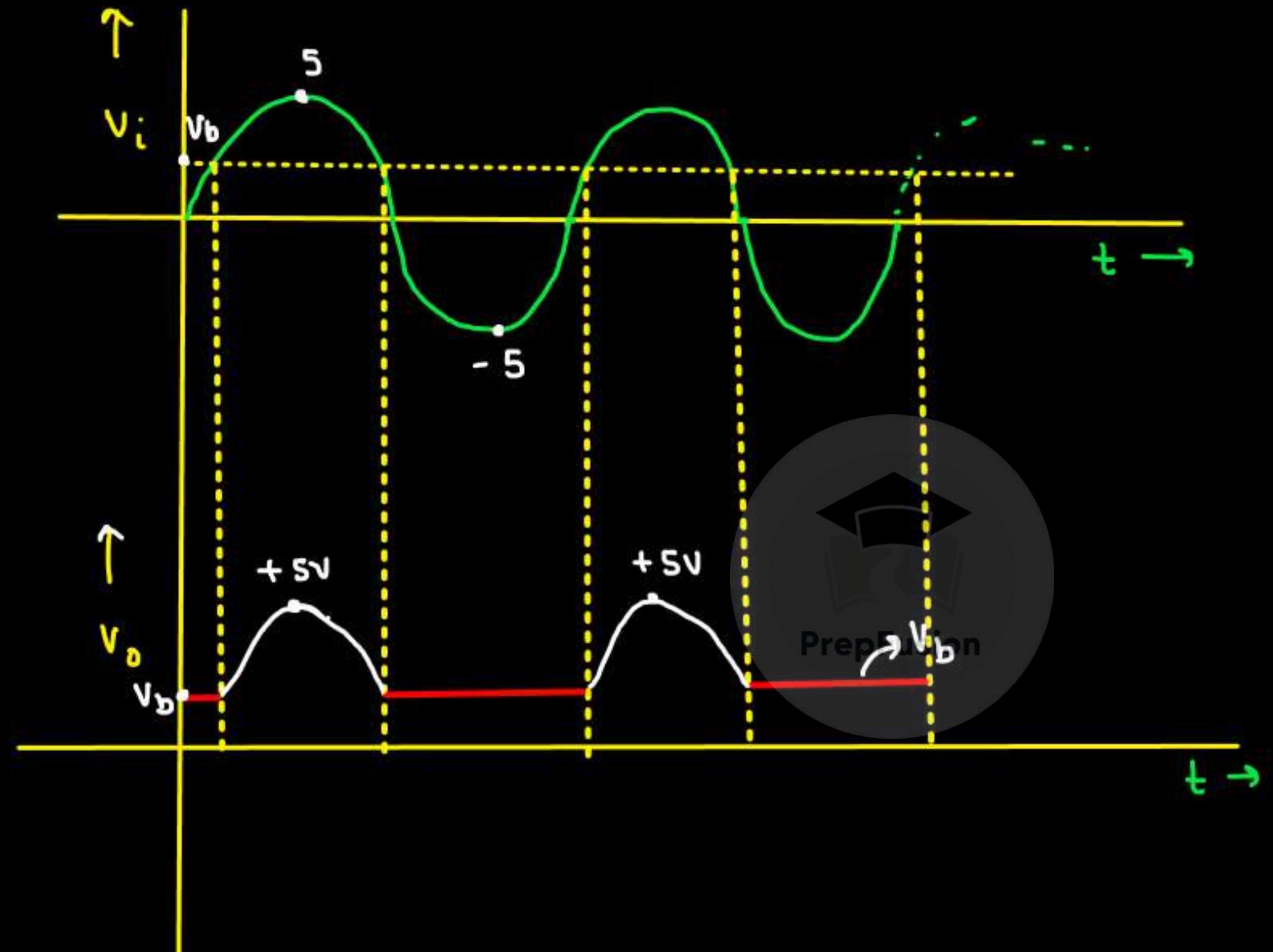

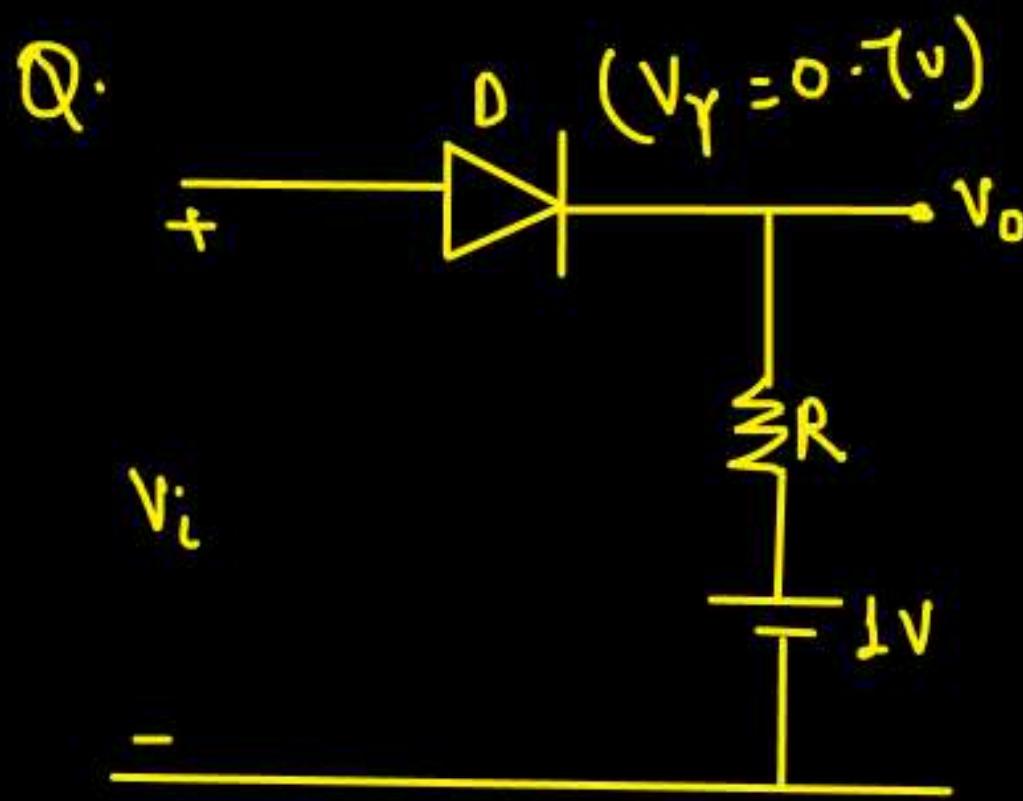

Draw Transfer characteristics.

→ D.C. Test




PrepFusion

(i) $V_i > 1.7V \Rightarrow$ diode ON


$$V_o = V_i - 0.7V$$

(ii) $V_i < 1.7V \Rightarrow$ diode OFF

$$V_o = 1V$$

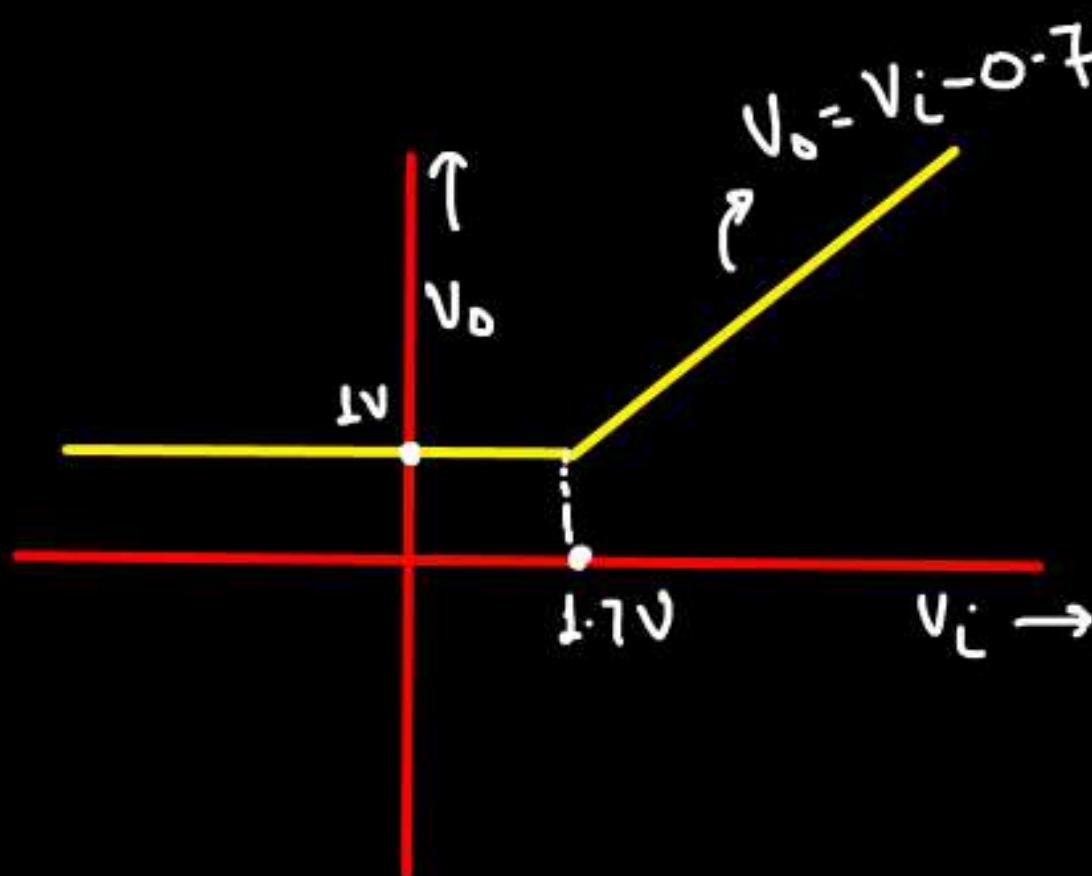

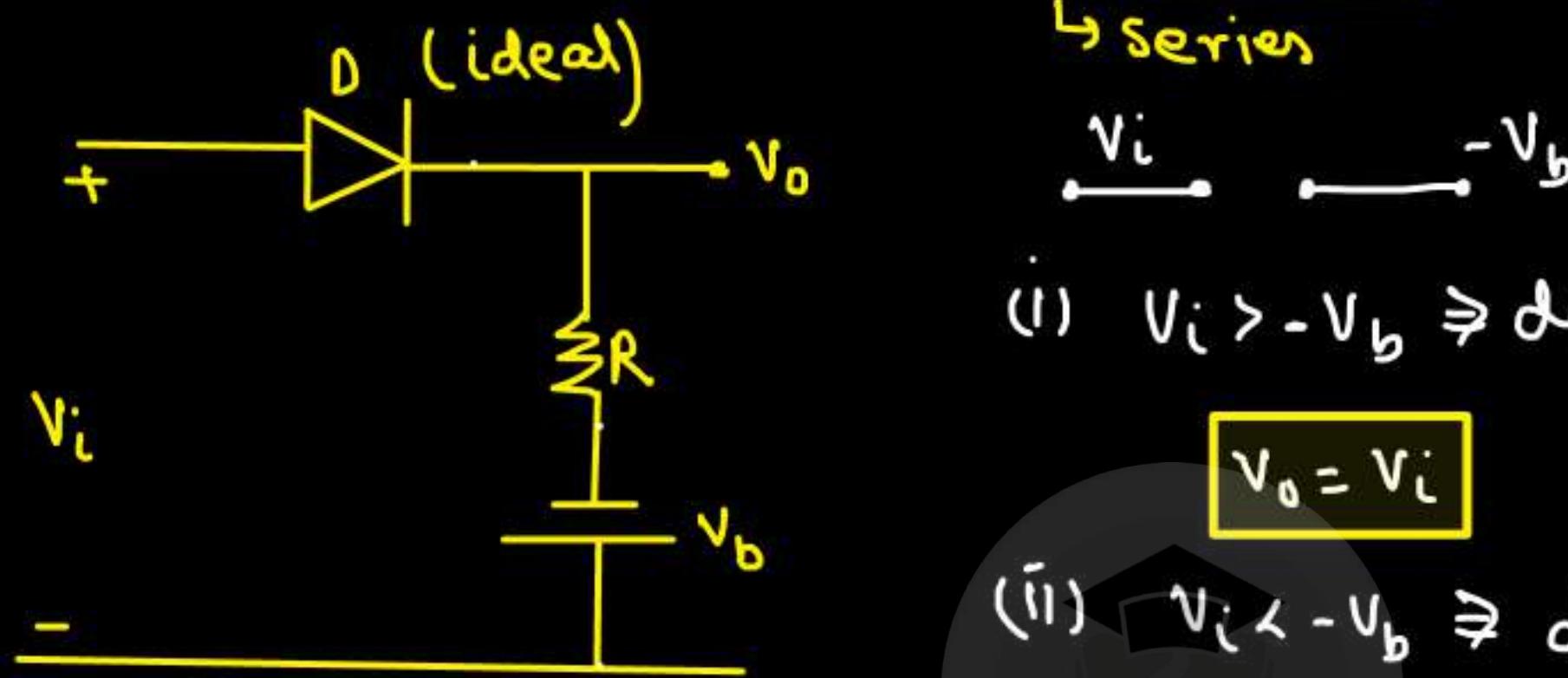4. Negative Clipper Circuit (Negative bias) :-





(i) $V_i > -V_b \Rightarrow$ diode ON

$$V_o = V_i$$


(ii) $V_i < -V_b \Rightarrow$ diode OFF

$$V_o = -V_b$$


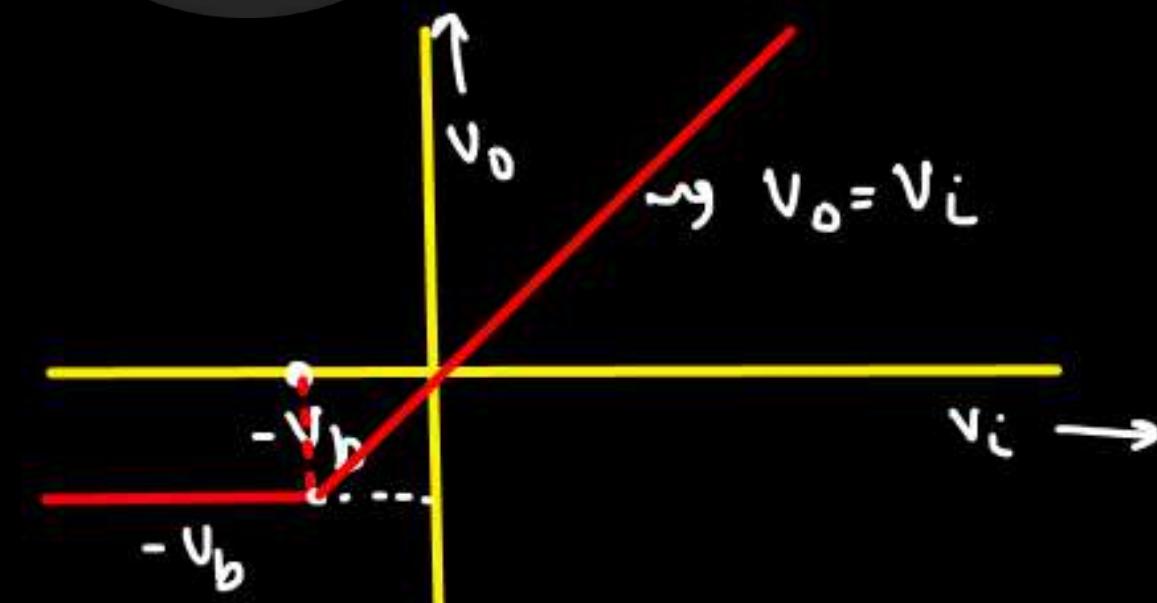


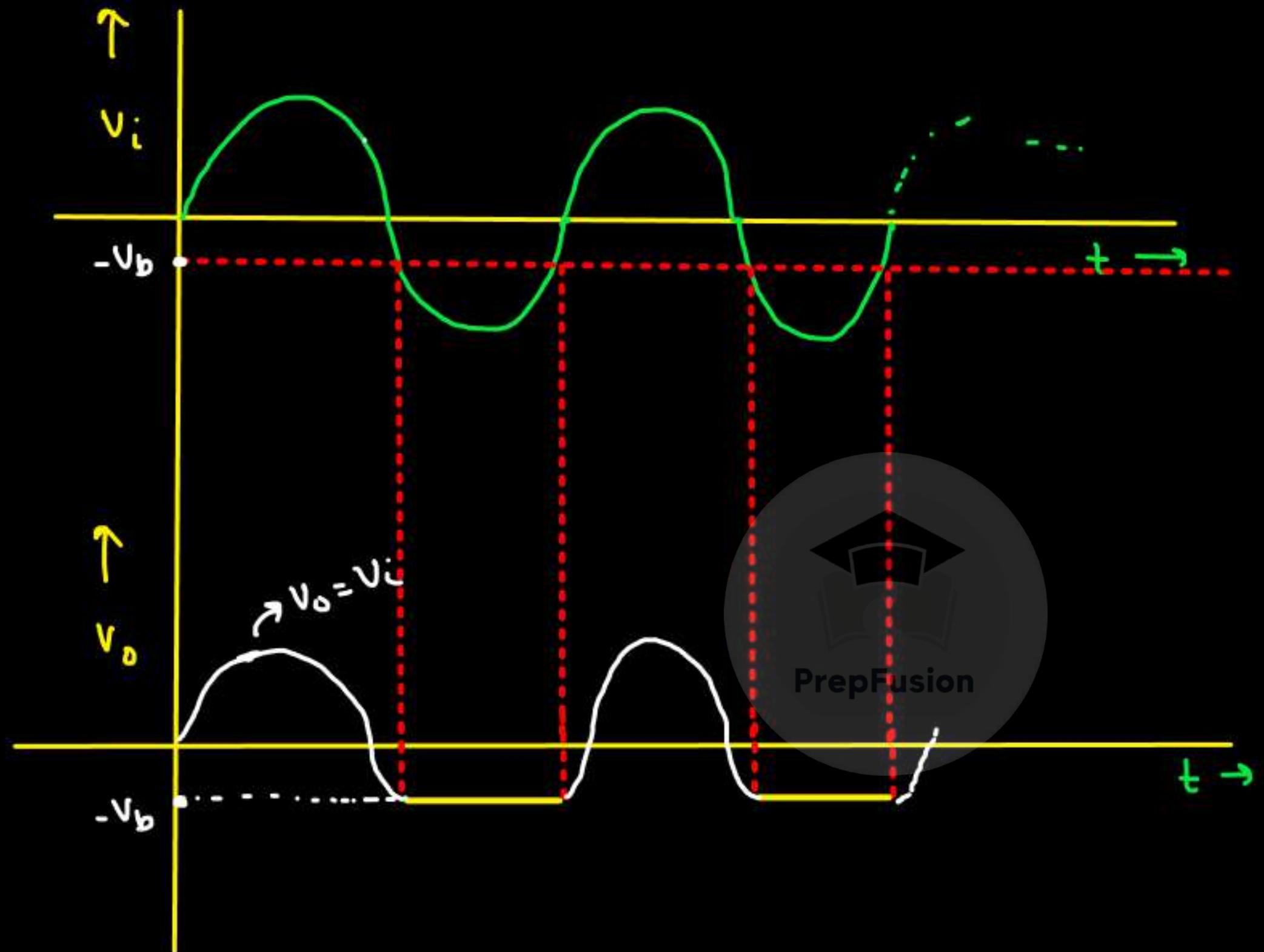

Q.

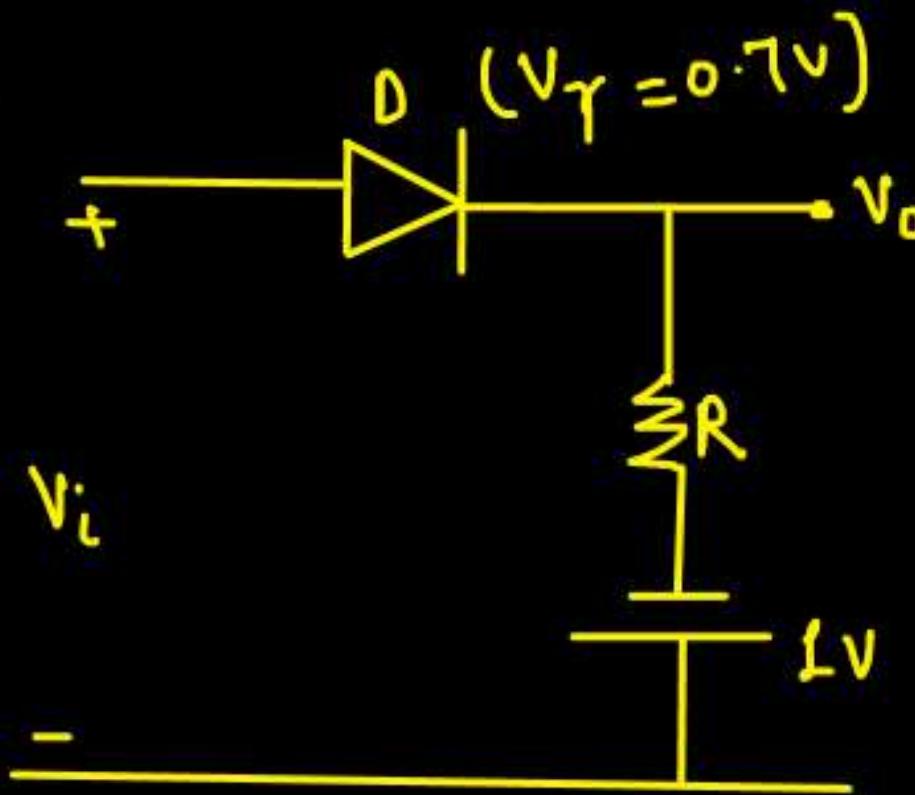

Draw Transfer characteristics.

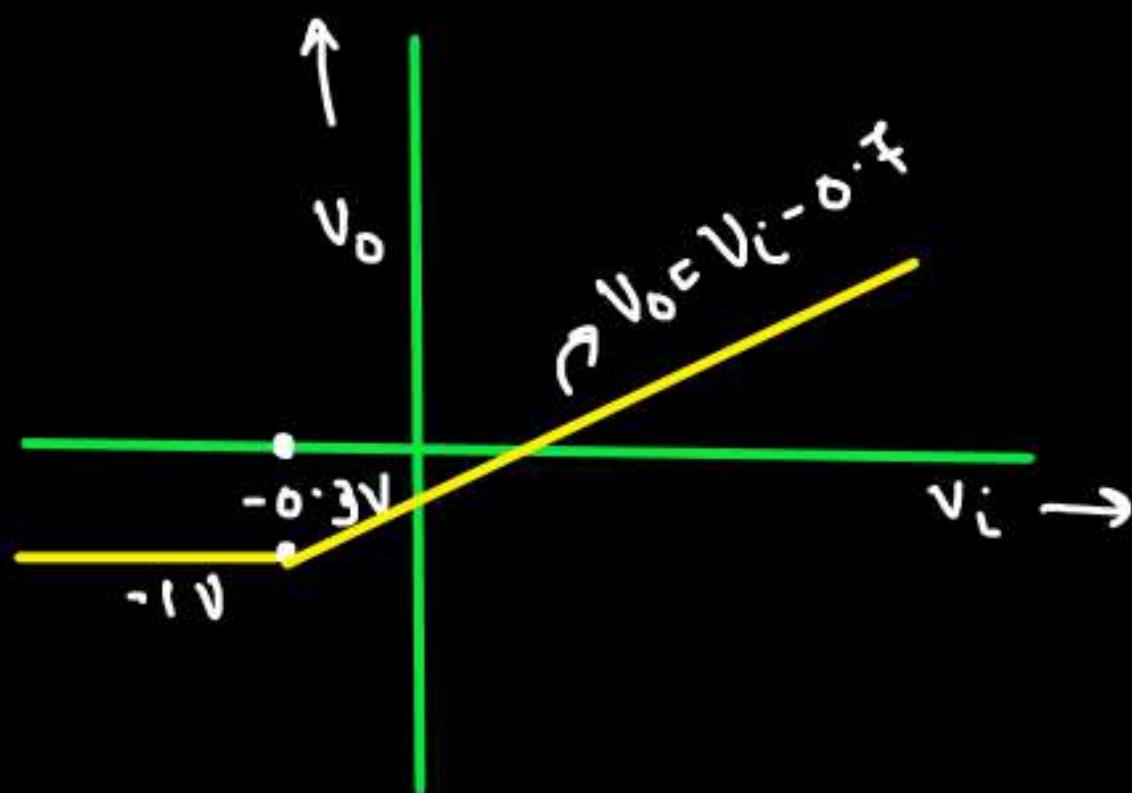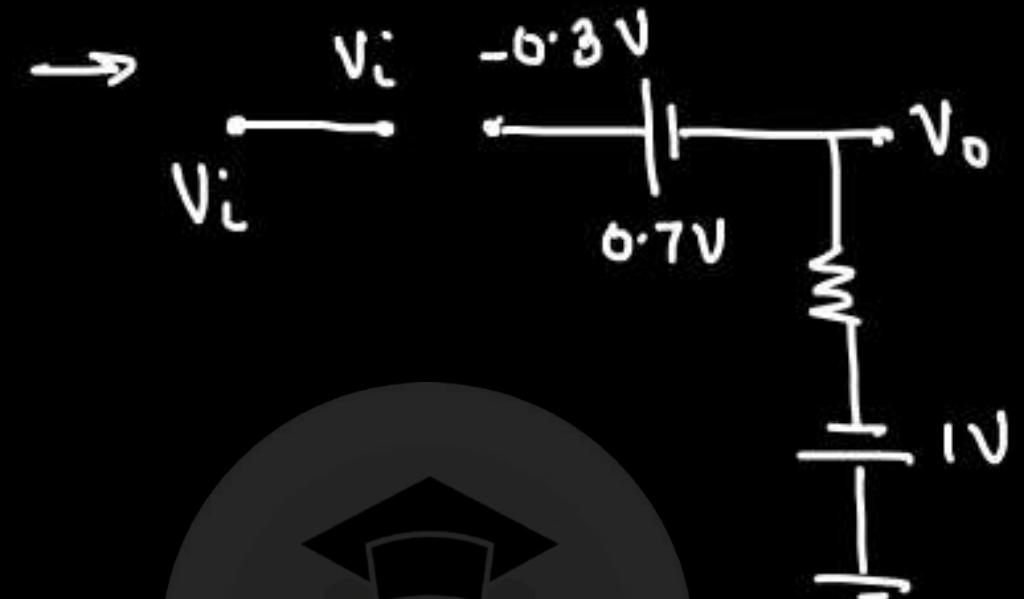

(i) $V_i > -0.3V$

PrepFusion
⇒ diode on


$$\Rightarrow V_o = V_i - 0.7$$

(ii) $V_i < -0.3V$

⇒ diode off

$$V_o = -1V$$

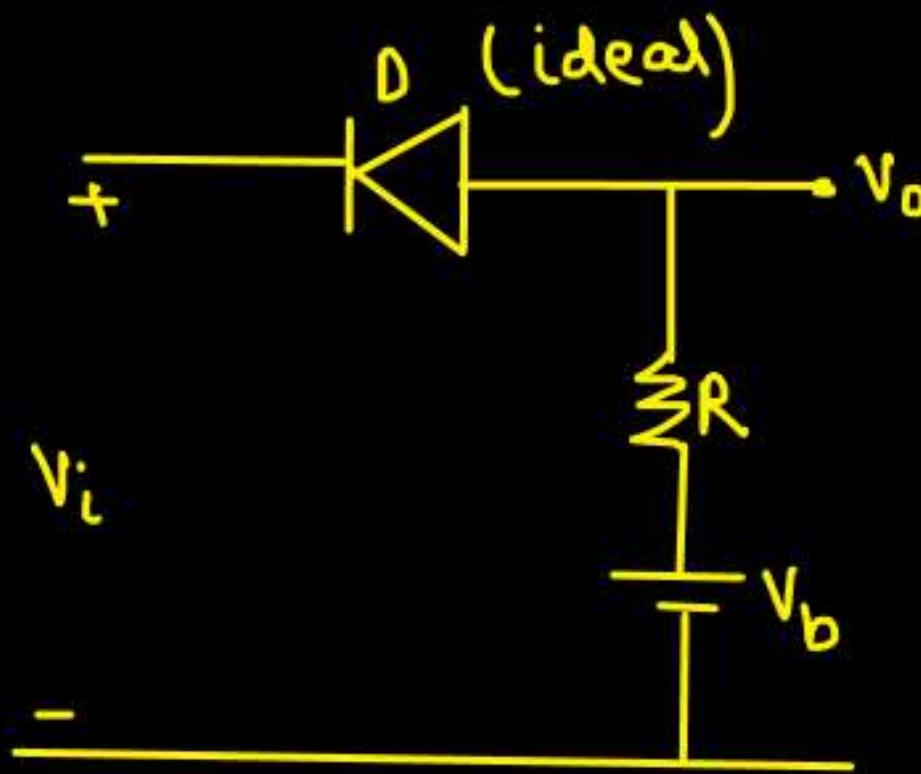5. ^{Series} Positive clipper ckt (Positive bias):-



(i) $V_i > V_b$


⇒ diode off


$$V_o = V_b$$

(ii) $V_i < V_b$




⇒ diode on

$$V_o = V_i$$

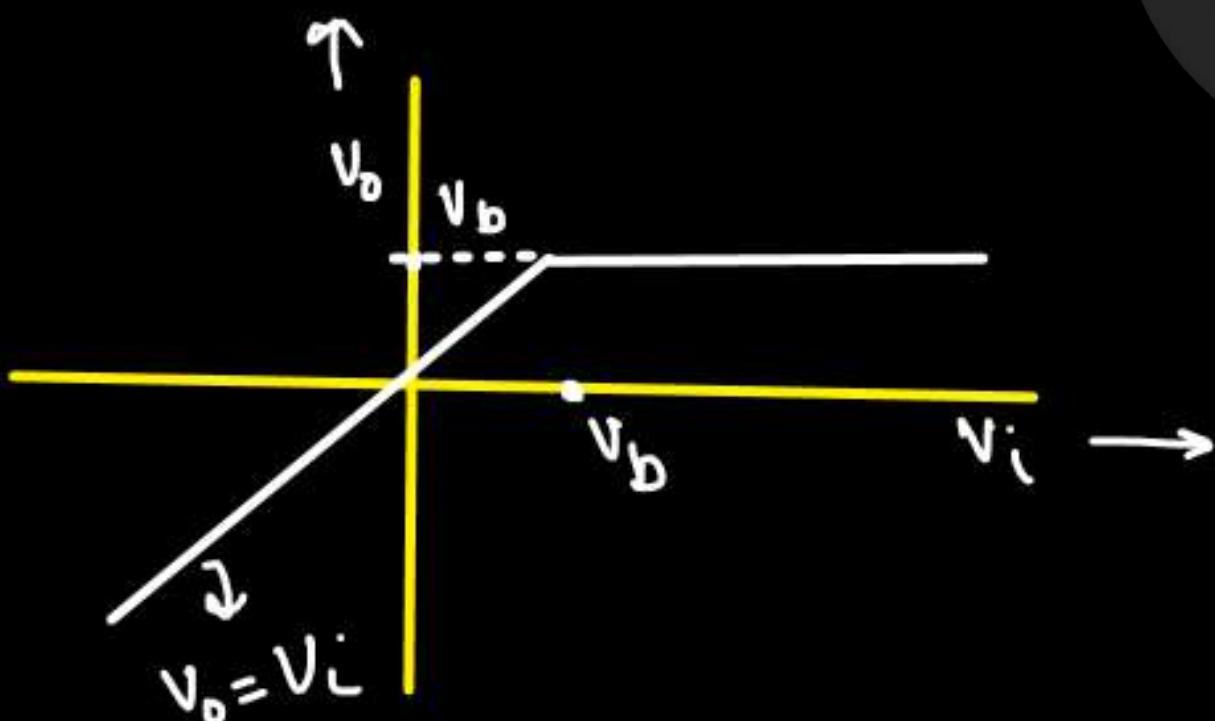

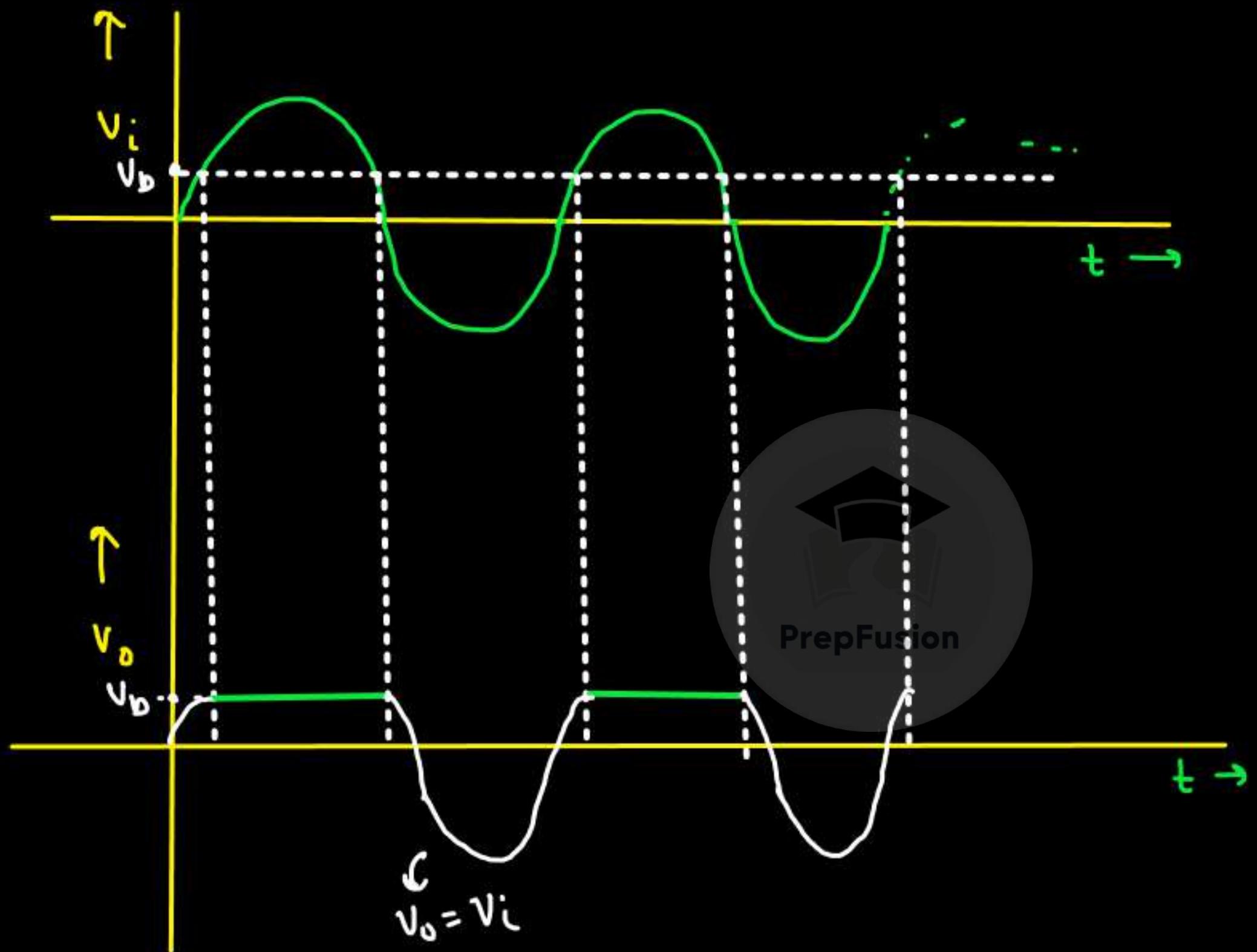

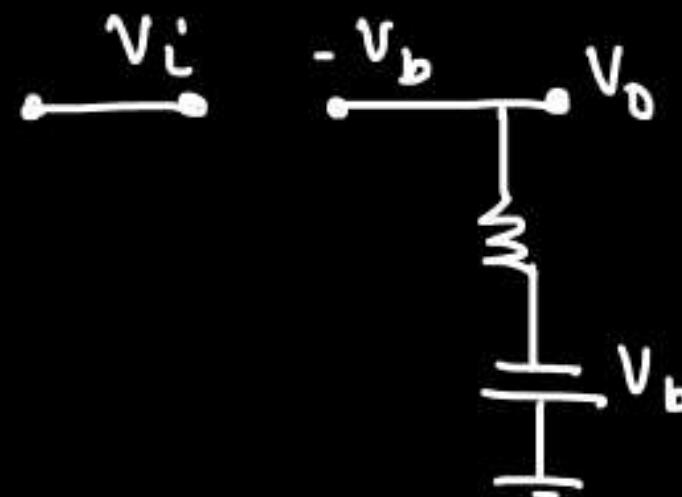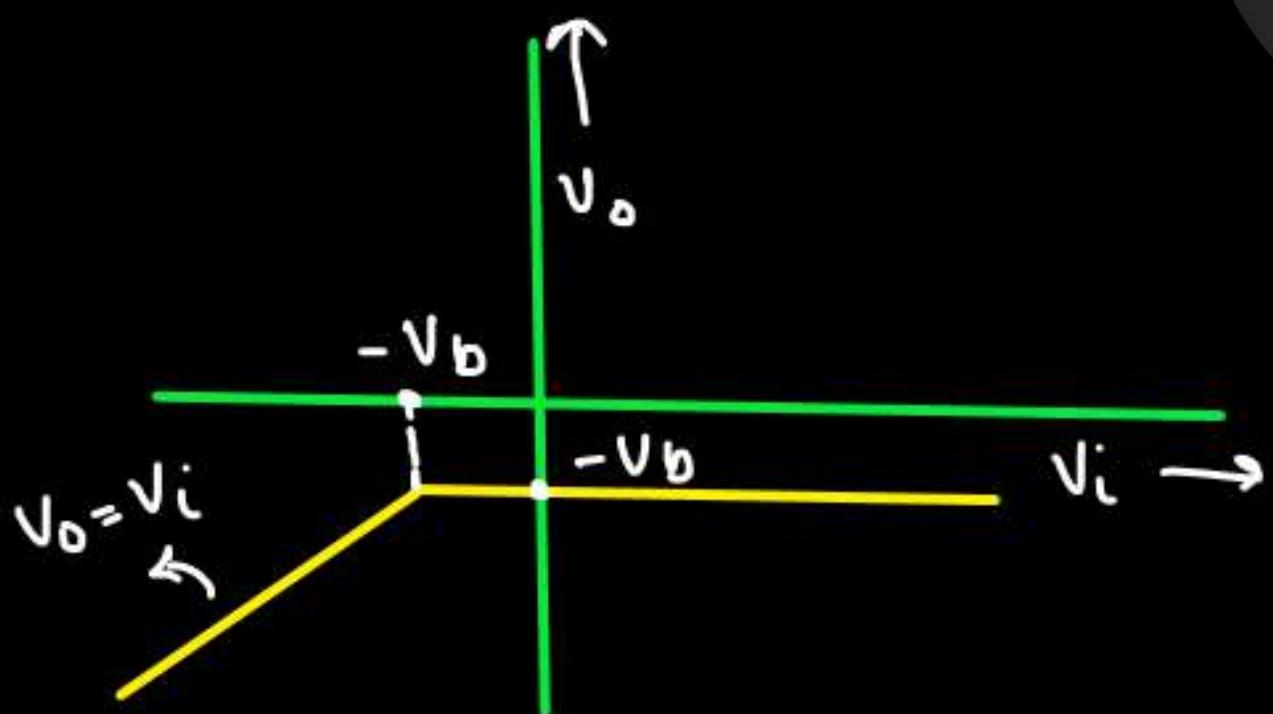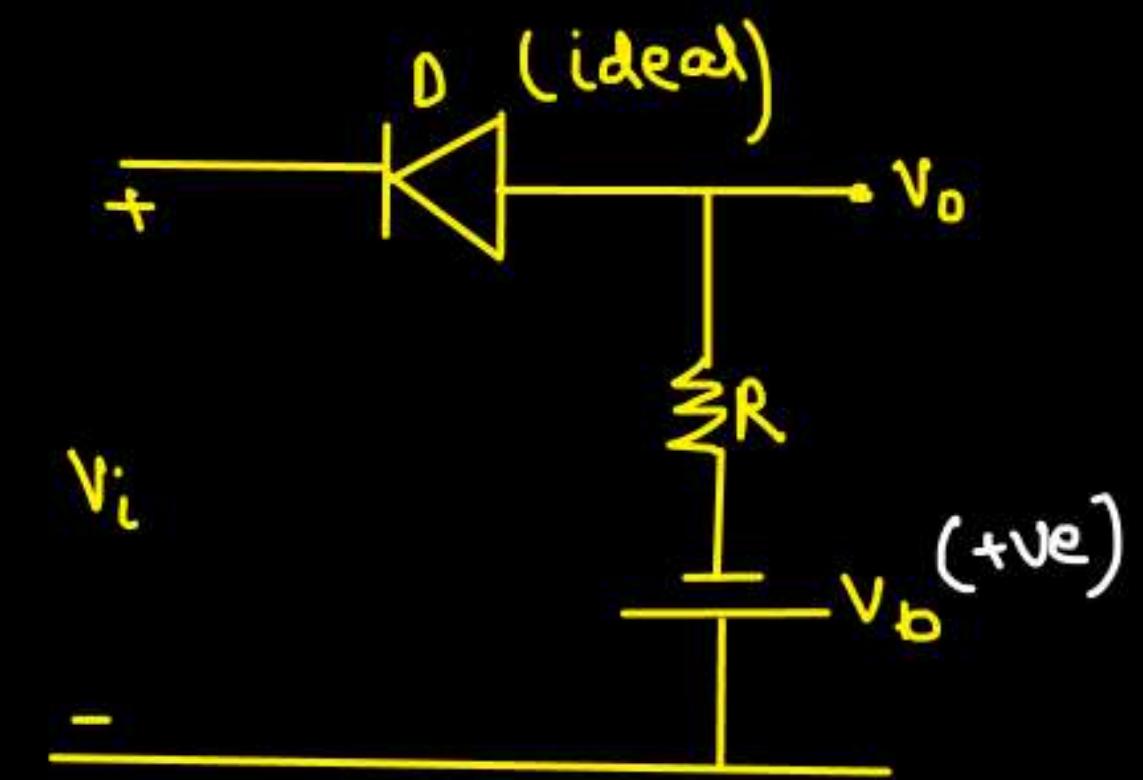G. Positive^ Clipper ckt (Negative bias) :-




(i) $V_i > -V_b$
 \Rightarrow diode off


Prep Fusion
 $V_o = -V_b$

(ii) $V_i < -V_b$
 \Rightarrow diode on



$V_o = V_i$



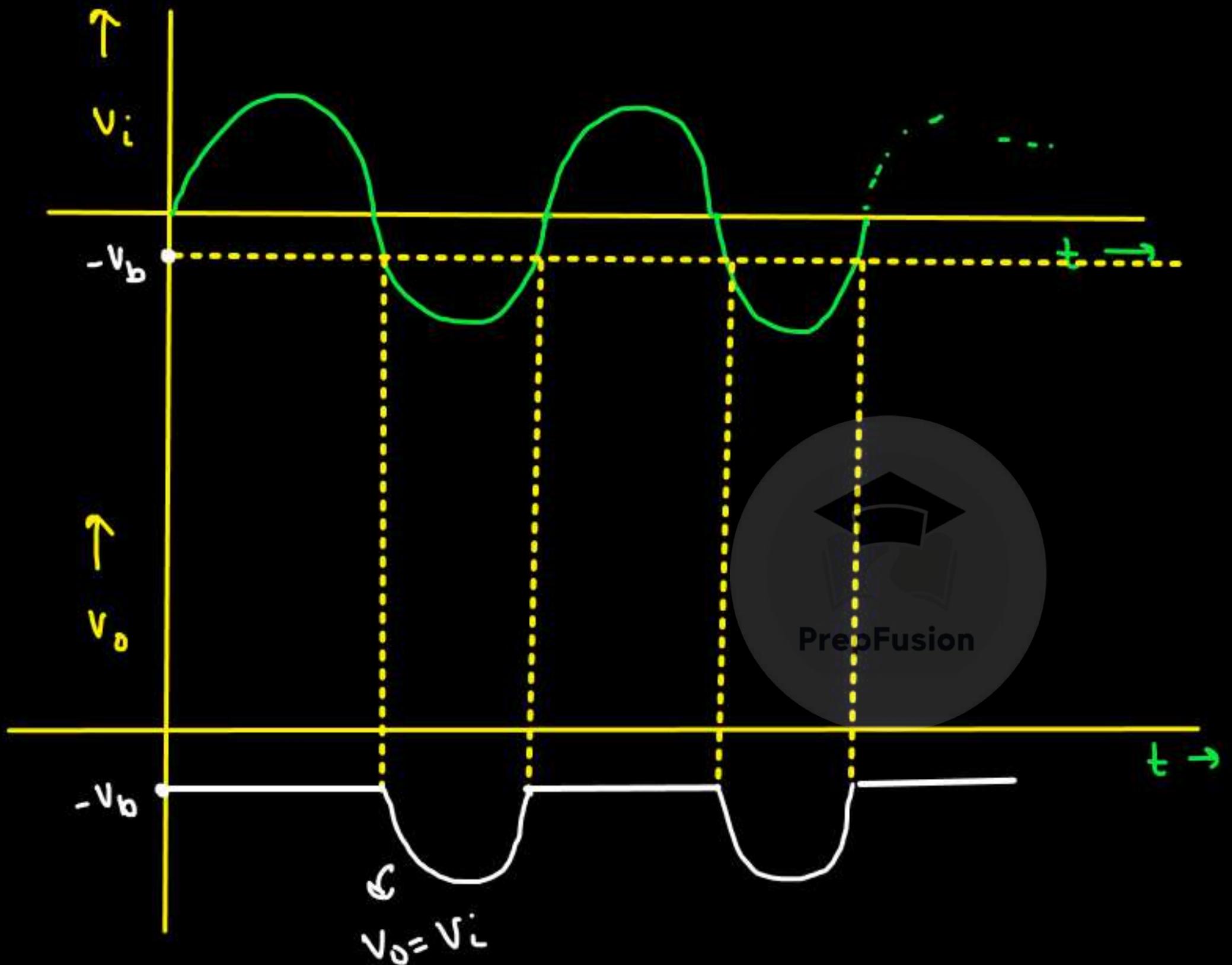

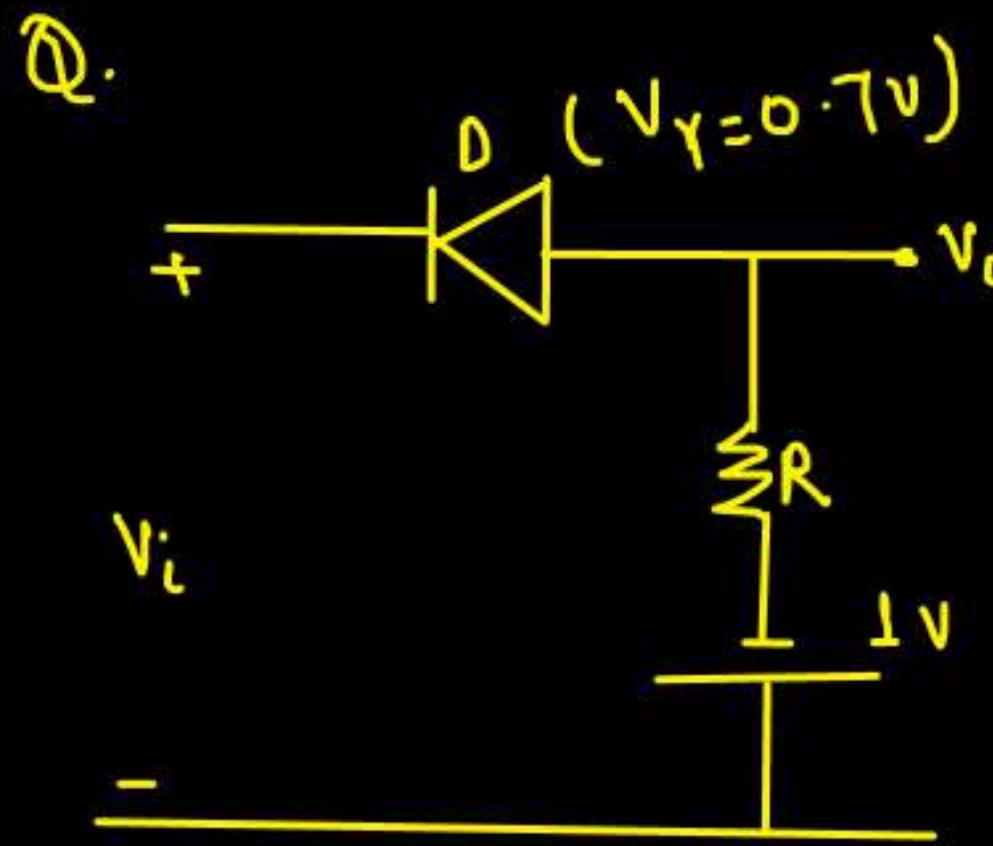

Draw Transfer characteristics.

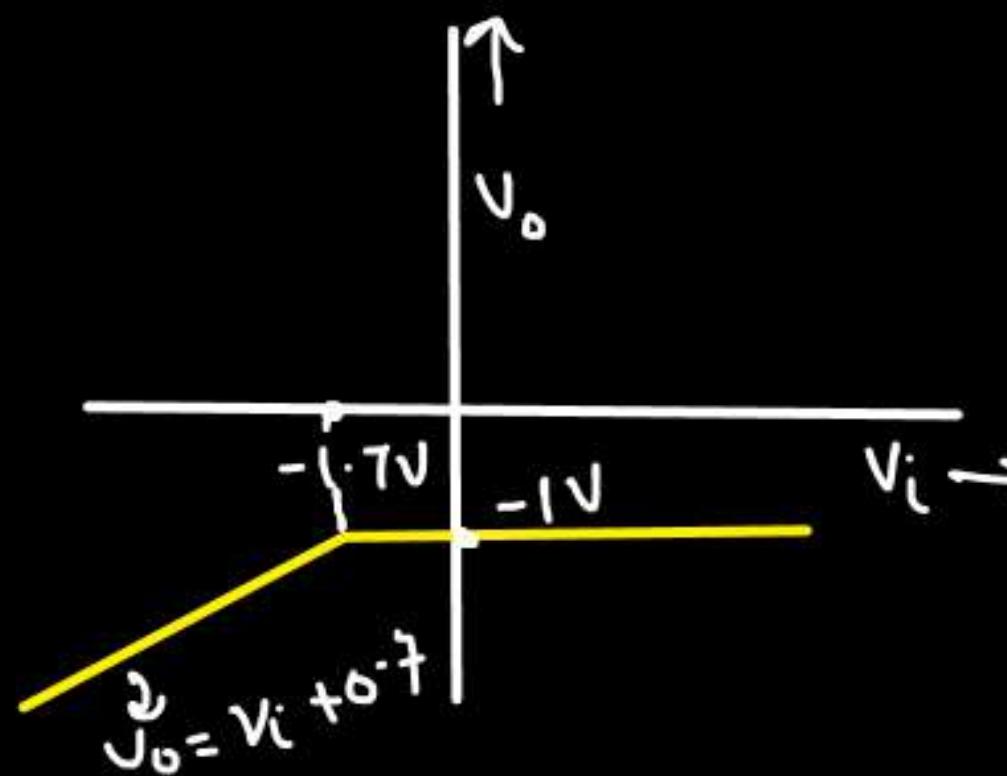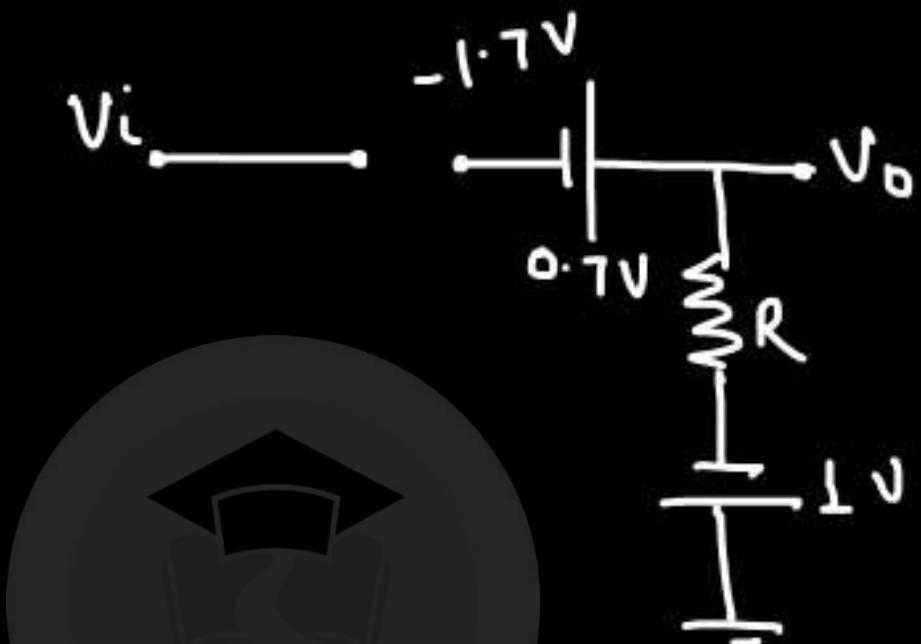


(i) $V_i > -0.7V \Rightarrow$ diode off



$$V_o = -1V$$

(ii) $V_i < -0.7V \Rightarrow$

$$V_o = V_i + 0.7$$

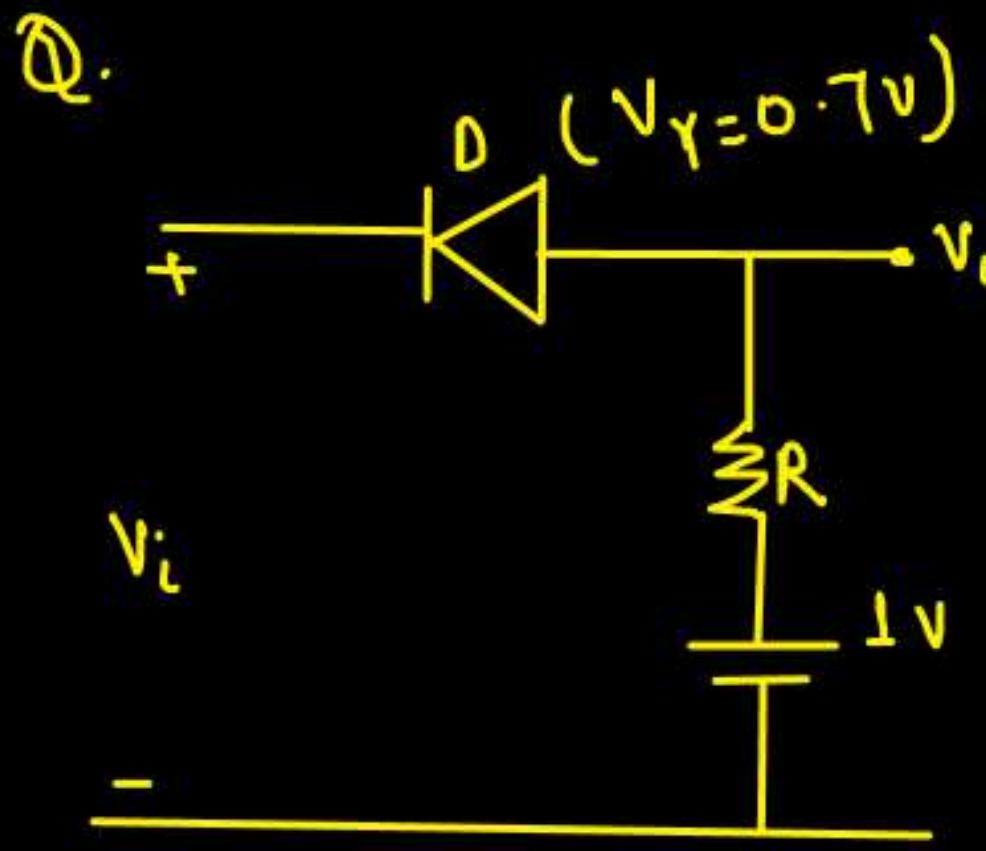

Draw Transfer characteristics.

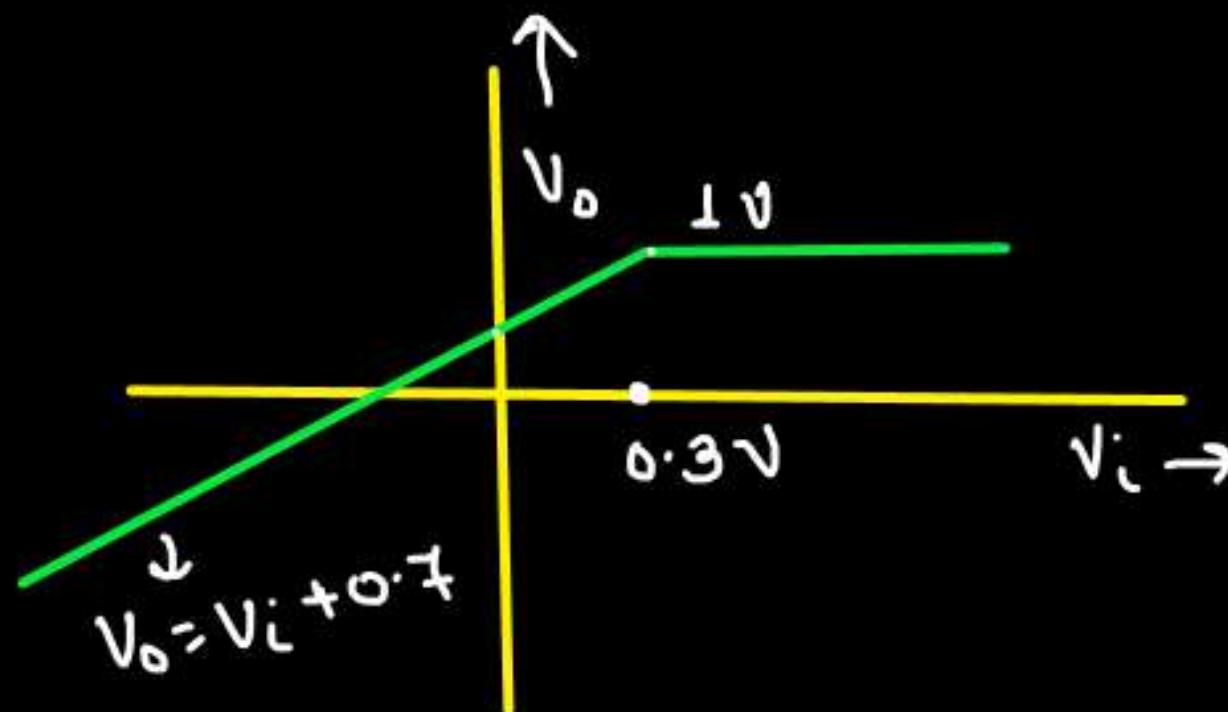
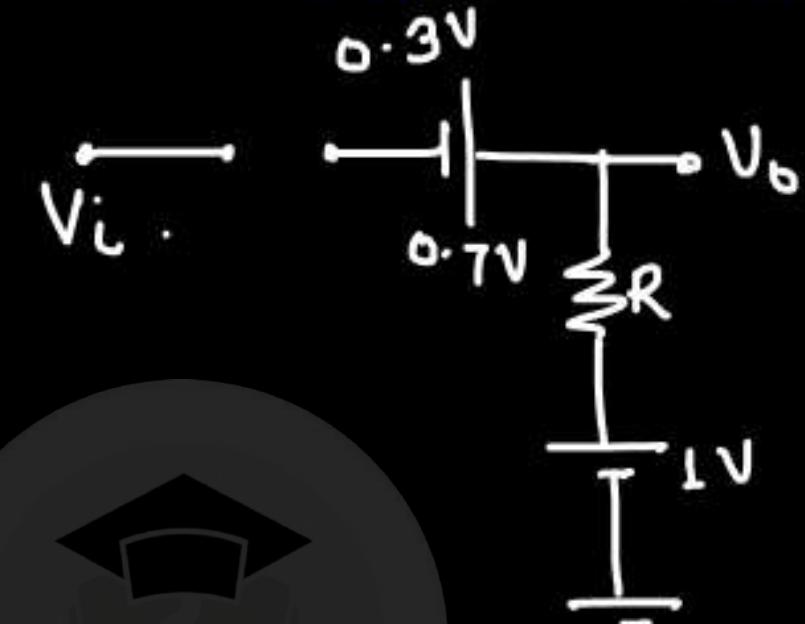


(i) $V_i > 0.3V$
PrepFusion
⇒ diode off ⇒ $V_o = 1V$

(ii) $V_i < 0.3V$
⇒ diode on ⇒ $V_o = V_i + 0.7V$

1. Positive Shunt Clipper Circ.

(Unbiased)

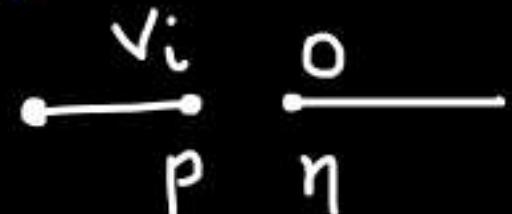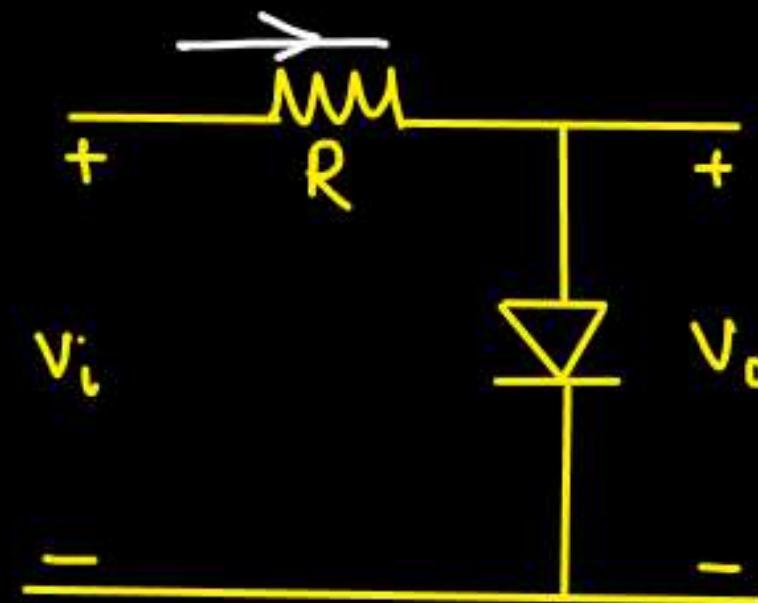

(i) $V_i > 0 \Rightarrow$ diode ON





Preclipping
 $V_0 = 0V$

(ii) $V_i < 0 \Rightarrow$ diode OFF




$V_0 = V_i$

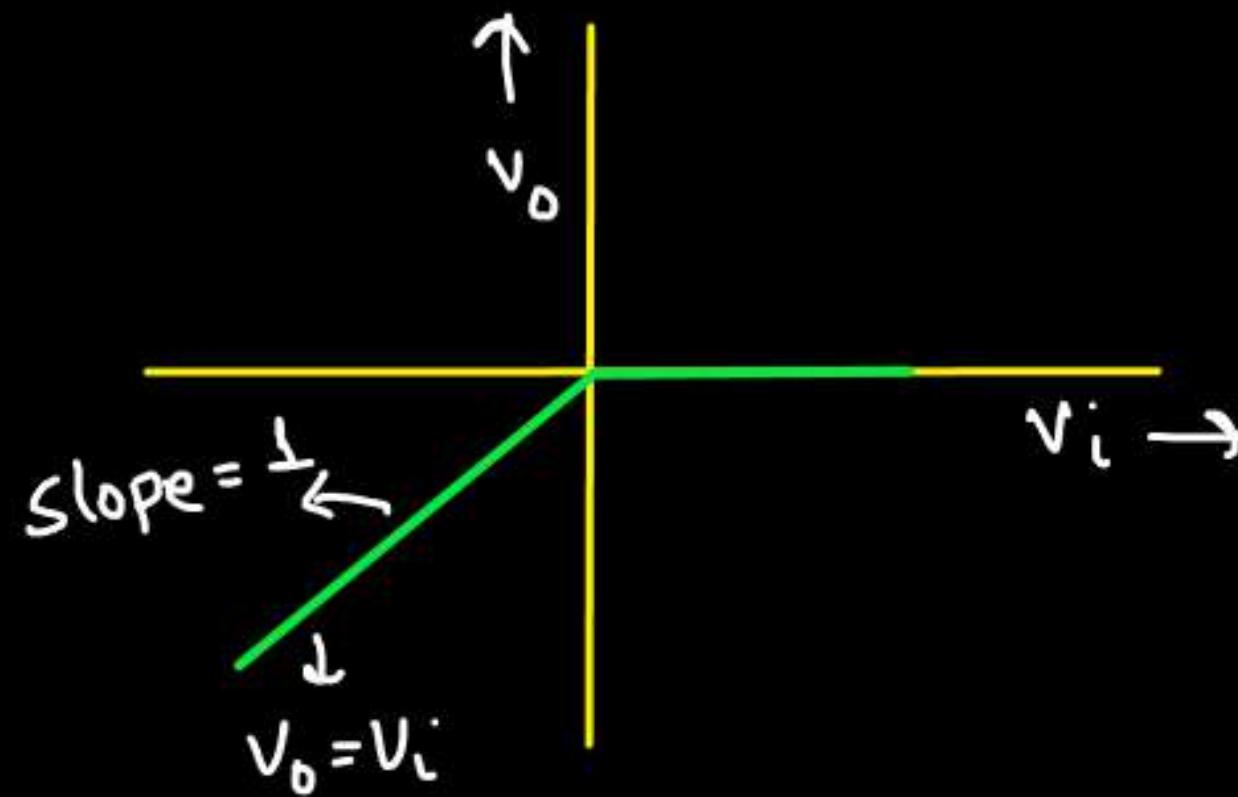

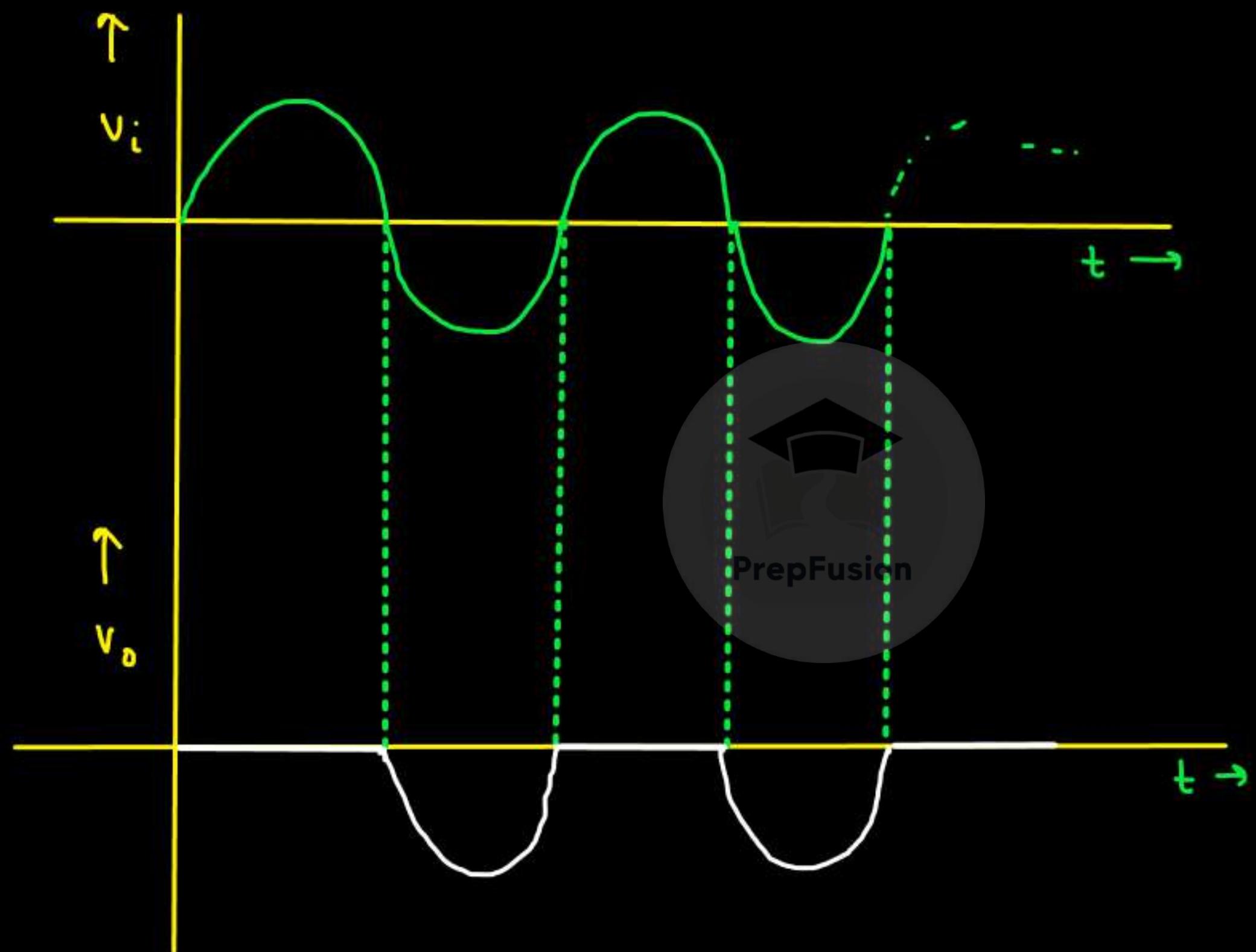


Q.

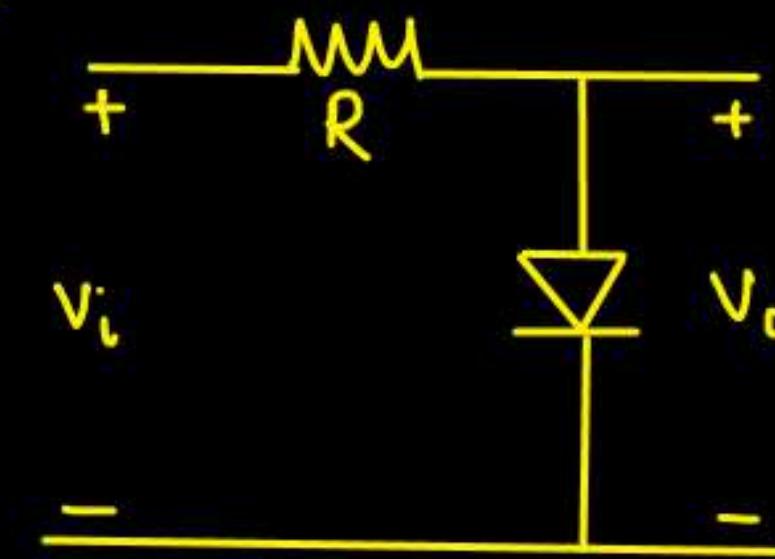

$$V_T = 0.7V$$



Draw Transfer characteristics.

→ O.C. Test

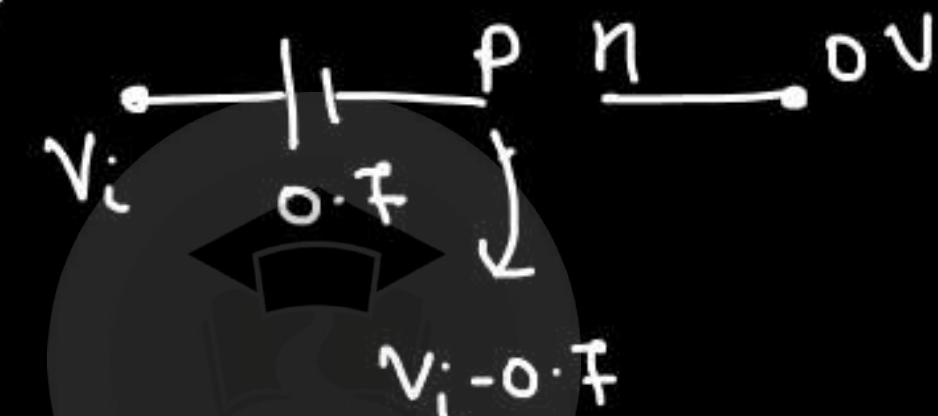

PrepFusion

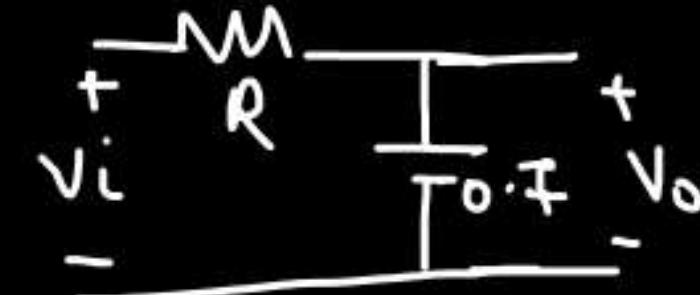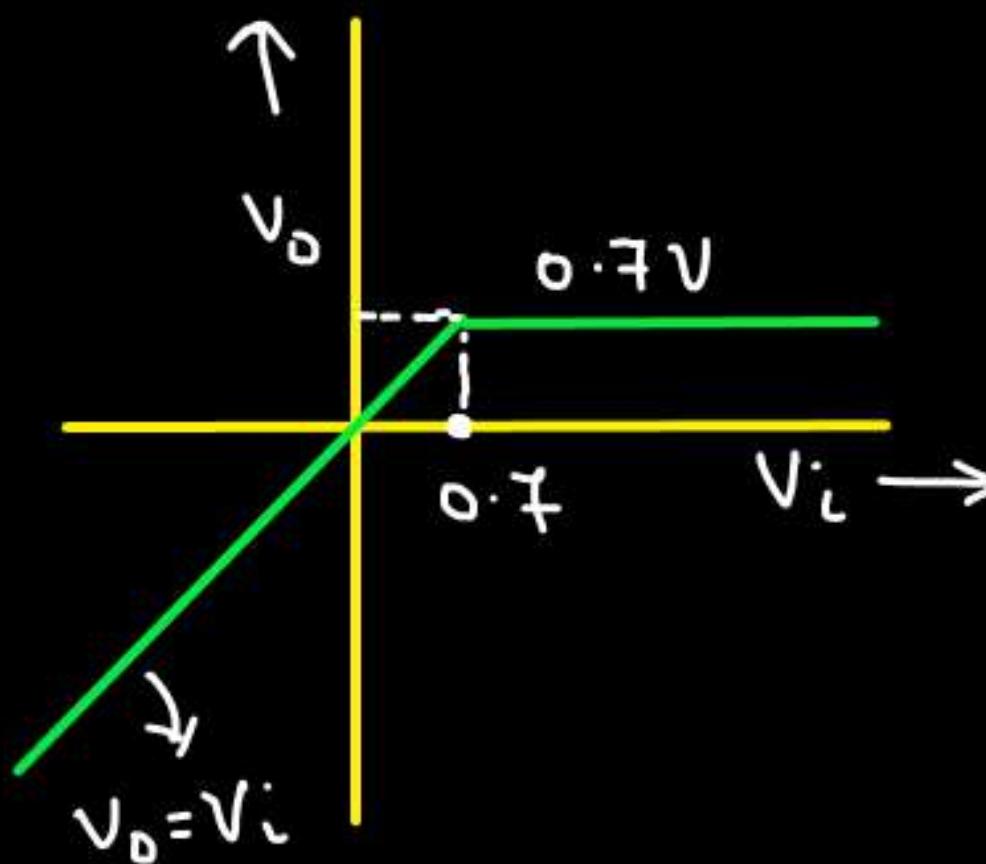(i) $V_i - 0.7 > 0 \Rightarrow V_i > 0.7 \Rightarrow \text{diode ON}$




$$V_o = 0.7V$$

(ii) $V_i < 0.7 \Rightarrow \text{diode OFF}$

$$V_o = V_i$$

2. Negative Shunt Clipper Ckt:-

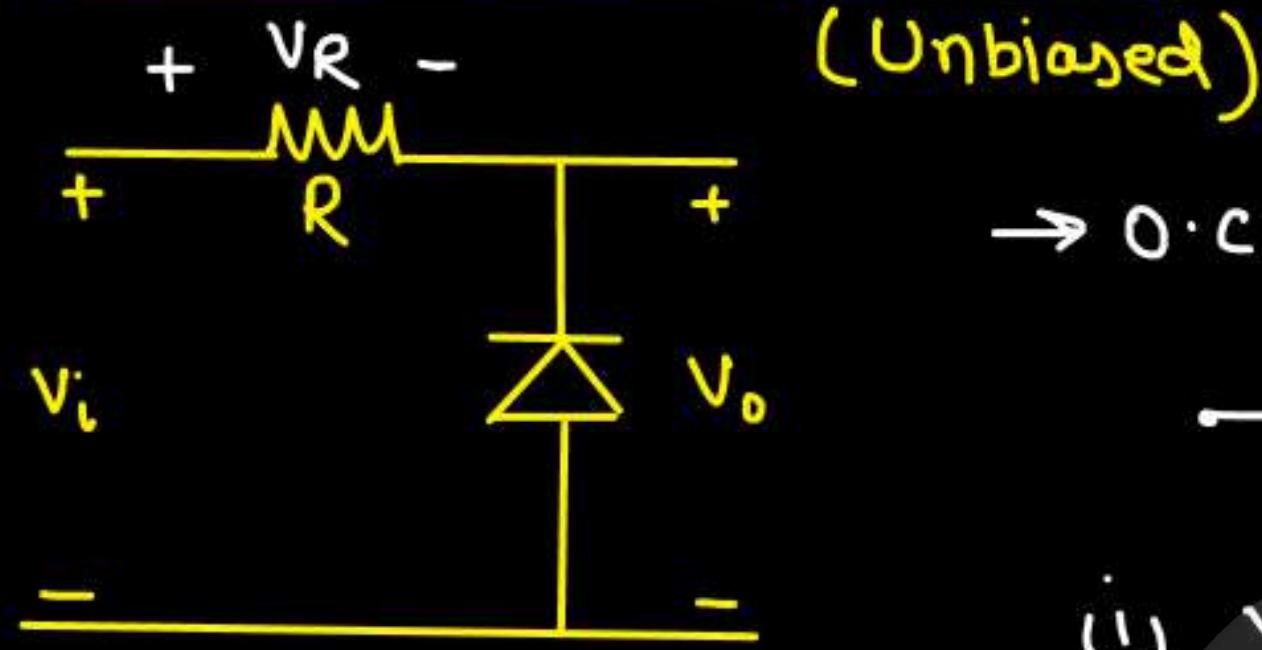


→ O.C. Test :-

$$\frac{V_i}{n} \xrightarrow{\text{P}} 0V$$


(i) $V_i > 0V \Rightarrow$ diode off

$$V_o = V_i$$

PrepFusion

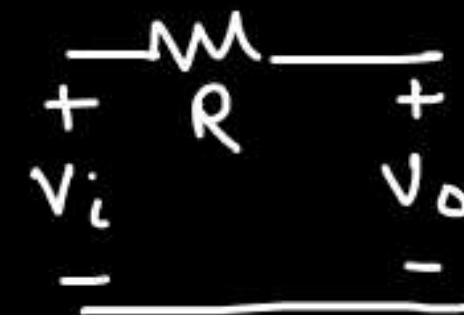


$$\Rightarrow V_R = 0V$$

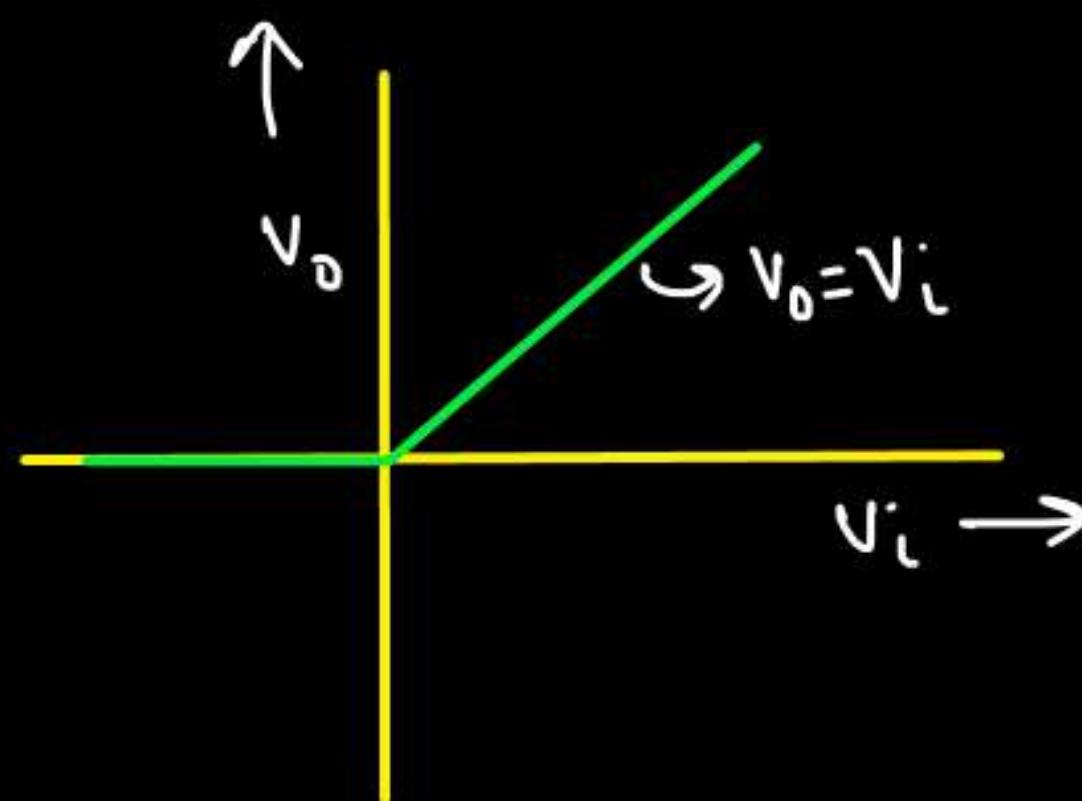


(ii) $V_i < 0V \Rightarrow$ diode on



$$V_o = 0V$$

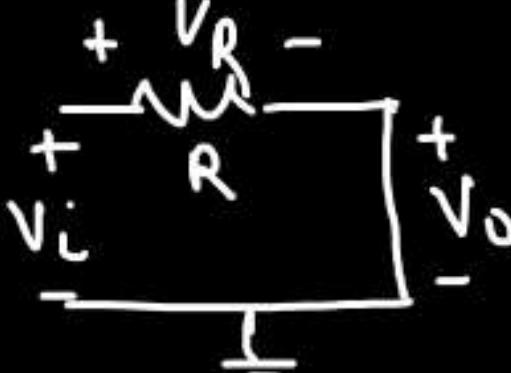


$$\Rightarrow V_R = V_i$$

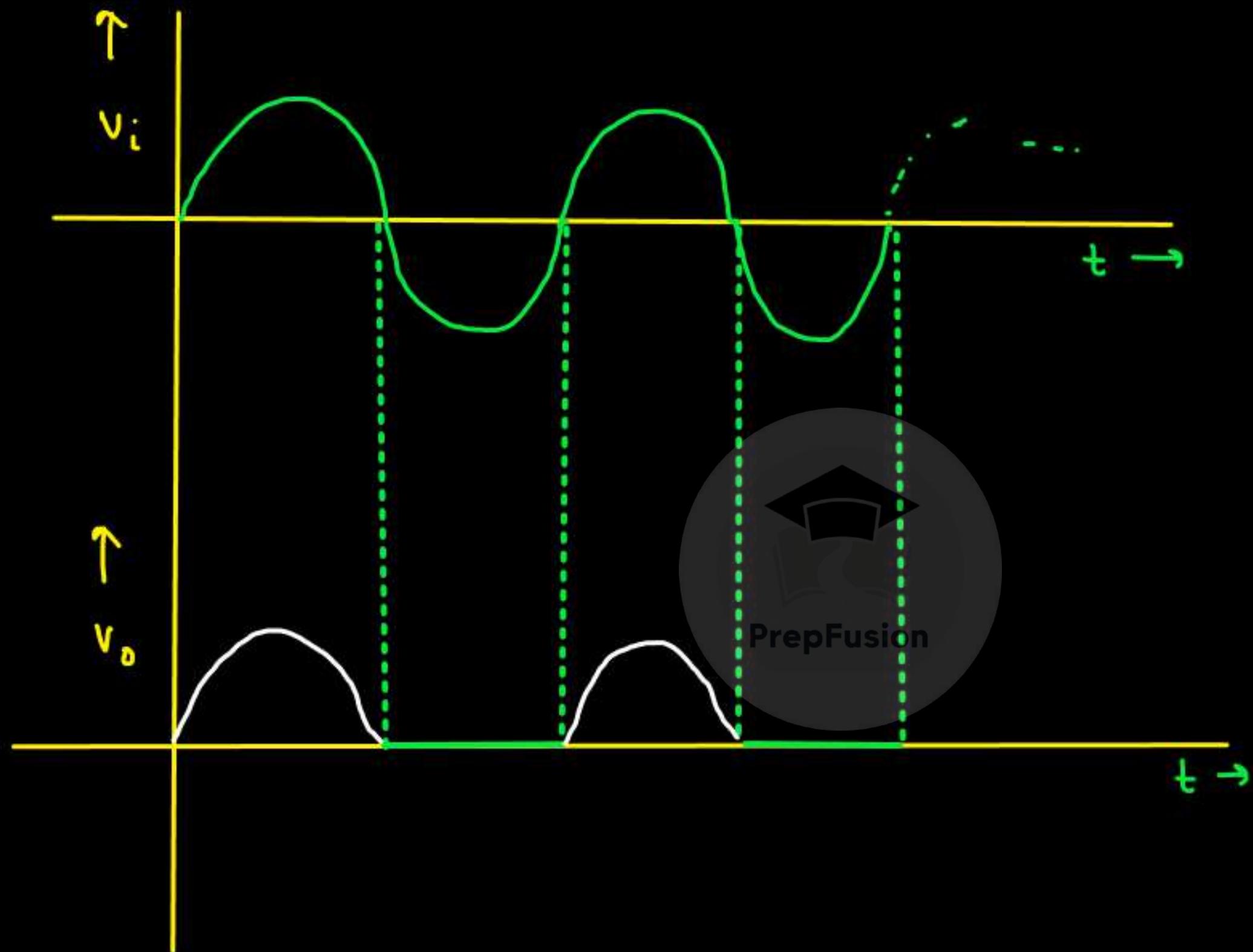

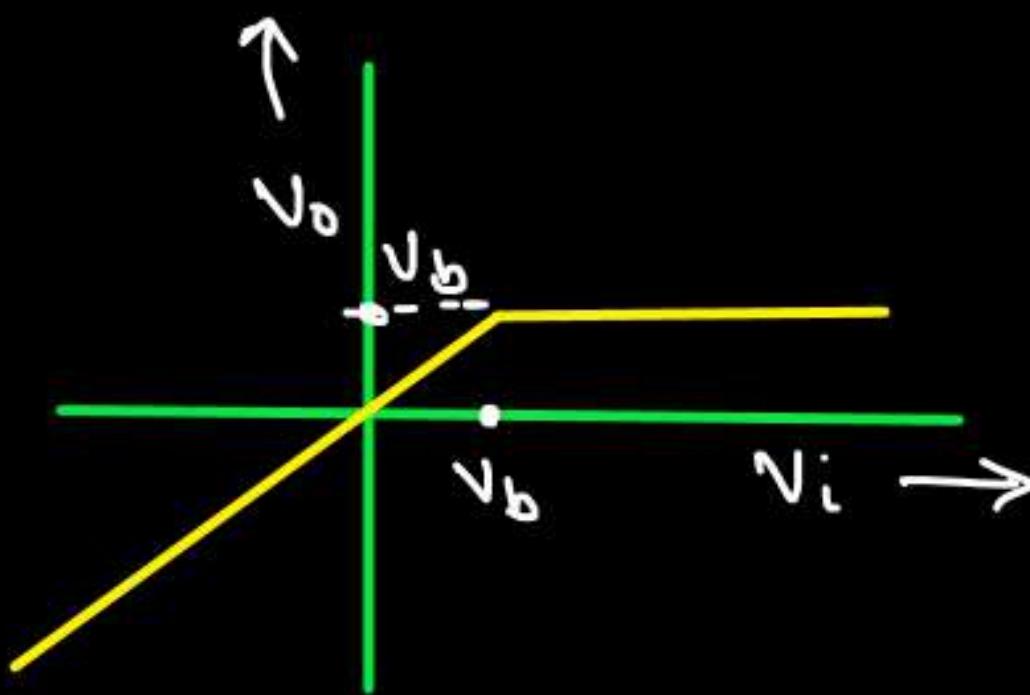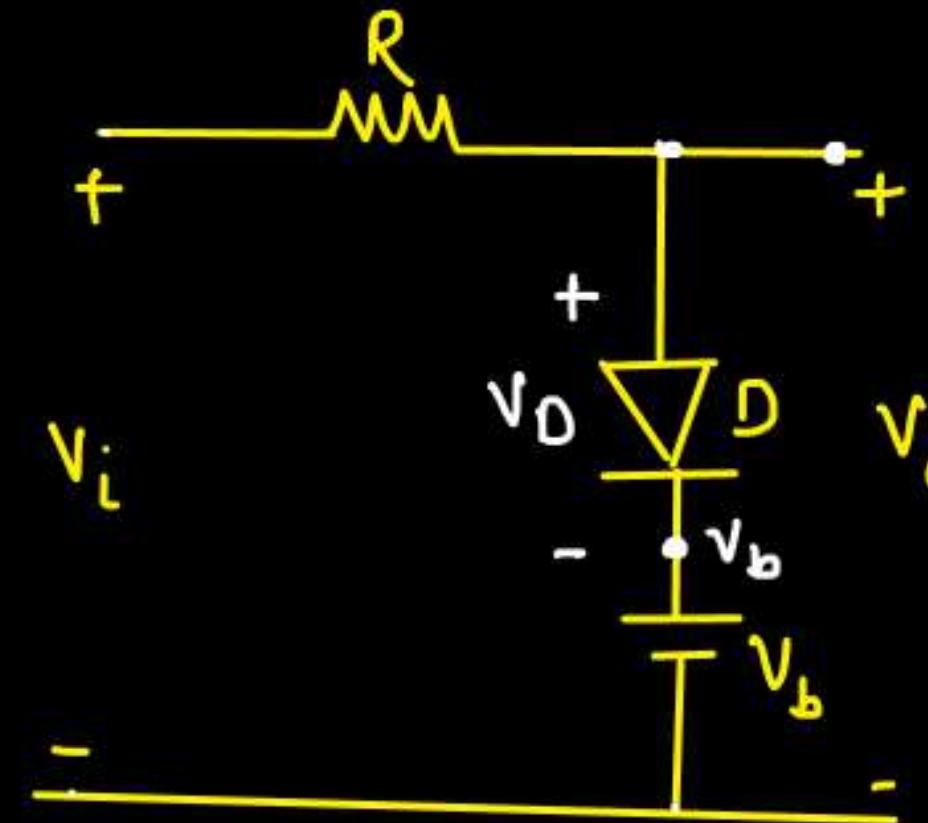3. Positive shunt clipper ckt (Positive bias) :-



(i) $V_i > V_b \Rightarrow$ diode ON

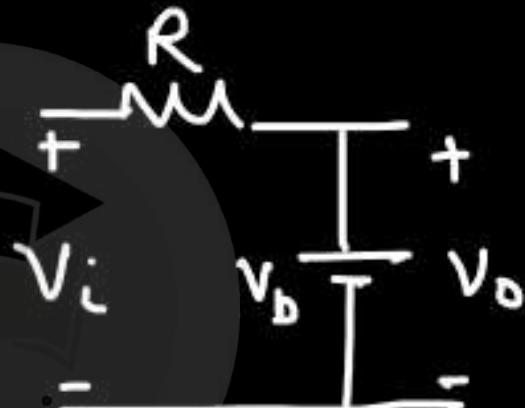


$$V_D = 0V$$

PrepFusion


$$V_D = V_b$$

(ii) $V_i < V_b \Rightarrow$ diode OFF

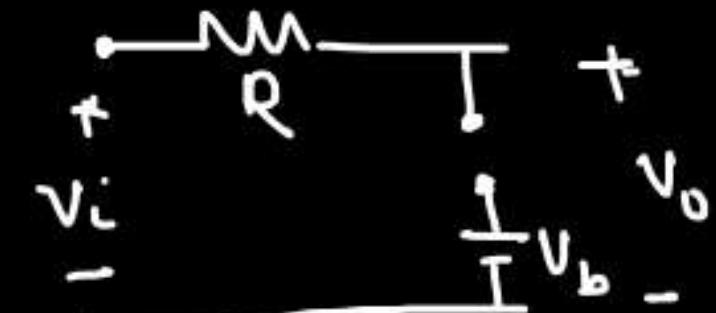


$$V_o = V_i$$

$$V_D = V_i - V_b$$

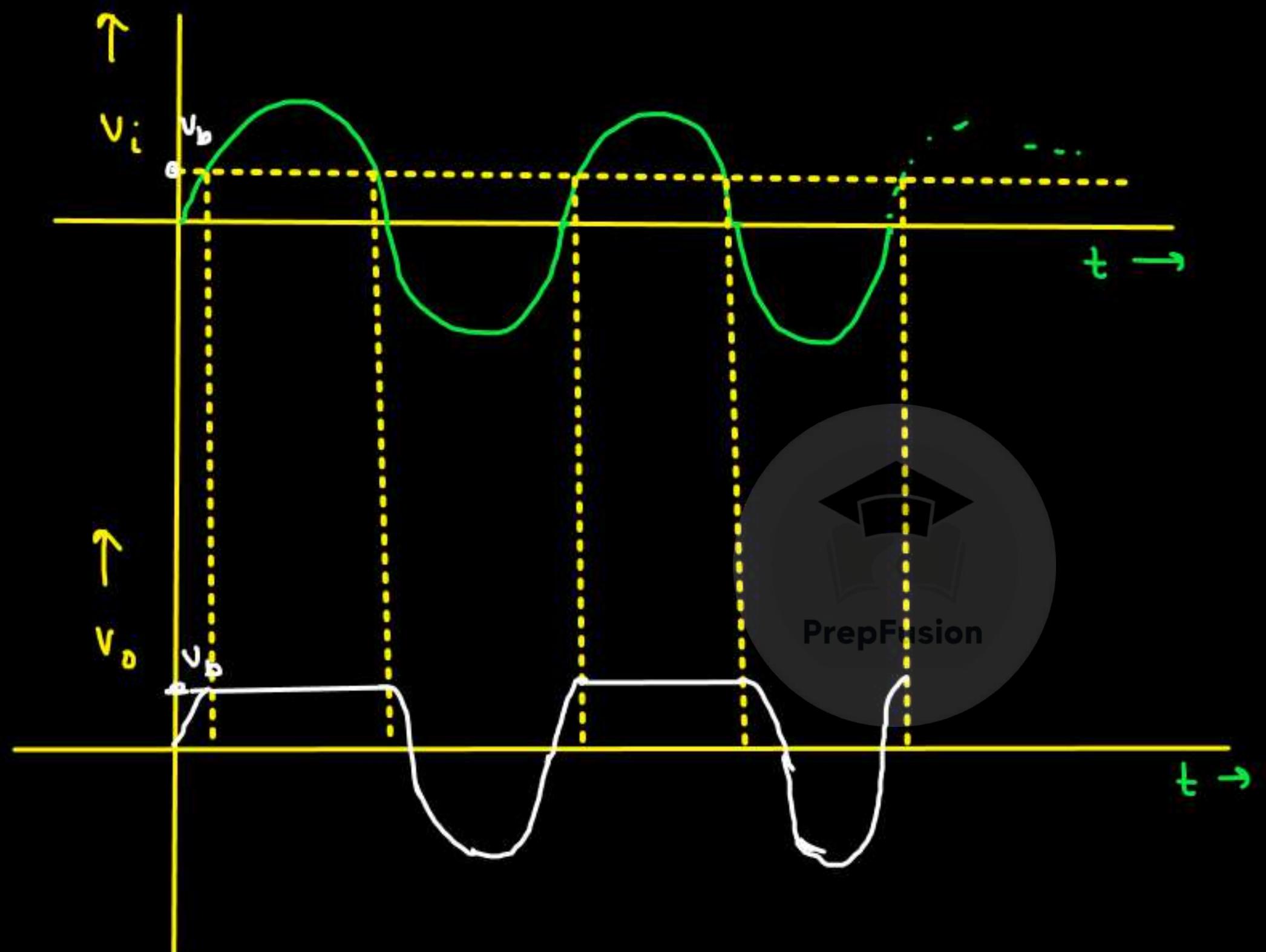

PrepFusion

Q.

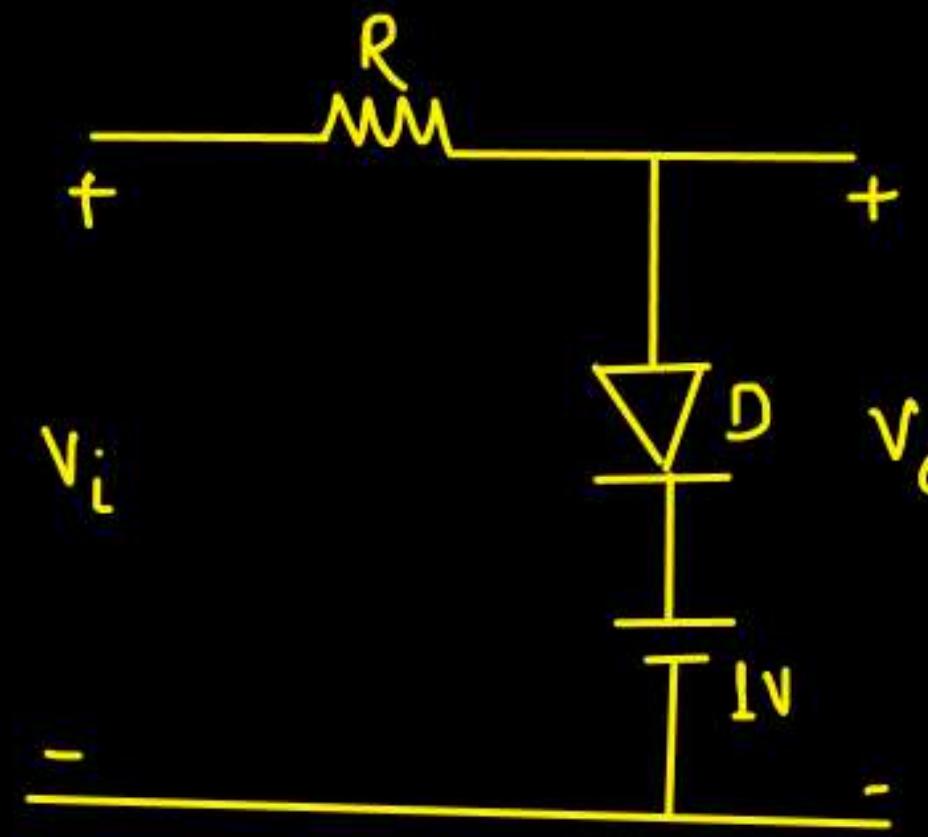

$$V_f = 0.7V$$


Draw Transfer characteristics.



(i) $V_i > 1.7V \Rightarrow$ diode on



PrepFusion

$$V_o = 1.7V$$

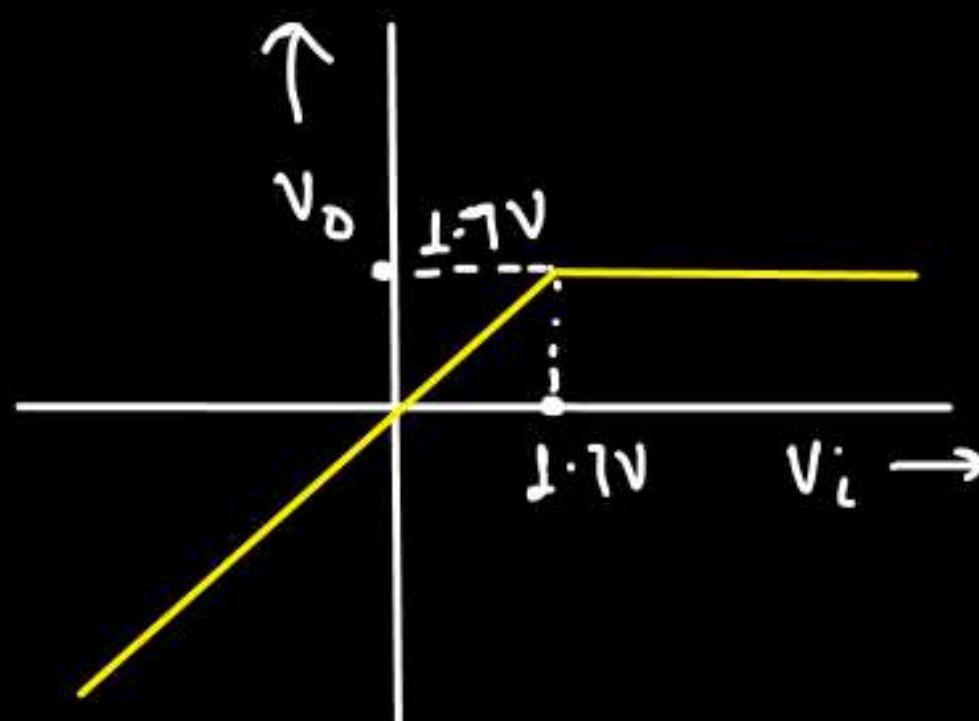


(ii) $V_i < 1.7V \Rightarrow$ diode off


$$V_o = V_i$$

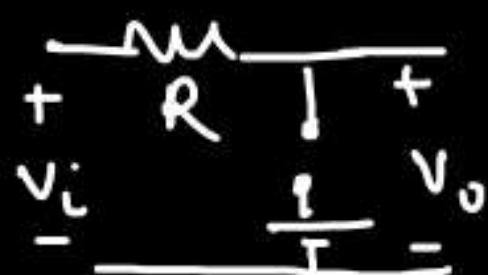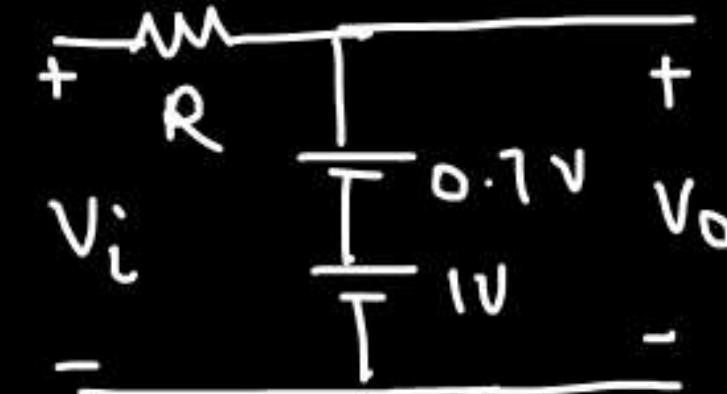

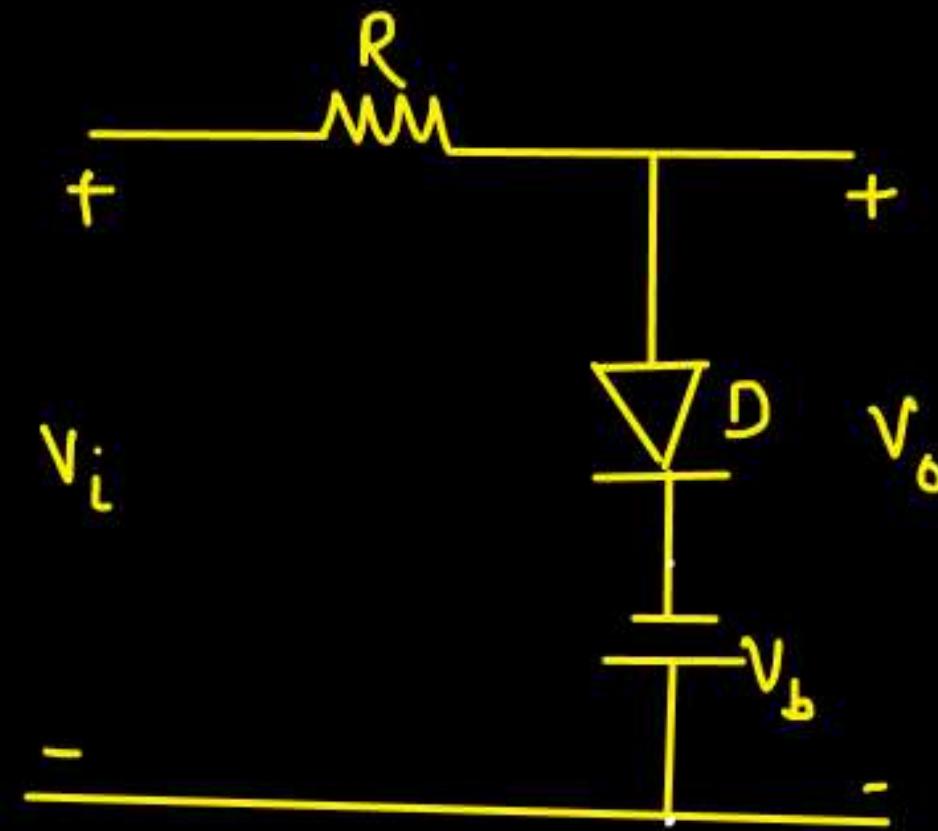4. Positive shunt Clipper ckt (Negative bias) :-



* O.C. Test


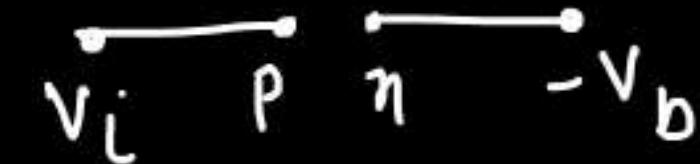



(i) $V_i > -V_b \Rightarrow$ diode ON

$$\Rightarrow V_o = -V_b$$


(ii) $V_i < -V_b \Rightarrow$ diode off

$$V_o = V_i$$

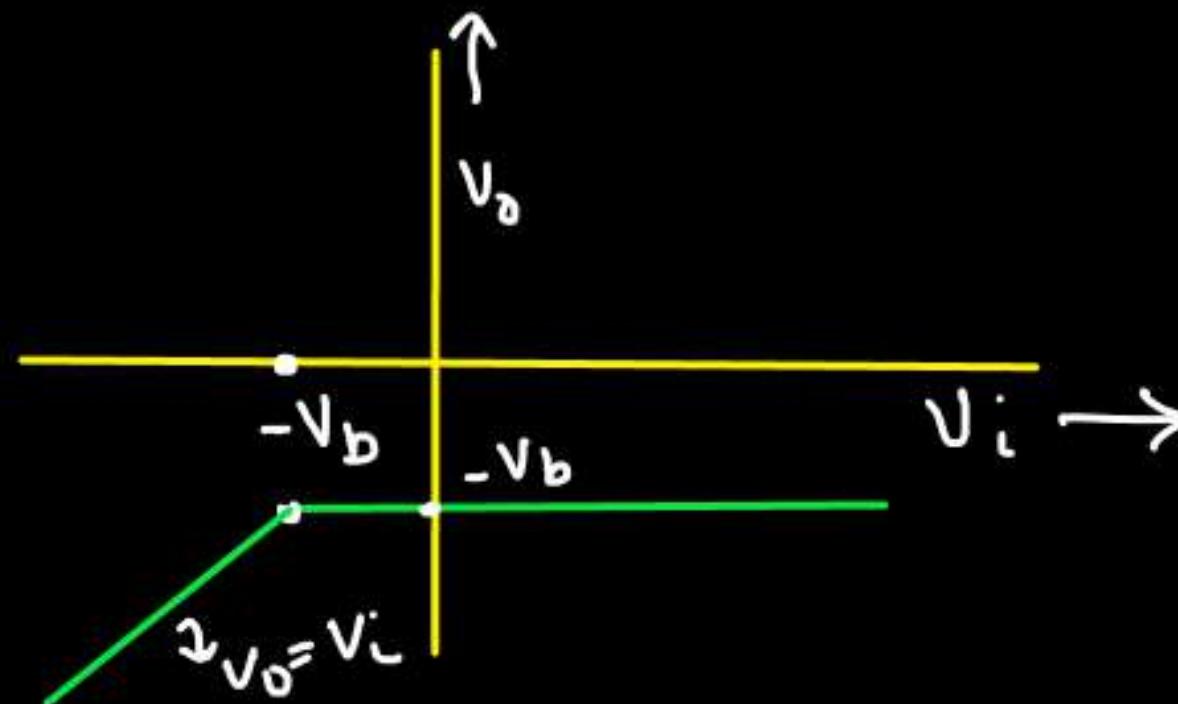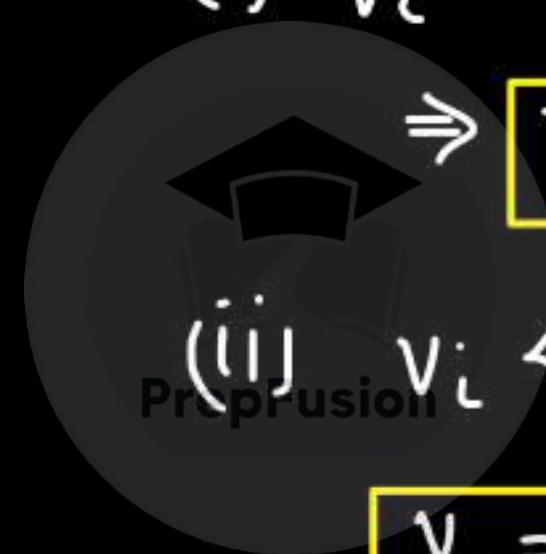

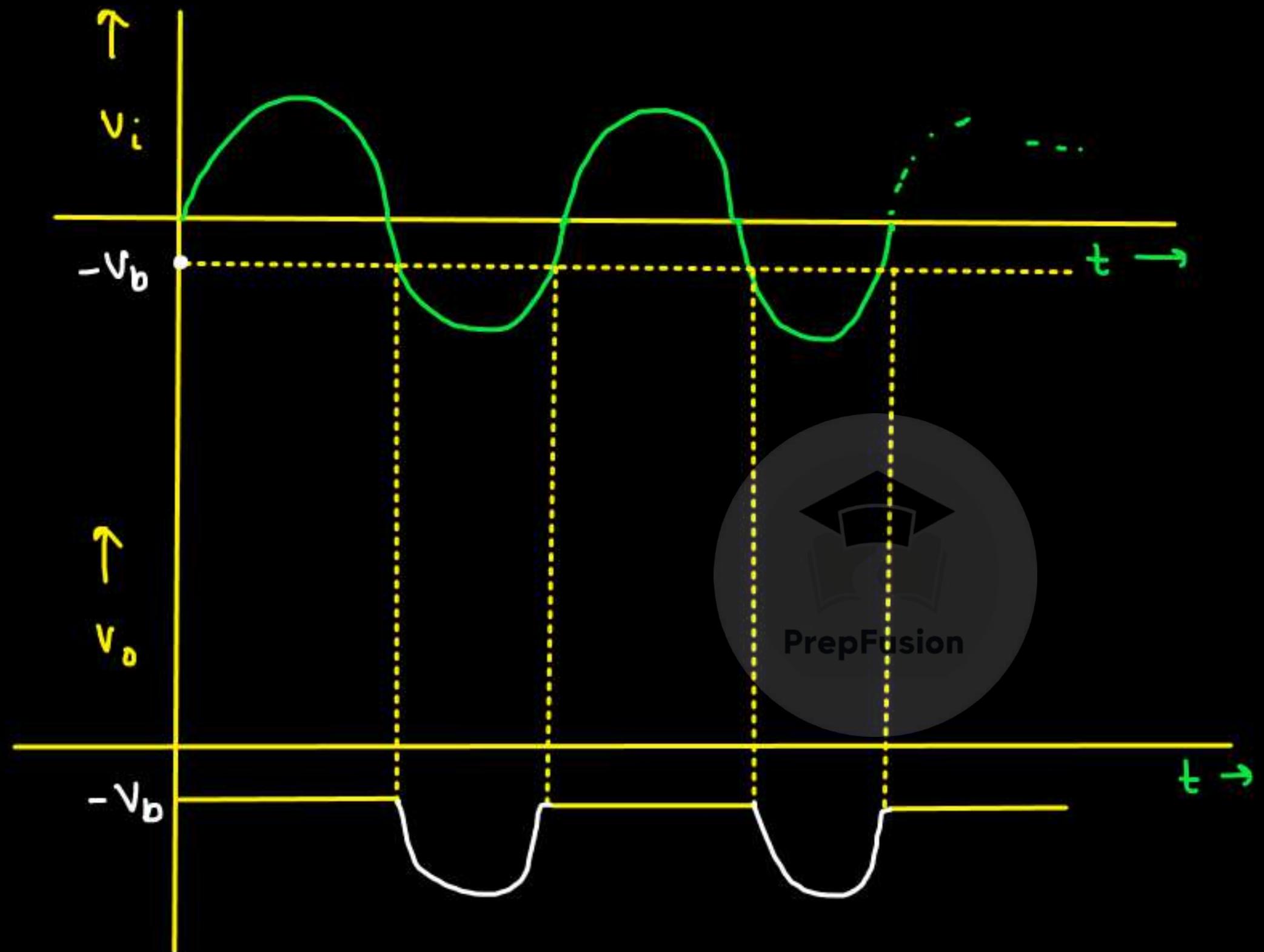


Q.

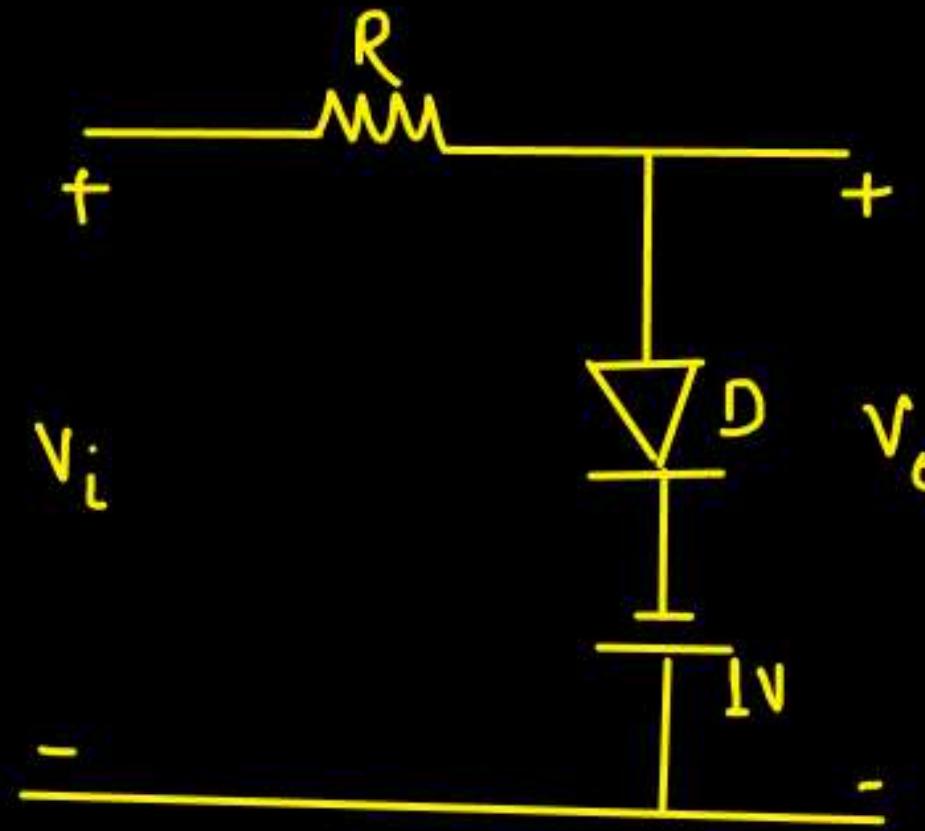

$$V_T = 0.7V$$


Draw Transfer characteristics.

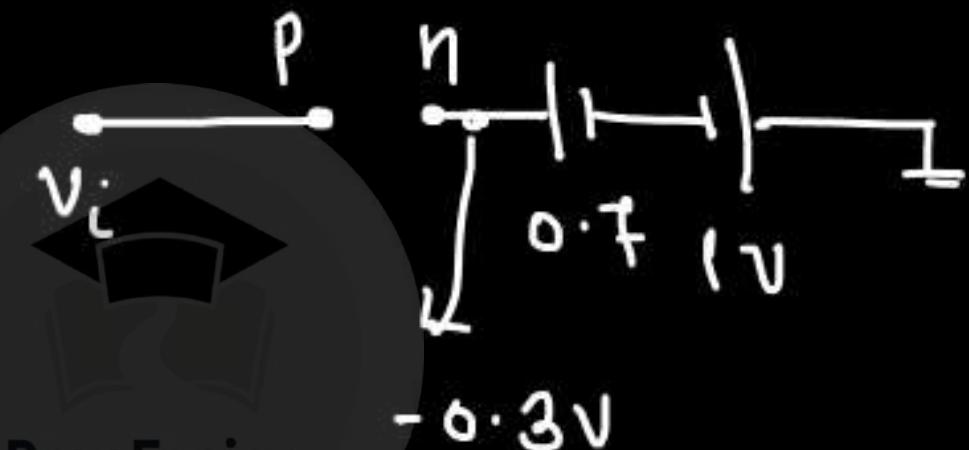

PrepFusion


(i) $V_i > -0.3V \Rightarrow$ diode ON

$$V_D = -0.3V$$

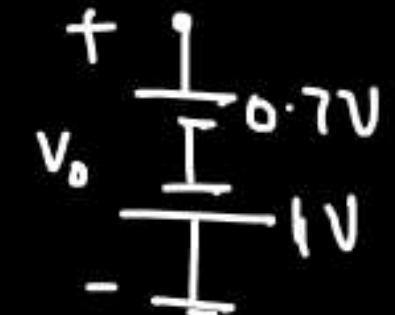


(ii) $V_i < -0.3V \Rightarrow$ diode off

$$V_D = V_i$$

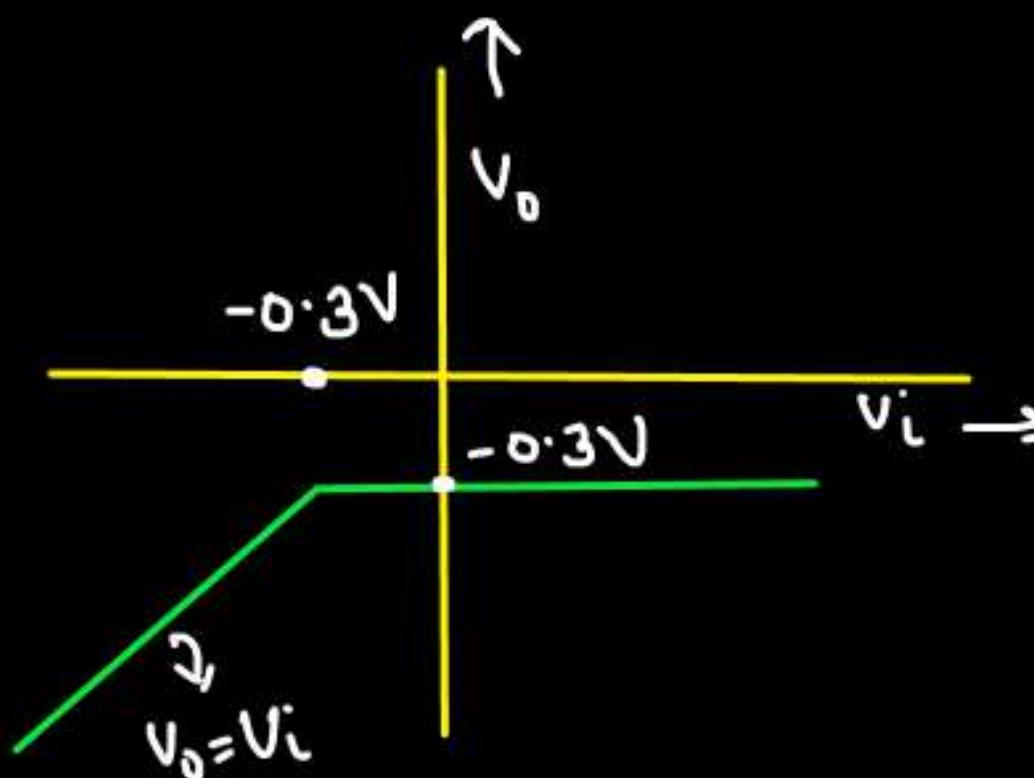

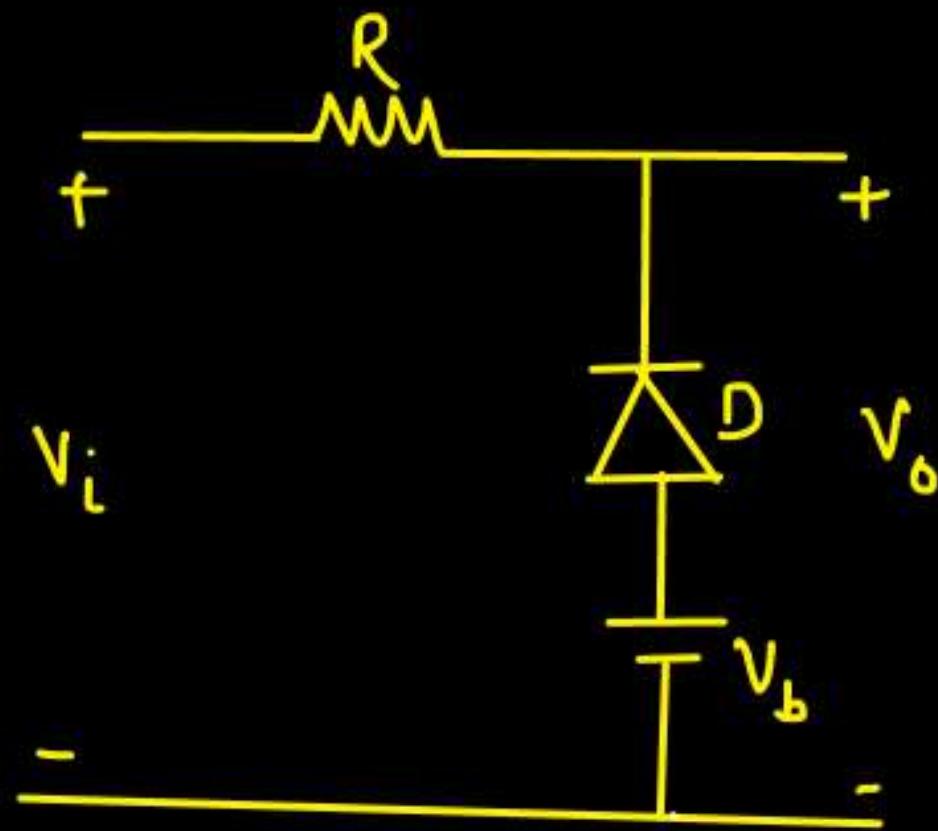5. Negative shunt clipper ckt (Positive bias) :-




(i) $V_i > V_b \Rightarrow$ diode off


$$V_o = V_i$$

(ii) $V_i < V_b \Rightarrow$ diode on


$$V_o = V_b$$

PrepFusion

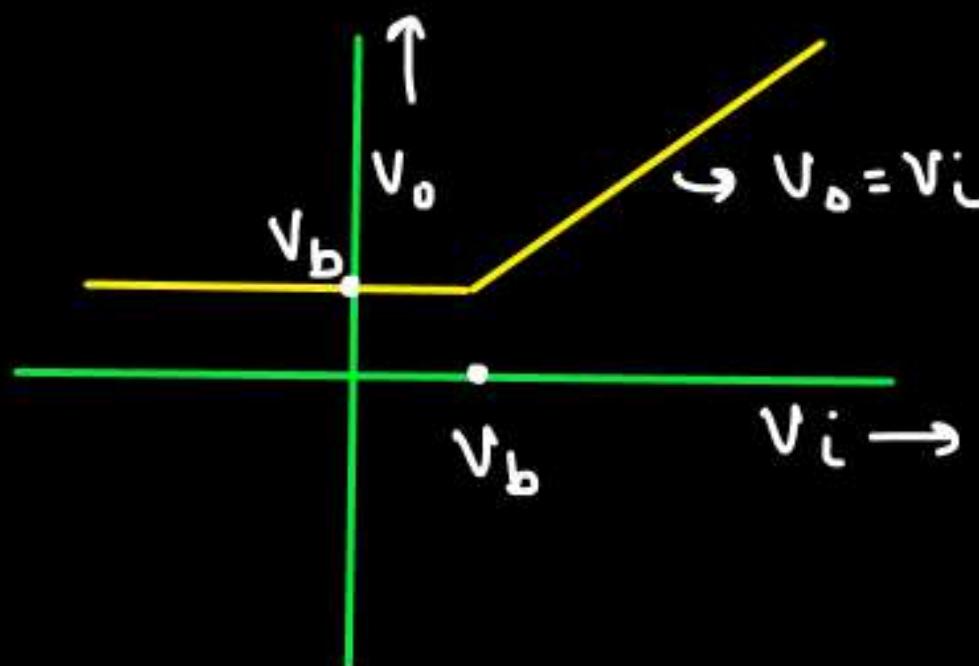


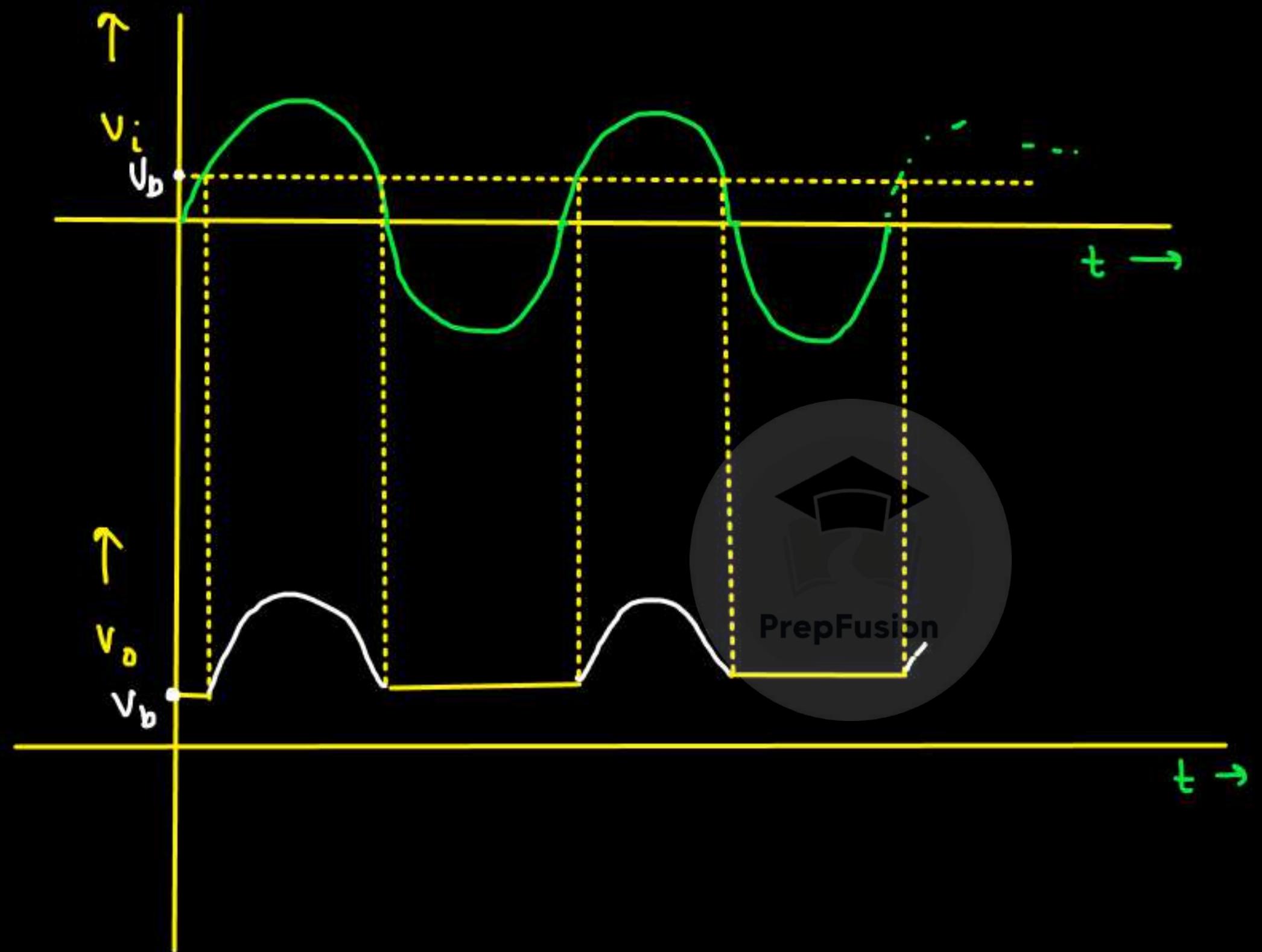


Q.

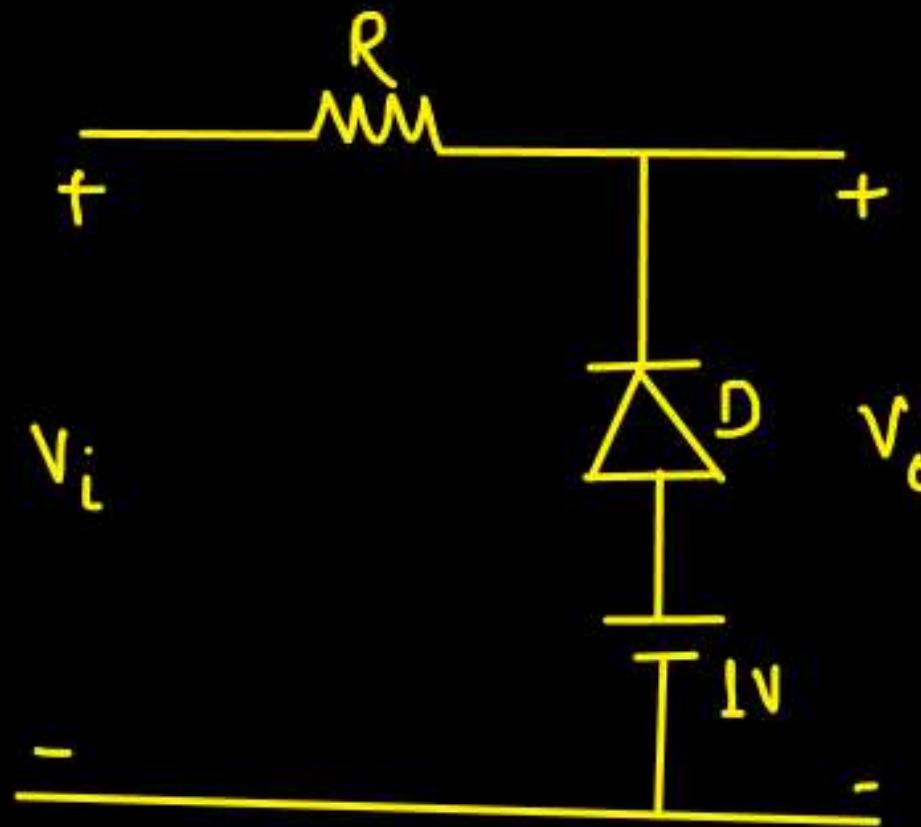

$$V_r = 0.7V$$

Draw Transfer characteristic.

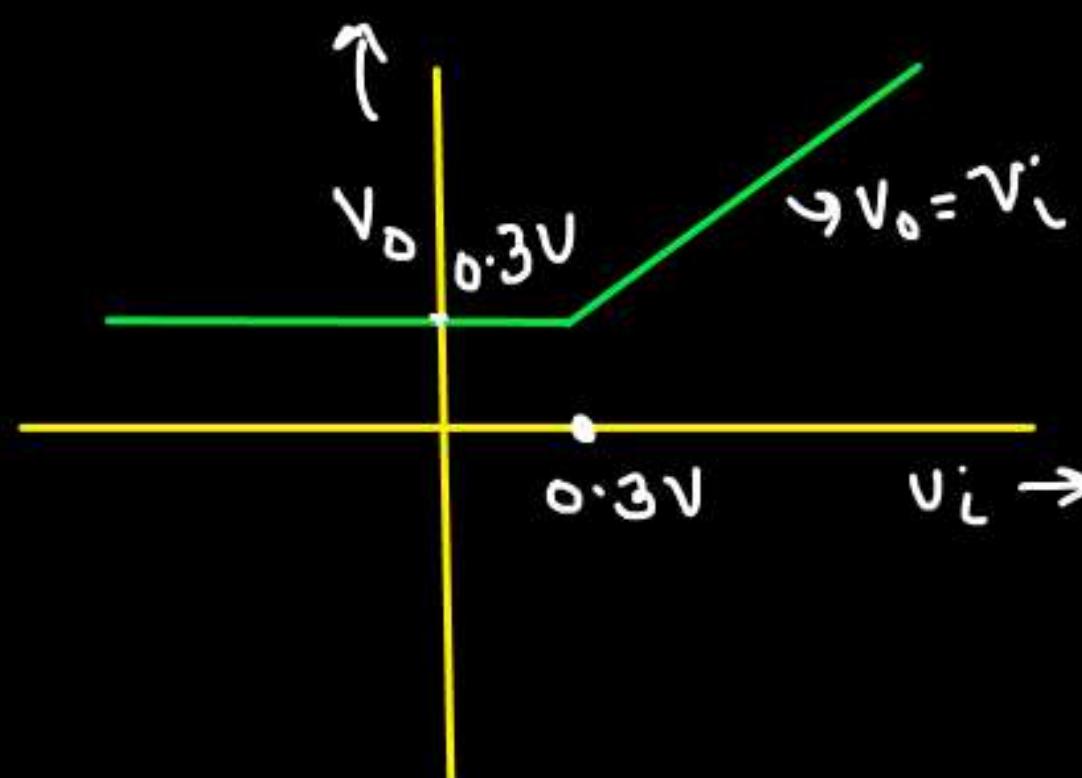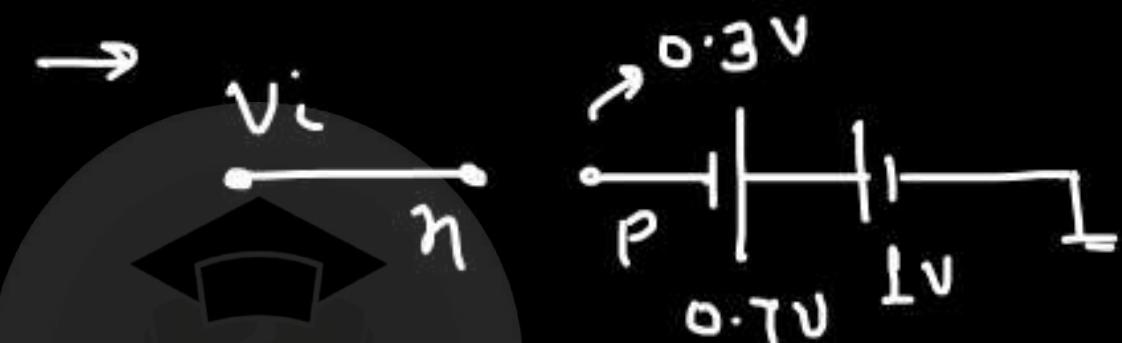


(i) $V_i > 0.3V \Rightarrow$ diode off



$$V_o = V_i$$

(ii) $V_i < 0.3V \Rightarrow$ diode ON

$$V_o = 0.3V$$

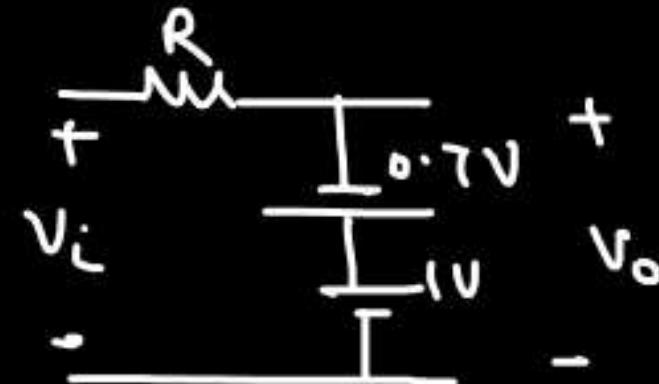

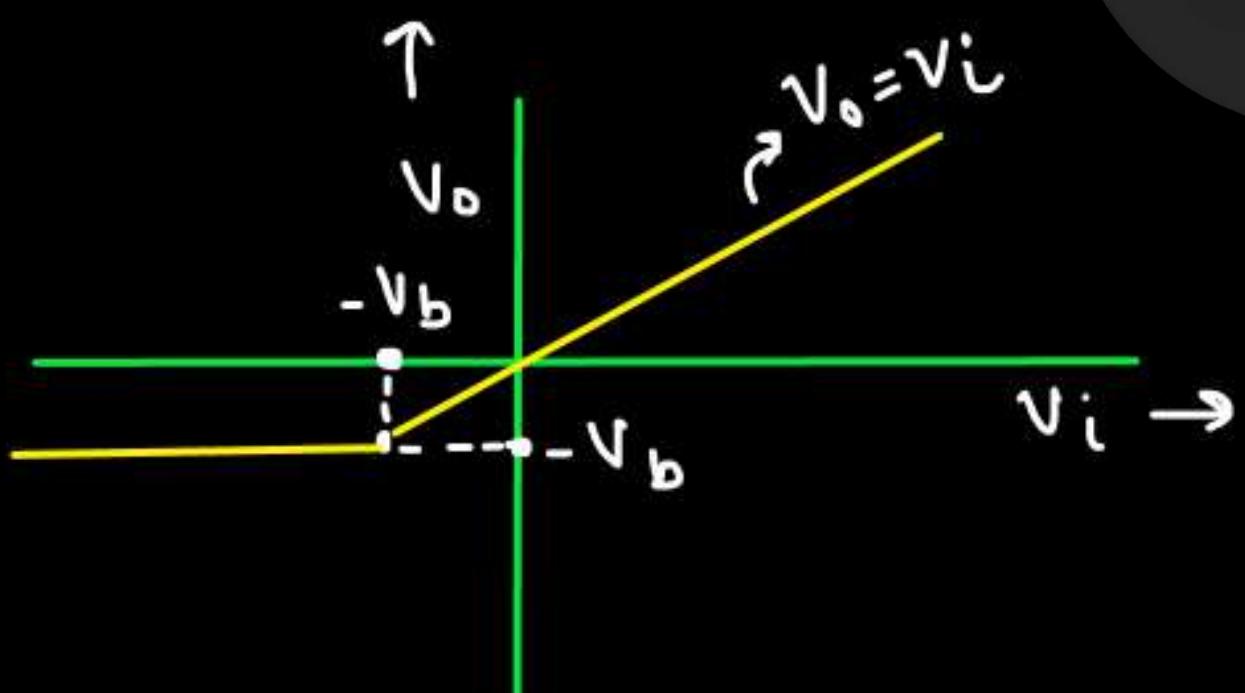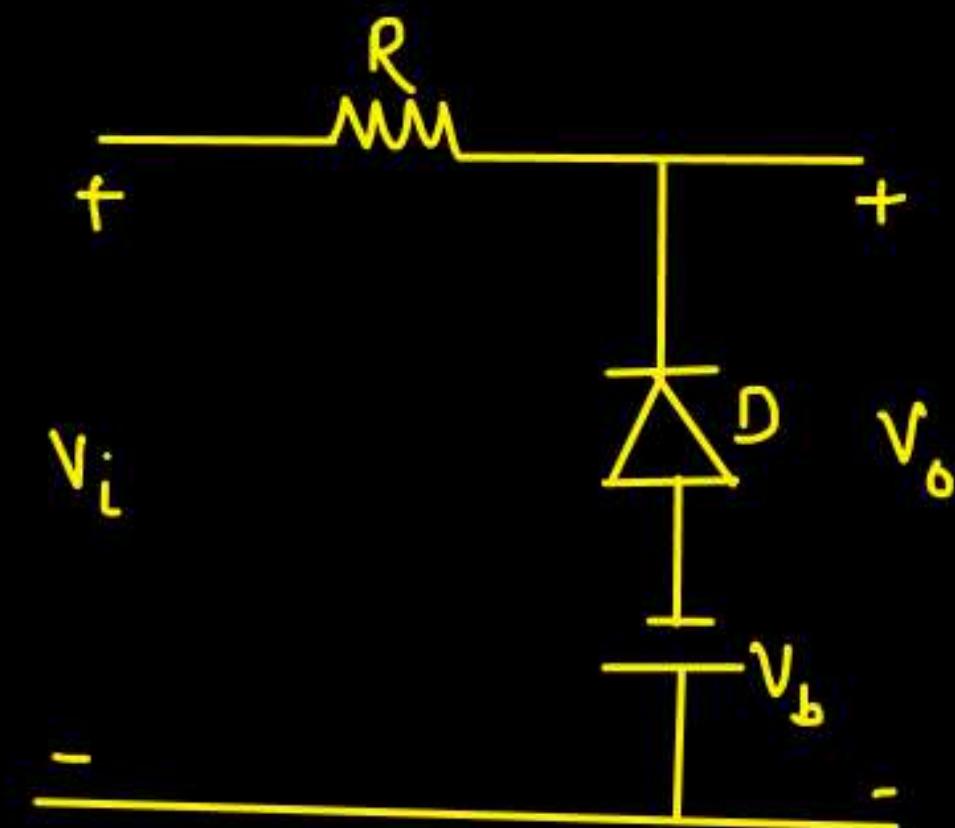5. Negative shunt Clipper ckt (Negative bias) :-




(i) $V_i > -V_b \Rightarrow$ diode off


$$V_o = V_i$$

(ii) $V_i < -V_b \Rightarrow$ diode on

$$V_o = -V_b$$

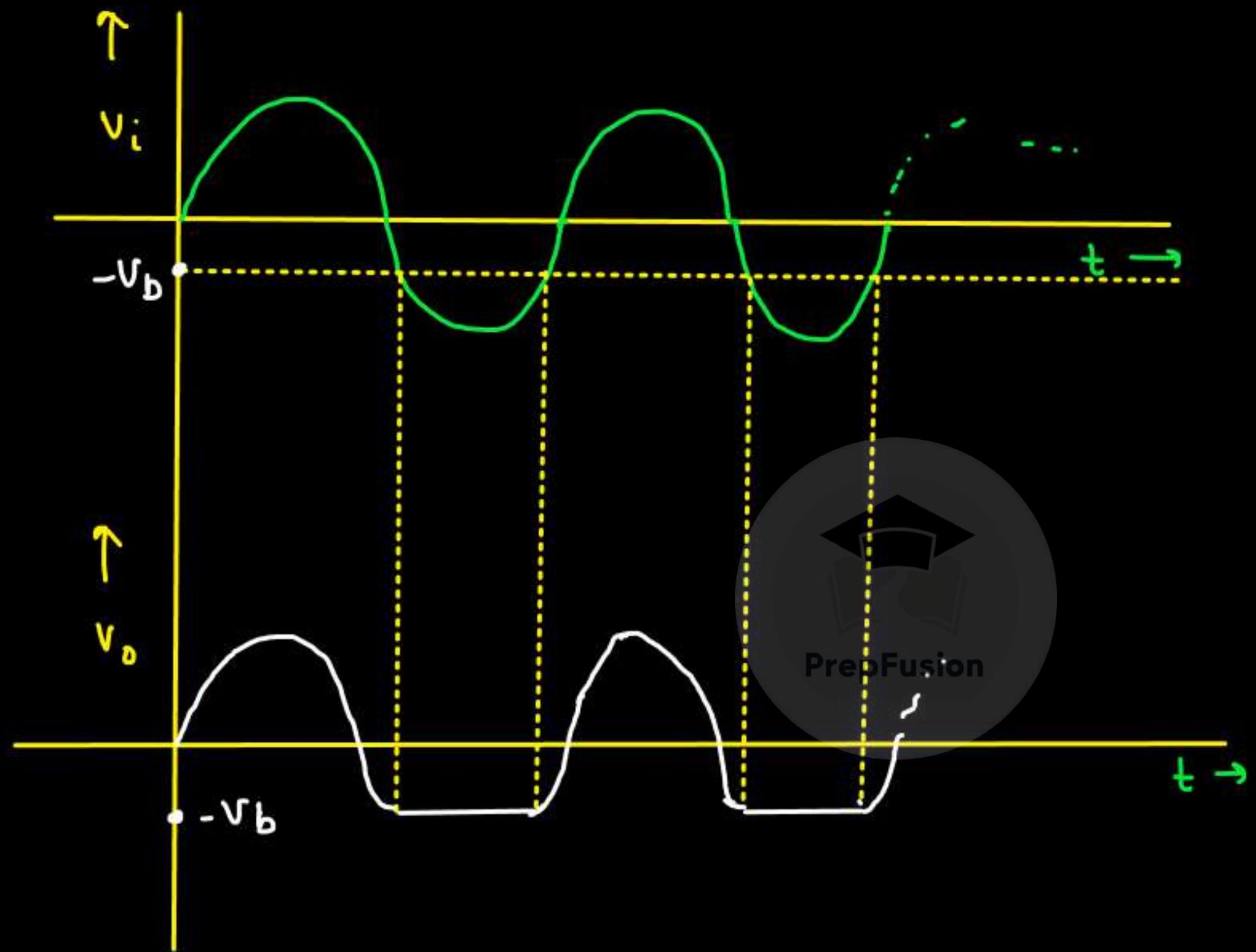

Q.

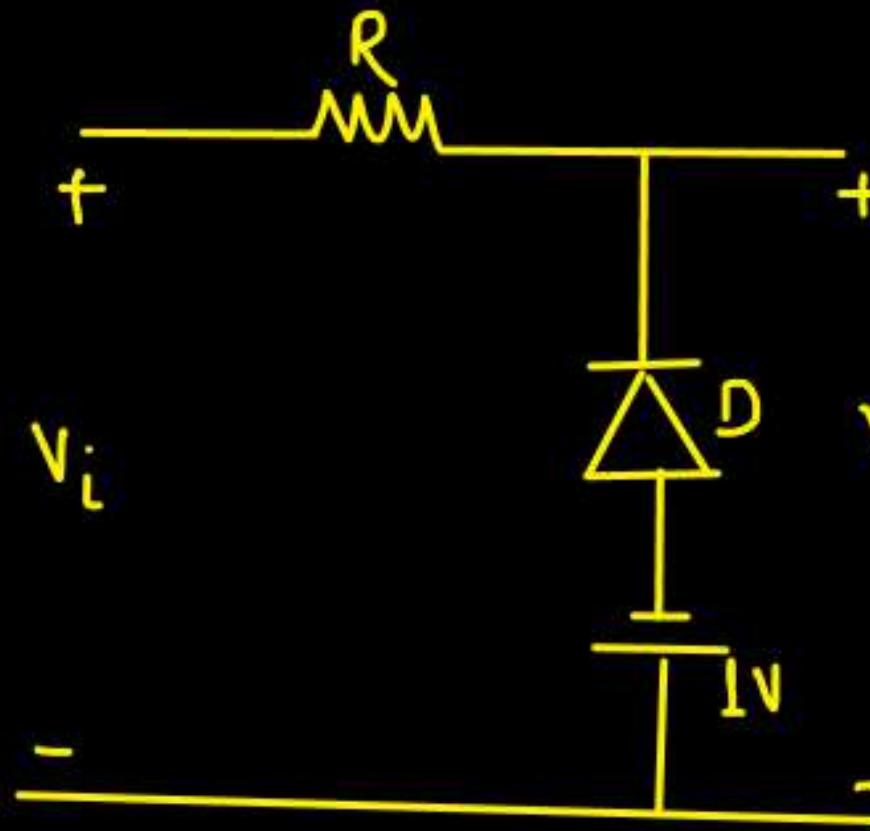

$$V_T = 0.7V$$

Draw Transfer characteristic.




(I) $V_i > -1.7V \Rightarrow$ diode off
PrepFusion

$$\Rightarrow V_o = V_i$$

(II) $V_i < -1.7V \Rightarrow$ diode on


$$\Rightarrow V_o = -1.7V$$

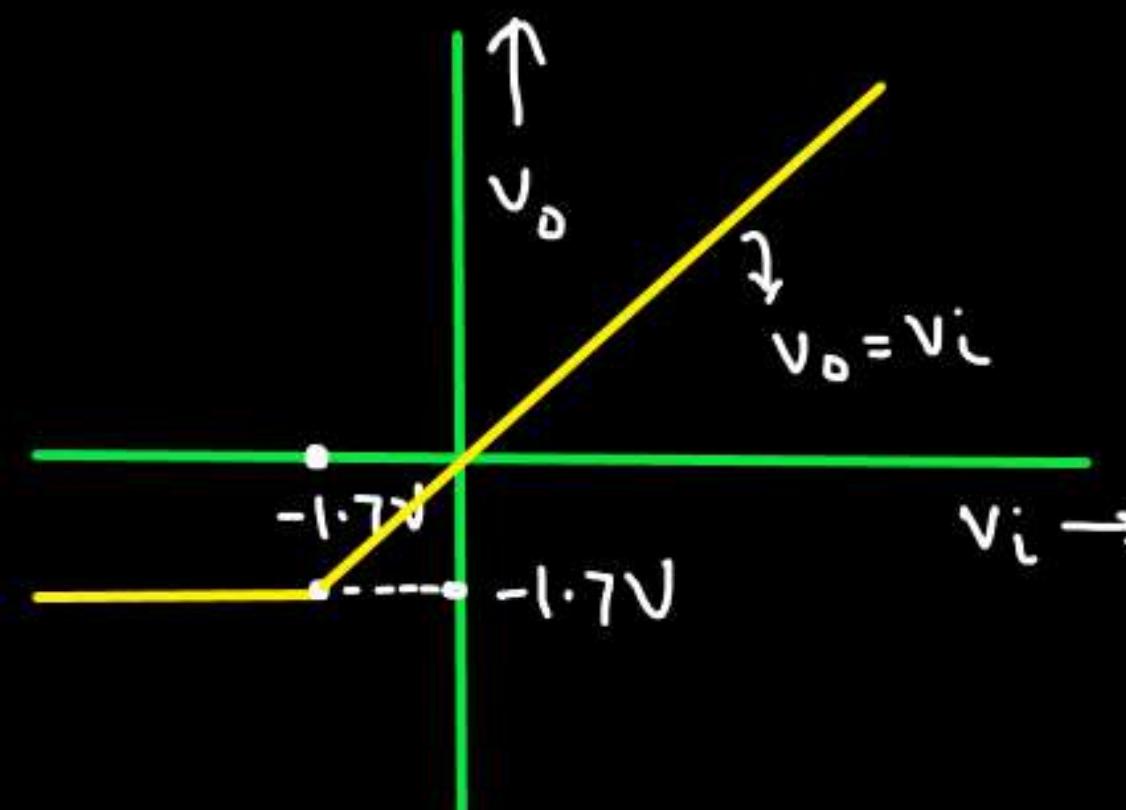

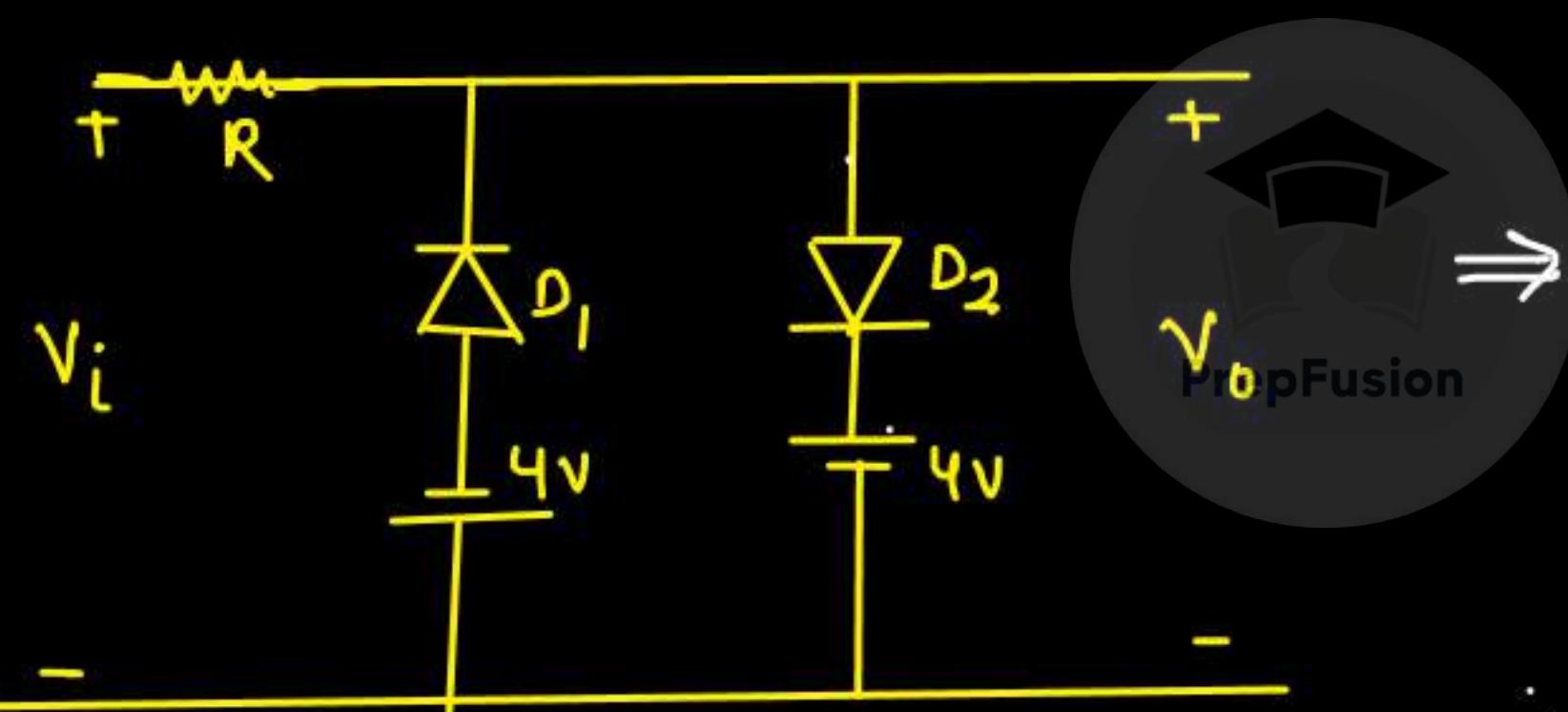Examples of Two level clipper ckt :-


Q. $V_{in} = 20 \sin \omega t$

Draw VTC and find max & min value of V_o .




(ii) $V_i \leq -4V \Rightarrow D_1 \text{ ON}, D_2 \text{ OFF}$

$$V_o = -4V$$

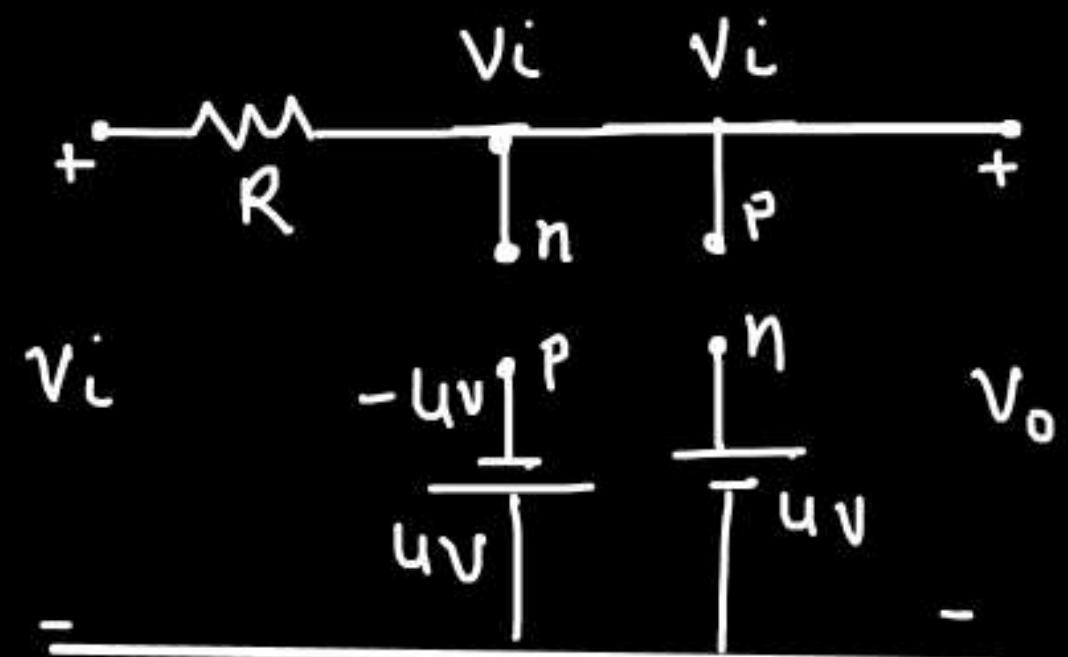


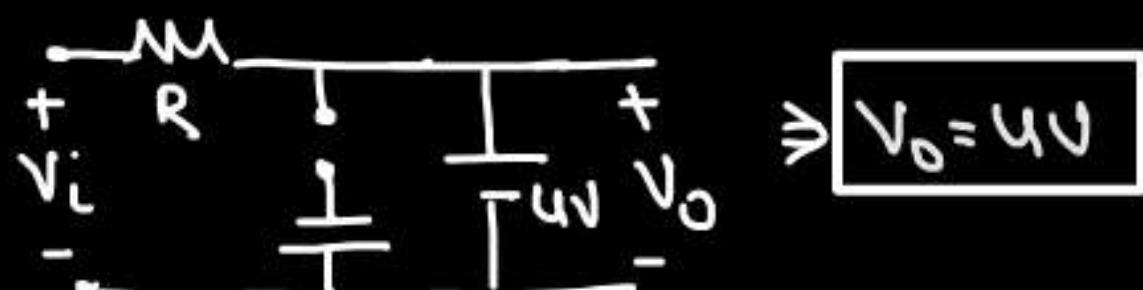(i) $V_i \geq 4V \Rightarrow D_2 \text{ ON}, D_1 \text{ OFF}$



(iii) $-4 < V_i < 4$

$\Rightarrow D_1$ and D_2 are off

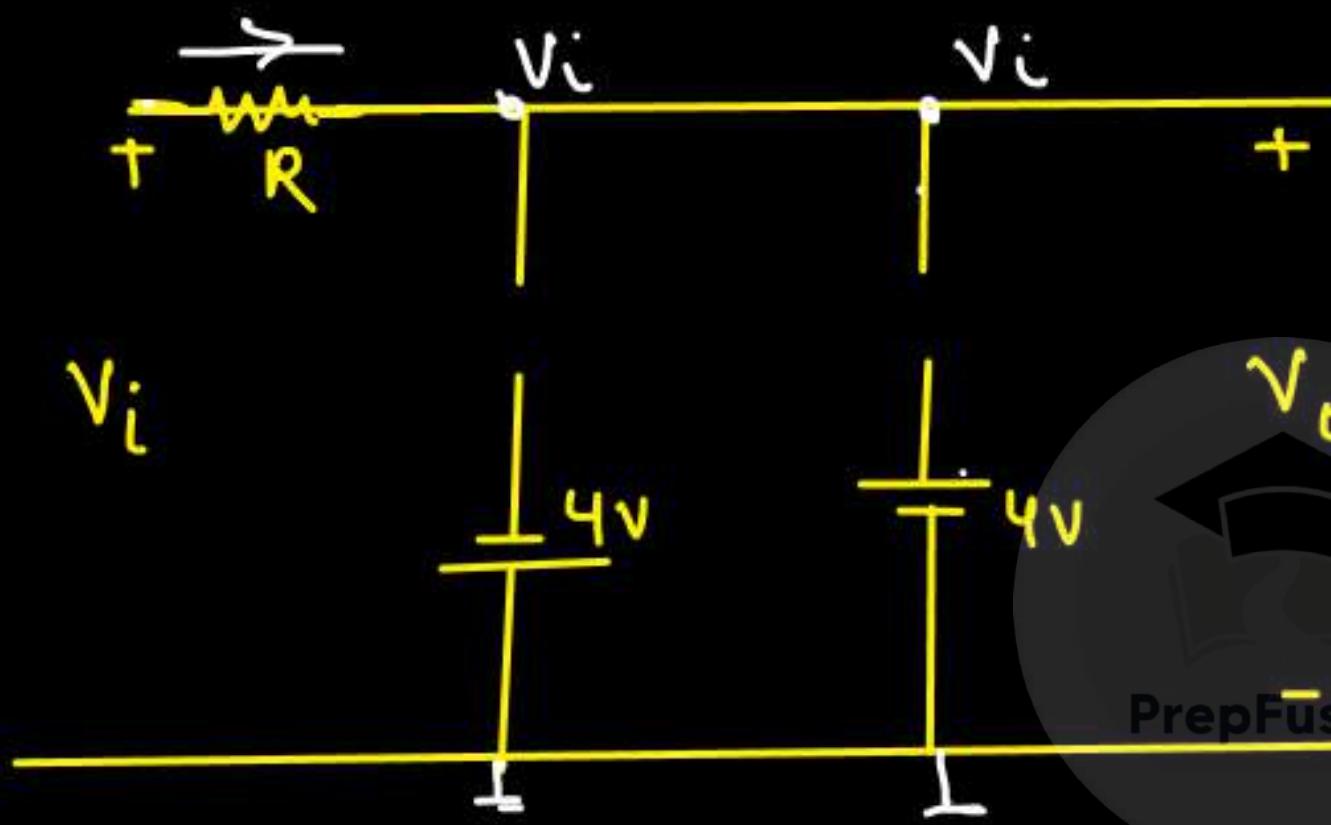


$$V_o = V_i$$

Conclusion:-


$$(i) V_i \geq 4V \Rightarrow V_o = 4V$$

$$(ii) V_i \leq -4V \Rightarrow V_o = -4V$$
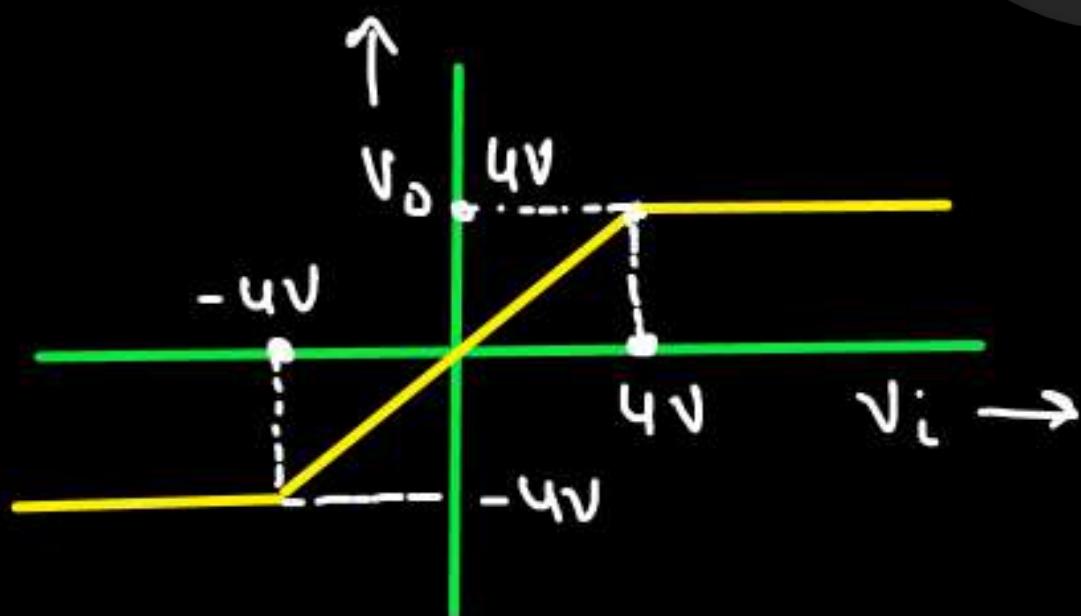
$$(iii) -4V \leq V_i \leq 4V \Rightarrow V_o = V_i$$




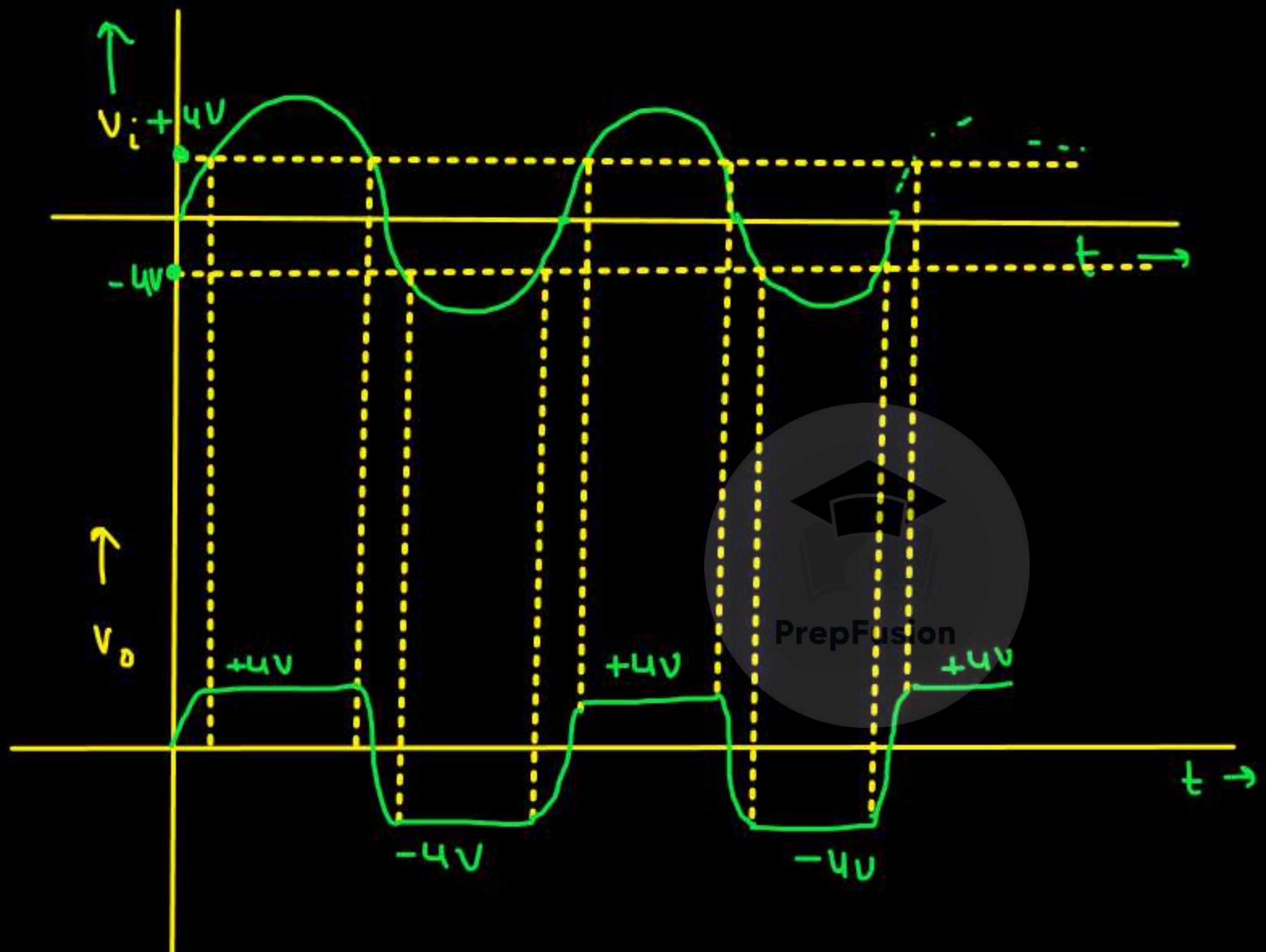
$$\begin{aligned} \text{max} &= +4V \\ \text{min} &= -4V \end{aligned}$$



Q. $V_{in} = L_0 \sin \omega t$

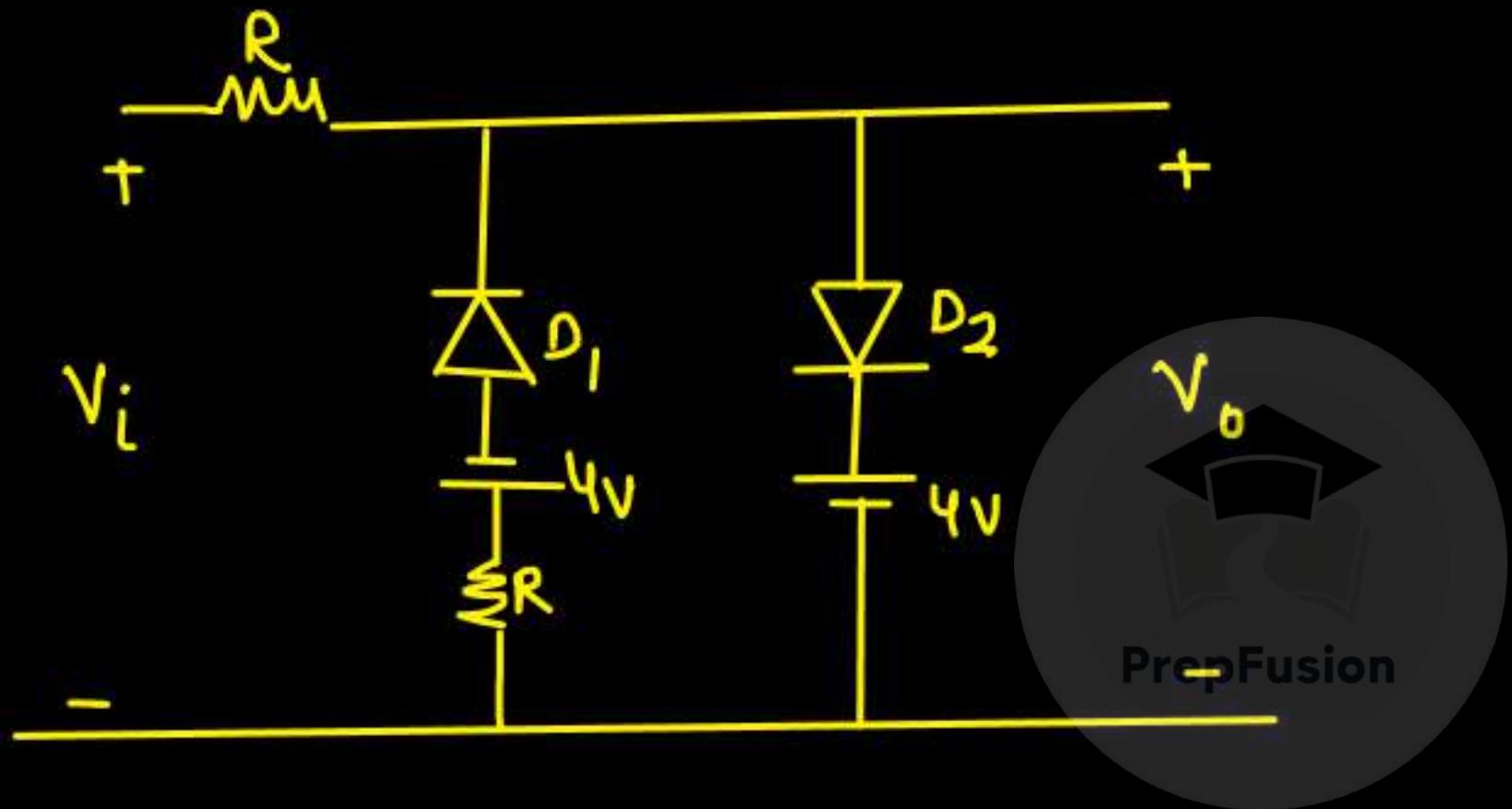Draw VTC and find max & min value of V_o .



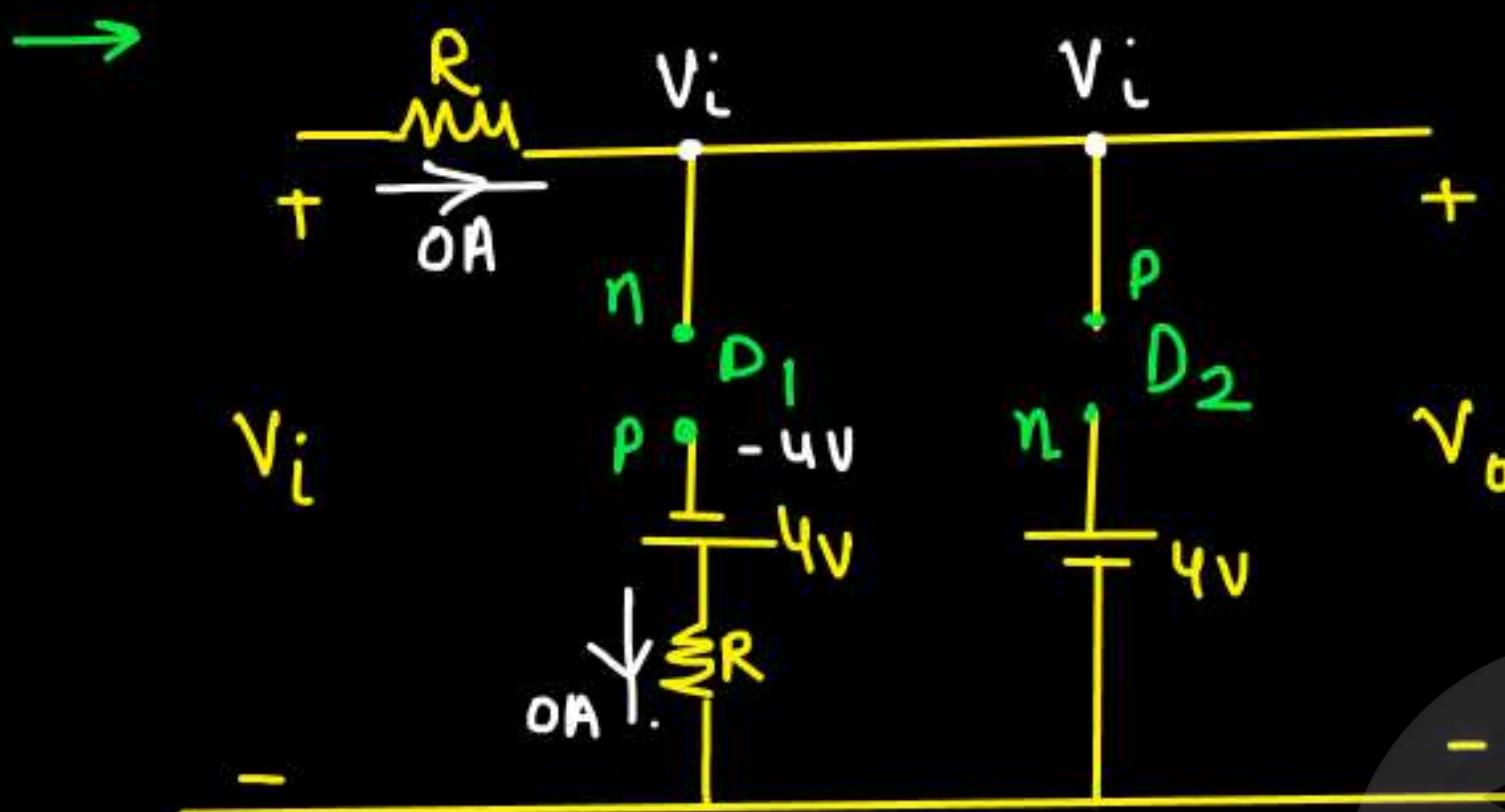


(i) $V_i > 4V$
 \Rightarrow diode D_2 ON
 diode D_1 OFF
 $V_D = 4V$

(ii) $-4V < V_{in} < 4V$
 $\Rightarrow D_1$ and D_2 OFF

$$V_0 = V_i \eta$$

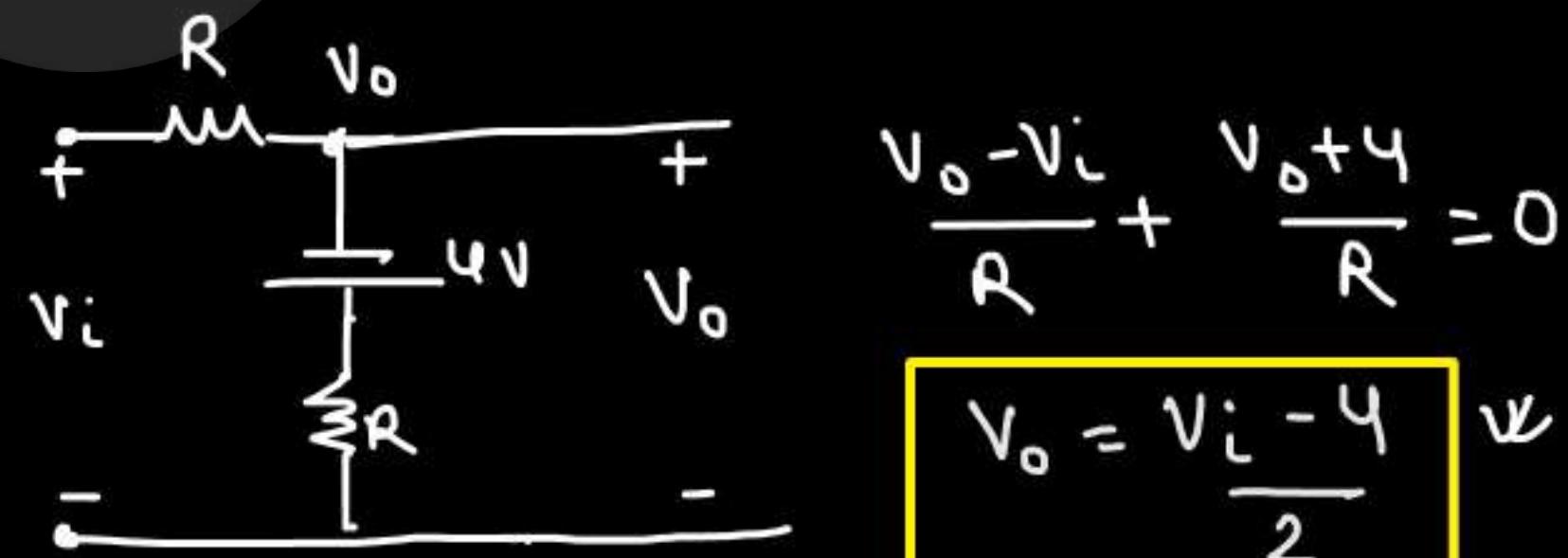(iii) $V_i \leq -4V$
 \Rightarrow diode D_1 ON
 diode D_2 OFF



LECTURE-1

 Watch on  YouTube


AIR 27 (ECE)

AIR 45 (IN)

$$(i) V_{in} \geq 4V \Rightarrow V_o = 4V$$

$$(ii) V_{in} \leq -4V \Rightarrow V_o = \frac{V_i - 4}{2}$$
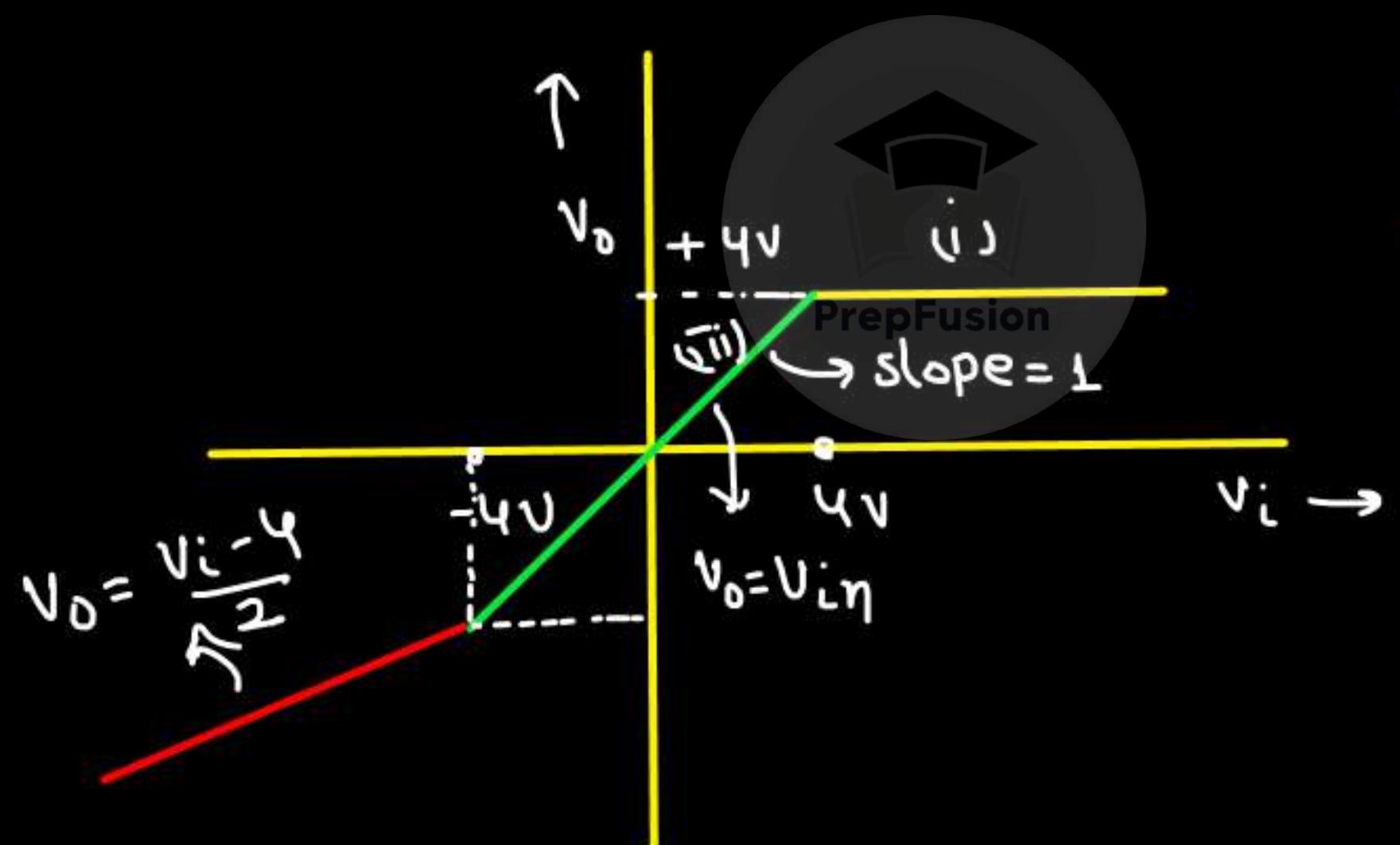
$$(iii) -4V < V_{in} < 4 \Rightarrow V_o = V_{in}$$




$$\max = 4V$$

$$\begin{aligned} \min &= \left(V_i\right)_{\min} - 4 \\ &= \frac{-10 - 4}{2} \\ &= -7V \end{aligned}$$

$$\min = -7V$$

Assignment - 2

Q.

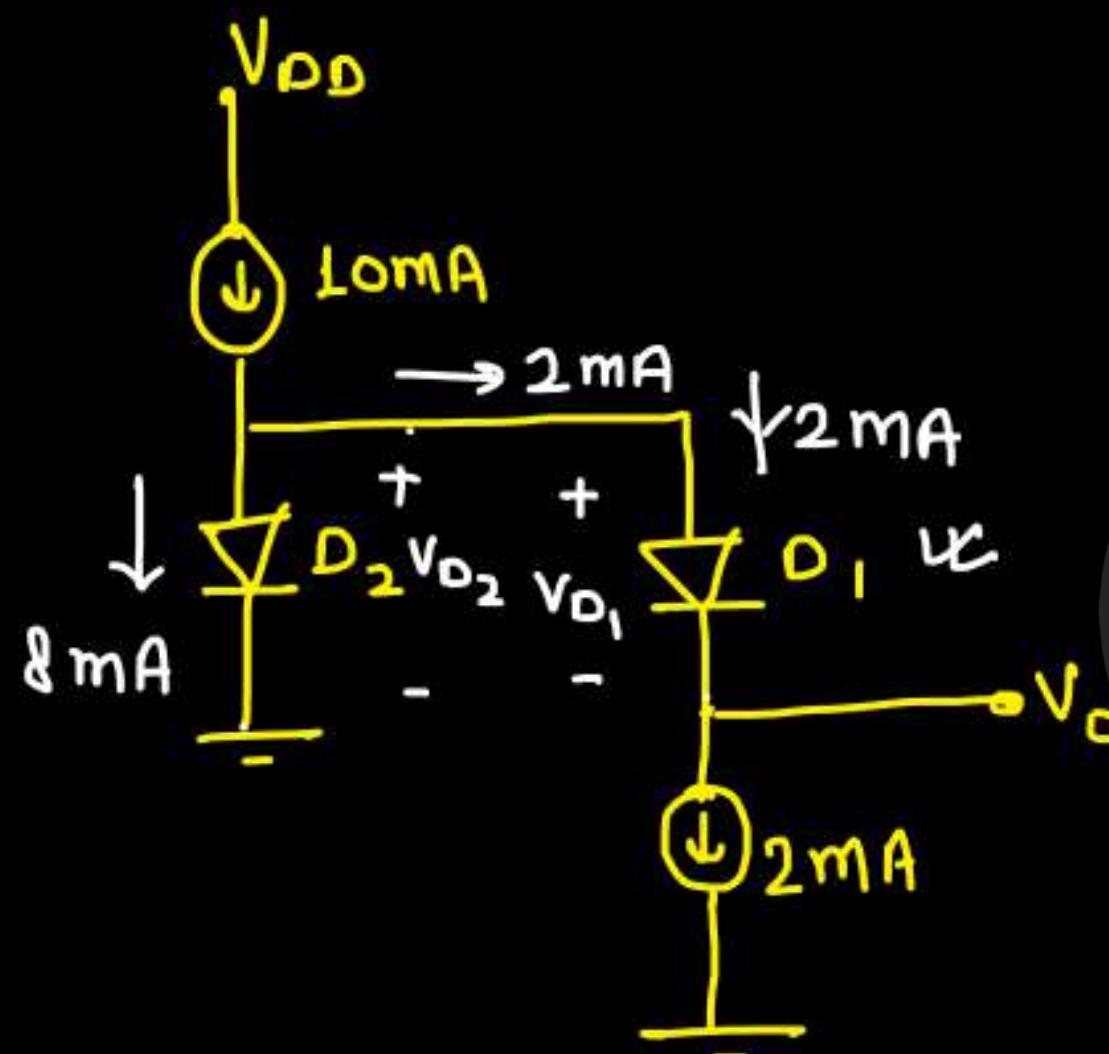

D₁ has 10 times the Jⁿ area of D₂.

find V_O.



$$I_S \propto J^n \propto \text{Area} (A)$$

$$A_{D_1} = 10 A_{D_2}$$

$$I_{S_1} = 10 I_{S_2} =$$

$$I_{D_1} = 2 \text{ mA} > I_{S_1} e^{V_{D_1}/V_T} \rightarrow \textcircled{1}$$

$$I_{D_2} = 8 \text{ mA} = I_{S_2} e^{V_{D_2}/V_T} \rightarrow \textcircled{2}$$

$$0 + V_{D_2} - V_{D_1} = V_O$$

$$V_O = V_{D_2} - V_{D_1}$$

$$\textcircled{2} \div \textcircled{1}$$


$$q = \frac{I_{S_2}}{I_{S_1}} e^{(V_{D_2} - V_{D_1})/V_T}$$

$$q = \frac{I}{I_0} e^{V_0/V_T}$$




$$V_0 = V_T \ln(40)$$

$$V_0 = 26 \ln(40) \text{ mV}$$

$$V_0 \approx 96 \text{ mV}$$

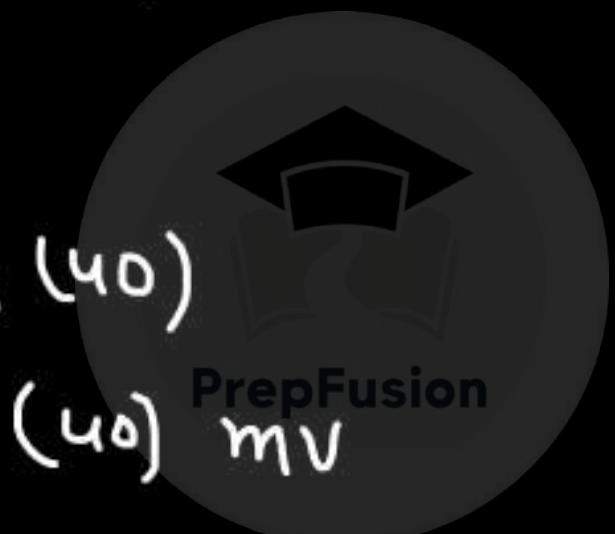


Q. $V_Z = 6V$, draw V_o .

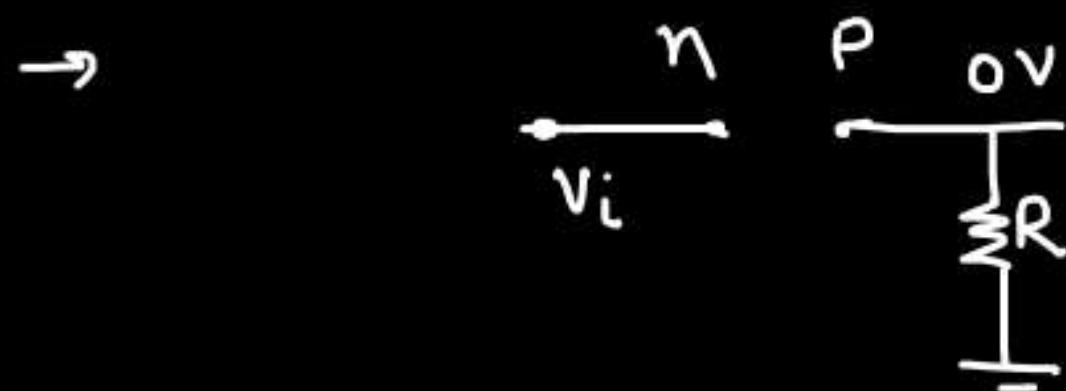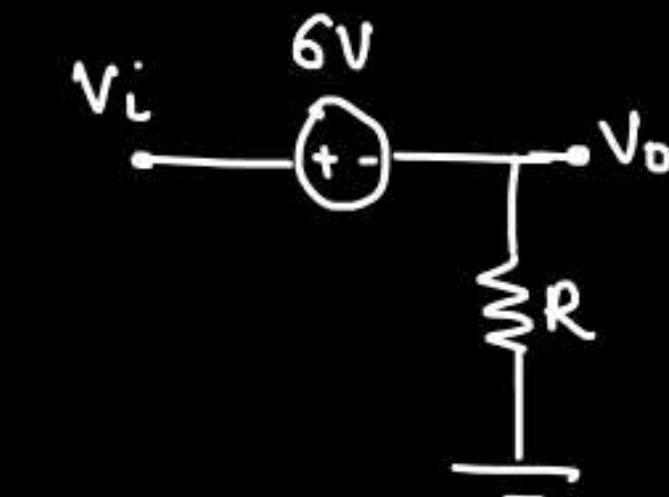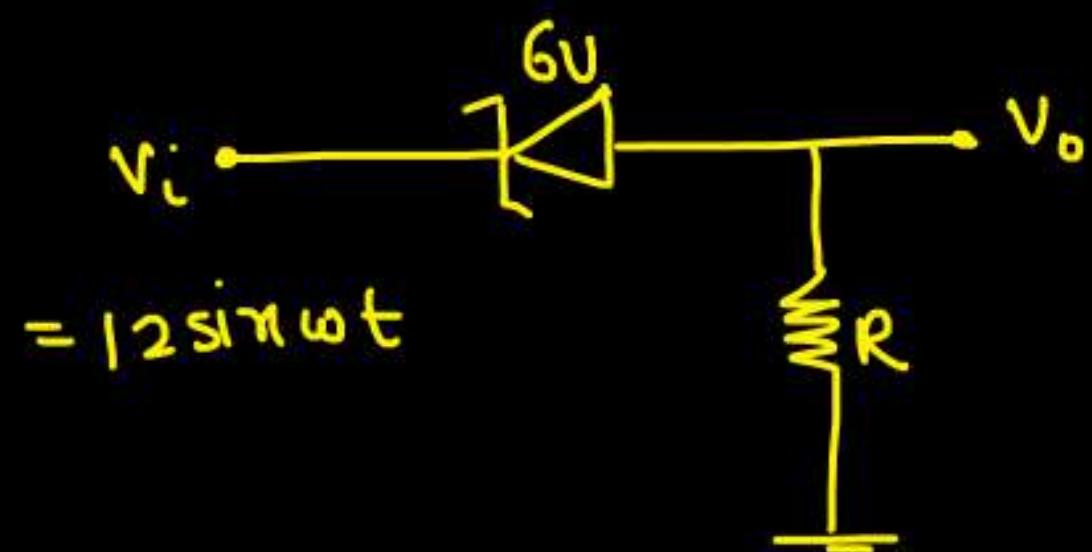


$V_i < 0 \Rightarrow$ diode ON \Rightarrow S.C. $\Rightarrow V_o = V_i$

$6V > V_i > 0 \Rightarrow$ diode R.B. and not in B.D. \Rightarrow diode O.C. $\Rightarrow V_o = 0$

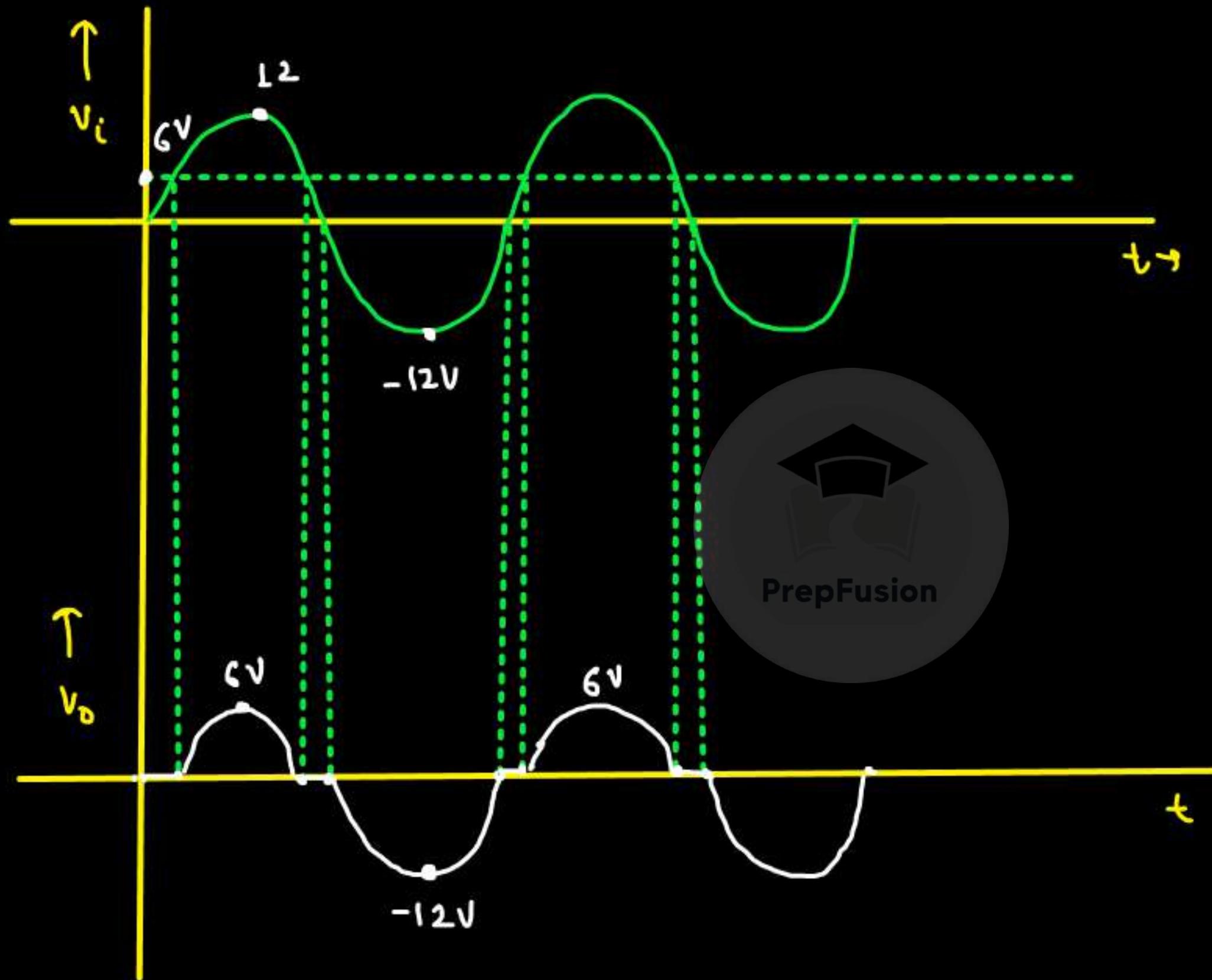
$V_i > 6V \Rightarrow$ diode goes into B.D. $\Rightarrow V_o = V_i - 6$





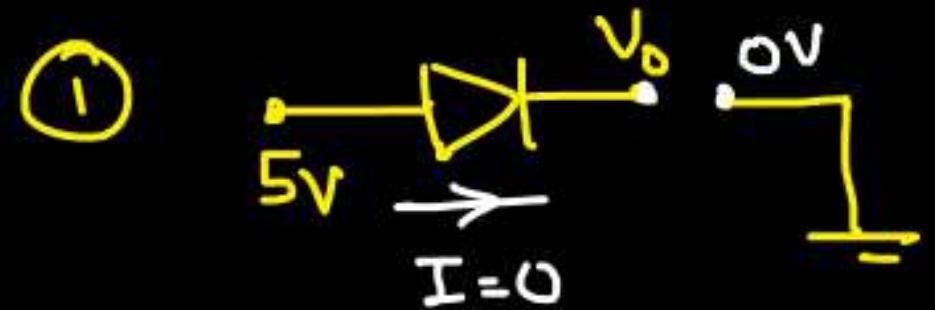
Q Tell whether the diode is ON, OFF or Breakdown. Find V_o .




diode off

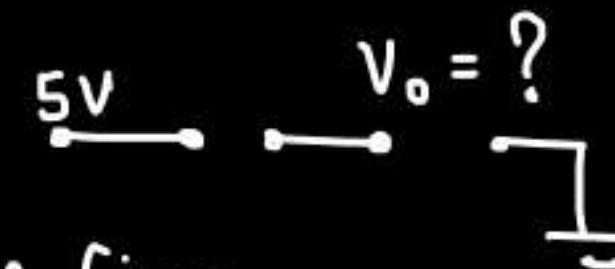


$V_o = \text{Can't define}$

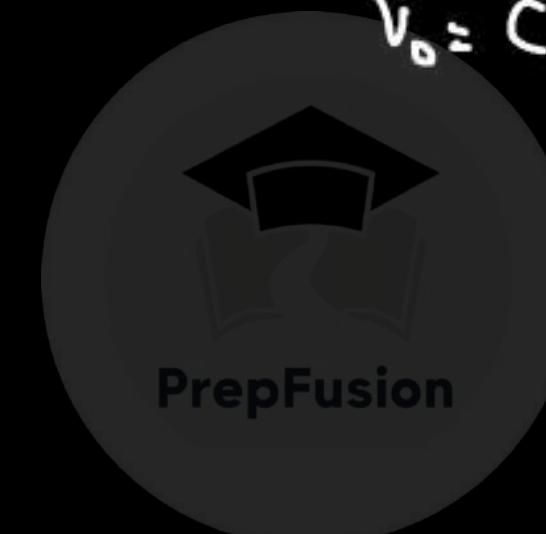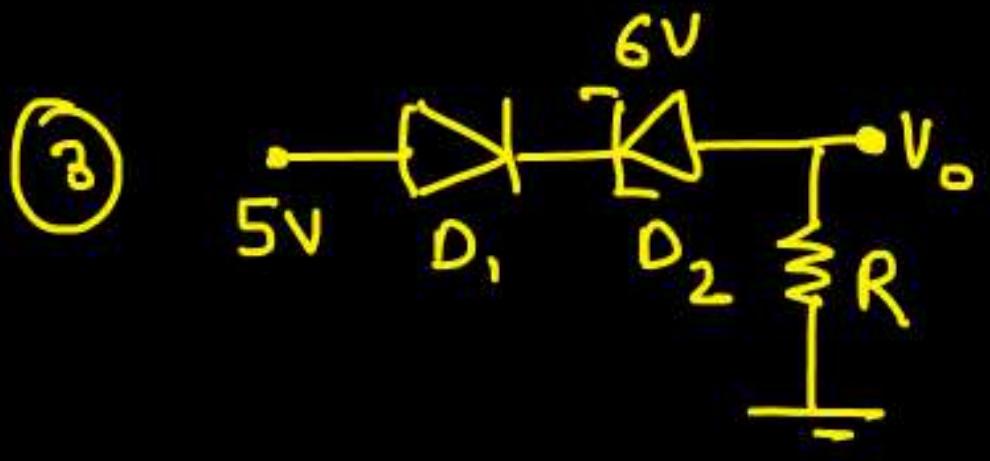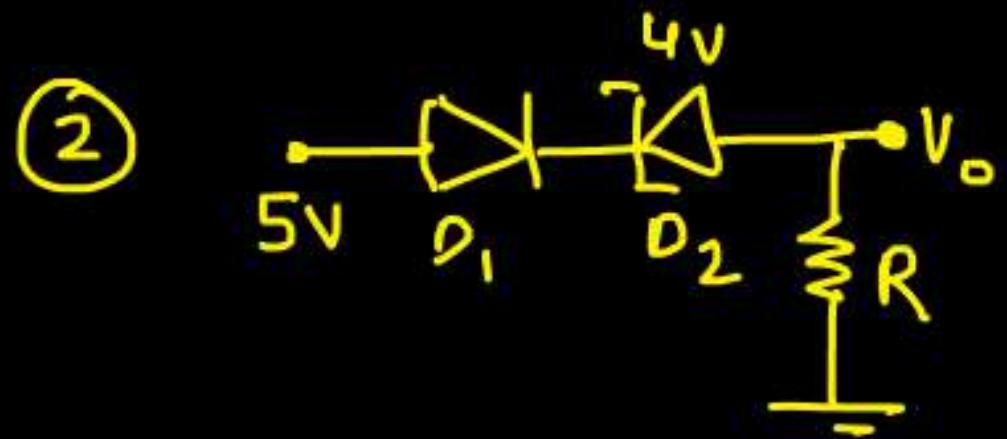


PrepFusion

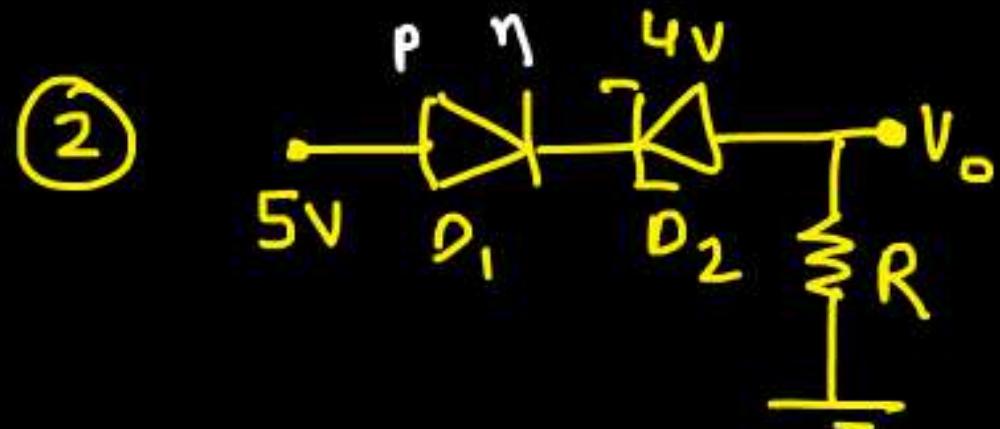

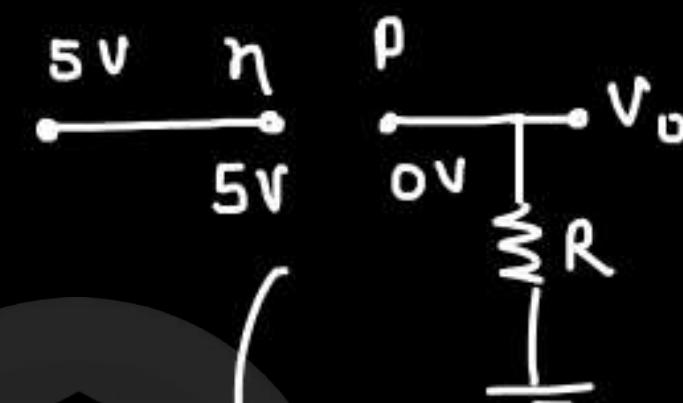
Assume D_1 is ON
and apply O.C. Test on D_2




R.B. \Rightarrow B.D.
↓
PrepFusion

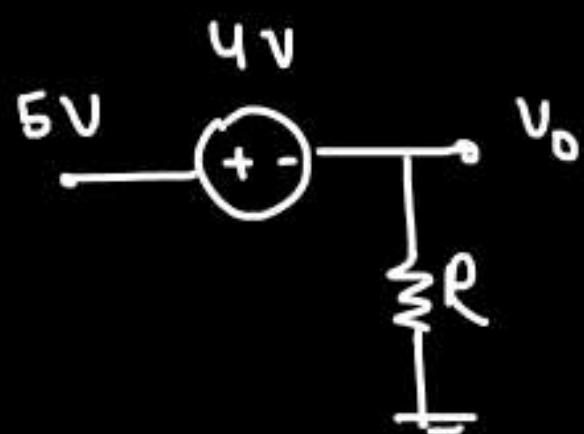


$$V_0 = 1V$$

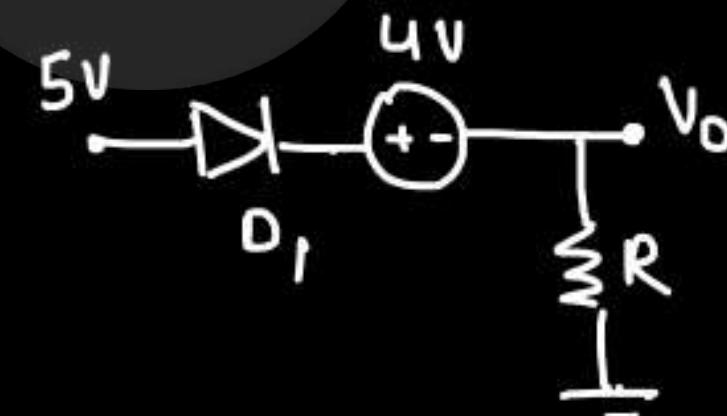

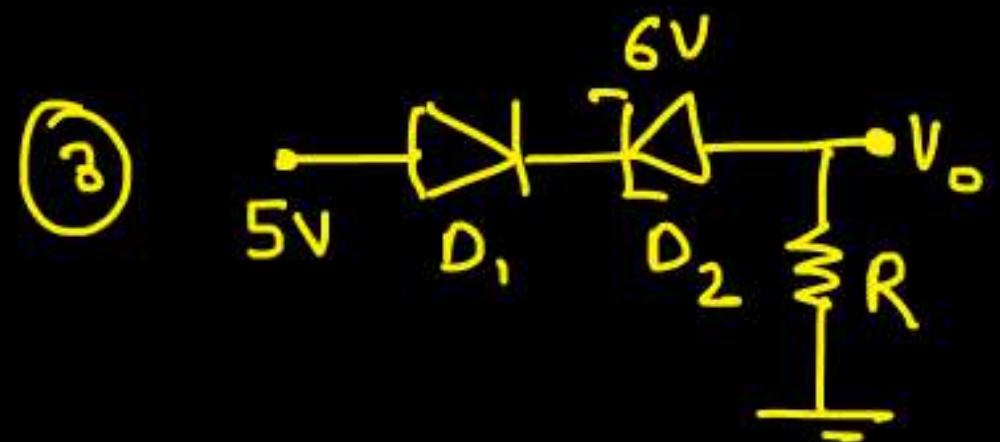By applying S.C./O.C.
Test on D_1 , I can
see that diode D_1
is ON \Rightarrow Assumption
was correct.




Assume D_1 is ON.

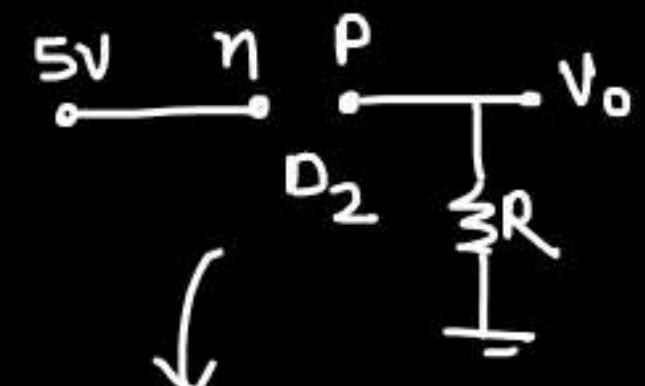

D_2 is R.B. and not in B.D.

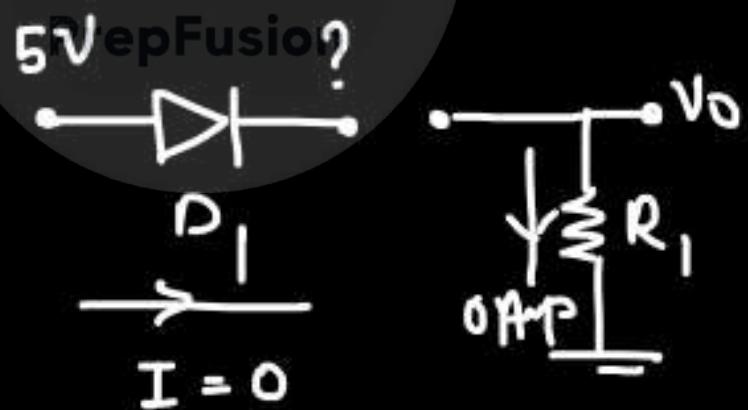
diode $D_2 \rightarrow$ OFF $\Rightarrow D_2$ O.C.




D_1 will also be OFF.

$$V_o = 0V$$


Revision Question :-

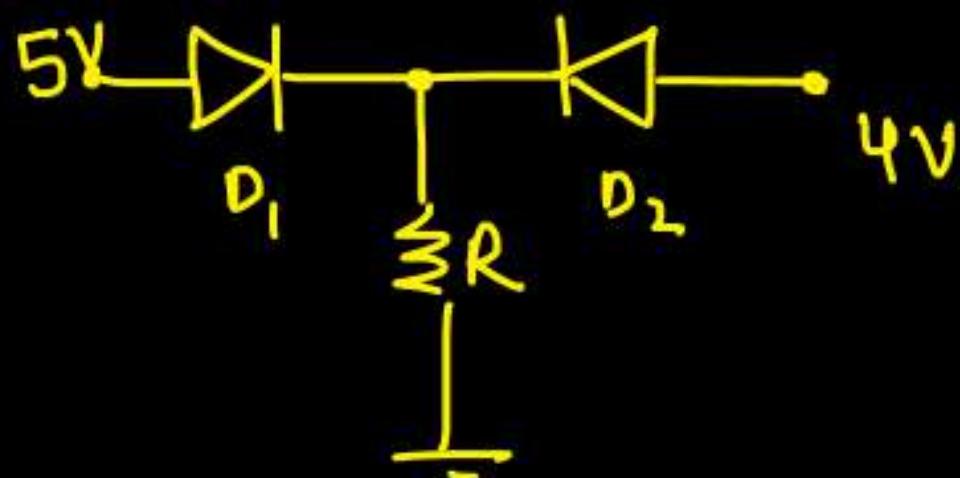

op^r cond'n of D₁ & D₂?

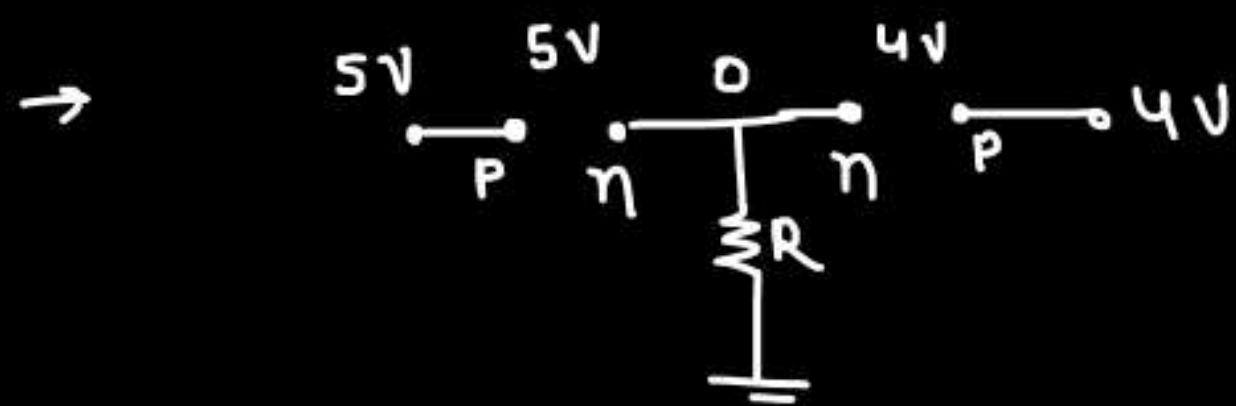


D₁ will be turned on initially.

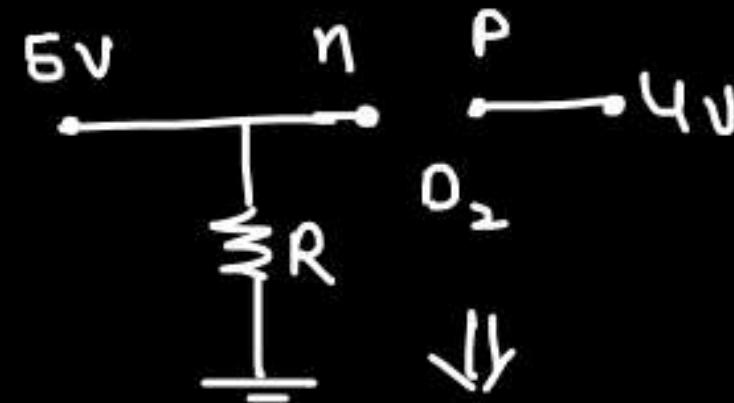

D₂ will be off


Q.

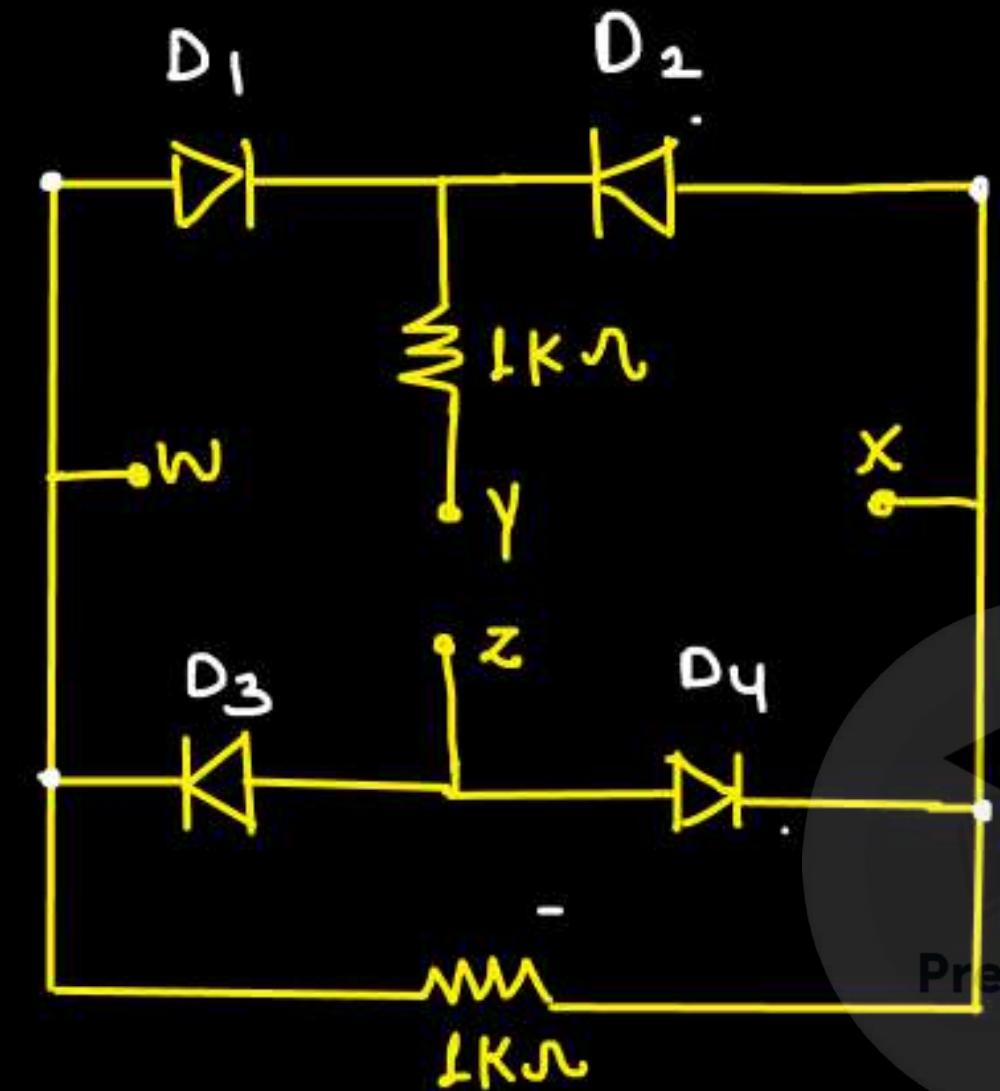

$$V_{yz} = 1000 \sin \omega t$$

Find V_{wx} = ?

PrepFusion

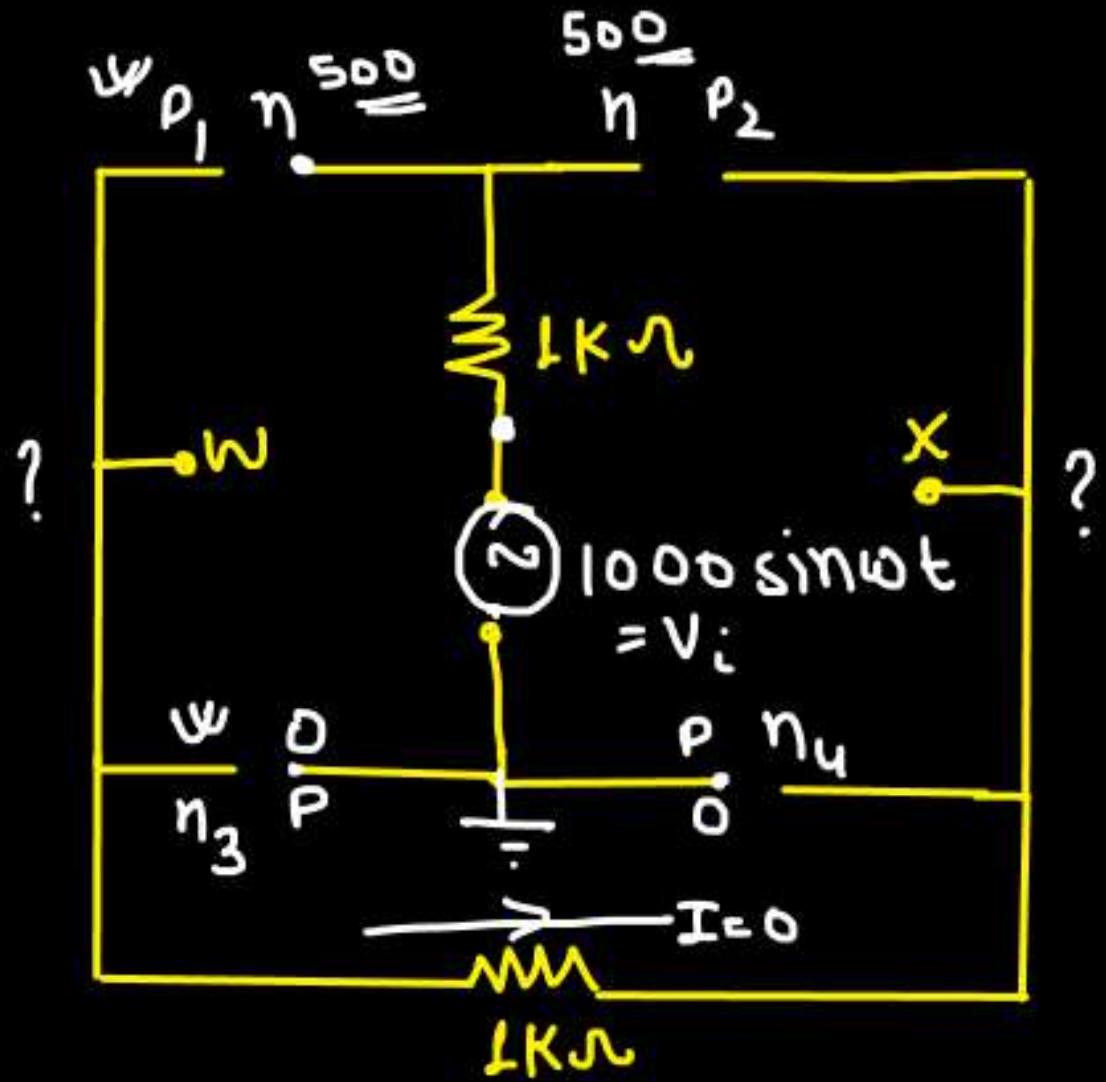

for $V_i \geq 0$

$$V_{n_3} = V_{n_4} = V_{P_1} = V_{P_2}$$

⇒ By cut analysis,

D_1, D_2, D_3, D_4 all are off

$$V_w = V_{n_3} = V_{P_1}$$

PrepFusion

$$V_x = V_{n_4} = V_{P_2}$$

if all diode are off ,

$$\text{then } V_{n_3} = V_{P_1} = V_{n_4} = V_{P_2}$$

$$\Rightarrow V_w = V_x$$




$$\Rightarrow V_{wx} < 0V$$

X wrong

$$V_w = 0V$$

$$V_x = 0V$$

12

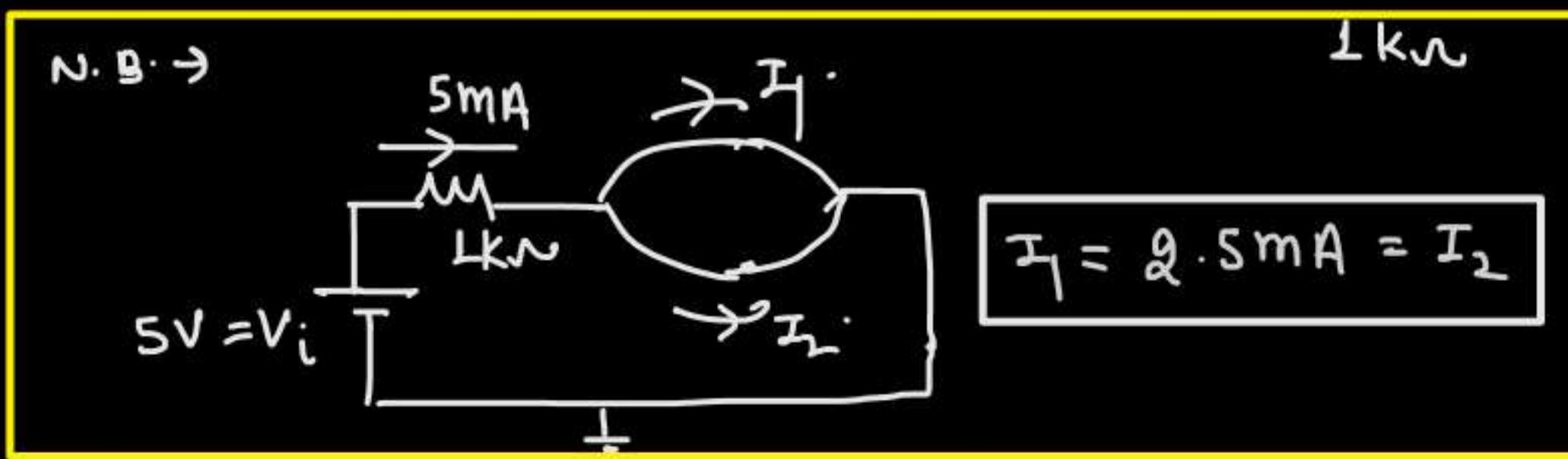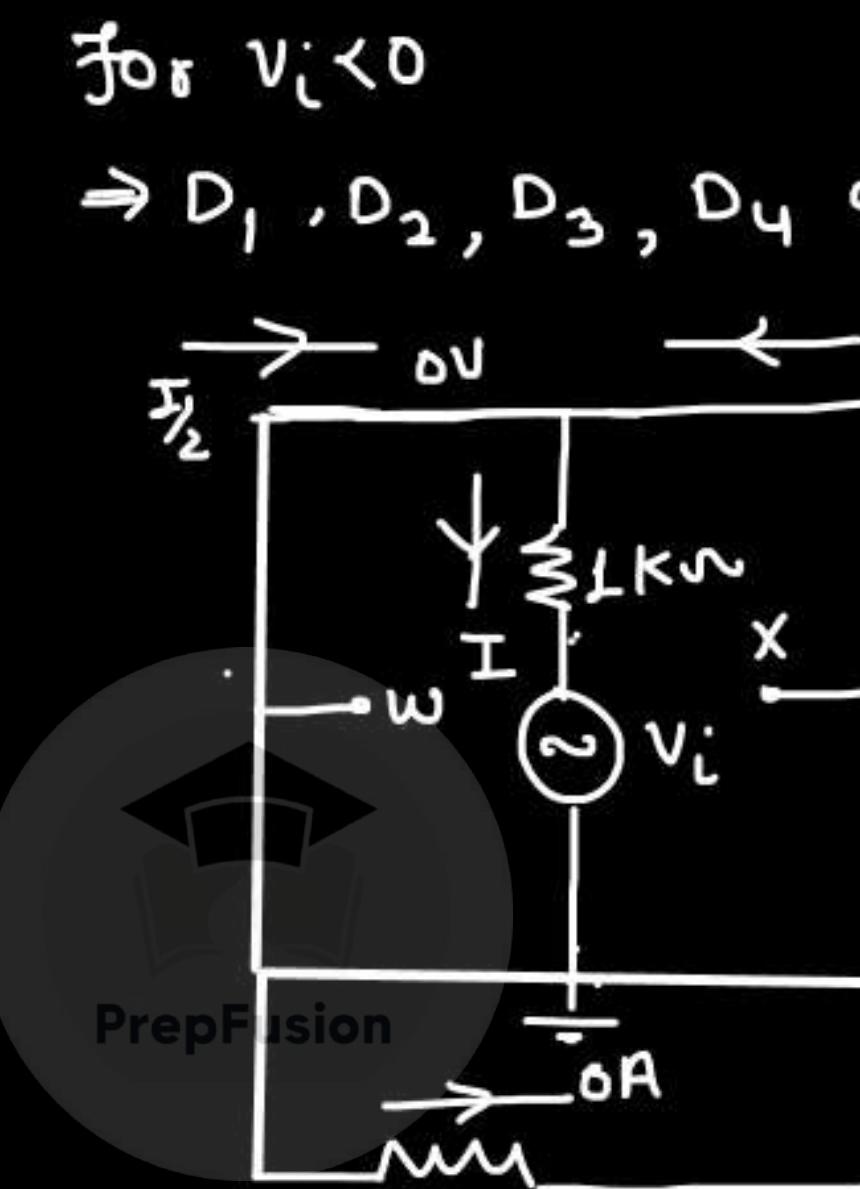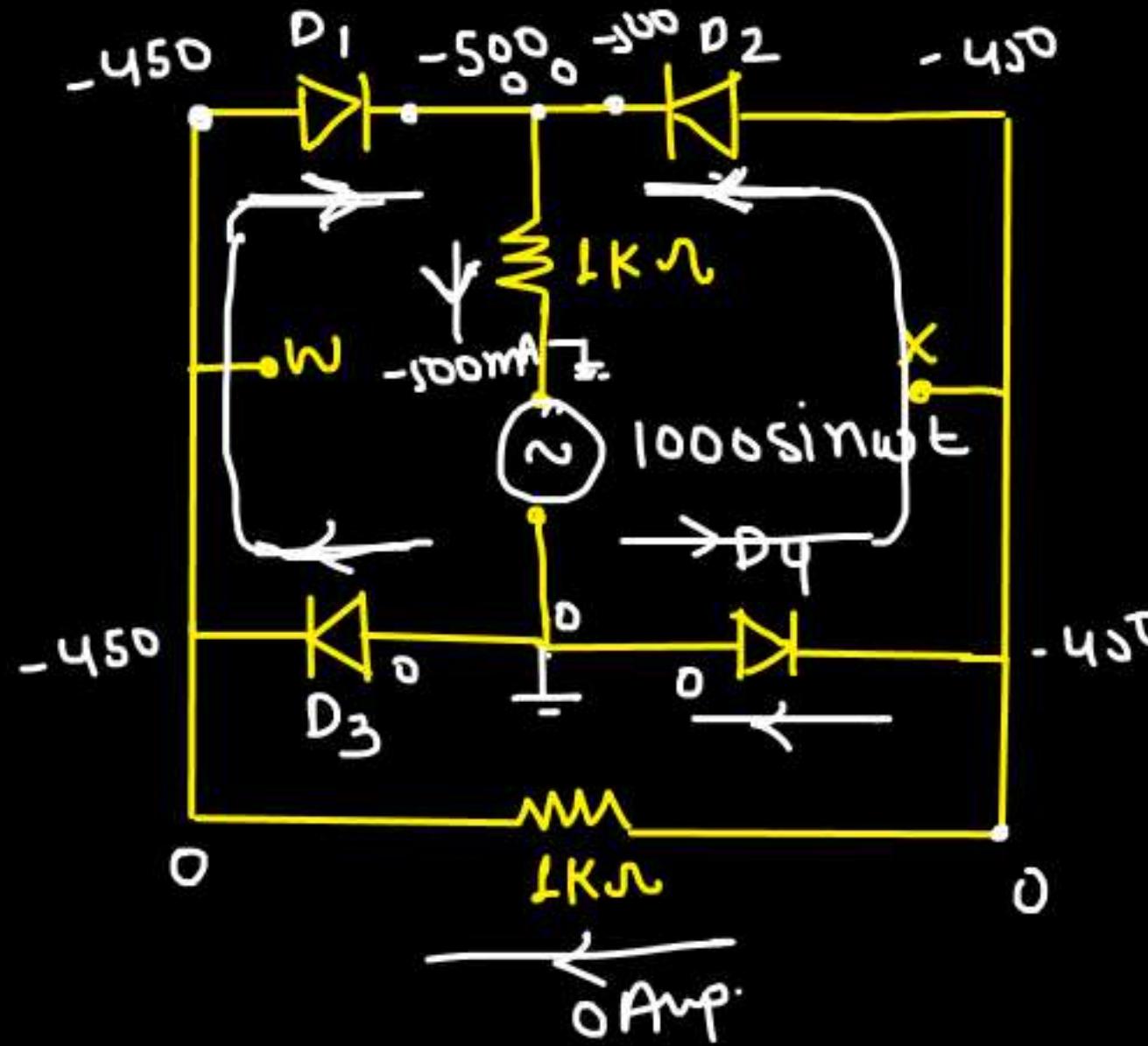


Q. For Zener, $V_Z = 6.8V$

For all the diodes $V_D = 0.7V$

$$V_i = 10 \sin 100\pi t$$


Find max and min values of o/p voltage.

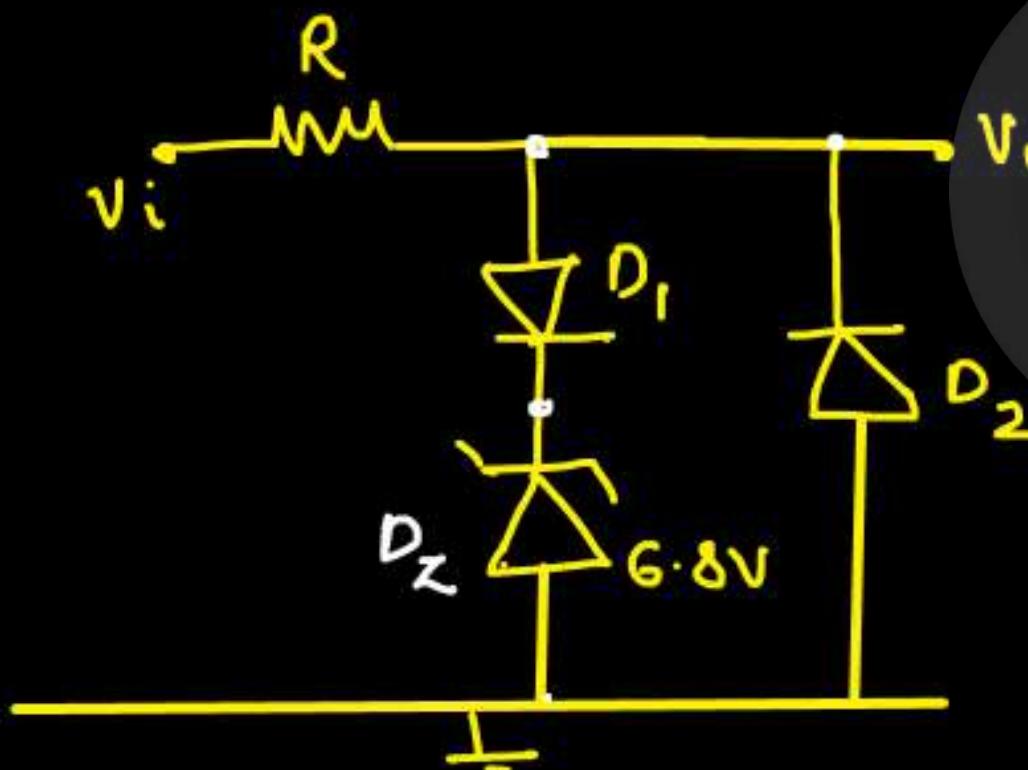

When $V_i > 0$ & $V_i < 7.5V$
⇒ diode D_2 , D_1 and D_Z are off

$$V_o = V_i$$

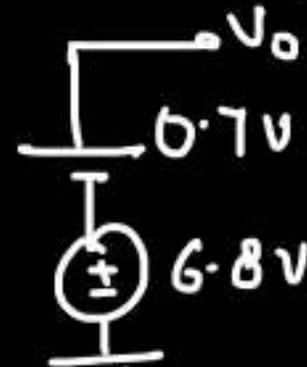↳ $V_i > 7.5V \Rightarrow D_Z$ and D_1 turns on



$$V_o = 7.5V \rightarrow \underline{\text{max}}$$



For $V_i < 0$ & $V_i > -0.7V$


D_1 , D_2 and D_3 are off

$$V_o = V_L$$


When $V_i < -0.7V$

diode D_2 turns on

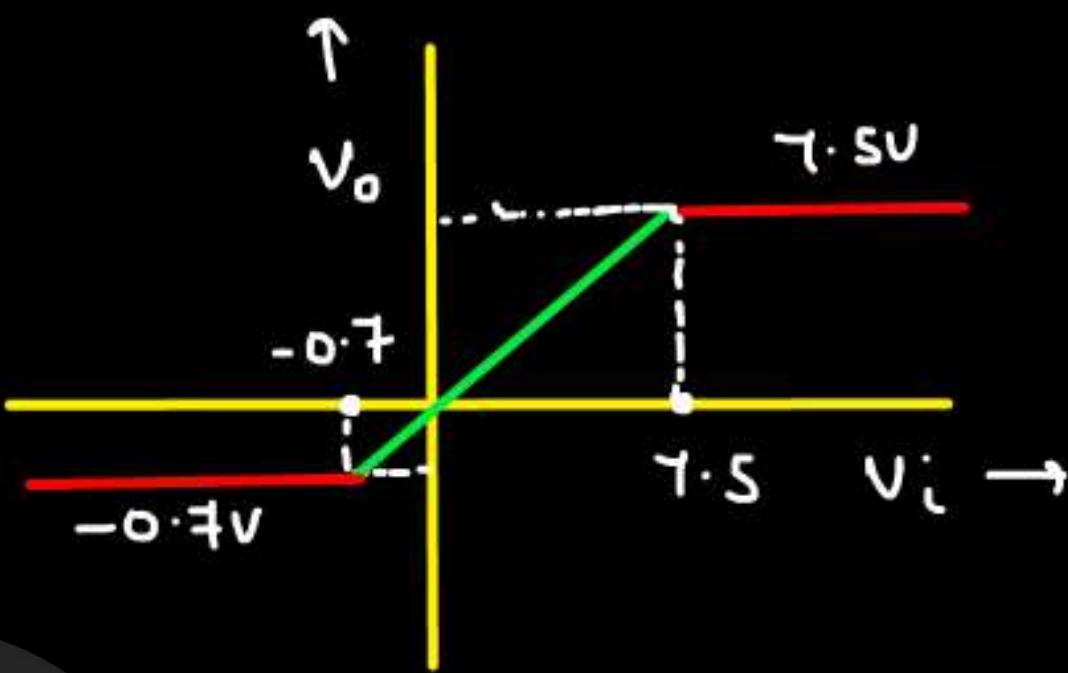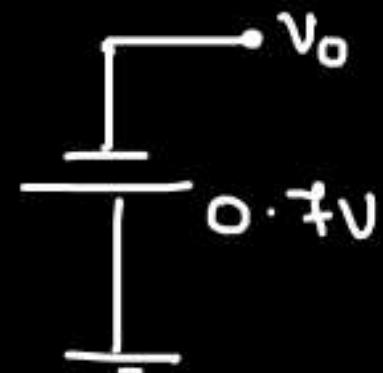


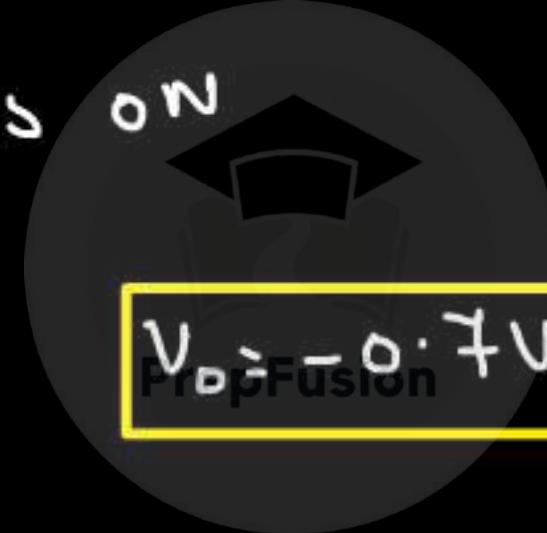
$$V_o \geq -0.7V \rightarrow \text{min}$$

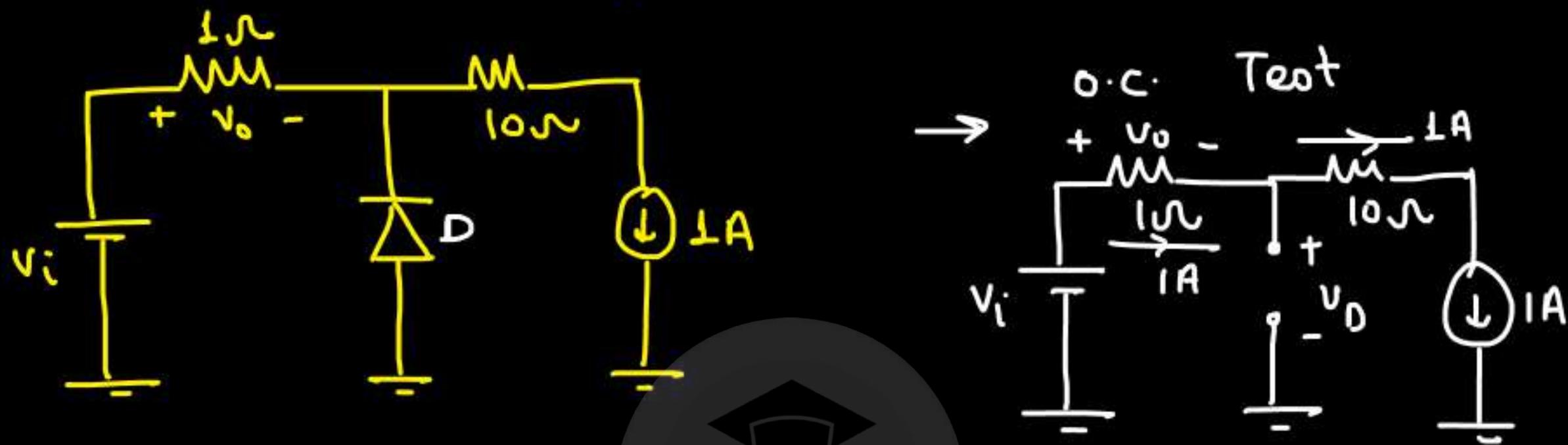Q. In the circuit the voltage V_D is given by -



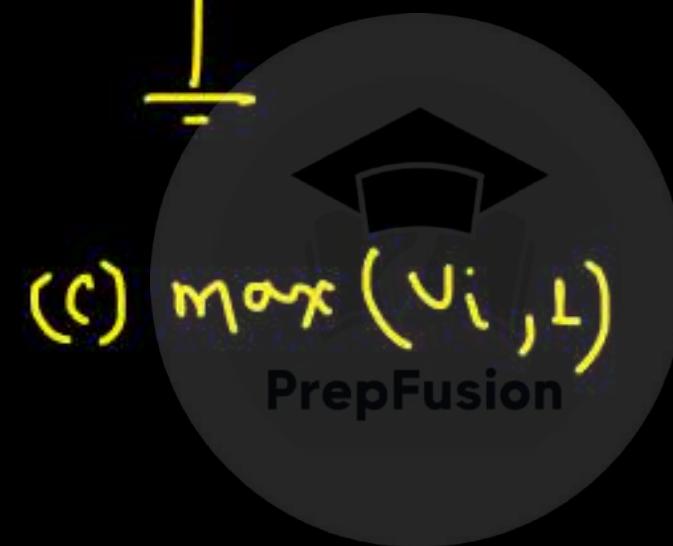- (a) $\min(V_i, 1)$
- (b) $\min(-V_i, 1)$



(c) $\max(V_i, 1)$

PrepFusion

$$(V_D)_{O.C.} = V_i - 1$$

↳ if $V_i < 1V \Rightarrow (V_D)_{O.C.} = -Ve$

∴

$$V_D = V_i$$

↳ diode ON

↳ if $V_i < 1V \Rightarrow V_D = V_i$

if $V_i > 1V \Rightarrow (V_D)_{0..C} = +ve$

↓
diode Turns off

$$V_o = 1 \times 1A = 1V$$

↳ $V_i > 1V \Rightarrow V_o = 1V$

$V_i < 1V \Rightarrow V_o = V_i$

option L: $V_o = \min(V_i, 1)$

but $V_i = 0.5V \Rightarrow V_o = 0.5V$

$\rightarrow V_o = \min(0.5, 1) = 0.5V$

but $V_i = 2V \Rightarrow V_o = 1V$



$\rightarrow V_o = \min(2, 1) = 1V$

PrepFusion

$$V_o = \min(V_i, 1)$$

W

Q. Draw VTC.

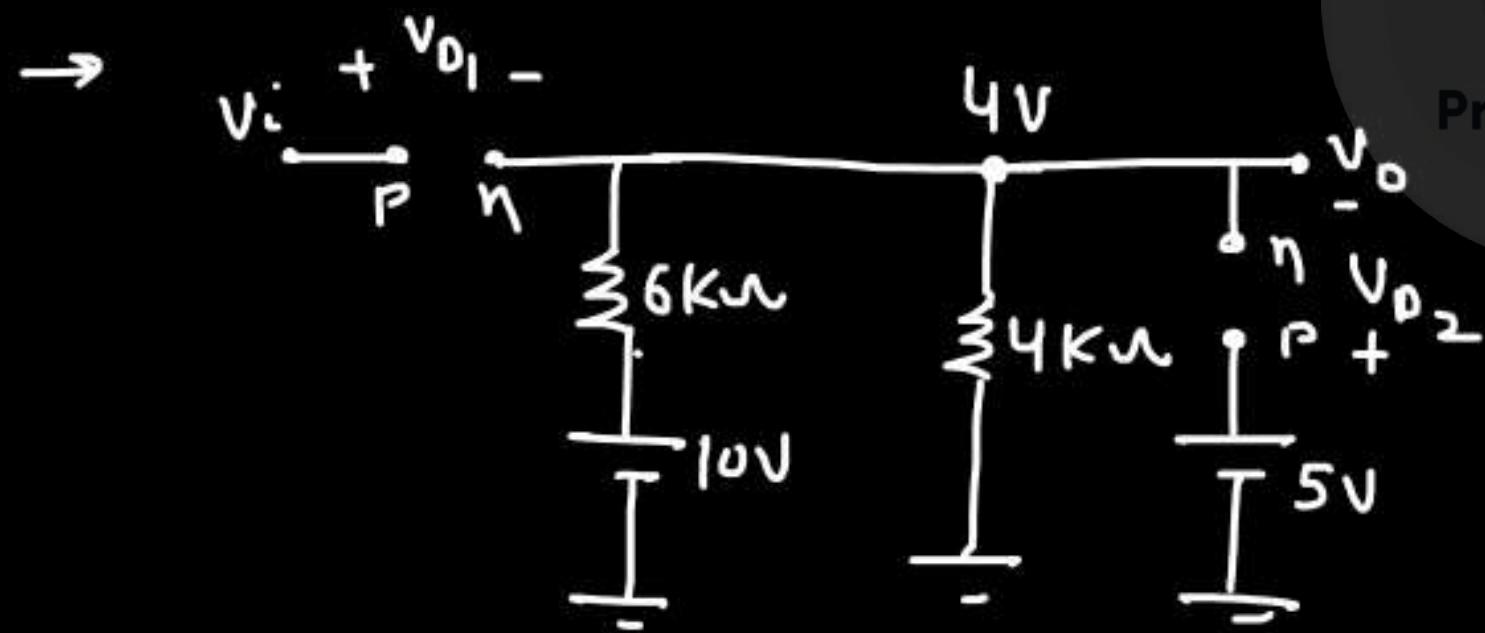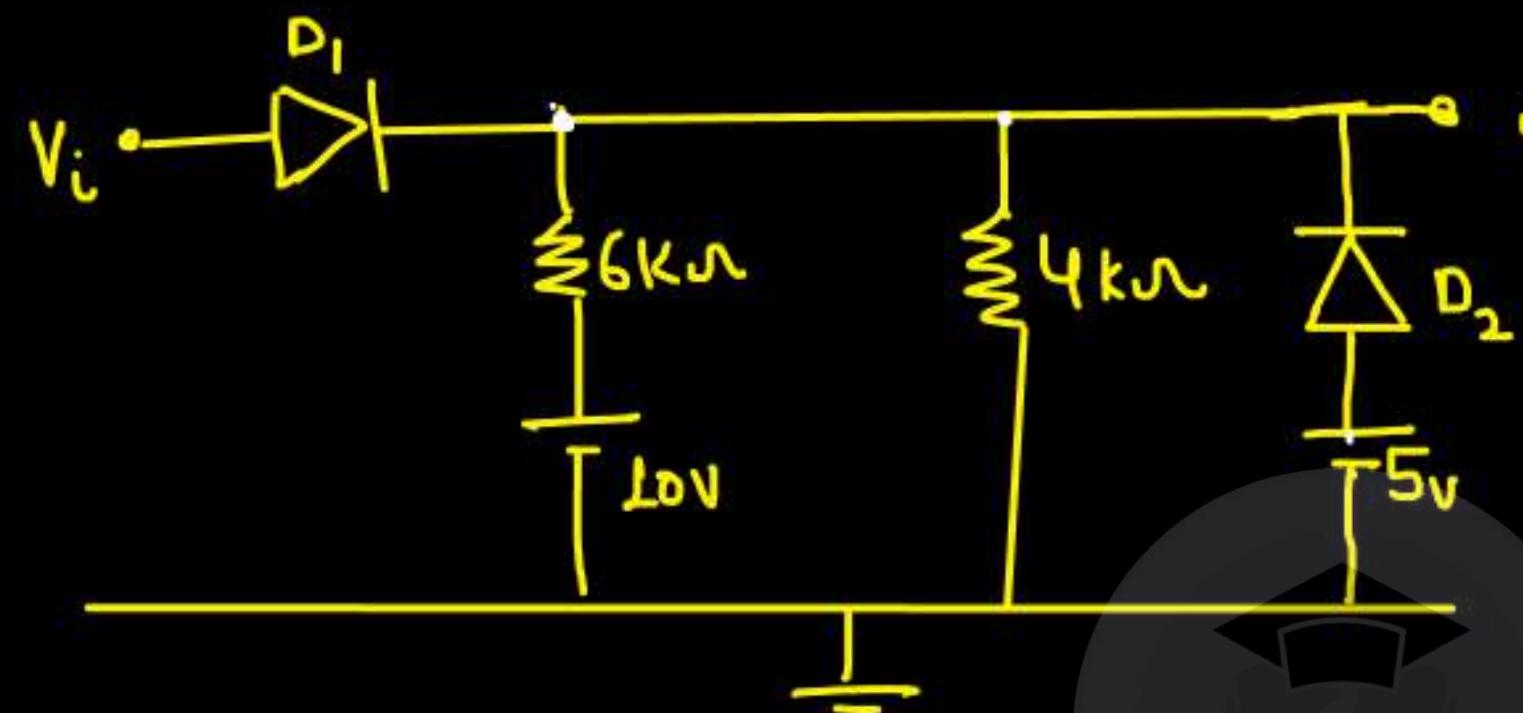


$$V_{D1} = V_L - 4$$

$$V_{D2} = 1V$$

if $V_i < 4V \Rightarrow$ diode D_1 off
diode D_2 = ON

$$V_o = 5V$$

(ii) $4V < V_i < 5V$

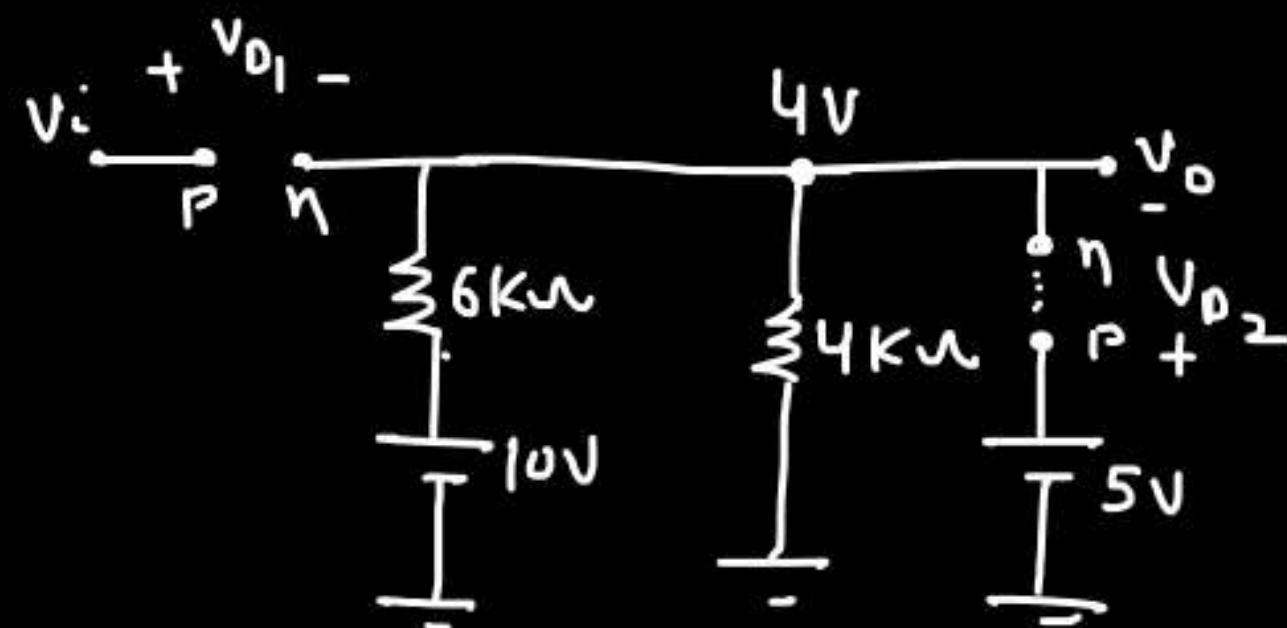

$$V_{D_2} = 1V$$

$$V_{D_1} = V_i - 4$$

$$\left. \begin{array}{l} \text{if } 4 < V_i < 5 \Rightarrow V_{D_1} < 1V \end{array} \right\}$$



D_2 will turn on first and then we will decide the cond'n of D_1

PreFusion




\hookrightarrow diode D_1 goes off

$$V_o = 5V$$

$$\Rightarrow V_i < 5V \Rightarrow V_o = 5V$$

(iii) $V_i > 5V$

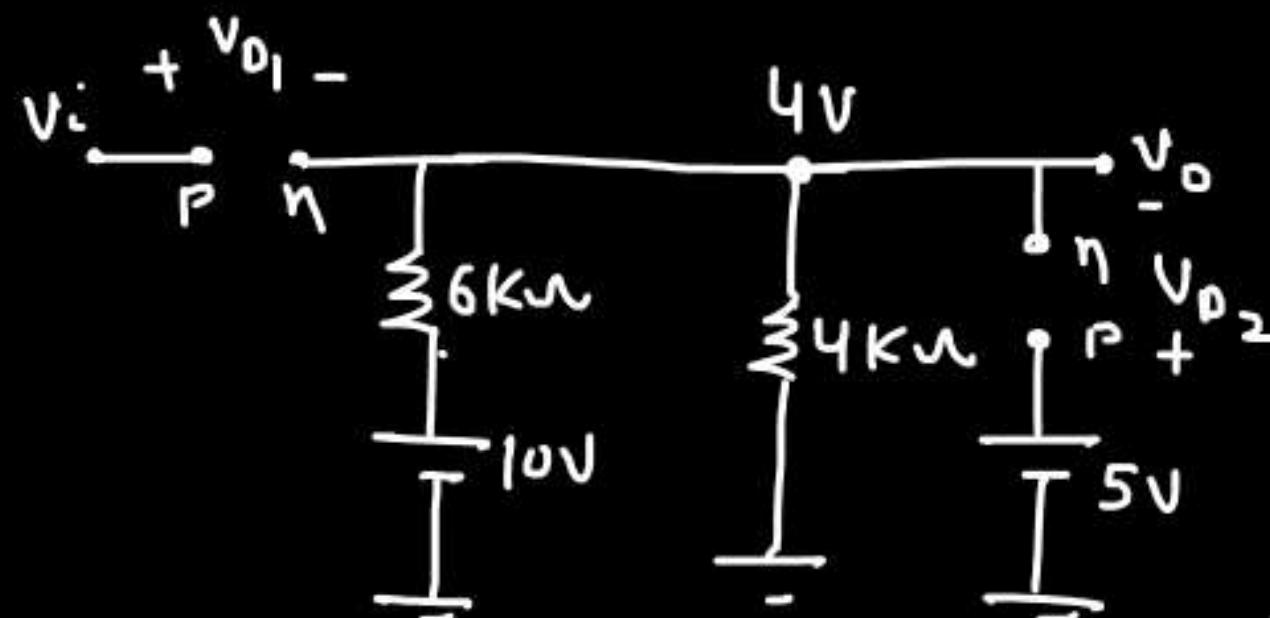

$$V_{D_1} = V_i - 4$$



$$V_{D_2} = 1V$$

$$V_{D_1} > LV \quad \{ V_i > 5V \}$$

$$\Rightarrow V_{D_1} > V_{D_2}$$

⇒ first D_1 will turn ON and then
we will decide the cond'n of D_2

PrepFusion

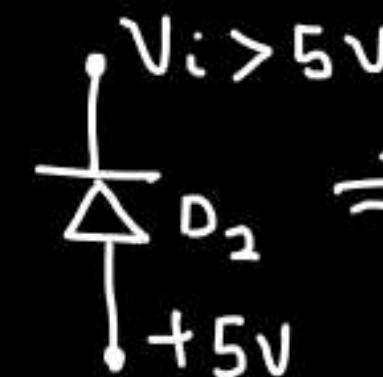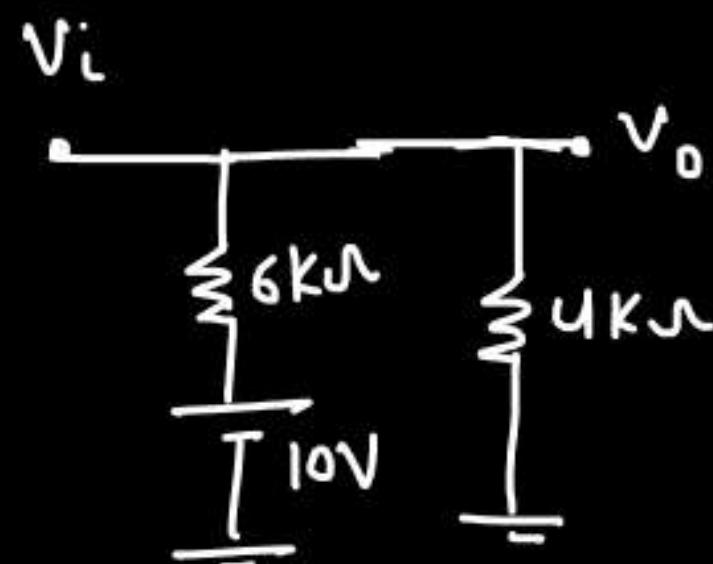


⇒ diode D_2 off


$$V_D = V_i$$

$$V_i < 5V \Rightarrow V_o = 5V$$

$$V_i > 5V \Rightarrow V_o = V_i$$

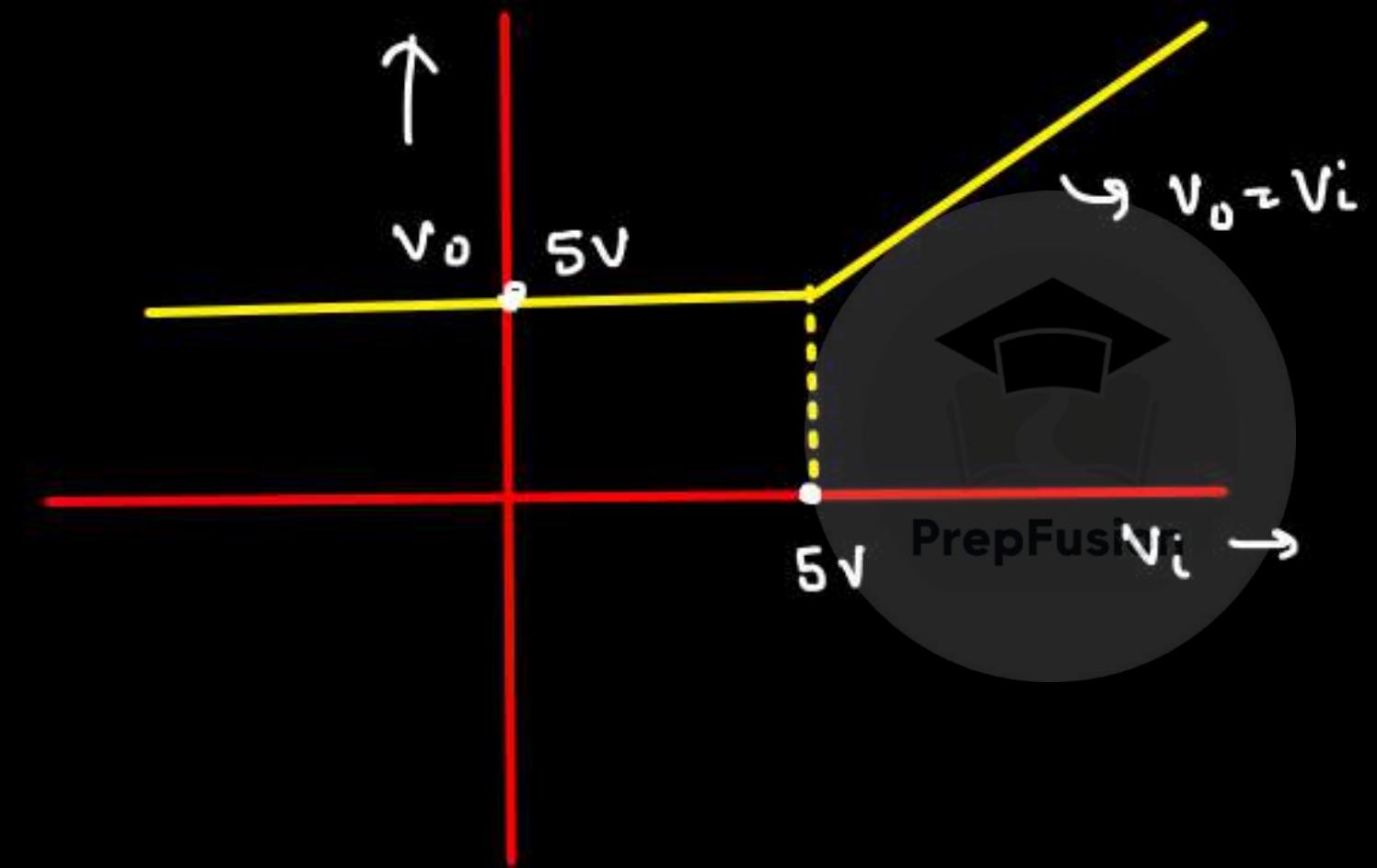


Q.

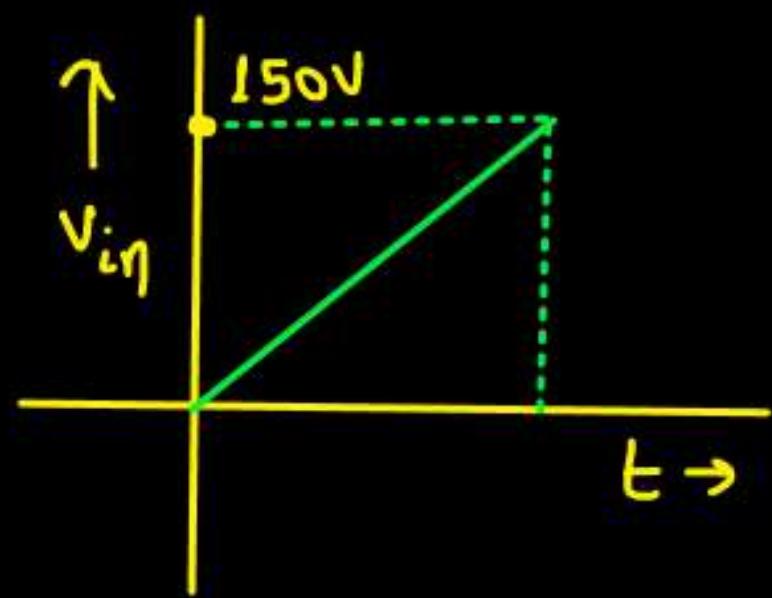

Draw VTC.

→ O.C. Test

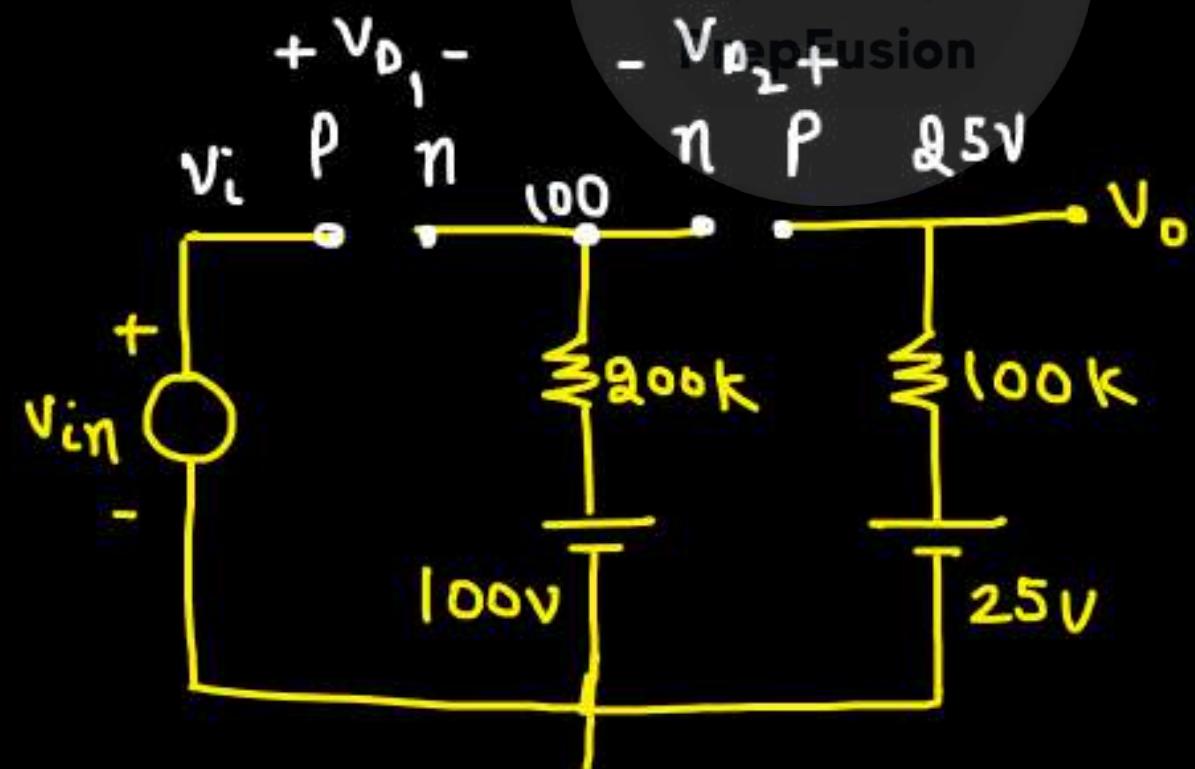

$$V_{D_1} = V_L - 100$$

$$V_{D_1} = V_i - 100$$


$$V_{D_2} = -15V$$

$\Rightarrow \mathfrak{L}_2$ is off

D₁ is off

$$V_D = 25V$$


(ii) $V_i > 100V$

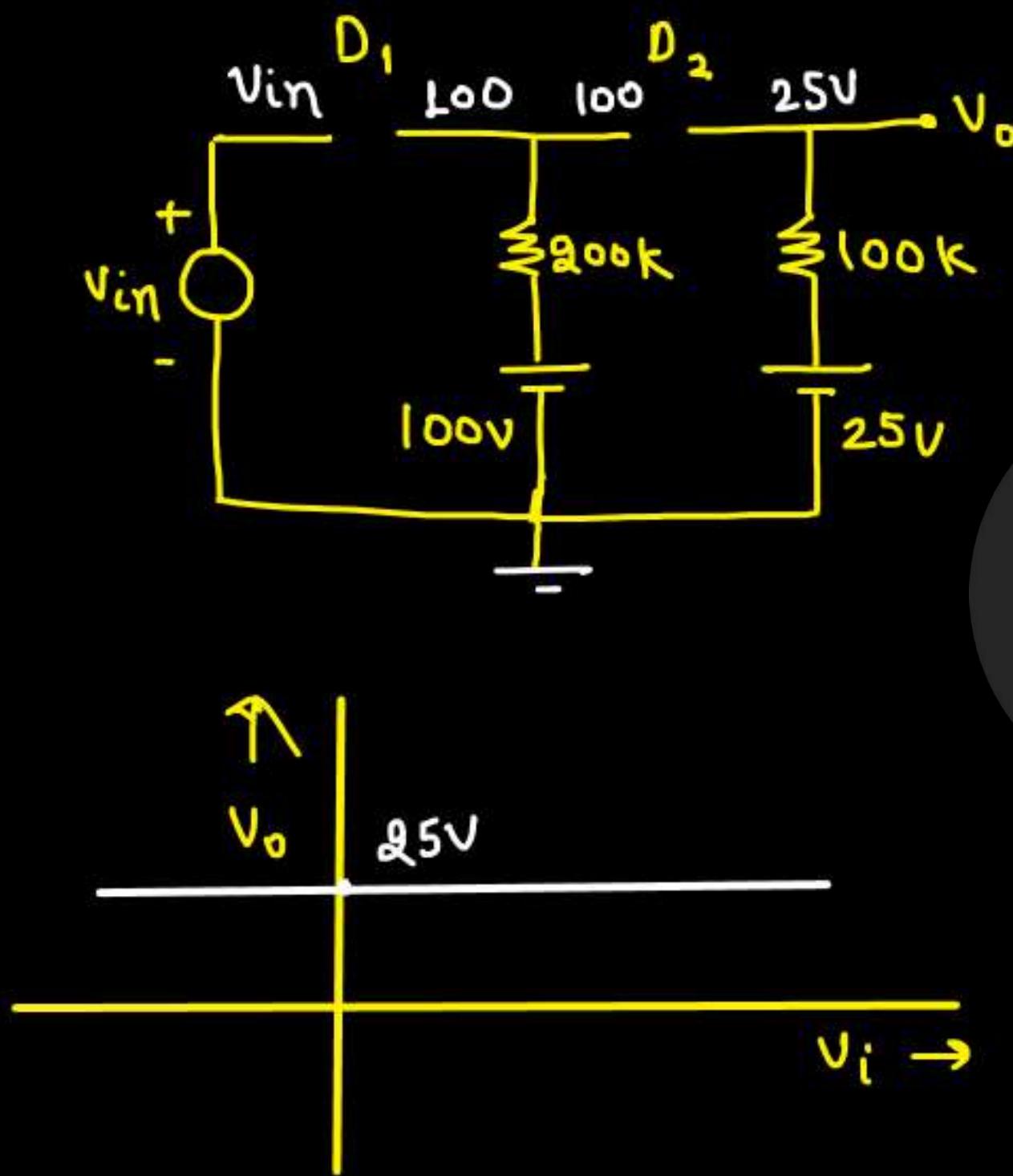

$V_{D_2} = -15V \rightarrow D_2 \text{ off}$



$$V_{D_1} = V_{in} - 100$$

\downarrow
 $D_1 \text{ on} =$

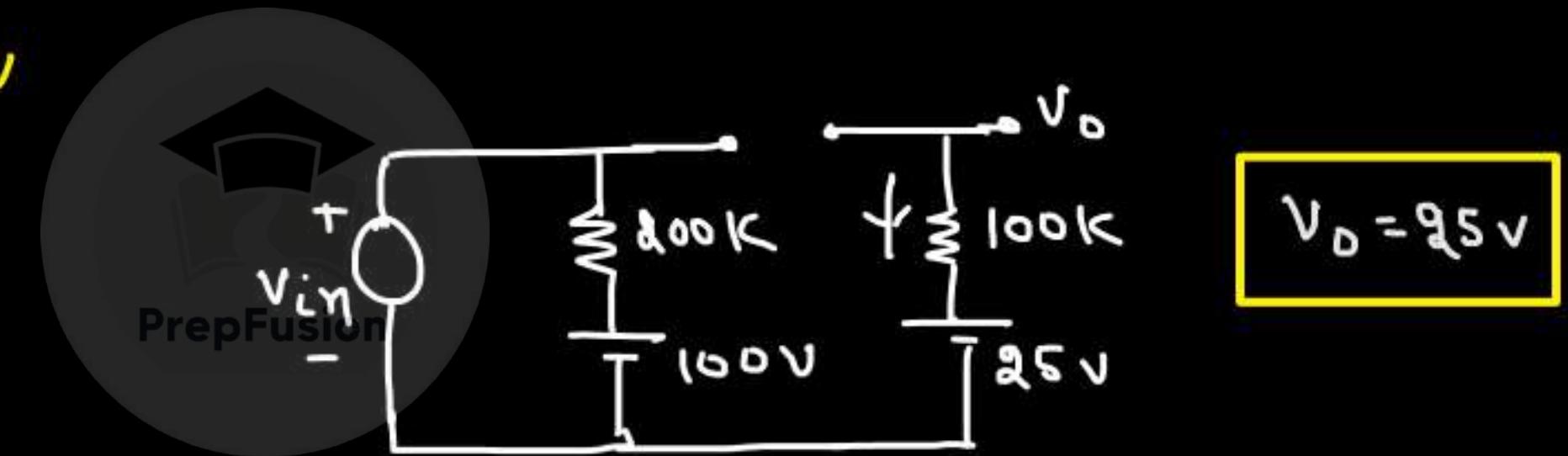


$$V_o = 25V$$

Q.

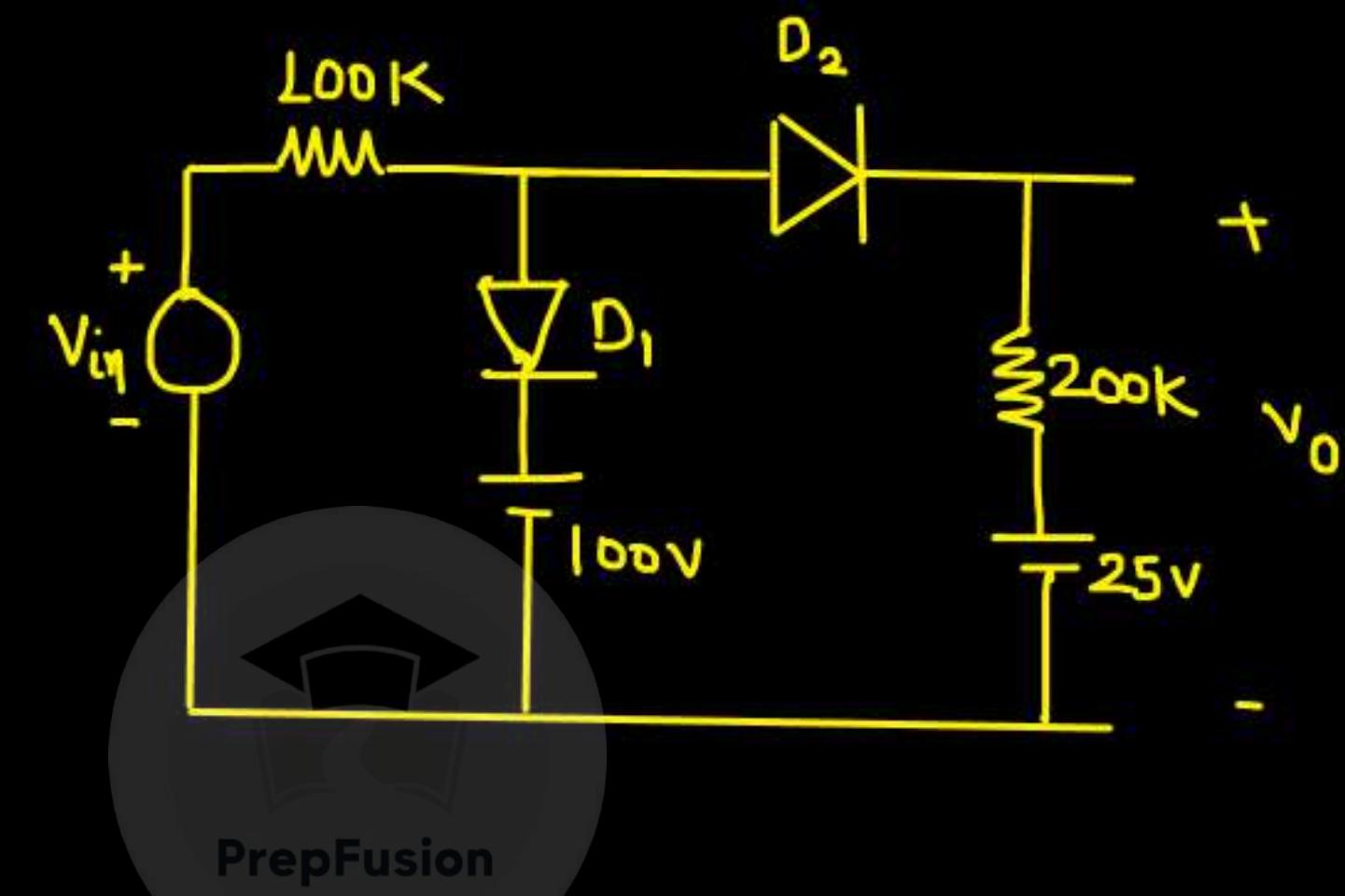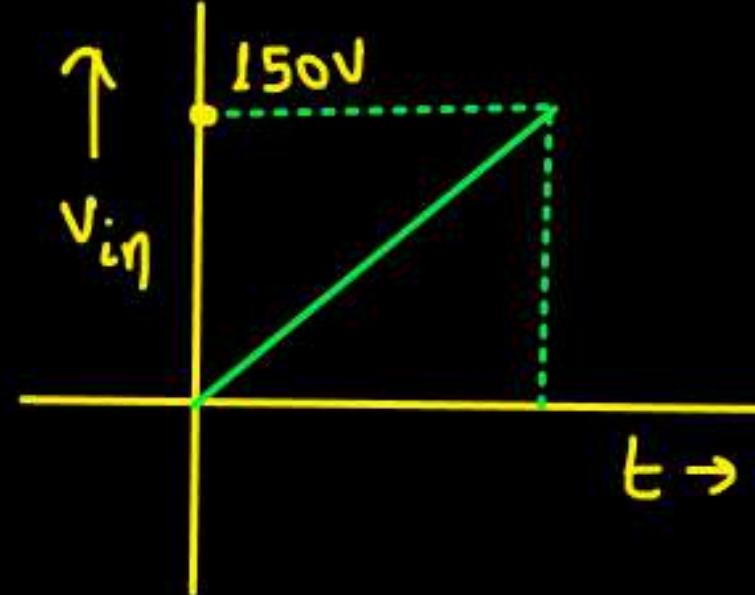

Draw VTC.

→ Applying O.C. Test

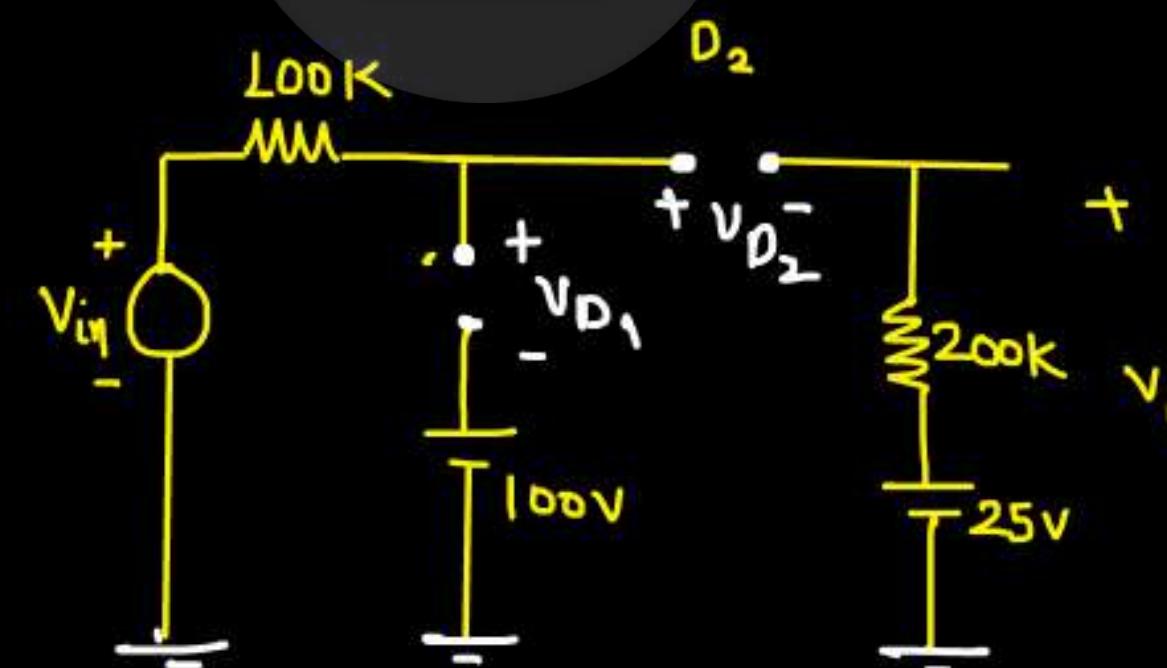

$$\begin{aligned}
 \text{(i)} \quad & V_i < 25\text{V} \\
 & V_{D1} = V_i - 100 \\
 & V_{D2} = V_i - 25 \\
 & \Rightarrow D_1 \text{ and } D_2 \text{ off} \\
 & V_o = 25\text{V}
 \end{aligned}$$

(ii) $25 < v_i < 100V$

$$v_{D_1} = v_{in} - 100V \leftarrow$$



$$v_{D_2} = v_{in} - 25V$$

\downarrow

D_2 turns on

D_1 turns off

$$v_o = \frac{2v_{in} + 25}{3}$$

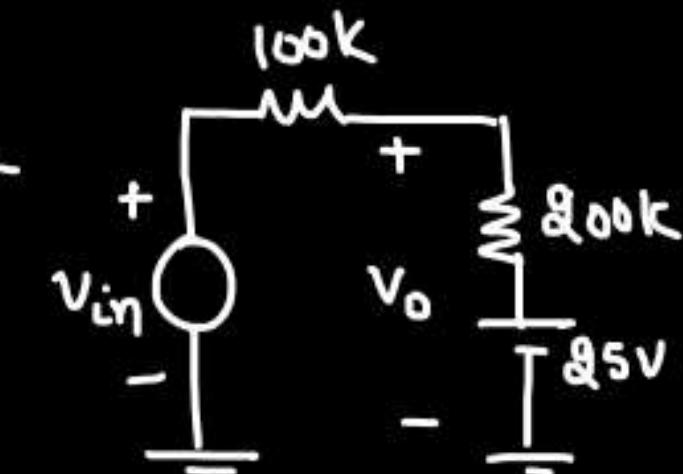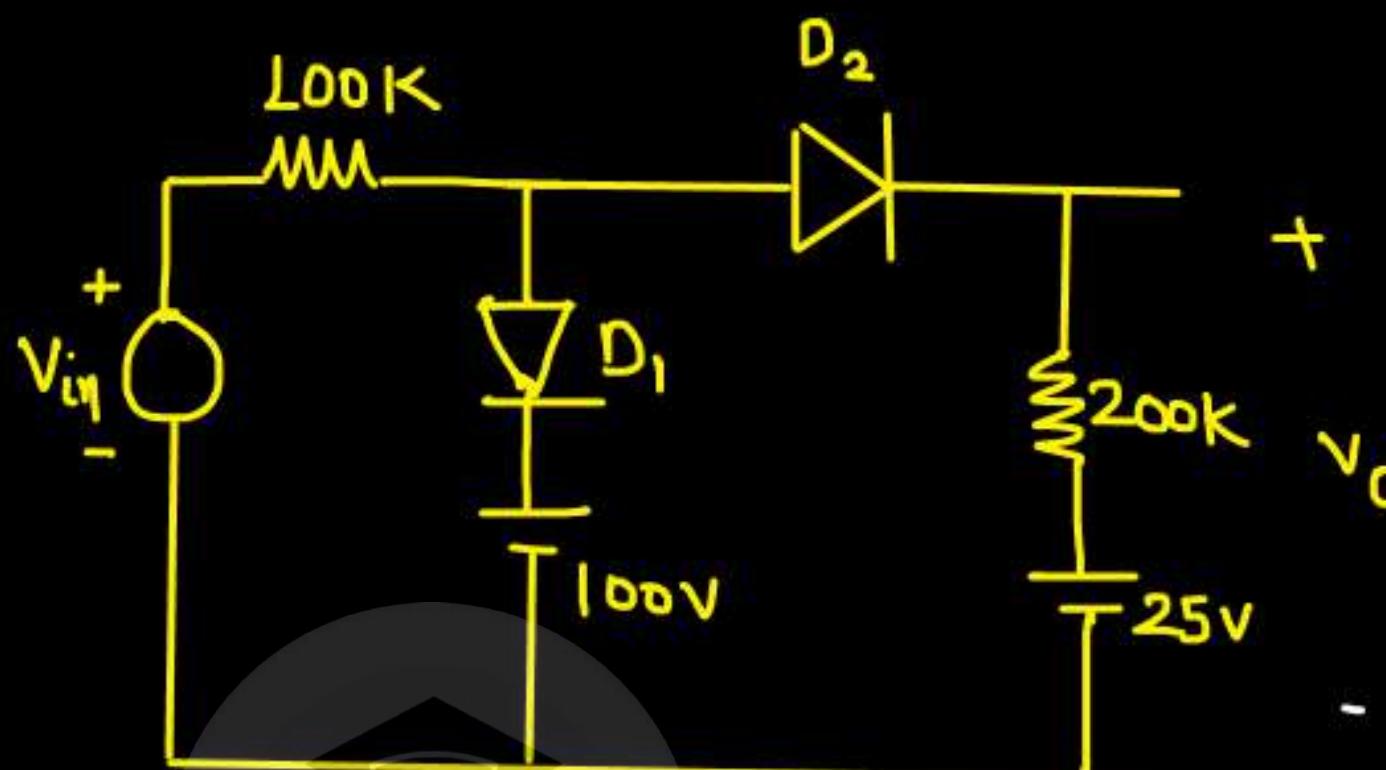


(iii) $v_i > 100V$

$$v_{D_1} = v_{in} - 100 \rightarrow +ve$$

$$v_{D_2} = v_{in} - 25 \rightarrow +ve$$

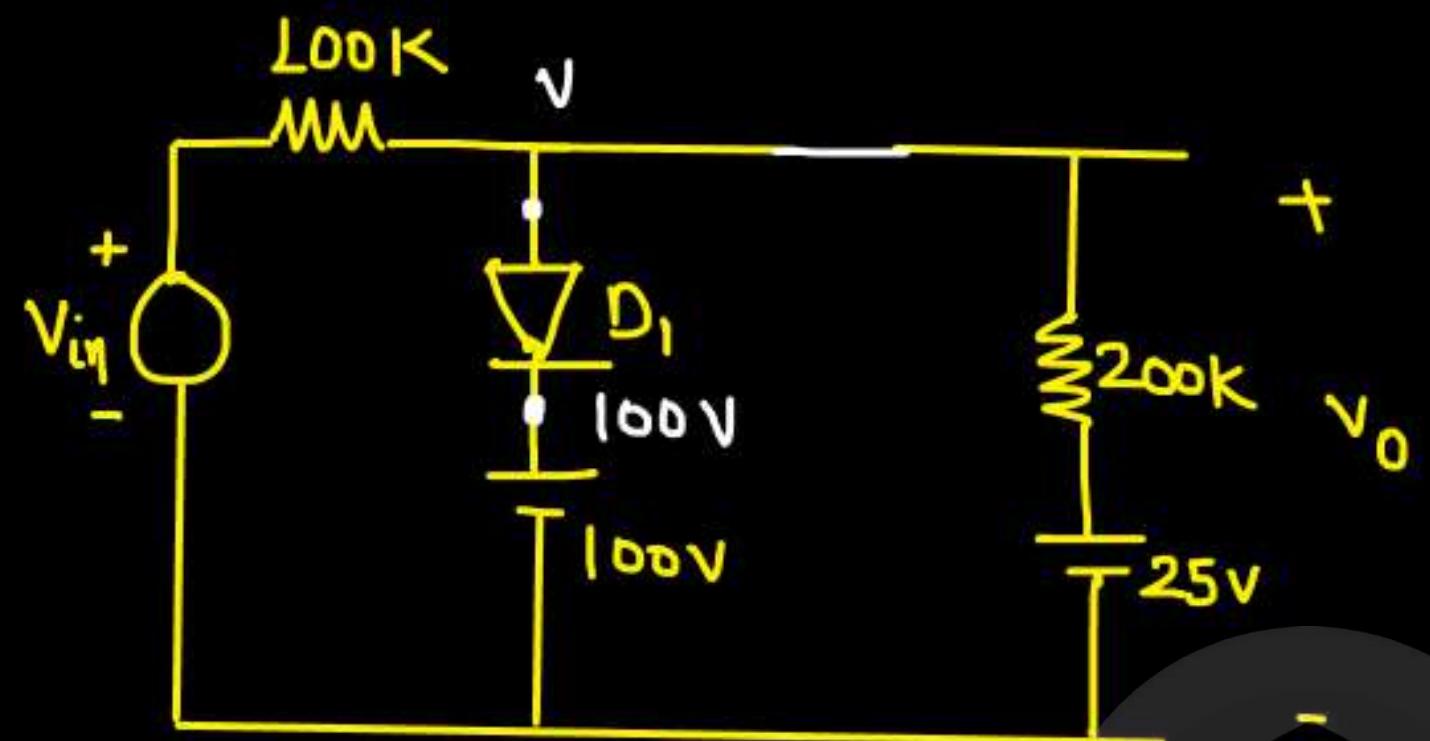\Rightarrow Here $v_{D_2} > v_{D_1} \Rightarrow$ So, first D_2 turns on, then we will decide about D_1 .



$$\frac{V - 25}{200k} + \frac{V - V_{in}}{100k} = 0$$

$$3V - 25 = 2V_{in}$$

$$V = \frac{2V_{in} + 25}{3}$$

$$V_{D1} = \frac{2V_{in} + 25}{3} - 100$$

if $V_{D1} > 0 \Rightarrow$ then only D_1 turns on

$$\frac{2V_{in} + 25}{3} > 100 \Rightarrow V_{in} > 137.5V$$

$$(iii) 100V < V_{in} < 137.5V$$

$\Rightarrow D_1$ is off

D_2 is on

$$\Rightarrow V_o = \frac{2V_{in} + 25}{3}$$

$$(iv) V_{in} > 137.5V$$

O.C. Test

$$V_{D_1} = V_{in} - 100V$$



$$V_{D_2} = V_{in} - 25V$$

\hookrightarrow Here, again D_2 will decide the cond'n of D_1 .


But from previous analysis, we know that D_1 turns on

when $V_i > 137.5V$




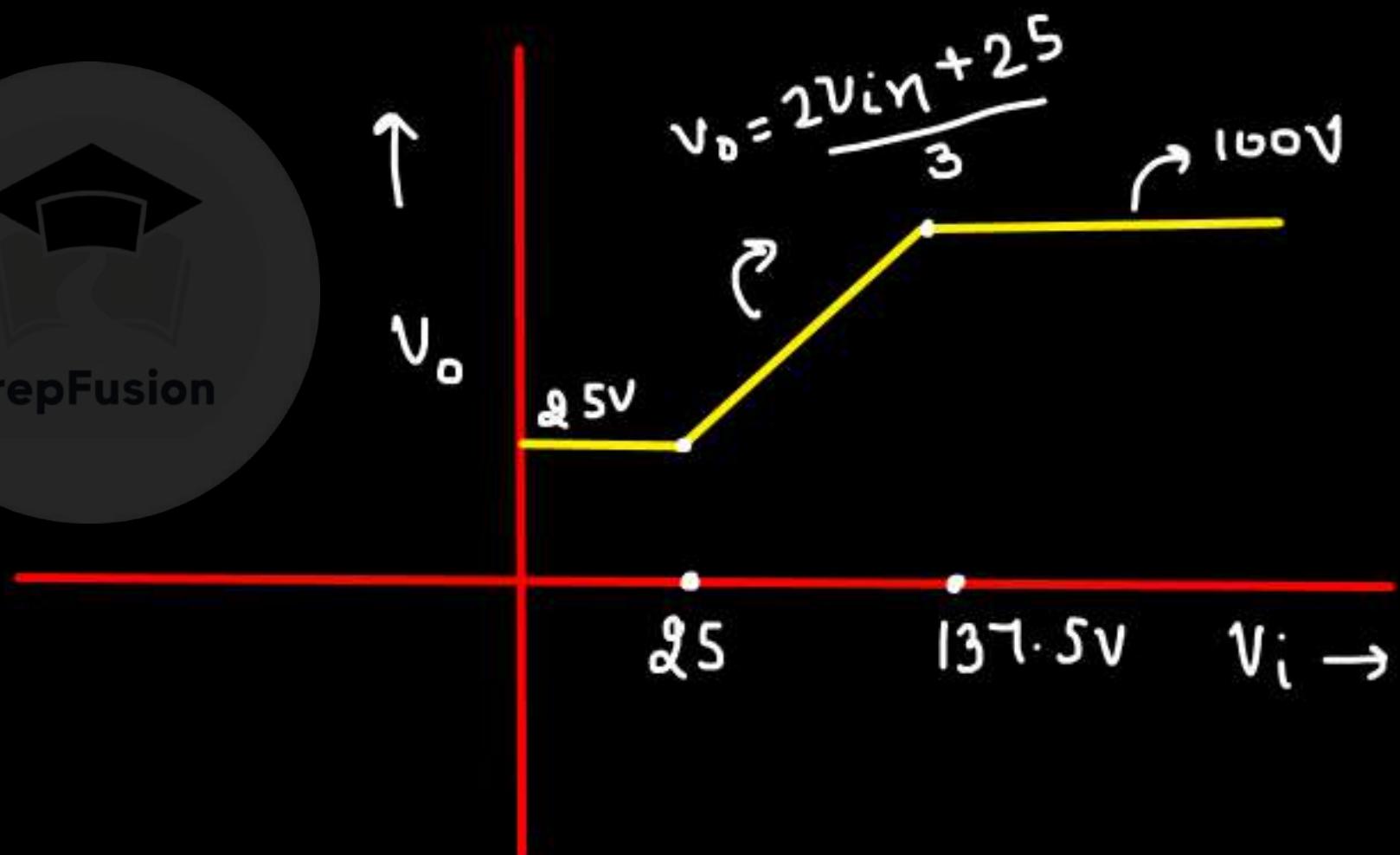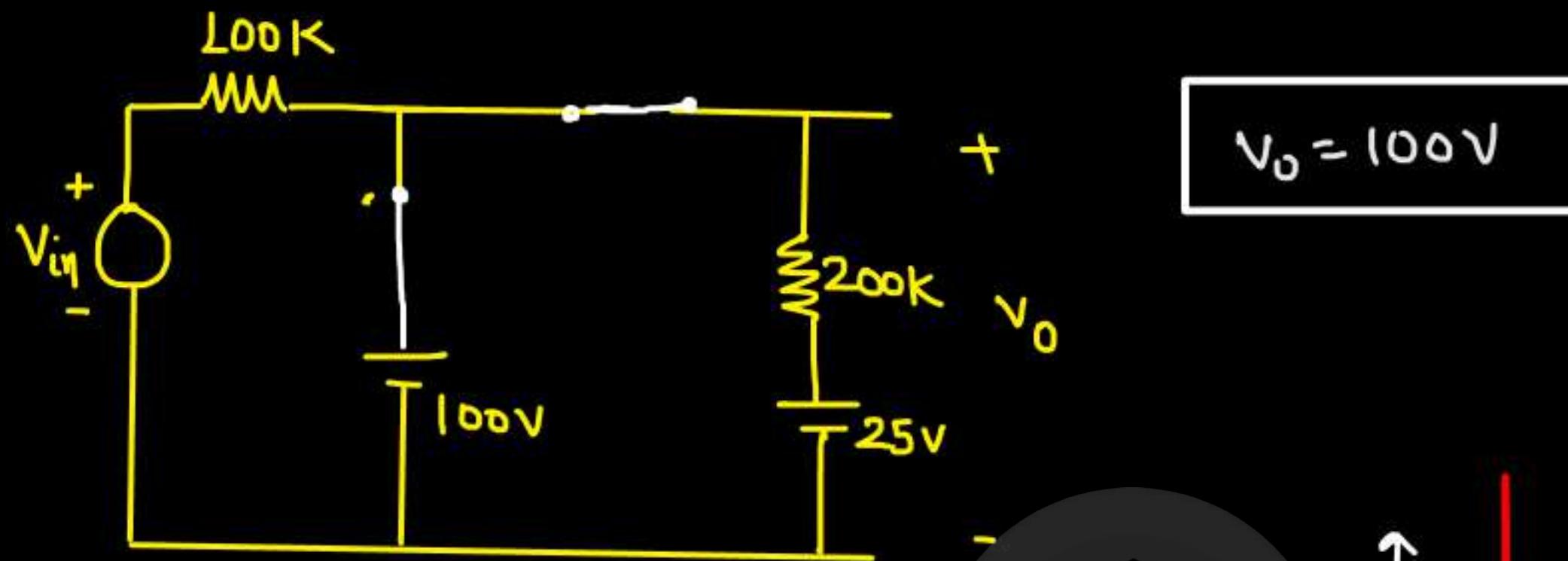

Q.

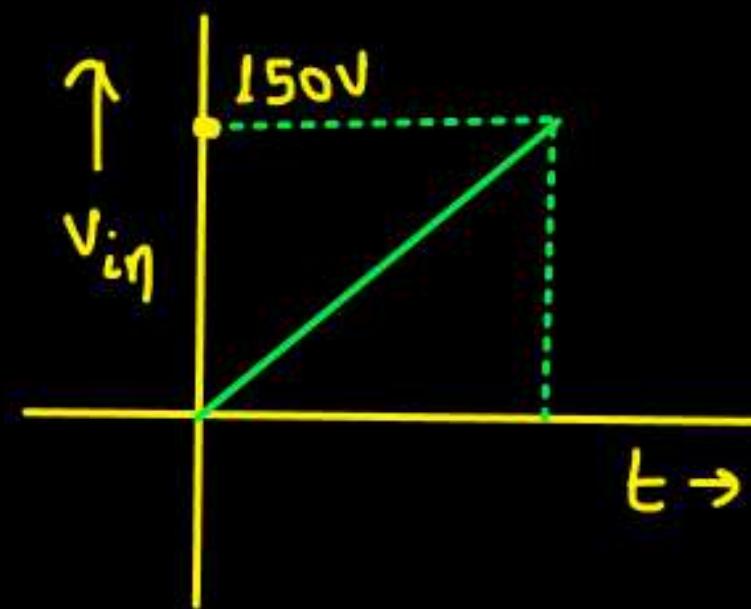

Draw VTC.

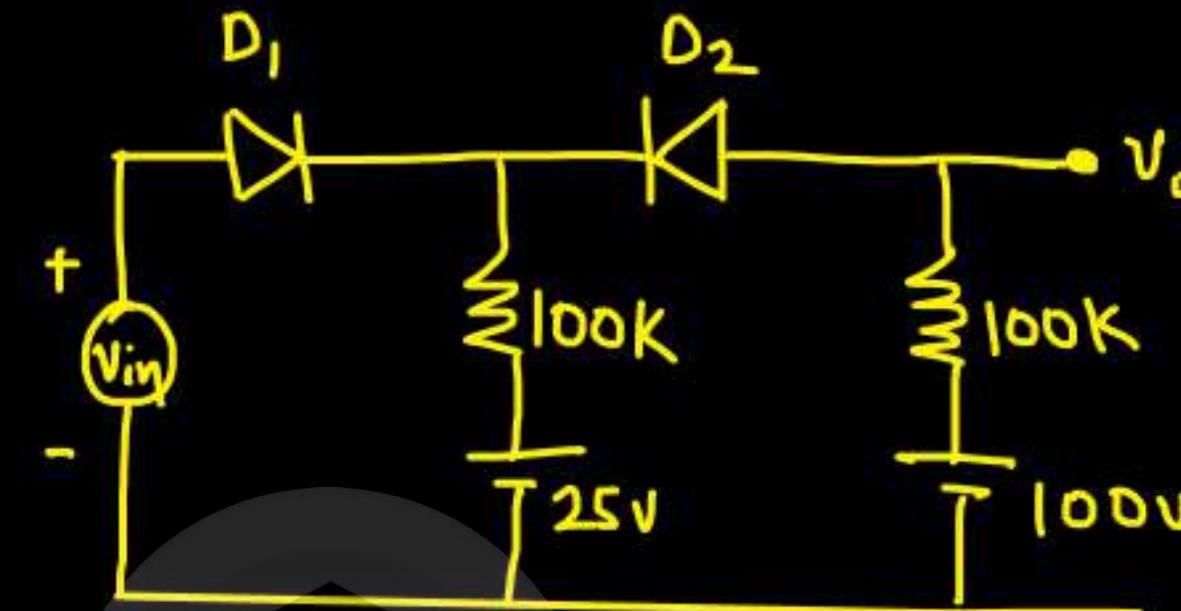

PrepFusion


→ O.C. Test →

$$(i) V_{in} < 25V$$

$$V_{D_1} = V_{in} - 25$$

$$V_{D_2} = 75V$$

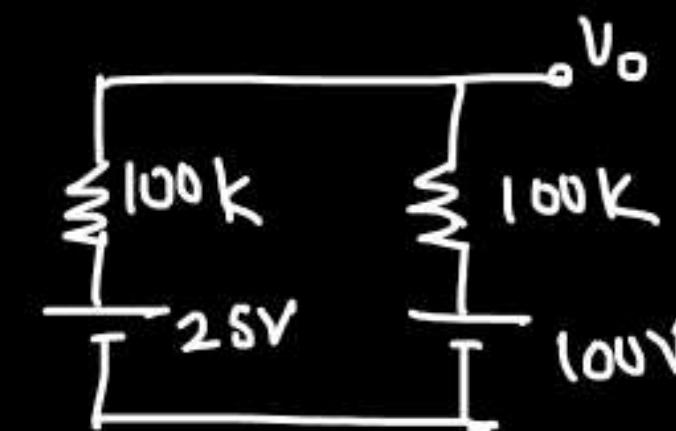$\Rightarrow D_1$ is off, D_2 is on \Rightarrow




$$V_o = 62.5V$$

$$(iii) 25V < V_i < 62.5V$$

$$V_{D_1} = V_i - 25V$$

$$V_{D_2} = 75V$$

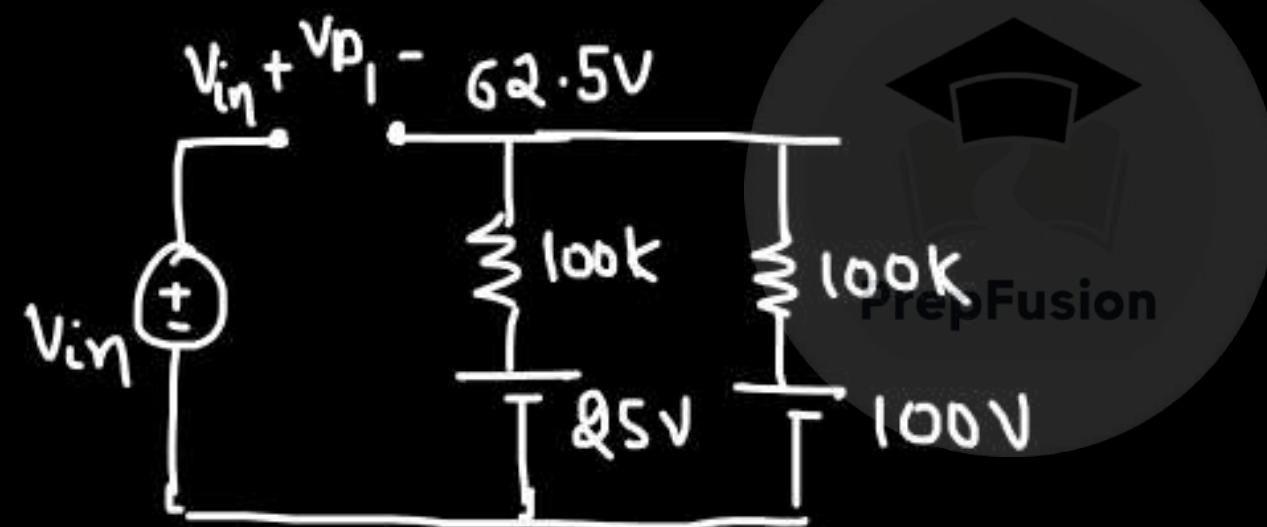\Rightarrow Here $V_{D_2} > V_{D_1} \Rightarrow$ first D_2 will turn on and decide the cond'n of D_1



$$U_{D_1} = V_{in} - 62.5V$$

$\Rightarrow V_{in} < 62.5V \Rightarrow D_1$ is off $\Rightarrow D_2$ is on

$$V_o \approx 62.5V$$

$$(iv) 100V > V_i > 62.5V$$

$$V_{D_1} = V_{in} - 25$$

$$V_{D_2} = 75V$$

∴

First D_2 turns on

↳ decide D_1 condⁿ

↳ from prev. analysis, we know D_1 is on for $V_i > 62.5V$


D_1 and D_2 are on

$$V_o = V_{in}$$

when D_1 is on, the o.c. potential across D_2 changes.

$$V_{D_2} = V_{in} - 100V$$

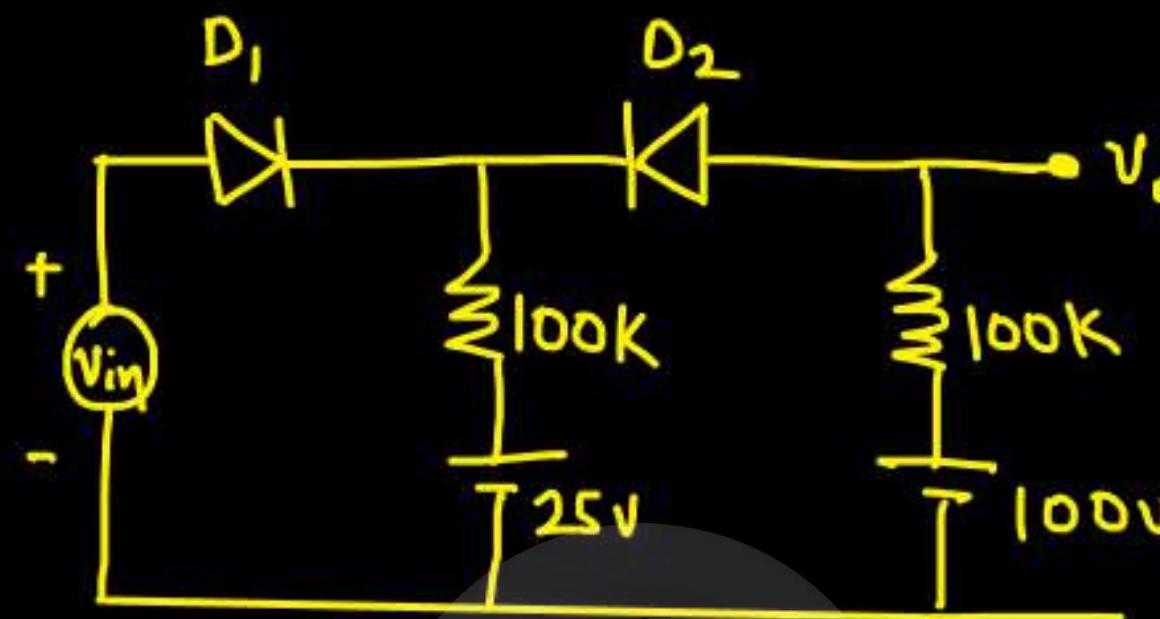and if $V_{in} > 100V \Rightarrow D_2$ will be off



PrepFusion

$$(v) V_{in} > 100V$$

$$V_{D_1} = V_{in} - 25V$$

$$V_{D_2} = 75V$$

if $V_{in} > 100V \Rightarrow D_1$ will turn ON first and then we will decide the working cond'n of D_2 .



if D_1 turns ON \Rightarrow

$$V_{D_2} = V_{in} - 100$$


and for $V_{in} > 100$

$\Rightarrow D_2$ is off

$V_o = 100V$

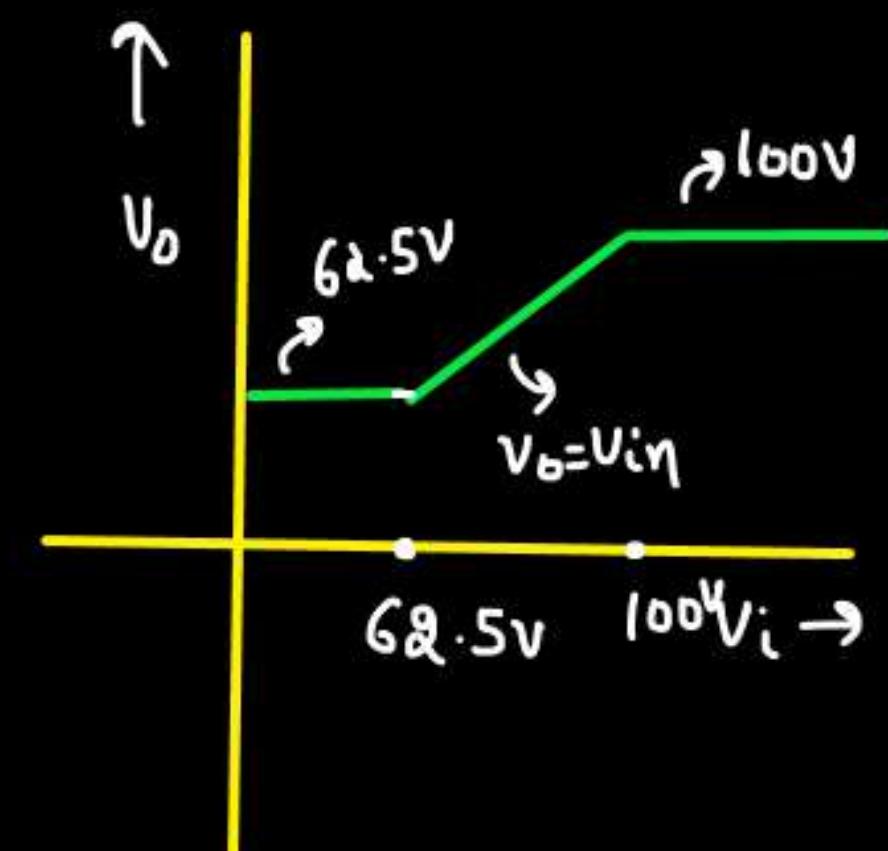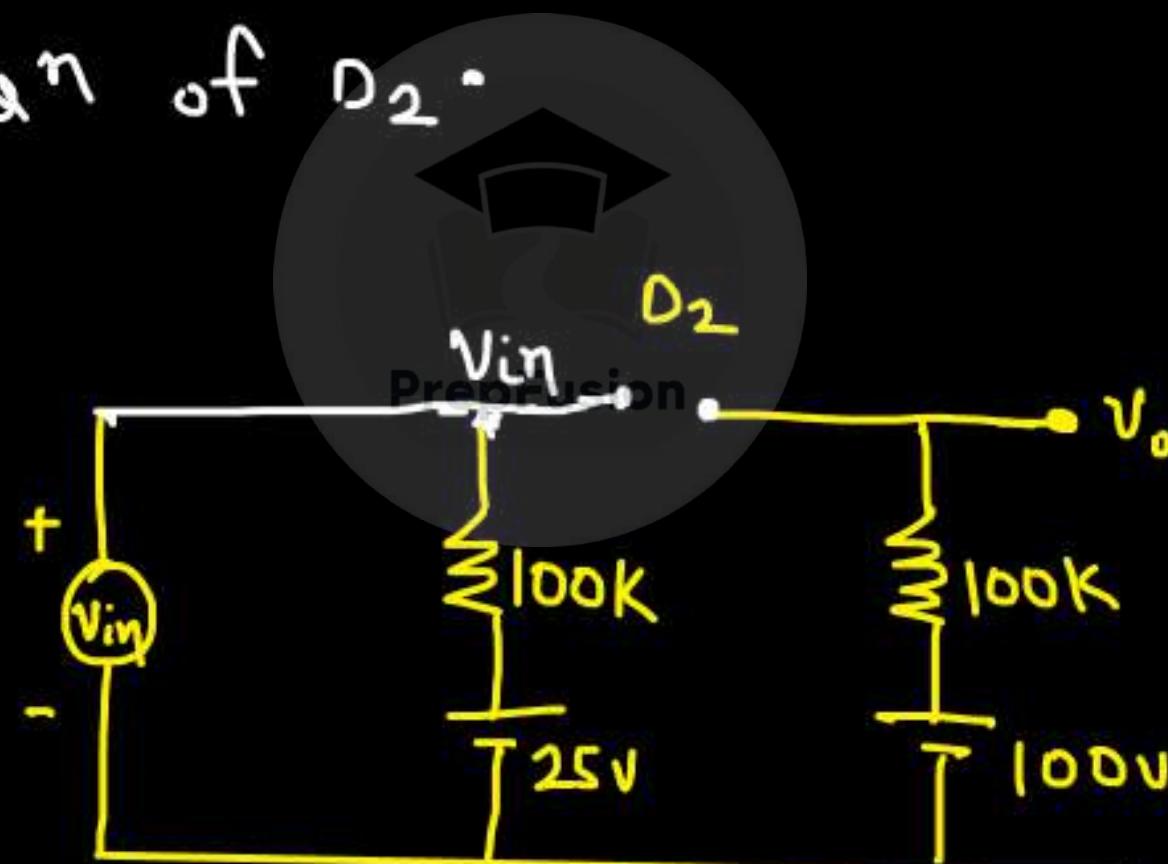


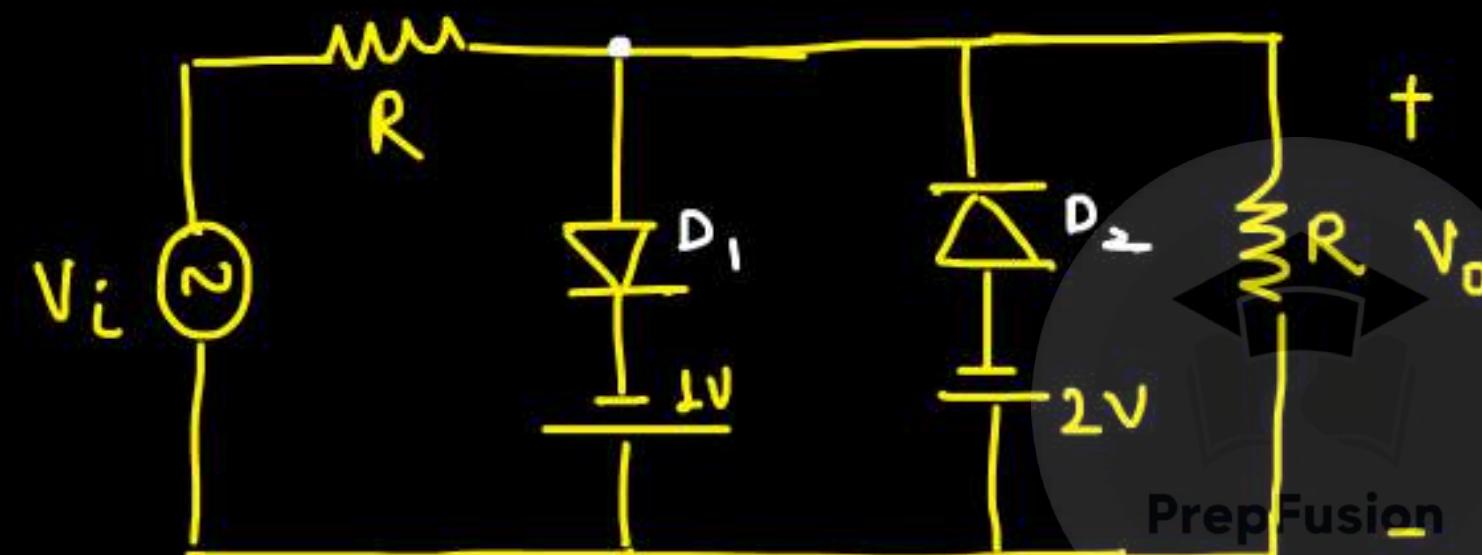Q. For o/p to be clipped, the i/p v_i should lie out of what range?



$$\rightarrow v_{o1} = v_i/2 + 1$$


$$v_{o2} = -2 - v_i/2$$

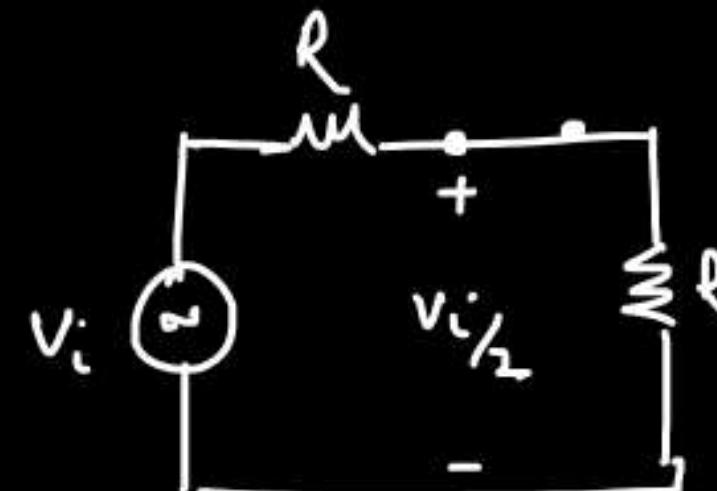


$$V_{D_1} = \frac{V_{in}}{2} + 1$$

$$V_{D_2} = -2 - \frac{V_{in}}{2}$$
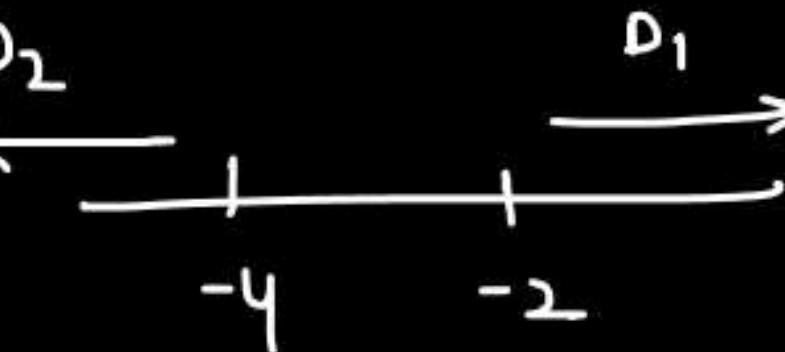
$$\Rightarrow \frac{V_{in}}{2} + 1 > 0 \Rightarrow \underline{\underline{\frac{V_{in}}{2} > -1}} \Rightarrow V_o = -1V$$





\Downarrow

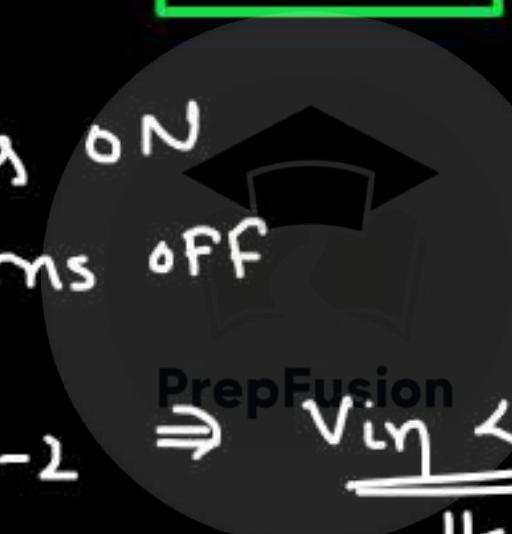

$\Rightarrow -2 - \frac{V_{in}}{2} > 0 \Rightarrow \underline{\underline{\frac{V_{in}}{2} < -2}} \Rightarrow V_o = -2V$

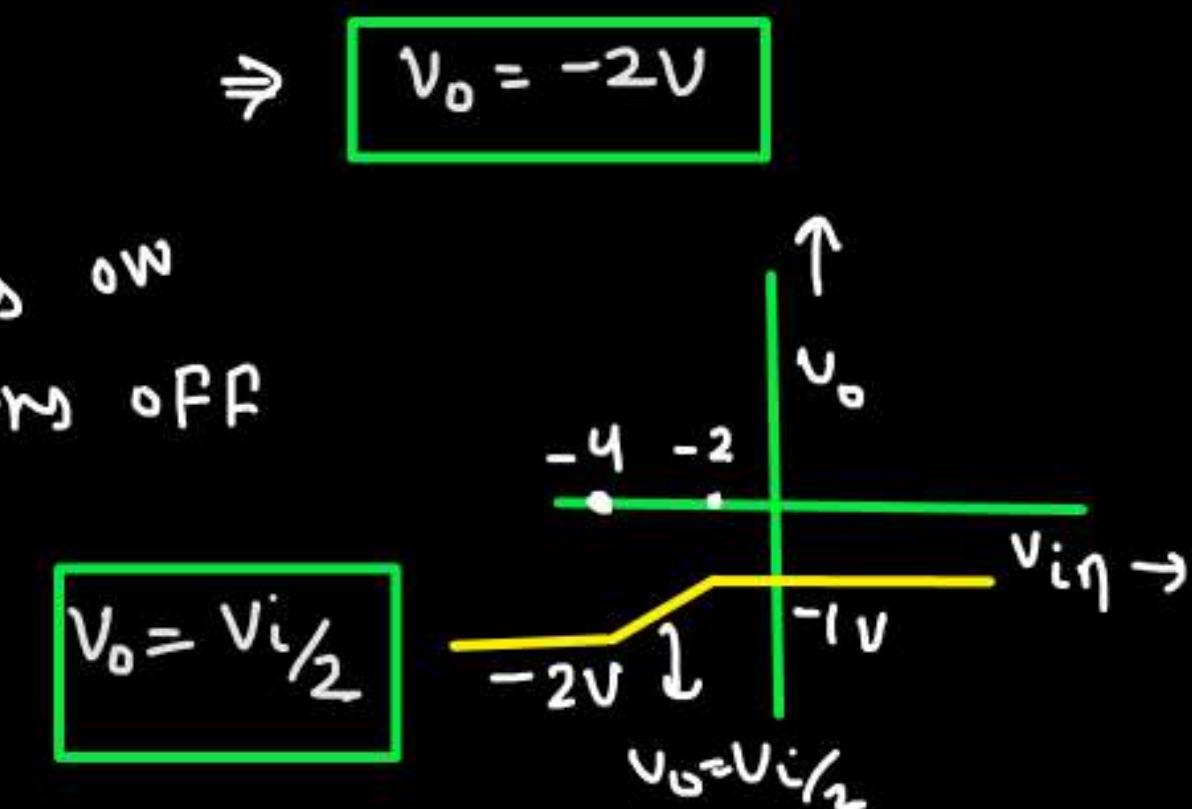$\Rightarrow -2 < V_{in} < -4 \Rightarrow D_1 \text{ and } D_2 \text{ OFF} \Rightarrow V_o = \frac{V_{in}}{2}$



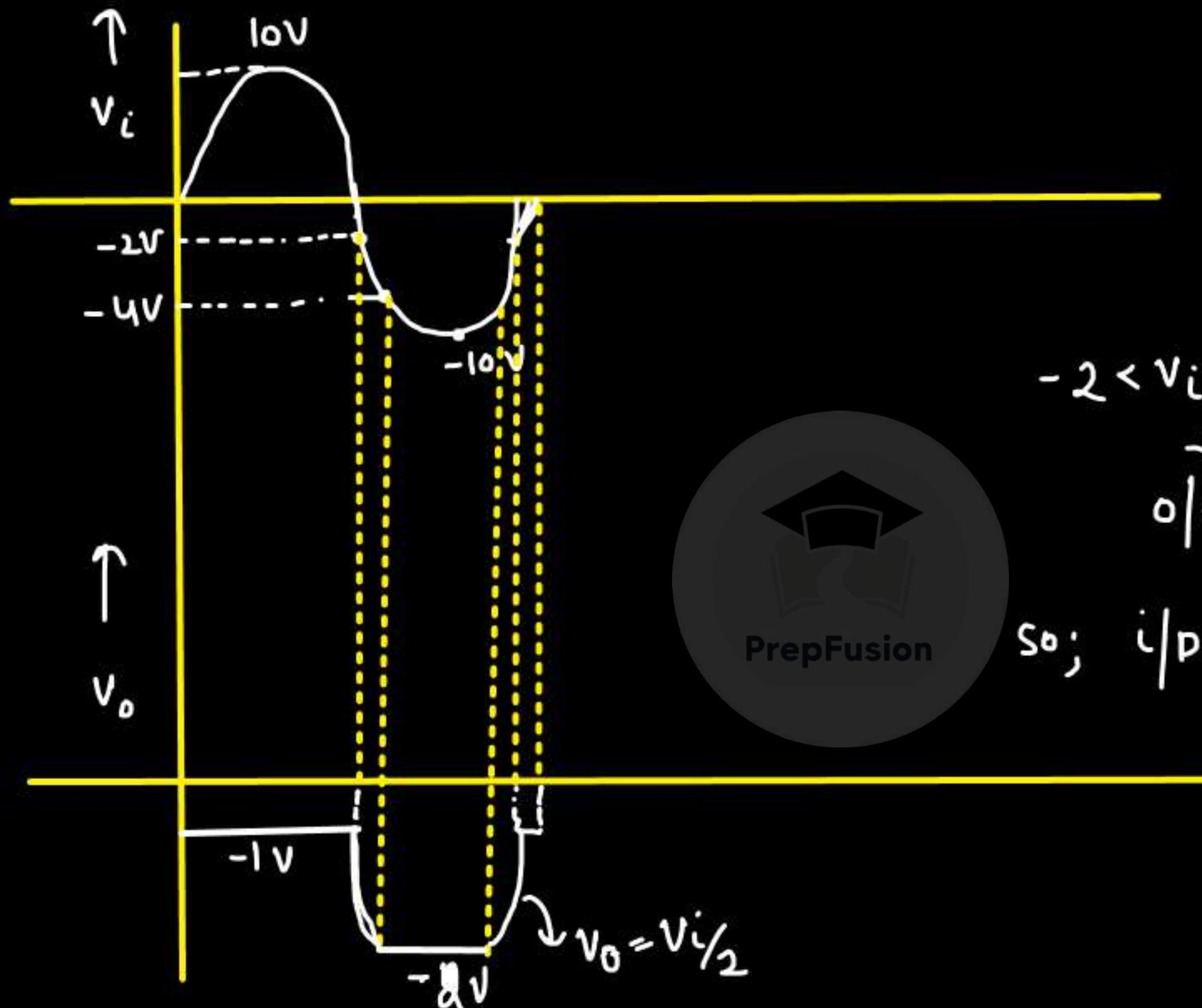

$$-2 < V_i < +2$$






O/P is not clipped.

So; i/p should lie out of
the range -2 to $+2V$
if it wants to be
clipped.

CLAMPER CIRCUIT

Definition :-

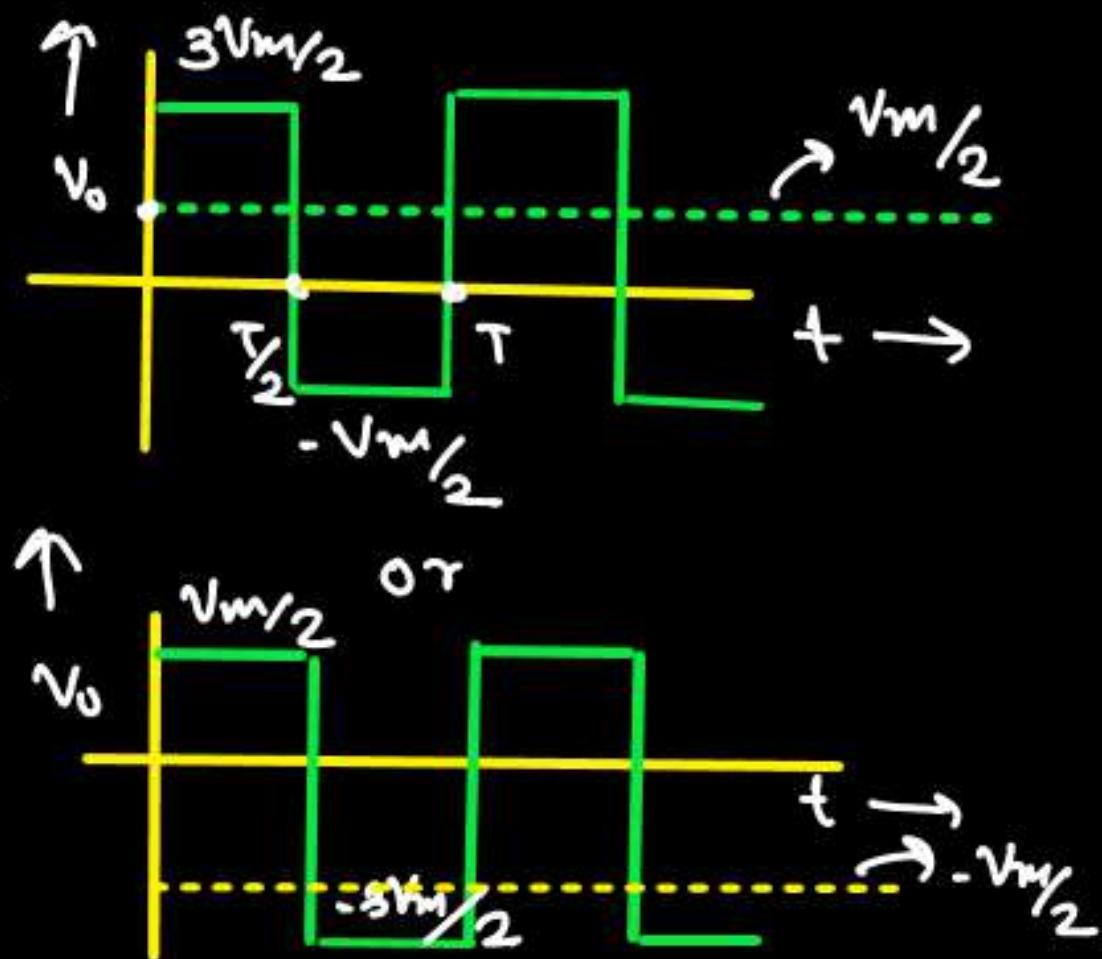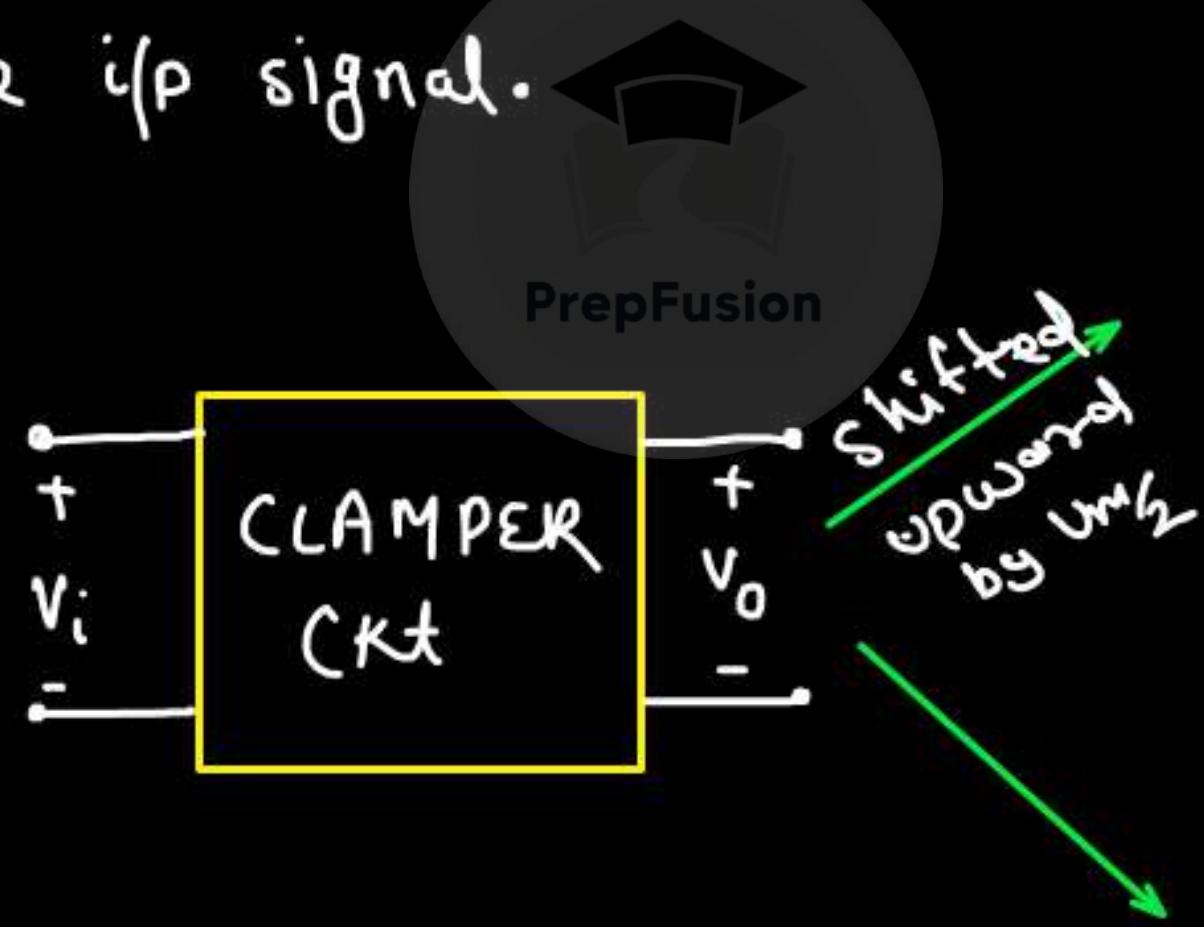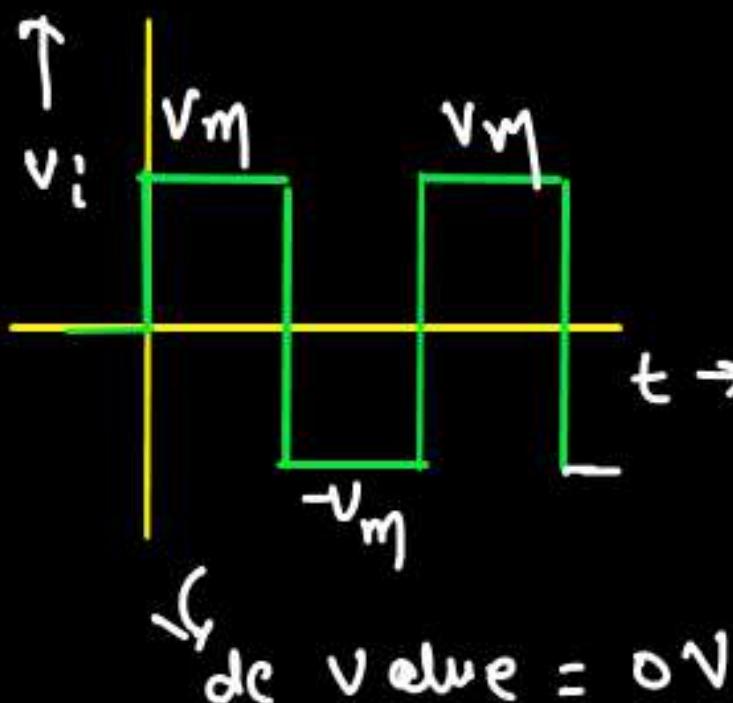Circuit that shift the waveform of input signal to a desired reference dc level without changing the actual appearance of the ip signal.



Classification

Positive
clamper

↓
shifts the
waveform upward


Negative
clamper

↳ shifts the
waveform
downward


Clamper ckt
with some bias

↳ Think of the ckt?

$$V_o = V_i + \text{dc value}$$

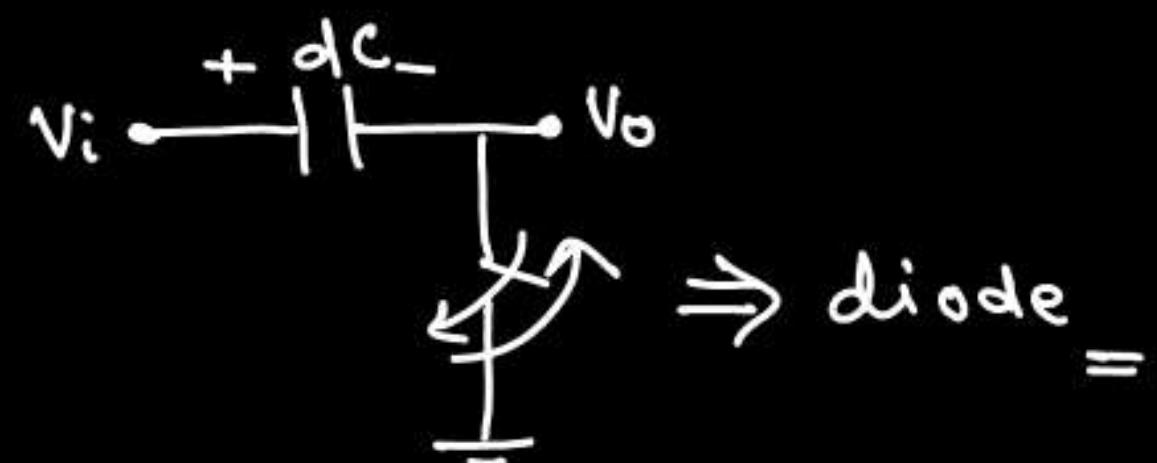

* Revision Question :-

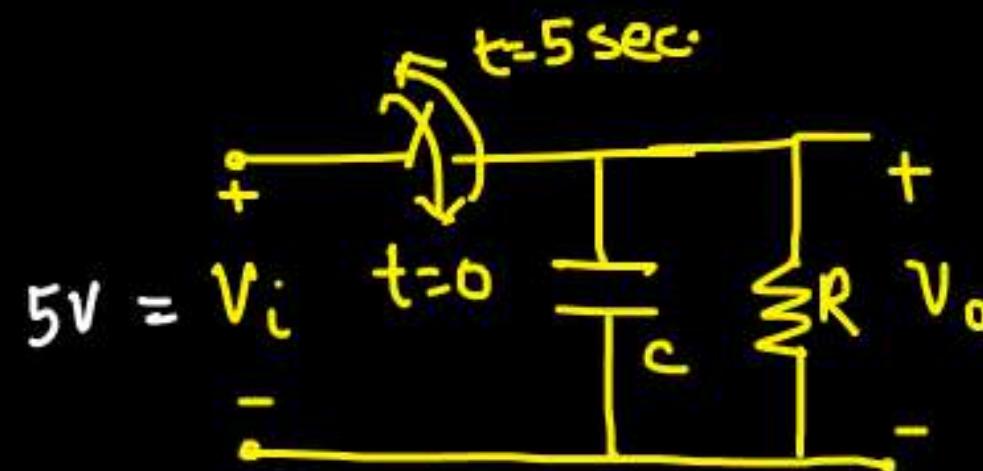


$$RC = 50 \text{ K sec.}$$

switch is first closed @ $t=0$
and opened again @ $t= 5 \text{ sec.}$

→

$$0 < t < 5 \text{ sec.}$$

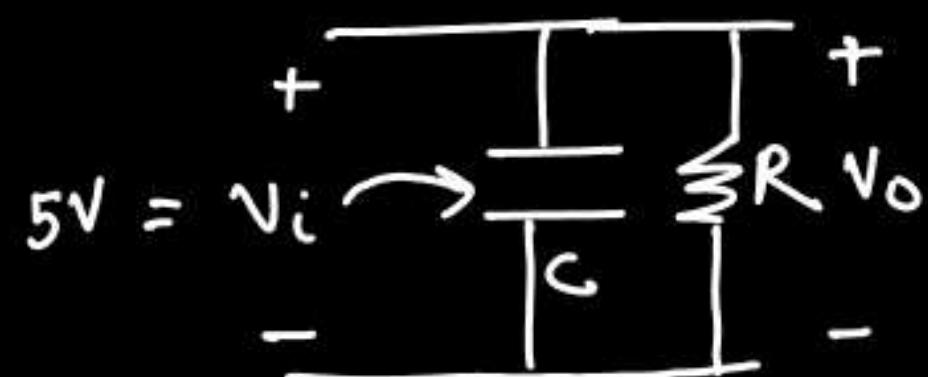


$$V_o(t=0^+) = 5V$$

$$V_o(t=1) = 5V$$

$$V_o(t=5^-) = 5V$$

$t > 5 \text{ sec.}$

$$V_o(t) = 5e^{-t/RC}$$

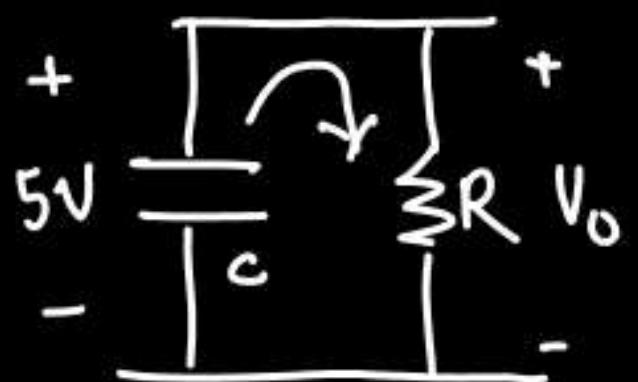

$$RC = 50 \text{ K sec.}$$

$$= 50 \times 10^3 \text{ sec.}$$


→ very large

since RC is very large, cap. will not
discharge very quickly and remain

@ 5V for a very long time.

$$V_o(t=5^+) = V_o(t=10) = V_o(t=15) = V_o(t=20 \text{ sec.}) = 5V$$

1. Positive clapper ckt :-


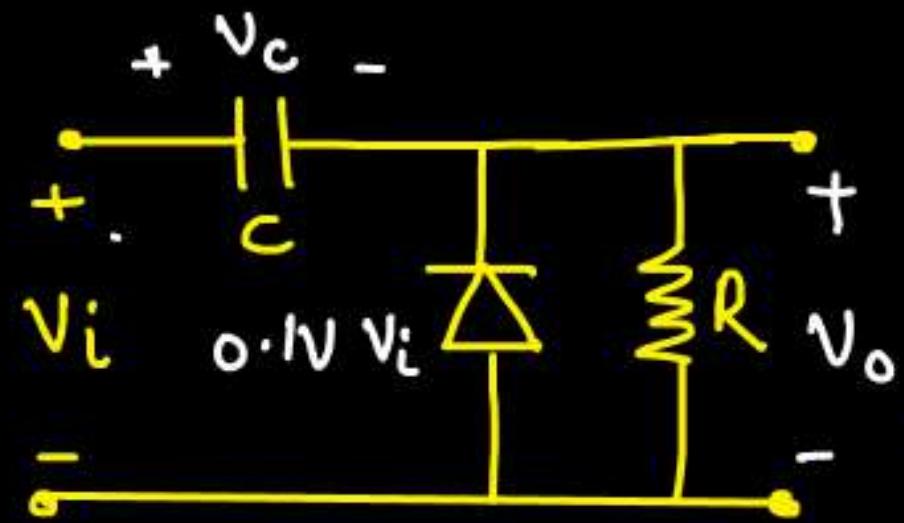


$RC \rightarrow \text{very large}$

$$@ t=0, V_C(0^+) = 0V$$

$$0 < t < \frac{T}{2}$$

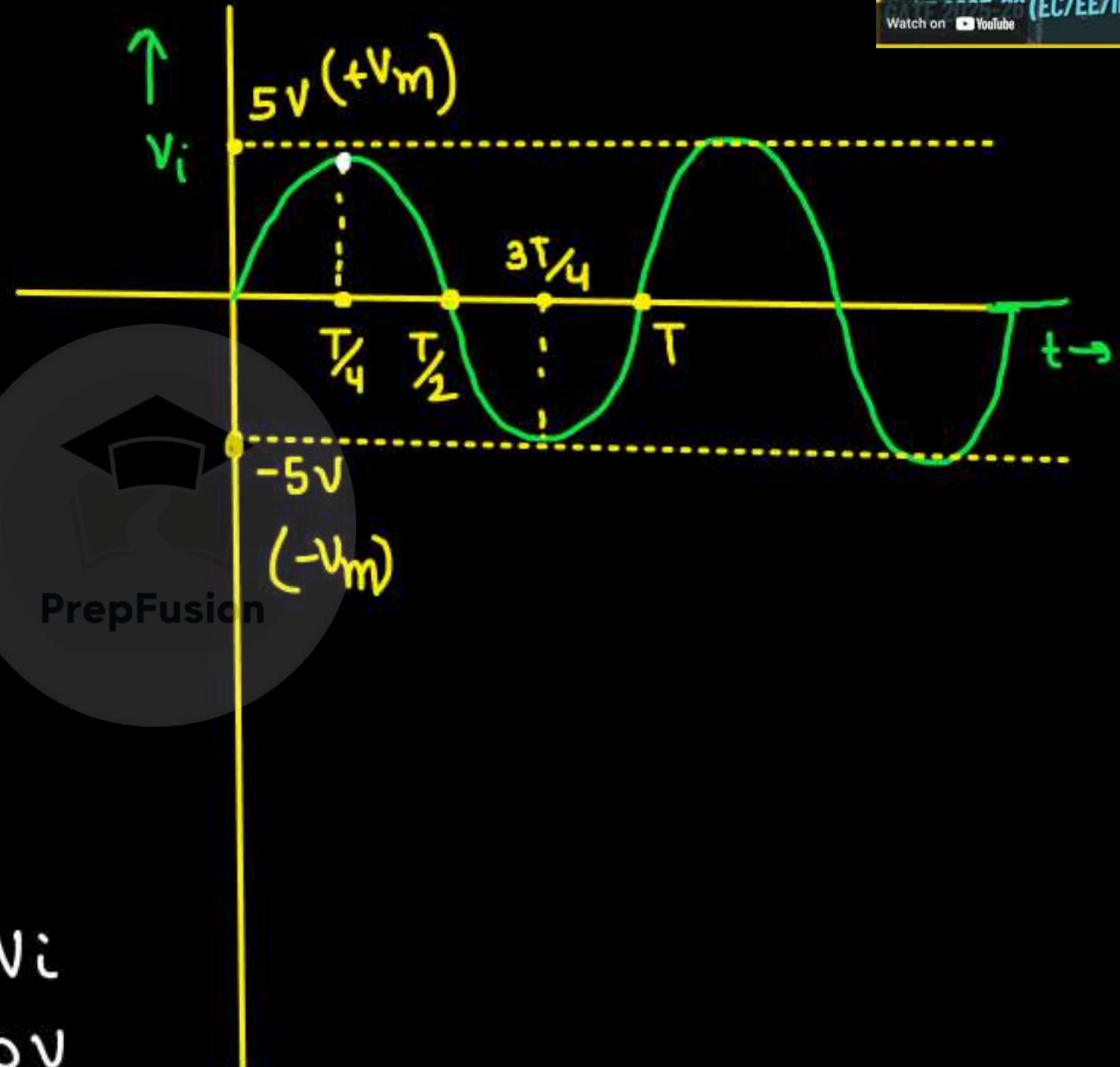
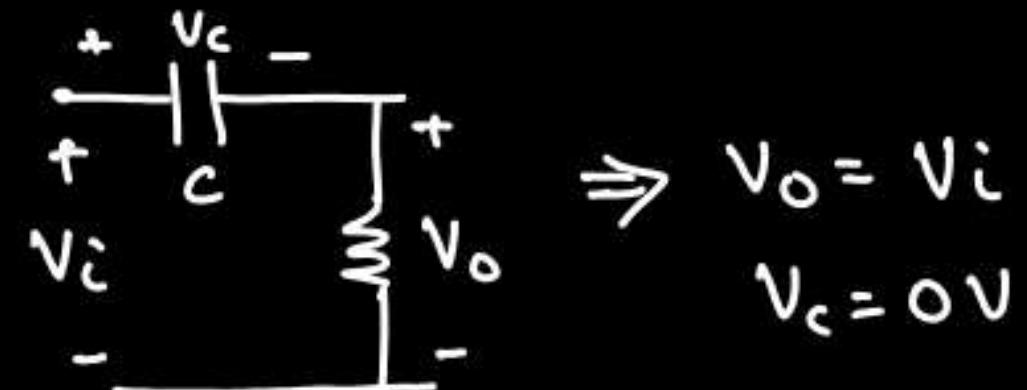
for $V_i > 0V \Rightarrow$ diode \Rightarrow off



For $t \geq T_2$ to $3T_4$

$$3T_4 > t > T_2$$

@ $t = T_2^+$ \Rightarrow diode turns ON

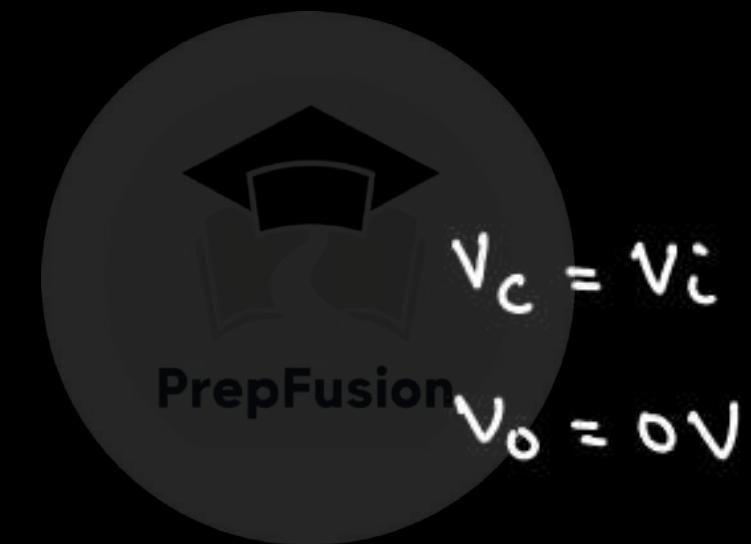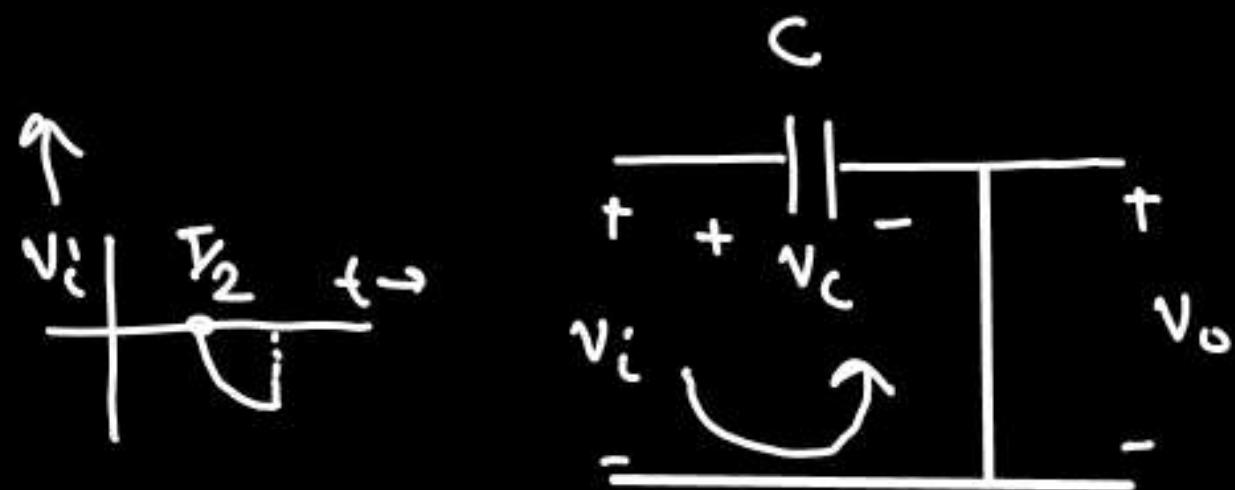


$$v_c(3T_4) = -v_m$$

$$v_o(3T_4) = 0V$$


@ $t = \frac{3T}{4}^+$

let $V_m = 5V$

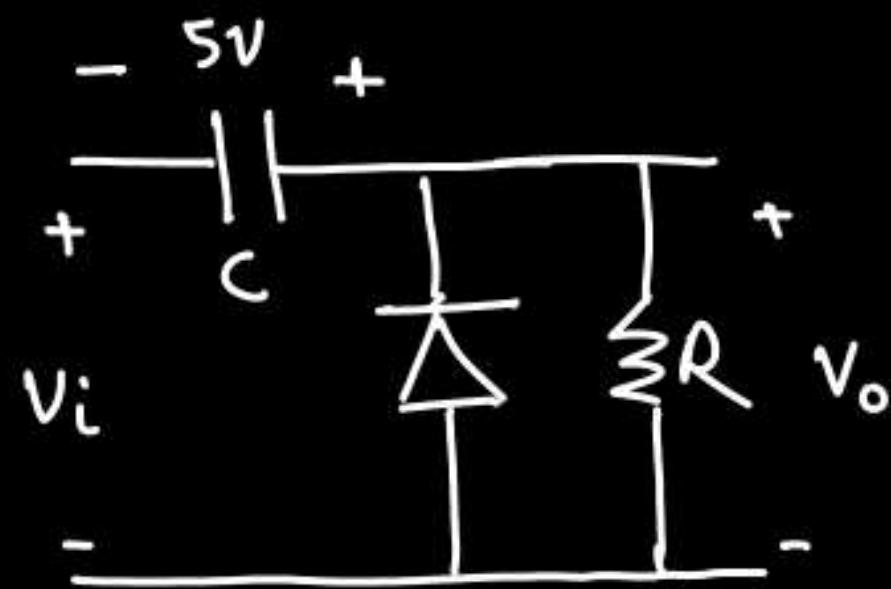

$$V_i\left(\frac{3T}{4}^+\right) = -4.9V \text{ (het)}$$

Diode turns off

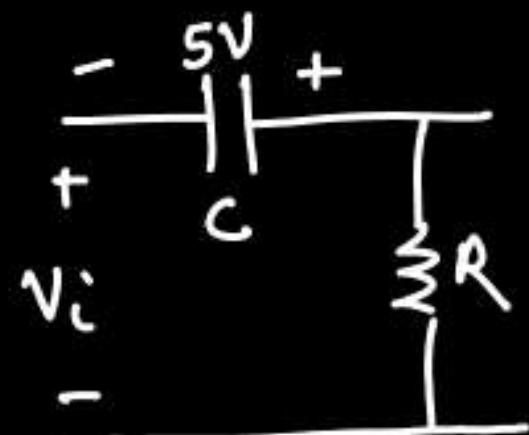

since RC is very large, cap. can neither charge nor discharge.

To turn on the diode $V_i + 5 < 0 \Rightarrow V_i < -5V$
↳ NOT possible




$\Rightarrow V_c = -5V$ (always)



$V_o = V_i + 5V$ ✗

Basic Semiconductor Physics | Analog Electro...
ANALOG ELECTRONICS
BASIC SEMICONDUCTOR PHYSICS
LECTURE- 1
GATE 2025-26 (EC/EE/IN)
Watch on YouTube
AIR 27 (ECE)
AIR 45 (IN)



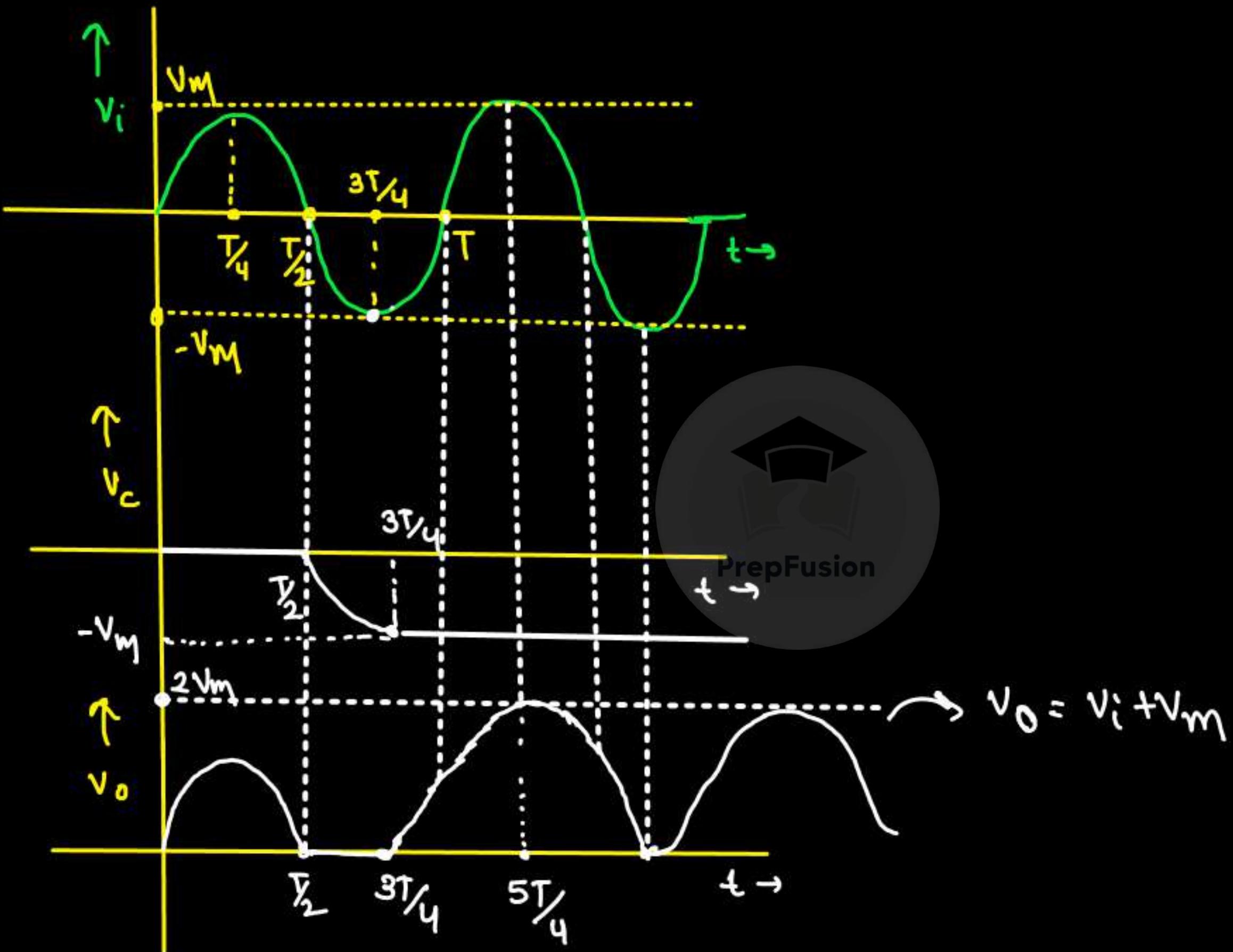




Q. Draw o/p waveform.

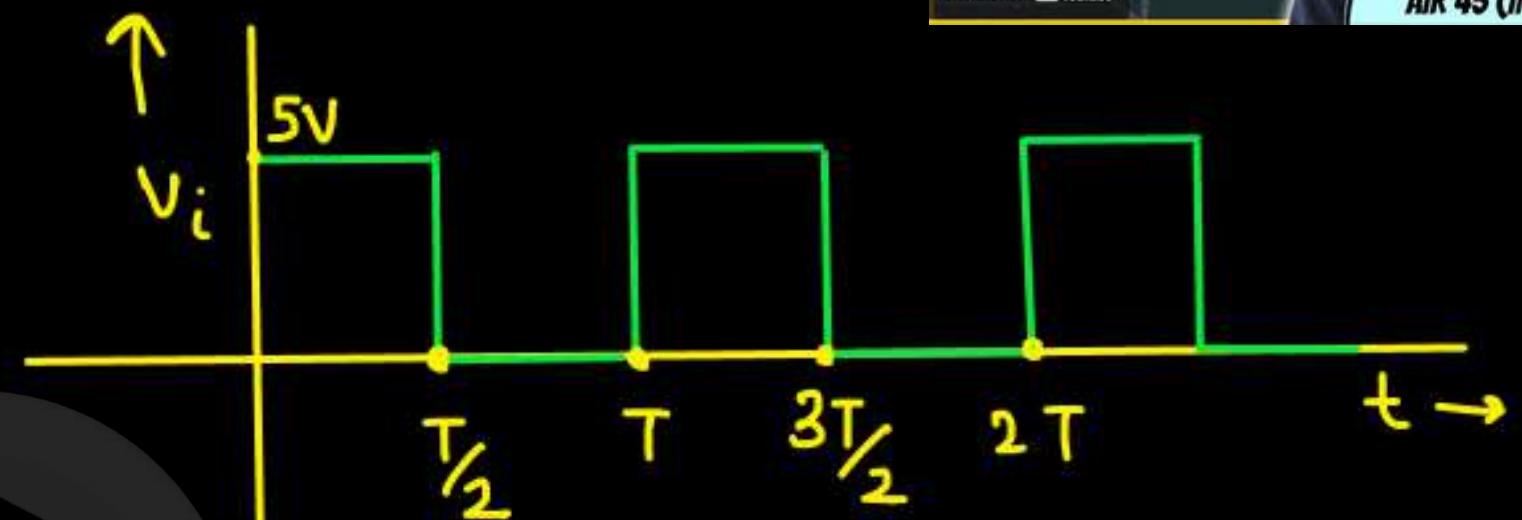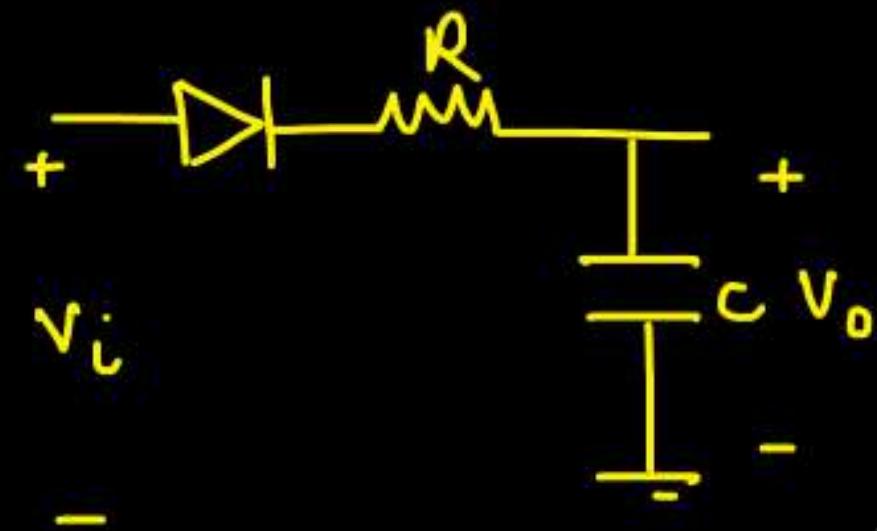


Given $\underline{T = 2RC}$

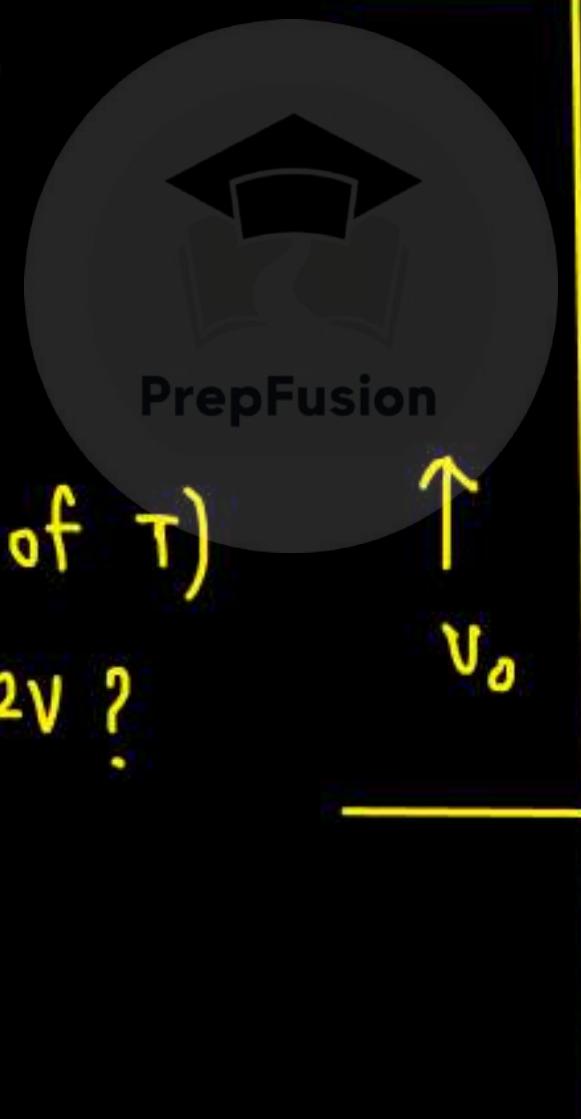Also, find the time (in terms of T) in which o/p reaches to 4.32V?




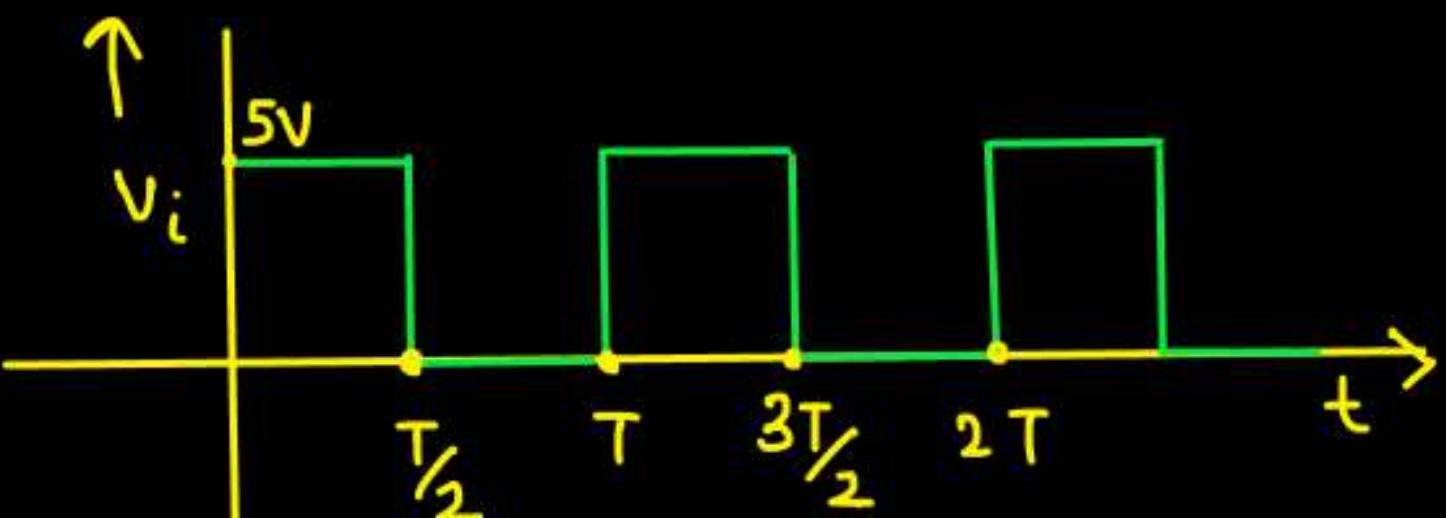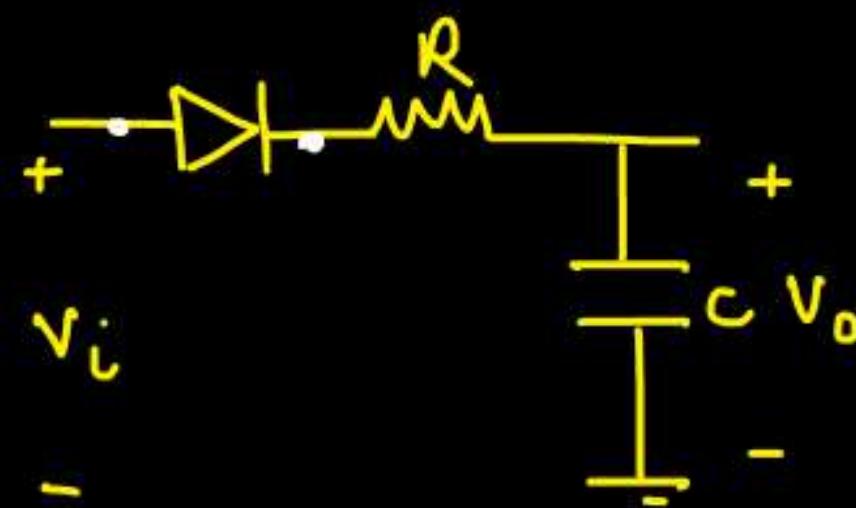


@ $t=0 \Rightarrow$ diode turns on

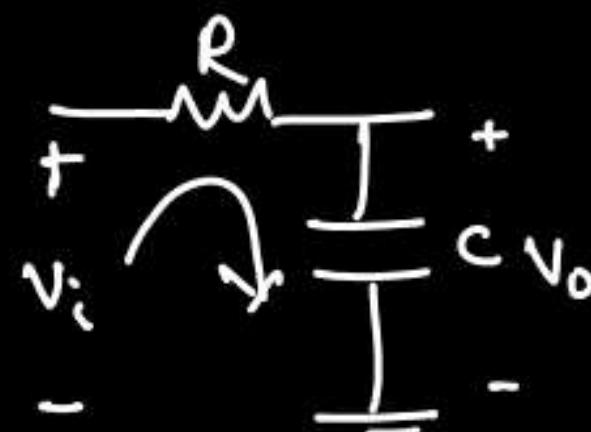
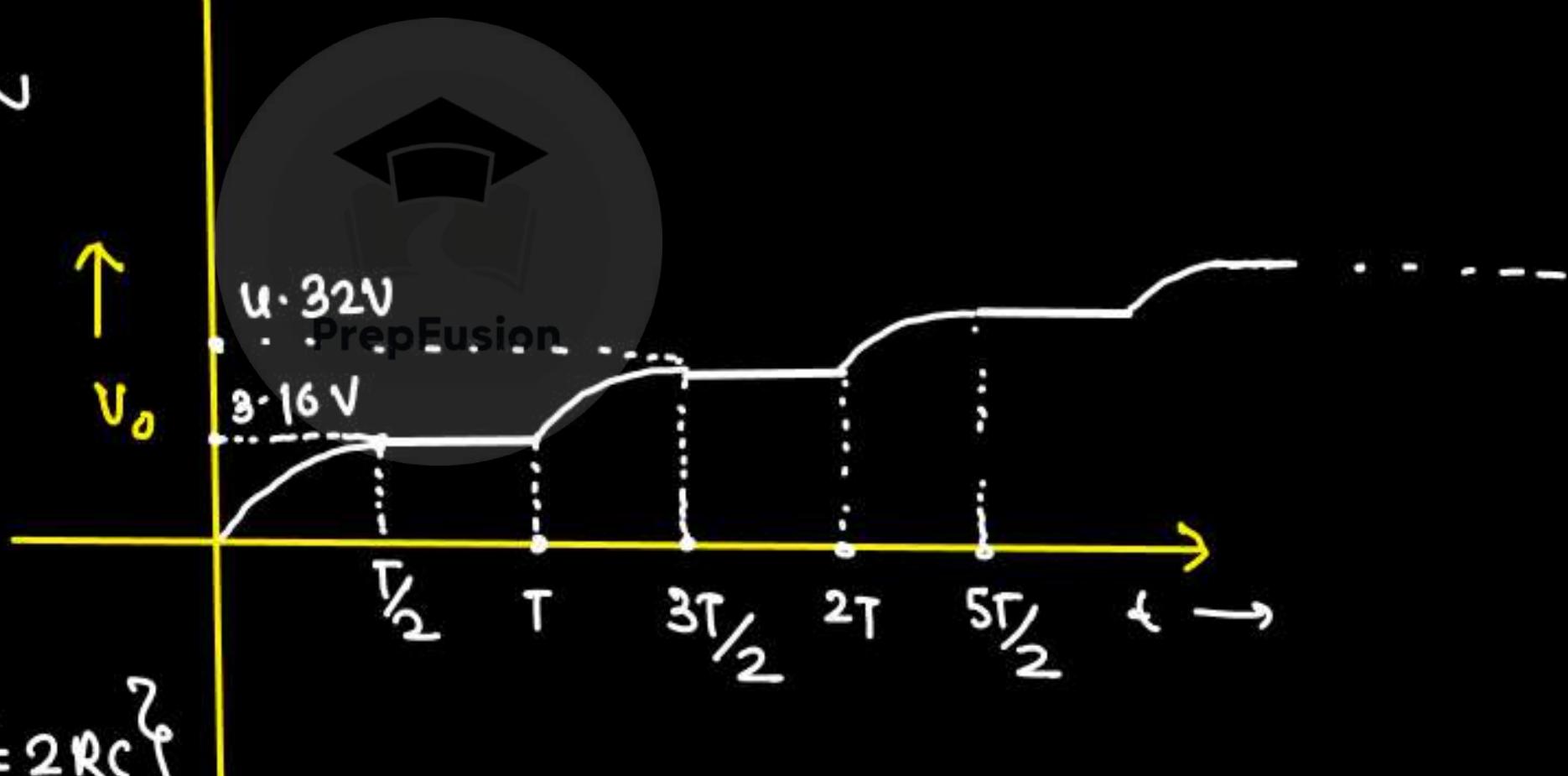
$$\begin{aligned}
 V_o &= 5(1 - e^{-t/RC}) \\
 &= 5\left(1 - e^{-T/2RC}\right) \quad \{ T = 2RC \} \\
 &= 5(1 - e^{-1}) = 3.16V
 \end{aligned}$$




@ $t = \frac{T}{2}^+$

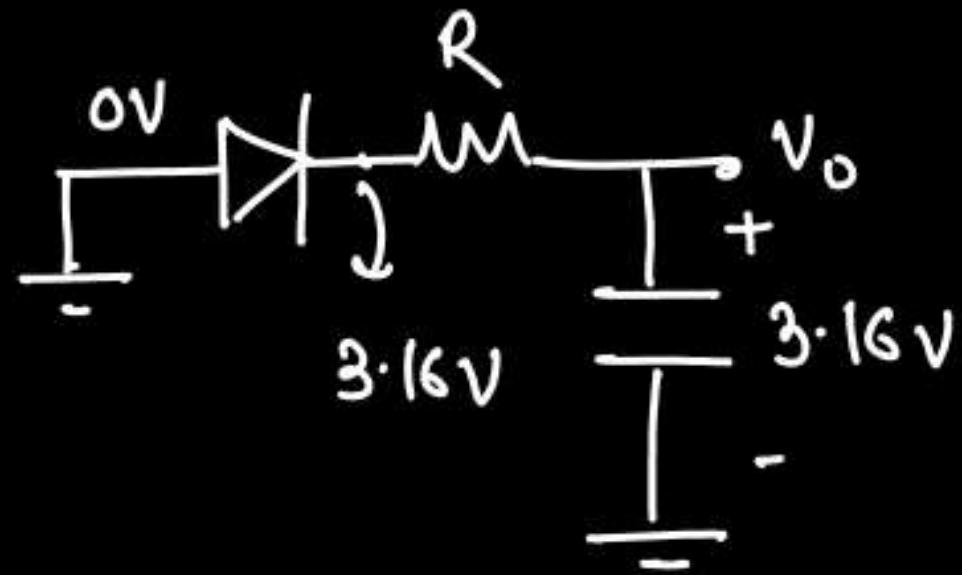

$\frac{T}{2} < t < T \Rightarrow$ diode off $\Rightarrow V_o = 3.16V$



① $t = T +$

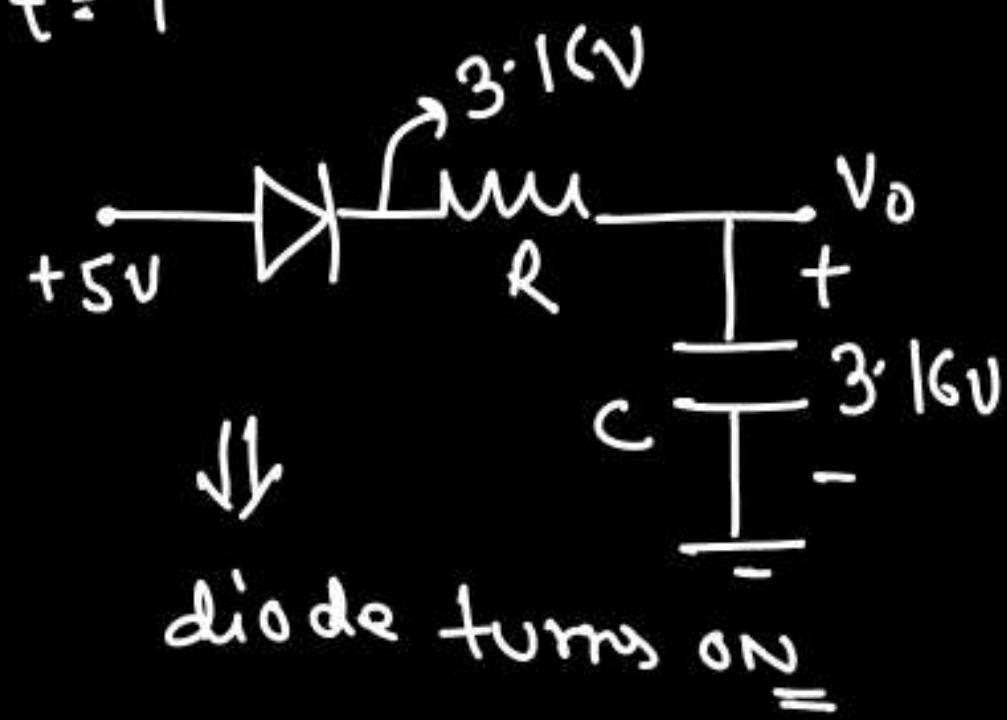

$$V_o = 5 + (3.16 - 5) e^{-\frac{(t-T)}{RC}}$$

$$V_o(3T/2) = 5 - 1.84 e^{-\frac{T}{2RC}} \quad \left\{ T = 2RC \right\}$$

$$V_o(3T/2) = 4.32 V$$

Basic Semiconductor Physics | Analog Electro...

ANALOG ELECTRONICS

BASIC SEMICONDUCTOR PHYSICS

LECTURE-1

GATE 2025-26 (EC/EE/IN)


AIR 27 (ECE)
AIR 45 (IN)

Watch on YouTube



For $\frac{3T}{2} < t < T$

$$V_i = 0$$

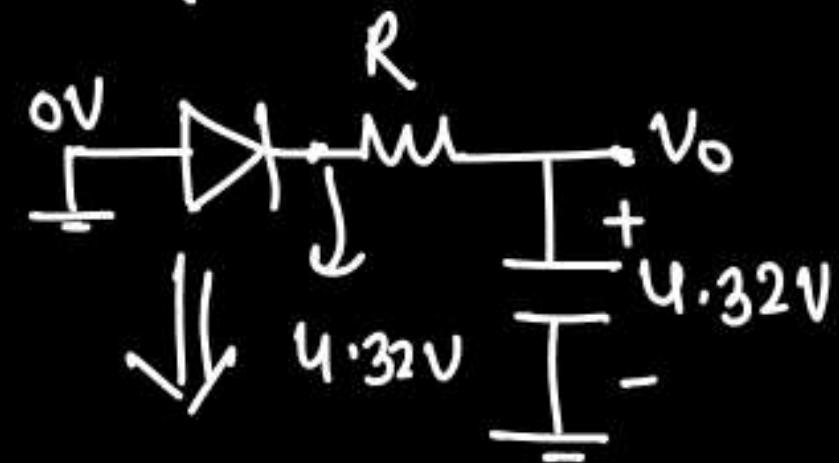


Diode off

$$V_o = 4.32V$$

=





2. Negative Clamper ckt :-

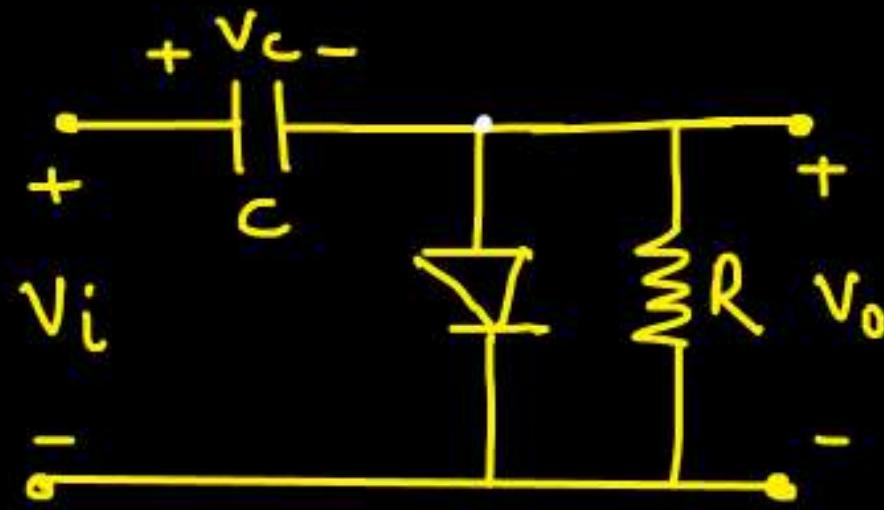

@ $t=0^+$

$$V_i > 0V, V_c(0^+) \approx 0V$$


⇒ diode turns ON

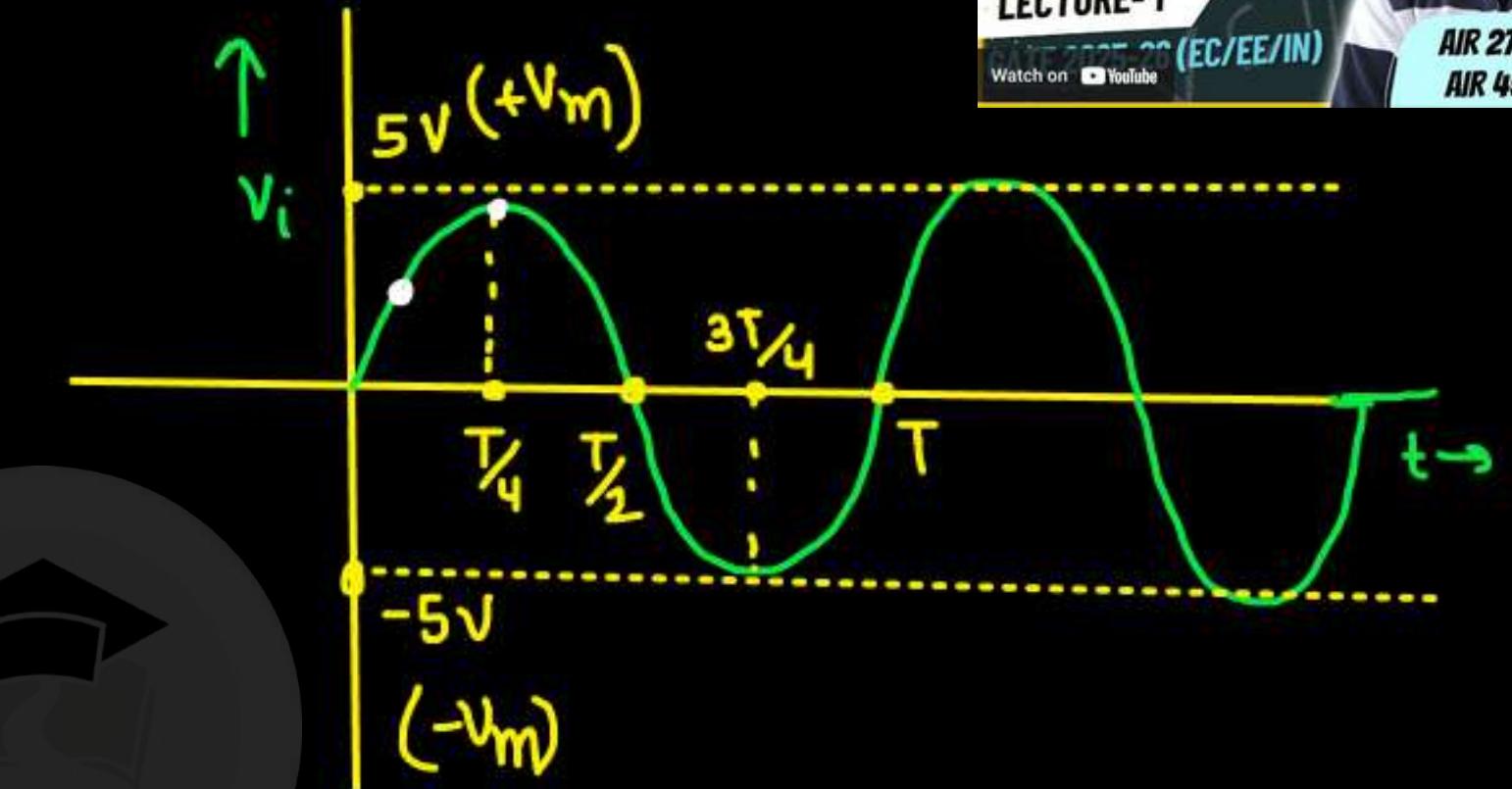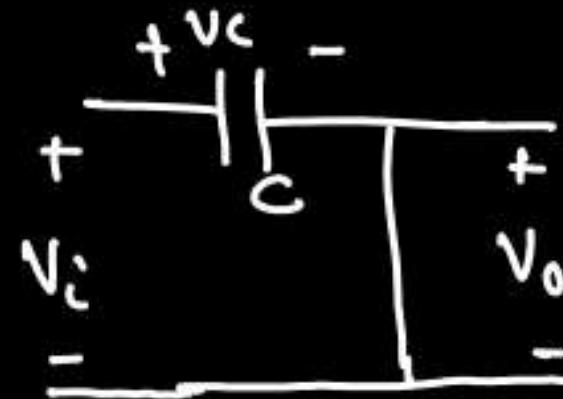

$$0 < t < T/4 \Rightarrow V_0 = 0V$$

$$V_c = V_i$$



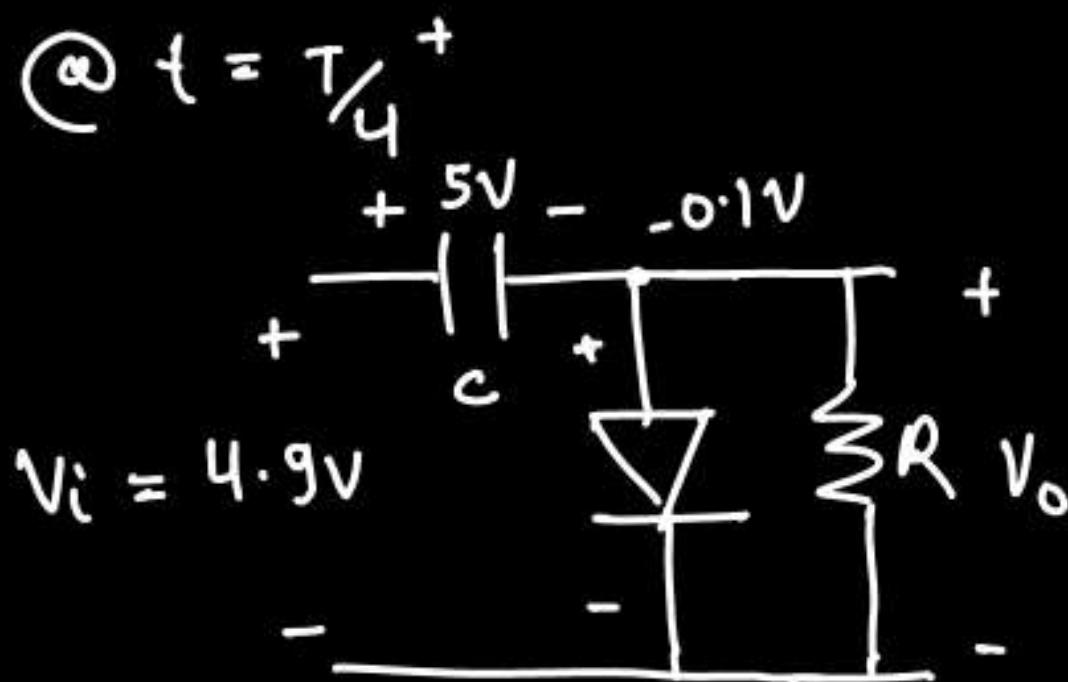

Diode turns off \Rightarrow cap. can neither charge nor discharge.
($RC \rightarrow$ very large)

for turning ON the diode;

$$V_i - 5V > 0 \Rightarrow V_i > 5V \Rightarrow \text{Not Possible}$$

\Downarrow
diode can never turn on



$V_c = 5v$ (always)

$$V_o = V_i - 5v$$

Basic Electronics
Basic Semiconductor Physics
LECTURE-1
Watch on YouTube

AIR 27 (ECE)
AIR 45 (IN)



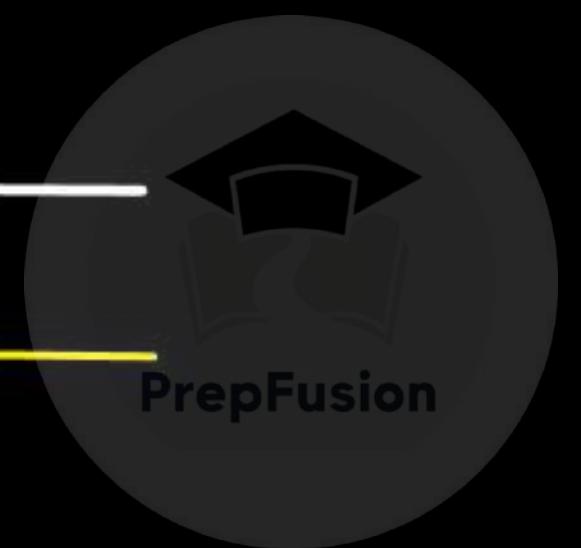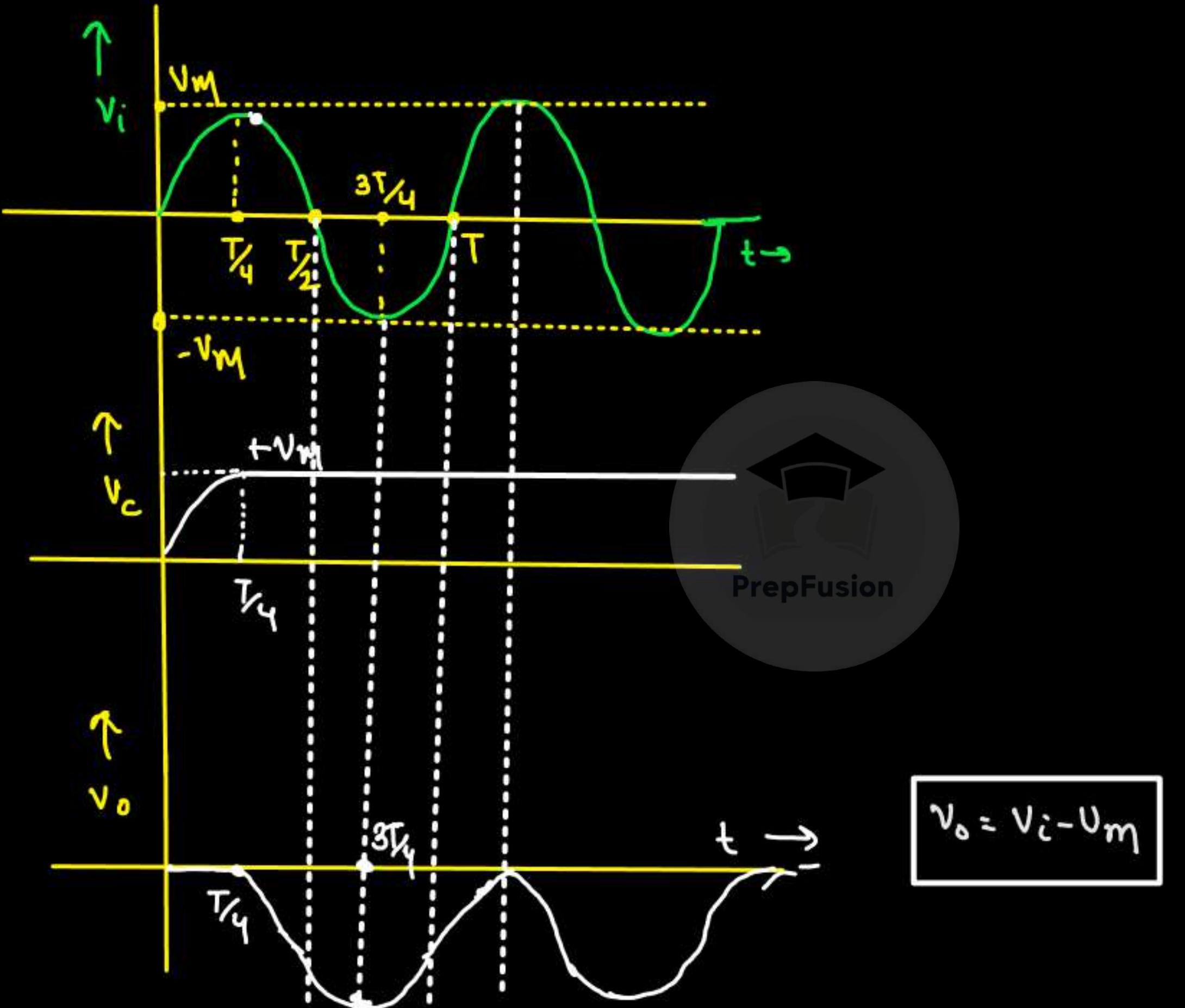



* How to solve clamper ckt in one step:-

- i) Turn on the diode nearest to the supply with desired max/min i/o voltage.
- ii) Find the cap. voltage (That will be its steady state voltage). Now you can write your steady state o/p.



PrepFusion

LECTURE-1

Watch on YouTube


AIR 27 (ECE)
AIR 45 (IN)

Eg. →

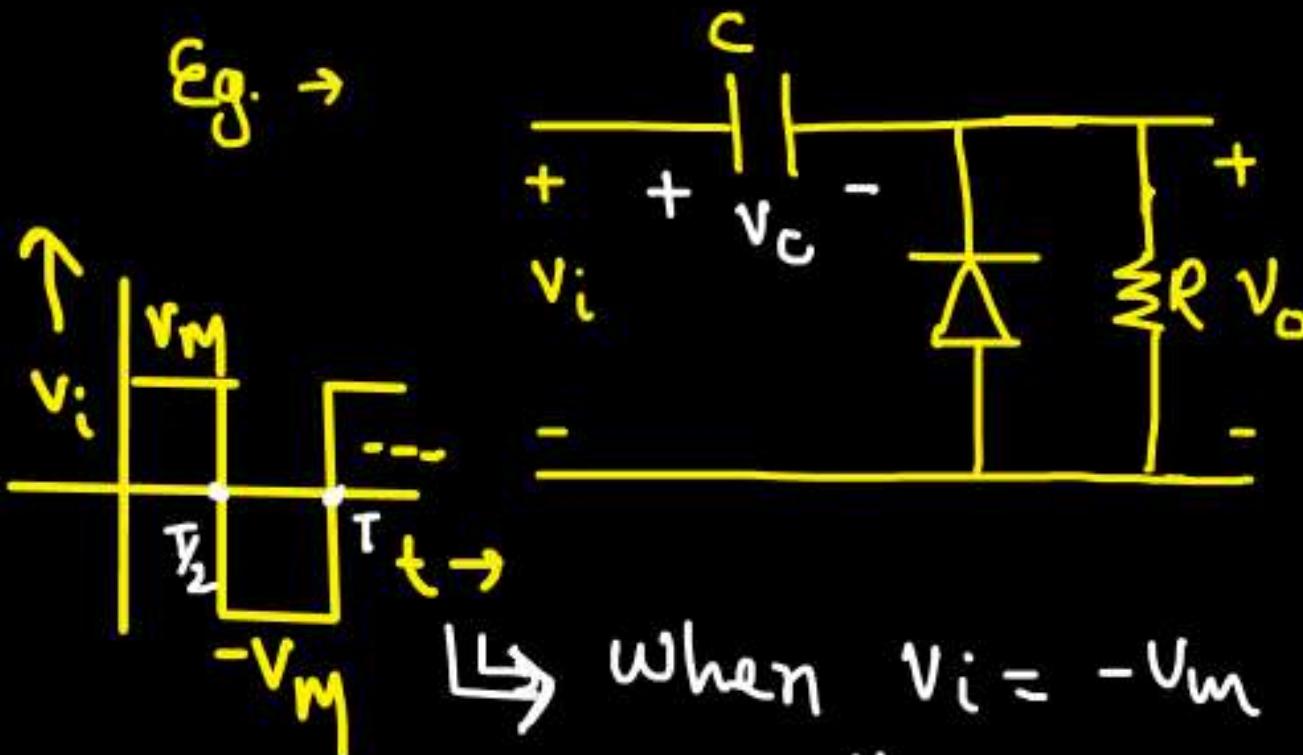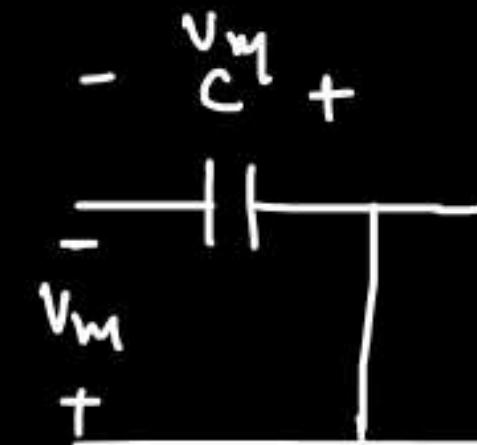Steady state v_o ? $RC \rightarrow$ very largeWhen $v_i = -v_m \Rightarrow$ diode turns ON

$$V_C = -v_m \rightarrow \text{steady state cap. voltage} =$$

⇒

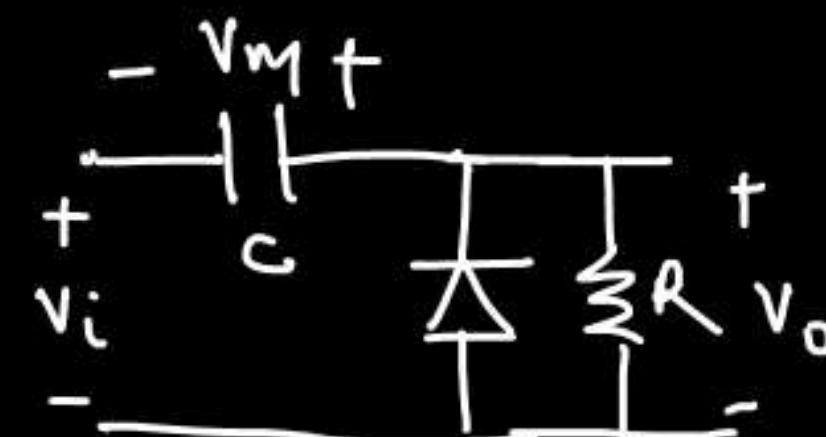


$$v_o = v_i + v_m$$

Exact Analysis:-

$$0 < t < T/2$$

$V_i = V_m \Rightarrow$ diode off

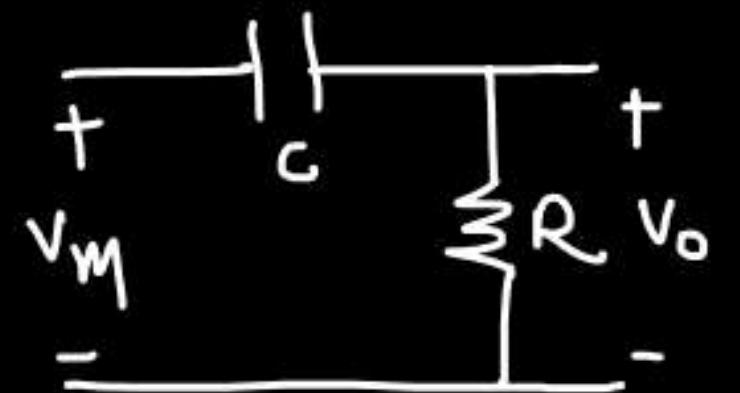


$$V_c = 0 \text{ V}$$

$$V_o = V_m$$

PrepFusion

$$T/2 < t < T$$

$V_i = -V_m \Rightarrow$ diode turns on

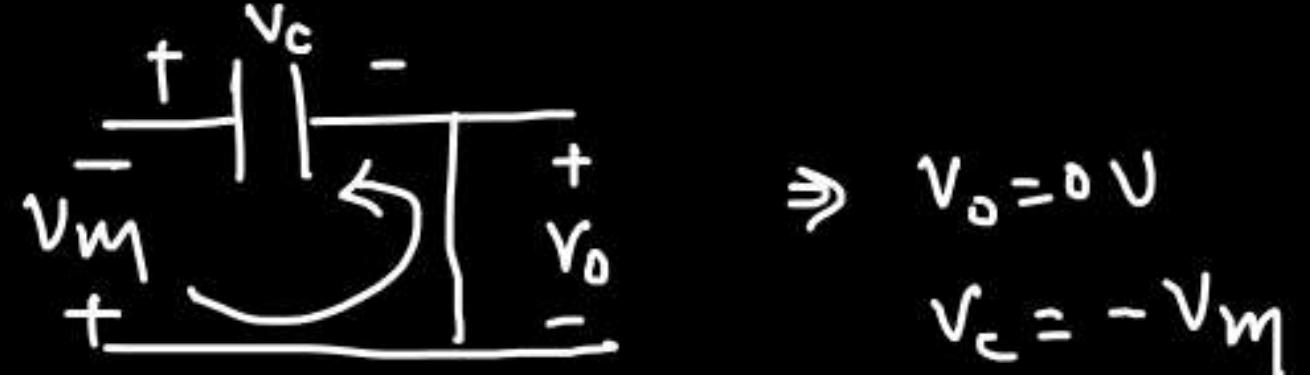


$$\Rightarrow V_o = 0 \text{ V}$$

$$V_c = -V_m$$

$$T < t < \frac{3T}{2}$$


$$V_i = +V_m$$

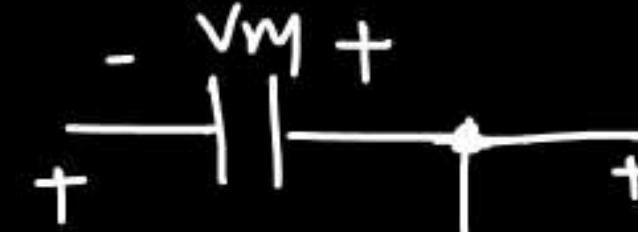

$$V_i = V_m$$

diode will be off

PrepFusion

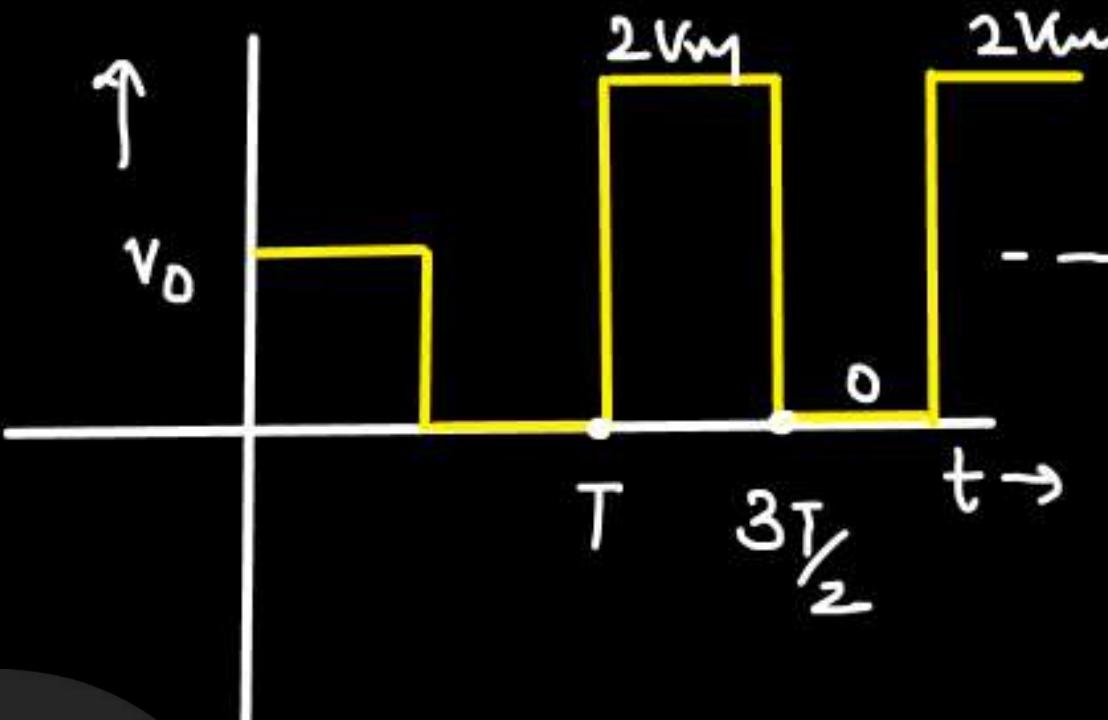


To turn on the diode $V_i + V_m < 0 \Rightarrow V_i < -V_m \Rightarrow$ NOT possible

diode will be always be off

$$\Rightarrow V_0 = V_i + V_m$$




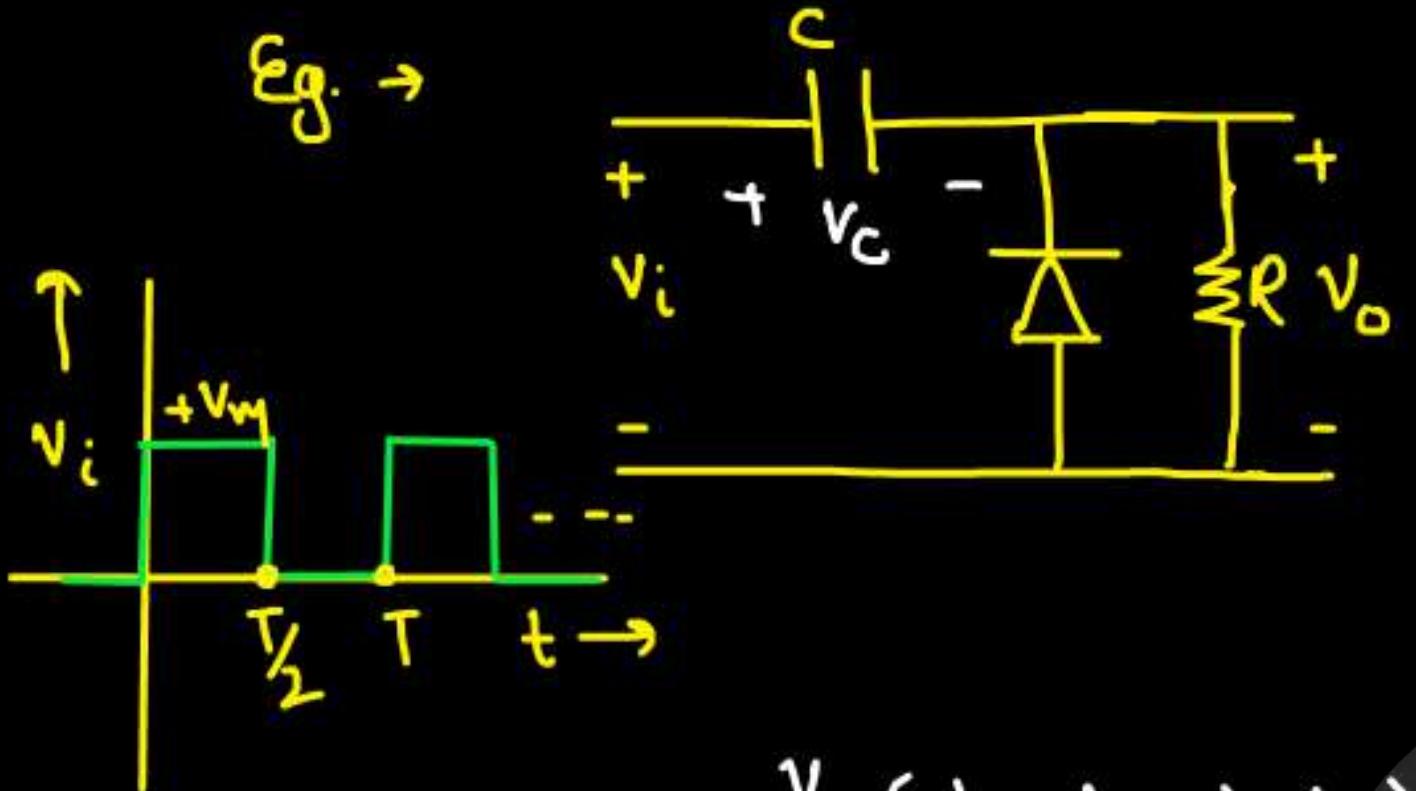


v_c (steady state) = 0 V

$$v_o = v_i$$

PrepFusion

Eg. →

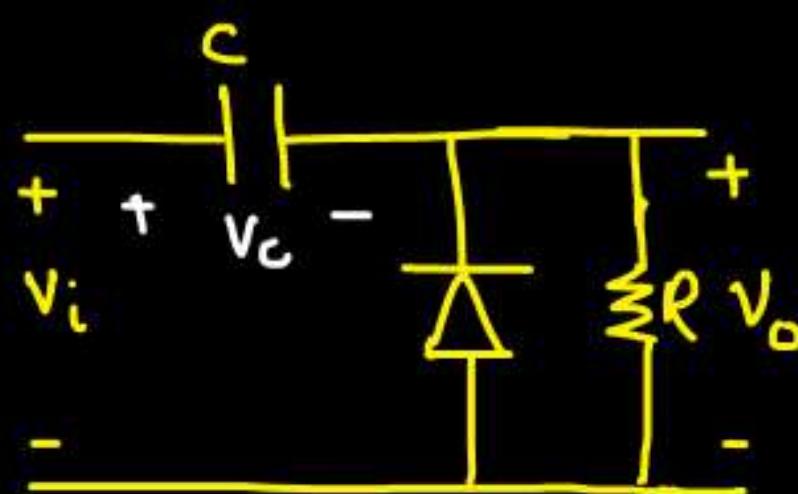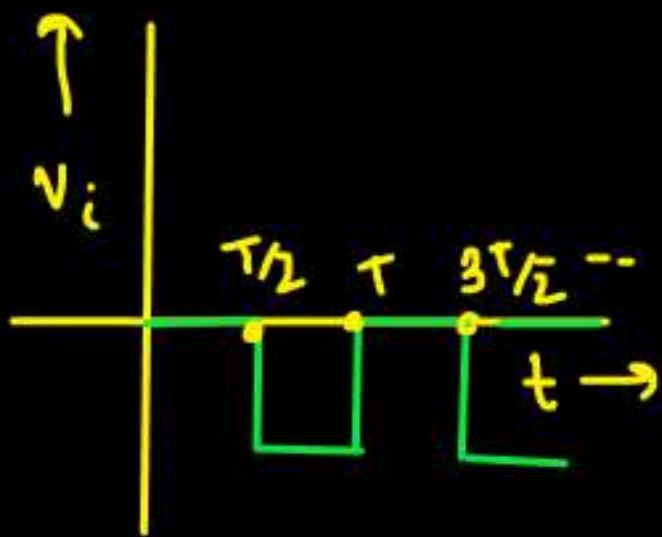


When $V_i = -V_m \Rightarrow$ diode turns on




$$\Rightarrow V_i - V_m \rightarrow V_o \Rightarrow V_o = V_i + V_m \rightarrow \text{Steady state of p-i}$$

Eg. →

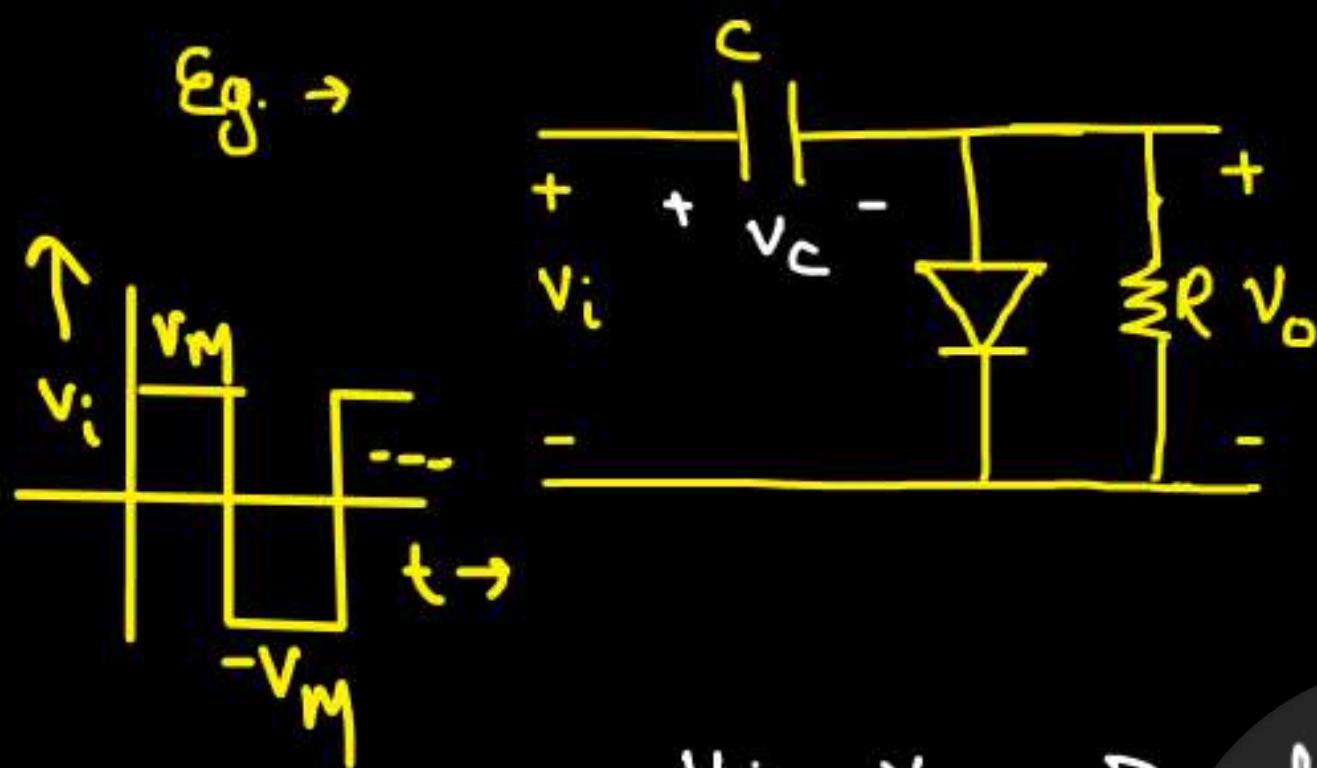


$v_i = v_m \Rightarrow$ diode turns on

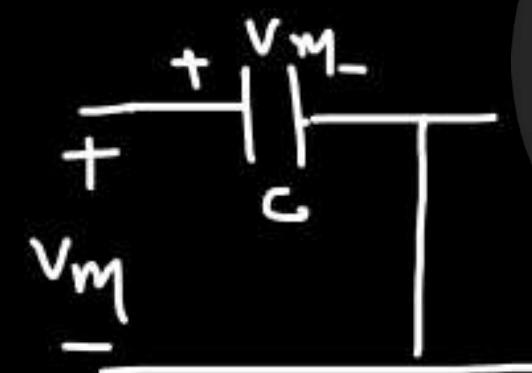



PrepFusion

$$v_c(s.s.) = +v_m =$$

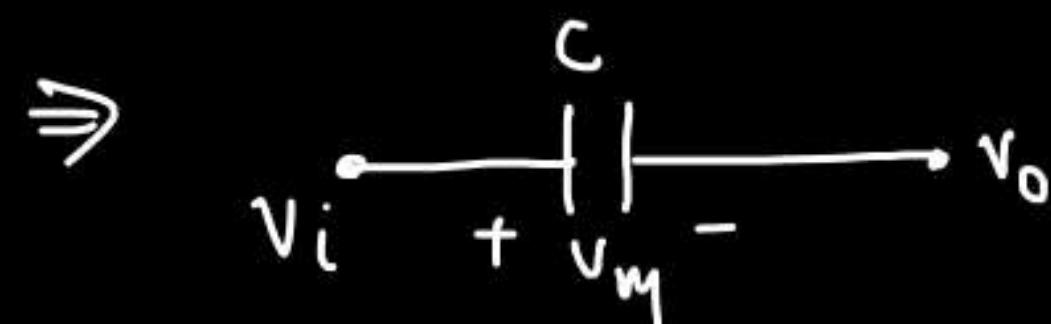


$$v_o(ss) = v_i - v_m$$

Eg. →

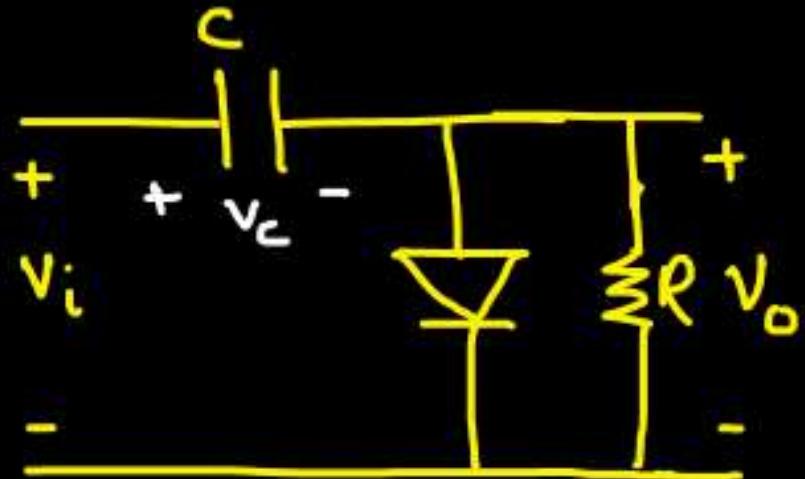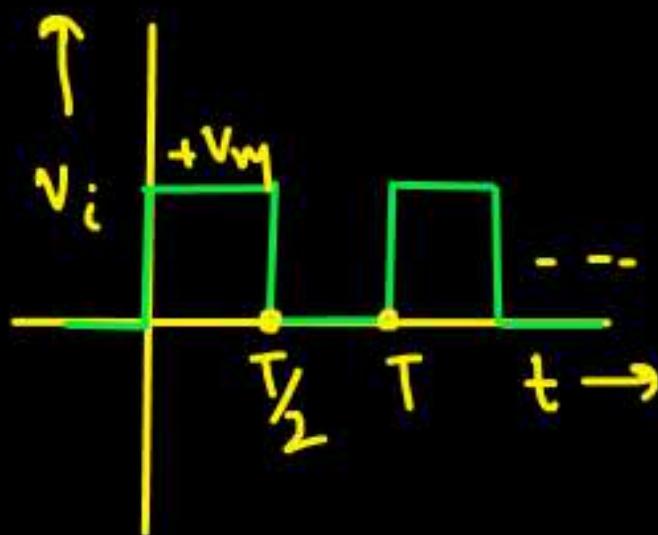


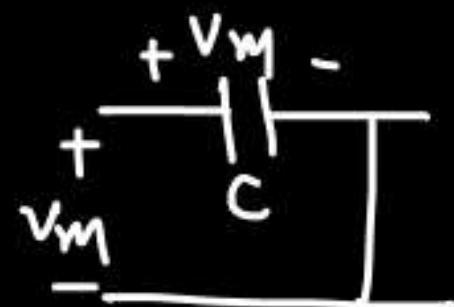$\Rightarrow V_i = V_m \Rightarrow$ diode turns ON



$V_C = V_m$


\Rightarrow

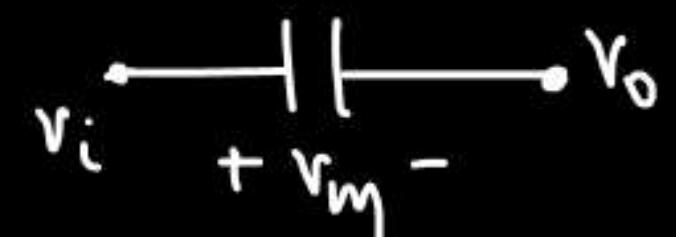

$$V_o = V_i - V_m$$



Eg. →

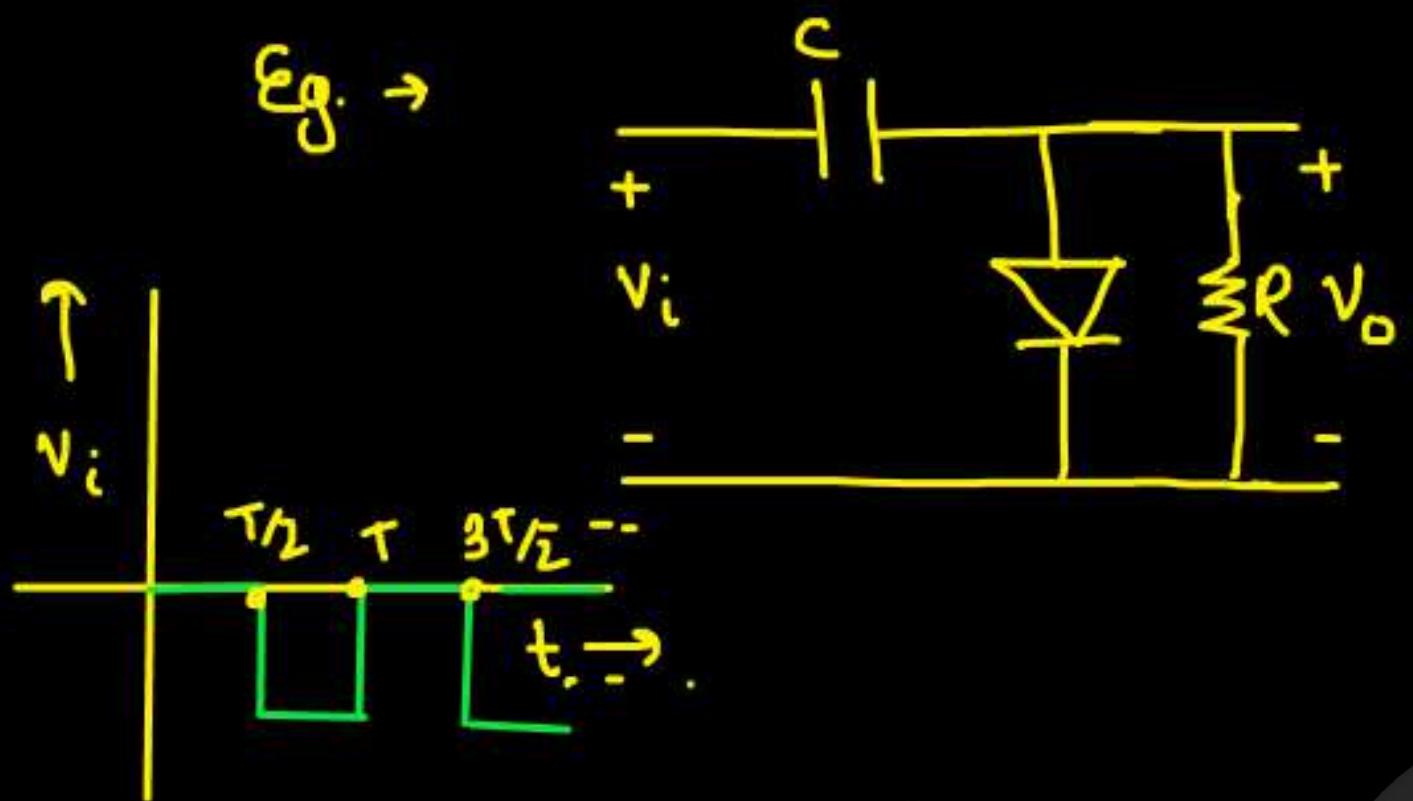


$$V_C (S-S) = 0V$$

$$V_O (S-S) = V_i$$




* Clamper circuit with the bias :-

Eg. \rightarrow

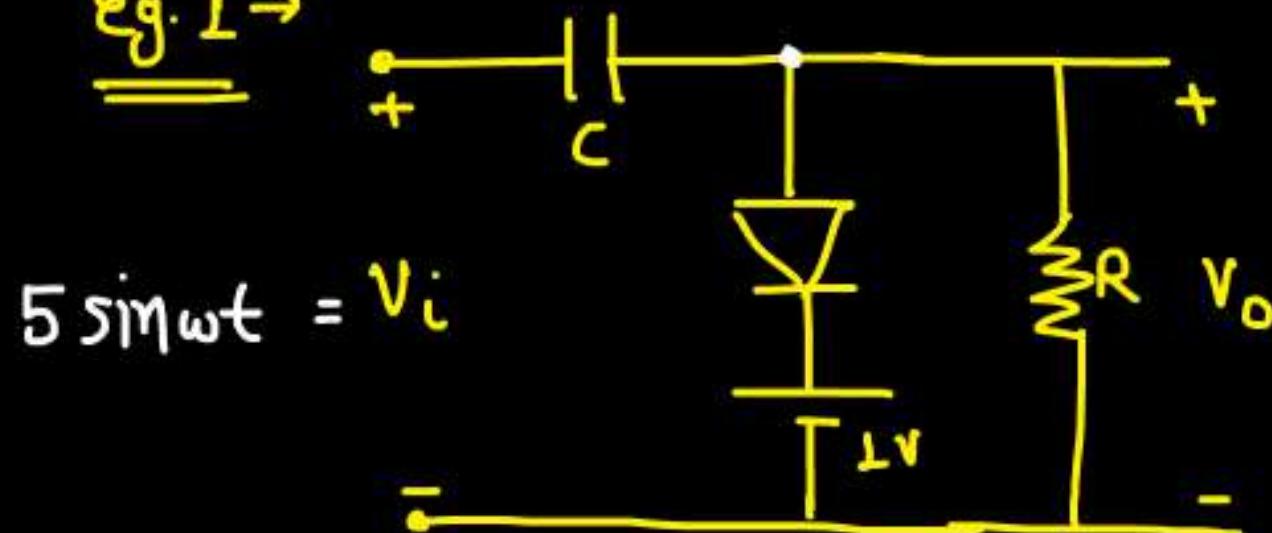

$$5 \sin \omega t = V_i$$

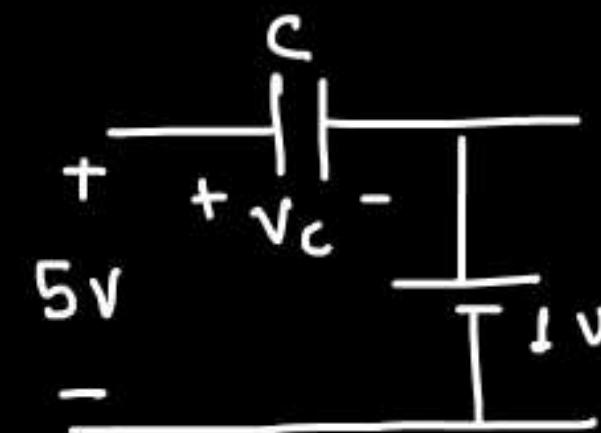\hookrightarrow when $V_i = +5V$ (max positive supply) \Rightarrow diode is ON



$$V_c (\text{ss}) = 5 - 1 = 4V$$



$$V_0 (\text{ss}) = V_i - 4$$


LECTURE-1


Watch on YouTube

 AIR 27 (ECE)
 AIR 45 (IN)

Exact Analysis:-

@ $t=0^+$

$v_i > 0 \Rightarrow$ diode turns ON

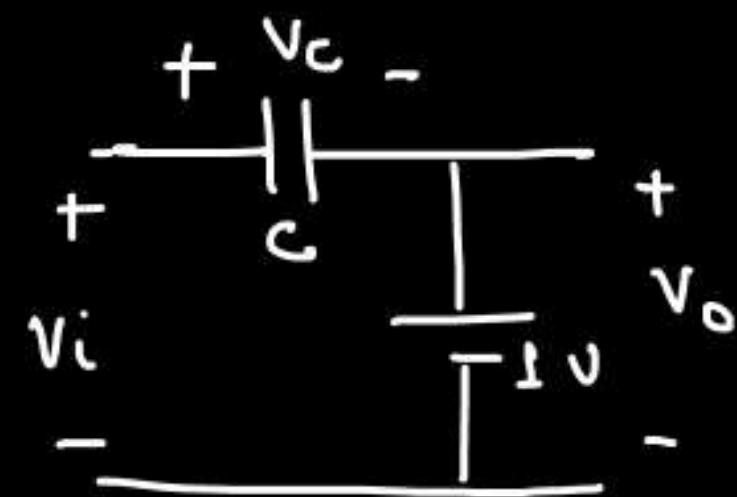

$0 < t < \frac{T}{4} \Rightarrow$ diode remain turned ON


$$v_i\left(\frac{T}{4}\right) = 5V$$

PrepFusion

$$v_c\left(\frac{T}{4}\right) = 4V$$

$$v_o\left(0 < t < \frac{T}{4}\right) = 1V$$

@ $t = T/4$

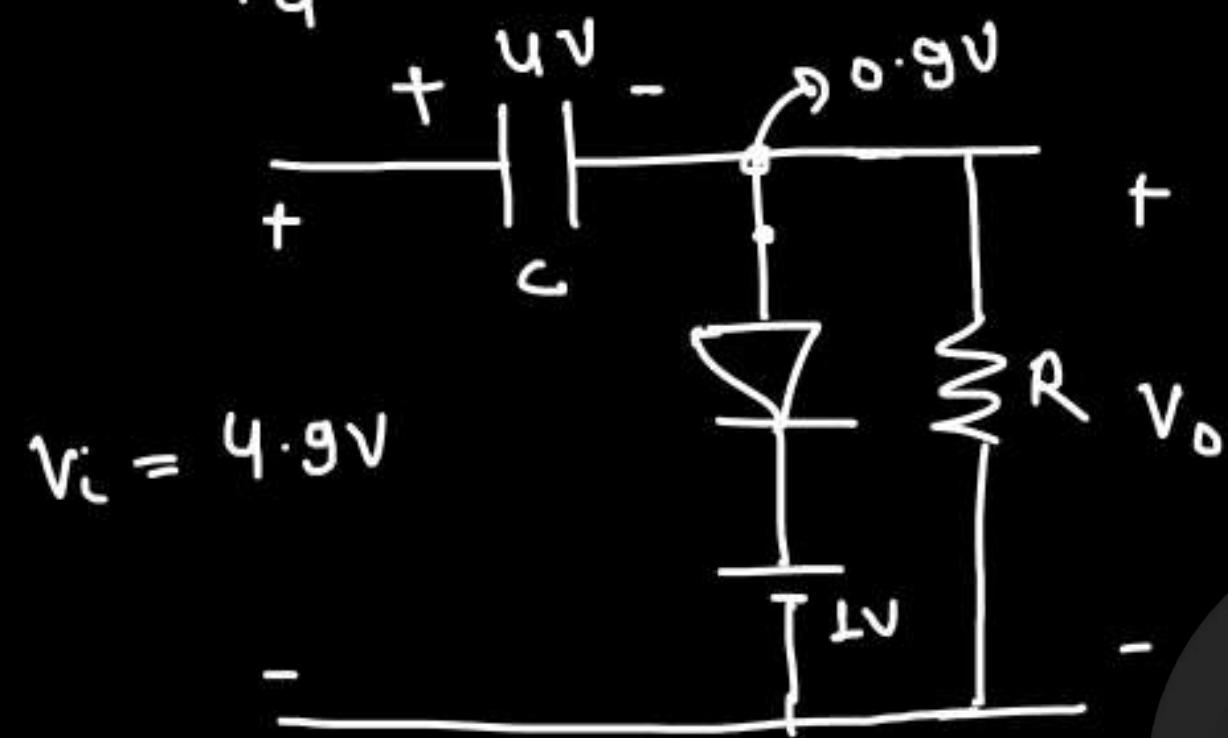

$$V_i (T/4) = 4.9V \{ \text{let} \}$$



diode turns off

$$\boxed{V_o = V_i - 4V}$$

To turn it on

$$V_i - 4 > 1$$



$$V_i > 5$$




Not possible

\Rightarrow diode will always
be off.



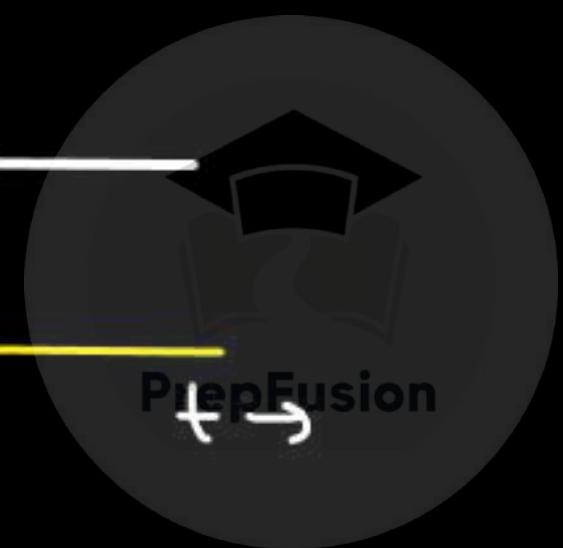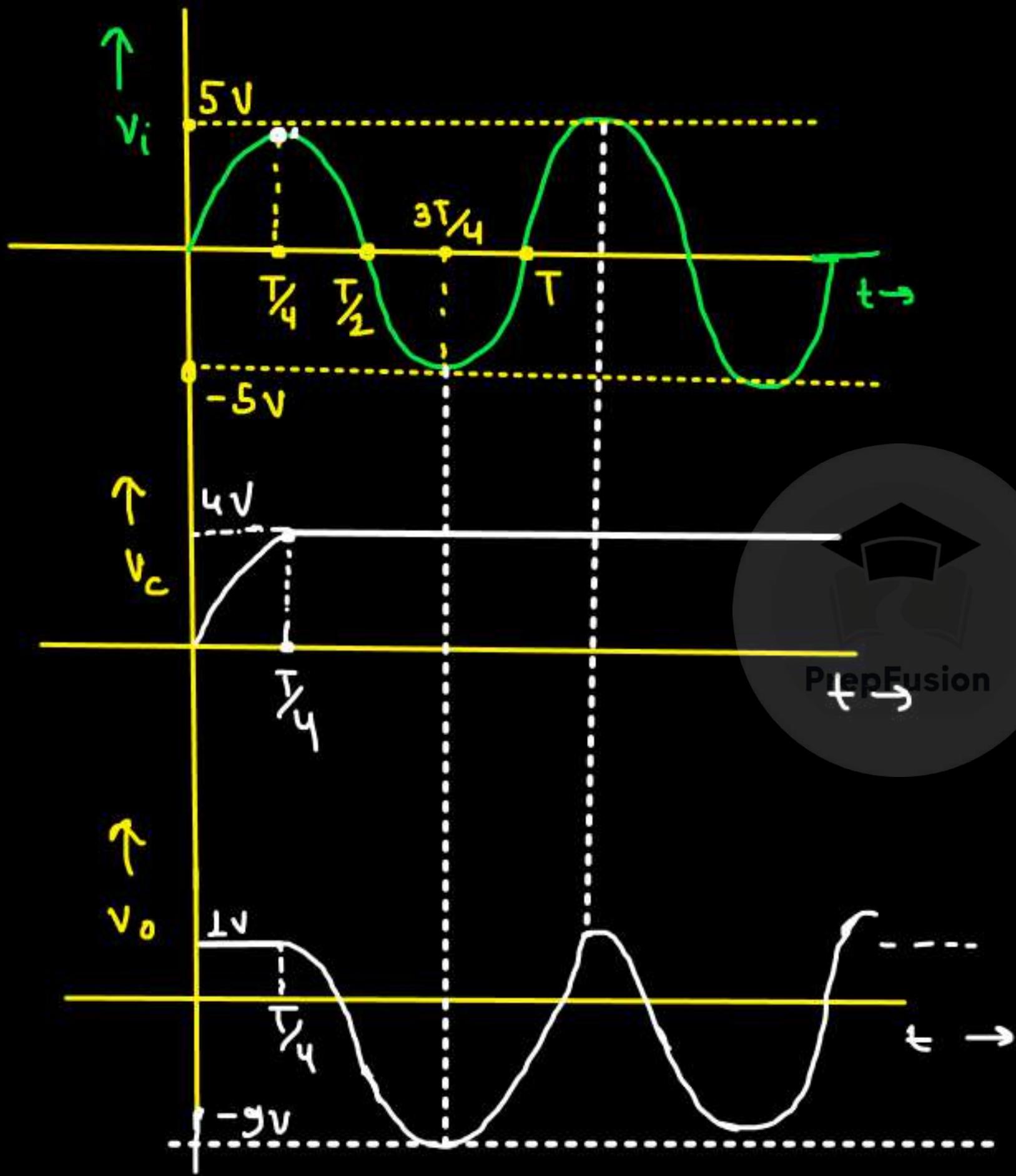


Eg. 2 →

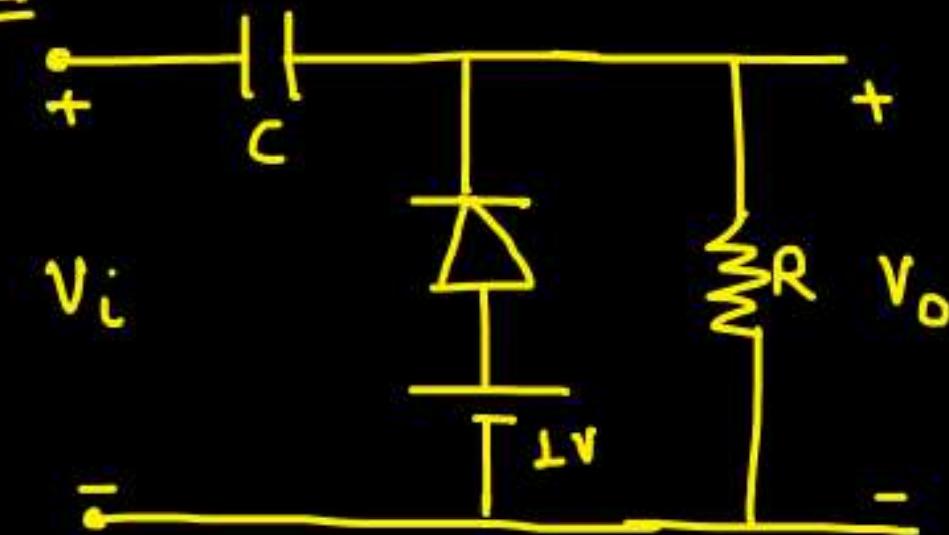

Find steady state V_o ?


$$V_i = 5 \sin \omega t$$

↳ $V_i = -5V \Rightarrow$ diode is ON

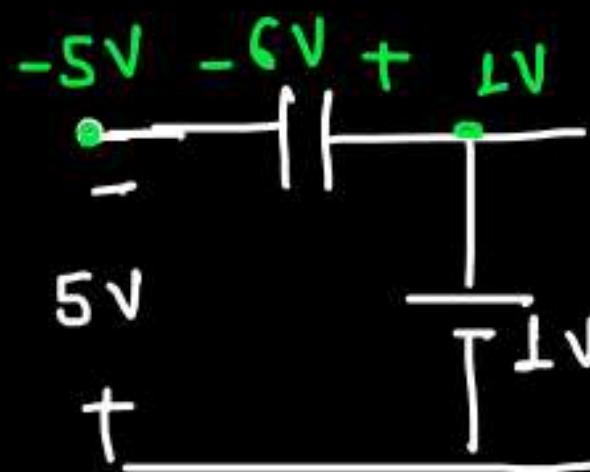

$$V_o(\text{c.s.}) = 5 \sin \omega t + 6$$

Eg. 3 →


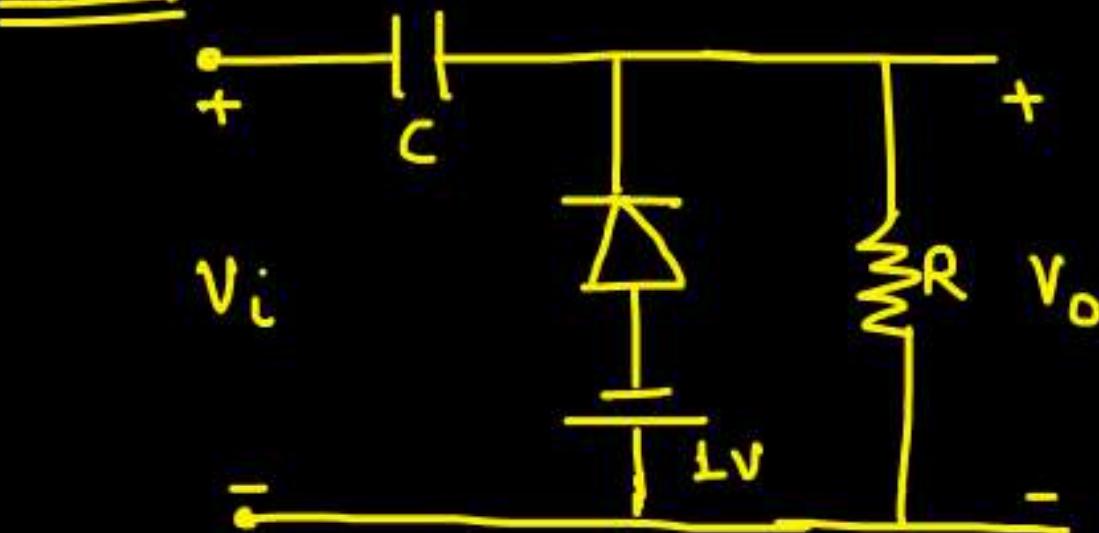


Find steady state V_o ?

$$V_i = 5 \sin \omega t$$

→


$V_L = -5V \Rightarrow$ diode is on

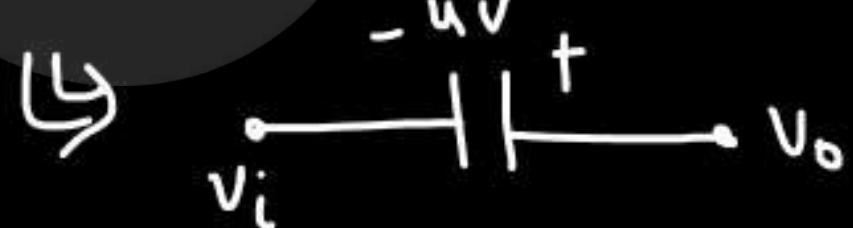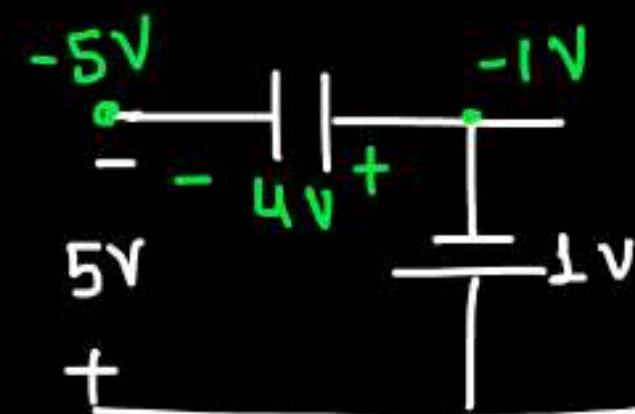

$$V_o = V_L + 4V$$



$$V_o = 5 \sin \omega t + 4$$

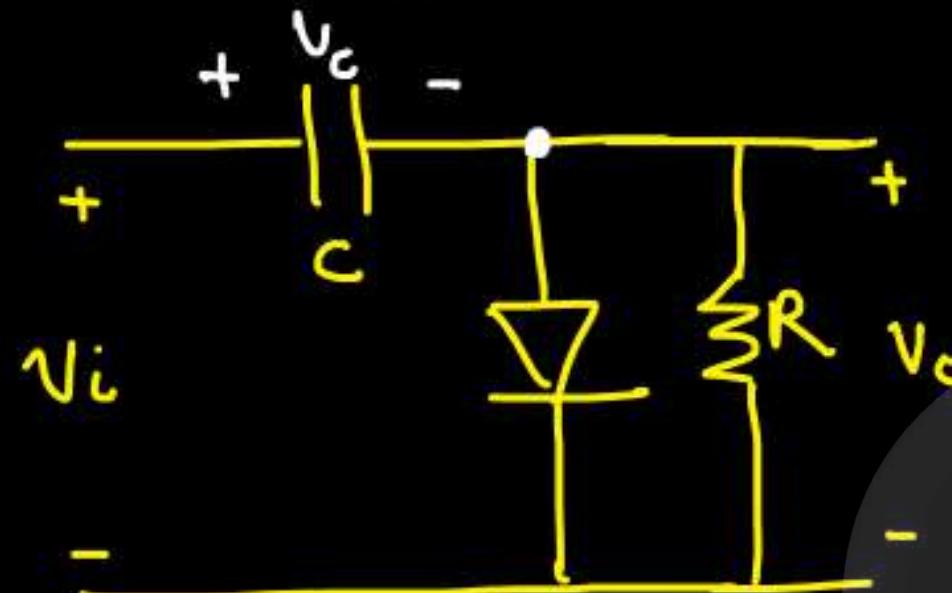Q. Find steady state o/p. Draw V_C waveform.
 $RC \rightarrow$ very large






$\rightarrow V_C = 7V$ (max^m positive supply)

↓
diode is ON

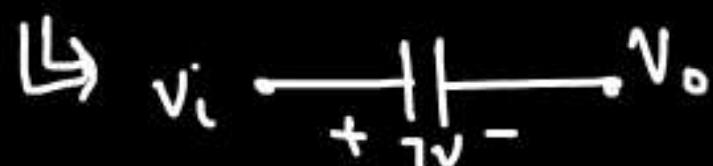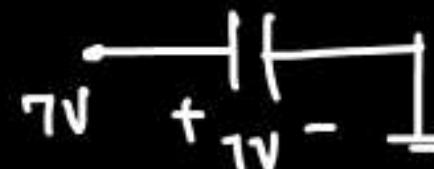

$V_o = V_i - 7V$ → steady state o/p

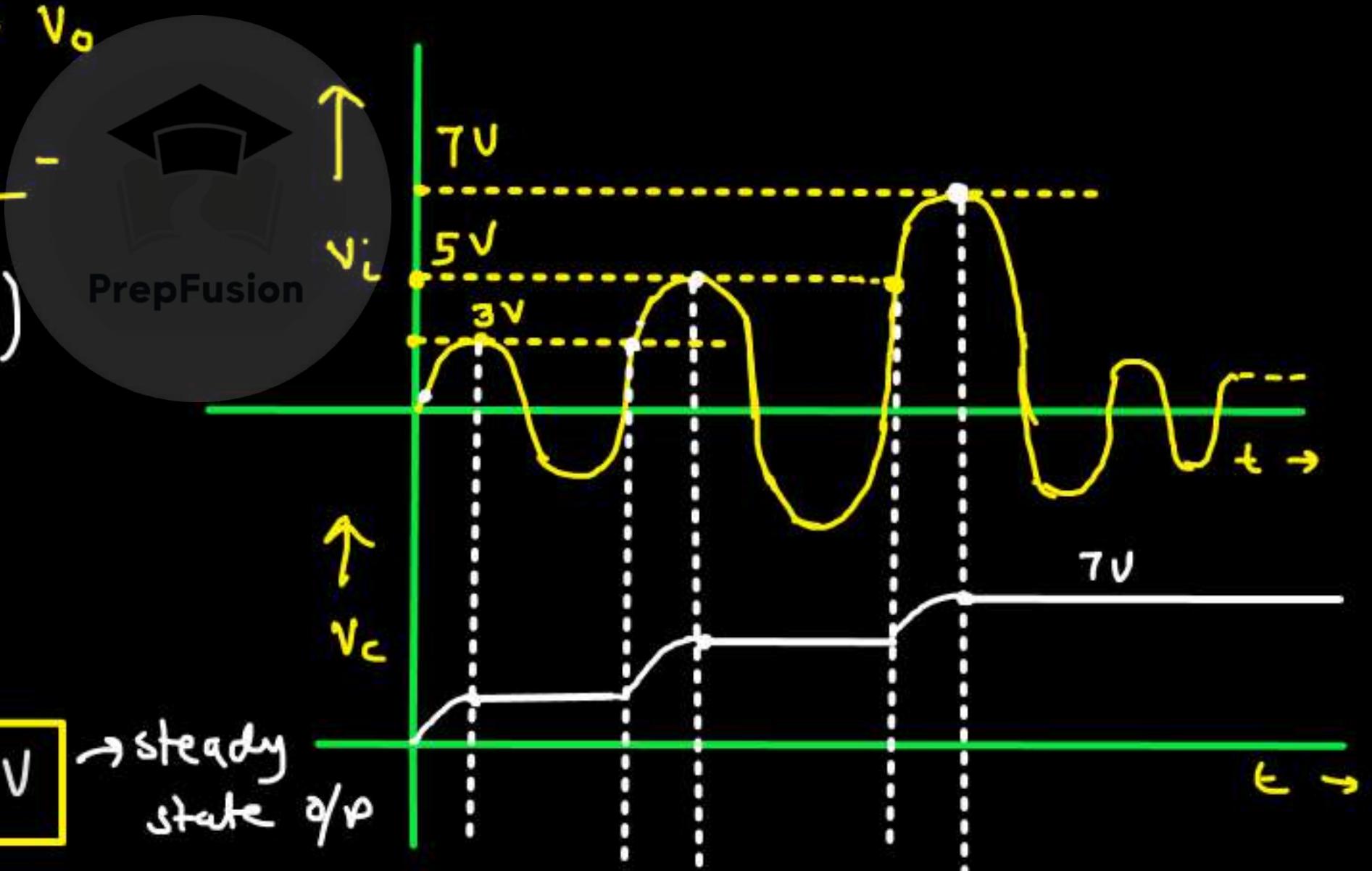

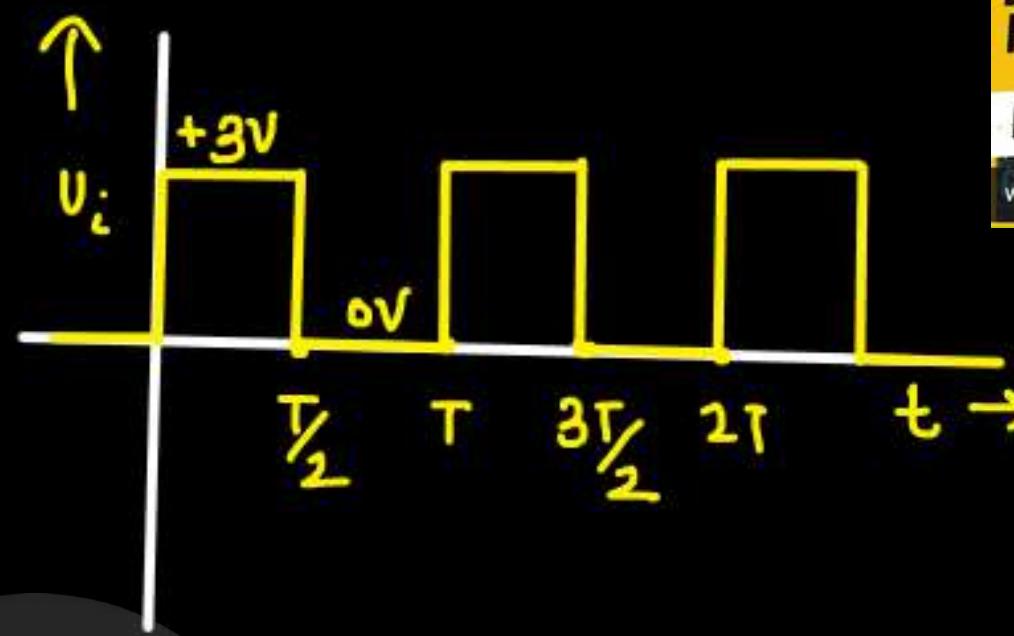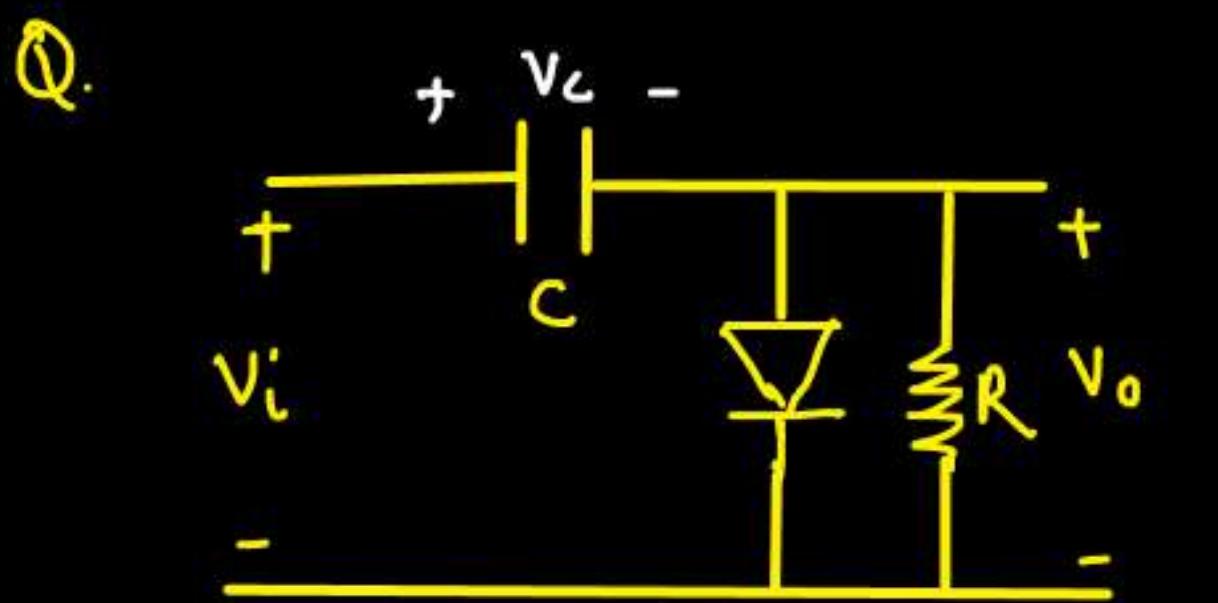



Given, $T = 2RC$

Find V_o @ $t = \frac{4\pi T}{4}$


$$0 < t < \frac{T}{2}$$

$\Rightarrow V_c = 3V \Rightarrow$ Diode turns ON

$$V_c = 3V, V_o = 0V$$

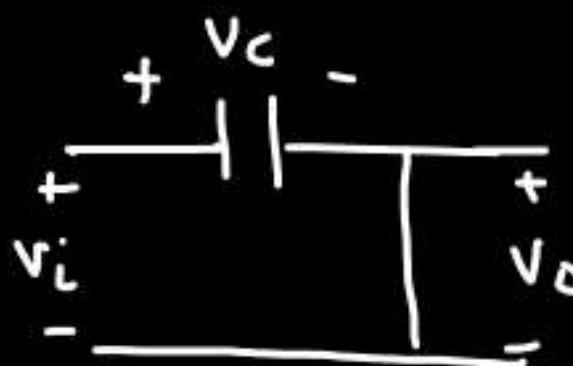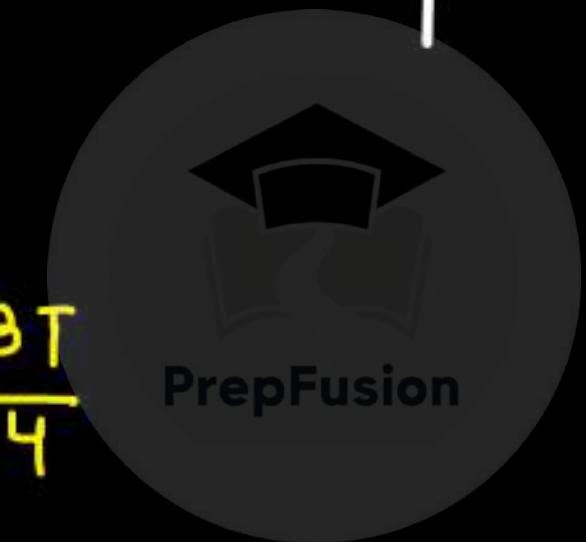

LECTURE-1

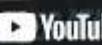
 Watch on  YouTube

AIR 27 (ECE)

AIR 45 (IN)

 $\text{@ } t = \frac{T}{2}^+$
 $\frac{T}{2} < t < T$

$V_i = 0V$

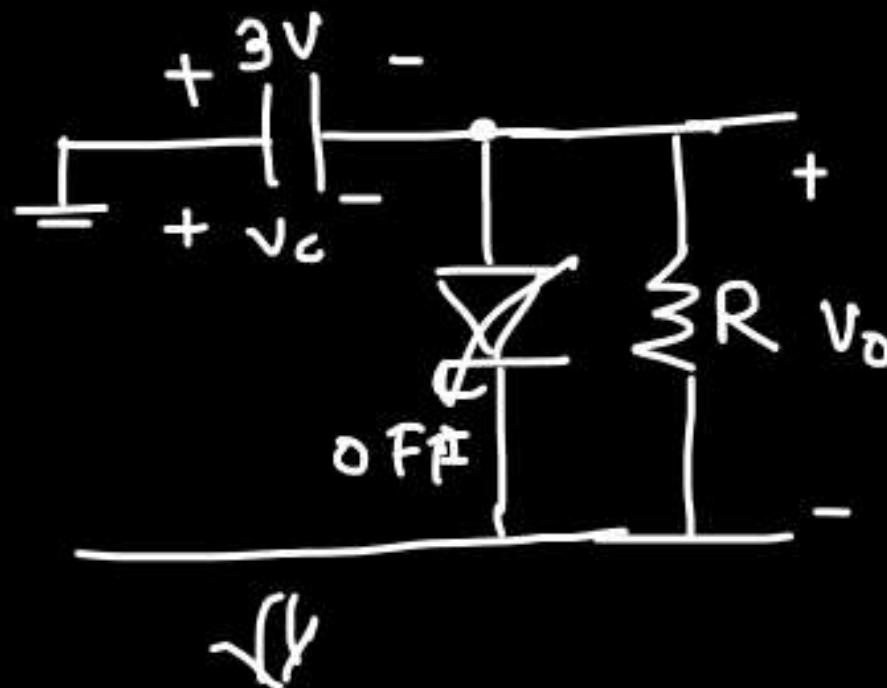
 \Rightarrow Diode turns ON

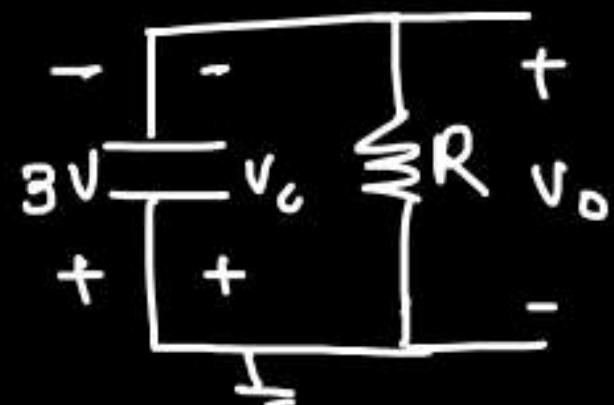

$V_o\left(\frac{T}{2}^+\right) = -3V$

$V_o = -V_c$

$V_o = -3 e^{-\left(t - \frac{T}{2}\right)/RC}$

$V_o(T) = -3 e^{-\frac{T}{2RC}} \quad \{ T = 2RC \}$

$= -3 e^{-1} = -1.1V$




$$V_o(T) = -1.1V$$

$$V_c(T) = 1.1V$$

@ $t = T^+$

$$V_i = 3V$$

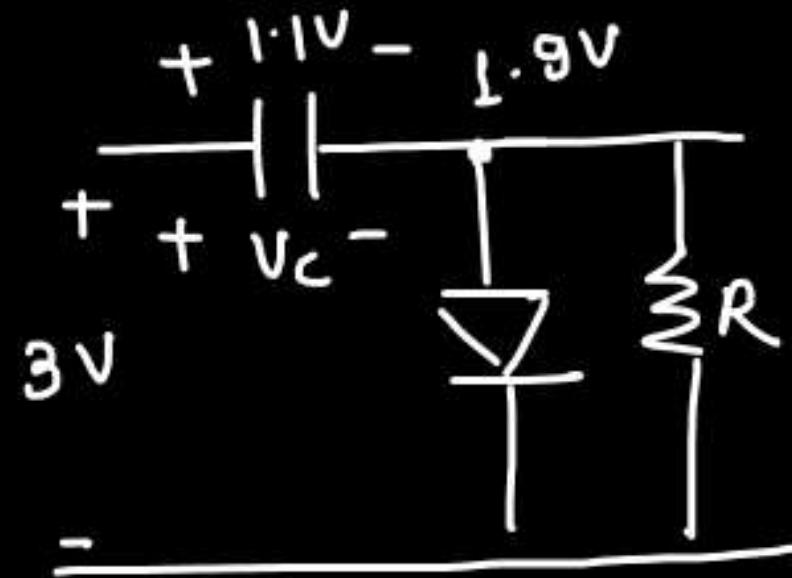




⇒ diode

Turns ON =

$$T < t < \frac{3T}{2}$$


$$V_c = 3V$$

$$V_o = 0V$$

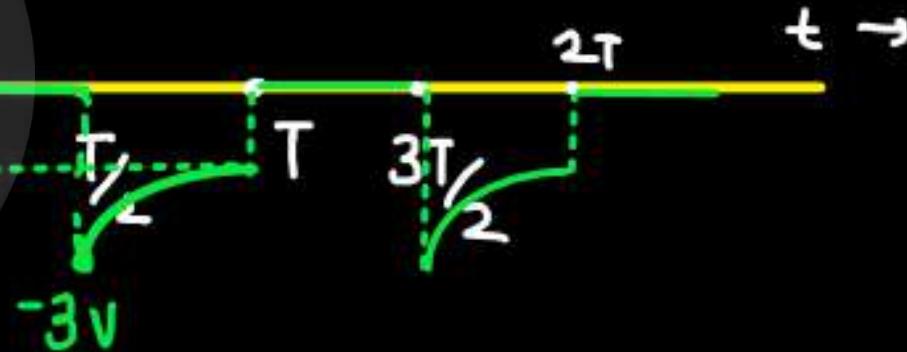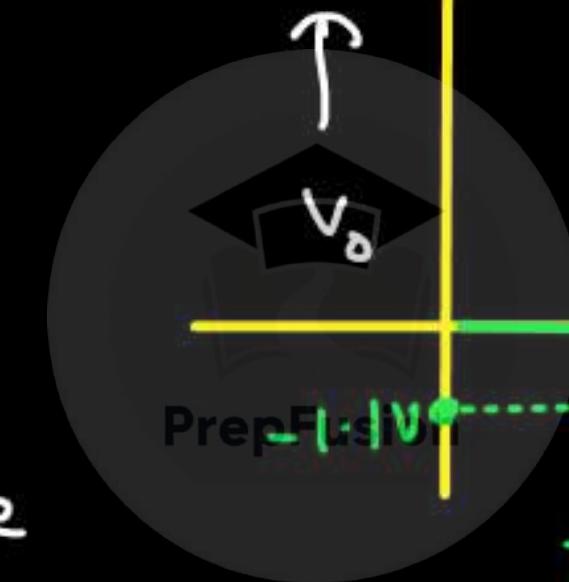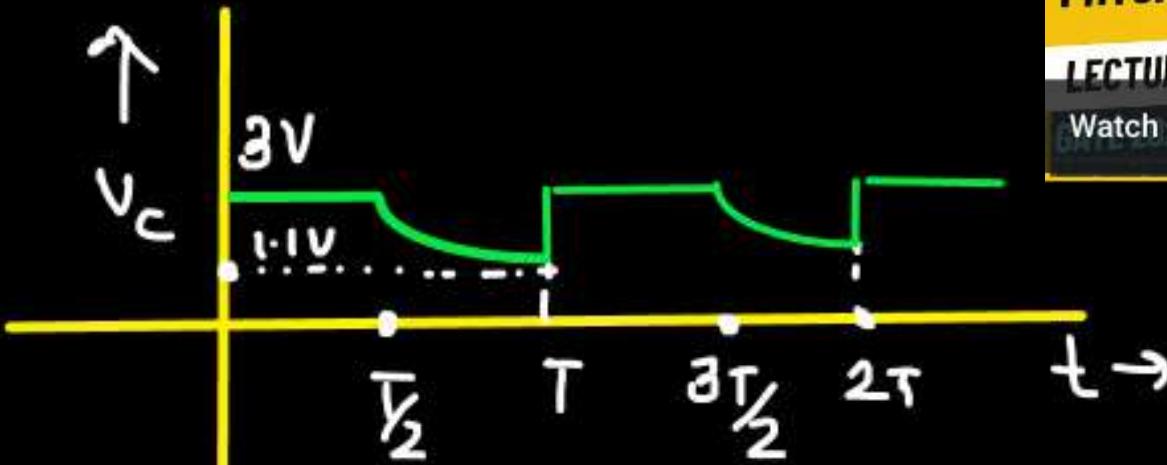

@ $t = \frac{3T}{2}^+$ ⇒ diode off

↓
cap. discharges

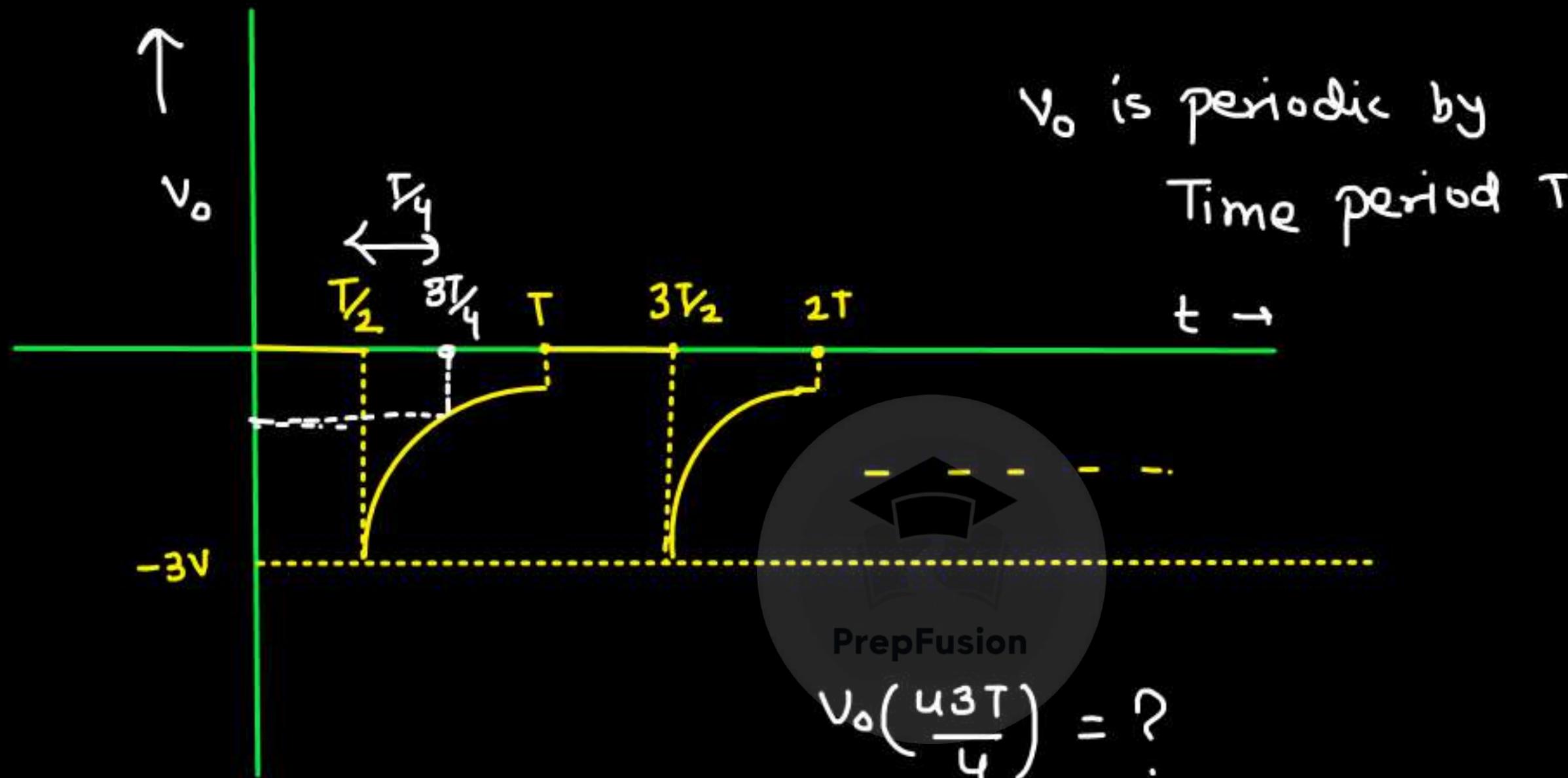

$$V_o\left[\frac{43T}{4}\right] = V_o\left[10T + \frac{3T}{4}\right] = V_o\left[\frac{3T}{4}\right]$$

$$V_o(t) = -3 e^{-\frac{(t - T/2)}{RC}}$$



$$v_o(3T_4) = -3 e^{-(3T_4 - T/2)/RC}$$

$$= -3 e^{-T/4RC} \quad T = 2RC$$

$$= -3 e^{-2RC/4RC}$$

$$= -3 e^{-V_2}$$



$$v_o(3T_4) = -1.8V \underset{\text{PrepFusion}}{=} v_o\left(\frac{43T}{4}\right)$$

$$v_o\left(\frac{43T}{4}\right) = -1.8V$$

Peak detector circuits:-

- ↳ Detects either the +ve peak or -ve peak

* Positive peak detector circuit

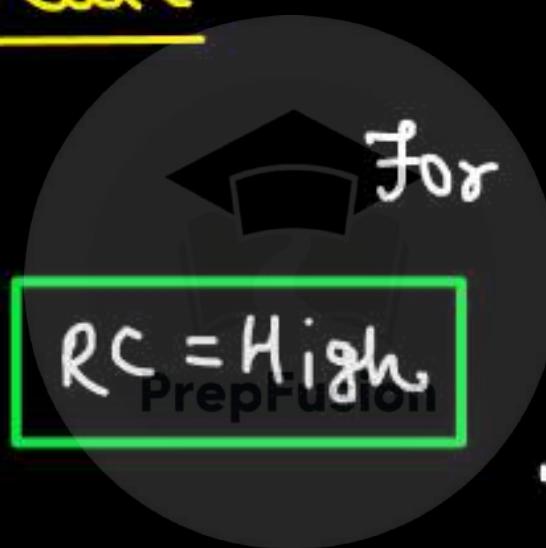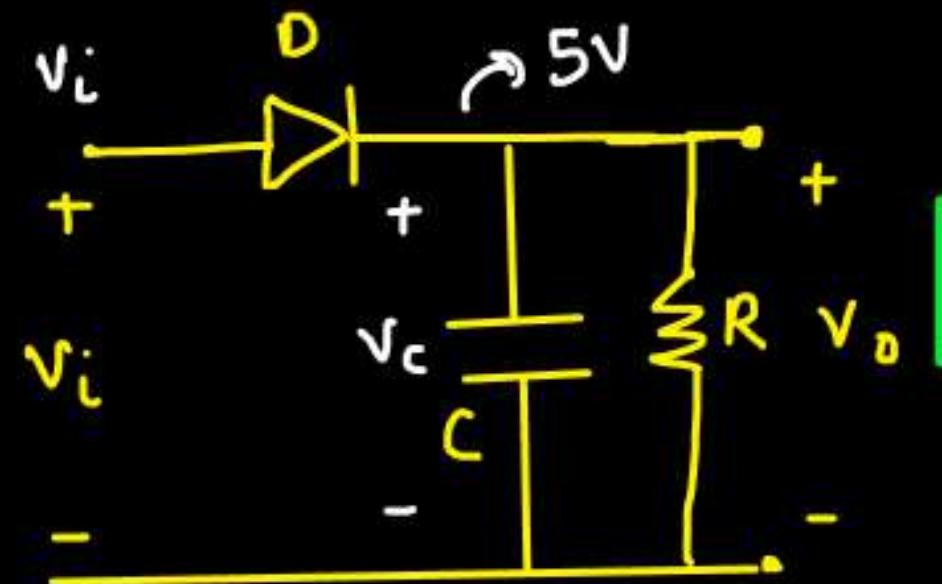

for $t=0^+$ $\Rightarrow V_i > 0V$

\Rightarrow Diode will be ON

$$V_c = V_i \quad \{0 < t < T/4\}$$

@ $t = T/4^+$


$$V_i = 4.9V \{ \text{let} \}, \quad V_c = 5V$$

To turn on the diode,
 $V_i > 5V \Rightarrow$ Not Possible
 \Rightarrow Diode will always be OFF

\Rightarrow Diode will be OFF $\Rightarrow V_c = 5V$

@ $t = T_4^+$

diode is off

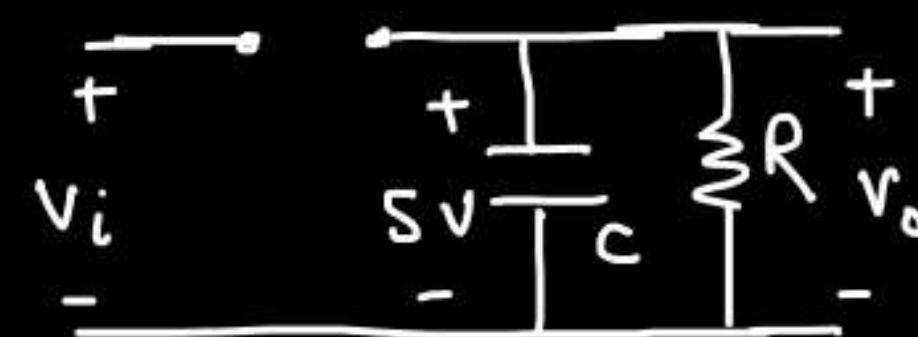


The cap. will not discharge
because RC value is very large

$$V_c (\text{s.s.}) = 5 \text{V}$$

PrepFusion



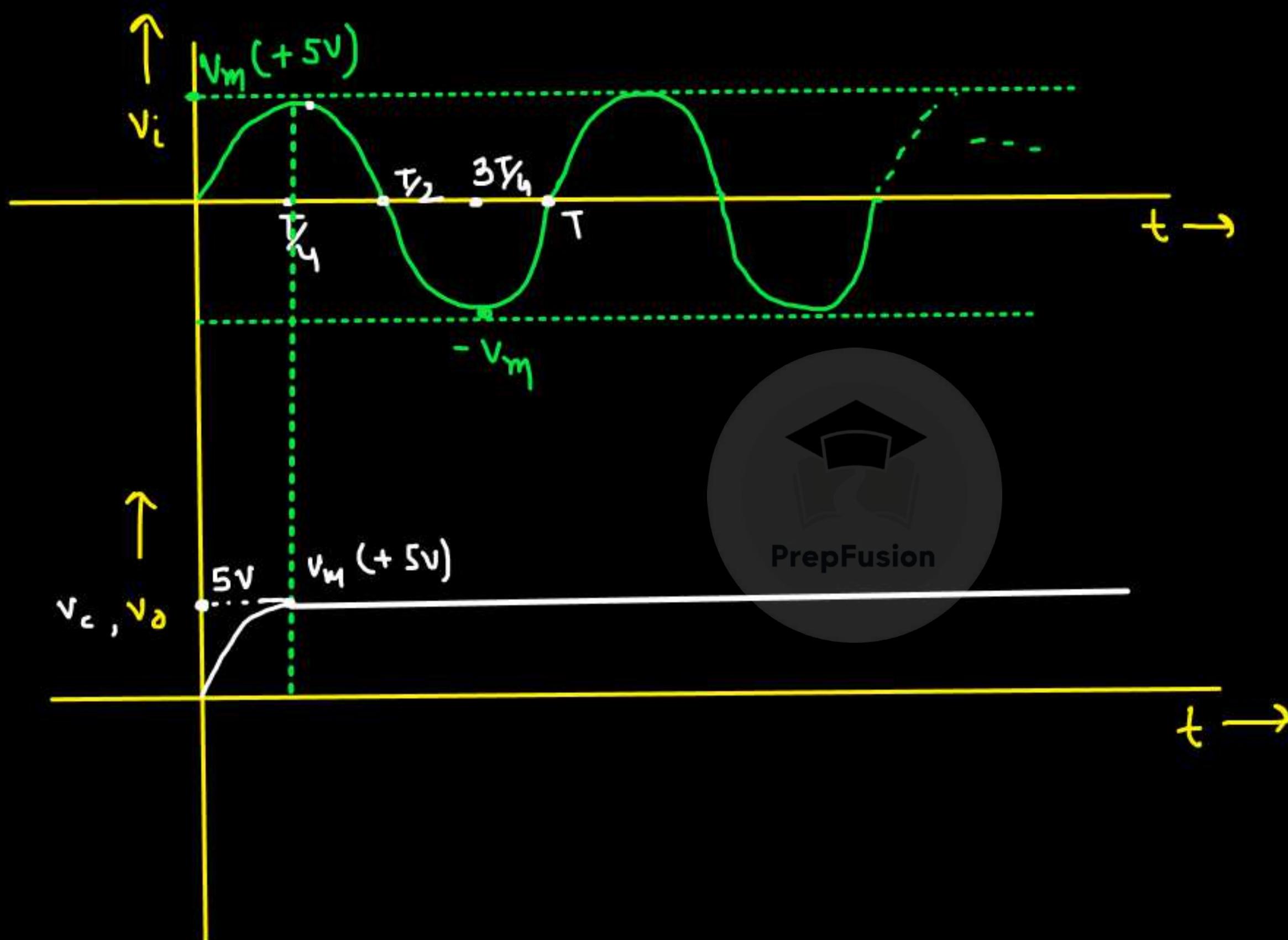


LECTURE-1

 Watch on  YouTube

 AIR 27 (ECE)
 AIR 45 (IN)

* Negative Peak Detector Circuit:-

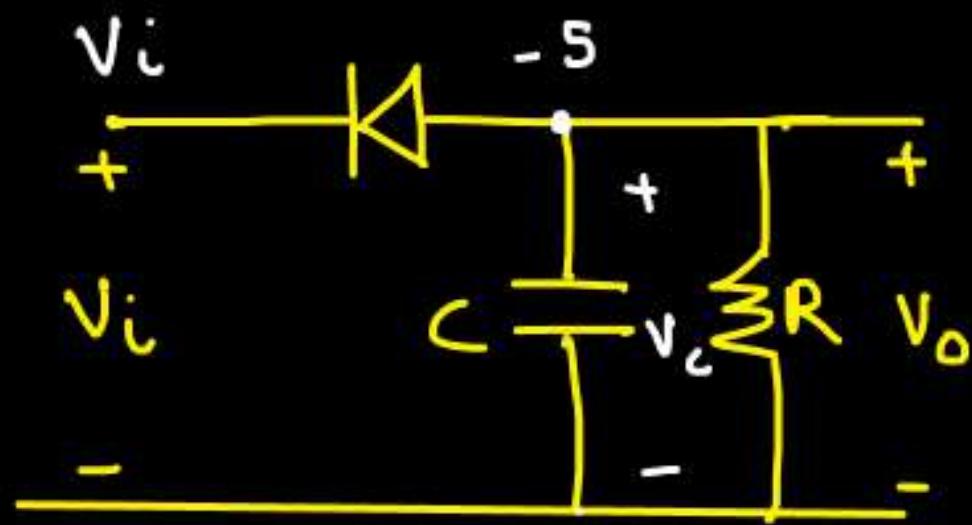

for $0 < t < T_2^+$ $\Rightarrow V_i = +ve \Rightarrow$ diode is off

$$V_o = V_c = 0V \quad \{ 0 < t < T_2^+ \}$$

@ $t = T_2^+$ $\Rightarrow V_i < 0 \Rightarrow$ diode will turn on =

$$V_c = V_i \quad \{ T_2^+ < t < 3T_4 \}$$

@ $t = \frac{3T}{4}^+$

$$V_L = -4.9V \quad \{ \text{Let} \}, \quad V_C = -5V$$

⇒ diode is off

To turn on the diode, $V_L < -5V$



NOT Possible




diode will always be off

$$V_C = -5V$$





→ steady state

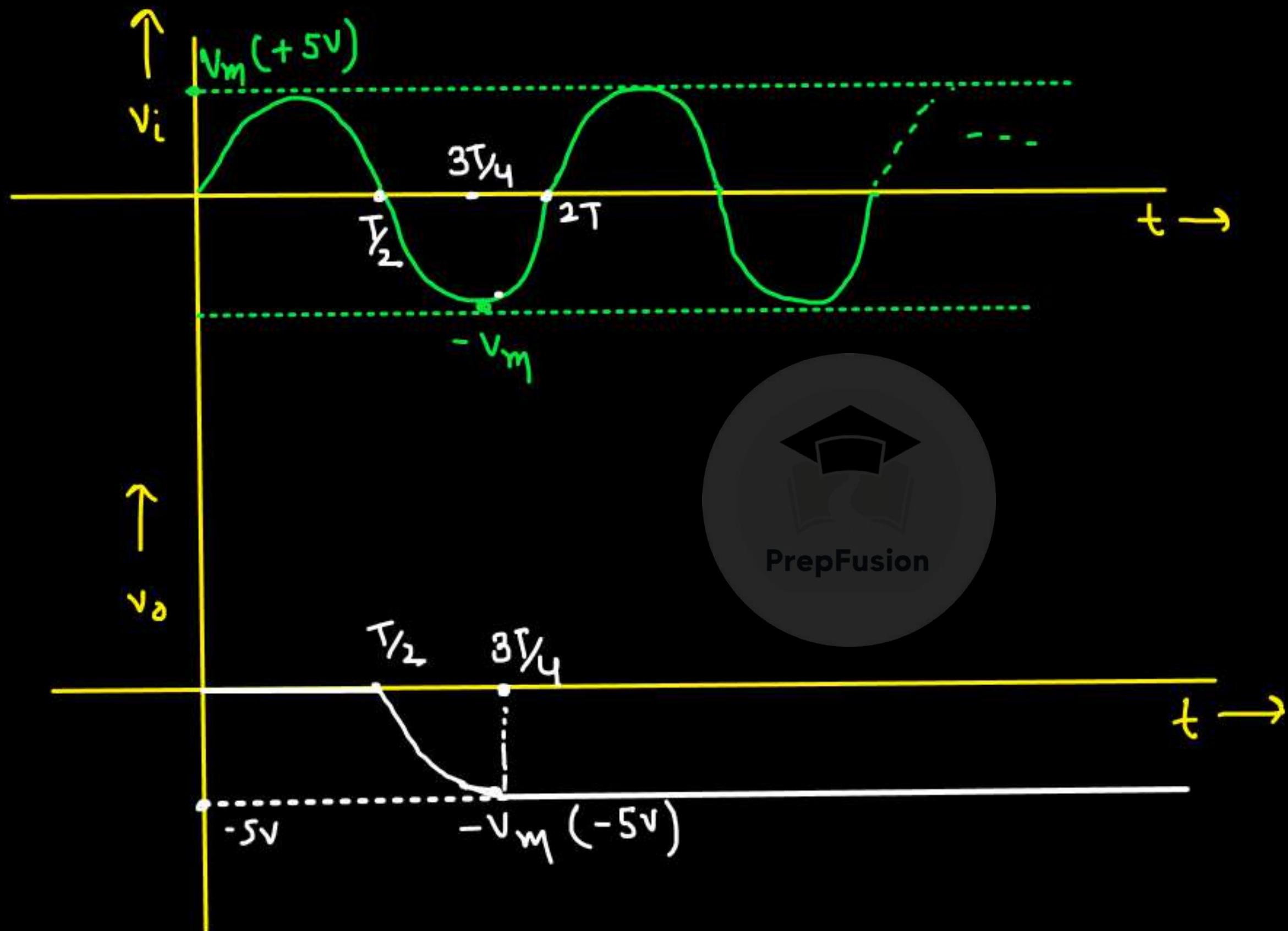{ since RC is very large, the cap. can't discharge further }







Given $V_i = V_m \sin \omega t$

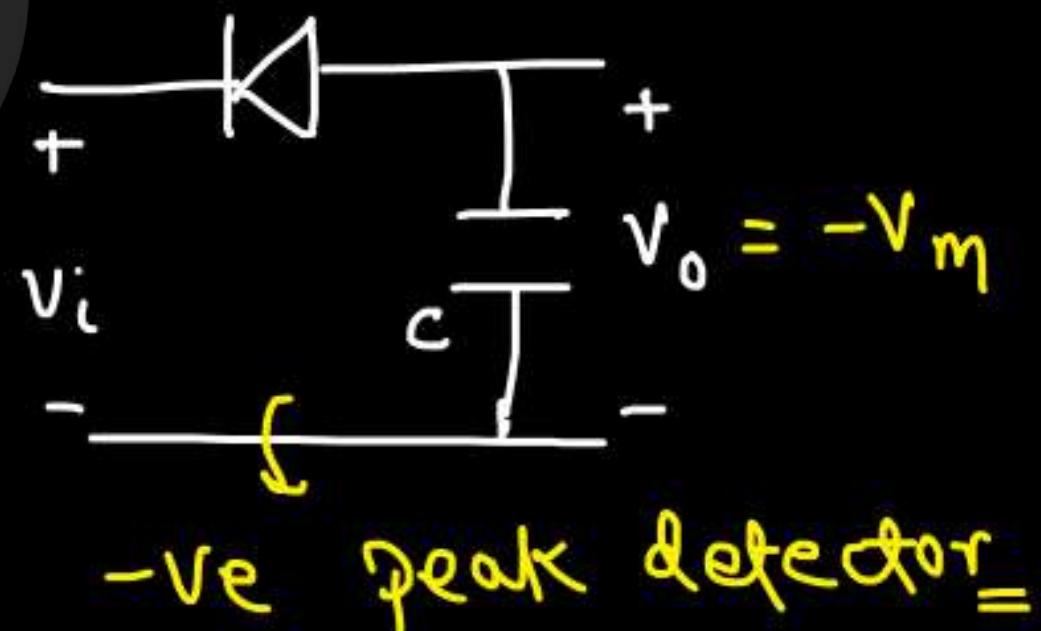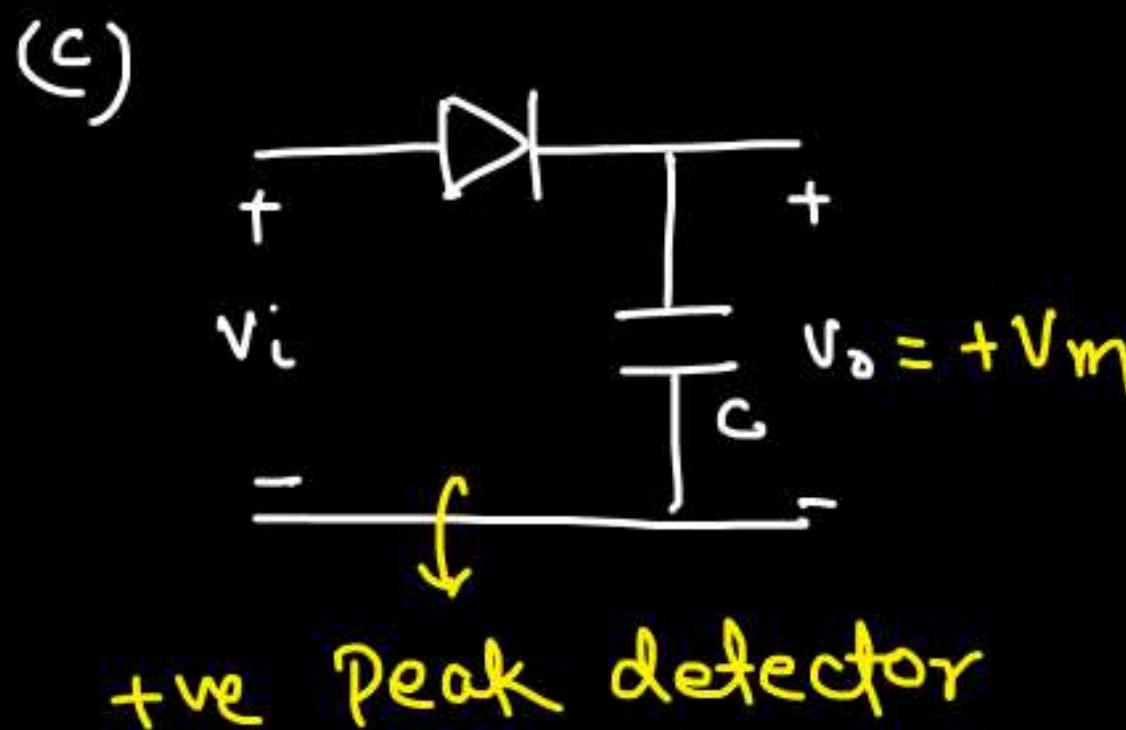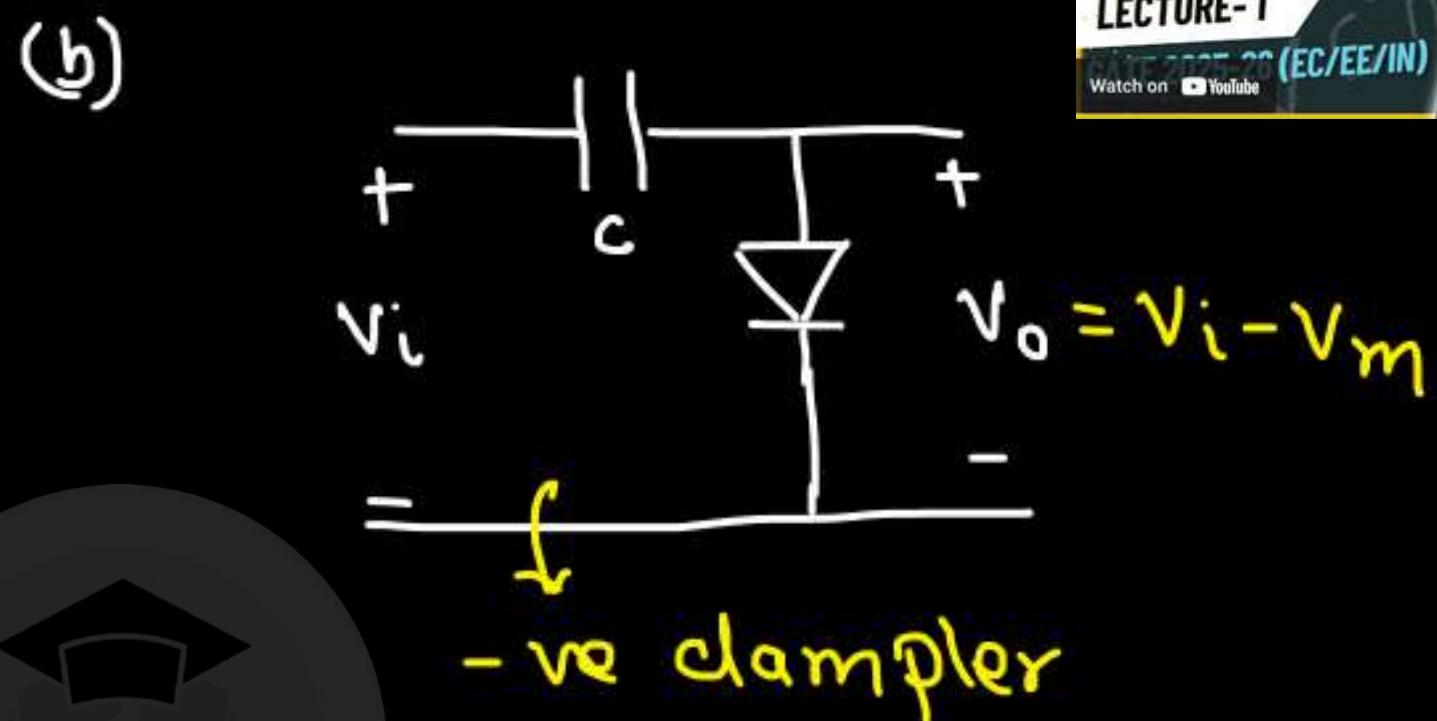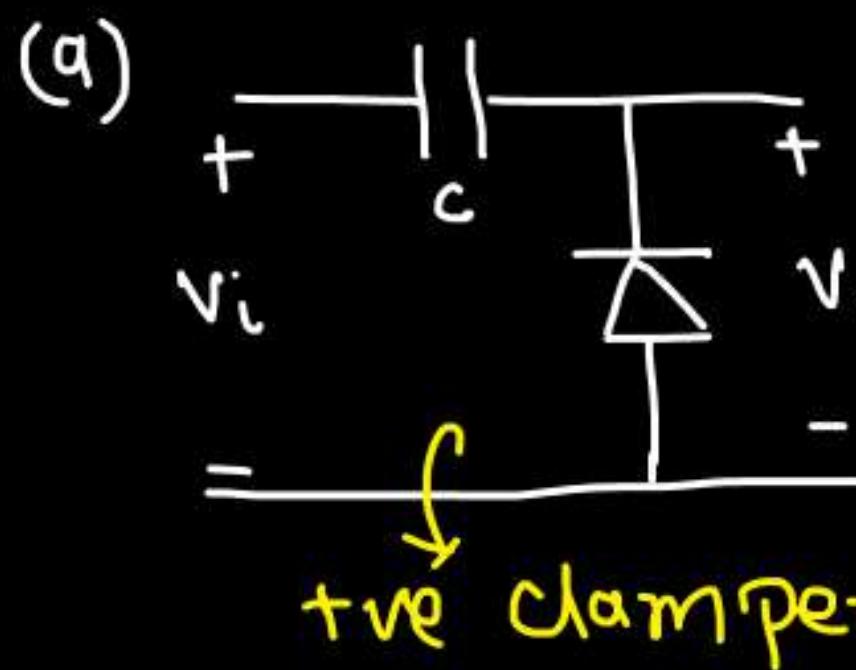


Q. Find the steady state o/p.

Draw V_o waveform.

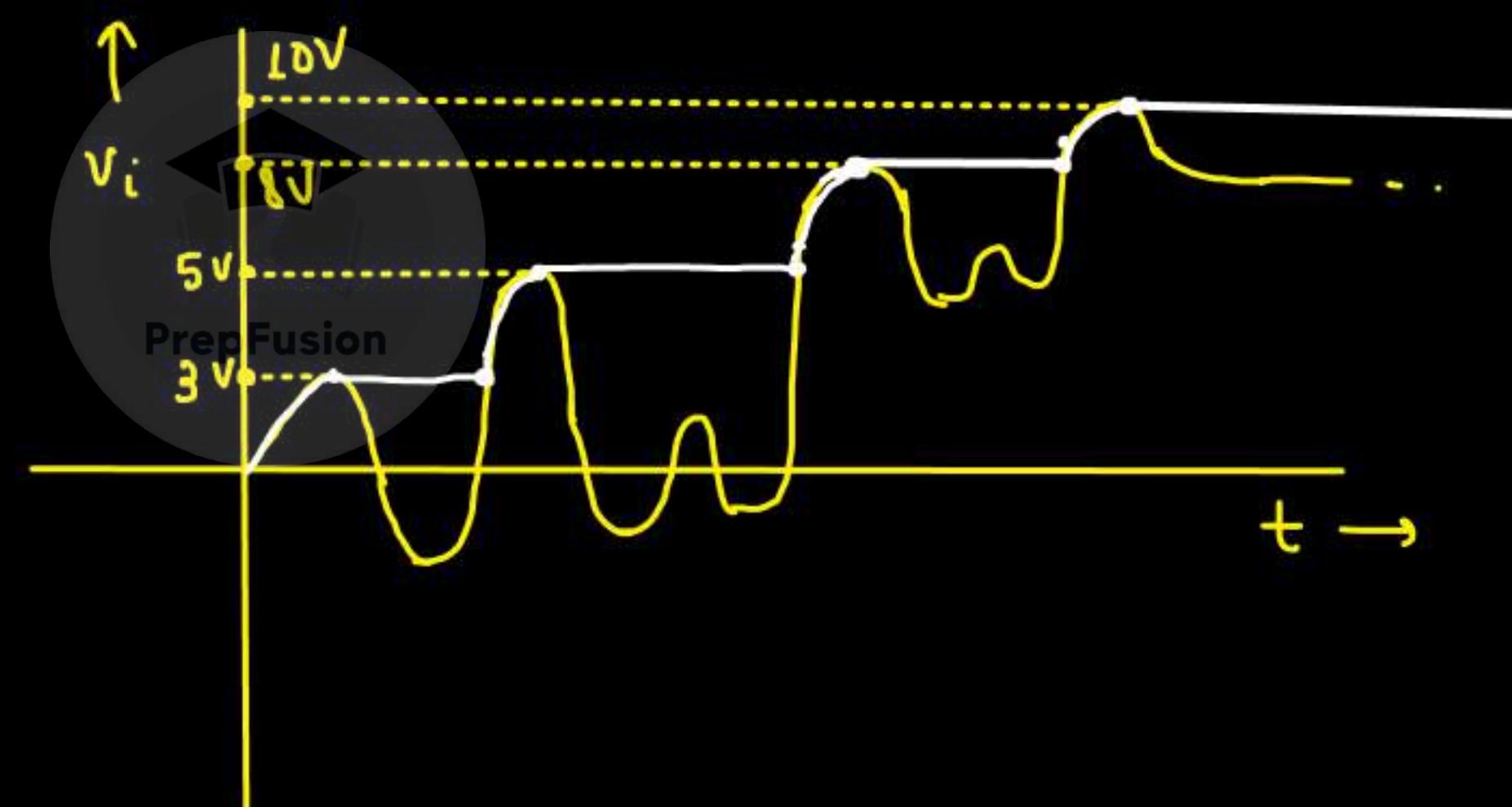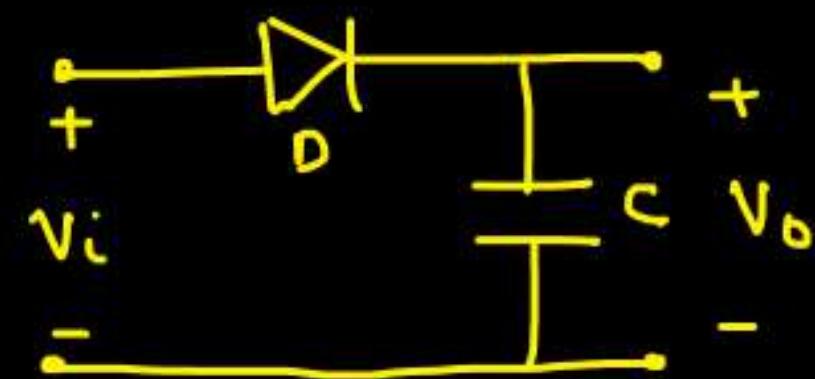


Q. Find the steady state o/p.


Draw V_o waveform.

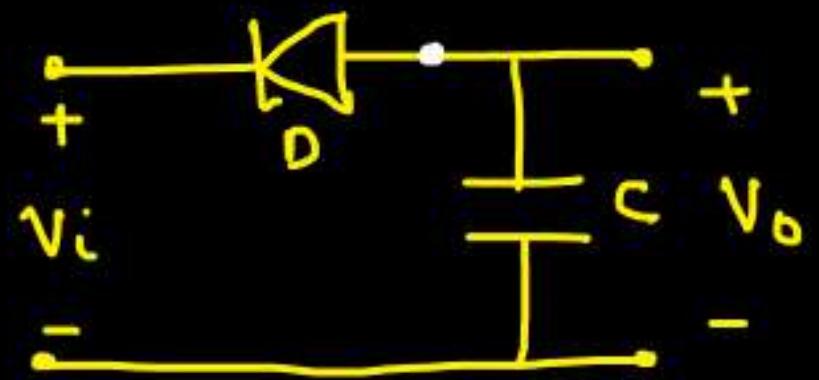

$$V_o(s) = -10V$$

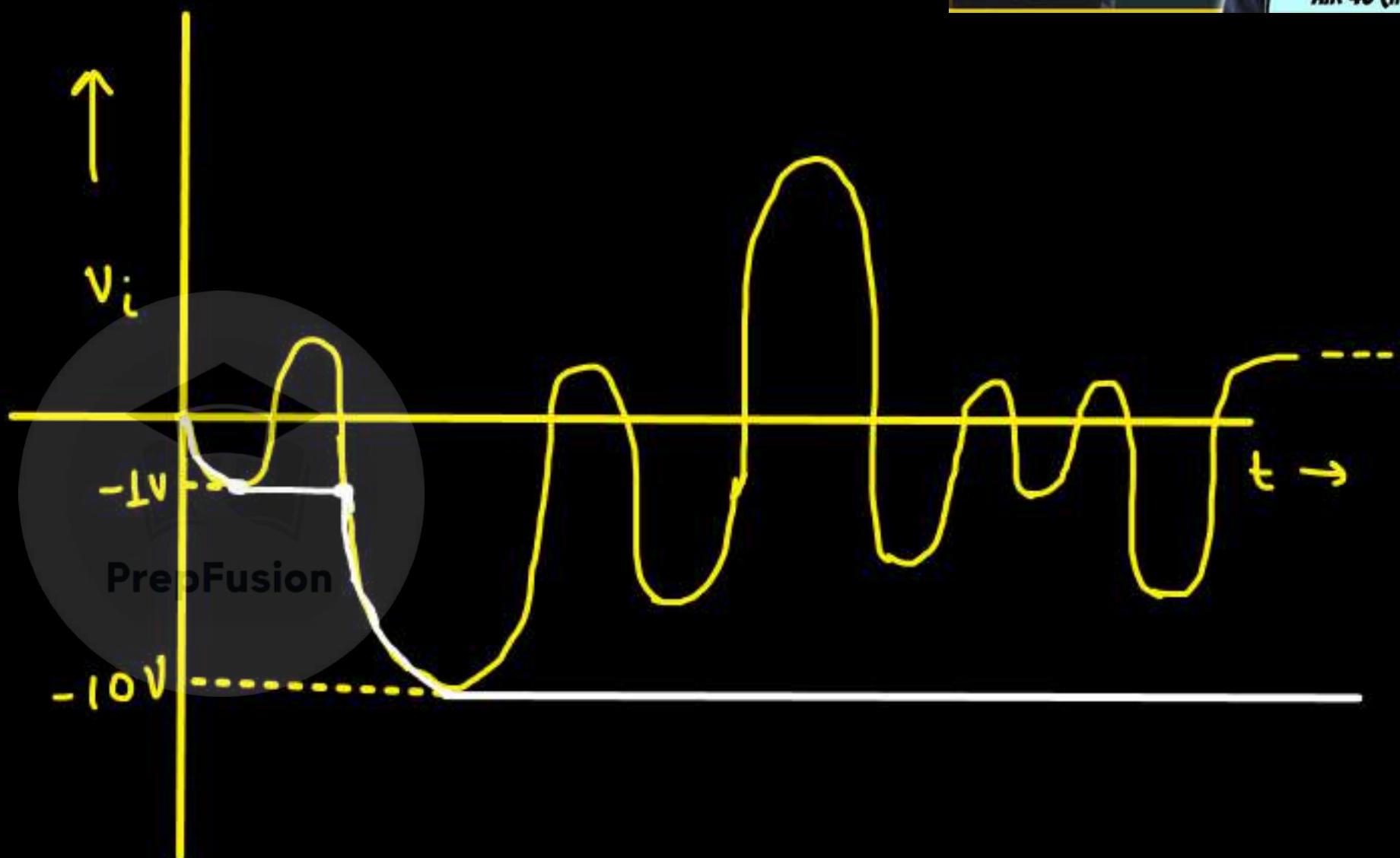


Q. Find the average of the given signal.

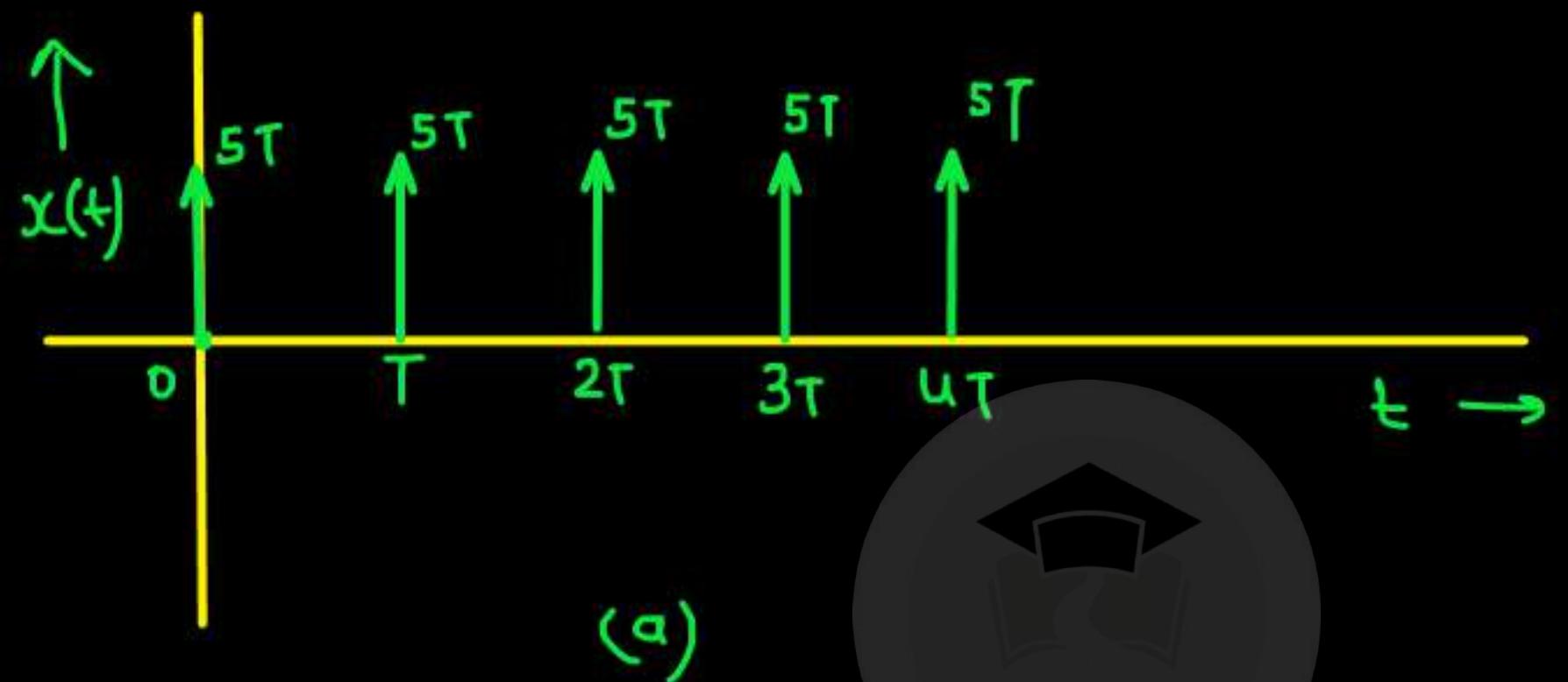

$$\Rightarrow \text{avg.} = \frac{\text{Area of one Time period}}{\text{Time period}}$$

$$= \frac{5T}{T} = 5 =$$

avg. = 5

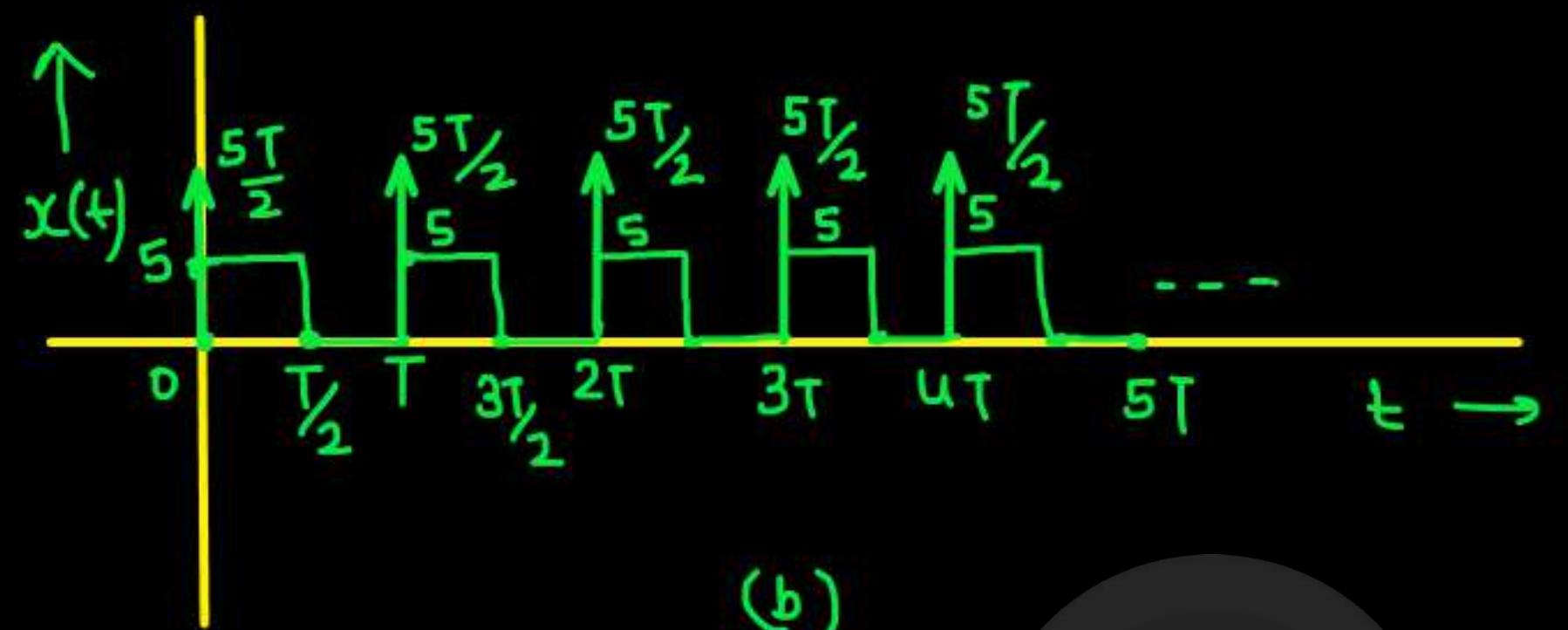

(b)

$$\text{Avg} = \frac{\frac{5T}{2} + \frac{5T}{2}}{T} = \frac{5T}{T} = 5$$




$\text{Avg} = 5$



Q. Cap. is initially charged to 3V.

The switch is closed @ $t=T$.

Find $i_c(t) = ?$

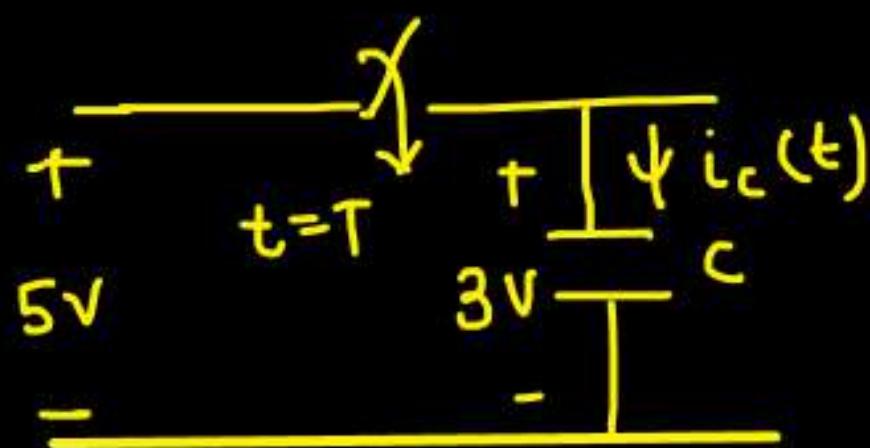

→

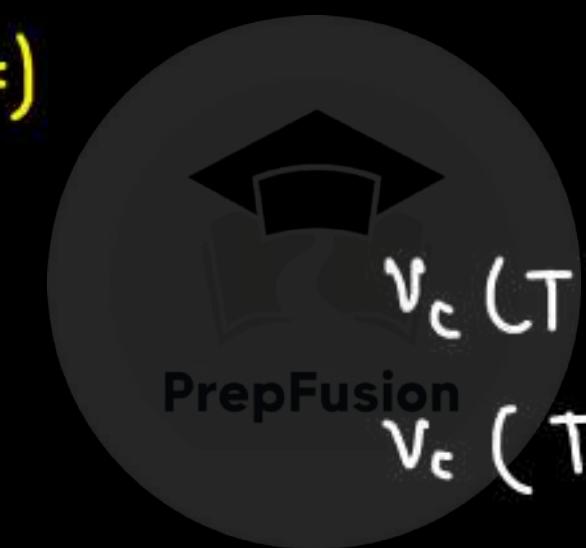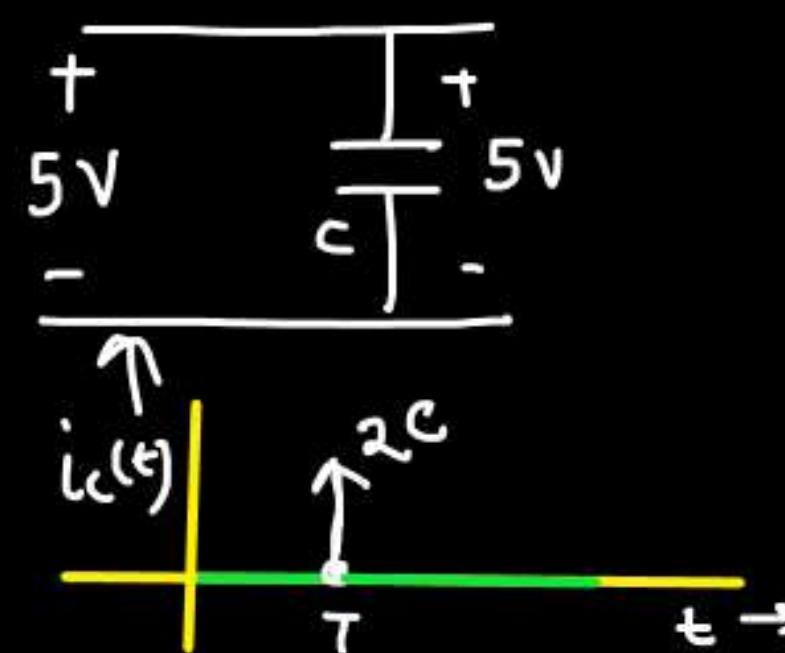


$$v_c(T^-) = 3V$$

$$v_c(T^+) = 5V$$


$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$i_c(t) = C \frac{[5-3]}{0}$$

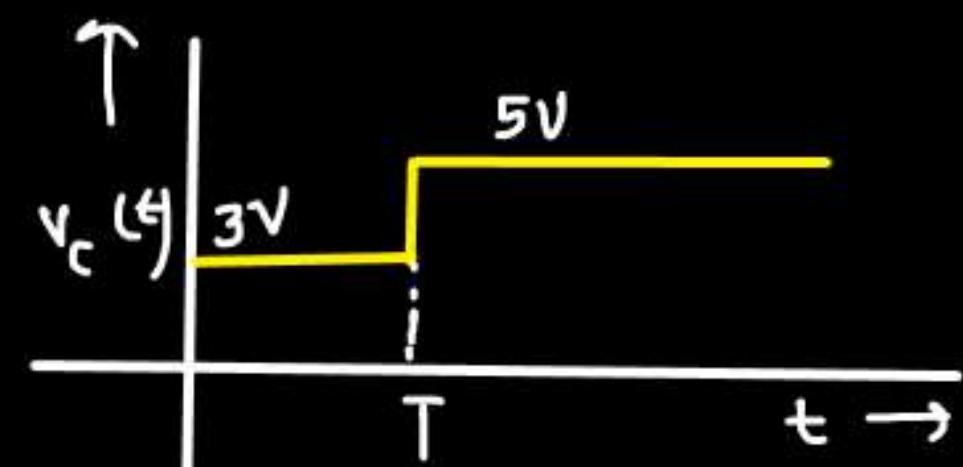

$$i_c(t) = 2C \delta(t-T)$$



Q. Find $(I_D)_{avg}$ at steady state.

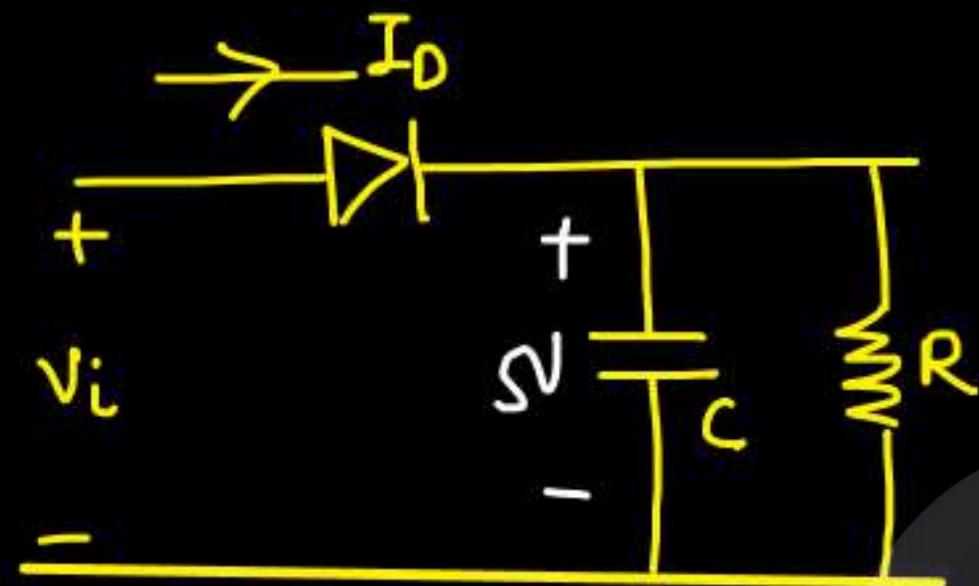

$$\text{Given } RC = 20T$$

$\rightarrow 0 < t < \frac{T}{2} \Rightarrow V_i = 5V \ni \text{diode is ON}$


$$\Rightarrow I_D = ?$$

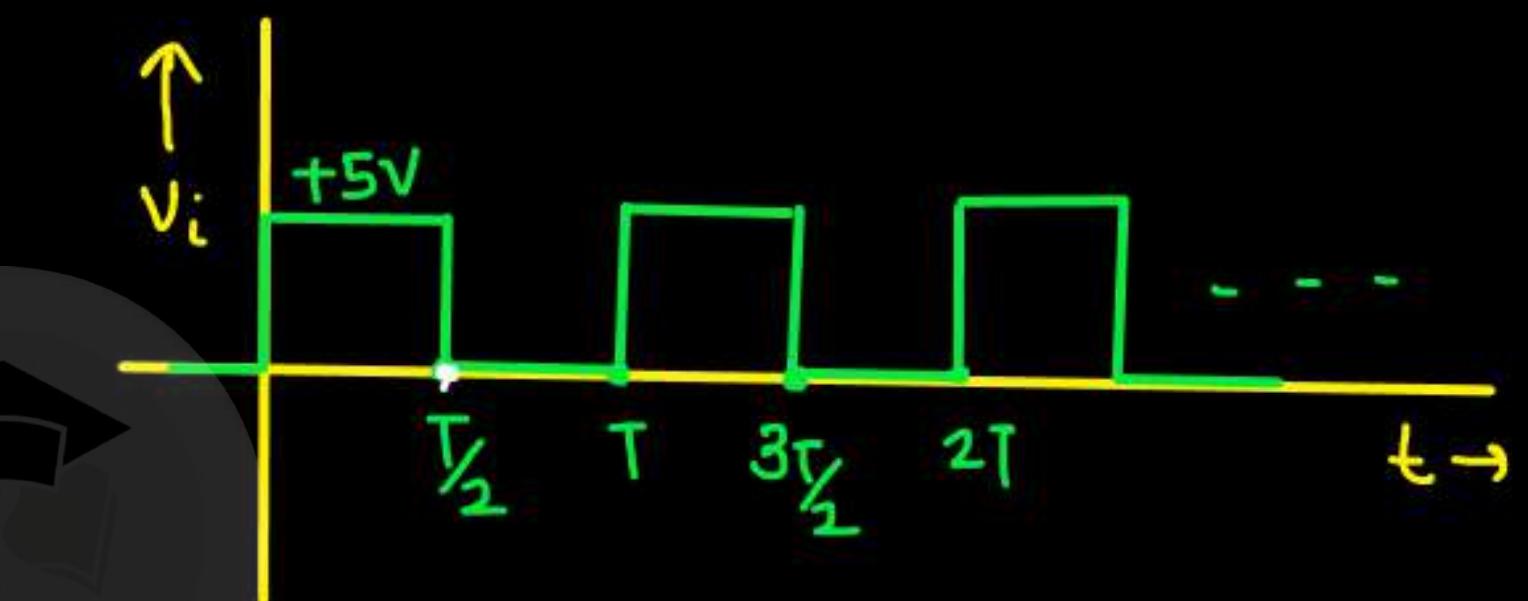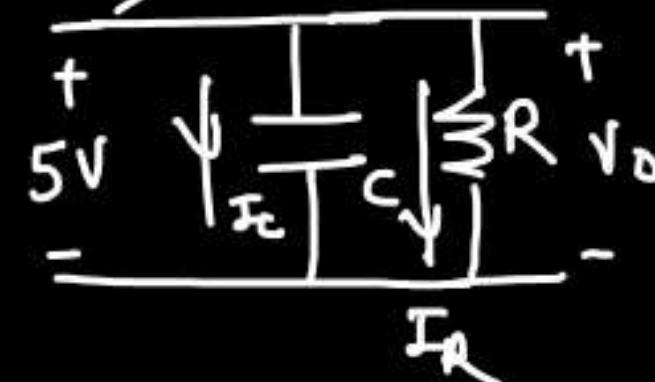

$$V_D = 5V$$

$$0 < t < \frac{T}{2}$$

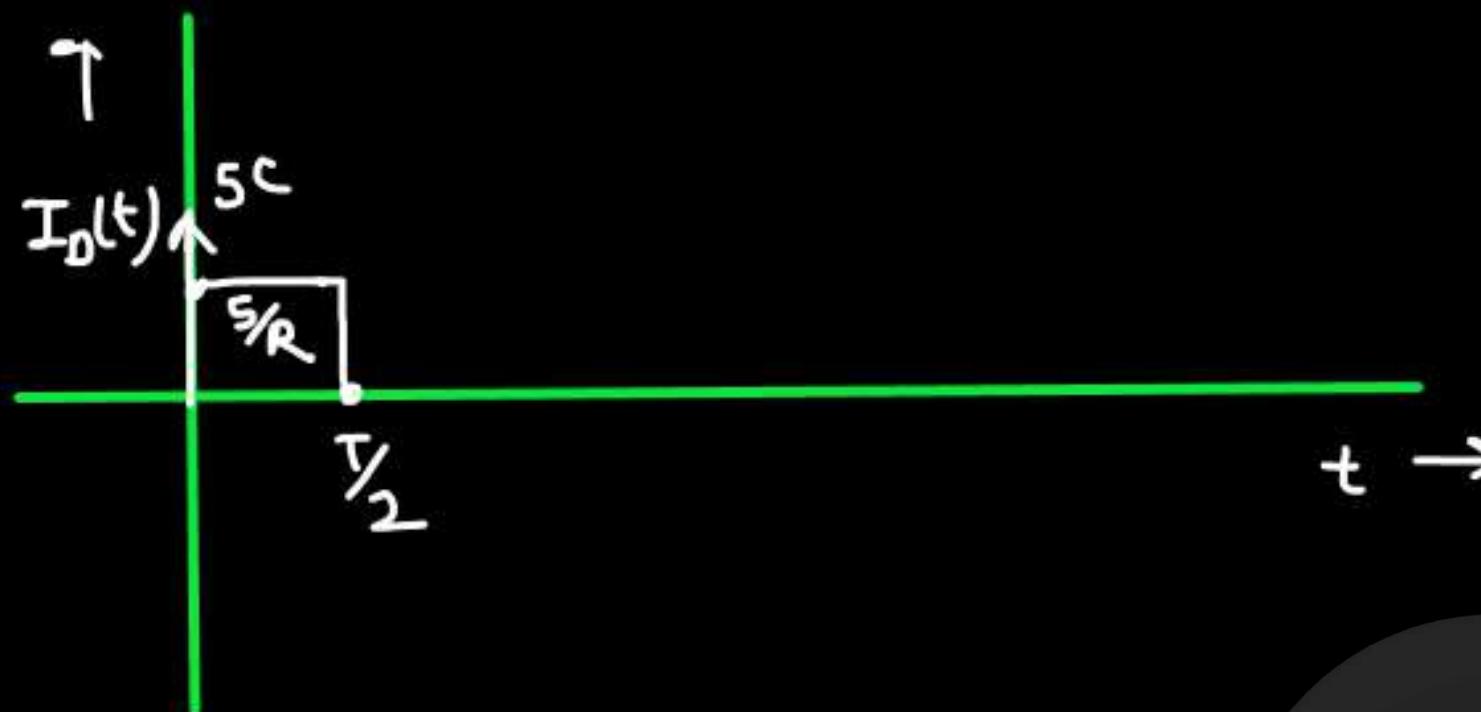
$$\begin{aligned} I_D(t) &= I_c(t) + I_e(t) \\ &= 5C \delta(t) + \frac{5}{R} \end{aligned}$$



$$e^{-\frac{t}{RC}} = 1 - \chi$$

For $T/2 < t < T$

$v_i = 0V \Rightarrow$ diode turns off

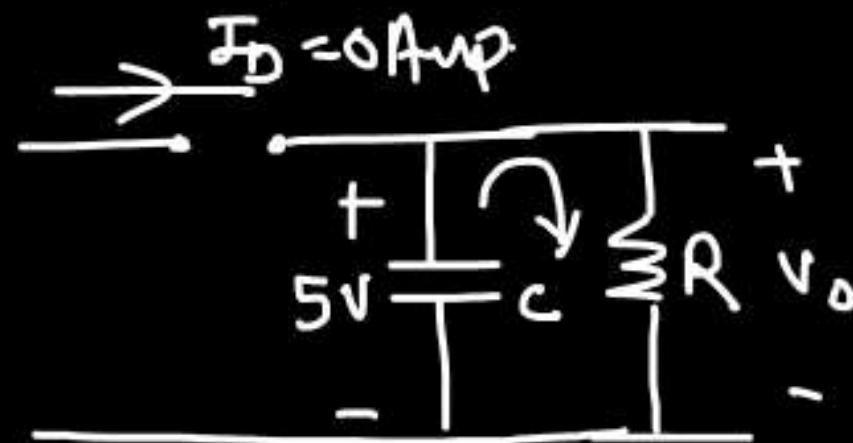



$$I_o = 0 \text{ A}$$



$$v_o(t) = 5 e^{-\frac{(t-T/2)}{RC}}$$


$$v_o(t) = 5 \left[1 - \frac{(t-T/2)}{RC} \right]$$
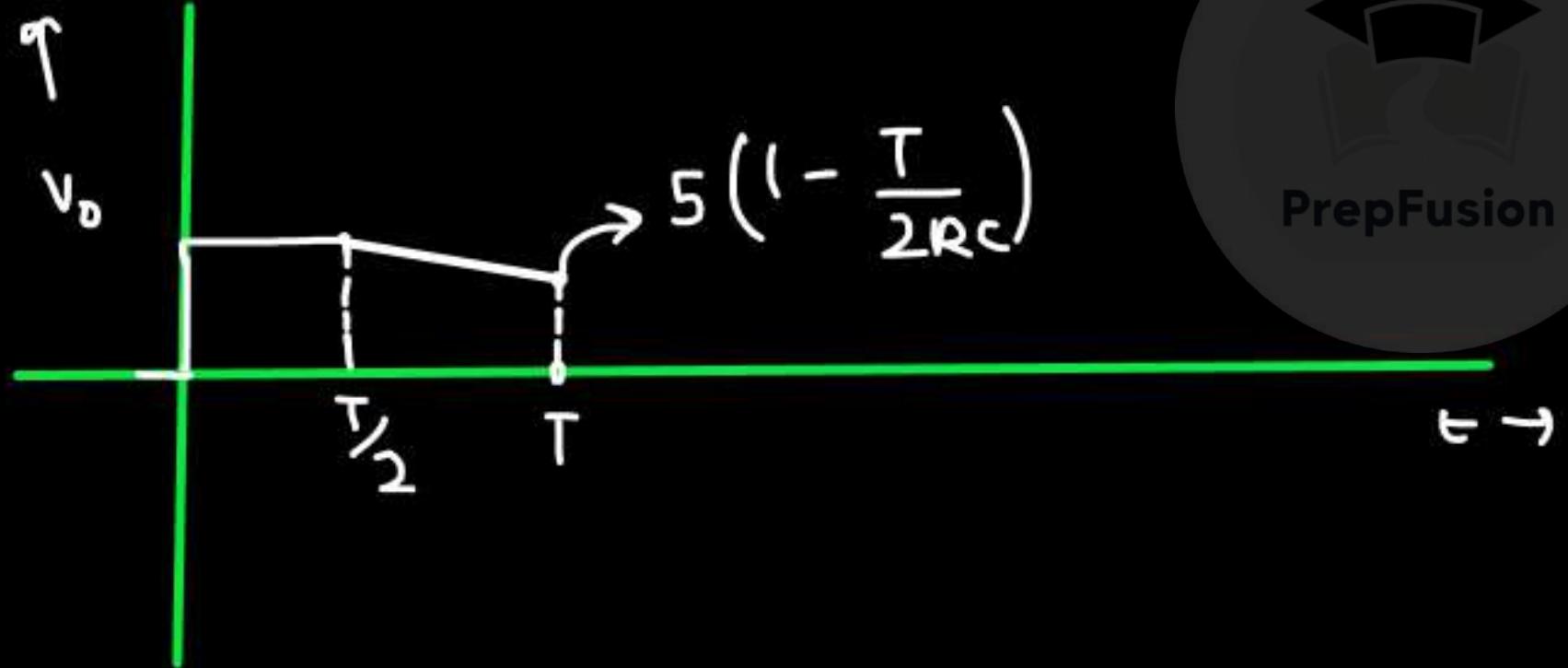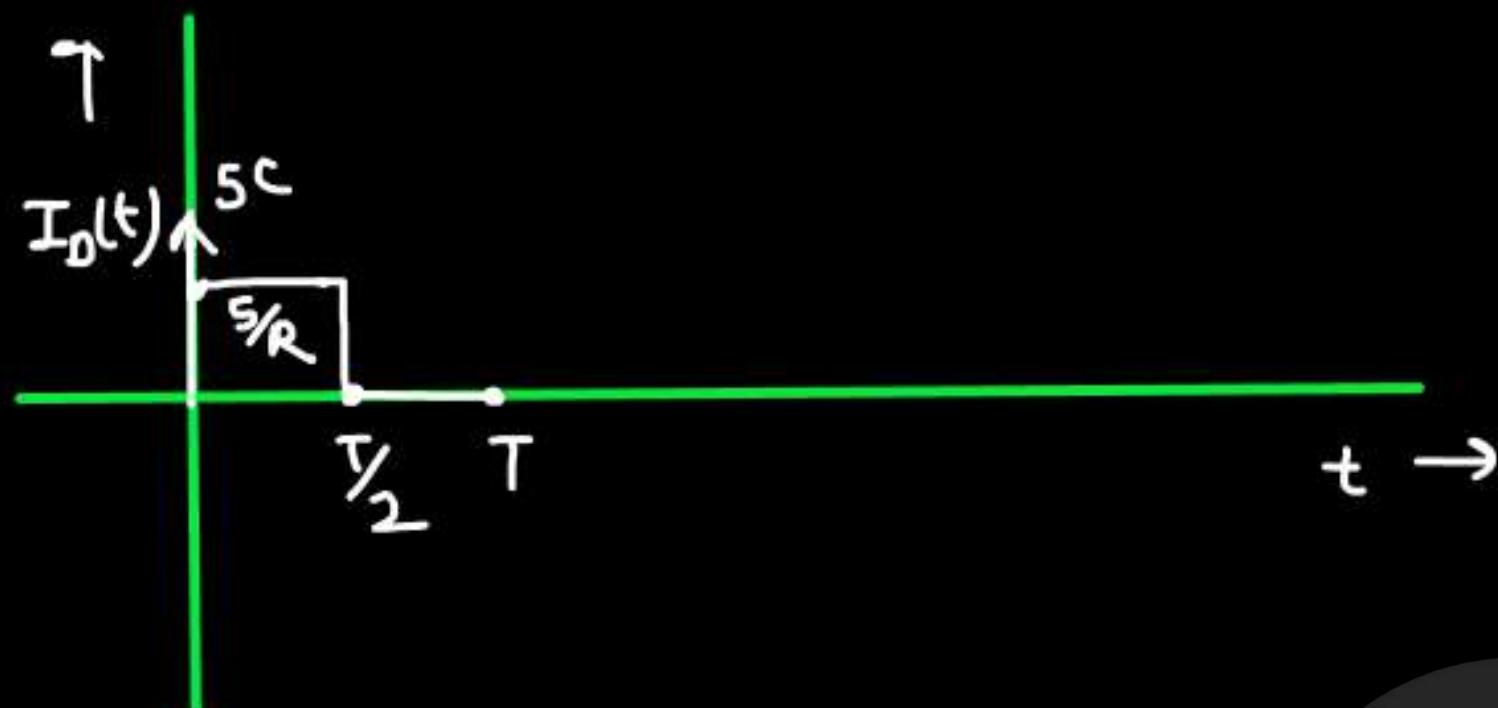
$$v_o(T) = 5 \left[1 - \frac{T}{2RC} \right] \leftarrow$$




$$\Rightarrow T < t < \frac{3T}{2}$$

$V_i = 5V$ diode turns on

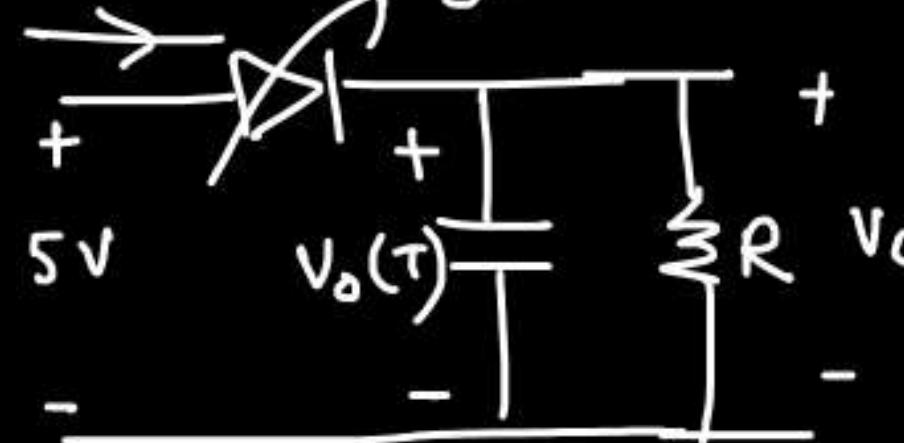

$$V_o(T^+) = 5V$$

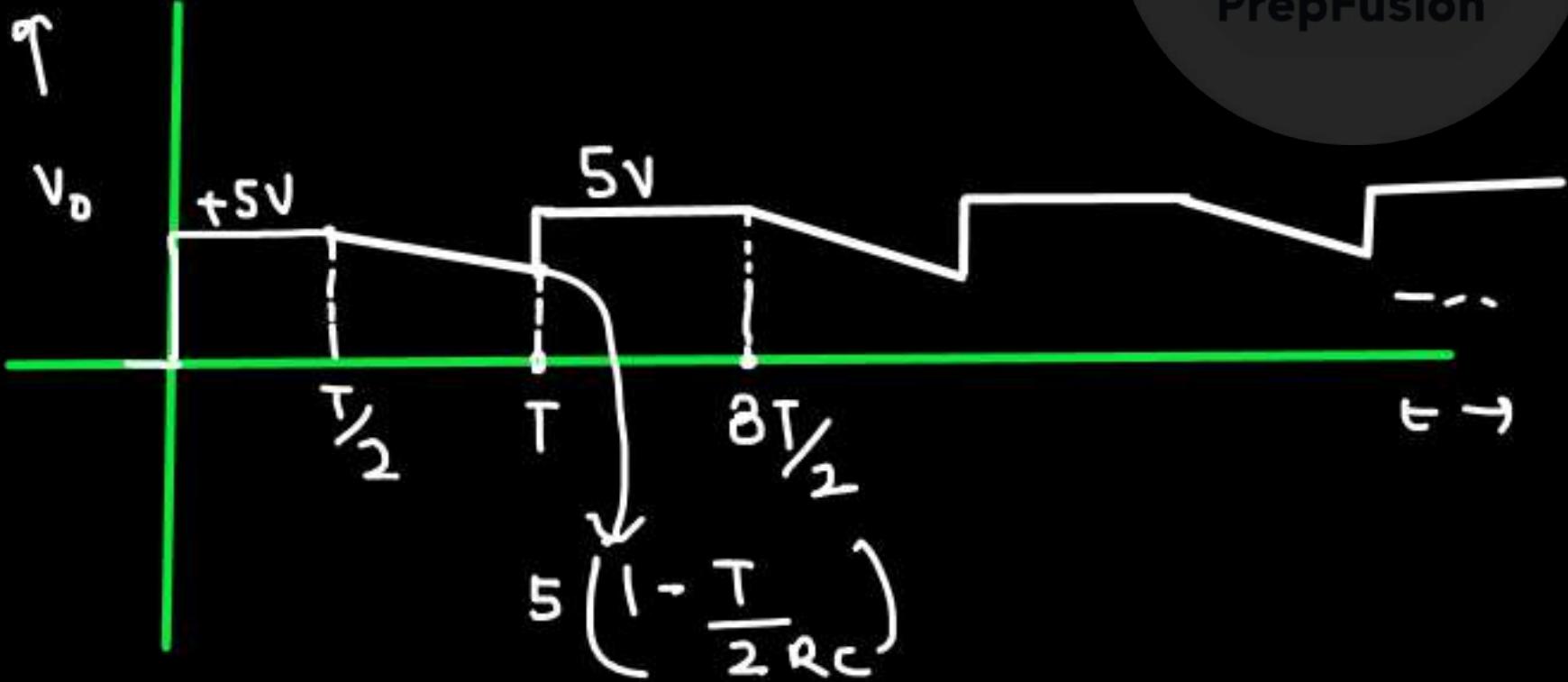


resistor current

$$I_D(t) = \frac{5}{R} + \frac{5T}{2R} \delta(t-T)$$

PrepFusion

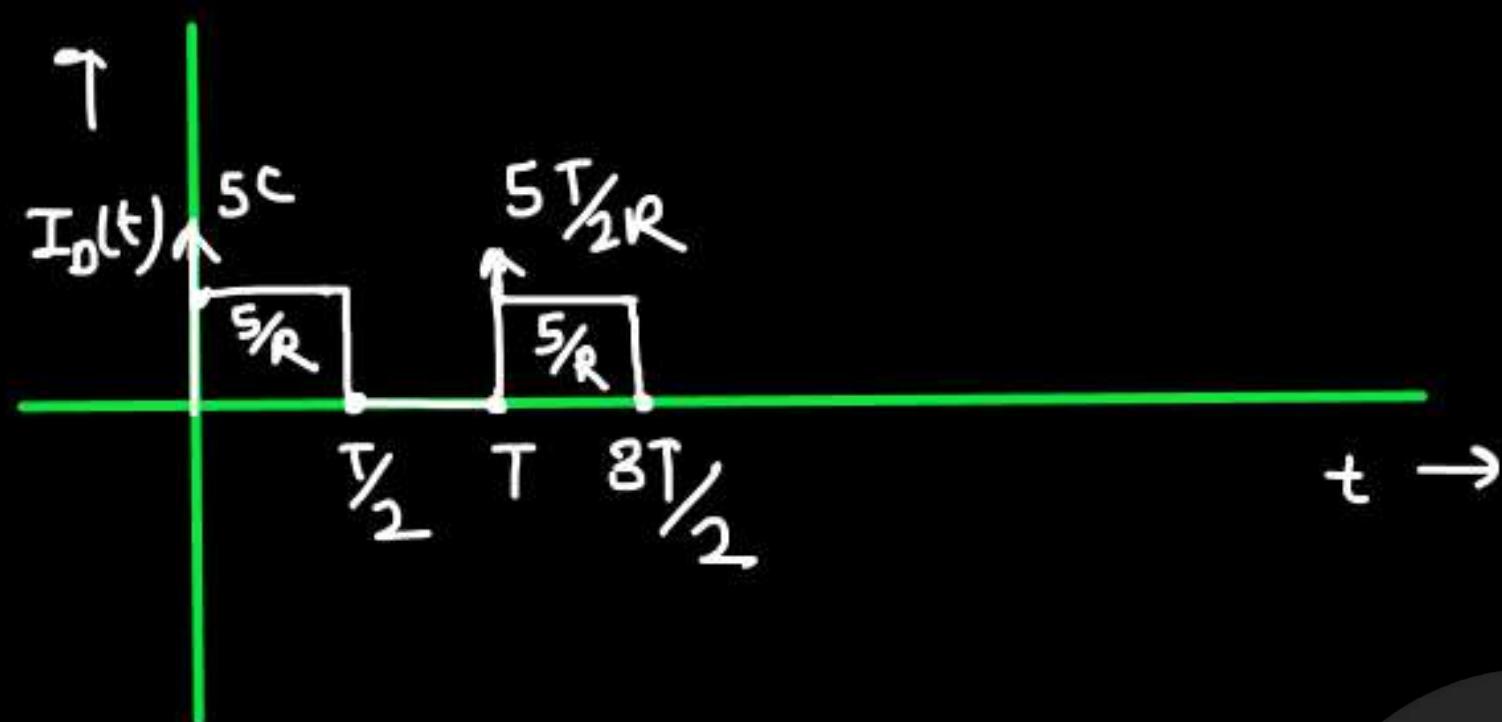
$$\begin{aligned} I_D(t) &= \frac{5}{R} + \frac{5T}{2R} \delta(t-T) \\ &= \frac{5}{R} + \frac{5}{2RC} \left(1 - \frac{T}{2RC}\right) \delta(t-T) \\ &= \frac{5}{2RC} \left(1 - \frac{T}{2RC}\right) \delta(t-T) \end{aligned}$$



For $3T/2 < t < 2T$

$v_i = 0V$, $v_o = +5V \Rightarrow$ diode will be off $I_D = 0$ A.s.

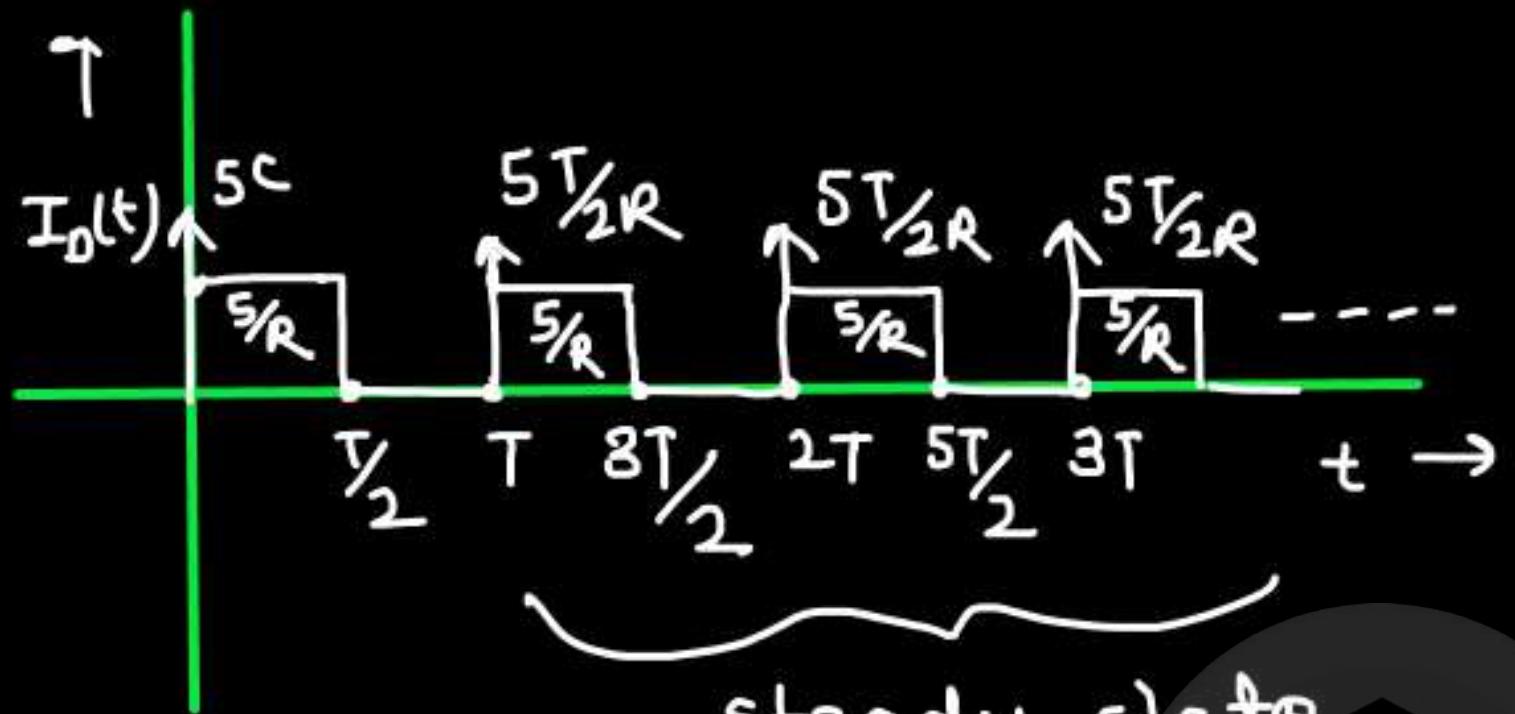$+ \frac{Q}{C} R \rightarrow$ it will discharge in the same manner as $T_2 < t < T$




Steady state

$$\left[I_D(t)_{\text{avg}} \right]_{\text{S.S.}} = \frac{\frac{5}{R} \left[\frac{3T}{2} - T \right]}{T} + \frac{\frac{5T}{2R}}{T} = \frac{\frac{5T}{2R} + \frac{5T}{2R}}{T}$$


$$\Leftrightarrow \left[I_D \right]_{\text{avg.}} = \frac{5}{R}$$

Q.

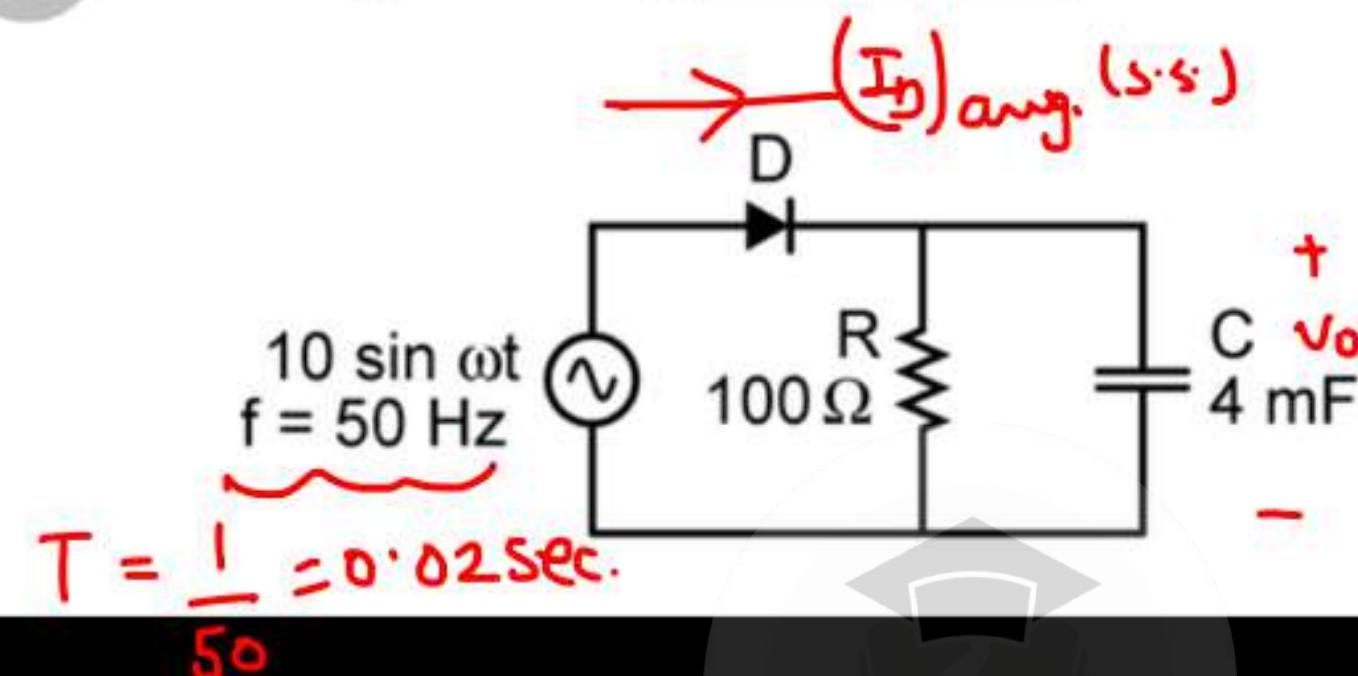The figure shows a half-wave rectifier. The diode D is ideal. The average steady-state current (in Amperes) through the diode is approximately _____.


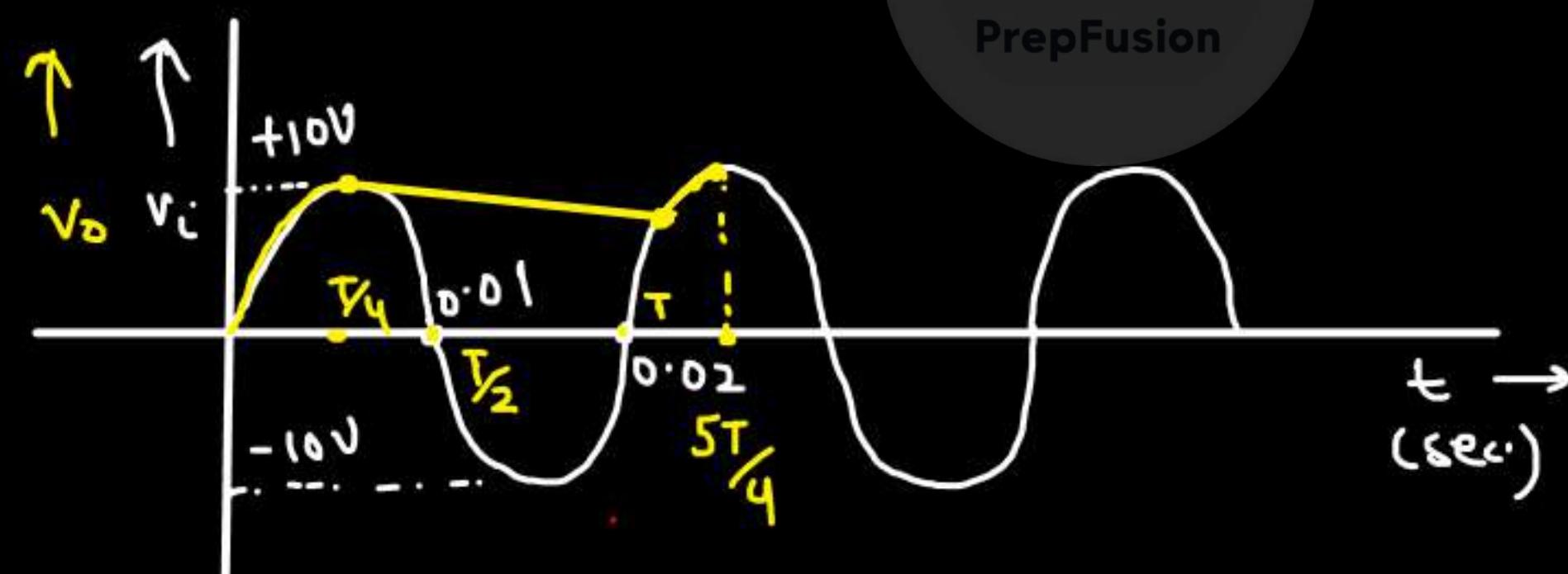
$$RC = 400 \text{ msec.} \\ = 0.4 \text{ sec.}$$



@ $t = \frac{T}{2}^+$


diode is off

$$V_o(t) = 10 e^{-(t - \frac{T}{4})/RC}$$




$$V_o(t) = 10 \left[1 - \frac{(t - \frac{T}{4})}{RC} \right] \quad \left\{ e^{-x} = 1 - x \right\}$$
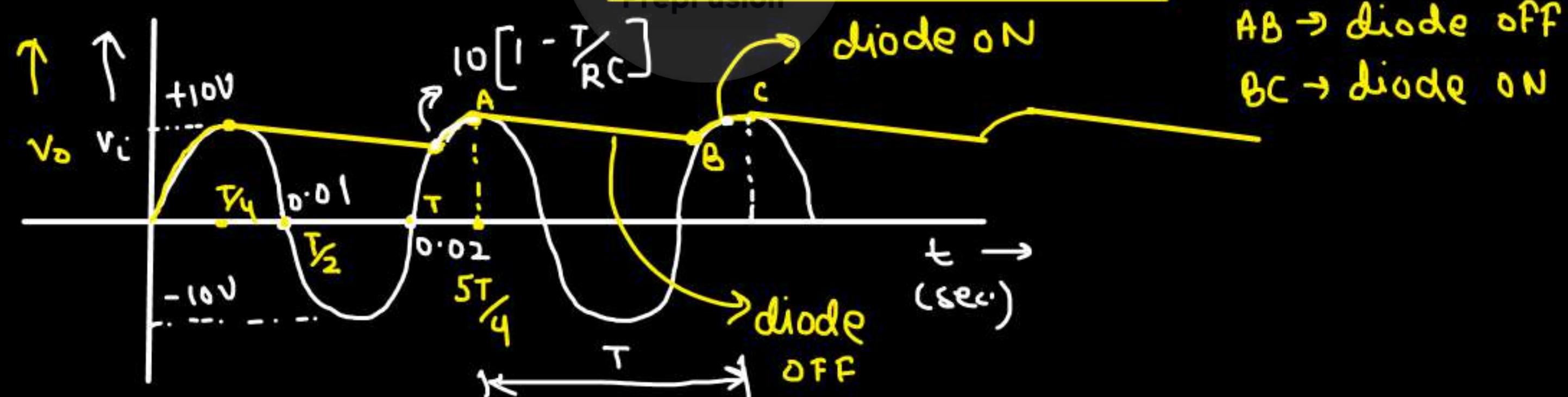
$$V_o\left(\frac{5T}{4}\right) = 10 \left[1 - \frac{\frac{T}{4}}{RC} \right] \approx 9.99V$$



$$V_o \left(\frac{5T}{4} \right) = 10V$$


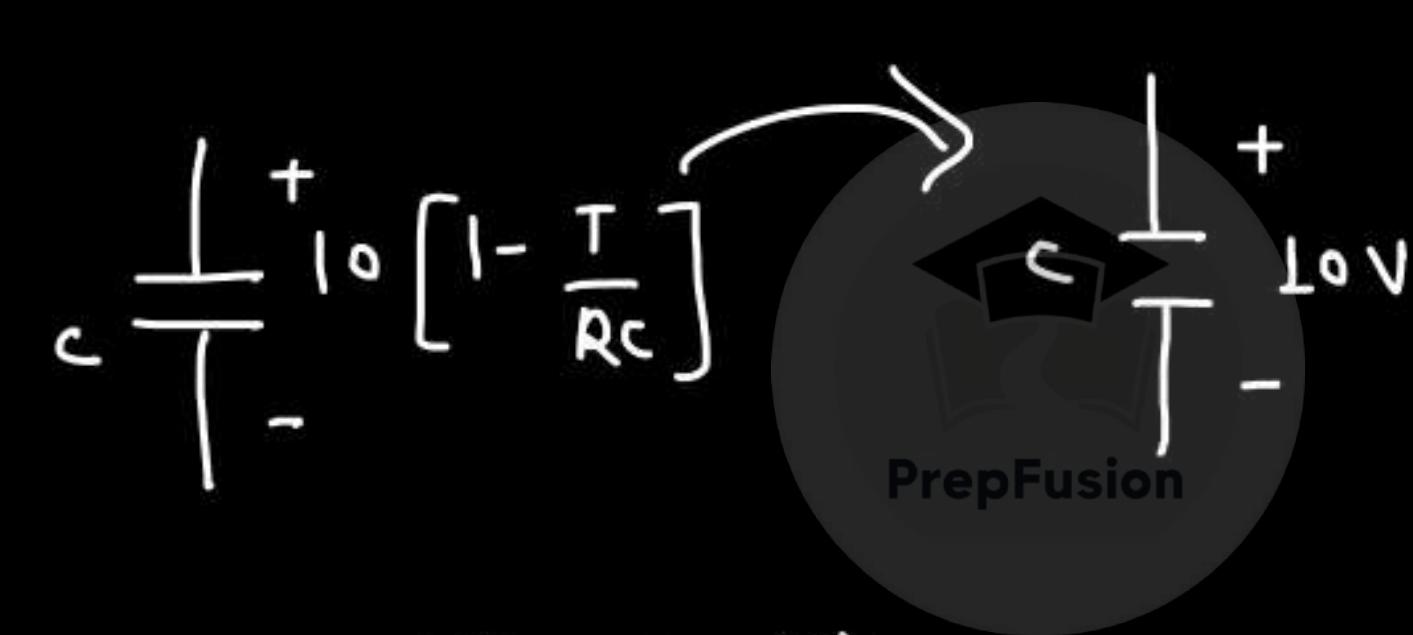
$$V_o \left(\frac{5T}{4} \right) = 10 \left[1 - \frac{T}{RC} \right] V$$



 PrepFusion

$$\begin{aligned}
 & C \frac{1}{T} \left[10 \left[1 - \frac{T}{RC} \right] \right] \\
 & \Rightarrow C \left[10 - \left[10 - \frac{10T}{RC} \right] \right] \\
 & = \frac{10T}{RC} C \delta \left(t - \frac{5T}{4} \right) \\
 & = \frac{10T}{R} \delta \left(t - \frac{5T}{4} \right)
 \end{aligned}$$
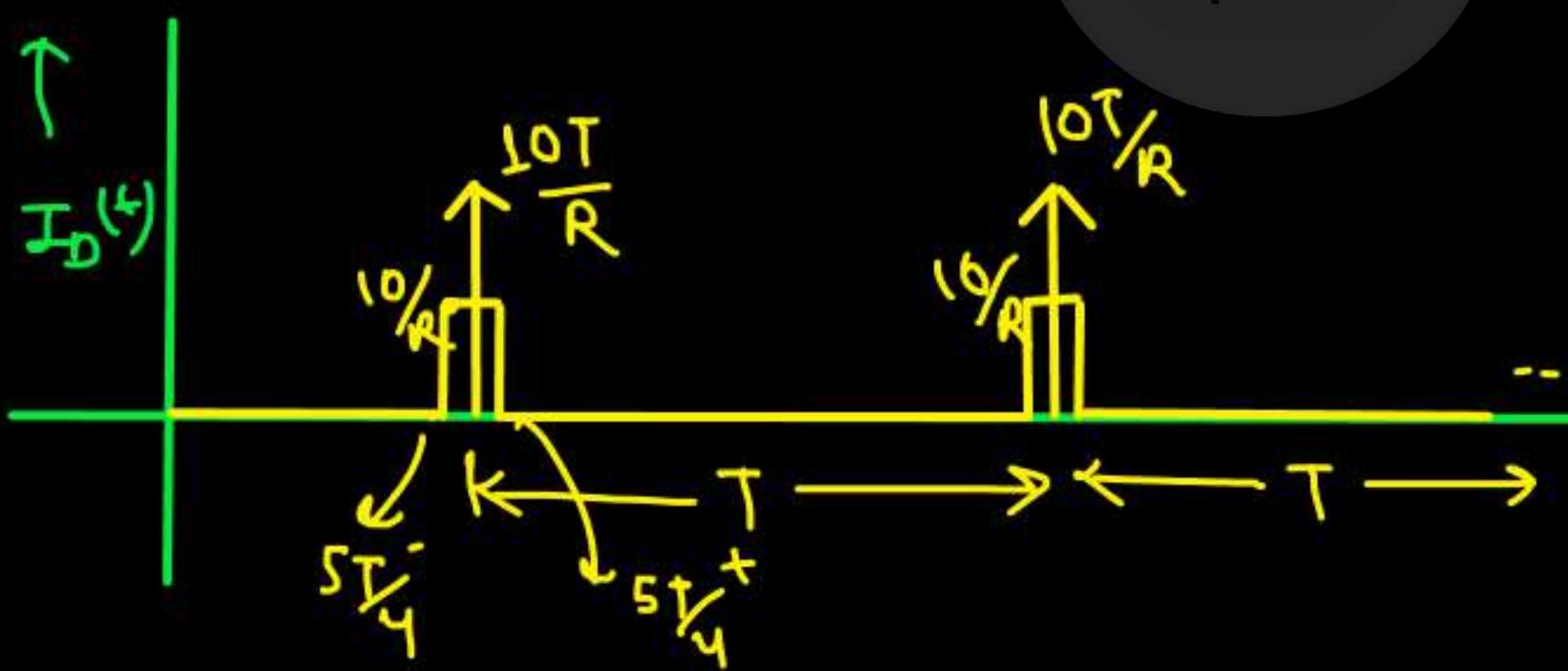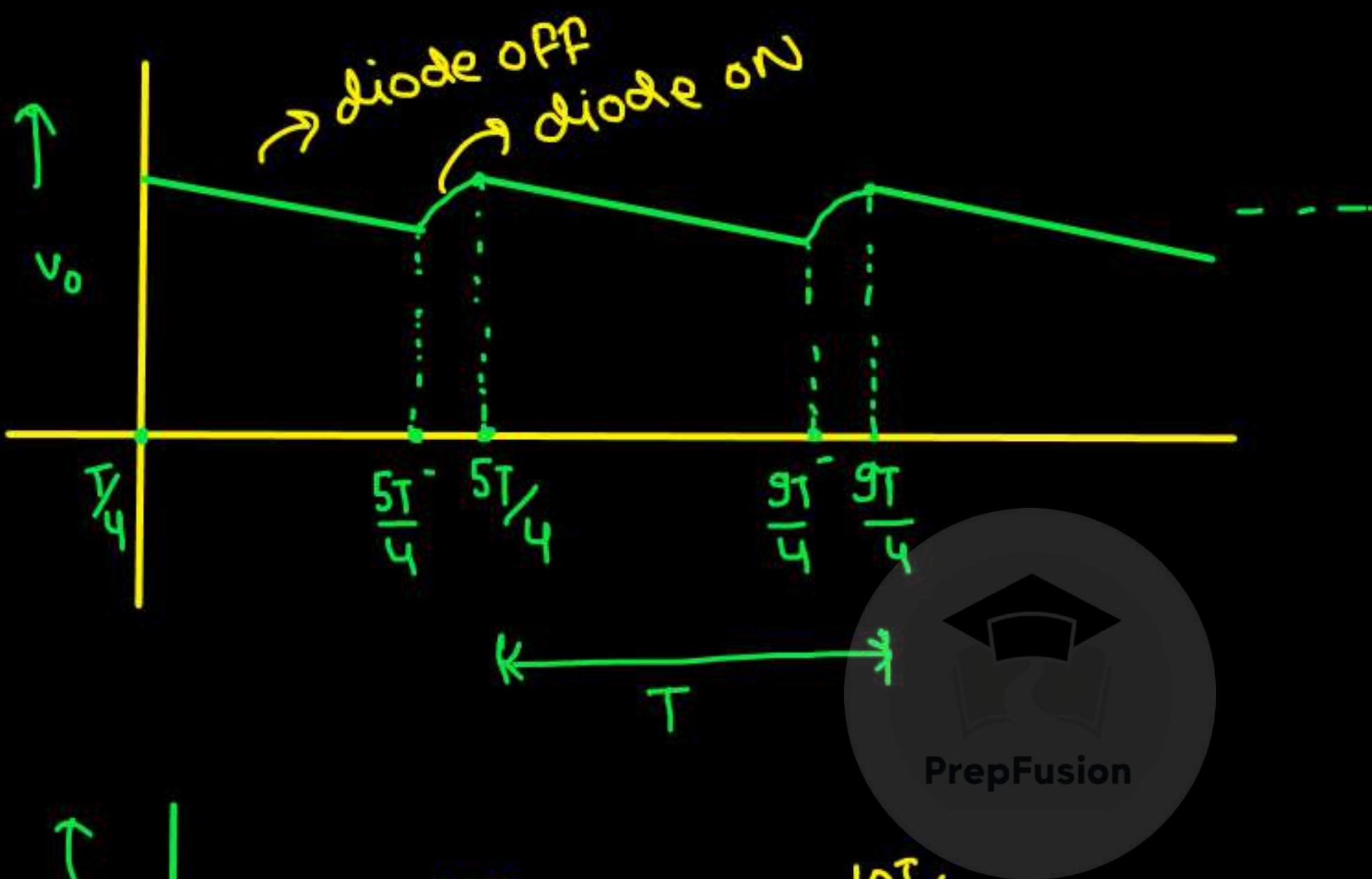
$$\begin{aligned}
 I_D(t) &= I_R(t) + I_C(t) \\
 &= \frac{10}{R} + \frac{10T}{R} \delta \left(t - \frac{5T}{4} \right)
 \end{aligned}$$



$$I_{D \text{ avg}} = \frac{\frac{10T}{R} + \frac{16}{100} \cdot \frac{10T}{R}}{T}$$

$$(I_D)_{\text{avg}} = \frac{10}{R}$$

$$= \frac{10}{100} \times 10 \\ = 0.1 \text{ Amp.}$$

Voltage Multiplier :-

Produces dc voltage greater than its max^m input voltage.




$k=1 \Rightarrow V_o = V_m \Rightarrow$ Positive peak detector

$k=2 \Rightarrow V_o = 2V_m \Rightarrow$ Voltage double

$k=3 \Rightarrow V_o = 3V_m \Rightarrow$ Voltage Tripler

$k=4 \Rightarrow V_o = 4V_m \Rightarrow$ Voltage Quadrupler

* Voltage doubler :-

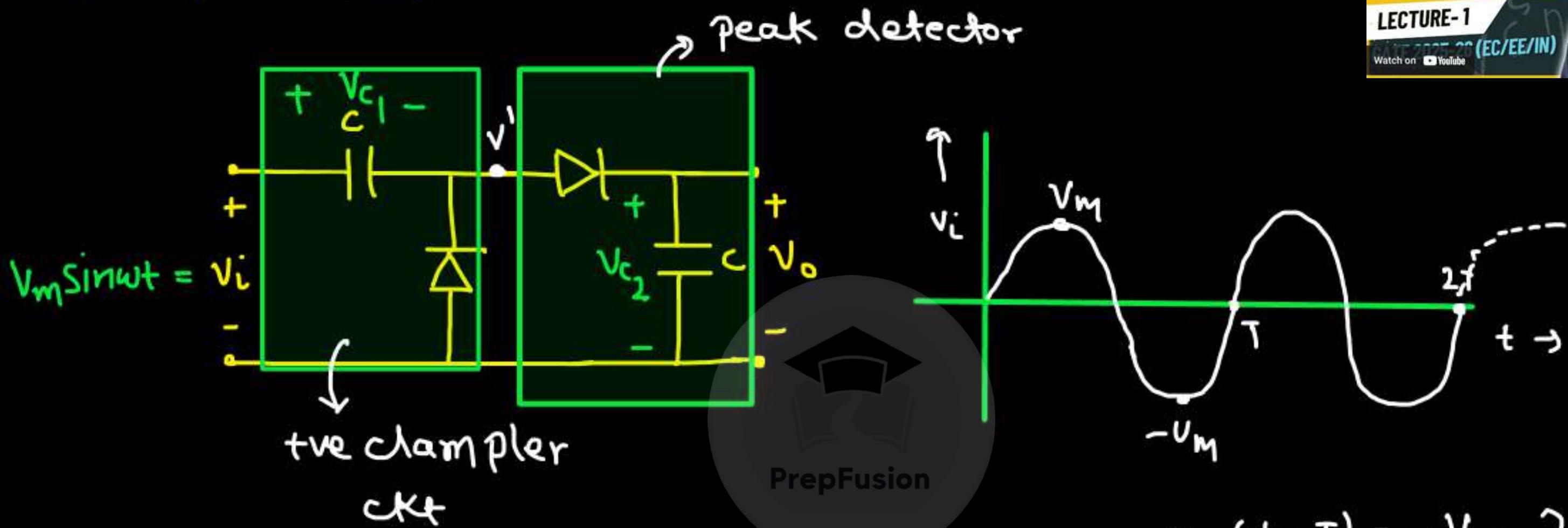


$$V^1 = V_i + V_m \Rightarrow \text{steady state}$$

$$V_{C_1} = -V_m \Rightarrow \text{steady state}$$

$$V_o = 2V_m \Rightarrow \text{steady state}$$
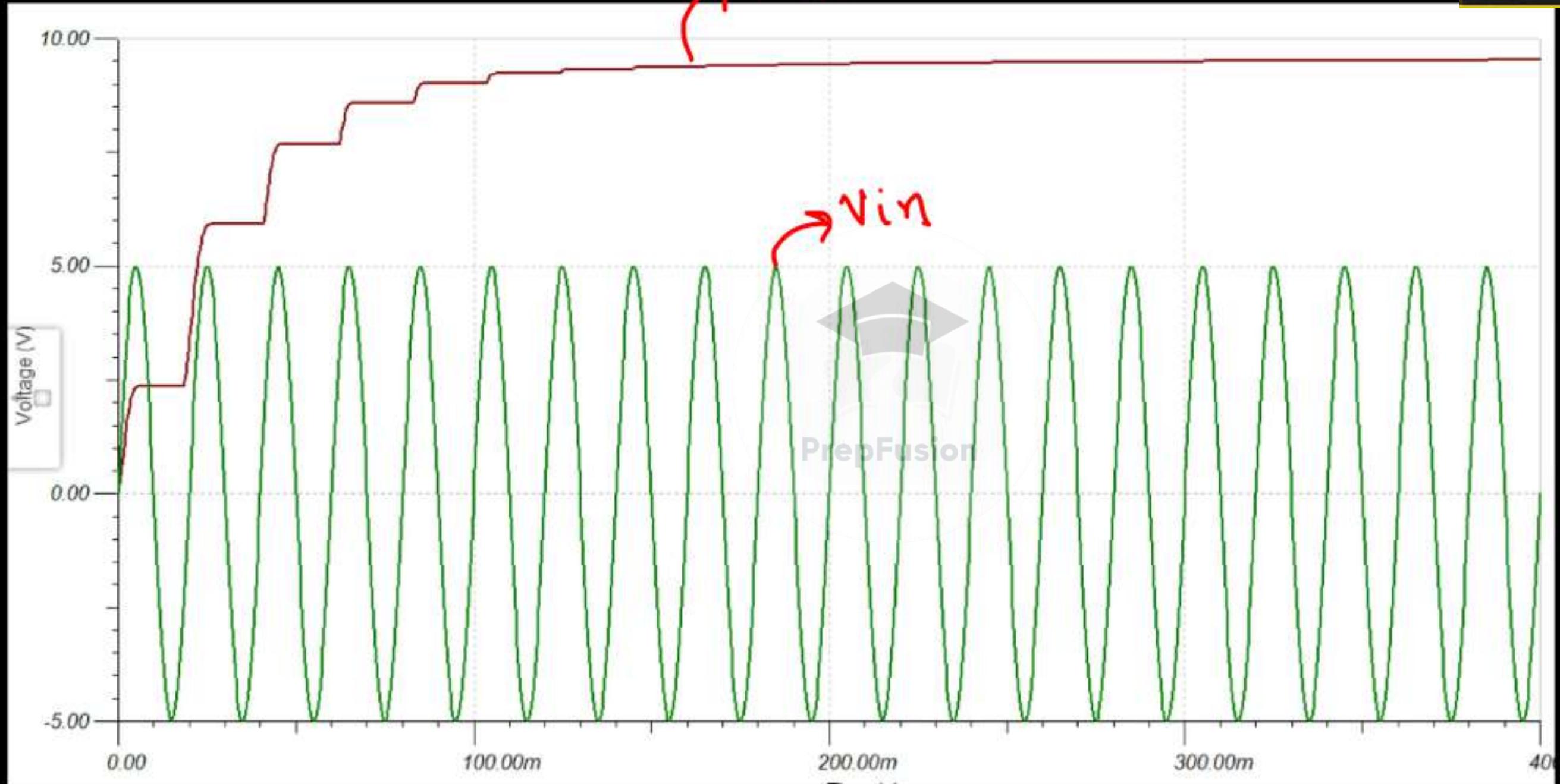
$$\left. \begin{aligned} V_{C_1}(t=T) &= -V_m \\ V_{C_2}(t=T) &= 2V_m \end{aligned} \right\} X$$






* Another Method to Solve Voltage Multipliers:-

- Turn on the diode nearest to the supply with peak voltage. Find steady state cap. voltage value.
- Repeat the same with other diode and find steady state cap voltage value of other cap.



Eg:-

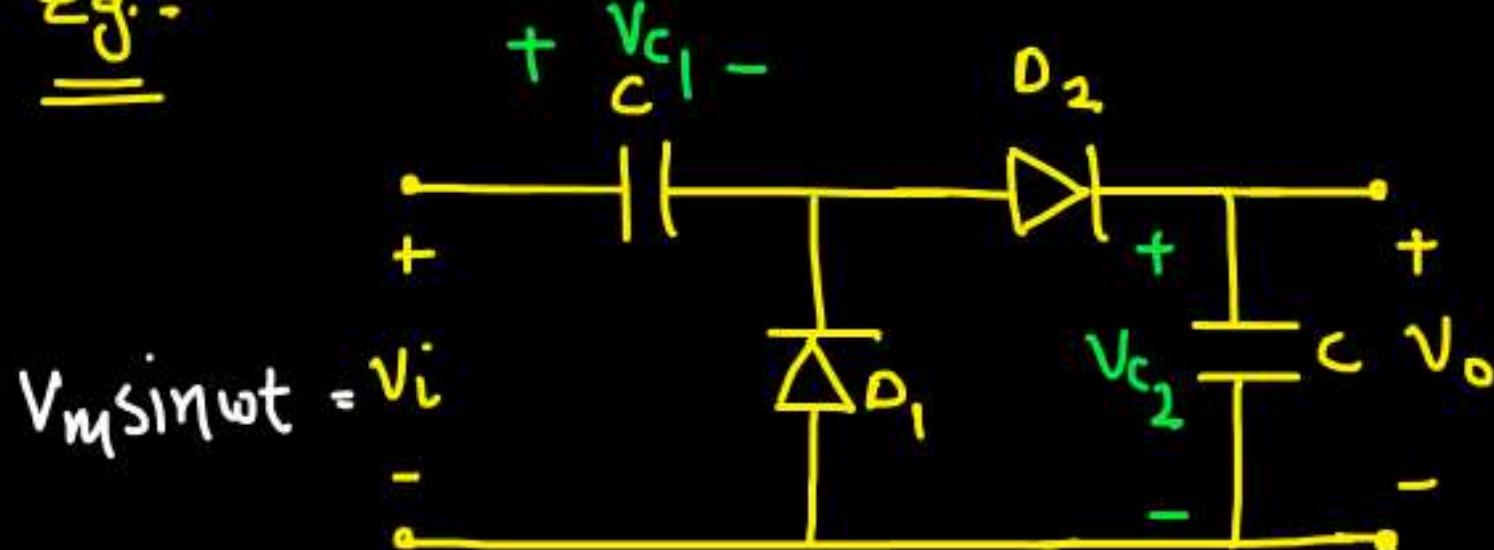


$$V_m \sin \omega t = V_i$$

→ Need to turn on D_1

when $V_i = -V_m$; D_1 will turn on

PrepFusion

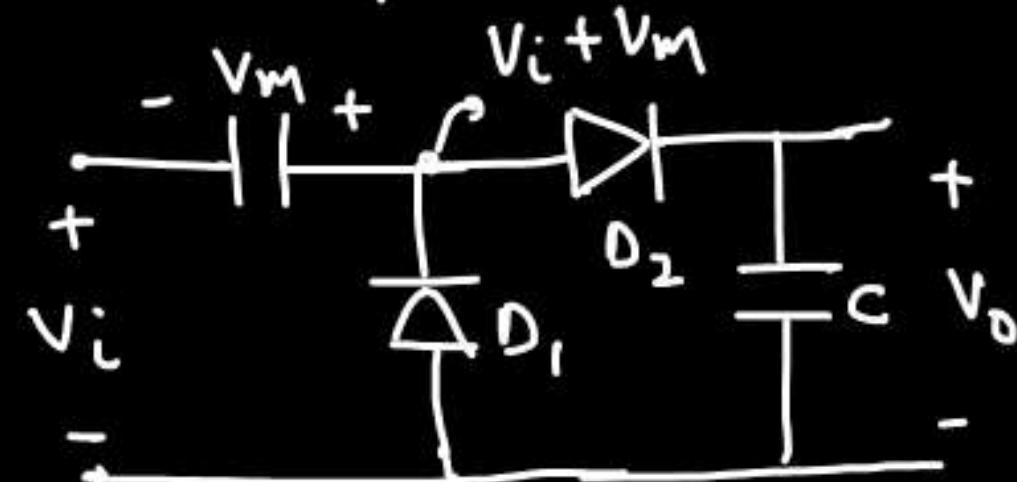$V_{c1} = -V_m \Rightarrow$ steady state voltage




⇒ need to turn on D_2

when $V_i = +V_m \Rightarrow D_2$ is on



$$V_o = 2V_m$$

Eg. 2

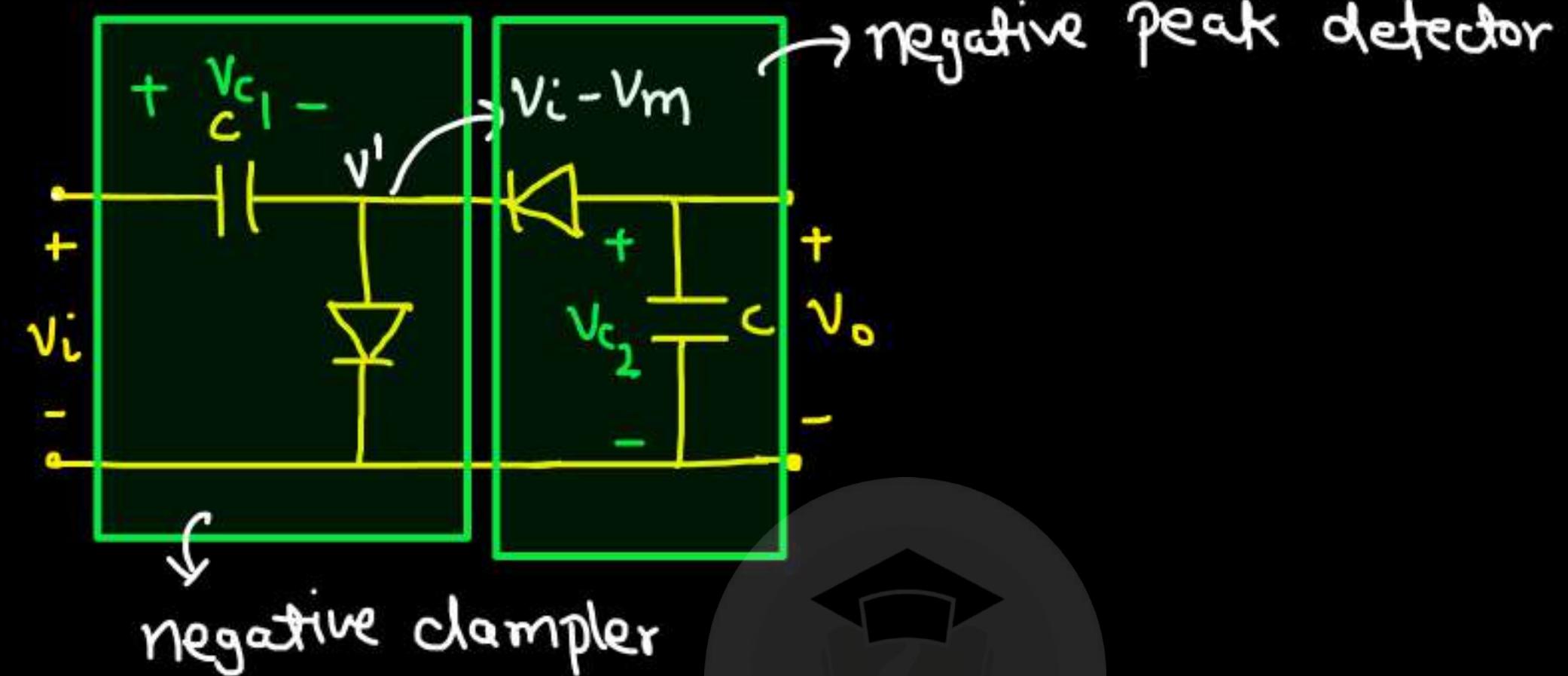

PrepFusion


$$V' = V_i - V_m$$

$$V' = V_m \sin \omega t - V_m$$

↳ negative peak is $-2V_m$

$$(V_0)_{S.S.} = -2V_m$$

$$(V_c)_{S.S.} = +V_m$$

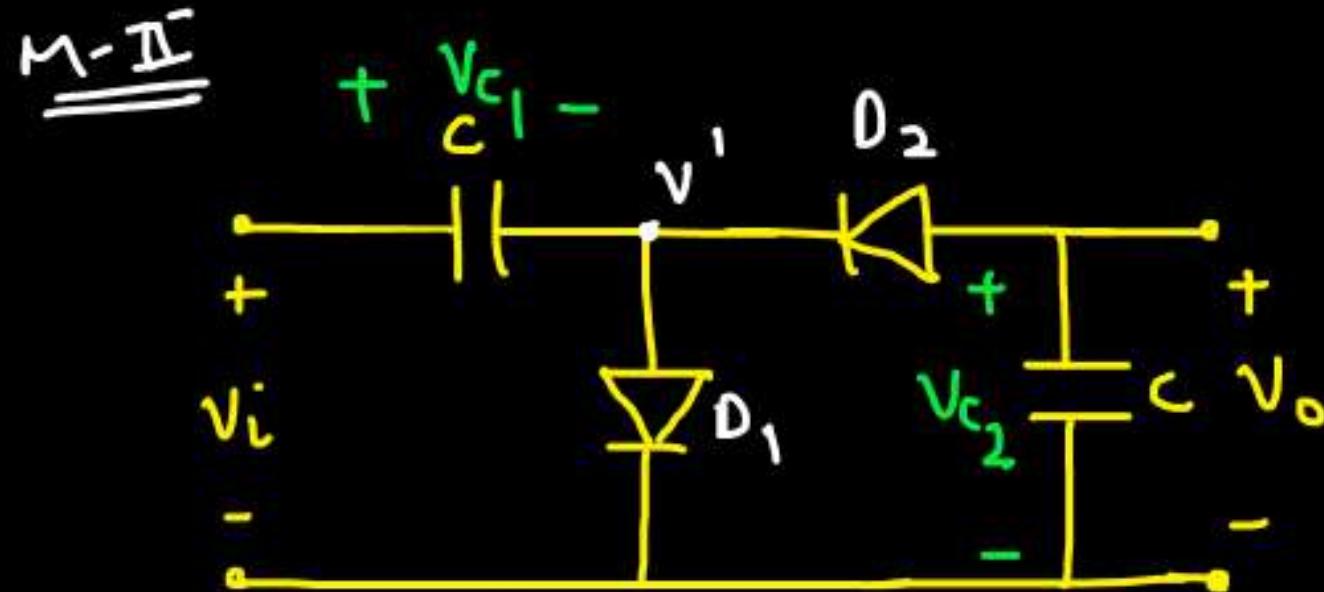


$V_i = V_m \Rightarrow$ diode D_1 turns ON

$$V_{C1} = +V_m =$$

$$V'_1 = V_i - V_m$$

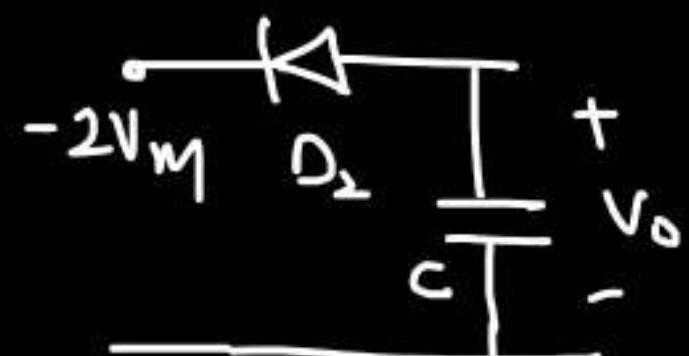
when $V_i = -V_m \Rightarrow$ diode D_2 is ON



$$(V_0)_{S.S.} = -2V_m = V_{C2}$$



Eg. 3

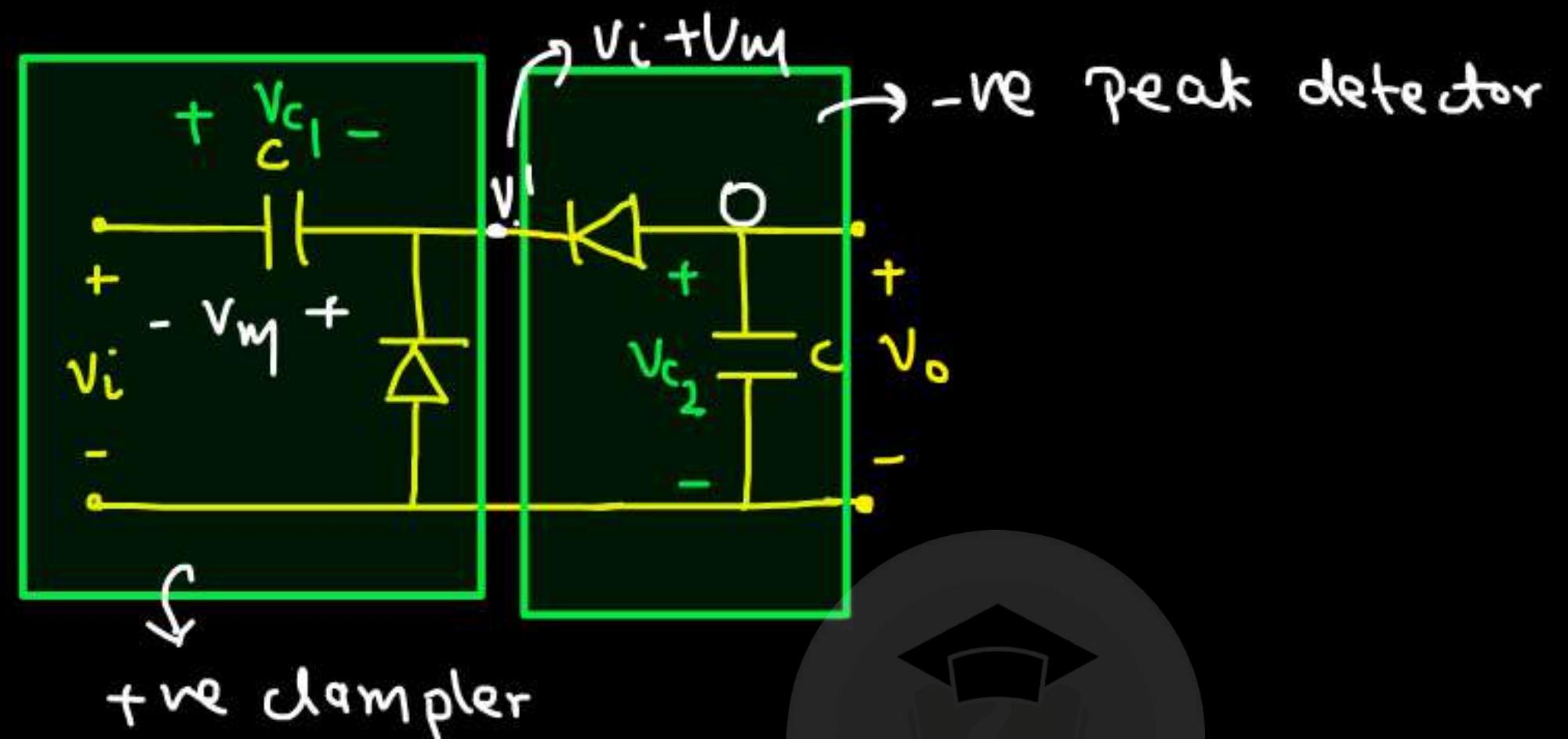

$$V^1 = V_i + V_m$$


$$V^1 = V_m \sin \omega t + V_m \Rightarrow \text{min value} = 0V$$

$$(V_o)_{S.S.} = 0V$$

$$(V_{c1})_{S.S.} = -V_m$$



Eg 4

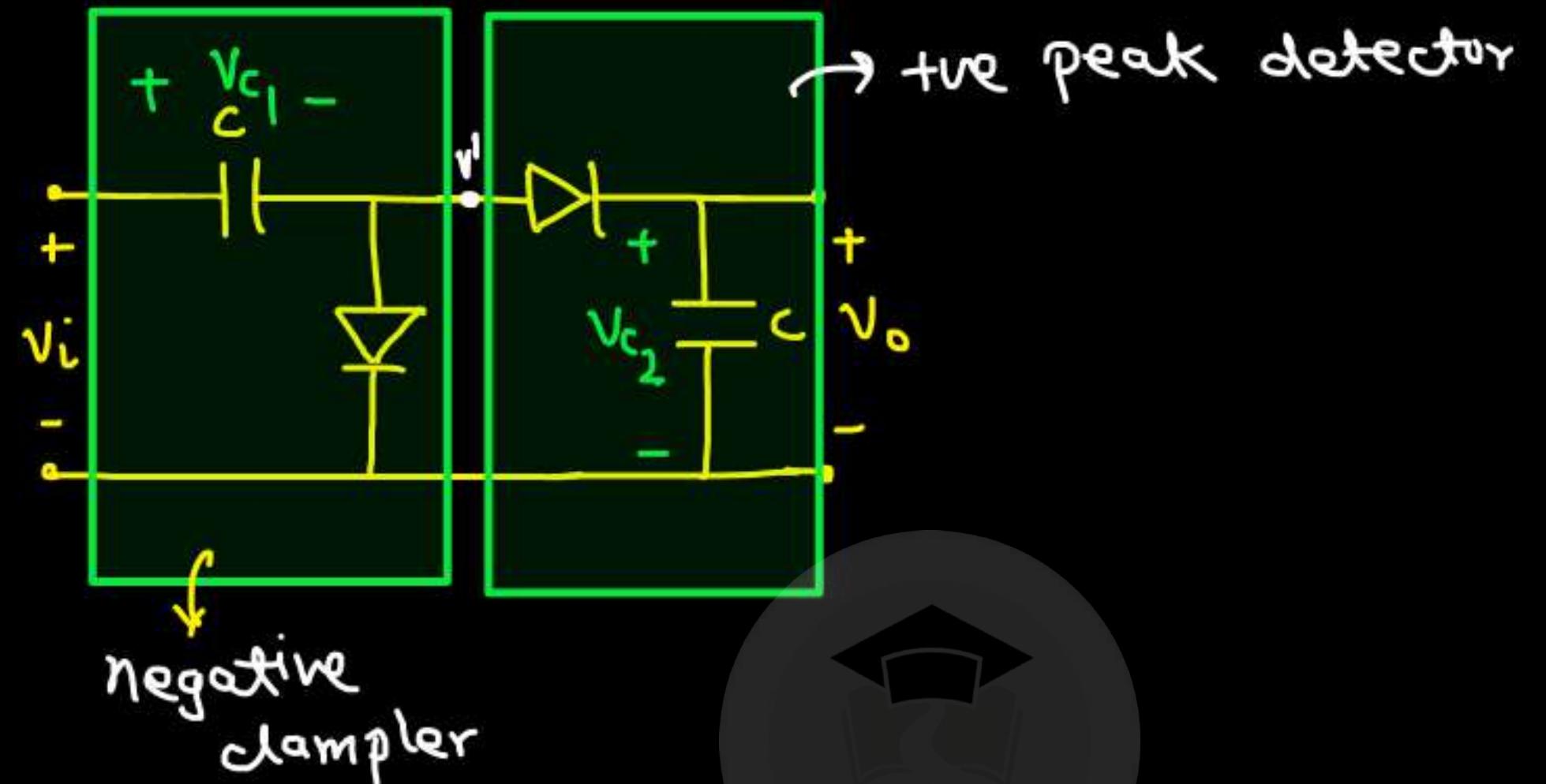


PrepFusion

$$V' = V_i - V_m = V_m \sin \omega t - V_m \Rightarrow \text{max value} = 0$$



$$\Rightarrow V_o = 0V$$

$$V_{c1} = V_m$$

Eg. 5 M-I

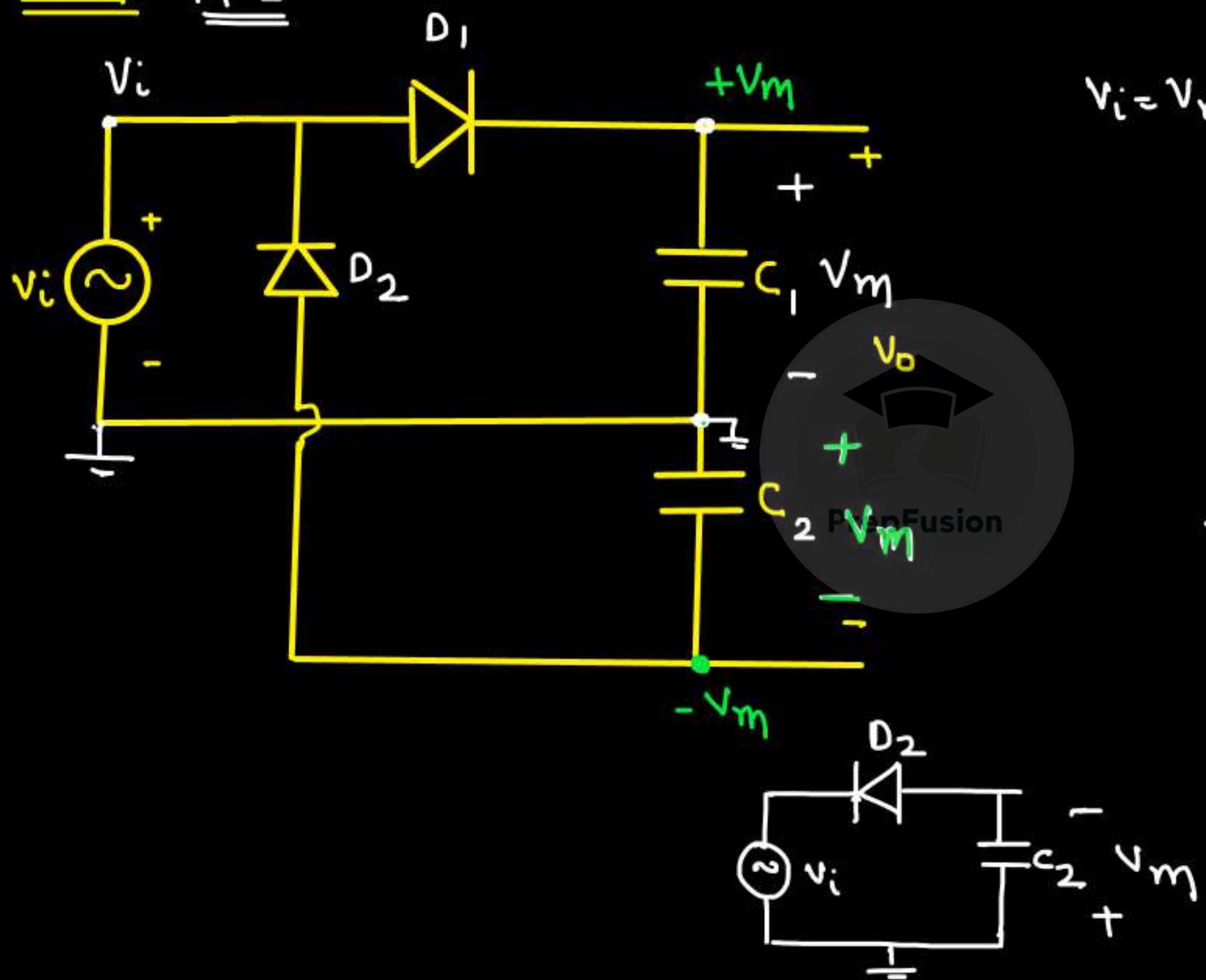


$$V_i = V_m \sin \omega t$$

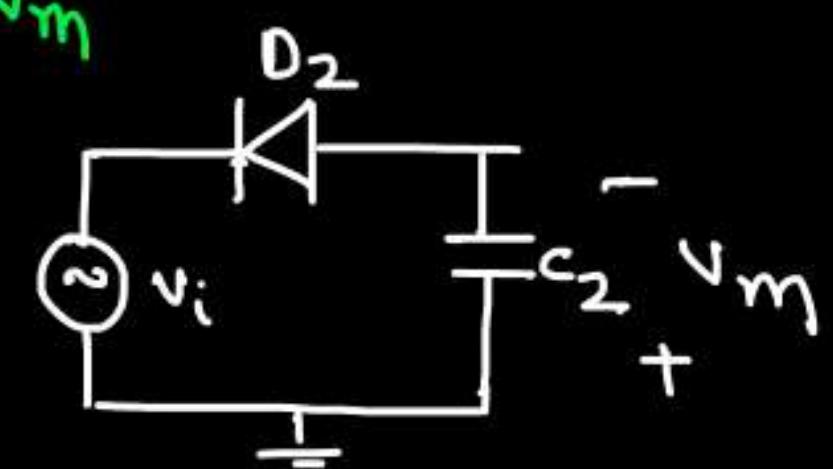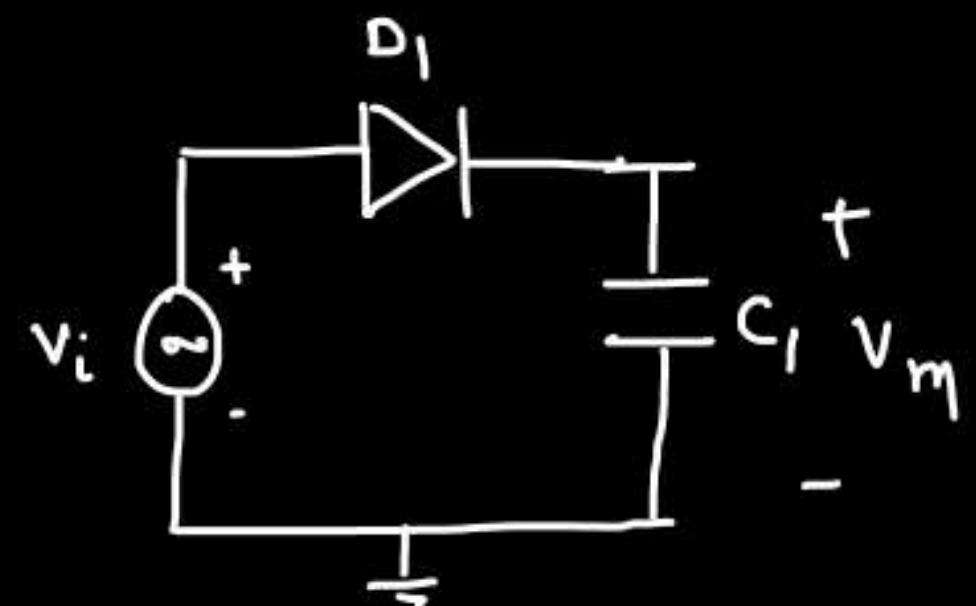

$$V_o = V_m - (-V_m)$$


$$V_o = 2V_m$$

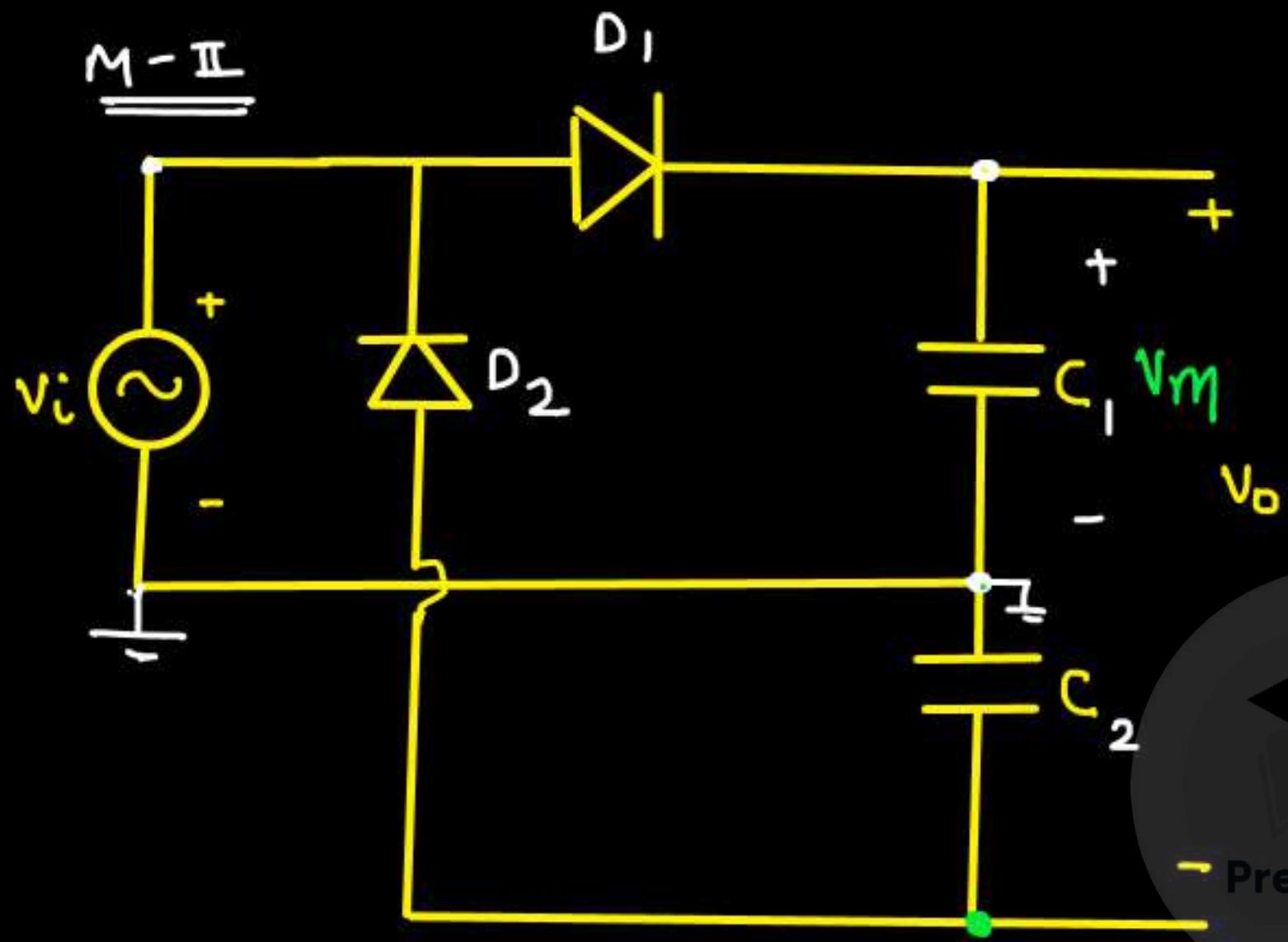



$$V_i = +V_m$$

$\Rightarrow D_1$ is ON

D_2 is OFF

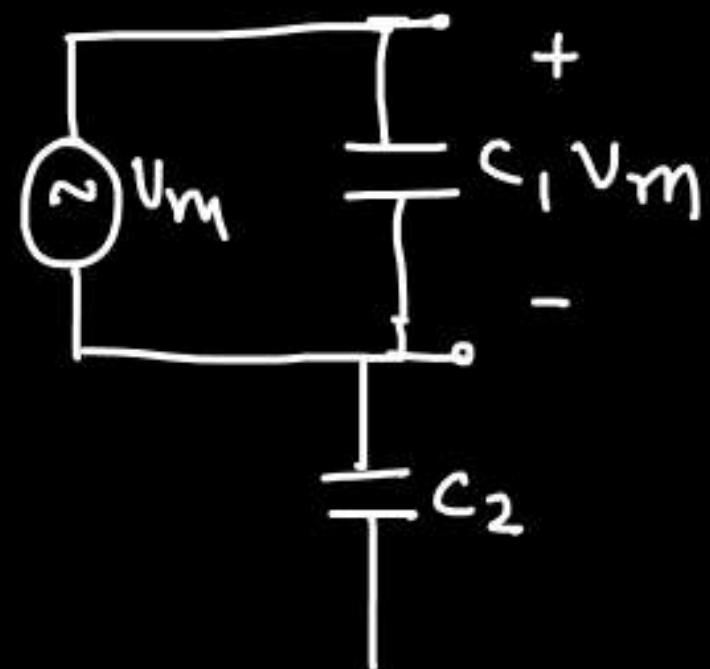

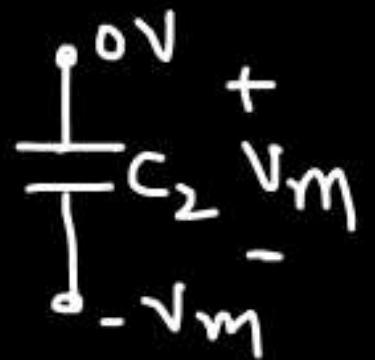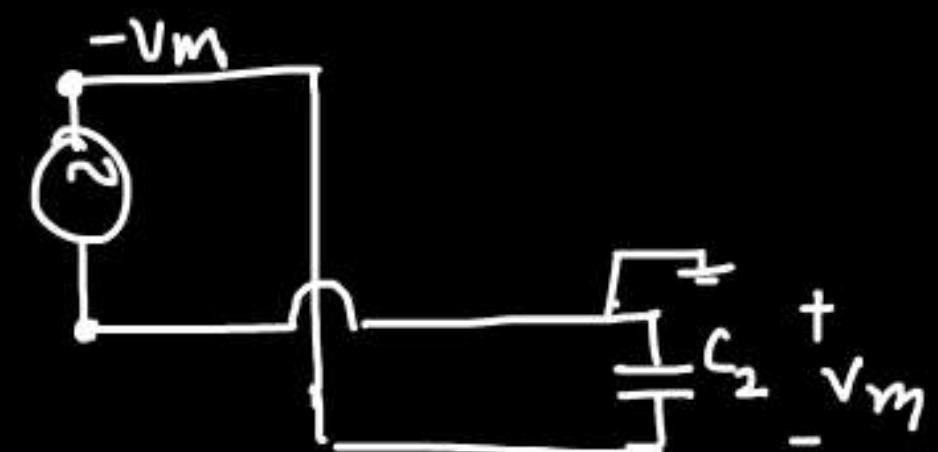$V_i = -V_m \Rightarrow D_1$ is OFF, D_2 is ON




Basic Semiconductor Physics | Analog Electro... Share 1/4

ANALOG ELECTRONICS

BASIC SEMICONDUCTOR PHYSICS



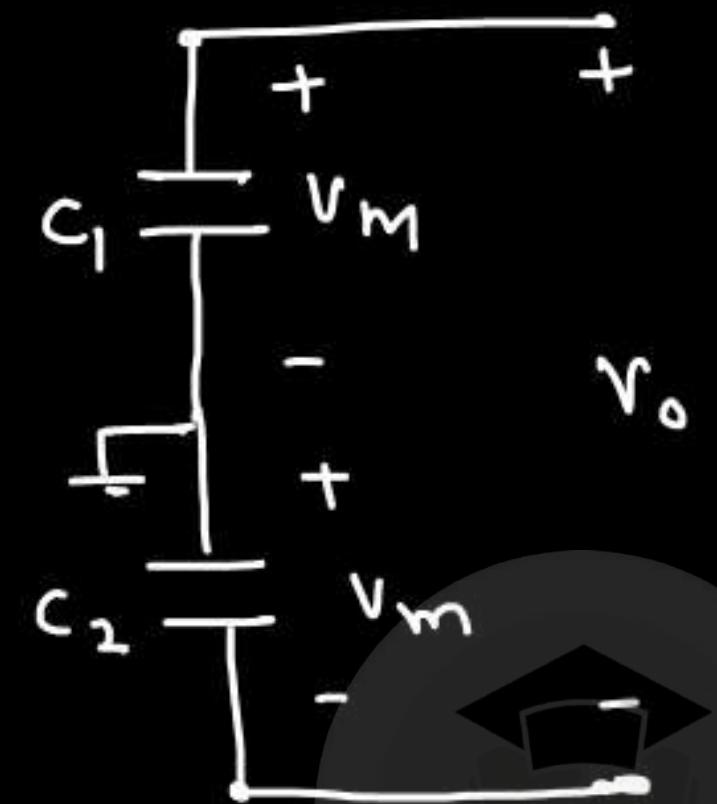
LECTURE-1
GATE 2025-26 (EC/EE/IN)
Watch on YouTube
AIR 27 (ECE)
AIR 45 (IN)



$$V_d = 2V_m$$


PrepFusion


* Voltage Tripler and Quadripller :-

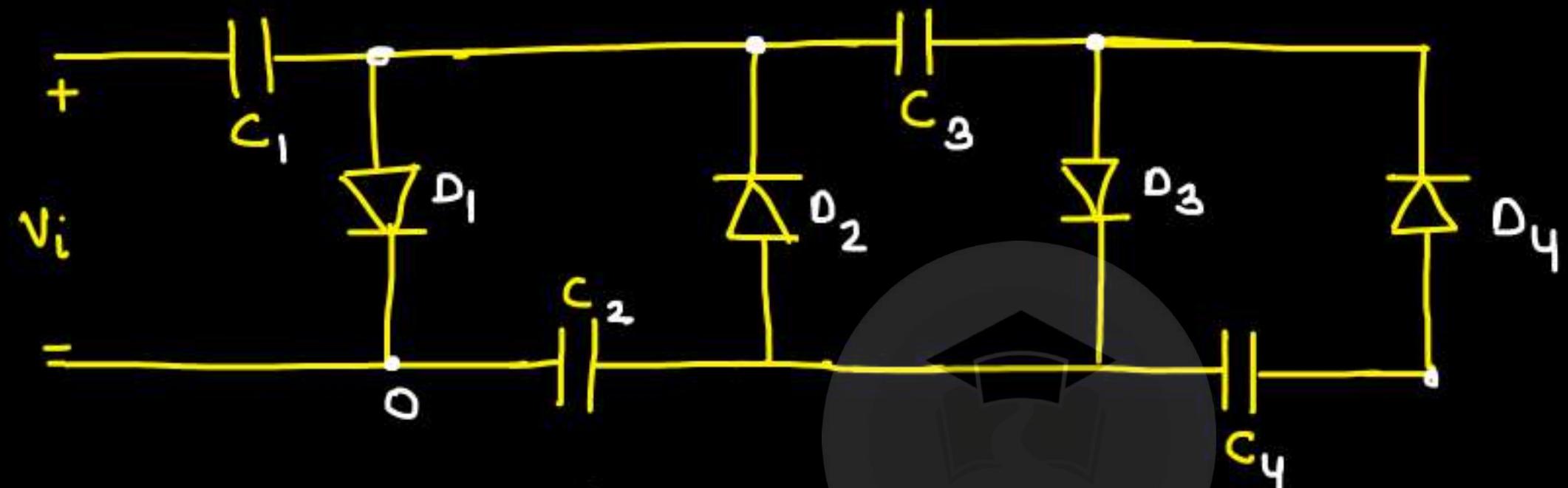

$\Rightarrow V_L = +V_m \Rightarrow D_1$ is ON, D_3 is ON, D_2 and D_4 is OFF
 $\Rightarrow C_1$ charges to $+V_m$

$$V_{C_1} = +V_m$$

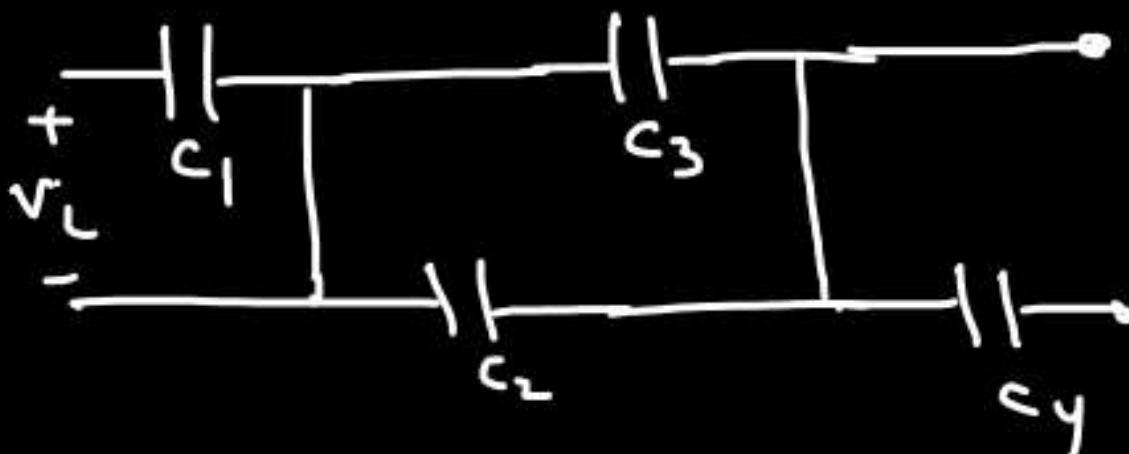


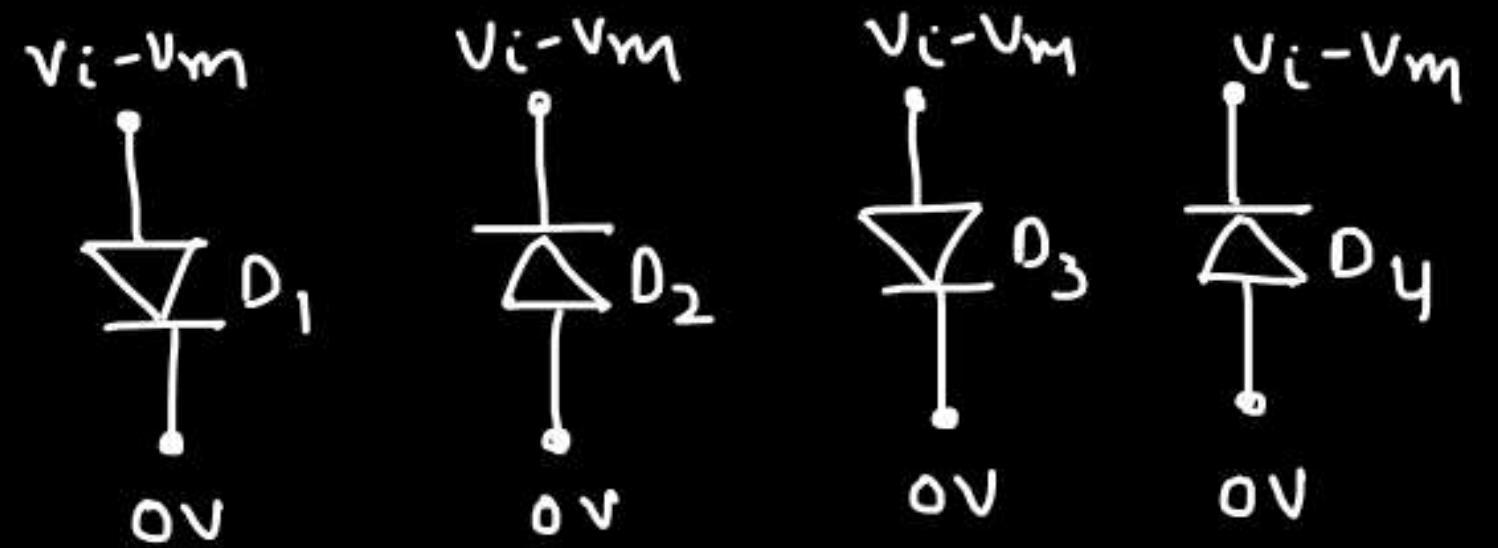

(ii) $V_i = -V_m$

D_1 and D_3 are off


D_2 and D_4 are on

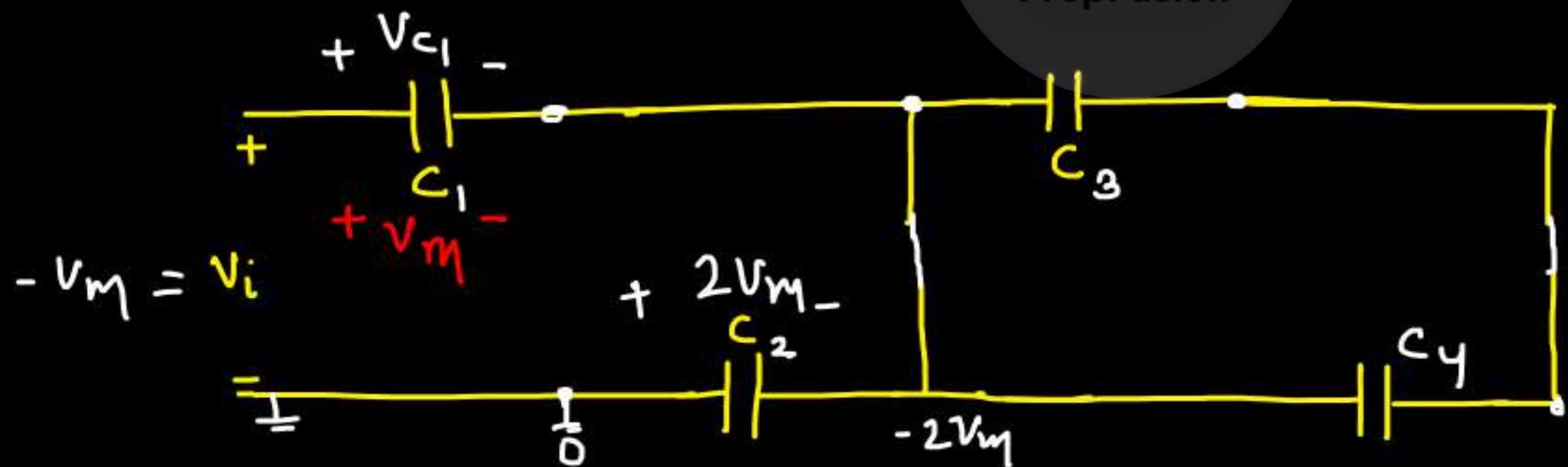


$-V_m = V_i$



C_4


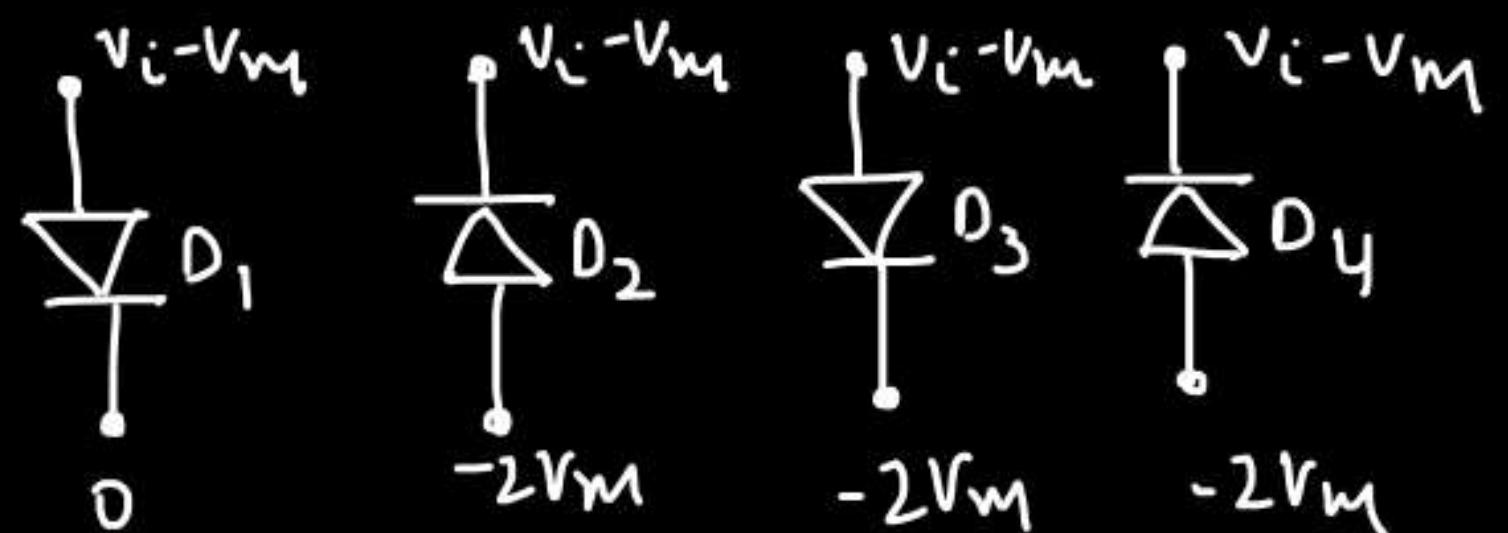


(iii)

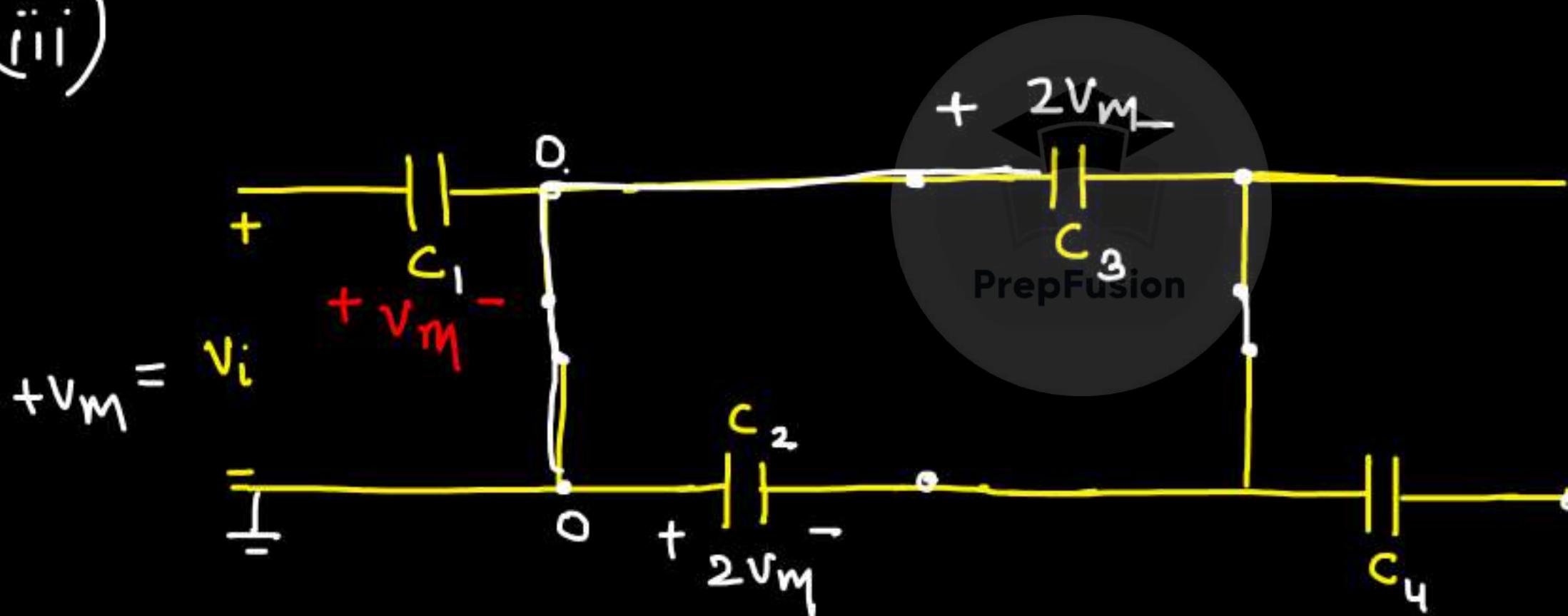


$$+V_m = V_i$$

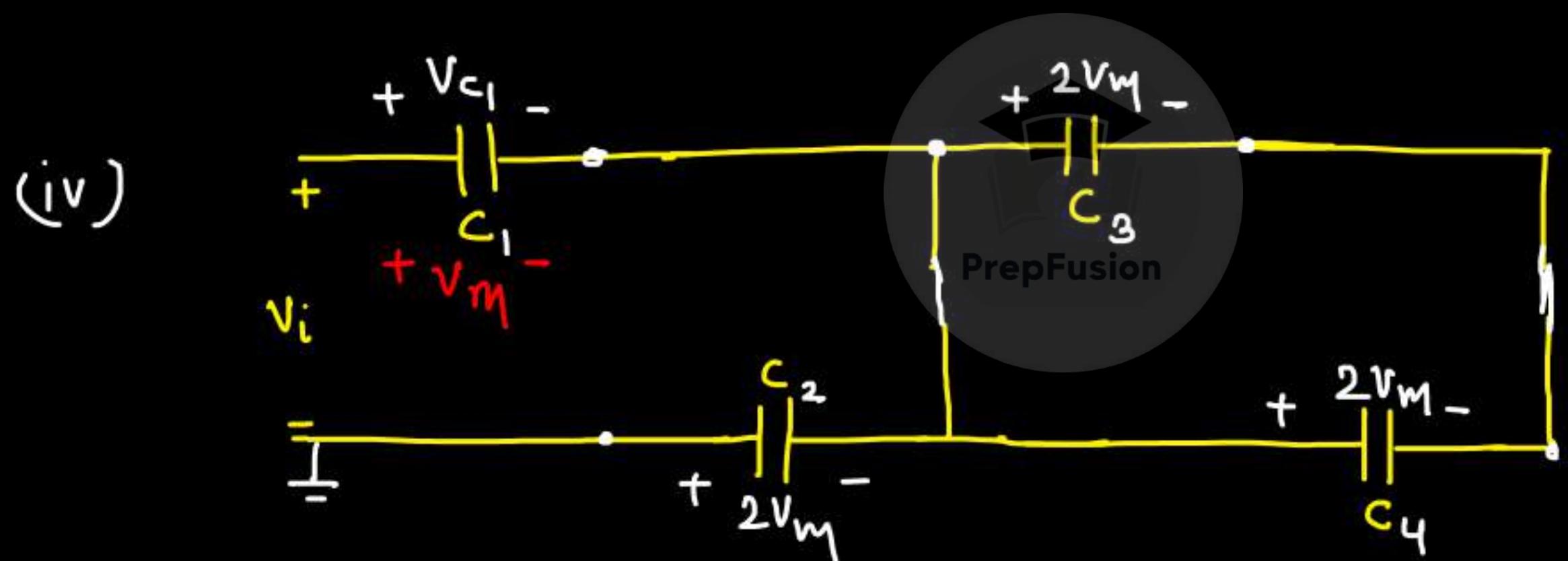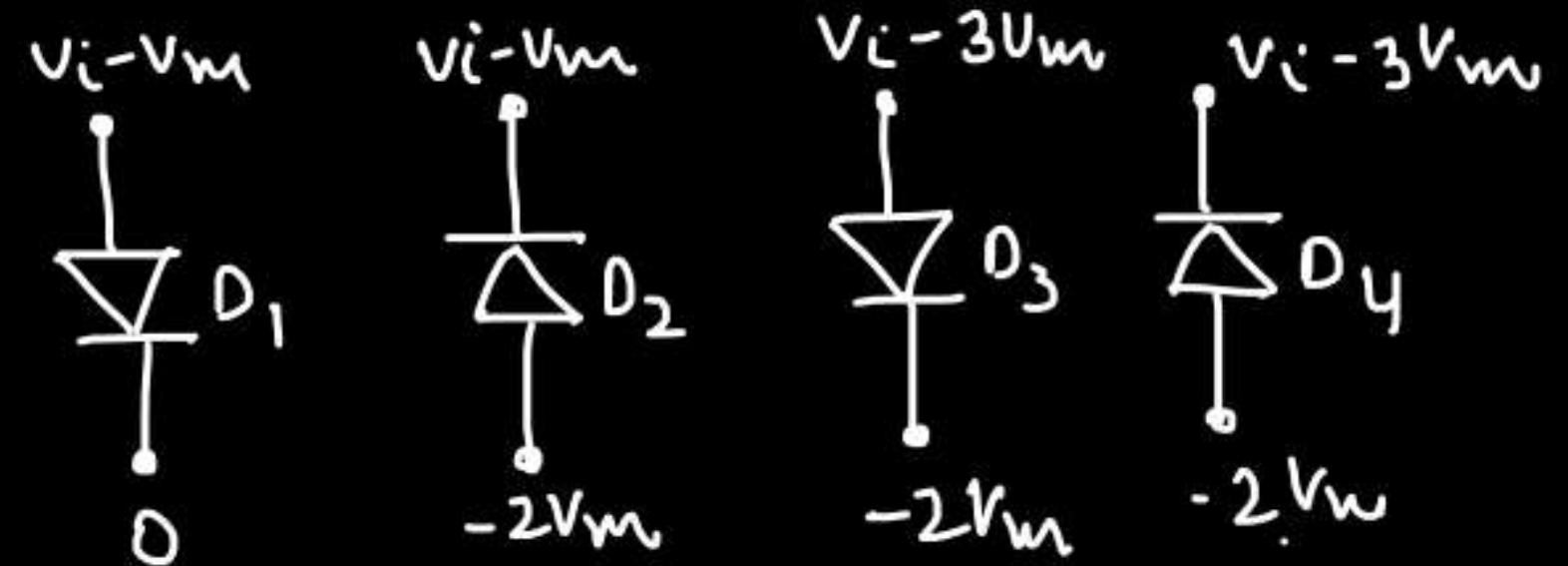$V_i = +V_m \Rightarrow D_1$ and D_3 are on, D_4 and D_2 are off




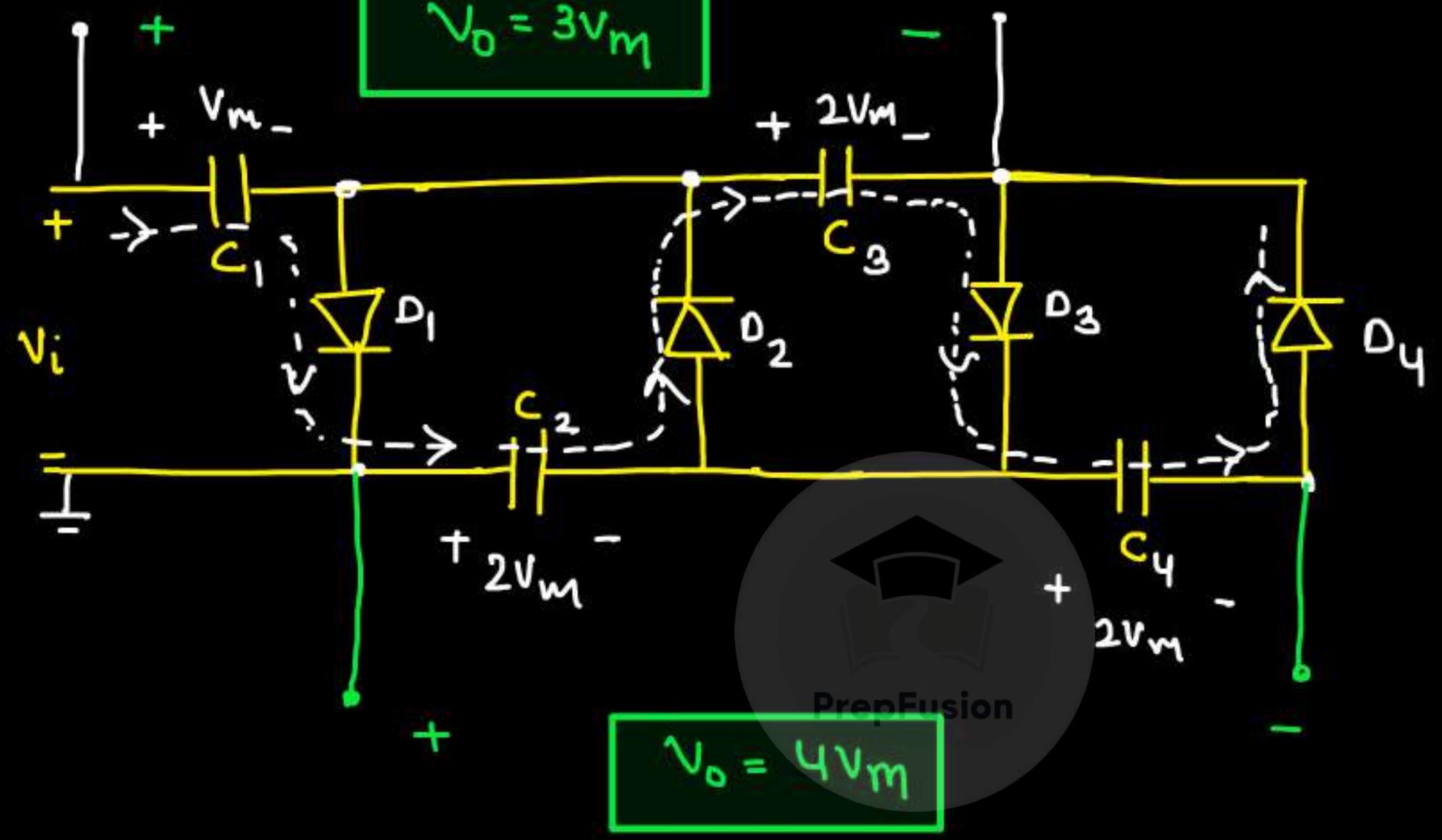$V_i = -V_m \Rightarrow D_1, D_3$ are OFF ; D_2, D_4 are ON




PrepFusion

e.g. 1

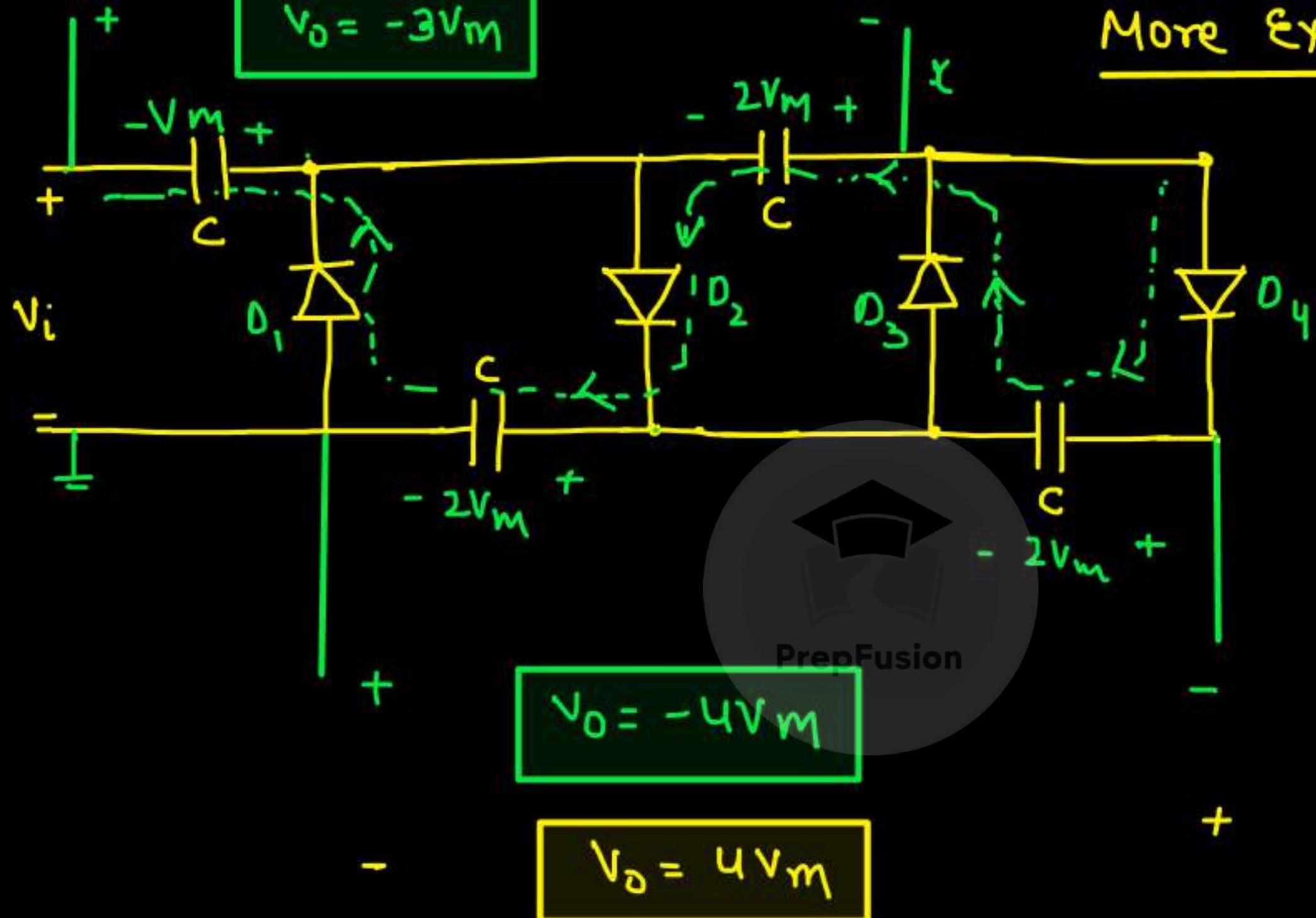


More Examples

Eg. 2

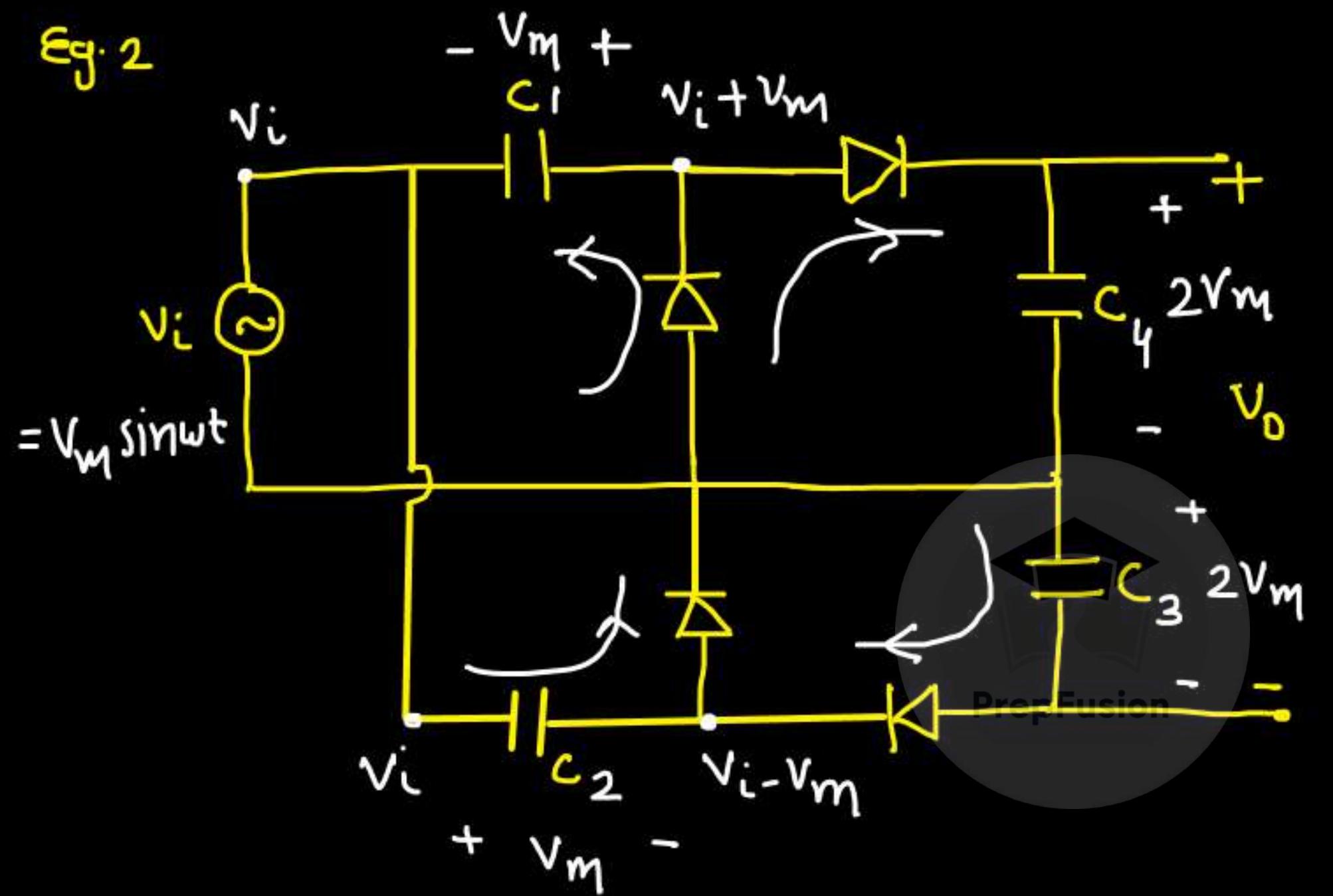


$$V_D = 2V_m + 2V_m$$

$$V_D = 4V_m$$

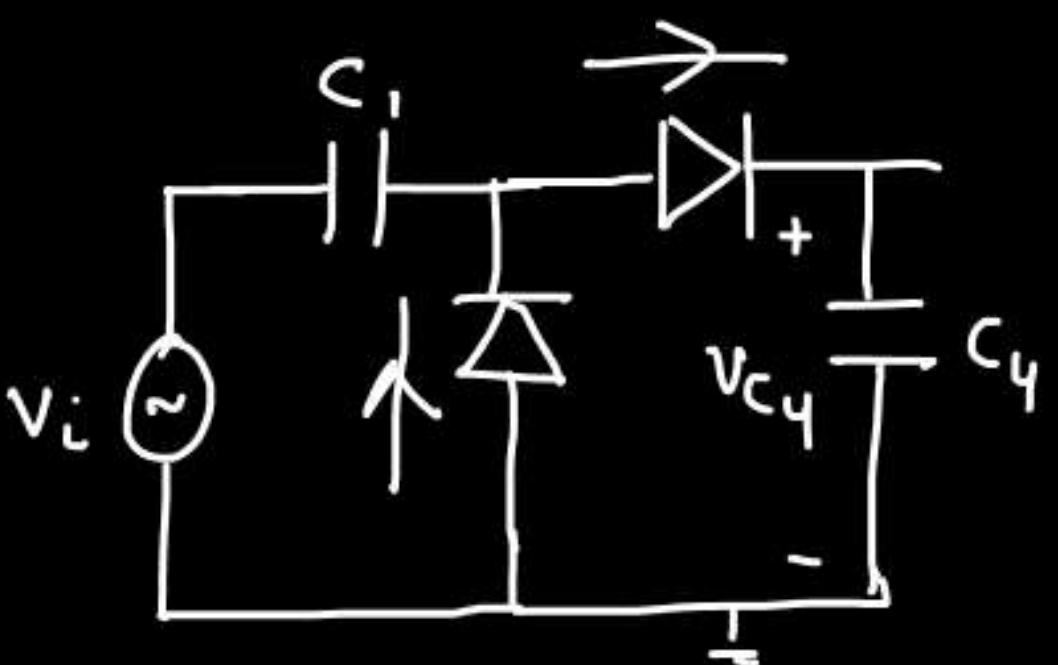

Eg.3

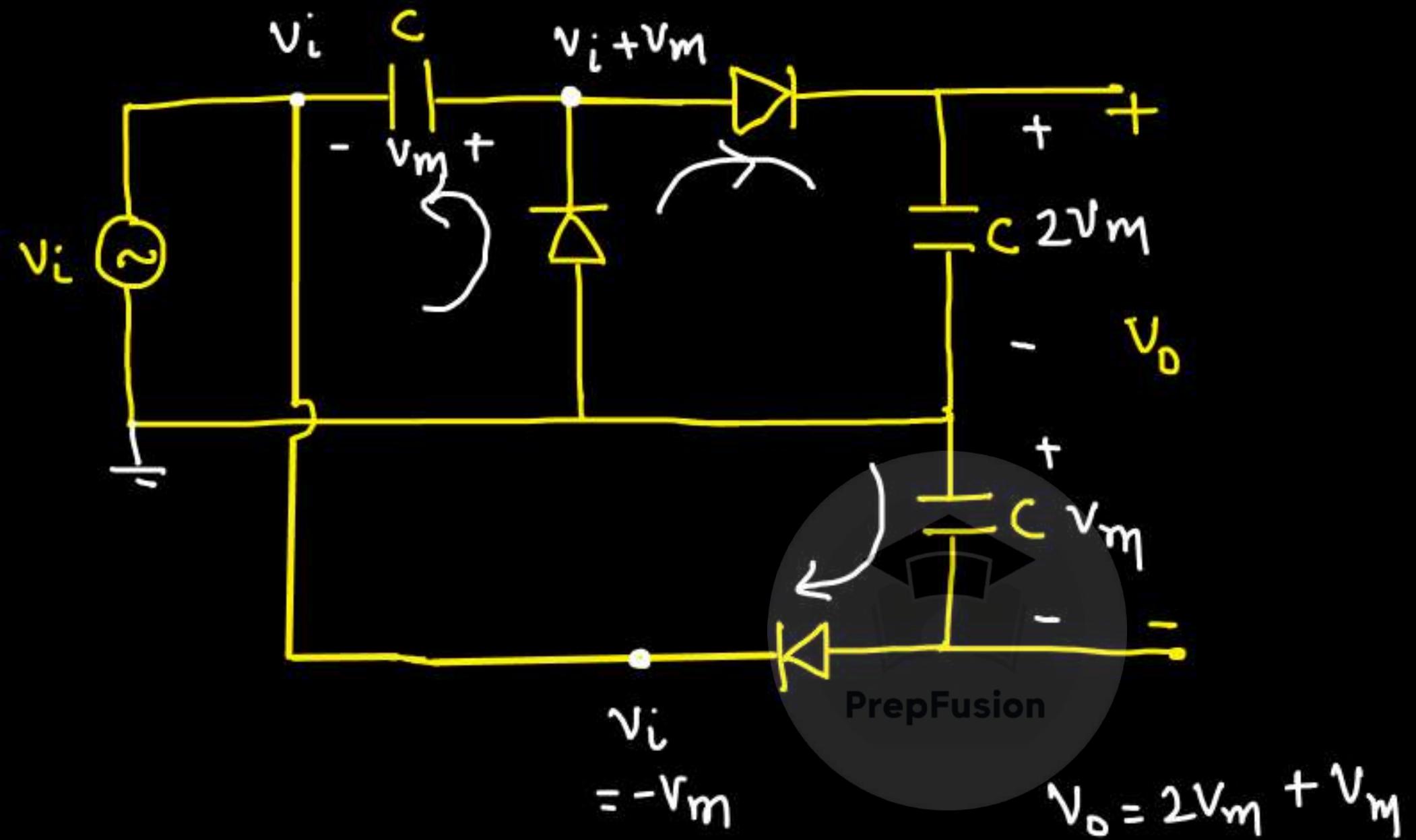


$$v_i = -v_m$$

$$v_o = 2v_m + v_m$$

$$v_o = 3v_m$$

Eg. 4

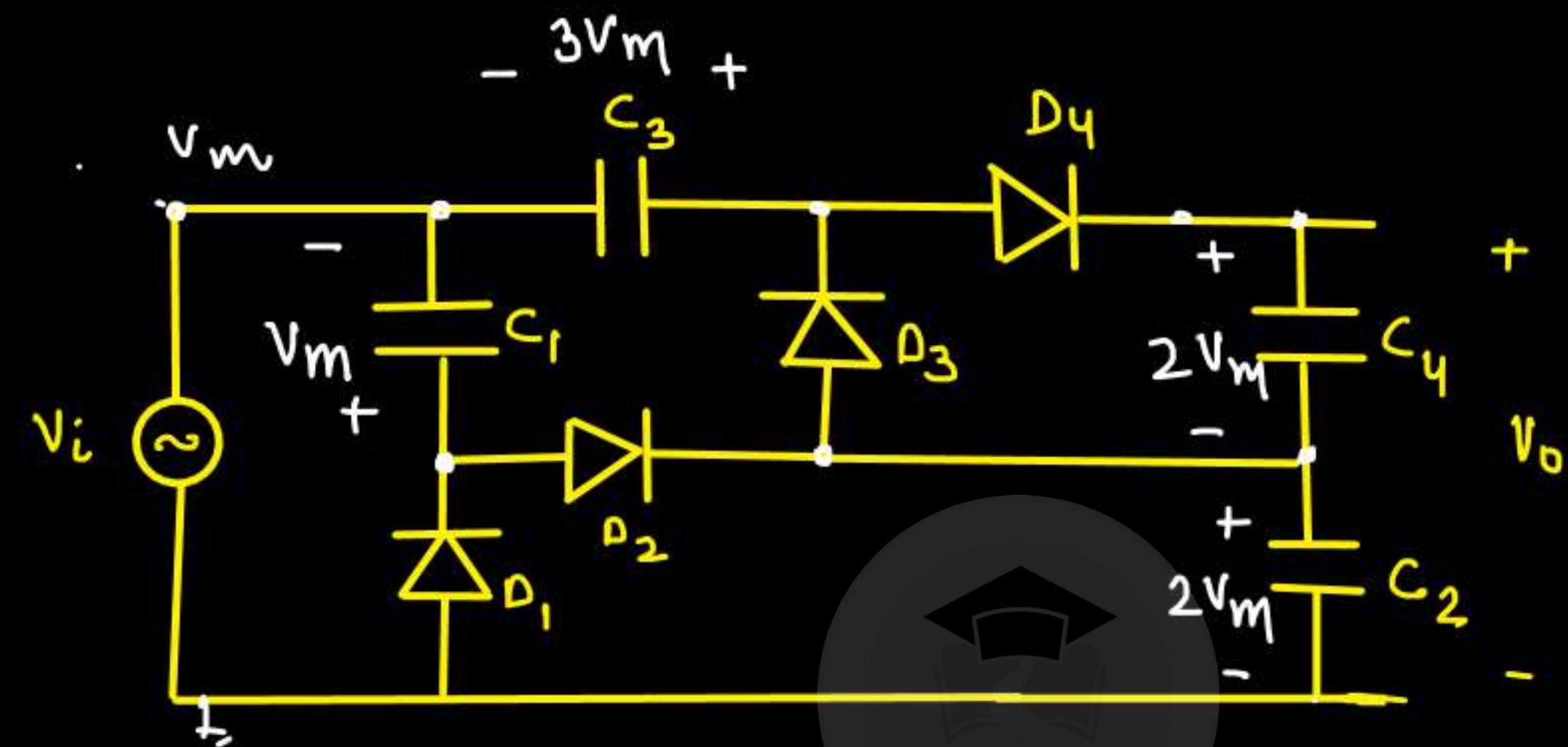


NEVER
CROSS
DIODE

- ① $v_i = -v_m$
- ② $v_i = +v_m$
- ③ $v_i = -v_m$
- ④ $v_i = +v_m$

$$v_o = 2v_m + 2v_m$$


$$v_o = 4v_m$$

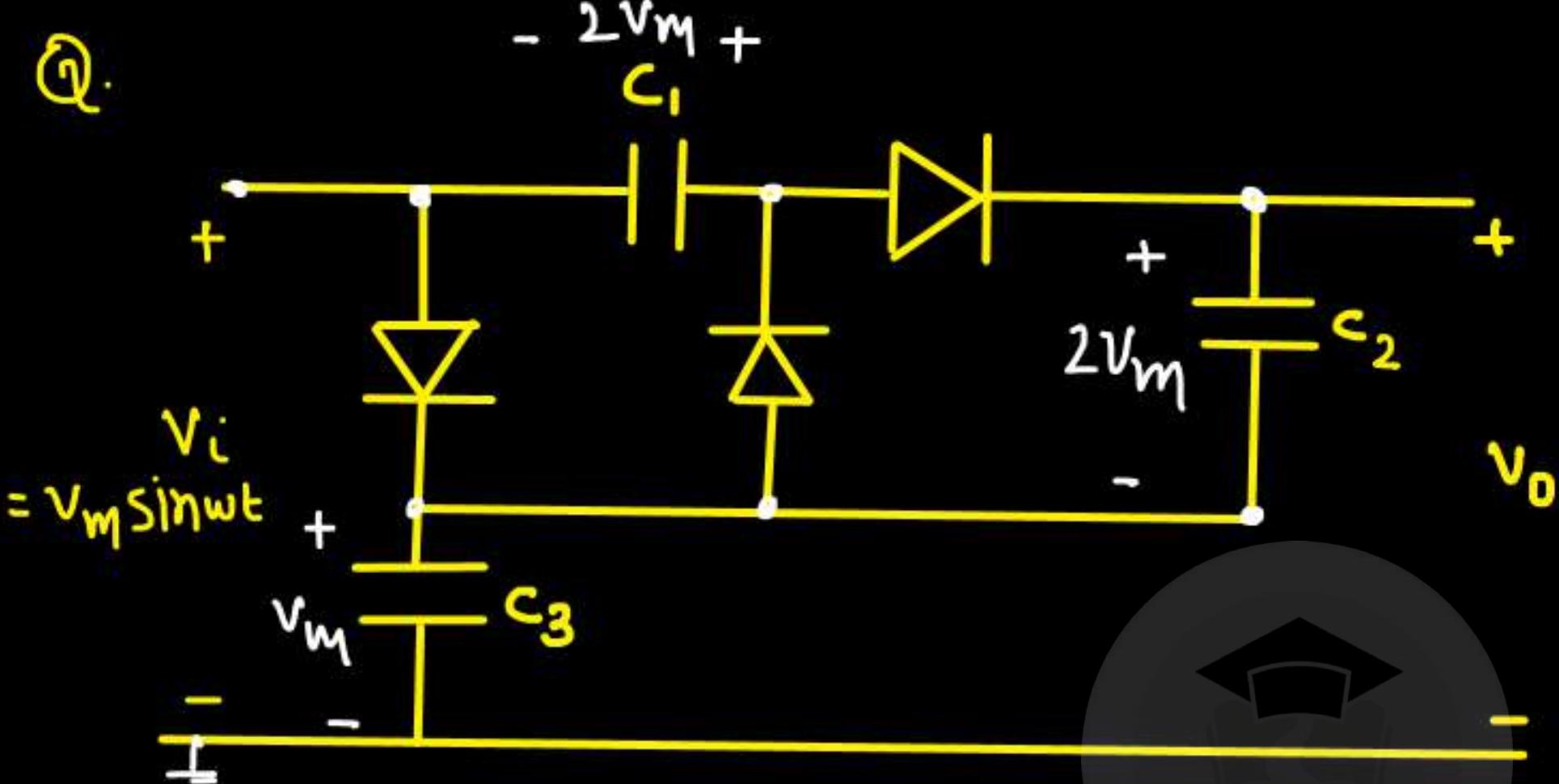

① $V_i = +V_m$

② $V_i = -V_m$


③ $V_i = +V_m$

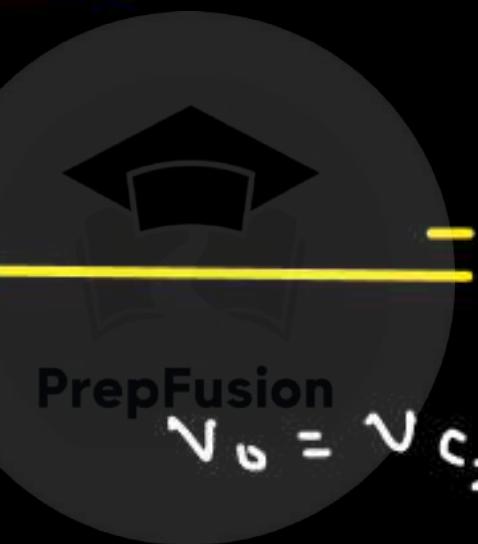

$$V_o = V_{C_2} + V_{C_3}$$

$$V_o = 2V_m + V_m$$

$$V_o = 3V_m$$

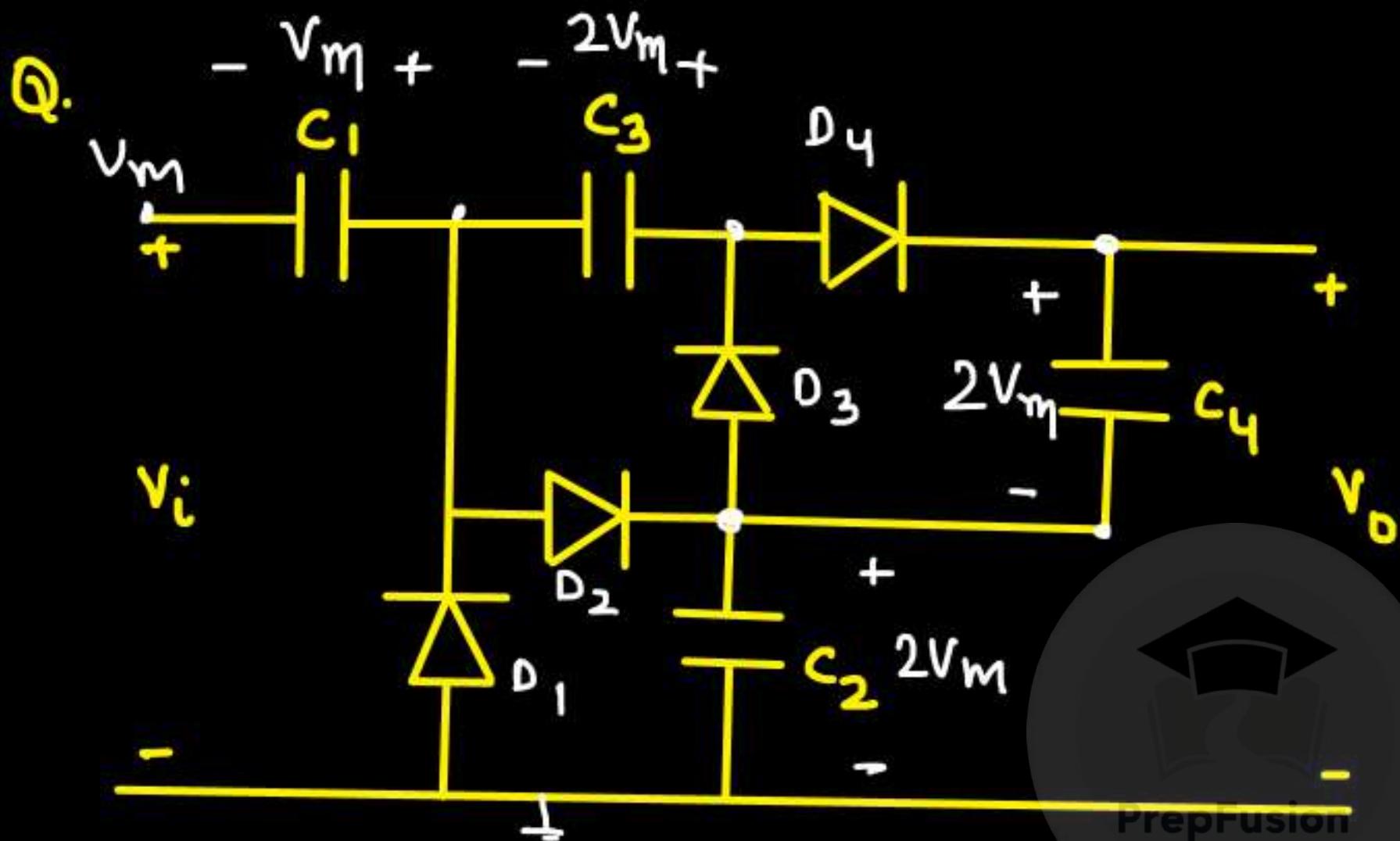

- ① $V_i = -V_m$
- ② $V_i = +V_m$
- ③ $V_i = -V_m$
- ④ $V_i = +V_m$



$$V_d = V_{C_4} + V_{C_2}$$

$$V_d = 2V_m + 2V_m$$


$$\boxed{V_d = 4V_m}$$

Assignment - 3

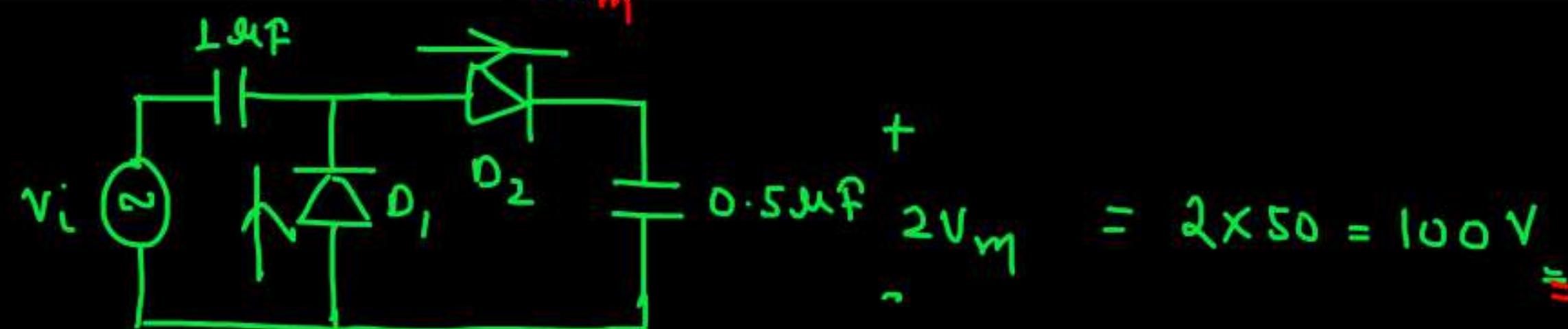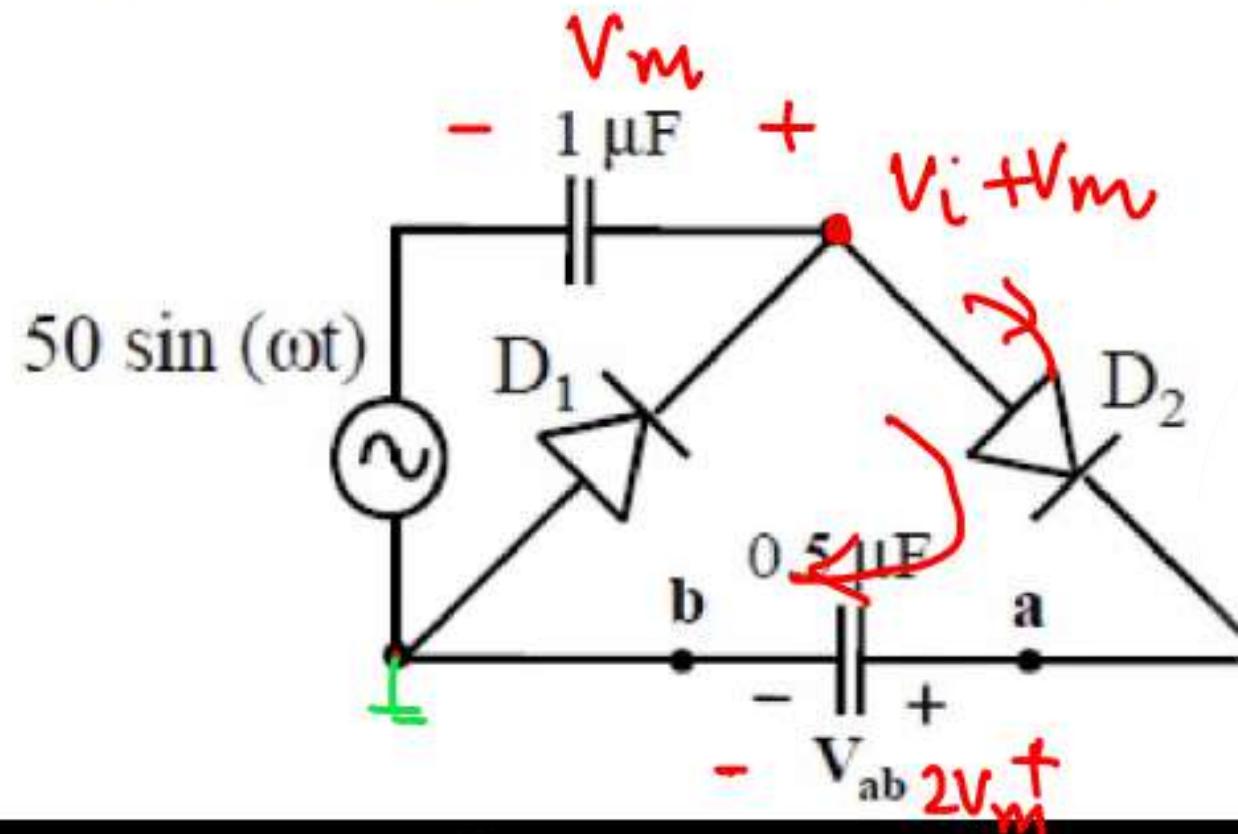In the circuit shown, assume that diodes D₁ and D₂ are ideal. In the steady state condition, the average voltage V_{ab} (in Volts) across the 0.5 μF capacitor is ____.



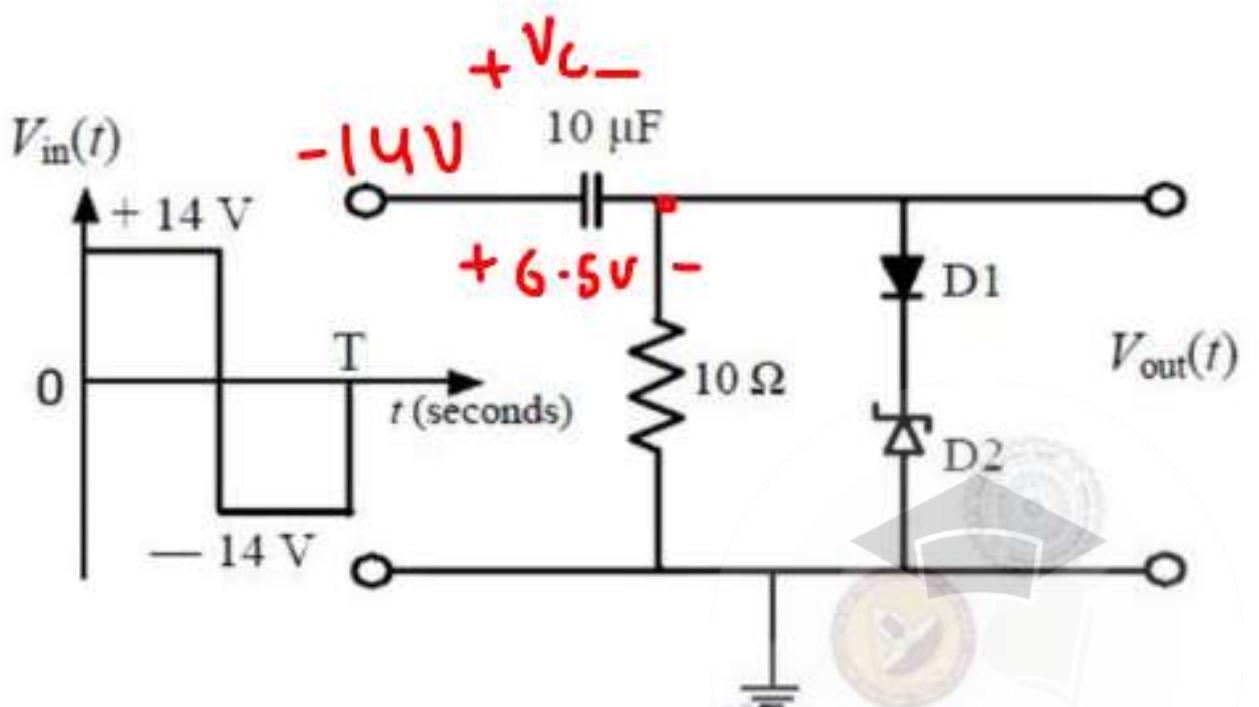In the figure, D1 is a real silicon *pn* junction diode with a drop of 0.7 V under forward bias condition and D2 is a Zener diode with breakdown voltage of -6.8 V. The input $V_{in}(t)$ is a periodic square wave of period T , whose one period is shown in the figure.



Assuming $10\tau \ll T$, where τ is the time constant of the circuit, the maximum and minimum values of the output waveform are respectively,

- (A) 7.5 V and -20.5 V
- (B) 6.1 V and -21.9 V
- (C) 7.5 V and -21.2 V
- (D) 6.1 V and -22.6 V

@ $t=0$
 $V_{in}=14$, $V_c=0$

D₁ turns on

D₂ goes into
B·D

