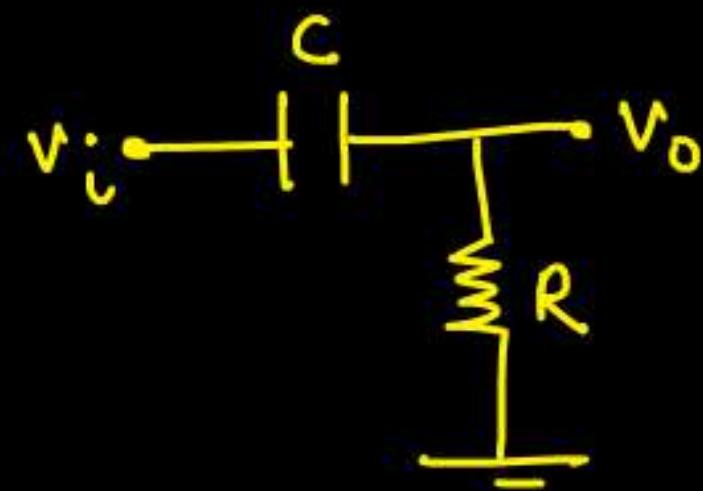


②




$$H(s) = \frac{SRC}{SRC + L}$$


Zero at 0
Pole at $-1/R_C$

$$H(0) = 0 = -\infty \text{ dB}$$

$$H(\infty) = 1 = 0 \text{ dB}$$

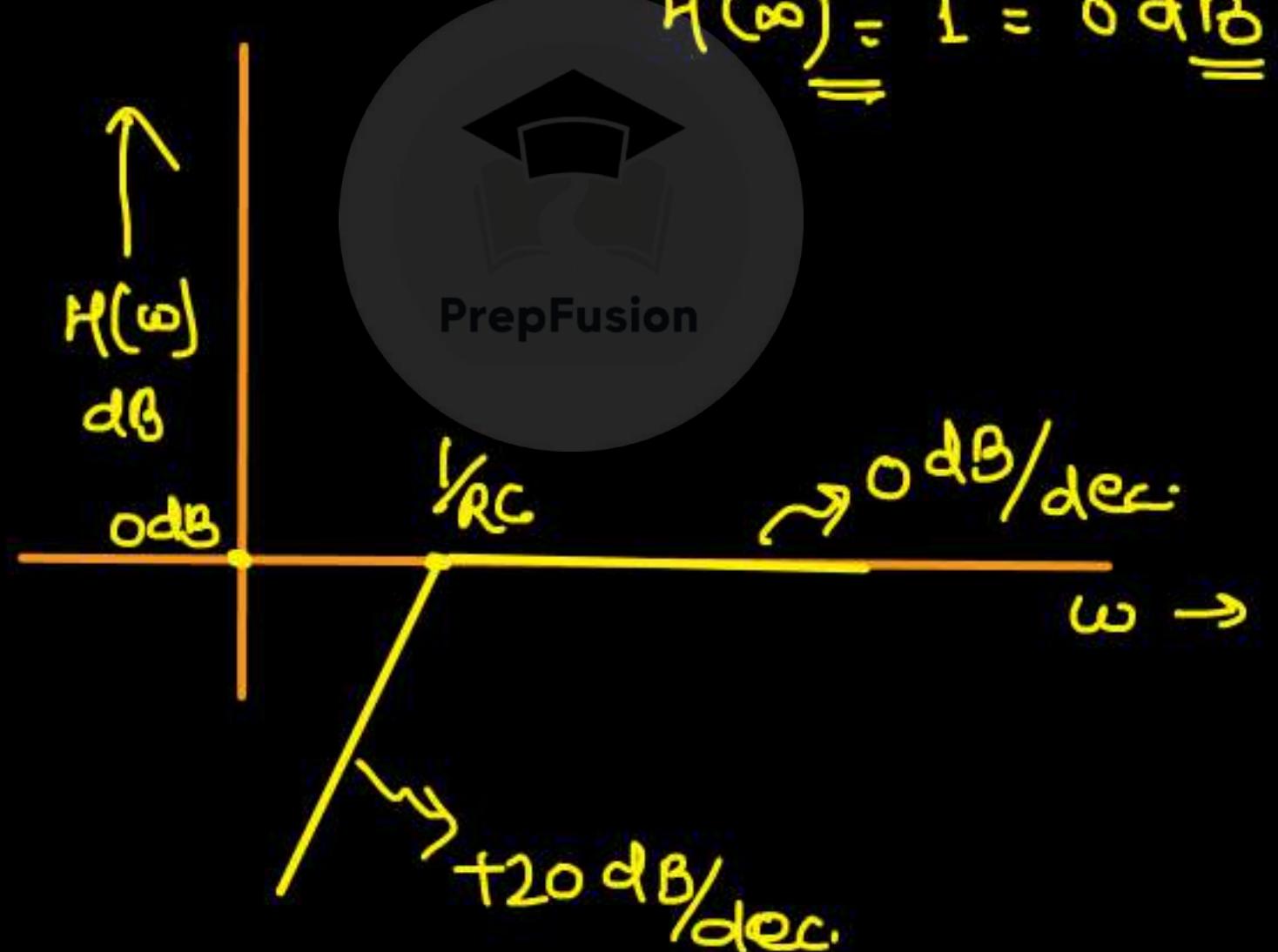


③

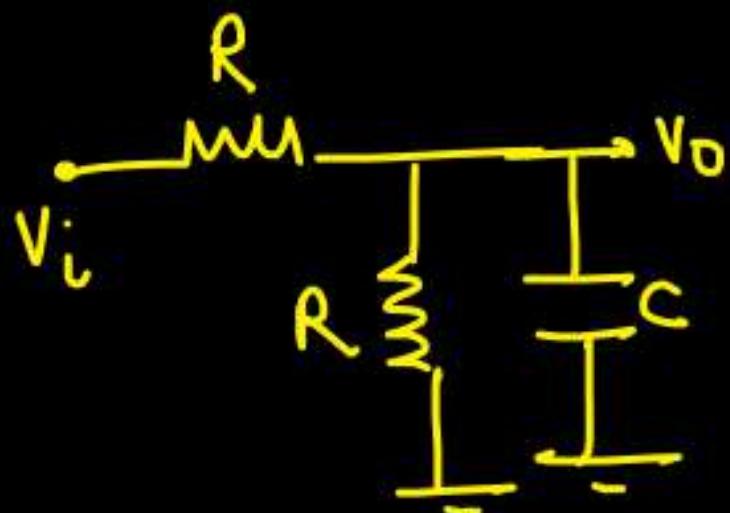


$$H(s) = \frac{1}{sRC + 1} \rightarrow \text{pole at } \frac{1}{RC}$$

$$H(0) = \frac{1}{2} e^{-Q_0 \log_{10} 2} =$$

$$H(\infty) = 0 = -\infty \text{ dB}$$

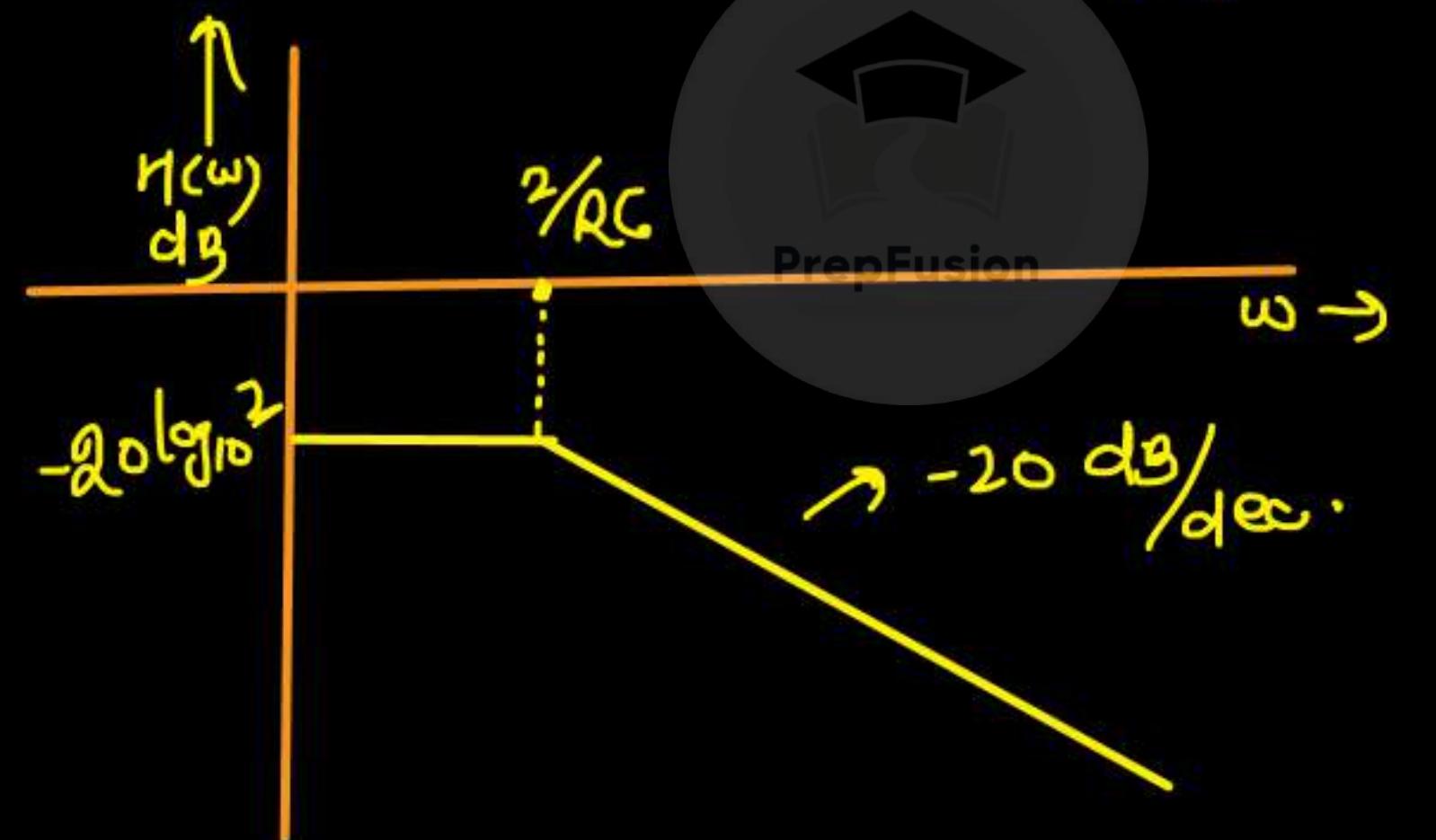

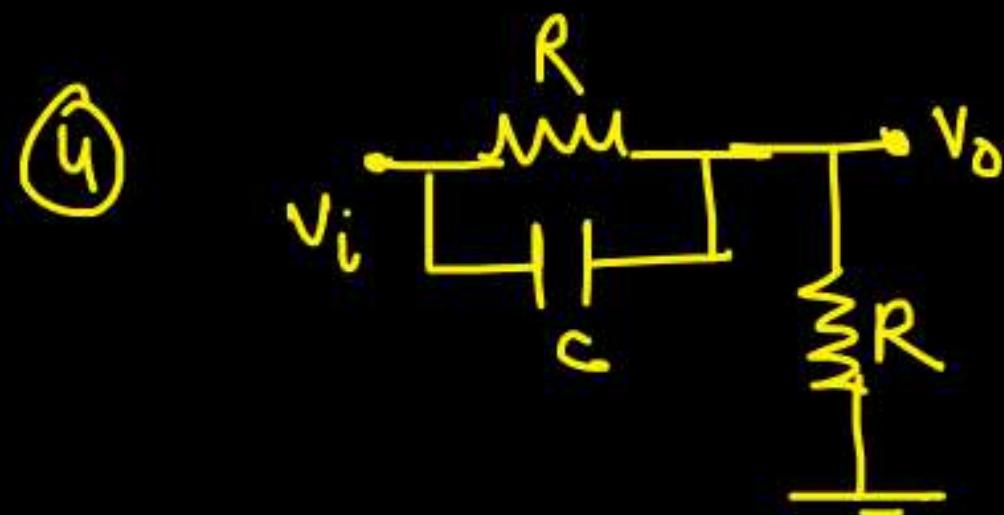


$$H(s) = \frac{SRC + L}{SRC + 2}$$

Zero = $\frac{L}{RC}$


Pole = $\frac{2}{RC}$

$$H(0) = \frac{1}{2} = -20 \log_{10} 2$$

$$H(\infty) = 1 = 0 \text{ dB}$$

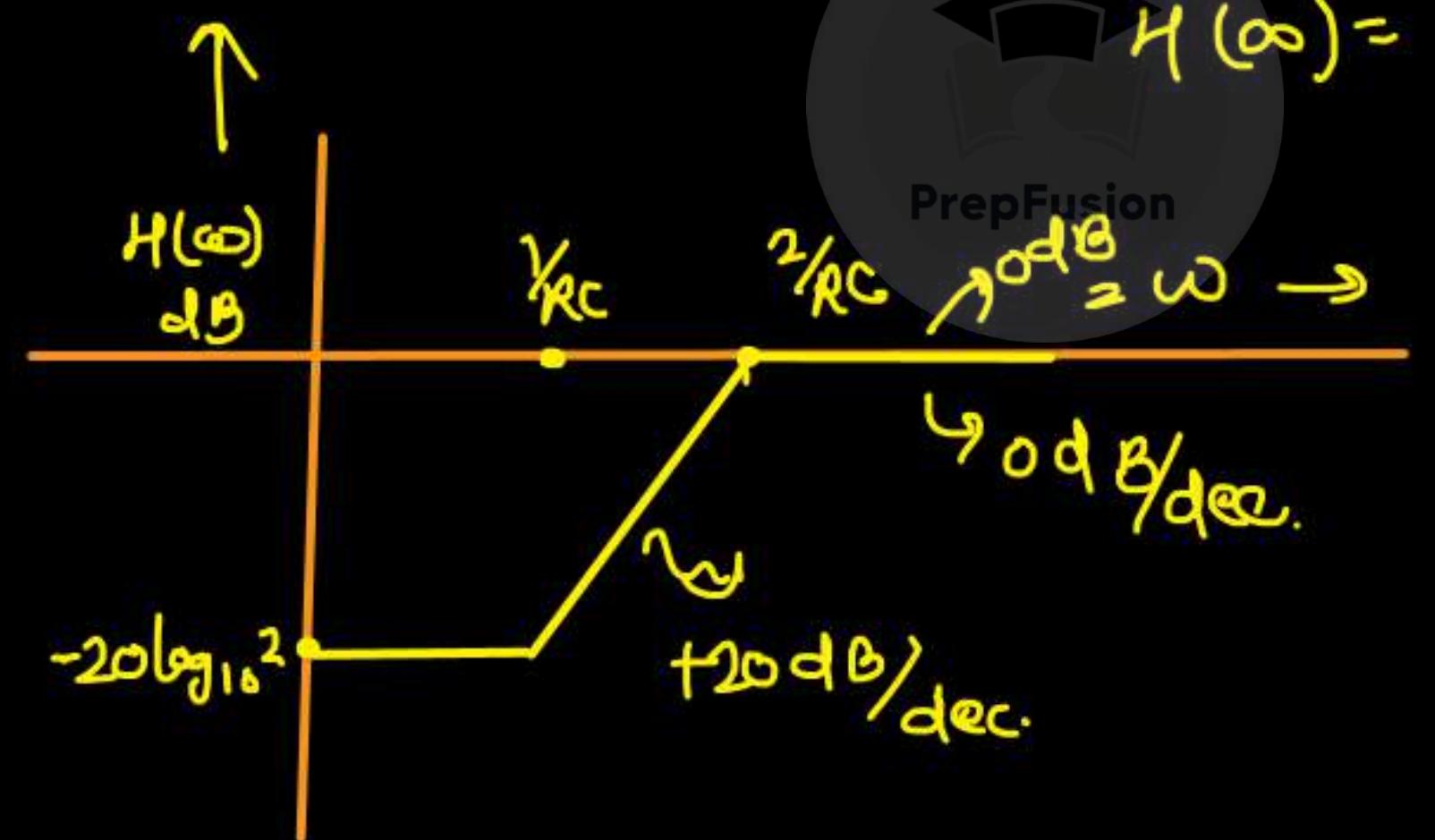


⑥

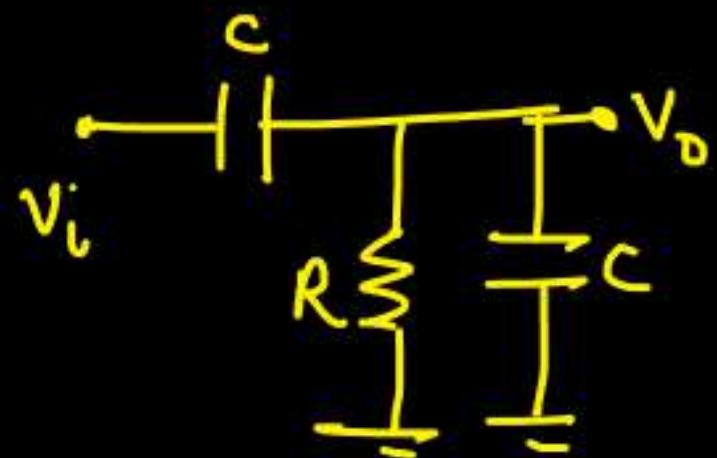


$$H(s) = \frac{SRC}{2SRC + L} \rightarrow \begin{matrix} \text{Zero at } 0 \\ \text{pole at } \frac{1}{2RC} \end{matrix}$$

$$H(0) = 0 = -\infty \text{ dB}$$
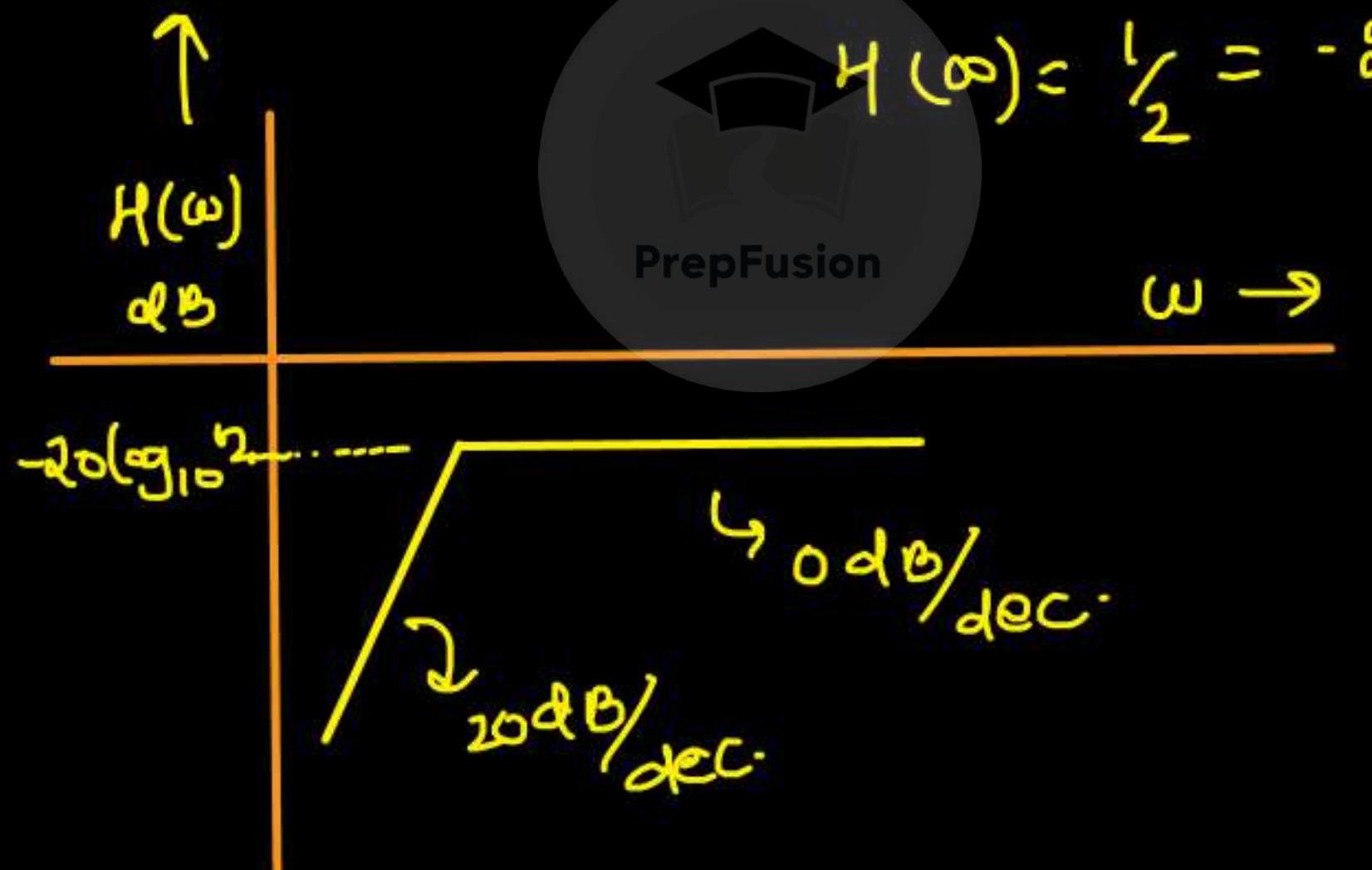
$$H(\infty) = \frac{1}{2} = -20 \log_{10}(2)$$




⑥

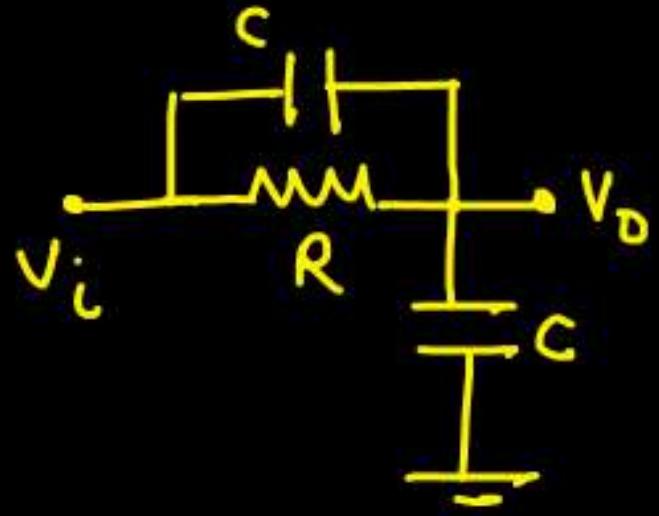

$$H(s) = \frac{SRC + L}{2SRC + L}$$

Zero $\rightarrow \frac{1}{RC}$


pole $\rightarrow \frac{1}{2RC}$

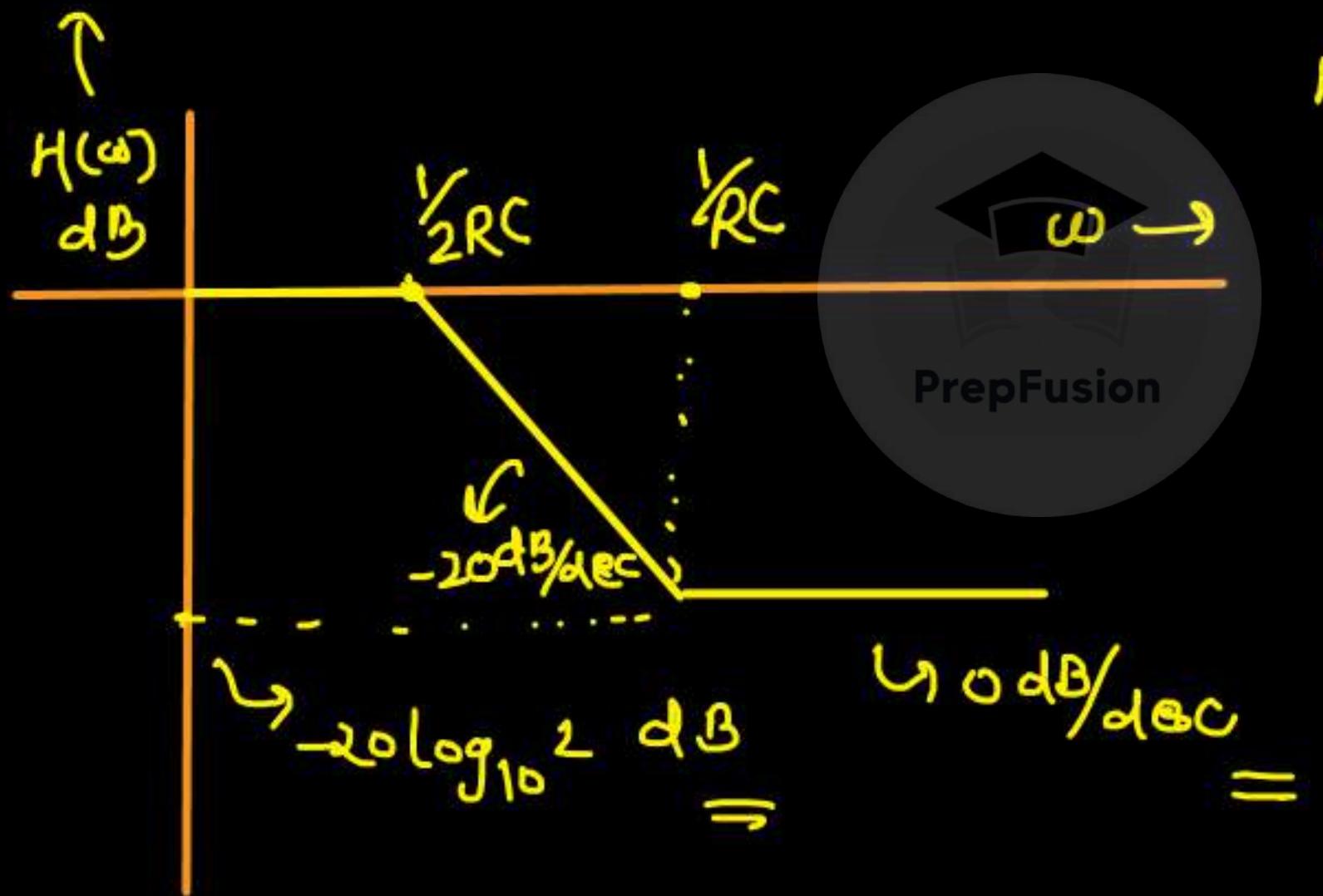


$$H(0) = \frac{1}{2} = 0 \text{ dB}$$

$$H(\infty) = \frac{1}{2} = -20 \log_{10} 2 \text{ dB}$$


⑦

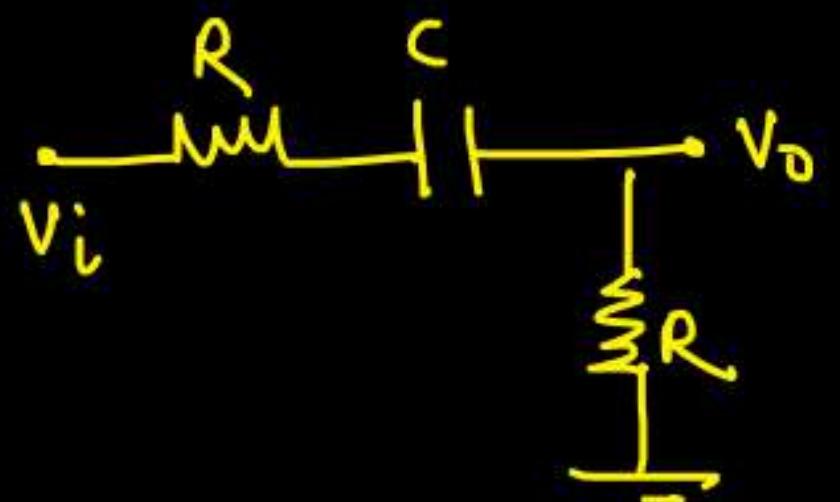


$$H(s) = \frac{SRC}{2SRC + L}$$

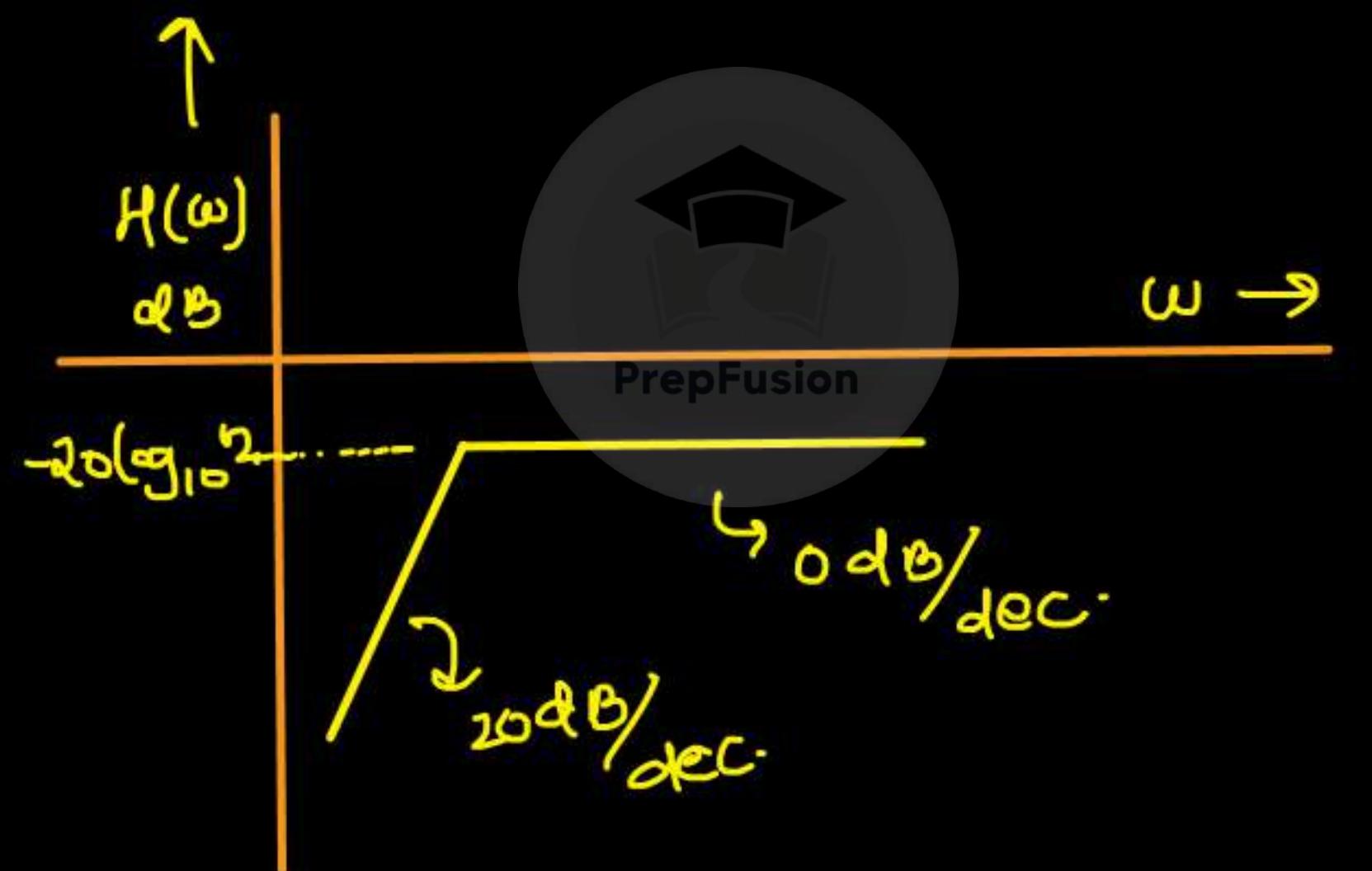


8

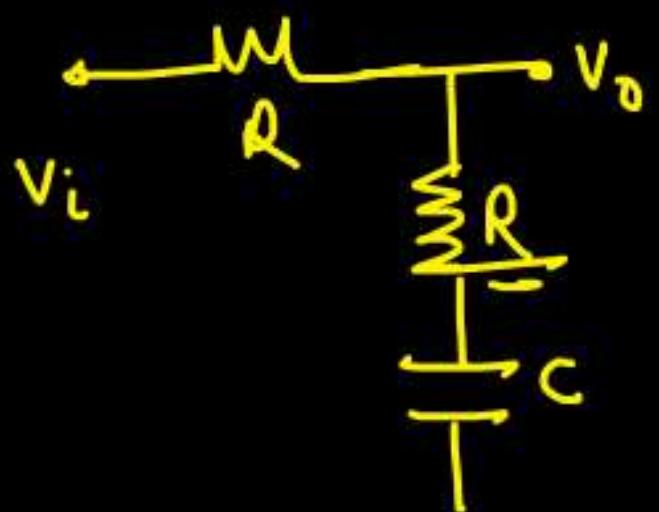



$$H(s) = \frac{SRC + L}{2SRC + L}$$

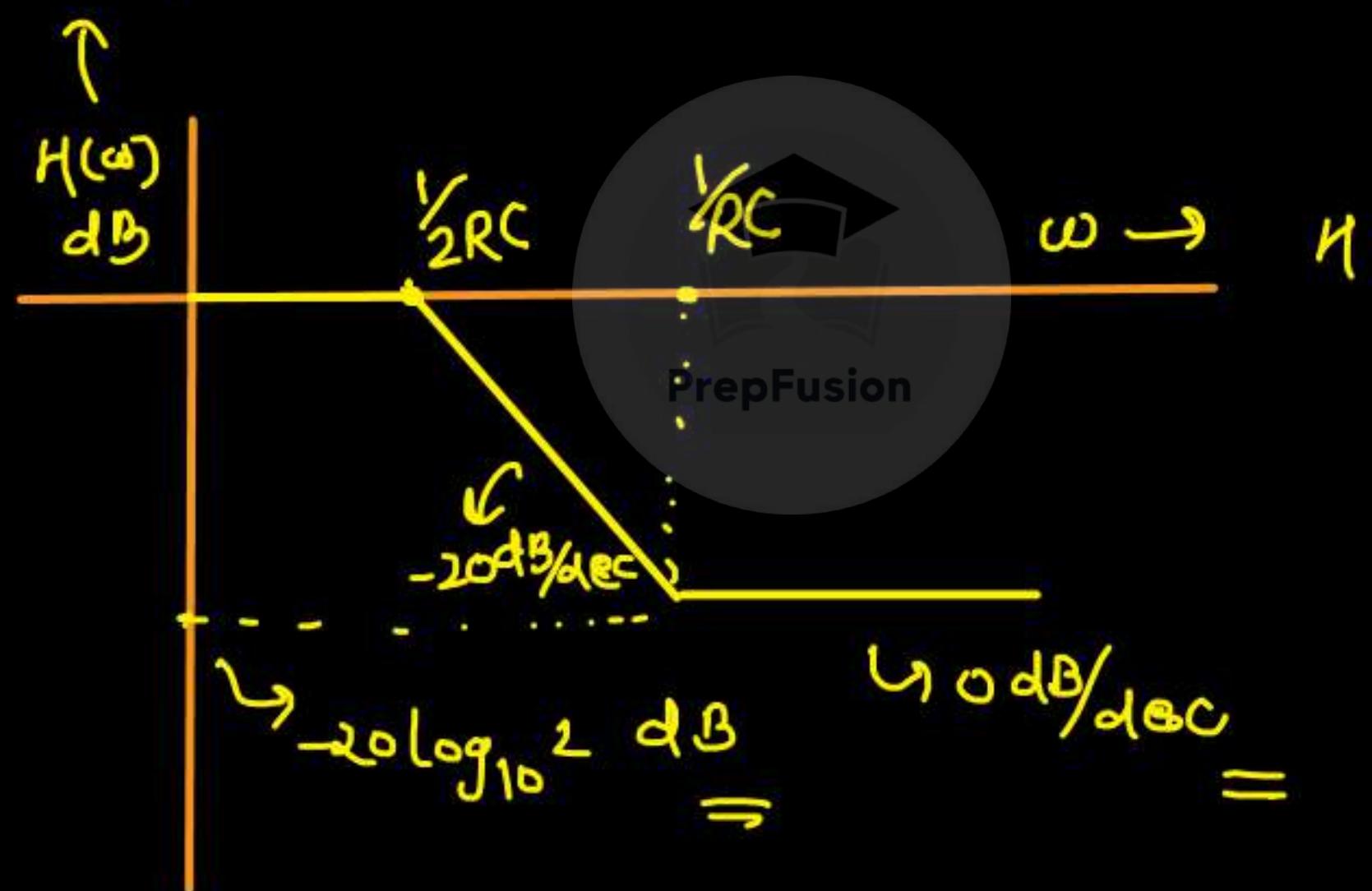

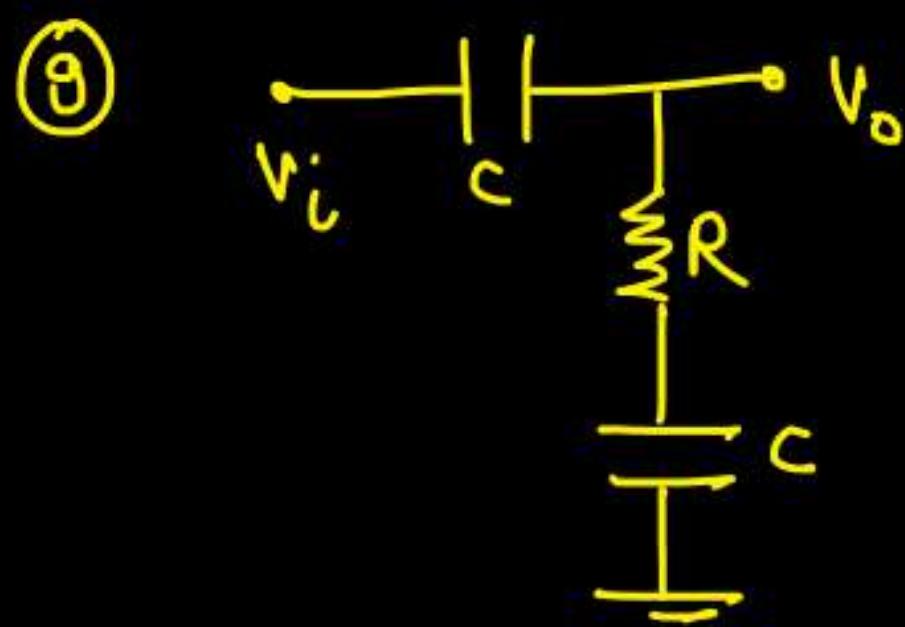

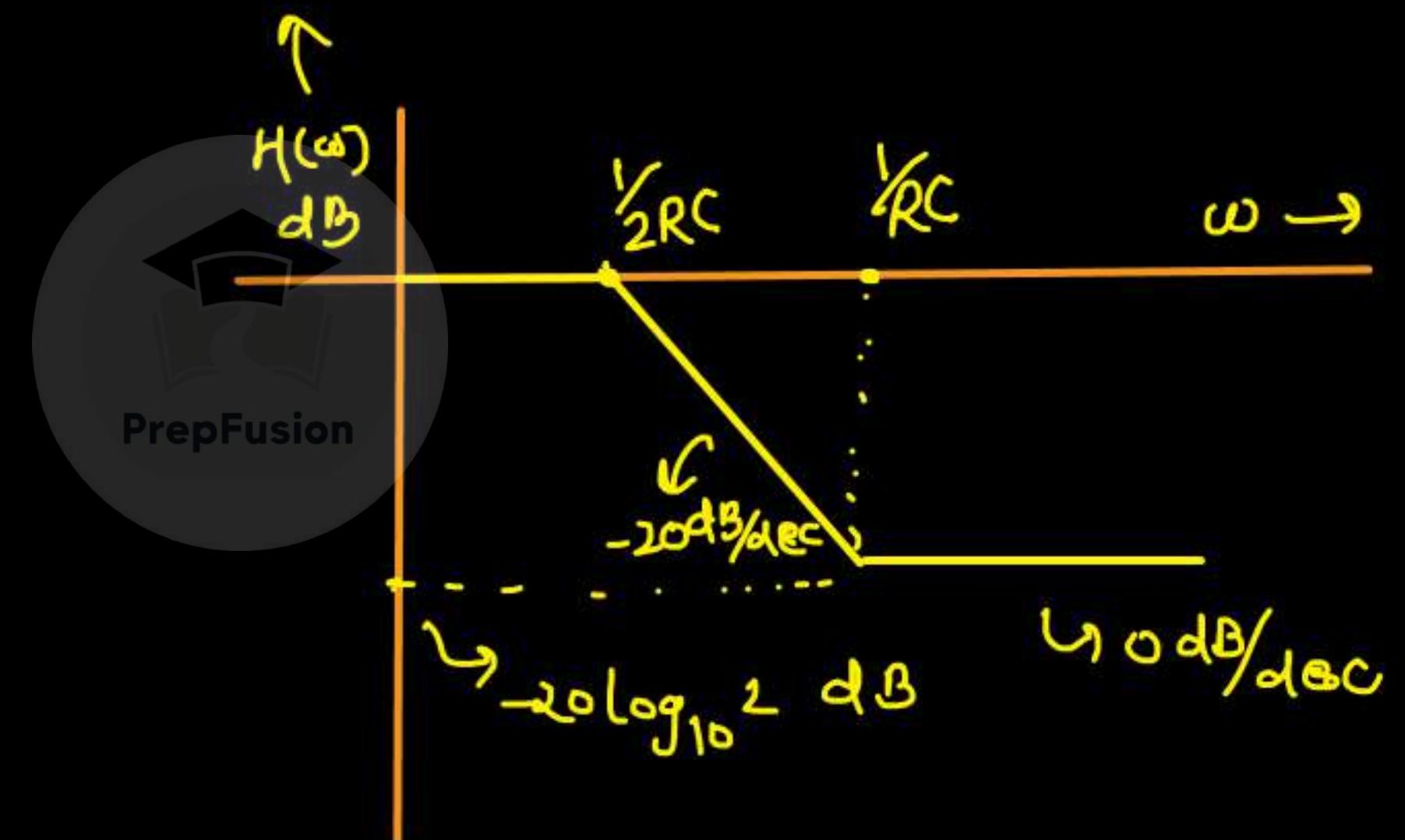
$$H(\zeta) = \frac{SRC + 1}{SRC + 2} \Rightarrow$$




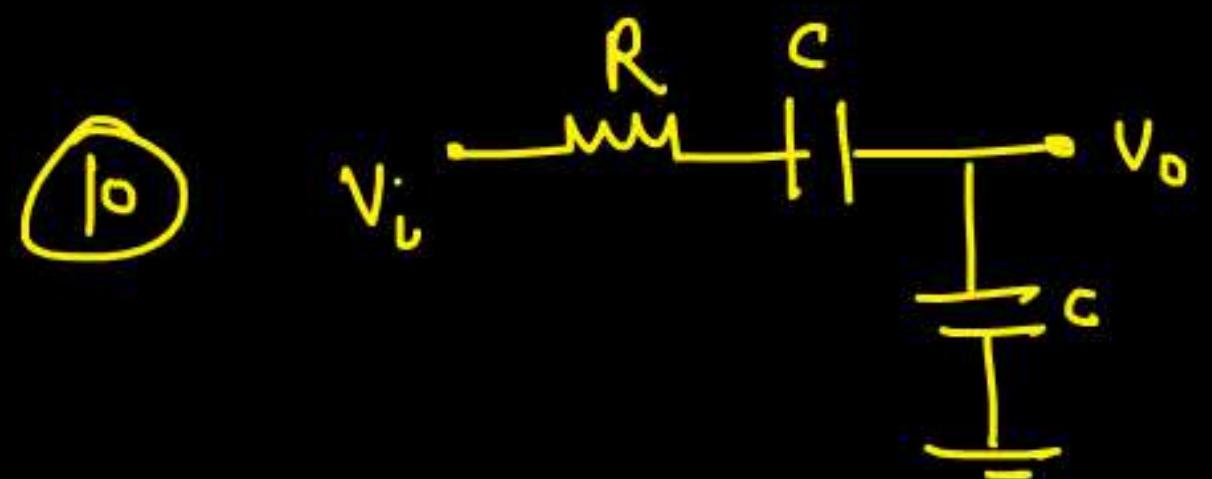

$$H(s) = \frac{1}{sRC + 2}$$

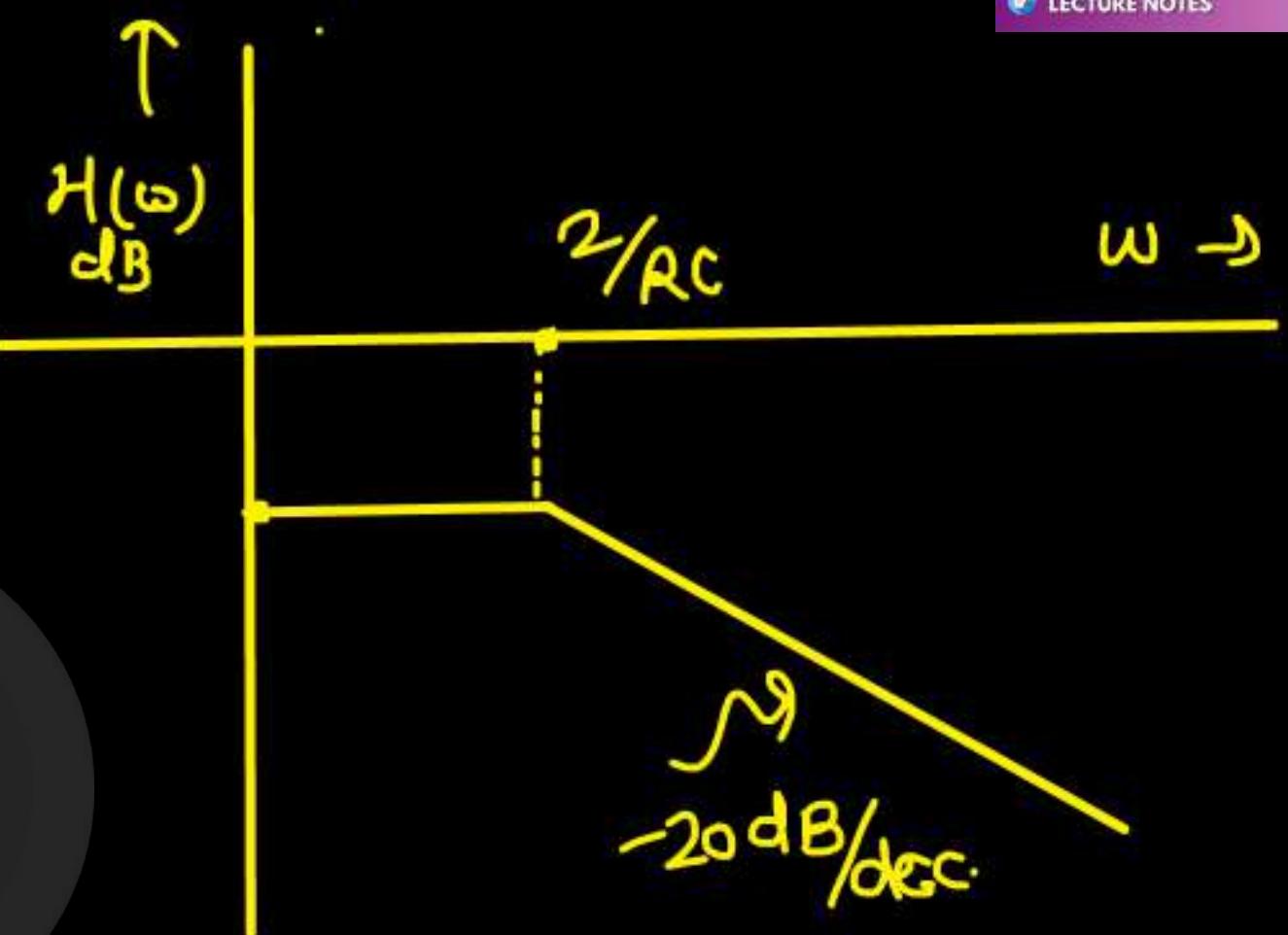

Q. Draw Bode plot for the given ckt.

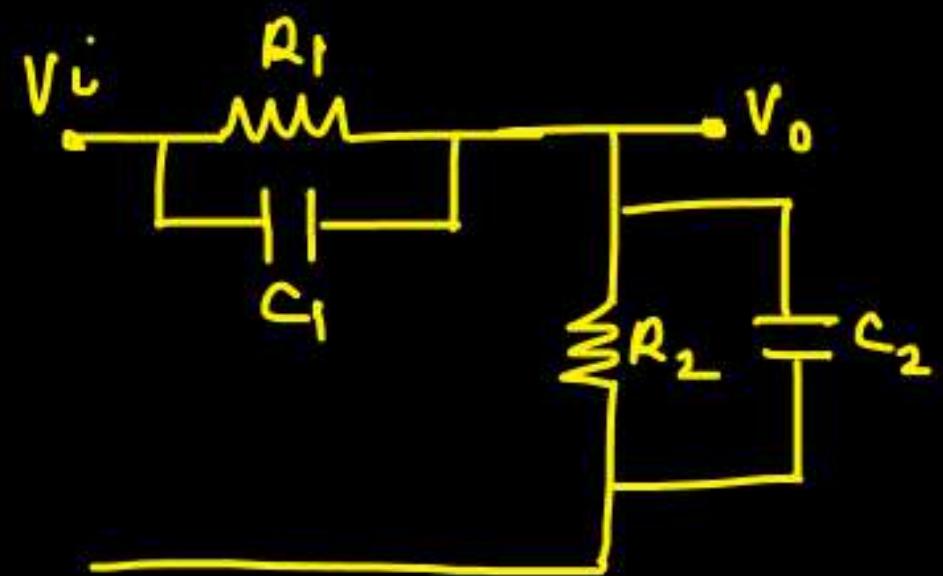

- (i) $R_1C_1 > R_2C_2$
- (ii) $R_1C_1 < R_2C_2$
- (iii) $R_1C_1 = R_2C_2$

→ Poles = $\frac{-1}{(R_1||R_2) \underbrace{(C_1+C_2)}$

Zero = $\frac{-1}{R_1C_1}$



$$(i) R_1 C_1 > R_2 C_2 \Rightarrow \frac{R_1}{R_2} > \frac{C_2}{C_1}$$

@ $\omega=0 \Rightarrow V_o(\omega=0) = \frac{R_2}{R_1+R_2} V_i(\omega=0)$


$$H(\omega=0) = \frac{R_2}{R_1+R_2} = \frac{1}{1 + R_1/R_2} Y_3$$

$$H(\omega=\infty) = \frac{C_1}{C_1+C_2} = \frac{1}{1 + C_2/C_1}$$


given: $\frac{R_1}{R_2} > \frac{C_2}{C_1}$

$H(\omega=0) < H(\omega=\infty)$

Assume pole $\omega < \omega_0$

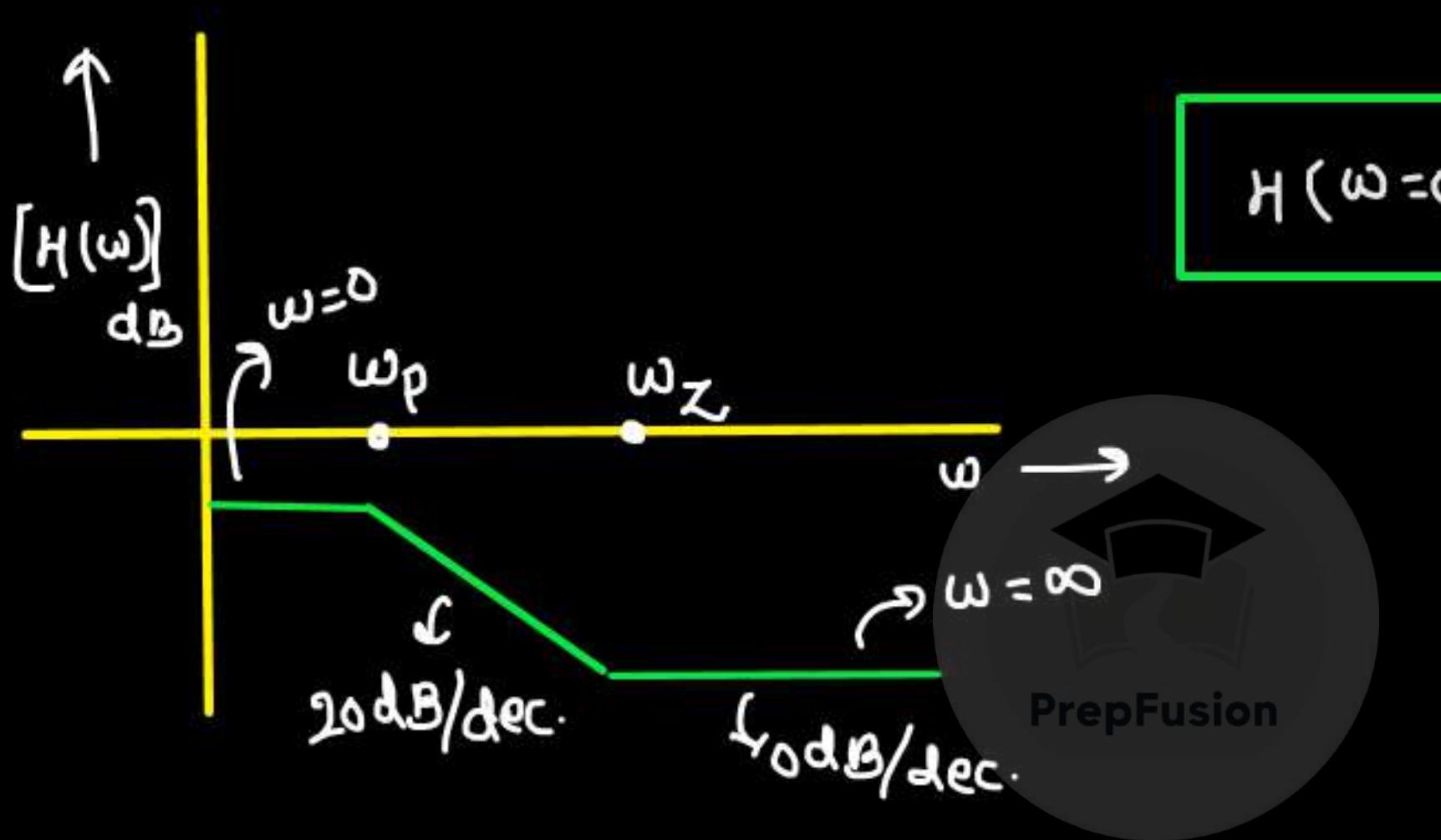

\Rightarrow zero \prec pole

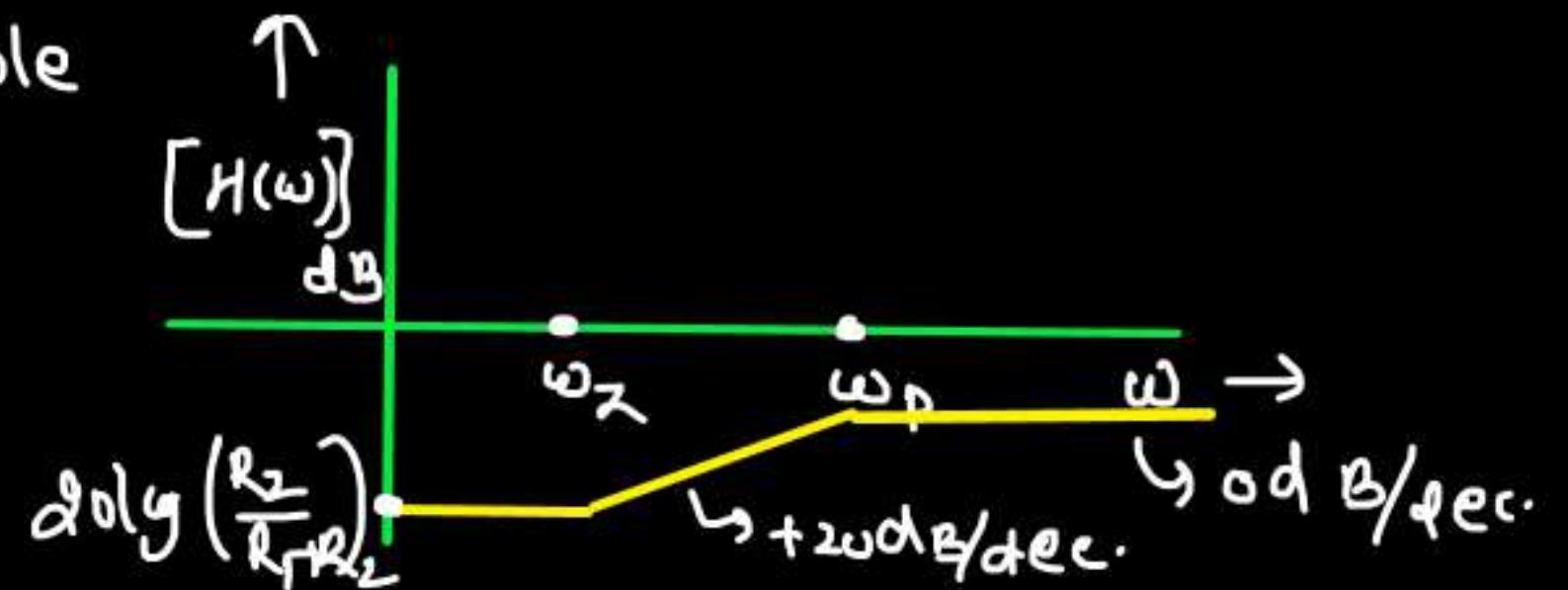

$$(ii) R_1 C_1 < R_2 C_2 \Rightarrow \frac{R_1}{R_2} < \frac{C_2}{C_1}$$

$$H(\omega=0) = \frac{R_2}{R_1+R_2} = \frac{1}{1+\frac{R_1}{R_2}}$$

$$H(\omega=\infty) = \frac{C_1}{C_1+C_2} = \frac{1}{1+\frac{C_2}{C_1}}$$

$$\frac{R_1}{R_2} < \frac{C_2}{C_1}$$

PrepFusion

$$H(\omega=\infty) < H(\omega=0)$$



zero > pole =

$$(iii) R_1 C_1 = R_2 C_2$$

$$H(\omega=0) = \frac{R_2}{R_1 + R_2}$$


$$H(\omega \rightarrow \infty) = \frac{C_1}{C_1 + C_2}$$

$$; \quad R_1 C_1 = R_2 C_2$$


$$\frac{R_1}{R_2} = \frac{C_2}{C_1}$$

$$\Rightarrow [H(\omega=0) = H(\omega=\infty)]$$

PrepFusion


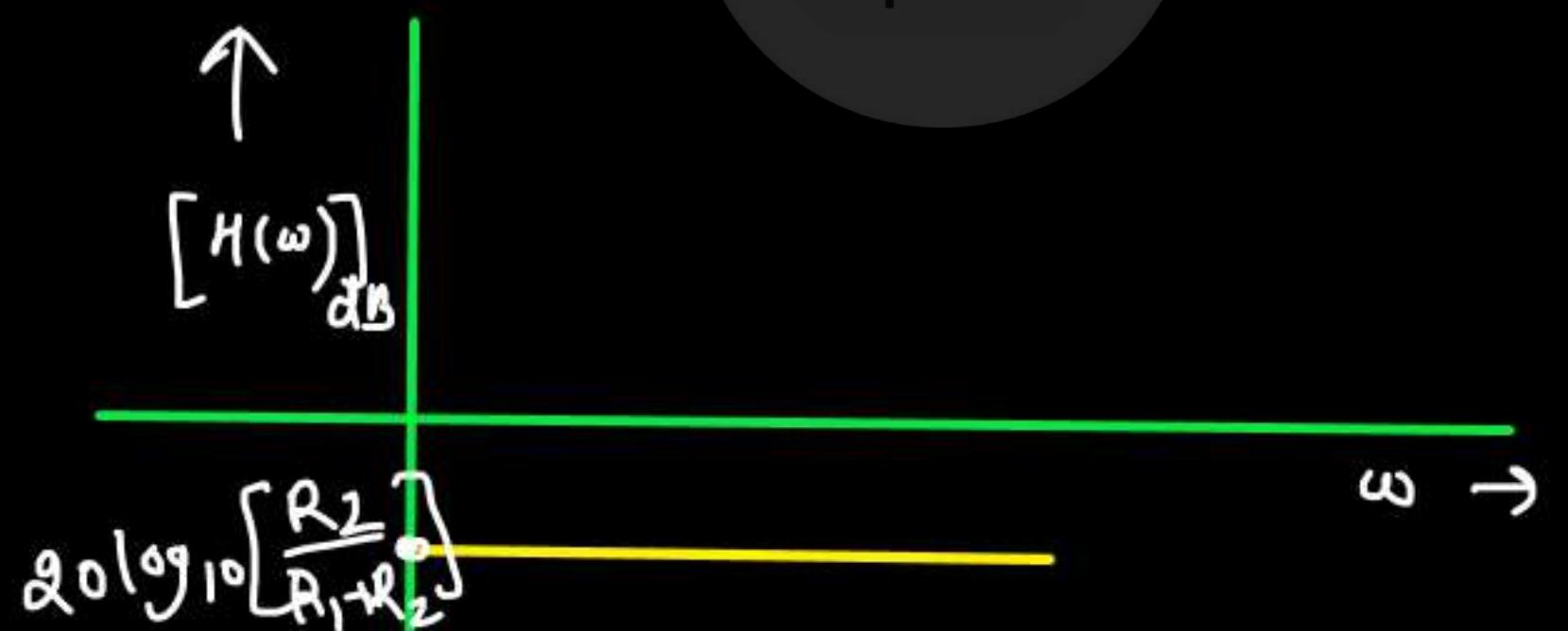



2nd order ckt:-

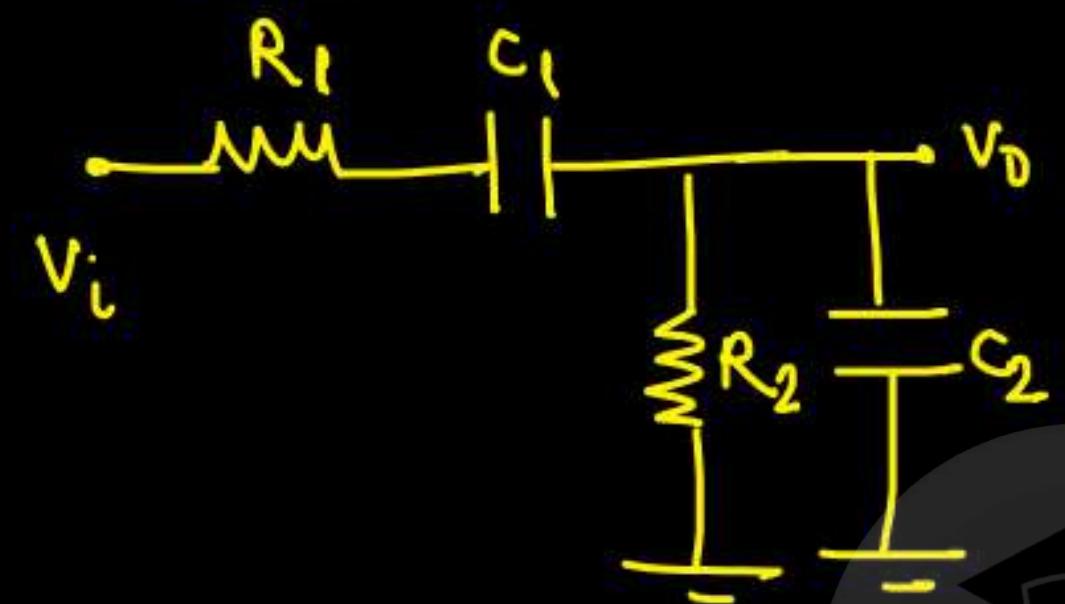

$$H(s) = \frac{AS}{s^2 + bs + C} \quad \begin{matrix} \rightarrow \text{Zero} = 0 \\ \text{pole} = \omega_0 \end{matrix}$$

$$H(0) = 0 = -\infty \text{ dB}$$

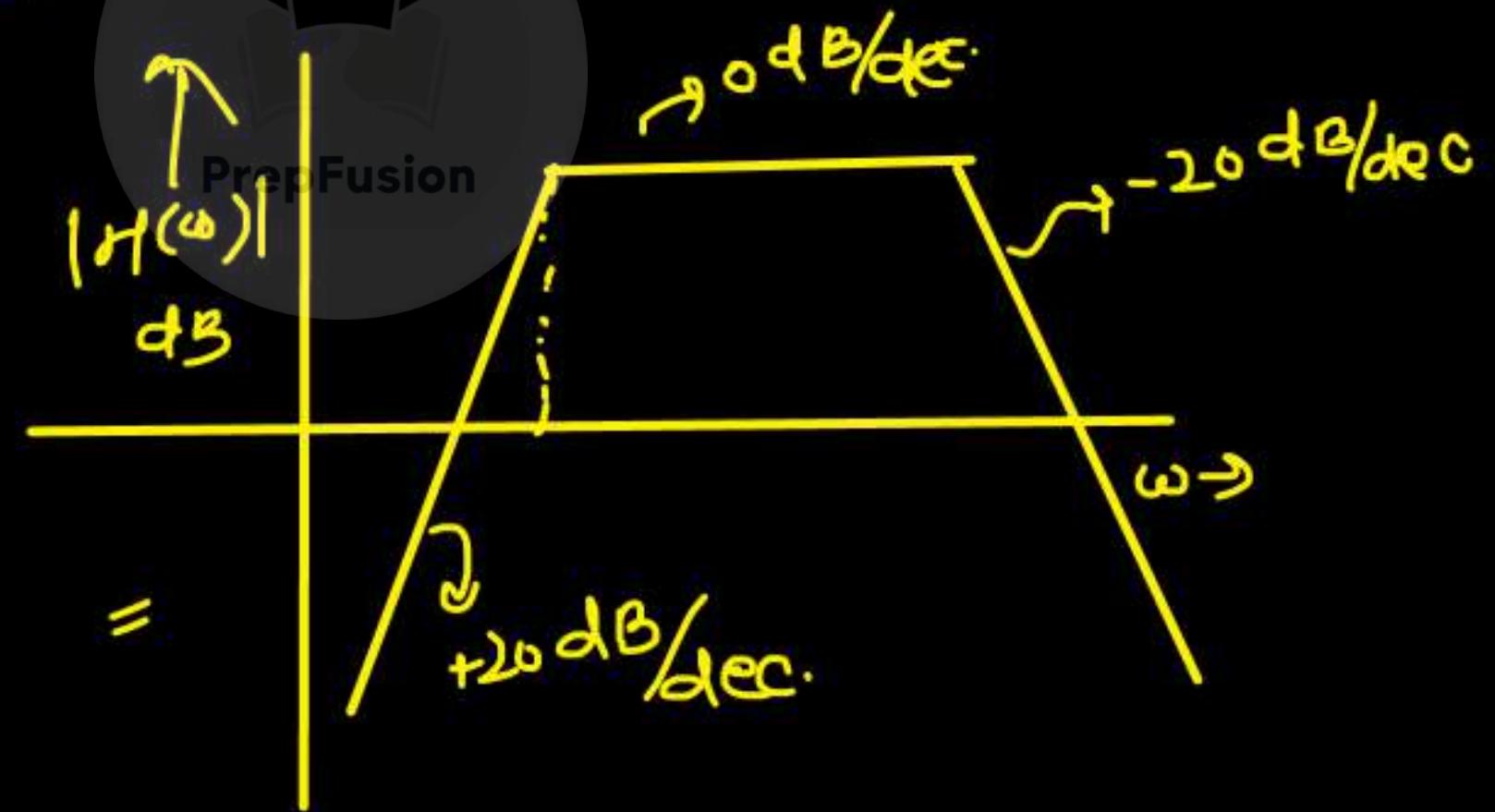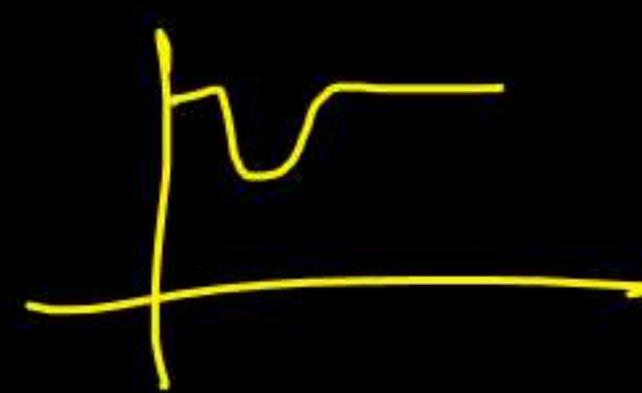

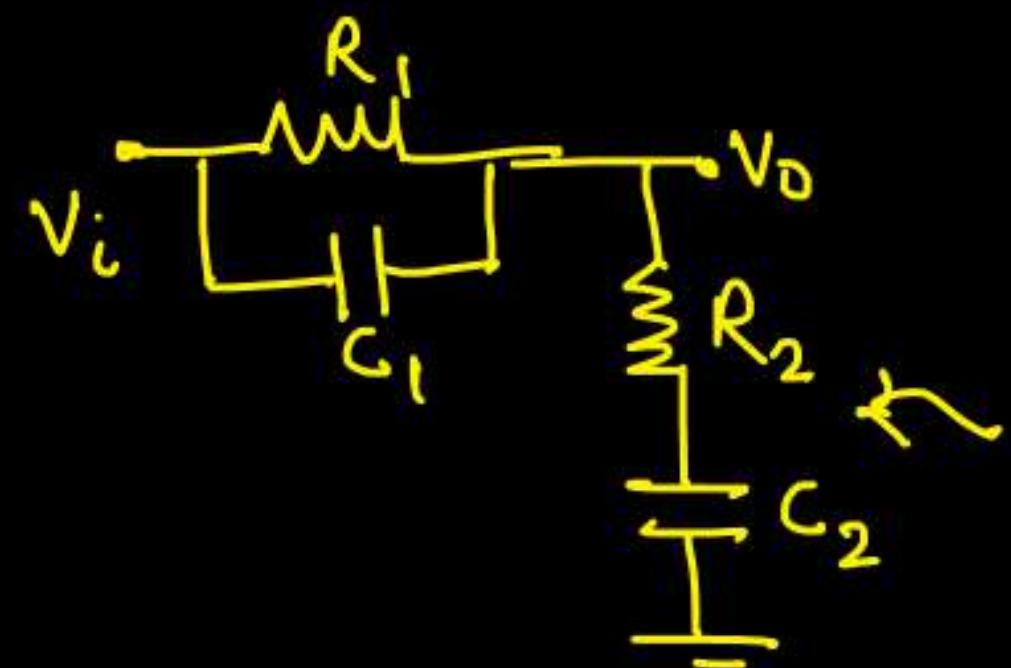

$$H(s) = \frac{A(sR_1C_1 + 1)(sR_2C_2 + 1)}{s^2 + bs + c} \xrightarrow{\text{PrepFusion}} \text{zero at } \frac{1}{R_1C_1}, \frac{1}{R_2C_2}$$

↔ poles = two


$$H(j\omega) = 1 = 0 \text{ dB}$$

$$H(\infty) = 1 = 0 \text{ dB}$$


① pole, pole, zero, zero

② zero, zero, f

X

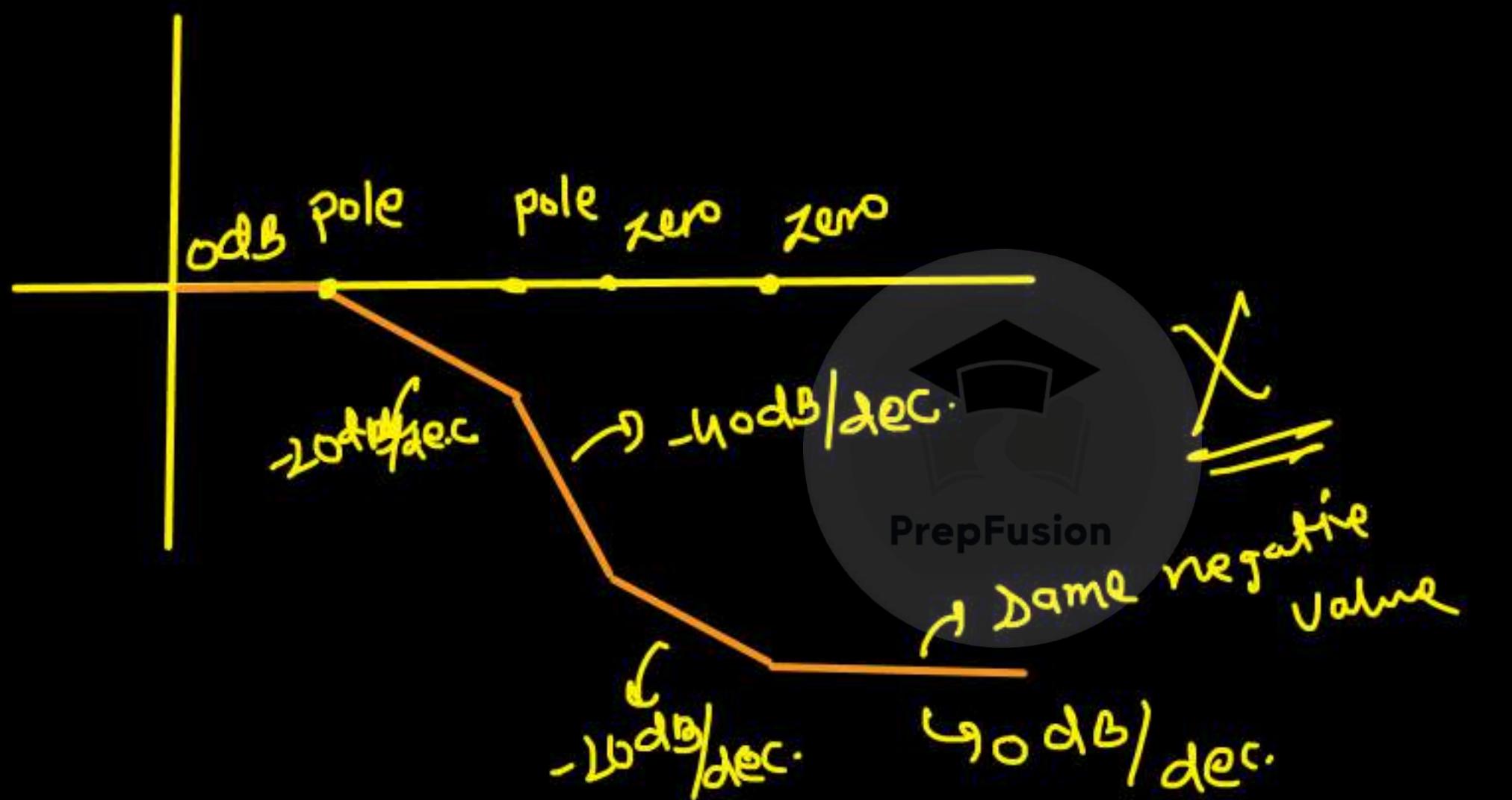


③ pole, zero, pole, zero

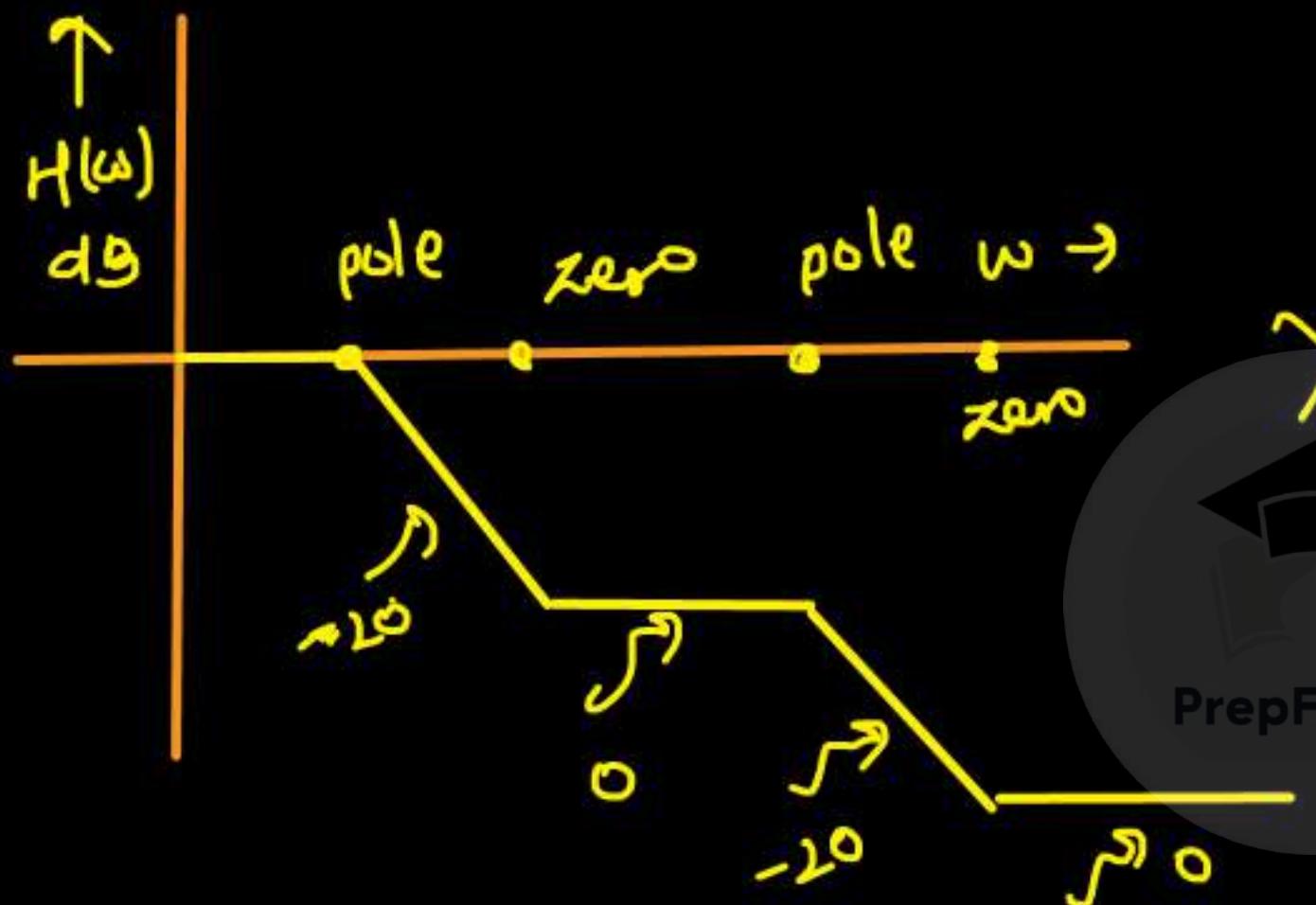

④ zero, pole, zero




⑤ pole, zero, zero, pole \Rightarrow

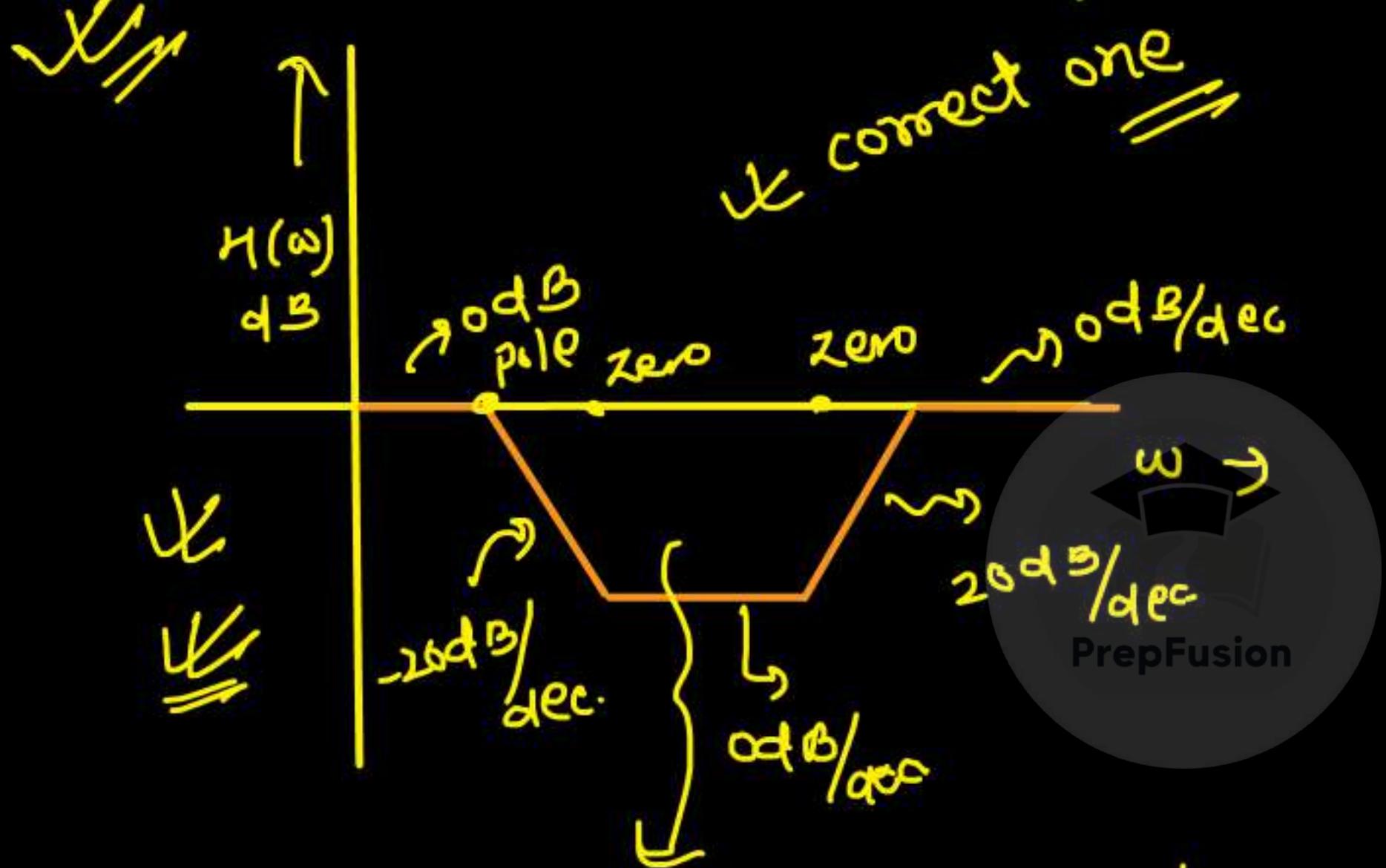

gain is always lesser
than \pm ($V_o \leq V_i$)

⑥ zero, pole, P \Rightarrow

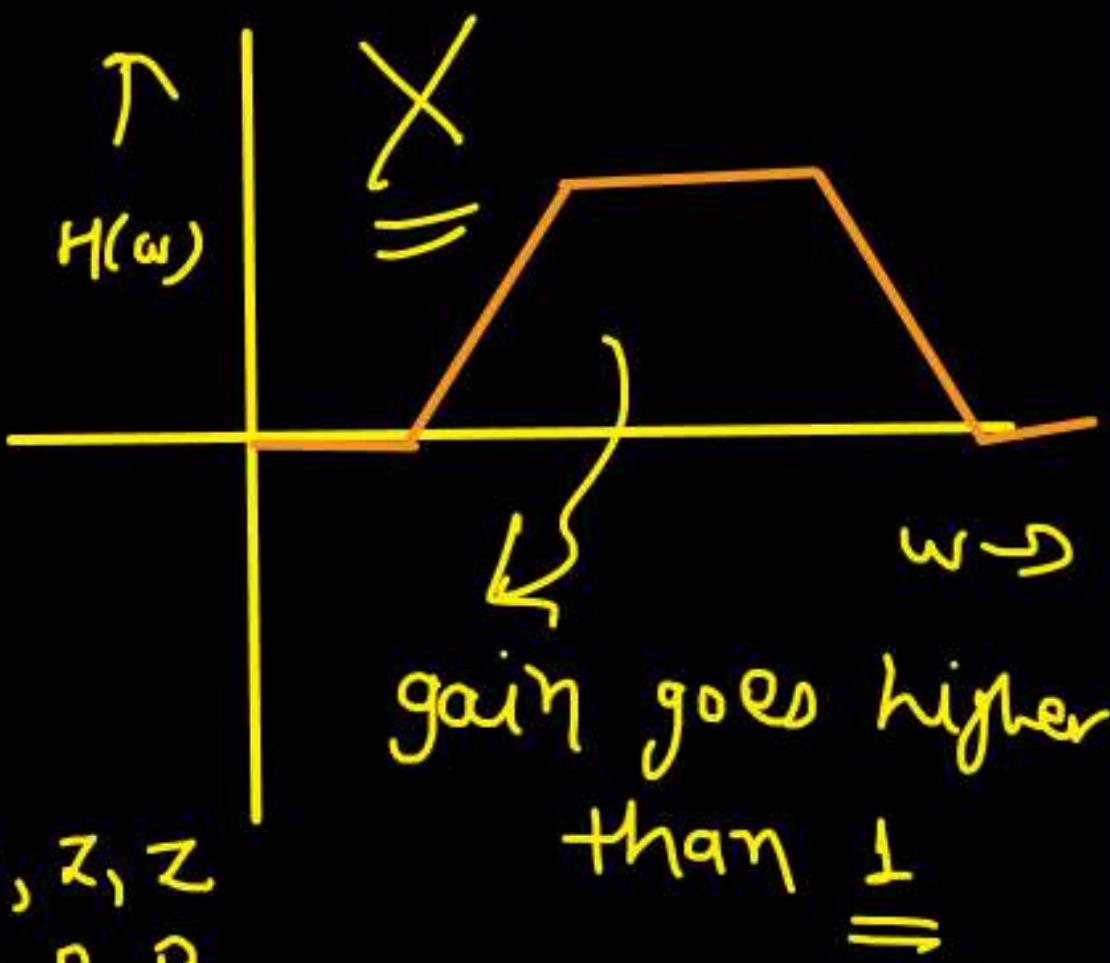

P, P, Z, Z


Z, Z, P, P

Z, P, Z, P

P, Z, P, Z

P, Z, Z, P \Rightarrow


Z, P, P, Z

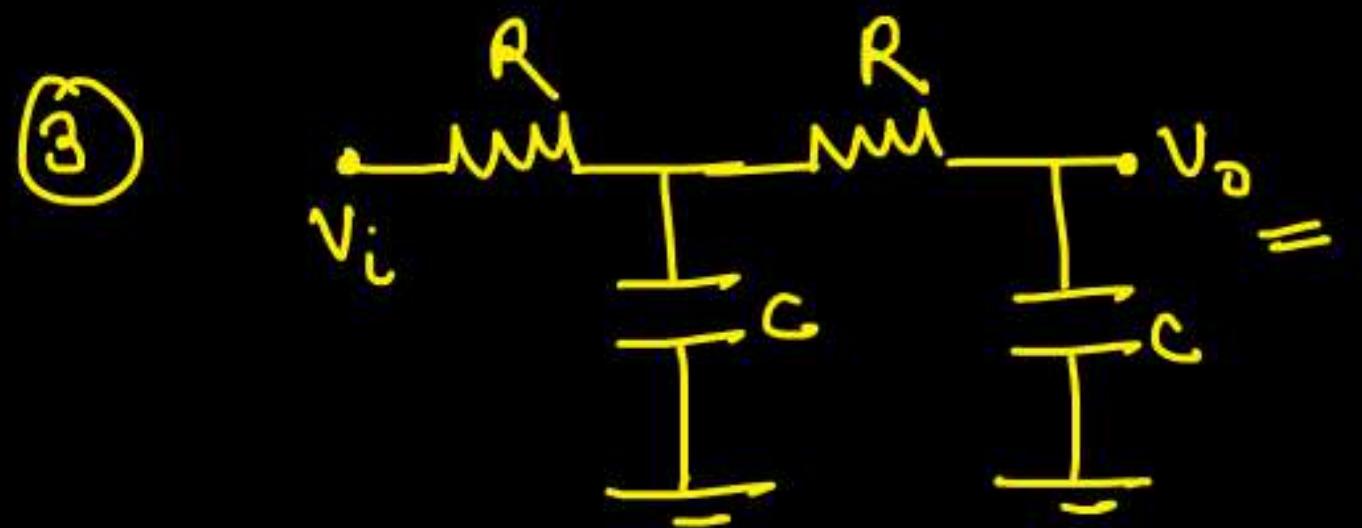


$$H(s) = \frac{A}{s^2 + bs + c}$$

$$H(0) = 1 = 0 \text{ dB}$$

$$H(\infty) = 0 = -\infty \text{ dB}$$

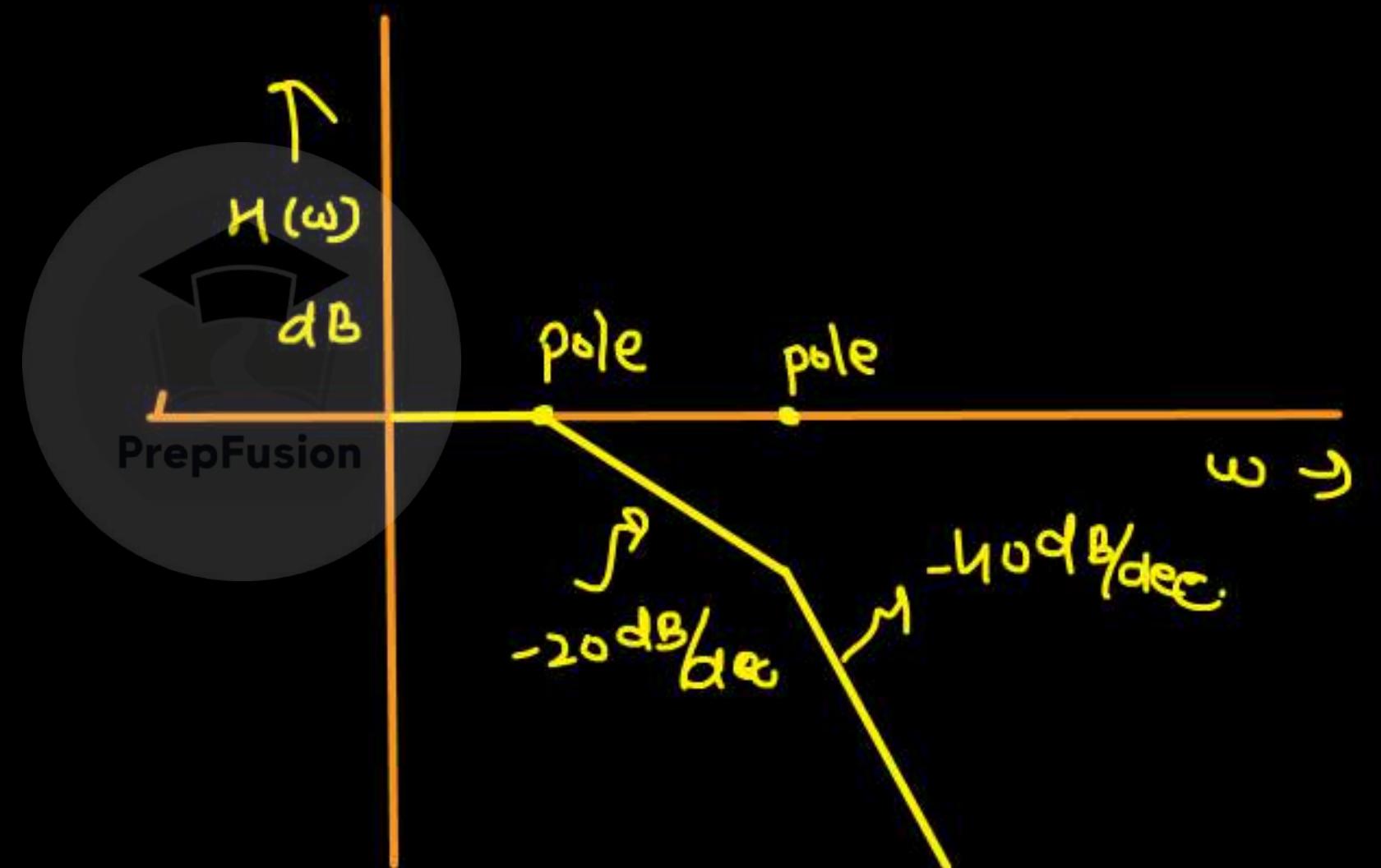

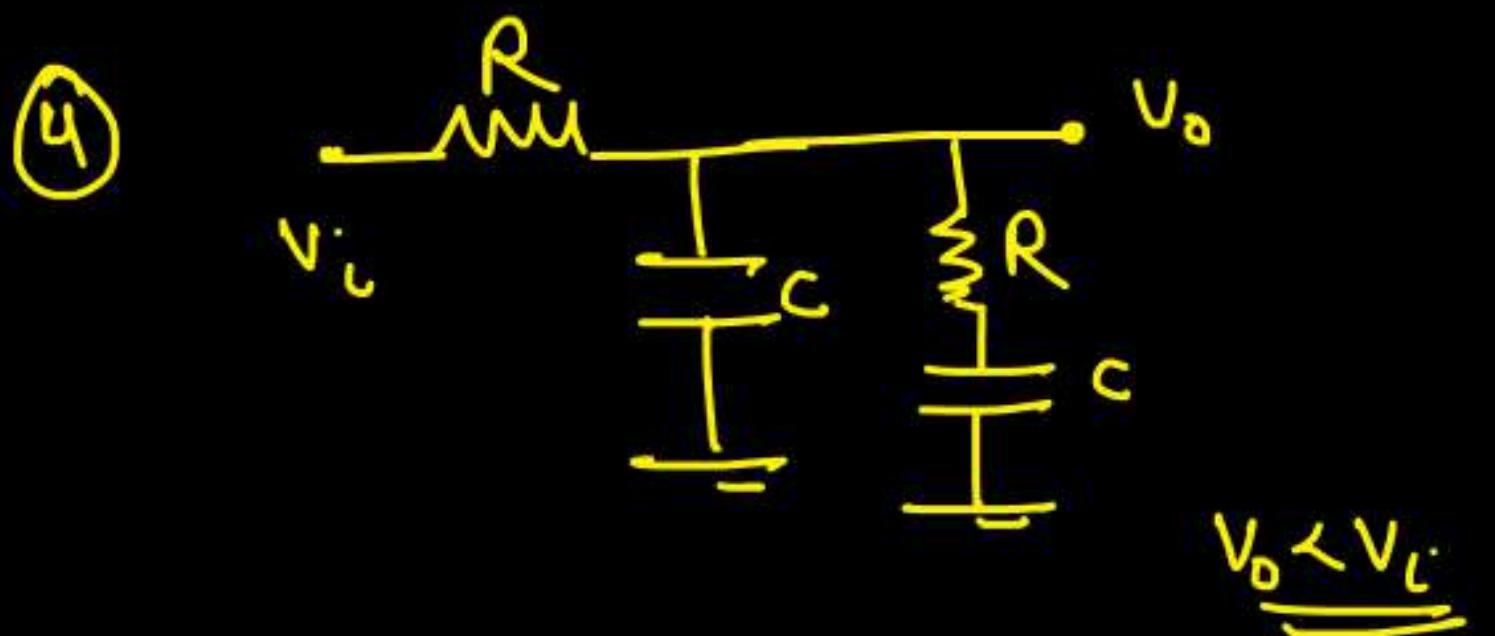

Two poles

(1) Zeros

$$R + \frac{1}{\omega} = 0 \Rightarrow \omega_z^2 = -\frac{1}{RC}$$

$$\omega = \infty \Rightarrow \frac{1}{C} = 0 \quad \underline{\underline{V_o = 0}} \Rightarrow \omega_z = \infty$$

$$H(0) = 1 = 0 \text{ dB} \quad H(s) = A \frac{(sRC + 1)}{(s^2 + \omega s + b)}$$


PrepFusion

$$H(\infty) = -\infty \text{ dB}$$

1 zero
2 poles


$$V_o < V_L \Rightarrow H(\omega) \Big|_{dB} \leq 0 \text{ dB}$$

① zero, pole, pole

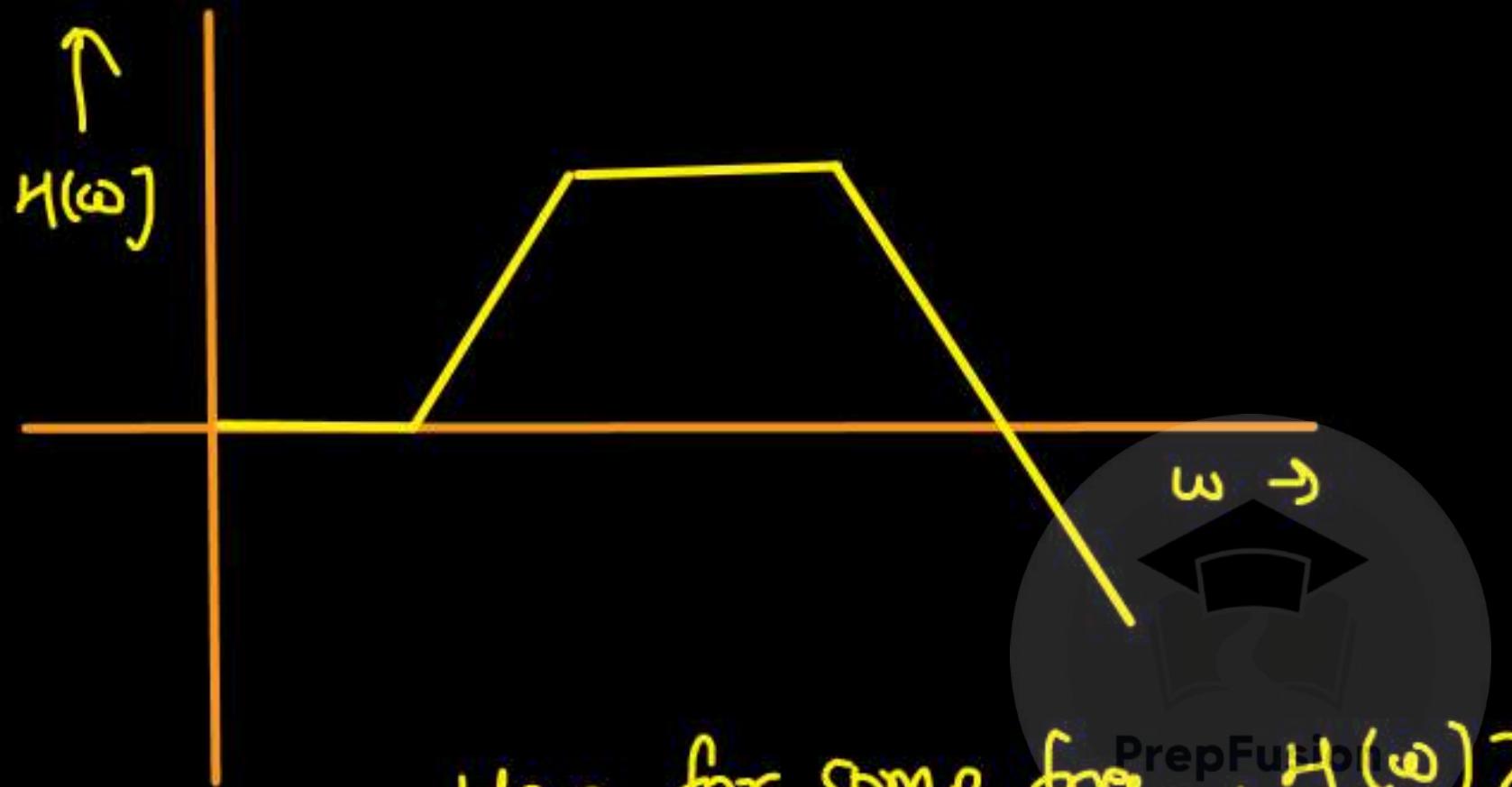

Here for some freq., $H(\omega) > 0$
 \hookrightarrow not possible

② pole, zero

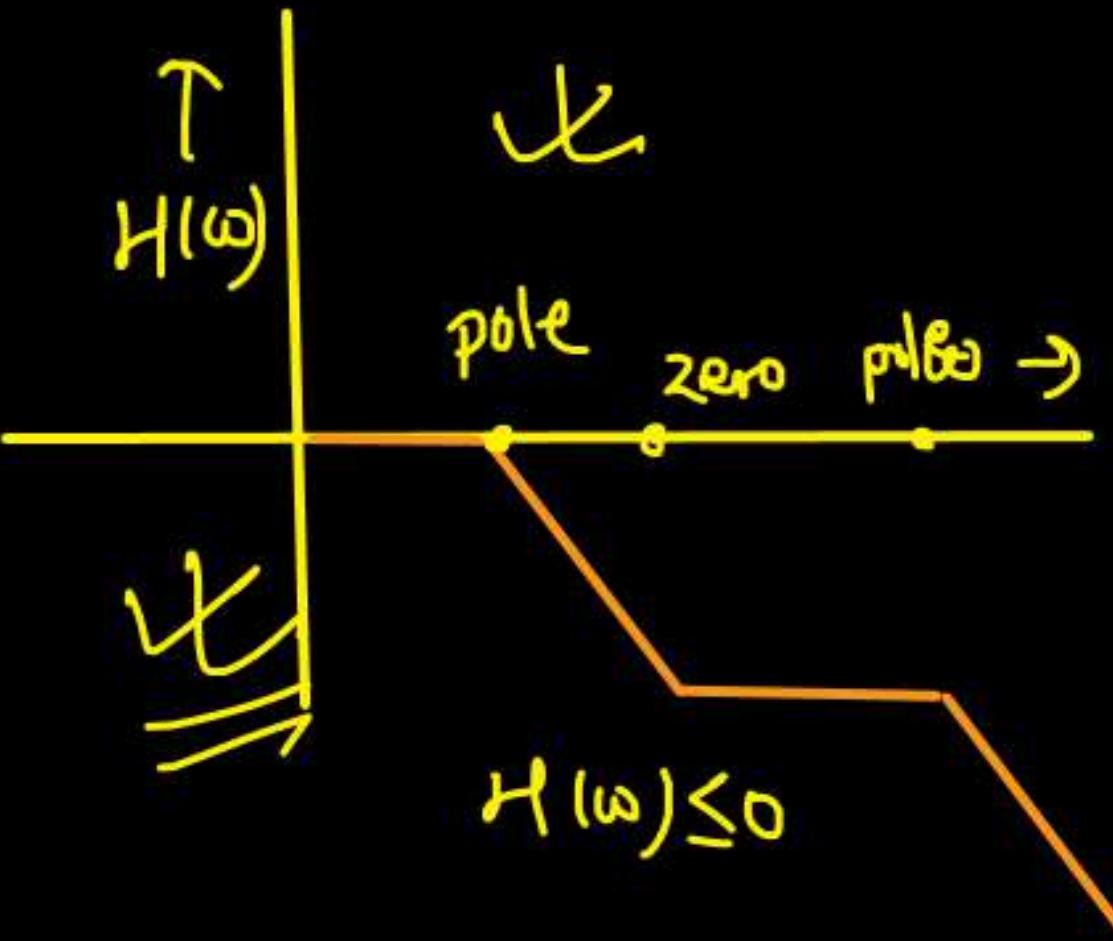


$$H(\omega) \leq 0$$



- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

③ Pole, Pole, Zero

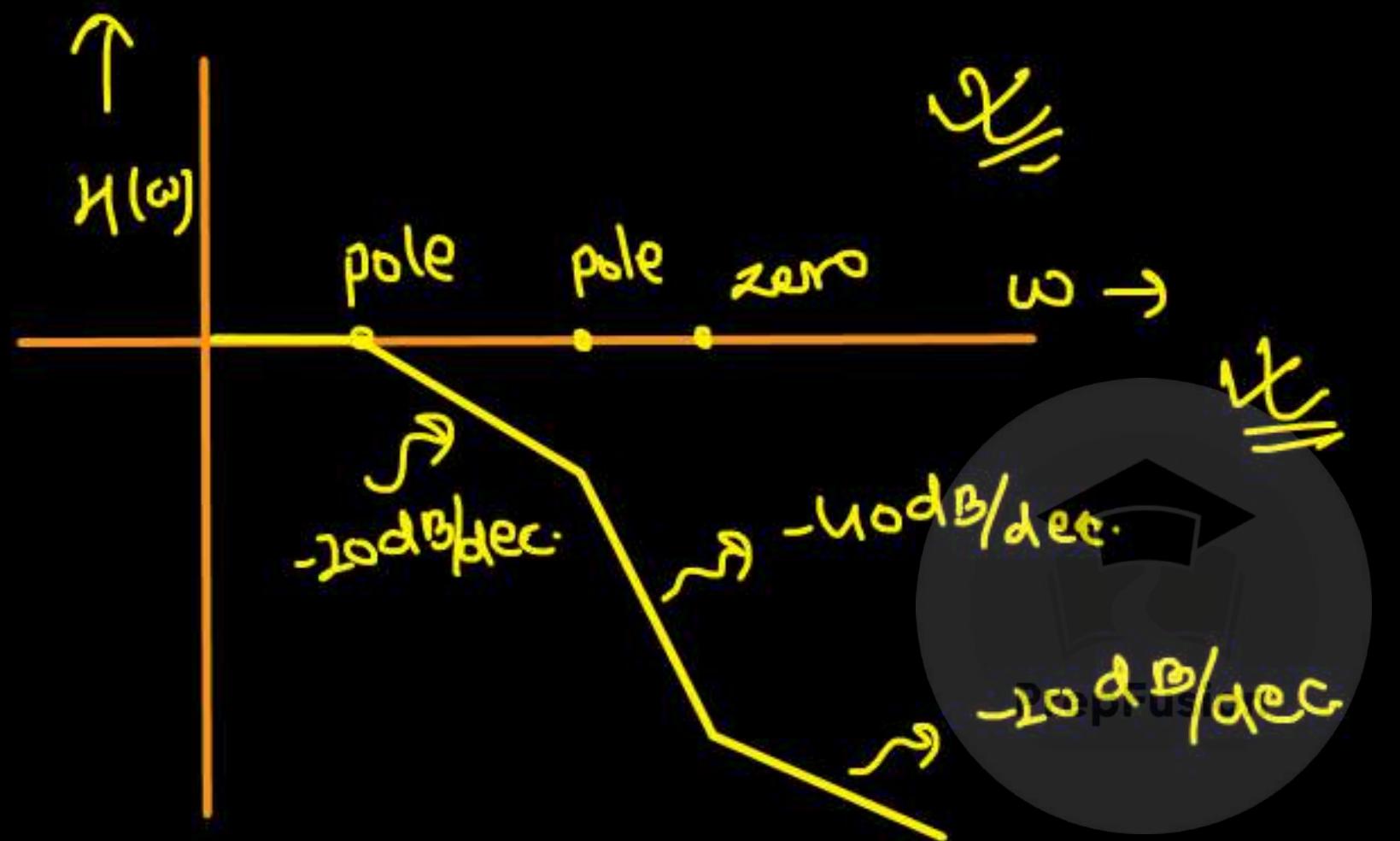


P, P, Z

P, Z, P

Z, P, P



Q. Draw the bode plot for given RC ckt.

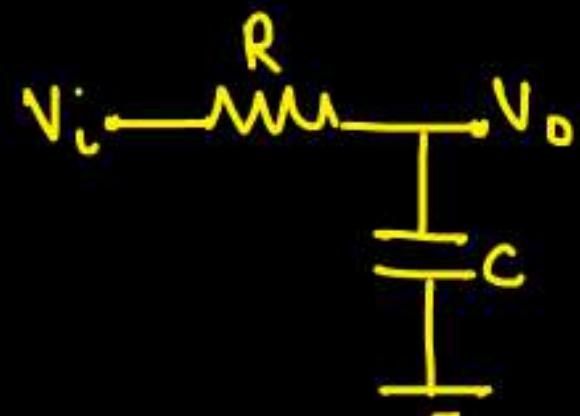

$$R = 2 \Omega$$

$$C = 1 F$$

For which value of V_i ckt will have the max^m attenuation?


$V_i = 50mV \sin\left(\frac{t}{\omega}\right) \rightarrow 0.25 \text{ rad/sec}$

and min^m

PrepFusion

$$V_i = 50mV \sin(2t) \rightarrow 2 \text{ rad/sec}$$
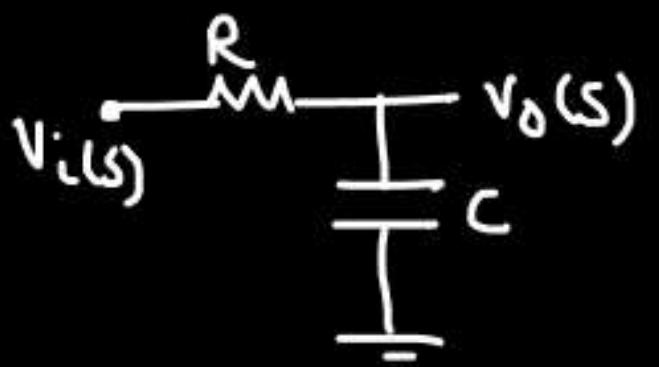
$$V_i = 50mV \sin(20t) \rightarrow 20 \text{ rad/sec}$$





$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCS}$$

$$\omega_p = -\frac{1}{RC}, \quad \omega_z = \infty$$

$$\omega_p = \frac{-1}{2\pi f} = -0.5 \text{ rad/sec}$$

PrepFusion

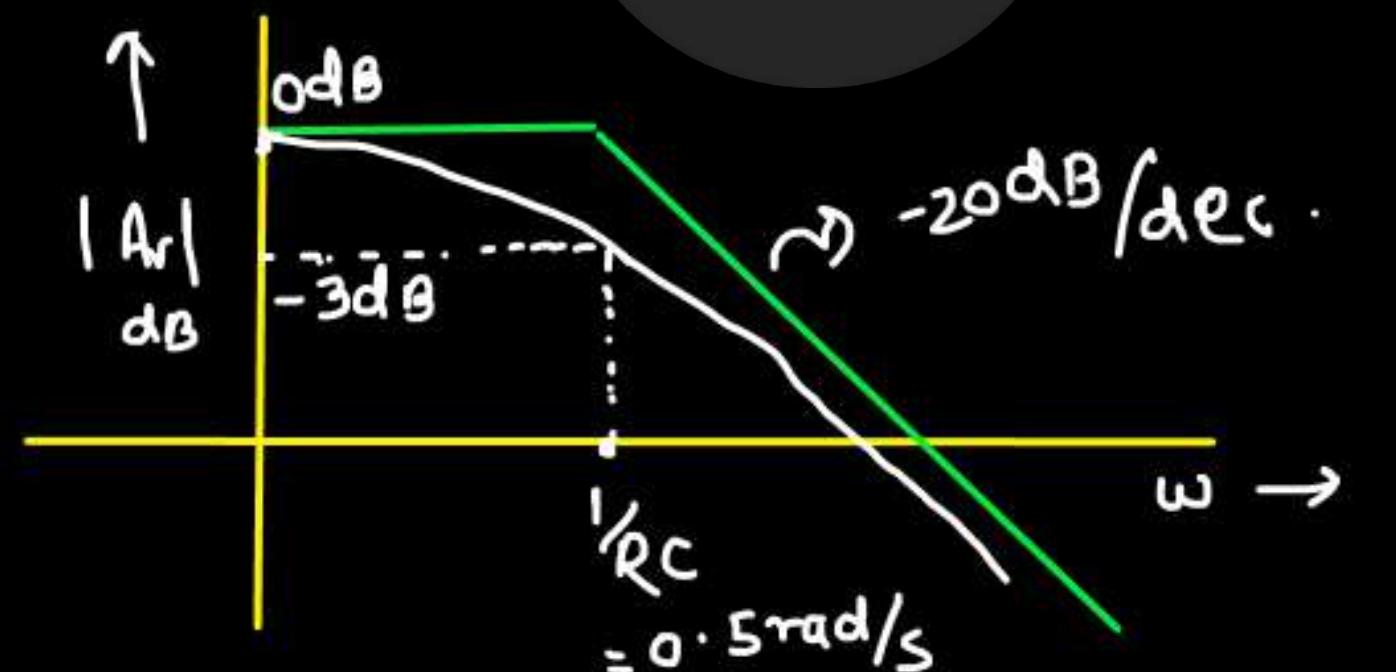

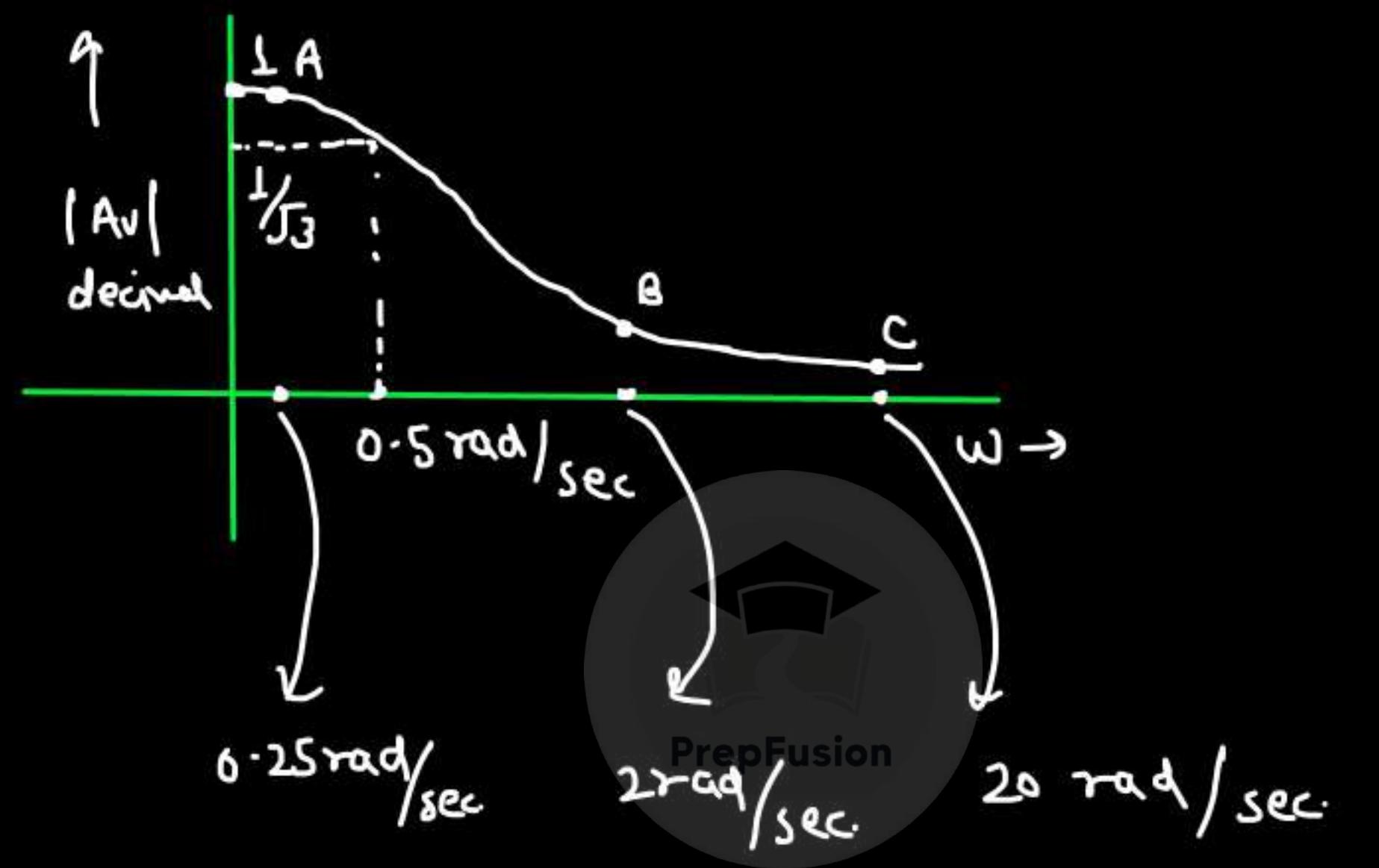


$$\left(\frac{V_o}{V_i} \right)_{0.25 \text{ rad/sec.}} > \left(\frac{V_o}{V_i} \right)_{2 \text{ rad/sec.}} > \left(\frac{V_o}{V_i} \right)_{20 \text{ rad/sec.}}$$


\Downarrow
max gain \Rightarrow min attenuation

min gain = max^m attenuation

Q. Plot the frequency response.

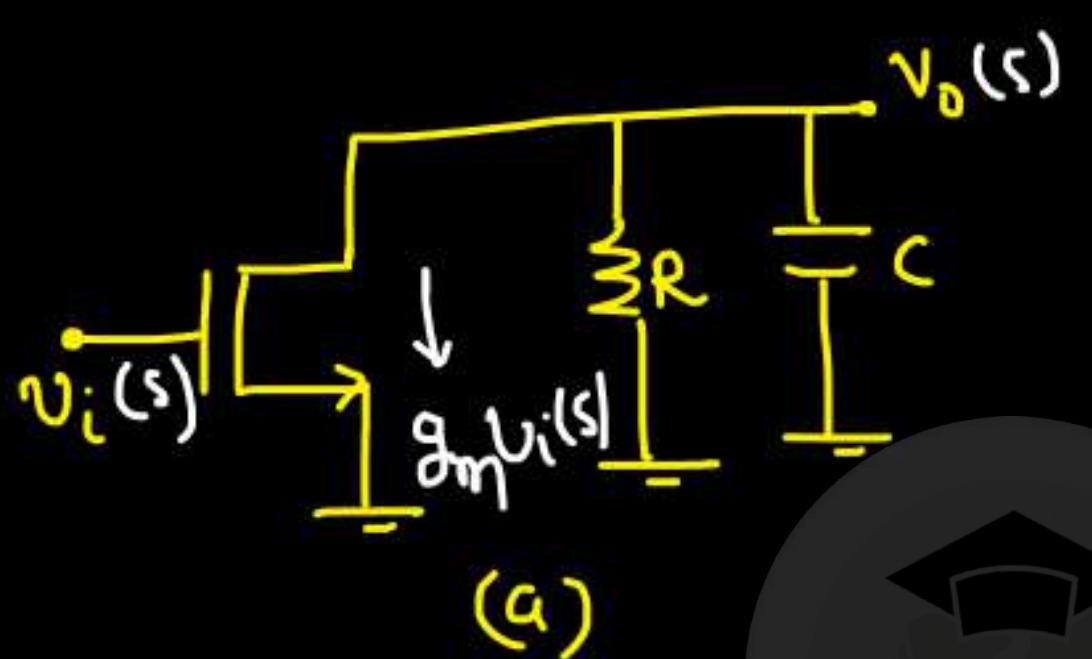


$$\frac{V_o(s)}{V_i(s)} = ?$$

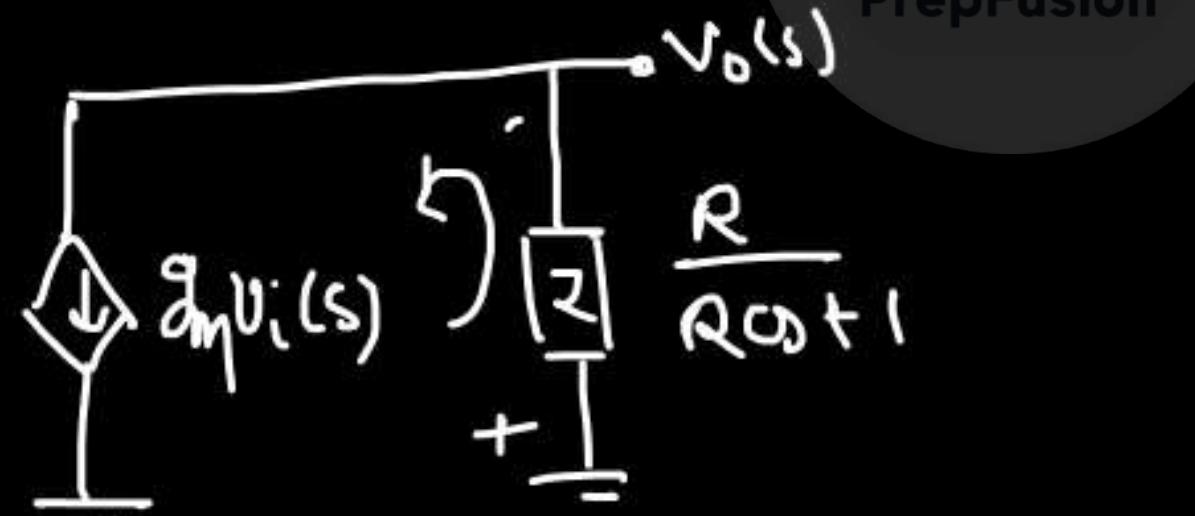

$$V_o(s) = -\frac{g_m \times R}{RCs + 1} V_i(s)$$

$$\frac{V_o(s)}{V_i(s)} = -\frac{g_m R}{RCs + 1}$$


$$\omega_p = -\frac{1}{RC} \quad |\alpha(\text{DC gain})| = g_m R$$

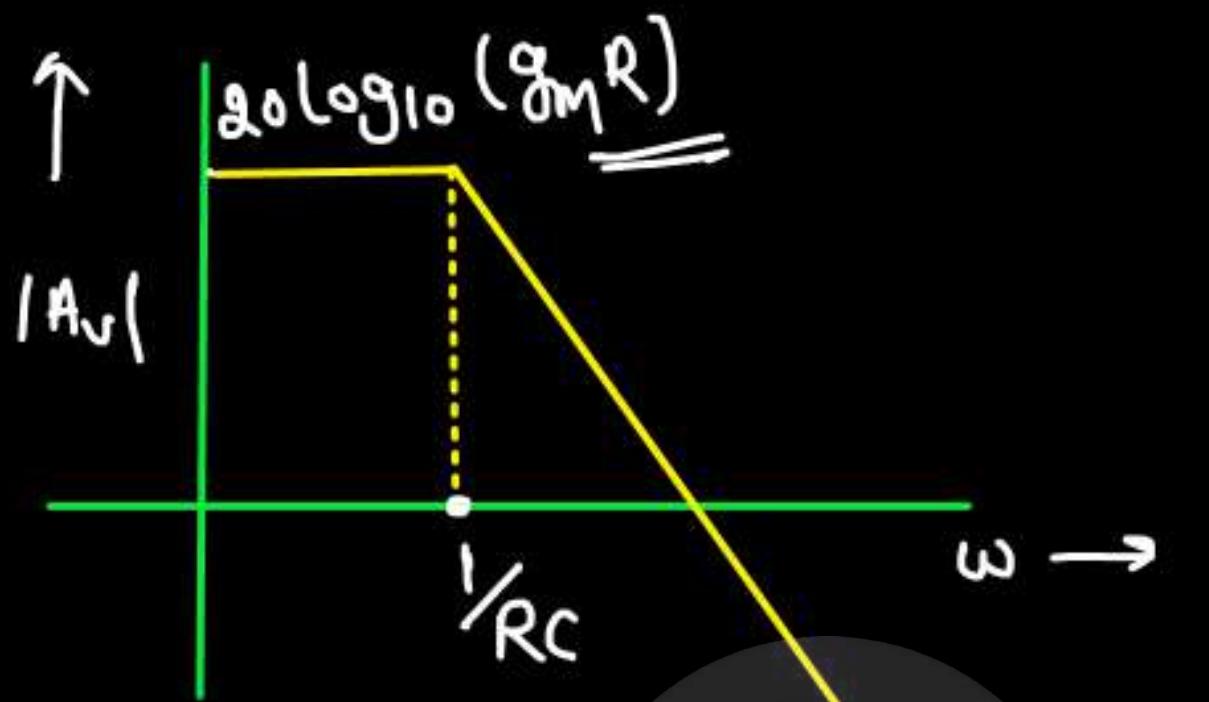

Let's assume $V_{i(s)} = 20mV \sin(\omega t)$

For better amplification,

$$\omega_i < \frac{1}{RC}$$

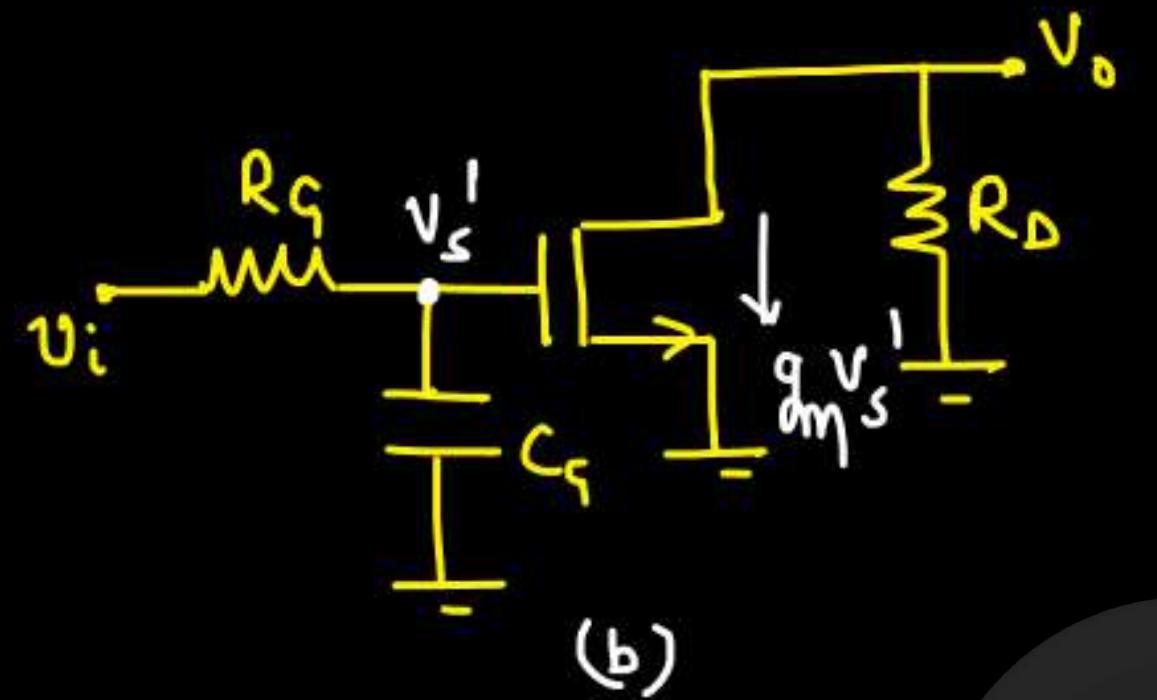


$$v_o = -g_m R_D v_s'$$

①

PrepFusion

$$v_s' = \frac{\frac{1}{C_Q s}}{\frac{1}{C_Q s} + R_Q} v_i = \frac{1}{R_Q C_Q s + 1} v_i$$
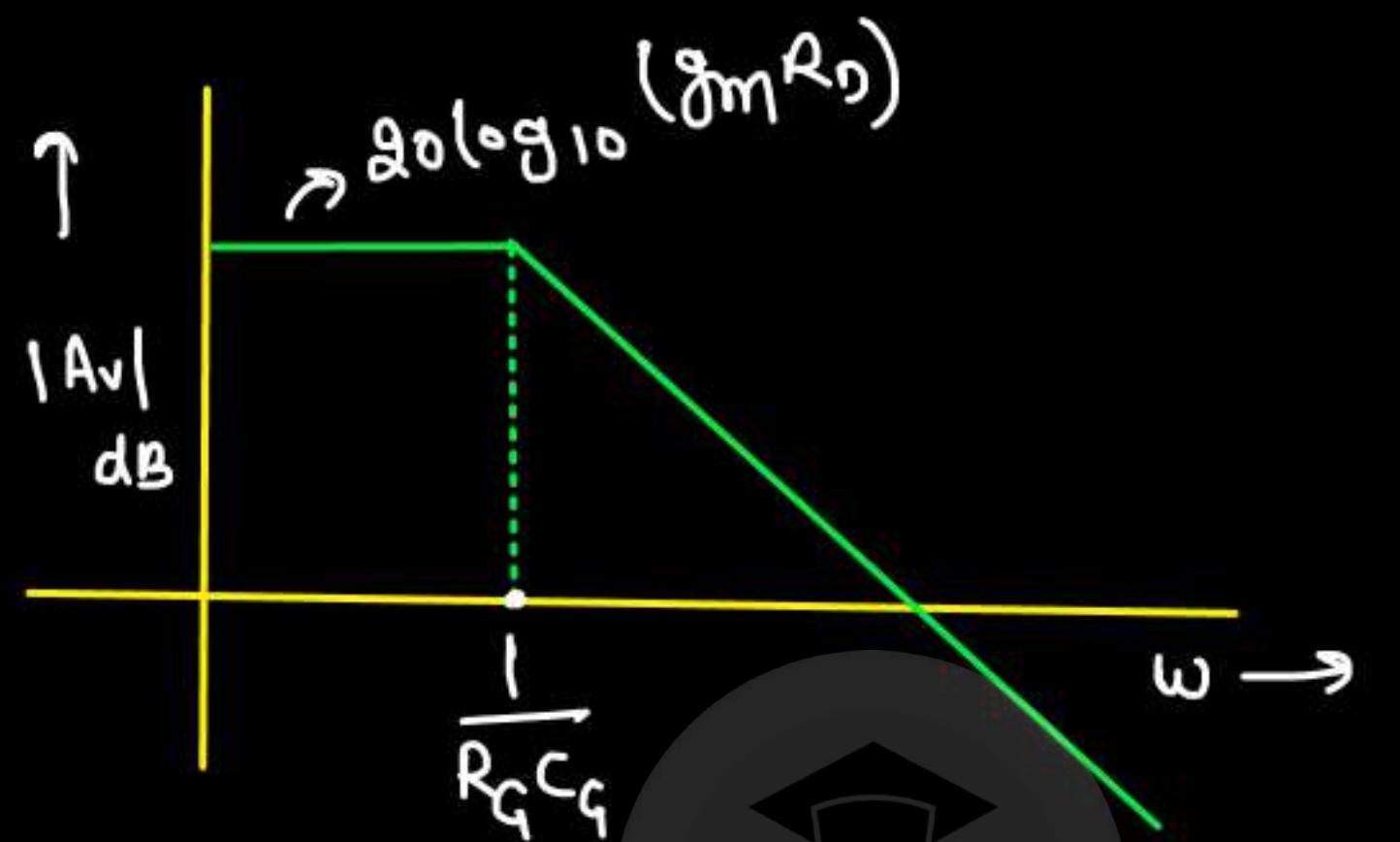
$$\frac{v_o}{v_i} = \frac{-g_m R_D}{R_Q C_Q s + 1}$$




$$V_i = V_m \sin(\omega_i t)$$



$$\omega_i \ll \frac{1}{R_0 C_0} \Rightarrow \text{for better amplification} =$$

Q.

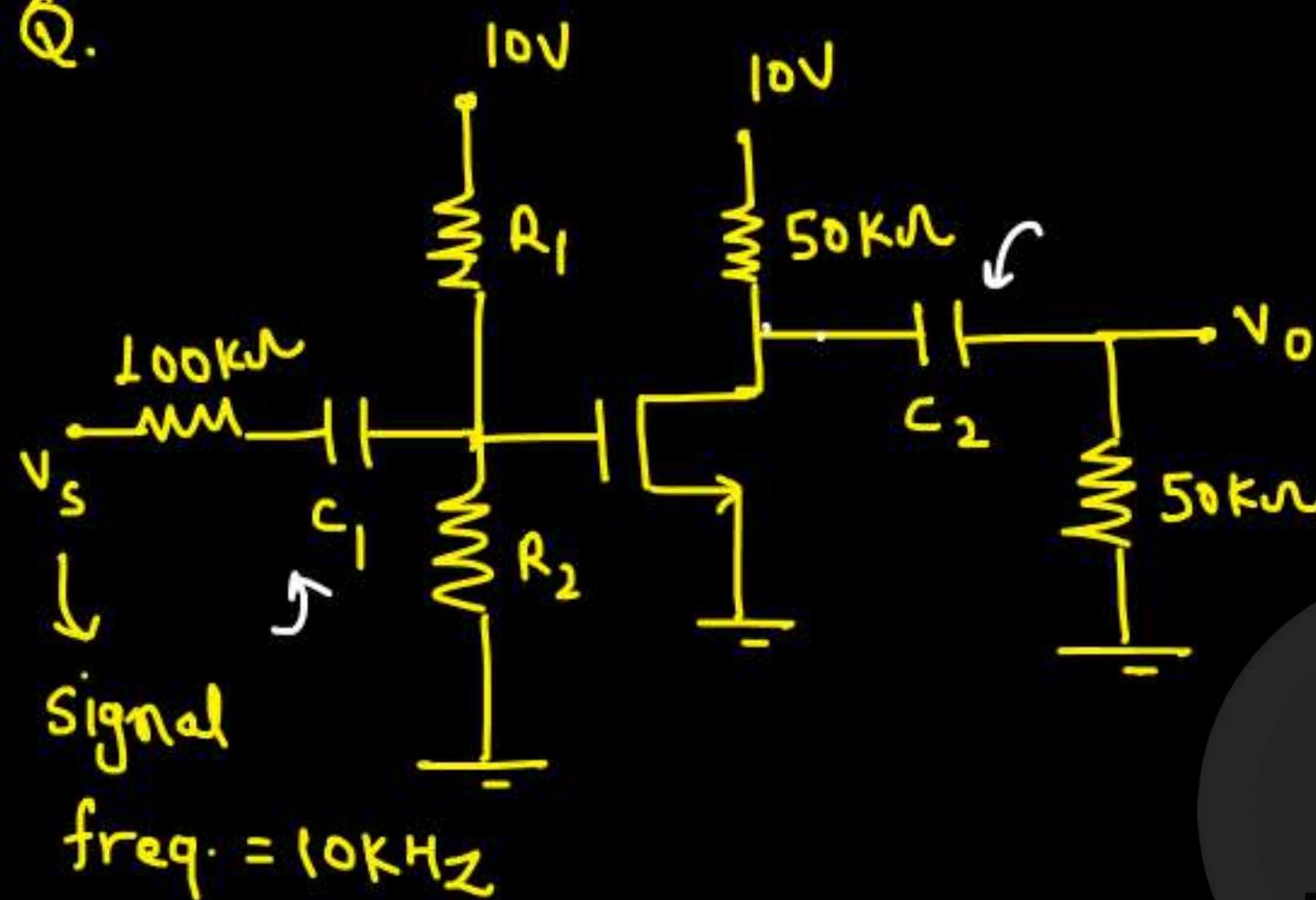

$C_1, C_2 \rightarrow$ coupling cap.

$$R_1 = 260\text{k}\Omega$$

$$R_2 = 740\text{k}\Omega$$


MOS is biased in sat.

How large you should choose C_1 and C_2 such that both cap. acts as short ckt @ signal freq. =

$$C_1 \gg C_{o1}$$

$$C_2 \gg C_{o2}$$

Determine C_{o1} and C_{o2} .

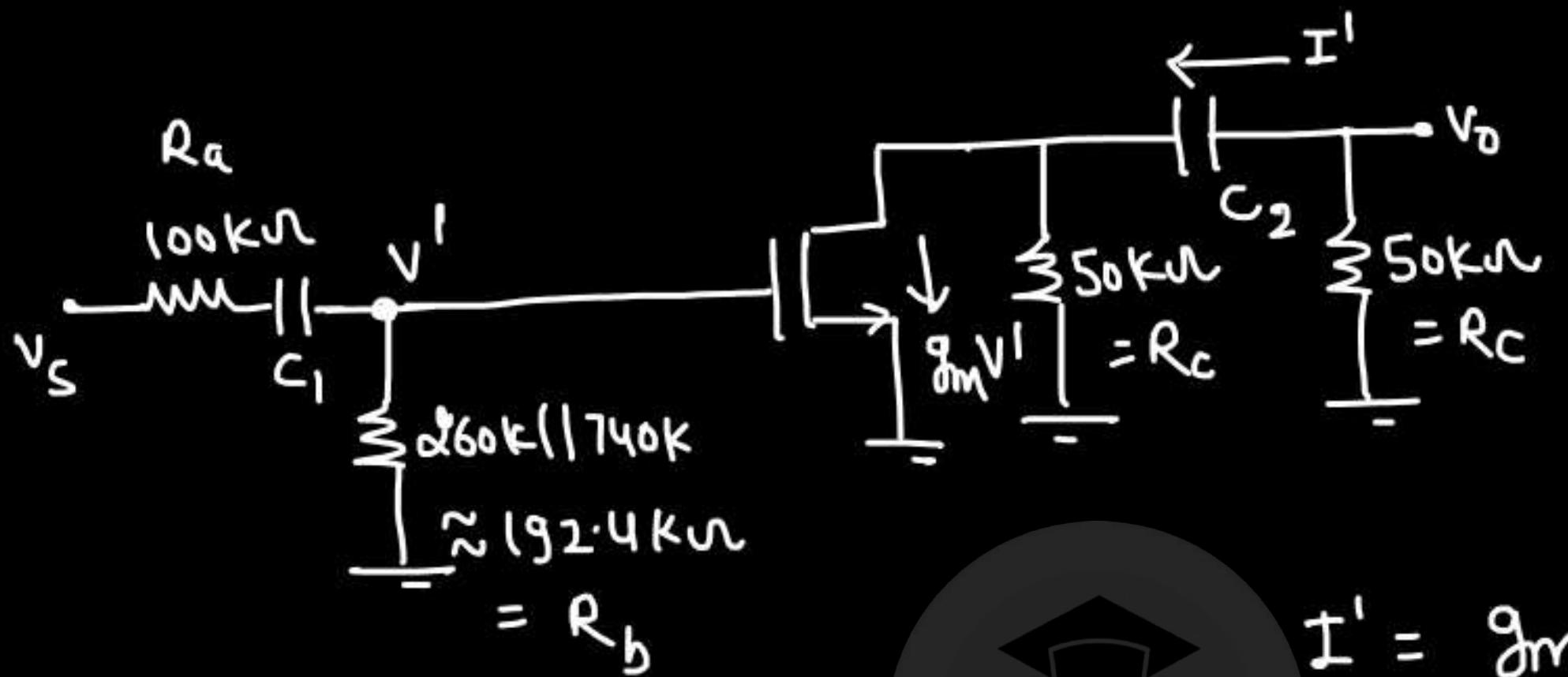

$$V' = \frac{R_b}{R_b + R_q + \frac{1}{C_1 s}} V_s(s)$$

$$V' = \frac{R_b C_1 s}{(R_b + R_q) C_1 s + 1} V_s(s)$$



$$I' = g_m V' \times \frac{R_c}{R_c + R_{ct} + \frac{1}{C_2 s}}$$

$$I' = g_m V' \times \frac{R_c C_2 s}{2 R_c C_2 s + 1} \quad \textcircled{2}$$

$$V_o = -I' R_c \quad \textcircled{3}$$

$$V_o(s) = - \frac{g_m R_c C_2 s}{2 R_c C_2 s + 1} \times \frac{R_b C_1 s}{(R_b + R_a) C_1 s + 1} V_i(s)$$

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = \frac{-g_m R_c R_b C_1 C_2 s^2}{(2 R_c C_2 s + 1)[(R_b + R_a) C_1 s + 1]}$$

An.

$$\omega_{Z_1} = \omega_{Z_2} = 0$$


PrepFusion

$$\omega_{P_1} = \frac{-1}{2 R_c C_2}$$

$$\omega_{P_2} = \frac{-1}{(R_b + R_a) C_1}$$

$$\omega_p = \frac{-1}{100k \times C_2}$$
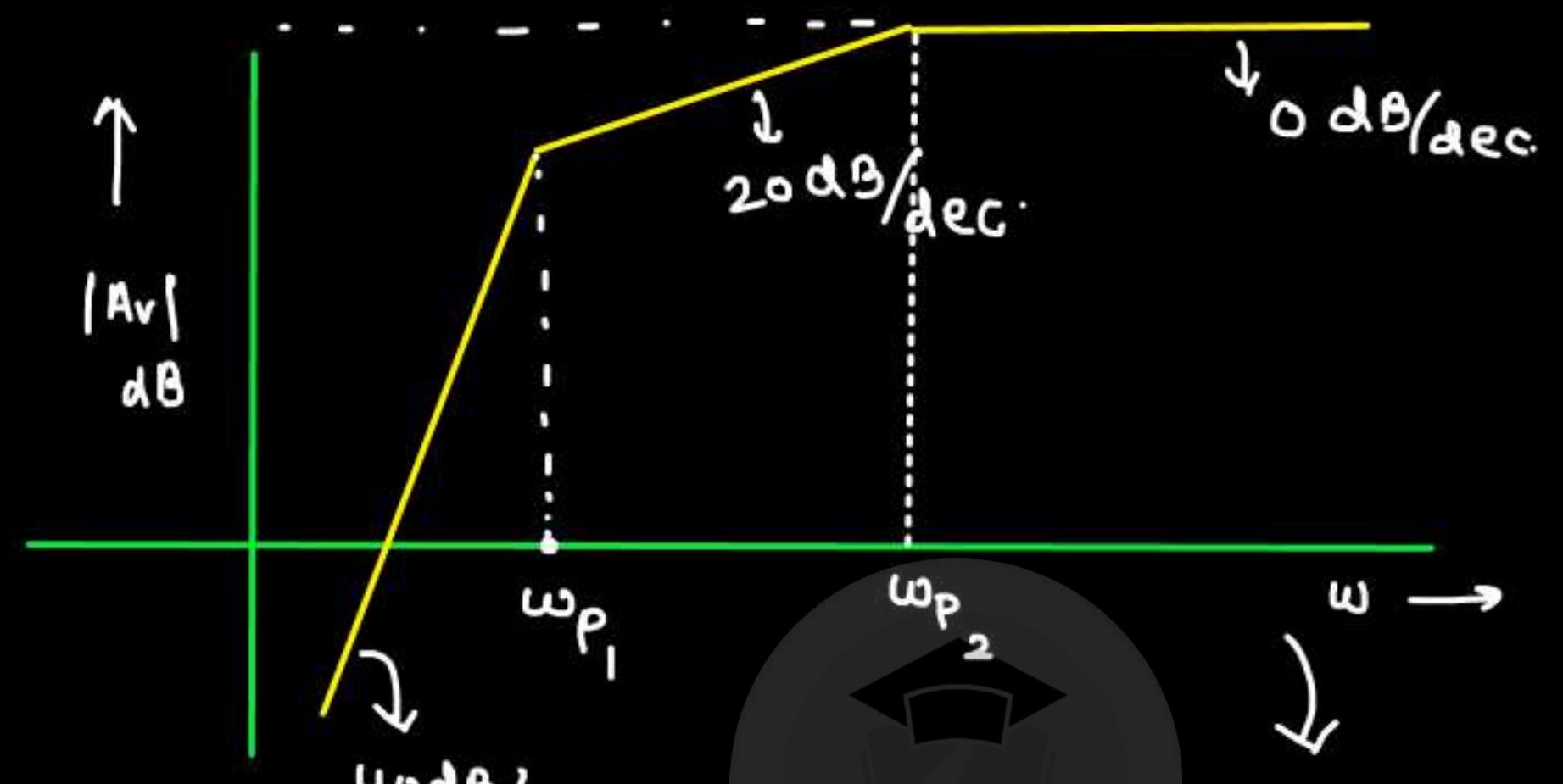
$$\omega_p = \frac{-1}{292.4k \times C_1}$$



$$\omega_{P_1} < 20k\pi$$

$$\frac{1}{100k \times C_2} < 20k\pi$$

∴ $C_2 > 159 \text{ pF}$

$$\omega_{P_2} < 20k\pi$$

$$\frac{1}{292.4k \times C_1} < 20k\pi$$

∴ $C_1 > 54.4 \text{ pF}$

$$= 20k\pi \text{ rad/sec}$$



$$\omega \rightarrow \\ 20 \text{ kHz}$$

Generally c_2 should be 1590 pF $[c_1, c_2 = 10C_0]$
 c_1 should be 544 pF


NOT ~~Imp.~~



⇒ High Freq. Model of MOS:-

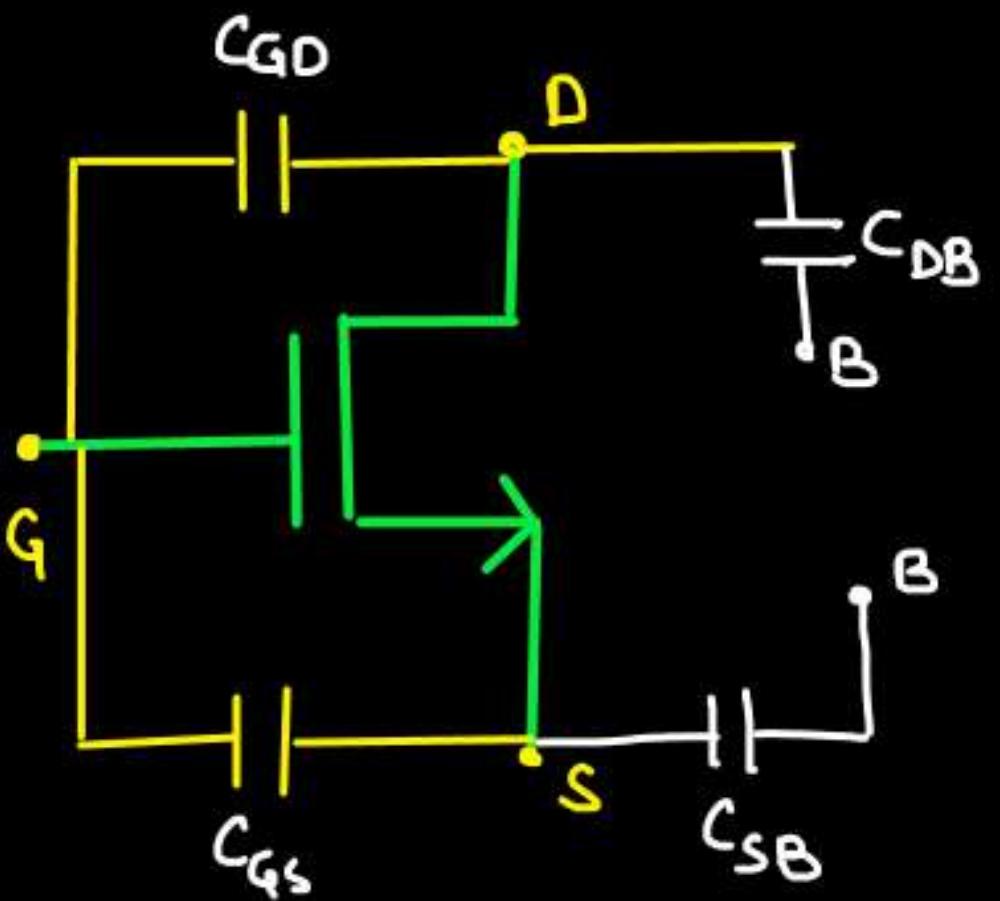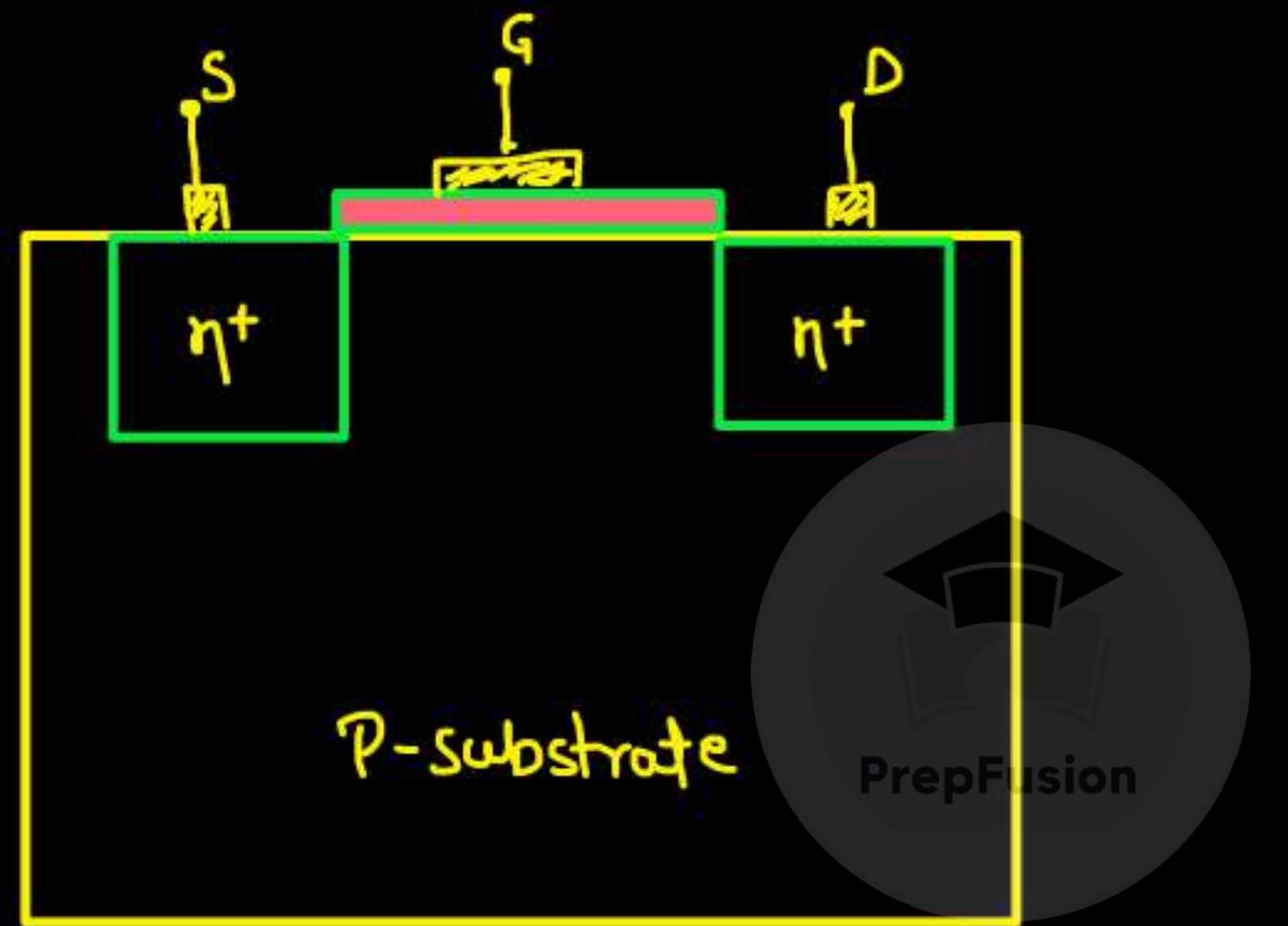

⇒

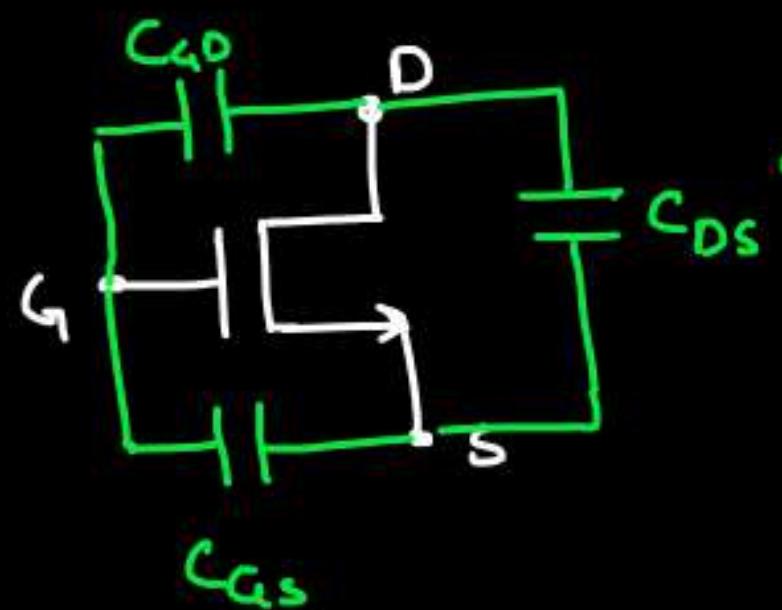

+nt @ Higher freq.

$C_{GS}, C_{GD}, C_{DS} \sim PF, fF$
(small) Range


$$@ \text{ low freq.} \Rightarrow \frac{1}{C_{GS}} = \frac{1}{\text{very low} \times \text{very low}} = \frac{1}{0} = \infty \Rightarrow 0^\circ \text{C}$$

$$@ \text{ High freq.} \Rightarrow \frac{1}{C_{GS}} = \frac{1}{\text{very low} \times \text{very high}} = \frac{1}{\text{considerable}} \Rightarrow \text{stays in action}$$

⇒ @ low and mid freq., Parasitic / Internal / Jⁿ cap. are open ckt.

@ High freq., They come in action

Q.

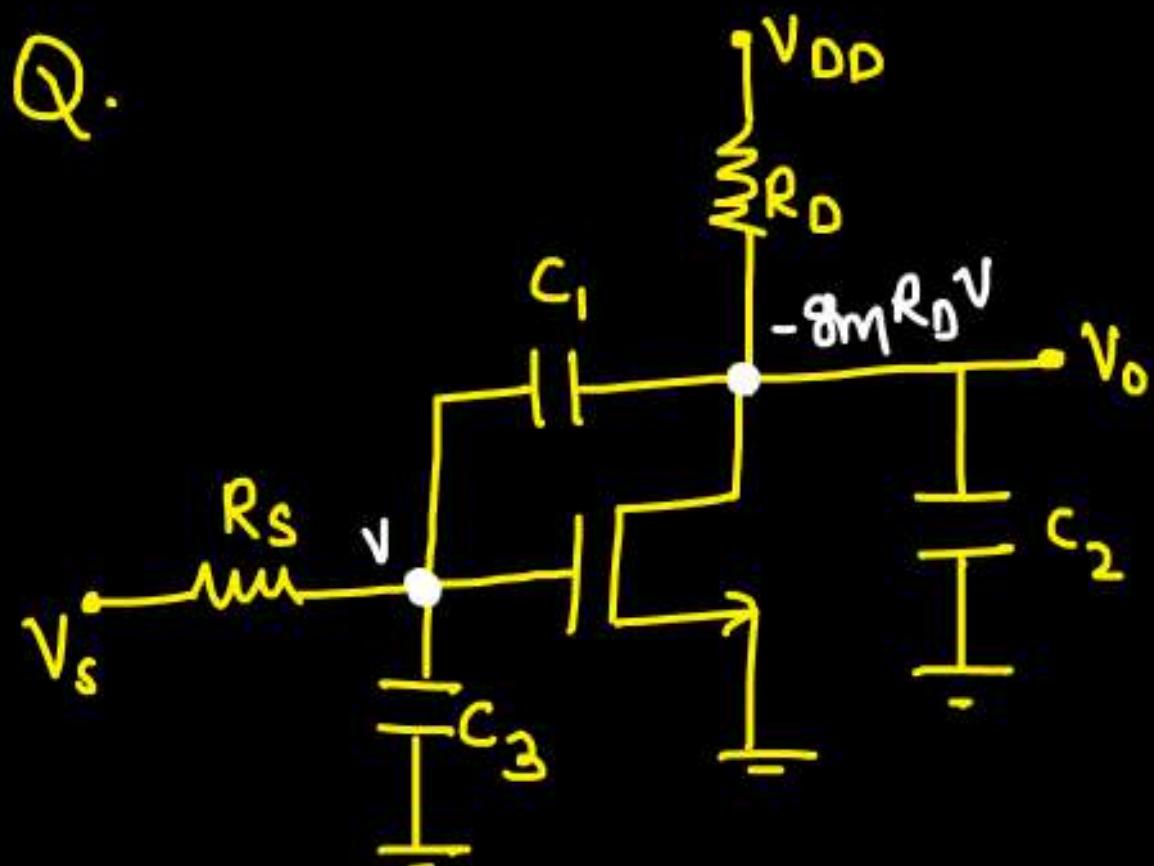


Given that C_1, C_2 & C_3
are parasitic cap.

[$C_1, C_2, C_3 \rightarrow$ very low value
pf]

Draw the freq. response.



PrepFusion

DC gain :-

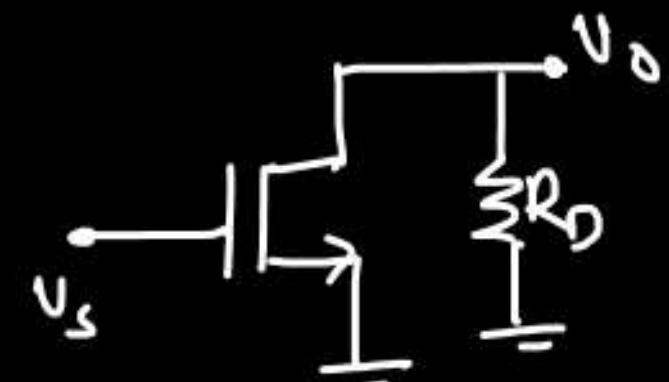

$$\frac{V_o}{V_s} = -g_m R_D$$

Applying Miller's Theorem :-

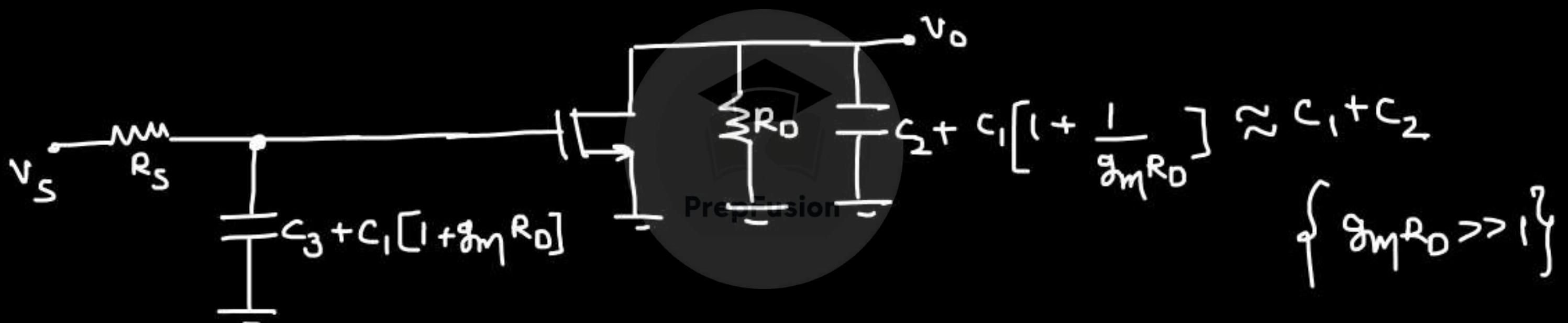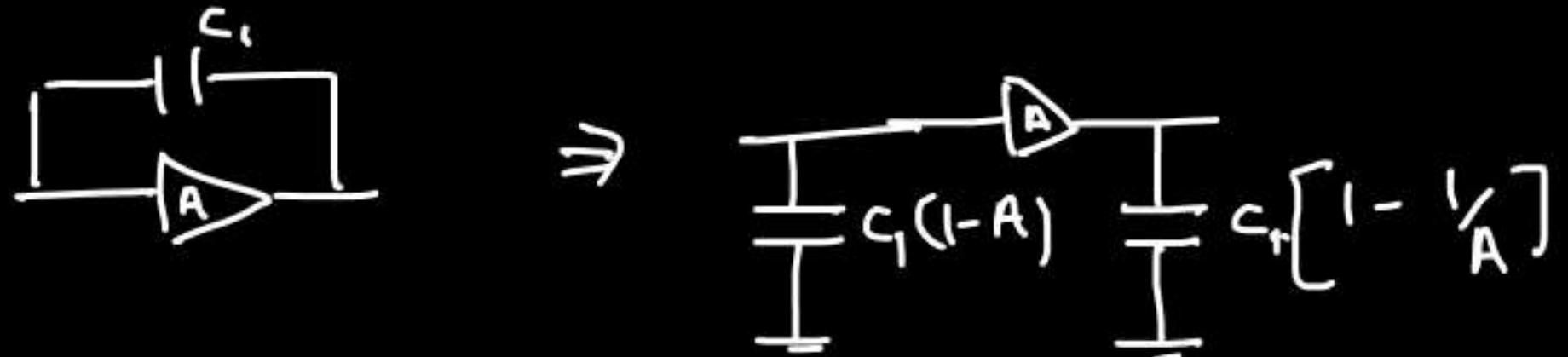


$$\frac{V_o(s)}{V_s(s)} = \frac{-g_m R_D}{\left[C_3 + C_1 (1 + g_m R_D) \right] R_s s + 1} \left\{ R_D (C_1 + C_2) s + 1 \right\}$$

$$\omega_{Z_1} = \infty$$


$$\omega_{Z_2} = 0$$

$$\omega_p = \frac{-1}{R_D(C_1 + C_2)}$$

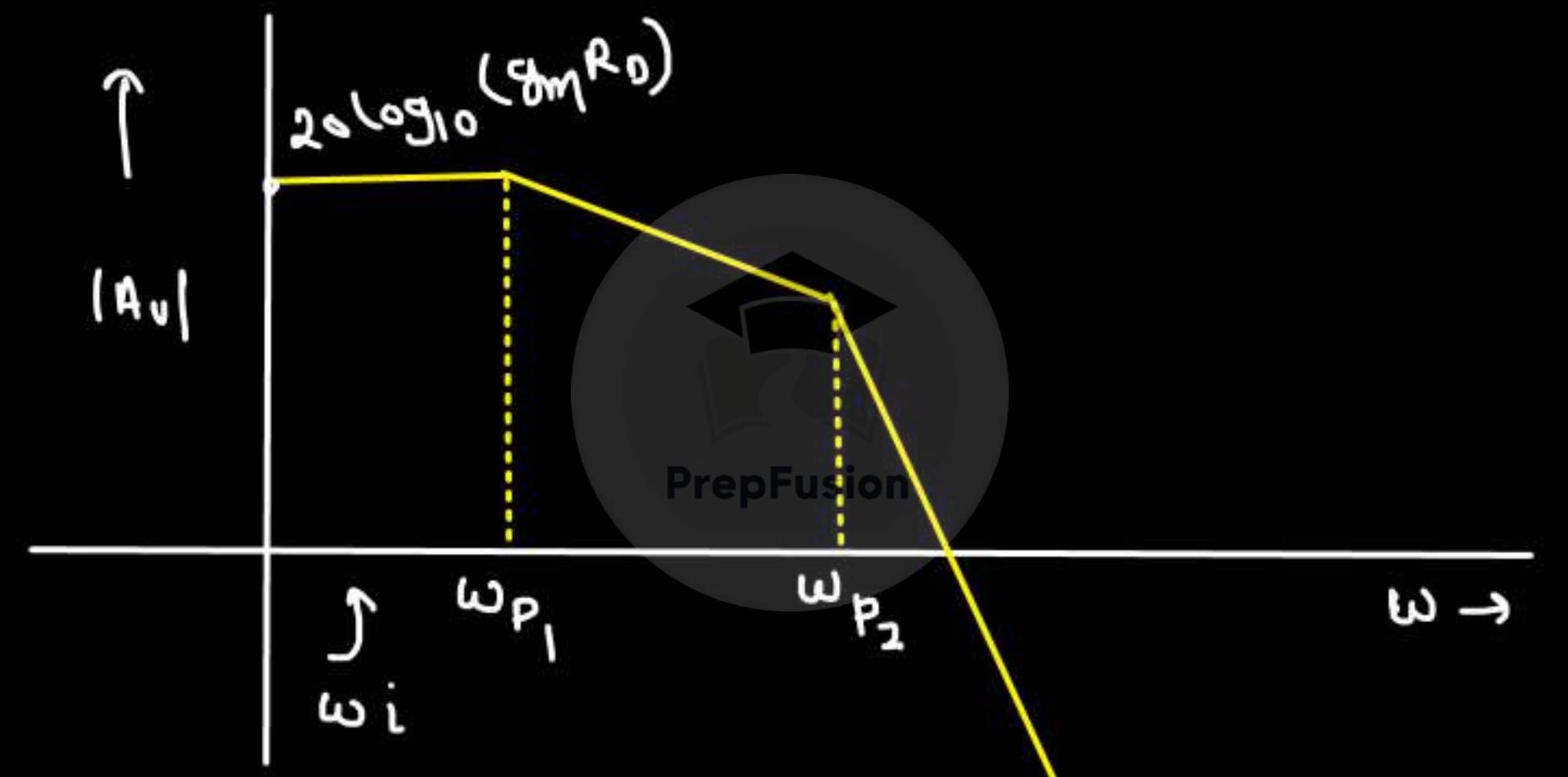
$$\omega_p = \frac{-1}{[C_0 + C_1(1 + g_m R_D)] R_S}$$



N.B. →

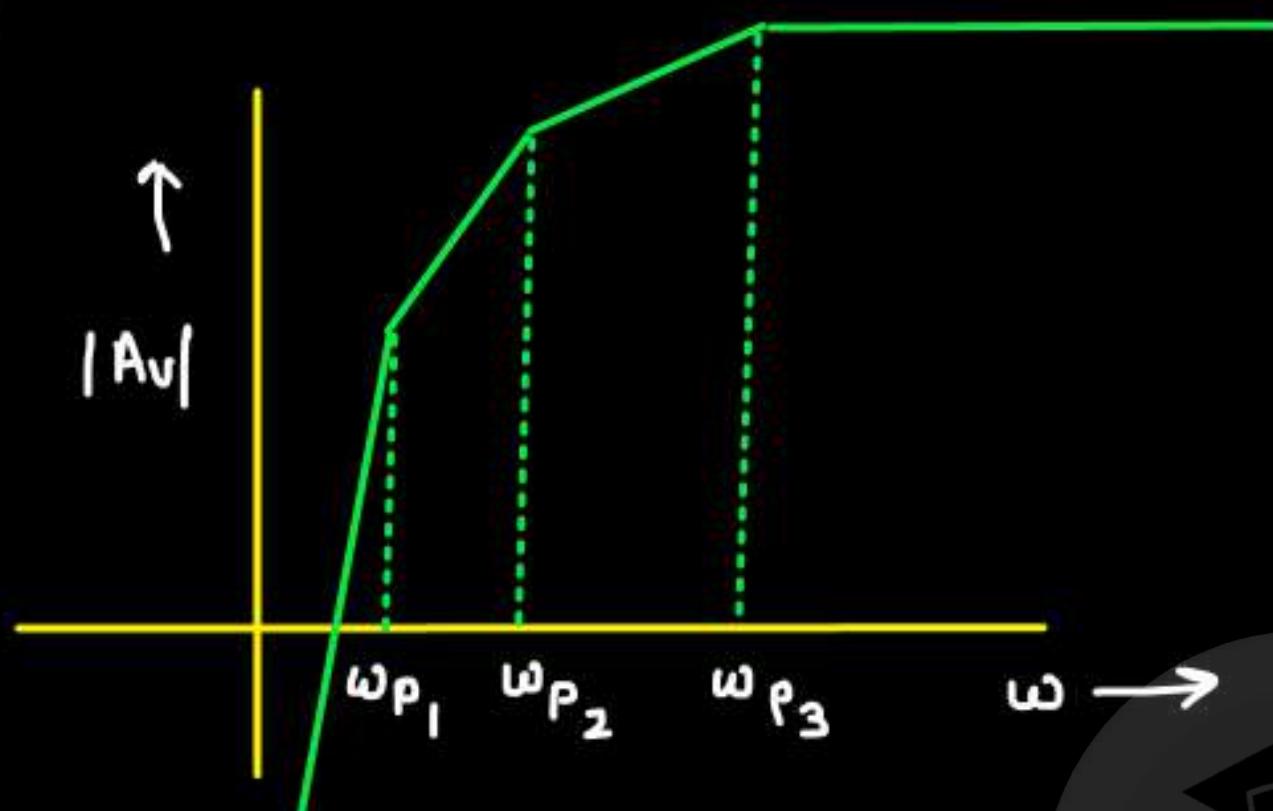

↓
3-dB cut-off freq. = ω_{P_3}

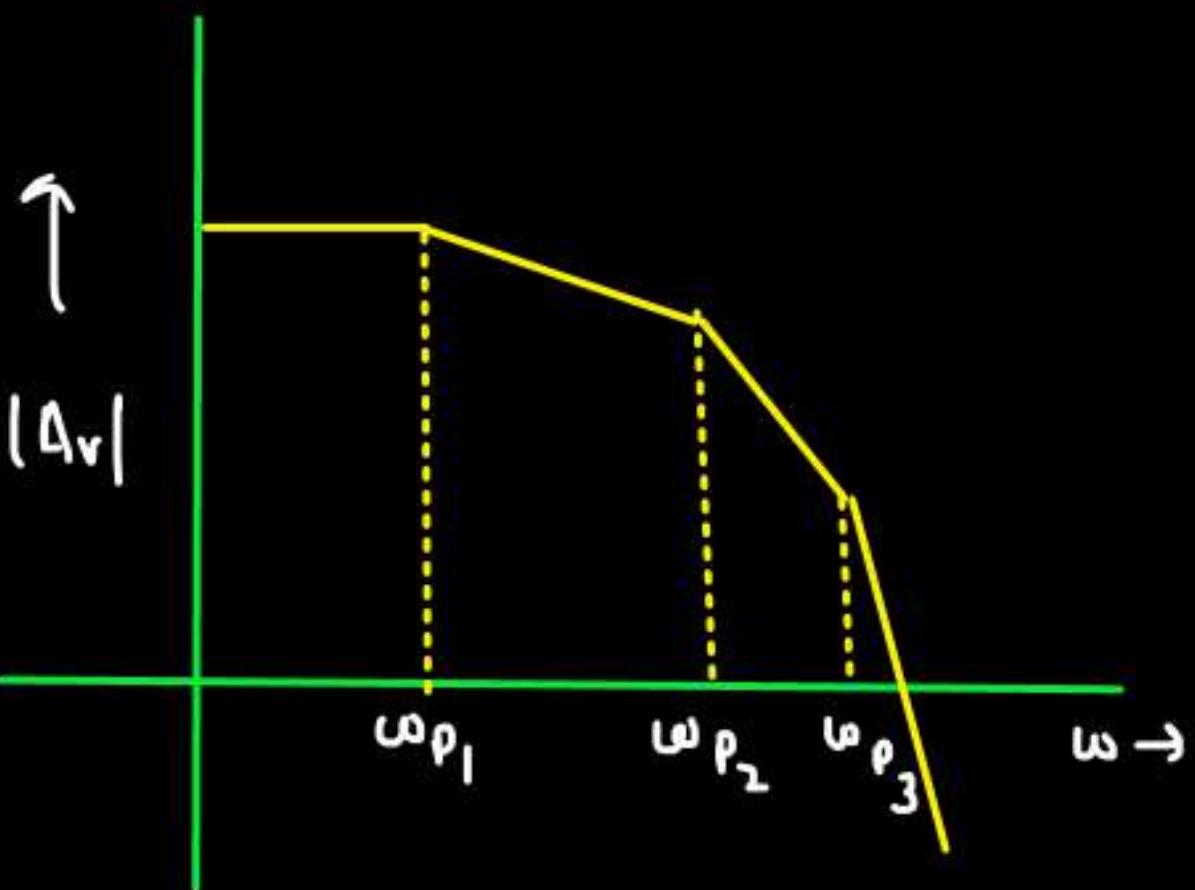

3-dB cut-off freq. = ω_{P_1}

Low Freq. Model of MOS:-

↓
coupling cap. will be in action
↓
(η_f or $\mu_f \rightarrow \underline{\text{High}}$)

@ low freq. $\Rightarrow \frac{I}{c_c s} = \frac{I}{\text{High} \times \text{low}}$ = will be in action

PrepFusion

Consider

@ High freq. $\Rightarrow \frac{I}{\text{High} \times \text{High}} = \frac{I}{\infty} = 0$ = cap. will act as S.C.

\Rightarrow @ low freq. \Rightarrow coupling cap. are in action


\Rightarrow @ High freq. & Mid freq. \Rightarrow coupling cap. is S.C.

Conclusion:-

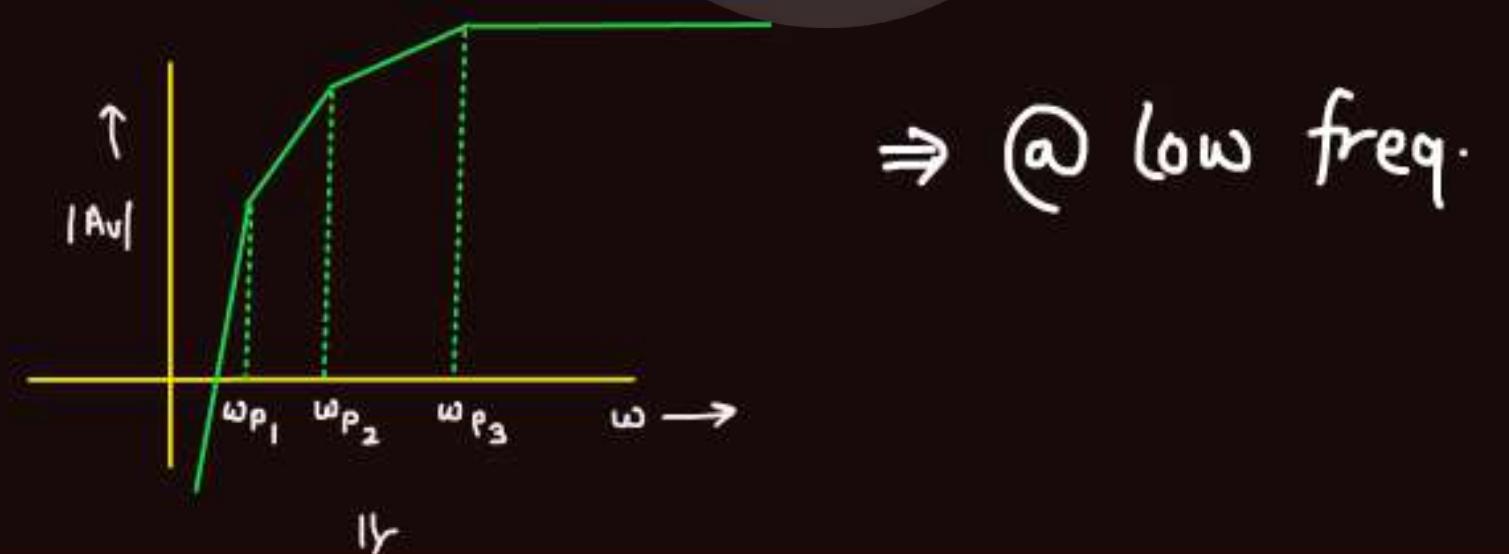(a) Coupling cap:-

- ↳ Will be in action @ low freq.
- ↳ Response will be of HPF.
- ↳ Will act as S.C. @ High and Mid freq.


Coupling \Rightarrow Low freq. \Rightarrow H.P. \Rightarrow 3-dB cut off freq. will be Highest pole



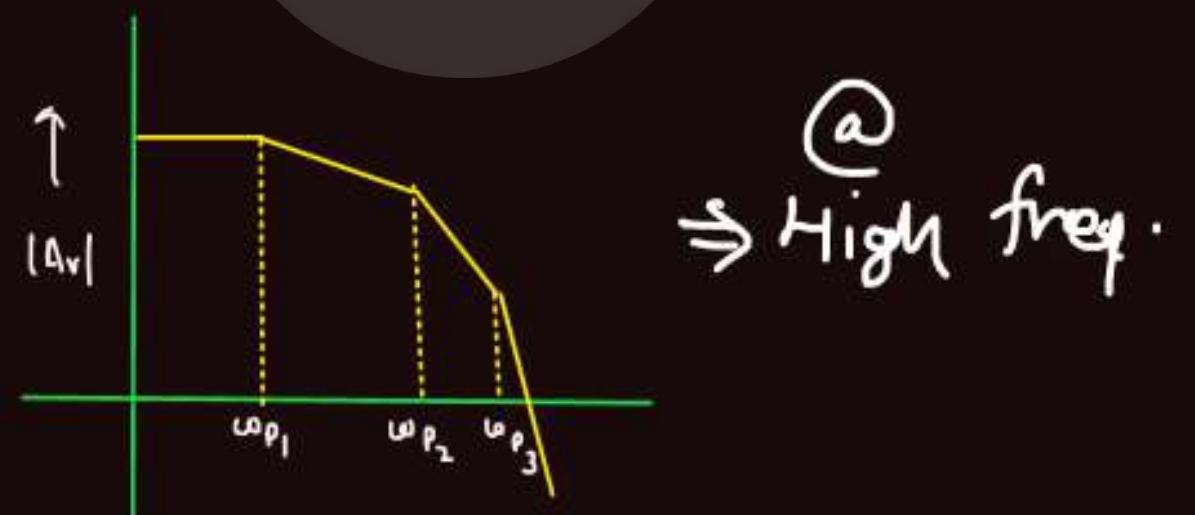
(b) Parasitic / Internal / J^n cap. -

- ↳ Will be in action @ High freq.
- ↳ Response will be of LPF
- ↳ Will act as o.c. @ low and Mid freq.

Parasitic / Internal / J^n cap. \Rightarrow High freq. \Rightarrow LPF \Rightarrow cut-off freq. will be min pole.



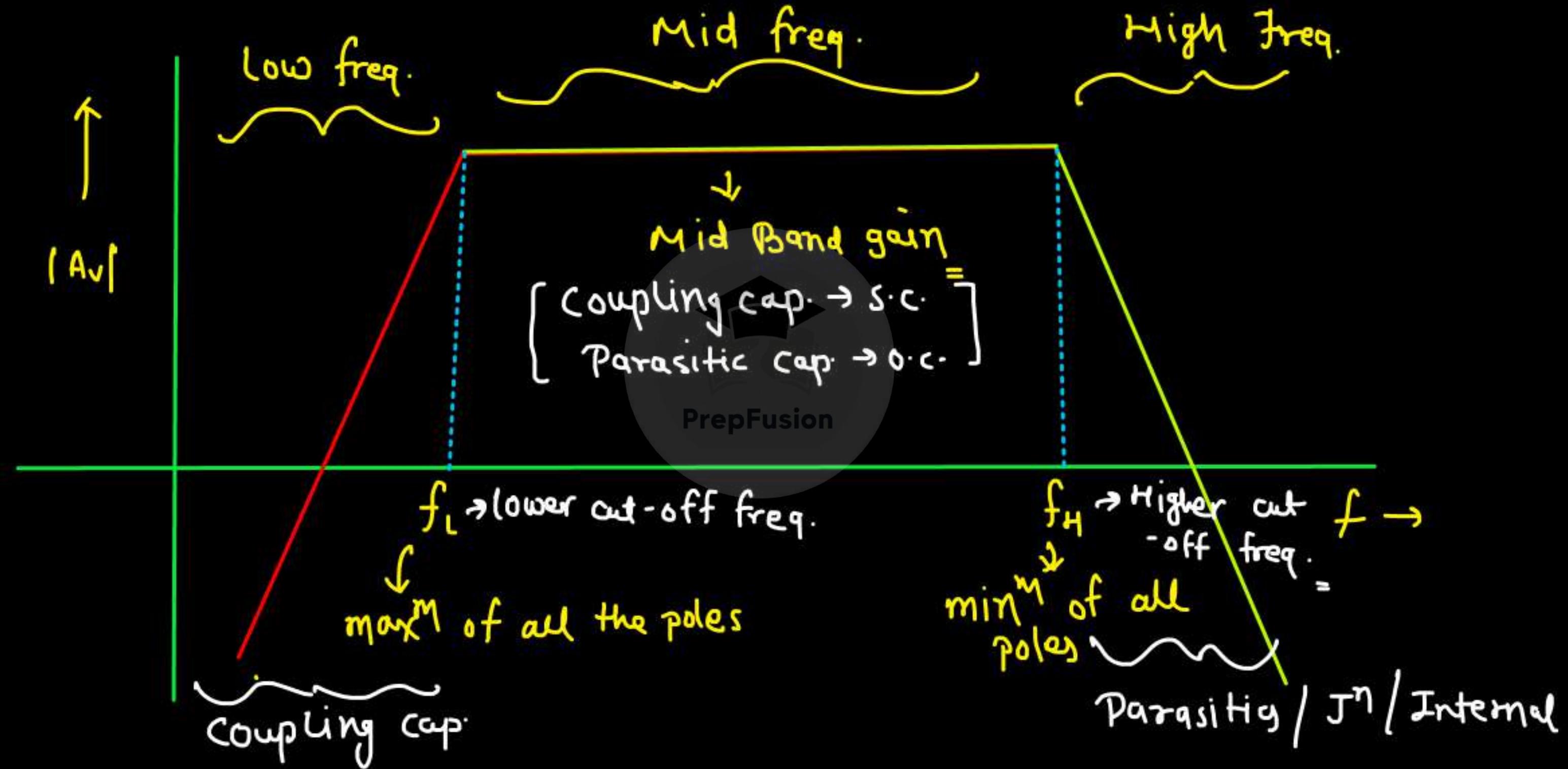⇒ Freq. Response of a RC Coupled MOS Amp:-



⇒ How to find a pole in MOS ckt.

- ① find the order of the ckt.
- ② nullify the i/p and find equivalent resistance across cap. [consider the other cap. shorted]

$$\omega_p = \frac{1}{C R_{eq}}$$



⇒ How to find a zero in MOS ckt.:

- ① NO hard and fast rule. Do intelligent analysis.


$$T(s) = \frac{A \left(\frac{s}{z_1} + 1 \right) \left(\frac{s}{z_2} + 1 \right) \dots \left(\frac{s}{z_n} + 1 \right)}{\left(\frac{s}{R_1} + 1 \right) \left(\frac{s}{R_2} + 1 \right) \dots \left(\frac{s}{R_n} + 1 \right)}$$

$\Rightarrow A = \frac{dc}{gain}$
($\omega=1$)

@ $s = -z_1 \Rightarrow T(s) = 0$


@ zero, T.F. becomes zero. $\frac{V_o(\omega)}{V_i(s)} \rightarrow 0 \Rightarrow V_o(s) \rightarrow 0$

Eg. →

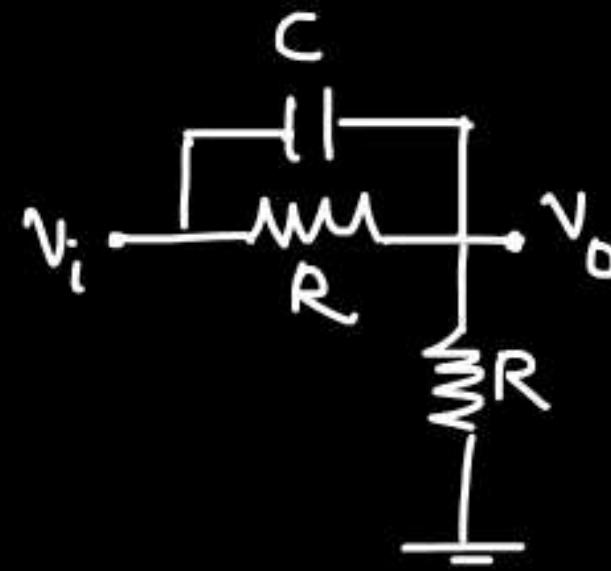

① Order = 1st

② Poles →

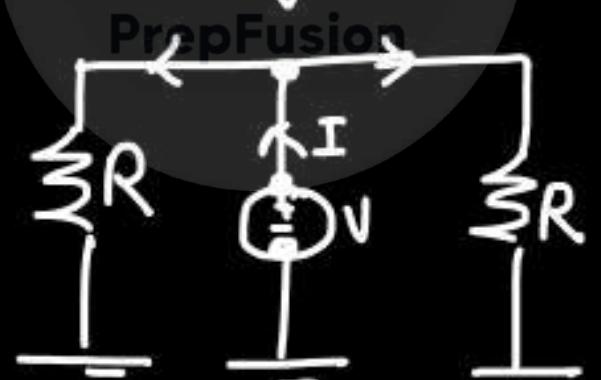


$$\Rightarrow R_{eq} = R/2$$

$$C_{eq} = C$$

$$\omega_p = \frac{-1}{R_{eq}C} = -\frac{2}{RC}$$

③ zero →

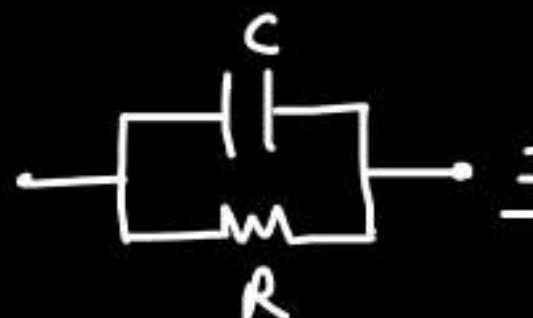

$$= \frac{R}{RCj + 1} = 0$$


$$\Rightarrow s_z = -\frac{1}{RC}$$

$$T.F. = \frac{A(sRC + L)}{\left(\frac{sRC}{2} + 1\right)} = \frac{2A(sRC + L)}{(sRC + 2)}$$

@ $\omega=0$ $T.F. = A$


in the given ckt

@ $\omega=0$

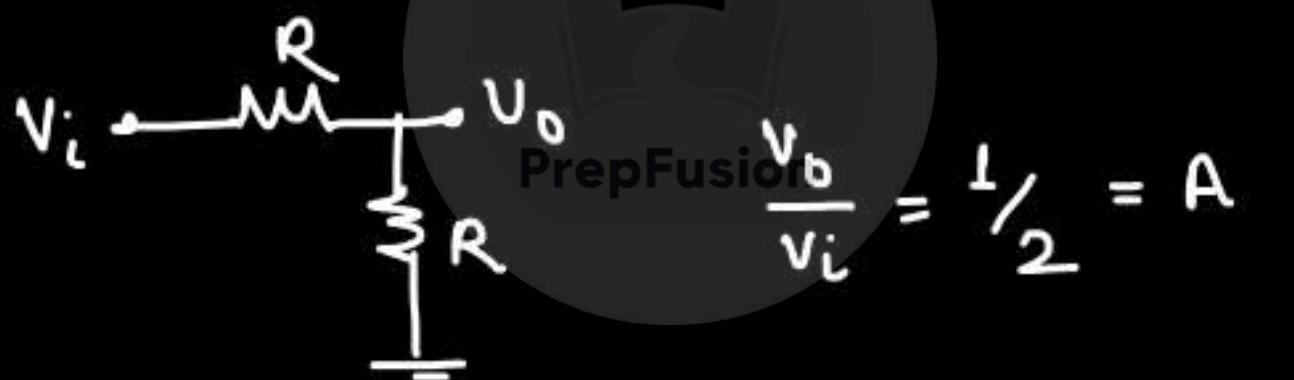

$T.F. = T(s) = \frac{sRC + 1}{sRC + 2}$

Q.

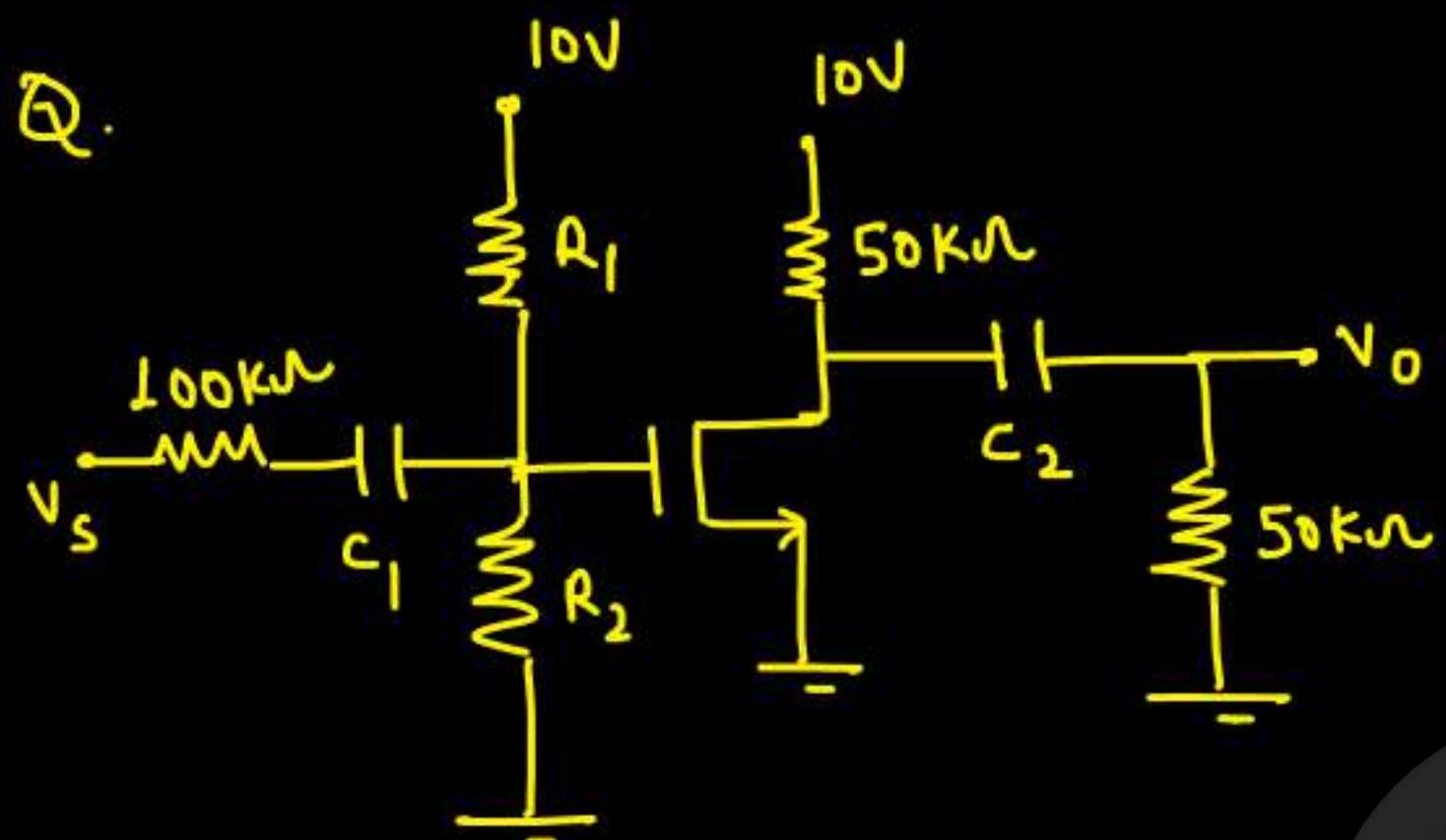

how freq. operation

(a) Determine the order of ckt.

(b) Find the location of poles.

(c) Determine 3-dB cut-off

PrepFusion


$$\text{freq. (kHz)} =$$

$$R_1 = 260 \text{ k}\Omega$$


$$R_2 = 740 \text{ k}\Omega$$

$$C_1 = 100 \text{ pF}$$

$$C_2 = 200 \text{ pF}$$

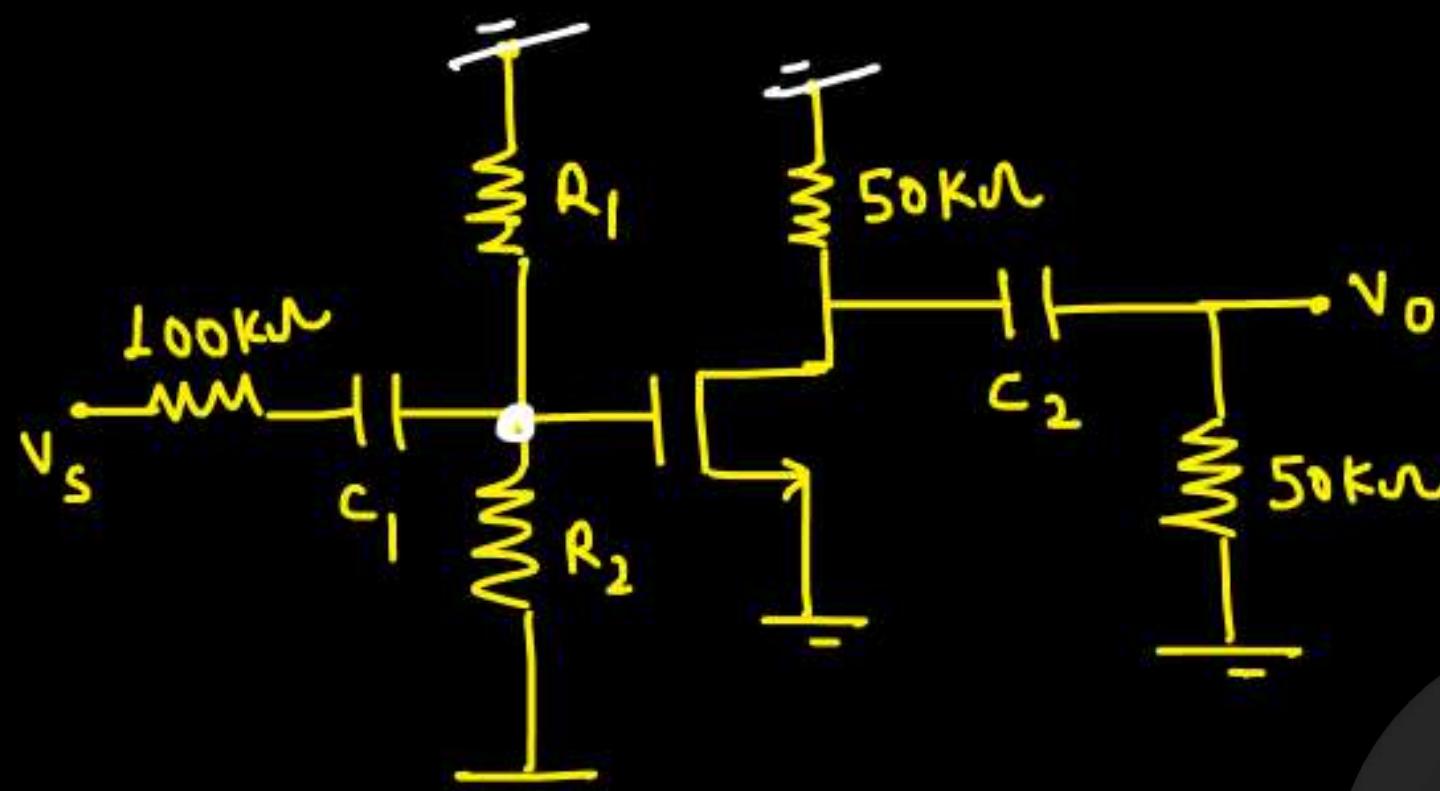

Pole because of C_2

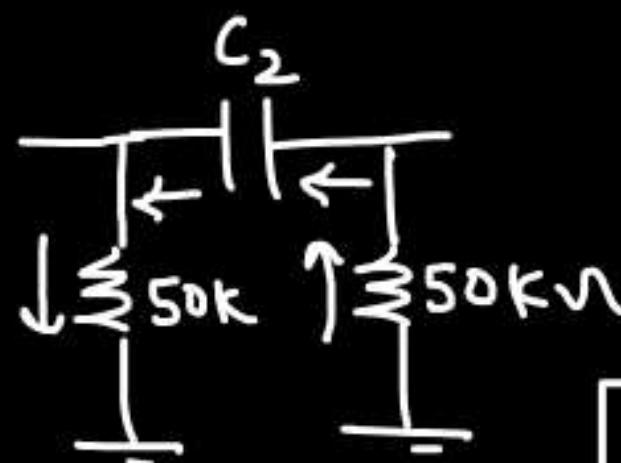

$$R_{eq} = 100k\Omega$$

$$C_2 = 100 \text{ pF}$$

$$\omega_{p_2} = \frac{1}{R_{eq} C_2} = 100 \text{ Krad/sec.}$$

① order = 2nd

② Poles : -

Pole because of C_1

→ S.C. C_2 , S.C. input v_s



Op Amp.

$$R_{eq} = 100k\Omega \parallel 260k \parallel 740k$$

$$= 192.4k\Omega$$

$$C_{eq} = C_1 = 100 \text{ pF} = 10^{-10} \text{ F}$$

$$R_{eq} = 192.4 + 100 = 292.4 \text{ k}\Omega$$

$$\omega_{p_1} = \frac{1}{R_{eq} C_1} = 34.2 \text{ Krad/sec.}$$

$$3\text{-dB cut-off freq.} = \max^M (\omega_{p_1}, \omega_{p_2}) \\ = 100 \text{ k rad/sec.}$$


$$\omega_{dB} = 15.91 \text{ kHz}$$

@ $\omega=0$, Because of C_2 , v_o is zero


@ $\omega=0$, Because of C_1 , v_o is zero

\Rightarrow You have two zeros @ $\omega=0$
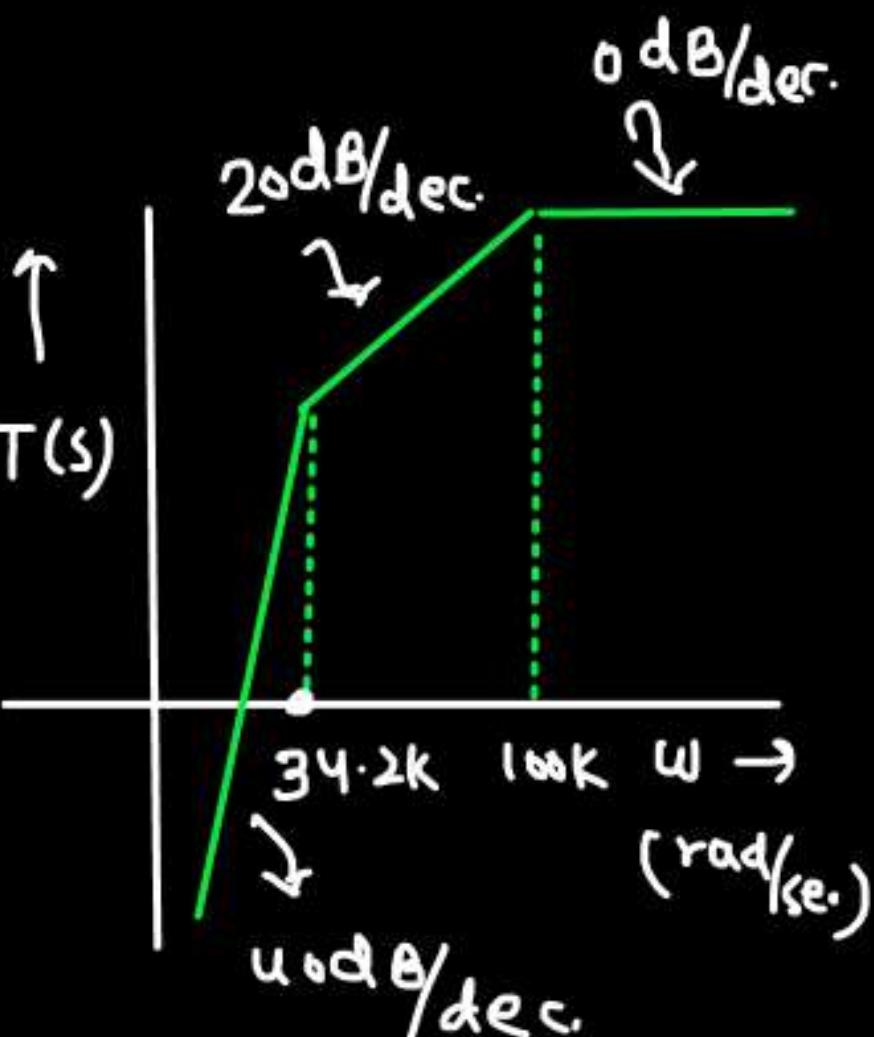
$$T(s) = \frac{K s^2}{\left(\frac{s}{34.2k} + 1\right) \left(\frac{s}{100k} + 1\right)}$$



Q.


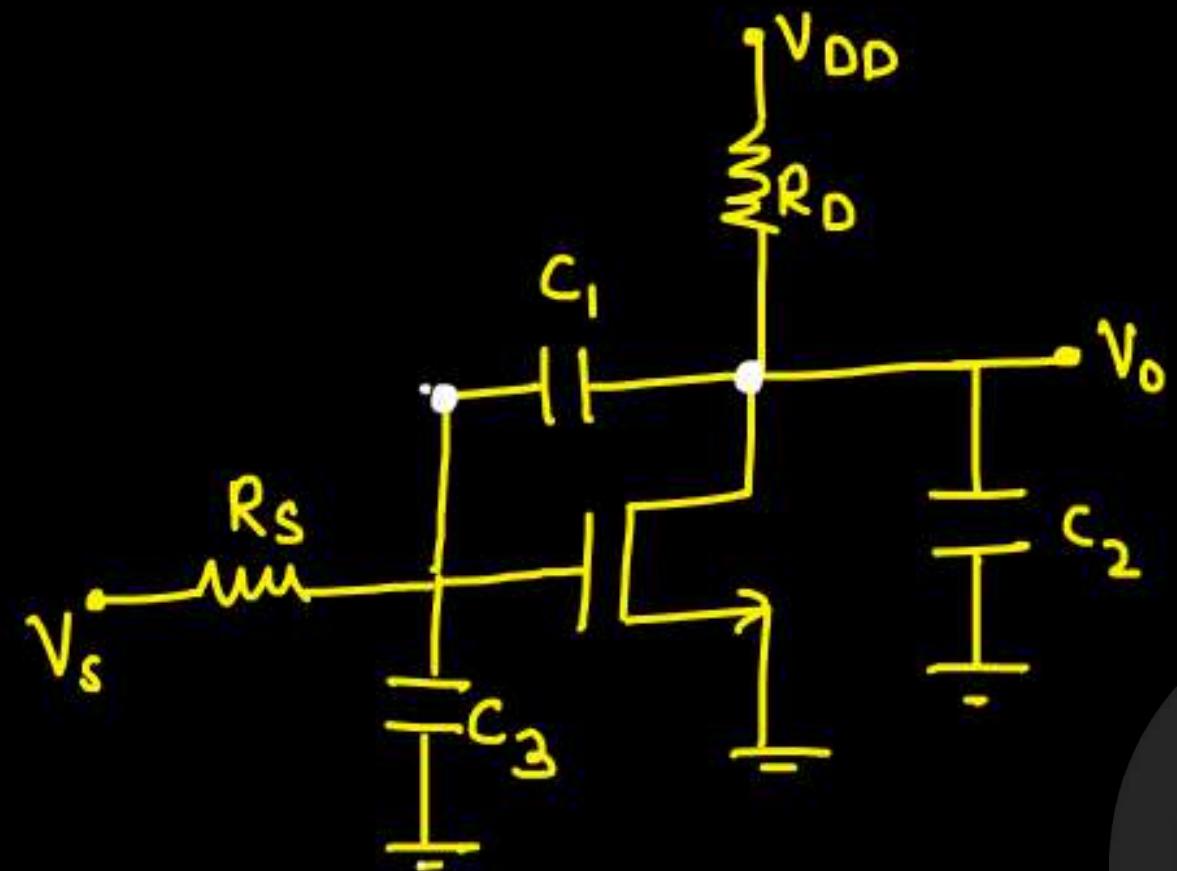


Given that C_1, C_2 & C_3
are parasitic cap.

[$C_1, C_2, C_3 \rightarrow$ very low value
pf]

(a) 2nd order

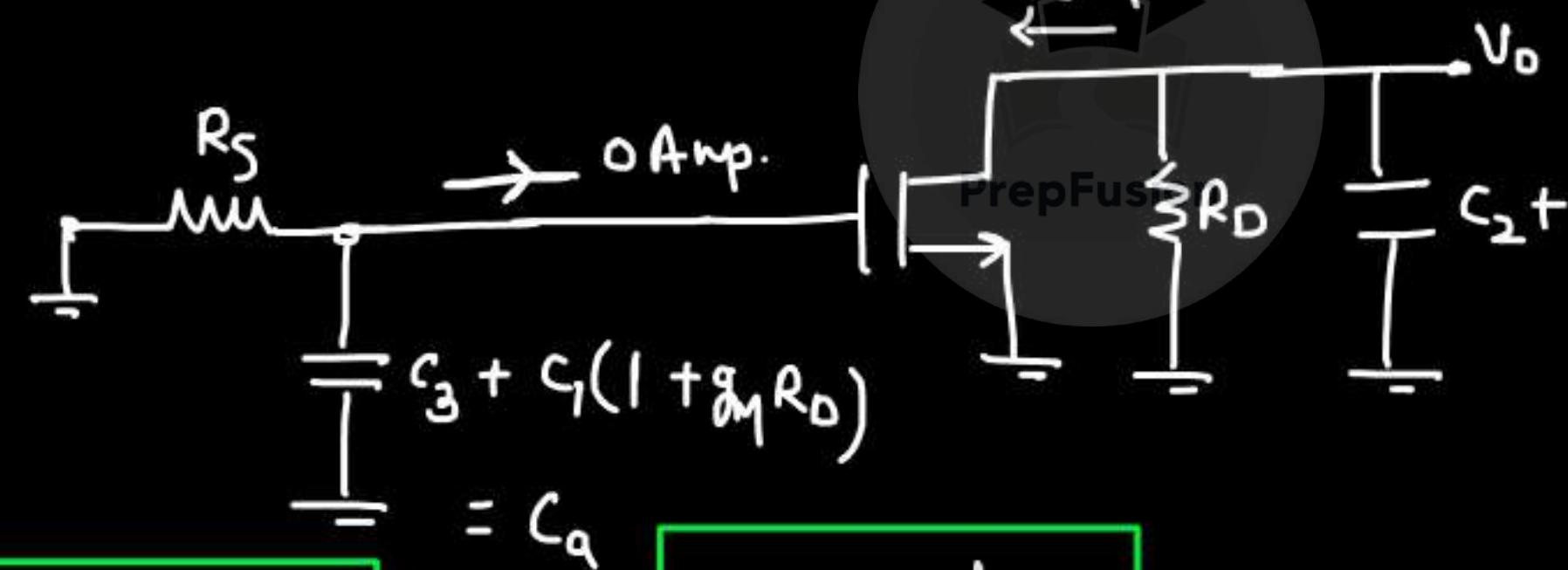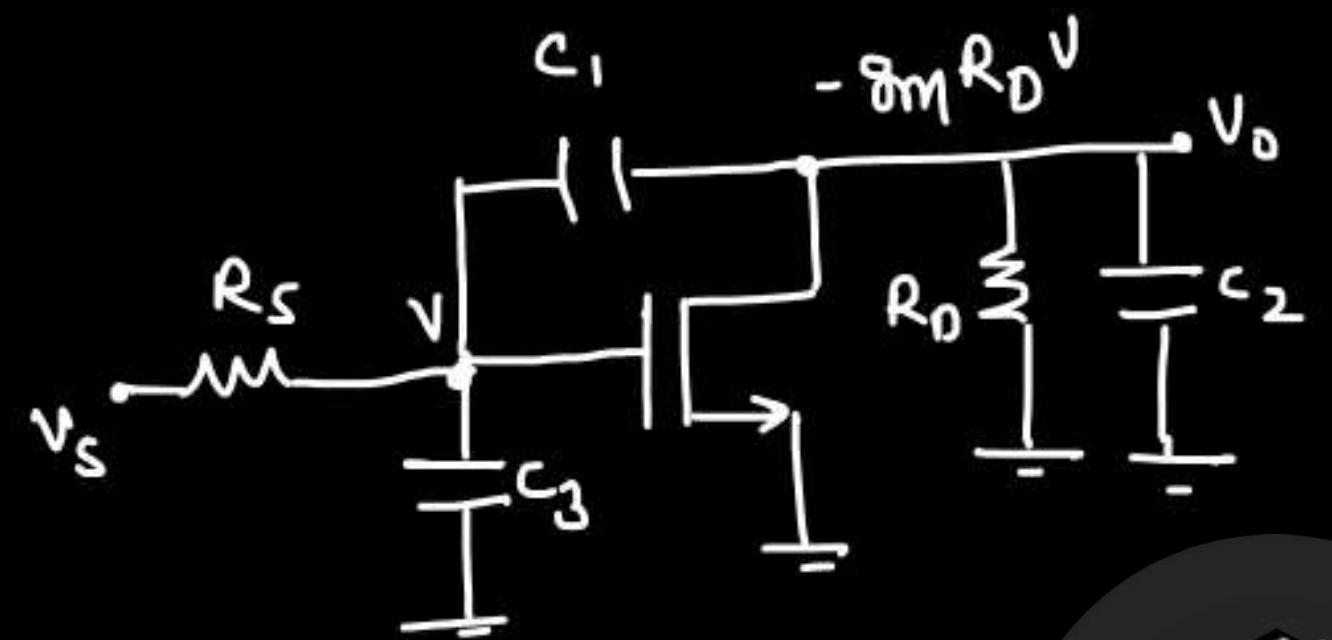- (a) Determine the order of the ckt.
 Prebusn
 (b) Determine the location of poles.
 (c) Draw freq. response.
 (d) Tell 3-dB cut-off freq.



$$\frac{1}{C_2 + C_1 \left[1 + \frac{1}{g_m R_D} \right]} \approx C_b = C_b$$

$$\omega_{P_1} = \frac{1}{R_s C_a}$$


$$\omega_{P_2} = \frac{1}{R_D C_b}$$

Because of C_2 , @ $\omega = \infty$, $V_0 = 0 \Rightarrow$ zero @ ∞


Because of C_3 , @ $\omega = \infty$, $V_0 = 0 \Rightarrow$ zero @ ∞

$$T.F. = \frac{-g_m R_D}{\{SR_S[C_3 + C_1(1 + g_m R_D)] + 1\} \{SR_D(C_1 + C_2) + L\}}$$

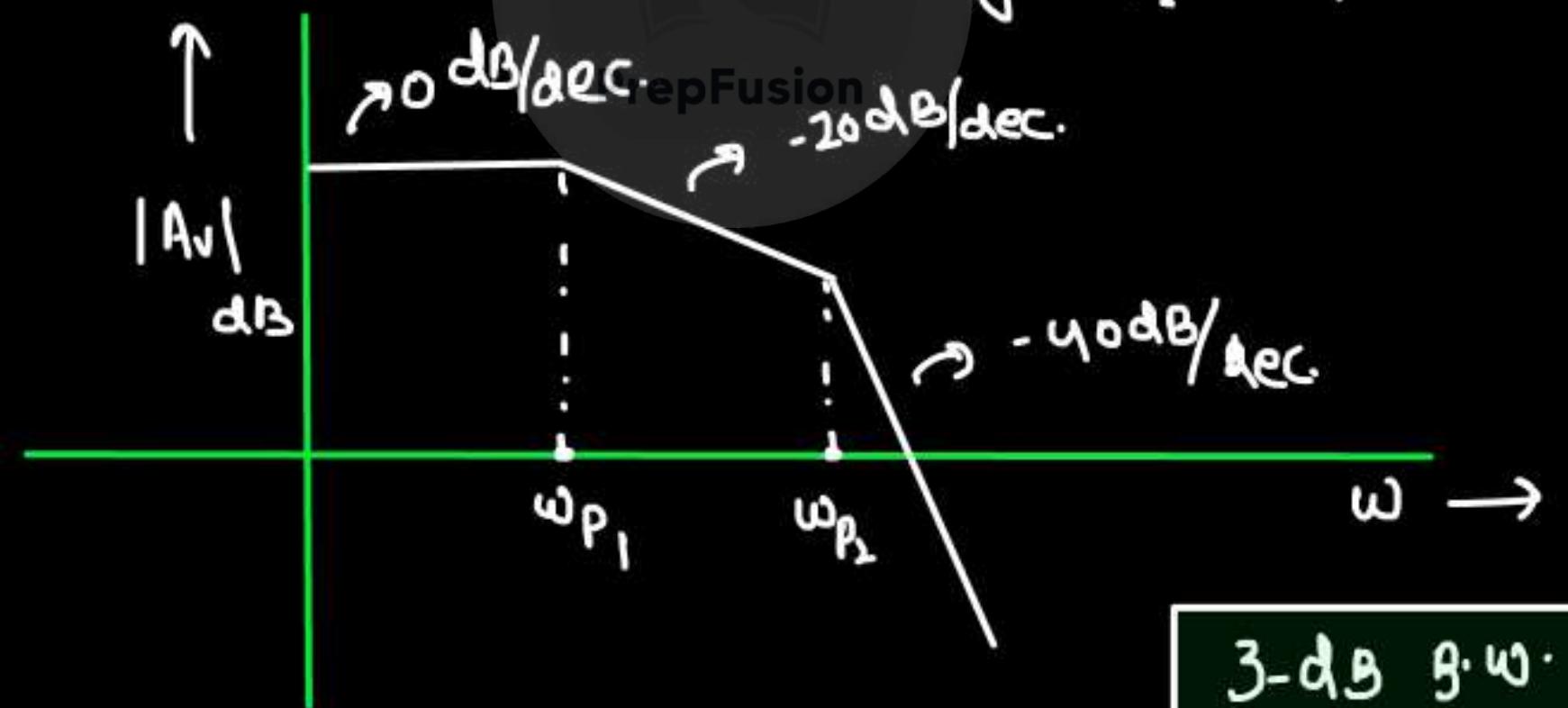considering $\omega_{p_2} > \omega_{p_1}$



③

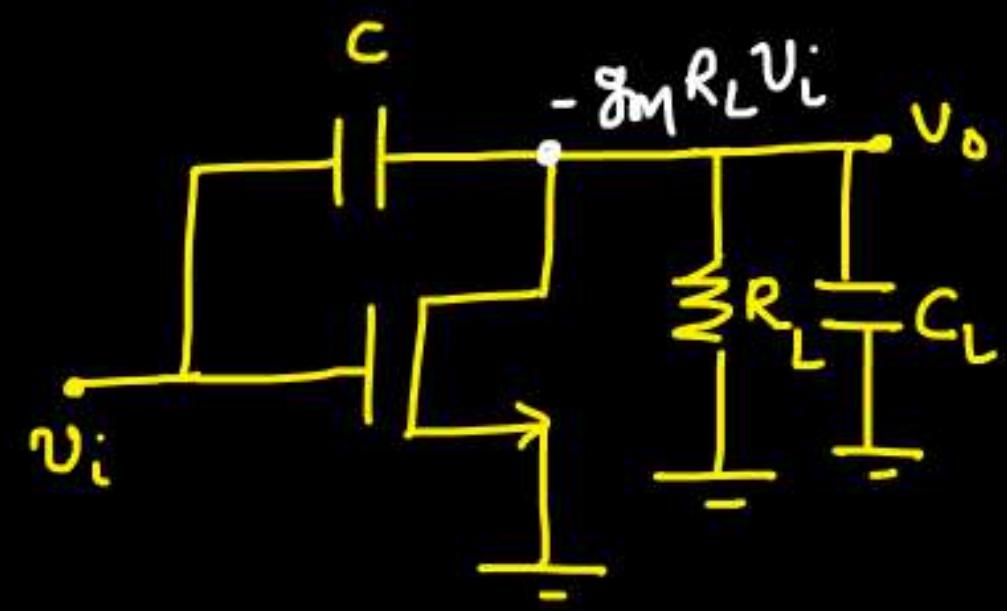

Q. Draw Bode plot. Considering


(a) $R_L C_L \gg \frac{C}{g_m}$

(b) $\text{No Load} =$

→ Compare your results.

⇒ 1st order

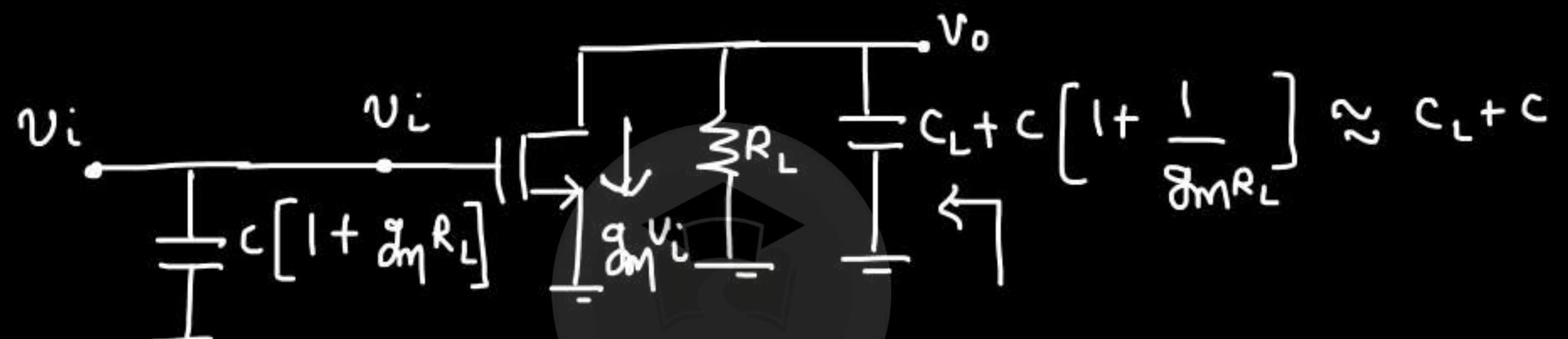(a) Since, C is very low
 \Rightarrow I can apply millers Theorem



$$A_V = G_m R_{out}$$

$$G_m = -g_m$$


$$R_{out} = R_L \left(1 + \frac{1}{(C_L + C) s} \right)$$

$$A_U = -g_m \left[R_L \left(1 + \frac{1}{(C_L + C) s} \right) \right]$$


$$A_V = \frac{-g_m R_L}{R_L [C_L + C] s + L}$$

$$\omega_p = \frac{1}{R_L [C_L + C]}$$

$$\omega_z = \infty$$

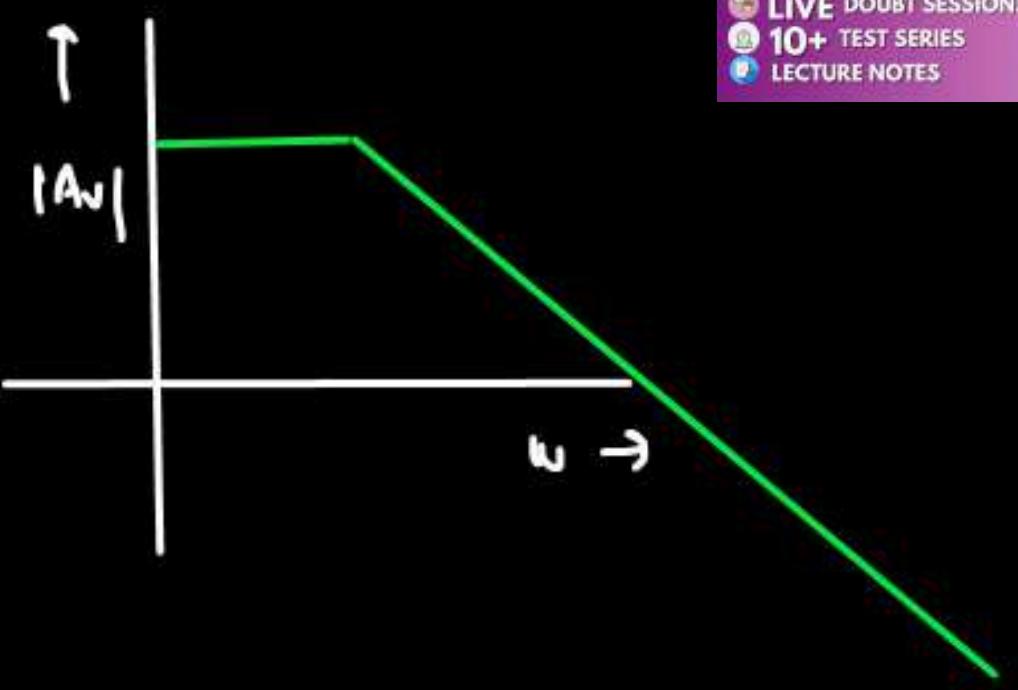

(b)

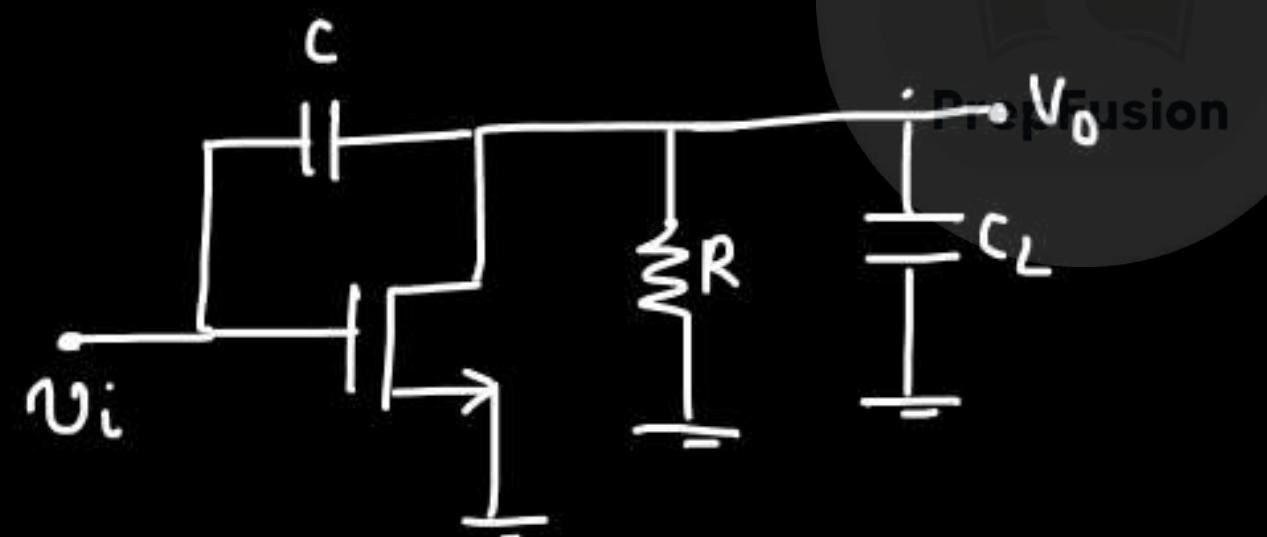

$$G_m = ?$$

$$I_{out} = -[g_m v_i - v_i \omega]$$

$$\frac{I_{out}}{v_{in}} = G_m = -[g_m - \omega]$$


$$R_{out} = R_L \parallel \frac{1}{(C_L + C)s}$$

$$A_V = \left[-\frac{g_m + CS}{R_L(C_L + C)S + L} \right]$$

$$A_V = \frac{-(g_m - C)}{R_L(C_L + C)S + L}$$


$$\omega_p = \frac{1}{R_L(C_L + C)}$$

$$\omega_z = \frac{g_m}{C}$$

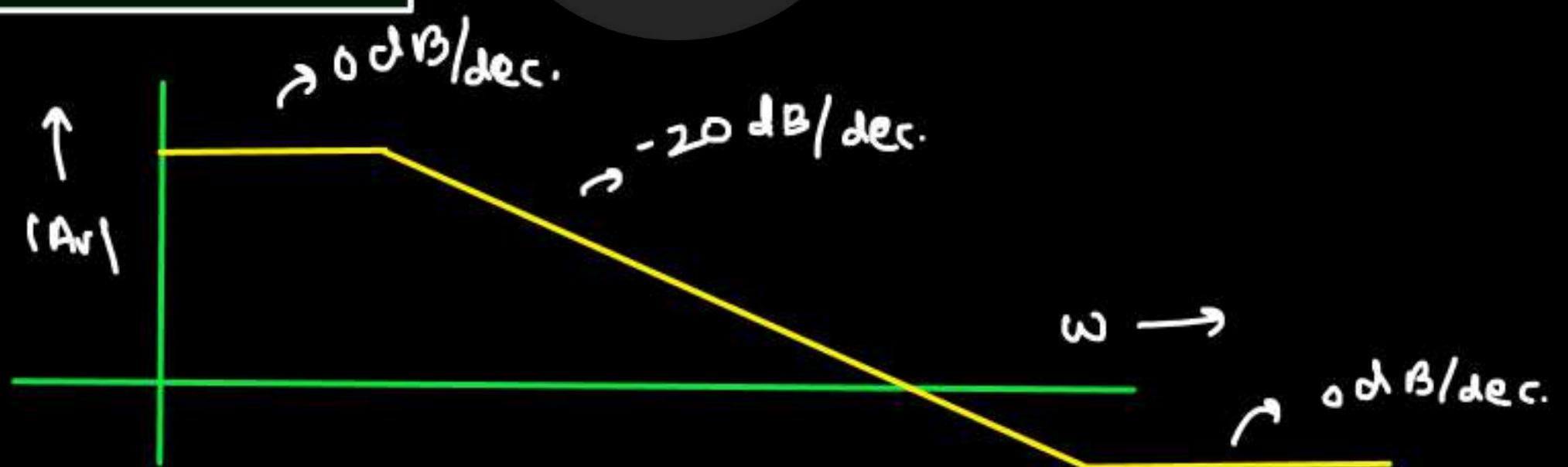



Frequency Response for Common Gate Amplifiers:-

(High frequency)

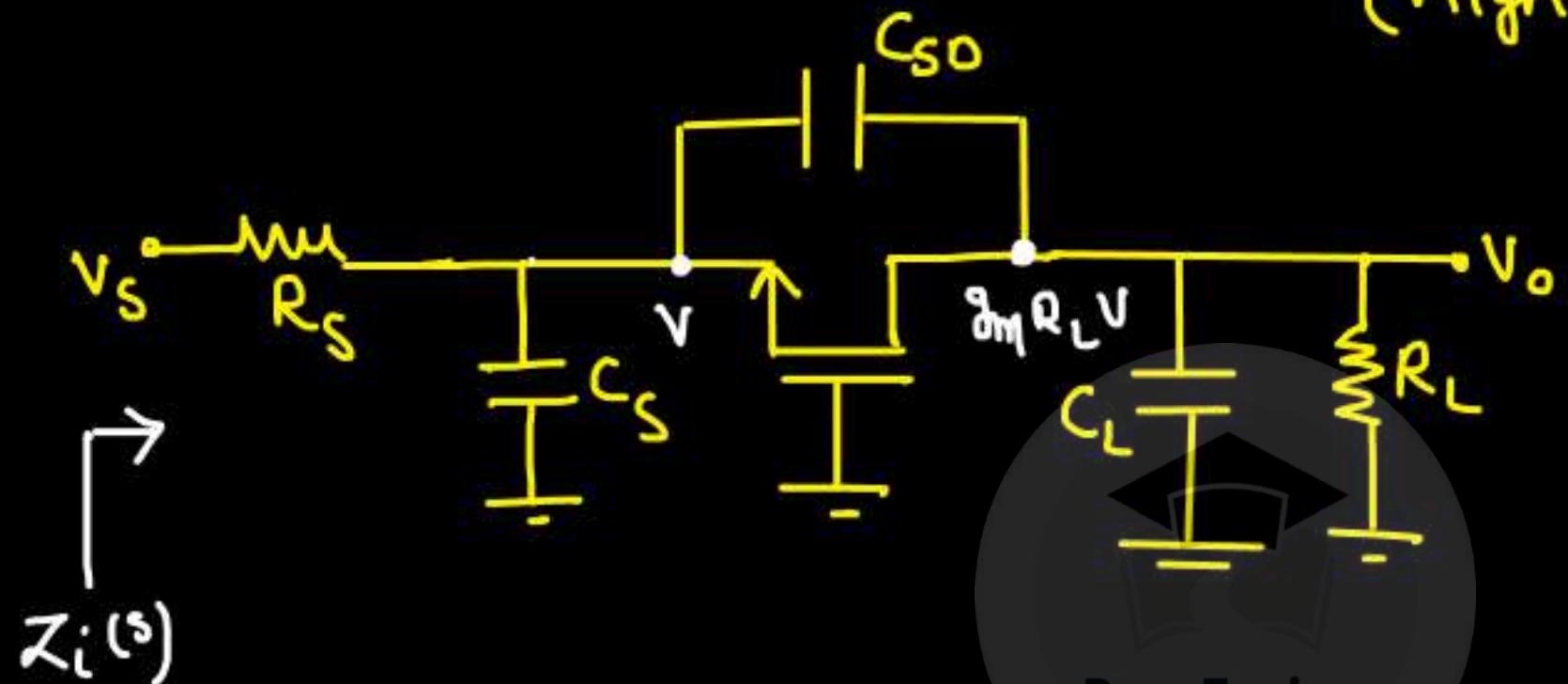

Order = 2nd

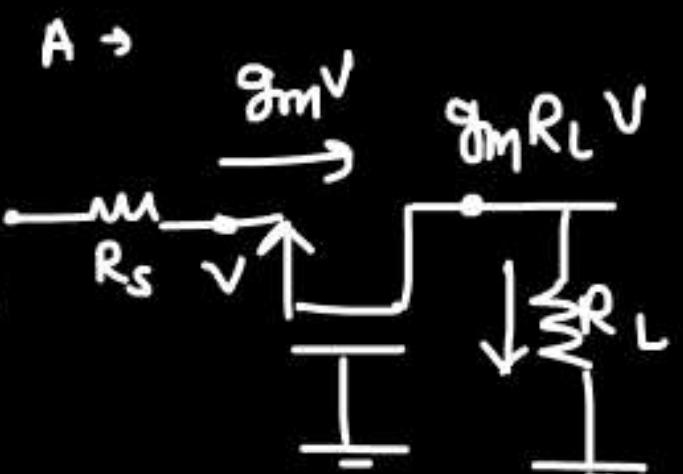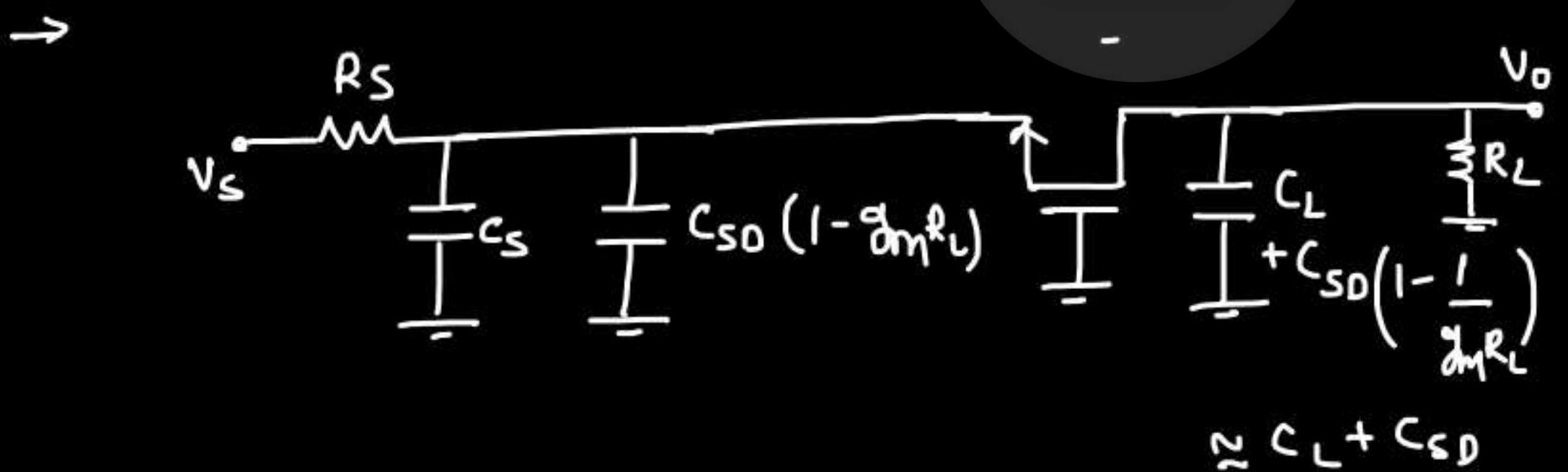
$C_{SD}, C_s, C_L \rightarrow$ Parasitics



$$A = g_m R_L$$

$$\omega_{Z_1} = \infty, \omega_{Z_2} = \infty$$

Poles:-
=

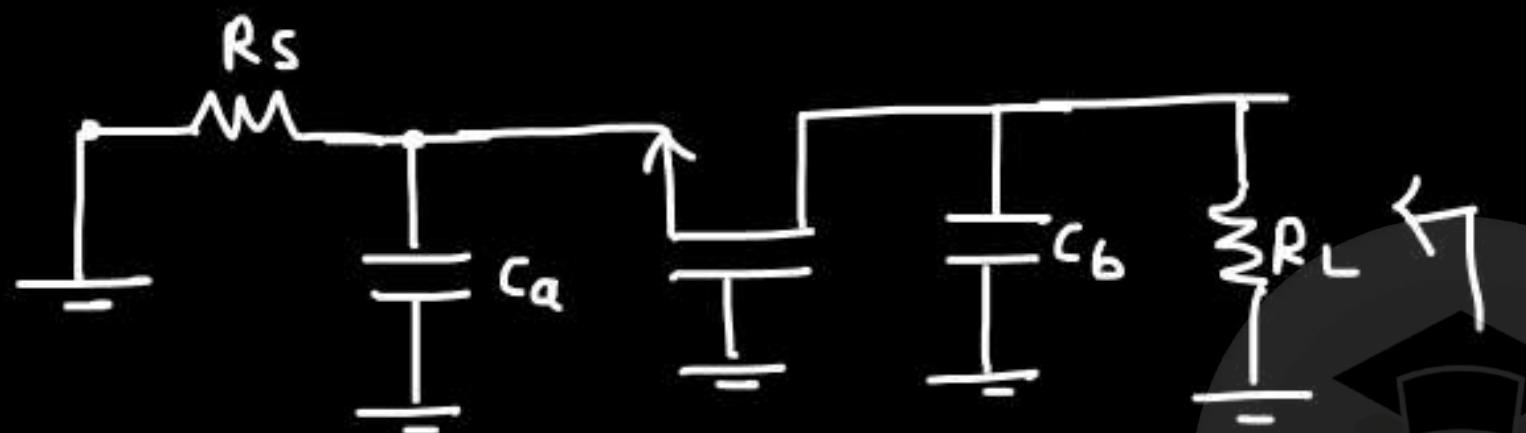

Equivalent res' across

$C_b \rightarrow R_L$

$$\omega_{P_2} \text{ or } \omega_{P_1} = \frac{1}{C_b R_L}$$

$$C_q = C_s + C_{SD} \left[1 - g_m R_L \right]$$


$$C_b = C_s + C_{SD} \left[1 - \frac{1}{g_m R_L} \right] \approx C_s + C_{SD}$$

Equivalent res' across $C_q \rightarrow R_s \parallel \frac{1}{g_m}$

$$\omega_{P_1} \text{ or } \omega_{P_2} = \frac{1}{C_q [R_s \parallel \frac{1}{g_m}]}$$

DC gain:-
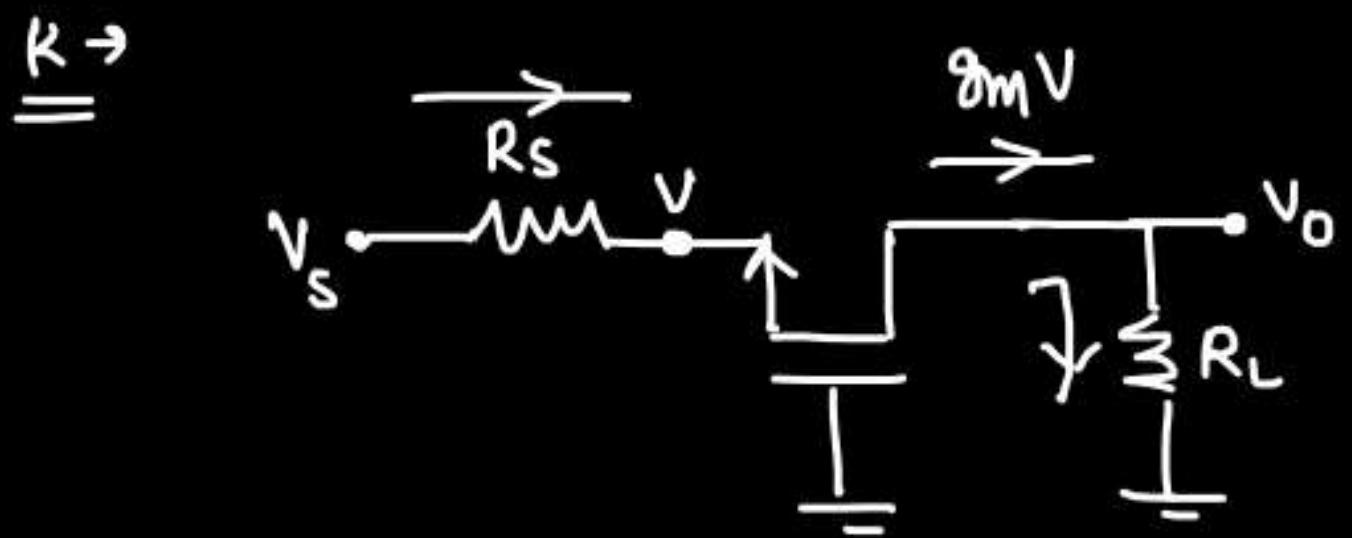
$$K = ? = \frac{V_o(\omega=0)}{V_s(\omega=0)}$$




$$V_s \xrightarrow{R_s} \frac{V_s}{R_s + \frac{1}{g_m}} \xrightarrow{\frac{1}{g_m} R_L} V_o$$

PreFusion

$$V_o = \frac{V_s}{R_s + \frac{1}{g_m}} \times R_L$$

$$\frac{V_o}{V_s} = \frac{g_m R_L}{1 + g_m R_s} = k$$

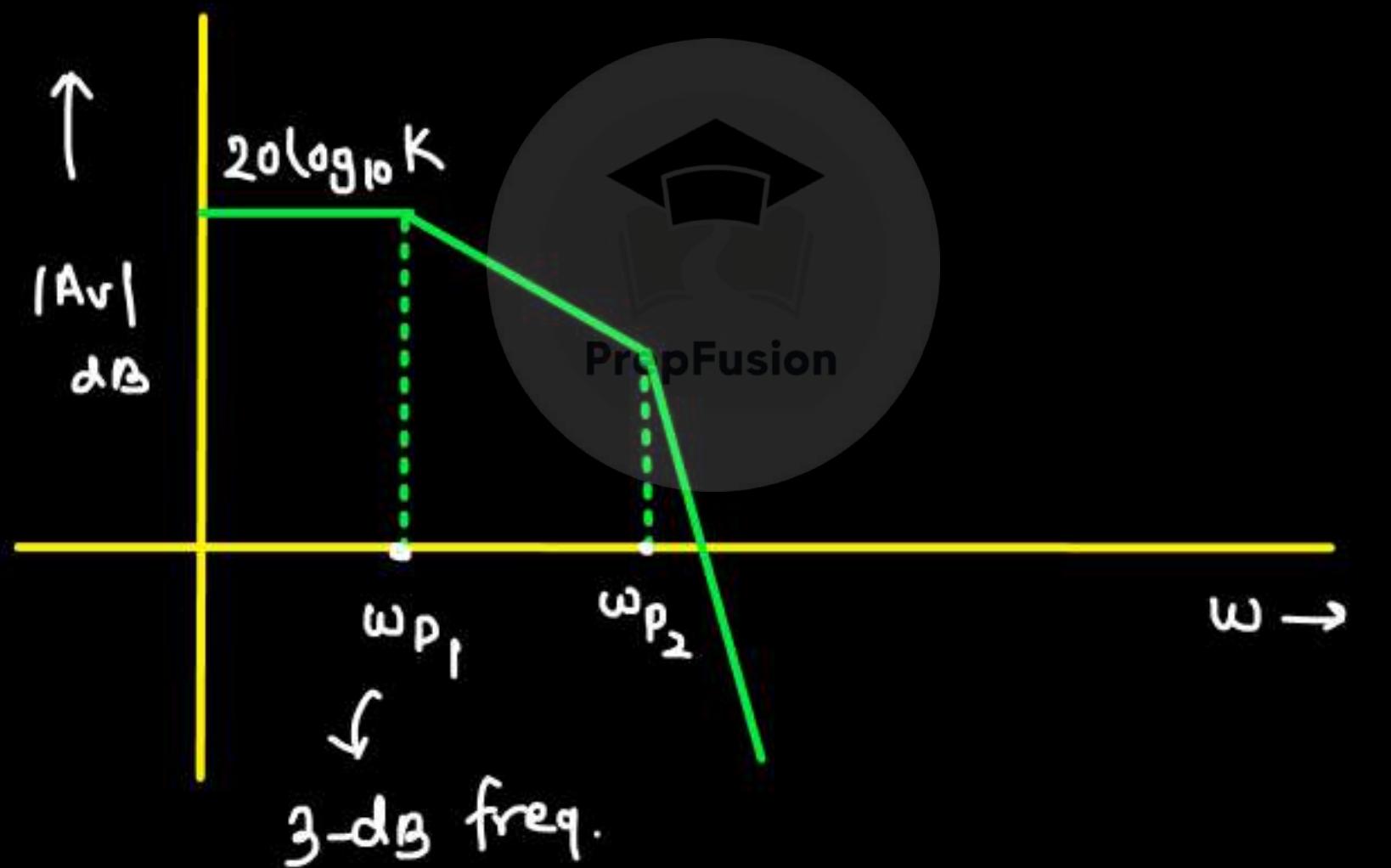
$$T(s) = \frac{K}{\left(\frac{s}{\omega_{P_1}} + 1\right) \left(\frac{s}{\omega_{P_2}} + 1\right)}$$



input resistance:-

$$Z_i(s) = R_s + \frac{1}{C_{as}} \parallel \frac{1}{g_m}$$

output impedance:-

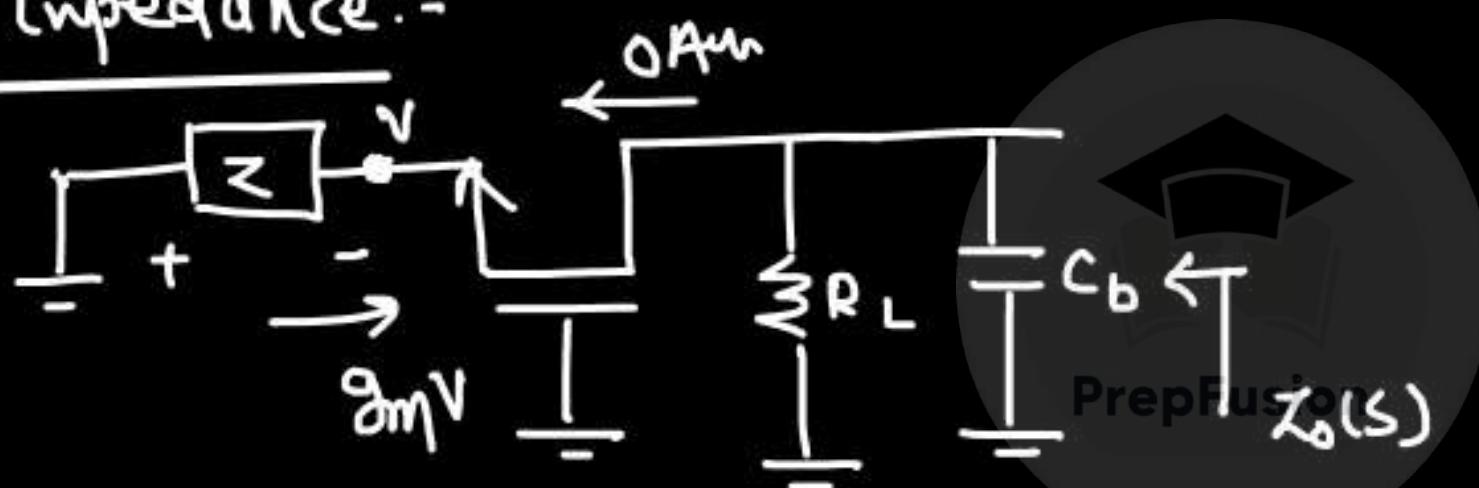

$$-g_m ZV = V$$


$$V[1 + g_m Z] = 0$$

$$V=0$$

$$Z_o(s) = \frac{1}{C_b s} \parallel R_L$$

Assignment - 10

Q.

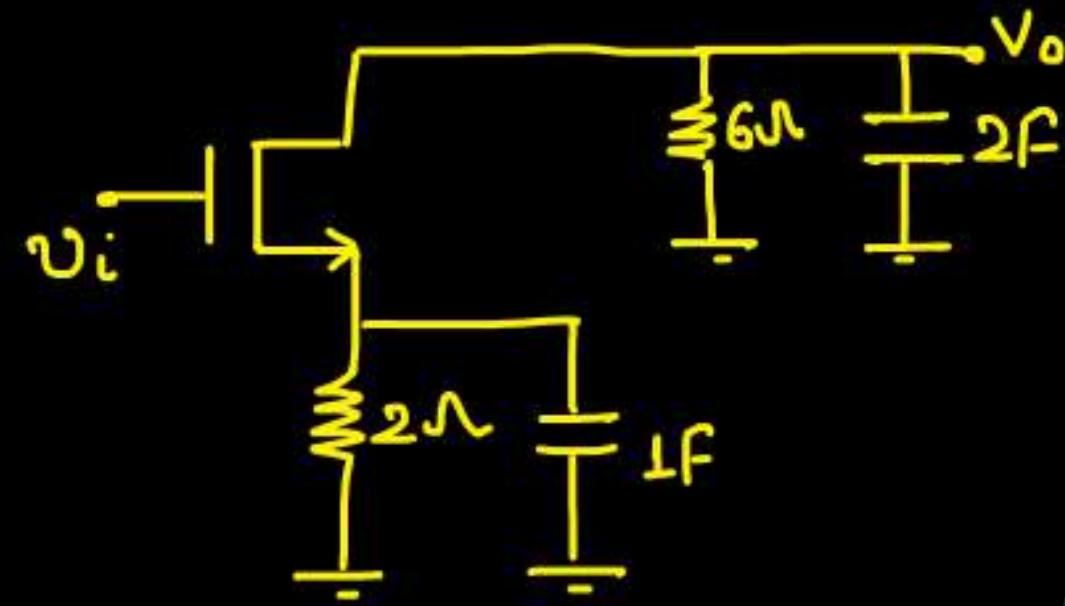

Given, $g_m = 0.5 \text{ S}$

N.B. → These are not the typical values of g_m , resistance and cap.


- ① Find 3-dB B.W. and freq. response.
- ② Tell the location of poles and zeros.
- ③ If Small signal i/p

$$V_i = 20mV \sin\left(\frac{3}{4}t\right)$$

Find V_o ?


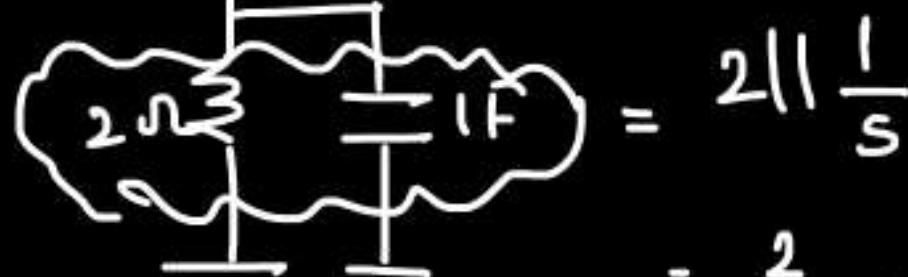
$$Z_L(s) = 6 \parallel \frac{1}{2s} = \frac{6}{(2s+1)}$$



$$= 2 \parallel \frac{1}{s}$$

$$= \frac{2}{2s+1} = Z(s)$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = -1 \cdot s \left(\frac{2s+1}{(2s+1)(s+1)} \right)}$$




$$\frac{V_o(s)}{V_i(s)} = \frac{-g_m Z_L(s)}{1 + g_m Z(s)}$$

$$= -0.5 \left(\frac{6}{2s+1} \right)$$

$$= \frac{1}{1 + 0.5 \left(\frac{2}{2s+1} \right)}$$
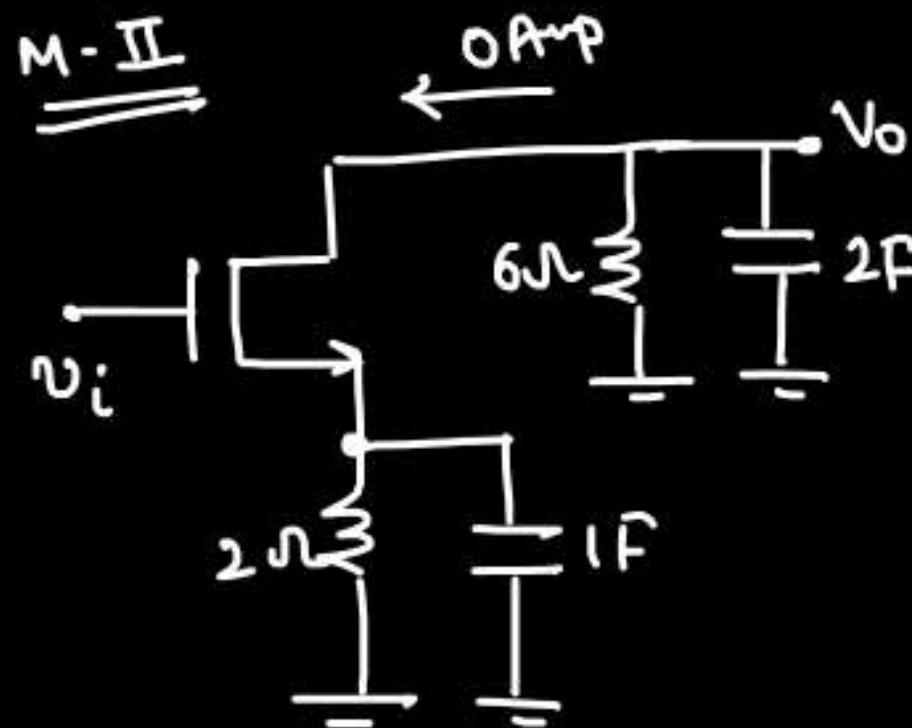
$$\frac{V_o(s)}{V_i(s)} = \frac{-\frac{3}{(2s+1)}}{1 + \frac{1}{2s+1}} = \frac{-3(2s+1)}{(2s+1)(2s+2)}$$



order = 2nd

Poles:-

$$\omega_{P_2} = \frac{1}{1F \left(2\Omega || \frac{1}{g_m} \right)} = \frac{1}{1F \left(2\Omega || 2e \right)} = -1 \text{ rad/sec.}$$

$$\omega_{P_1} = \frac{1}{g_F(s)} = -\frac{1}{10} \text{ rad/sec.}$$

DC gain:-

$$K = -\frac{g_m R_L}{1 + g_m R_S} = -\frac{3}{1 + 1} = -1.5$$

Zeros:- PrepFusion


$$\omega_{Z_1} = \infty \quad (2F)$$

$$\omega_{Z_2} = ? \Rightarrow 2\Omega || \frac{1}{j\omega} = \infty \Rightarrow \frac{2}{2s+1} = \frac{1}{0}$$

$$T(s) = \frac{-1.5(2s+1)}{(12s+1)(s+1)}$$

$$\omega_{Z_2} = -1/2$$


Freq. response:-

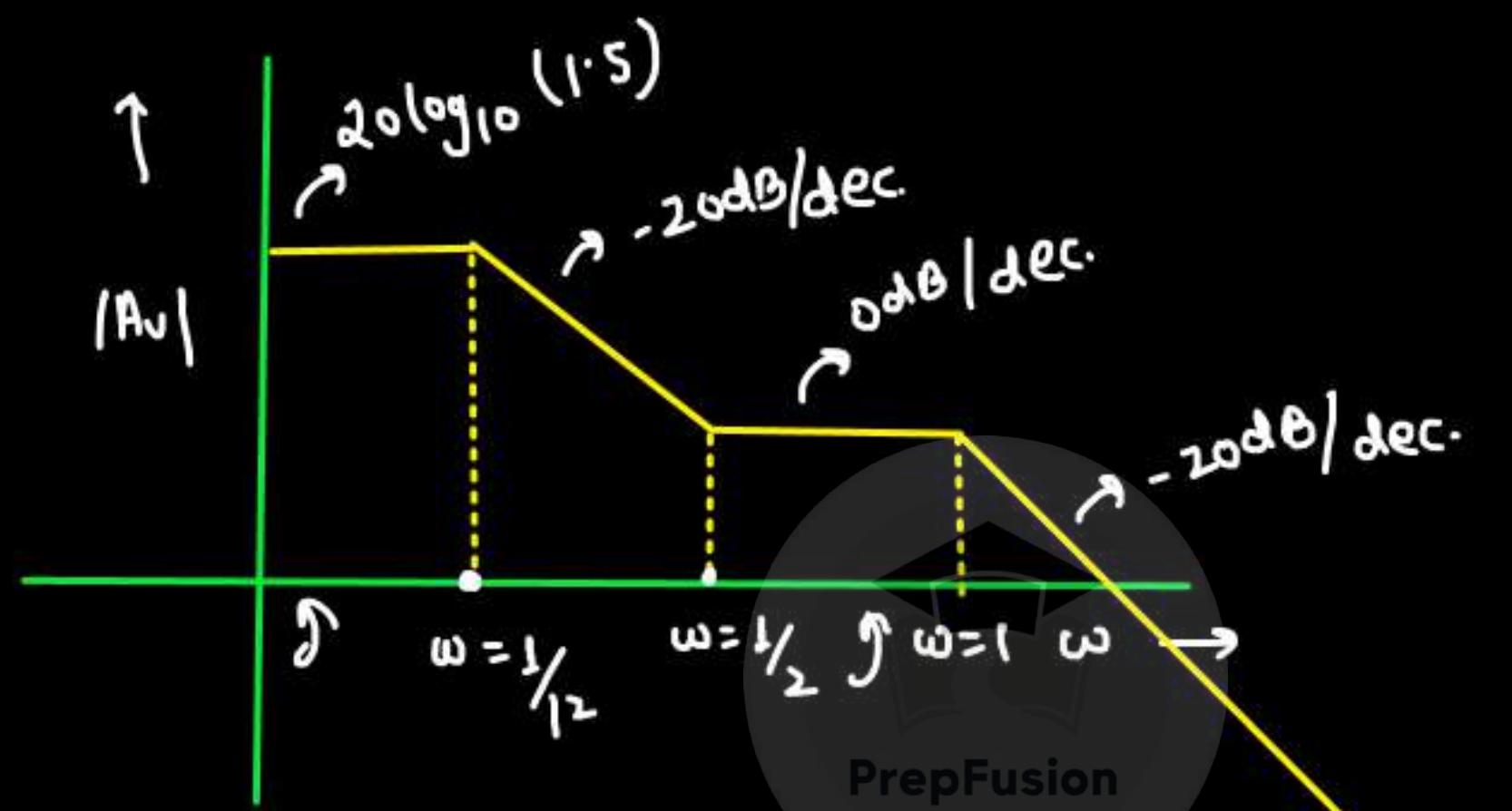

$$3\text{-dB BW} / \text{cut-off freq} = \frac{1}{\sqrt{2}} \text{ rad/sec.}$$

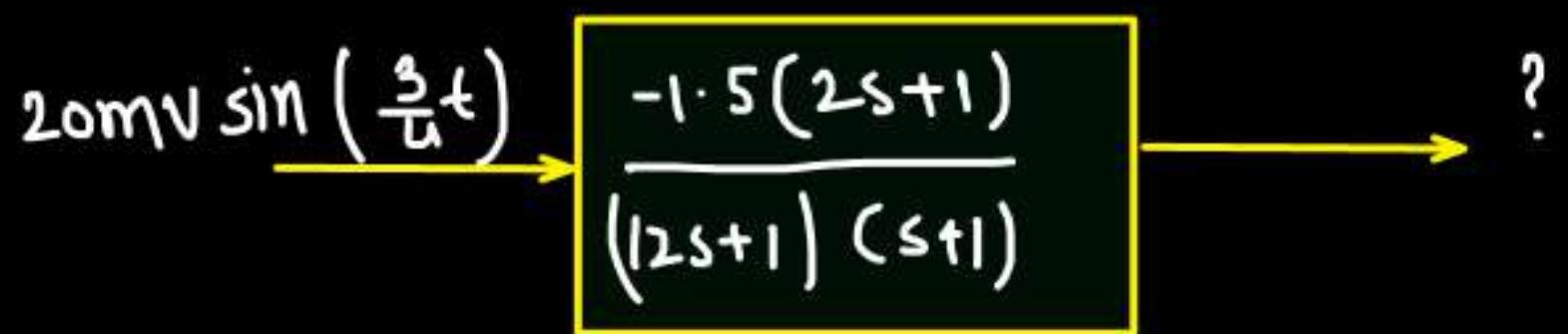
(iii) $V_i = 20mV \sin\left(\frac{3}{4}t\right); \omega_i = \frac{3}{4} \text{ rad/sec.}$

$$\frac{V_o(s)}{V_i(s)} = \frac{-1.5(2s+1)}{(12s+1)(s+1)}$$



$$\rightarrow T(j\frac{3}{4}) = \frac{-1.5\left(2j \times \frac{3}{4} + 1\right)}{\left(12 \times j \frac{3}{4} + 1\right)\left(j \frac{3}{4} + 1\right)} = \frac{-1.5(j6 + 4) \times 4}{(j36 + 4)(j3 + 4)}$$

$|T(j\frac{3}{4})| = -0.24$

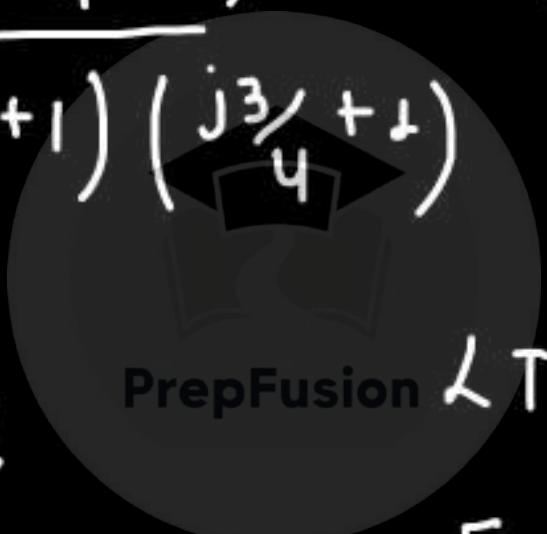


$\angle T(j\frac{3}{4}) = -244.2^\circ$

$$\left[-(80 + \tan^{-1}\left(\frac{6}{4}\right)) - \tan^{-1}\left(\frac{36}{4}\right) - \tan^{-1}\left(\frac{3}{4}\right) \right]$$

$\Rightarrow V_o(t) = 4.8mV \sin\left(\frac{3}{4}t - 244.2^\circ\right)$


Q.

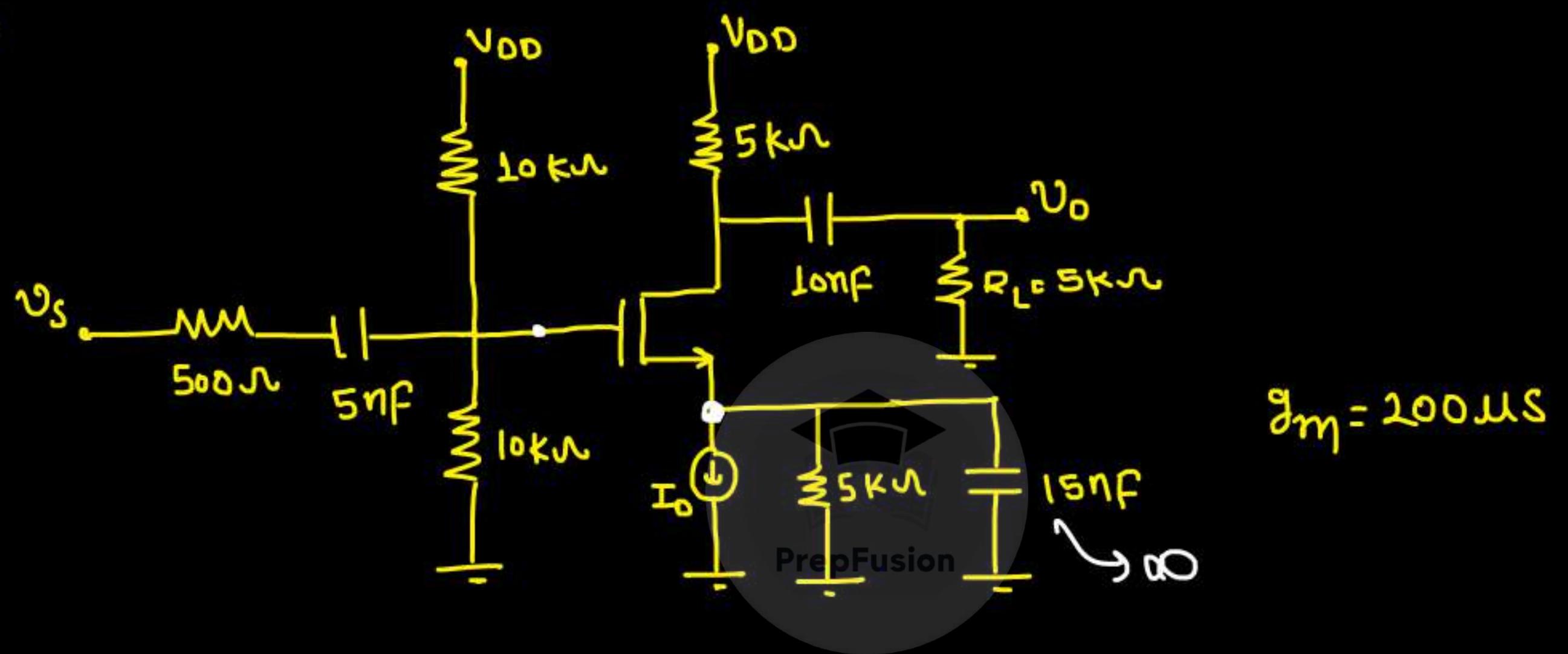

- Find the location of poles and zeros.
- Find the 3-dB cut-off frequency.


→ $\omega_{z1} = 0, \omega_{z2} = 0$ $\omega_{z3} = \frac{-1}{15n\mu F \times 5k} = -13.33 \text{ K rad/sec.}$

Req. across 5nF :-

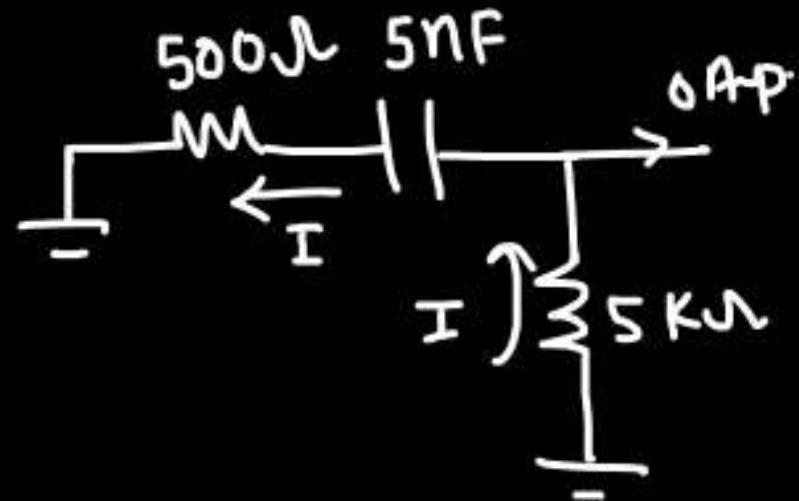

$$\omega_{P_3} = \frac{L}{5n \times 5.5K} = -36.36 \text{ Krad/sec.}$$

15nF :-

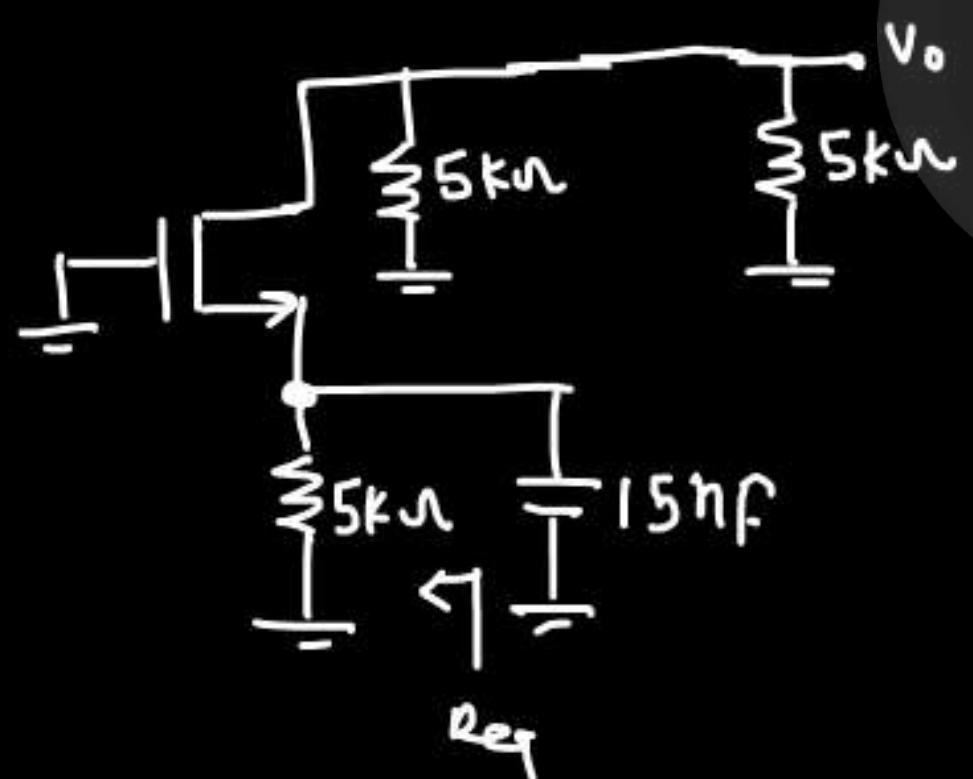


$$Req = 5K \parallel \frac{1}{8M} = 5K \parallel 5K = 2.5K$$

$$\omega_P = \frac{1}{(15n \times 2.5K)}$$

$$[8M = 200\mu S]$$

$$\omega_{P_2} = -26.67 \text{ Krad/sec.}$$

ω_{nf} :-

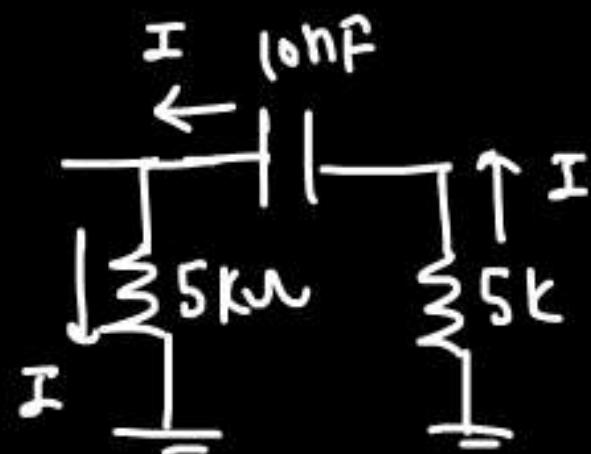


$$\omega_{pi} = \frac{1}{|A_n| \times 10k} = -10k \text{ rad/sec}$$


$$T(s) = \frac{A_n s^2 \left(\frac{s}{13.33k} + 1 \right)}{\left(\frac{s}{10k} + 1 \right) \left(\frac{s}{26.67k} + 1 \right) \left(\frac{s}{36.36k} + 1 \right)}$$

PrepFusion

3-dB cut-off freq. = 36.36 k rad/sec.

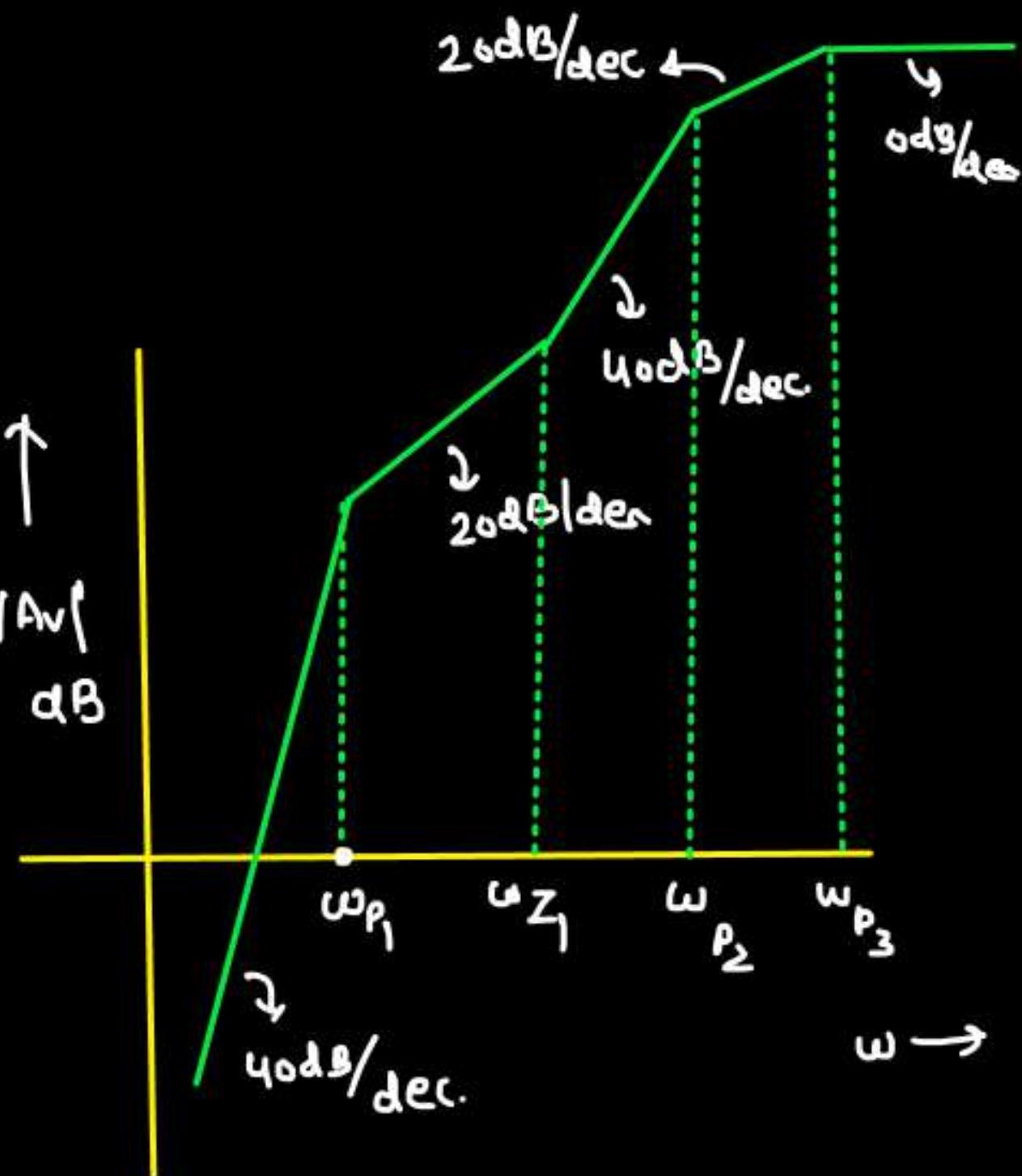


Q.

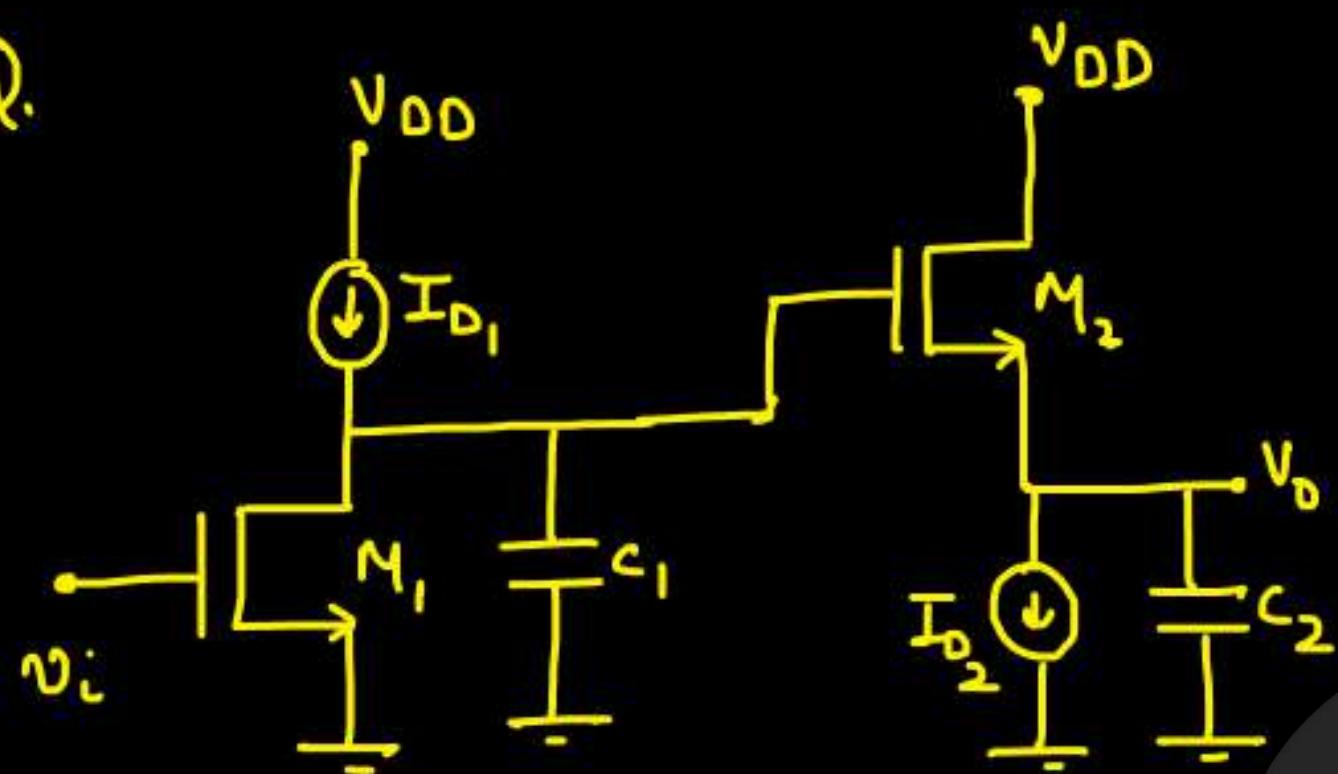

Write down the frequency response intuitively.


→ order = 2^{nq}

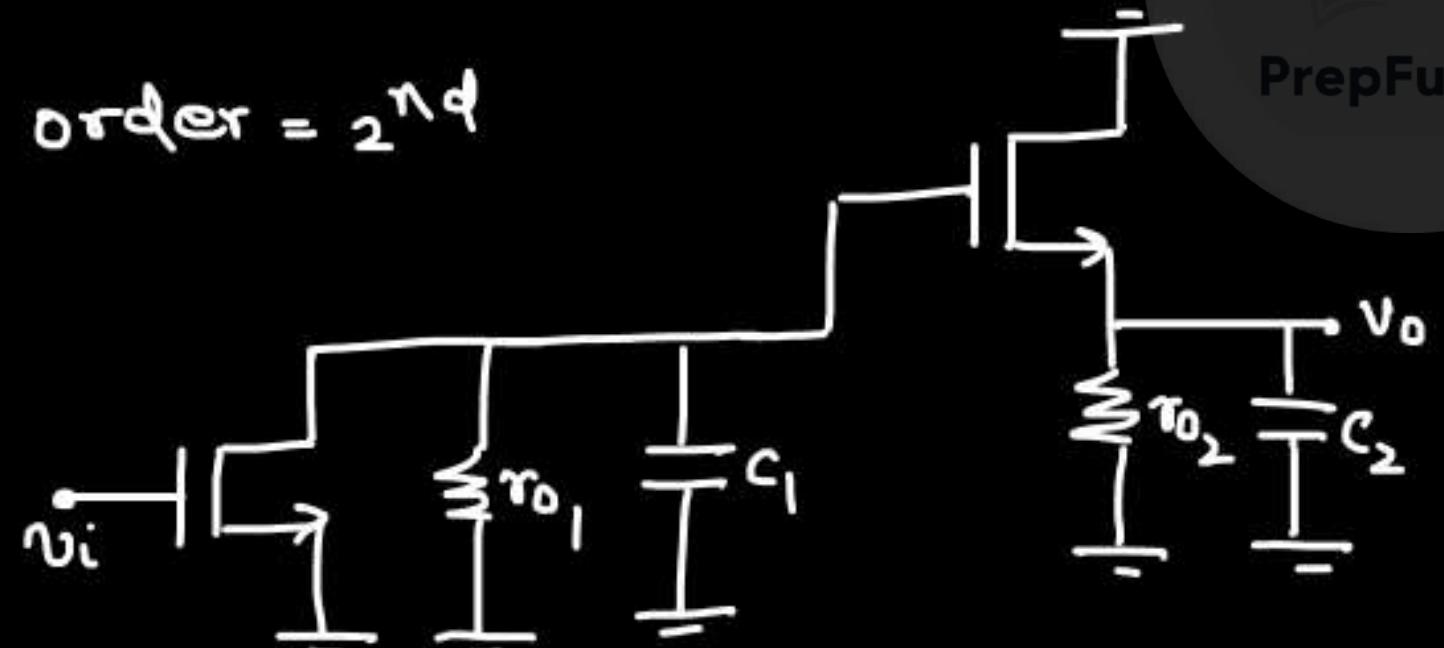

$$\omega_{P_1} \text{ or } \omega_{P_2} = \frac{-1}{r_{o_1} C_1}$$


$$\omega_{P_2} \text{ or } \omega_{P_1} = \frac{-1}{C_2 \left[\frac{1}{g_{m2}} || r_{o_2} \right]}$$
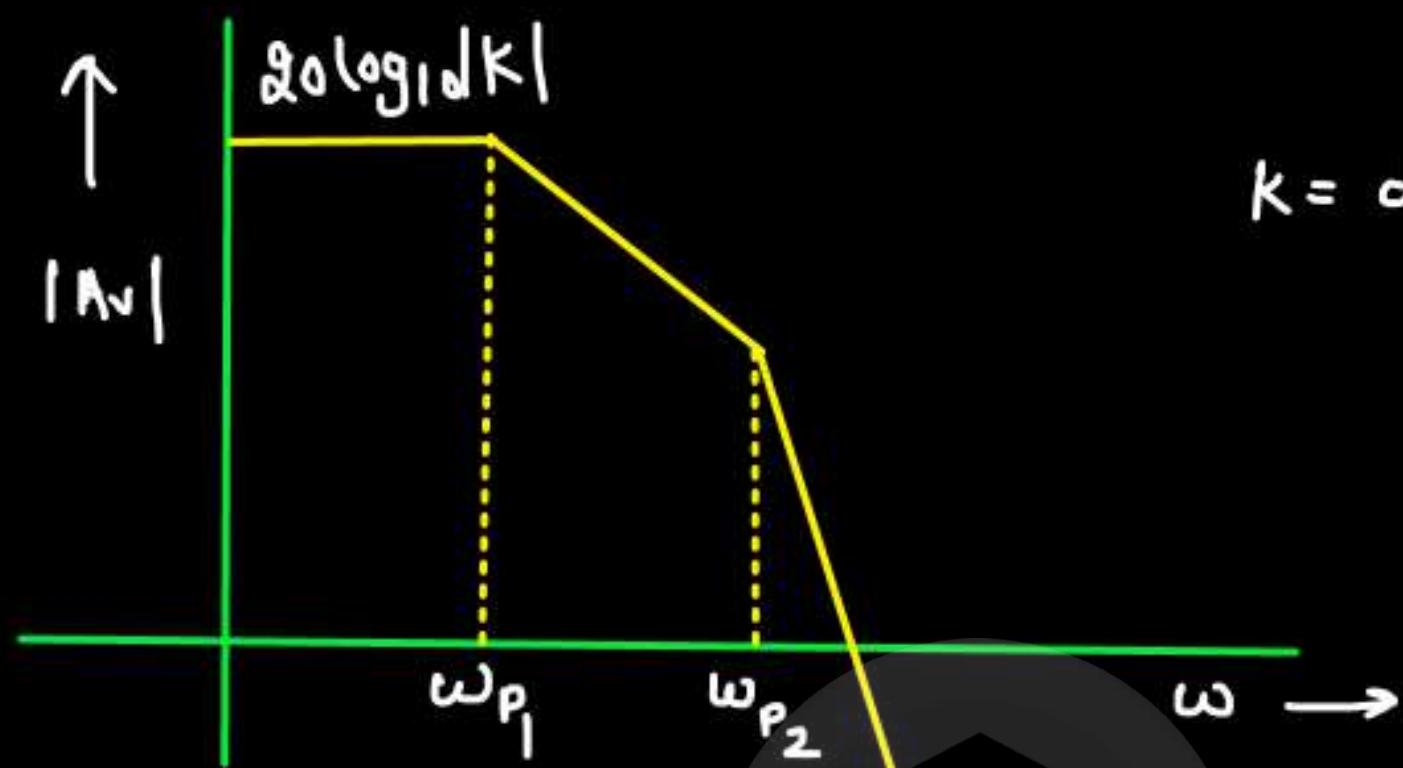
$$\omega_{Z_1} = \infty, \omega_{Z_2} = \infty$$



PrepFusion

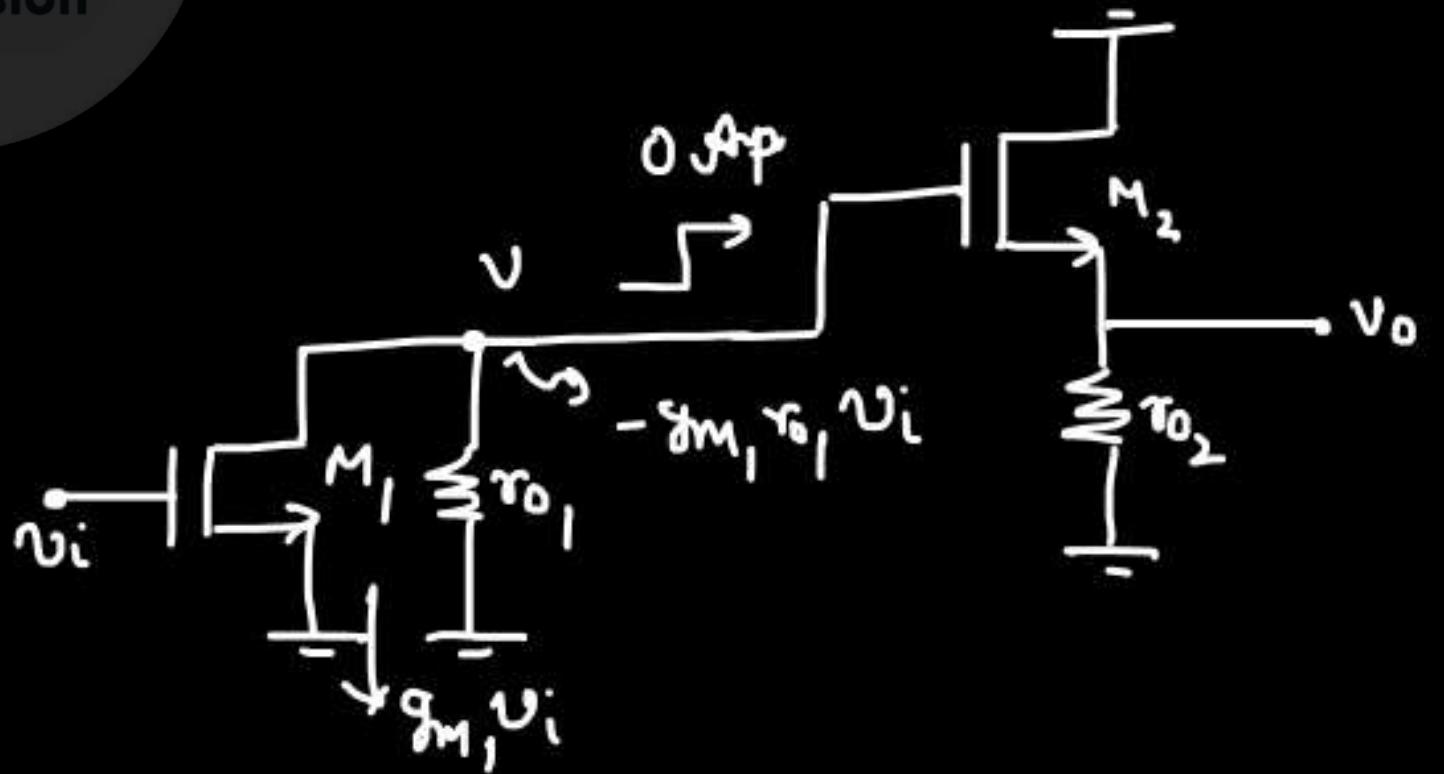
$$\frac{V_o}{V_i} = \frac{-g_m 2 r_{o2}}{1 + g_m r_{o2}} \times g_m r_{o1} = K$$




Q. Find (a) DC gain

- (b) 3-dB Bandwidth ($\omega_{3\text{-dB}}$)
- (c) 3-dB Unity gain Bandwidth (ω_{UgB})

[Make Necessary Approximations]

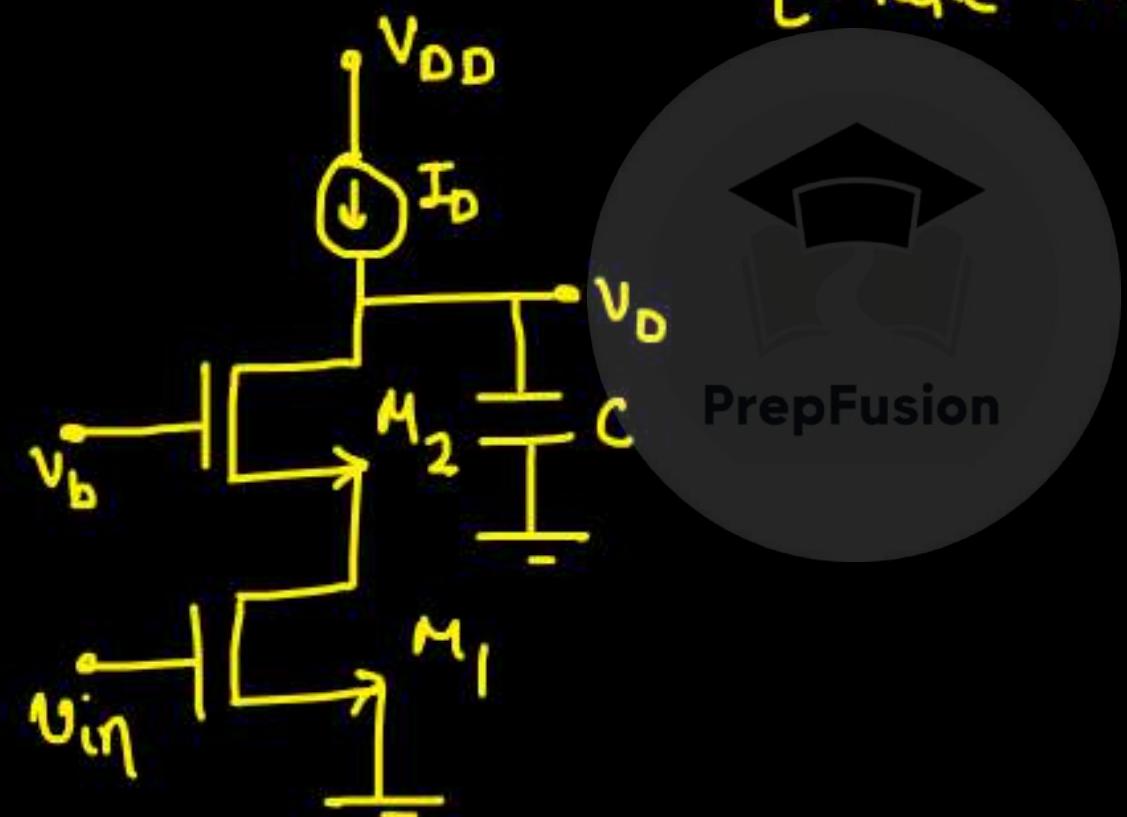

(a) DC gain (Small signal gain) :-

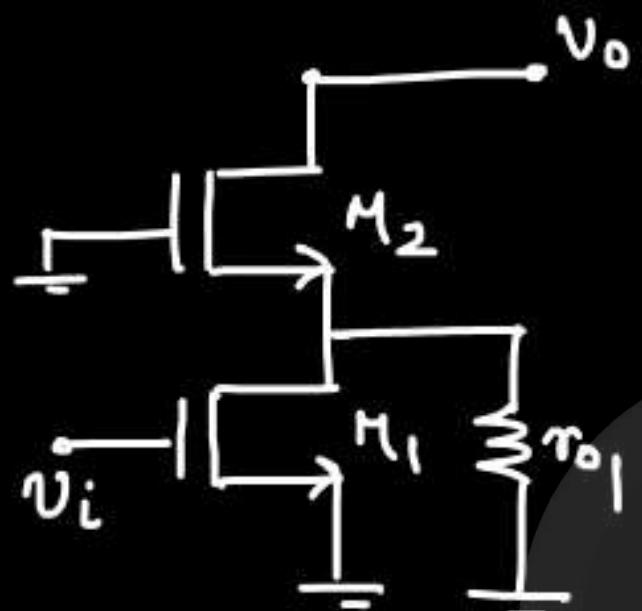

$$\Delta V = -G_m R_{out}$$

$$\Delta V \approx -g_m g_m r_{o_2} r_{o_1}$$


$$R_{out} = g_m r_{o_2} r_{o_1} + r_{o_2} + r_{o_1}$$

(ii) 1st order :-

$$\omega_z = \omega$$

$$\omega_p = \frac{1}{C[g_m r_{o_2} r_{o_1}]}$$
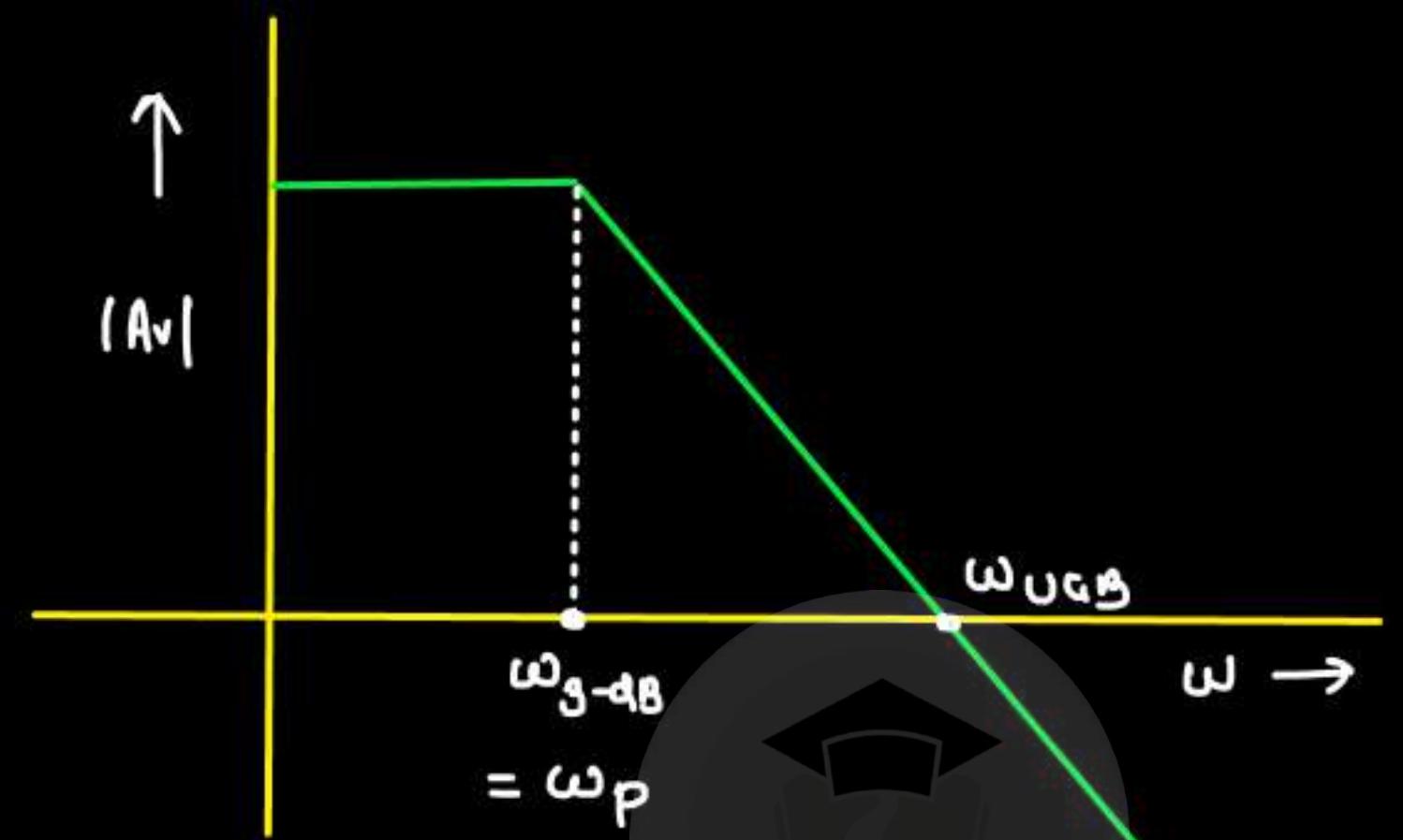
$$T(s) = \frac{-g_m g_m r_{o_1} r_{o_2}}{1 + s C g_m r_{o_2} r_{o_1}}$$



Preprusion

$$3\text{-dB B.W.} = \omega_p = \frac{-1}{C [g_m n_2 r_o + r_{o2} + r_{o1}]} \approx \frac{-1}{C g_m r_{o2} r_{o1}}$$

Unity gain B.W. → For a low Pass filter, the freq. @ which the gain is unity (0 dB).

$$@ \omega = \omega_{UAB}$$

$$|T(j\omega_{UAB})| = L$$

$$\frac{g_m_1 g_m_2 r_{o2} r_{o1}}{\sqrt{L_f \omega_{UAB}^2 C^2 g_m_2^2 r_{o2}^2 r_{o1}^2}} = L$$

$$g_m_1^2 g_m_2^2 r_{o2}^2 r_{o1}^2 = \omega_{UAB}^2 C^2 g_m_2^2 r_{o2}^2 r_{o1}^2$$

PrepFusion

$$\omega_{UAB} = \frac{g_m_1}{C}$$

For a stable config. →

Gain Bandwidth product is constant.


3-dB Bandwidth × DC gain = Unity gain BW × ω_L

$$\omega_{UGB} = A_v \times \omega_{3-dB}$$

For the given problem,

$$\omega_{UGB} = \frac{g_m_1 g_m_2 r_o_2 r_o_1}{C g_m_2 r_o_2 r_o_1} = \frac{g_m_1}{C}$$

Q.

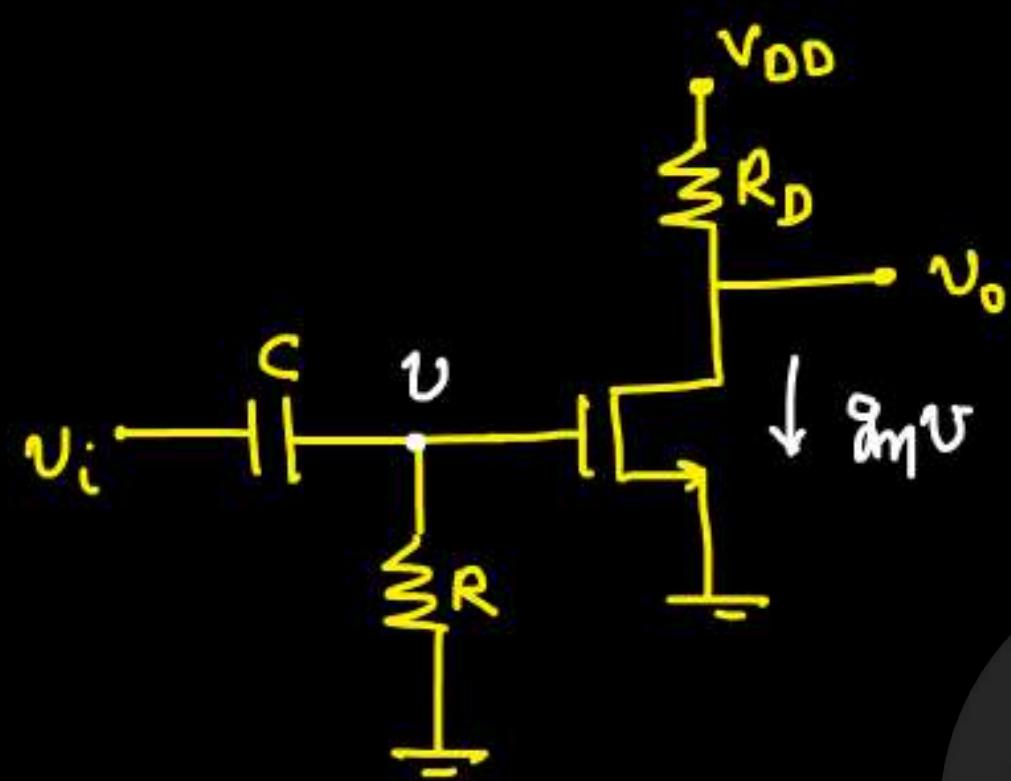

$$V_o = -g_m R_D v \rightarrow \textcircled{1}$$



$$v = \frac{R_C}{1 + R_C} v_i \rightarrow \textcircled{2}$$

$$\frac{V_o}{V_i} = -g_m R_D \left(\frac{R_C}{R_C + 1} \right)$$

- Q. (a) Find 3-dB B.W.
 (b) Find 3-dB cut-off freq.
 (c) Find the freq. @ which the gain is unity.

$$\omega_Z = 0$$

$$\omega_P = -\frac{1}{RC}$$

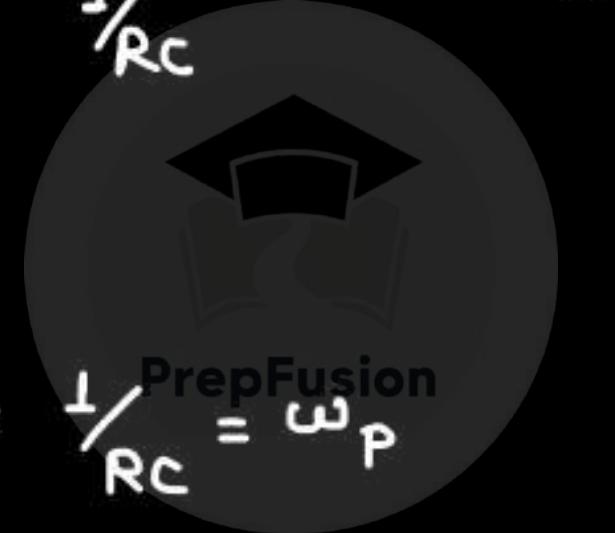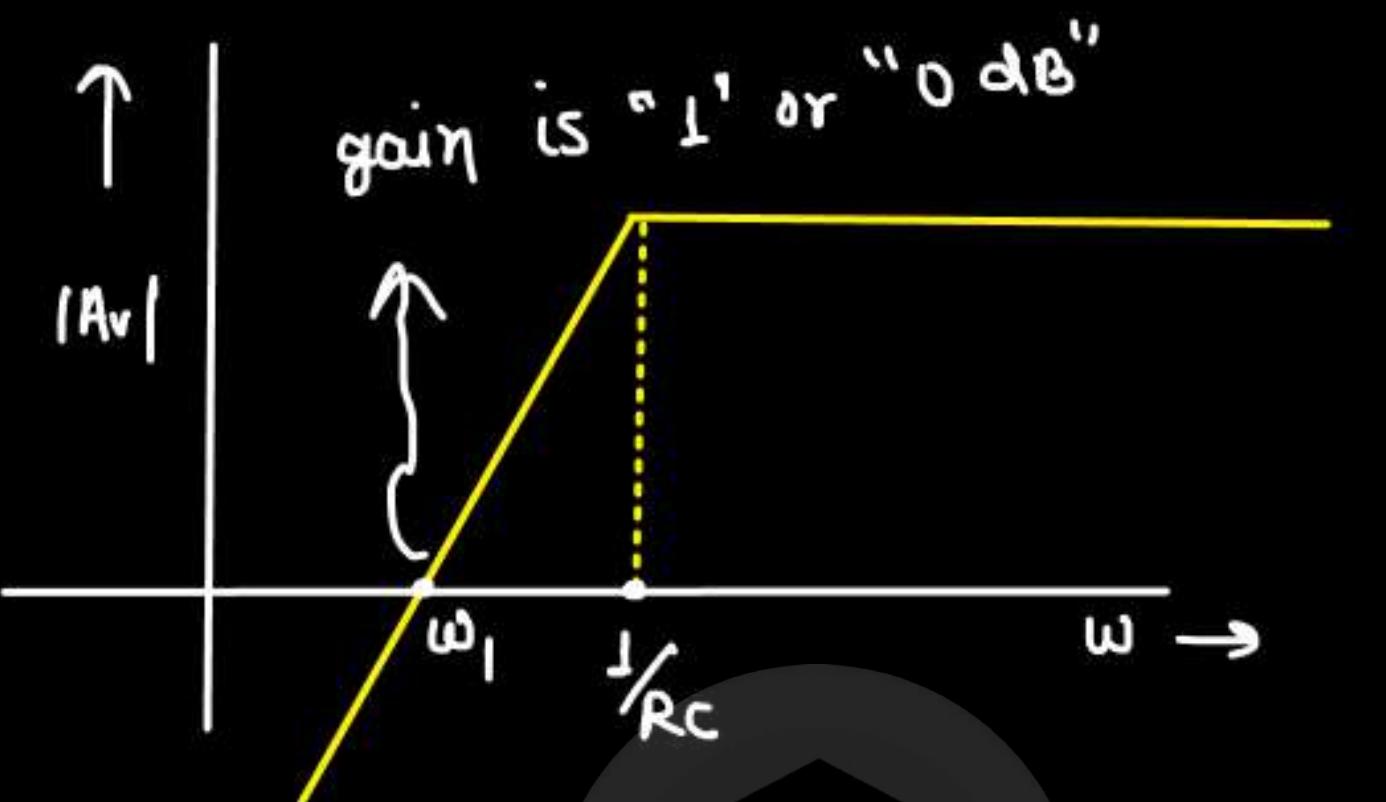

$$\textcircled{1} \quad \text{3-dB cut-off freq.} = \frac{1}{R_C} = \omega_p$$

$$\textcircled{2} \quad \text{3-dB B.W.} = \infty - \frac{1}{R_C} = \infty$$

$$\omega_1 = ?$$

$$@ \omega = \omega_1$$

$$|T(j\omega_1)| = L$$

$$\frac{g_m R_D \times R_C \omega_1}{\sqrt{1 + \omega_1^2 R^2 C^2}} = 1$$

$$\frac{g_m^2 R_D^2 R^2 C^2}{g_m R_D} \omega_1^2 = 1 + \omega_1^2 R^2 C^2$$

$$\omega_1^2 [g_m^2 R_D^2 R^2 C^2 - 1] = 1$$

$$\omega_1 = \frac{1}{R_C \sqrt{g_m^2 R_D^2 - 1}}$$


generally $g_m R_D \gg L$

$$\omega_1 \approx \frac{1}{R_C \times g_m R_D}$$

Differential Amplifier

↳ Why do we need differential Amplifier?

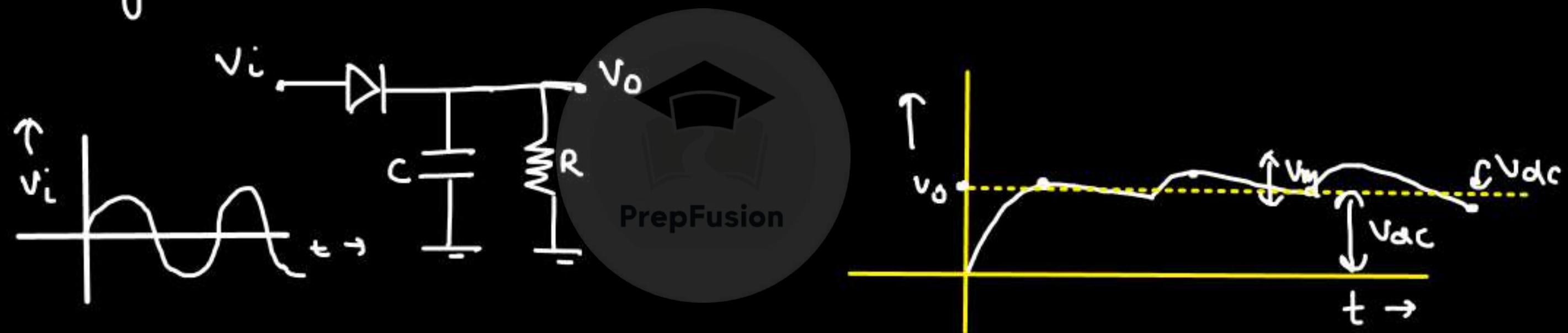
- * Generally the dc supply we use , have some small ripple.



This supply $V_o = V_{dc} + V_m$
 will be fed to the Transistors. dc o/p ripple (small signal noise)

Q. All the supplies have some ripples (V_{m_1}, V_{m_2}) .

Find small signal o/p.

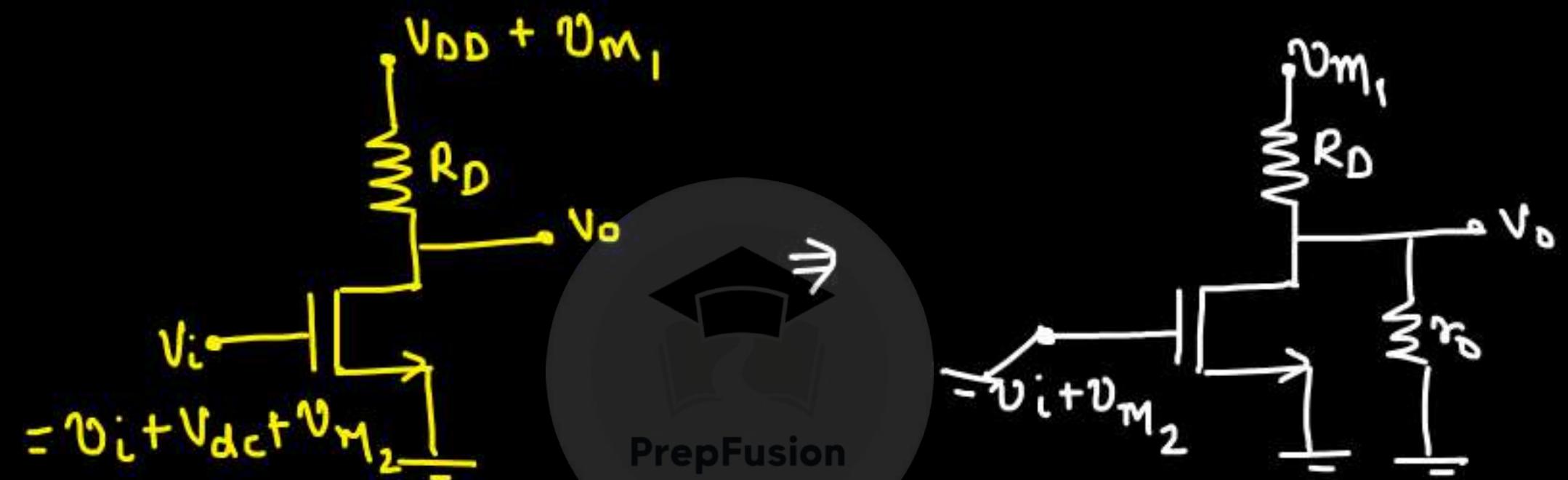

$$V_o = -g_m (V_i + V_{m_2}) (R_D \parallel r_0) + \frac{r_0}{r_0 + R_D} V_{m_1}$$

$$V_o = -g_m (R_D \parallel r_0) V_i - g_m (R_D \parallel r_0) V_{m_2} + \frac{r_0}{r_0 + R_D} V_{m_1}$$

$$v_o = \underbrace{g_m (R_D || r_o) v_i}_{\text{desired}} - \underbrace{g_m (R_D || r_o) v_{m_2} + \frac{r_o}{r_o + R_D} v_{m_1}}_{\text{Noise}}$$


To eradicate the noise part, we use differential amp.



Basic Idea:-

- ↳ At input, you have "signal + Noise"
 - ↳ At output, you have "signal + Noise"
- you want amplified o/p, but no noise \Rightarrow

$$[v_o = \underline{A} v_i]$$



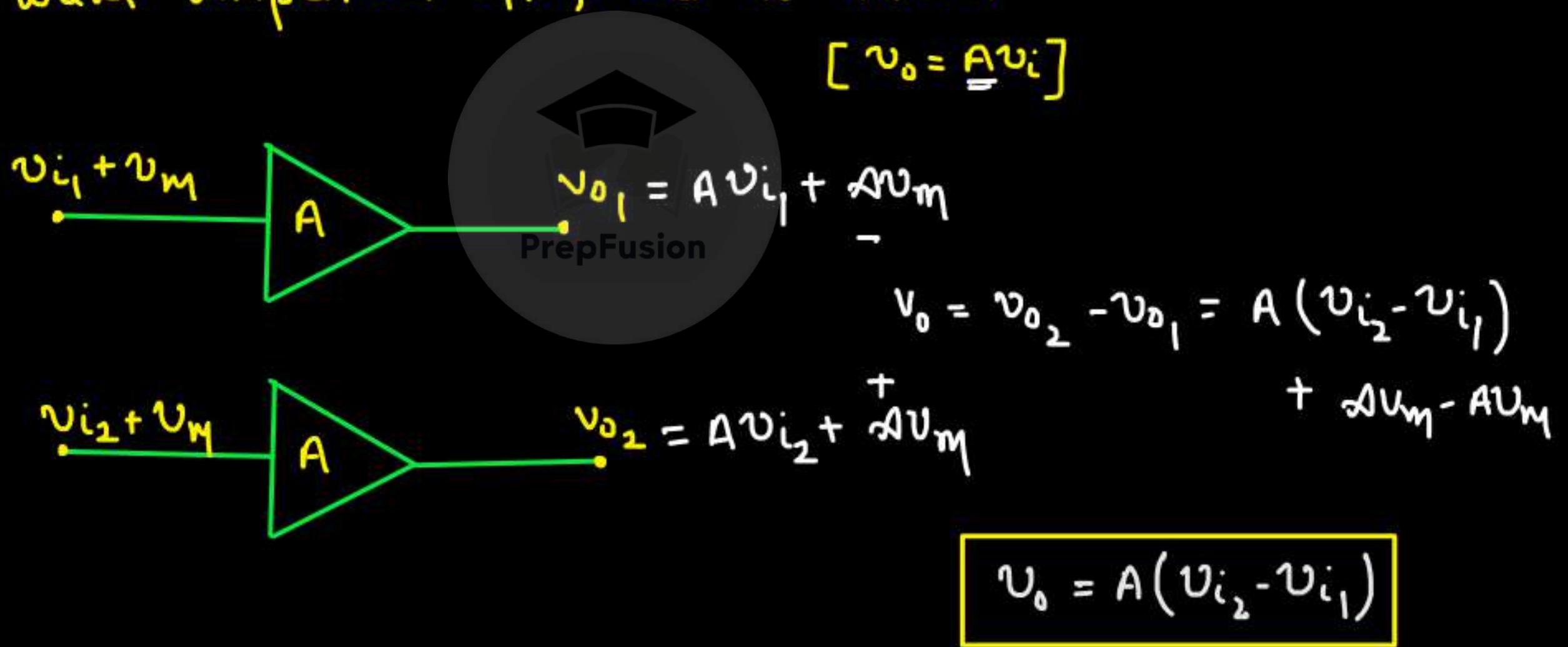


if $v_{i_2} = v_{i_1}$ and $v_{i_1} = -v_{i_2}$

$$v_o = A v_i \rightarrow \text{desired o/p}$$

Here v_{i_2} and v_{i_1} are differential signals.

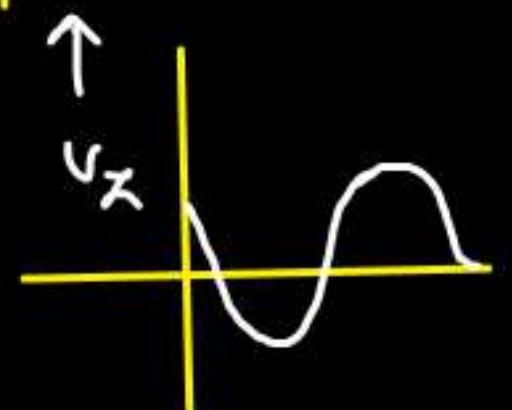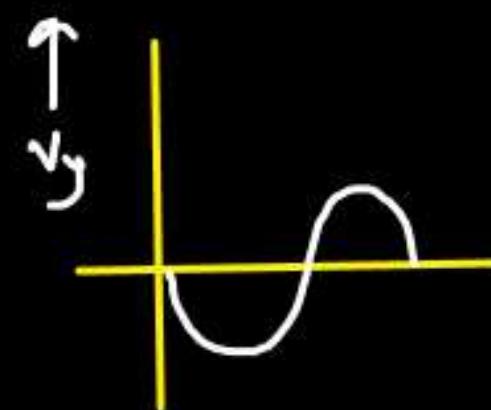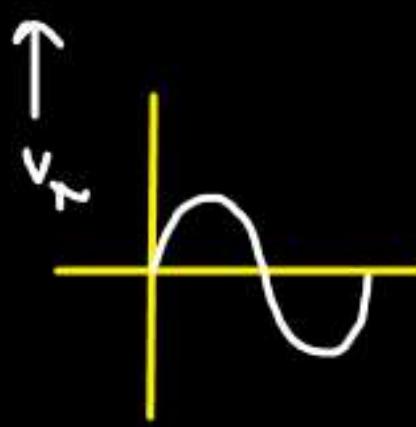
- Same amplitude
- Same dc level
- PreFusion
→ opposite in phase



⇒ v_x & v_y are differential signals.


⇒ v_x & v_z are not differential signals.

How to generate differential Signal :-

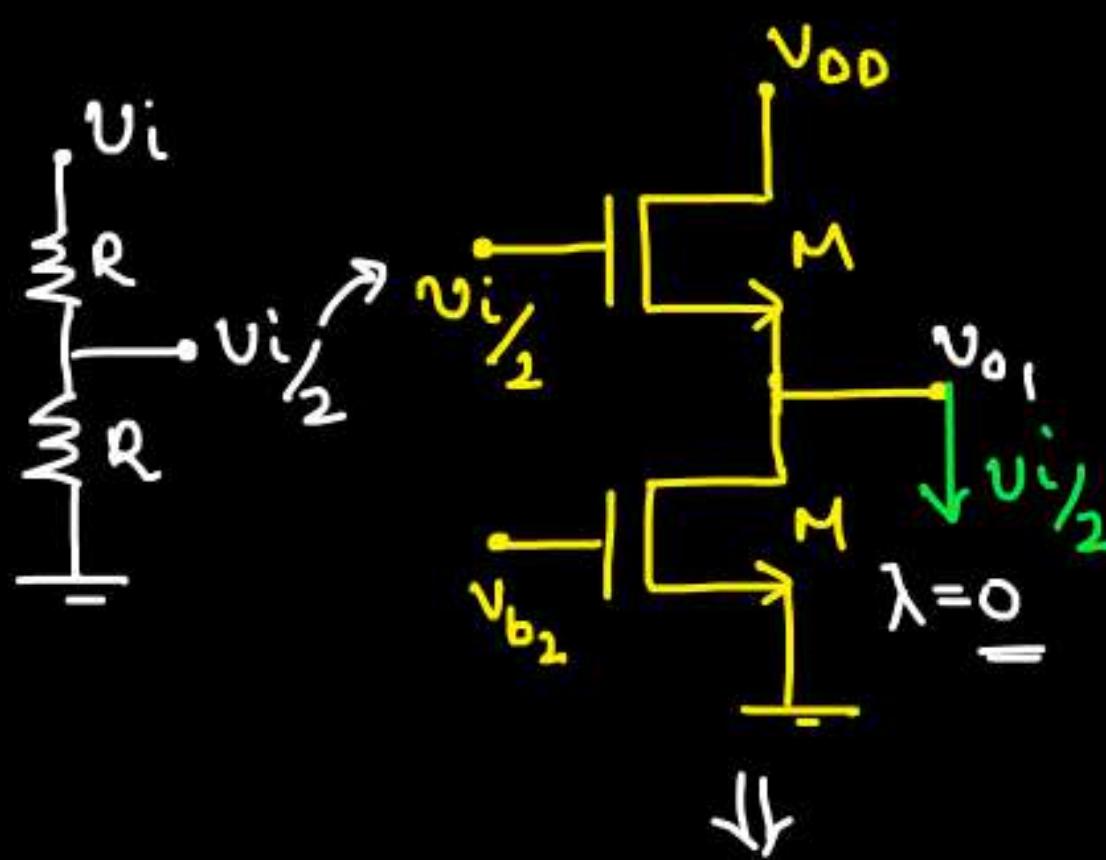


$$g_m \left(\frac{v_i}{2} - v_{o1} \right) = 0$$

$v_{o1} = \frac{v_i}{2}$

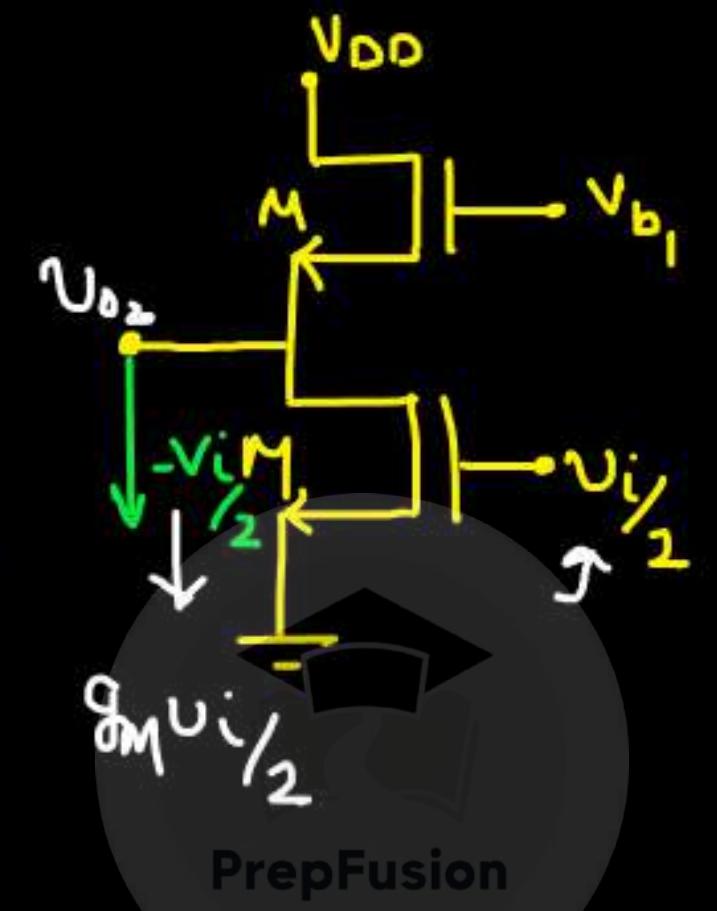


$$v_{o2} = - g_m \frac{v_i}{2} \left[\frac{1}{g_m} \right]$$

$v_{o2} = - \frac{v_i}{2}$

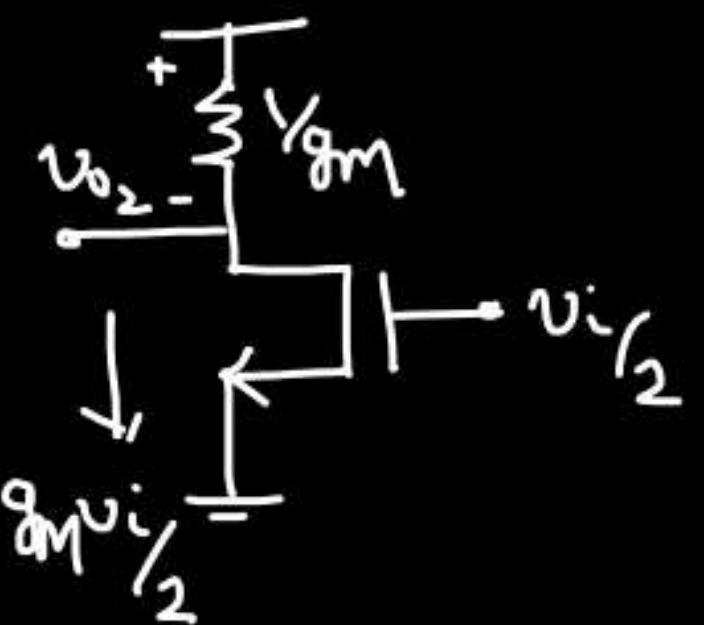

Differential Amplifier:-

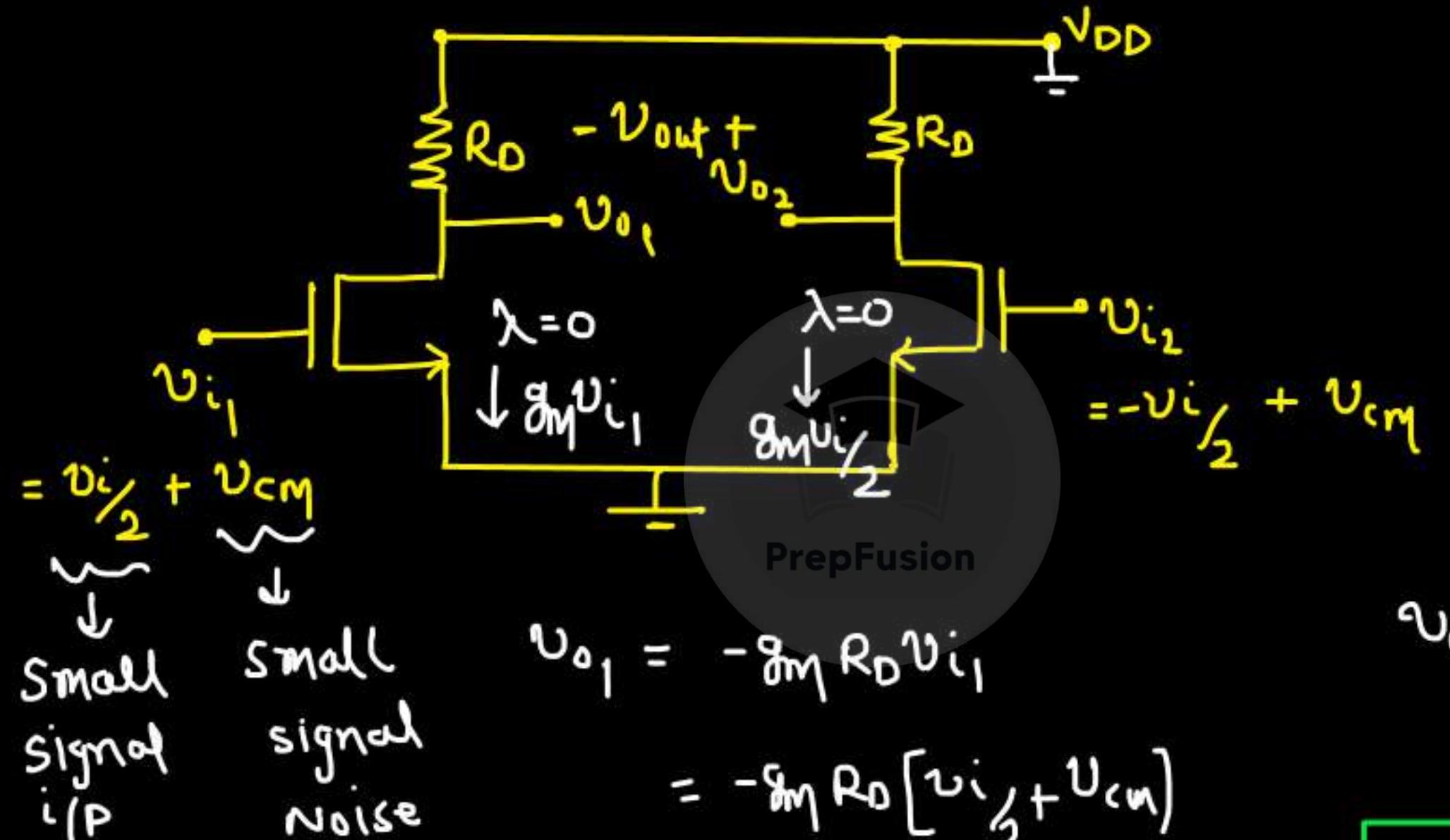

$$V_{o_1} = -g_m R_D \frac{V_i}{2} - g_m R_D V_{cm}$$


$$V_{o_2} = g_m R_D \frac{V_i}{2} - g_m R_D V_{cm}$$

$$V_o = V_{o_2} - V_{o_1}$$


$$= g_m R_D \frac{V_i}{2} - g_m R_D V_{CM} - \left[-g_m R_D \frac{V_i}{2} - g_m R_D V_{CM} \right]$$

$$V_o = g_m R_D V_i$$

$$\frac{V_o}{V_i} = g_m R_D$$

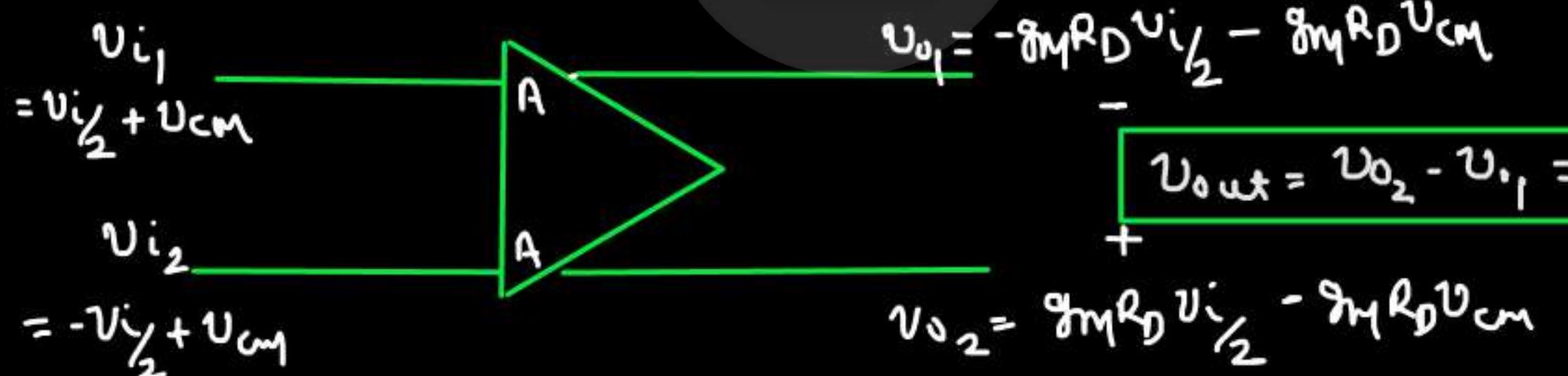

Some Common Terms:-

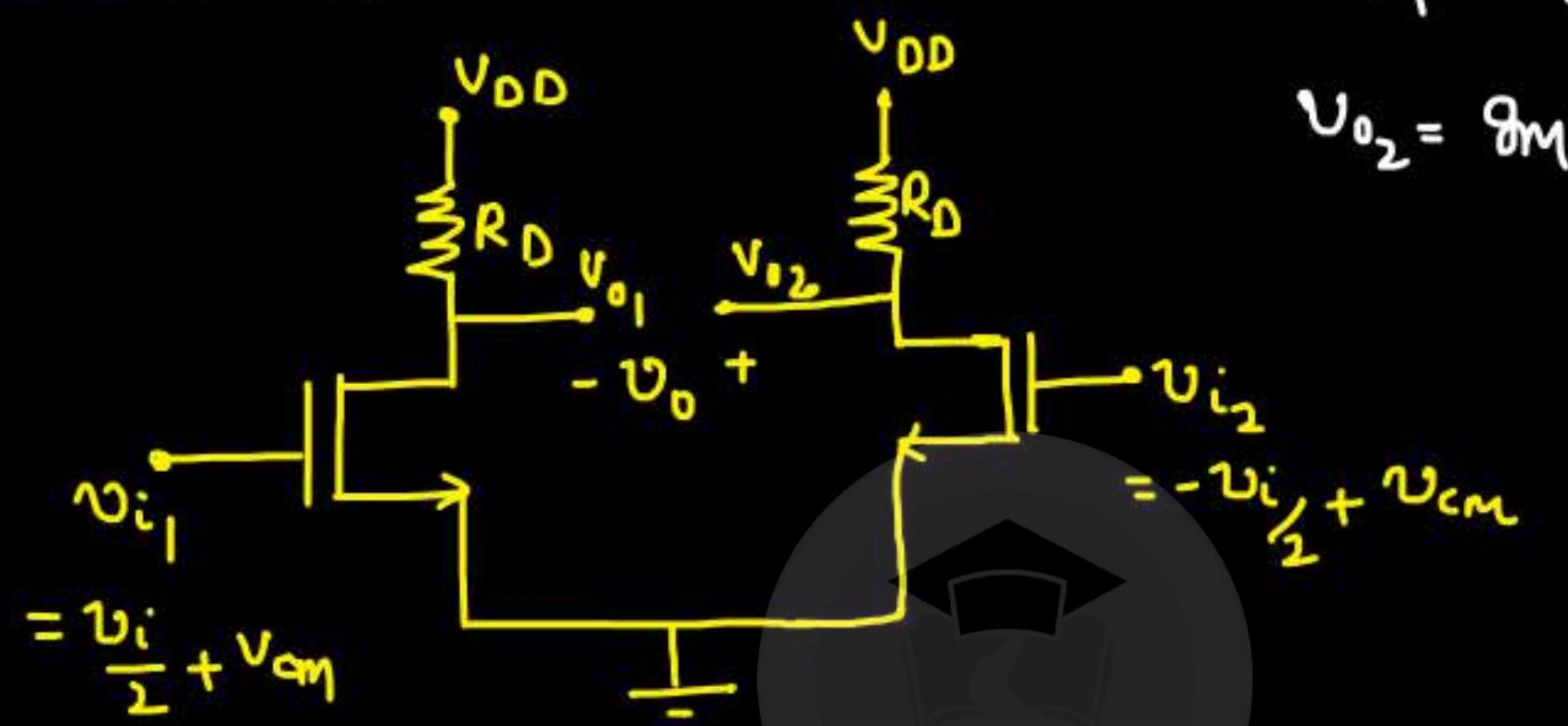


PrepFusion

- * differential input $(V_i)_d = V_{i1} - V_{i2} = V_i$
- * differential output $(V_o)_d = V_{o2} - V_{o1} = g_m R_D V_i$
- * differential gain $(A_v)_d = \frac{(V_o)_d}{(V_o)_i} = g_m R_D$

⇒ HOW TO FIND **Differential Gain** :-

Put $v_{i_1} = v_{i/2}$ and $v_{i_2} = -v_{i/2}$ { if $v_{i_1} - v_{i_2} = v_i$ }

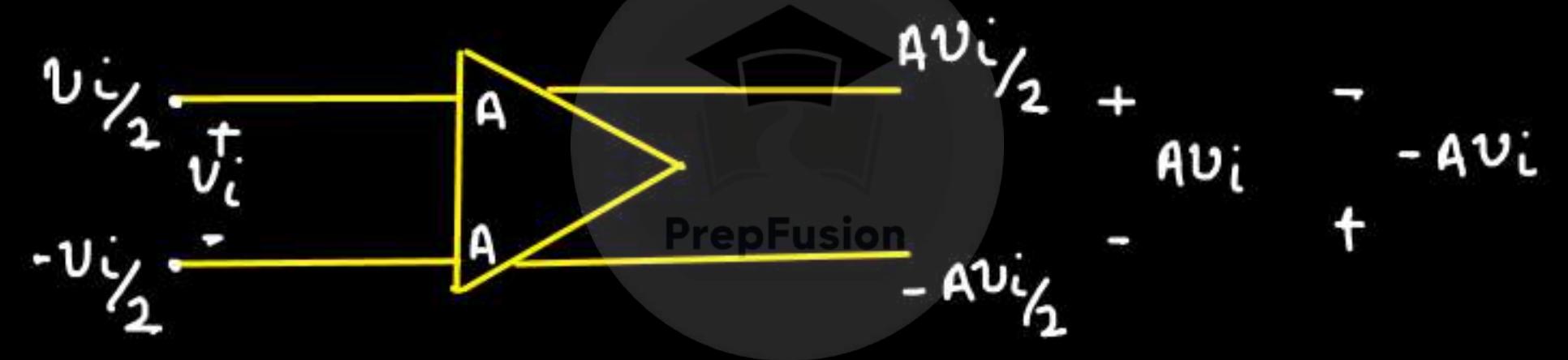Calculate $v_o = v_{o_2} - v_{o_1}$ OR $v_{o_1} - v_{o_2}$



Here $A = -g_m R_D$

* Common mode input (v_i)_{CM} = $\frac{v_{i1} + v_{i2}}{2} = \frac{2v_{CM}}{2} = v_{CM}$

* Common mode output (v_o)_{CM} = $v_{o1} + v_{o2} = -2g_m R_D v_{CM} = -g_m R_D v_{CM}$


* Common mode gain (A_v)_{CM} = $\frac{(v_o)_{CM}}{(v_i)_{CM}} = -g_m R_D$

How To FIND common mode gain :-

→ Apply $v_{i1} = v_{i2} = v_{CM}$

Find v_{o1} and v_{o2} and take average $\rightarrow (v_o)_{CM}$
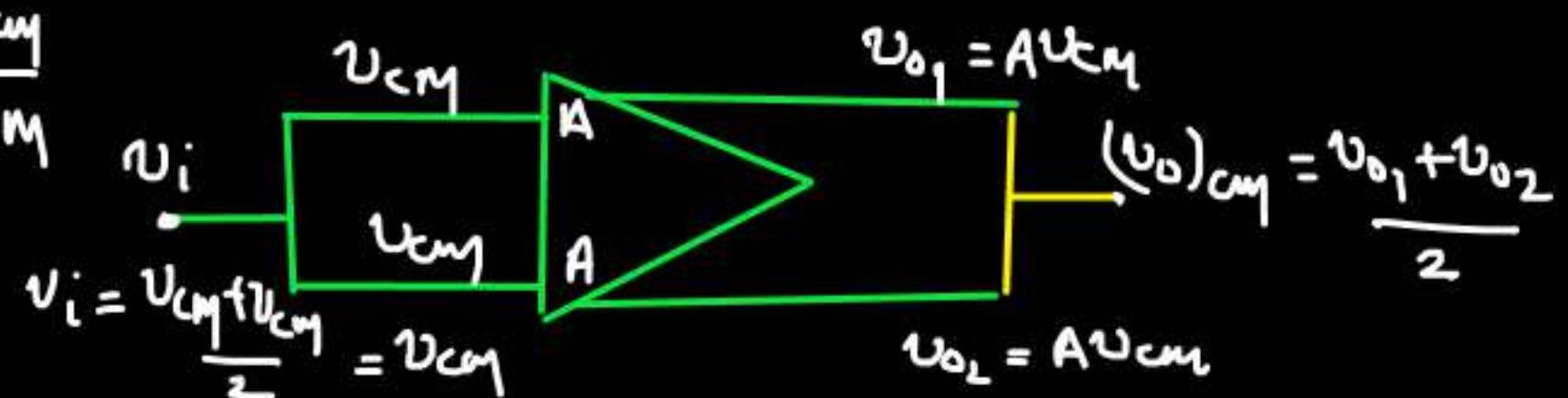
$$\text{gain} = \frac{(v_o)_{CM}}{v_{CM}}$$



HOW TO FIND [Common-Mode Differential gain]:-


$$[(A)_{CM-DM}]$$

Apply $v_{i_1} = v_{i_2} = v_{CM}$

Find v_{o_1} & v_{o_2} and $(v_o)_{CM-DM} = v_{o_2} - v_{o_1}$ or $v_{o_1} - v_{o_2}$

$$(A)_{CM-DM} = \frac{(v_o)_{CM-DM}}{v_{CM}}$$

Preassumption

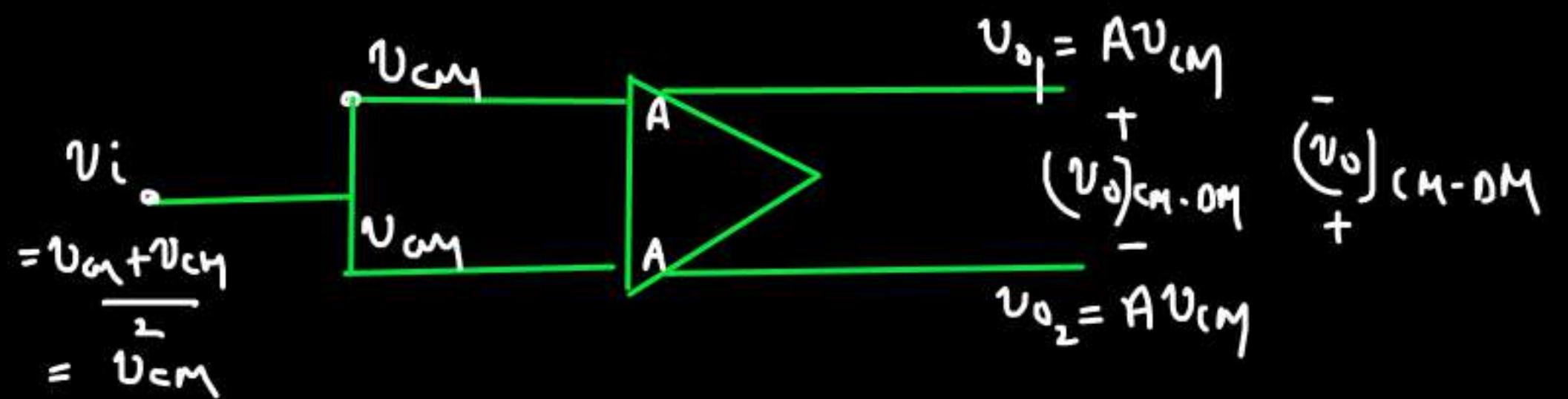

Common Mode Rejection Ratio:-

(CMRR)

Shows the ability of rejecting common mode input.

*#

$$CMRR = \left| \frac{A_d}{A_{CM-DM}} \right| = \left| \frac{\text{Differential gain}}{\text{Common-Mode differential gain}} \right|$$


PrepFusion

MORE CMRR \Rightarrow Less sensitive to noise


$CMRR \rightarrow \infty \Rightarrow A_{CM-DM} = 0 \Rightarrow$ No noise in the output


- Q. for the given config (a) and (b). find
- Differential Gain
 - Common-Mode Gain
 - Common-Mode Differential Gain
 - CMRR

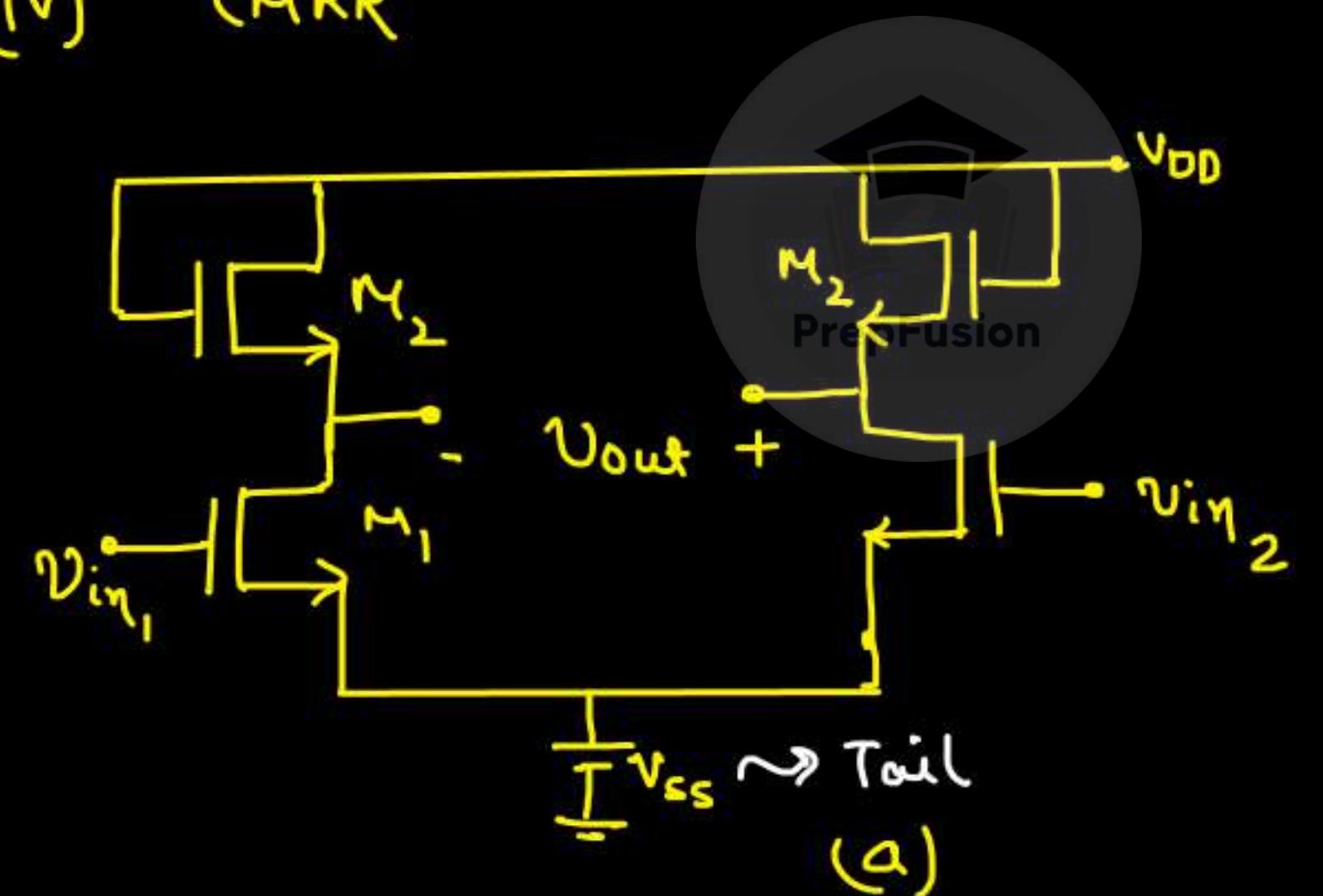N.B. - $\lambda \neq 0$ for M_2
 $\lambda = 0$ for M_1




$$v_{in} = v_{in1} - v_{in2}$$

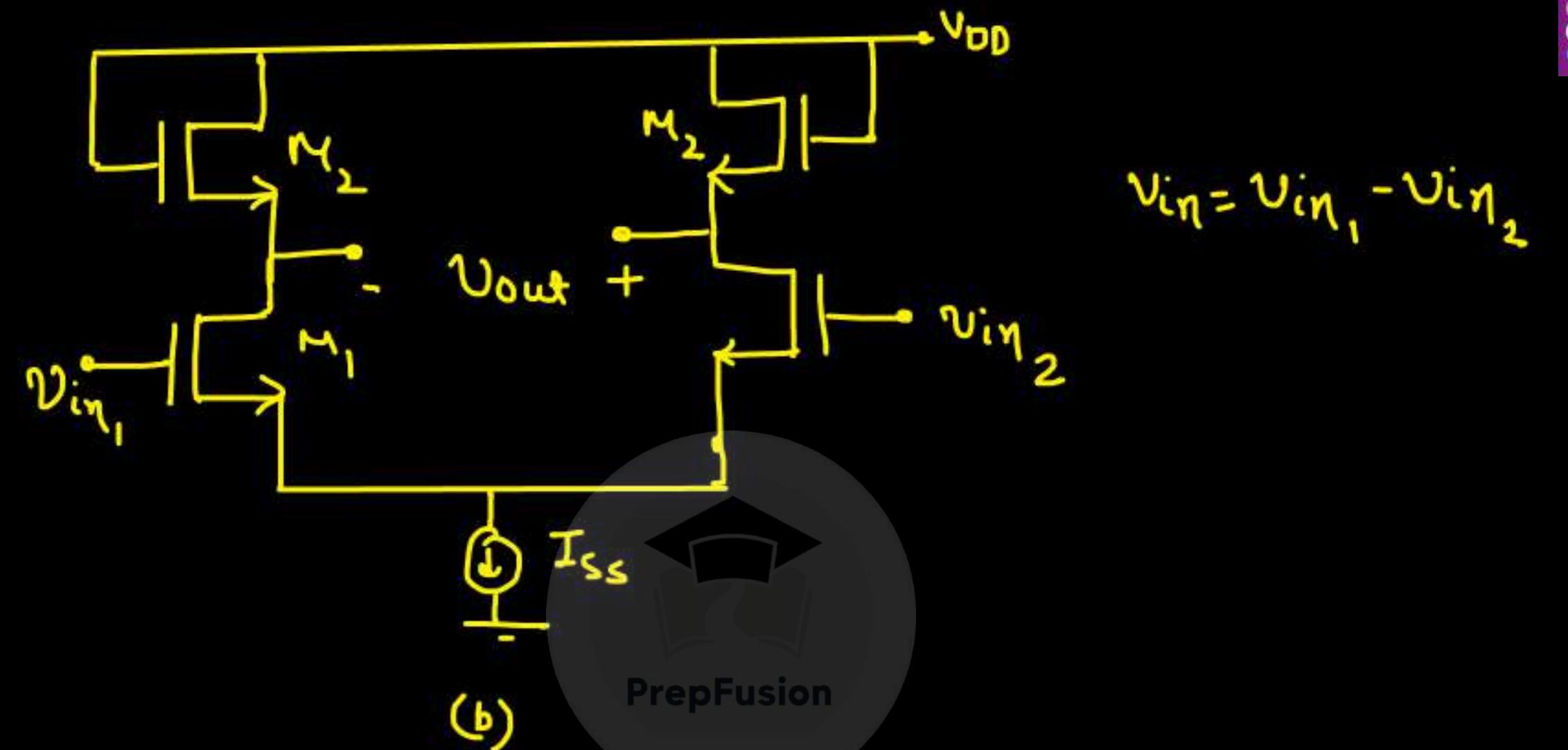

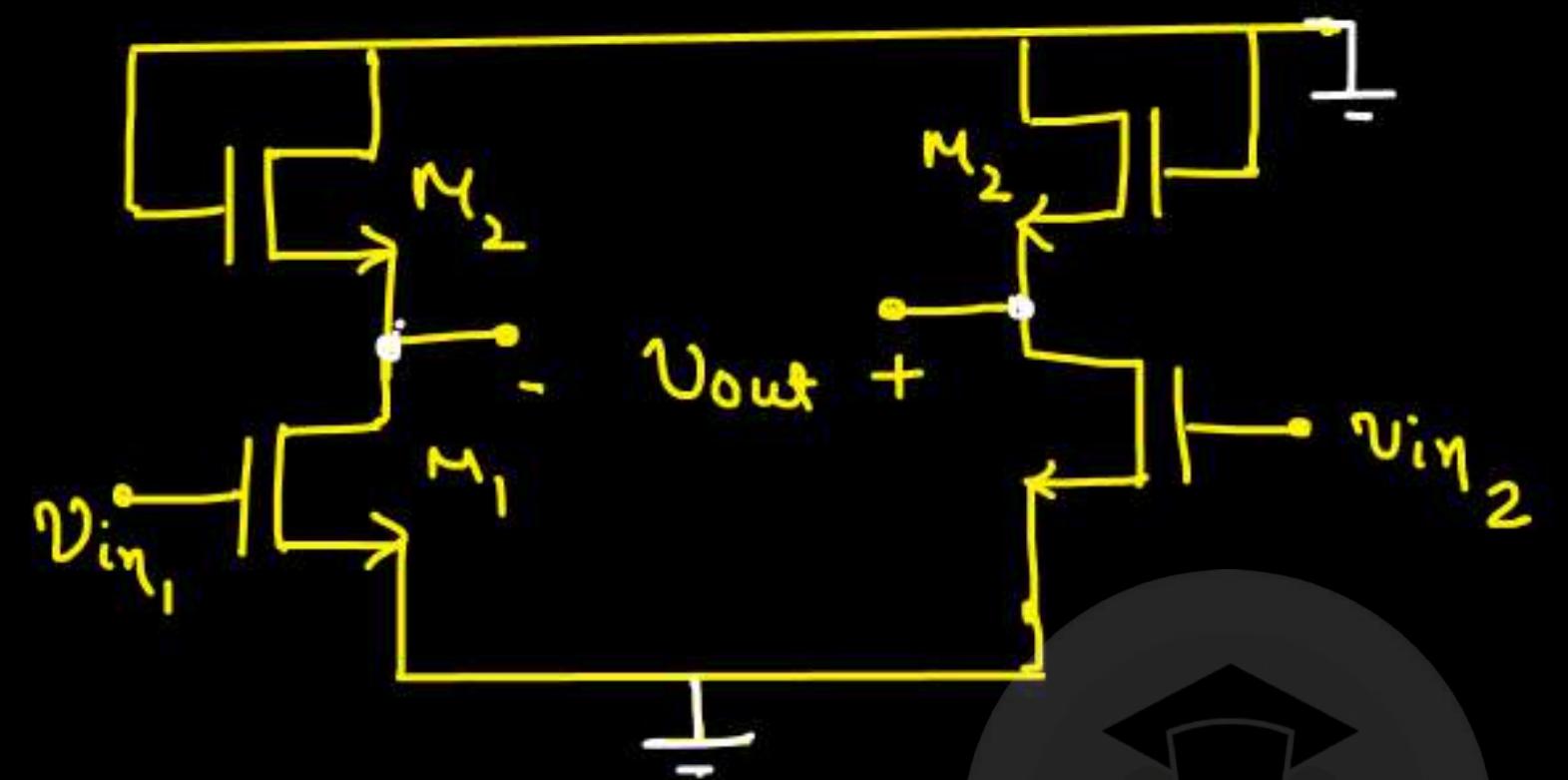


(a)

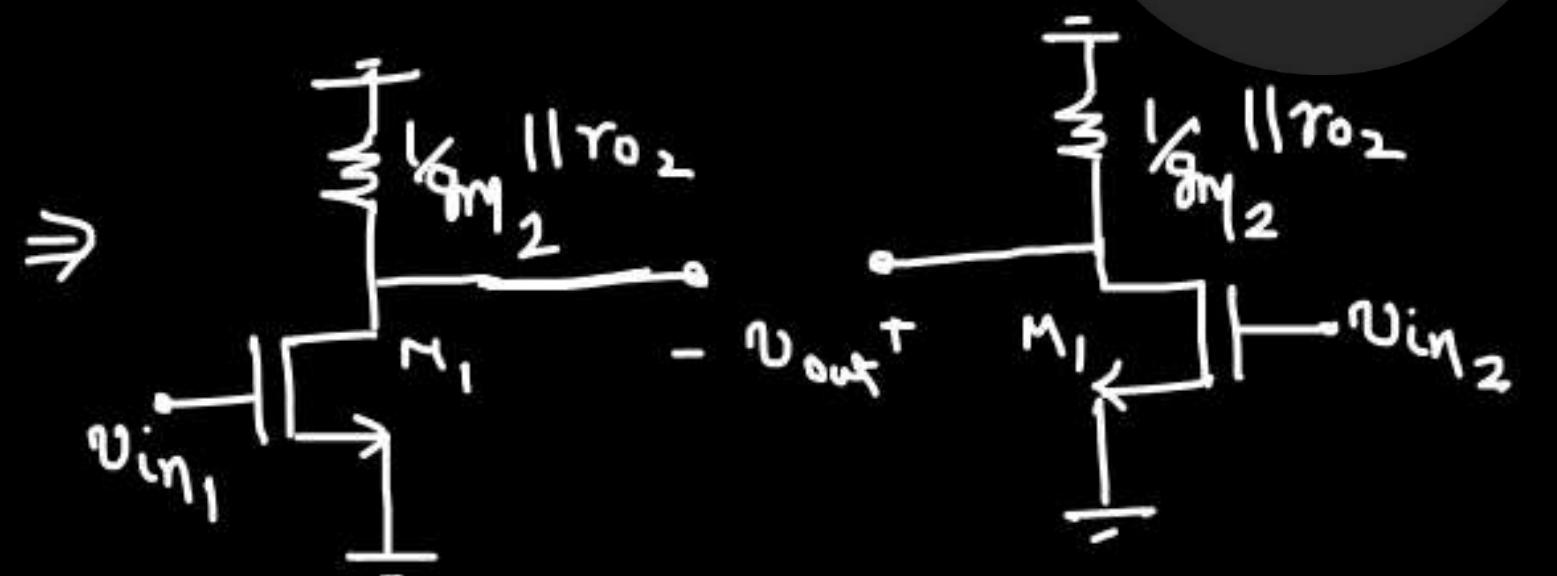

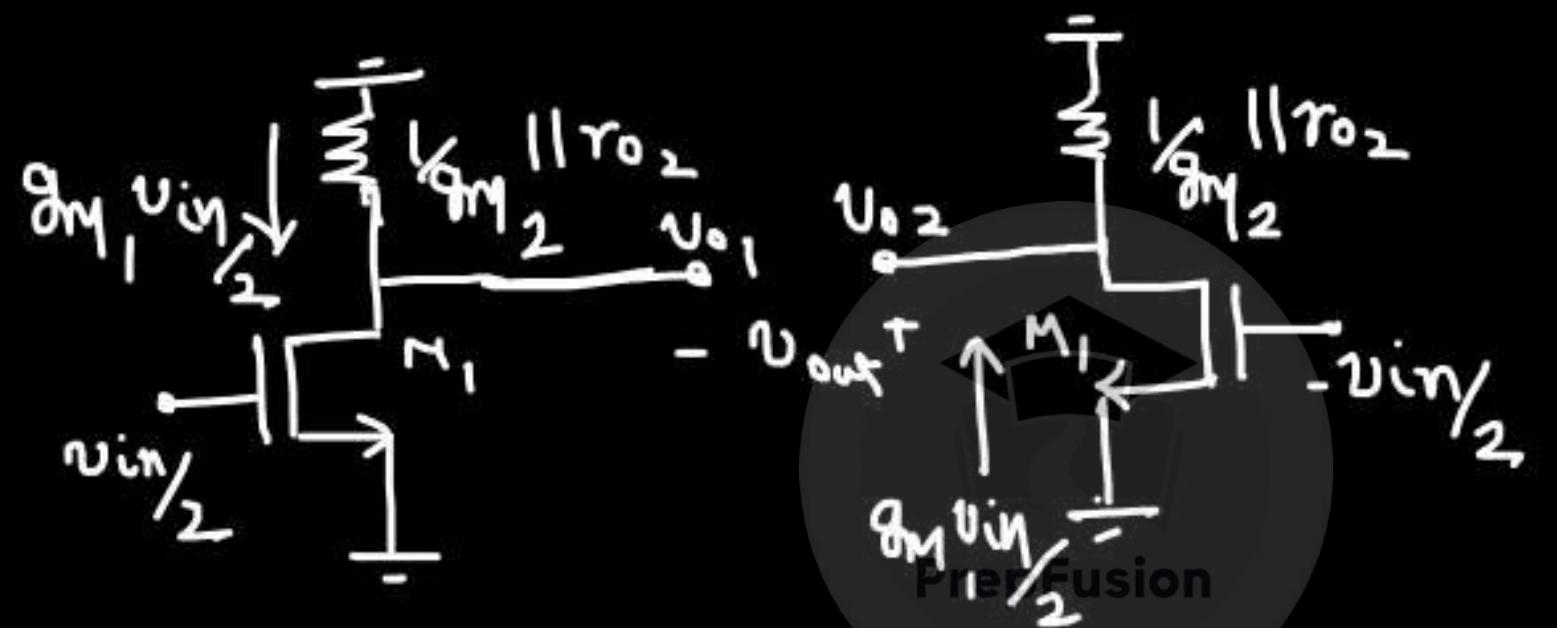(I) Differential gain :-

$$U_{i_1} = \frac{U_{in}}{2}, \quad U_{i_2} = -\frac{U_{in}}{2} \quad [U_{in_1} - U_{in_2} = U_{in}]$$



$$U_{o_1} = -g_{m_1} \left[\frac{1}{g_{m_2}} || r_{o_2} \right] \frac{U_{in}}{2}$$

$$U_{o_2} = g_{m_1} \left[\frac{1}{g_{m_2}} || r_{o_2} \right] \frac{U_{in}}{2}$$



$$\Rightarrow (U_o)_d = g_{m_1} \left[\frac{1}{g_{m_2}} || r_{o_2} \right] U_{in}$$

$$\Rightarrow (U_i)_d = \frac{U_{in}}{2} - \left(-\frac{U_{in}}{2} \right) = U_{in}$$

$$(\Delta V)_d = g_{m_1} \left[\frac{1}{g_{m_2}} || r_{o_2} \right] U_{in}$$

(II) Common - Mode gain: -

$$V_{i1} = V_{i2} = V_{CM}$$

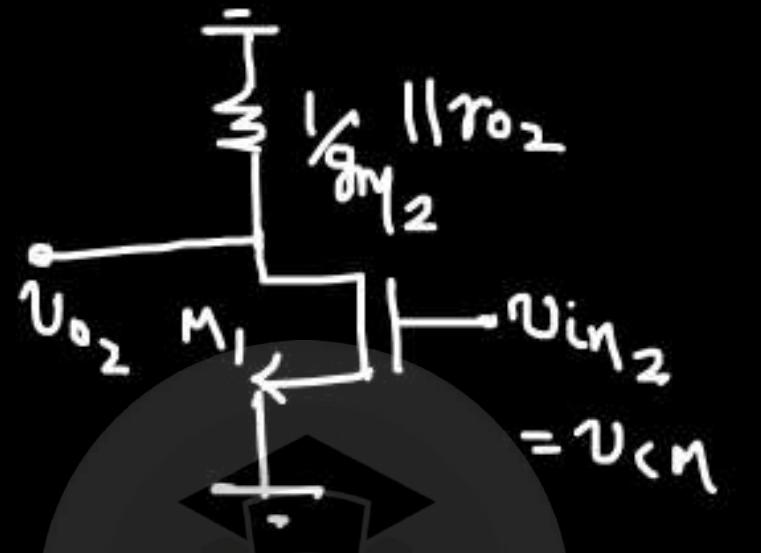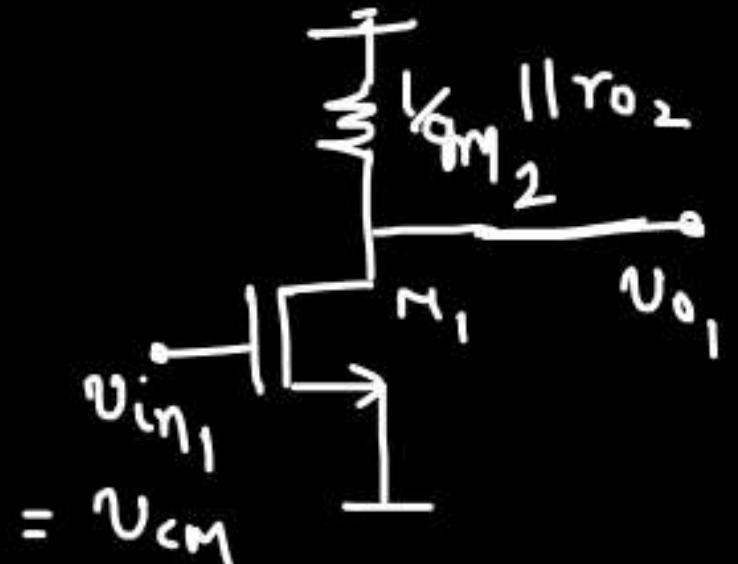

$$V_{o1} = -g_{m1} \left[\frac{1}{g_{m2}} || r_o2 \right] V_{CM}$$

$$(V_o)_{CM} = \frac{V_{o1} + V_{o2}}{2}$$

$$V_{o2} = -g_{m1} \left[\frac{1}{g_{m2}} || r_o2 \right] V_{CM}$$

$$(V_o)_{CM} = -g_{m1} \left[\frac{1}{g_{m2}} || r_o2 \right] V_{CM}$$

$$(\alpha_v)_{CM} = -g_{m1} \left[\frac{1}{g_{m2}} || r_o2 \right]$$

$$(V_i)_{CM} = \frac{V_{CM} + V_{CM}}{2} = V_{CM}$$

Common Mode Differential gain:-

$$V_{i_1} = V_{i_2} = V_{CM}$$

$$V_{o_1} = -g_m \left[\frac{1}{g_m} || r_o \right] V_{CM}$$

$$V_{o_2} = -g_m \left[\frac{1}{g_m} || r_o \right] V_{CM}$$

$$(V_o)_{CM-DM} = V_{o_2} - V_{o_1} = 0$$

PrepFusion


$$(V_i)_{CM-DM} = V_{CM} + \frac{V_{CM}}{2} = V_{CM}$$

$$(\alpha_v)_{CM-DM} = \frac{0}{V_{CM}} = 0$$



CMRR :-

$$\begin{aligned} CMRR &= \left| \frac{(\alpha)_d}{(\alpha)_{CM-DM}} \right| \\ &= \left| \frac{(\alpha)_d}{0} \right| \end{aligned}$$

$$CMRR = \infty$$

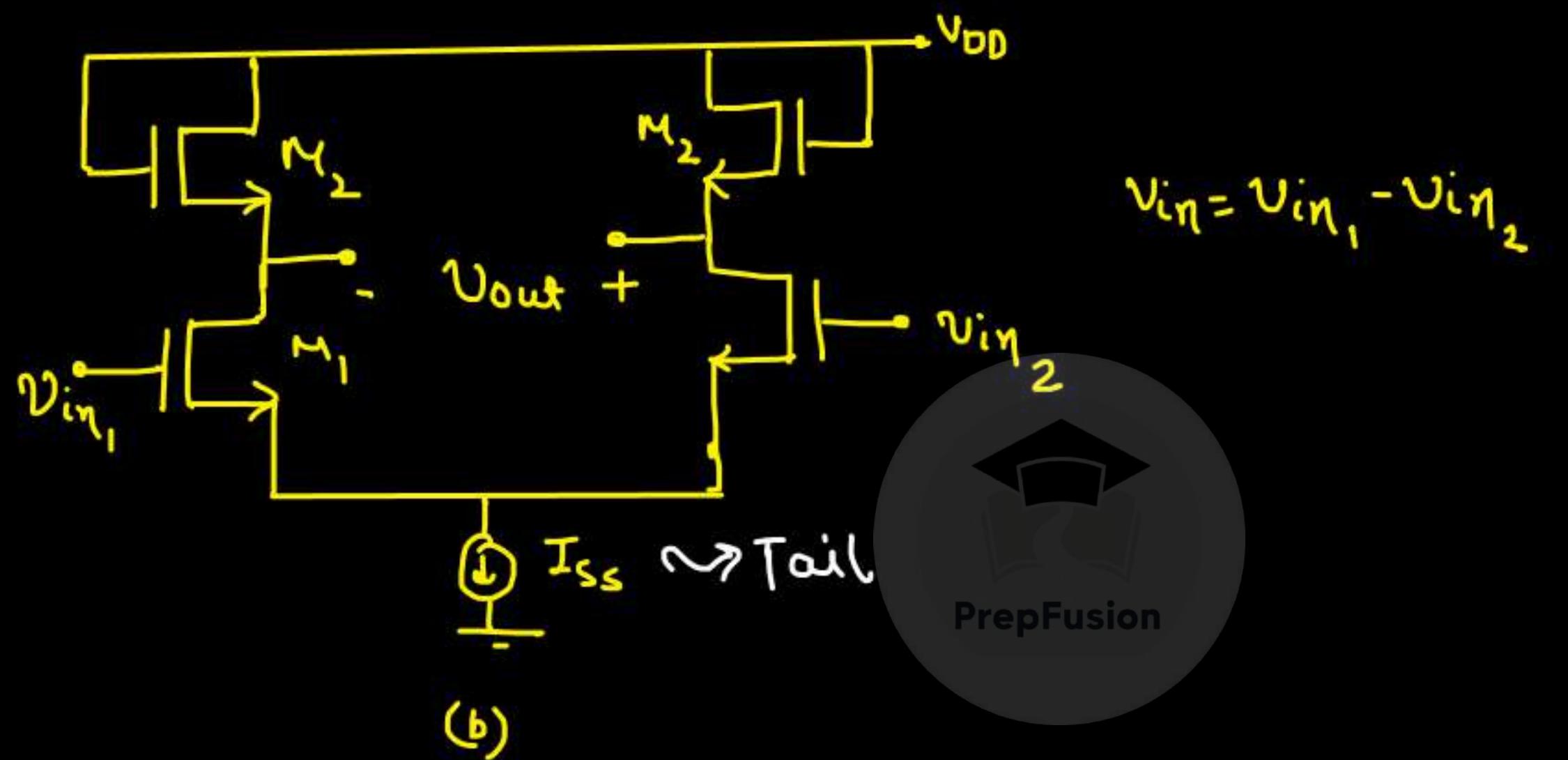


(I) Differential gain :-

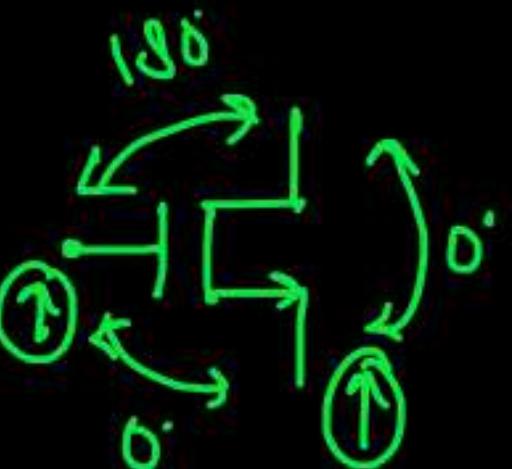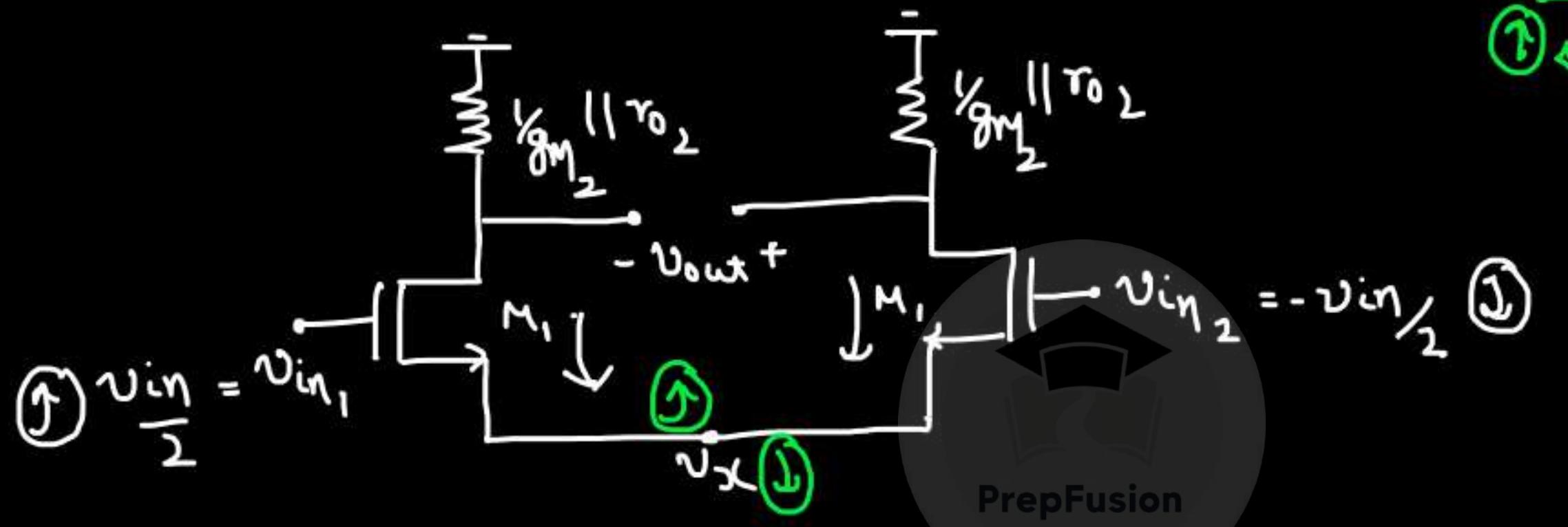

$$gm(V_{in} - v_n) = - gm\left(-\frac{V_{in}}{2} - v_n\right)$$

$$v_n = 0$$

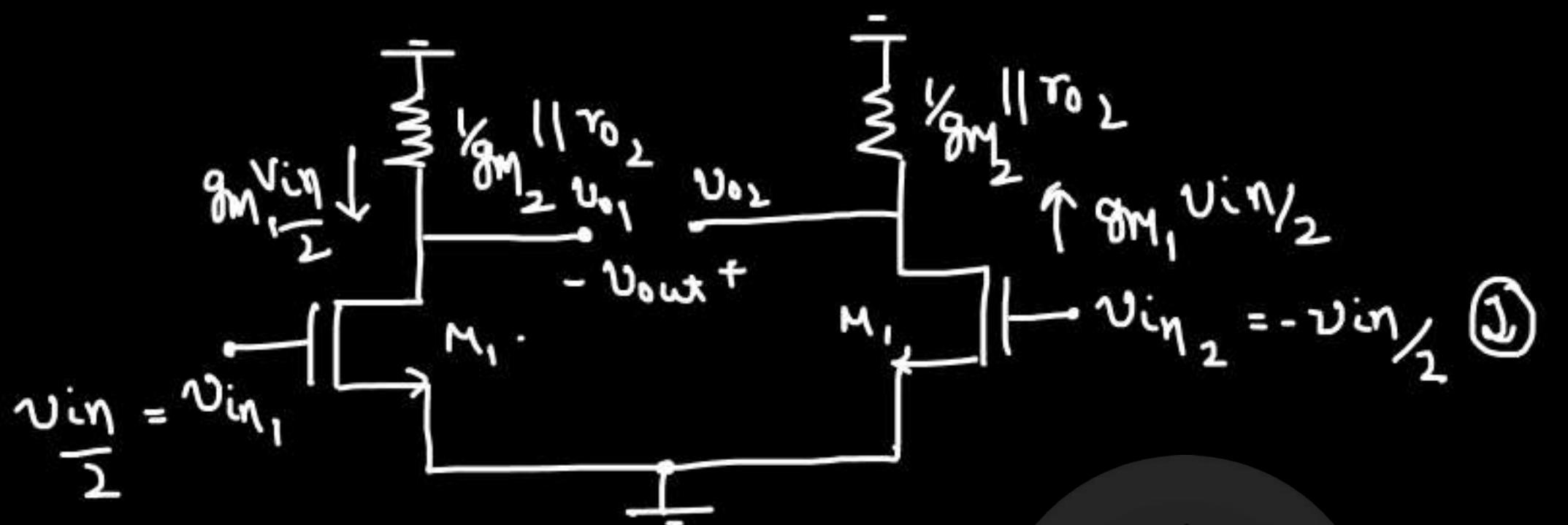

$v_{out_2} = g_m \left[\frac{1}{g_m} \| r_o \right] v_{in_2}$

Preparation

$v_{out_1} = -g_m \left[\frac{1}{g_m} \| r_o \right] v_{in_1}$


$A_v = g_m \left[\frac{1}{g_m} \| r_o \right]$

$(v_{out})_d = g_m \left[\frac{1}{g_m} \| r_o \right] v_{in}$

$(v_{in})_d = v_{in}$



(II) Common Mode Gain:-

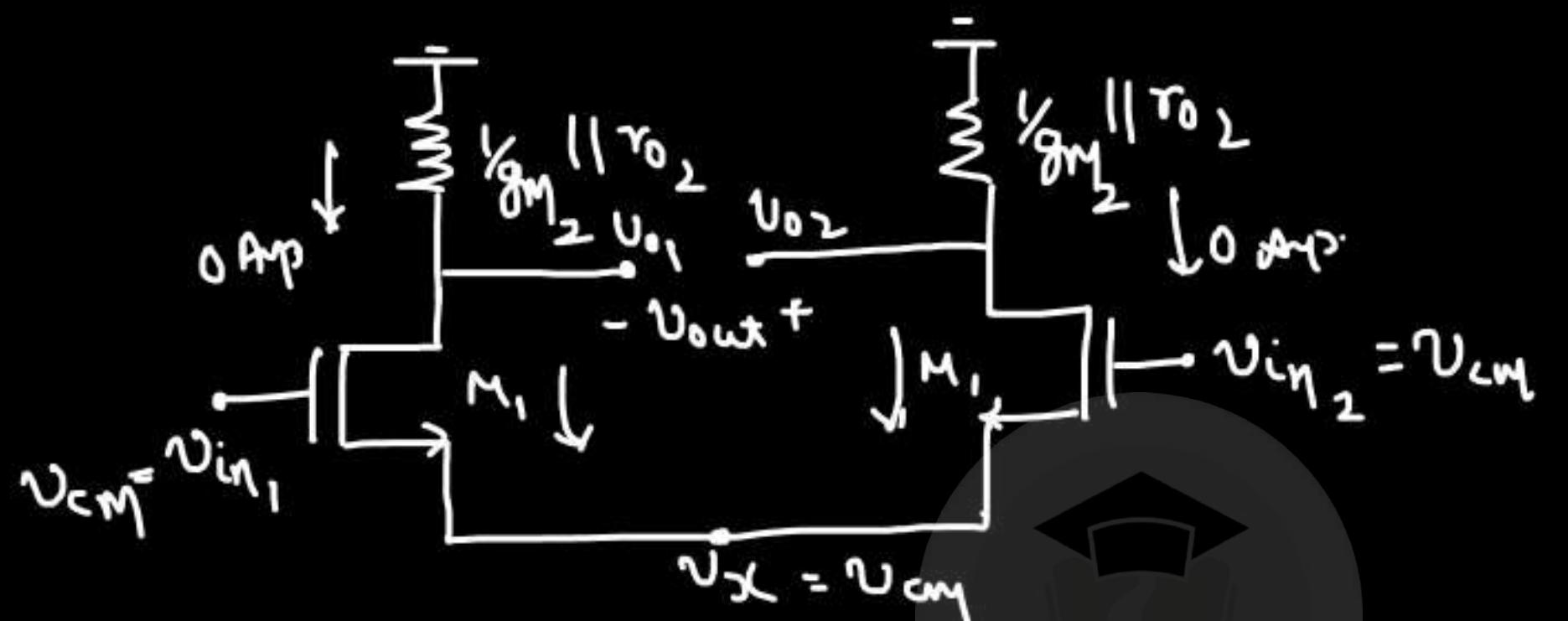

$$g_m M_1 (V_{cm} - V_x) = - g_m M_1 (V_{cm} - V_n)$$

$$2g_m M_1 (V_{cm} - V_n) = 0$$

$$V_x = V_{cm}$$

$$V_{01} = V_{02} = 0$$

$$(V_0)_{cm} = \frac{V_{01} + V_{02}}{2} = 0$$

$$(\Delta v)_{cm} = \frac{0}{V_{cm}} = 0$$

N.B.- Common Mode gain shows the amount of noise present in the ckt.

It's good to have as low as common mode gain.

(III) Common - Mode Differential gain :-

$$V_{o_1} = 0$$

$$V_{o_2} = 0$$

$$(V_o)_{CM-DM} = V_{o_2} - V_{o_1} = 0$$

$$\boxed{(A)_{CM-DM} = 0}$$

N.B.- When there is no Mismatch in Transistors

Voltage source as tail

$$\textcircled{1} \quad (\Delta V)_d = g_{m_1} \left[\frac{1}{g_{m_2}} \parallel r_o \right]$$

$$\textcircled{2} \quad (\Delta V)_{CM} = -g_{m_1} \left[\frac{1}{g_{m_2}} \parallel r_o \right]$$

$$\textcircled{3} \quad (\Delta V)_{CM-DM} = 0$$


Current source as tail

$$\textcircled{1} \quad (\Delta V)_d = g_{m_1} \left[\frac{1}{g_{m_2}} \parallel r_o \right] \rightarrow \boxed{\text{Same}}$$

$$\textcircled{2} \quad (\Delta V)_{CM} = 0 \rightarrow \boxed{\text{Advantage}}$$


$$\textcircled{3} \quad (\Delta V)_{CM-DM} = 0 \rightarrow \boxed{\text{Same}}$$

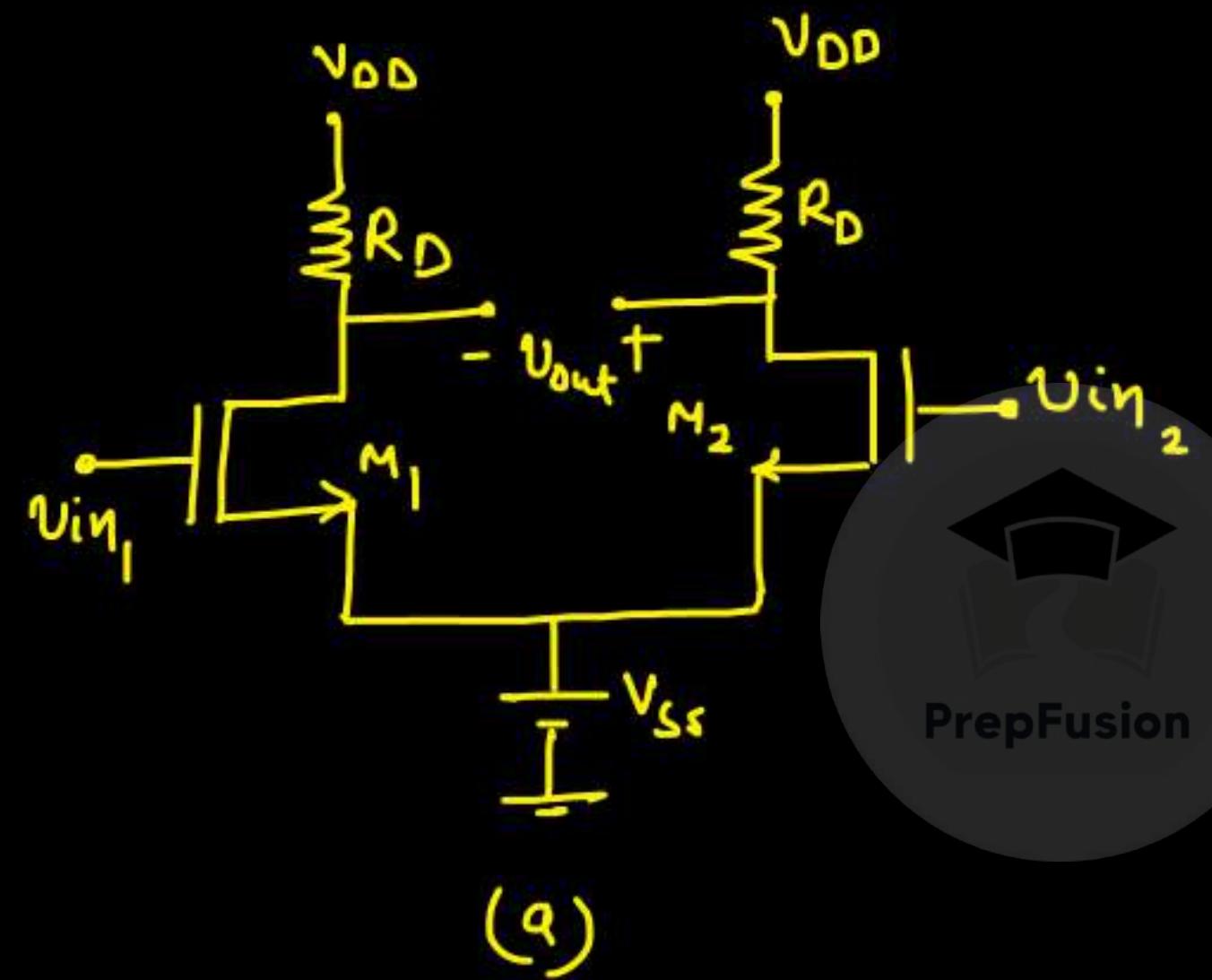⇒ finding the same parameters when there is mismatch:-



$$v_{in} = v_{in_1} - v_{in_2}$$

(a) Differential gain :-

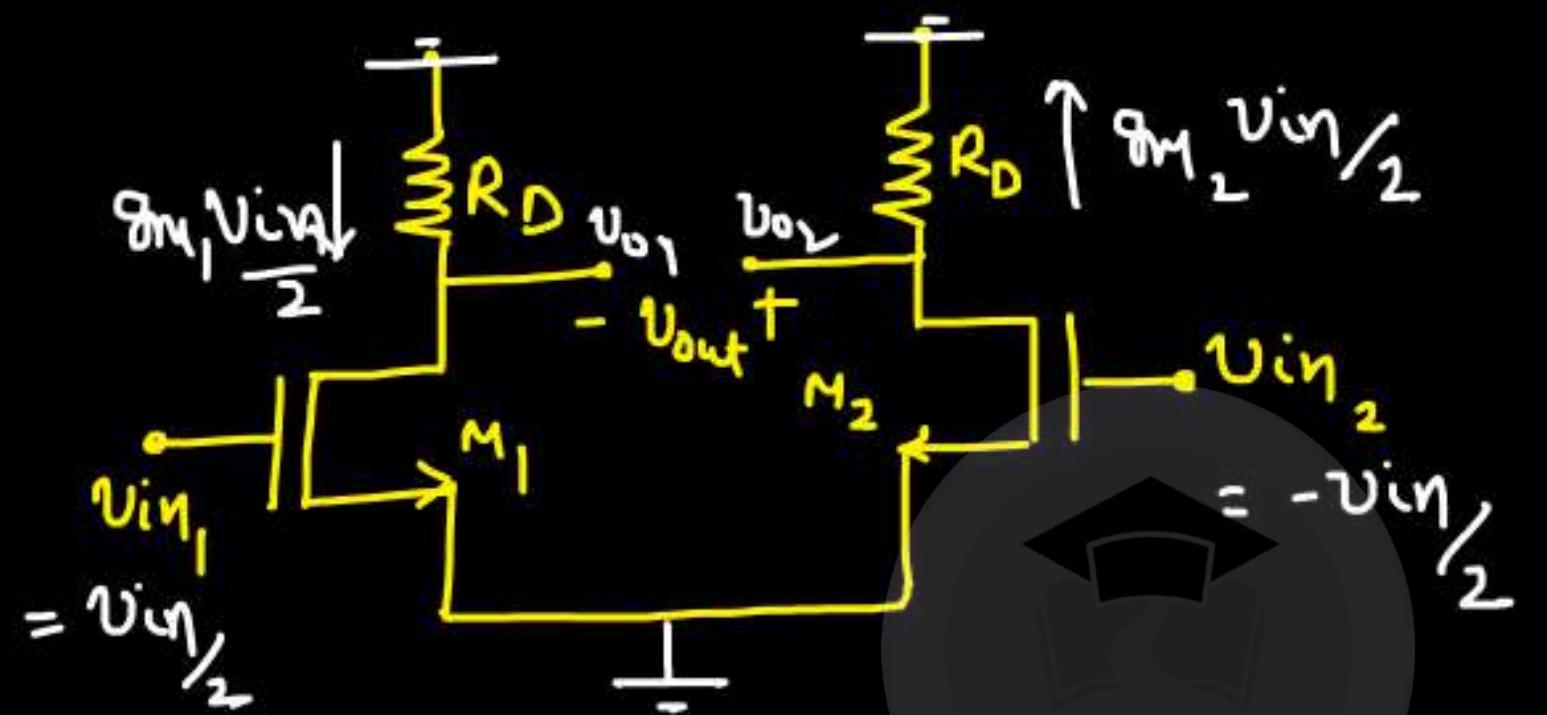

$$v_{o2} = g_{m2} R_D \frac{v_{in}}{2}$$


$$v_{o1} = -g_{m1} R_D \frac{v_{in}}{2}$$

$$(v_o)_d = v_{o2} - v_{o1} = (g_{m2} + g_{m1}) R_D \frac{v_{in}}{2}$$

$$(v_i)_d = v_{in}$$

$$(A_v)_d = \left(\frac{g_{m1} + g_{m2}}{2} \right) R_D$$

(b) Common - Mode Gain :-

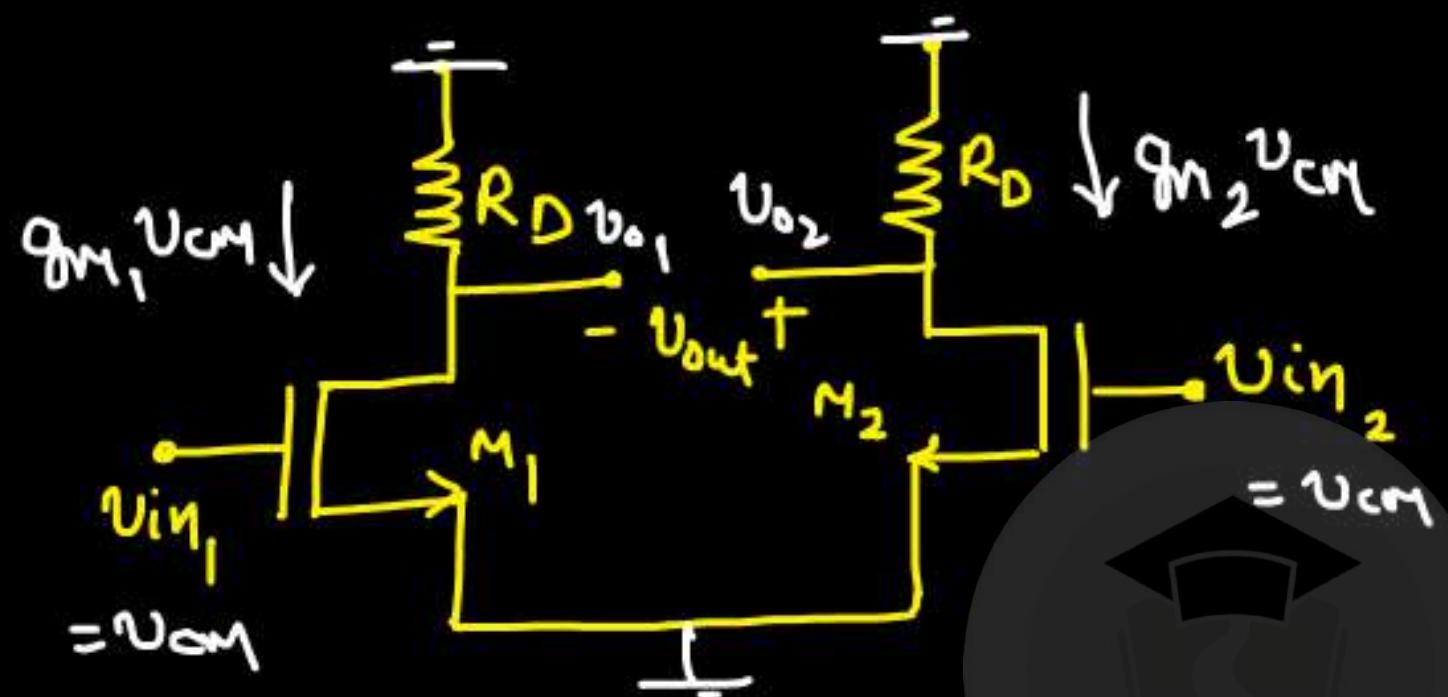

PrepFusion

$$U_{o2} = -g_{m2} R_D V_{cm}$$

$$U_{o1} = -g_{m1} R_D V_{cm}$$


$$(U_o)_{cm} = -\frac{(g_{m1} + g_{m2})}{2} R_D V_{cm}$$

$$(V_i)_{cm} = V_{cm}$$

4

$$(\Delta V)_{cm} = -\frac{(g_{m1} + g_{m2})}{2} R_D$$


(c) Common Mode Differential Gain:-

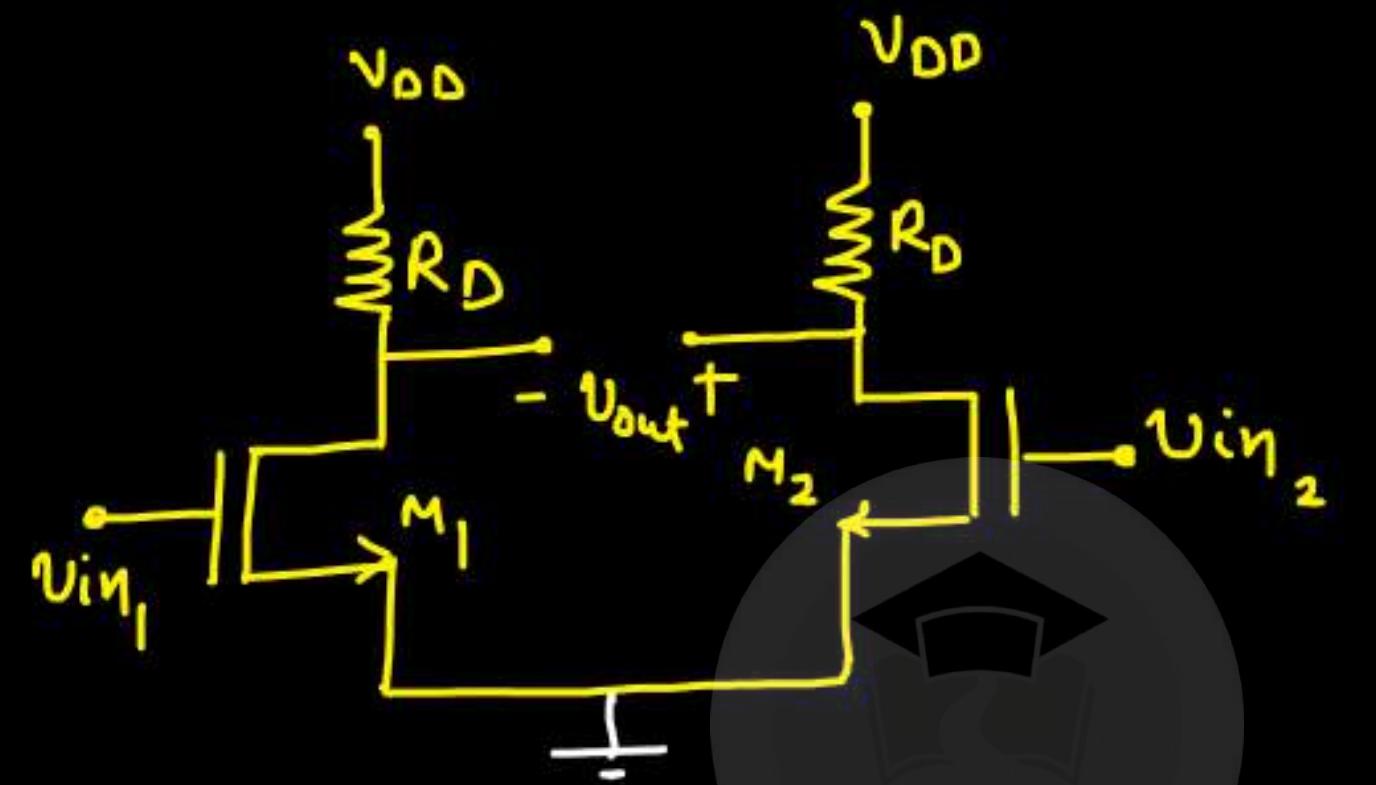


$$(V_o)_{CM-DM} = (g_m - g_m) R_D V_{CM}$$

$$(V_i)_{CM} = V_{CM}$$

∴ $(\Delta v)_{CM-DM} = (g_m - g_m) R_D$

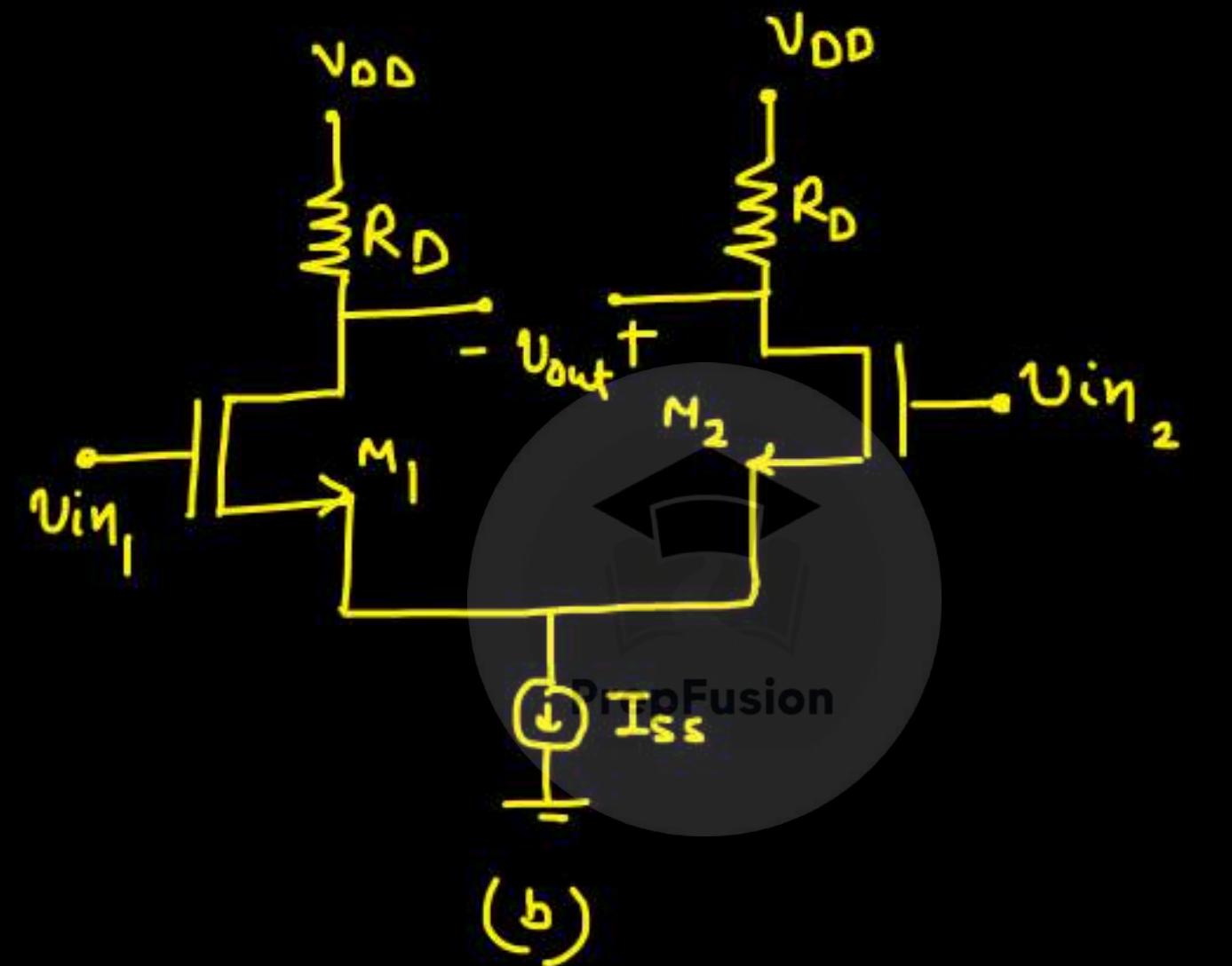

(a) Differential Gain:-

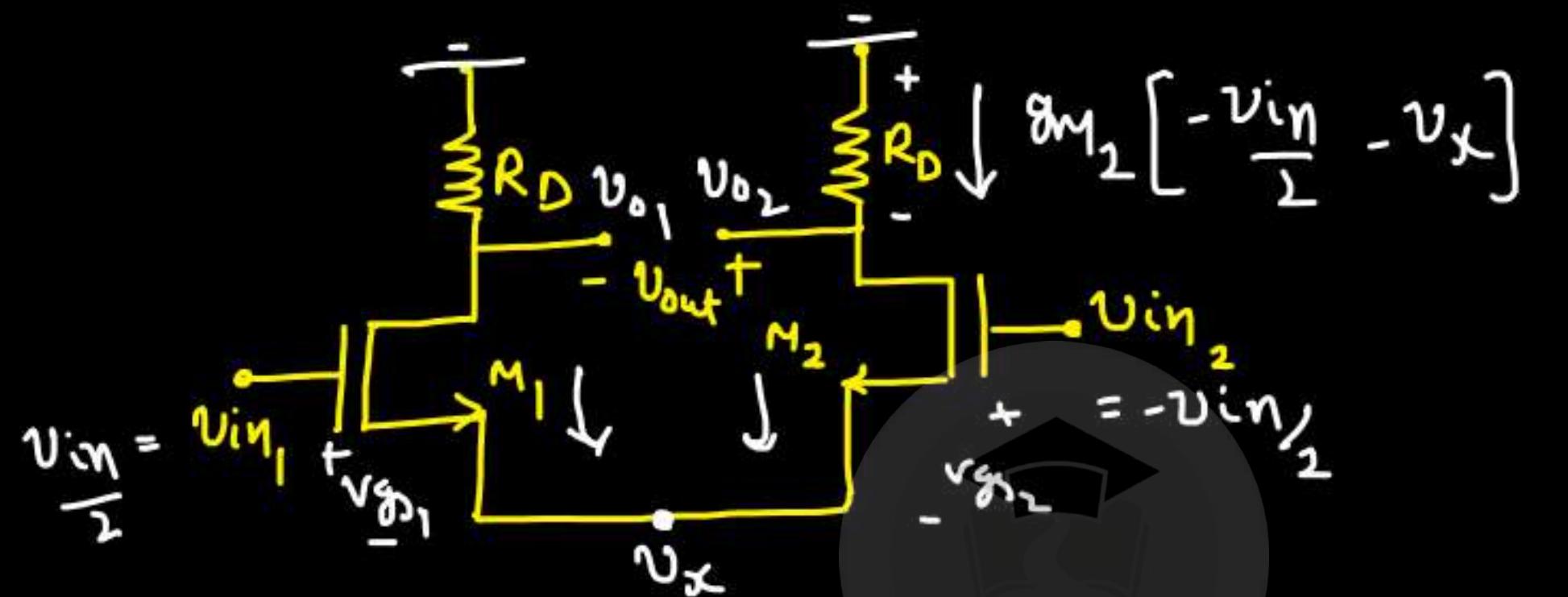

PrepFusion

$$g_m_1 \left[\frac{v_{in}}{2} - v_x \right] = -g_m_2 \left[-\frac{v_{in}}{2} - v_x \right]$$

$$g_m_1 \frac{v_{in}}{2} - g_m_1 v_x = g_m_2 \frac{v_{in}}{2} + g_m_2 v_x$$

$$\frac{(g_m_1 - g_m_2)}{g_m_2 + g_m_1} \frac{v_{in}}{2} = v_x \quad \text{--- (1)}$$

$$v_{o2} = g_m_2 R_D \left[\frac{v_{in}}{2} + v_x \right]$$

$$v_{o1} = -g_m_1 R_D \left[\frac{v_{in}}{2} - v_x \right]$$

$$(v_o)_d = g_m_2 R_D \left[\frac{v_{in}}{2} + v_x \right] + g_m_1 R_D \left[\frac{v_{in}}{2} - v_x \right]$$

$$(v_o)_d = \frac{[g_m_2 + g_m_1]}{2} R_D v_{in} + [g_m_2 - g_m_1] R_D v_x$$

$$\begin{aligned} &= \frac{[g_m_1 + g_m_2]}{2} R_D v_{in} + [g_m_2 - g_m_1] R_D \frac{[g_m_1 - g_m_2]}{[g_m_1 + g_m_2]} \frac{v_{in}}{2} \\ &= \frac{\{ [g_m_1 + g_m_2]^2 R_D - [g_m_2 - g_m_1]^2 R_D \}}{g_m_1 + g_m_2} v_{in}/2 \end{aligned}$$

PrepFusion

$$= \frac{[4g_m_1 g_m_2]}{g_m_1 + g_m_2} R_D \frac{V_{in}}{2}$$

$$(V_o)_d = \left[\frac{2g_m_1 g_m_2}{g_m_1 + g_m_2} \right] R_D V_{in}$$

$$(V_i)_d = V_{in}$$

$$(\Delta V)_d : \frac{2g_m_1 g_m_2}{g_m_1 + g_m_2} R_D$$

CURRENT SOURCE as a tail :-


$$(\Delta V)_d = \left(\frac{2g_m_1 g_m_2}{g_m_1 + g_m_2} \right) R_D$$

VOLTAGE SOURCE as a tail :-

$$(\Delta V)_d = \left(\frac{g_m_1 + g_m_2}{2} \right) R_D \rightarrow \text{Advantage}$$

$$(\Delta V)_d_{V.S.} > (\Delta V)_d_{C.S.} \rightarrow \text{In case of mismatch}$$

(b) Common mode gain :-

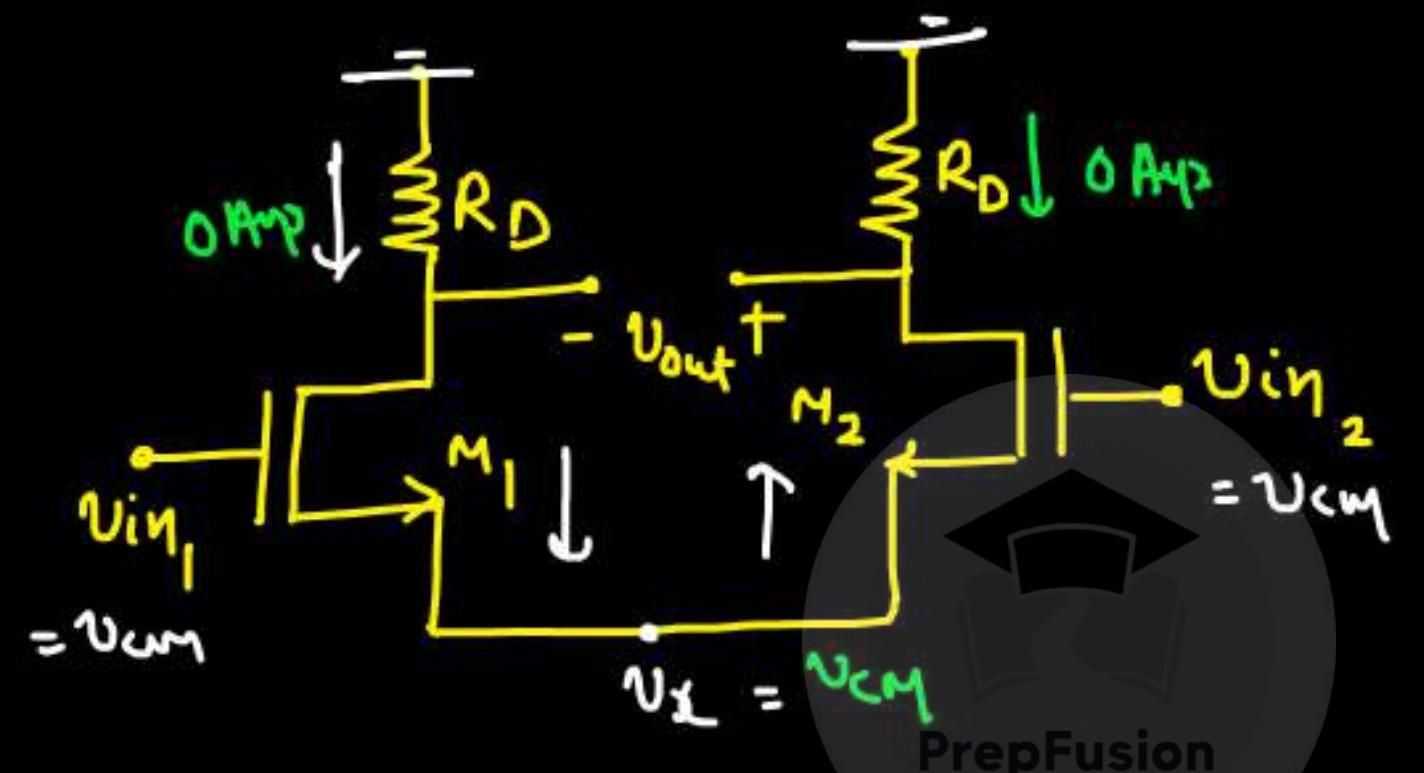

$$g_m_1 (U_{cm} - U_x) = - g_m_2 (U_{cm} - U_x)$$

$$(g_m_1 + g_m_2) U_{cm} = (g_m_2 + g_m_1) U_x$$

$\star \star$ $U_x = U_{cm}$

$(\Delta V)_{cm} = 0$

$$(\Delta V)_{cm \rightarrow v.s.} = - \left(\frac{g_m_1 + g_m_2}{2} \right) R_D$$

$$(\Delta V)_{cm \rightarrow c.s.} = 0$$

Advantage =

(c) Common-Mode Differential Gain :-

$$V_{o_1} = V_{o_2} = 0$$

$$(A_v)_{CM-DM} = 0$$


$$(A_v)_{CM-DM \rightarrow V.S.} = (g_m 1 - g_m 2) R_D$$

$$(A_v)_{CM-DM \rightarrow C.S.} = 0$$

↓
Advantage

PrepFusion




★ Some important Concepts :-

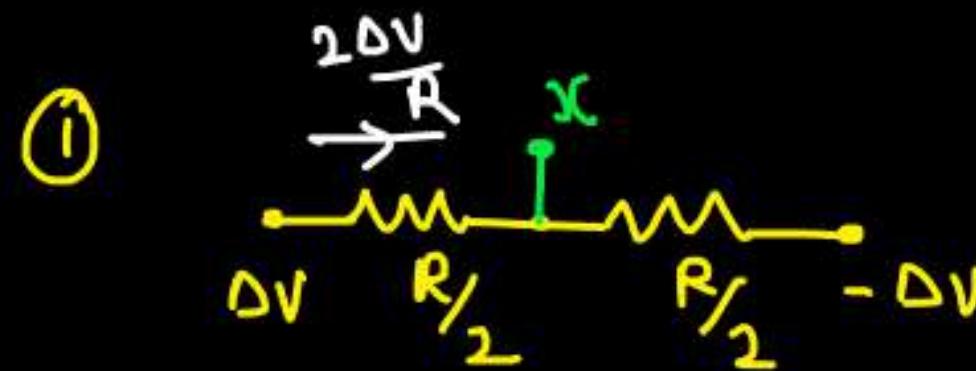


potential @ node x ?

$$\rightarrow V_x = \frac{\Delta V(R/2)}{R} + (-\Delta V)(R/2)$$

$V_x = 0$

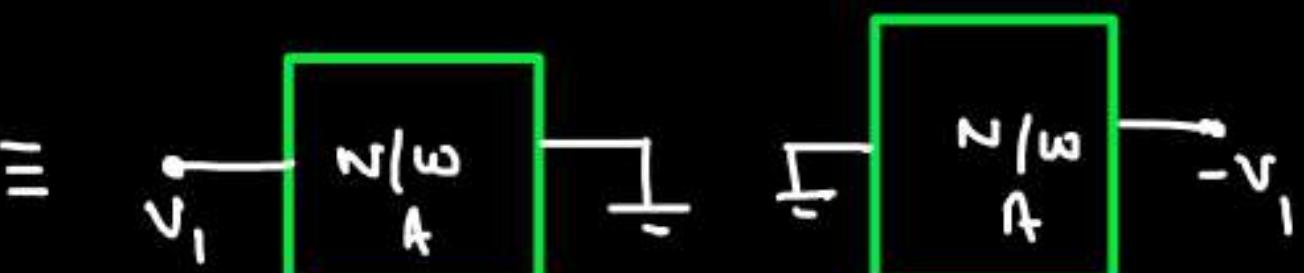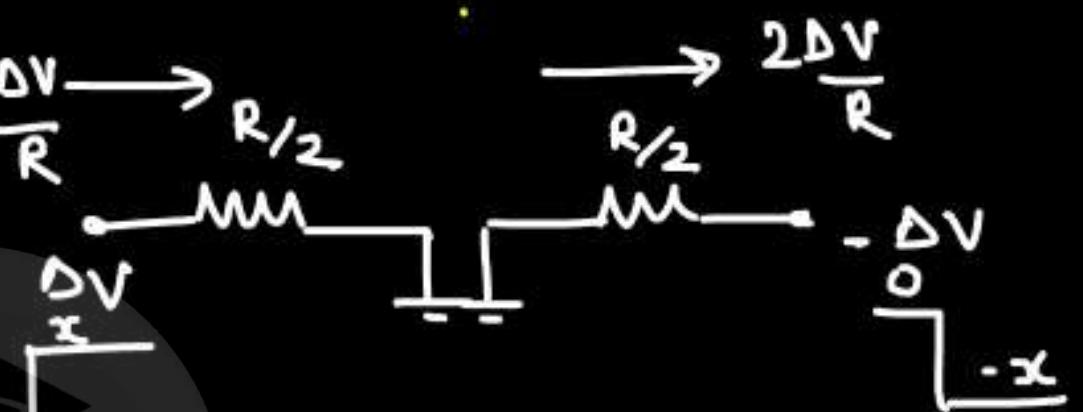
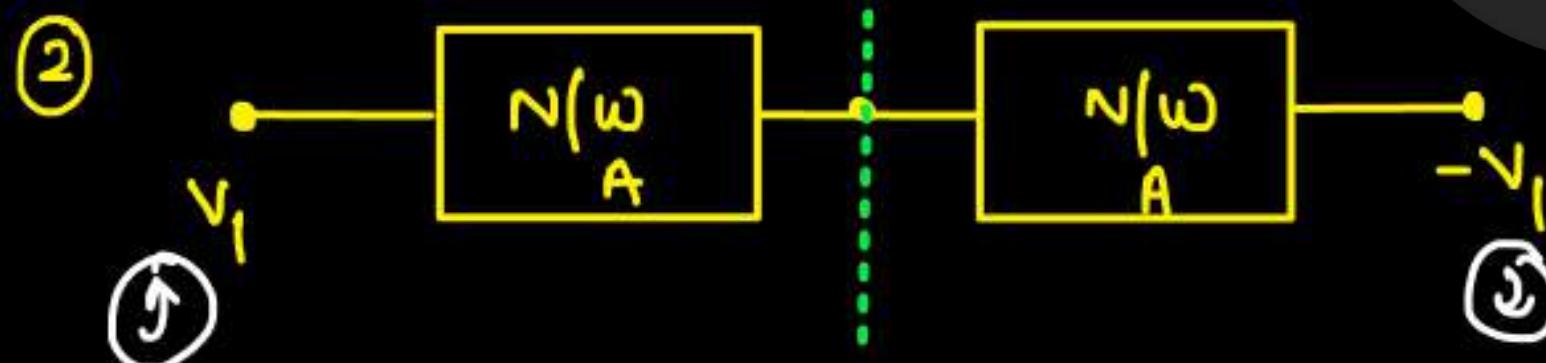


③

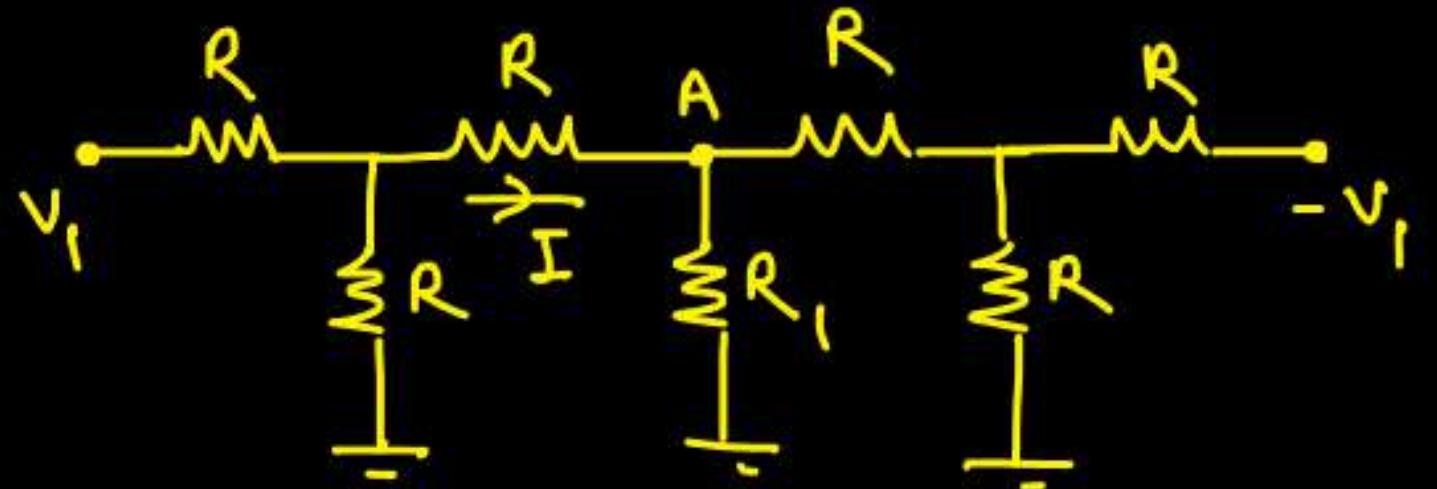


Find the potential @ node A.

Find current I.

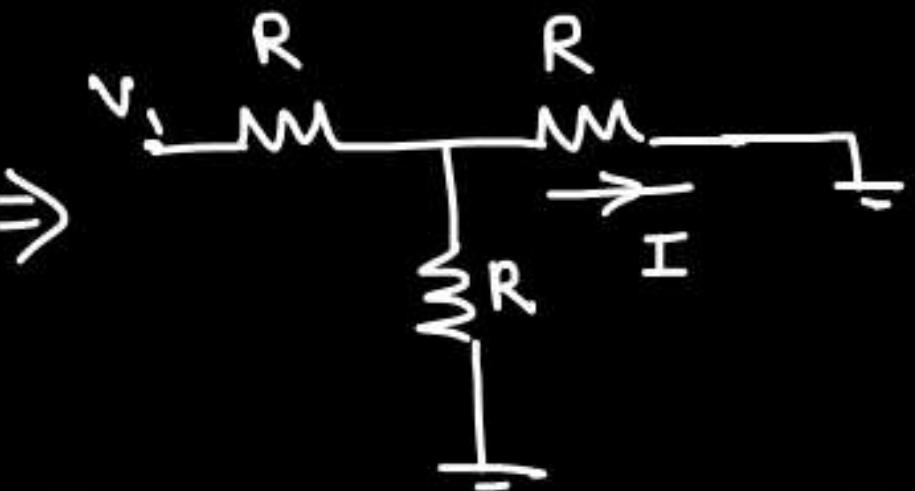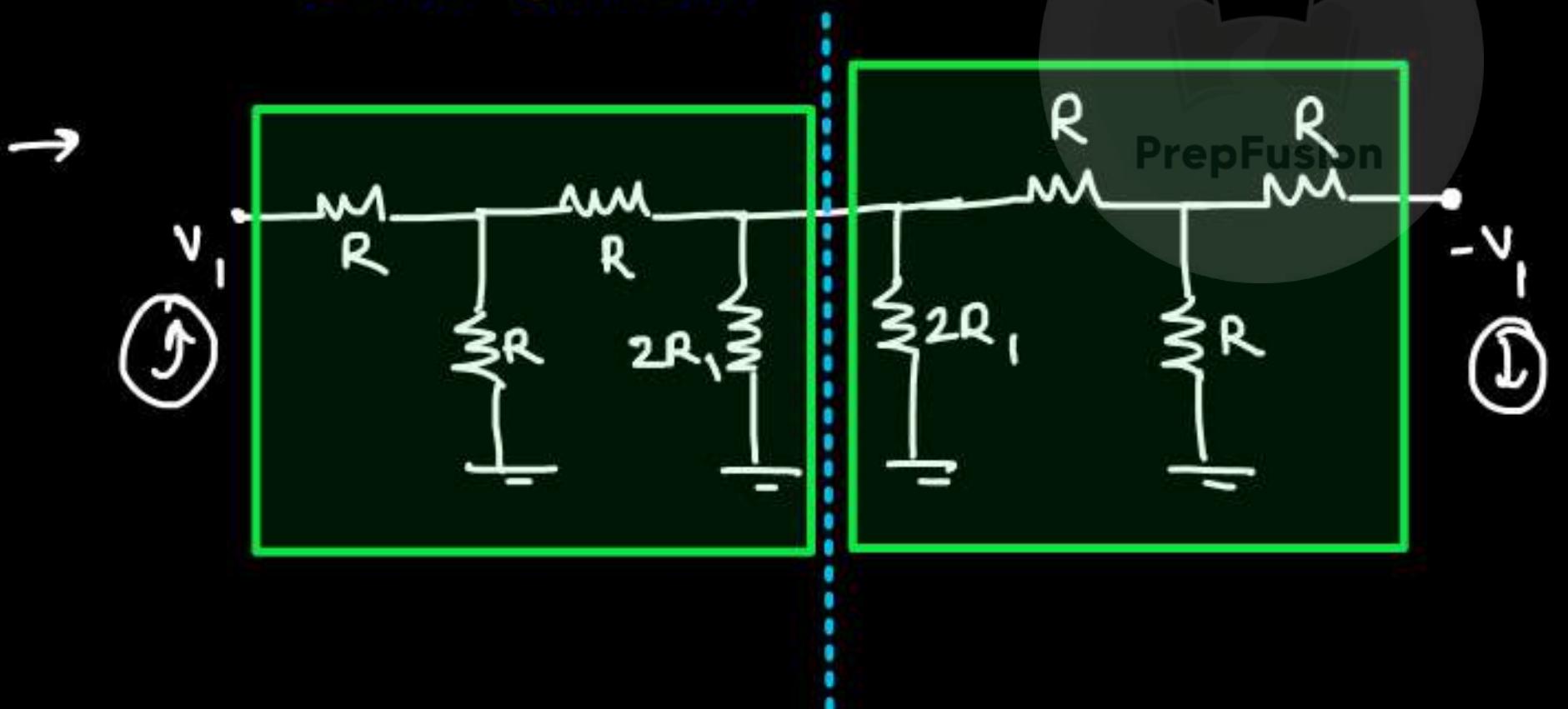


$$I = \frac{2V_1}{3R} \times \frac{1}{2} = \frac{V_1}{3R}$$

④

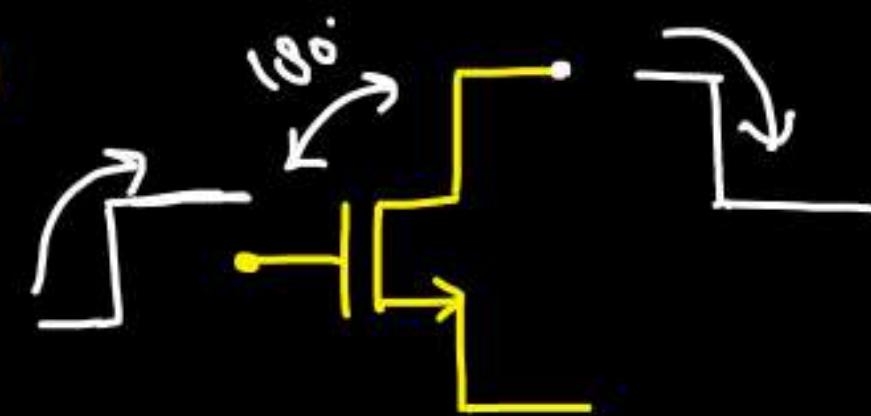

$$A_V = -g_m R_D$$


⑤

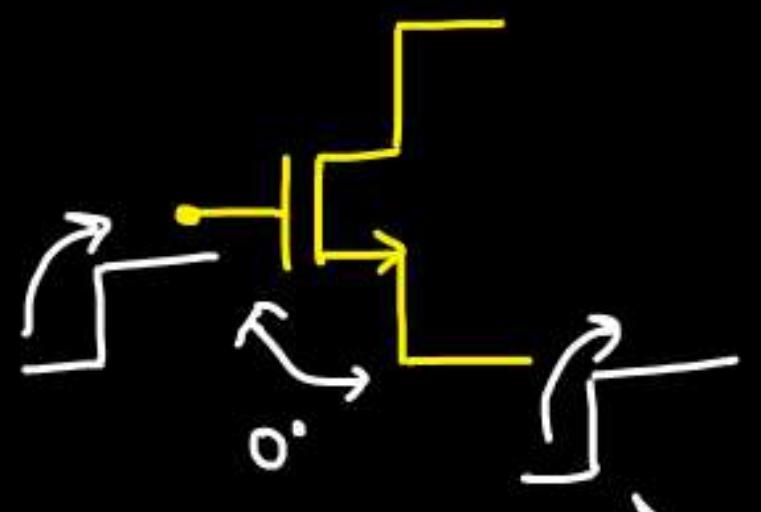

$$A_V = \frac{g_m R_S}{1 + g_m R_S}$$

PrepFusion

⑥

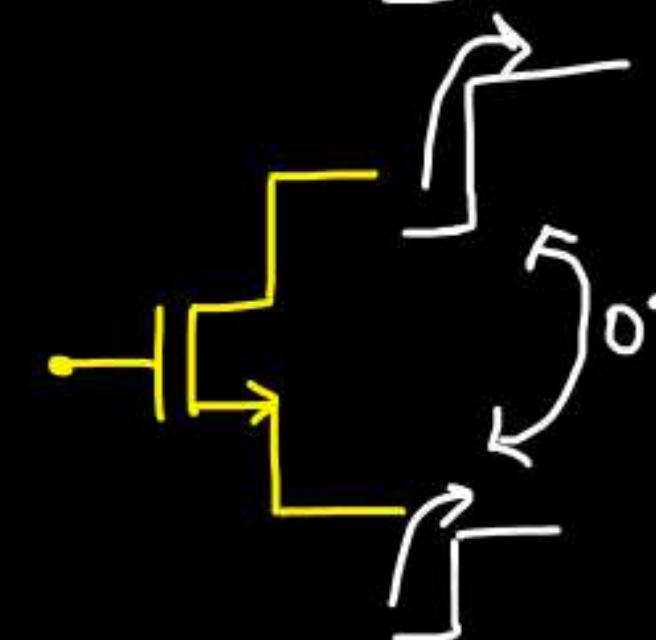


$$A_V = g_m R_D$$

⑦




≡

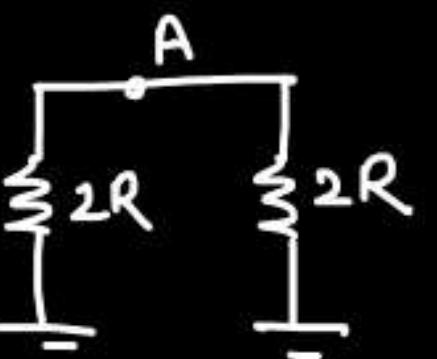


⑧




≡

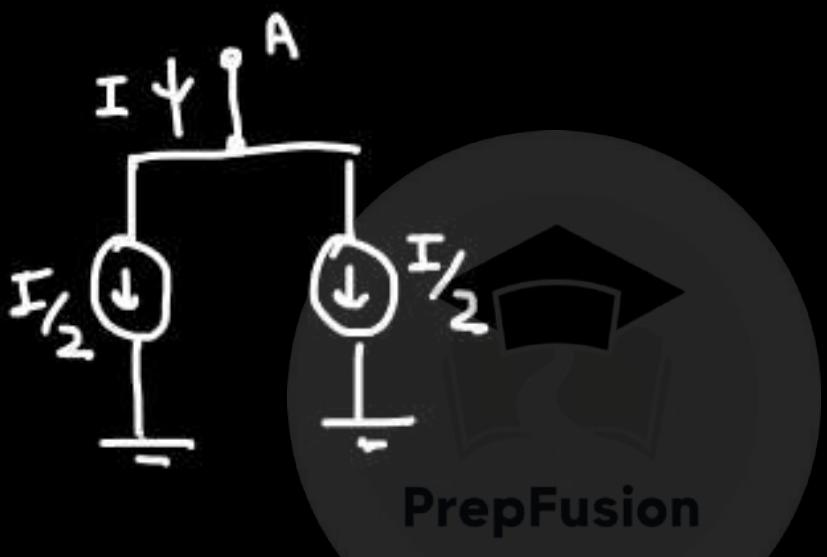


⑨

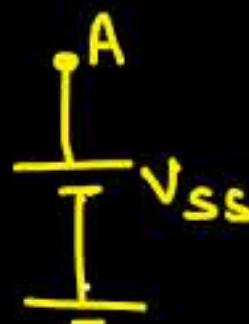


≡

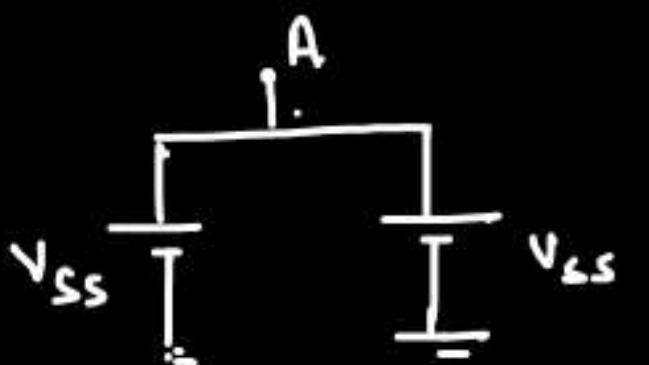


10

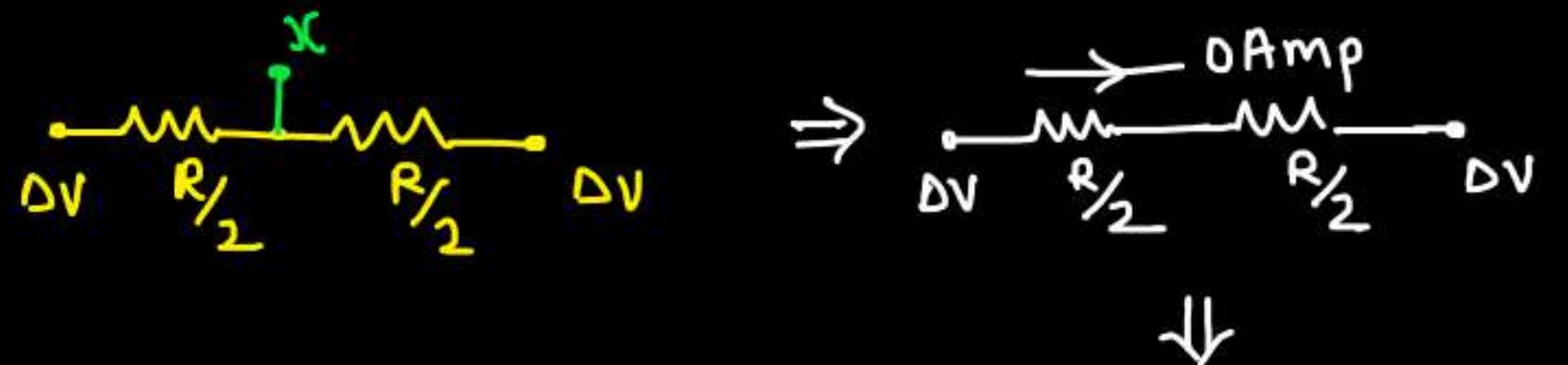

11


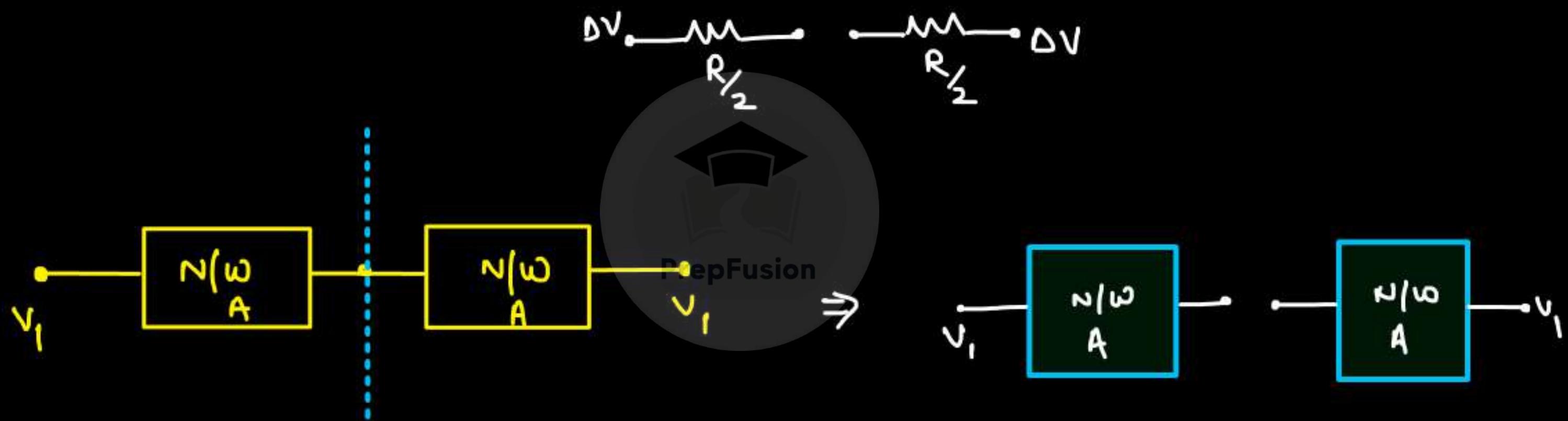


12

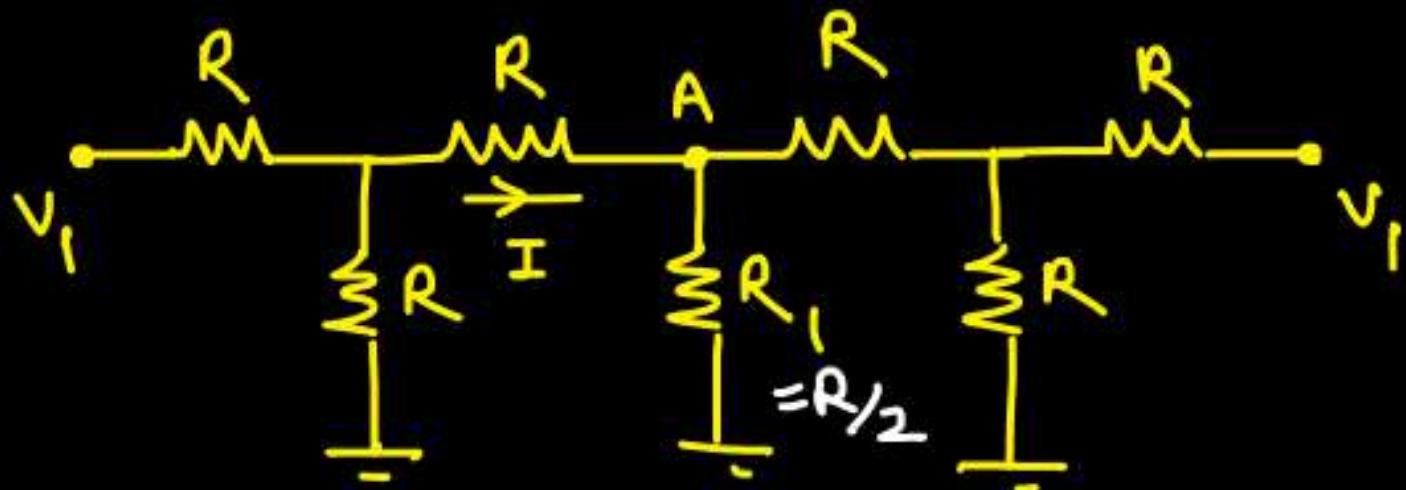

$$R_1 = R/2$$


Find current $I = ?$

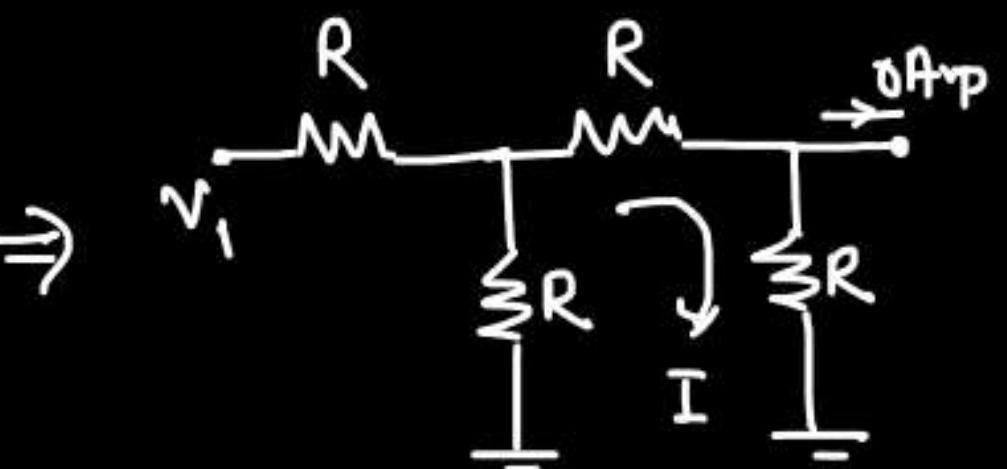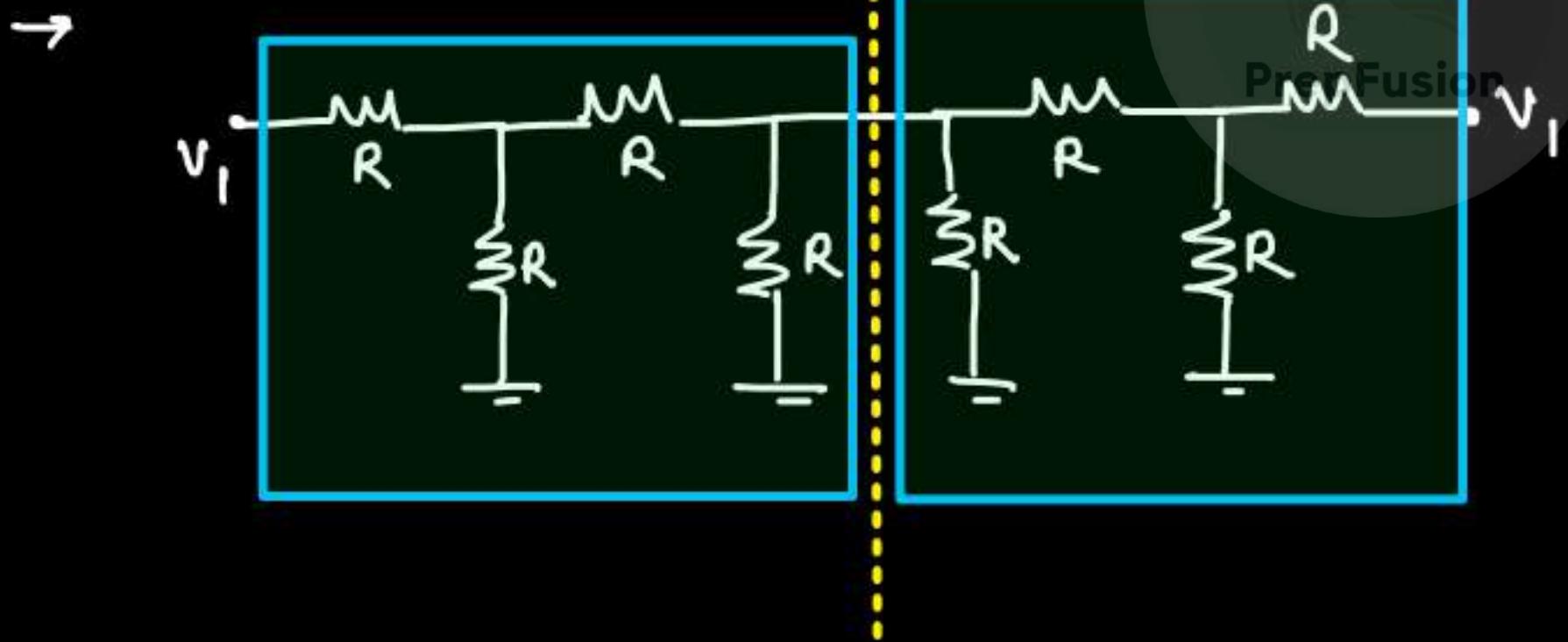

$$I = \frac{3V_1}{5R} \times \frac{R}{3R} = \frac{V_1}{5R}$$


⇒ Concept of Half ckt:-

(a) For Differential Gain:-

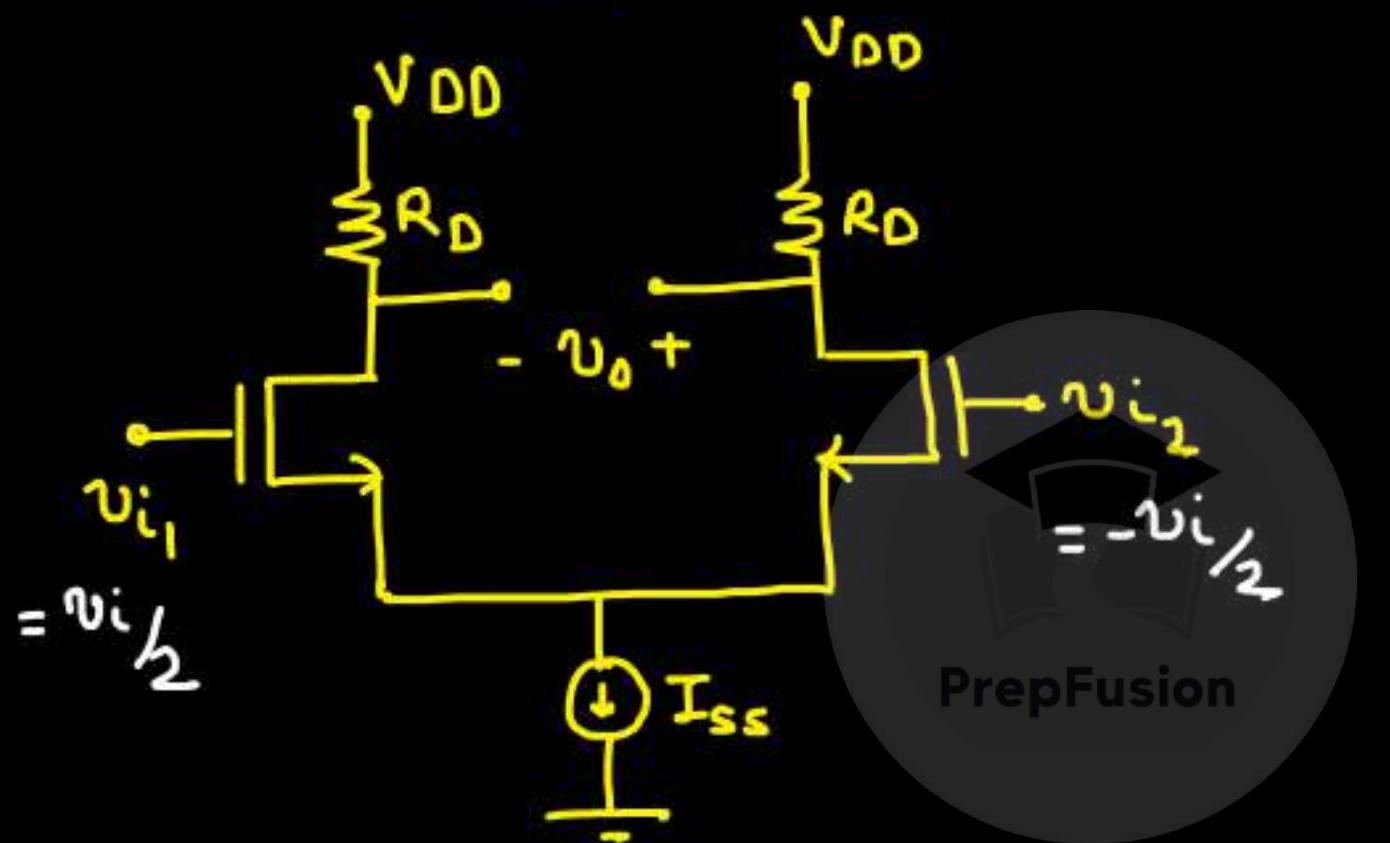


$$v_{i_1} - v_{i_2} = v_{in}$$

Small signal Model :-

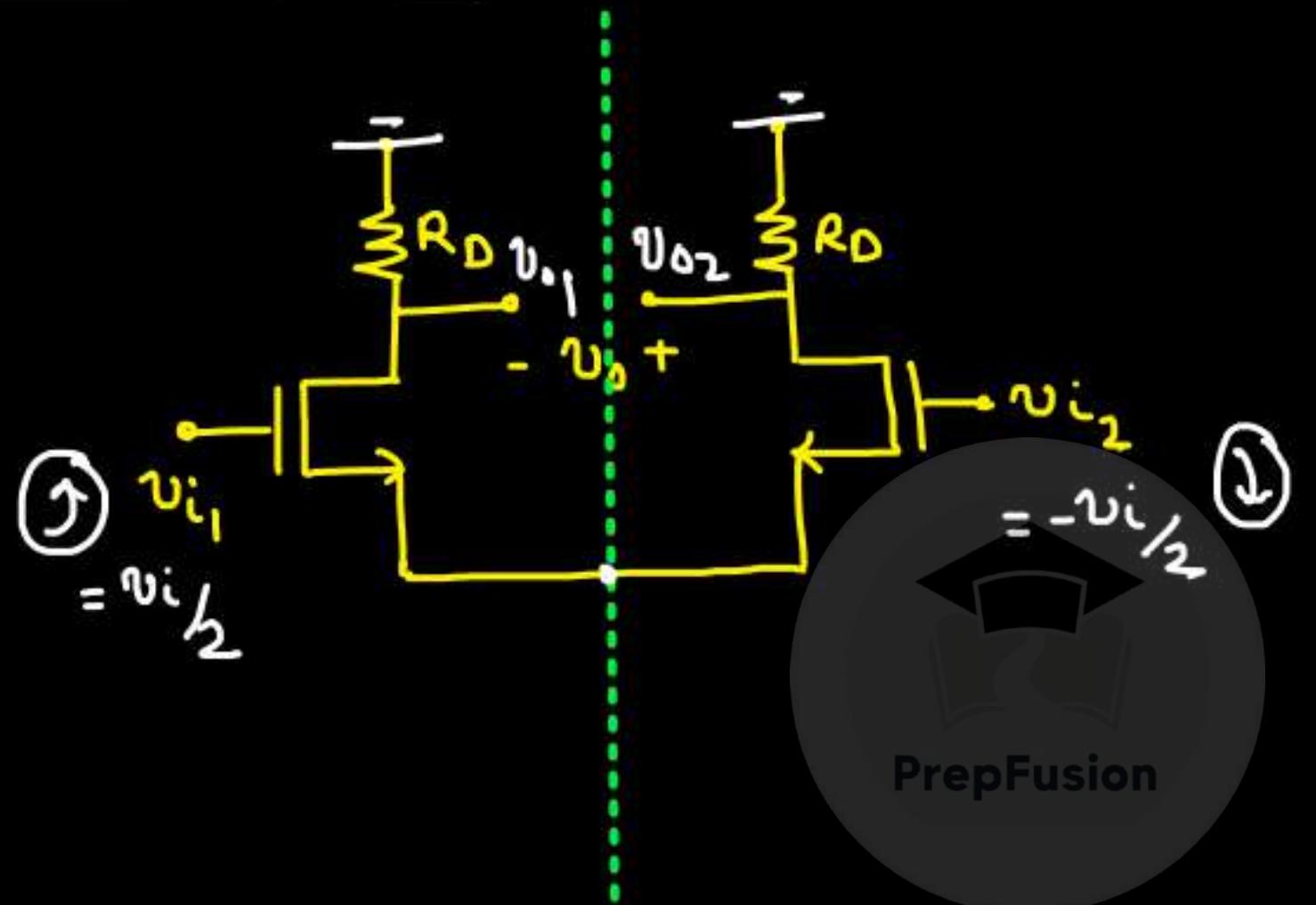

PrepFusion

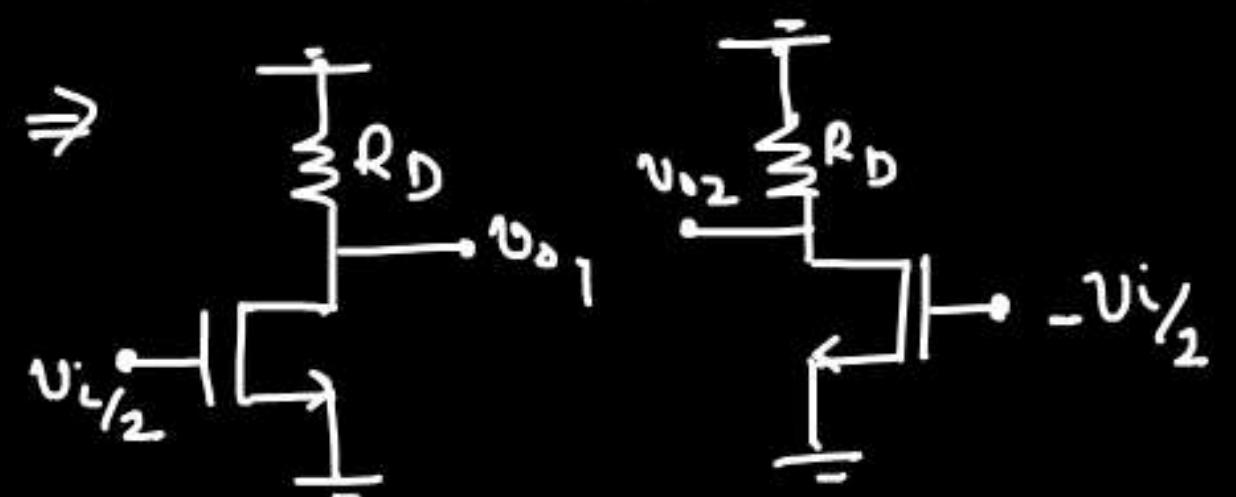


$$v_{o_1} = -g_m R_D v_{i_2}$$

$$v_{o_2} = g_m R_D v_{i_2}$$

$$v_o = g_m R_D v_i$$

$$(\Delta V)_d = g_m R_D$$


For common Mode gain :-

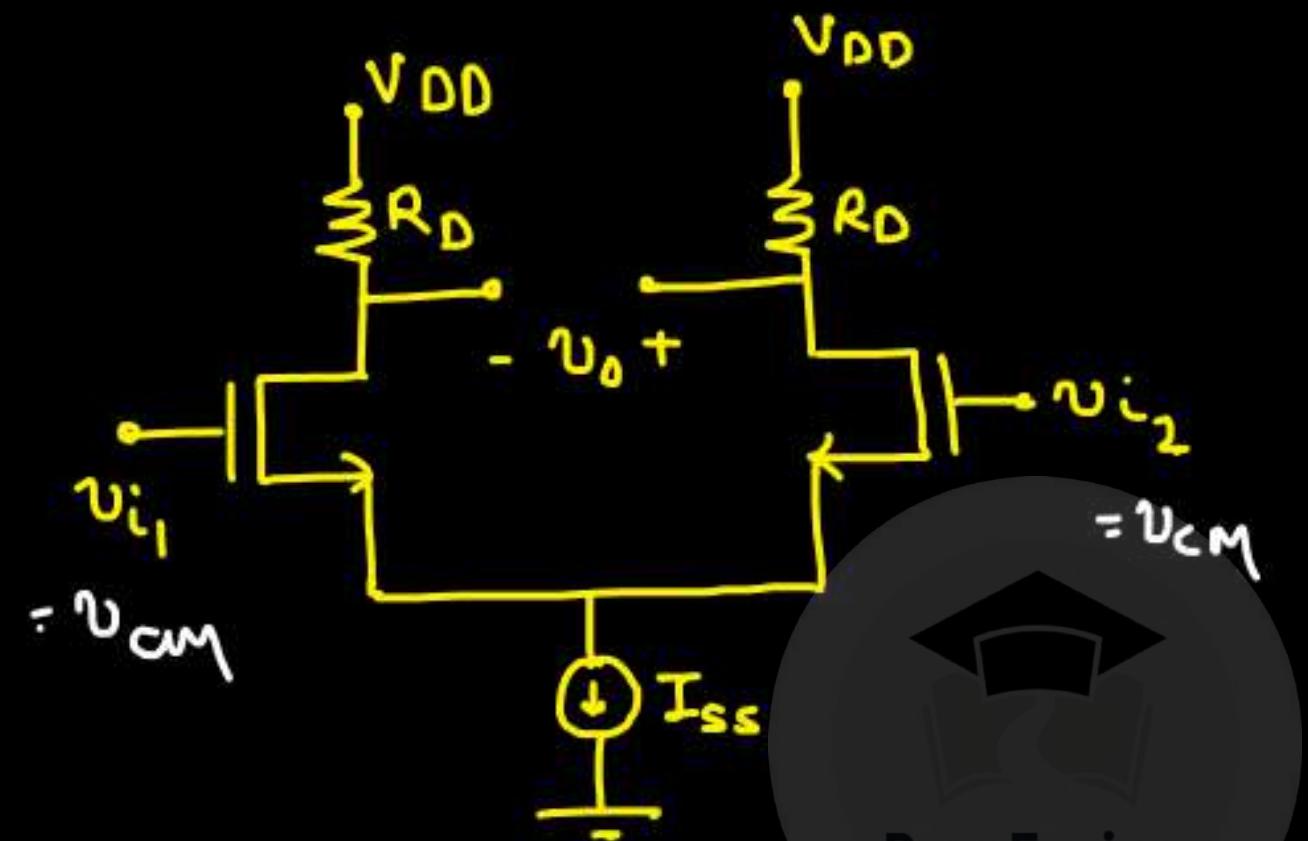

$$U_{i_1} - U_{i_2} = U_{in}$$

PrepFusion

Small Signal Model :-

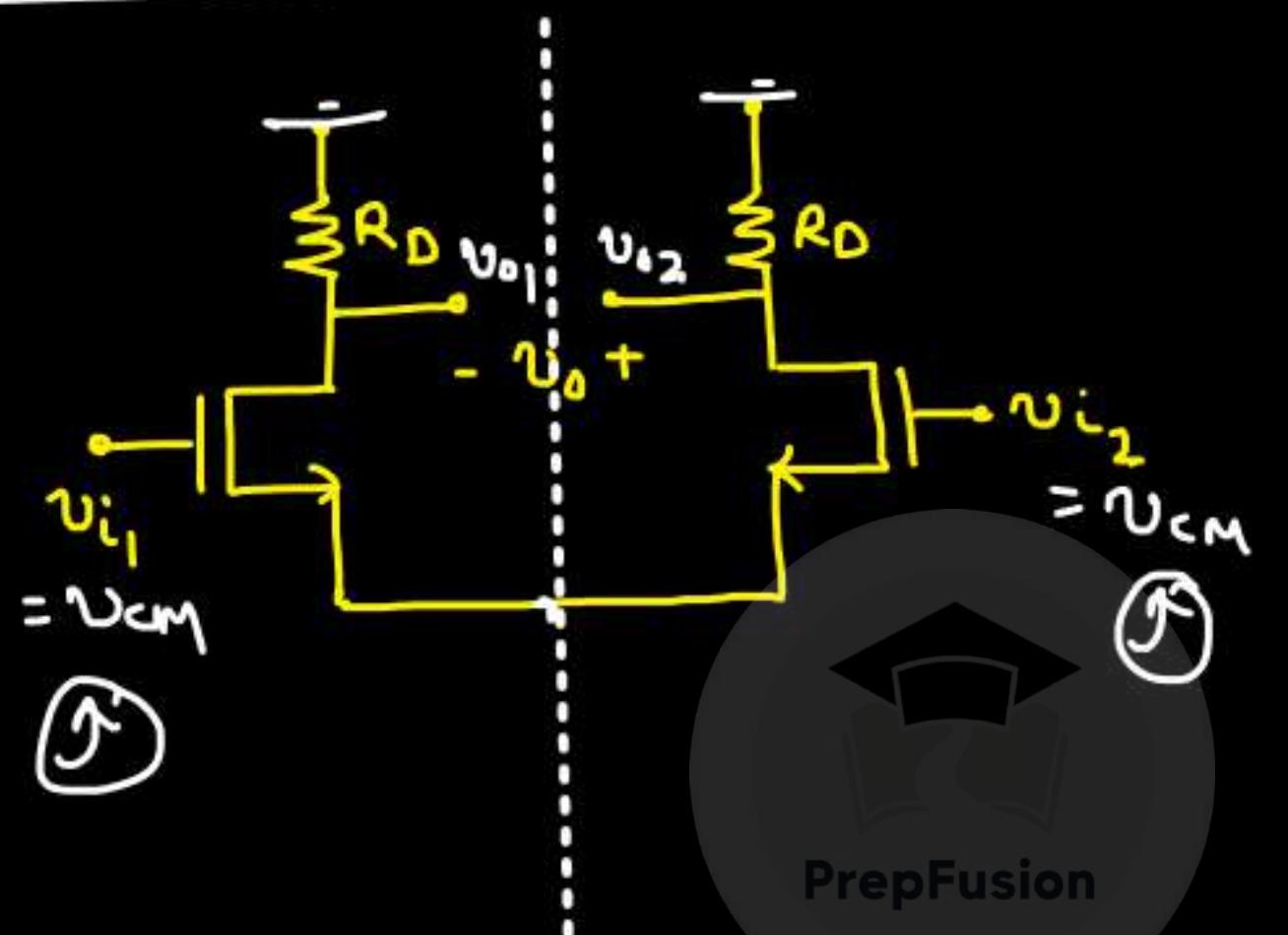


$$(v_o)_{CM} = \frac{v_{o_2} + v_{o_1}}{2}$$

$$(v_i)_{CM} = v_{CM}$$

PrepFusion

Same Half ckt
for CM-DM

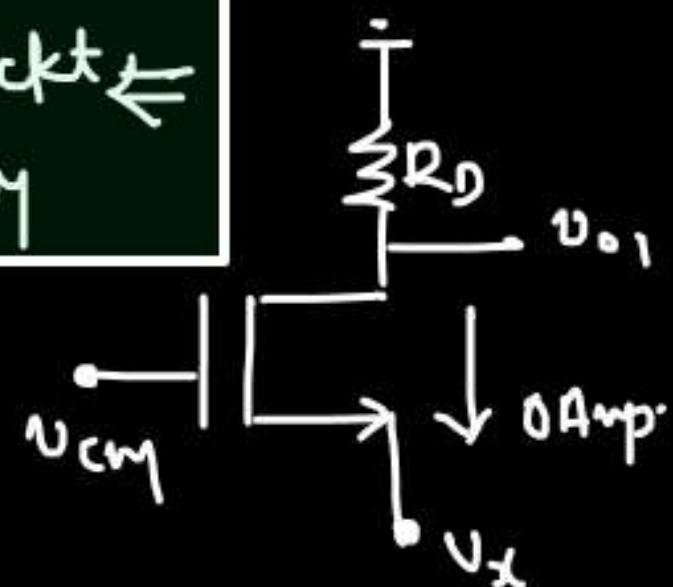

$$v_{o_1} = 0$$


$$v_{o_2} = 0$$

$$(Av)_{CM} = 0$$

$$g_m(v_{CM} - v_x) = 0$$

$$v_x = v_{CM}$$

Q.

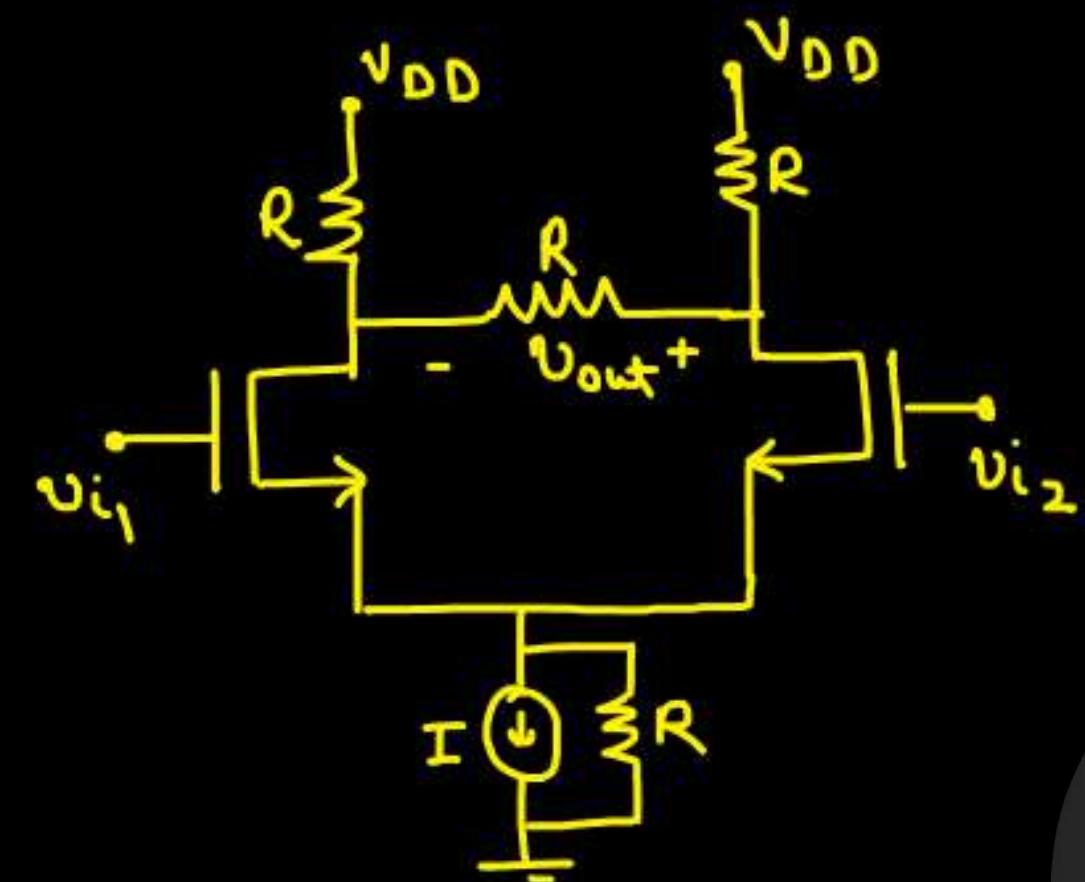


Find


- Differential Gain
- Common-Mode Gain
- Common-Mode Differential Gain
- CMRR

PrepFusion

(q) Differential gain:-

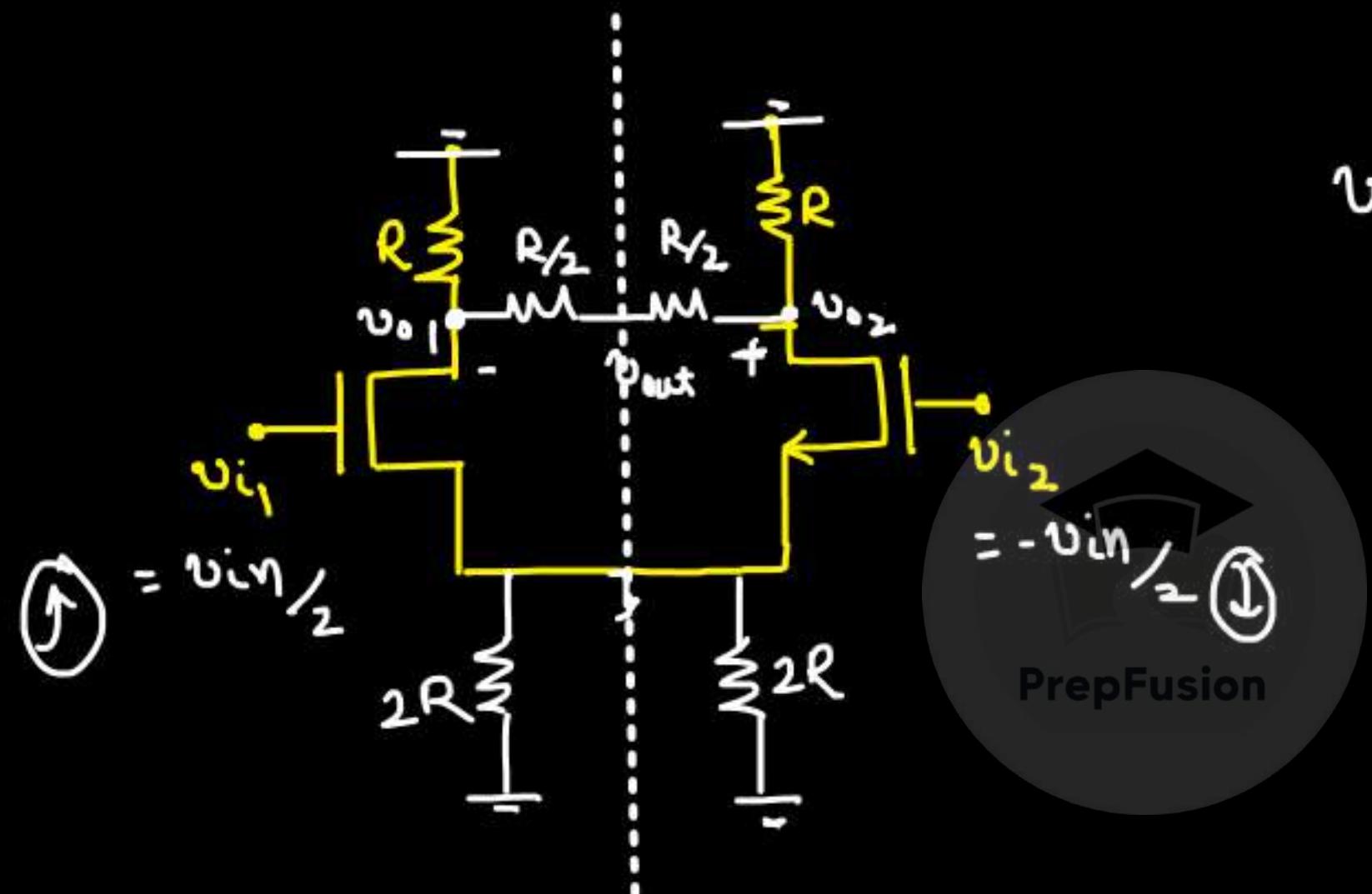

$$v_{out} = v_{o2} - v_{o1}$$

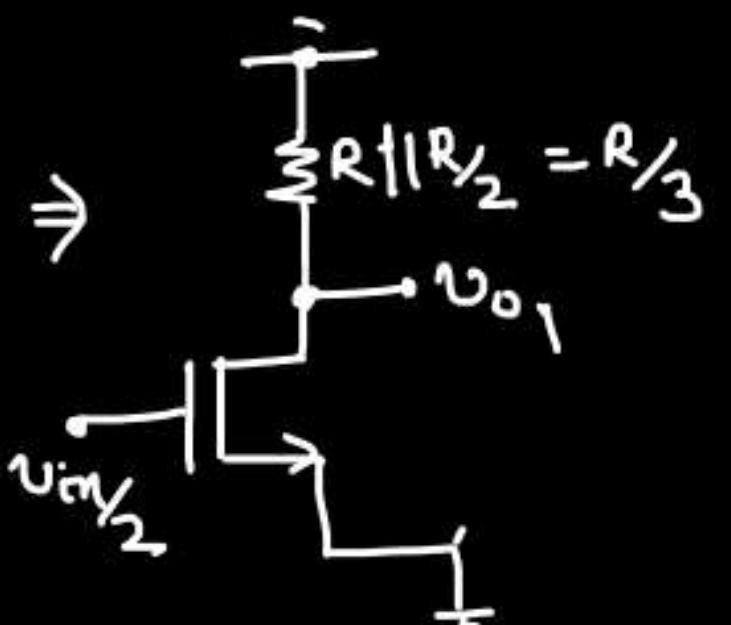

↓

$$\Delta V = g_m R_{\frac{1}{3}}$$

$$\begin{aligned} (v_o)_d &= g_m R_{\frac{1}{3}} v_{in} \\ (v_i)_d &= v_{in} \end{aligned}$$


$$v_{o1} = -g_m R_{\frac{1}{3}} v_{in}$$

$$v_{o2} = g_m R_{\frac{1}{3}} v_{in}$$

(b) Common Mode gain :-

$$(v_o)_{CM} = \frac{v_{o_1} + v_{o_2}}{2}$$

$$(v_i)_{CM} = v_{CM}$$

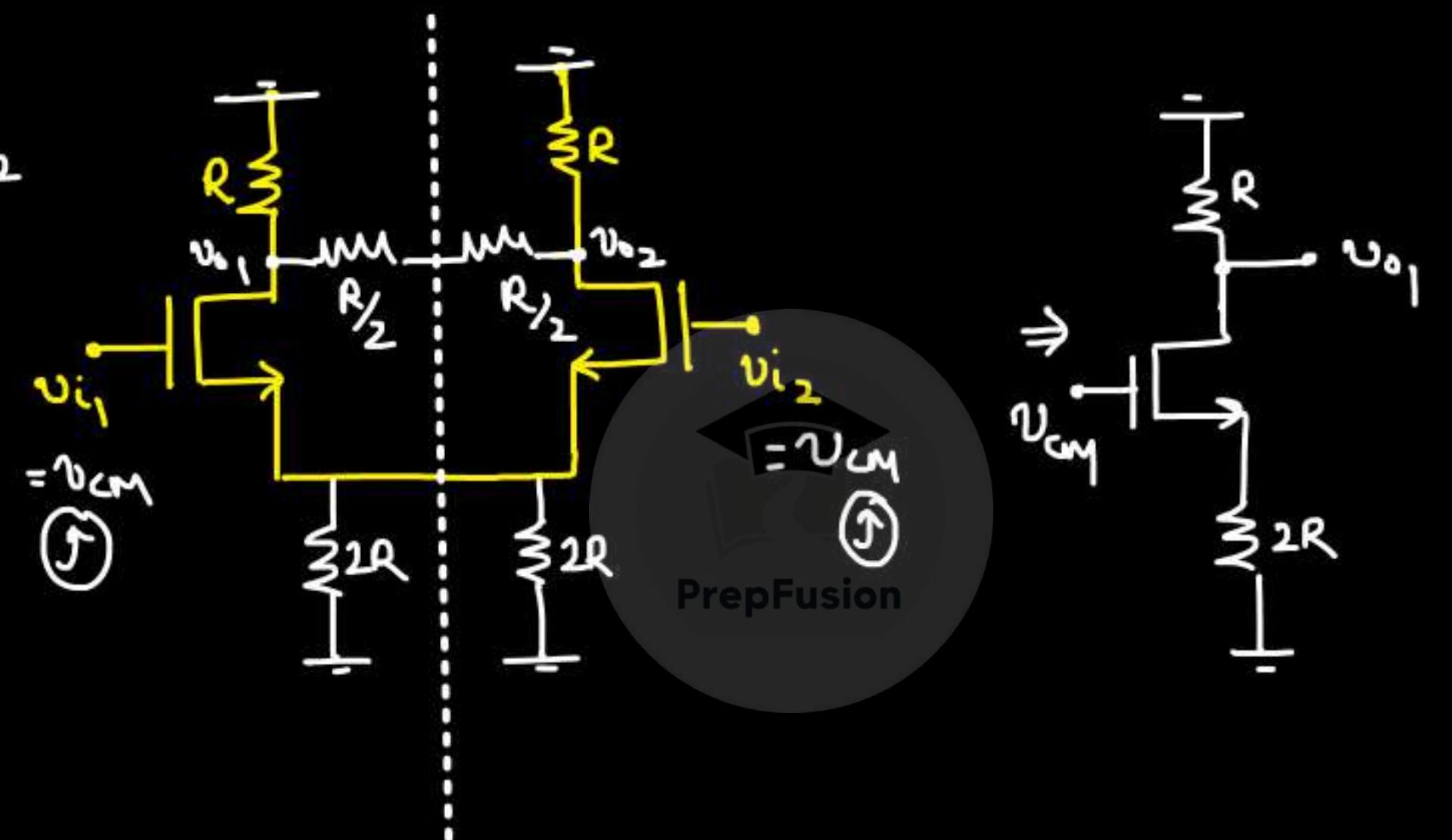

$$(\Delta v)_{CM} = -\frac{g_m R}{1 + 2g_m R}$$

$$(v_o)_{CM} = -\frac{g_m R}{1 + 2g_m R} v_{CM}$$

$$v_{o_1} = -\frac{g_m R}{1 + 2g_m R} v_{CM}$$

$$v_{o_2} = -\frac{g_m R}{1 + 2g_m R} v_{CM}$$

(c) Common Mode Differential Gain :-


$$(V_o)_{CM-DM} = V_{o_2} - V_{o_1}$$
$$= 0$$

$$(\Delta v)_{CM-DM} = 0$$



⇒ Large Signal Analysis of differential amplifier:-

(DC)

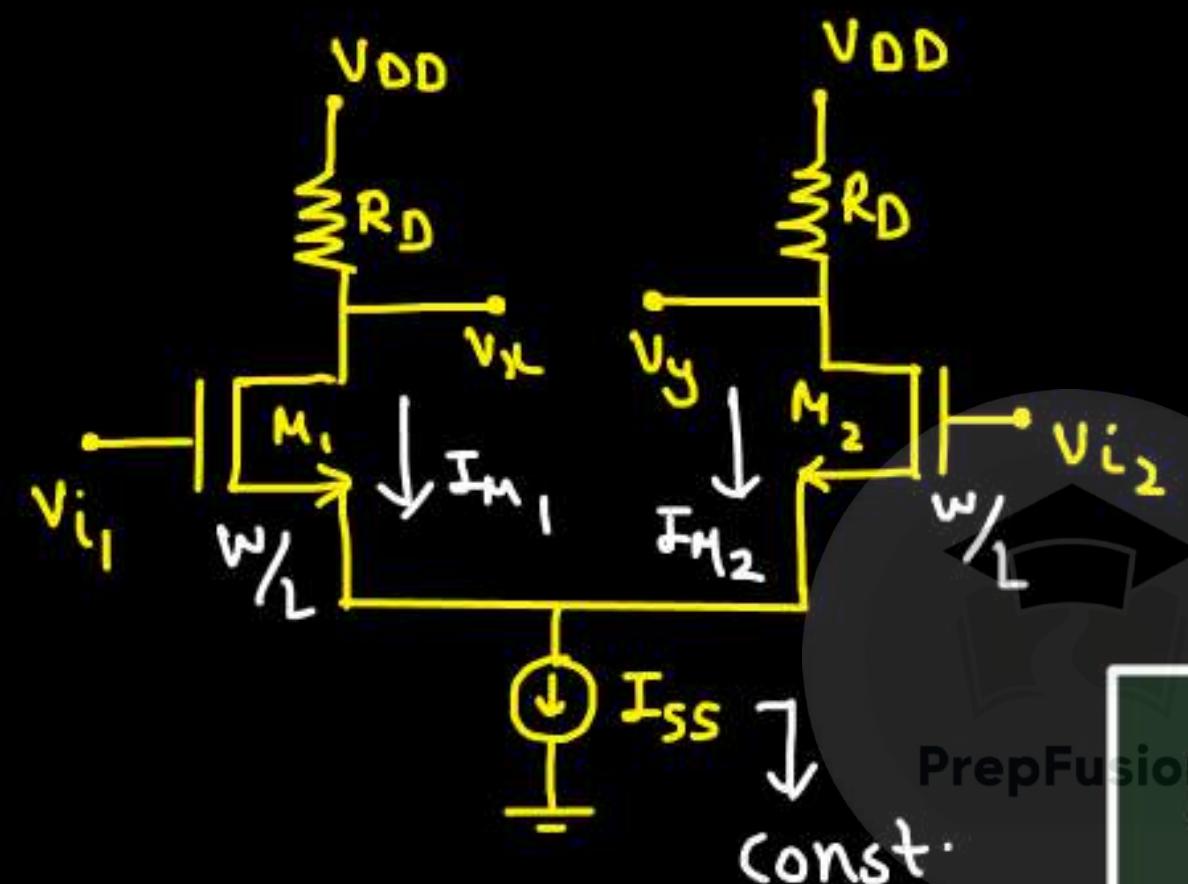

$$I_{M_1} + I_{M_2} = I_{SS}$$

$$V_x = V_{DD} - I_{M_1} R_D$$

$$V_y = V_{DD} - I_{M_2} R_D$$

Let

@ some $V_{i_1} = V_a \Rightarrow I_{M_1} = I_{SS}, I_{M_2} = 0 \text{ A.P.}$

$$V_x = V_{DD} - I_{SS} R_D$$

$$V_y = V_{DD}$$


$$V_{xy} = - I_{SS} R_D$$

PrepFusion

if $V_{i_1} \uparrow \Rightarrow I_{M_1} \uparrow \Rightarrow V_x \downarrow$

\downarrow
 $I_{M_2} \downarrow \Rightarrow V_y \uparrow$

$$V_{xy} = V_x - V_y$$

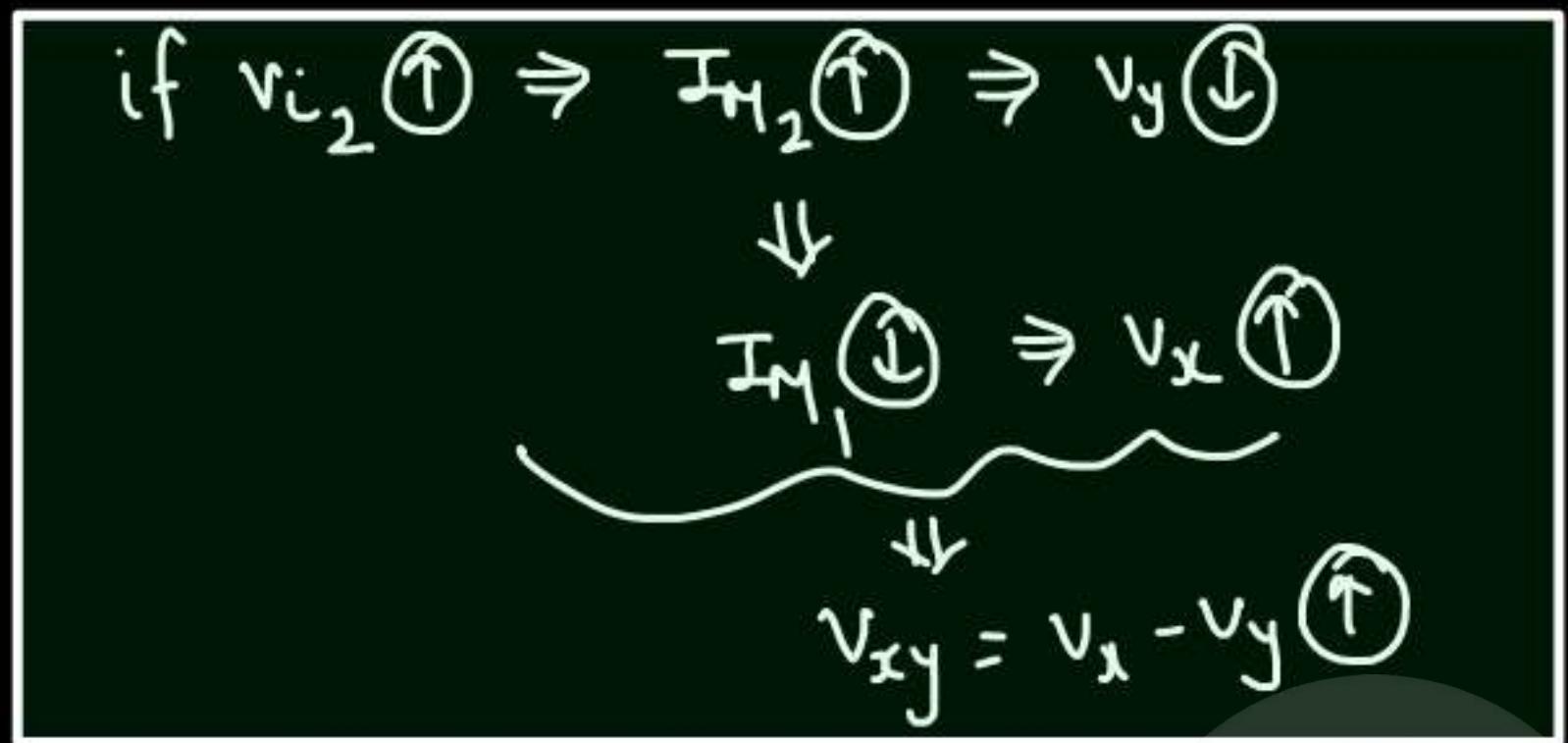

let @ Some $V_{i_1} = V_b$

$$I_{M_2} = I_{ss}$$


\downarrow

$$I_{M_1} = 0 \text{ Amp}$$

$$V_y = V_{DD} - I_{ss} R_D$$

$$V_x = V_{DD}$$

$$V_{xy} = I_{ss} R_D$$

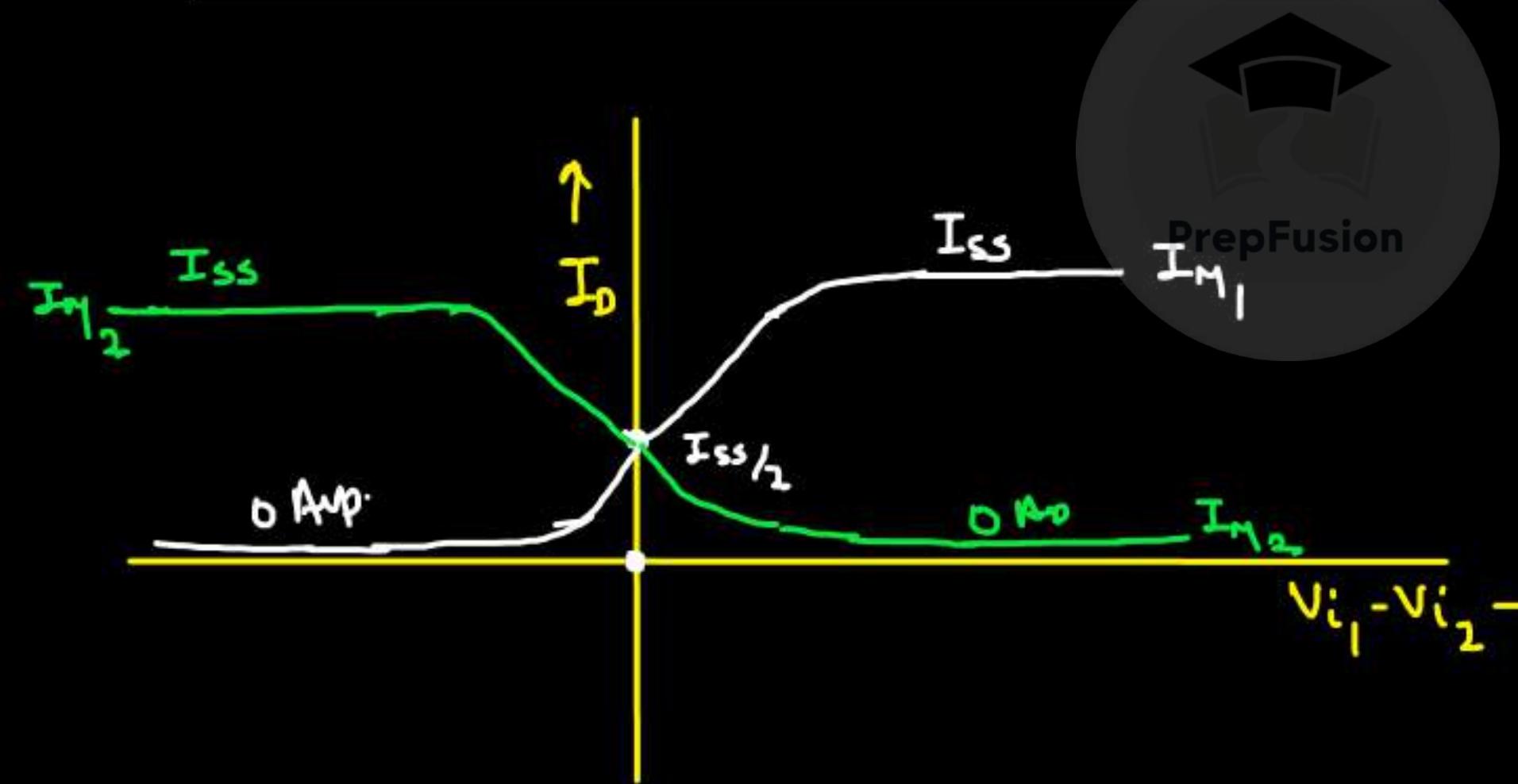


if $V_{i_1} - V_{i_2} > 0$

$\Rightarrow V_{i_1} > V_{i_2}$

if $V_{i_1} - V_{i_2} < 0$

$\Rightarrow V_{i_1} < V_{i_2}$

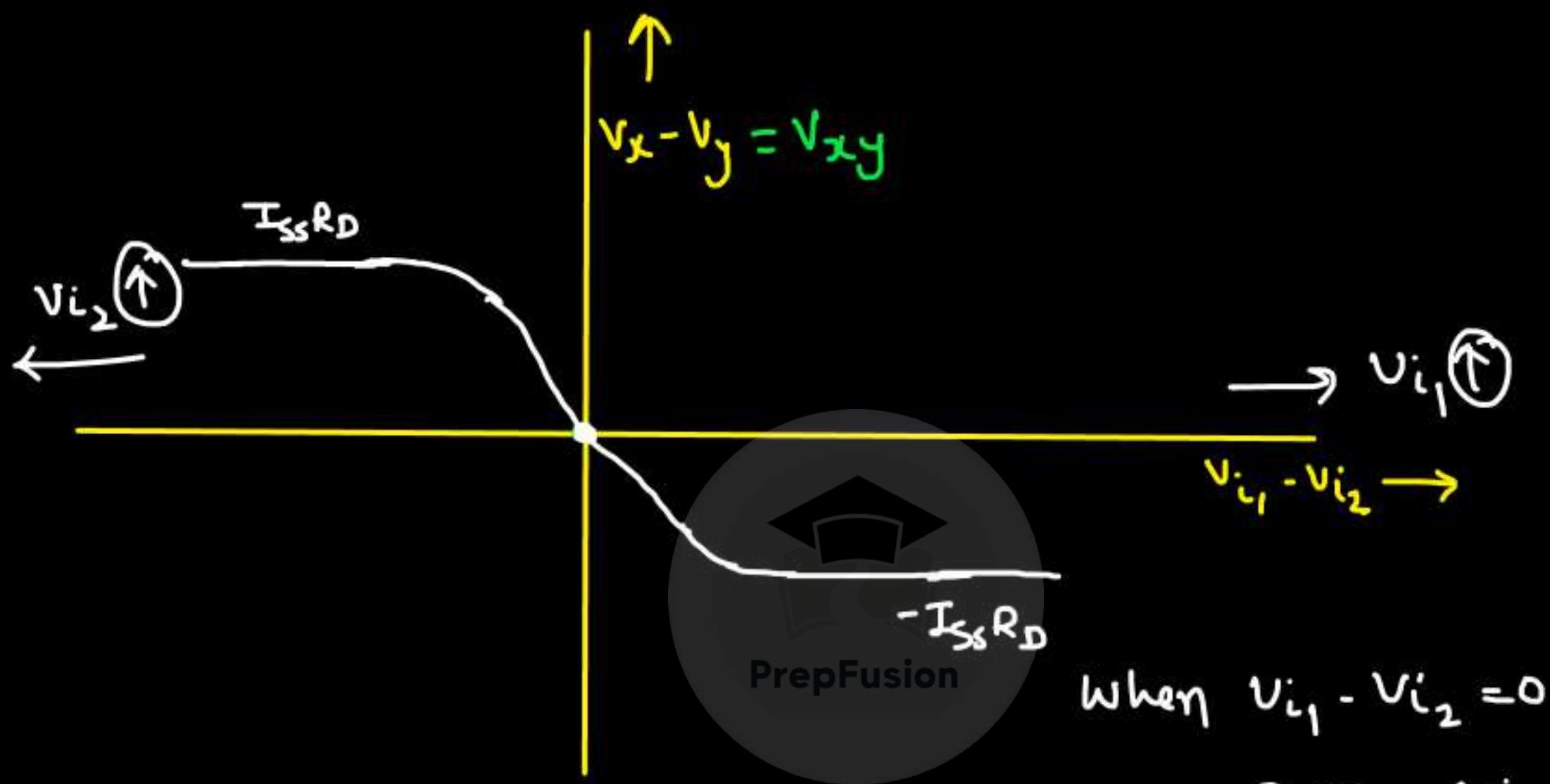

if $V_{i_1} > V_{i_2} \Rightarrow V_x < V_y \Rightarrow V_{xy} = -ve$

if $V_{i_2} > V_{i_1} \Rightarrow V_x > V_y \Rightarrow V_{xy} = +ve$

when $V_{i_1} - V_{i_2} = 0$

$\Rightarrow V_{i_1} = V_{i_2} \Rightarrow I_{M_1} = I_{M_2} = I_M$


$$V_x = V_{DD} - I_M R_D$$

$$V_y = V_{DG} - I_M R_D$$

$$V_{xy} = 0$$

Assignment - 11

Q.

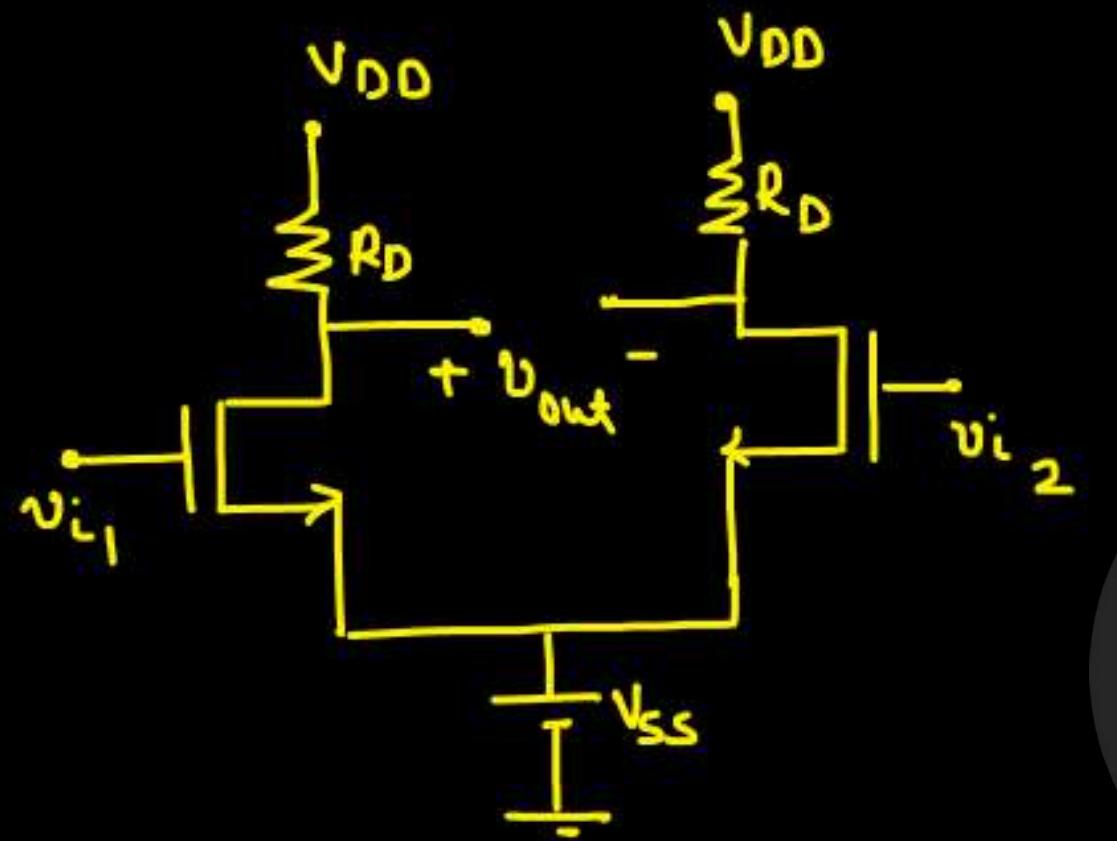

Find


(a) Differential gain

(b) Common-Mode gain

$$v_{i1} - v_{i2} = 2v_{in}$$

PrepFusion

⇒ (a)

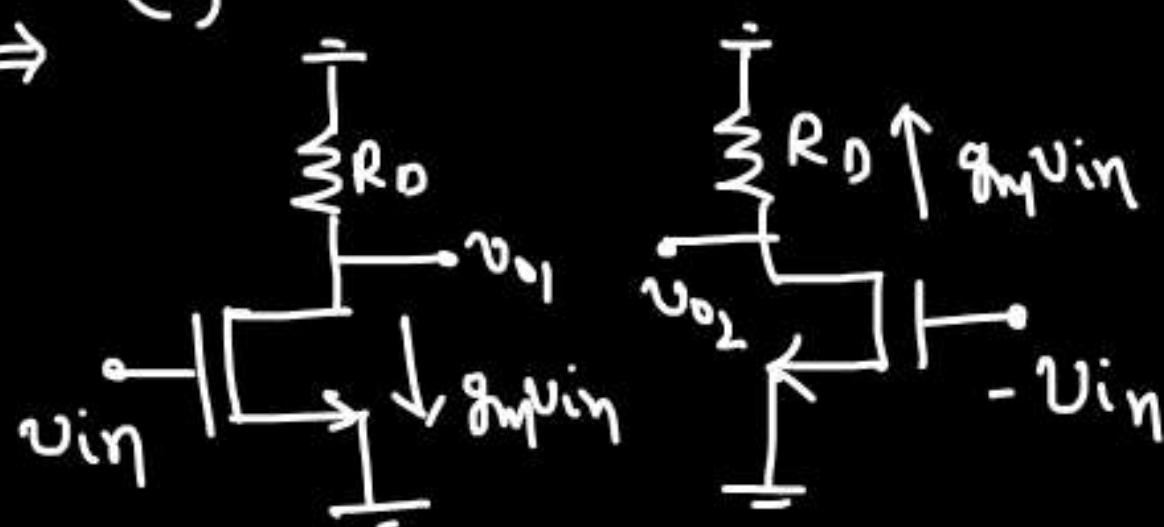

$$v_{o1} = -g_m R_D v_{in}$$


$$v_{o2} = g_m R_D v_{in}$$

$$(v_o)_d = v_{o1} - v_{o2} = -2g_m R_D v_{in}$$

$$(v_i)_d = 2v_{in}$$

$$(\partial v) = -g_m R_D$$

(b)

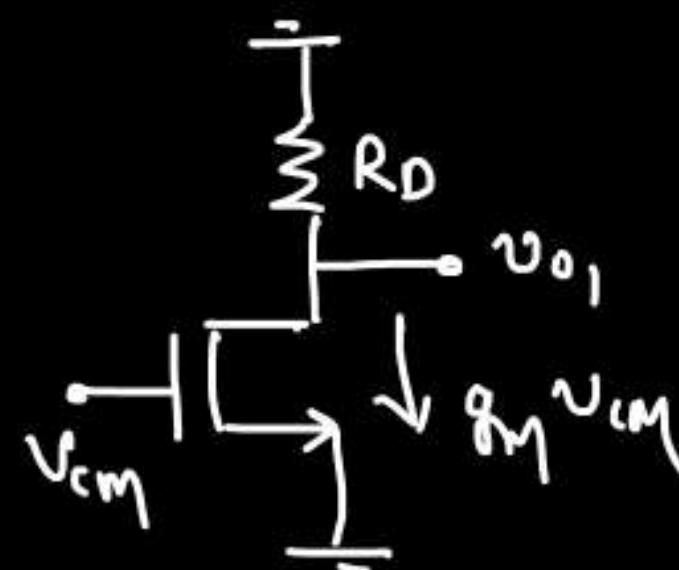

$$v_{o1} = -g_M R_D v_{cm}$$


$$v_{o2} = -g_M R_D v_{cm}$$

$$(A_v)_{cm} = -g_M R_D v_{cm}$$

$$(Av)_{cm} = -g_M R_D$$

PrepFusion


Q. 2

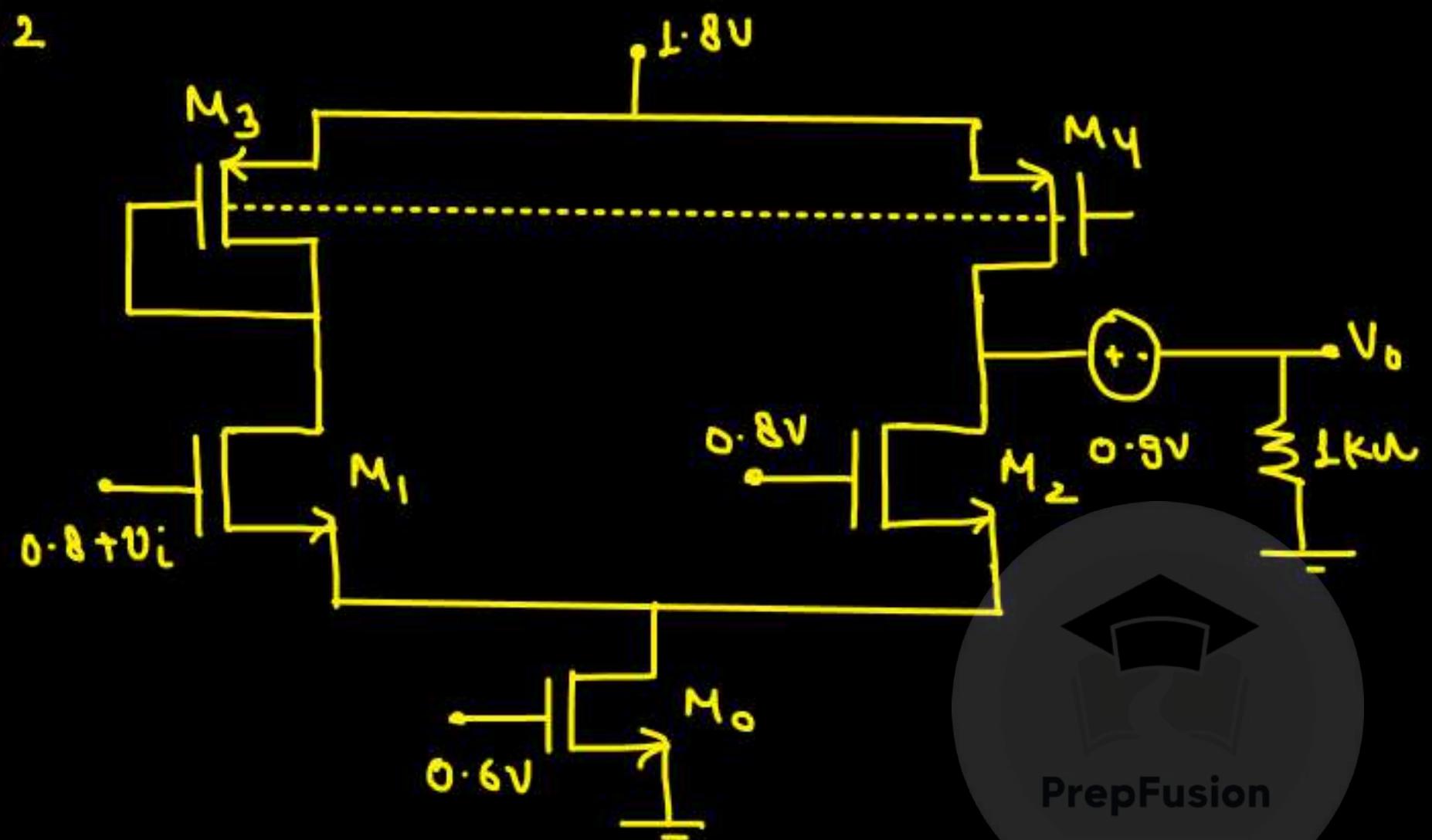

$M_0 - M_4$ all are biased in sat. region.

For all Transistors $\delta_m = 25\text{mS}$, $\lambda = 0$

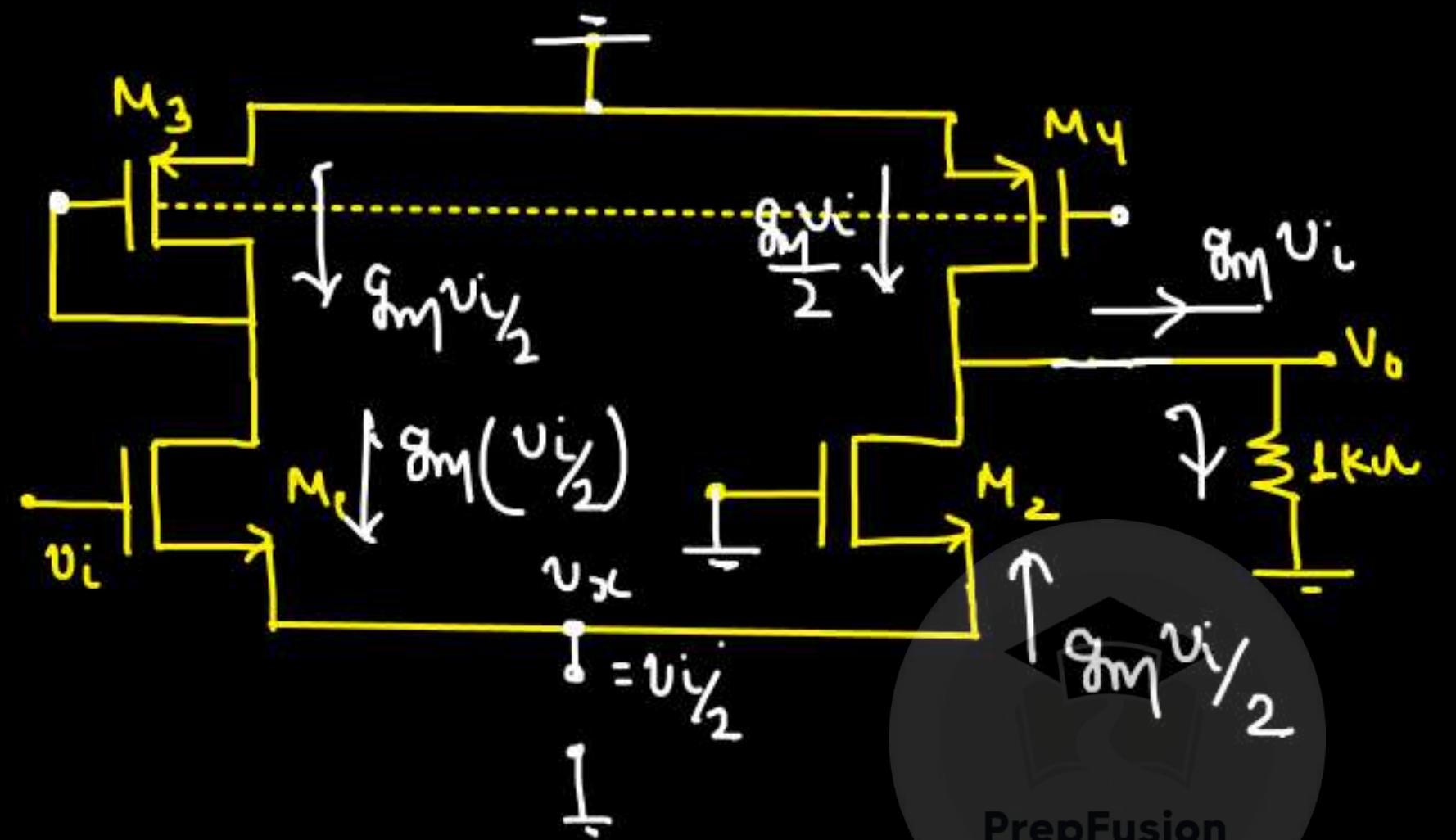Find small signal voltage gain $(\frac{V_o}{v_i})$



$$g_m(v_i - v_x) = g_m v_x$$

$v_x = v_{y1/2}$

PrepFusion

for M_3 and M_4
both g_m & v_{gs} are
same

$$\Rightarrow (i_a)_{M_3} = (i_a)_{M_4}$$


$$V_o = g_m V_i (1k \Omega)$$

$$\frac{V_o}{V_i} = 25m (1k)$$

$$\frac{V_o}{V_i} = 25 \text{ v/V}$$




Q.

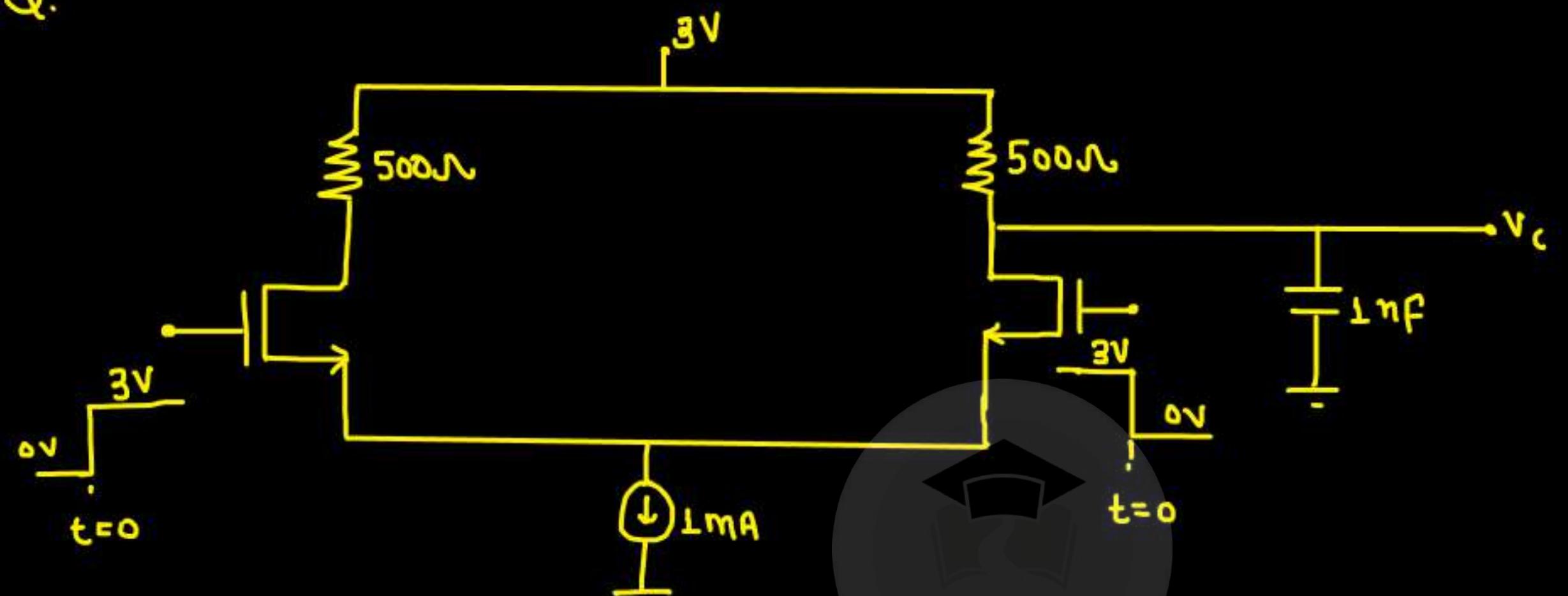

Find the time at which V_c node reaches to 2.9V

for $t < 0$:-

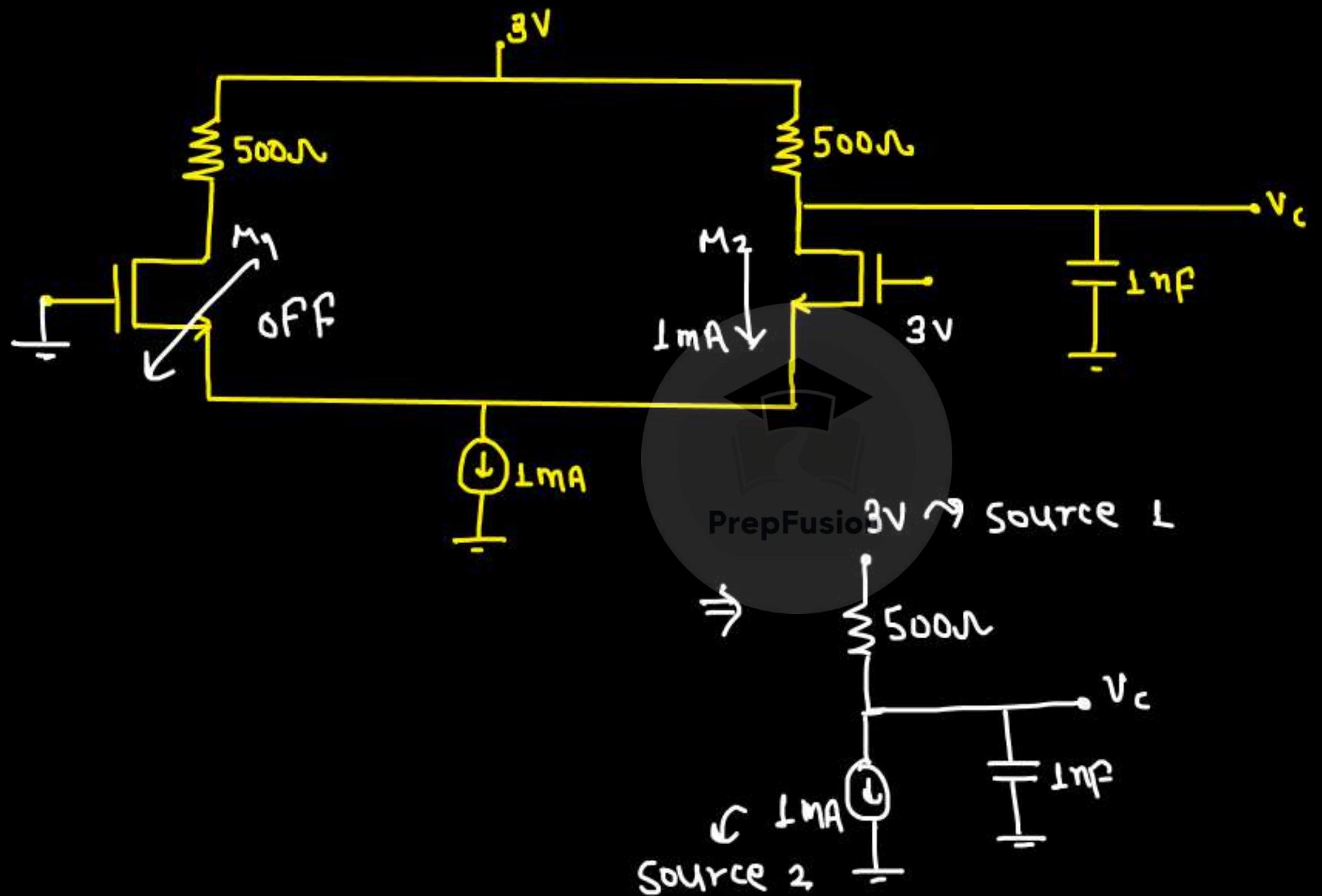


$$v_c(-\infty) = 0V$$


$$v_c(0^+) =$$

$$V_C = 0^\circ \quad (\text{S.S.})$$


@ S.S. \Rightarrow Cap. $0^\circ C$

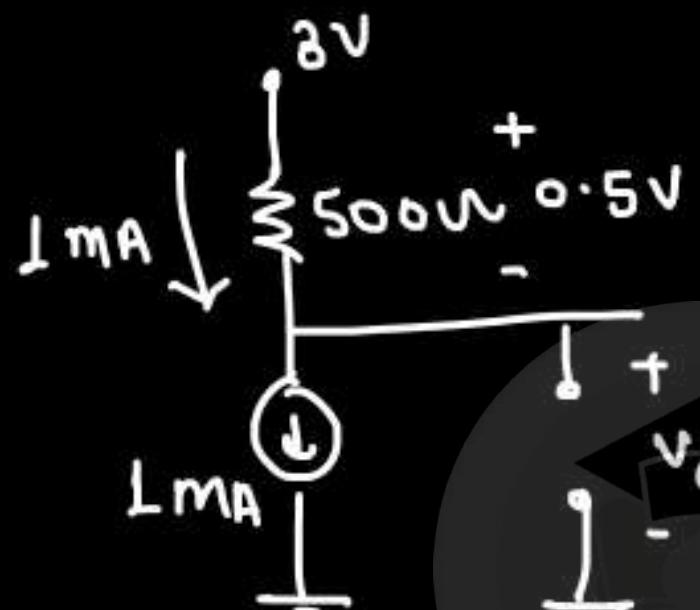


$$V_C(0^\circ) = 2.5V$$

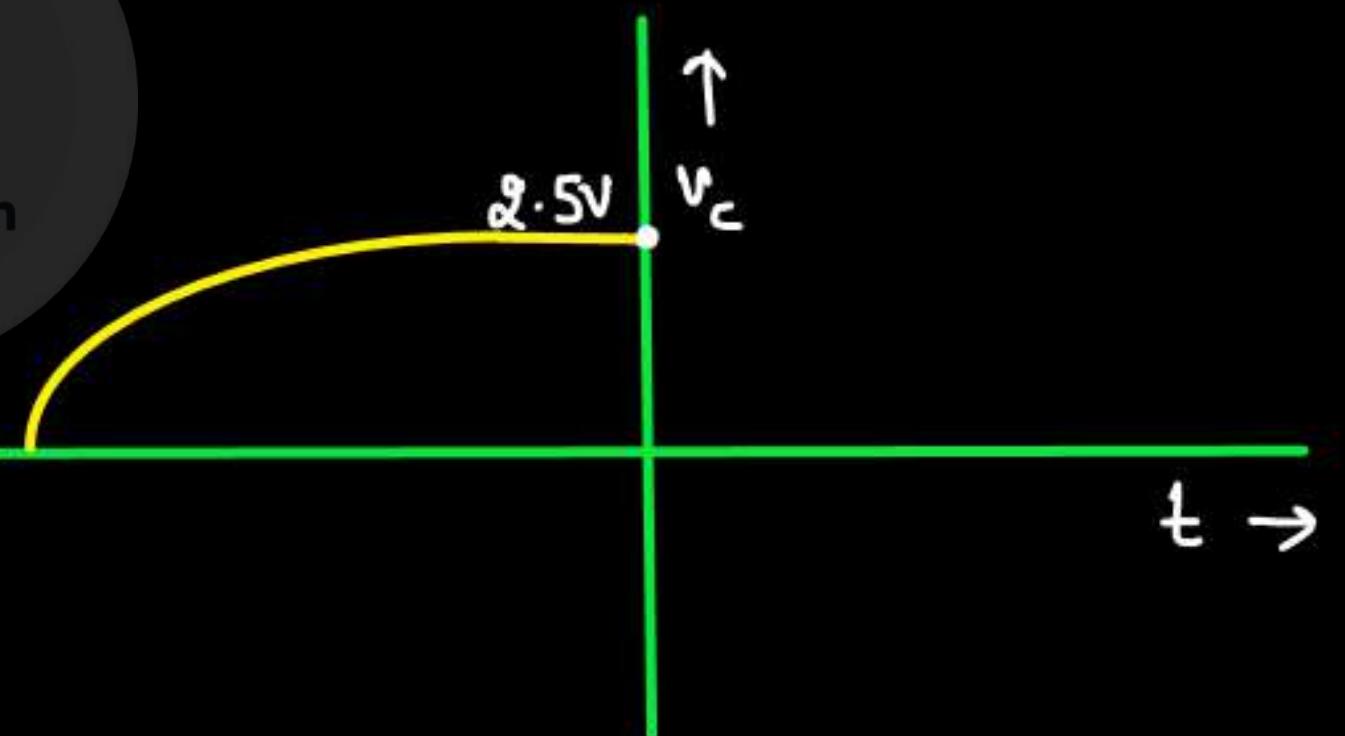


for $t > 0$

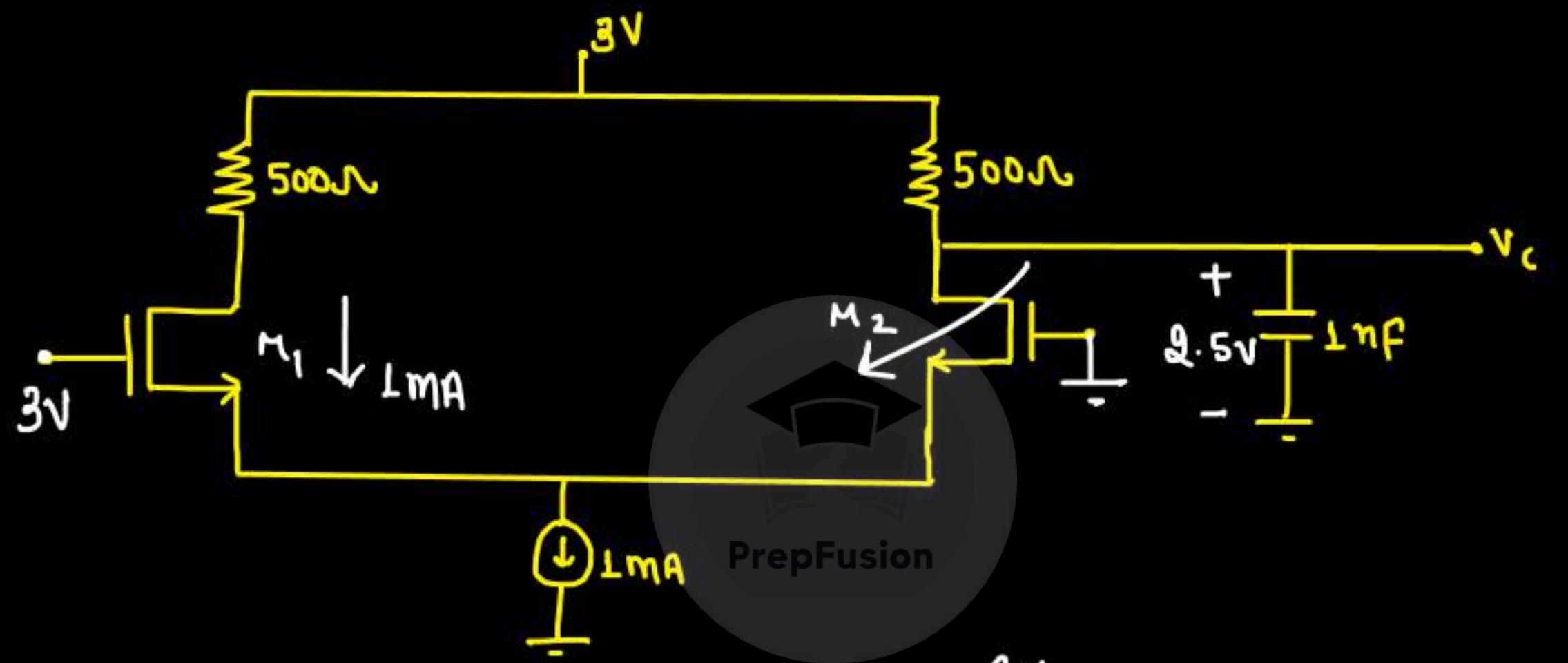

M_2 is off

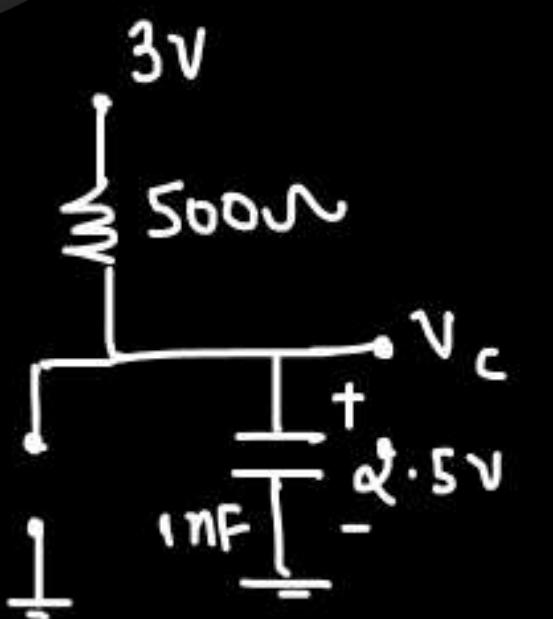

⇒

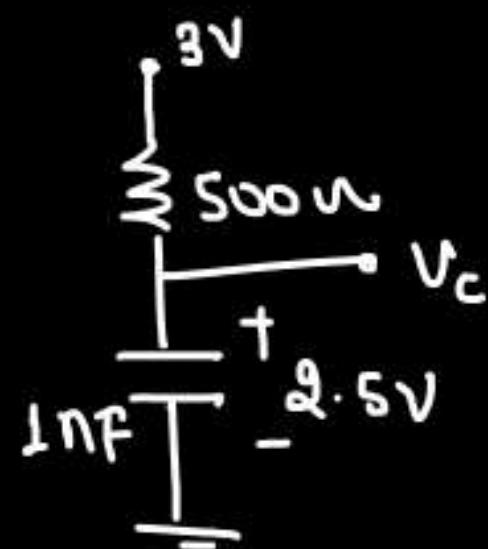

$$V_c(0^+) = 2.5V$$

$$V_c(\infty) = 3V$$

$$\tau = RC = 500 \times 1nF = 0.5 \mu\text{sec.}$$

$$V_c(t) = 3 - 0.5 e^{-t/0.5\mu}$$

Let @ $t = t_1$, $V_c(t_1) = 2.9V$


PrepFusion

$$2.9 = 3 - 0.5 e^{-t_1/0.5\mu}$$


$$t_1 = 0.5 \ln(5) \mu\text{sec.}$$

$$t_1 = 0.8 \mu\text{sec.}$$

ANS

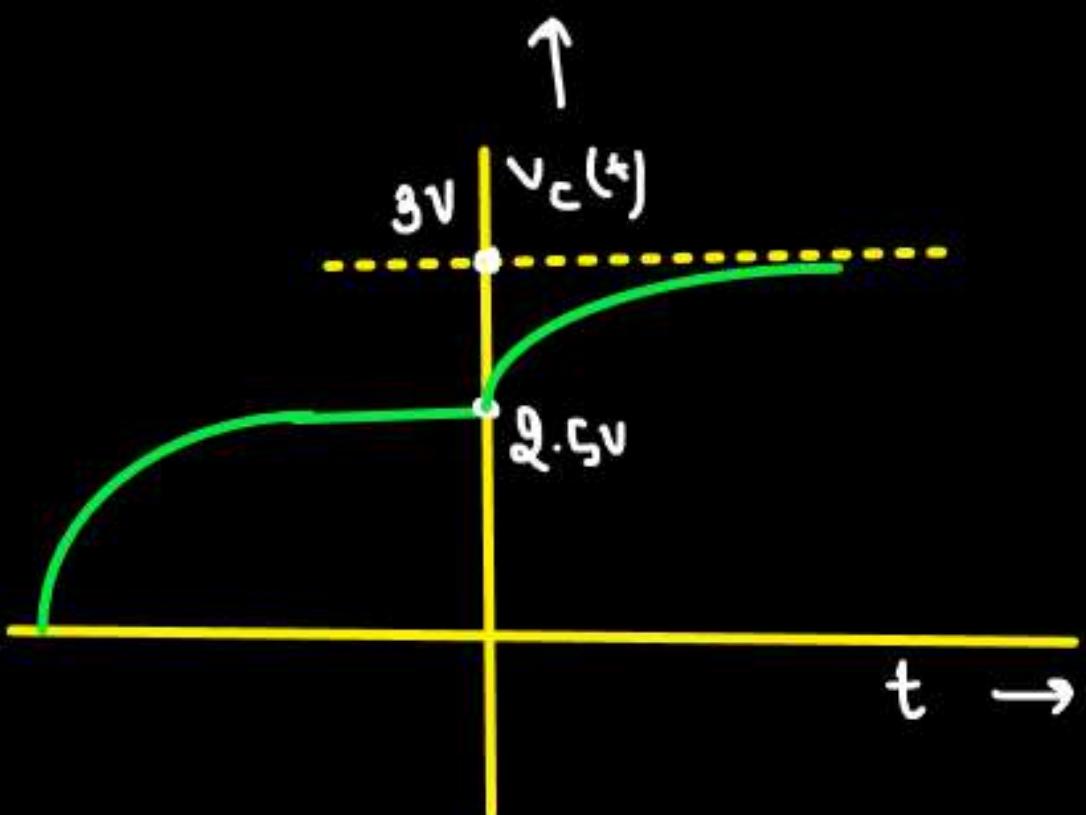

Q.

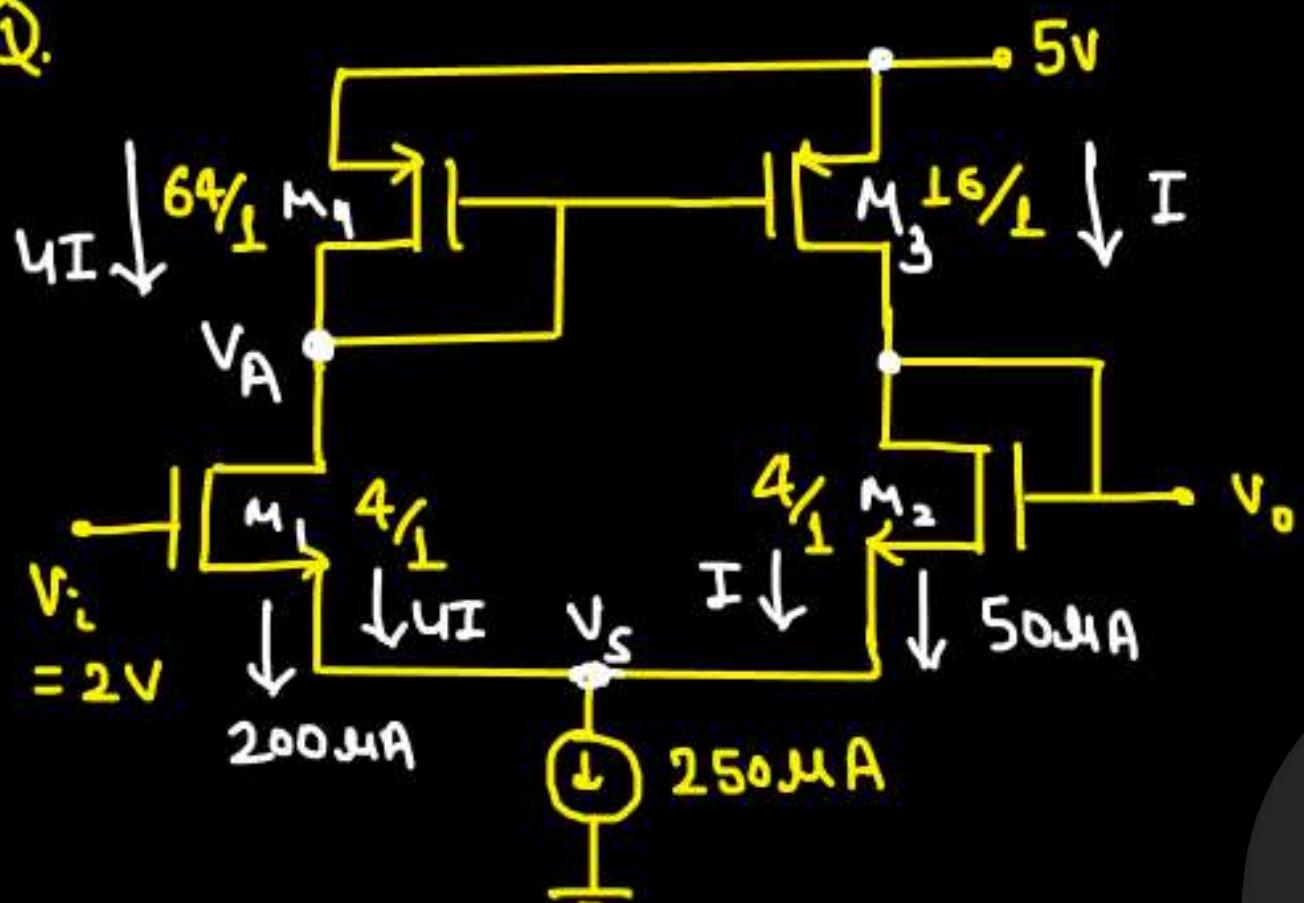

M₄ and M₃ are in Current Mirror. [M₃ should be in sat.]

Assuming M₃ to be in sat.

⇒ M₄ and M₃ are in C.M.

$$4I + I_c \leq 250\mu A$$

$$I = 50\mu A$$

$$\mu_n C_{ox} = 400 \mu A/V^2, \quad V_{TN} = 0.5V$$

$$\mu_p C_{ox} = 100 \mu A/V^2, \quad V_{TP} = 0.5V$$

Find Output Voltage V_o.

Both M_1 and M_2 are having same source potential

∴ M_1 is in saturation


$$I_{M_1} = 200 \mu A$$

$$\Rightarrow 200 \mu A = \frac{400 \mu A \times 4}{2} \left(2 - V_s - 0.5 \right)^2$$

$$0.5 = 1.5 - V_s$$

∴ $V_s = 1V$



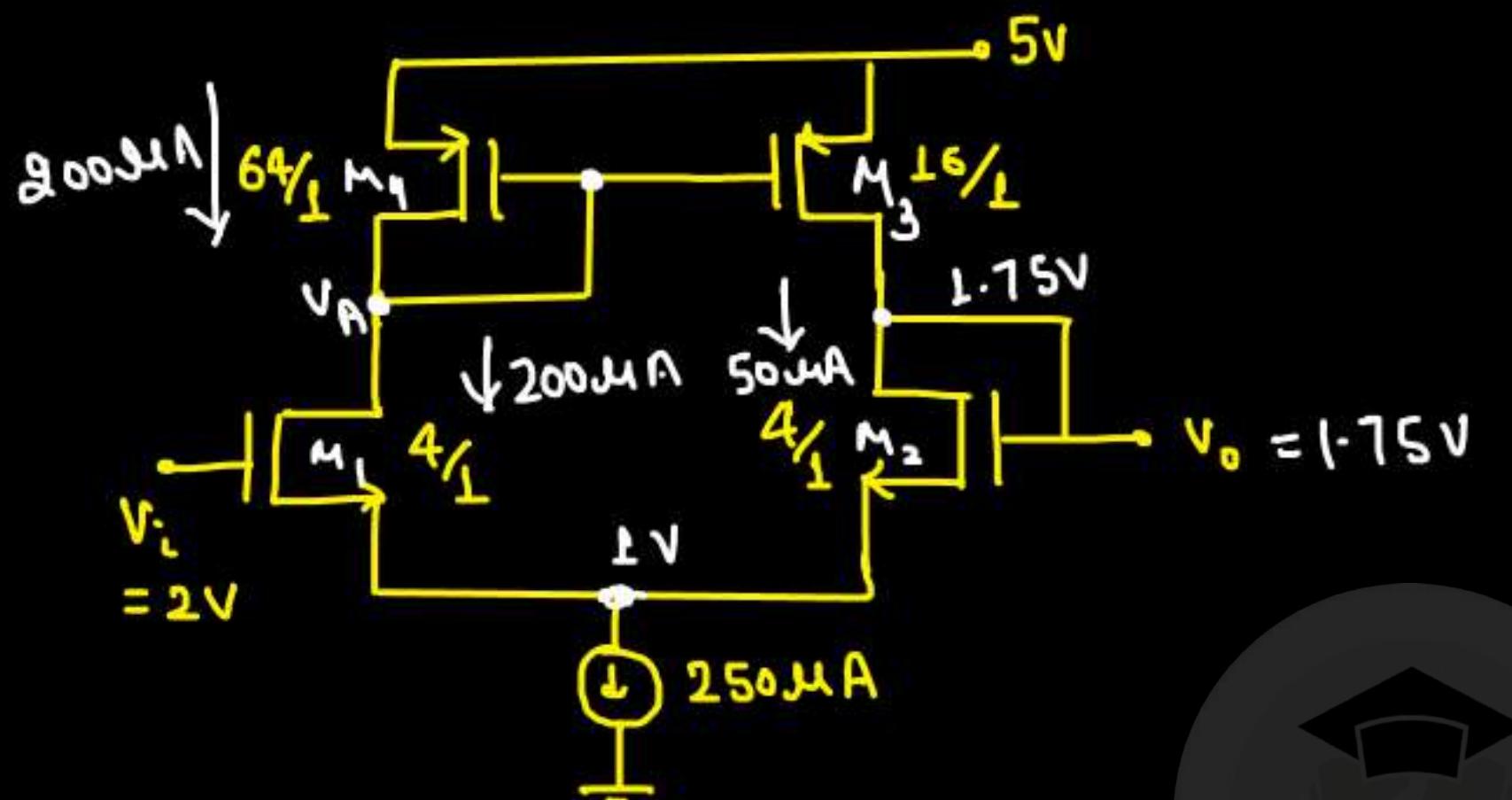

M₂ is in sat.

$$I_{M_2} = 50\mu A$$

$$\Rightarrow 50\mu A = \frac{400\mu A \times 4}{2} [V_o - 1 - 0.5]^2$$

$$V_o = 1.75V$$

⇒ correct? ⇒ NOT SURE ⇒ Take care of Assump.



Check:- if M_1 and M_3 are in sat. or NOT.

$$I_{M_4} = 200 \mu A \quad [\text{Sat.}]$$


$$\Rightarrow 200\mu A = \frac{100\mu A \times 64}{2} [5 - V_A - 0.5]^2$$

$$0.25 = 4.5 - V_A$$

$$V_A = 4.25V$$

PrepFusion

For M_1 :-

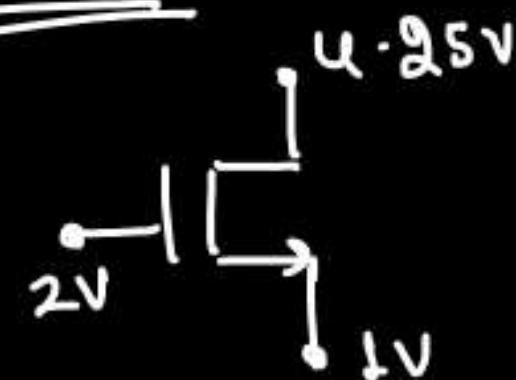

$$V_{DS} = 4.25V$$


$$V_{GS} = 1V$$

$$V_T = 0.5V$$

$$V_{OV} = 0.5V$$

$V_{DS} > V_{OV} \Rightarrow M_1$ is in sat \Rightarrow assumption correct

For M_3 :

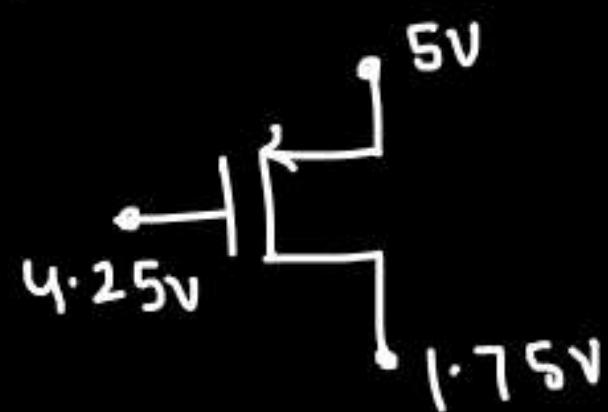

$$V_{SD} = 0.75$$

$$V_T = 0.5$$

$$V_{OV} = 0.25$$

$$V_{SD} = 3.25$$

$\Rightarrow V_{SD} > V_{OV} \Rightarrow$ sat. region



Assumption correct


\Rightarrow all Tr M_1, M_2, M_3 and M_4 are in sat.

$V_D = 1.75V$

Ans.


=

Q.


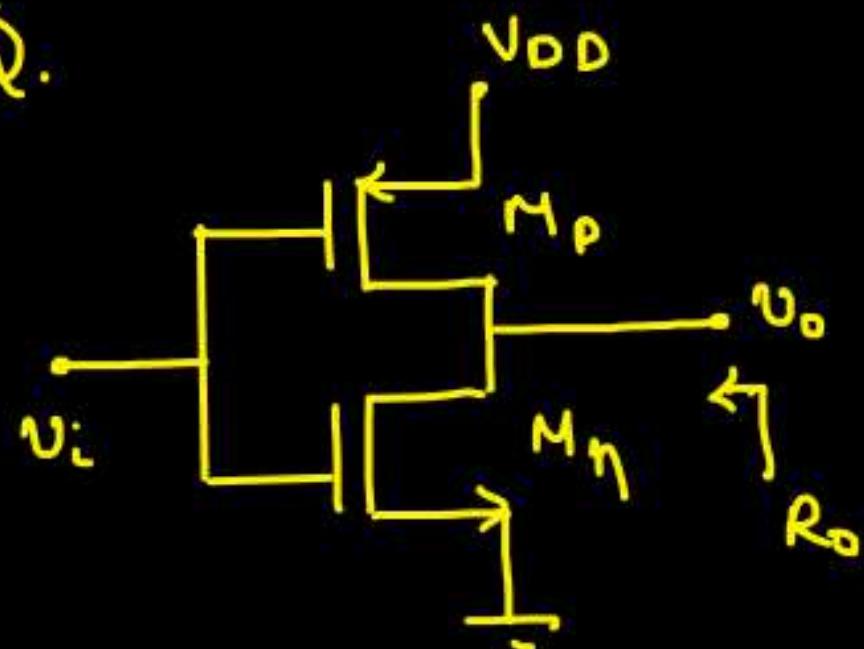


- ① Find the small signal voltage gain.
- ② Find Small signal o/p resistance.


⇒

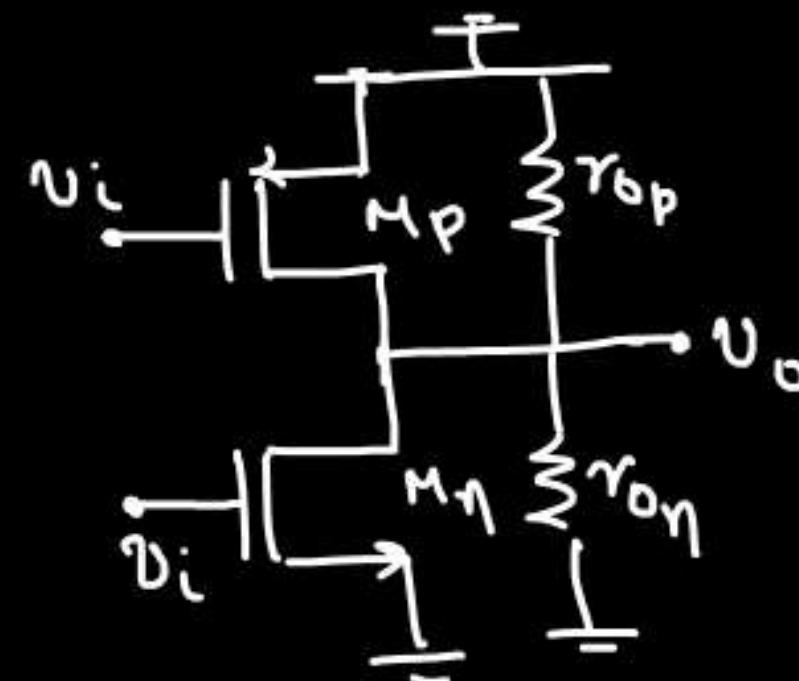

Applying super position :-

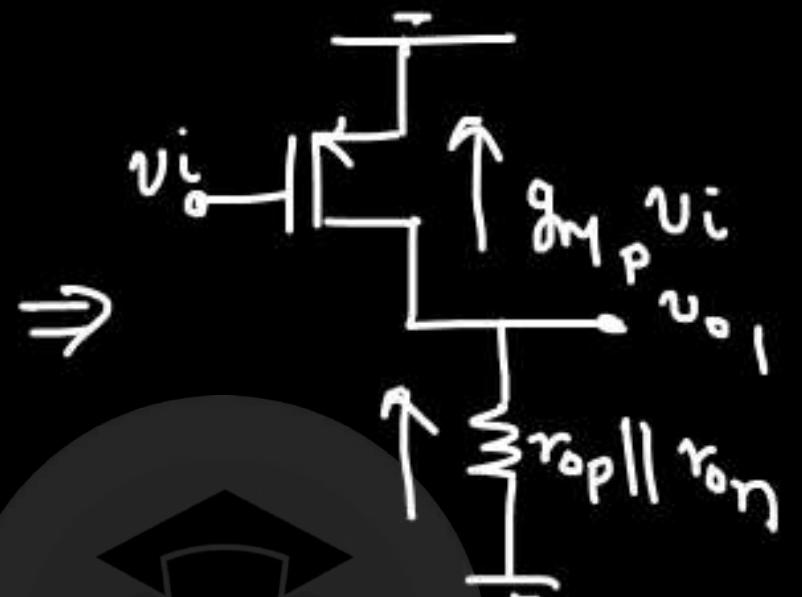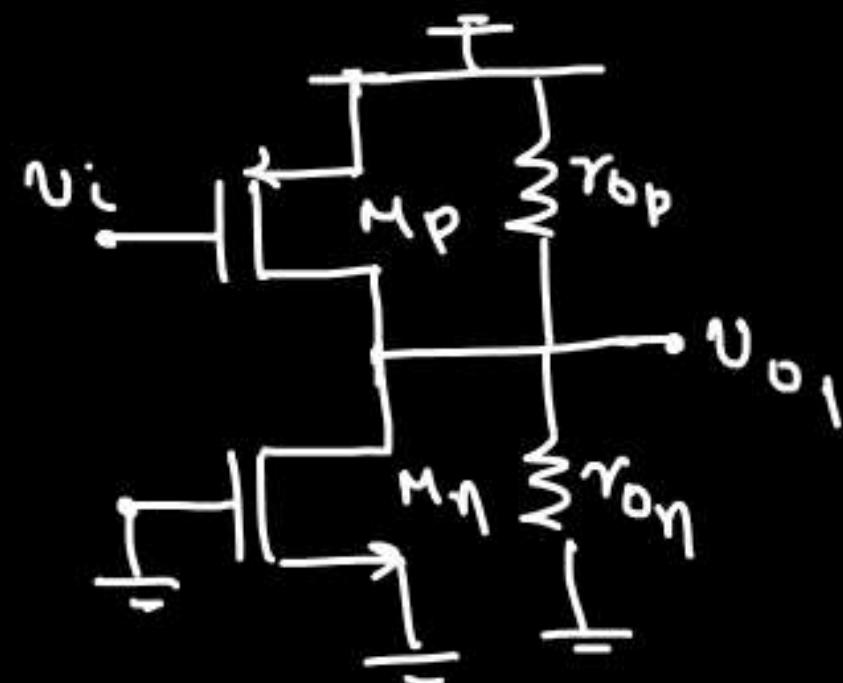

PrepFusion $U_{o1} = -g_{mP}(r_{op} || r_{on})v_i \quad \textcircled{1}$

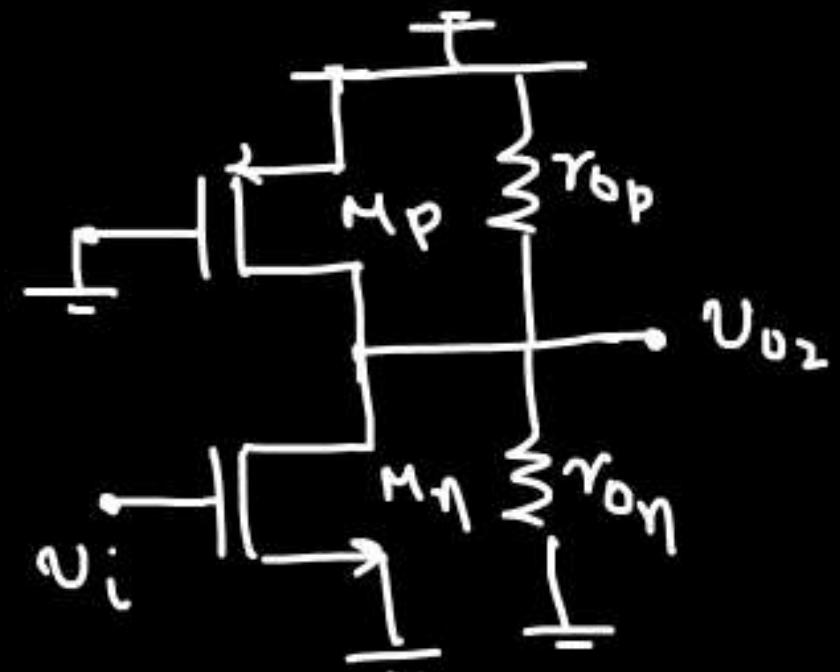

\Rightarrow
 $U_{o2} = -g_{mN}(r_{op} || r_{on})v_i$ $\textcircled{2}$


$$U_o = U_{o1} + U_{o2}$$

$$v_o = -(\text{g}_{\text{m}_p} + \text{g}_{\text{m}_n})(r_{\text{o}_p} \parallel r_{\text{o}_n}) v_{\text{in}}$$

$$\frac{v_o}{v_{\text{in}}} = -(\text{g}_{\text{m}_p} + \text{g}_{\text{m}_n})(r_{\text{o}_p} \parallel r_{\text{o}_n})$$

ANS

O/P impedance :-

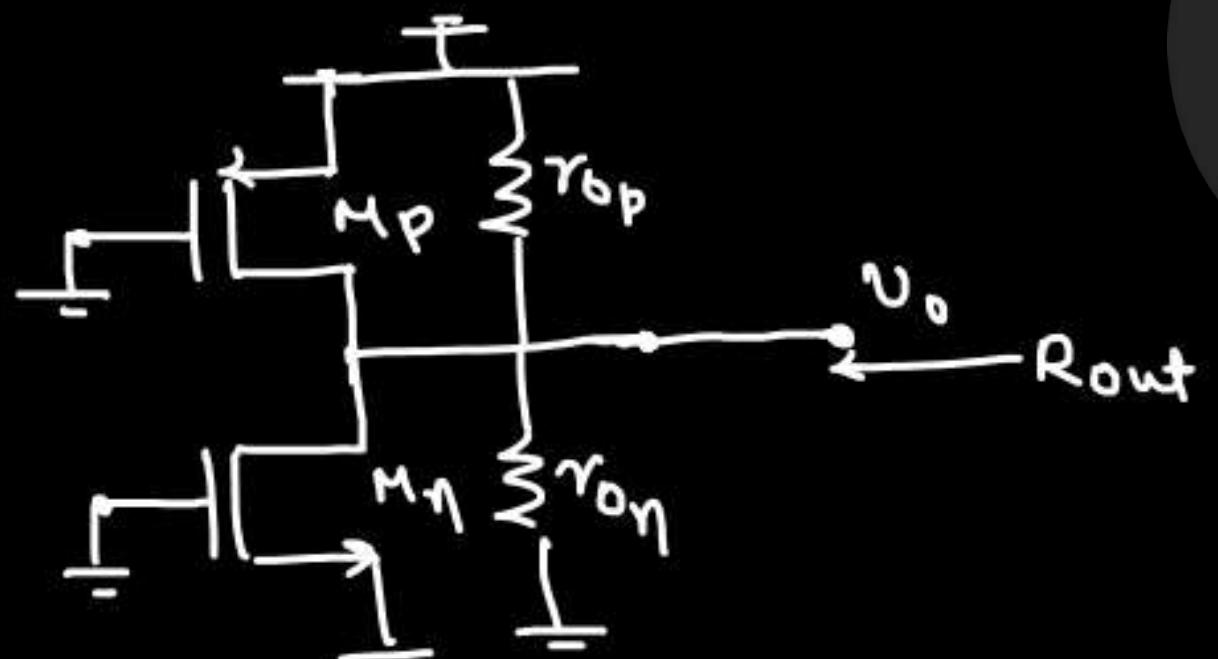

$$R_{\text{out}} = r_{\text{o}_p} \parallel r_{\text{o}_n}$$

w

Q. For a n-channel enhancement type MOS,

$$W/L = 10$$

$$\mu_n C_{ox} = 1 \text{ mA}/\sqrt{2}$$

$$V_T = 1 \text{ V}$$

$$V_{GS} = 2 - \sin(2t) \text{ V}$$

$$V_{DS} = 1 \text{ V}$$

max^m value of drain to source current = ?

- (a) 40 mA
(c) 15 mA

- (b) 20 mA
(d) 5 mA





$$V_{GS} = 2 - \sin(2t) \text{ V } \left\{ 1 < V_{GS} < 3 \right\}$$

$$V_{DS} = 1 \text{ V}$$



more V_{GS} \Rightarrow more I_D

$$(I_D)_{\text{Max}} = ?$$

@ $(V_{GS})_{\text{Max}} \Rightarrow (I_D)_{\text{Max}}$

$$(V_{GS})_{\text{Max}} = 2 - (-1) = 3 \text{ V}$$
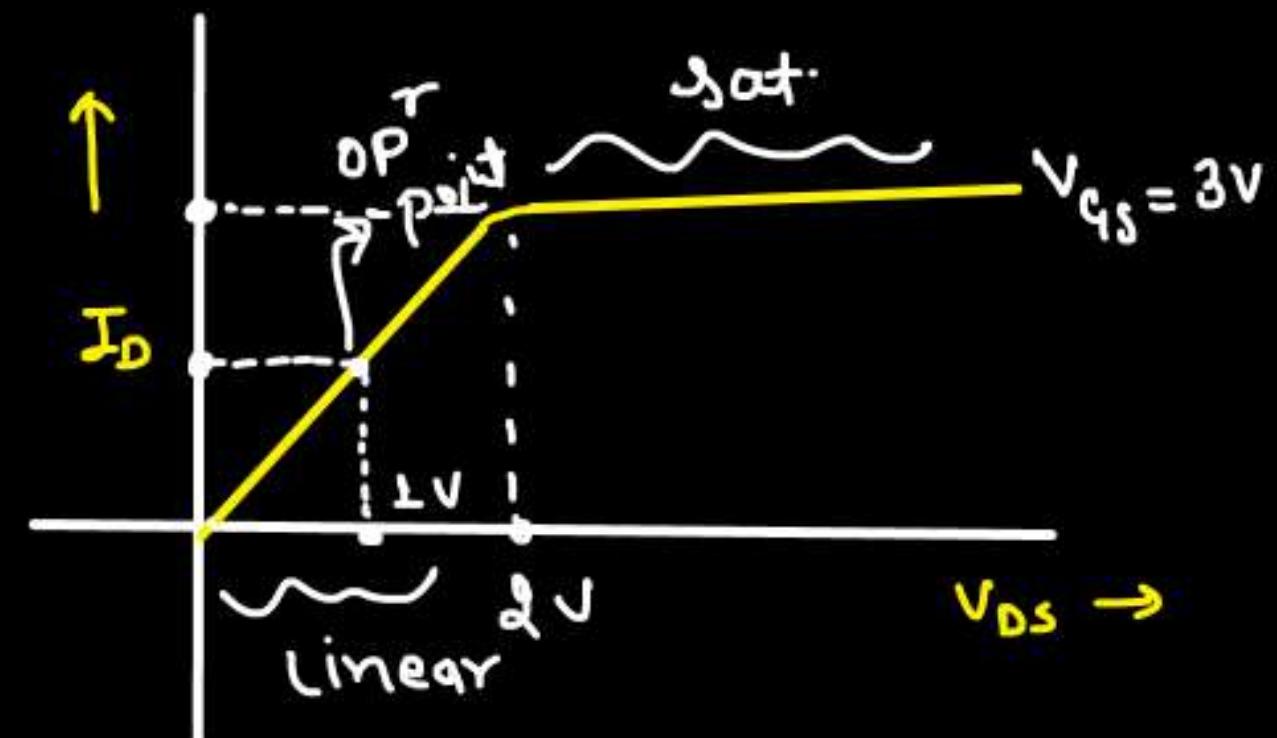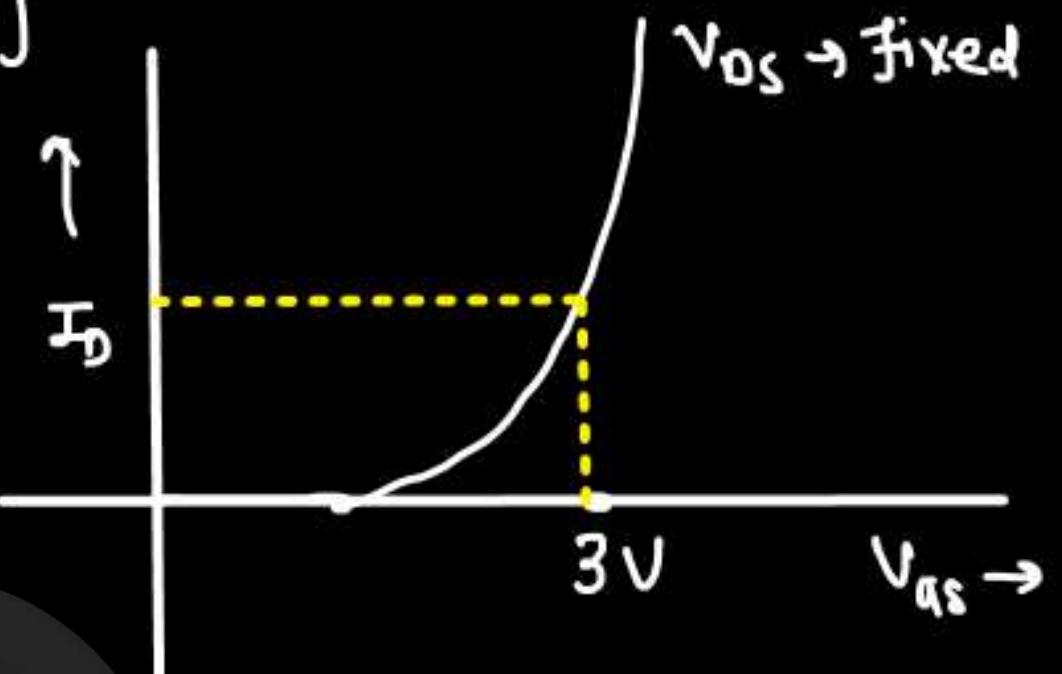
$$(I_D)_{\text{Max}} = \frac{1 \text{ m} \times 10}{2} (3 - 1)^2 = 20 \text{ mA}$$



$$(V_{GS})_{\text{max}} = 3V$$

$$V_{DS} = 1V \quad \checkmark$$

$$V_T = 1V$$

$$V_{OV} = 3 - 1 = 2V \quad \checkmark$$



$V_{DS} < V_{OV} \Rightarrow$ Mos is working in linear region for $\max V_{GS}$

$$(I_D)_{\text{max}} = 10m \left[(2)(1) - \frac{1^2}{2} \right]$$

$$(I_D)_{\text{max}} = 15mA \quad \checkmark$$


Ans.

Q.

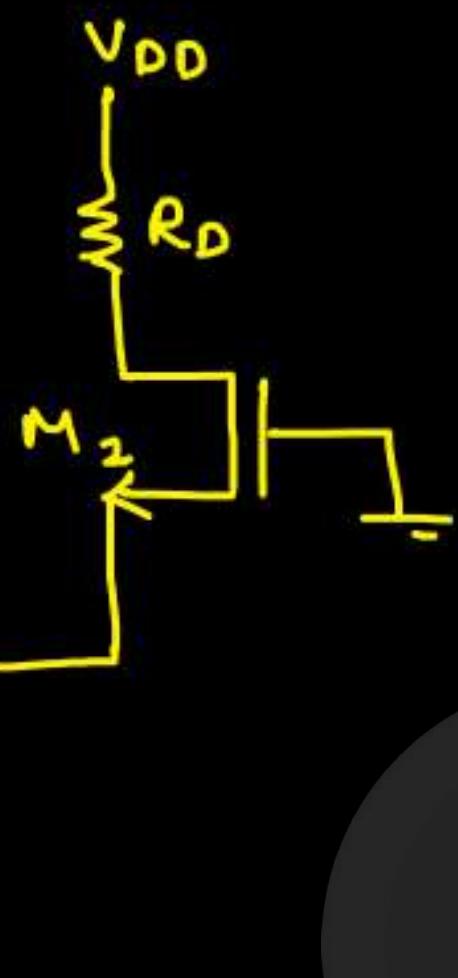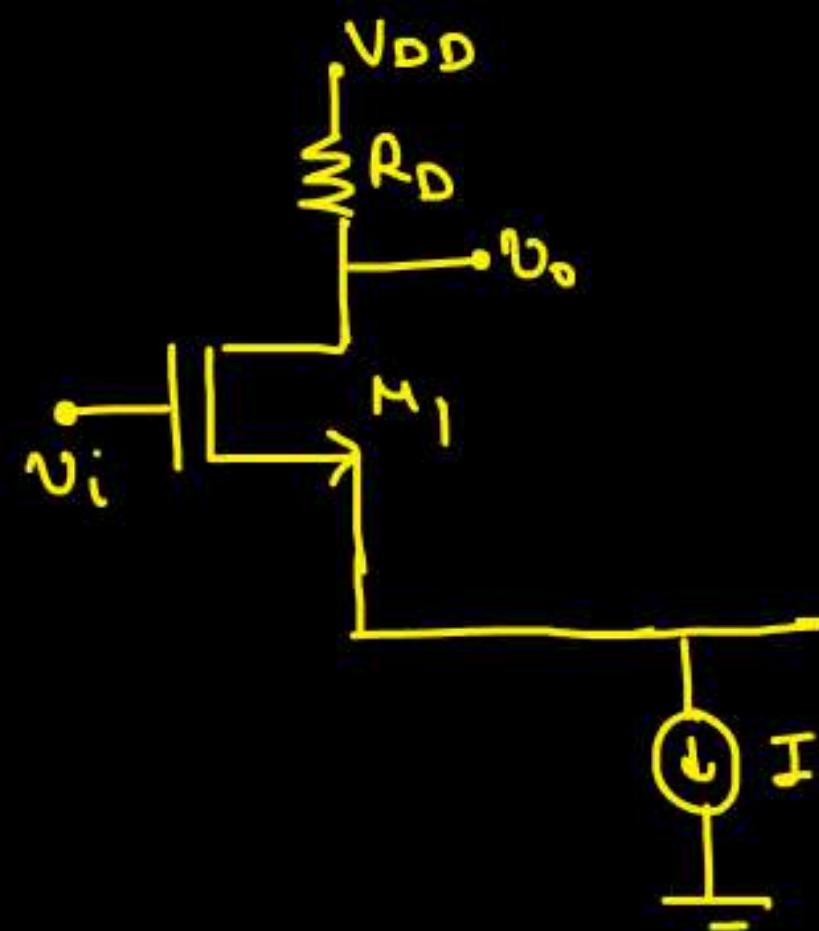

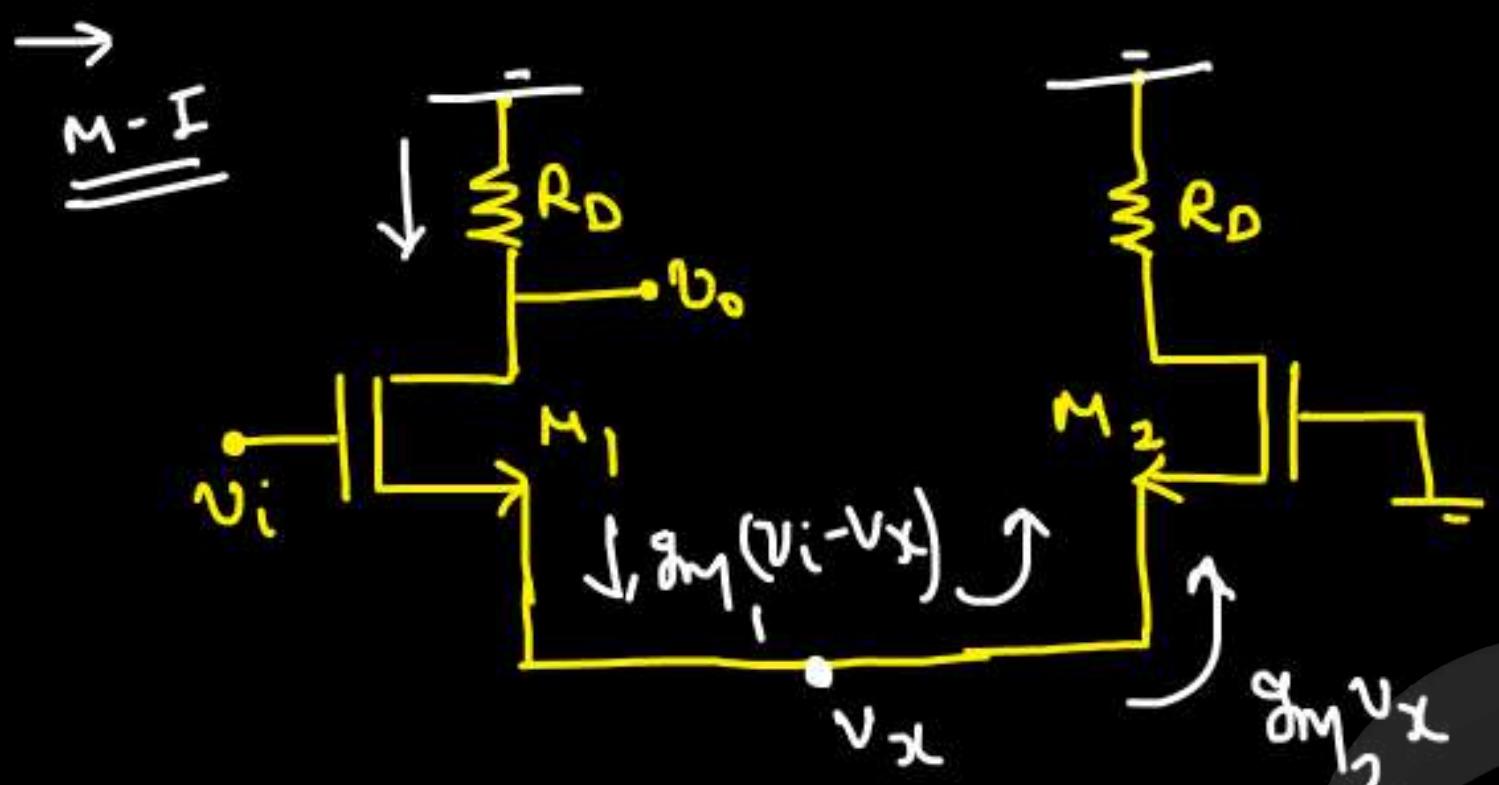Take $\lambda = 0$
Find small signal
voltage gain $\frac{V_o}{V_i}$.





$$g_{m_1}(v_i - v_x) = g_{m_2} v_x$$

$$v_x = \frac{g_{m_1}}{g_{m_1} + g_{m_2}} v_i$$

$$\frac{v_o}{v_i} = ?$$


$$v_o = -g_{m_1} R_D (v_i - v_x)$$

$$v_o = -g_{m_1} R_D \left(v_i - \frac{g_{m_1} v_i}{g_{m_1} + g_{m_2}} \right)$$


$$v_o = -g_{m_1} R_D \left[\frac{g_{m_2}}{g_{m_1} + g_{m_2}} \right] v_i$$

$$\frac{v_o}{v_i} = -\frac{g_{m_1} g_{m_2}}{g_{m_1} + g_{m_2}} R_D$$

M-II

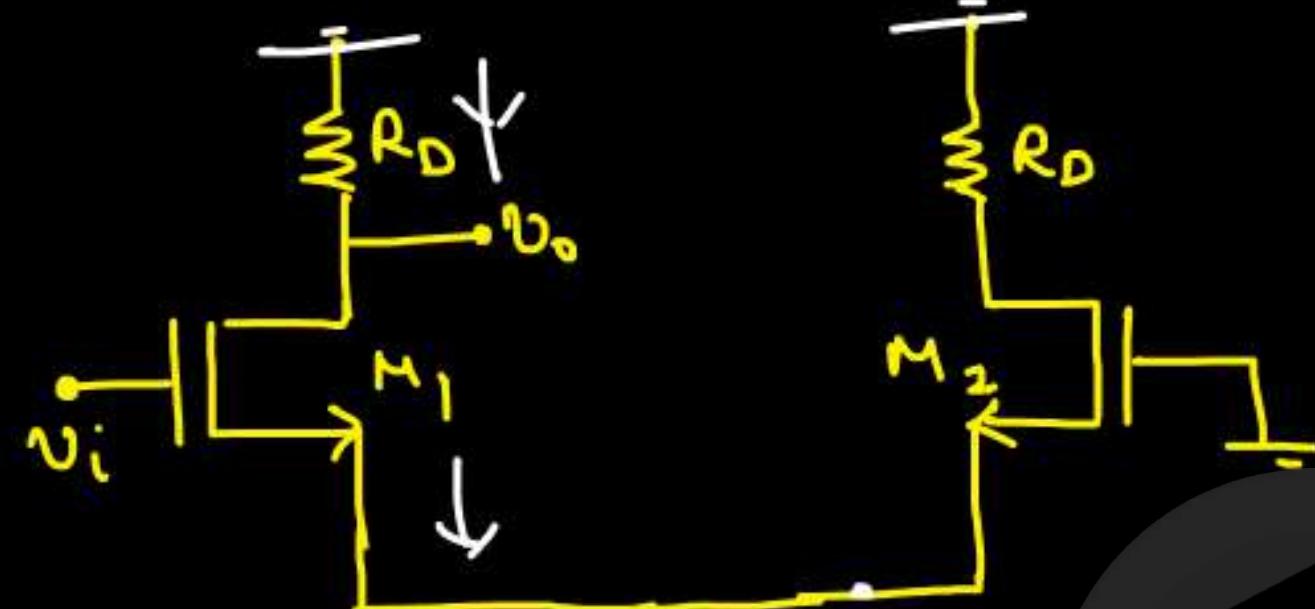
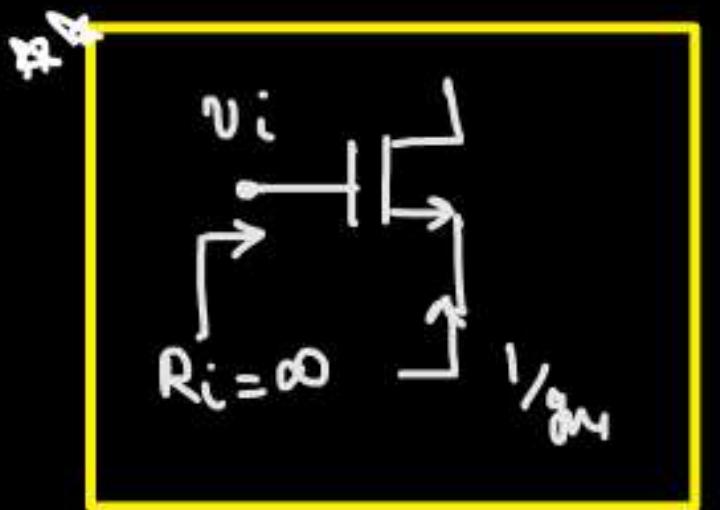
$$-\frac{V_i}{\frac{1}{g_m_1} + \frac{1}{g_m_2}} R_D = V_o$$




Ans

$$\frac{V_o}{V_i} = -\frac{g_m_2 g_m_1}{g_m_2 + g_m_1} R_D$$

⇒ Building 2 - Stage OP-Amp:-

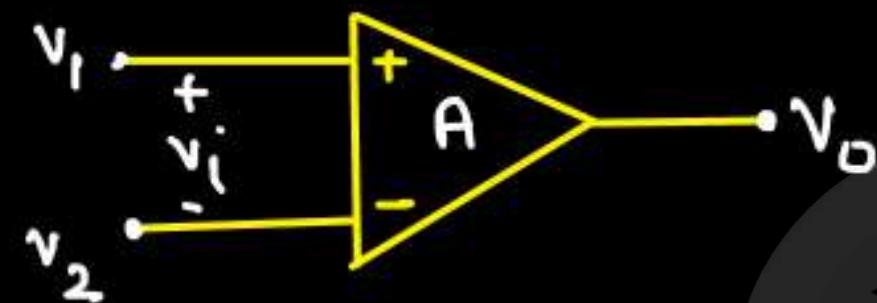* What is OP-Amp? (operational amplifier)




$$V_0 = A(V_+ - V_-)$$

$$V_0 = A(V_1 - V_2)$$


$$V_0 = A V_i$$

High _

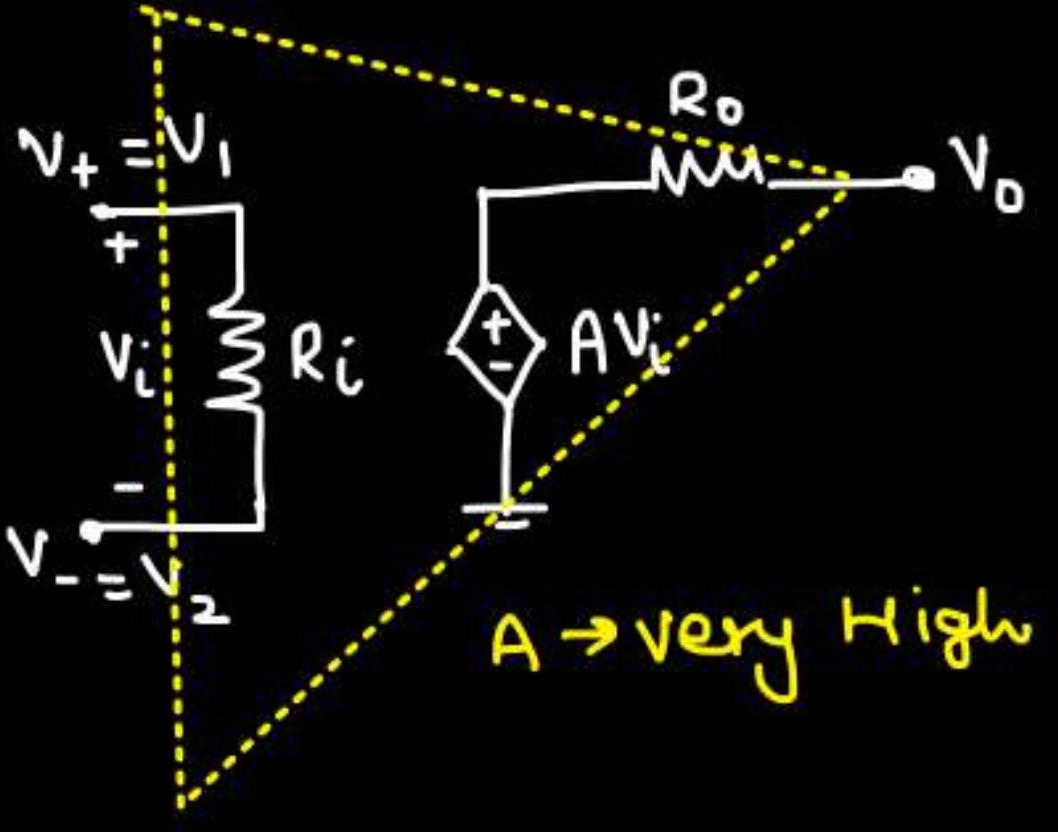

$R_i \rightarrow$ very High (∞)

$R_o \rightarrow$ very low (0)

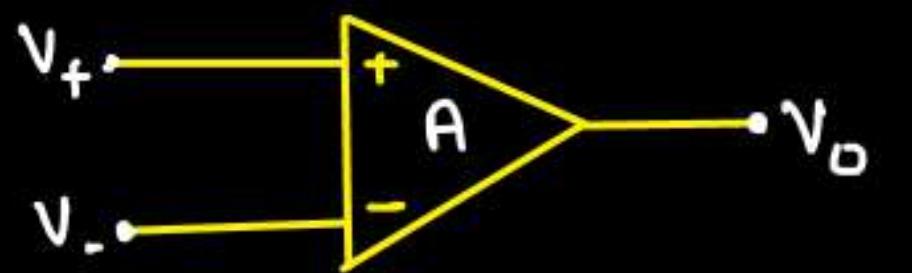

Ans
 $V_o = A(V_+ - V_-)$



PrepFusion


Target :-

Designing High input impedance, Low o/p impedance
and a High gain amplifier.

(double ended, single ended o/p)
o/p




⇒ What we have studied?

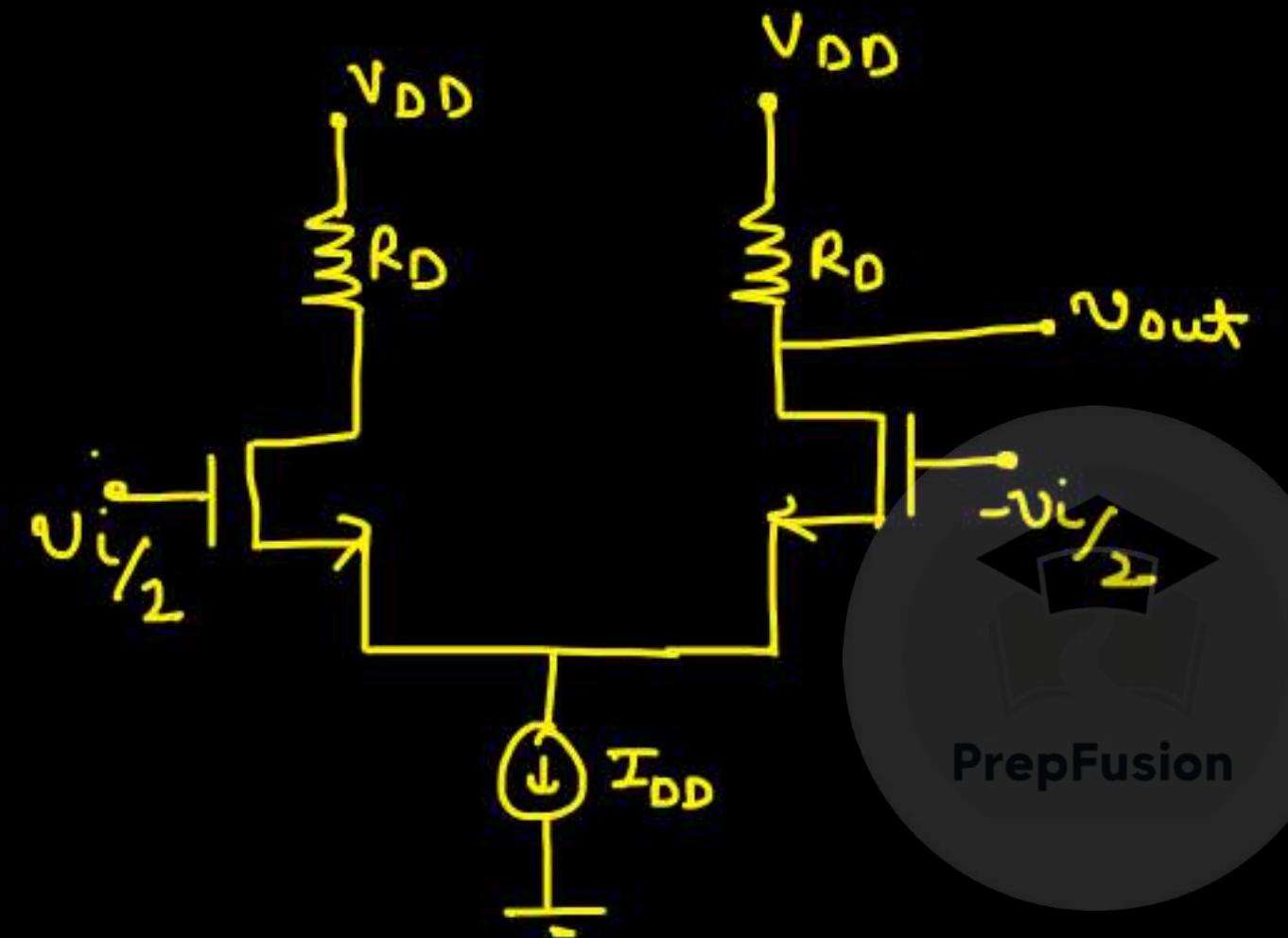

- (i) gain = ? = $\frac{V_o}{V_i}$
- (ii) i/p impedance = ?
- (iii) o/p impedance = ?

(ii) gain :-

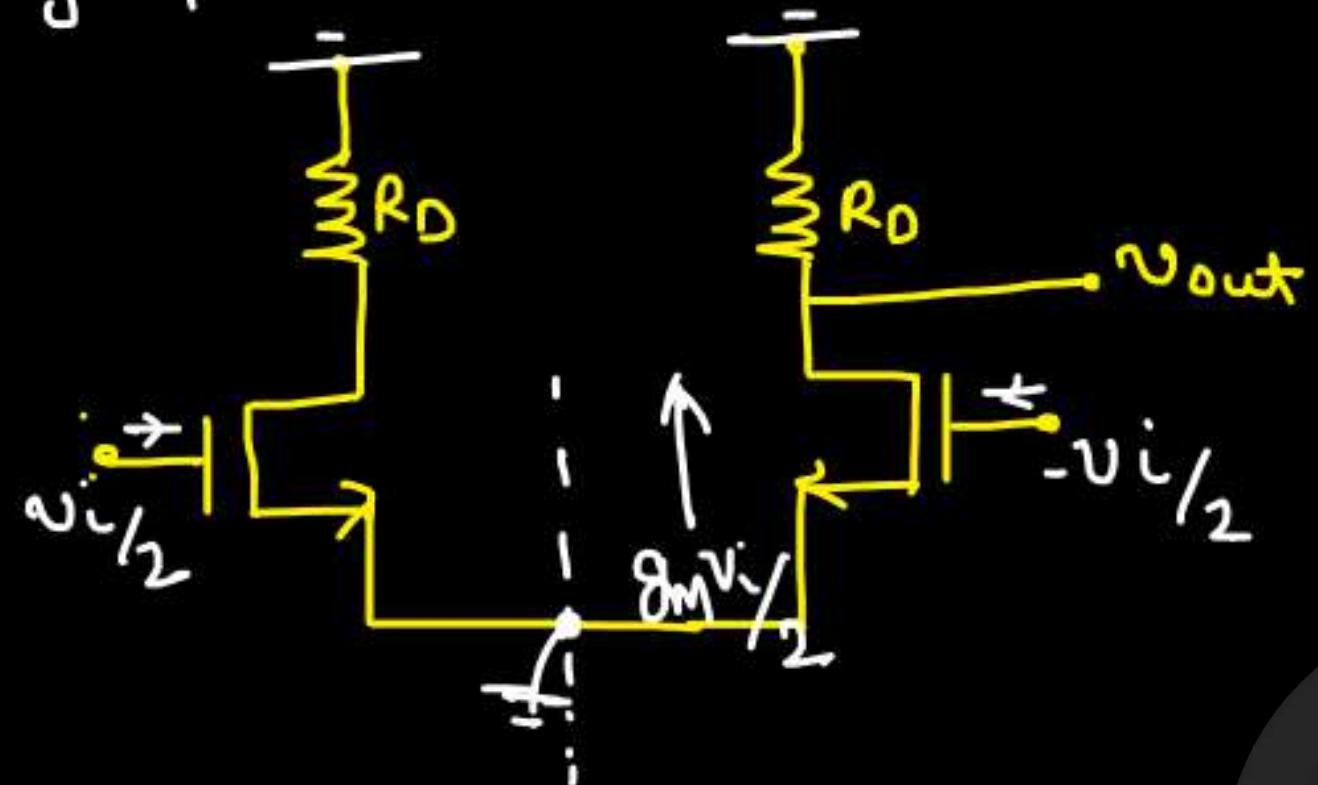

$$v_o = \frac{g_m v_i}{2} R_D$$

$$\frac{v_o}{v_i} = \frac{g_m R_D}{2} \Rightarrow \text{NOT VERY HIGH} = (X)$$

(iii) Input Impedance :-


$$\frac{v_i}{I_i} = \frac{v_i}{0} = \infty$$

⇒ High Input Impedance (v)



(iii) O/P impedance:-

(Let's take $\lambda \neq 0$)

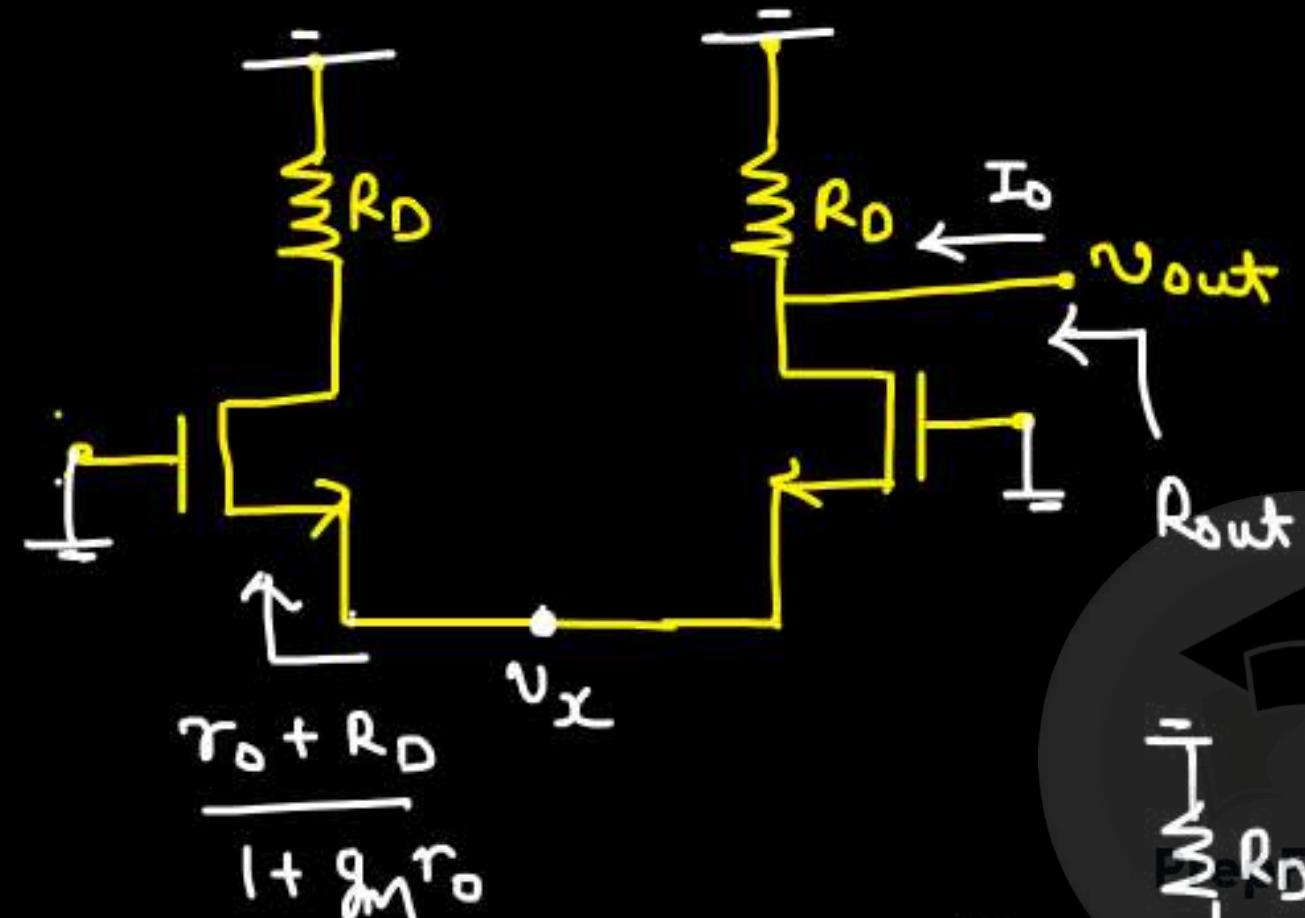


$$\frac{r_o + R_D}{1 + g_m r_o}$$

$$R_{out} = R_x || R_D$$

$$R_{out} = (2r_o + R_D) || R_D$$
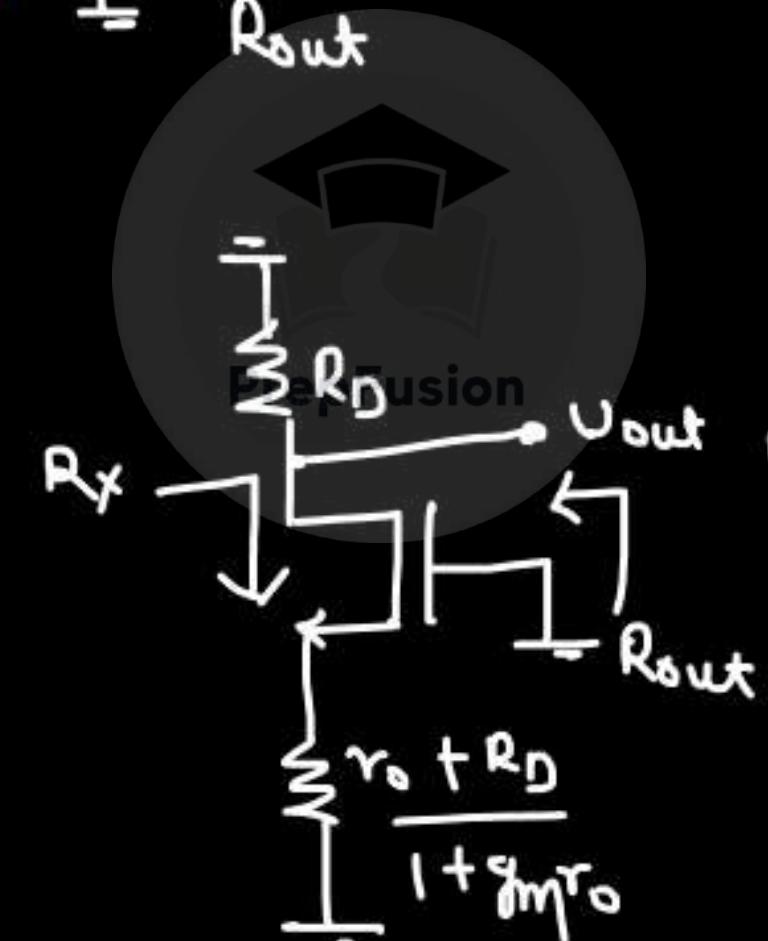
$$\approx R_D \Rightarrow \text{low} (\checkmark)$$




$$R_x = g_m r_o \left(\frac{r_o + R_D}{1 + g_m r_o} \right) + r_o + \left(\frac{r_o + R_D}{1 + g_m r_o} \right)$$

$$= \frac{r_o + R_D}{1 + g_m r_o} [1 + g_m r_o] + r_o$$

$$R_x = 2r_o + R_D$$

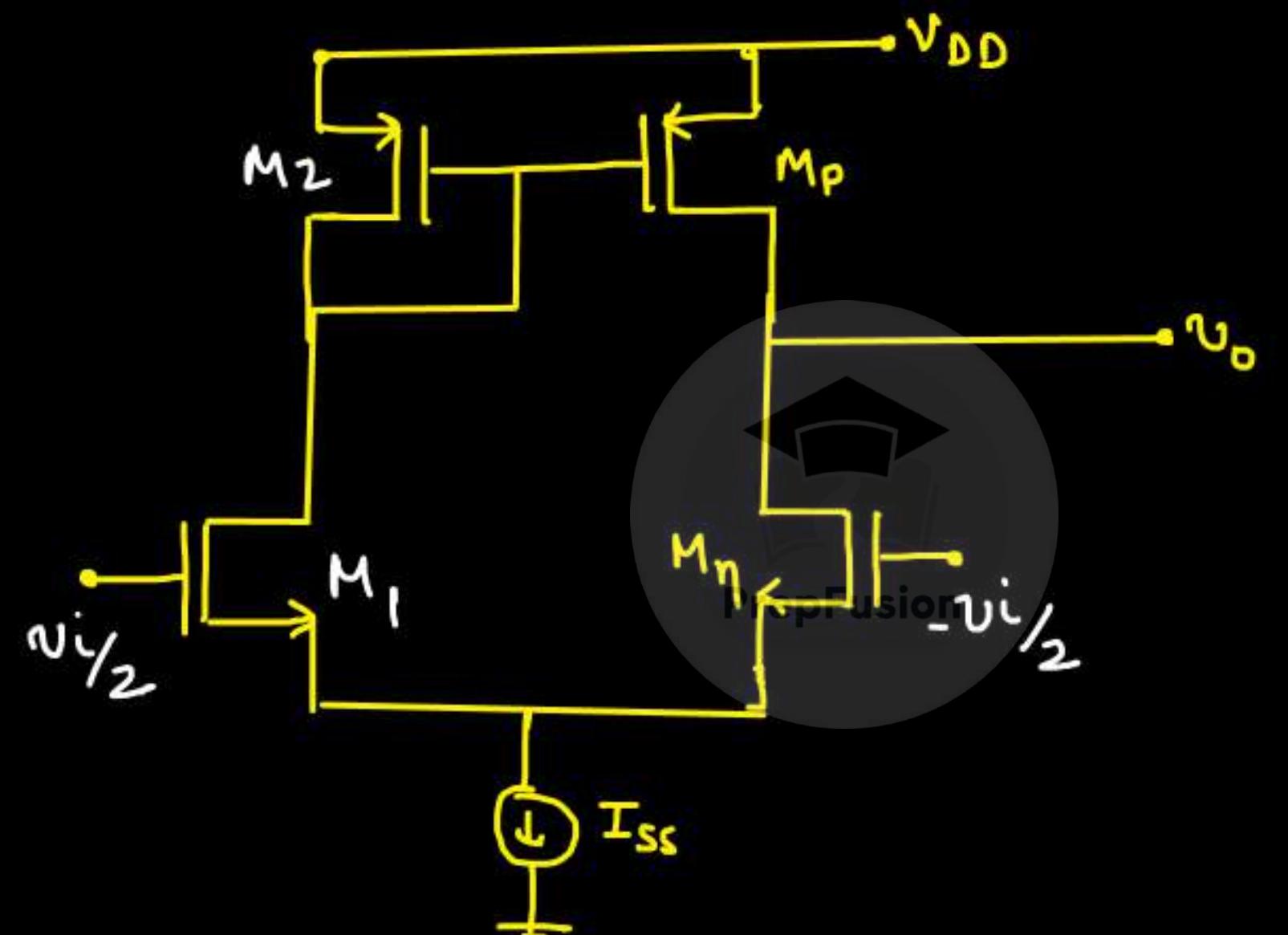
Differential Amplifier with active load :-



For ease of calculation, we will take $\lambda = 0$ for $M_1 \& M_2$
 $\lambda \neq 0$ for $M_n \& M_p$

Voltage Gain :-


$$\underline{G_m \rightarrow}$$

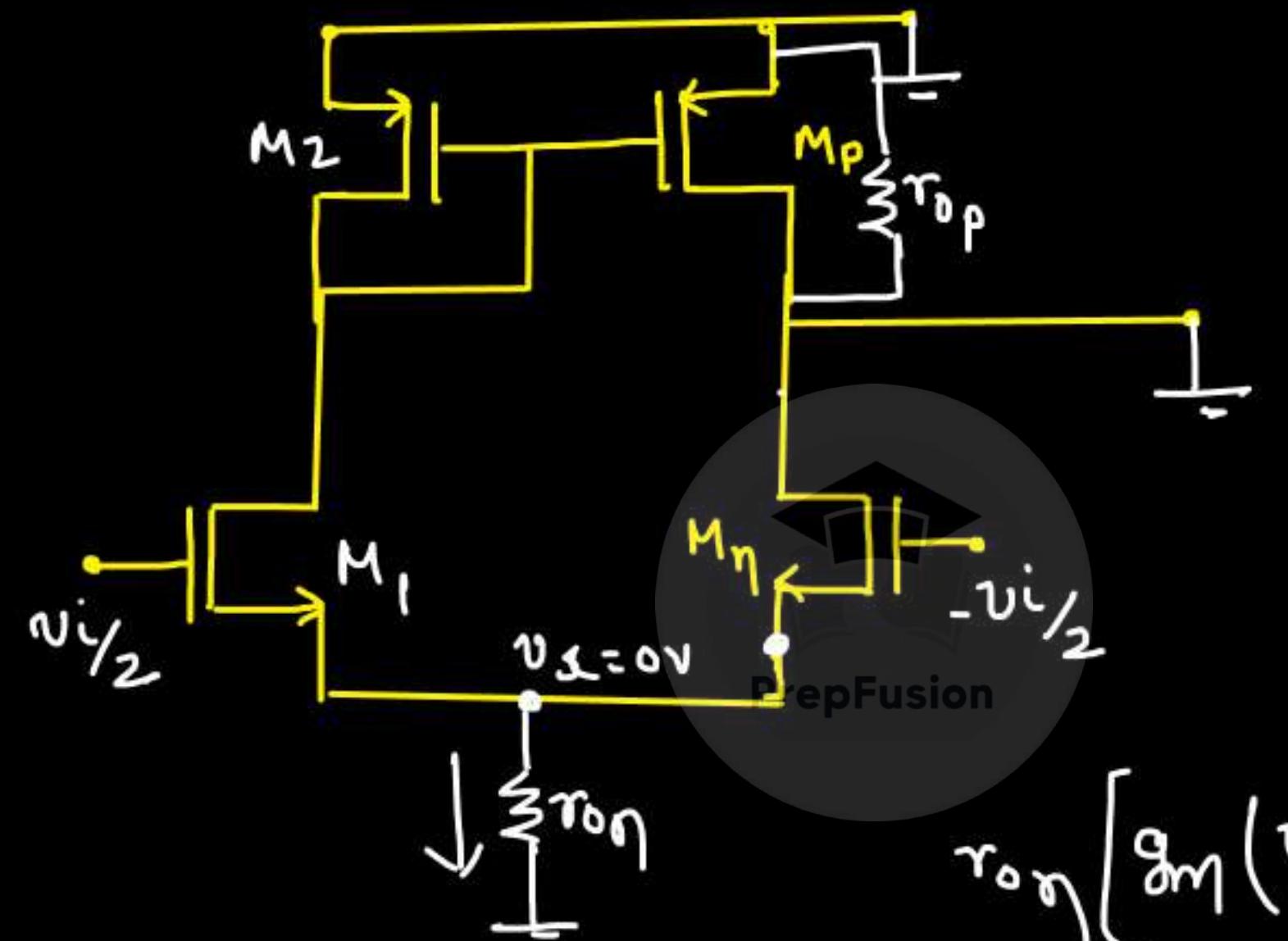

$$r_{o\eta} [g_m \left(\frac{v_i}{2} - v_x \right) + g_m \left(-\frac{v_i}{2} - v_x \right)] = v_x$$

$$-2g_m r_{o\eta} v_x = v_x$$
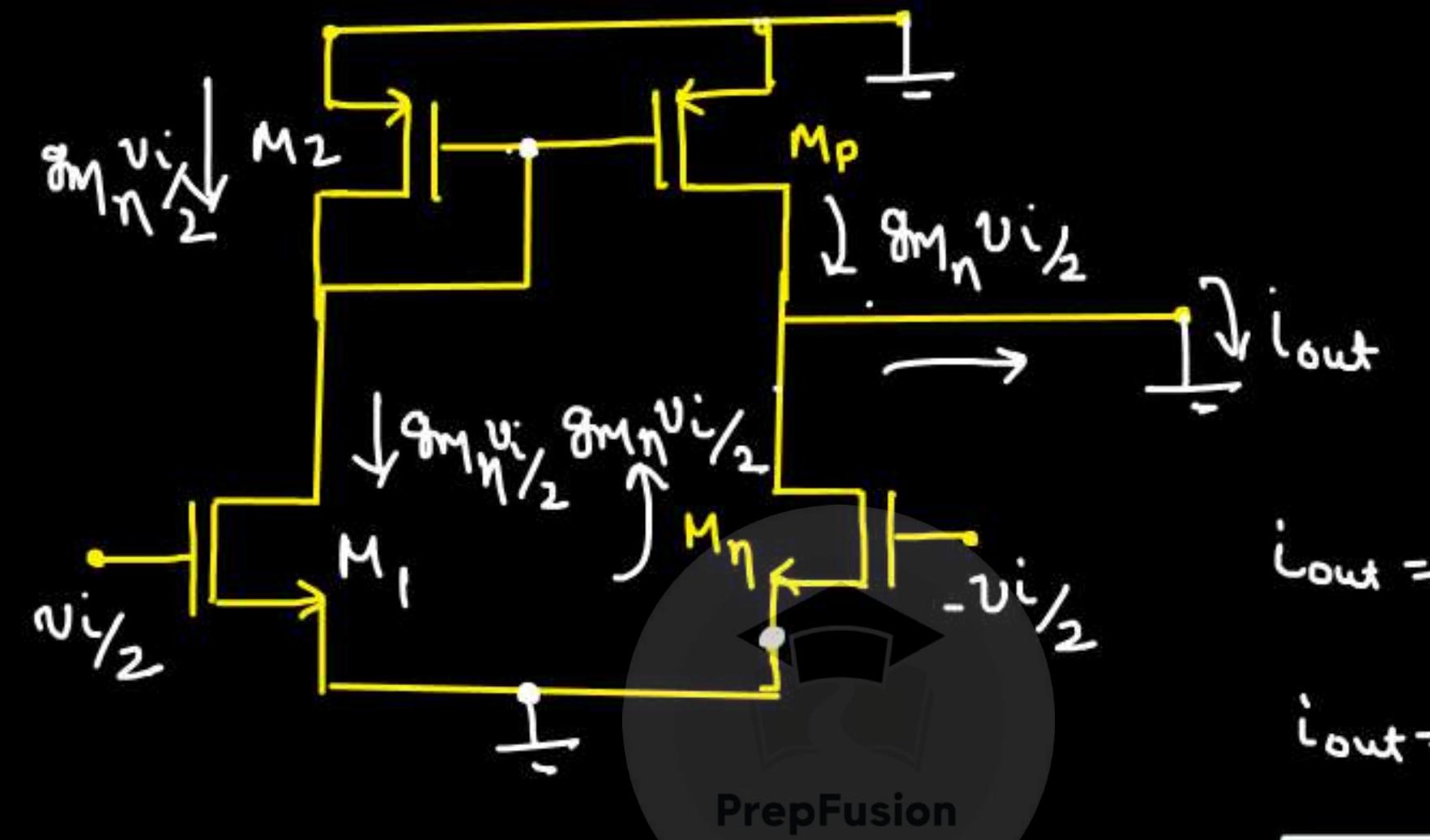
$$v_x [1 + 2g_m r_{o\eta}] = 0 \Rightarrow v_x = 0$$





$$i_{out} = g_{m\eta} v_{i/2} + g_{m\eta} v_{i/2}$$

$$i_{out} = g_{m\eta} v_i$$


$$G_m = g_{m\eta}$$

R_{out} :-

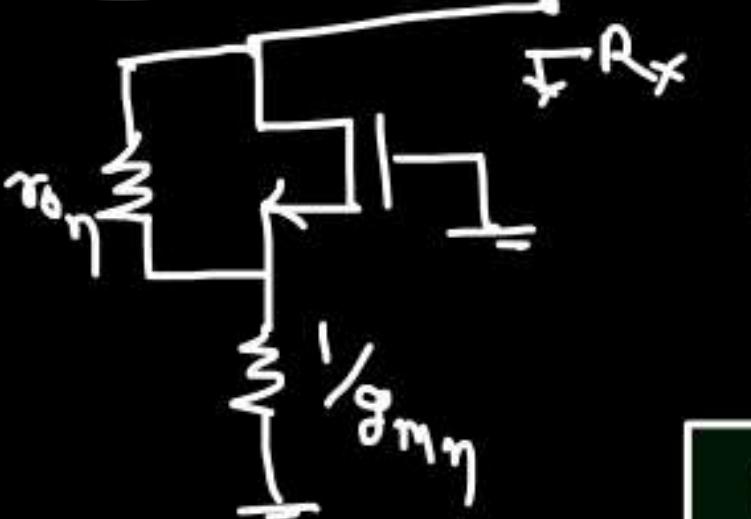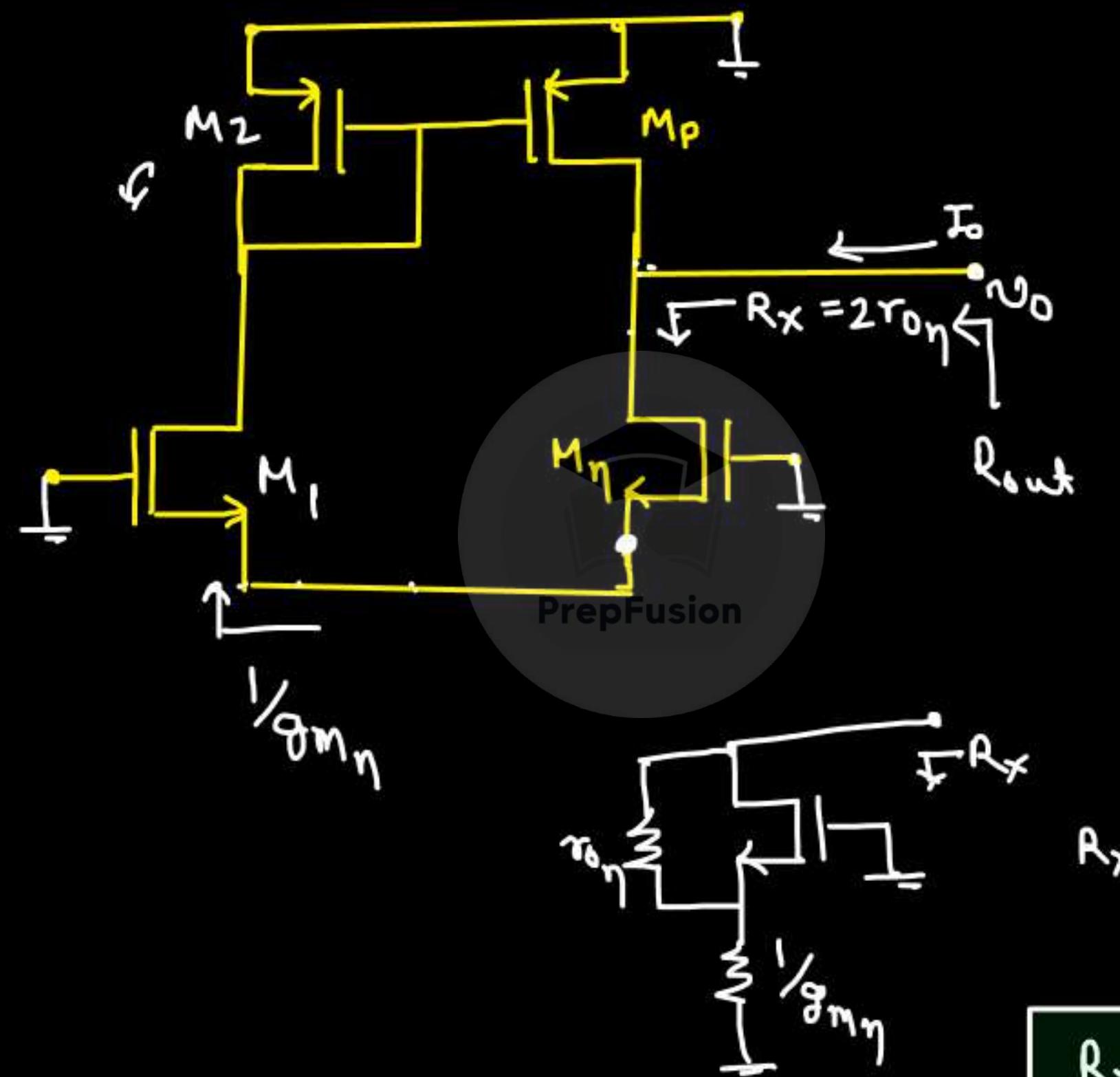

$$R_x = g_{m\eta} r_{0\eta} \times \frac{1}{g_{m\eta}} + r_{0\eta} + \frac{1}{g_{m\eta}}$$
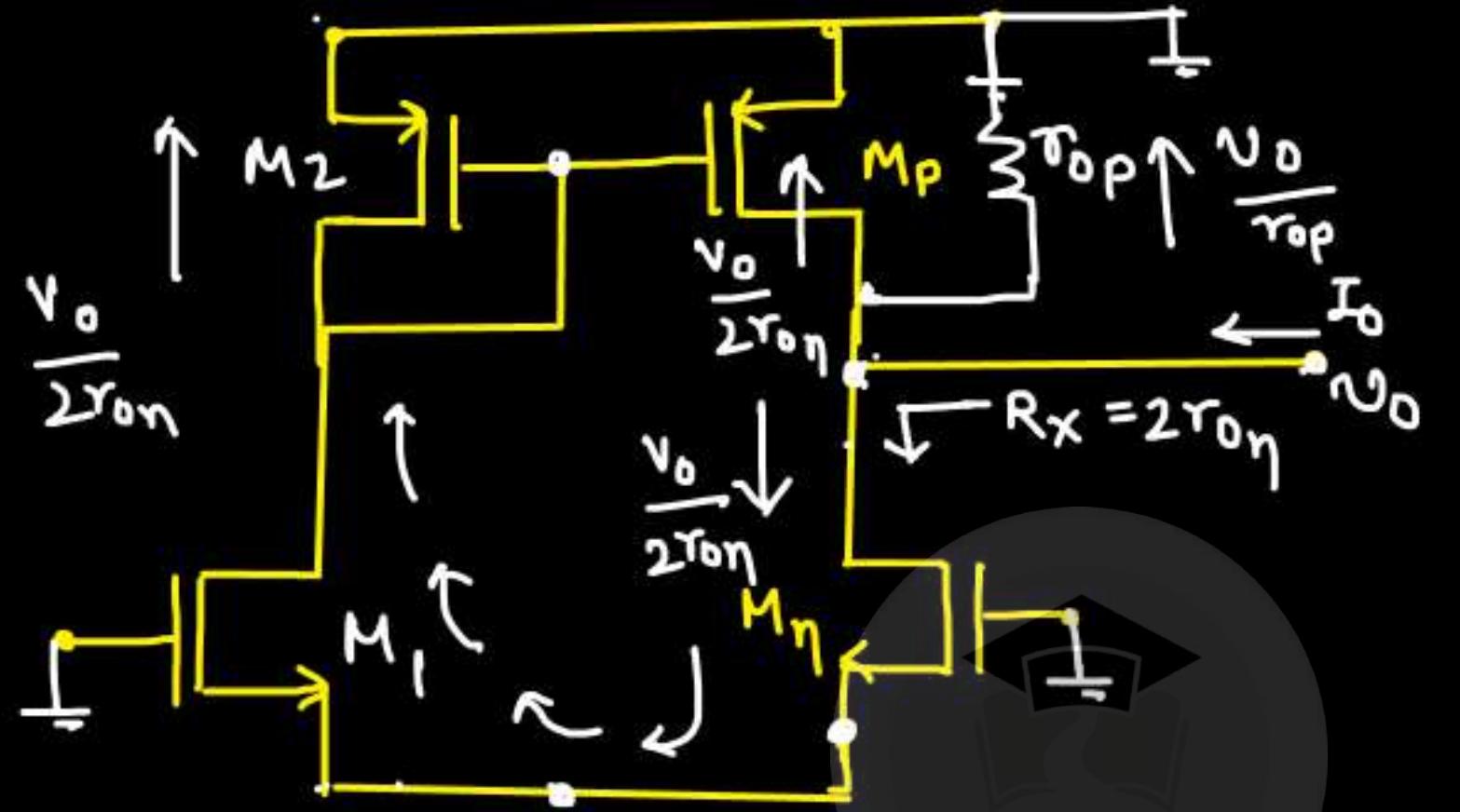
$$R_x = 2r_{0\eta} + \frac{1}{g_{m\eta}} \approx 2r_{0\eta}$$



PrepFusion

$$\frac{V_o}{\tau_{op}} + \frac{V_o}{2\tau_{o\eta}} + \frac{V_o}{2\tau_{o\eta}} = I_o \Rightarrow \frac{V_o}{\tau_{op}} + \frac{V_o}{\tau_{o\eta}} = i_o$$

$$\frac{V_o}{i_o} = R_{out} = \tau_{op} \parallel \tau_{o\eta}$$

\approx High (Not Desired)


$$A_V = g_m n (r_{op} \parallel r_{on}) \Rightarrow \text{High}$$

(desired)


Input impedance $R_i = \infty \Rightarrow \text{High}$

(desired)

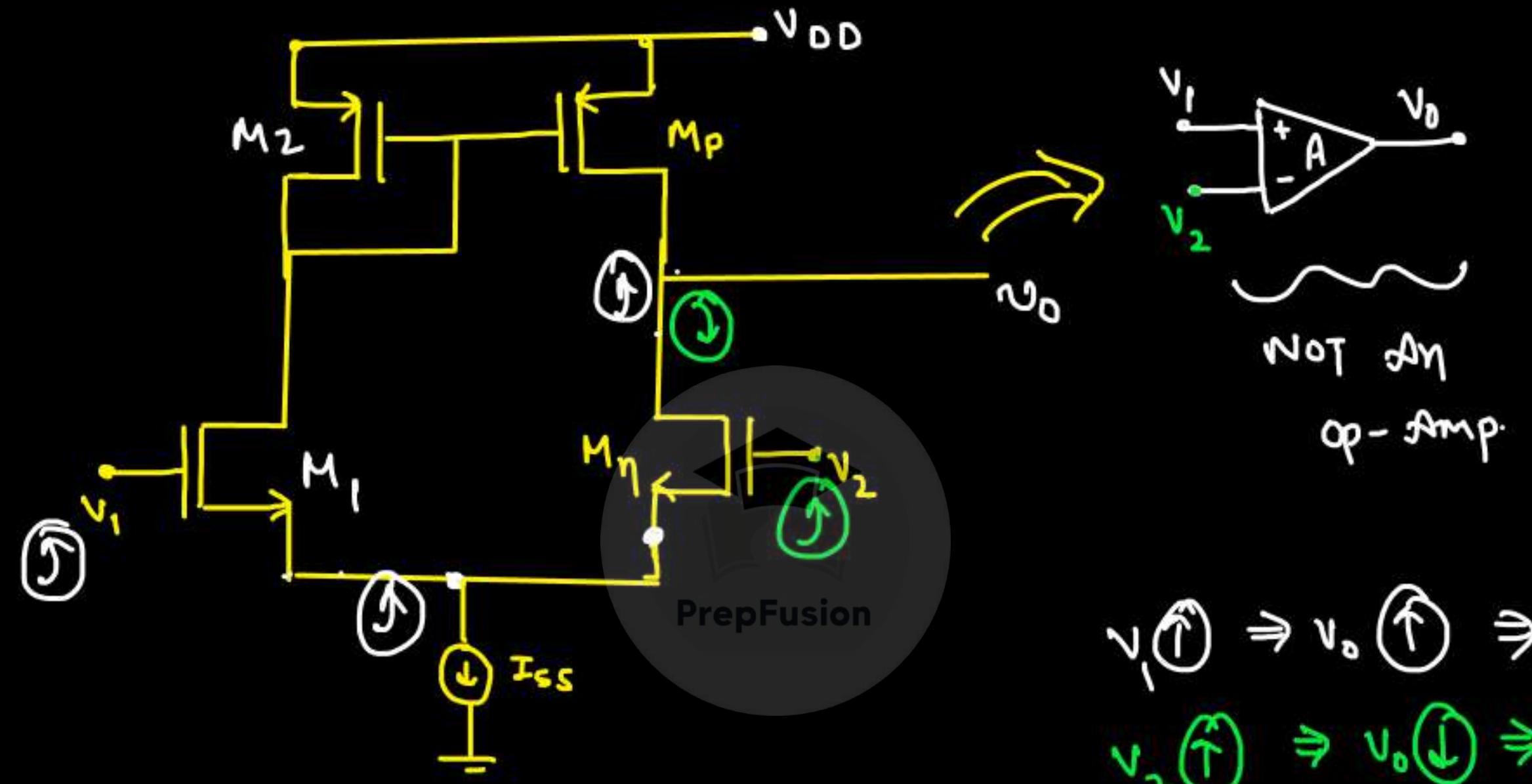
Matter of concern \Rightarrow O/P impedance



① Common Source

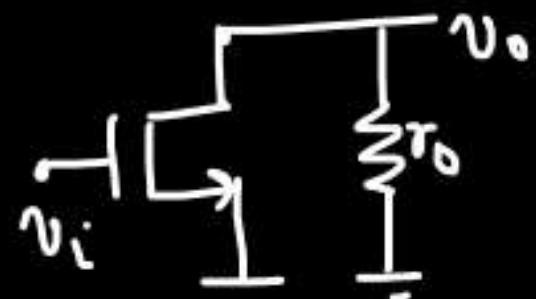

② Common Gate

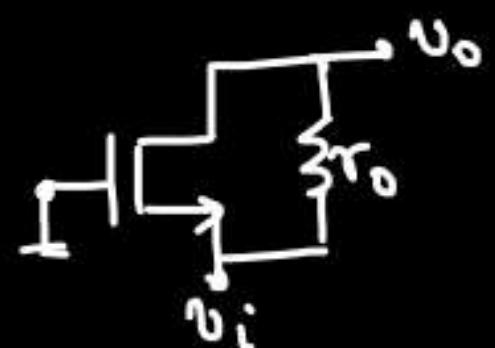

③ Common drain



Gain

$$-g_m r_o$$

o/p impedance

$r_o \rightarrow \text{High}$


$$1 + g_m r_o$$

PrepFusion


$r_o \rightarrow \text{High}$

$$\frac{g_m r_o}{1 + g_m r_o} \approx 1$$
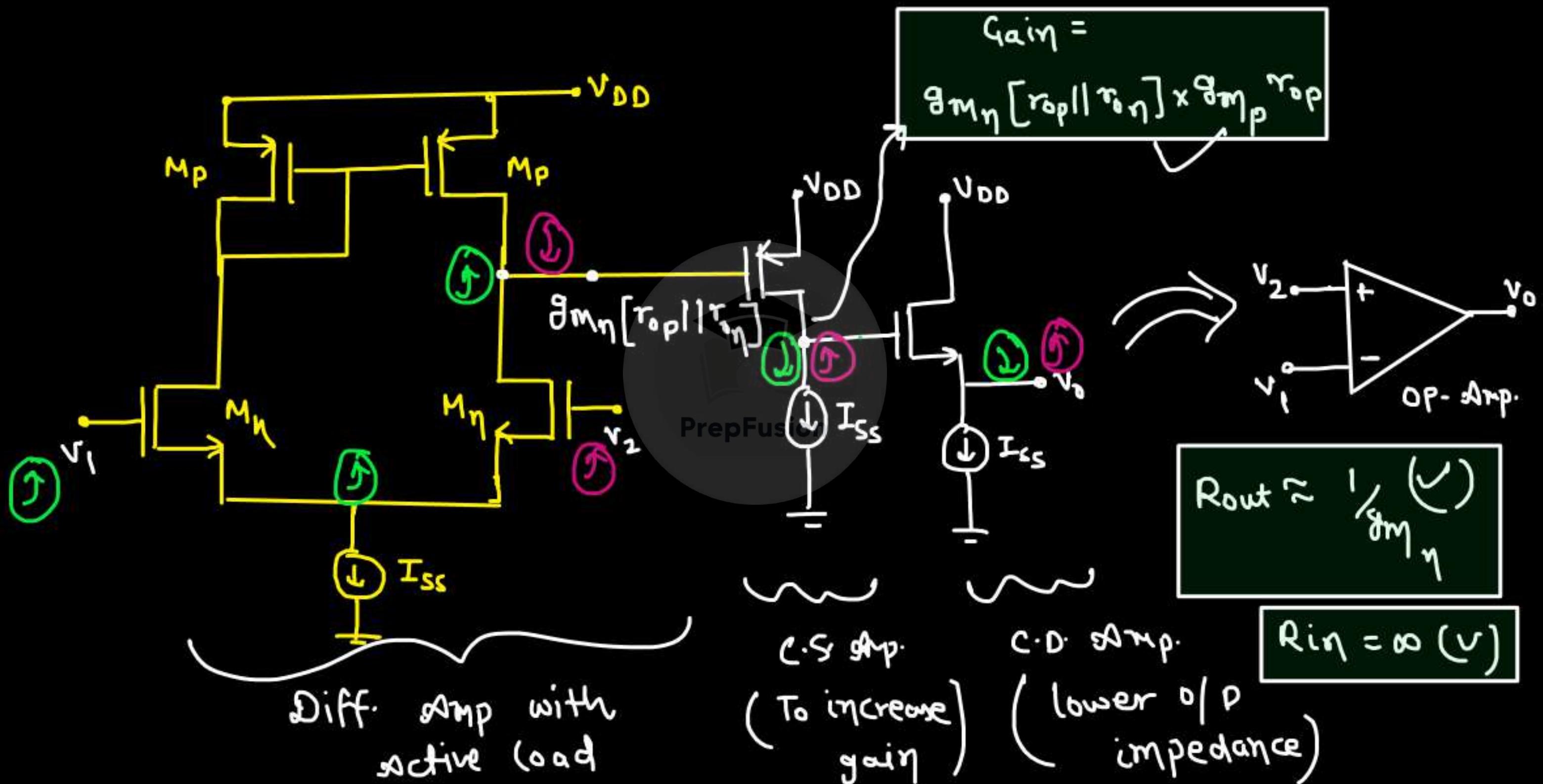
$$r_o \parallel \frac{1}{g_m} \approx \frac{1}{g_m} \rightarrow \text{low}$$



Final design :-

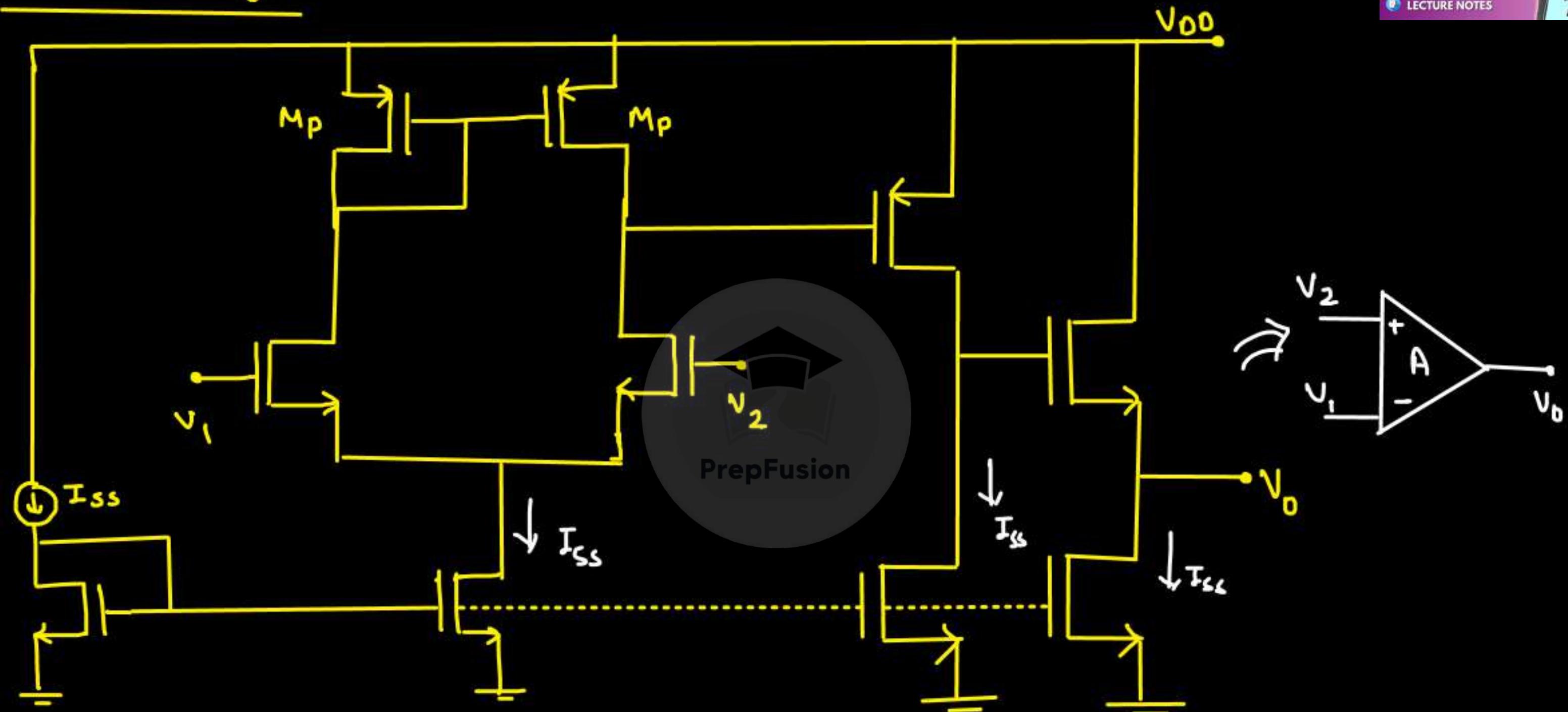



Some Basics of OP-Amp:-

$$V_o = A V_d$$

$$-V_{sat} < V_o < +V_{sat}$$

$$-V_{sat} < A V_d < +V_{sat}$$
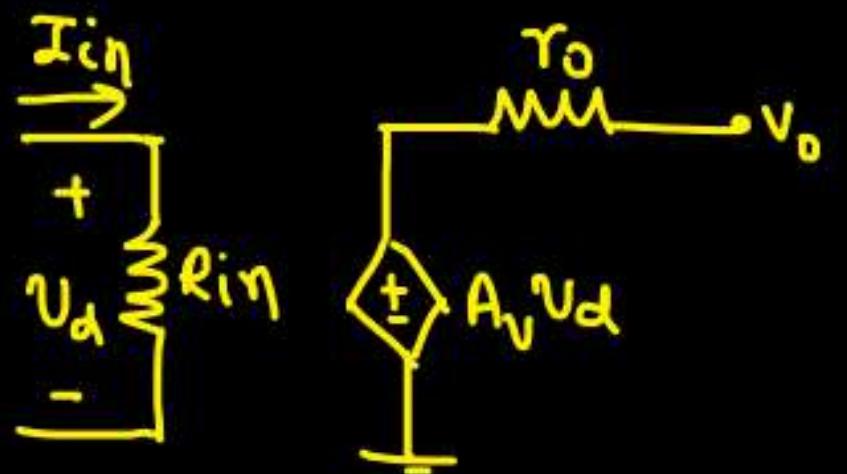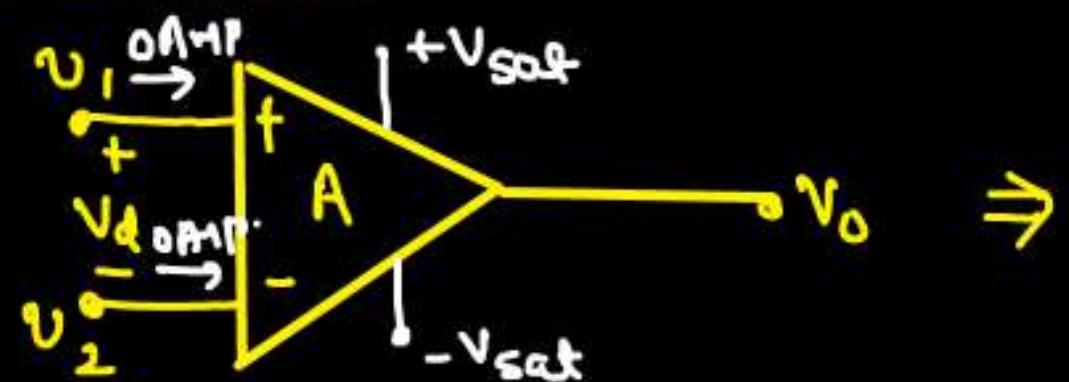
$$\frac{-V_{sat}}{A} < V_d < \frac{+V_{sat}}{A}$$



$$V_o = A (V_1 - V_2)$$

$\text{V}_+ = \text{V}_1 \uparrow \Rightarrow \text{V}_o \uparrow$
 $\text{V}_- = \text{V}_2 \uparrow \Rightarrow \text{V}_o \downarrow$

* For an OP-amp, o/p can never go above tve Sat. voltage. and can never go below -ve sat. voltage

For an ideal op-amp \Rightarrow

$$\begin{aligned} R_{in} &= \infty \\ I_{in} &= 0 \\ r_o &= 0 \\ A_v &= \infty \end{aligned}$$

$$\text{CMRR} = \infty$$

$$\text{slew rate} = \infty$$

Let, $A = 10^3 \text{ V/V}$; $\pm V_{\text{sat}} = \pm 5 \text{ V}$

$$(i) V_d = 1 \text{ mV}$$

$$V_o = AV_d = 10^3 \times 1 \text{ mV} = 1 \text{ V}$$

$$(ii) V_d = -3 \text{ mV}$$

$$V_o = -3 \text{ mV} \times 10^3 = -3 \text{ V}$$

$$(iii) V_d = -5 \text{ mV}$$

$$V_o = -5 \text{ mV} \times 10^3 = -5 \text{ V}$$

$$(iv) V_d = 7 \text{ mV}$$

$$V_o = 7 \text{ mV} \times 10^3 = 7 \text{ V} \times 5 \Rightarrow 35 \text{ V}$$




$$(v) V_d = -6 \text{ mV}$$

$$\begin{aligned} V_o &= -6 \text{ mV} \times 10^3 \\ &= -6 \text{ V} \times \\ &\Rightarrow -5 \text{ V} \end{aligned}$$

$$V_o = A V_d$$

$$\frac{V_o}{V_d} = A$$


$$\tan \theta = A$$

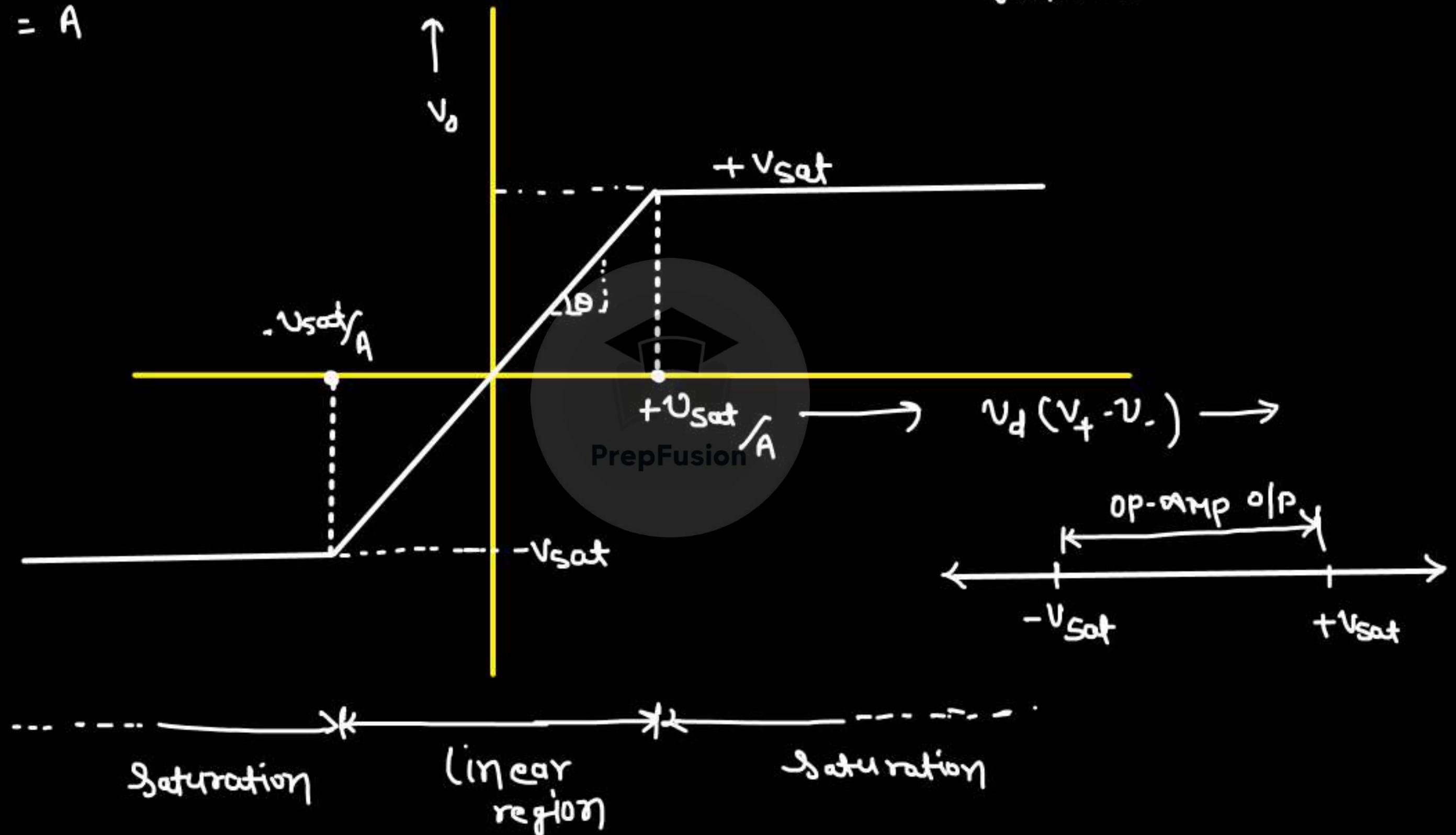

Feedback:-

Taking a fraction of the o/p of an amplifier and connecting it back to the i/p. This fed-back signal can be connected in a way that it either adds to the normal input or subtracts from it.


System w/o any feedback:-

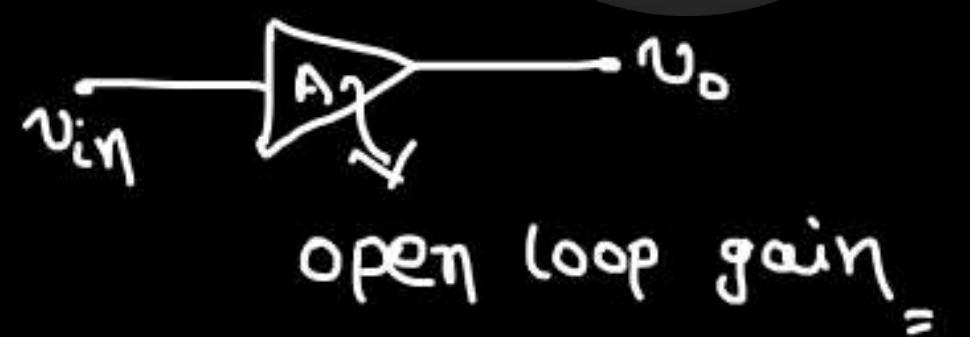

open loop gain =

$$v_o = A v_{in}$$

① Positive feedback :-

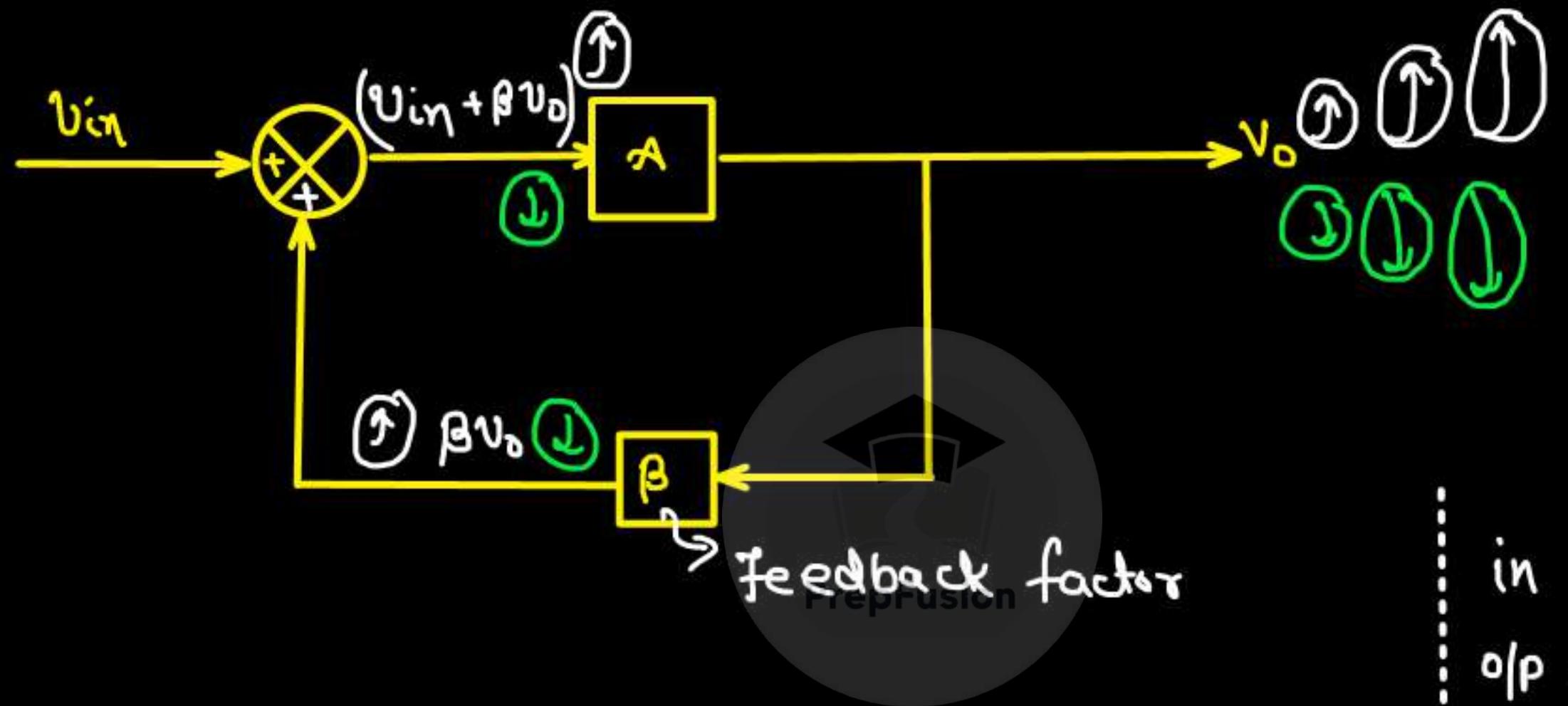

$$V_o = A(V_{in} + \beta V_o)$$

$$V_o - A\beta V_o = AV_{in}$$


$$\frac{V_o}{V_{in}} = \frac{A}{1-A\beta}$$

Closed loop gain

in positive fib, if
o/p increases, then it
keeps on increasing
and results in unstable
o/p.

positive fib s/s are
unstable.

② Negative feedback:-

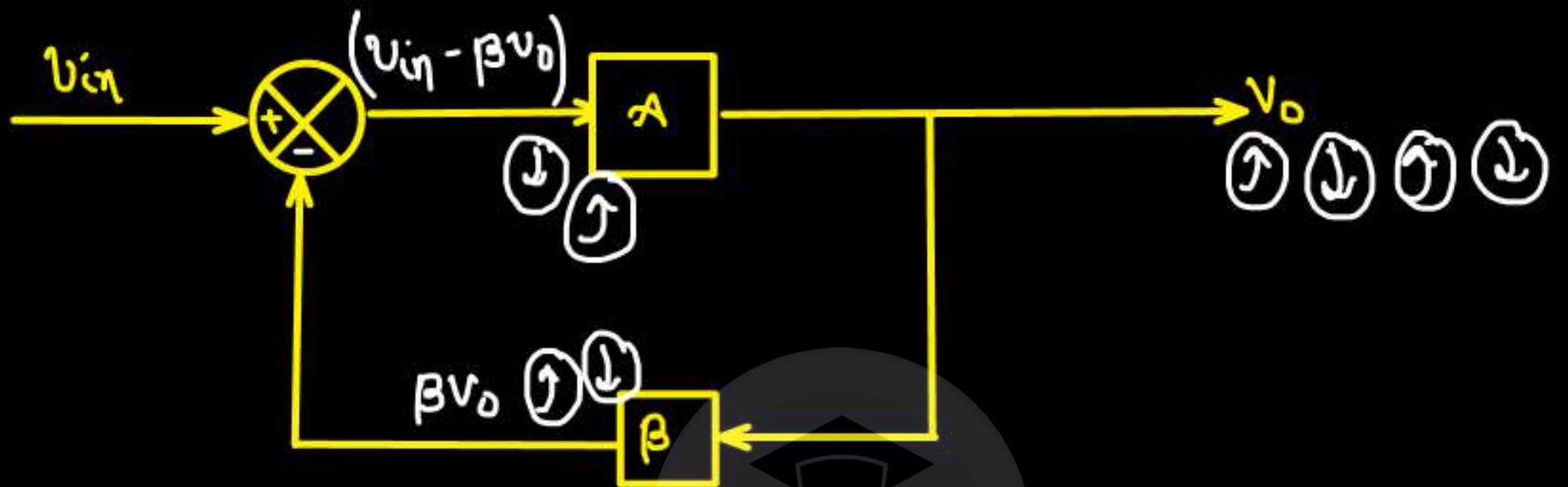


$$(V_{in} - \beta V_o) A = V_o$$

$$\frac{V_o}{V_i} = \frac{A}{1 + A\beta} \text{ closed loop gain}$$

in negative f/b, you get
a stable o/p.


Eg →

①

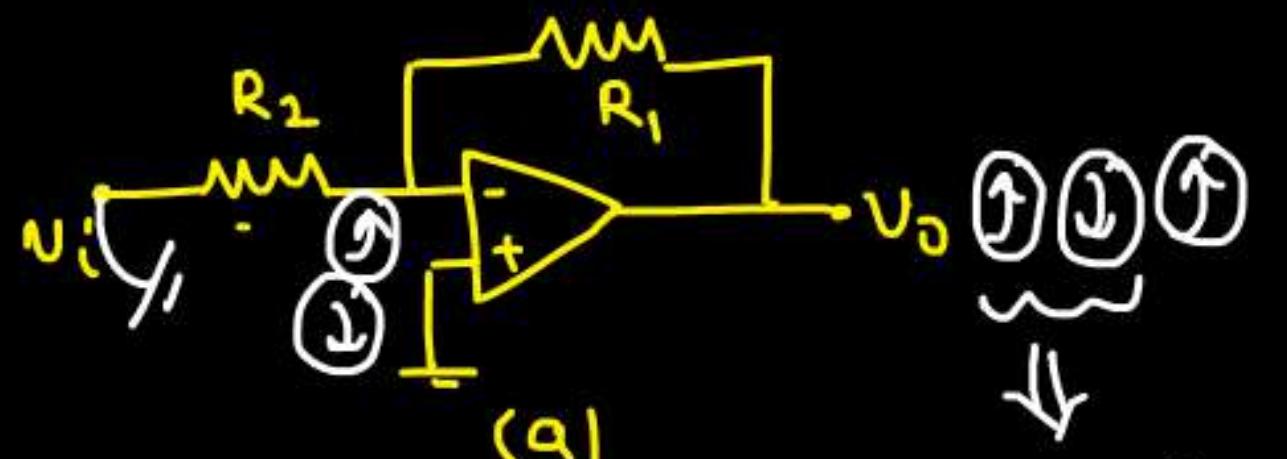


(a)

↓
Negative f/b

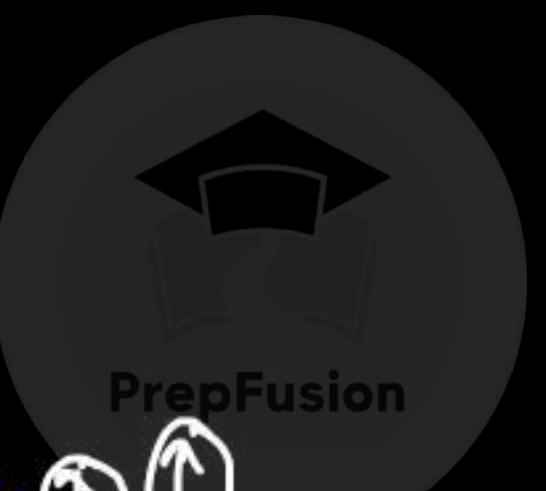

PrepFusion

②

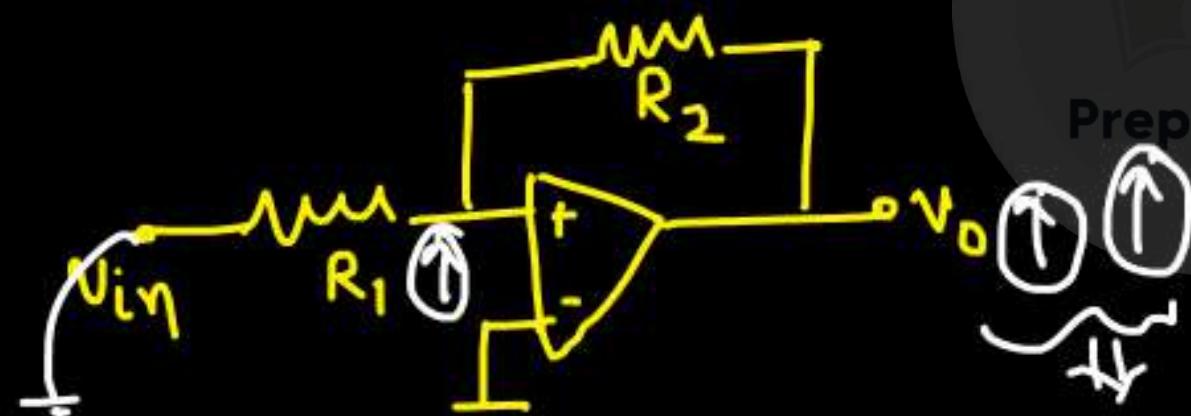


positive f/b

$$V_o = A(V_+ - V_-)$$

When you check
the type of f/b,
nullify the i/p

* Advantages of feedback:-

1. Gain stability:-

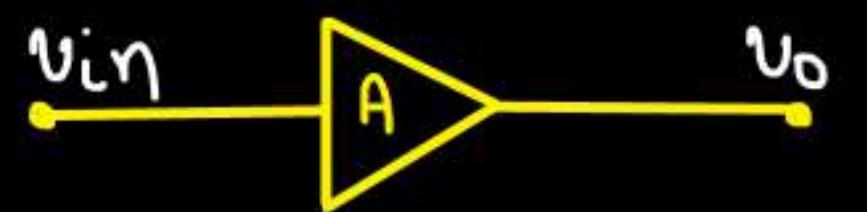


open-loop

$$V_o = A V_{in}$$

Let's assume, your gain $A = 10^3 \rightarrow 10^4$
Let; $V_{in} = 1mV$

$$\begin{aligned} V_o &= A V_{in} \\ &= 1V \rightarrow 10V \end{aligned}$$

Introducing negative f/b :-

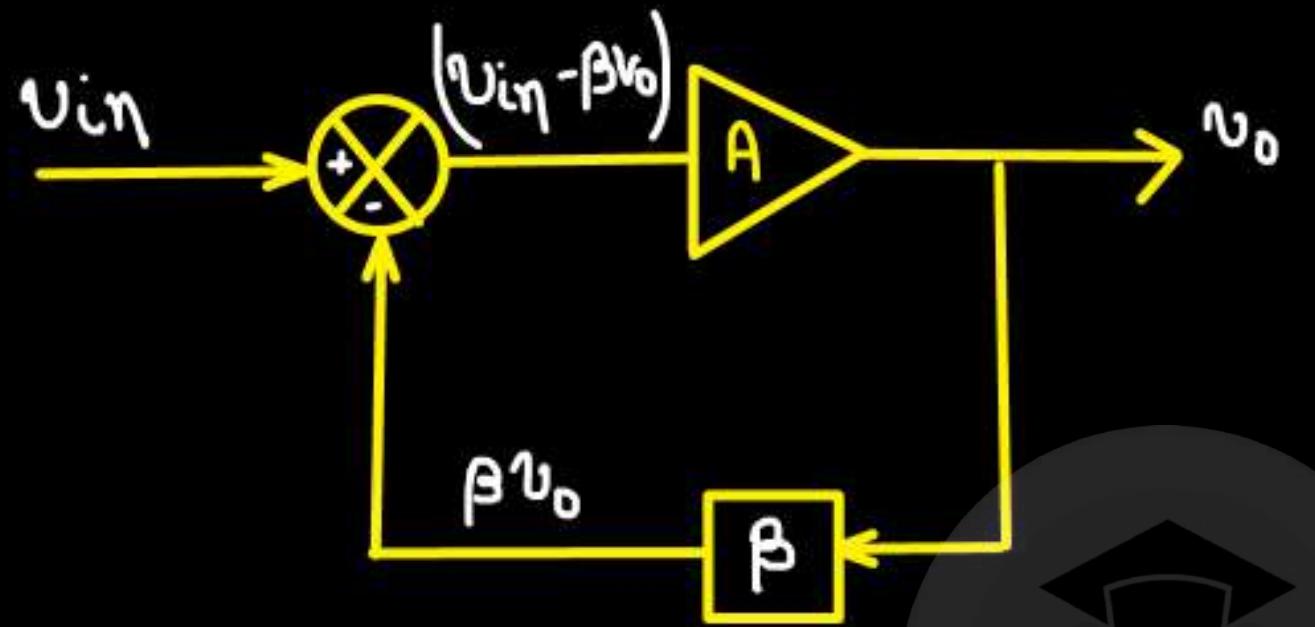

$$V_o = A(V_{in} - \beta V_o)$$

$$\frac{V_o}{V_{in}} = \frac{A}{1 + AB}$$


β is designed such that $\alpha\beta \gg 1$

$$\frac{V_o}{V_{in}} \approx \frac{A}{\alpha\beta} \approx \frac{1}{\beta} \Rightarrow \text{constant}$$

\Rightarrow Here you are getting a constant gain.

Example:-


Before f/b:-

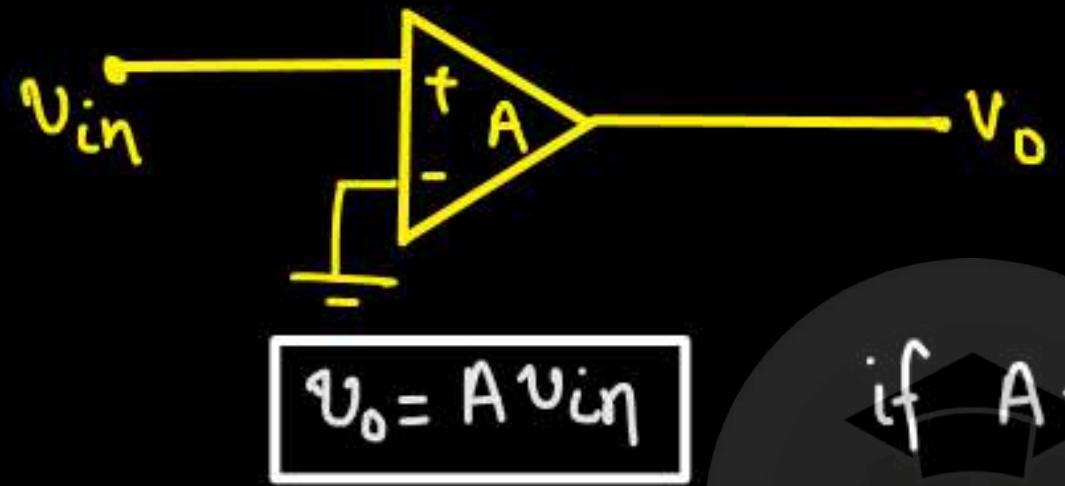

if $A \rightarrow \text{variable}$, then $V_o \rightarrow \text{variable}$

PrepFusion

After f/b:-

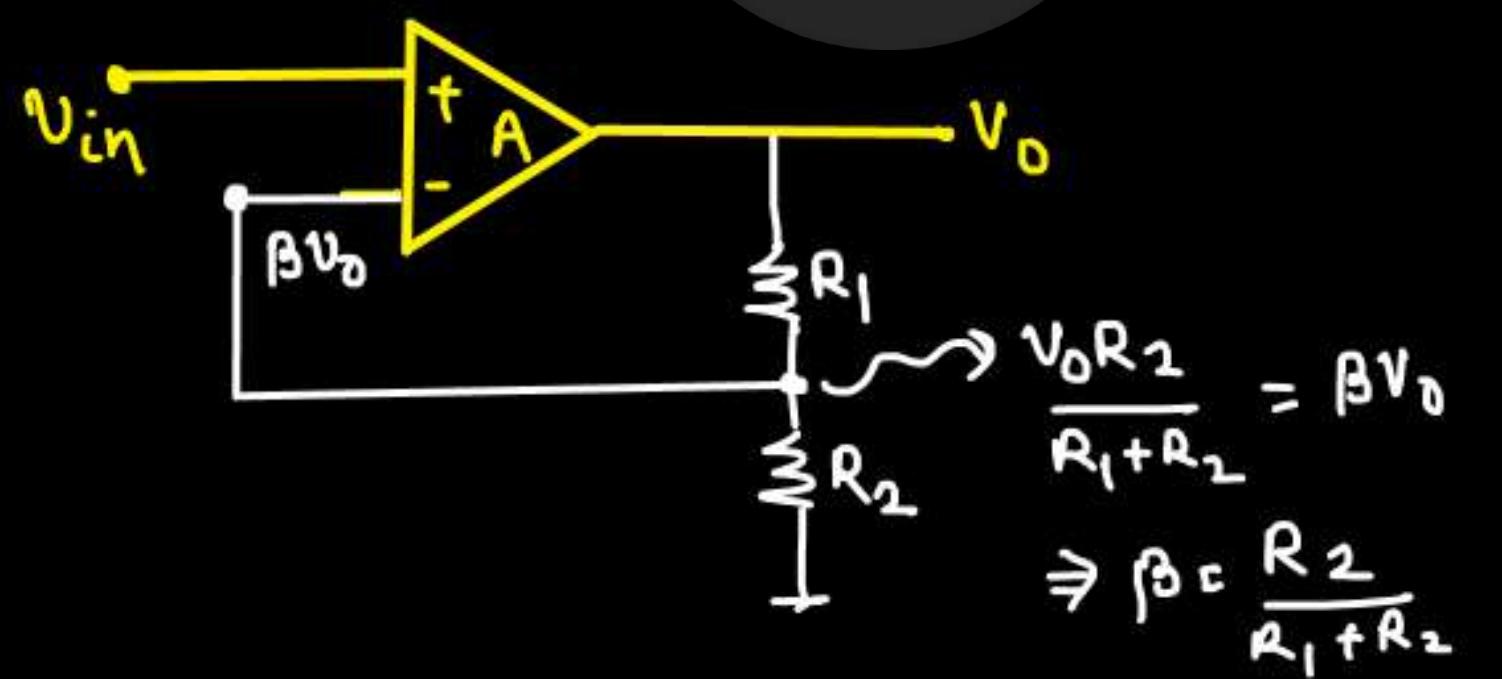

$$(V_{in} - \beta V_o) A = V_o$$

$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta}$$

$$\frac{V_o}{V_{in}} \approx \frac{1}{\beta} = 1 + \frac{R_1}{R_2}$$

⇒ Loop gain :-

$$(A_v)_{w/o \text{ f/b}} = A \rightarrow \text{open loop gain}$$

$$(A_v)_{\text{with neg f/b}} = \frac{A}{1 - A\beta} \rightarrow \text{closed loop gain}$$

$A\beta = \text{Loop gain}$

PrepFusion

Q. An Amplifier is connected in negative f/b.
if the percentage change is open loop gain is
10%. then what will be the % change in closed
loop gain. Loop gain is 99.



$$\text{Closed loop gain } A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} \quad \textcircled{1}$$

$$\frac{DA_{OL}}{A_{OL}} \times 100\% = 10\%$$

$$\frac{DA_{OL}}{A_{OL}} = 0.1$$

$$\frac{DA_{CL}}{A_{CL}} = ?$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$$

$$\Delta A_{CL} = \frac{(1 + A_{OL}\beta) \Delta A_{OL} - A_{OL}\beta \Delta A_{OL}}{(1 + A_{OL}\beta)^2}$$

$\beta \rightarrow \text{constant}$

$$\Delta A_{CL} = \frac{\Delta A_{OL}}{(1 + A_{OL}\beta)^2}$$

$$\frac{\Delta A_{CL}}{A_{CL}} = \frac{\Delta A_{OL}}{(1 + A_{OL}\beta)^2} \times \frac{(1 + A_{OL}\beta)}{A_{OL}}$$

$$\left\{ A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} \right\}$$

**

$$\boxed{\frac{\Delta A_{CL}}{A_{CL}} = \frac{\Delta A_{OL}/A_{OL}}{(1 + \alpha\beta)}}$$

Given $\alpha\beta = 99$


$$\frac{\Delta A_{CL} \cdot 1}{A_{CL}} = \frac{\Delta A_{OL}/A_{OL} \cdot 1}{1 + 99}$$

$$= \frac{10 \cdot 1}{100}$$


$$\frac{\Delta A_{CL}}{A_{CL}} = 0.1 \cdot 1$$

PrepFusion

Q. Increase in $B\cdot\omega_0$:-

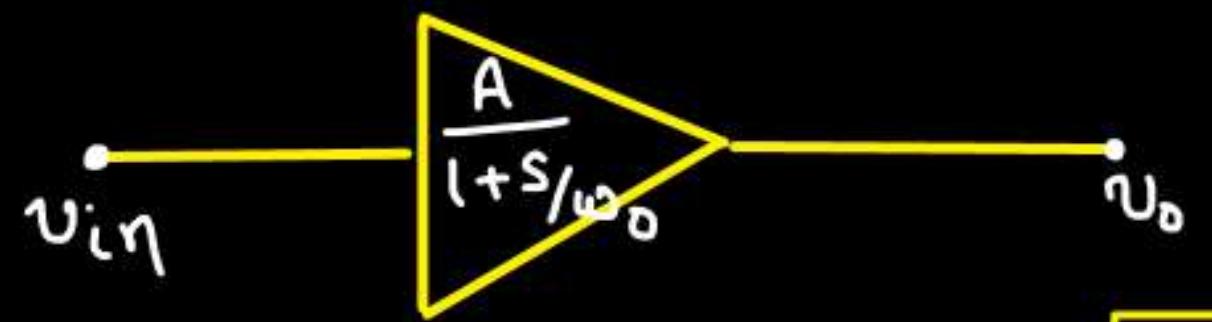

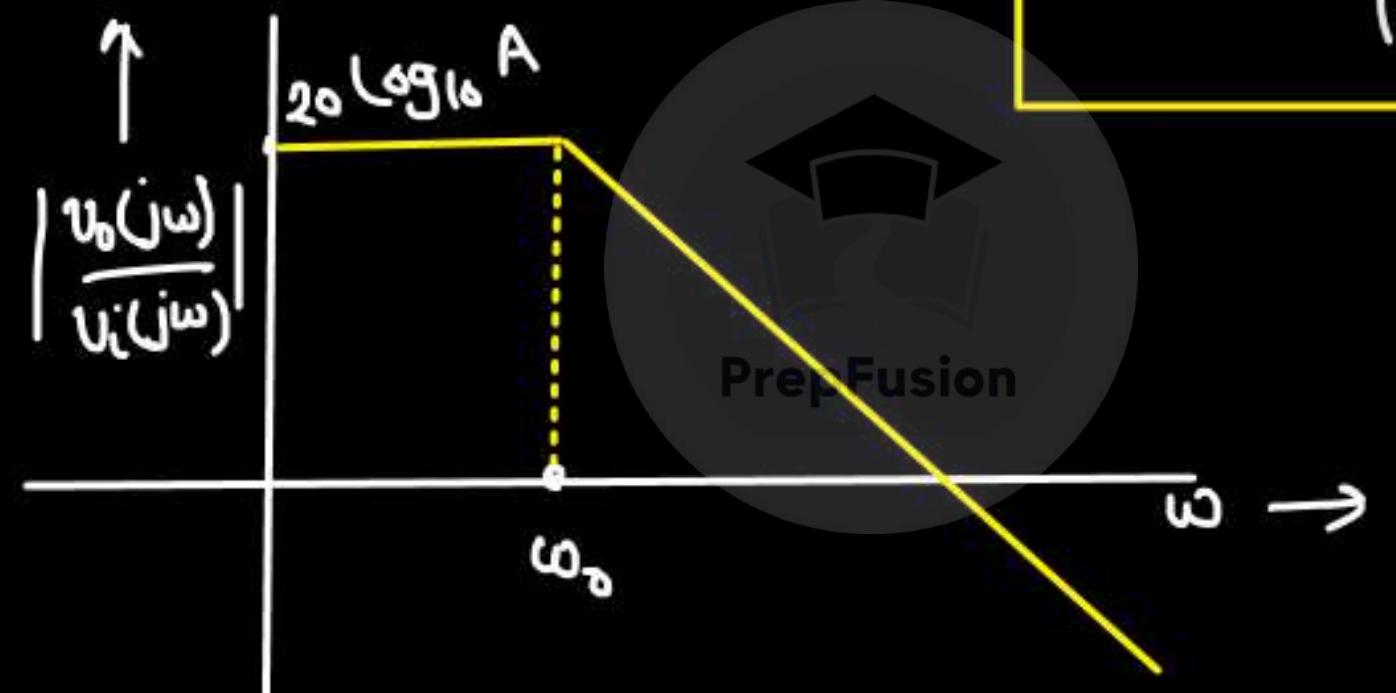
$$u_o(s) = \frac{A}{1+s/\omega_0} u_i(s)$$



$B\cdot\omega_0 = \omega_0 \{ \text{getting a good gain} \}$

Introducing feedback:-

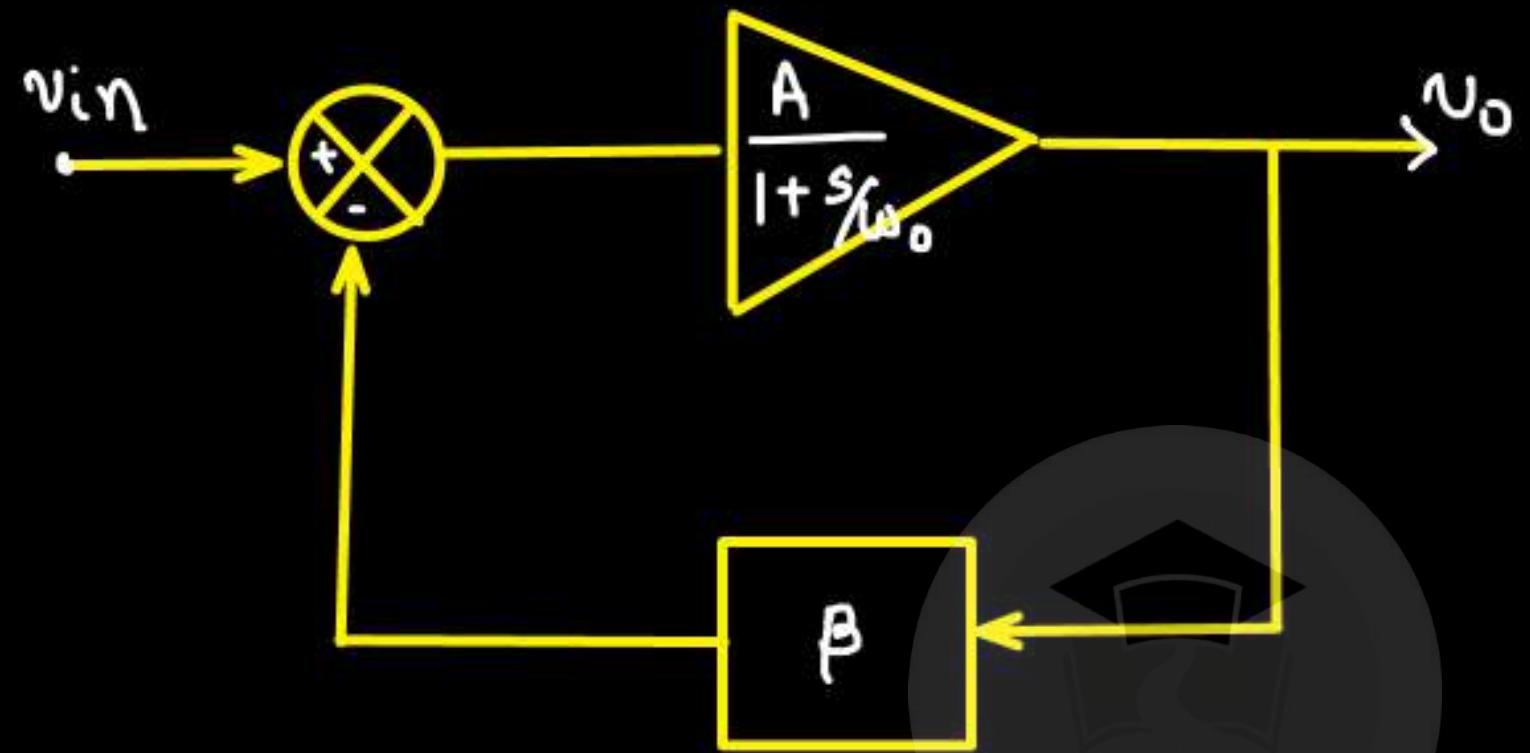

$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{A}{1+s/\omega_0}}{1 + \frac{\alpha\beta}{1+s/\omega_D}} = \frac{A}{A\beta + 1 + s/\omega_D} = \frac{A\omega_0}{s + \omega_0(1 + A\beta)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\omega_0}{s + \omega_0(1 + \alpha\beta)}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{A}{1 + \alpha\beta}}{\frac{s}{\omega_0(1 + \alpha\beta)} + 1}$$

dc gain = $\frac{A}{1 + \alpha\beta}$


PrepFusion

Bandwidth = $\omega_0(1 + \alpha\beta)$

For open loop:- DC gain = A , $B \cdot \omega_c = \omega_0$


For closed loop:- DC gain = $\frac{A}{1 + \alpha\beta}$, $B \cdot \omega_c = \omega_0(1 + \alpha\beta)$

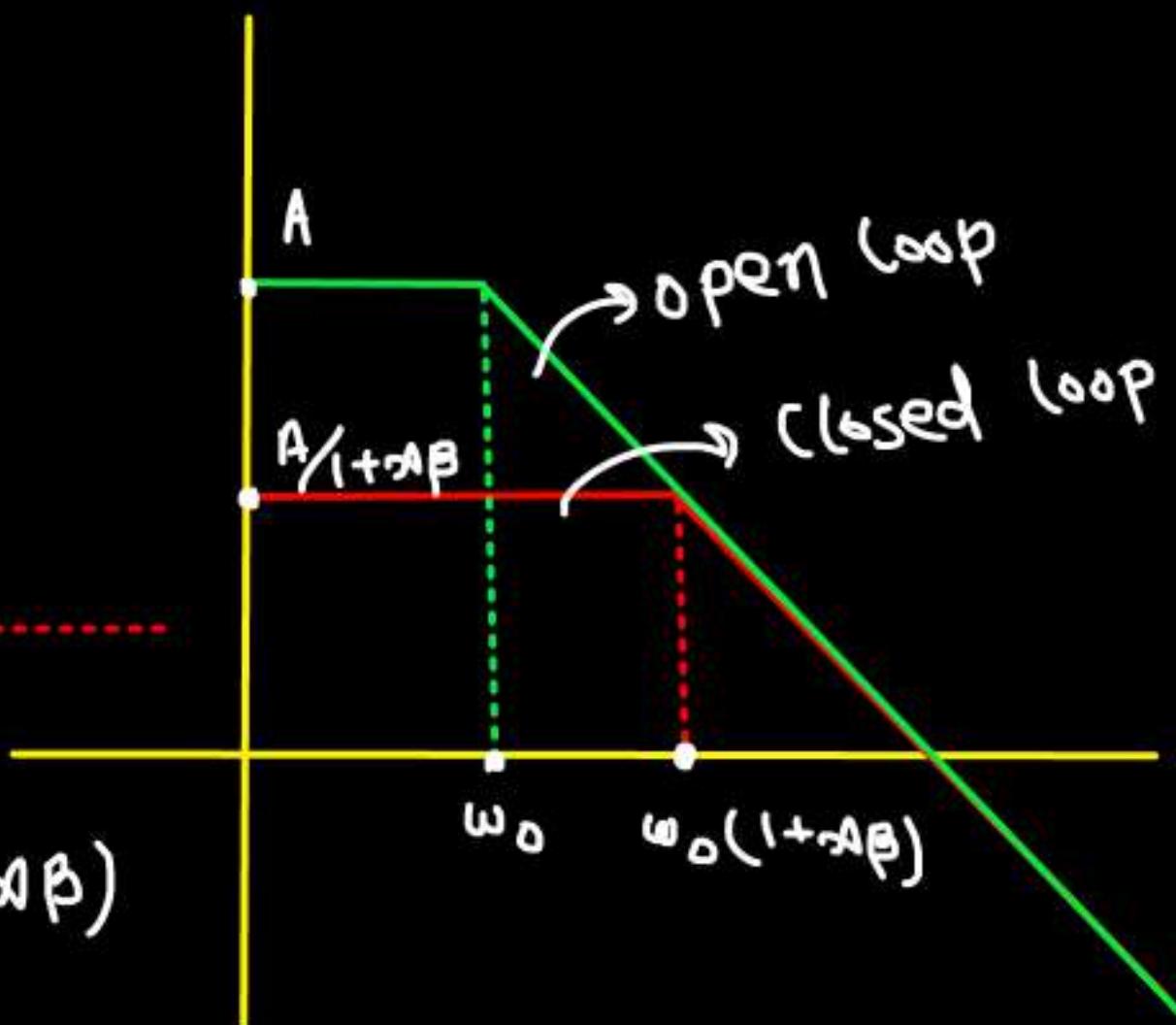in both cases $G_B \cdot \omega_c = \alpha\omega_0$




(iii) Increase in linearity:-

Before f/b:-

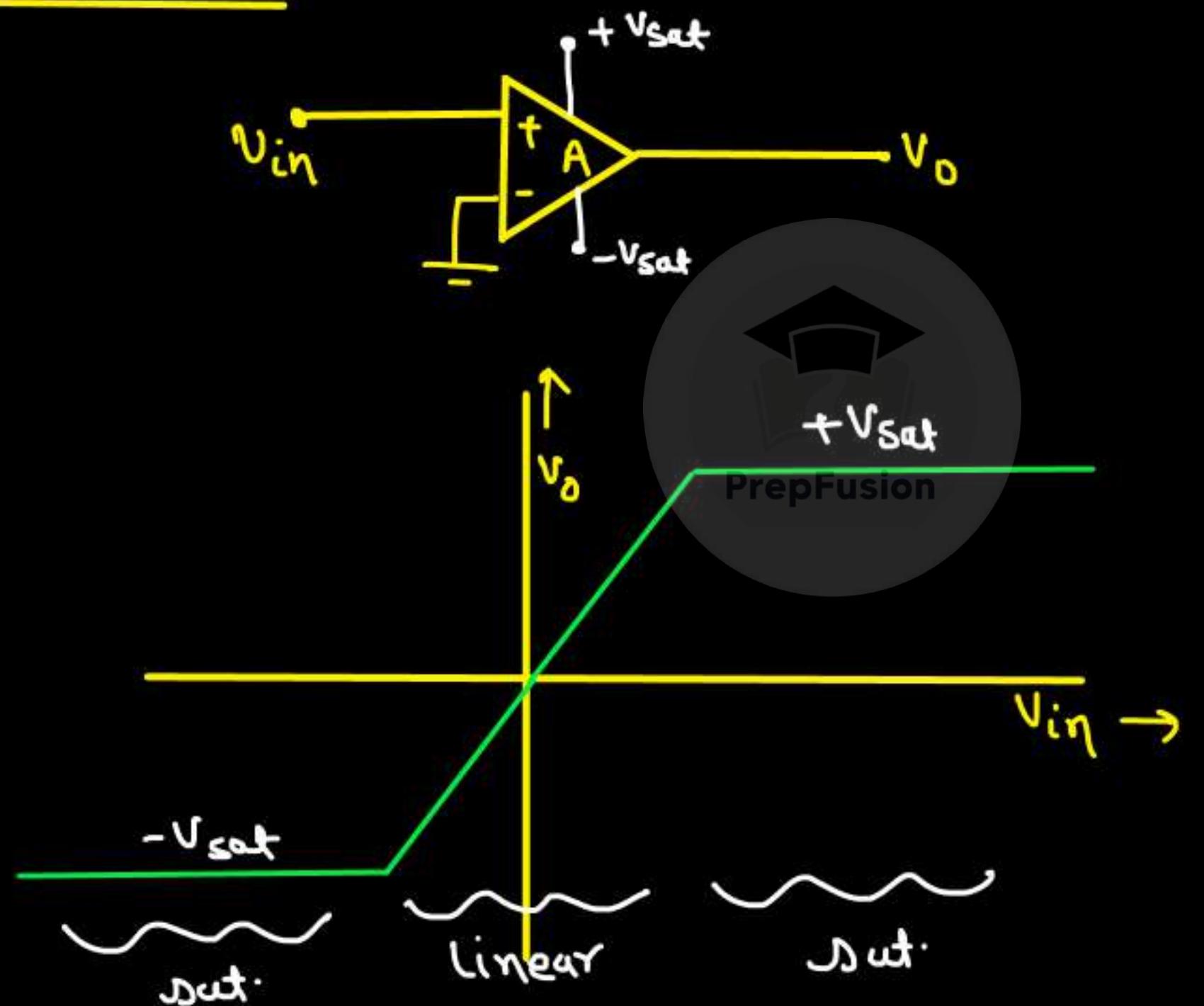


After f/b:-

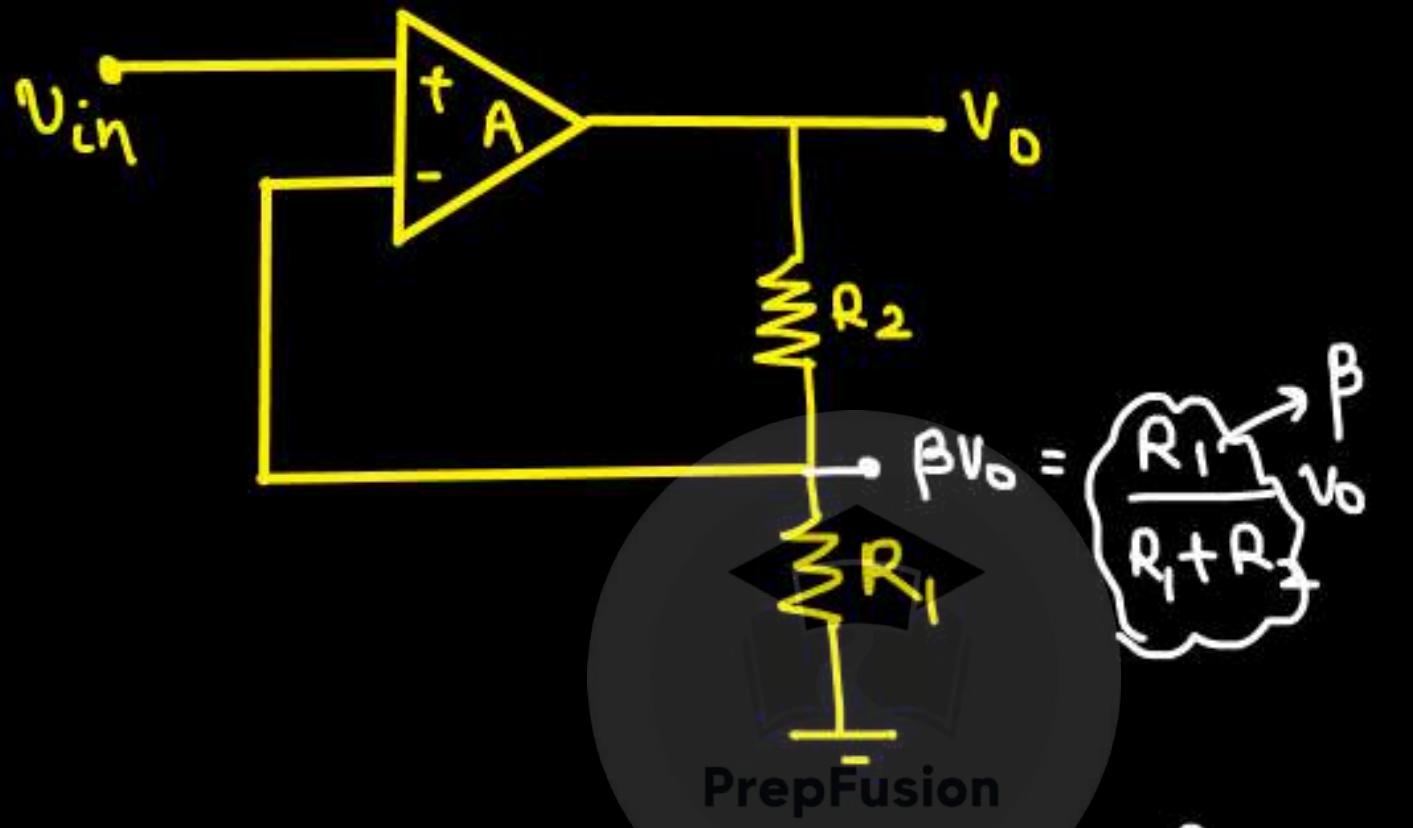

$$\frac{V_o}{V_{in}} = \frac{A}{1 + A\beta} \approx \frac{1}{\beta} = \frac{1 + R_2}{R_1}$$
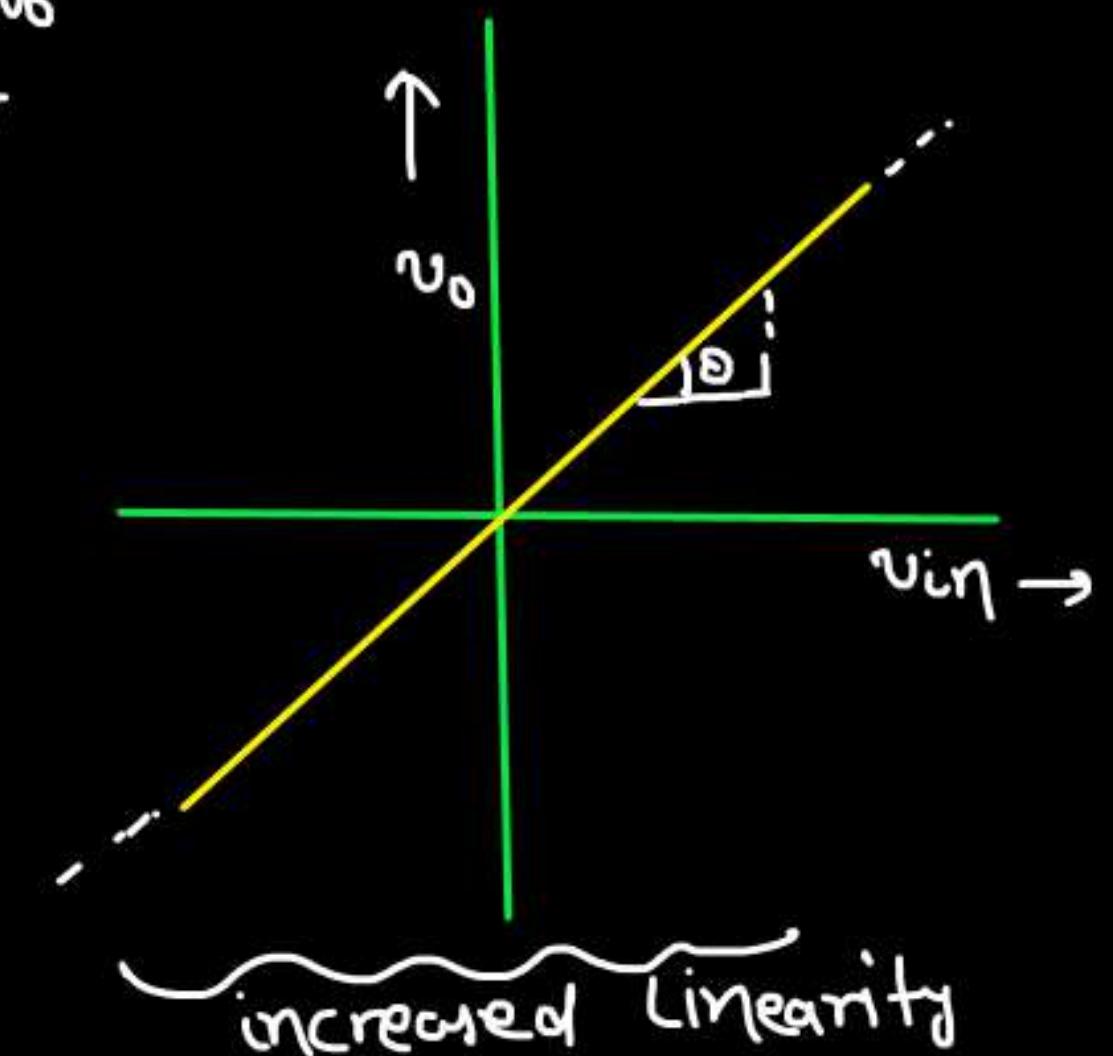
$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$



⇒ In Negative f/b:-

- ① S/S → stable [Gain is constant]
- ② Gain → Reduces
- ③ $B \cdot \omega$ → Increases
- ④ Linearity → Increases
- ⑤ Time constant → decreases $\left[B \cdot \omega \propto \frac{1}{\tau} \right]$

PrepFusion

* open loop gain = A


After f/b:-

$$\text{(i) Closed loop gain (Neg f/b)} = \frac{A}{1 + A\beta} = \frac{\text{open loop gain}}{1 + \text{loop gain}}$$

$$\text{(ii) Closed loop gain (pos f/b)} = \frac{A}{1 - A\beta} = \frac{\text{open loop gain}}{1 + (\text{loop gain})}$$


PrepFusion

* How to find loop gain?

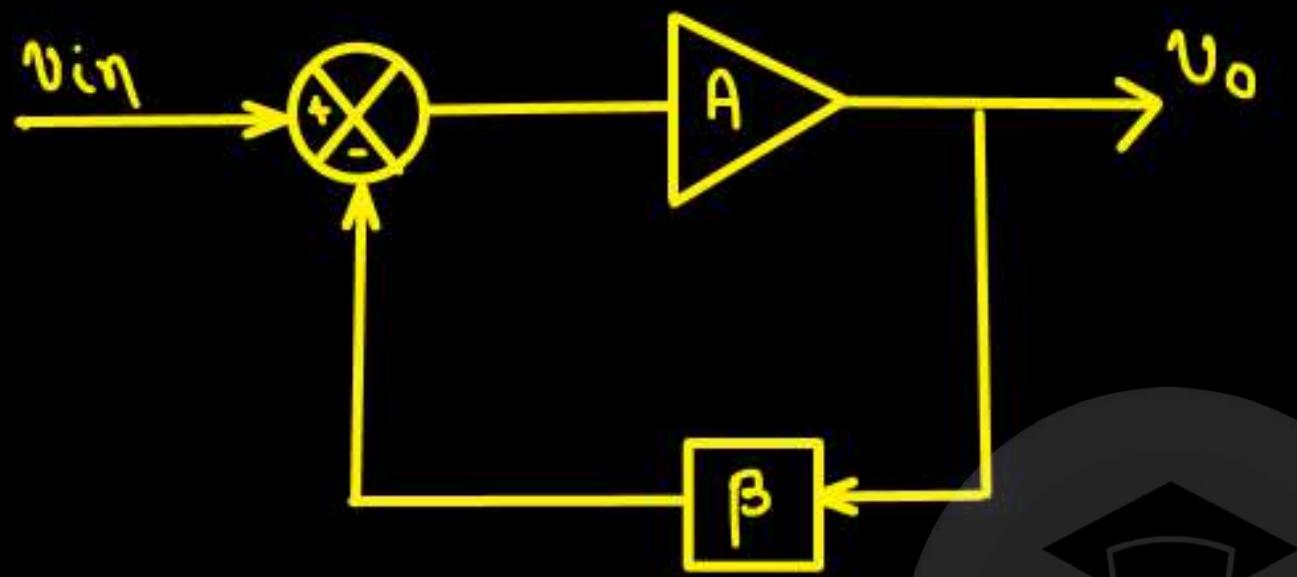

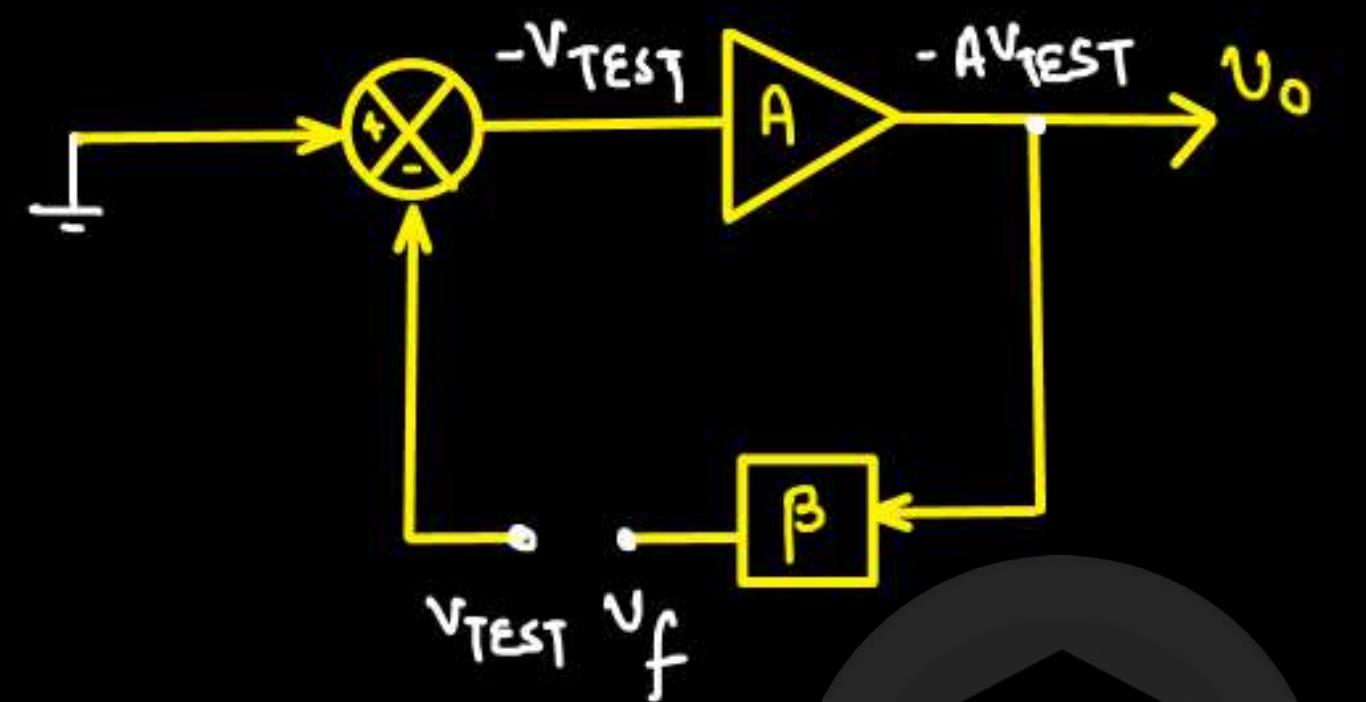- (i) Nullify the IP.
- (ii) Break the loop in feedback path.
- (iii) Mark the open end as v_f and v_{TEST} . (v_{TEST} should go towards the input side)
- (iv) Loop gain $\alpha\beta = -\frac{v_f}{v_{TEST}}$






$$V_f = -\beta(AV_{TEST})$$


PrepFusion

$$\frac{-V_f}{V_{TEST}} = \alpha\beta$$

Example:

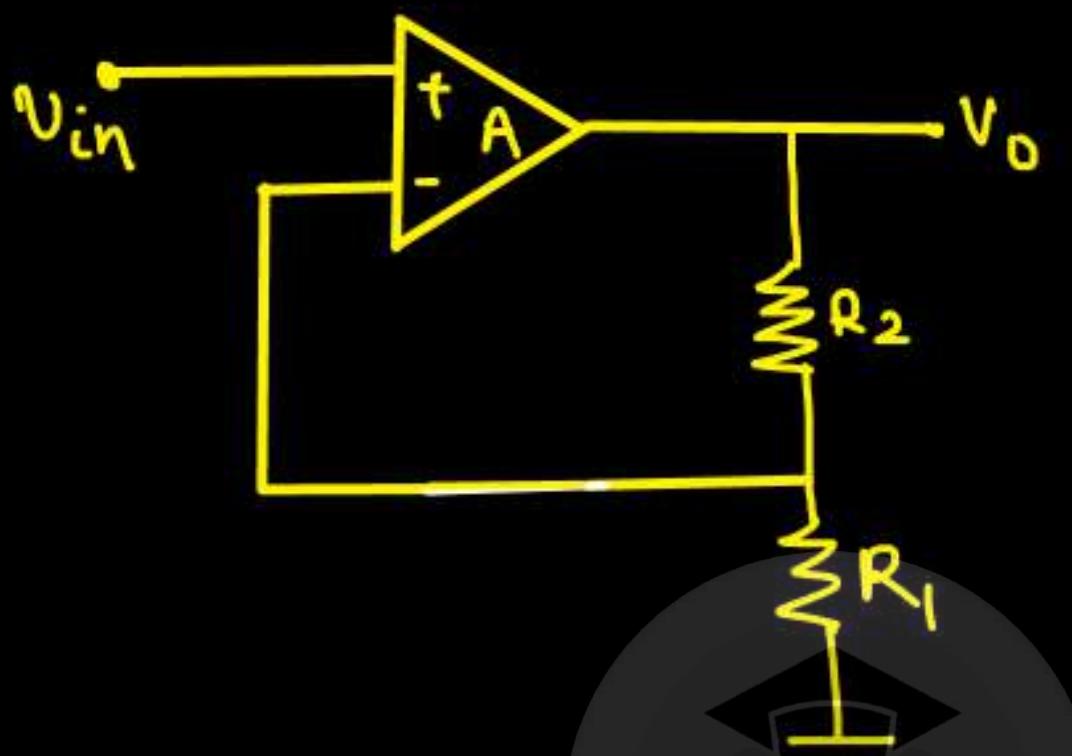

loop gain = ?

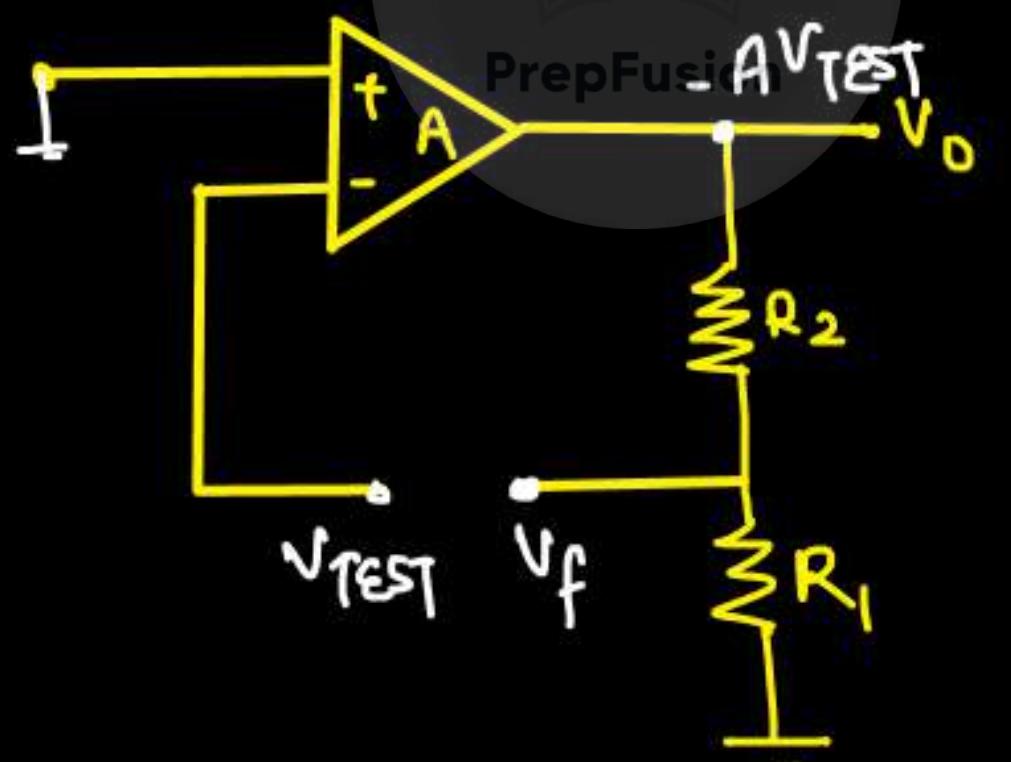

$$-AV_{TEST} \times \frac{R_1}{R_1 + R_2} = V_f$$


$$\boxed{-\frac{V_f}{V_{TEST}} - \text{loop gain} = \frac{AR_1}{R_1 + R_2}}$$

Types of Amplifiers:-


- (i) Voltage amplifiers :-
- (ii) Transresistance amplifiers:-
- (iii) Transconductance amplifiers:-
- (iv) Current amplifiers:-



(i) Voltage Amplifiers:-

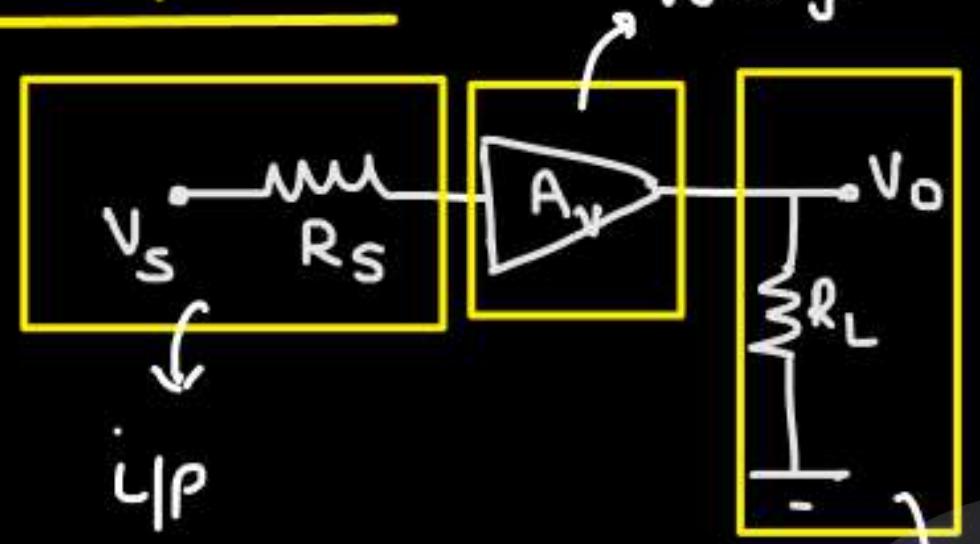

O/P

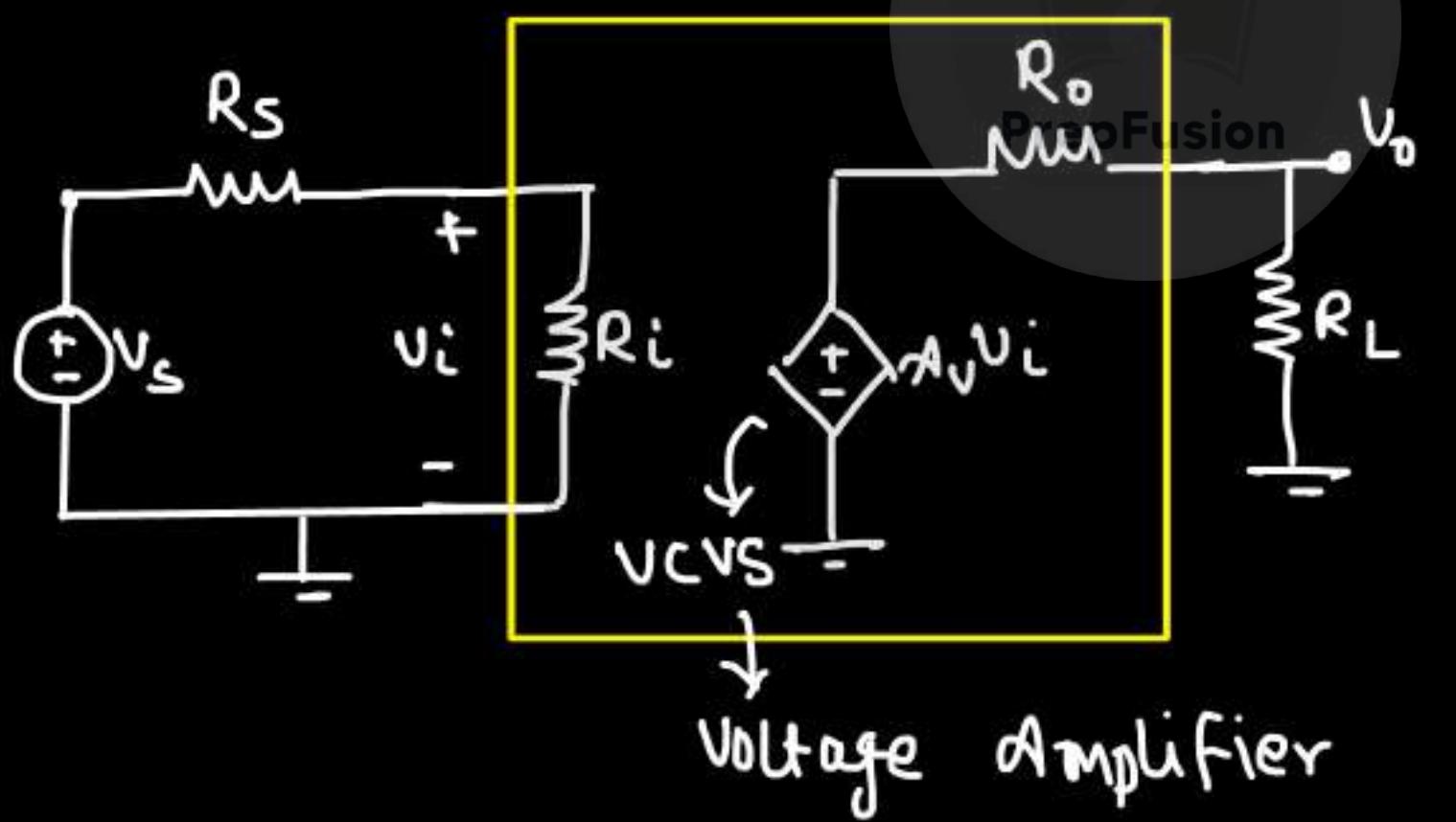

$$V_i = \frac{R_s}{R_s + R_L} V_s$$

$$V_o = \frac{A_v \times V_i \times R_L}{R_L + R_o}$$

$$V_o = A_v \left[\frac{R_s}{R_s + R_L} \right] V_s \times \frac{R_L}{R_L + R_o}$$

$$\frac{V_o}{V_s} = A_v \left[\frac{R_i}{R_i + R_s} \right] \left[\frac{R_L}{R_L + R_o} \right]$$

For an ideal voltage amplifier :-

* * *

$R_i = \infty$	\rightarrow High
$R_o = 0$	\rightarrow Low


if $R_i = \infty$, $R_o = 0$

$$\frac{V_o}{V_s} = A_v$$




Unit of $A_v = \frac{V}{V}$

(iii) Trans-resistance amplifier:-

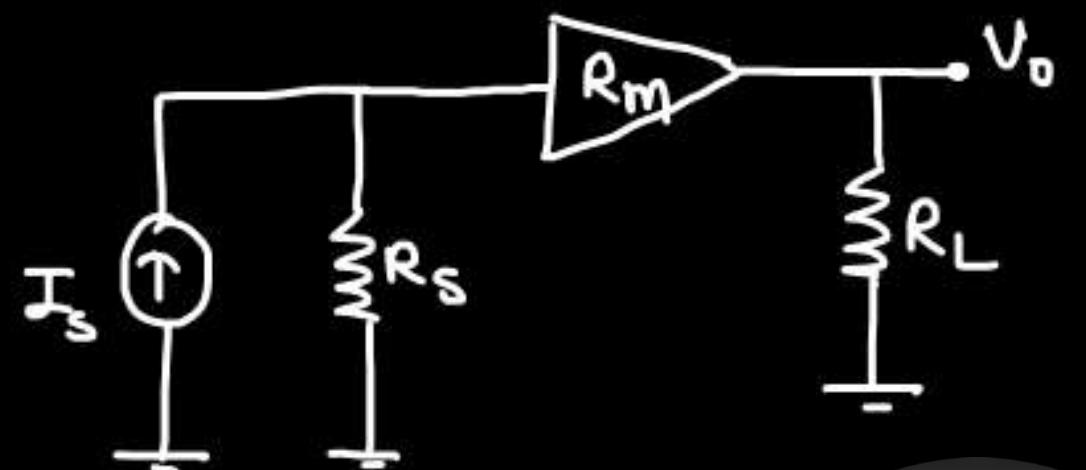

$$R_m = \frac{V_o}{I_s} = \text{ohm}$$

ampere

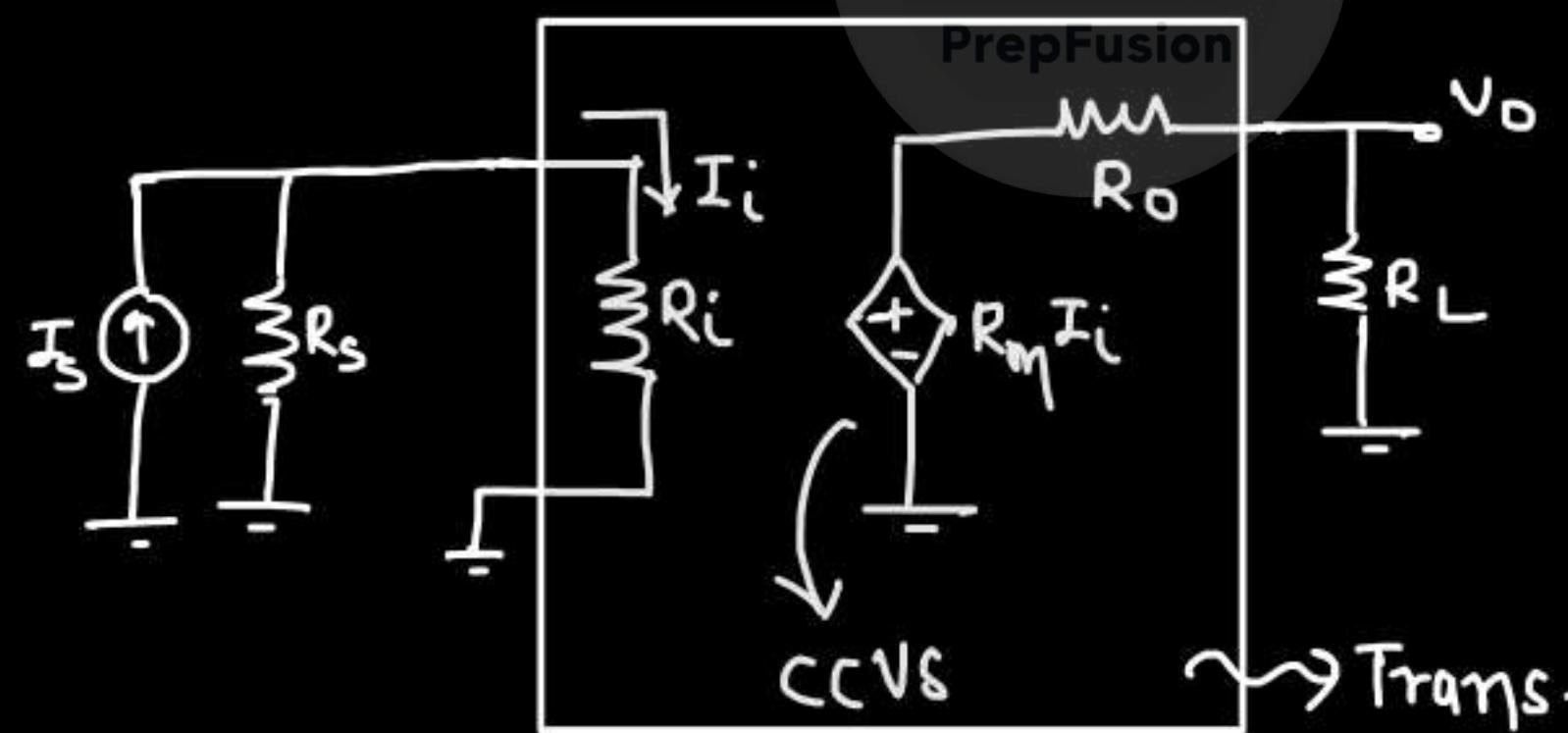

$$I_i = \frac{R_s}{R_s + R_i} I_s$$

$$V_o = \frac{R_L}{R_L + R_o} \times R_m I_i$$

$$V_o = (R_m) \left(\frac{R_L}{R_L + R_o} \right) \left(\frac{R_S}{R_S + R_i} \right) I_s$$

$$\frac{V_o}{I_s} = (R_m) \left(\frac{R_L R_S}{(R_L + R_o)(R_S + R_i)} \right)$$

For ideal Transresistance amplifier,

PrepFusion

$$R_i = 0 \Omega \rightarrow \text{low}$$


$$R_o = 0 \Omega \rightarrow \text{low}$$

if $R_i = 0$ and $R_o = 0$


$$\frac{V_o}{I_s} = R_m$$

Unit of $R_m \rightarrow \text{ohm}$

(iii) Transconductance Amplifier :-

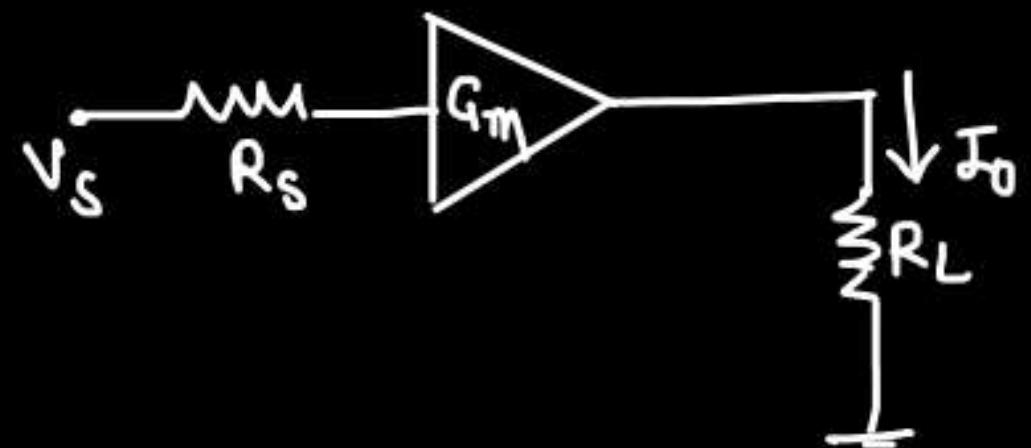
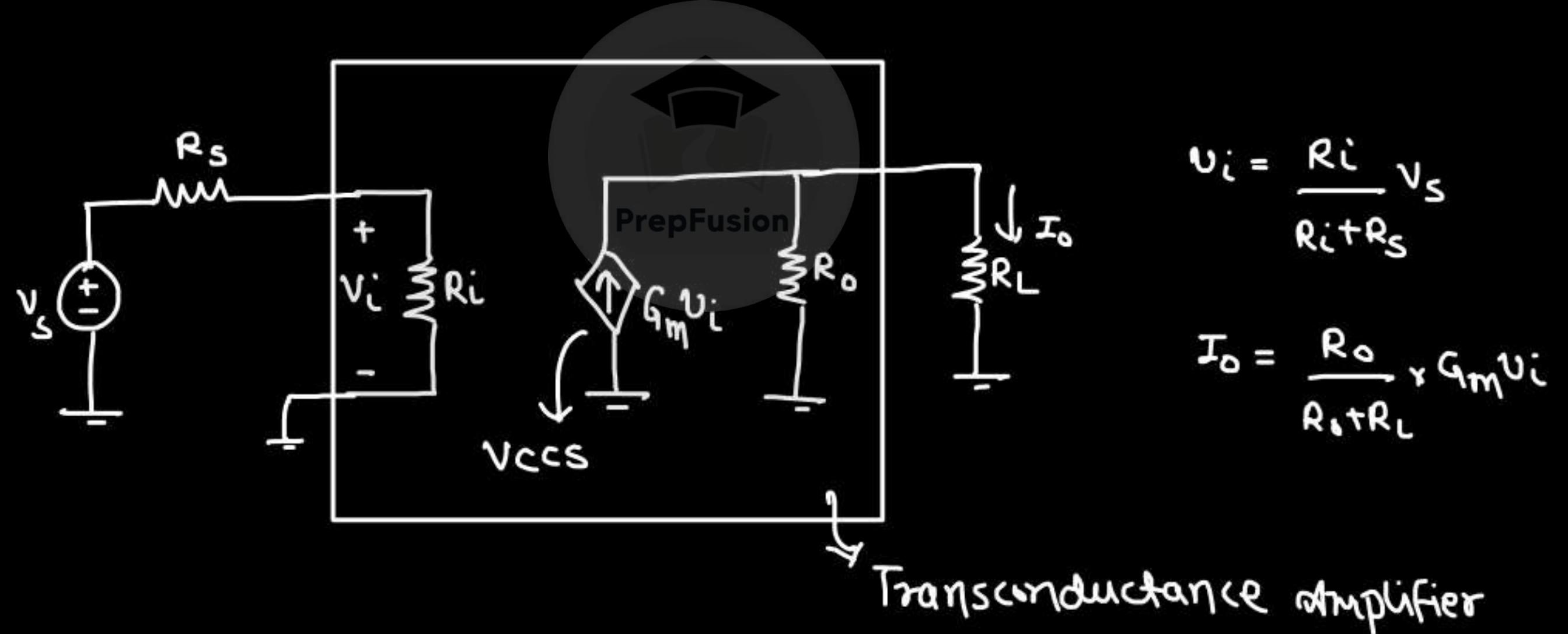
$$G_m \rightarrow \frac{\text{Current}}{\text{Voltage}} = \frac{A}{V} = mho = S$$



$$I_o = (G_m) \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_i}{R_i + R_s} \right) v_s$$

$$\frac{I_o}{v_s} = G_m \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_i}{R_i + R_s} \right)$$

For ideal Transconductance amplifier ;

PrepFusion

$$R_i = \infty$$


$$R_o = \infty$$

$$R_i = \infty, R_o = \infty$$


$$\frac{I_o}{v_s} = G_m$$

Unit of $G_m \rightarrow \text{mho/s}$

(iv) Current Amplifier:-

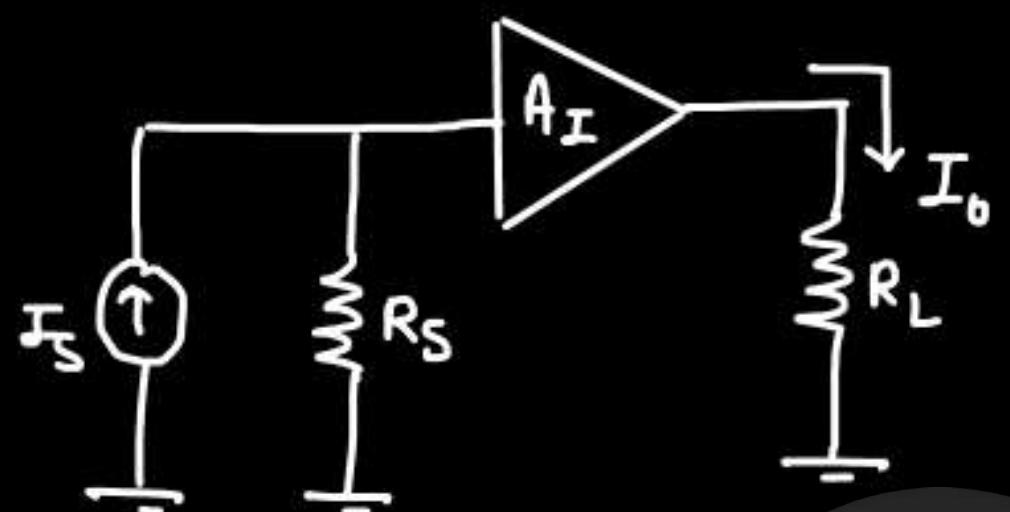

$$I_L = \frac{R_s}{R_s + R_i} I_s$$

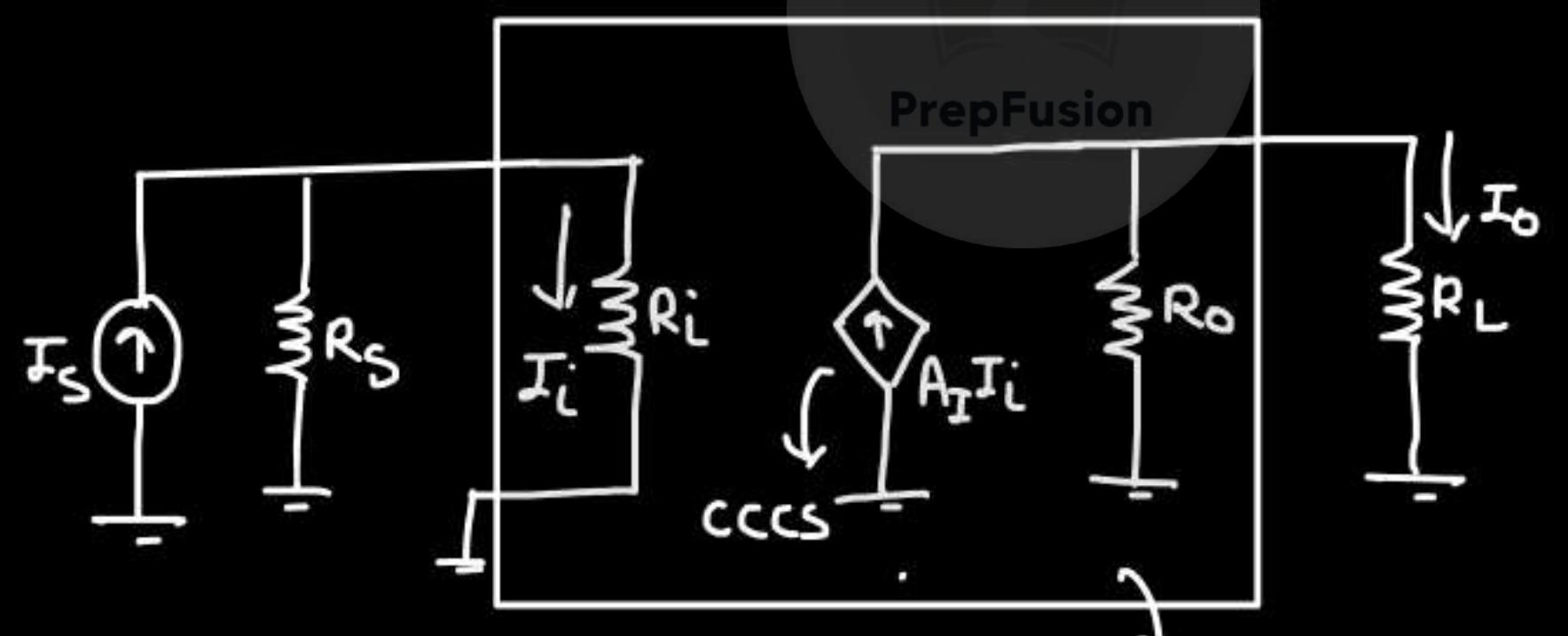

$$I_o = \frac{R_o}{R_o + R_L} A_I I_i$$

Current Amplifier

$$I_o = A_I \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_s}{R_s + R_i} \right) I_s$$

$$\frac{I_o}{I_s} = A_I \left(\frac{R_o}{R_o + R_L} \right) \left(\frac{R_s}{R_s + R_i} \right)$$

for ideal current amplifier,

PrepFusion

$$R_i = 0$$


$$R_o = \infty$$

$$R_i = 0, R_o = \infty$$



$$\frac{I_o}{I_s} = A_I$$

Type of Amplifier	Input Resistance	Output Resistance
(i) Voltage Amplifier	∞	0
(ii) Transresistance Amp.	0	0
(iii) Transconductance amp	∞	∞
(iv) Current Amplifier	0	∞



Alternative feedback Model :-

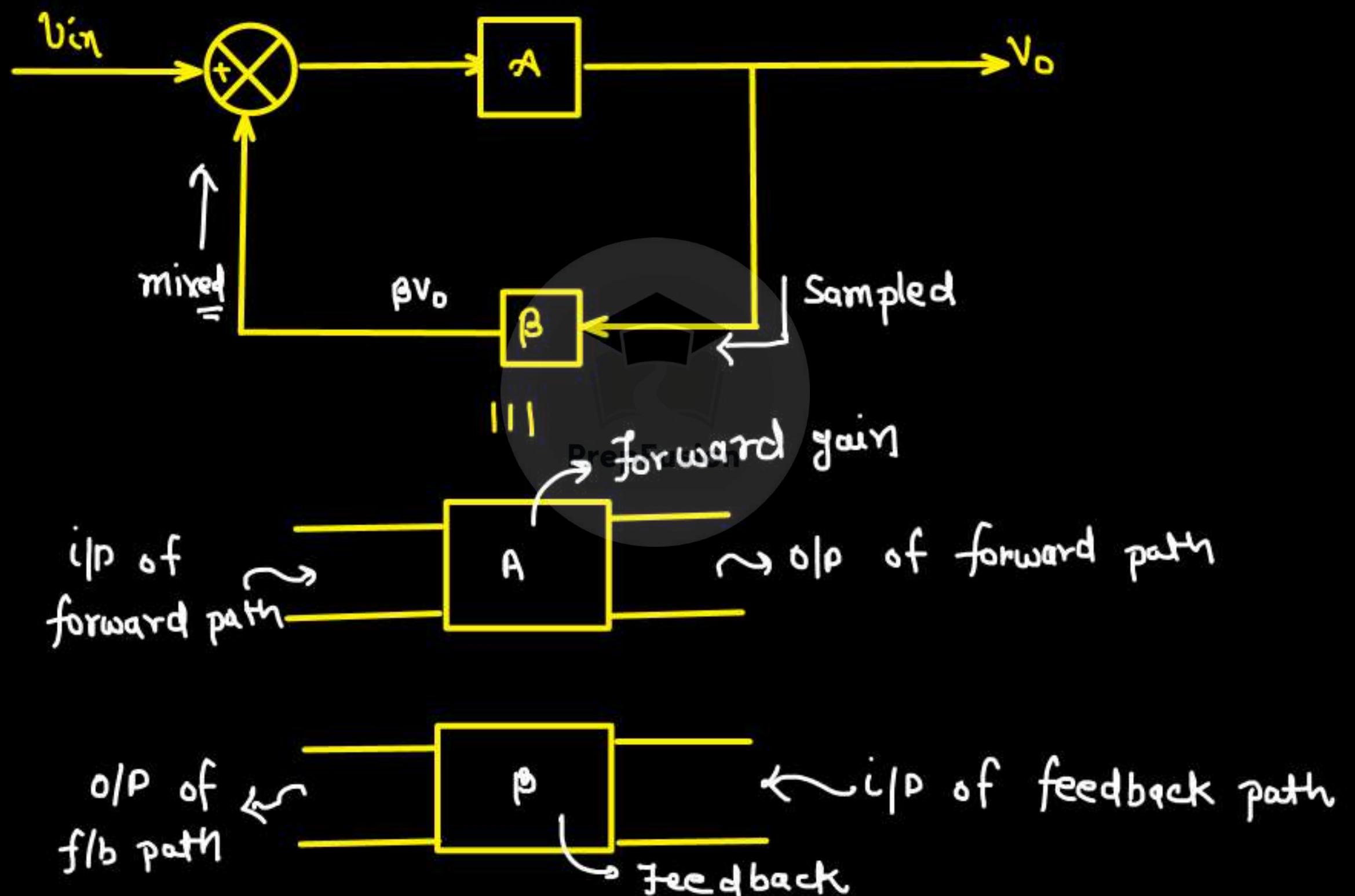

* Series Connection of 2-Two port N(ω):-

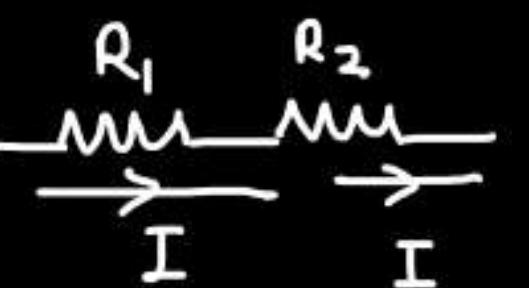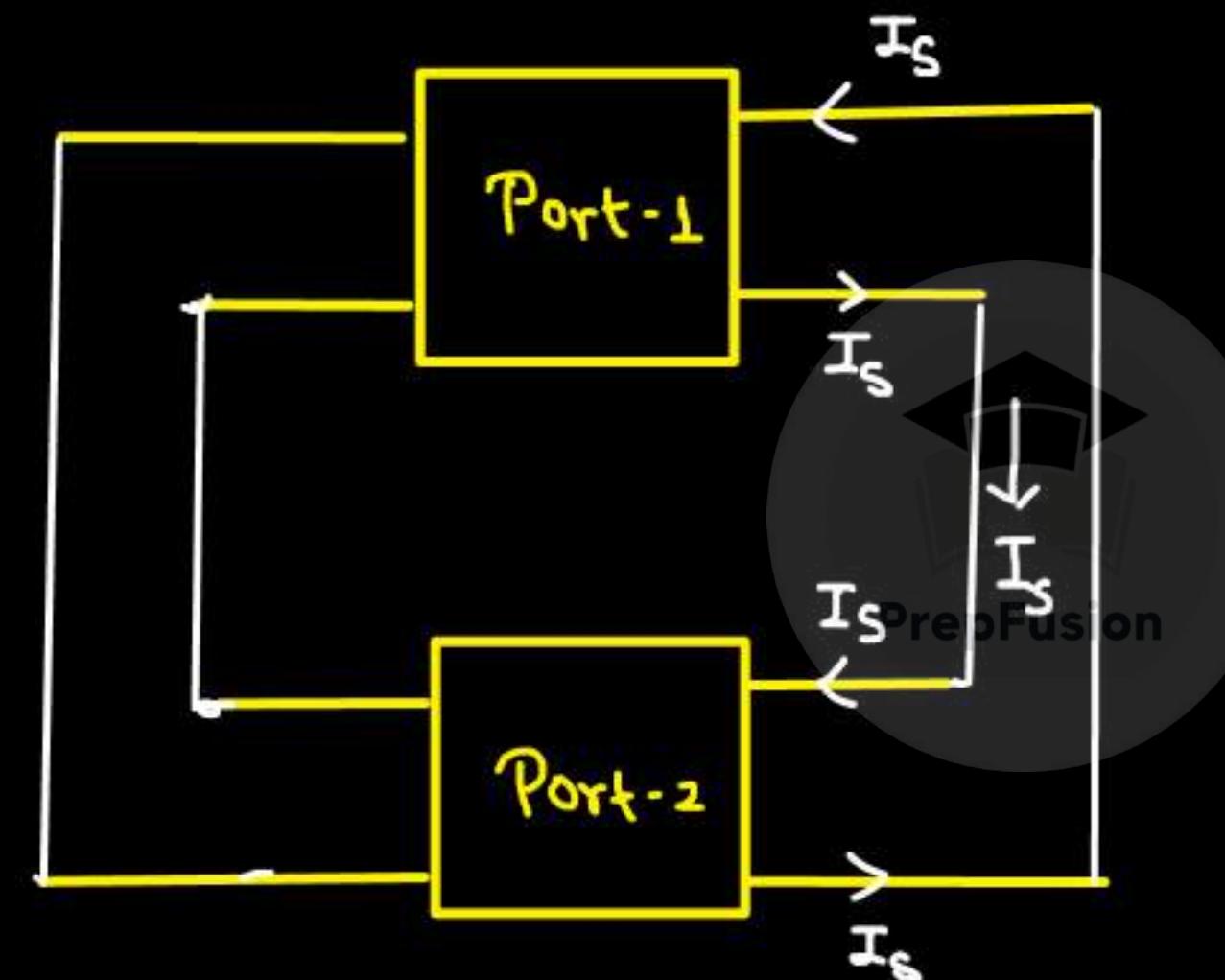


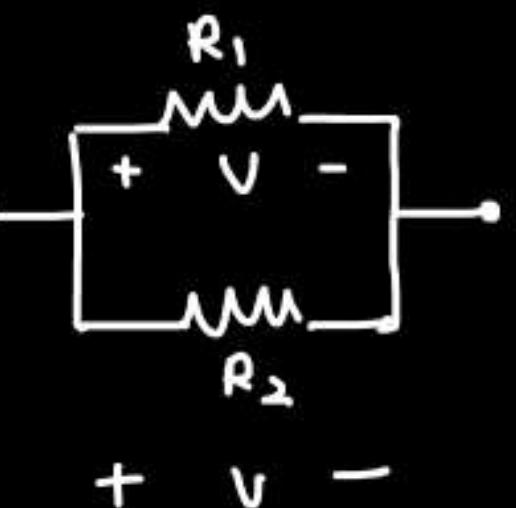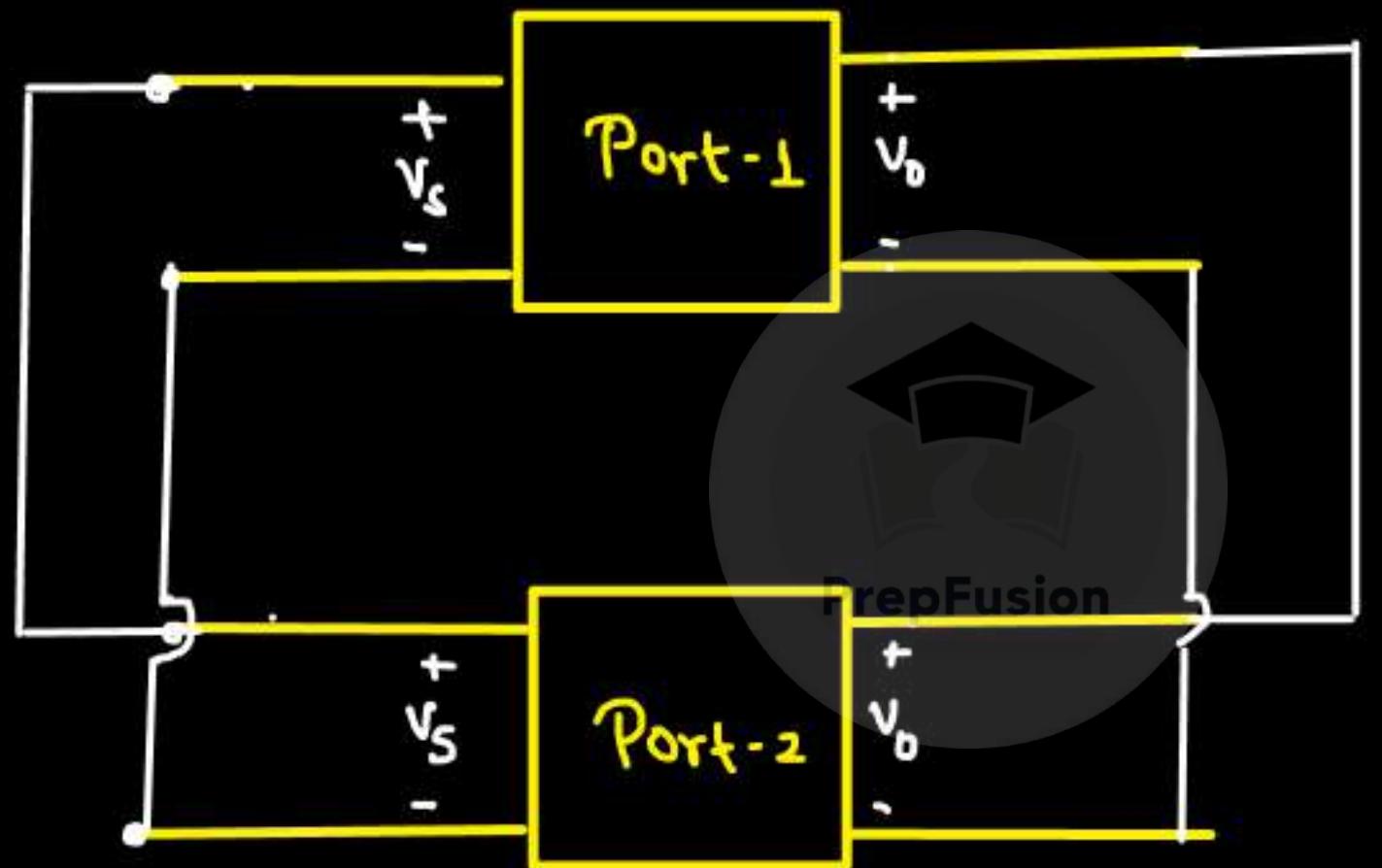* Parallel Connection of 2 - Two Port Networks.. (Shunt)



★ Important Points to remember:-

1. Series Connection :-

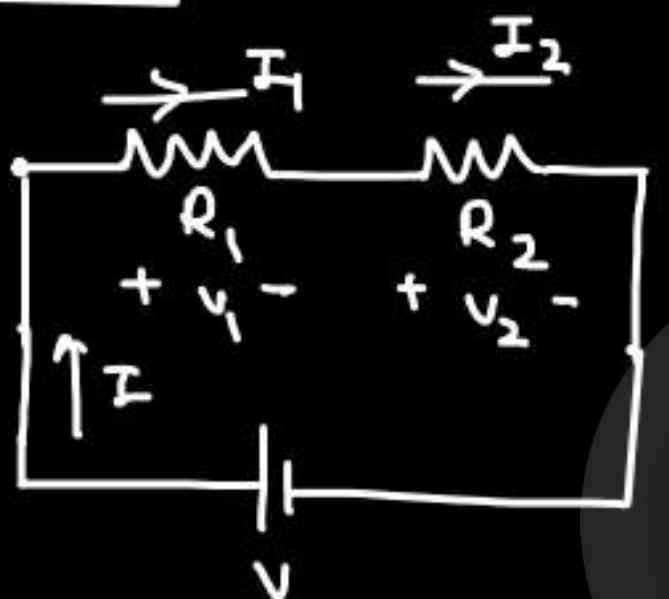


$I = I_1 = I_2 \rightarrow$ current same

$V = V_1 + V_2 \rightarrow$ voltage mixed

Series = current sampled, voltage mixed

2. Parallel connection :-

(Shunt)

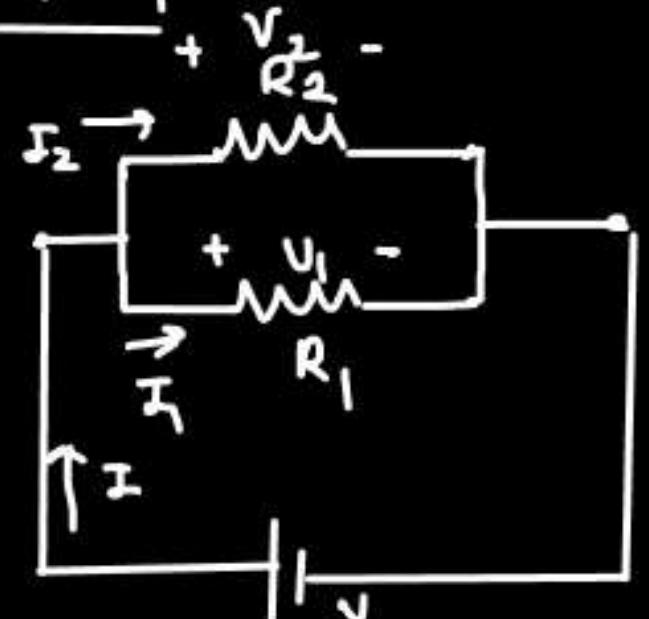


$V = V_1 = V_2 \rightarrow$ voltage same

$I = I_1 + I_2 \rightarrow$ current mixed

Parallel = voltage sampled, current mixed

For a two port N/W:-

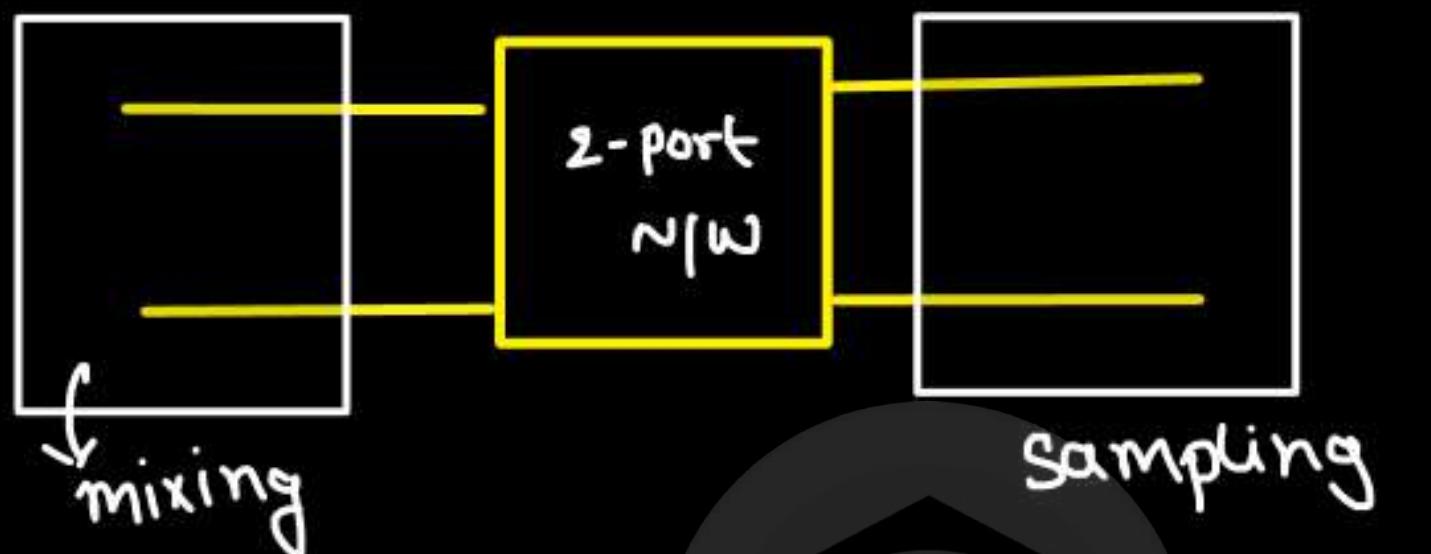

* Decode the following:-

- ① Voltage Sampling \rightarrow Shunt connection
- ② Current Mixing \rightarrow Shunt connection
- ③ Voltage Mixing \rightarrow Series connection
- ④ Current Sampling \rightarrow Series connection

⑤ Series connection \rightarrow Current Sampling, Voltage mixing

⑥ Shunt Connection \rightarrow Voltage Sampling, Current mixing

⑦ Series connection at input \rightarrow Voltage mixing

⑧ Series connection at output \rightarrow Current Sampling

⑨ Shunt connection at input \rightarrow Current mixing

⑩ Shunt connection at output \rightarrow ^{PreFusion} Voltage Sampling

Conclusion:-

① $i/p \rightarrow$ mixing, $o/p \rightarrow$ sampling

② Series \rightarrow Current Sampling, Voltage mixing

③ Shunt \rightarrow Voltage Sampling, Current mixing

⇒ Feedback Topologies :-

O/P - I/P

I/P - O/P

O/P - I/P

① Voltage - Voltage | Series - Shunt | Voltage - Series


② Voltage - Current | Shunt - Shunt | Current - Shunt

③ Current - Voltage | Series - Series | Voltage - Series

④ Current - Current | Shunt - Series | Current - Series

* Voltage - Voltage feedback Topology :-

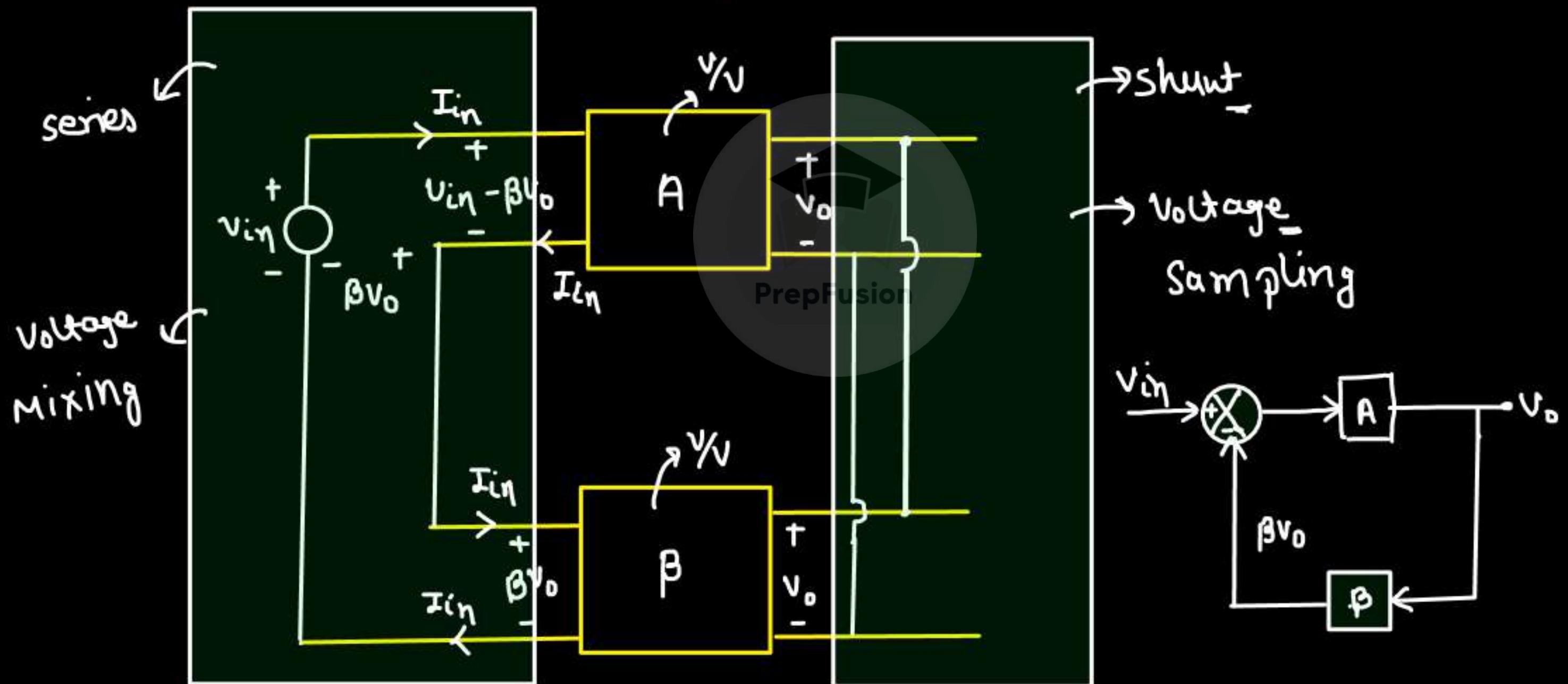(Series - Shunt) ↳ from o/p voltage is sensed and fed back to the i/p




open loop gain = A

open loop input resistance = R_{in}

open loop output resistance = R_o

① Closed loop Gain :-

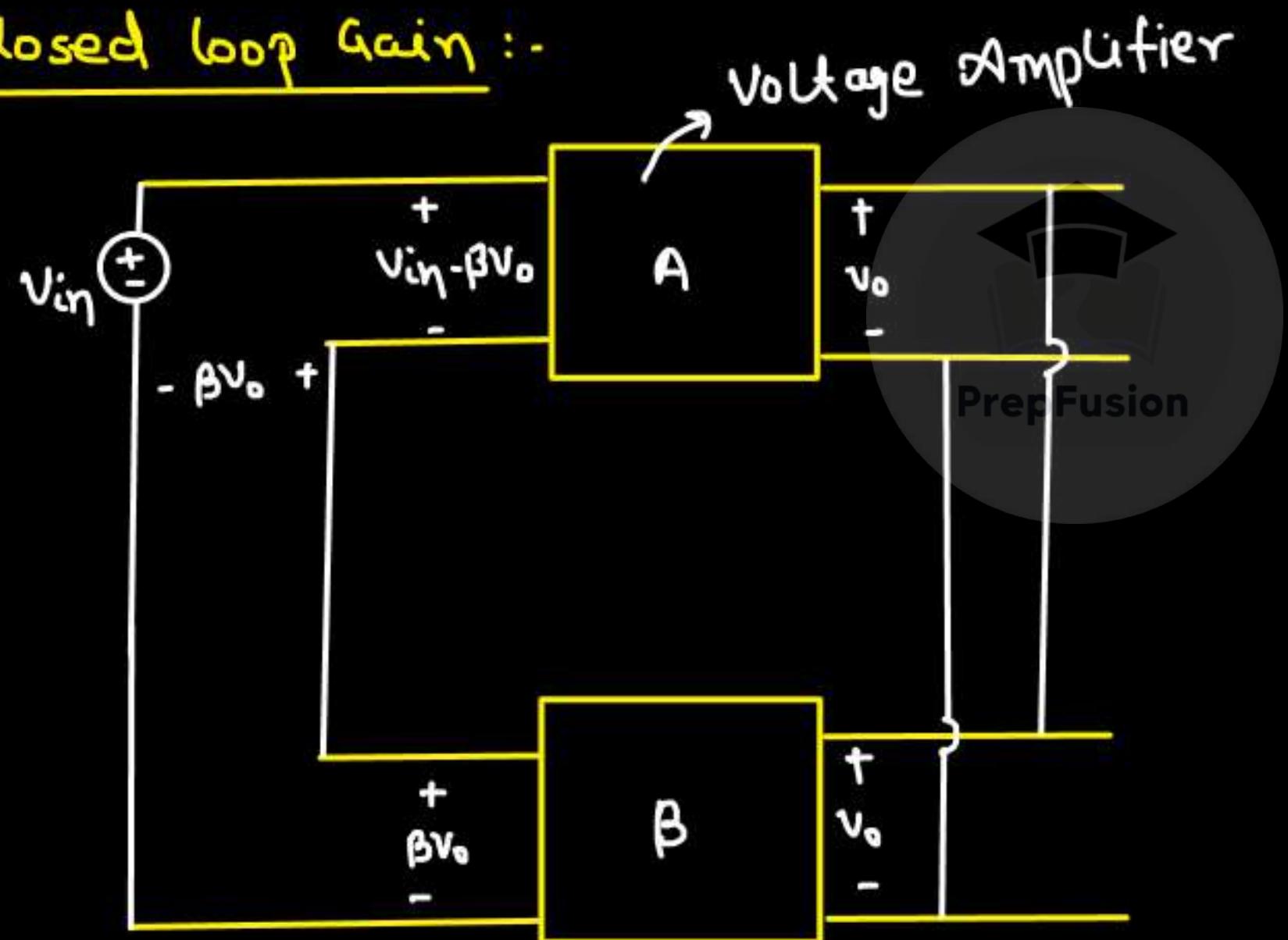


$$CLG = \frac{V_{in}}{V_o} = (AV)_f$$

$$A(V_{in} - \beta V_o) = V_o$$

$$\frac{V_o}{V_{in}} = (AV)_f = \frac{A}{1 + A\beta}$$

② Closed loop input impedance :-

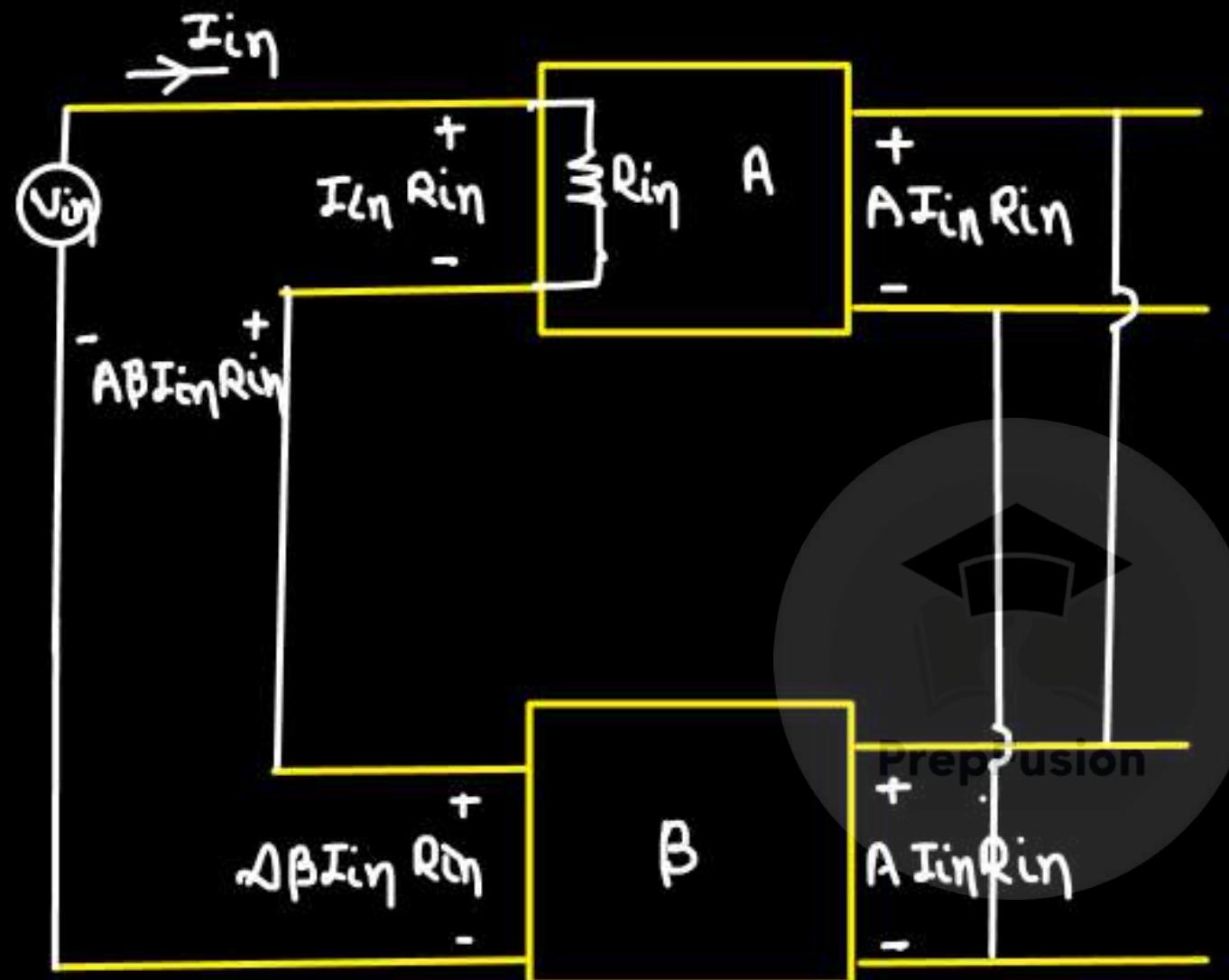


$$(R_{in})_f = \frac{V_{in}}{I_{in}}$$

$$V_{in} = I_{in}R_{in} + A\beta I_{in}R_{in}$$

$$\frac{V_{in}}{I_{in}} = (R_{in})_f = R_{in}(1 + A\beta)$$

③ Closed - Loop Output Impedance :-

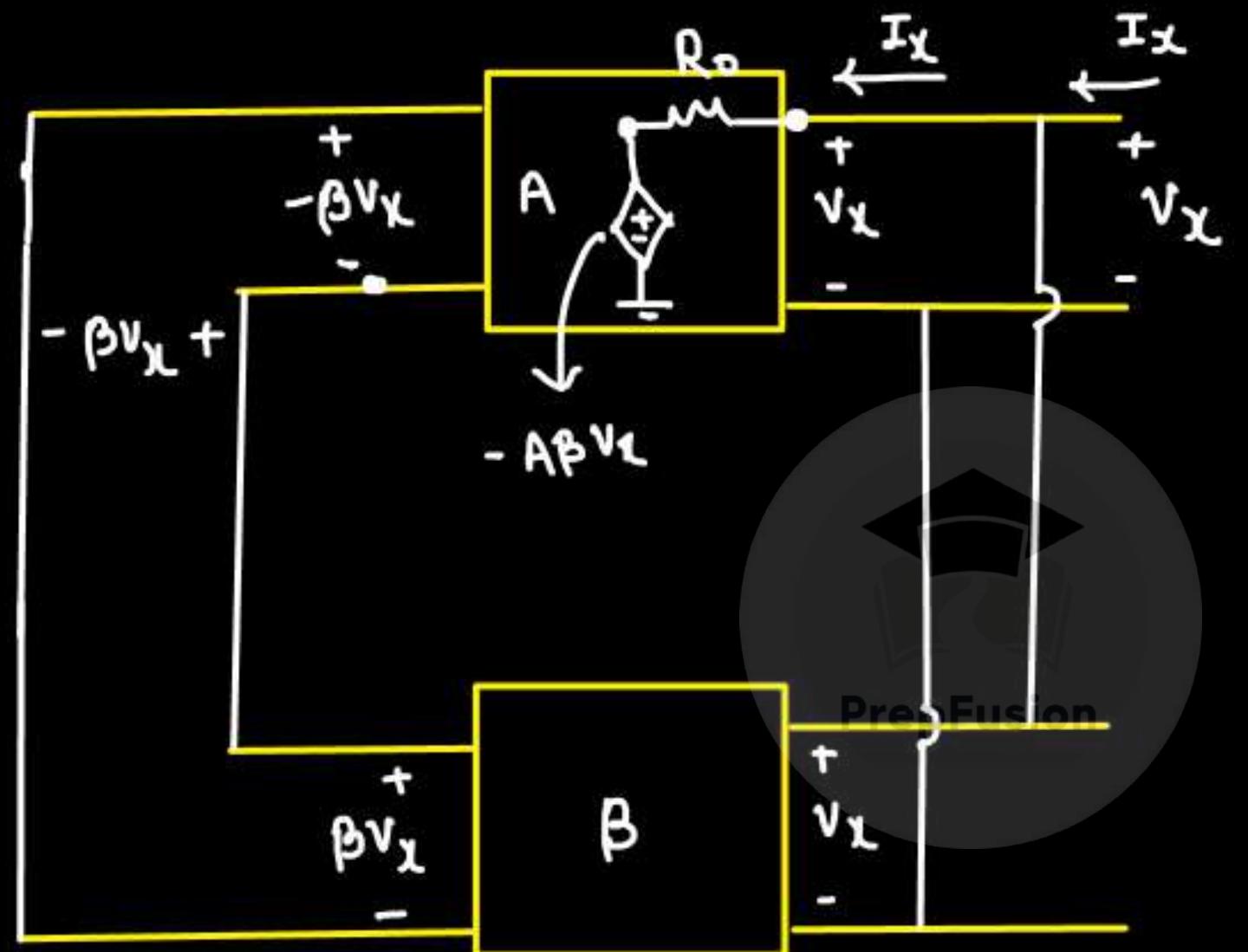

$$(R_o)_f = \frac{V_x}{I_x}$$

Assumption :-


R_o is very small, so complete I_x will be flowing through R_o .
(NOT in f/b path)

$$\frac{V_x - (-A\beta V_x)}{R_o} = I_x$$

$$\Rightarrow (R_o)_f = \frac{V_x}{I_x} = \frac{R_o}{1 + A\beta}$$

Example :-

Q.

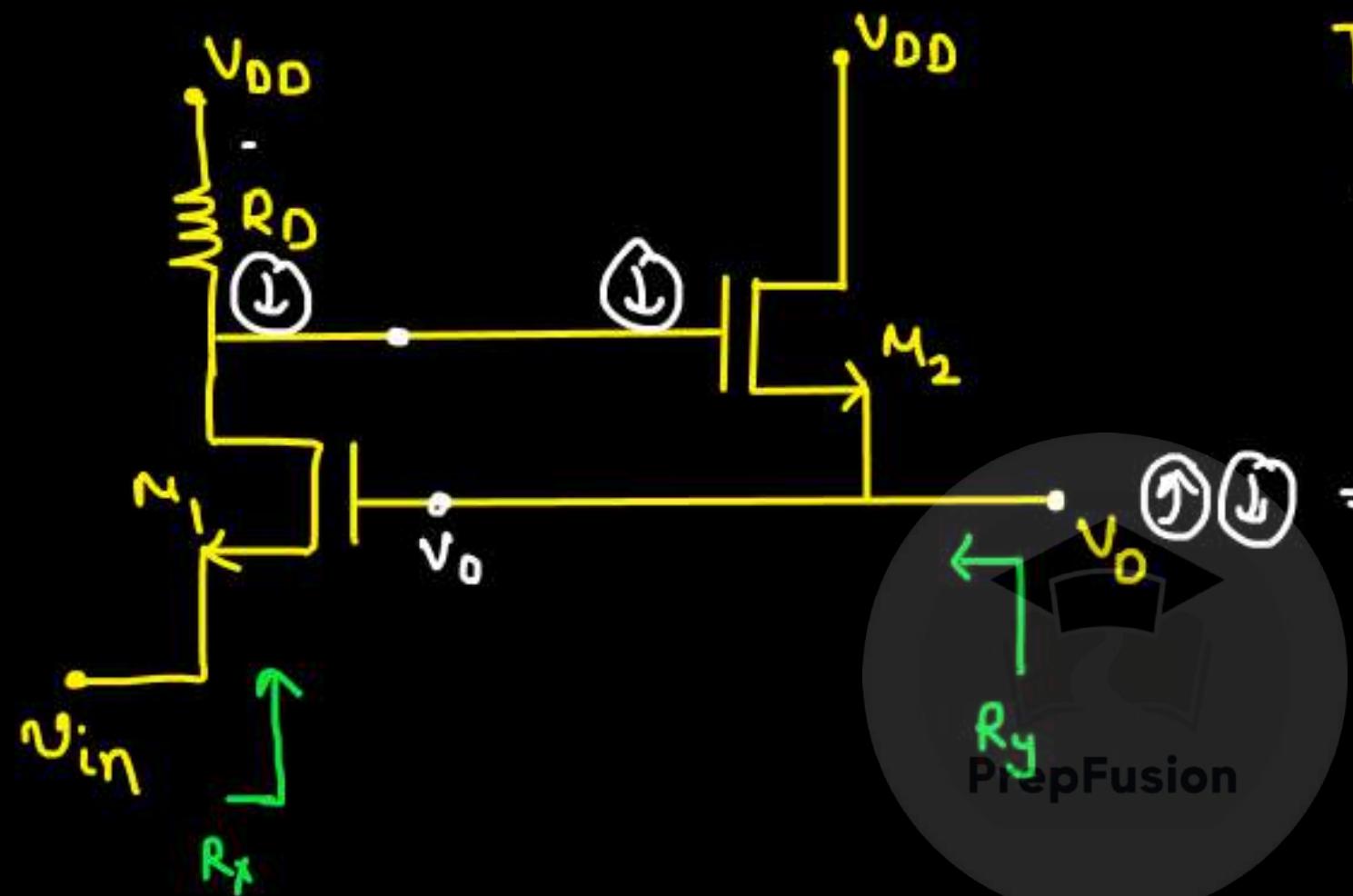

Take $\lambda = 0$

Find R_x , R_y and $\frac{V_o}{V_i} = ?$

Negative f/b

Topology \rightarrow Voltage -
Voltage
f/b

* Short-cut to find f/b Topology:-

① For sampling, always look at o/p voltage

if there is voltage sampling


$$V_f = \beta V_o \quad , \quad I_f = G_m V_o$$

if we put $V_o = 0V \Rightarrow$ There should be no f/b that is coming towards the i/p side.

\Rightarrow if that is so, that means there is voltage sampling
o/w current sampling

② For mixing, always check the i/p current. If current is mixed, then there is current mixing, o/w voltage mixing.

M-I w/o the concept of f/b topology:-

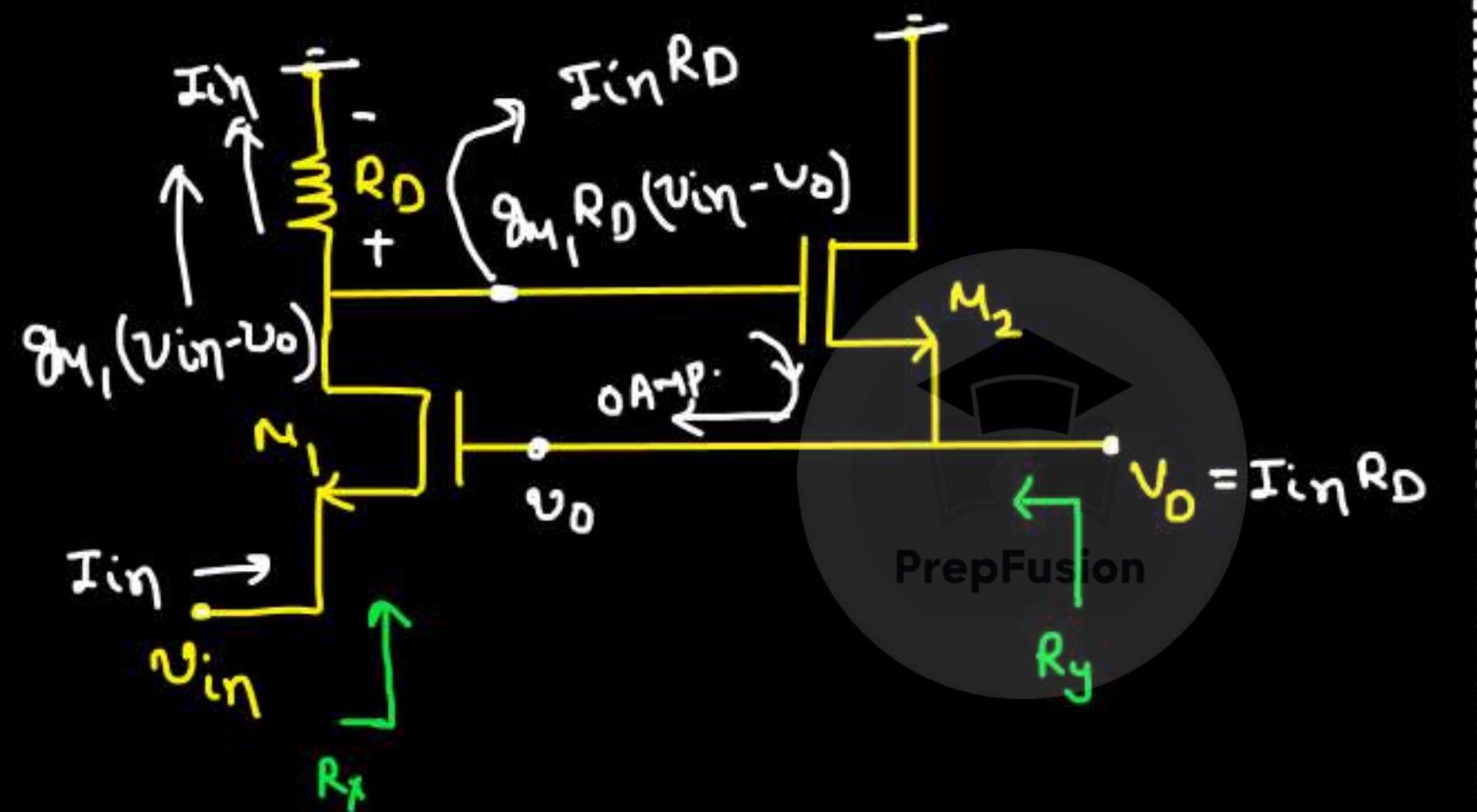

$$g_{m1} R_D (V_{in} - V_D) = V_D$$


$$\frac{V_D}{V_{in}} = \frac{g_{m1} R_D}{1 + g_{m1} R_D}$$

$$R_x = \frac{V_{in}}{I_{in}}$$

$$g_{m1} (V_{in} - I_{in} R_D) = I_{in}$$

$$g_{m1} V_{in} = (g_{m1} R_D + 1) I_{in}$$
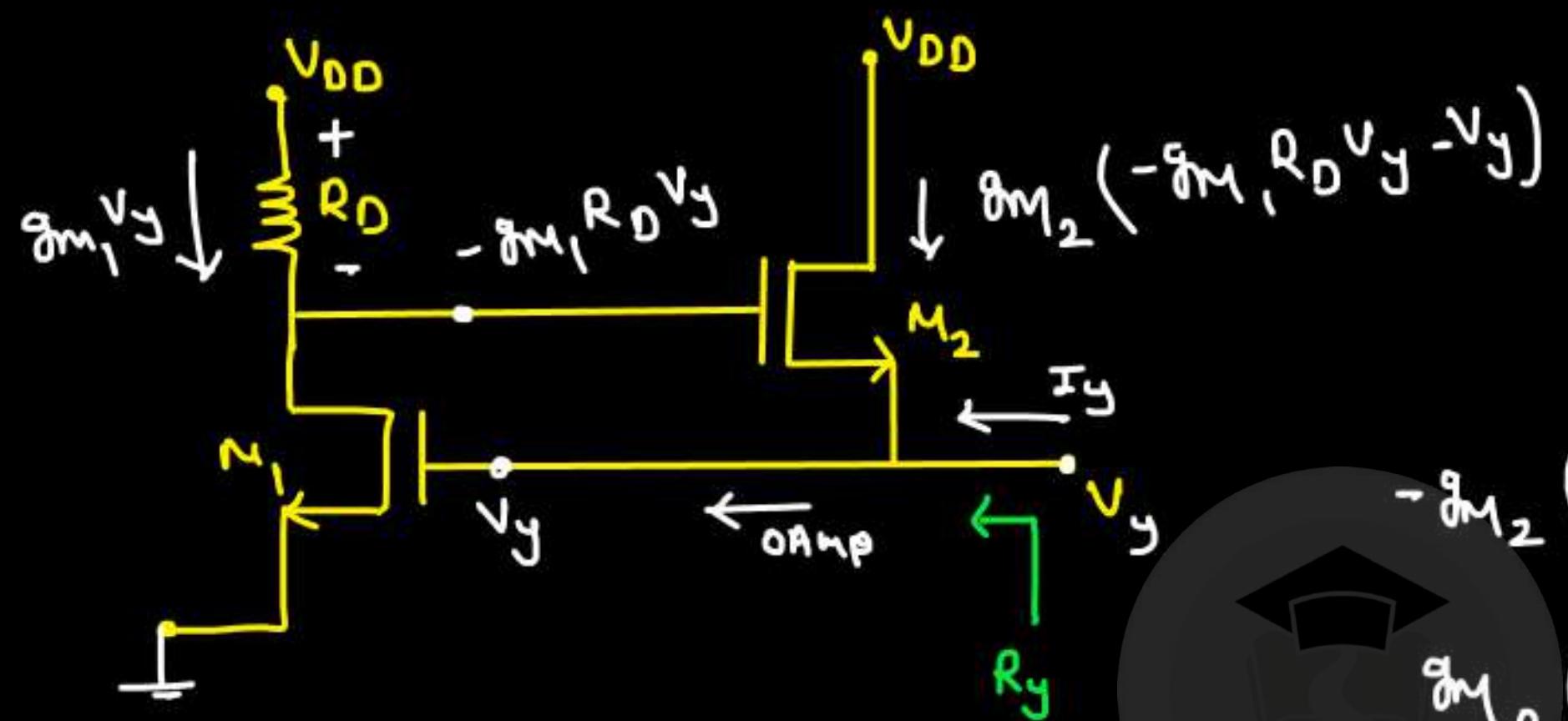
$$\frac{V_{in}}{I_{in}} = R_x = \frac{1}{g_{m1}} (1 + g_{m1} R_D)$$




$$-g_m2(-g_m1 R_D V_y - V_y) = I_y$$

$$g_m2(g_m1 R_D + 1) V_y = I_y$$

PrepFusion



$$R_y = \frac{V_y}{I_y} = \frac{g_m2}{1 + g_m1 R_D}$$

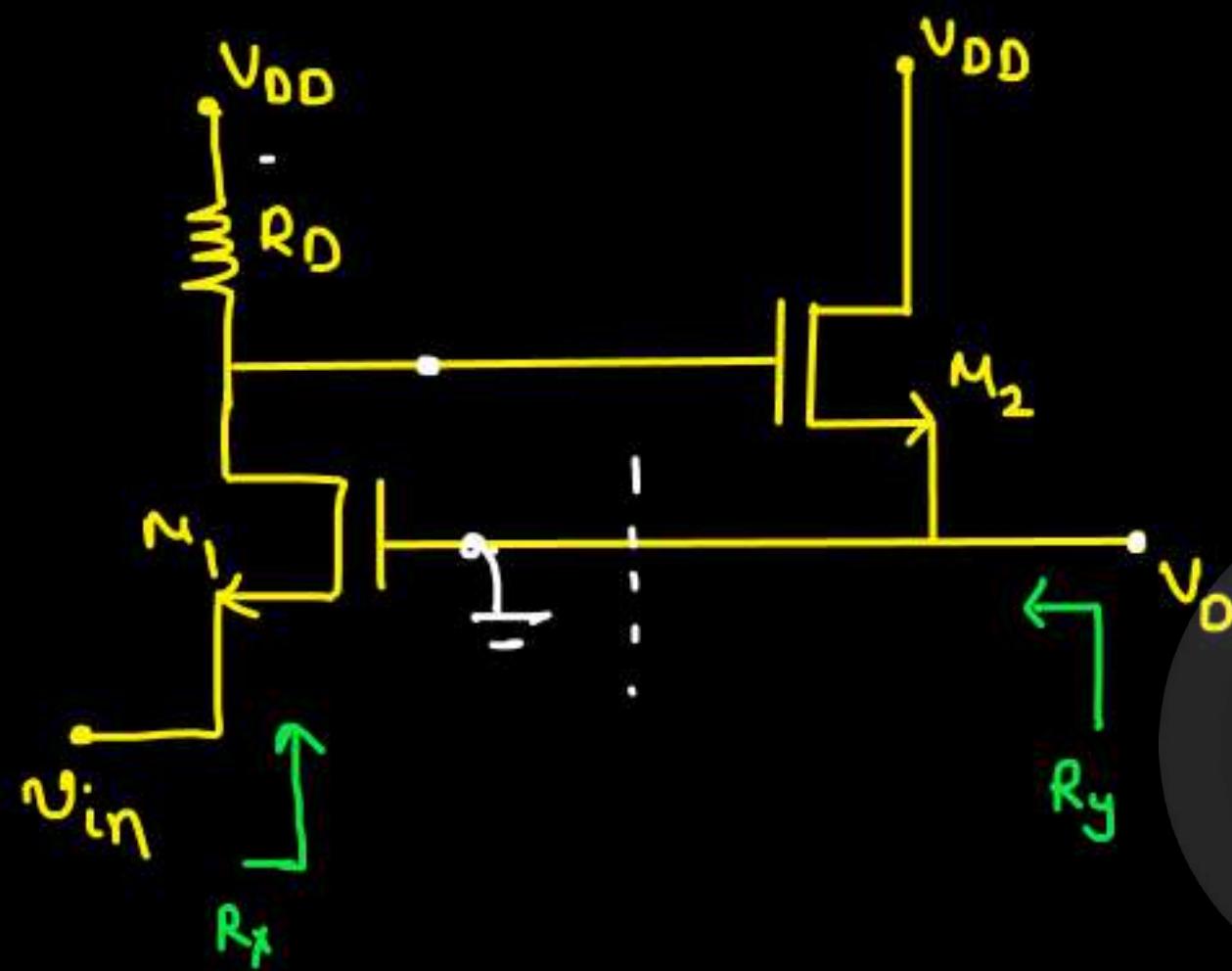* with the concept of feedback Topology :-




→ Voltage - Voltage f/b

* open loop gain = ? = A

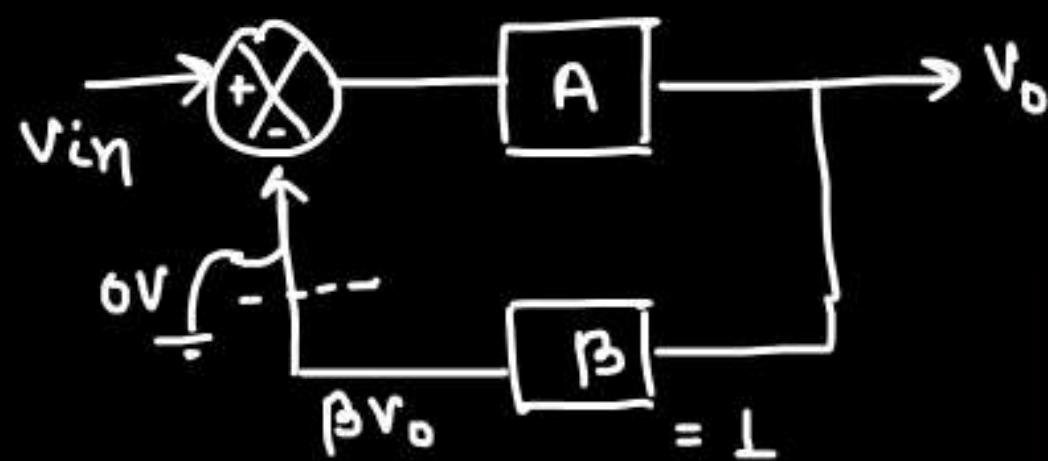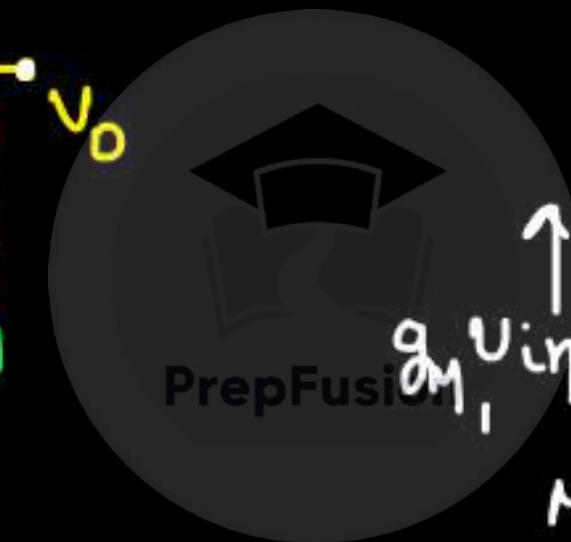

$$(R_x)_{0 \cdot L} = \frac{1}{g_m 1}$$

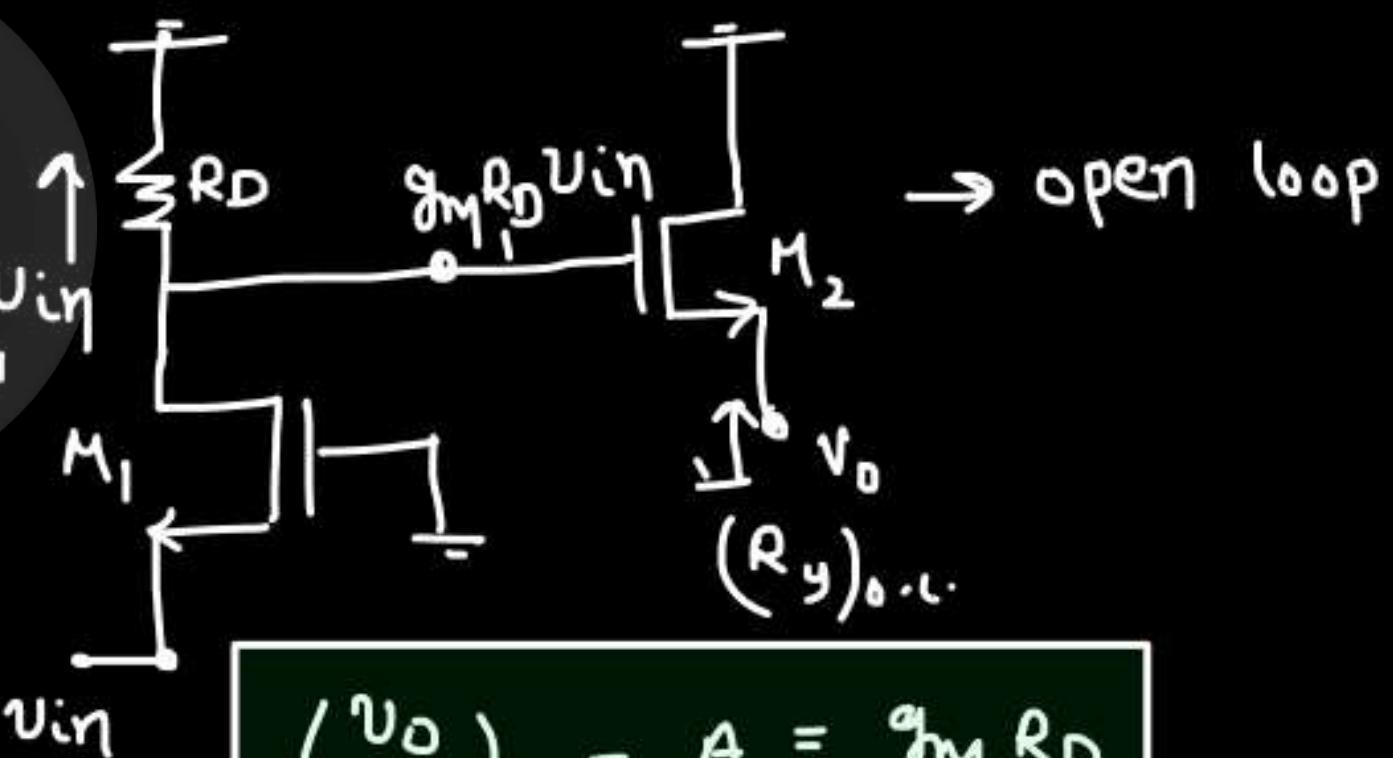

$$\left(\frac{v_o}{v_{in}} \right)_{0 \cdot L} = A = g_m 1 R_D$$

$$\beta = L$$

$$(R_y)_{0 \cdot L} = \frac{1}{g_m 2}$$

For Voltage - Voltage f/b Topology :-

(in case of Neg. f/b)

① Close loop gain

$$(\mathcal{A}_v)_f = \frac{A}{1 + \alpha\beta} = \frac{g_m R_D}{1 + g_m R_D}$$

② Close loop input impedance $R_X = (R_X)_{o.v.} (1 + \alpha\beta)$

PrepFusion


$$R_X = \frac{1}{g_m} (1 + g_m R_D)$$

③ Closed loop o/p impedance

$$R_Y = \frac{(R_Y)_{o.v.}}{1 + \alpha\beta} = \frac{1/g_m}{1 + g_m R_D}$$

★ Voltage - Current fb :-

(Shunt - Shunt)

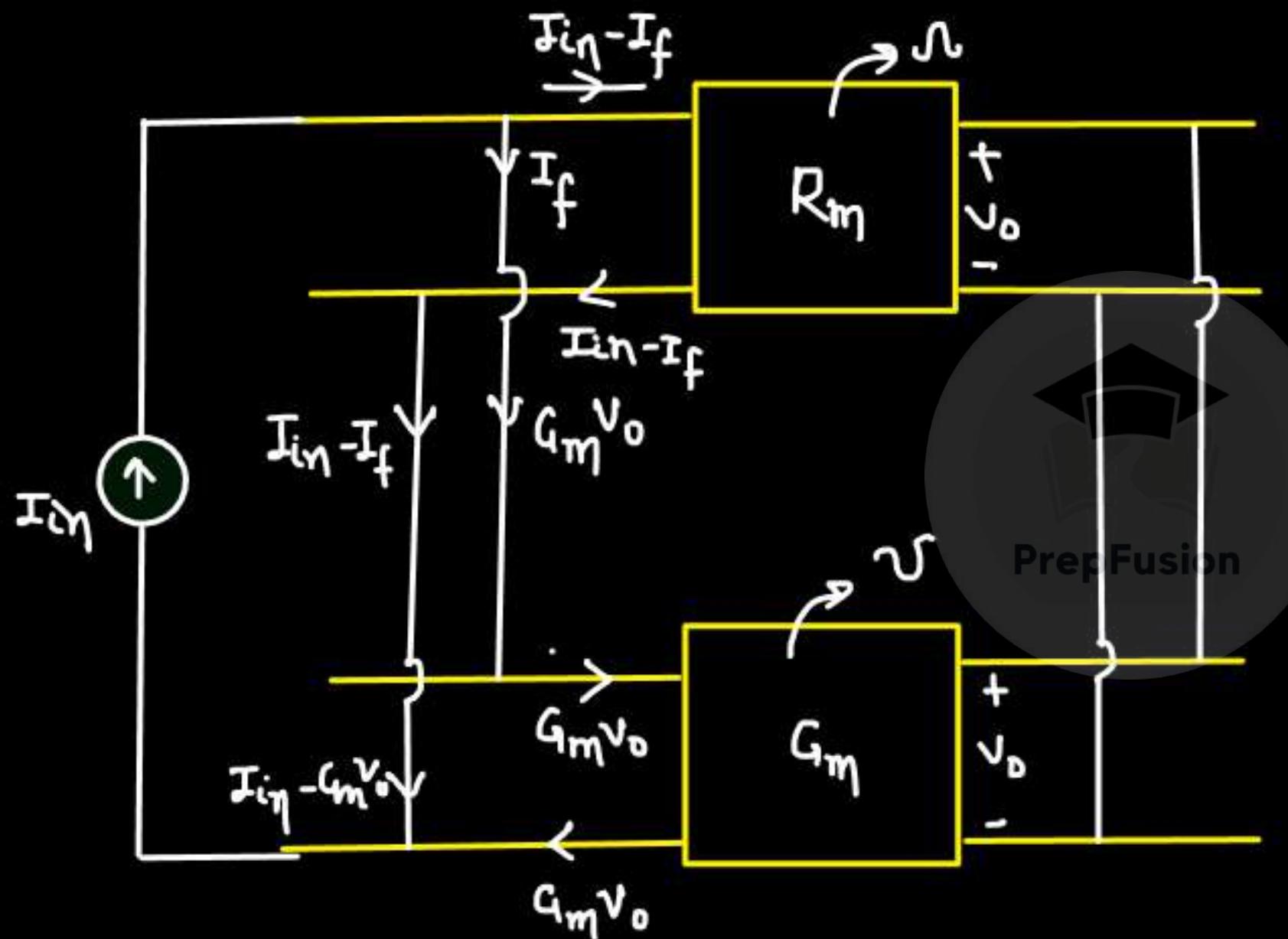


Open loop gain $\rightarrow R_m (\infty)$

Open loop input impedance $\rightarrow R_{in}$

Open loop output impedance $\rightarrow R_o$

① Closed loop gain:

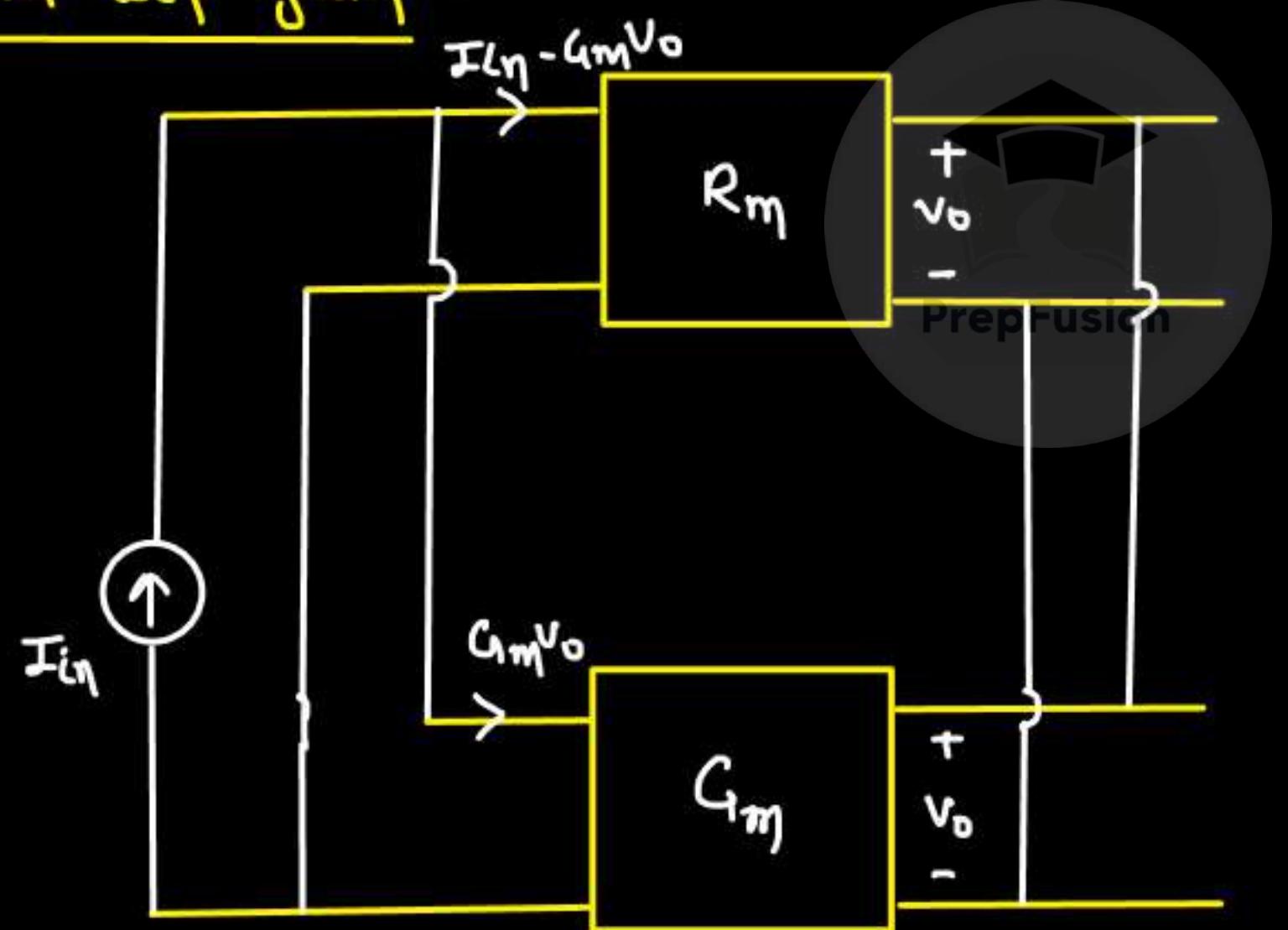


Closed loop gain

$$(\mathcal{A}_R)_f = \frac{V_o}{I_{in}}$$

$$(I_{in} - G_m V_o) R_m = V_o$$

$$\frac{V_o}{I_{in}} = (\mathcal{A}_R)_f = \frac{R_m}{1 + G_m R_m}$$

② Closed loop input Resistance :-

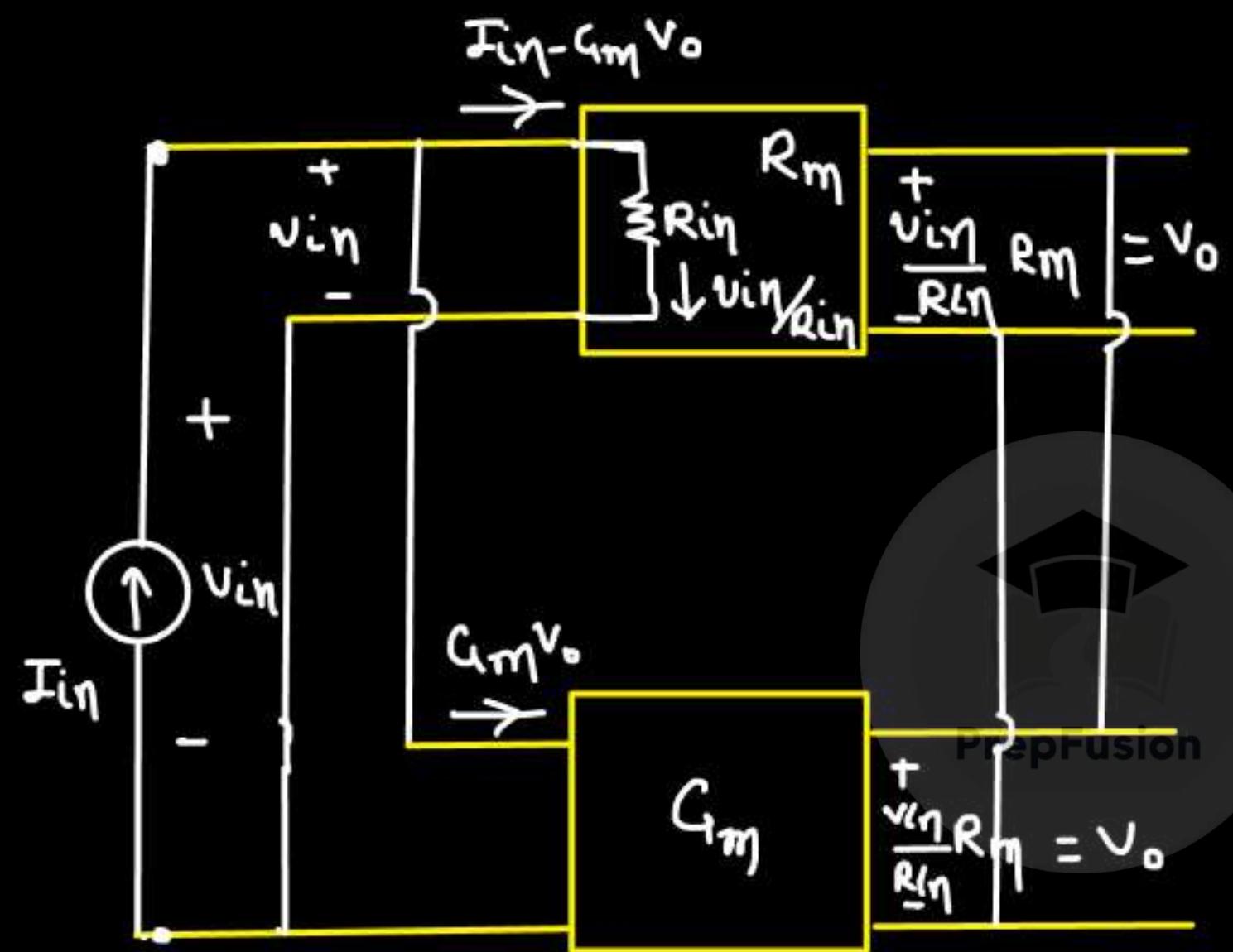

$$(R_{in})_f = \frac{V_{in}}{I_{in}}$$

$$\frac{V_{in}}{R_{in}} = I_{in} - G_m V_o$$


$$\frac{V_{in}}{R_{in}} = I_{in} - \frac{G_m V_{in}}{R_{in}} R_m$$

$$V_{in} [1 + G_m R_m] = R_{in} I_{in}$$

★

$$(R_{in})_f = \frac{R_{in}}{1 + G_m R_m}$$

③ Closed Loop Output Impedance:-

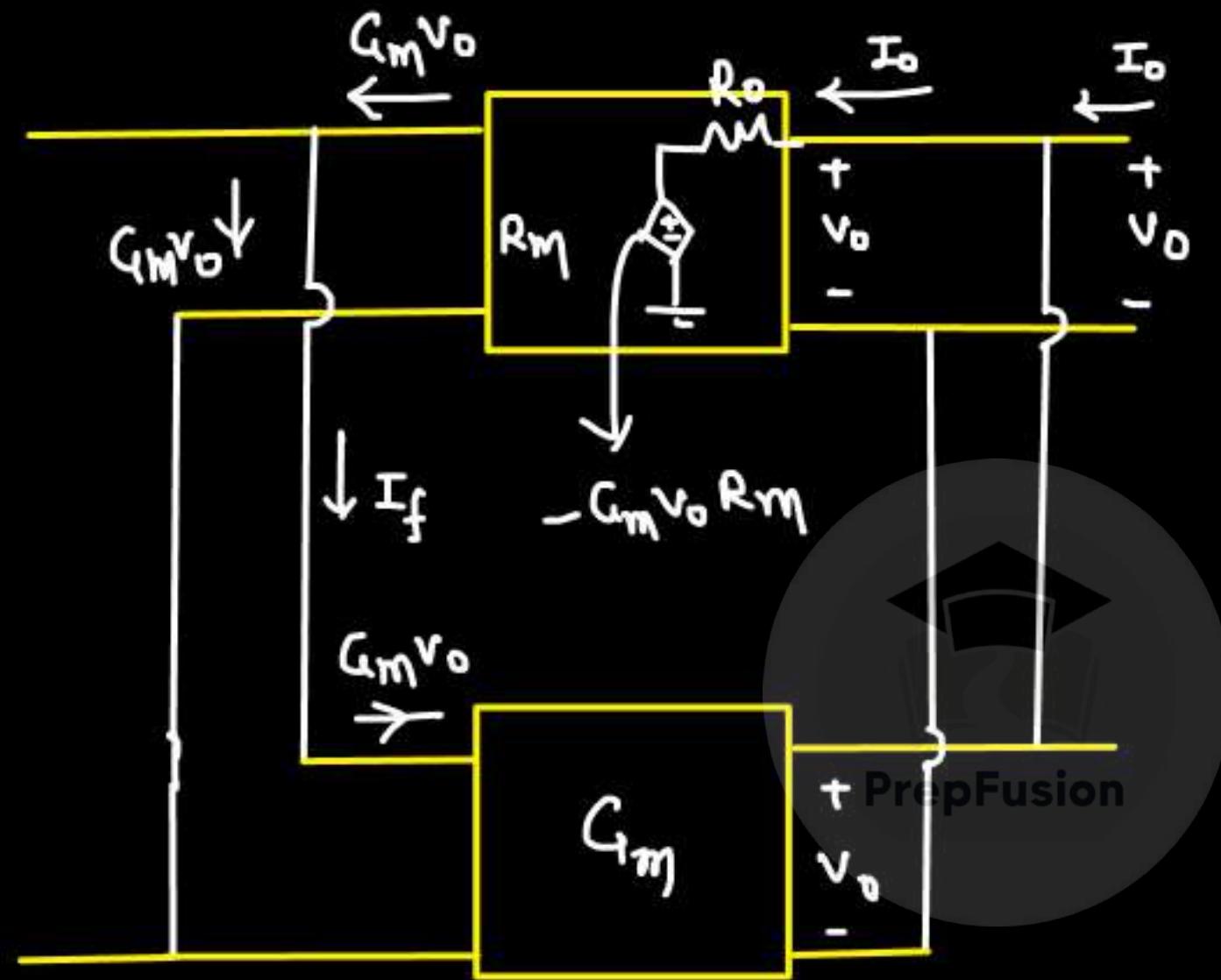

$$(R_o)_f = \frac{V_o}{I_o}$$

Assumption:-


Complete I_o is flowing through R_o .

$$\frac{V_o + G_m V_o R_m}{R_o} = I_o$$

BB

$$\frac{V_o}{I_o} = (R_o)_f = \frac{R_o}{1 + G_m R_m}$$


Eg:-

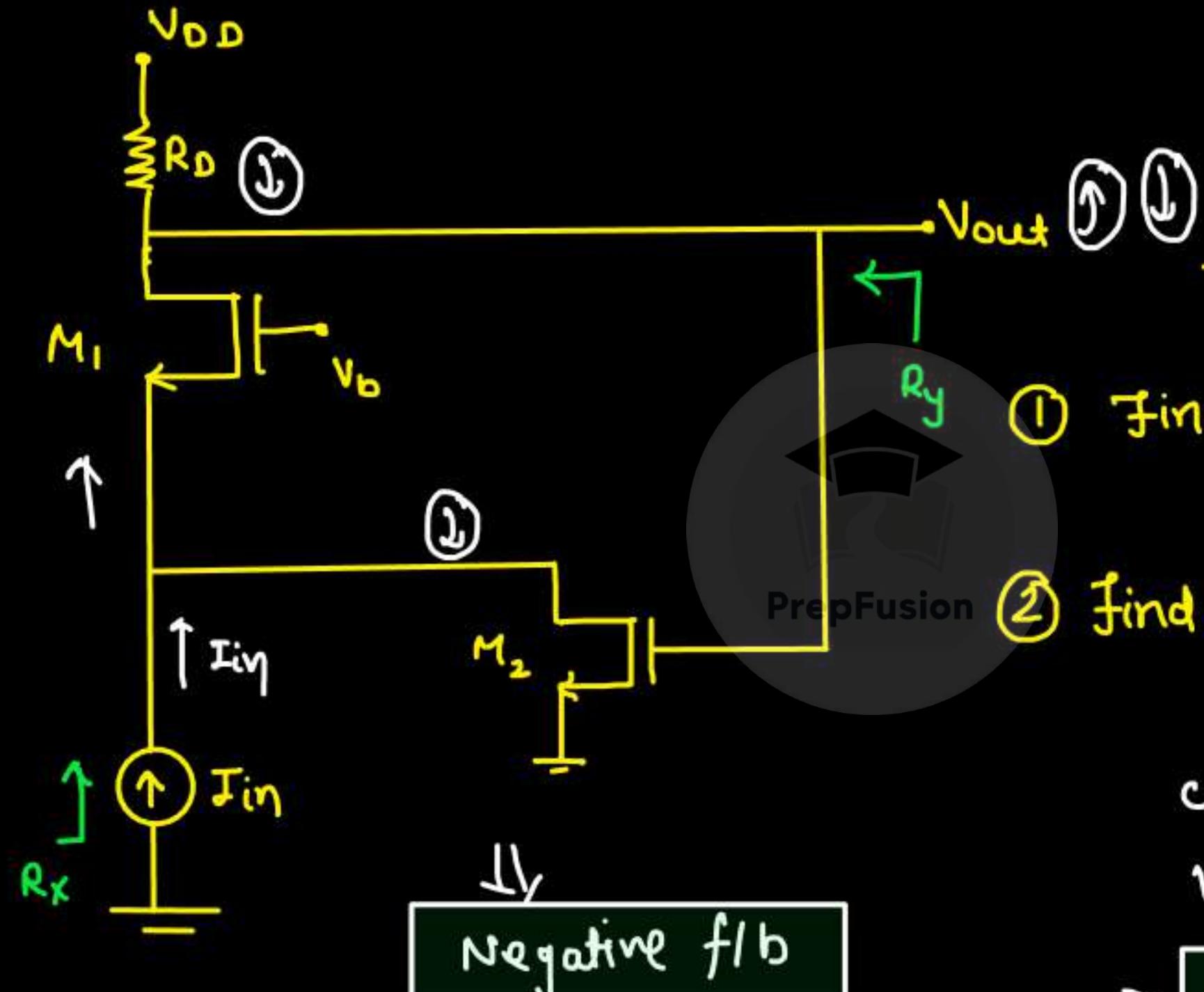

current mixing
voltage sampling


⇒ Voltage Current f/b

M-I w/o using the concept of f/b

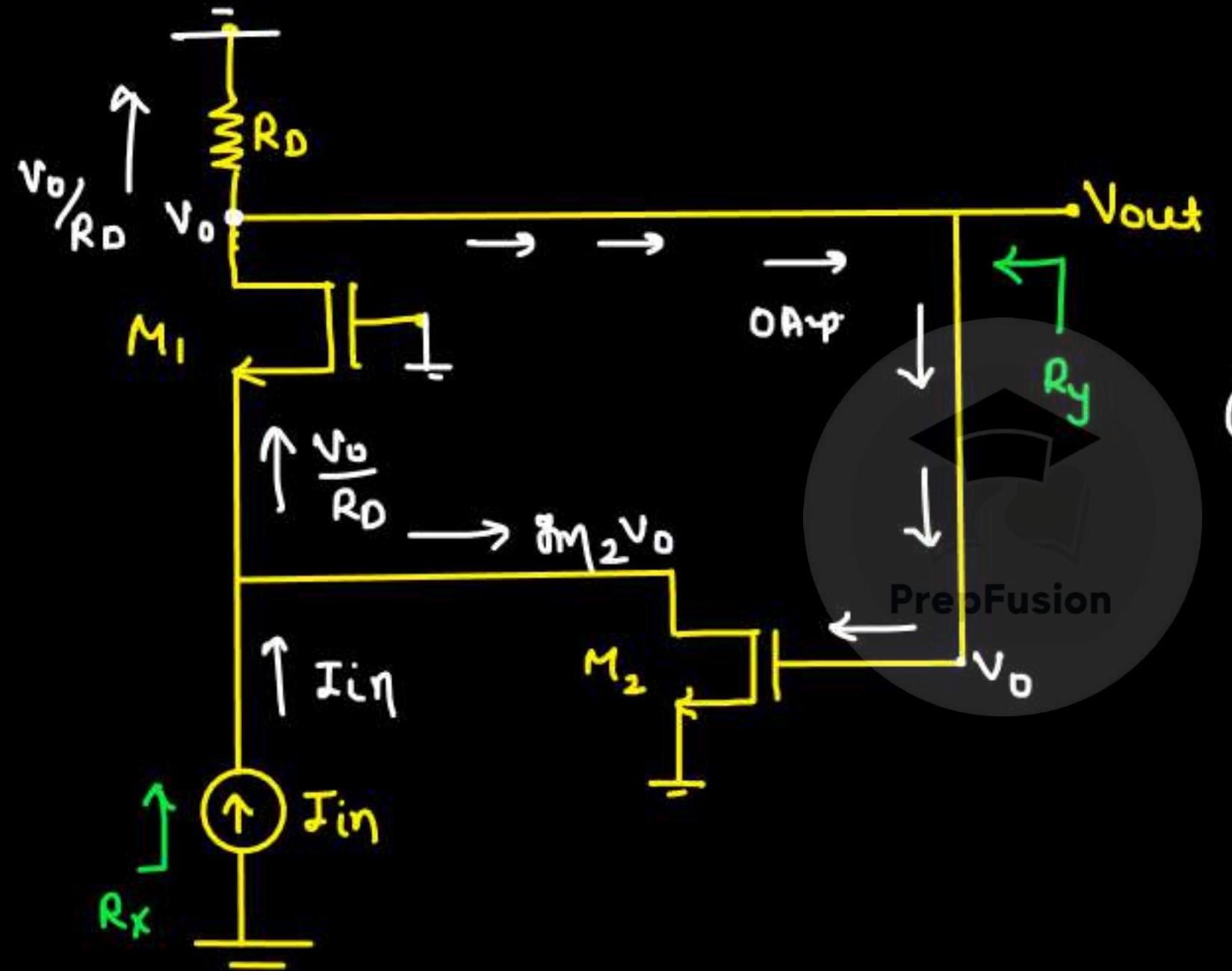

$$① \quad I_{in} = g_{m_2} V_o + \frac{V_o}{R_D}$$

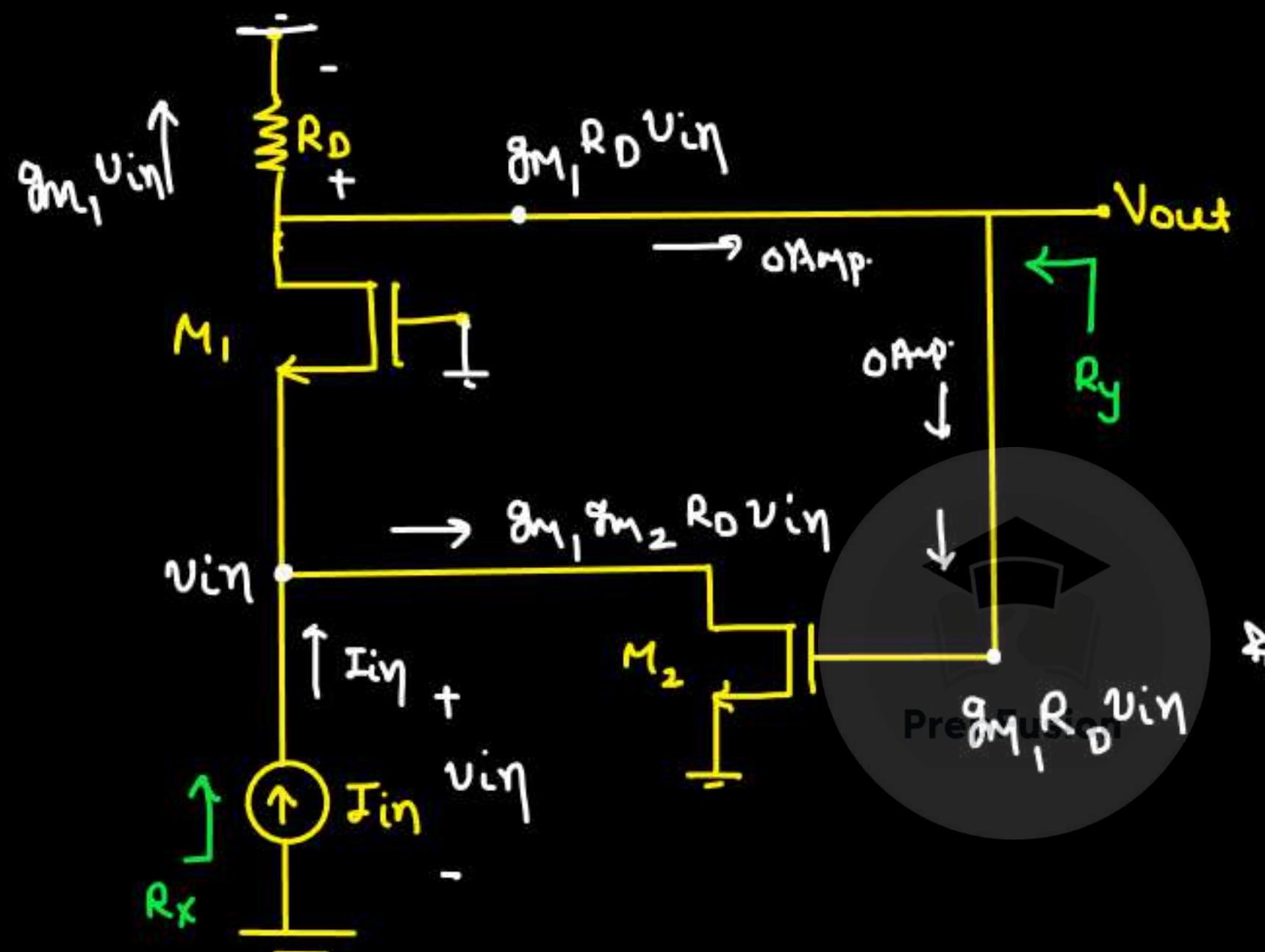
$$\frac{V_o}{I_{in}} = \frac{R_D}{g_{m_2} R_D + 1}$$



$$R_x = \frac{V_{in}}{I_{in}}$$

$$I_{in} = g_m_1 V_{in} + g_m_1 g_m_2 R_D V_{in}$$
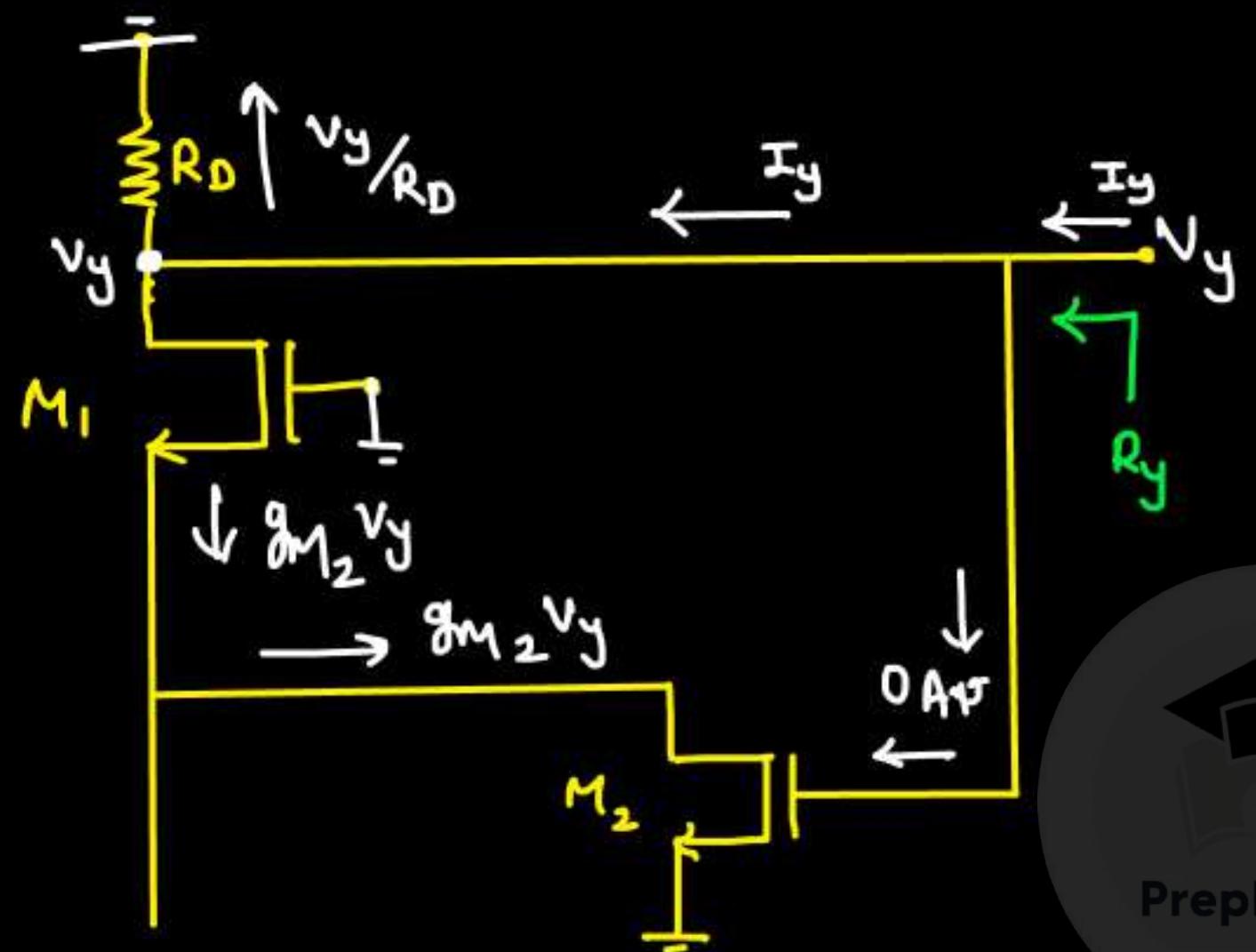
$$\frac{V_{in}}{I_{in}} = \frac{1/g_m_1}{1 + g_m_2 R_D}$$




$$I_y = \frac{V_y}{R_D} + g_{m_2} V_y$$

$$R_y = R_D \parallel \frac{1}{g_{m_2}}$$

$$R_y = \frac{R_D}{1 + g_{m_2} R_D}$$




M-II with the concept of f/b topology:-

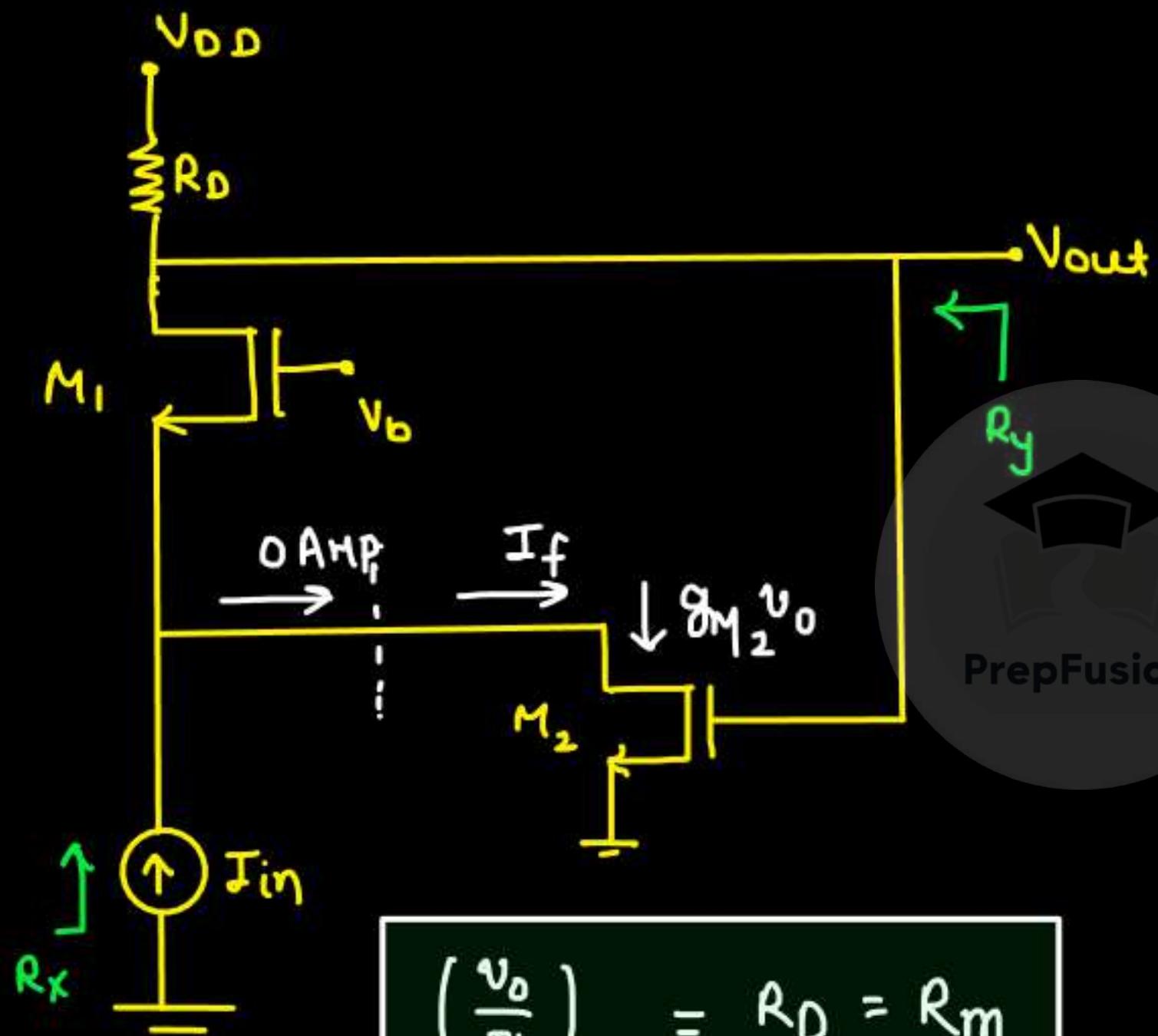


$$\left(\frac{V_o}{I_{in}} \right)_{O.L.} = R_D = R_m$$

$$(R_x)_{O.L.} = \frac{1}{g_m_1}$$

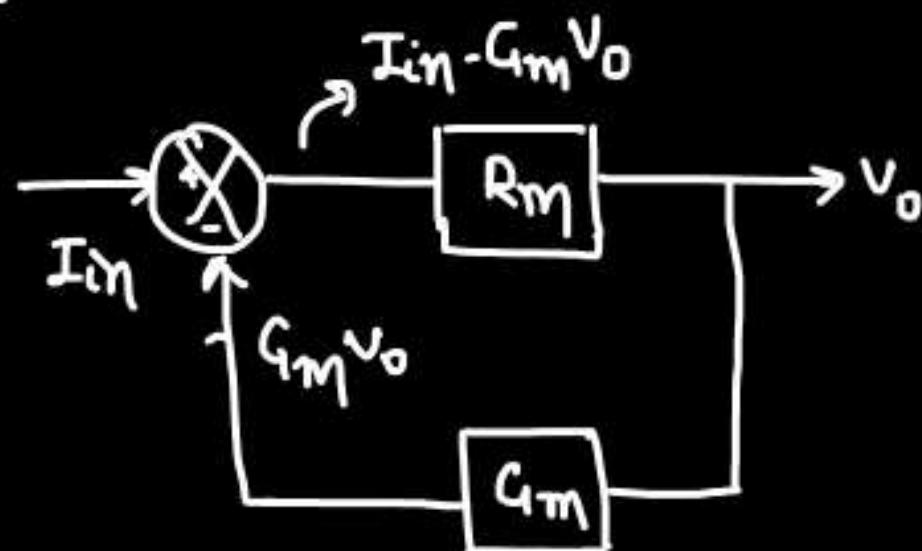

open-loop \rightarrow

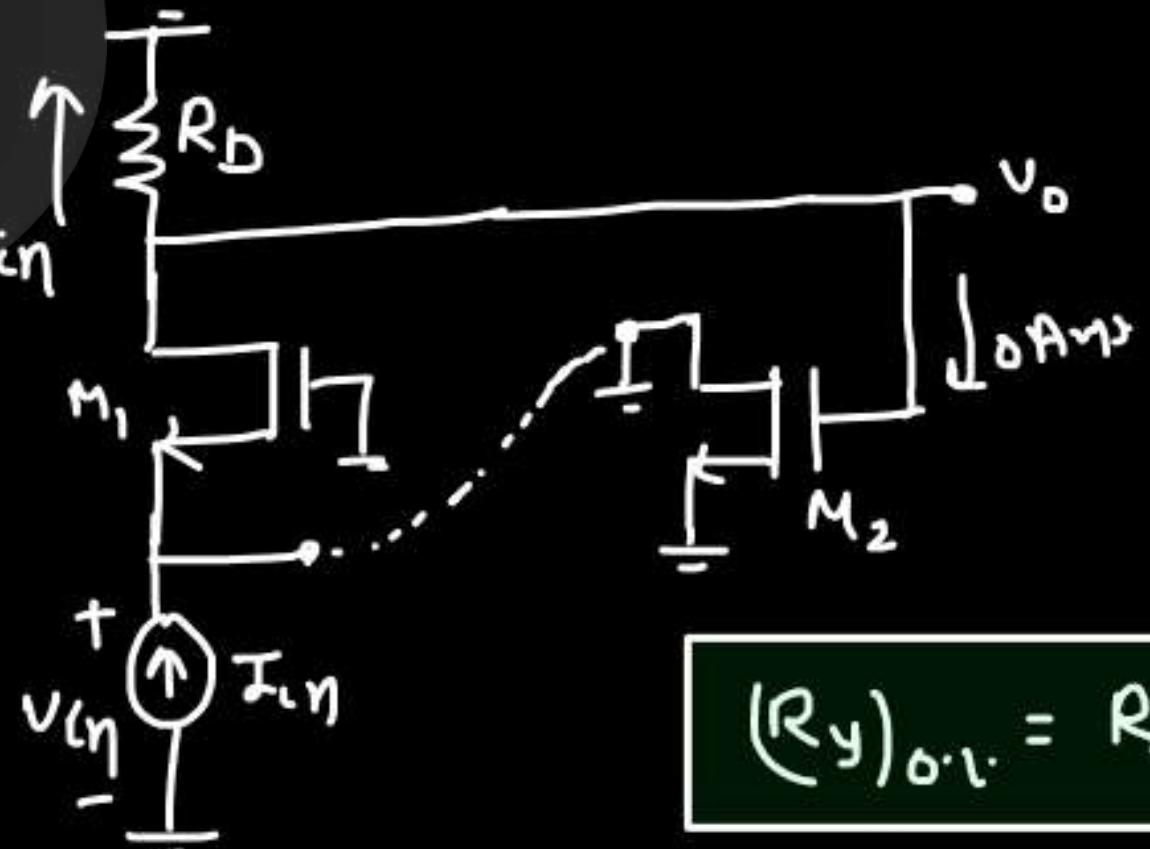

$$(R_y)_{O.L.} = R_D$$

$$I_f = g_m V_o$$

$$\frac{I_f}{V_o} = G_m = g_m$$

① Closed loop gain $\gamma = \frac{R_m}{1 + G_m R_m} = \frac{R_D}{1 + g_m R_D}$


② Closed loop input impedance

PreFusion

$$(R_{in})_f = \frac{1/g_m}{1 + g_m R_D}$$

③ $(R_o)_f = \frac{R_D}{1 + g_m R_D}$

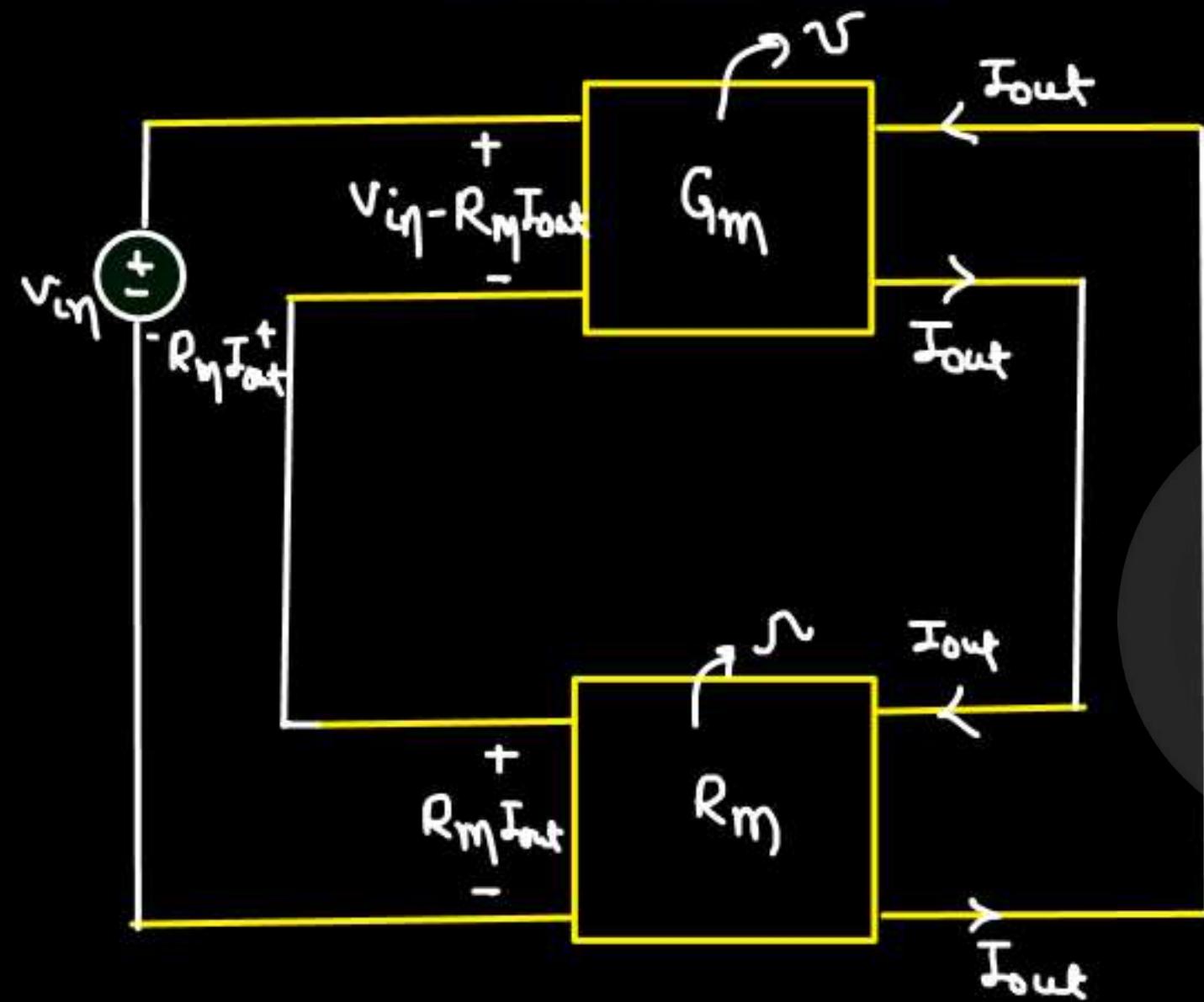* Current-Voltage feedback :- (series-series)



open loop gain = G_m

open loop i/p impedance = R_{in}

loop o/p impedance = R_o

① Closed loop gain = $\frac{G_m}{1 + G_m R_m}$


② Closed loop input impedance

$$(R_i)_f = R_{in} (1 + G_m R_m)$$

③ Closed loop o/p impedance :-


$$(R_o)_f = R_o (1 + G_m R_m)$$


Eg. →

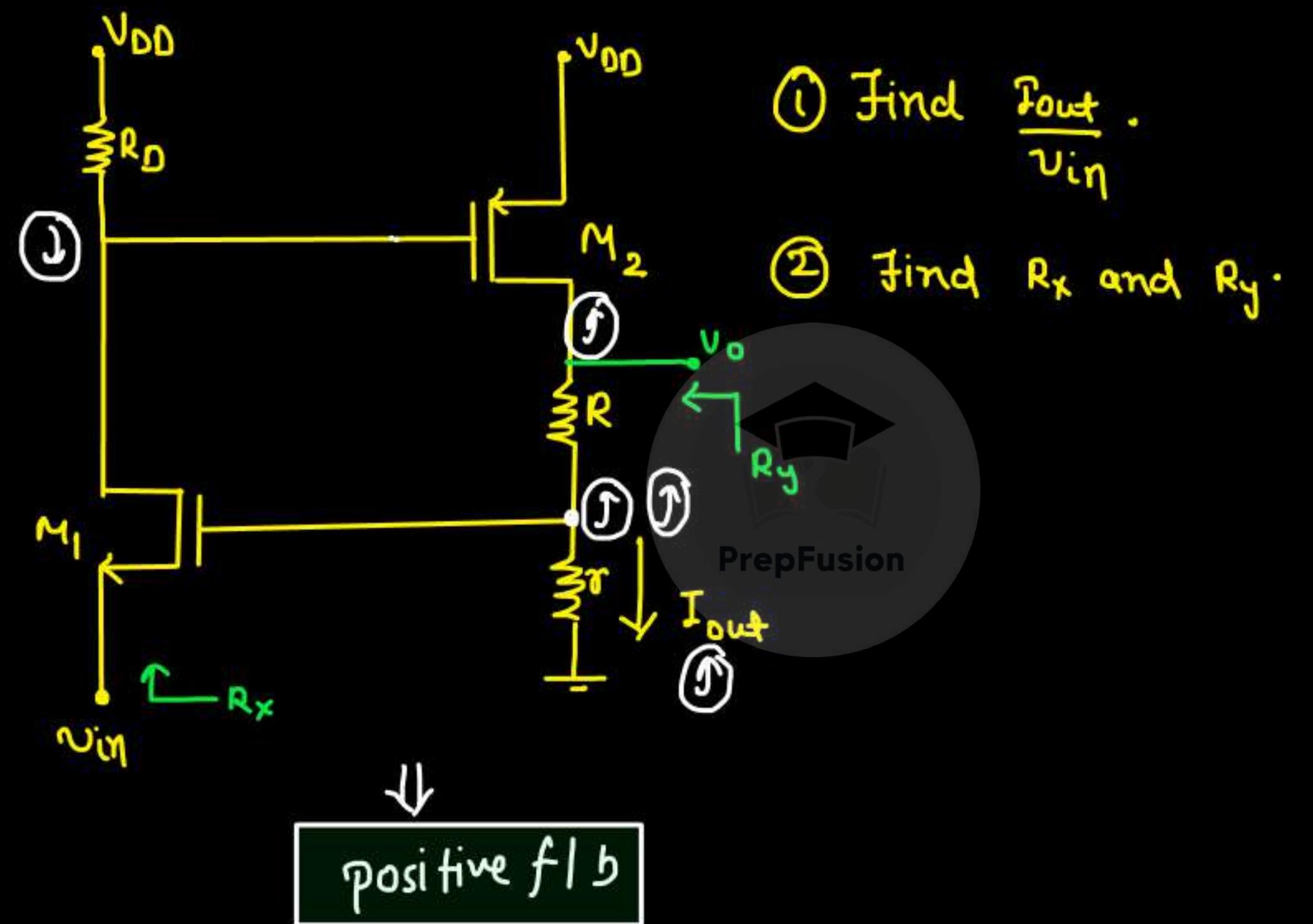

M-I

w/o the concept of feedback:-

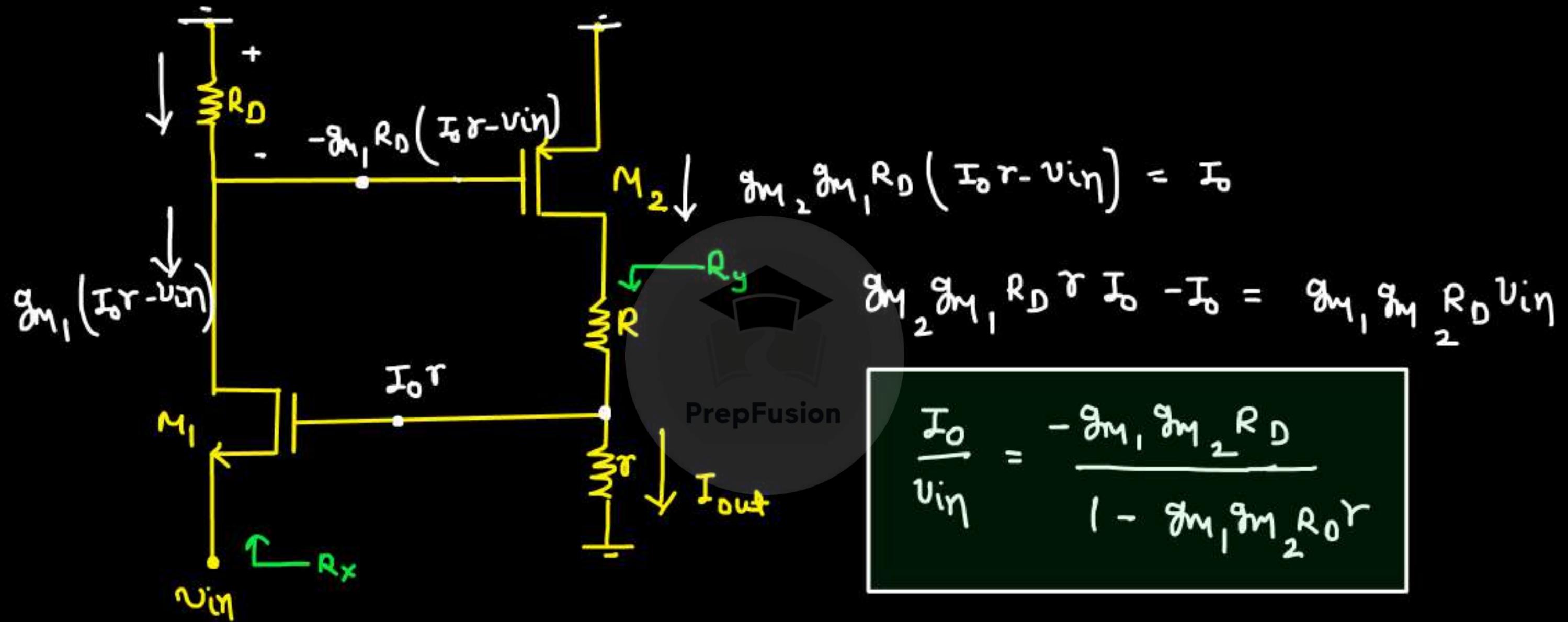


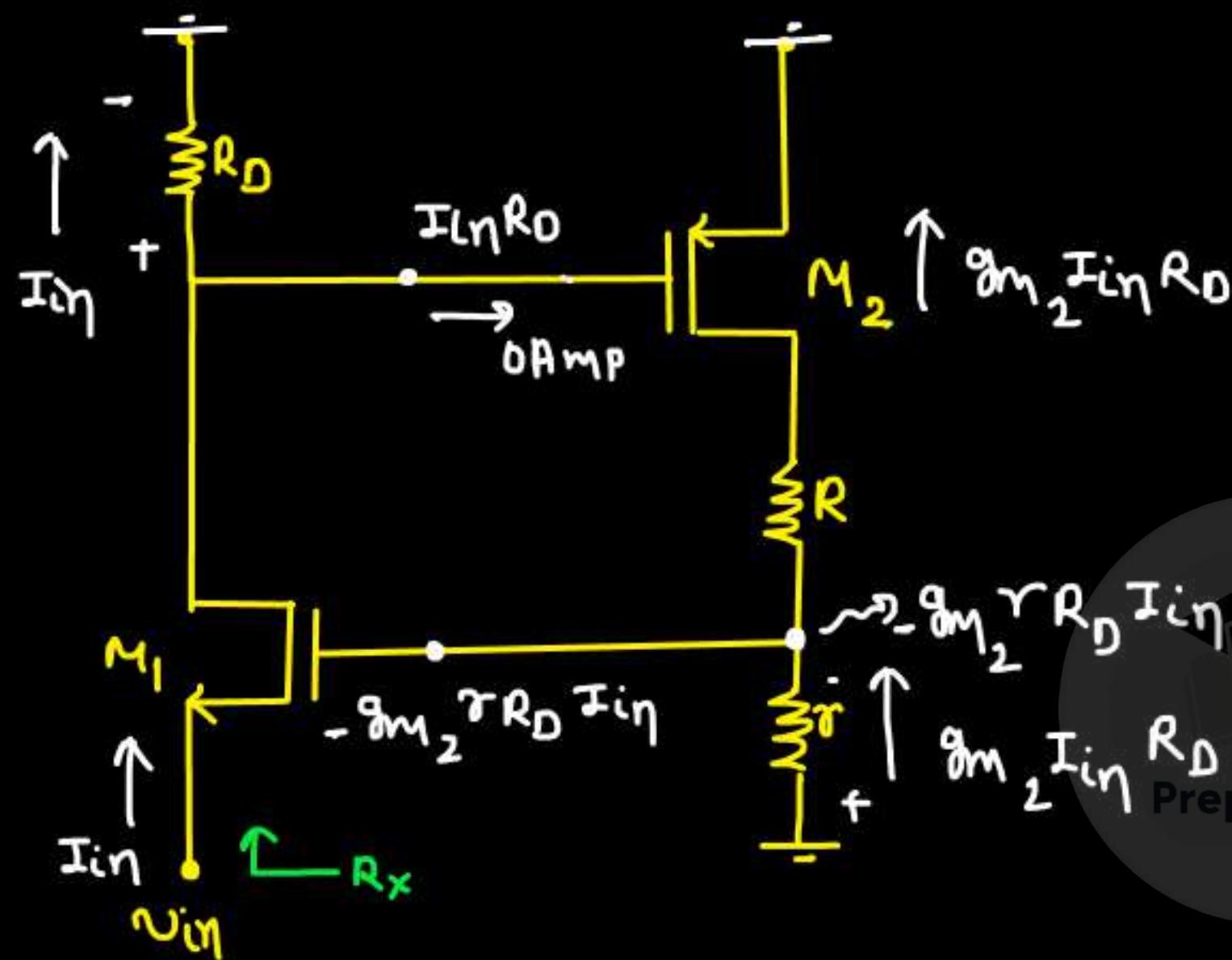

$$g_m (v_{in} + g_m r R_D I_{in}) = I_{in}$$

$$g_m v_{in} = I_{in} [1 - g_m, g_m r R_D]$$
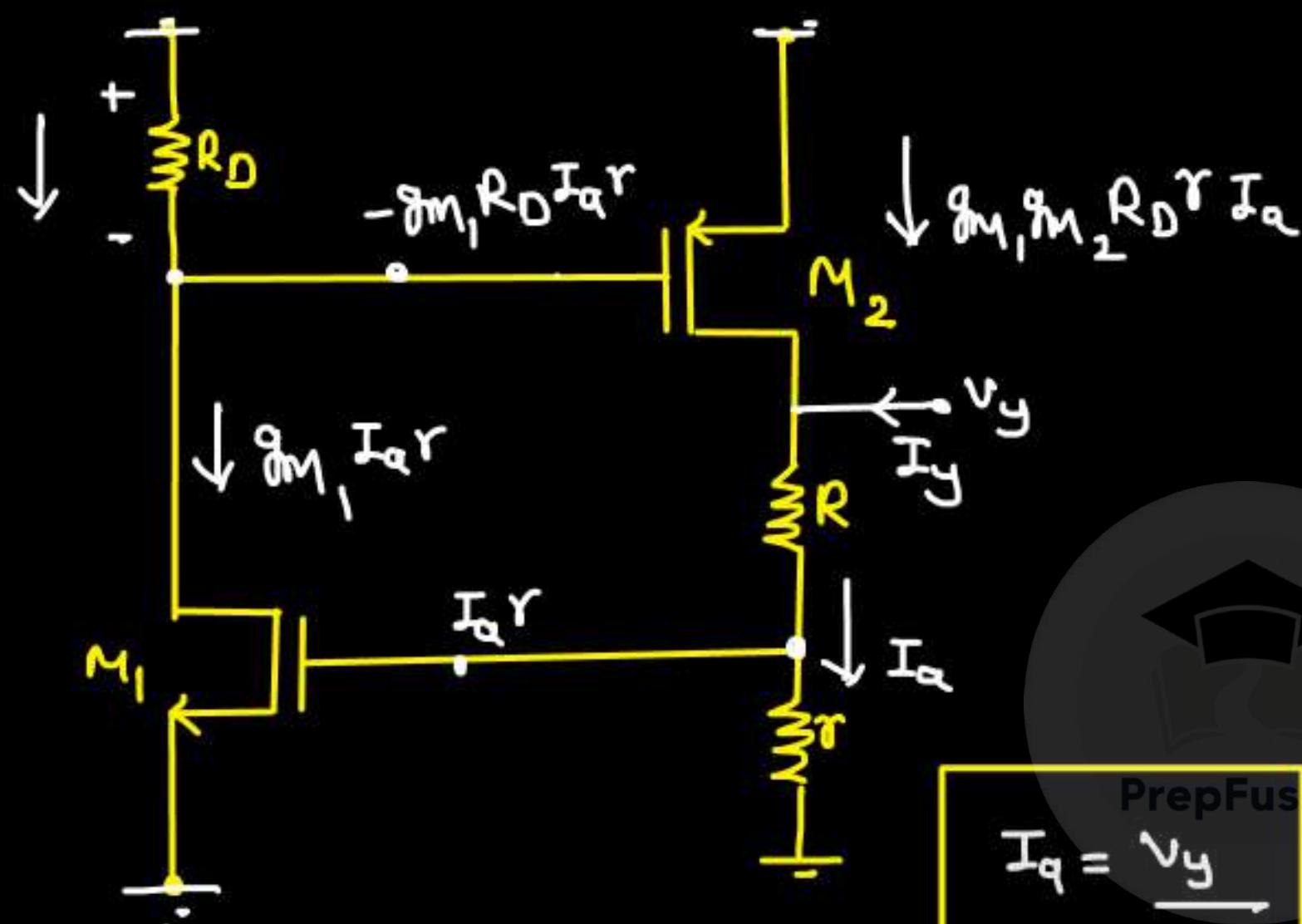
$$\frac{v_{in}}{I_{in}} = \left[1 - g_m, g_m r R_D \right] \frac{1}{g_m}$$



$$R_y = \frac{v_y}{I_y}$$

PrepFusion

$$I_q = \frac{v_y}{r + R}$$


$$\begin{aligned} & \downarrow \frac{g_m_1 g_m_2 R_D r}{I_y} v_y \\ & \downarrow v_y \\ & \downarrow I_q \end{aligned}$$

$$I_y + \frac{g_m_1 g_m_2 R_D r v_y}{r + R} = \frac{v_y}{r + R}$$

$$\frac{v_y}{I_y} > R_y = \frac{r + R}{1 - g_m_1 g_m_2 R_D r}$$


$$I_y = \left(\frac{1 - g_m_1 g_m_2 R_D r}{r + R} \right) v_y$$

M-I with the concept of f/b Topology:-

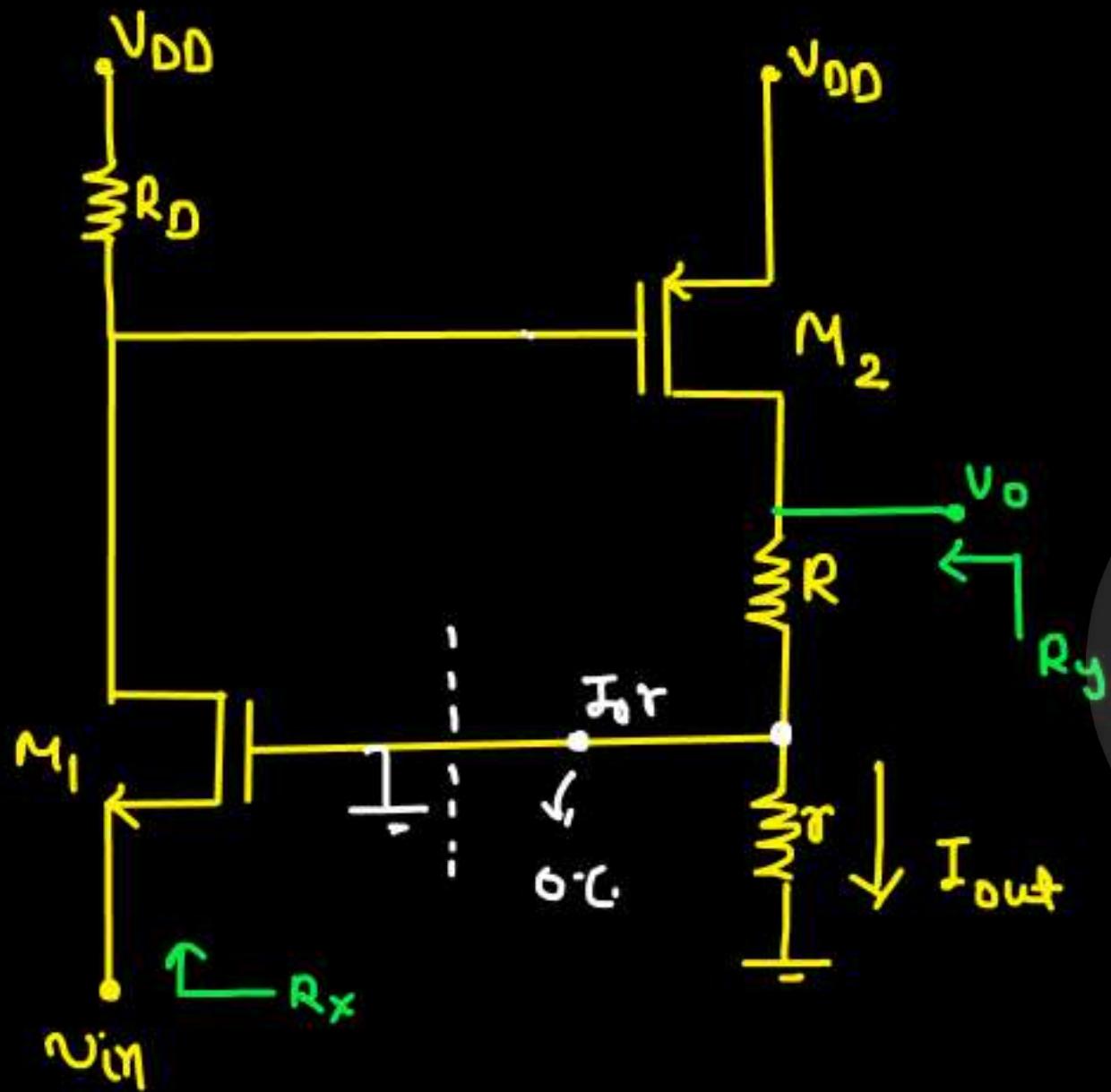

Current - Voltage f/b

Voltage mixing , Current sampling

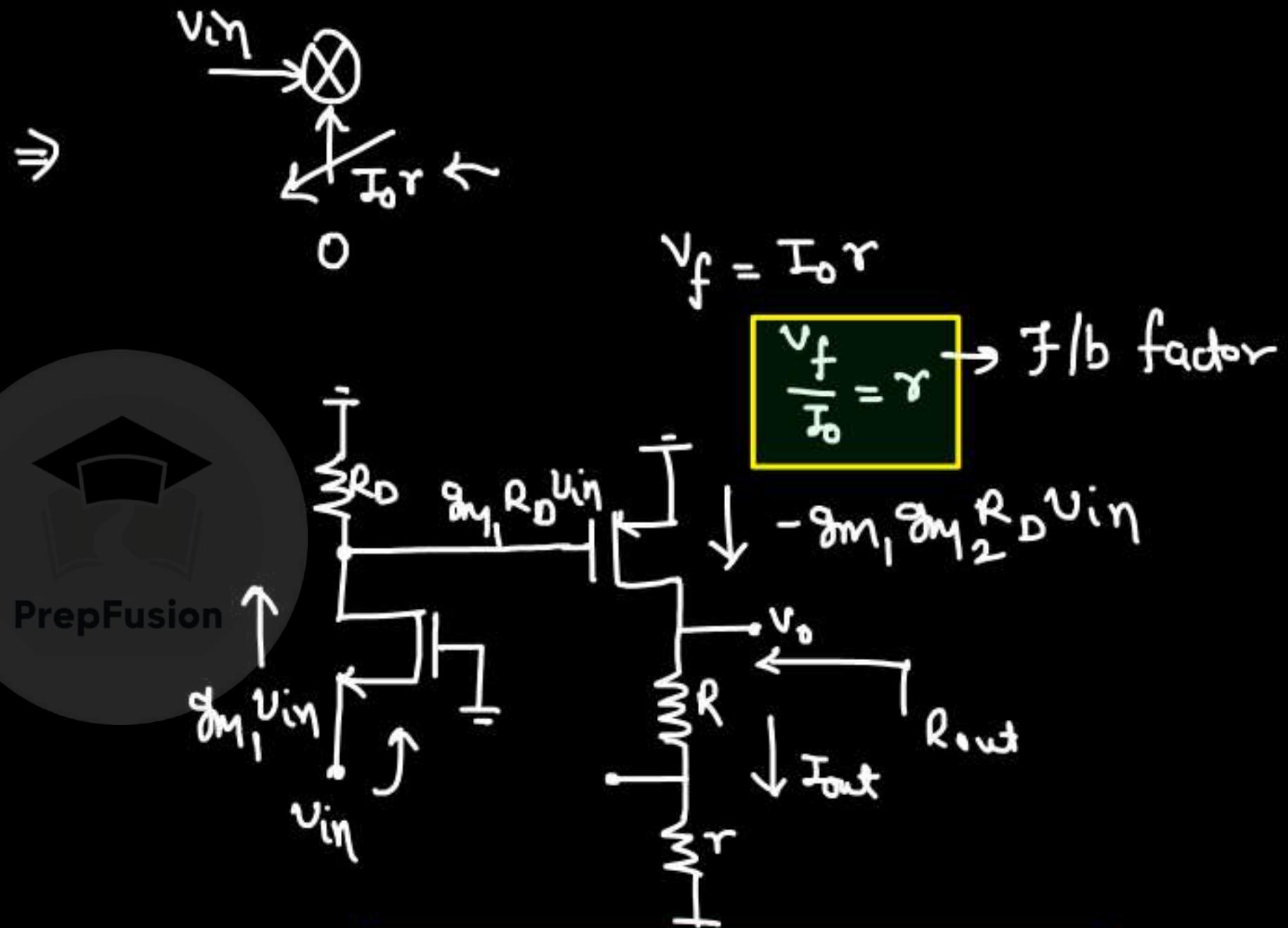

$$\left(\frac{I_{out}}{V_{in}} \right)_{0.L.} = -g_{m1} g_{m2} R_D$$




- 100 HRS. CONTENT
- 400+ QUESTIONS
- LIVE DOUBT SESSIONS
- 10+ TEST SERIES
- LECTURE NOTES

AIR 27 (ECE)
AIR 45 (IN)

$$(R_{in})_{0-L} = \frac{1}{g_m 1}$$

$$(R_o)_{0-L} = R + r$$

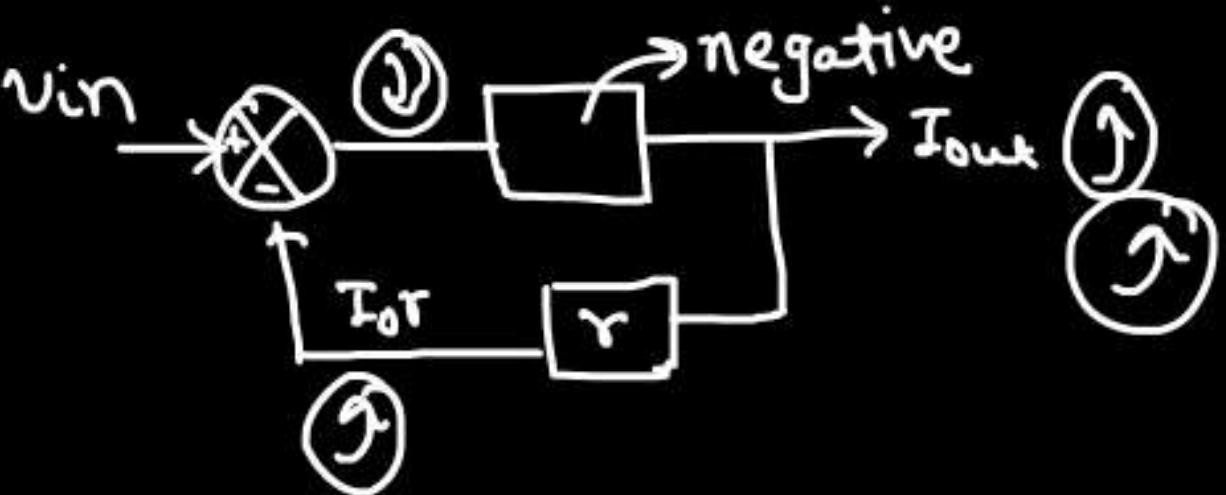


* Closed loop gain = $\frac{-g_m 1 g_m 2 R_D}{1 - g_m 1 g_m 2 R_D Y}$

Preprusion

* $R_x = \frac{1}{g_m 1} [1 - g_m 1 g_m 2 R_D Y]$

* $R_y = (R + r) [1 - g_m 1 g_m 2 R_D Y]$

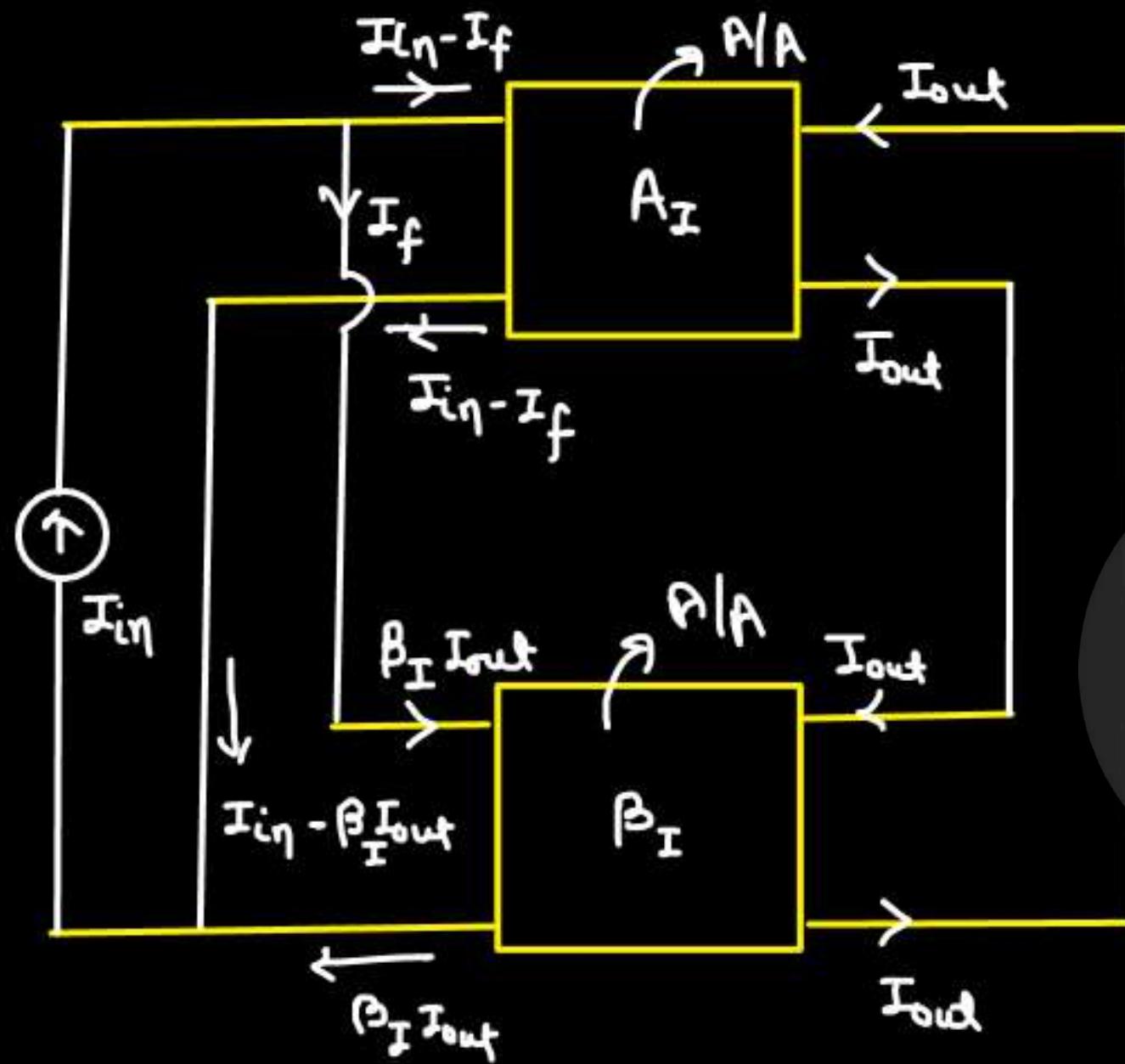* Current-Current feedback:- (Shunt-Series)



open loop gain = A_I

open loop i/p impedance = R_{in}

open loop o/p impedance = R_o

① Closed loop gain = $\frac{A_I}{1 + A_I \beta_I}$


② Closed loop i/p impedance

$$= R_{in} / \\ 1 + A_I \beta_I$$

③ Closed loop o/p impedance

$$= R_o [1 + A_I \beta_I]$$

Eg. →

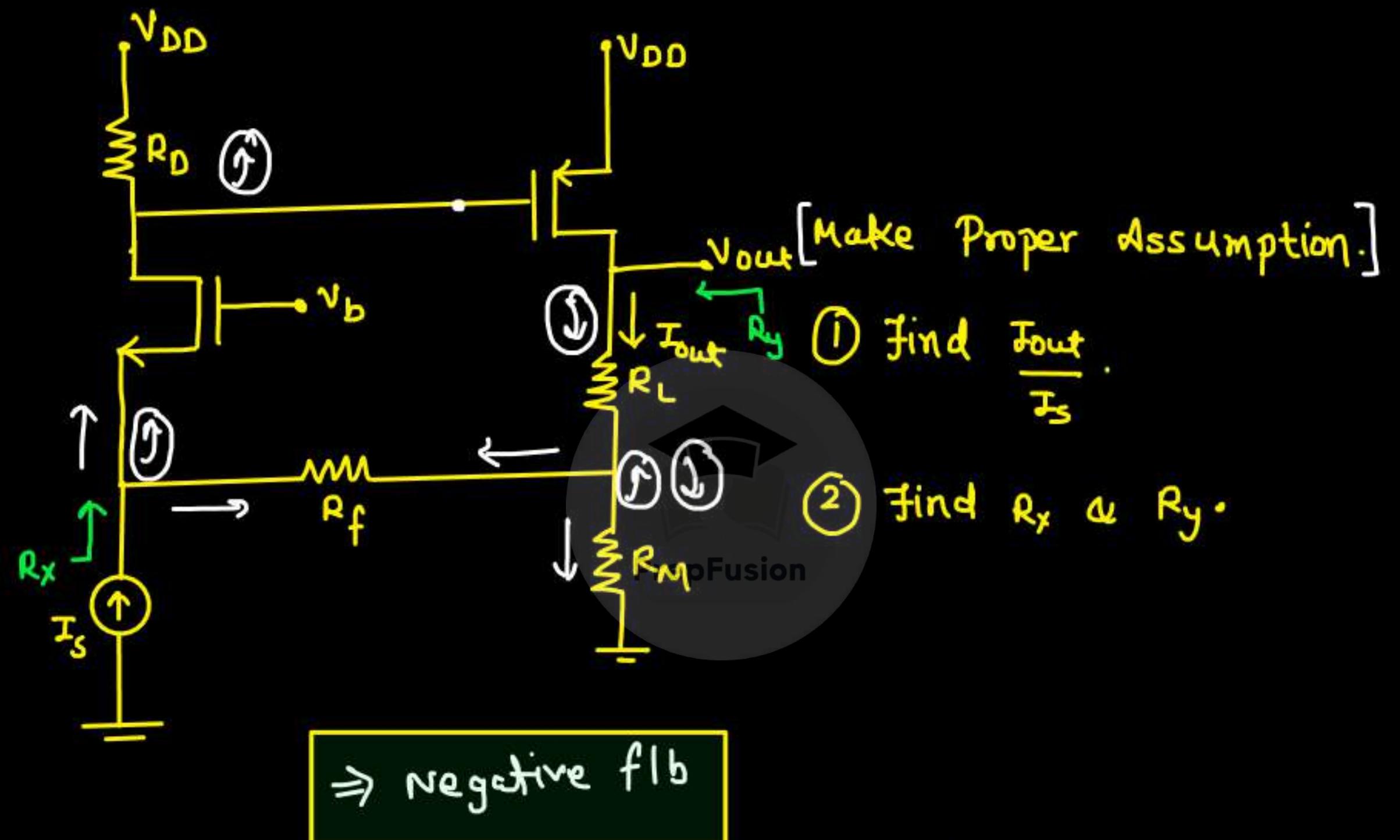


current mixing, current - sampling ⇒

Current - Current f/b Topology

M-I

w/o the concept of f/b Topology :-

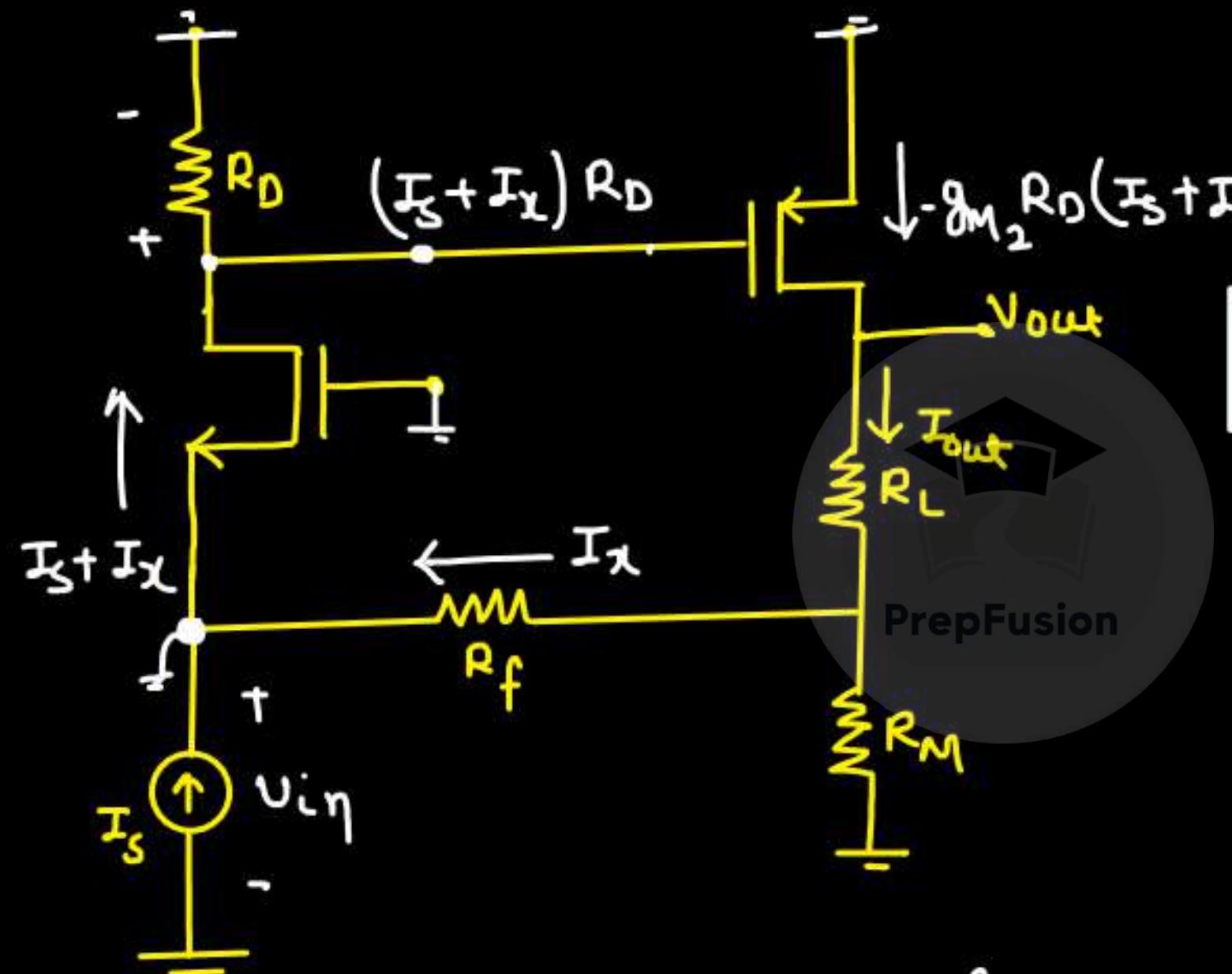

$$\frac{I_{out}}{I_s} = ?$$

CURRENT - CURRENT f/b

$R_{in} \rightarrow$ very low

$\frac{V_{in}}{I_s} \rightarrow$ very low


I can take $V_{in} \rightarrow 0$

$$I_x = \frac{R_M}{R_M + R_f} I_{out}$$

$$-g_m R_D \left(I_S + \frac{R_M}{R_M + R_f} I_{out} \right) = I_{out}$$

$$-g_m R_D I_S = I_{out} \left[1 + \frac{g_m R_D R_M}{R_M + R_f} \right]$$

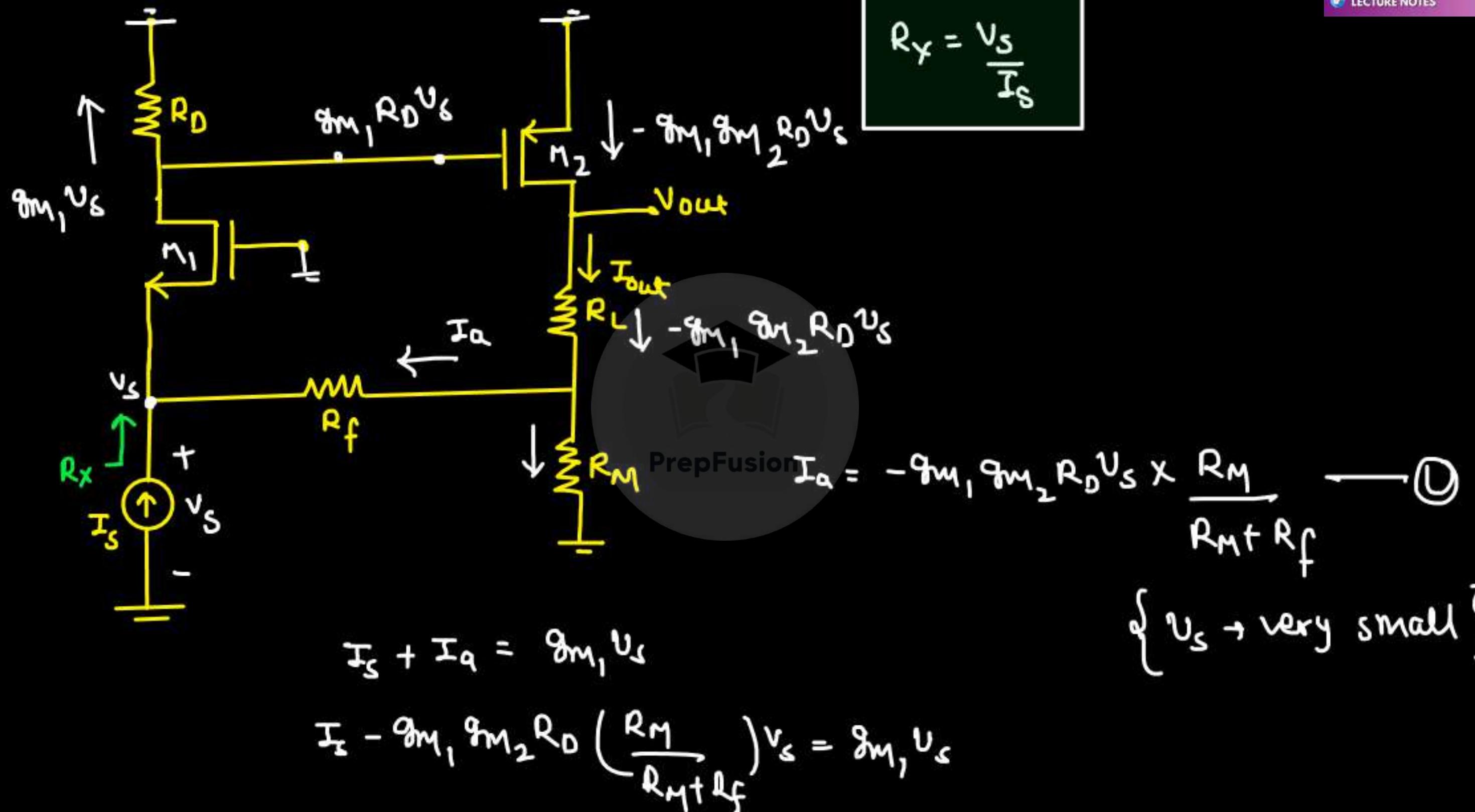
$$\frac{I_{out}}{I_S} = \frac{-g_m R_D}{1 + g_m R_D \left(\frac{R_M}{R_M + R_f} \right)}$$



$$I_S = \left[g_{m_1} + g_{m_1} g_{m_2} R_D \left(\frac{R_M}{R_M + R_f} \right) \right] V_S$$

$$R_x = \frac{V_S}{I_S} = \frac{1/g_{m_1}}{1 + g_{m_2} R_D \left(\frac{R_M}{R_M + R_f} \right)}$$

PrepFusion

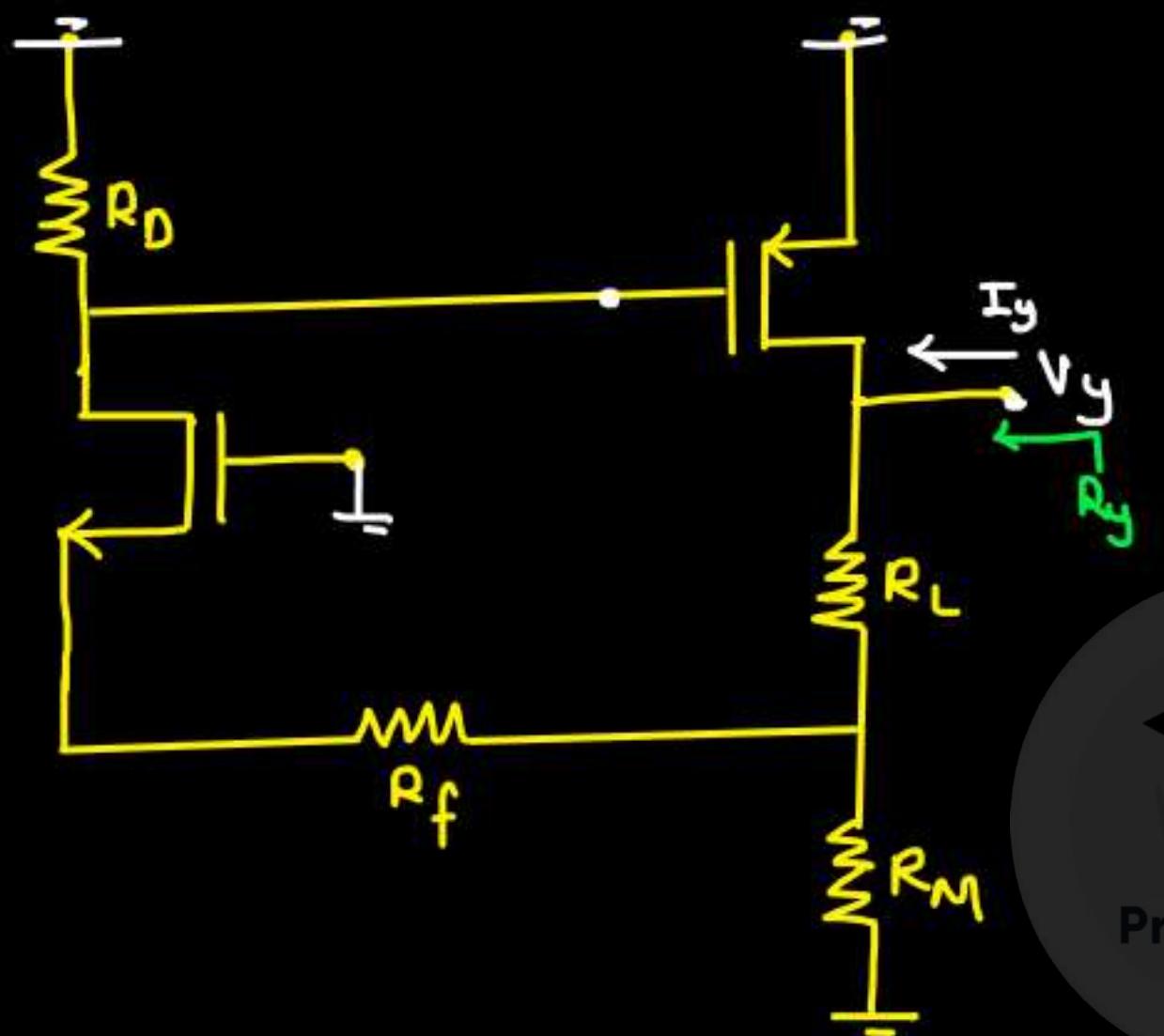


$$R_y = \frac{V_y}{I_y}$$


complex
expression =



with the concept of f/b Topology:-

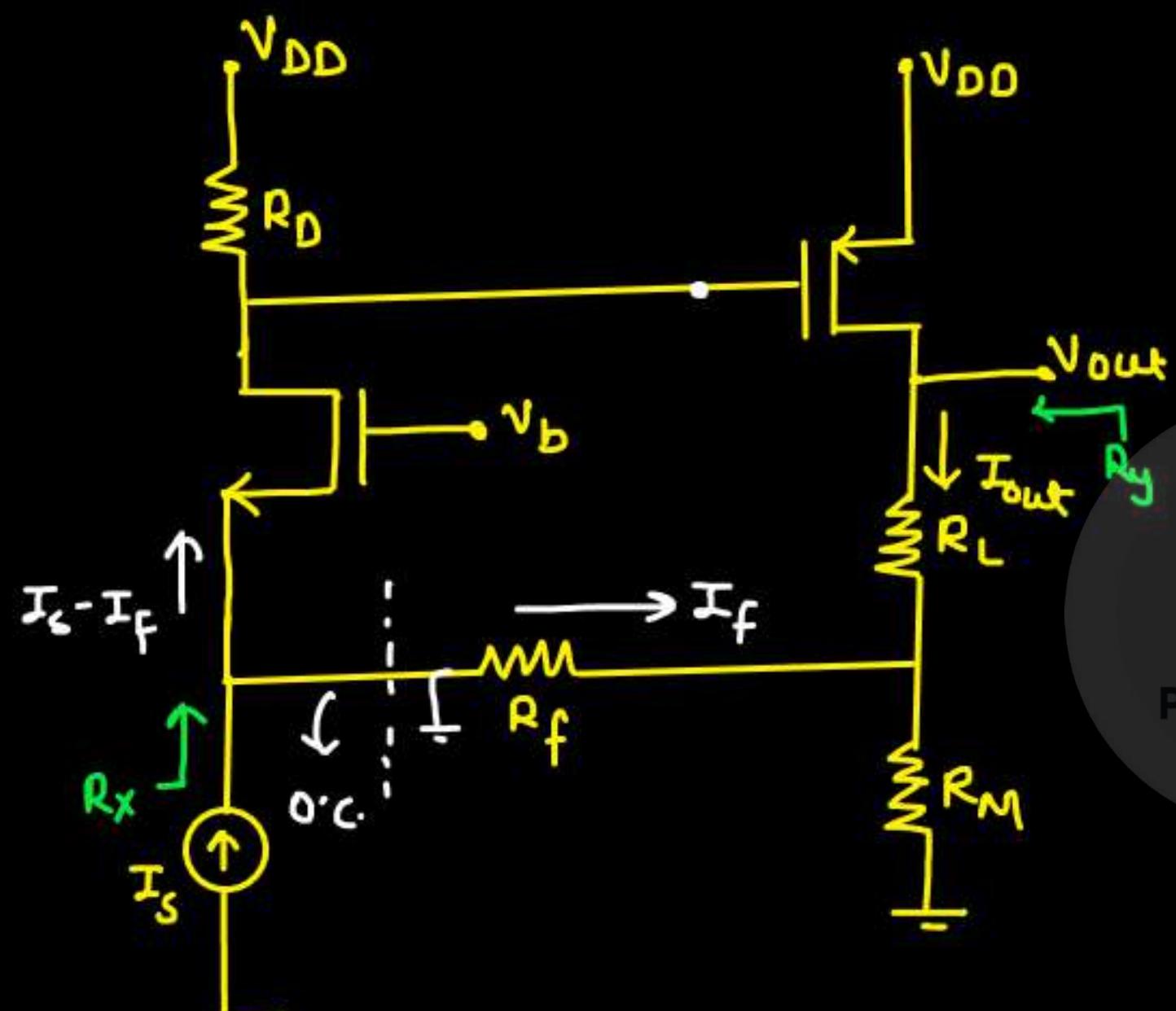

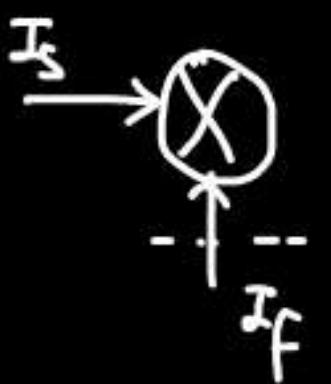
$$\left(\frac{I_{out}}{I_s}\right)_{0.L.} = -g_{M_2} R_D$$




$$I_f = -\frac{R_M}{R_M + R_f} I_{out}$$

$$R_f$$

$$\beta_I = -\frac{R_M}{R_M + R_f}$$

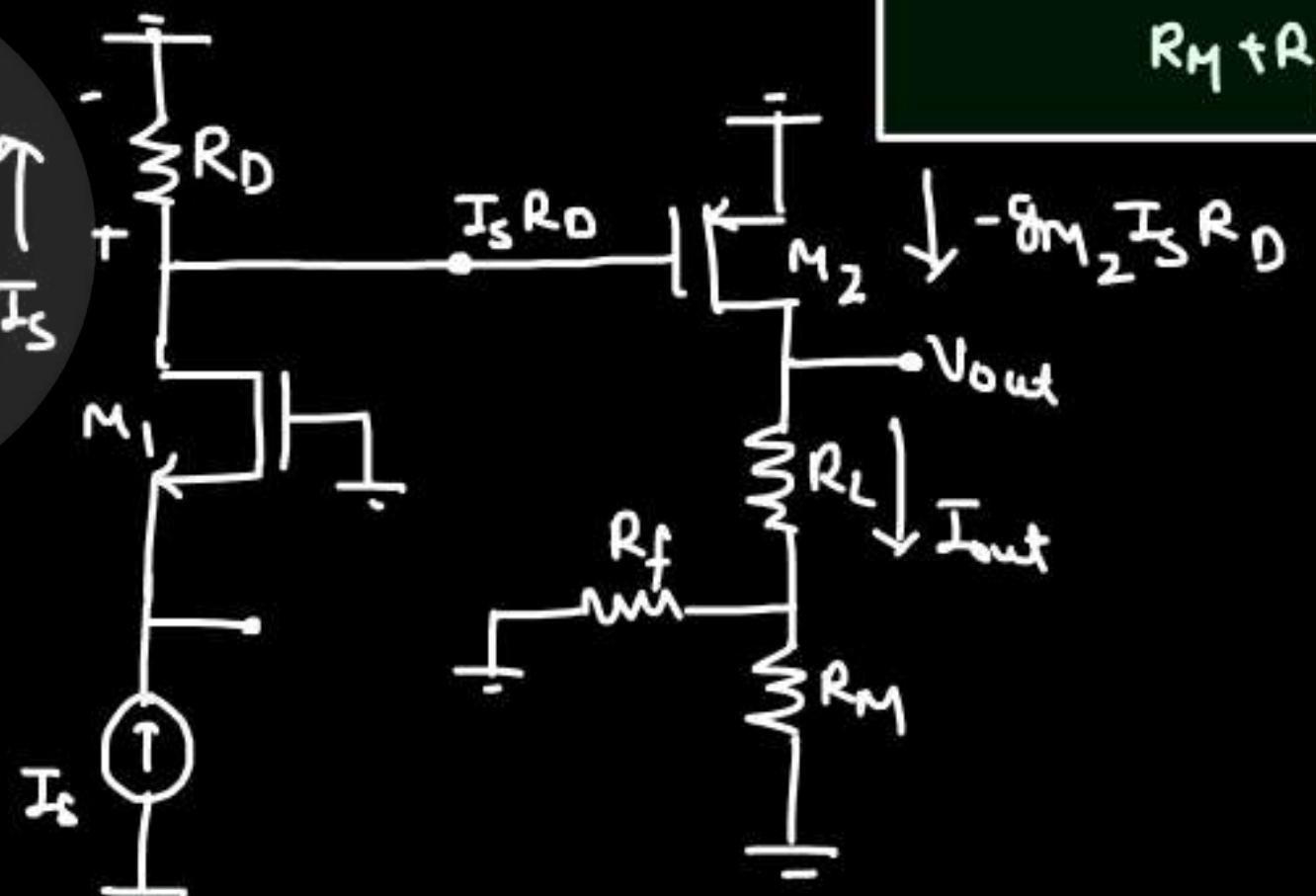

$$I_{out} = -g_{M_2} I_s R_D$$

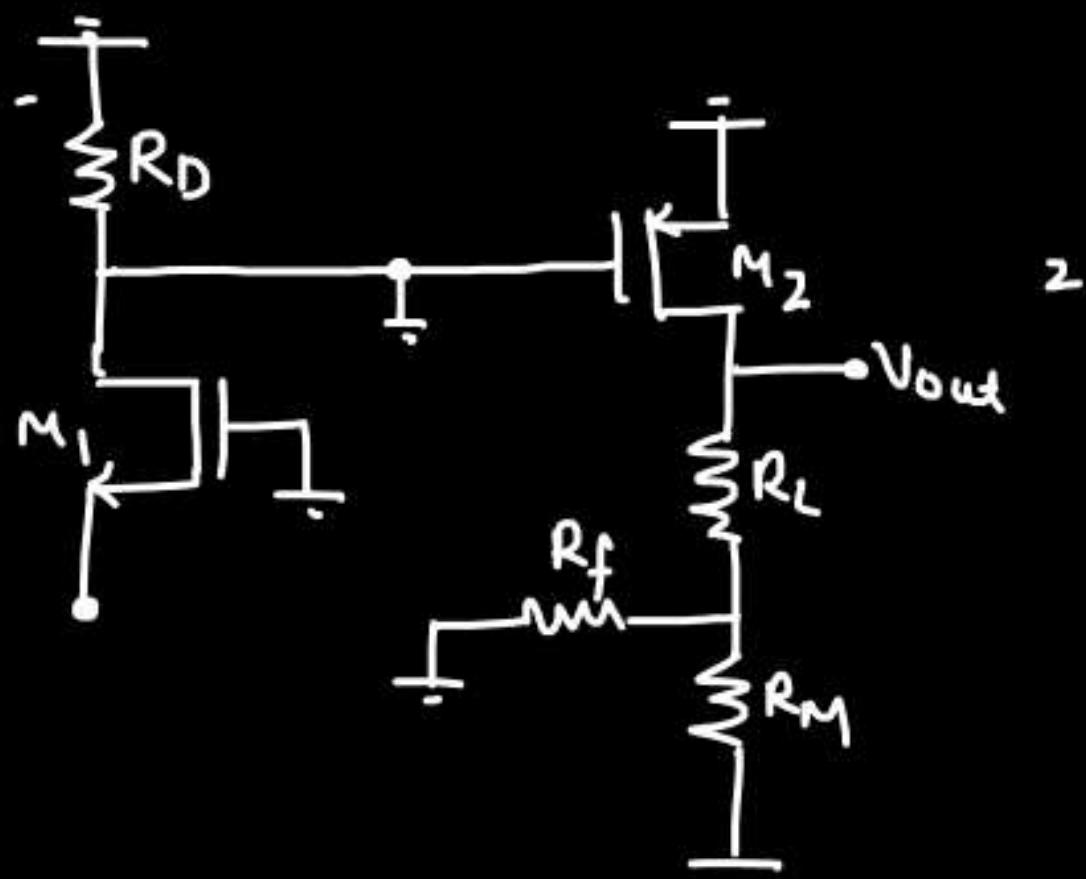


$$(R_i)_{o \cdot L} = \frac{1}{g_m 1}$$

$$(R_o)_{o \cdot L} = (R_L + R_M || R_f)$$



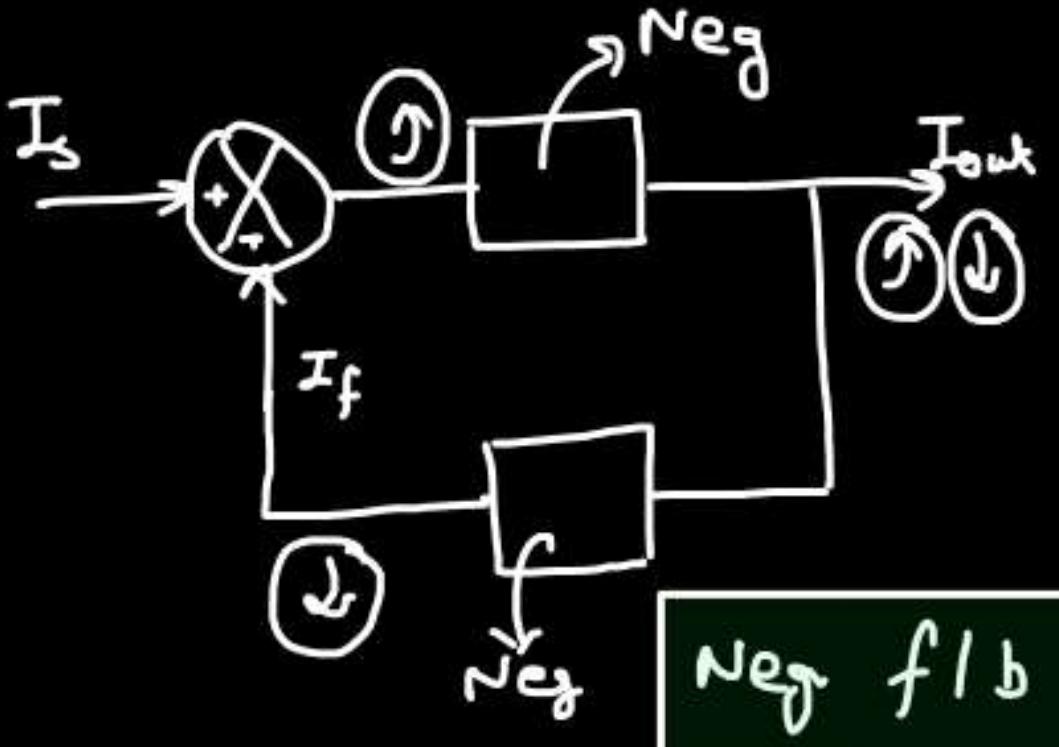① Closed loop gain = $\frac{-g_m 2 R_D}{(1 + g_m 2 R_D \left(\frac{R_M}{R_M + R_f} \right))}$ PrepFusion




② $R_x = \frac{1/g_m 1}{(1 + g_m 2 R_D \left(\frac{R_M}{R_M + R_f} \right))}$


③ $R_y = (R_L + R_M || R_f) \left(1 + g_m 2 R_D \left\{ \frac{R_M}{R_M + R_f} \right\} \right)$





- ⌚ 100 HRS. CONTENT
- ❓ 400+ QUESTIONS
- 🕒 LIVE DOUBT SESSIONS
- 📝 10+ TEST SERIES
- 🌐 LECTURE NOTES


Type of feedback Topology	Forward gain (open loop)	Feedback factor (β)	Closed loop Gain	Closed loop Input impedance	Closed loop O/P impedance
1. Voltage - voltage	A_V	β_V	$\frac{\alpha_V}{1 + \alpha_V \beta_V}$	$R_{in} (1 + \alpha_V \beta_V)$	$R_o \frac{1}{1 + A_I \beta_I}$
2. Voltage - current	R_m	G_m	$\frac{R_m}{1 + G_m R_m}$	$\frac{R_{in}}{1 + G_m R_m}$	$\frac{R_o}{1 + G_m R_m}$
3. Current - voltage	G_m	R_m	$\frac{G_m}{1 + R_m G_m}$	$R_{in} (1 + G_m R_m)$	$R_o (1 + G_m R_m)$
4. Current - current	A_I	β_I	$\frac{A_I}{1 + A_I \beta_I}$	$\frac{R_{in}}{1 + A_I \beta_I}$	$R_o (1 + A_I \beta_I)$

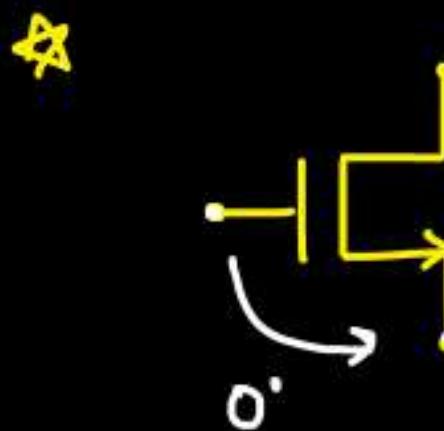

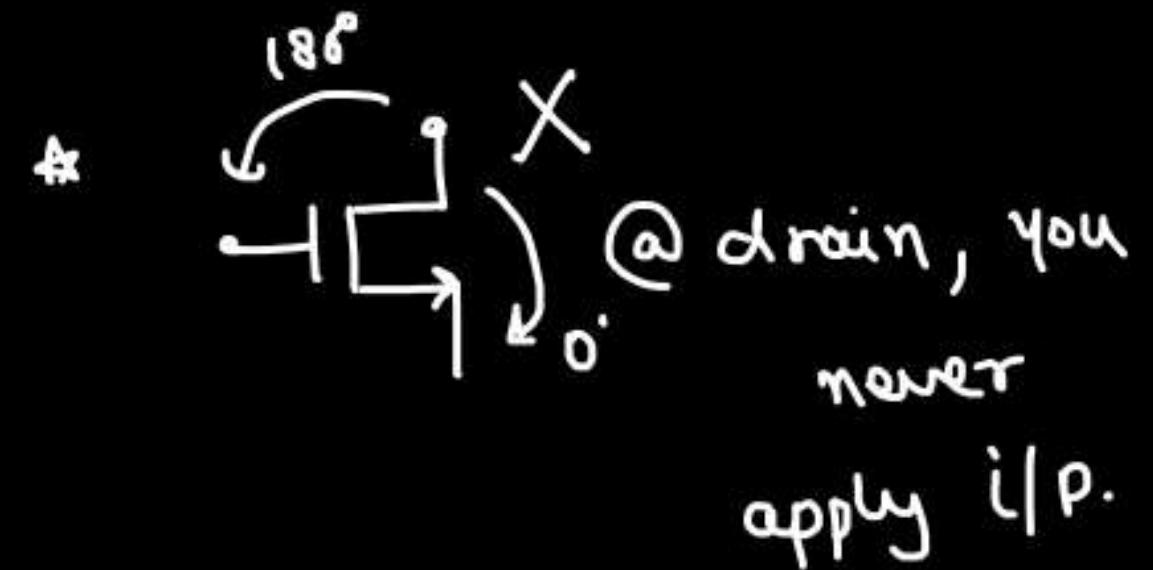* 

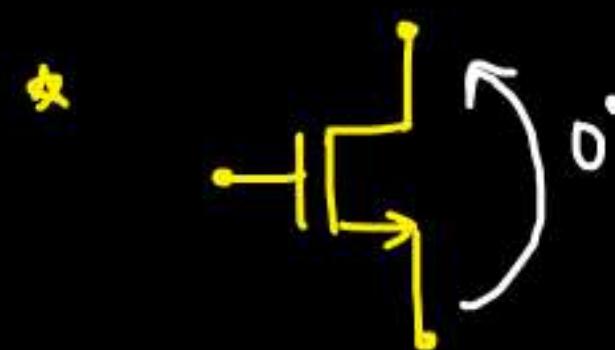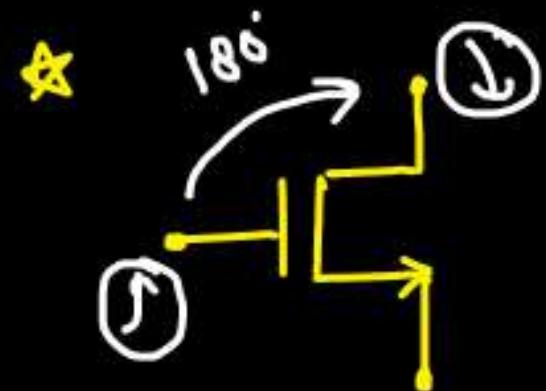

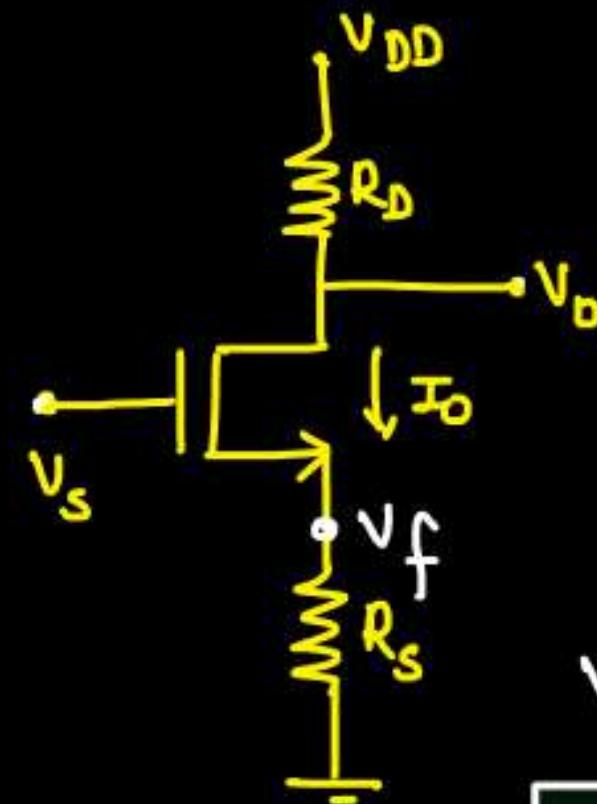Q. Determine the type of feedback and feedback factor.



$$V_f = I_o R_S$$


(a)

Current sampled

Voltage mixing

Current - Voltage

$$R_{in} = \frac{V_f}{I_o} = R_S$$

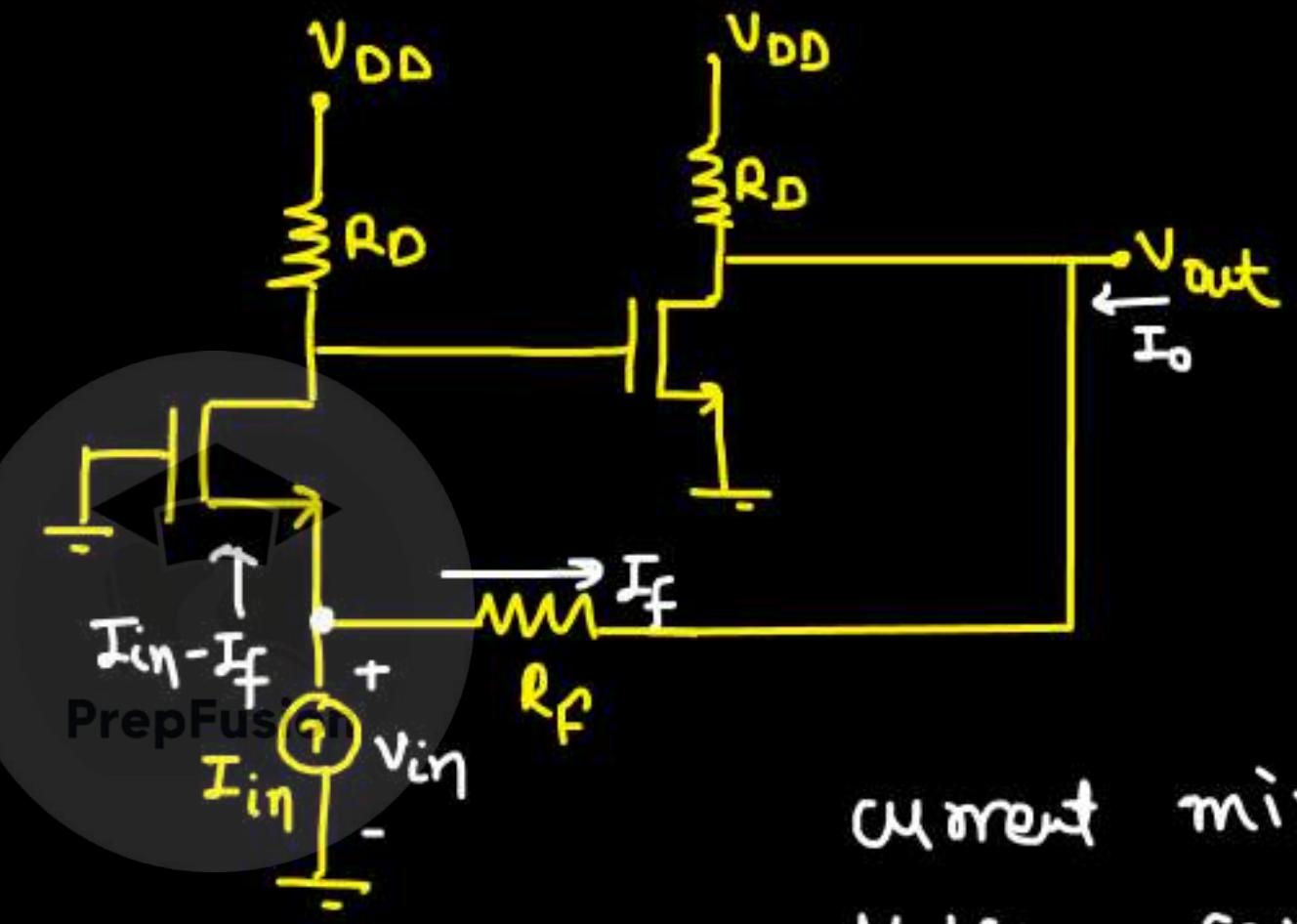

(b)

$$\frac{V_D}{R_f} = -I_f$$


$$\frac{I_f}{V_D} = -\frac{1}{R_f}$$

current mixing


Voltage Sampling

→ Voltage - Current

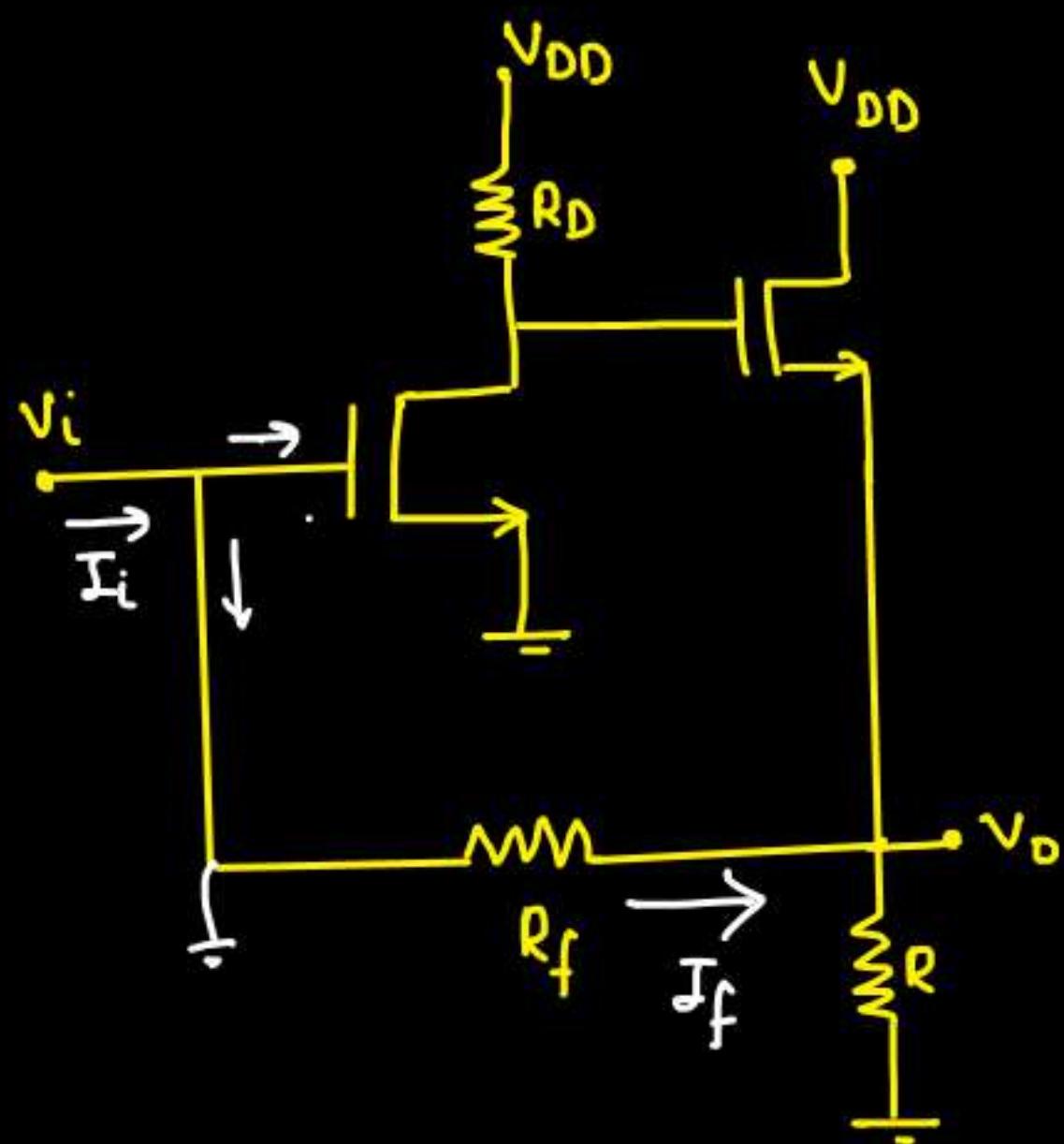← $(R_{in})_f \rightarrow \text{low} \Rightarrow V_{in} \rightarrow 0$



(c)
current mixing
Voltage Sampling

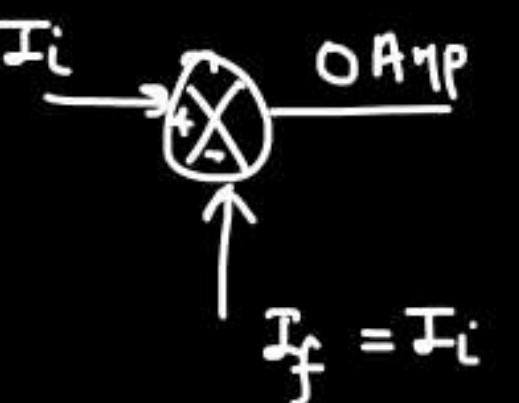

$$I_f = -\frac{V_o}{R_f}$$


$$\frac{I_f}{V_o} = -\frac{1}{R_f}$$



Voltage - Current

$R_{in} \rightarrow \text{low} \Rightarrow V_{in} \rightarrow \text{low}$

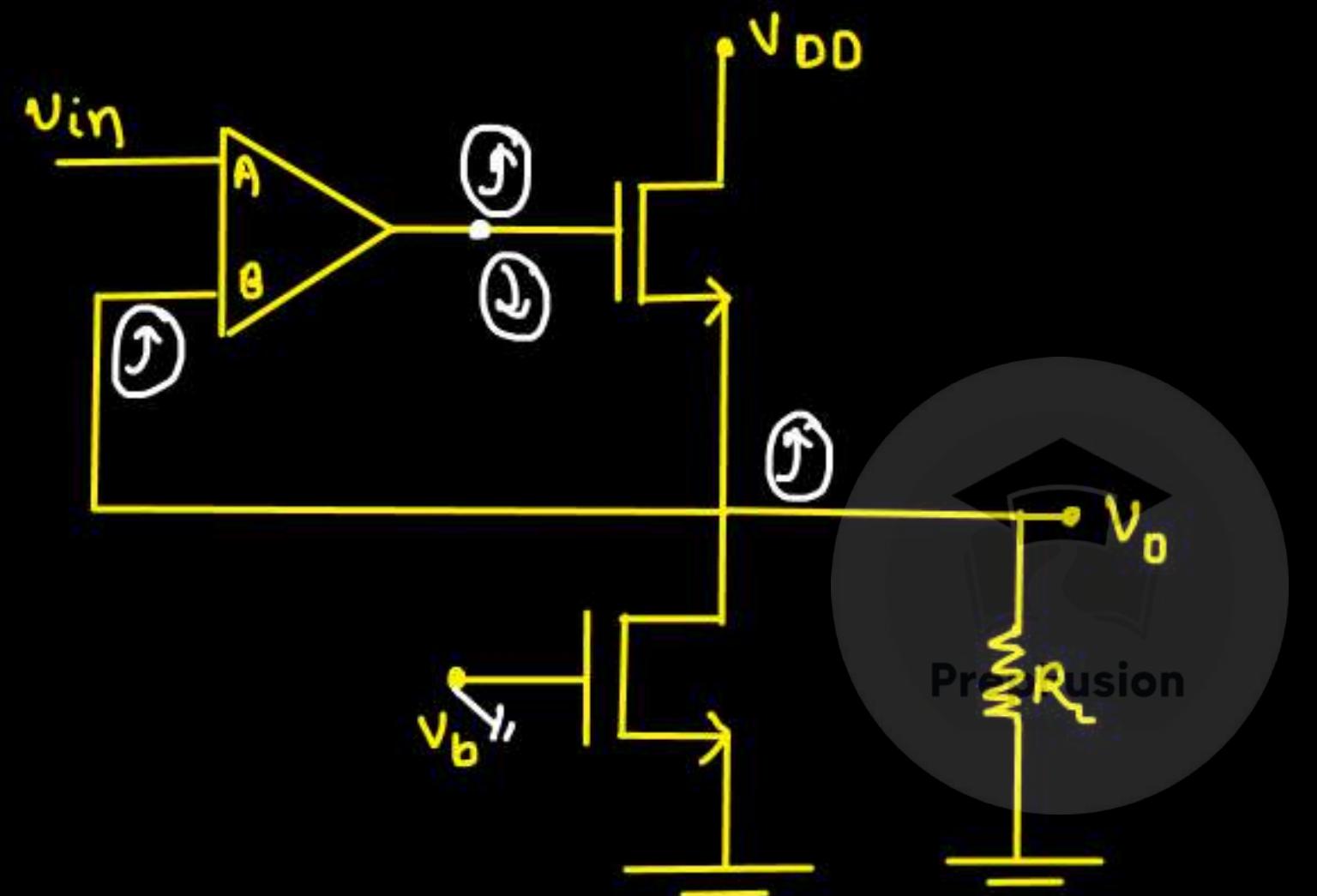Q. Determine the sign of A and B for Negative f/b.





(a)

$$\text{Neg f/b} \rightarrow 180^\circ, 540^\circ - \dots (2n+1)180^\circ$$

$$\text{Pos f/b} \rightarrow 0^\circ, 360^\circ - \dots 360^\circ n =$$


B \rightarrow -ve
A \rightarrow +ve

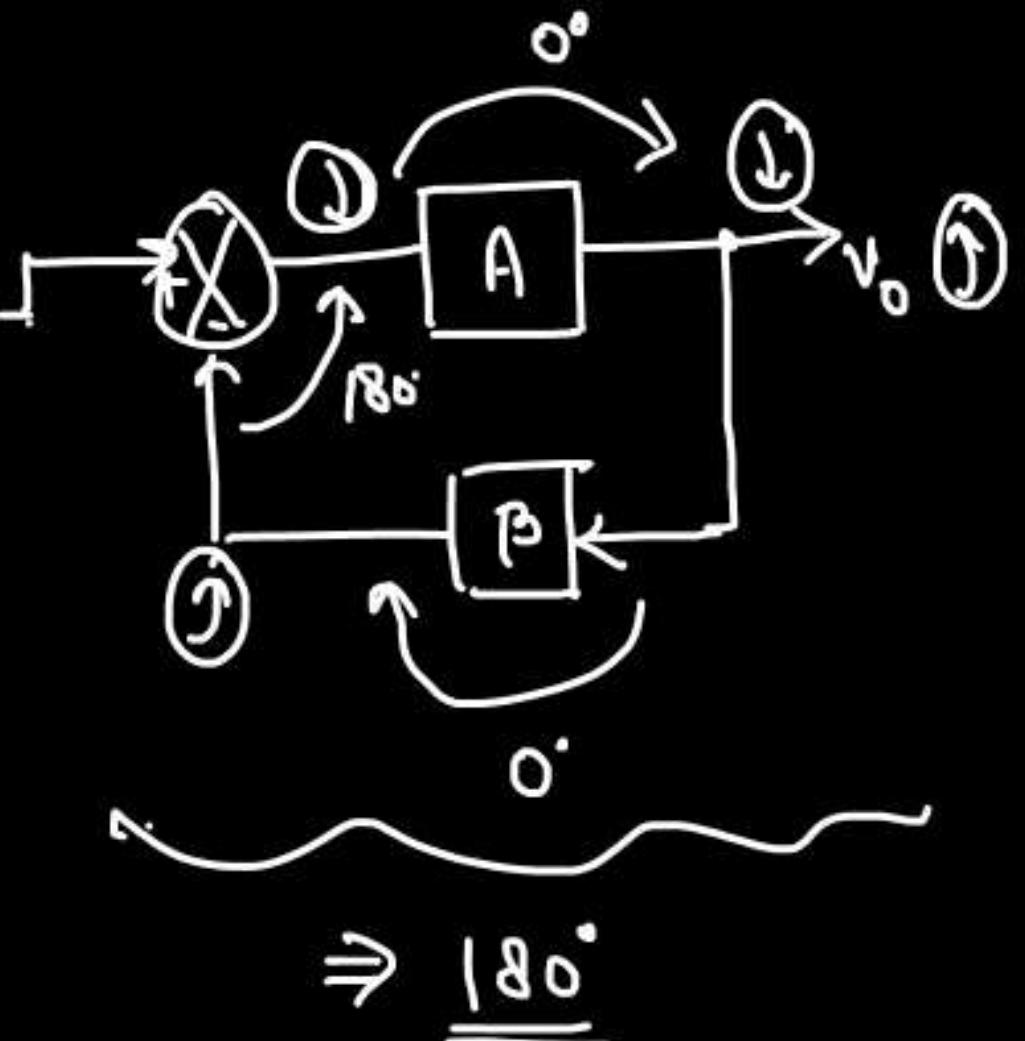

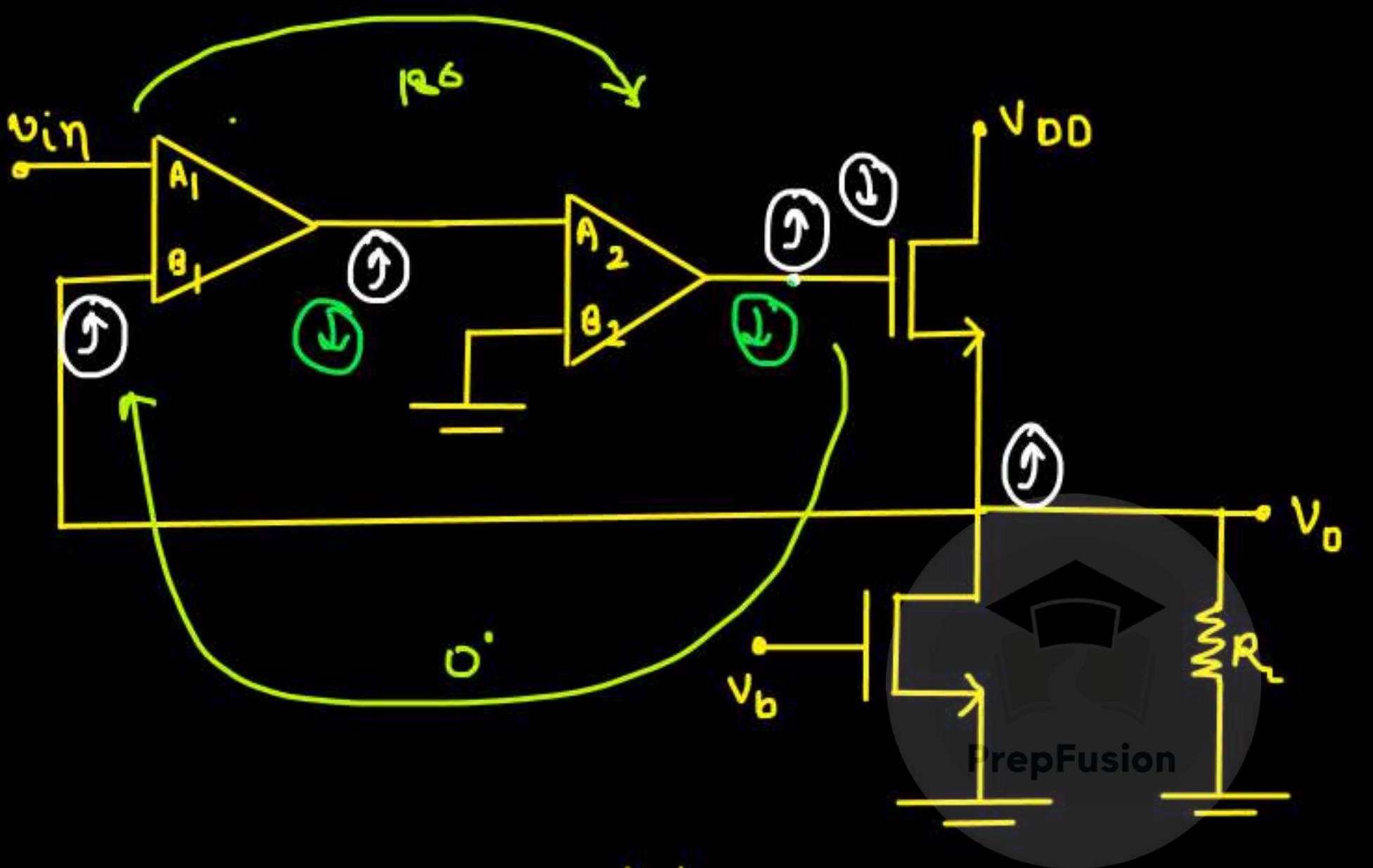


(b)

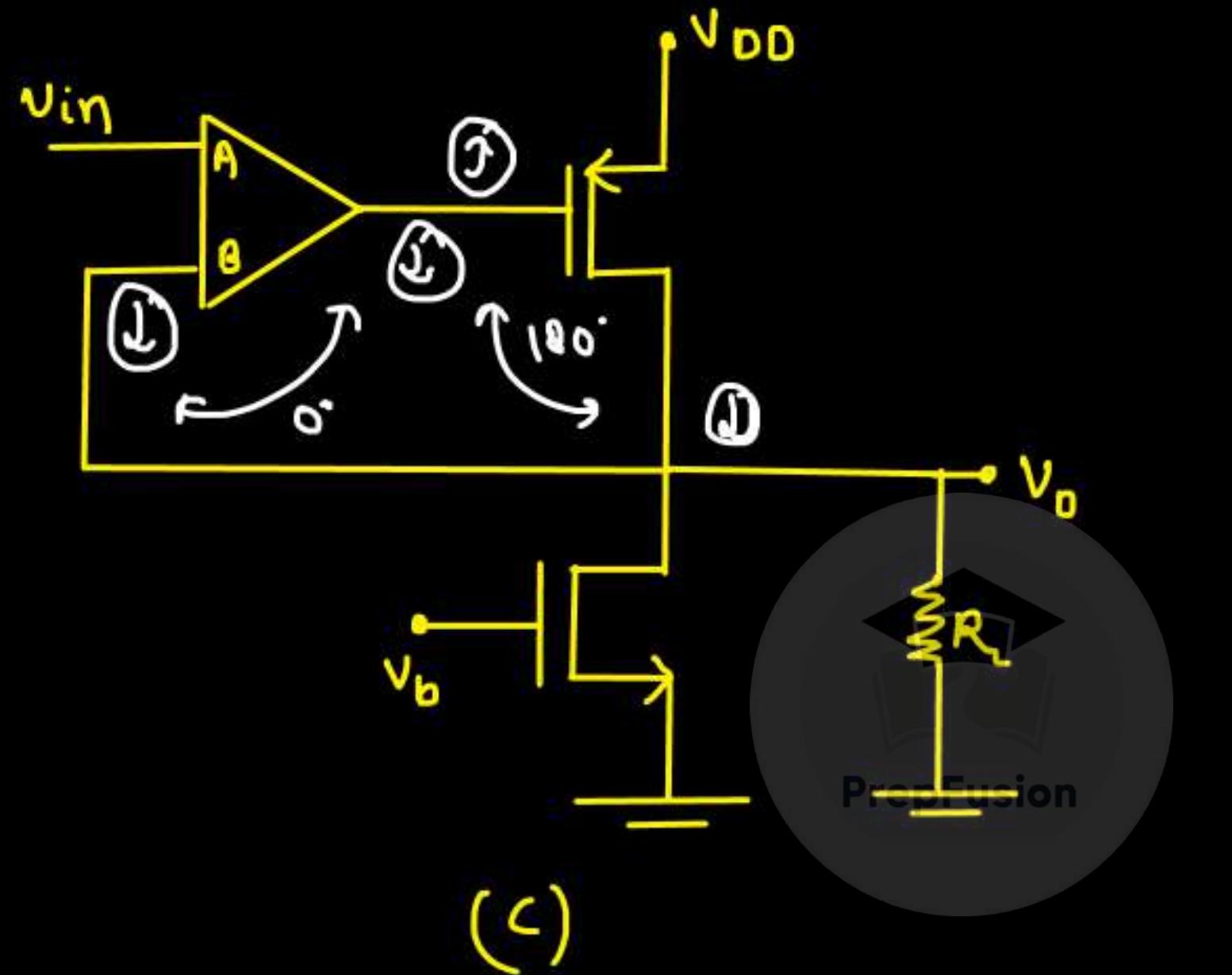- ① if $A_1 = -ve$, $B_1 = +ve \Rightarrow A_2 = -ve, B_2 = +ve$
- ② if $A_1 = +ve, B_1 = -ve \Rightarrow A_2 = +ve, B_2 = -ve$





$B = +ve$

$A = -ve$

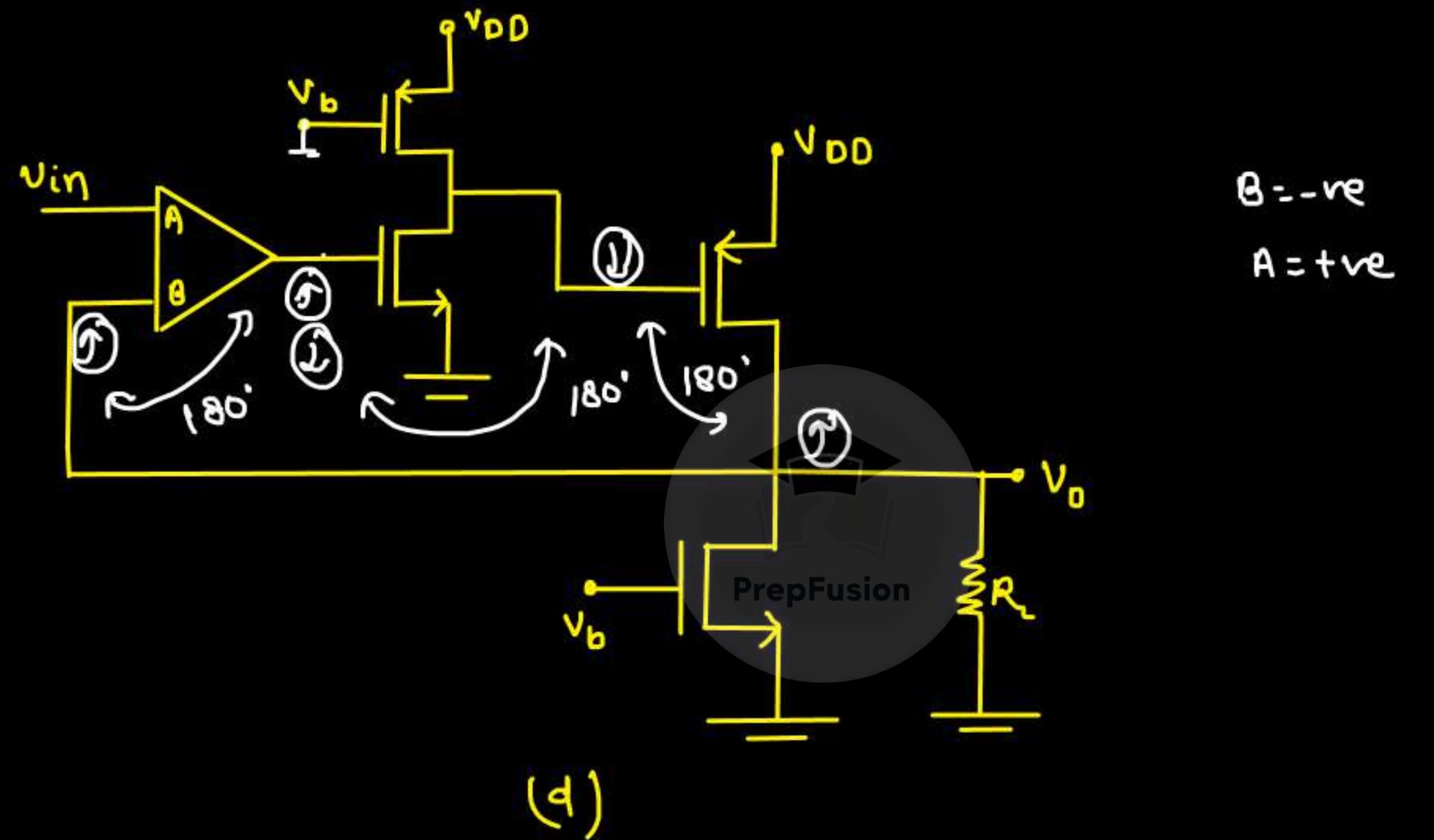

Introduction to Op-Amp:-

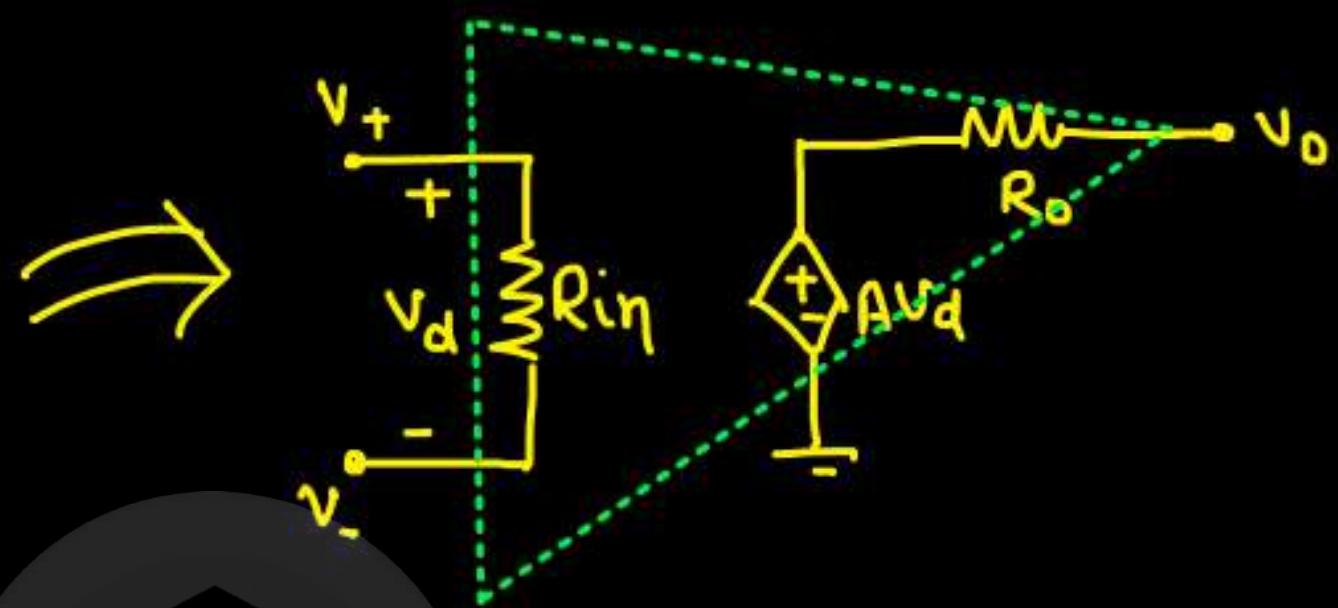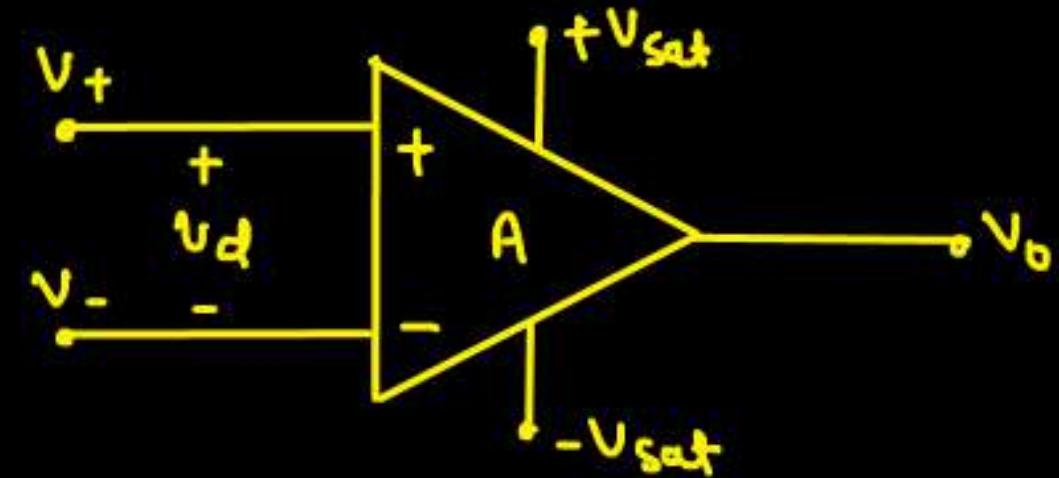

$$V_o = A V_d$$

$$V_o = A (V_+ - V_-)$$

$V_+ \uparrow \Rightarrow V_o \uparrow$

$V_- \uparrow \Rightarrow V_o \downarrow$

$V_- \rightarrow$ Inverting

$V_+ \rightarrow$ Non-Inverting

PrepFusion

$R_{in} \rightarrow$ High

$A \rightarrow$ High

$R_o \rightarrow$ Low

N.B. - O/P of an op-amp can't keep on increasing or decreasing. It will saturate @ some point.

Q. Let $\pm V_{sat} = \pm 5V$

Gain of op-Amp (A) = $10^3 V/V$

Find output voltage for the given differential voltage (V_d)?

where $V_d = V_+ - V_-$

(a) $V_d = 2mV$

$$V_o = AV_d \\ = 10^3 \times 2m$$

$V_o = 2V$

 ✘

(c) $V_d = -3mV$

$$V_o = AV_d \\ = 10^3 \times (-3)m$$

$V_o = -3V$

 ✘

(b) $V_d = 5mV$

$$V_o = AV_d \\ = 10^3 \times 5m$$

$V_o = 5V$

 ✘

(d) $V_d = -5mV$

$$V_o = AV_d \\ = 10^3 \times (-5m)$$

$V_o = -5V$

 ✘

$$(e) v_d = 7mV$$

$$v_o = Av_d$$

$$= 10^3 \times 7m$$

$$= 7V \times$$

$$v_o = 5V$$

$$(f) v_d = -8mV$$


$$v_o = Av_d$$

$$= 10^3 \times (-8m)$$

$$v_o = -8V$$

$$v_o = -8V$$

Transfer characteristics :-

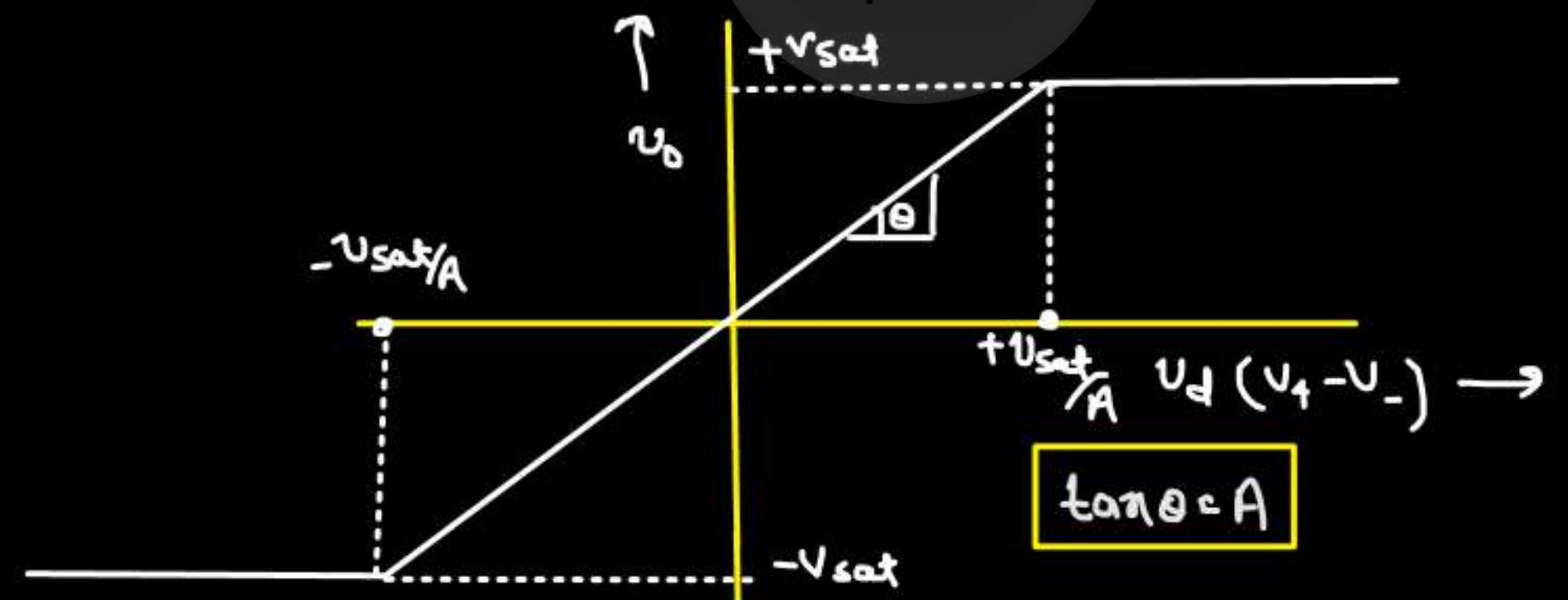

$$-V_{sat} \leq v_o \leq V_{sat}$$



For ideal op-amp:

$$A = \infty$$

$$R_{in} = \infty$$

$$R_o = 0$$

$$I_i = 0 \text{ Amp}$$

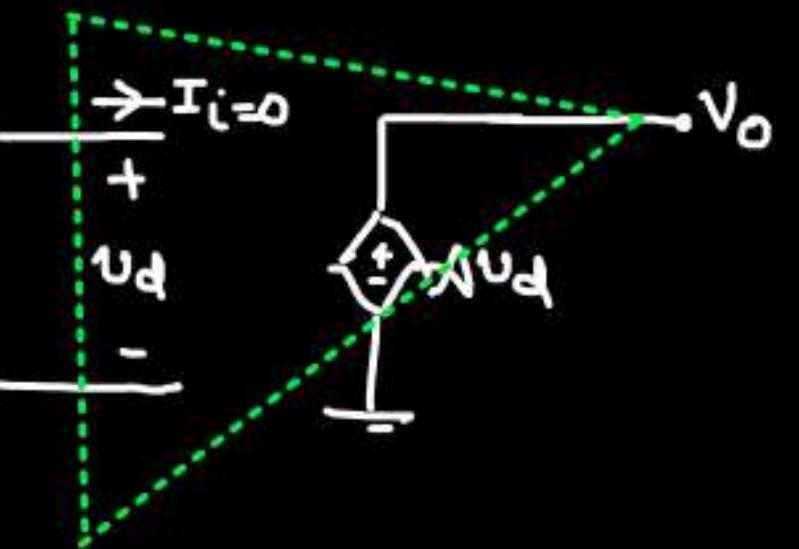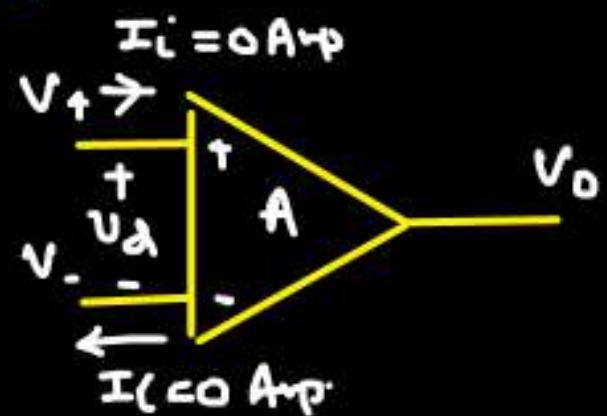

Q. Let gain of op-amp $A = \infty$, $\pm V_{sat} = \pm 5V$

Find V_0 for following differential voltage (V_d)?

$$V_d = V_+ - V_-$$

PrepFusion

(a) $V_d = 3mV$

$$\begin{aligned} V_0 &= AV_d \\ &= \infty \times 3mV \\ &= \infty \times \end{aligned}$$

V0 = +5V

(b) $V_d = -2mV$

$$\begin{aligned} V_0 &= AV_d \\ &= \infty (-2mV) \\ &= -\infty \times \end{aligned}$$

V0 = -5V

(c) $V_d = 7mV$

$$\begin{aligned} V_0 &= AV_d \\ &= \infty (7mV) \\ &= \infty \times \end{aligned}$$

V0 = +5V


(d) $V_d = -6mV$

$$\begin{aligned} V_0 &= \infty \times (-6) \\ &= -\infty \times \end{aligned}$$


V0 = -5V

Ideal characteristics of MOS:-

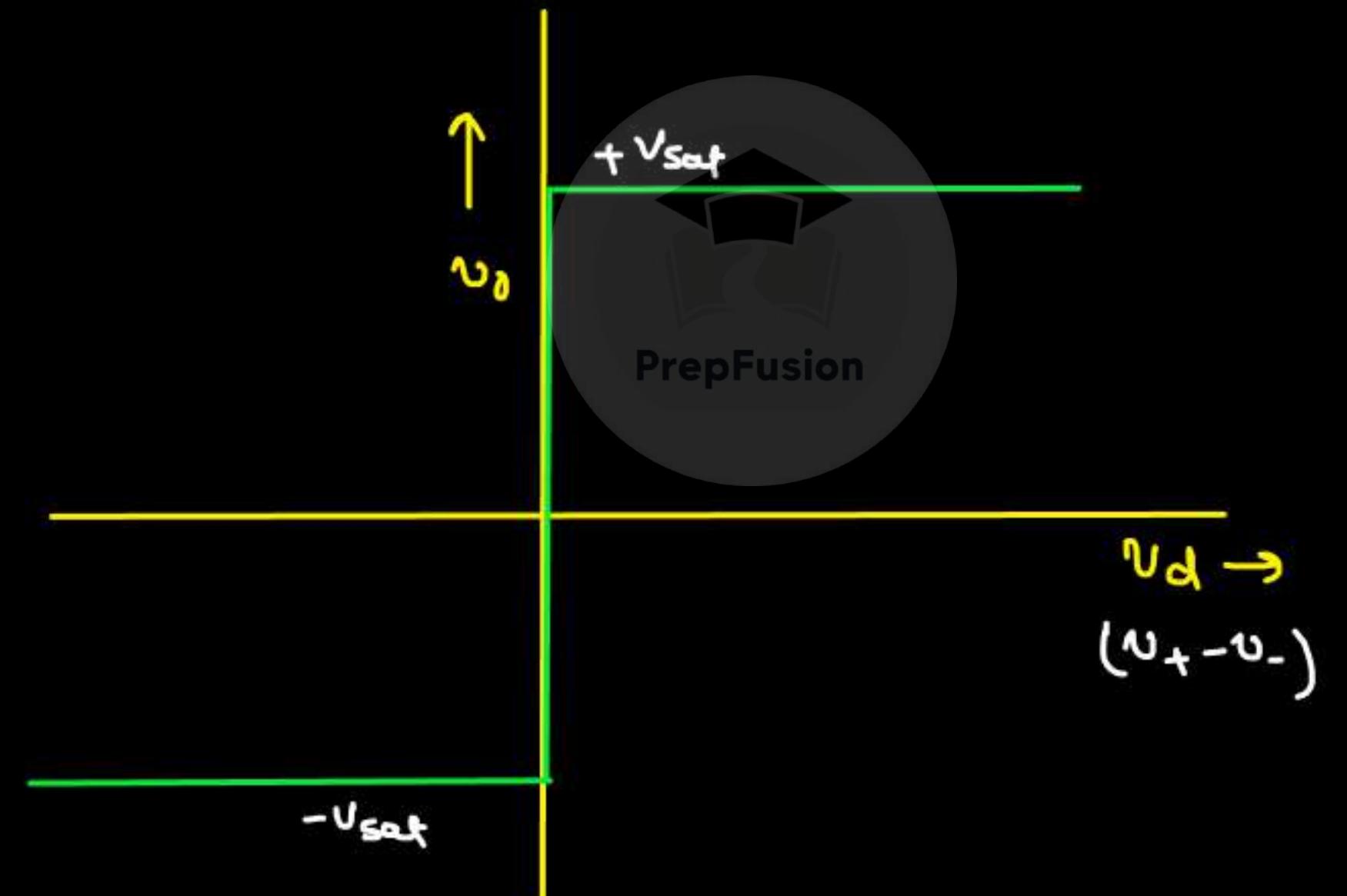
- (i) if $v_d > 0 \Rightarrow v_+ > v_- \Rightarrow v_o = +v_{sat}$
- (ii) if $v_d < 0 \Rightarrow v_+ < v_- \Rightarrow v_o = -v_{sat}$



* OP-Amp as a Comparator :-

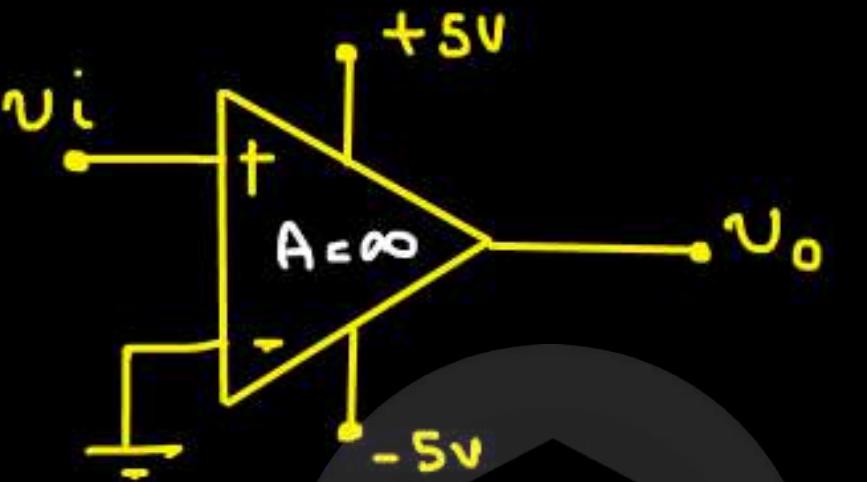

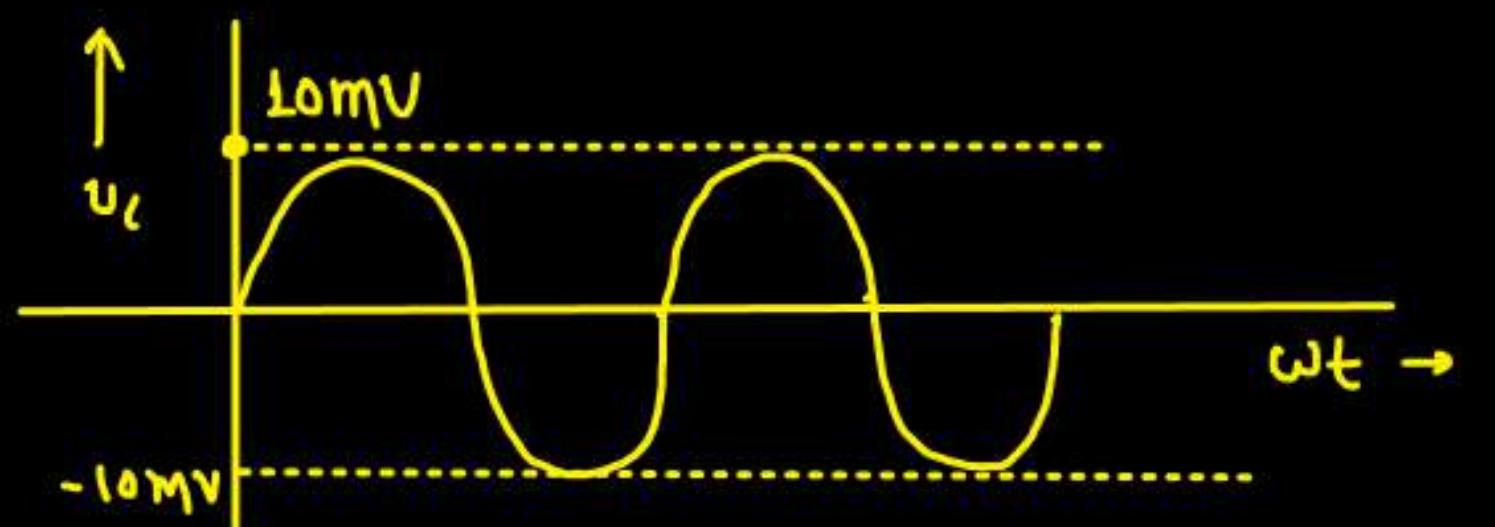Given op-amp is ideal.
PrepFusion
Find V_0 for the given input V_i




\Rightarrow if $V_+ > V_- \Rightarrow V_0 = +V_{sat}$


$\hookrightarrow V_i > 0 \Rightarrow V_0 = +V_{sat}$

\Rightarrow if $V_+ < V_- \Rightarrow V_0 = -V_{sat}$

$V_i < 0 \Rightarrow V_0 = -V_{sat}$

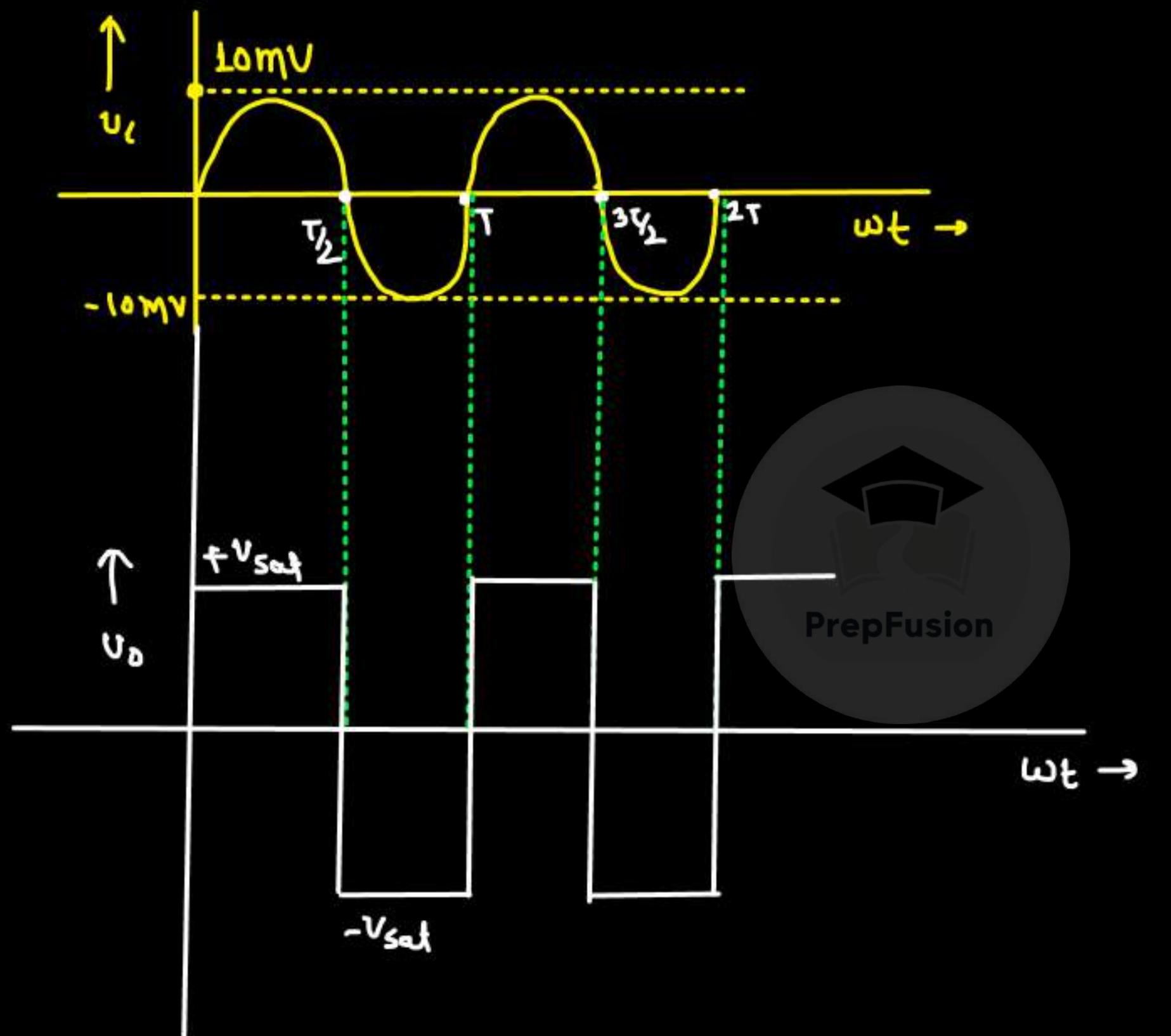


Q.

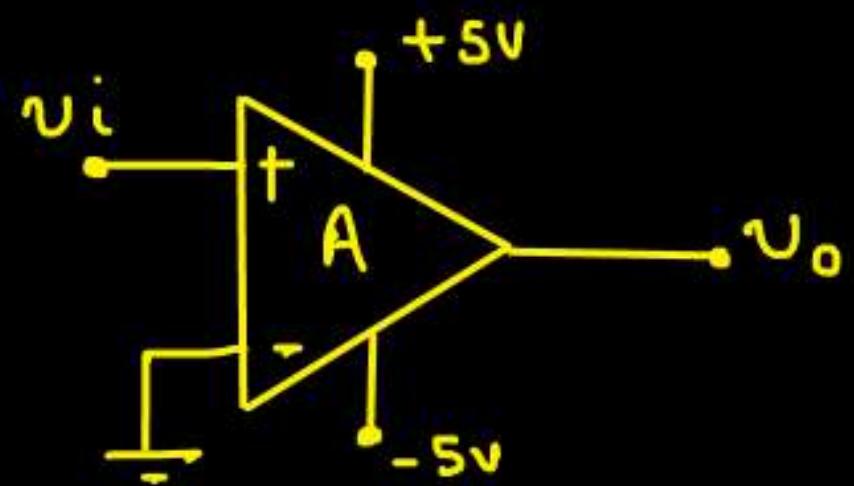

Given OP-Amp has a gain $A = 10^3 \text{ V/V}$

Find u_o for the given i/p u_i

PrepFusion

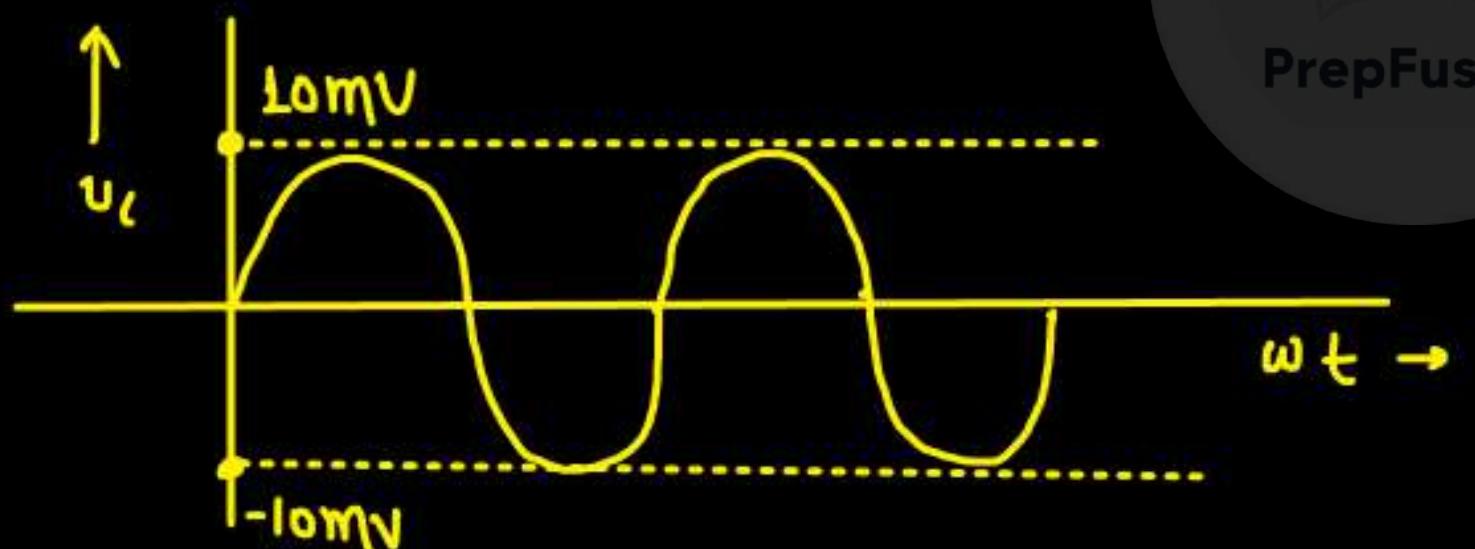


$$u_o = Au_d$$

$$u_o = 10^3(u_i - 0)$$


$$u_o = 10^3 u_i$$

* * *


$$+5V < u_o < -5V$$

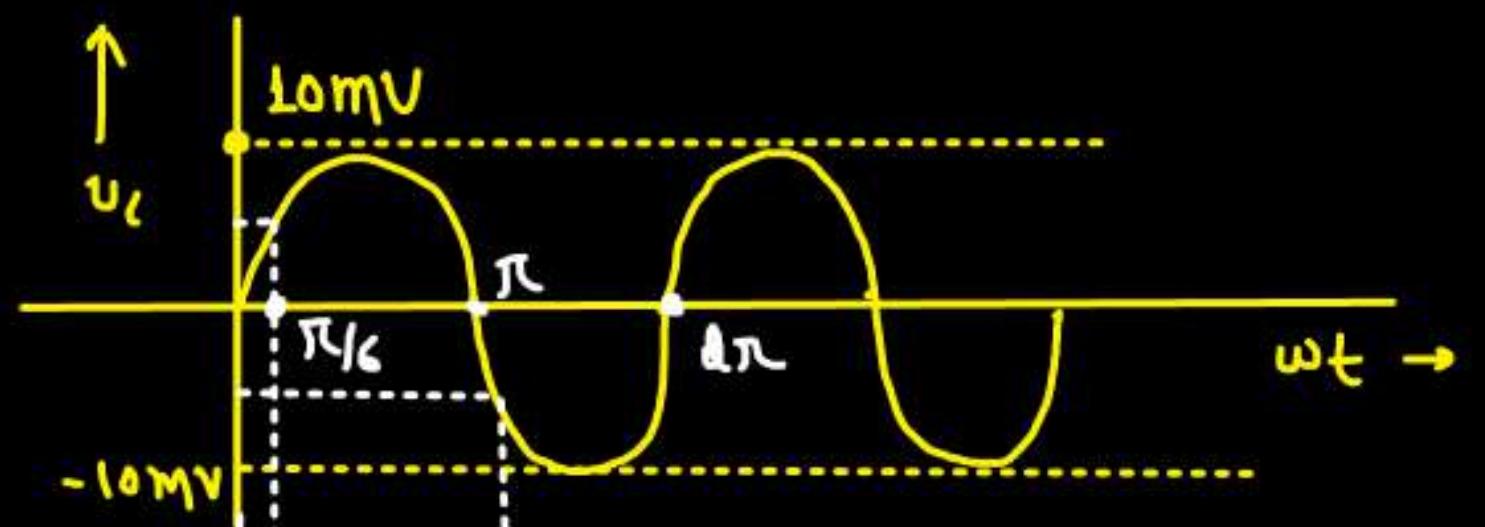
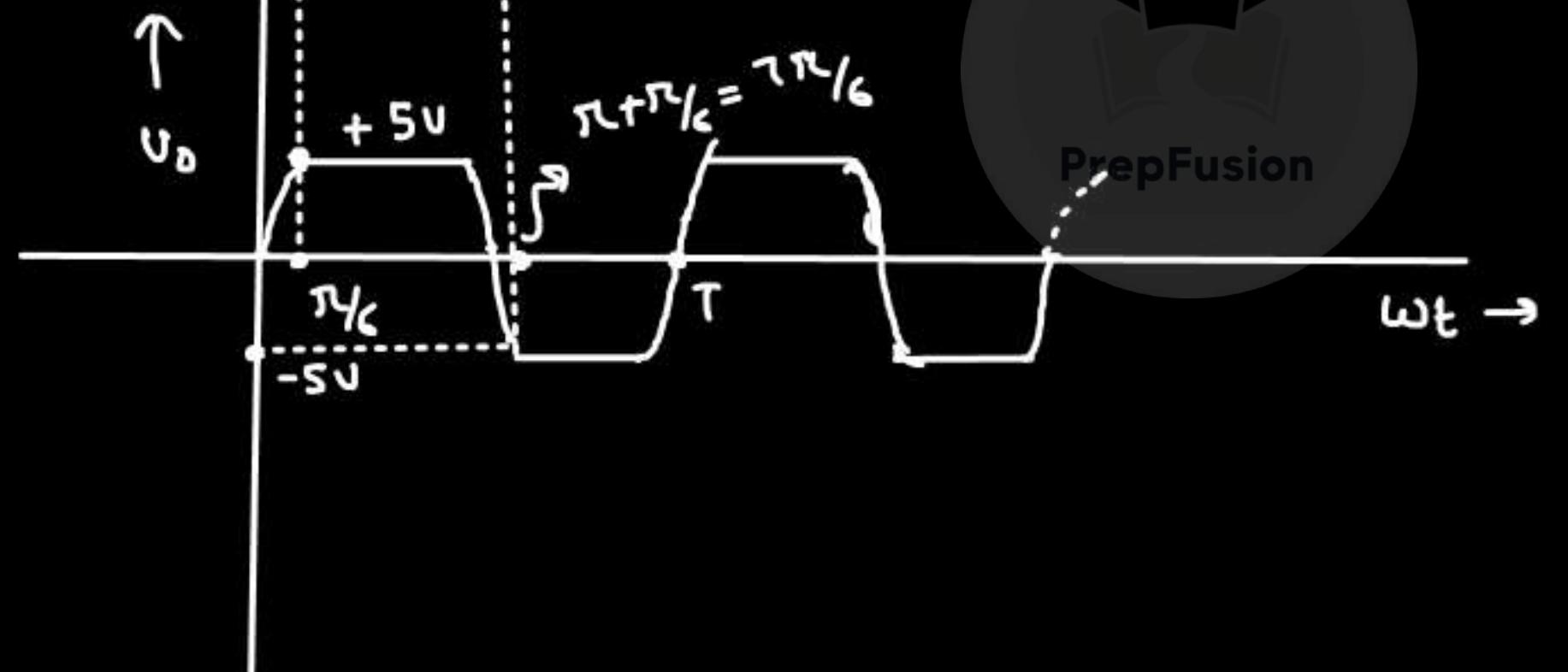
$$\begin{aligned}
 & 10\text{mV} \sin \omega t \\
 &= 10\text{mV} \times \sin\left(\frac{\pi}{6}\right) \\
 &= 5\text{mV}
 \end{aligned}$$



Q.

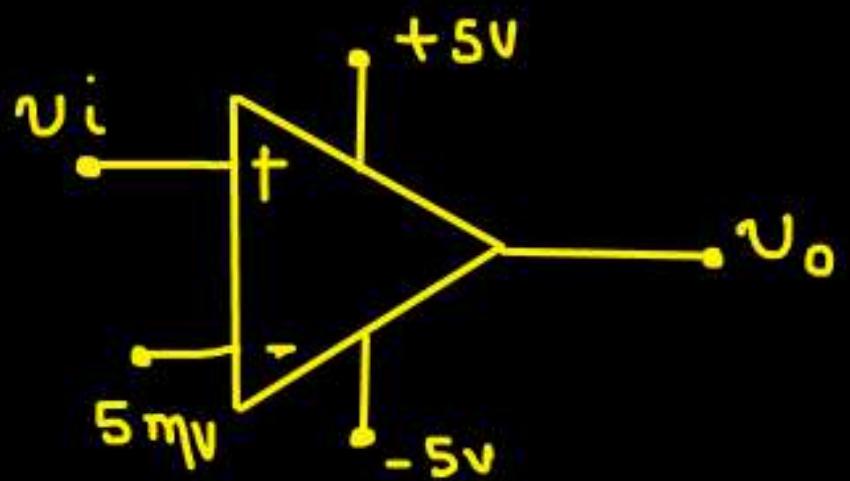

Given op-Amp is ideal.


Find U_o for the given i/p U_i




⇒

$$U_i > 5mV \Rightarrow U_o = +U_{sat}$$

$$U_i < 5mV \Rightarrow U_o = -U_{sat}$$

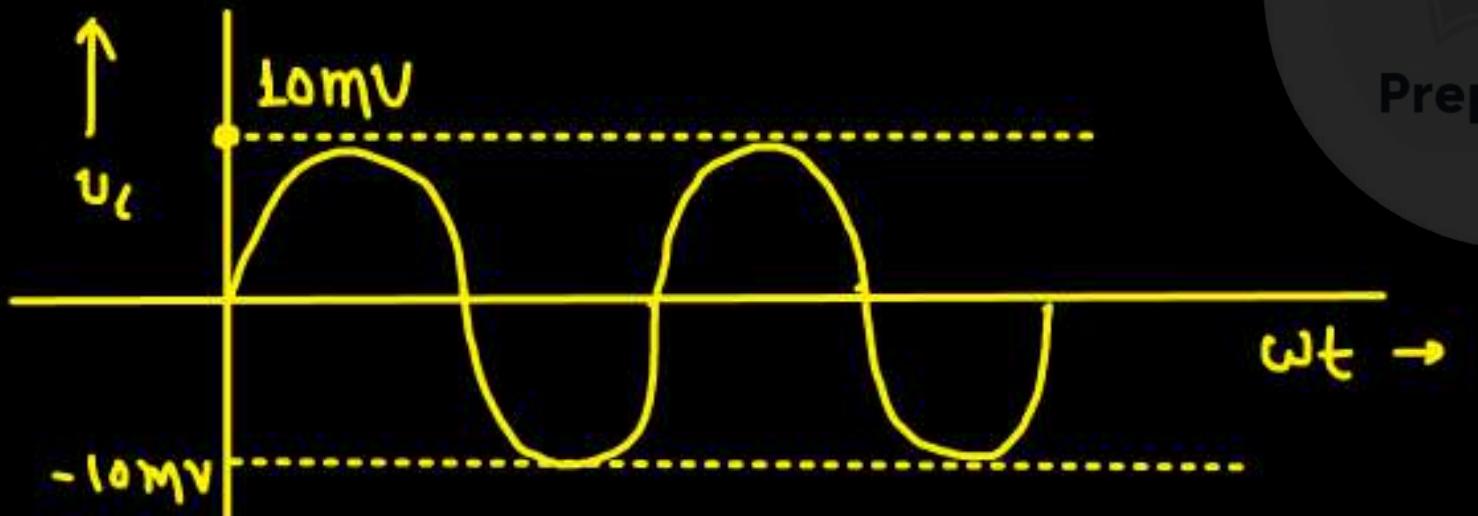

Find the avg. value of o/p ?

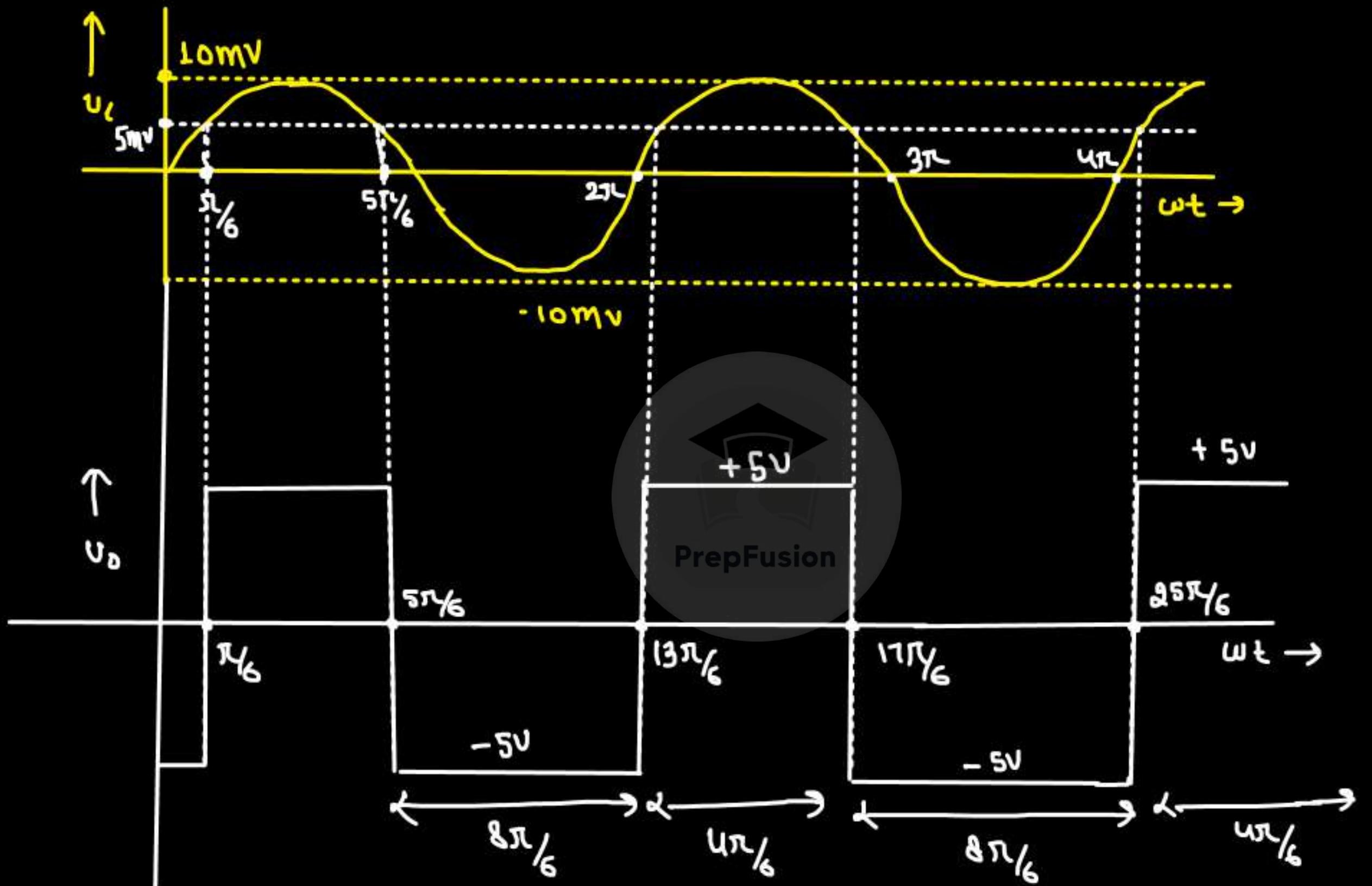



$$(\text{Average})_{\text{O/p}} = \frac{\text{Area of a Time period}}{\text{Time period}}$$

$$= \frac{-5 \times \frac{8\pi}{6} + 5 \times \frac{4\pi}{6}}{2\pi}$$


$(\text{Average})_{\text{O/p}} = -1.67 \text{ V}$

Revision:-


Q. Graph of $y=x$ is given. Plot $y=x-2$

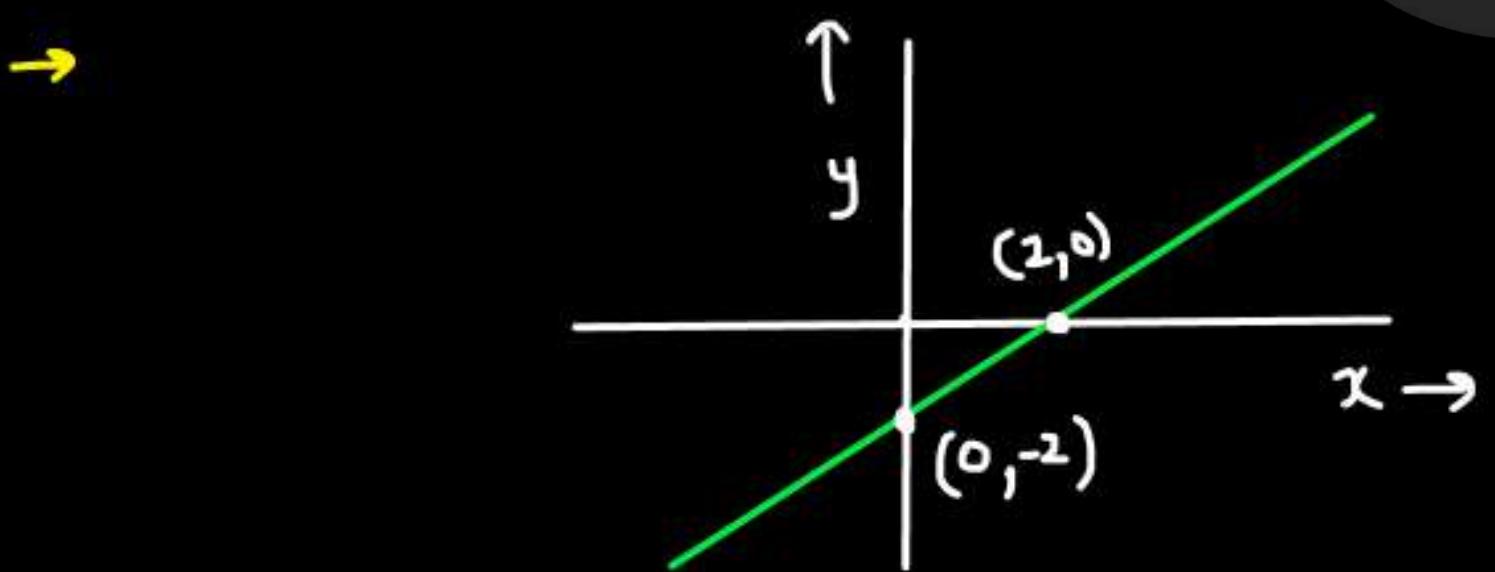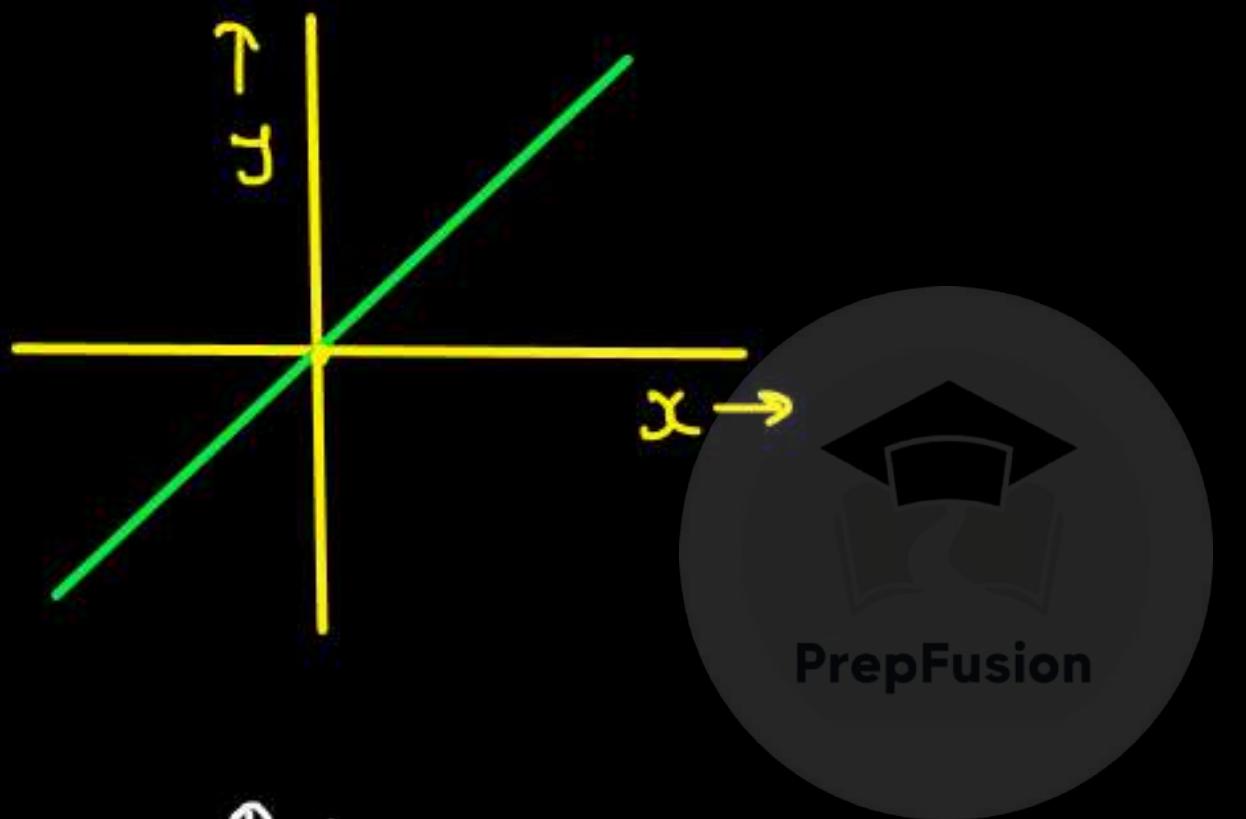

Q.

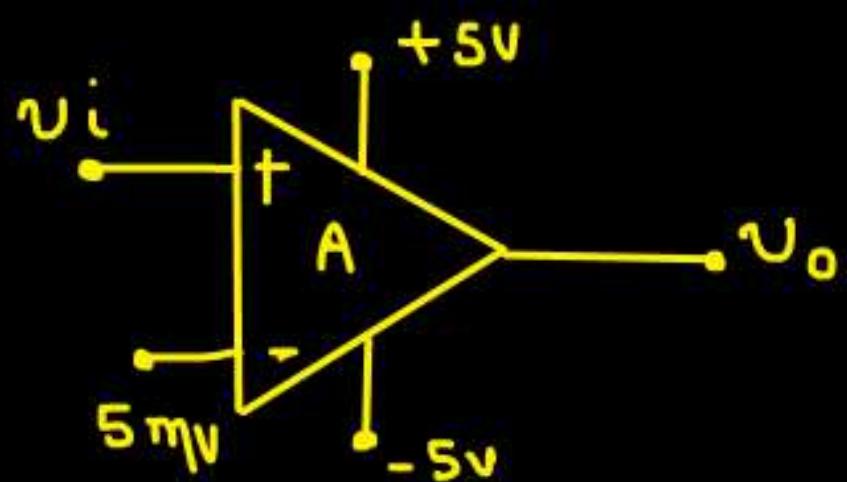

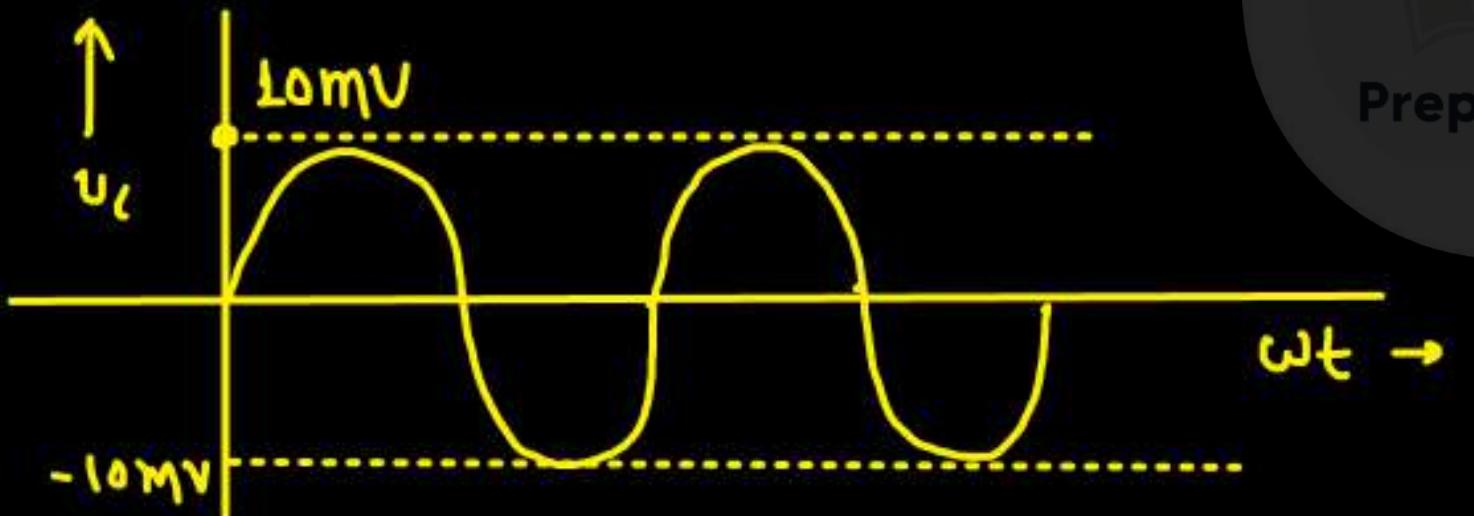Given op-amp is having $A = 10^3 \text{ V/V}$
Find v_o for the given i/p v_i




PrepFusion

$$v_o = 10^3 (v_i - 5mV)$$

※

$$-5V \leq v_o \leq +5V$$

$$v_i = 10mV \sin \omega t$$

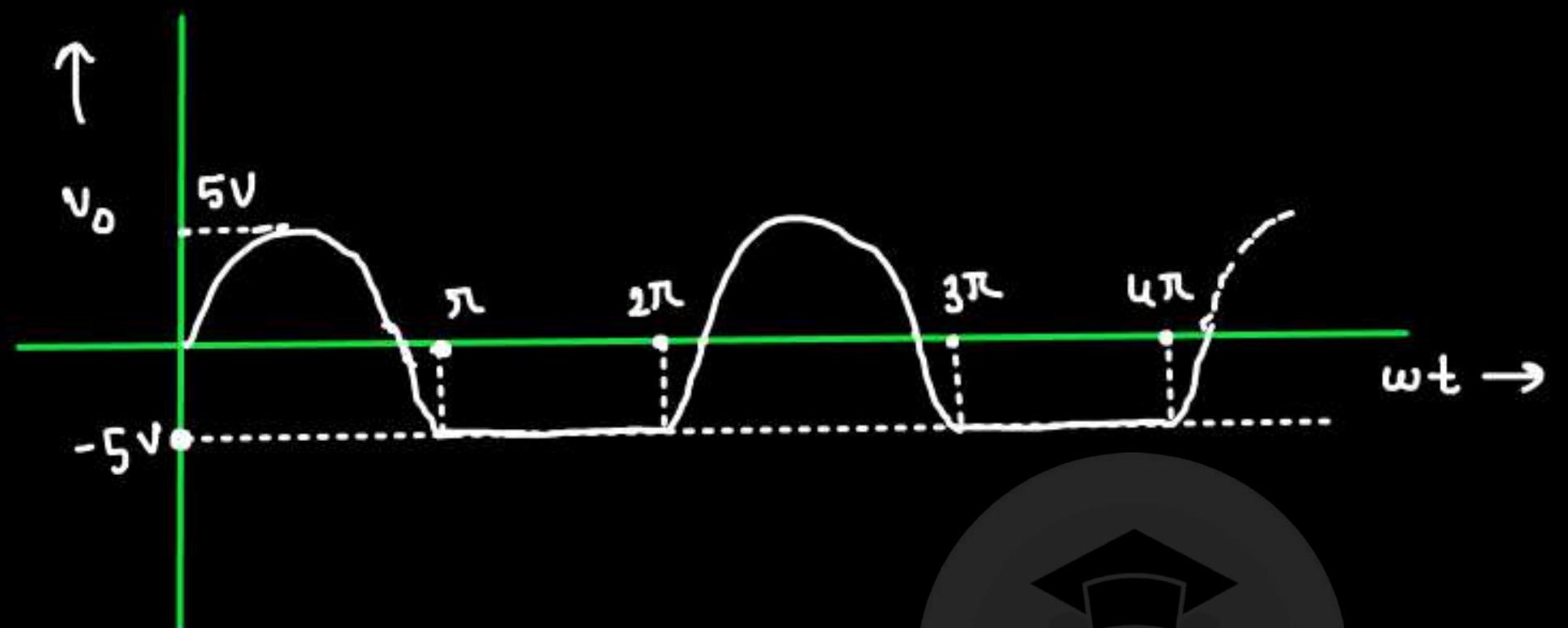

$$V_o = 10^3 (U_i - 5mV)$$

$$-5 = 10^3 (10mV \sin \omega t - 5mV)$$


$$-5 = 10 \sin \omega t - 5$$

$$10 \sin \omega t = 0$$


$$\omega t = \pi, 2\pi, 3\pi, 4\pi$$

⇒ Basics of feedback :- Considering α and β to be positive

① Negative feedback:-

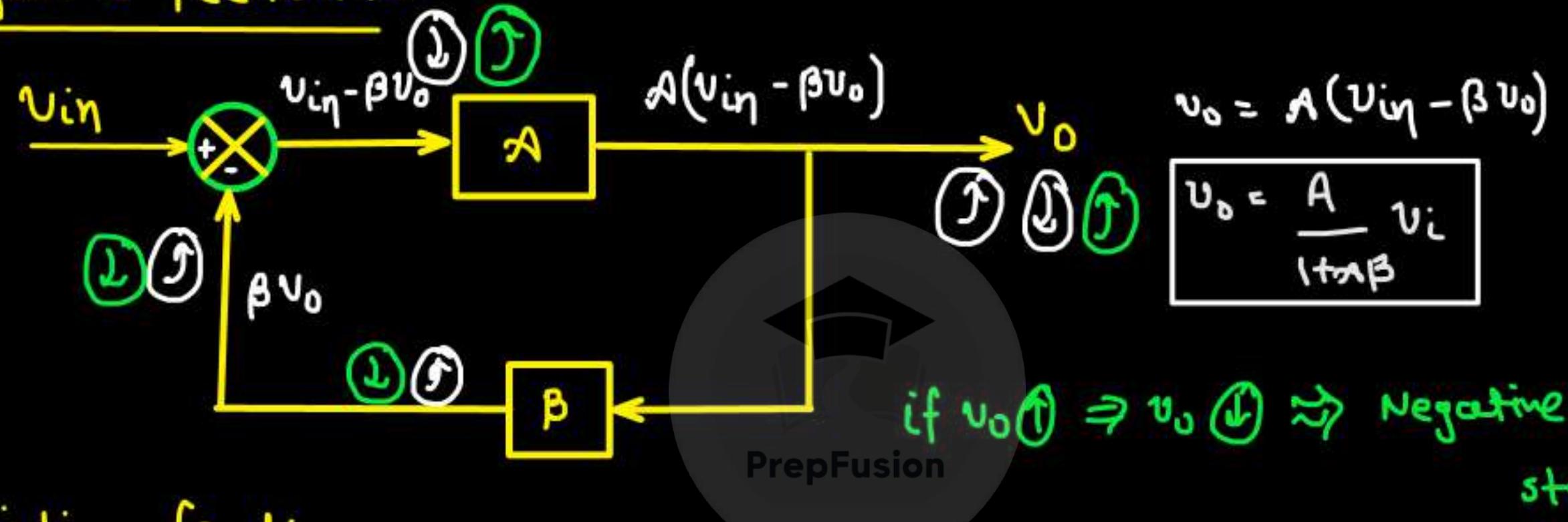


② Positive feedback:-

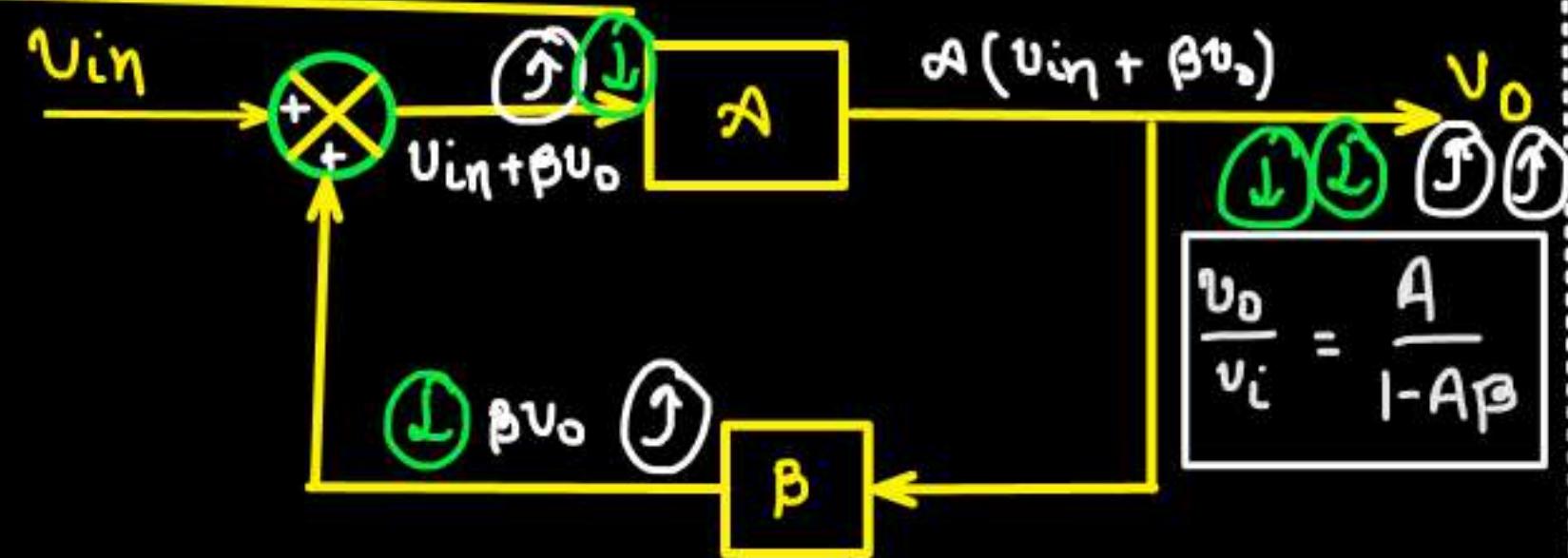

if $v_o \uparrow \Rightarrow v_o \downarrow$
OR
 $v_o \downarrow \Rightarrow v_o \uparrow$ ⇒ positive fb
s/s is unstable

⇒ Concept of Virtual Short:-

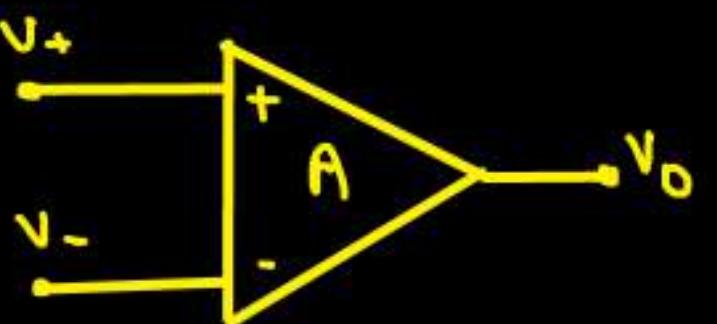


$$V_o = A (V_+ - V_-)$$

if $A = \infty$

$$\frac{V_o}{A} = V_+ - V_-$$

$$V_+ - V_- = \frac{V_o}{\infty}$$

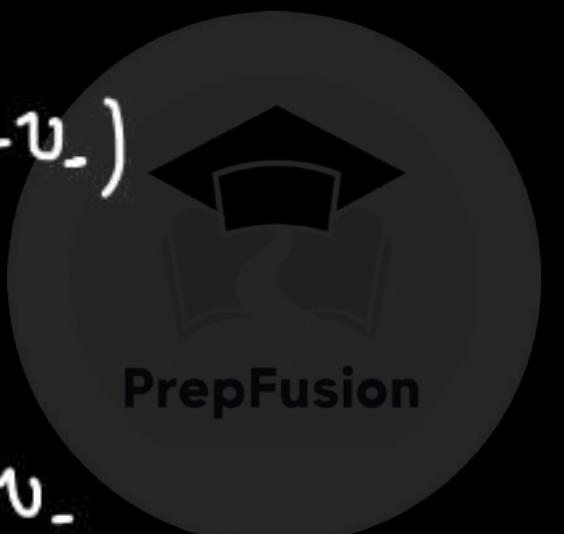

For positive f/b, V_o = unstable

for negative f/b , $v_o = \text{stable}$

$$v_+ - v_- = \frac{v_o}{\beta} \rightarrow \text{stable}$$

$$v_+ - v_- = 0$$

$$v_+ = v_-$$

Concept of virtual short :-

In case of Negative f/b; Inverting terminal (v_-) potential is equal to the potential of Non-inverting terminal (v_+).

$$v_+ = v_-$$

★ Virtual short is not valid when -

- (i) There is a positive feedback.
- (ii) Gain A is finite
- (iii) When o/p is saturated ($\pm V_{sat}$) .




* Different OP-Amp Configurations:

⇒ OP-Amp in Negative feedback:-


① Non-inverting Amplifier :-

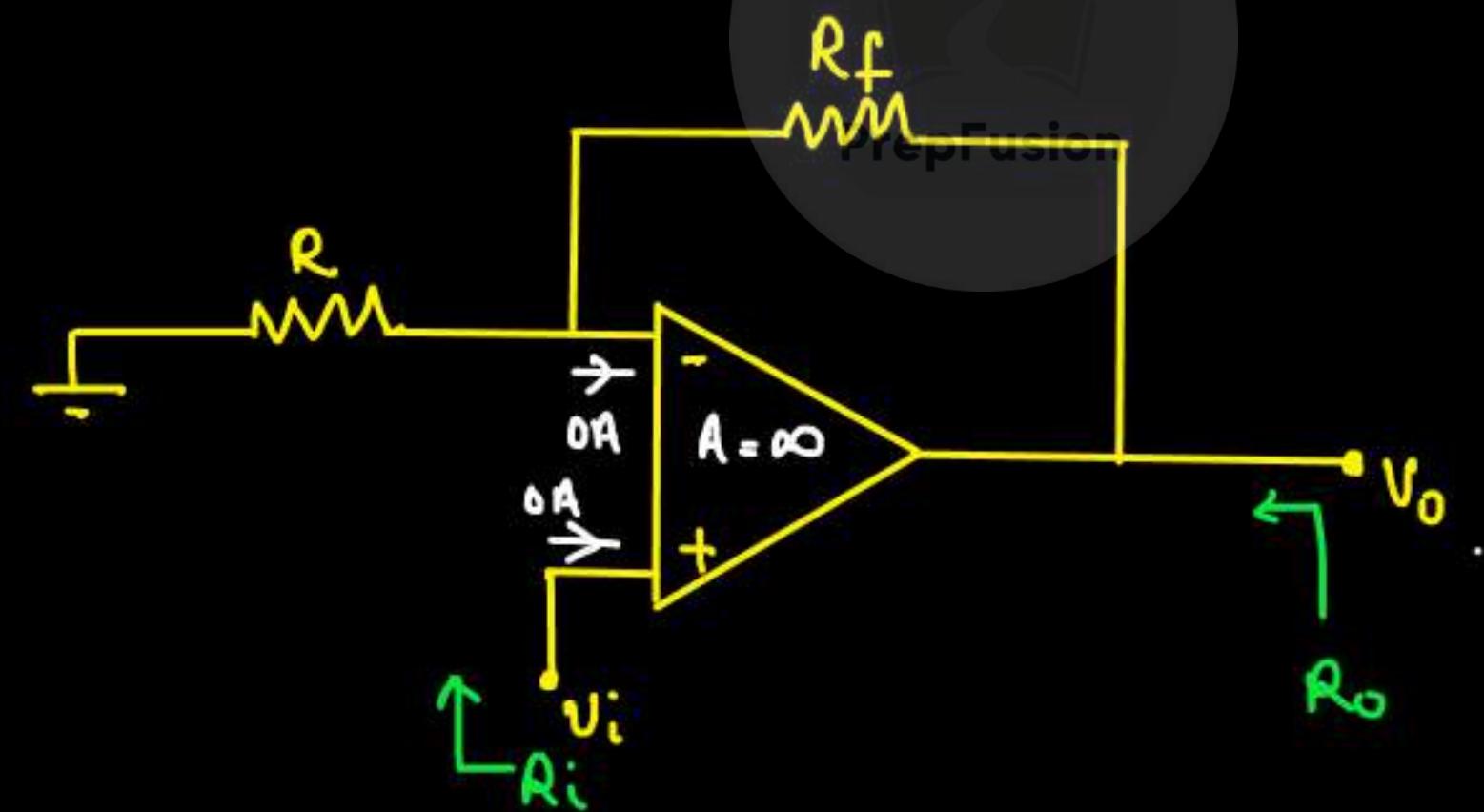↳ i/p is connected to non-inverting (v_+) terminal.



Considering ideal
OP-Amp

(a) Voltage gain ::

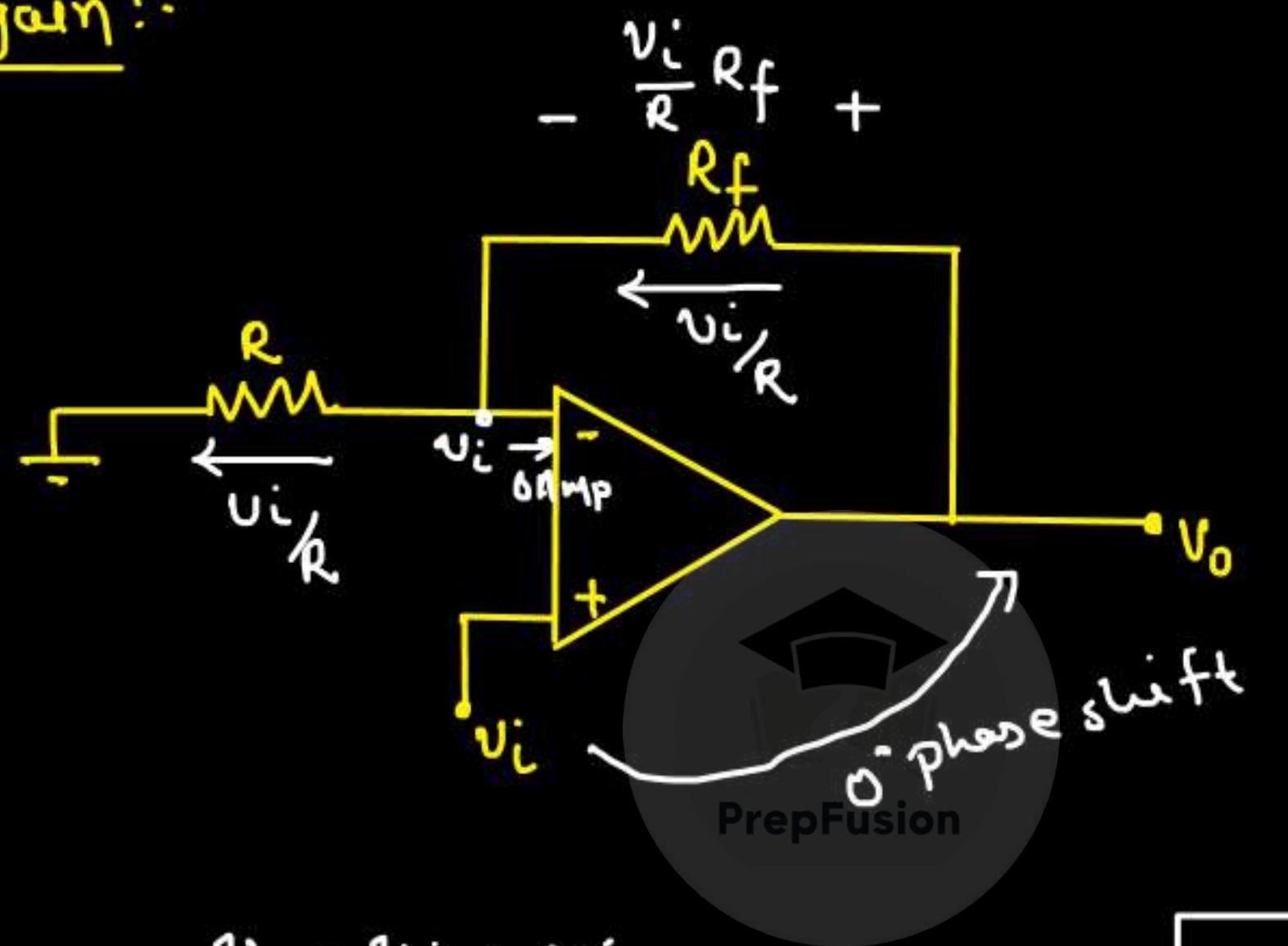

$$V_o = V_i + \frac{V_i}{R} R_f$$


$$V_o = \left[1 + \frac{R_f}{R} \right] V_i$$

$$\Rightarrow \frac{V_o}{V_i} = 1 + \frac{R_f}{R}$$

Gain of Non inverting amplifier

R_i

(b) Input Resistance :-

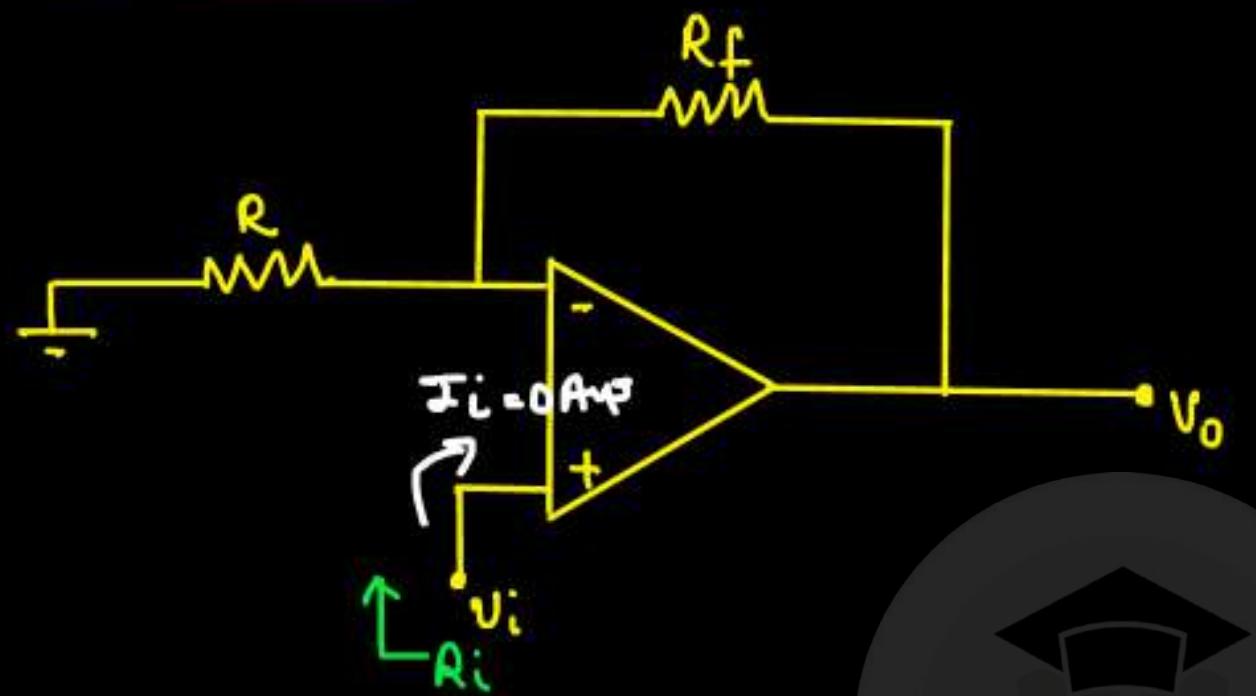


$$R_i = \frac{V_i}{I_i} = \frac{V_i}{0}$$

$$R_i = \infty$$




(c) Output Resistance :-

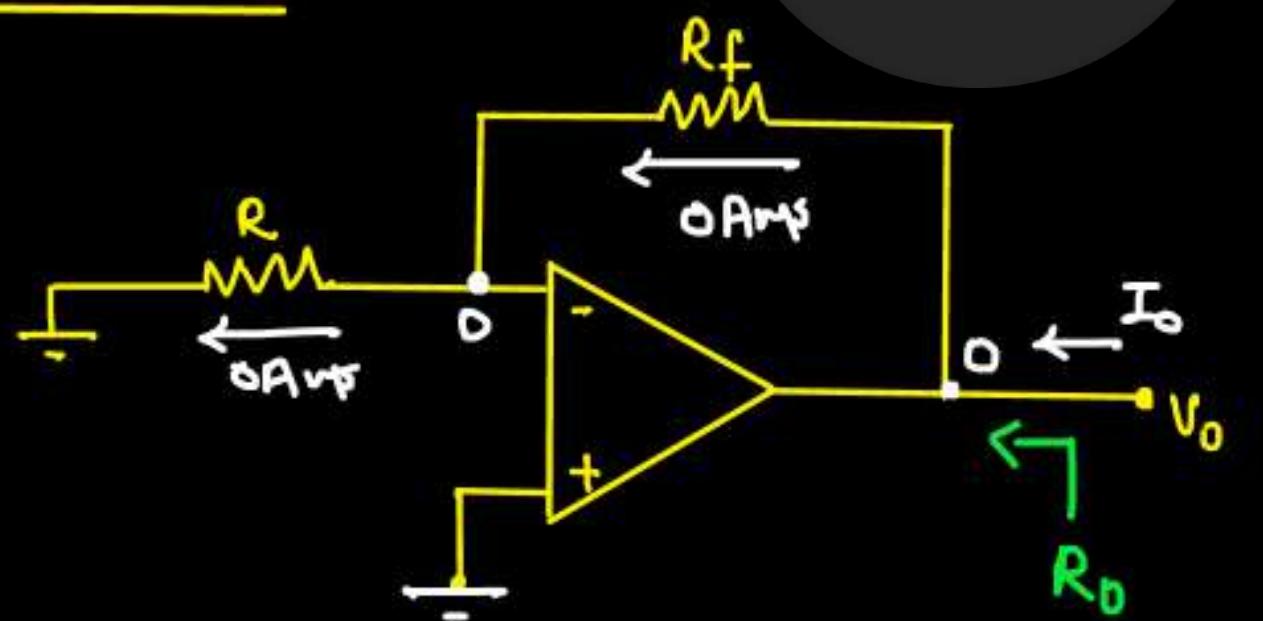


$$R_o = \frac{V_o}{I_o} = \frac{0}{I_o}$$

$$R_o = 0$$

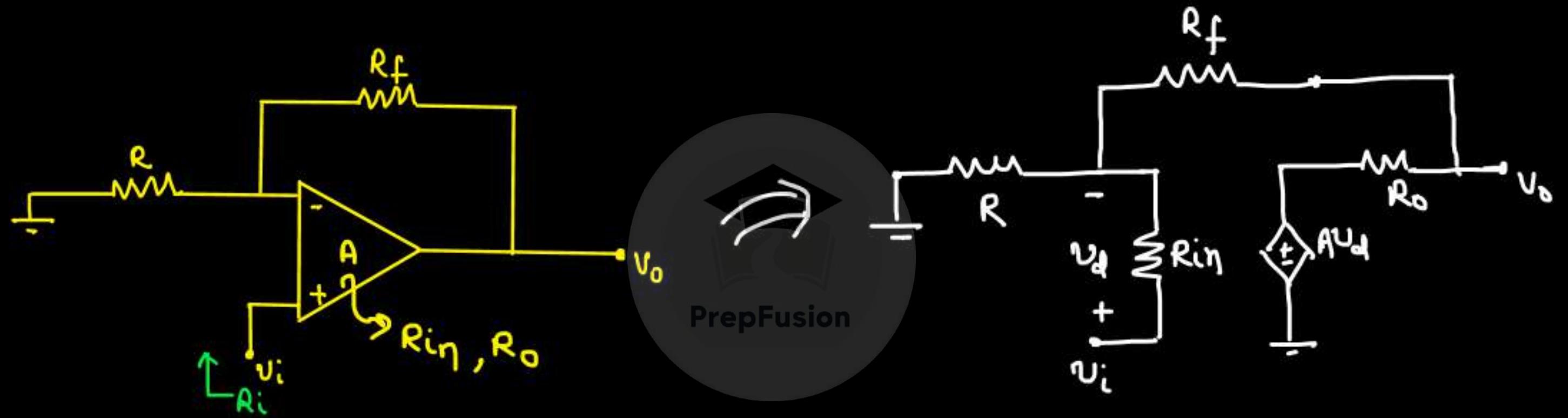★ Non-inverting Amplifier considering Non-ideal OP-Amp [R_{in} , A , R_o]



(a) Voltage gain :-

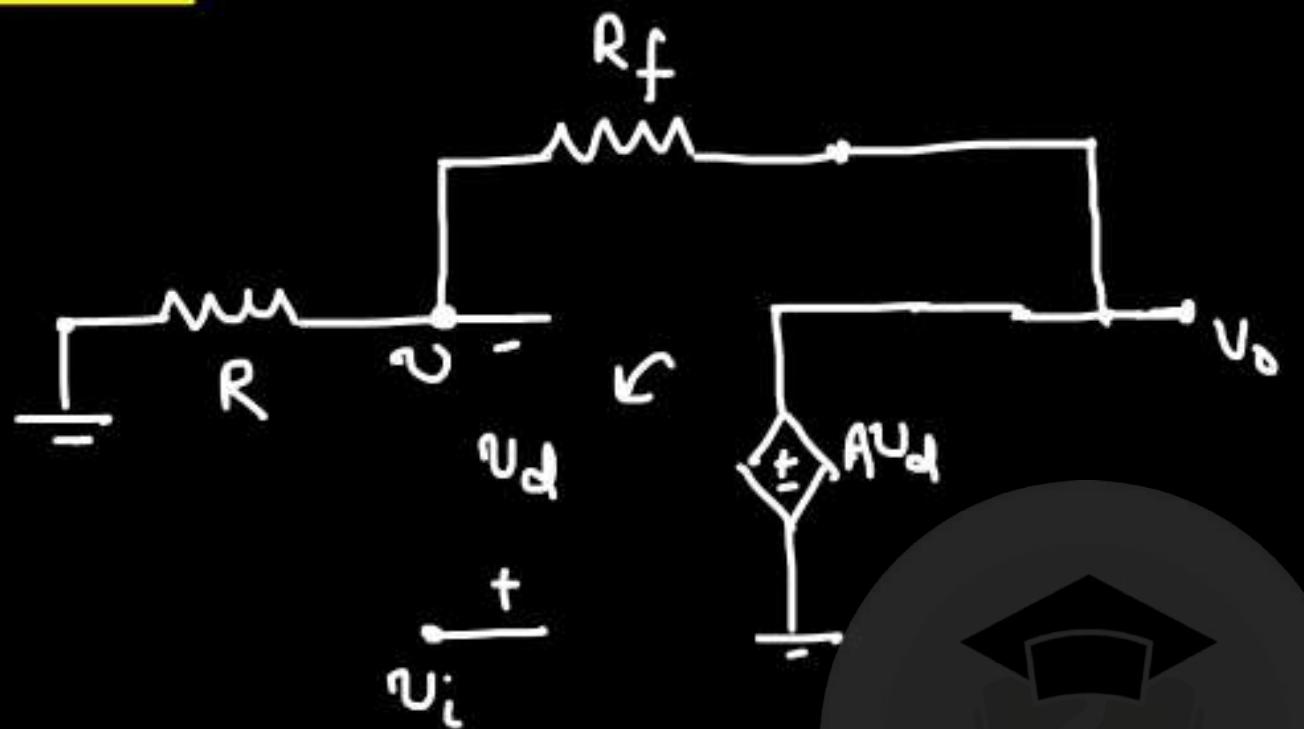

For opamp →

$R_{in} \rightarrow \text{High}$

$R_o \rightarrow 0$


So, assuming $R_{in} \rightarrow \infty$, $R_o \rightarrow 0$

$$V_o = AU_d$$

$$V_o = A [U_i - U] \quad \textcircled{1}$$

$$U = \frac{V_o \times R}{R + R_f}$$
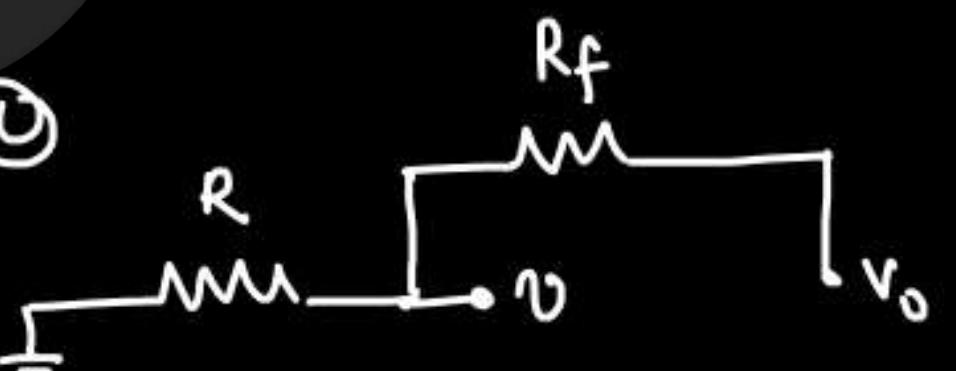
$$U = \beta V_o \quad \textcircled{2} \quad \text{where } \beta = \frac{R}{R + R_f}$$



By eqn ① and ②

$$v_o = A [v_i - \beta v_o]$$

$$v_o [1 + \alpha \beta] = A v_i$$

*
$$\frac{v_o}{v_i} = \frac{A}{1 + \alpha \beta}$$


where $\beta = \frac{R}{R + R_f}$

if A is very large (∞)

$$\frac{v_o}{v_i} = \frac{A}{\alpha \beta} = \frac{1}{\beta} = \frac{R + R_f}{R} = 1 + \frac{R_f}{R}$$

$$\frac{v_o}{v_i} = 1 + \frac{R_f}{R}$$

(b) Input Resistance :-

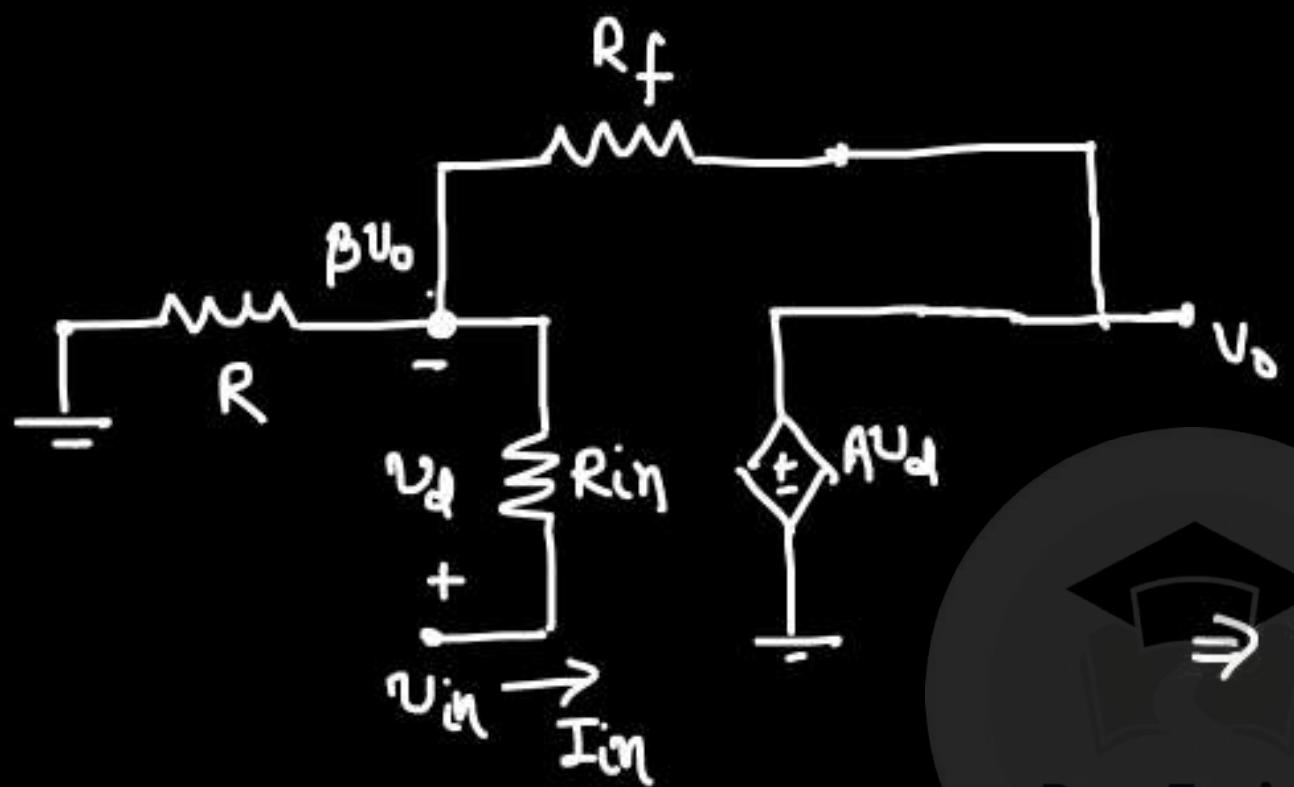

$$(R_{in})_f = \frac{U_i}{I_i}$$

$$\beta = \frac{R}{R + R_f}$$

PrepFusion

$$\Rightarrow \frac{U_{in} - \beta U_o}{R_{in}} = I_{in}$$

$$U_{in} - \beta U_o = I_{in} R_{in}$$

$$U_{in} - \beta \left(\frac{A}{1 + \alpha \beta} \right) U_{in} = I_{in} R_{in}$$

$$U_{in} \left[1 - \frac{\alpha \beta}{1 + \alpha \beta} \right] = I_{in} R_{in}$$


★

$$\frac{U_{in}}{I_{in}} = (R_{in})_f = R_{in} [1 + \alpha \beta]$$

if $A \rightarrow \text{very large} \rightarrow \infty$

$$(R_{in})_f = \infty$$

(c) Output Impedance (R_o):-

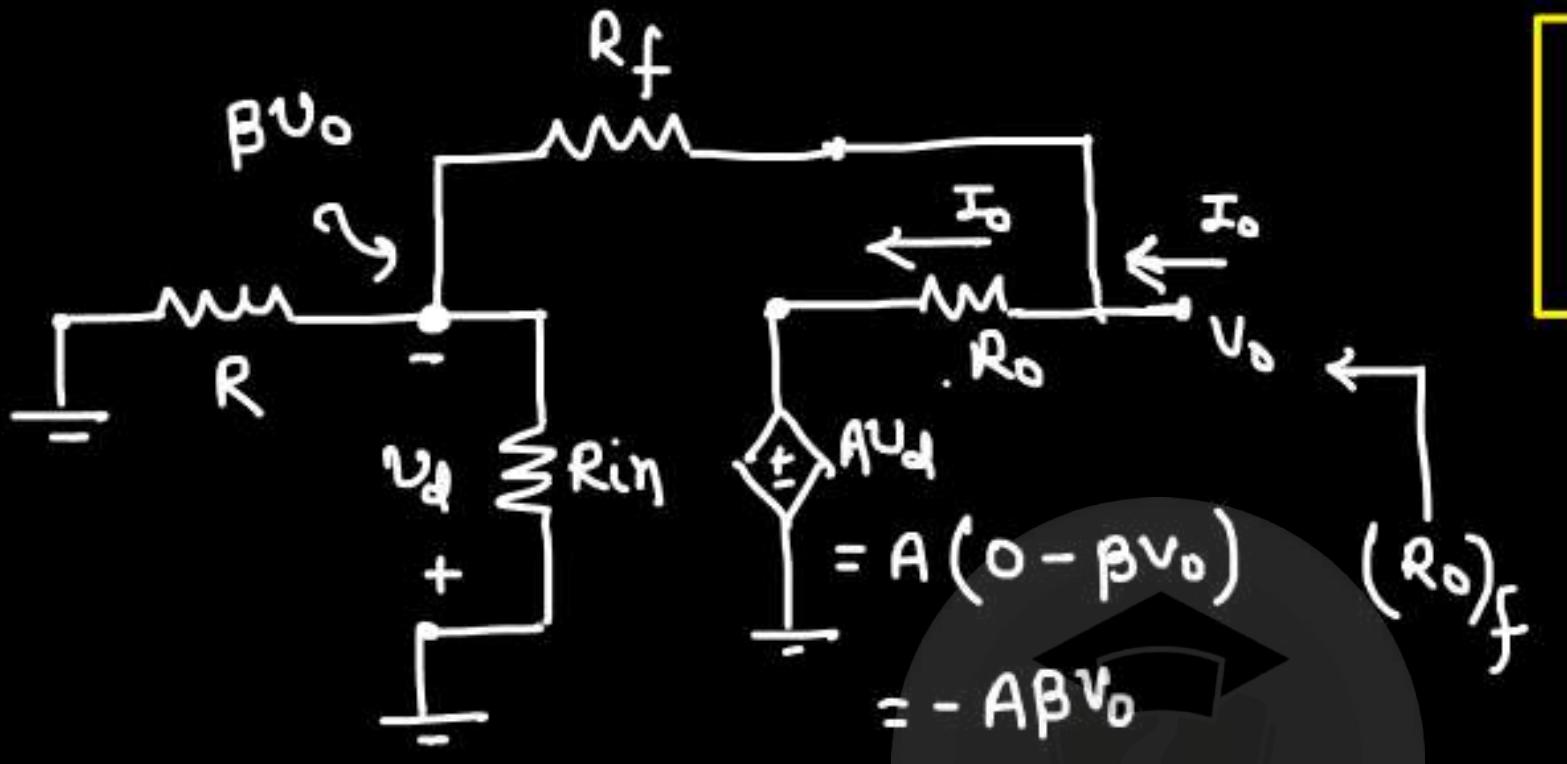

$$(R_o)_f = \frac{v_o}{I_o}$$

PrepFusion

$$\frac{v_o - (-A\beta v_o)}{R_o} = I_o$$


if $A \rightarrow \infty$

$$\frac{v_o}{I_o} = \frac{R_o}{1 + A\beta} = (R_o)_f$$



$$R_o f = 0 \Omega$$

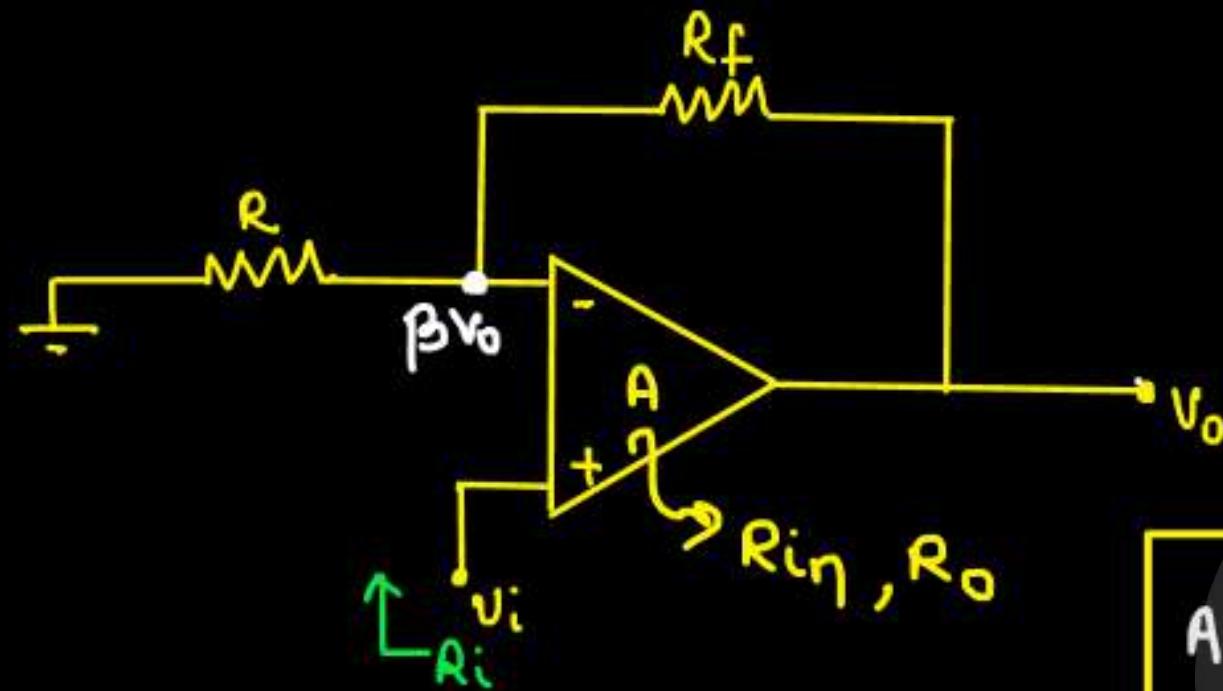* Understanding feedback topology in Non-inv. Amp:-



Voltage mixing
Voltage sampling

⇒ Voltage - voltage fb Topology


⇒ Voltage amplifier

$R_{in} \rightarrow$ High , $R_o \rightarrow$ low

$$\beta = \frac{R}{R+R_f}$$

$$A(V_i - \beta V_o) = V_o$$

PreFusion

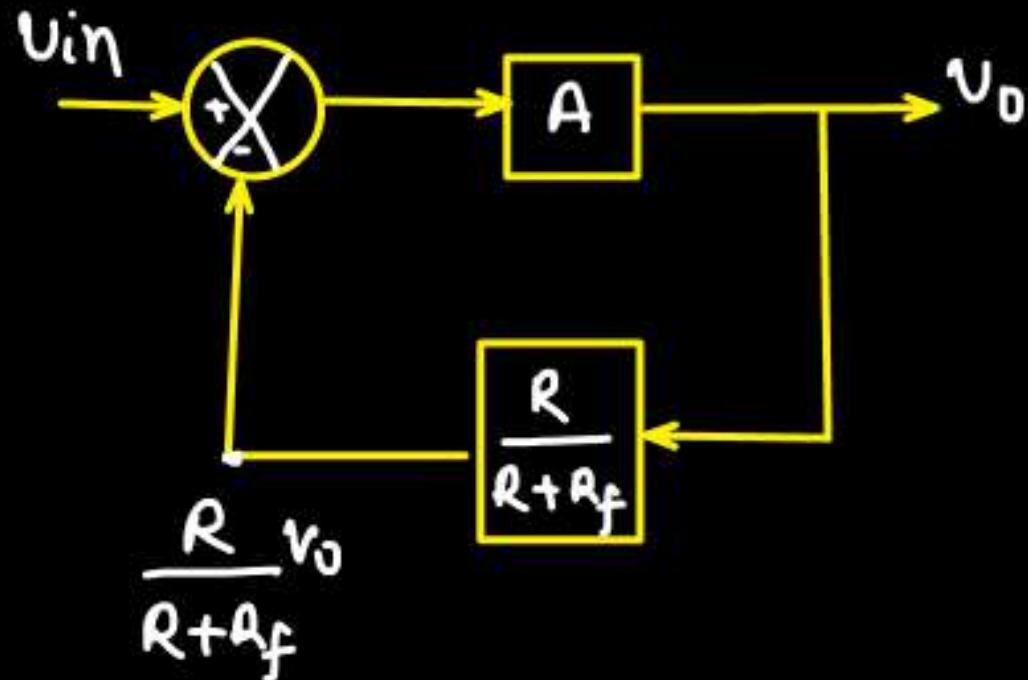


$$(A_v)_f = \frac{A}{1+A\beta}$$

$$(R_{in})_f = R_{in}(1+A\beta)$$

$$(R_o)_f = \frac{R_o}{1+A\beta}$$

② Inverting Amplifier:-


↳ v_p is applied at inverting terminal.

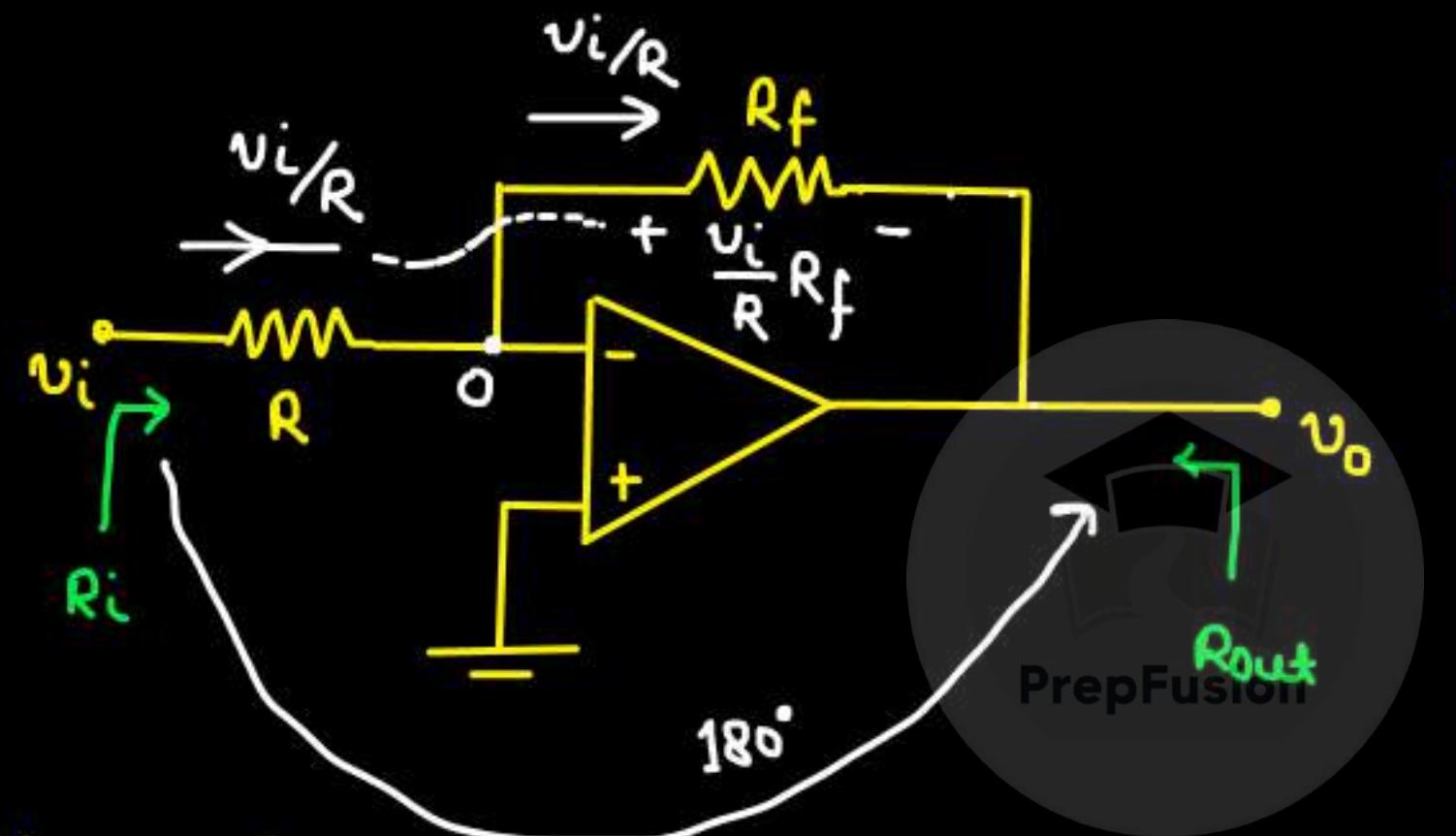

(a) Voltage gain :-

$$-\frac{v_i}{R} R_f = v_o \Rightarrow \frac{v_o}{v_i} = -\frac{R_f}{R}$$

(b) Input Resistance :-

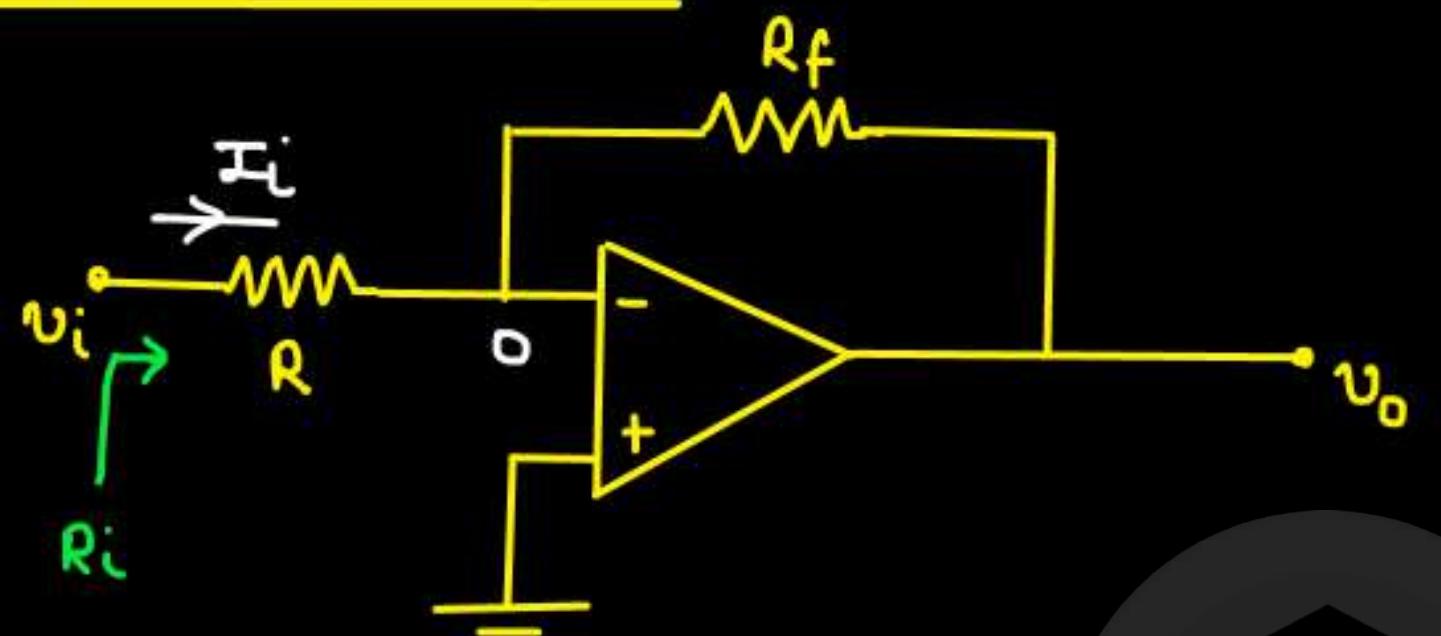


$$R_i = \frac{v_i}{I_i}$$

$$\frac{v_i}{I_i} = R$$

$$\frac{v_i}{I_i} = R_i = R$$




(c) Output Resistance :-

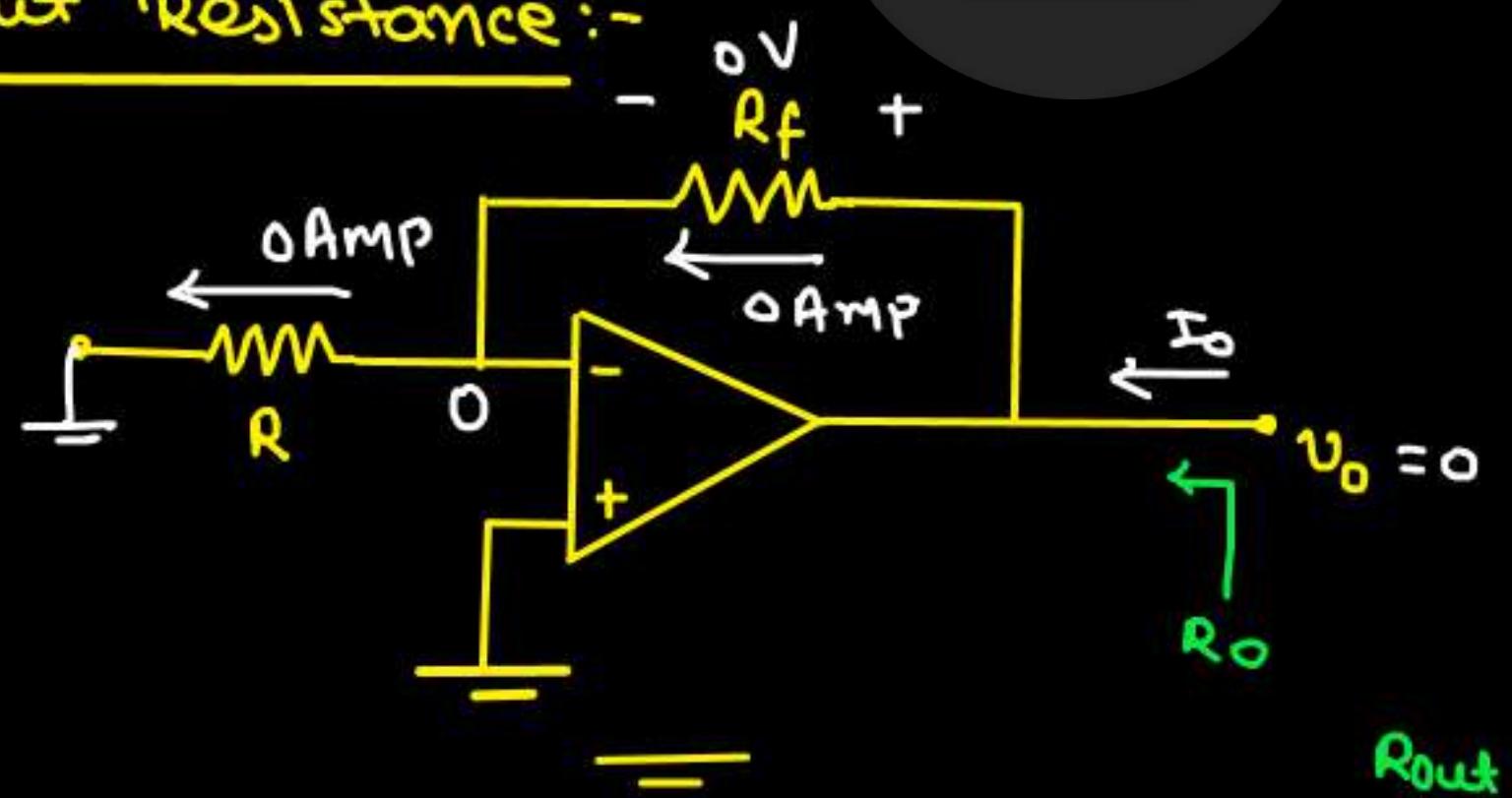


$$R_o = \frac{v_o}{I_o} = \frac{0}{I_o} = 0$$

$$R_o = 0 \Omega$$


Rout

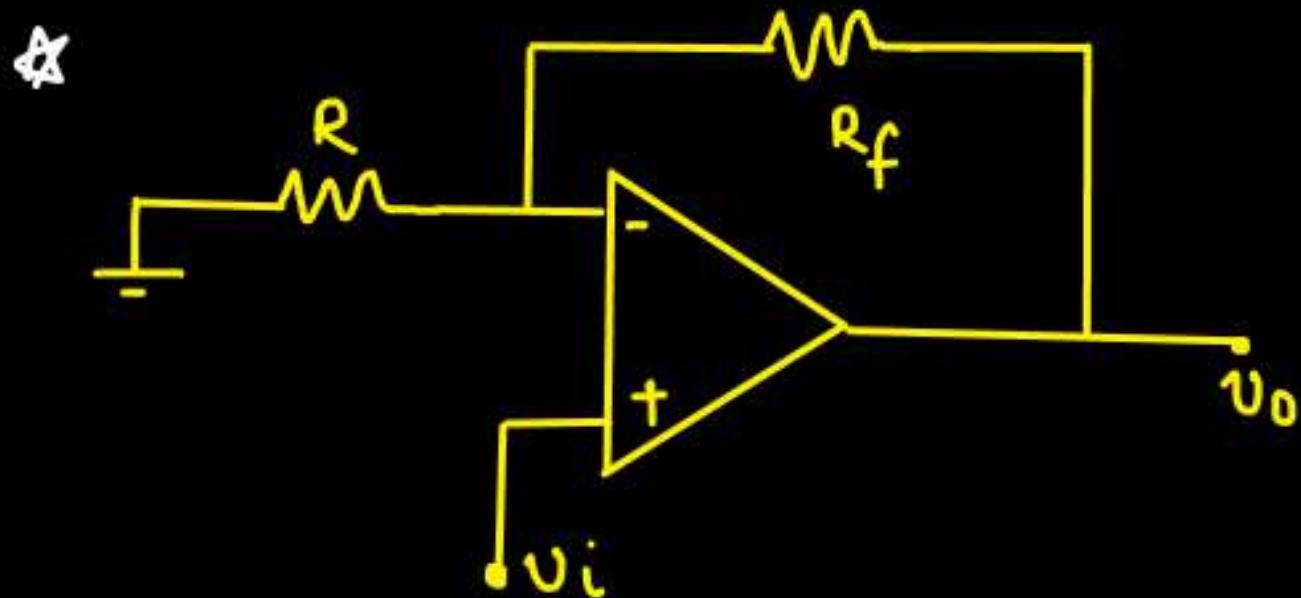




$$\frac{U_o}{U_i} = 1 + \frac{R_f}{R}$$

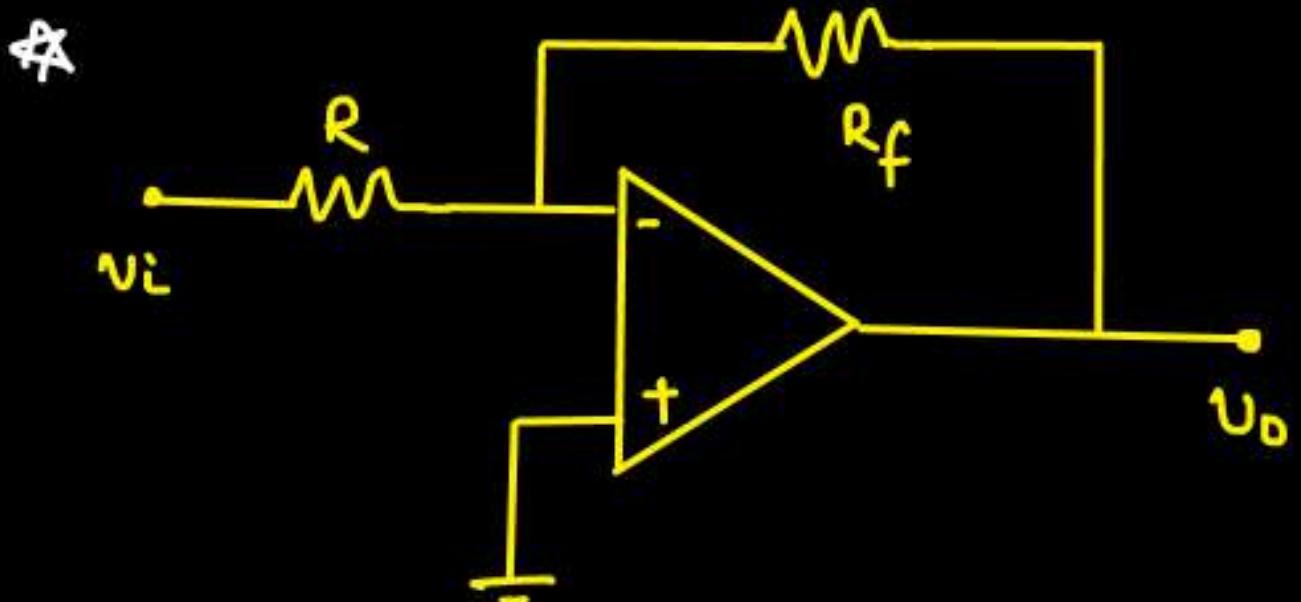



$$\frac{U_o}{U_i} = -\frac{R_f}{R}$$

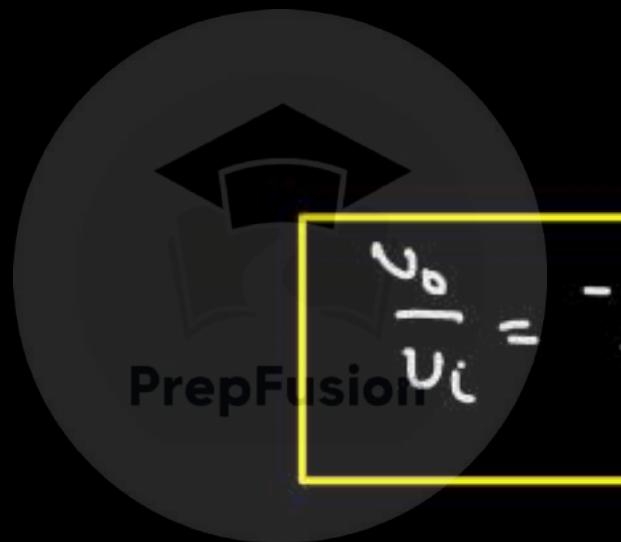

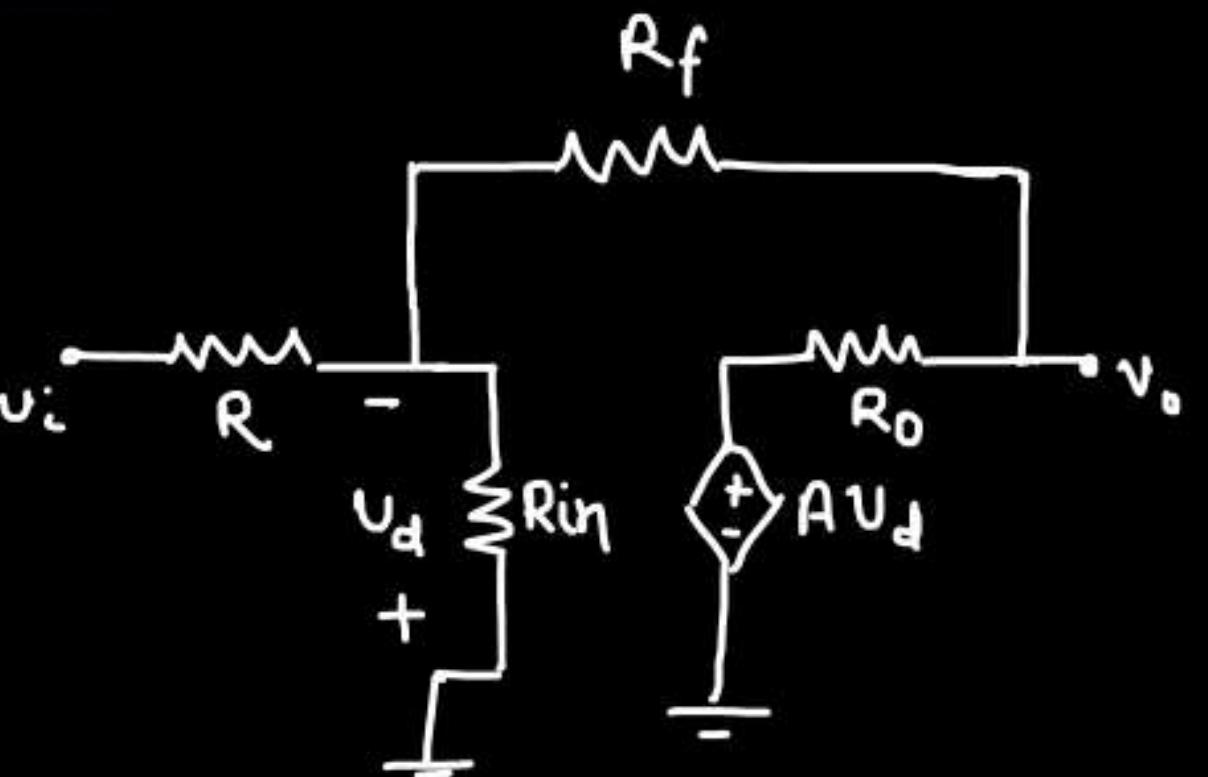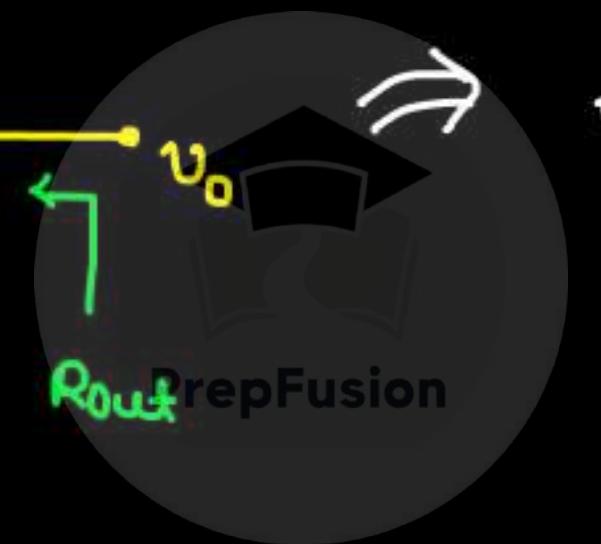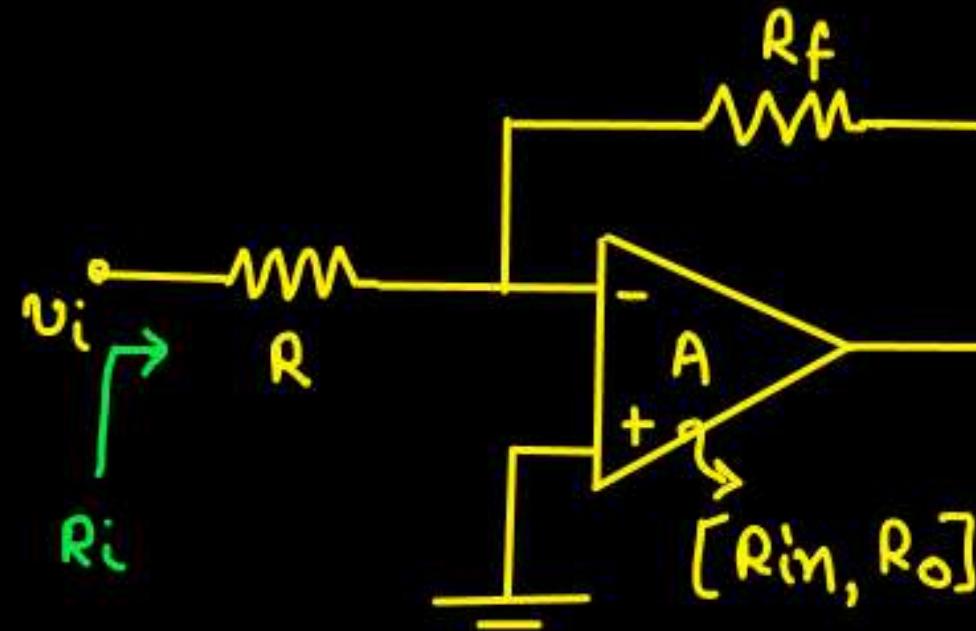★ Inverting Amplifier considering Non-Ideal OP-Amp [R_{in} , A, R_o]



(a) Voltage gain :-

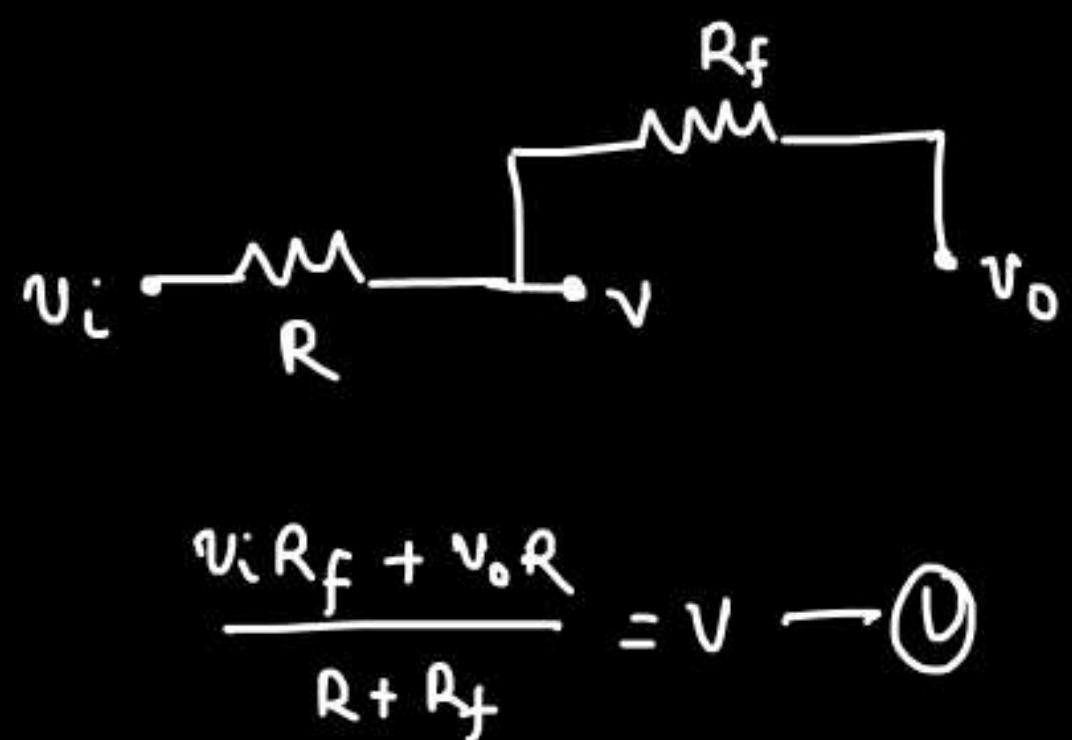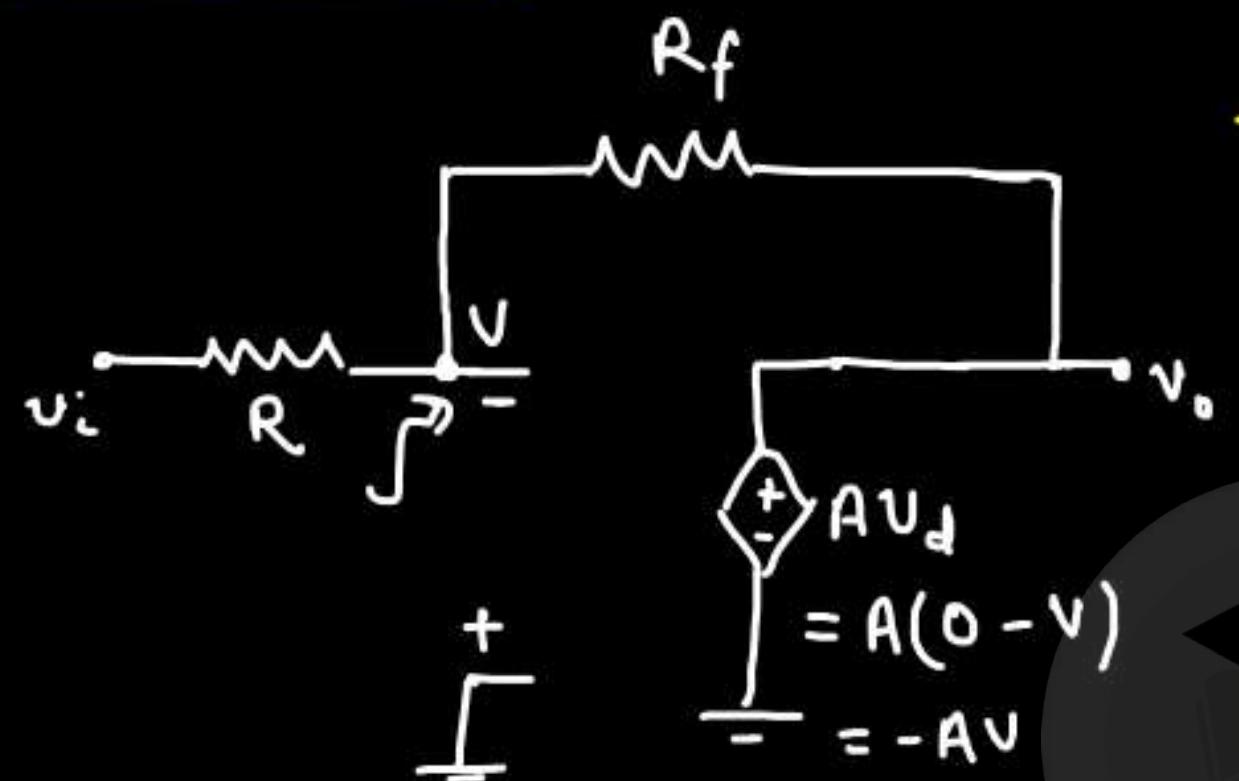

Let; $R_i = \infty$

$R_o = 0$

$$V_o = -AV$$

By eq η ①

$$V_o = -A \left[\frac{v_i R_f + V_o R}{R + R_f} \right]$$

$$[R + R_f] V_o = -A R_f v_i - A R V_o$$


$$V_o [R + R_f + A R] = -A R_f v_i$$

$$\boxed{\frac{V_o}{V_i} = \frac{-A R_f}{R_f + (1+A)R}}$$


if $A \rightarrow \infty$

$$\boxed{\frac{V_o}{V_i} = \frac{-A R_f}{A R} = -\frac{R_f}{R}}$$

(b) Input Resistance: -


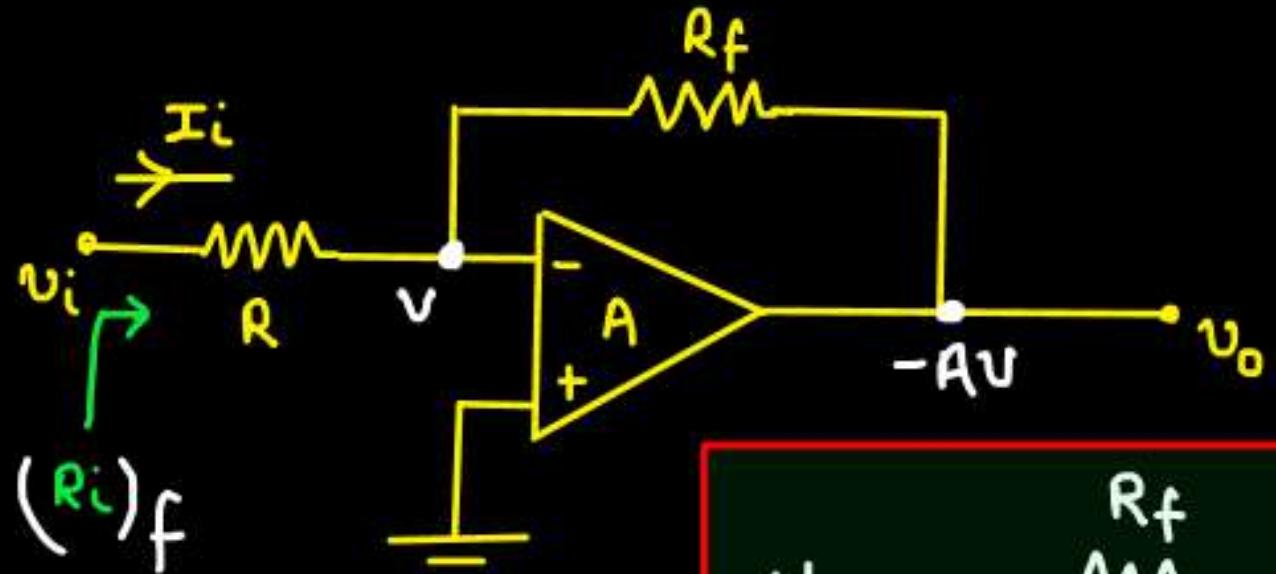


$$\frac{v_i}{I_i} = (R_i)_f$$

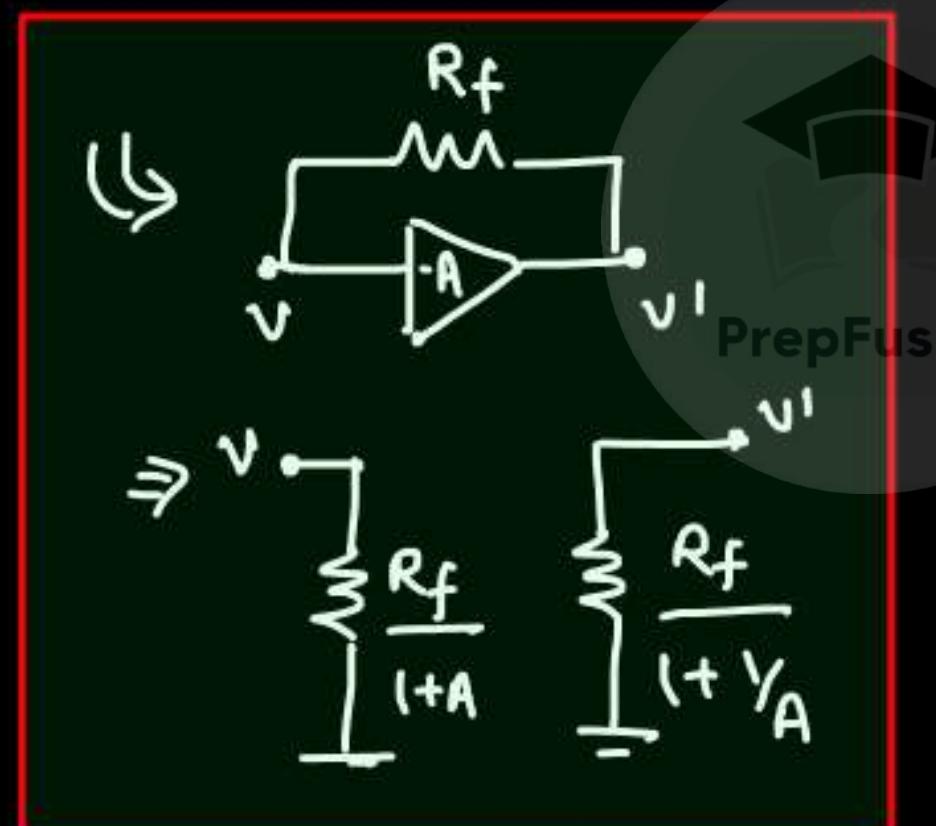


**

$$\Rightarrow (R_i)_f = R + \left[\frac{R_f}{1+A} || R_{in} \right]$$

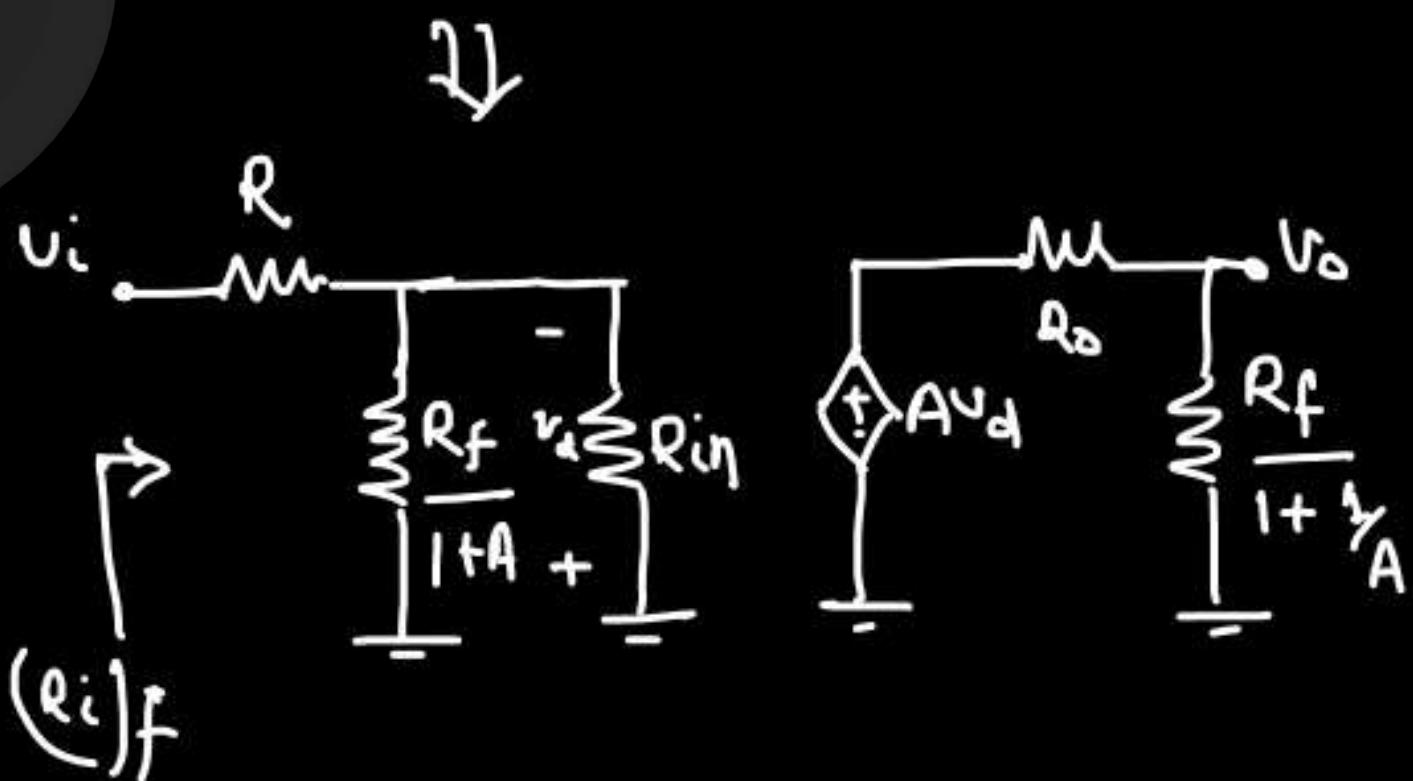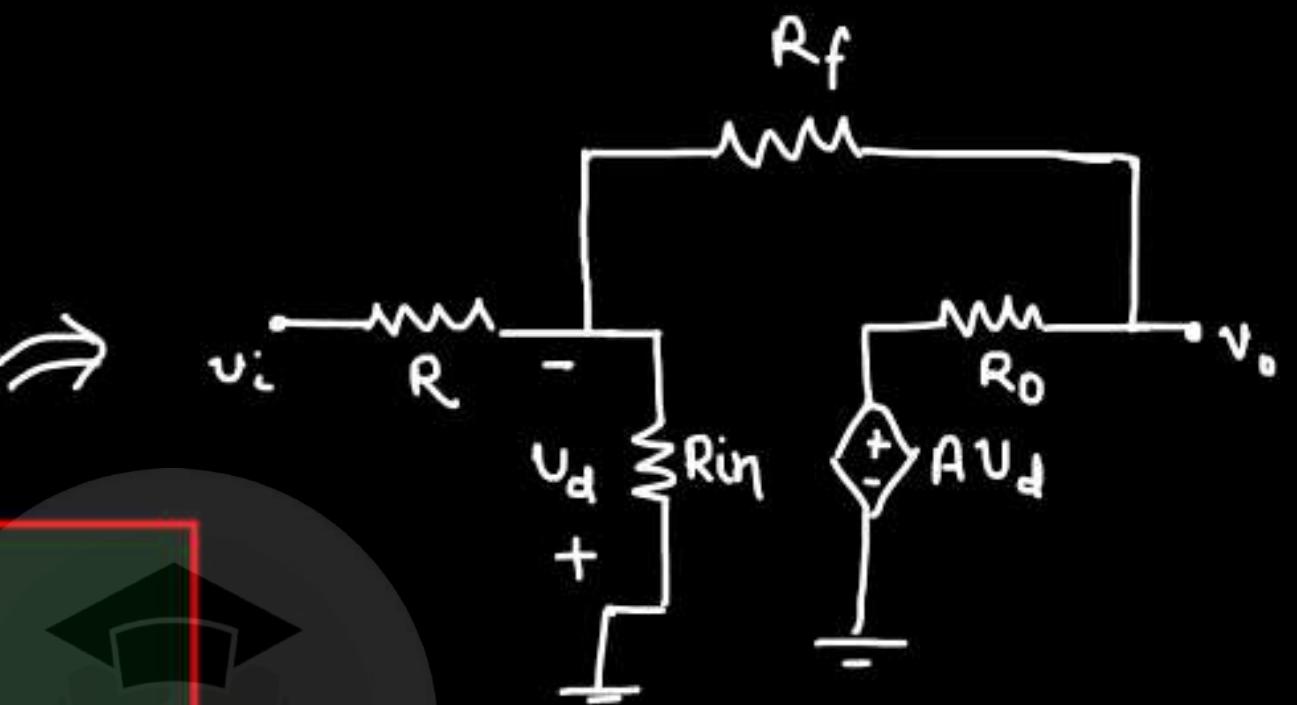

(C) Output Resistance :-

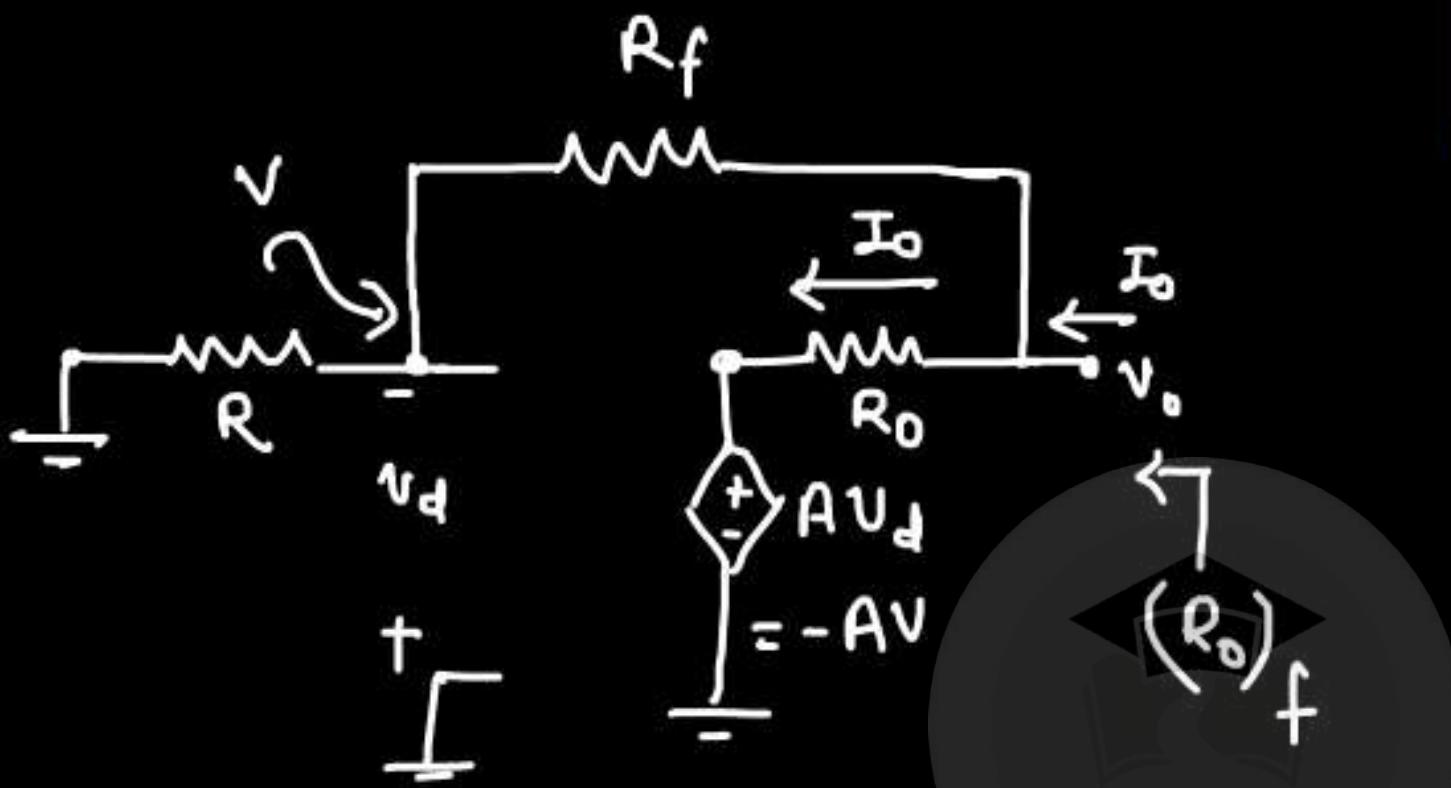

$$(R_o)_f = \frac{V_o}{I_o}$$

Assumption:-

R_o is too small, so it takes all the I_o current

$$\frac{V_o - (-Av)}{R_o} = I_o$$

$$V_o + Av = I_o R_o$$


$$V_o + A \left[\frac{R}{R+R_f} \right] V_o = I_o R_o$$

$$(R_o)_f = \frac{V_o}{I_o} = \frac{R_o}{1 + \frac{A R}{R + R_f}}$$

$A \rightarrow \infty$

$$(R_o)_f = 0$$

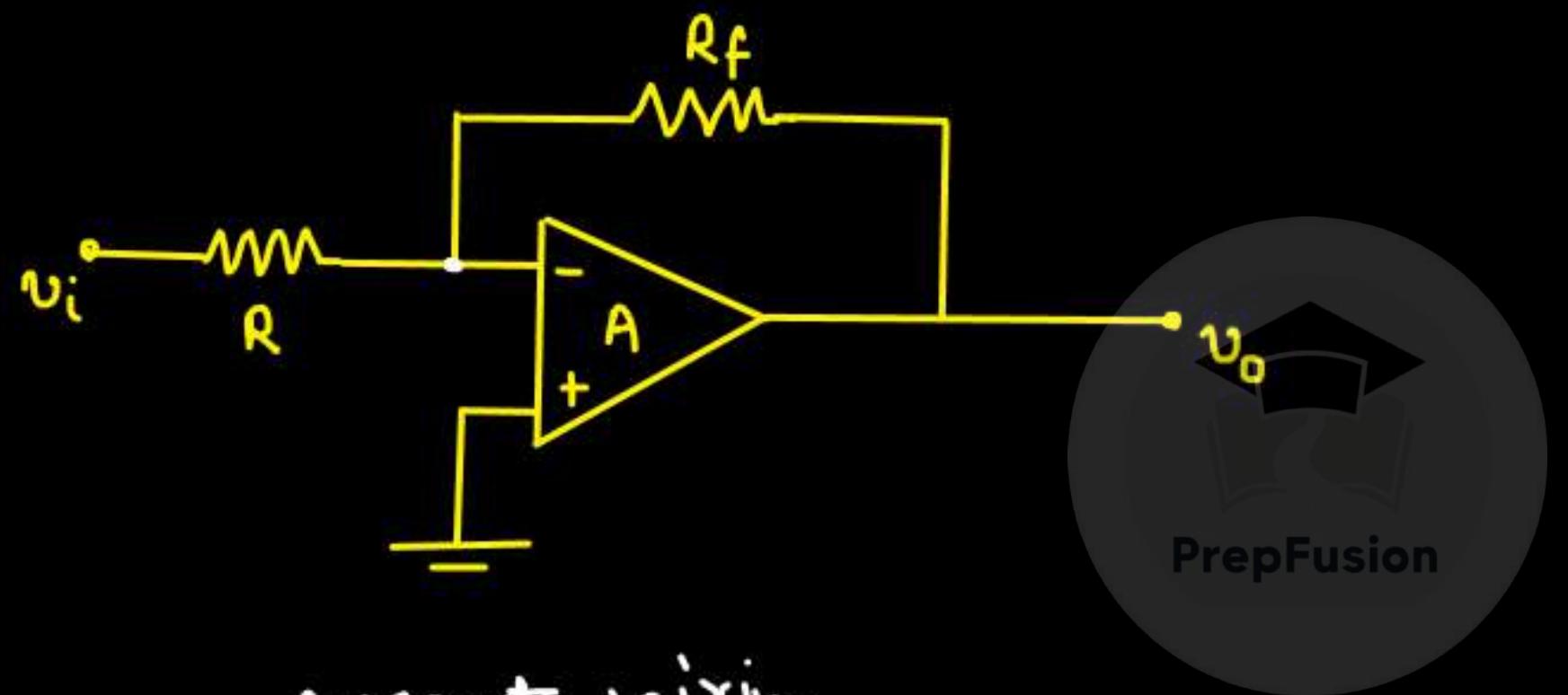* Understanding Inverting amplifier with the concept of feedback Topology :-




Current-mixing
Voltage-Sampling


Voltage - Current FB Topology



Transresistance amplifier

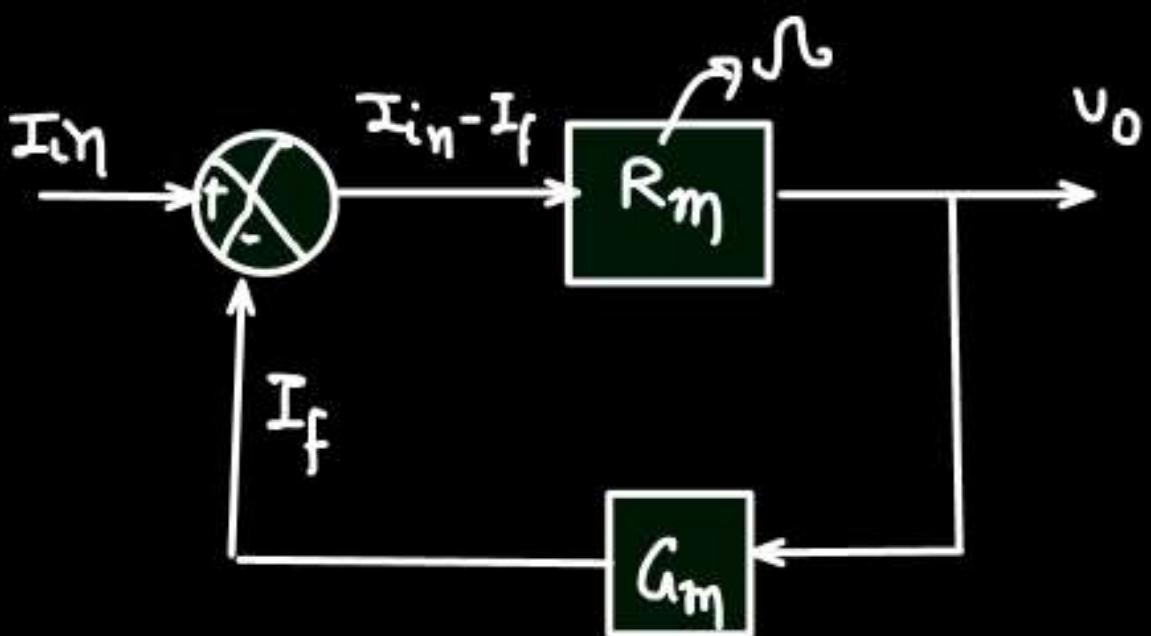


Q.

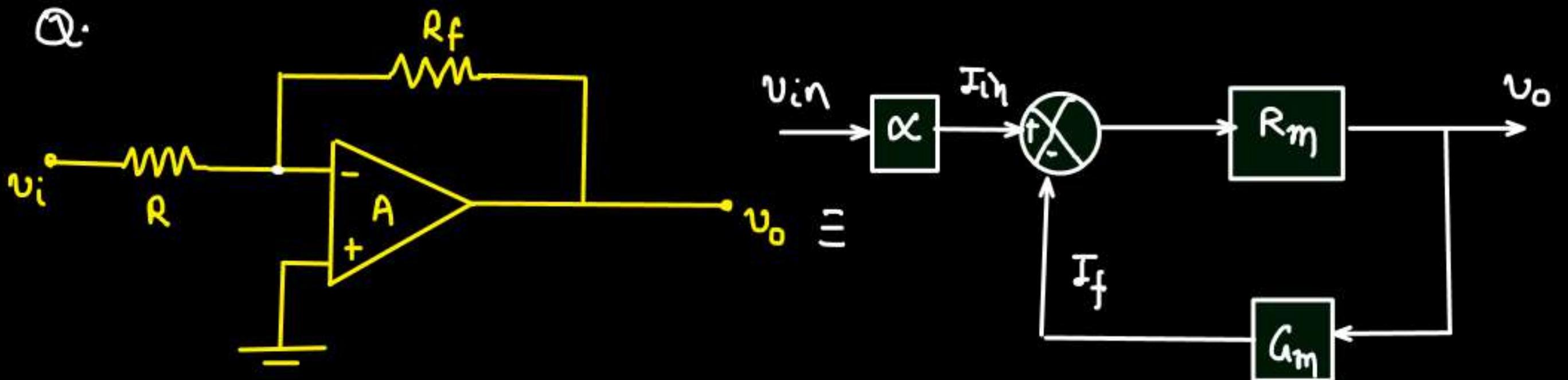

Find α , R_m and G_m ?

PrepFusion

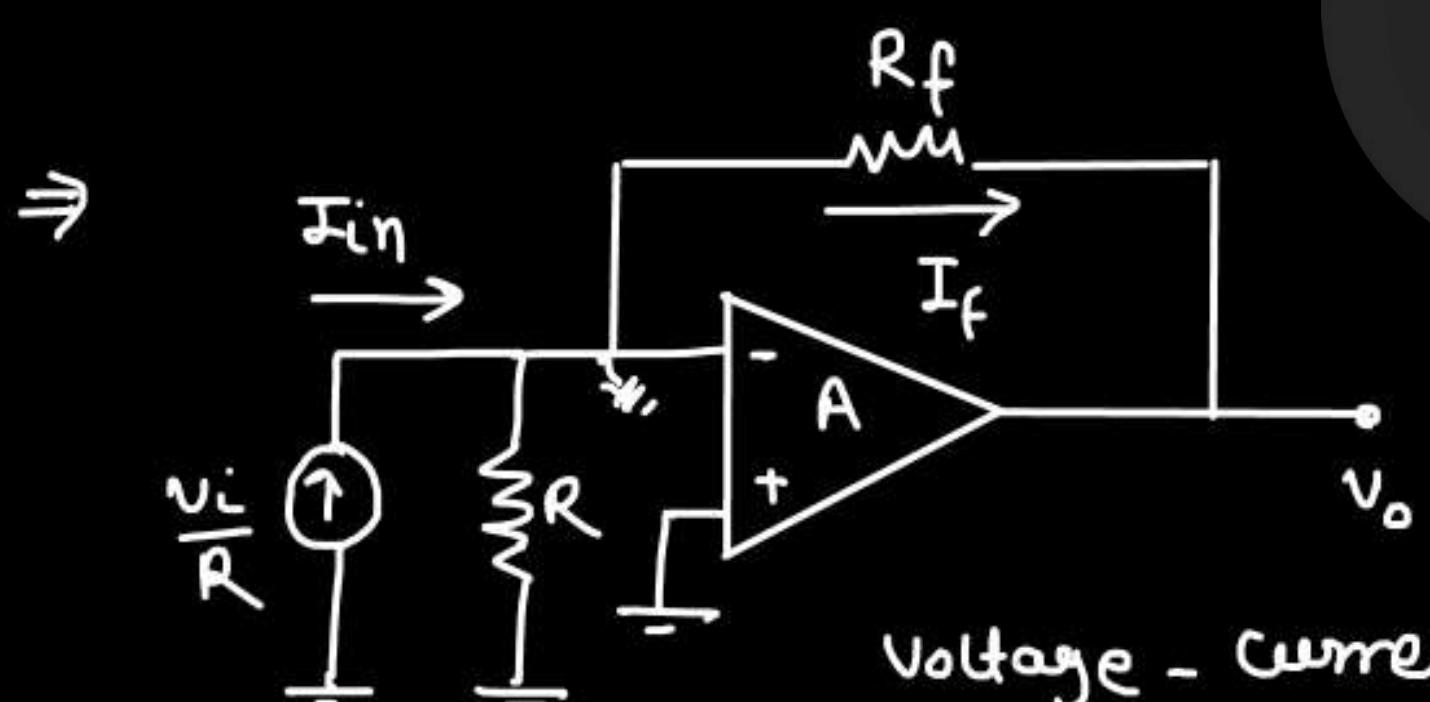

Voltage - current
 $\Rightarrow R_i \rightarrow \text{low}$, $R_o \rightarrow \text{low}$

$$\alpha v_{in} = I_{in}$$

$$I_{in} = \frac{v_{in}}{R}$$


$$I_f = -\frac{v_o}{R_f}$$

$$G_m = \frac{I_f}{v_o} = -\frac{1}{R_f}$$


$$G_m = -\frac{1}{R_f}$$

$$\alpha = \frac{1}{R}$$

open loop :-

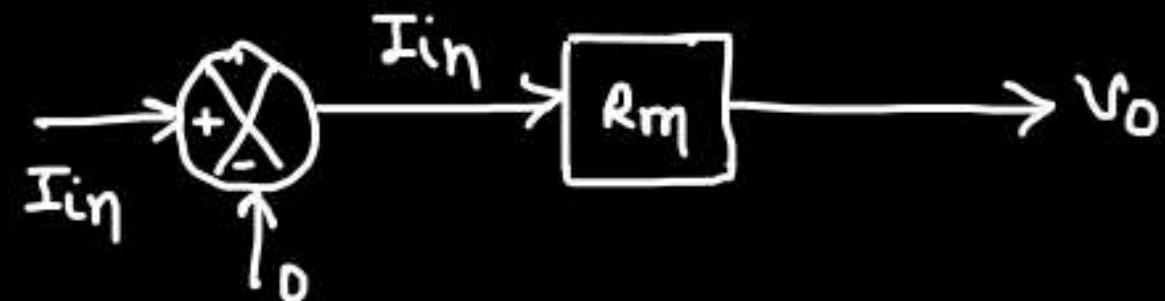

$$I_{in} R_m = v_o$$

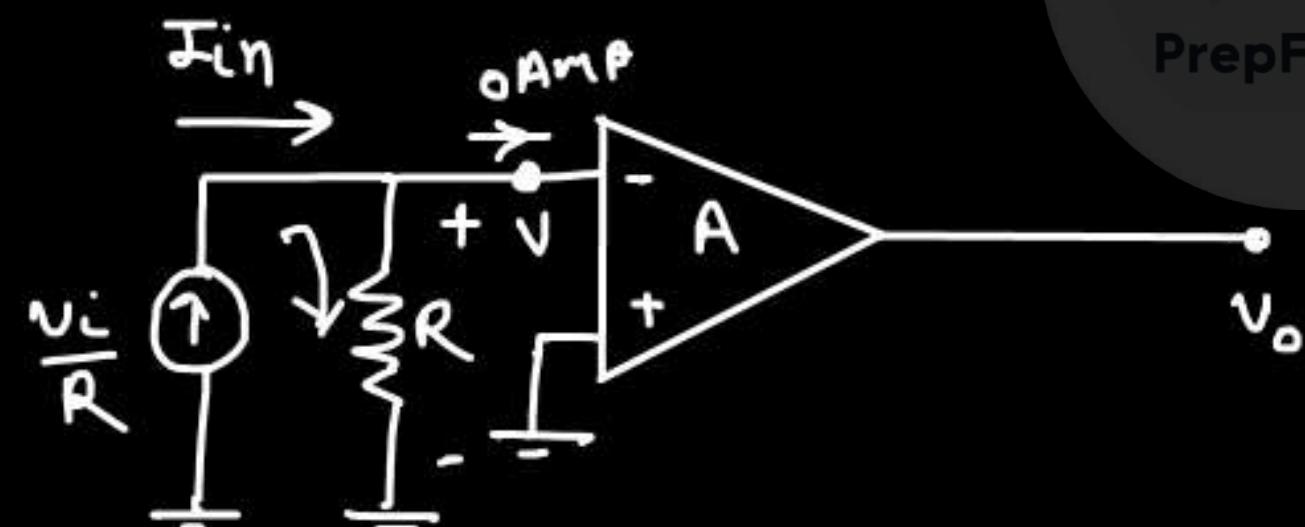


$$v = I_{in} R$$


$$v_o = -Av$$

$$v_o = -A [I_{in} R]$$

$$\frac{v_o}{I_{in}} = -AR = R_m$$

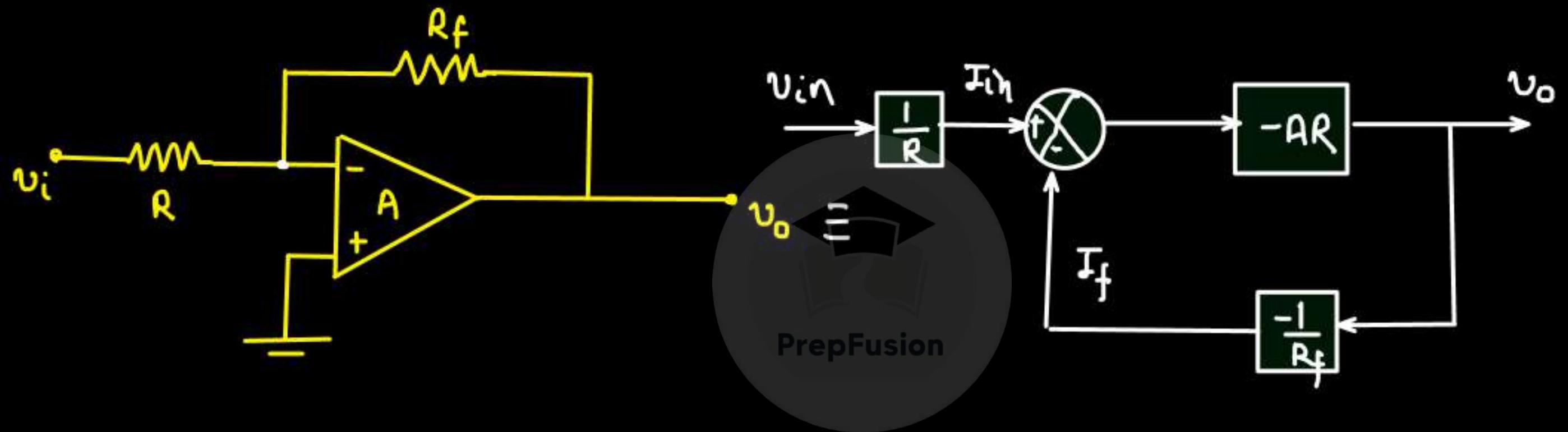

★ Voltage follower using OP-Amp:-

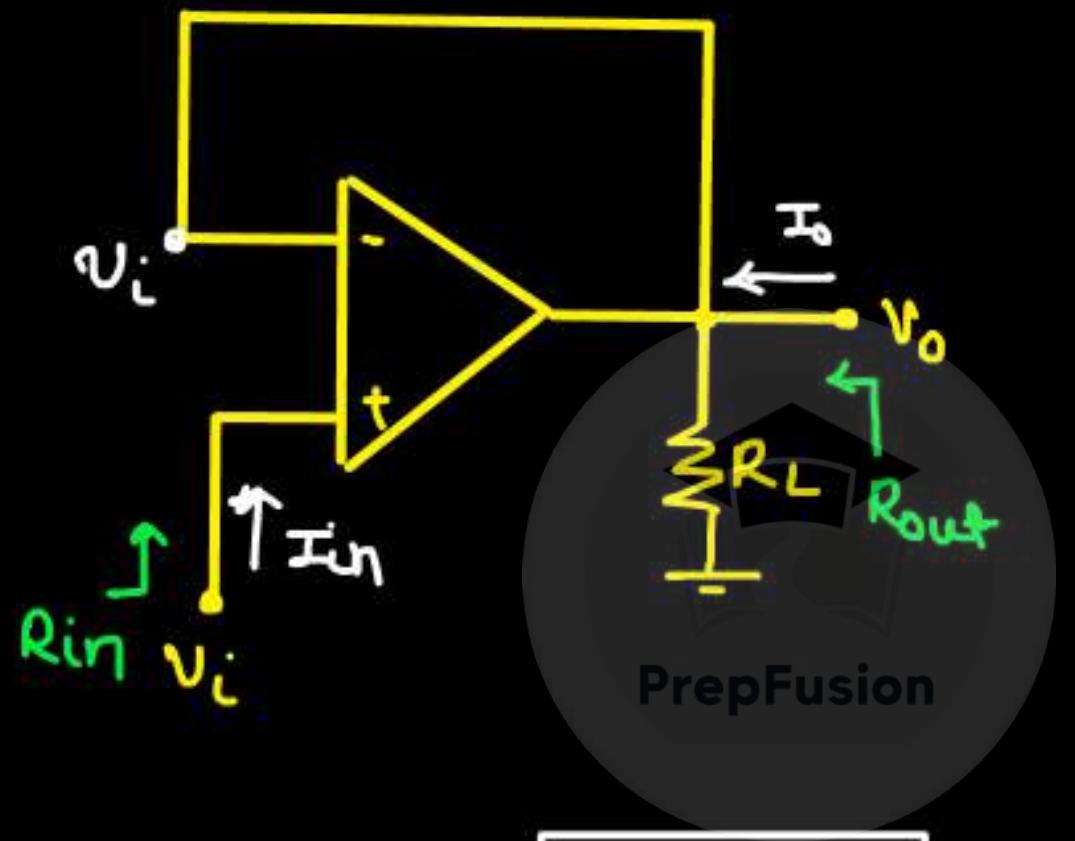


(a) Voltage gain :- $v_o = v_i \Rightarrow \frac{v_o}{v_i} = 1 \Rightarrow$ Voltage follower

(b) $R_{in} = \frac{v_i}{I_i} = \frac{v_i}{0} = \infty$

(c) $R_{out} = \frac{v_o}{I_o} = \frac{0}{I_o} = 0$

* Considering non-ideal Op-Amp:-

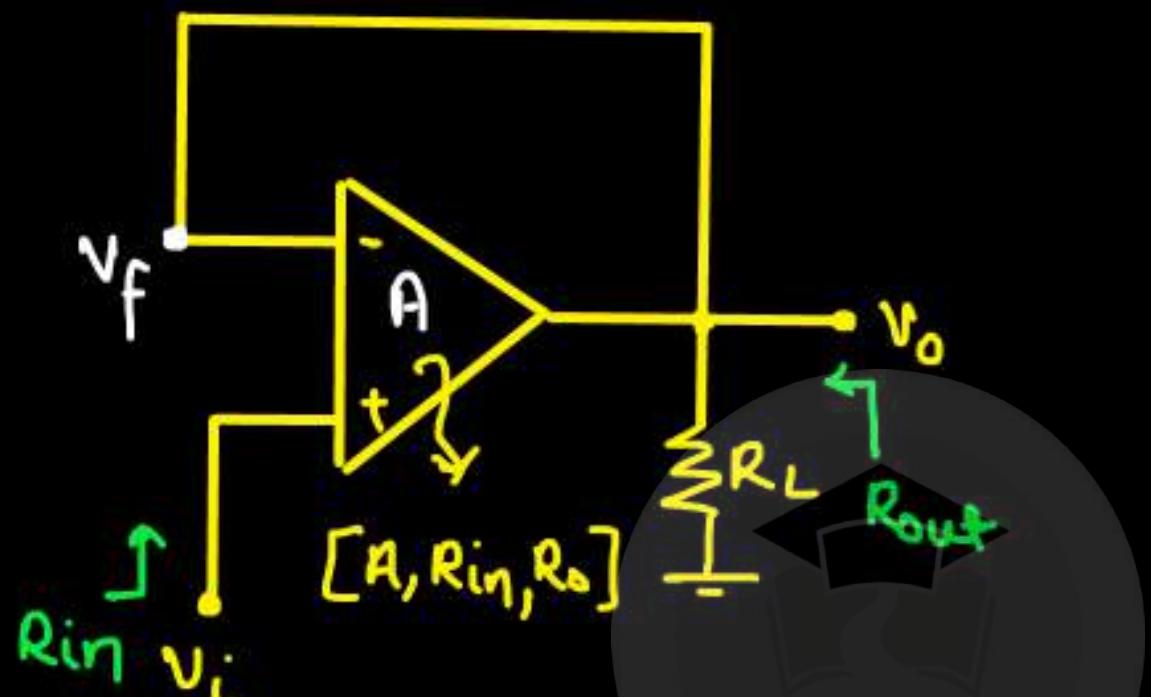

Voltage - mixing
Voltage - Sampling

↓
Voltage Amplifier


* feedback factor $\beta = 1$

(a) Voltage gain = $\frac{A}{1 + \alpha\beta} = \frac{A}{1 + A}$

(b) Input Impedance = $R_{in} (1 + \alpha)$

(c) Output Impedance = $\frac{R_o}{1 + A}$

(a) Voltage gain :-

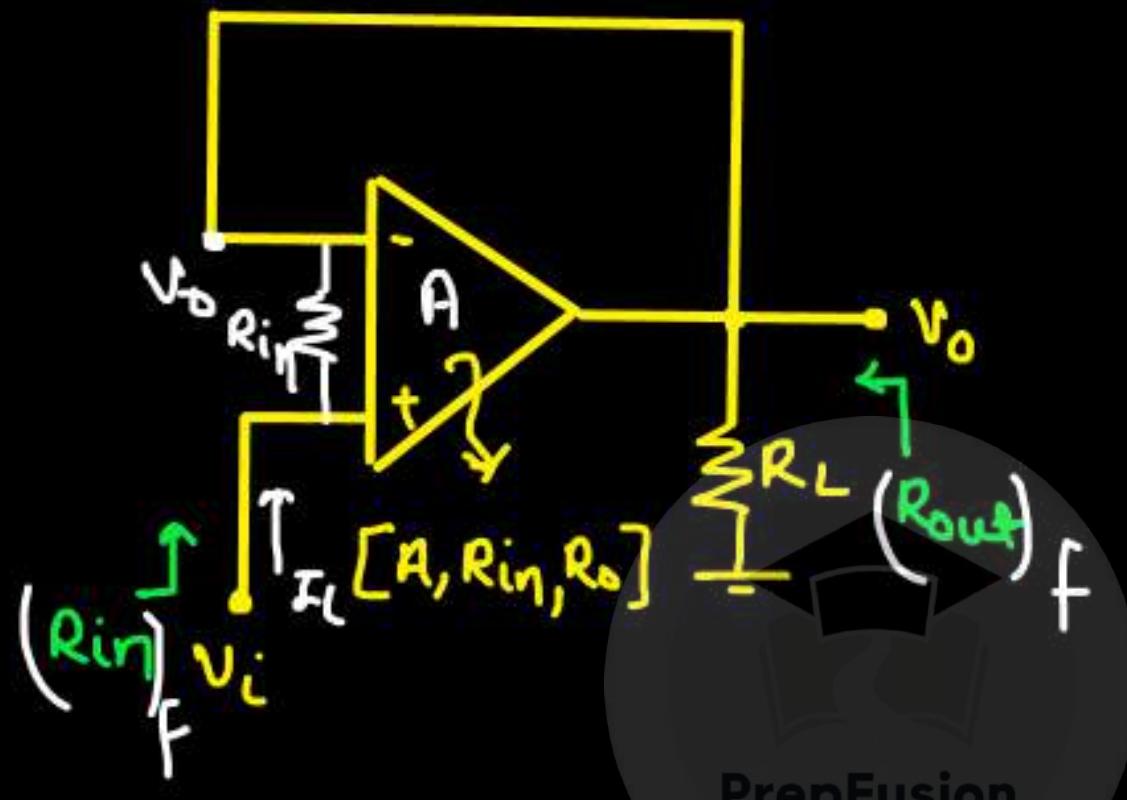


$$V_o = A[V_i - V_o]$$

$$V_o = \frac{A V_i}{1+A}$$

(b) Input Impedance :-

$$(R_{in})_f = \frac{V_i}{I_i}$$


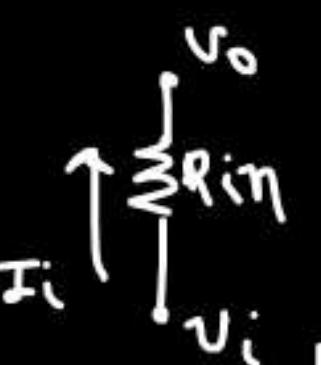


$$V_i - V_o = I_{in} R_{in}$$

$$V_i - \frac{A}{1+A} V_i = I_{in} R_{in}$$

$$(R_{in})_f = R_{in} (1+A)$$

(C) Output Impedance :-

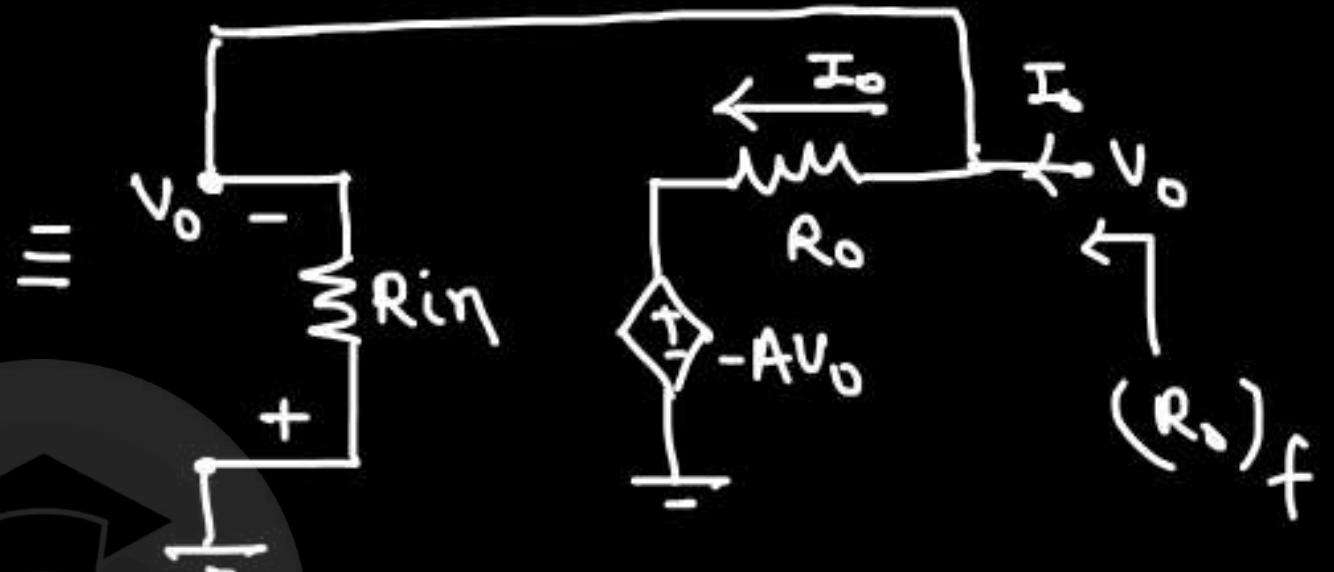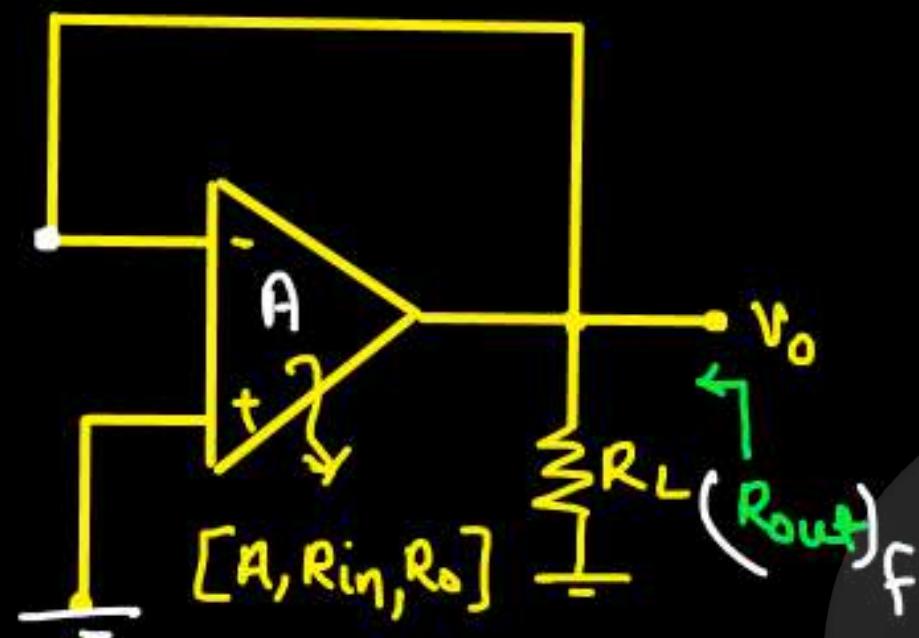

PrepFusion


$$\frac{V_o - (-AV_o)}{R_o} = I_o$$

$$\frac{V_o}{I_o} = \frac{R_o}{1+A}$$

$$(R_o)_f = \frac{R_o}{1+A}$$

→ OP-Amp Applications :-

① Inverting Adder :-

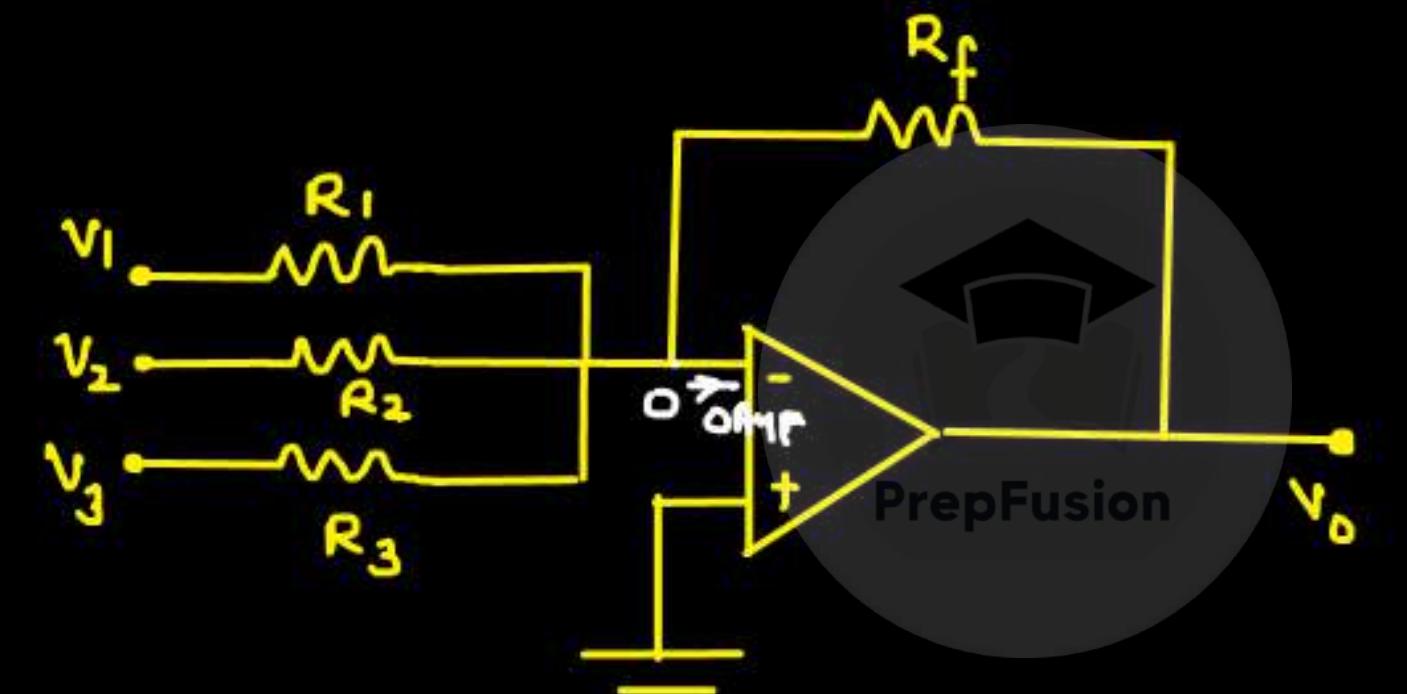

$$\left(\frac{0 - V_1}{R_1}\right)_+ + \left(\frac{0 - V_2}{R_2}\right)_+ + \left(\frac{0 - V_3}{R_3}\right)_+ + \left(\frac{0 - V_0}{R_f}\right)_+ = 0$$


$$V_0 = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

if $R_1 = R_2 = R_3 = R$

$$V_o = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$



② Non-inverting Adder:-

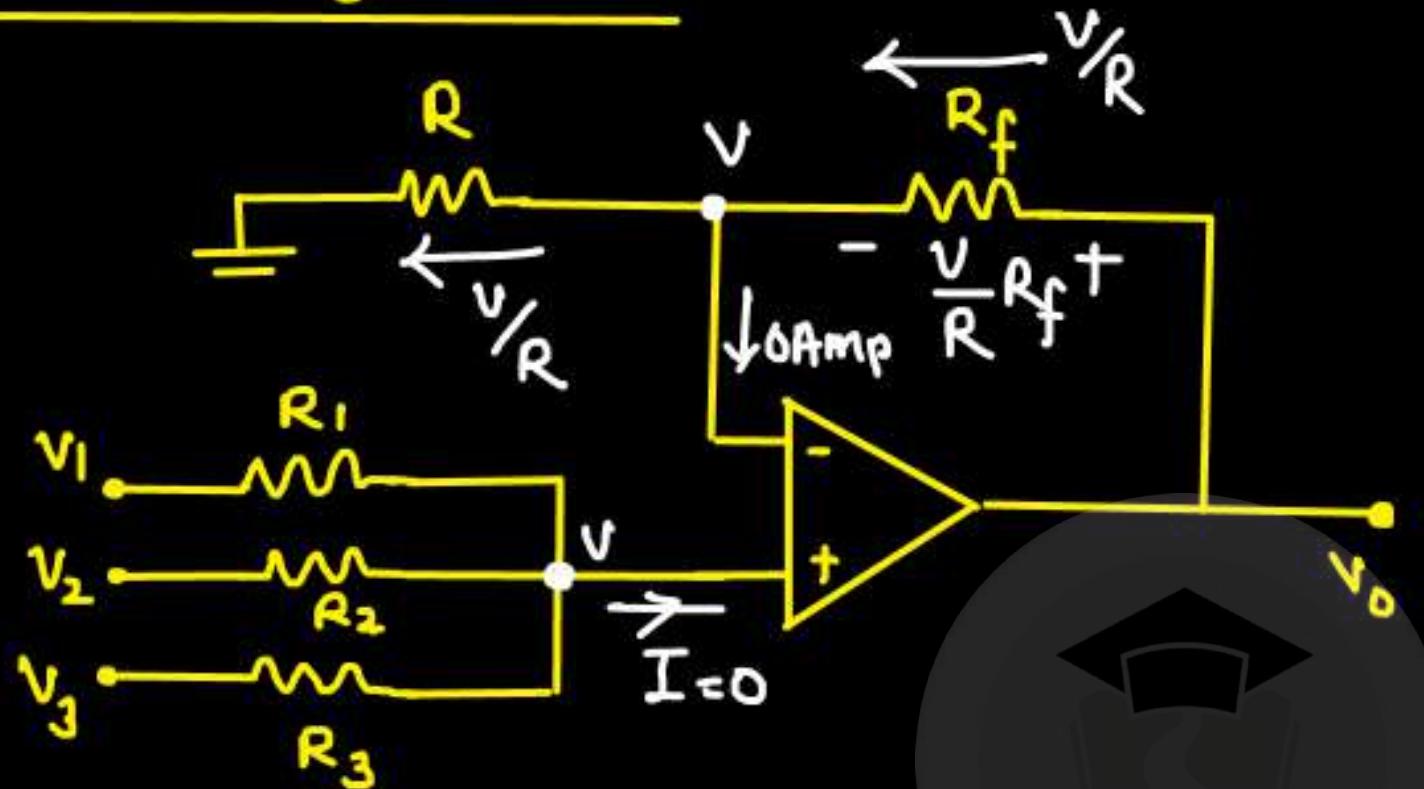

Take $R_1 = R_2 = R_3 = R$ Preprusion

$$\frac{V - V_1}{R_1} + \frac{V - V_2}{R_2} + \frac{V - V_3}{R_3} = D$$

$$V_0 = V + \frac{V}{R} R_f$$

$$V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$V_0 = \left(1 + \frac{R_f}{R} \right) V - \textcircled{O}$$

Take $R_1 = R_2 = R_3 = R$

$$\frac{3V}{R} = \frac{V_1 + V_2 + V_3}{R}$$

$$V = \frac{V_1 + V_2 + V_3}{3} \quad \text{--- } ②$$


By eqn ① and ②

$$V_o = \left(1 + \frac{R_f}{R}\right) \left(\frac{V_1 + V_2 + V_3}{3} \right)$$

if $R_f = 2R$

$$V_o = V_1 + V_2 + V_3$$

③ Differential Amplifier :-

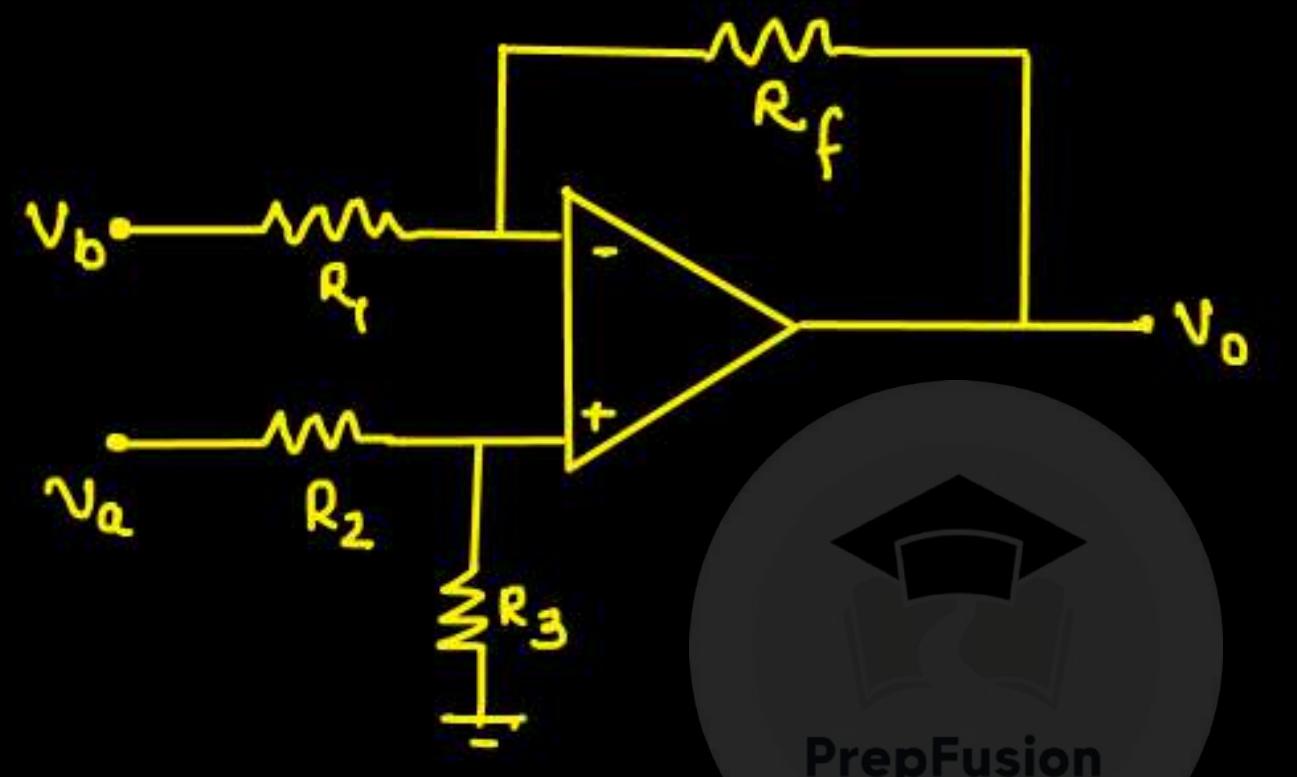


Take

$$\frac{R_1}{R_f} = \frac{R_2}{R_3}$$

Applying Superposition Theorem:-

(1)

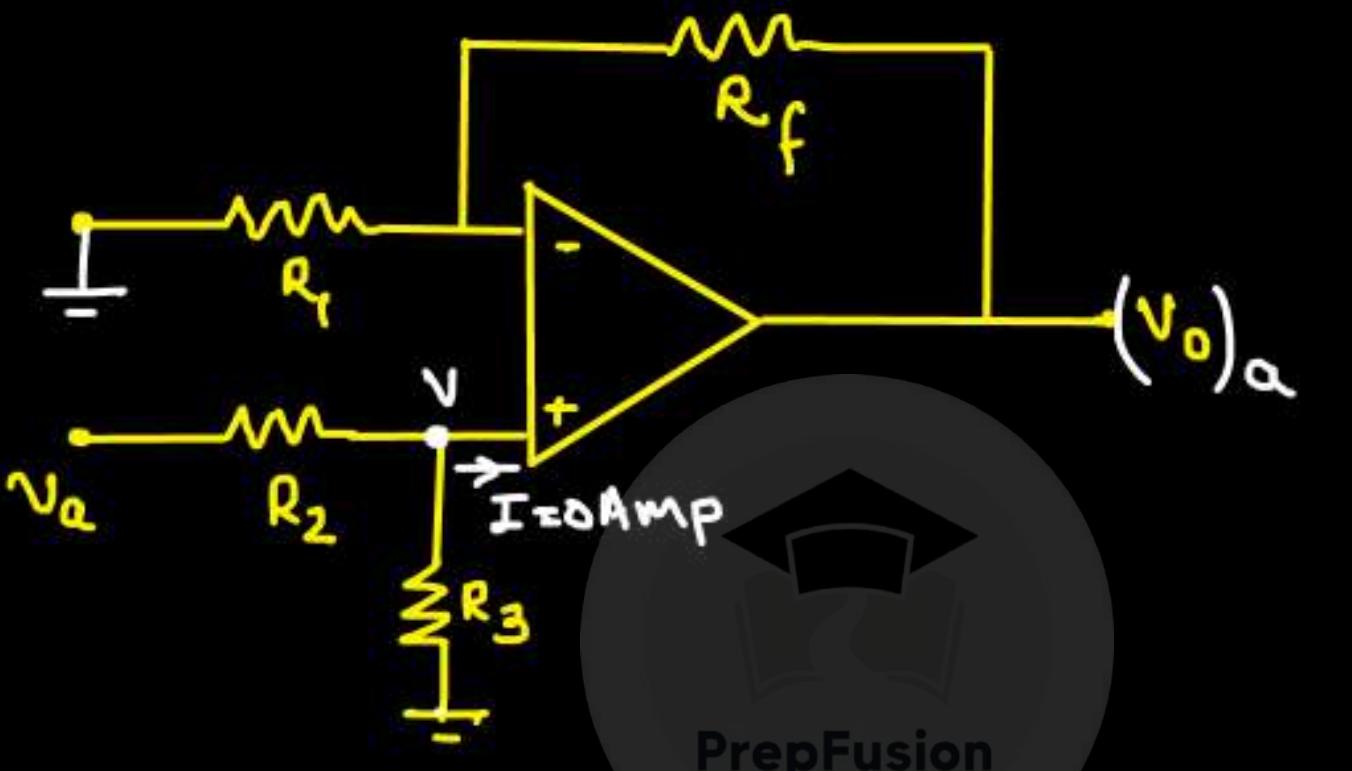


$$(v_o)_a = \left(1 + \frac{R_f}{R}\right)v - ①$$

$$v = \frac{R_3}{R_3 + R_2} v_a - ②$$

$$v = \frac{R_3}{R_3 + R_2} v_a$$
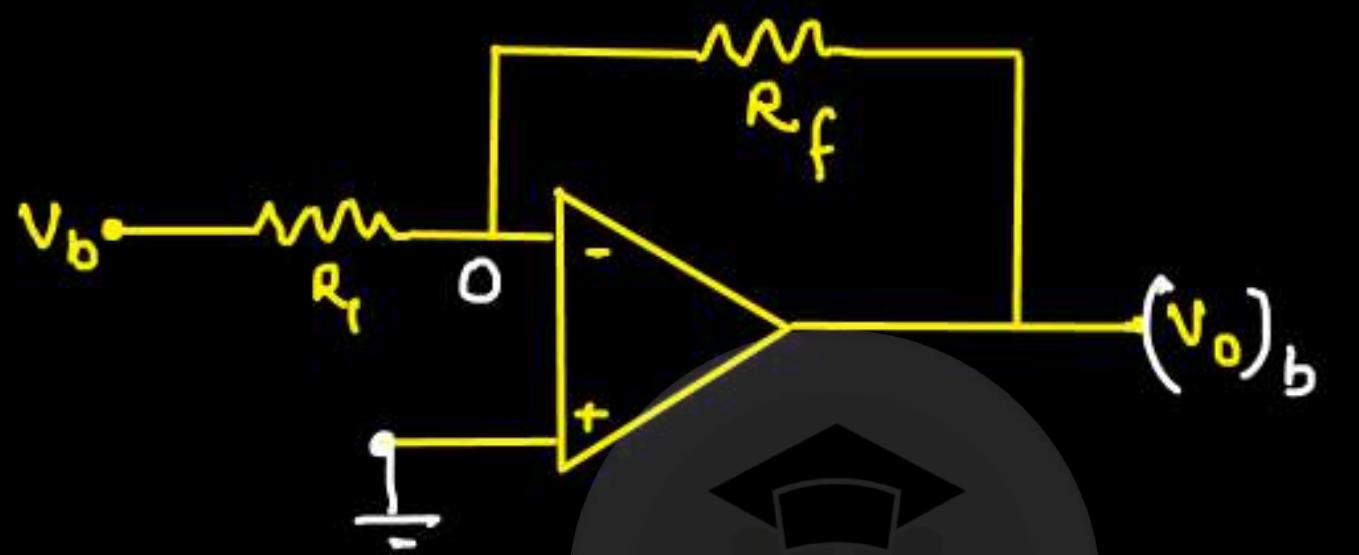
$$(V_o)_a = \left[1 + \frac{R_f}{R_1} \right] \left[\frac{R_3}{R_3 + R_2} \right] V_a \quad \text{--- (3)}$$



$$(V_o)_b = -\frac{R_f}{R_1} V_b \quad \text{PrepFusion} \quad \text{--- (4)}$$

$$V_o = (V_o)_a + (V_o)_b$$

$$V_o = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{R_3}{R_3 + R_2} \right) V_a - \frac{R_f}{R_1} V_b$$

Given

$$\frac{R_1}{R_f} = \frac{R_2}{R_3}$$


$$V_o = \left[1 + \frac{R_f}{R_1} \right] \left[\frac{1}{1 + \frac{R_2}{R_3}} \right] V_a - \frac{R_f}{R_1} V_b$$

$$= \left[\frac{R_1 + R_f}{R_1} \right] \left[\frac{R_f}{R_f + R_1} \right] V_a - \frac{R_f}{R_1} V_b$$

PrepFusion

$$V_o = \frac{R_f}{R_1} [V_a - V_b]$$

* Conclusion:-

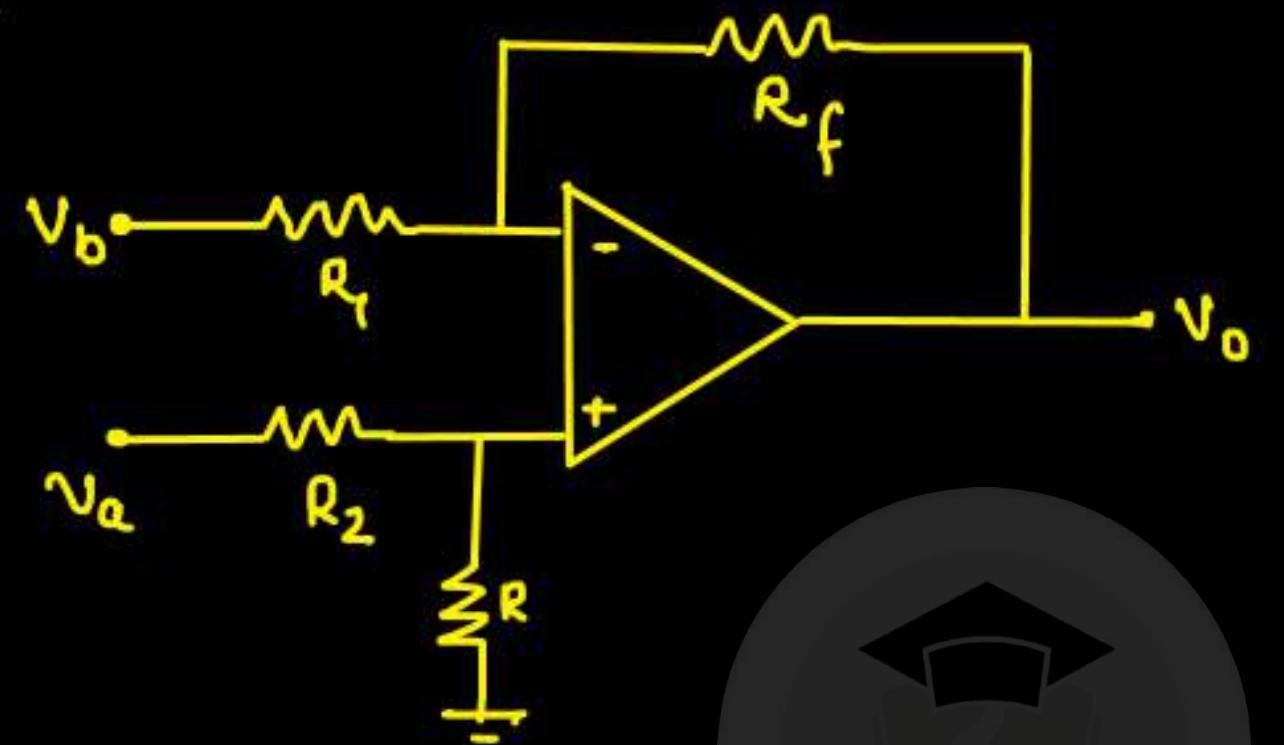


if $\frac{R_1}{R_f} = \frac{R_2}{R_3}$

PrepFusion

$$V_o = \frac{R_f}{R_1} (V_a - V_b)$$

$$V_o \propto (V_a - V_b)$$

④ Instrumentation Amplifier:-

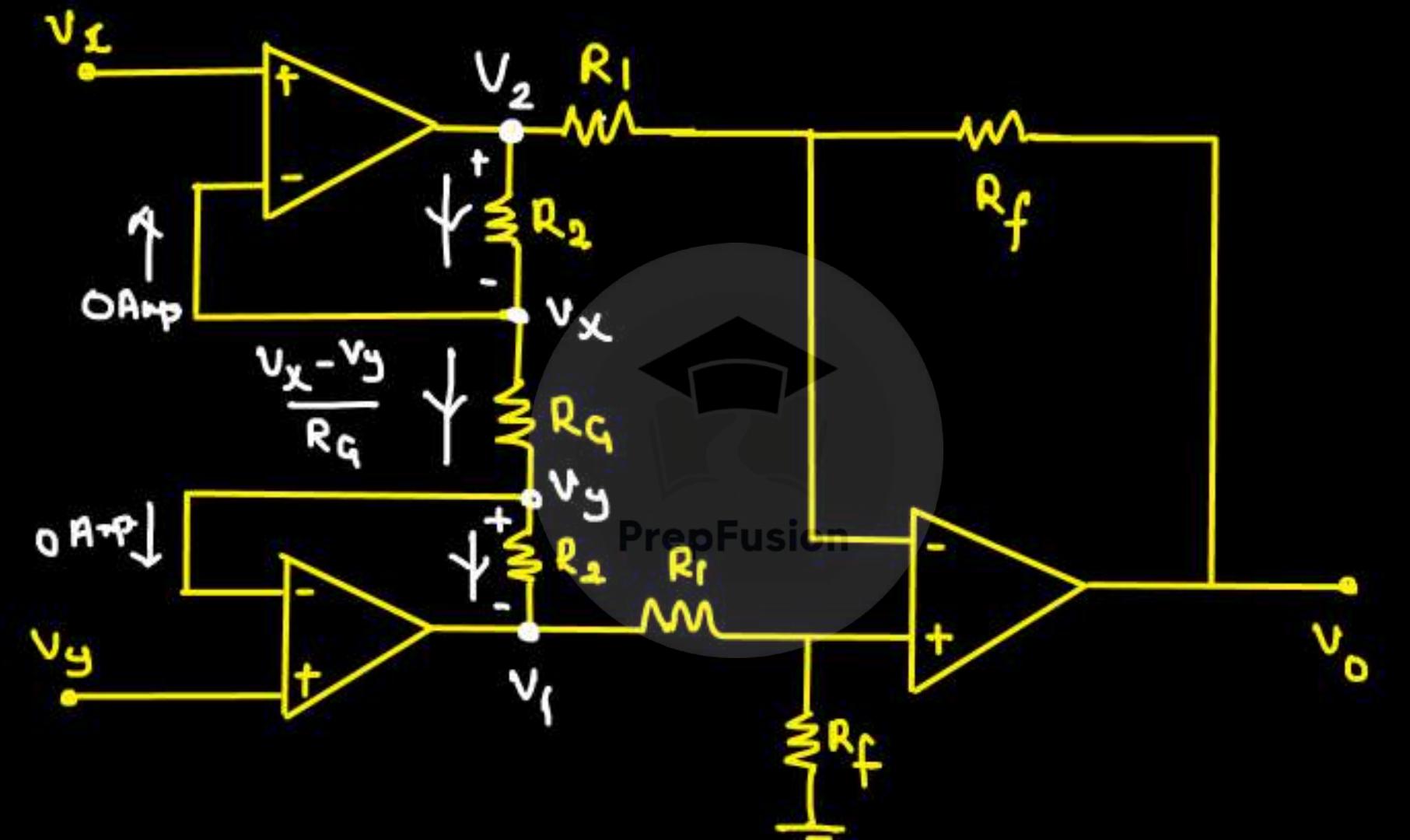

$$V_o = \frac{R_f}{R_i} (V_x - V_y) \quad \textcircled{1}$$

$$V_2 = V_x + R_2 \left(\frac{V_x - V_y}{R_Q} \right) \quad \text{--- (2)}$$

$$V_1 = V_y - R_2 \left(\frac{V_x - V_y}{R_Q} \right) \quad \text{--- (3)}$$


$$V_o = \frac{R_f}{R_1} \left[V_y - \frac{R_2}{R_Q} (V_x - V_y) - V_x + \frac{R_2}{R_Q} (V_x - V_y) \right]$$

PrepFusion

$$= \frac{R_f}{R_1} \left[(V_y - V_x) + \frac{R_2}{R_Q} (V_y - V_x) + \frac{R_2}{R_Q} (V_y - V_x) \right]$$

$$\boxed{V_o = \frac{R_f}{R_1} \left[\left(1 + 2 \frac{R_2}{R_Q} \right) (V_y - V_x) \right]}$$

Conclusion:-


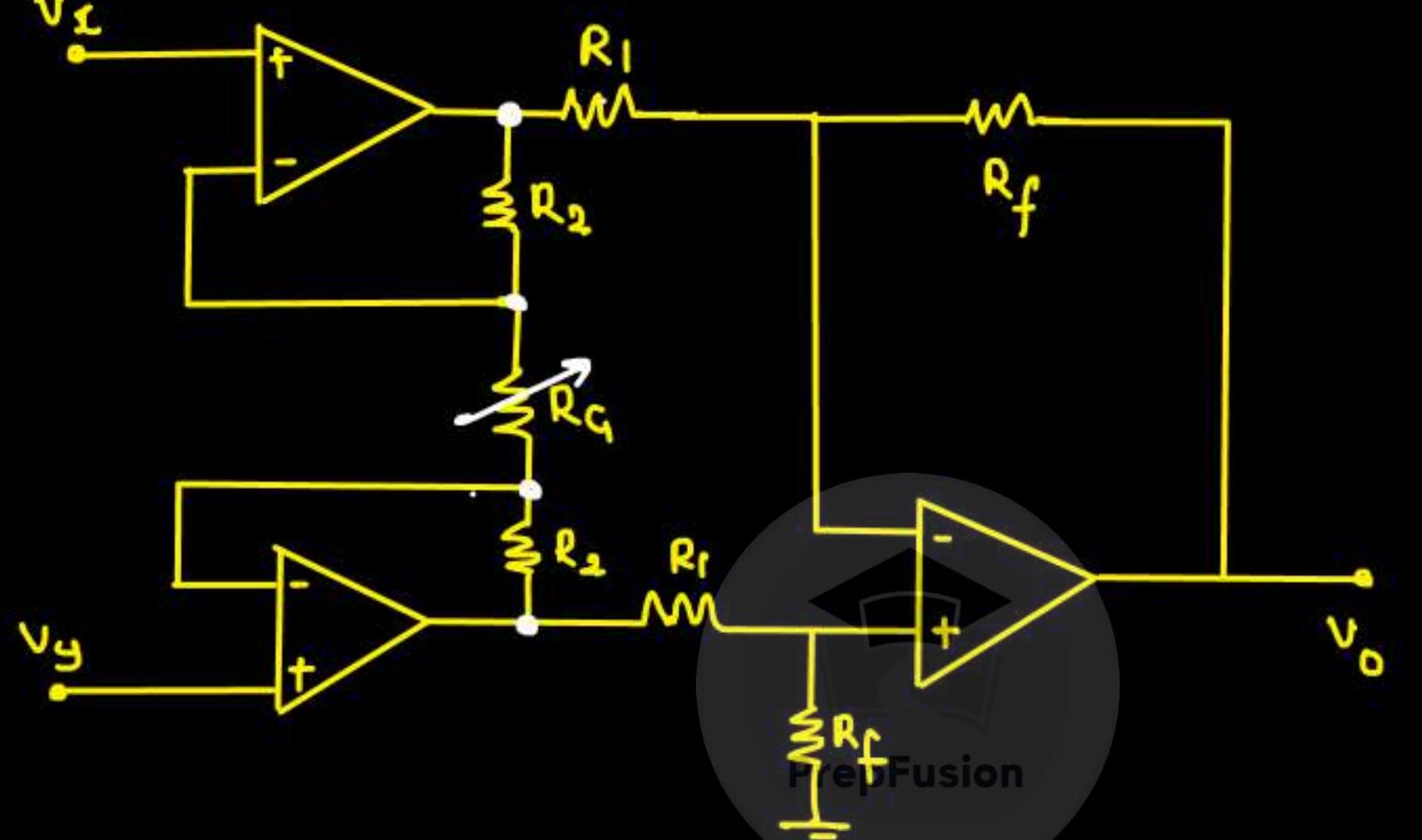


$$V_o = \frac{R_f}{R_1} \left[1 + \frac{2R_2}{R_g} \right] [V_y - V_x]$$

$$V_o \propto (V_y - V_x)$$

↳ I.A. is a kind of differential amplifier with Higher gain.

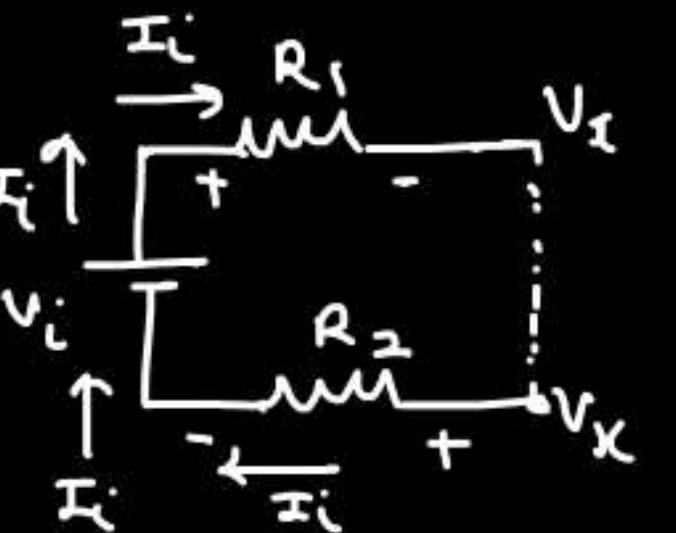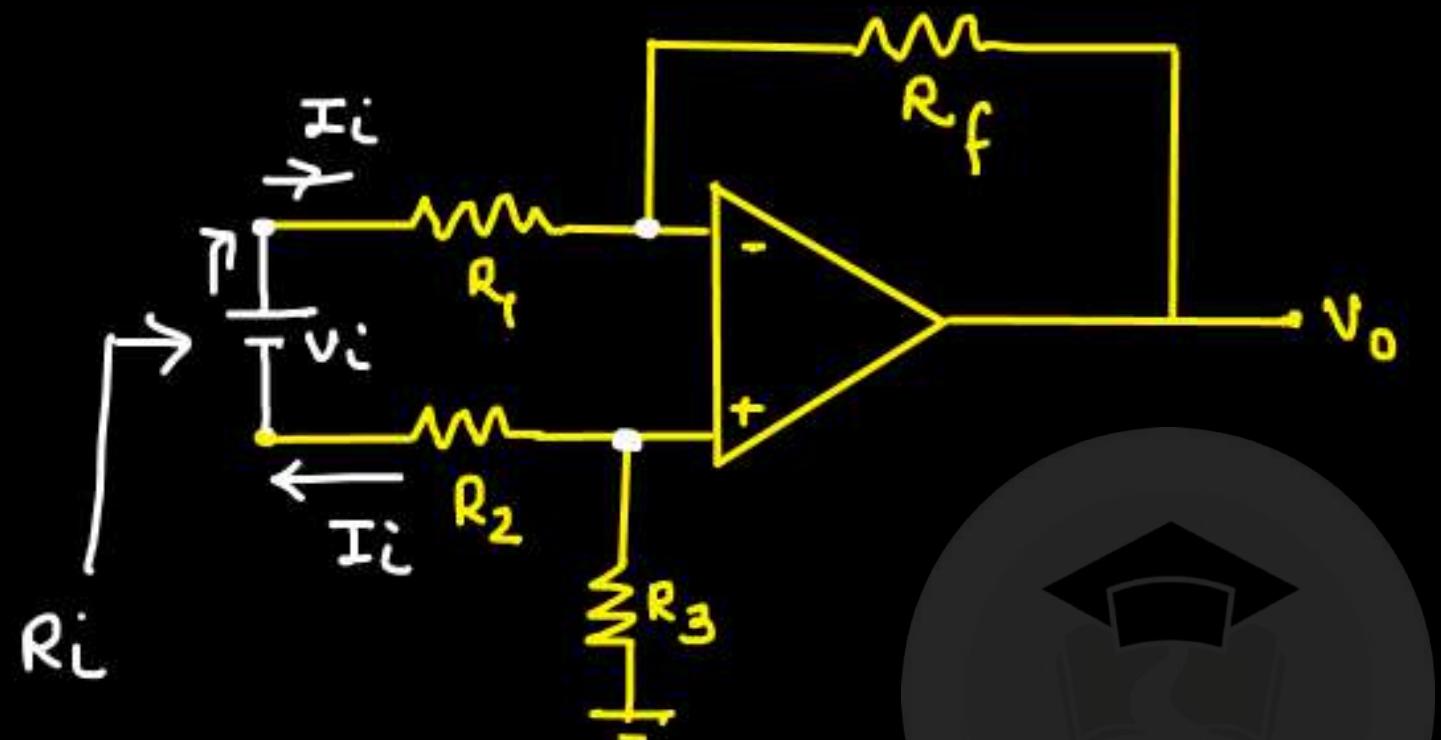* Input Impedance of differential amplifier:-




$$v_x - I_i R_2 + v_i - I_i R_1 = v_x$$

$$v_i = I_i (R_1 + R_2)$$

$$R_i = R_1 + R_2$$

Input Impedance of J.A.

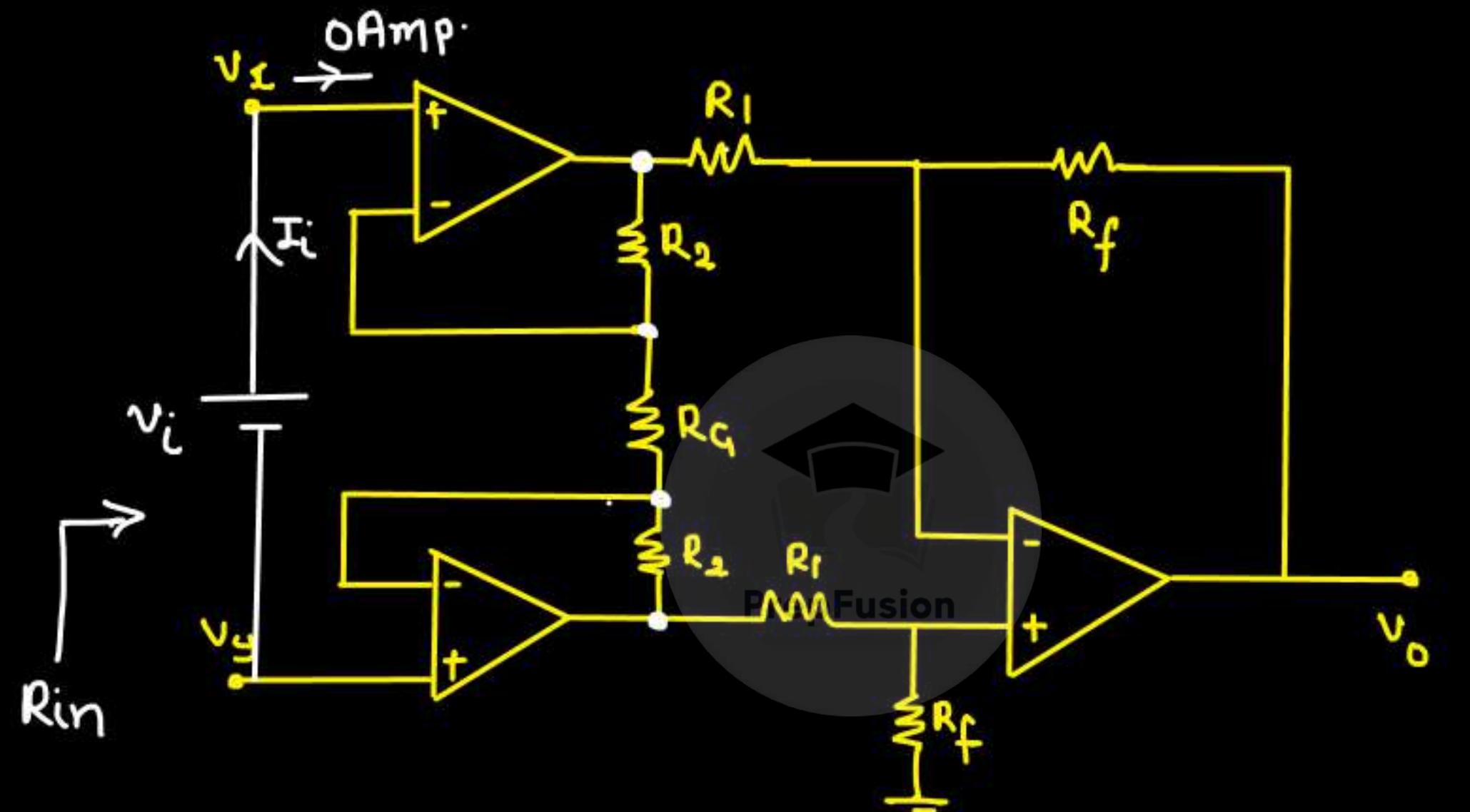

$$R_{in} = \frac{v_i}{I_i} = \frac{v_i}{0} = \infty$$

* Advantages of Instrumentation Amplifier:-

① High gain, High CMRR, High i/p impedance


$$(Gain)_{I\cdot A} = \left[1 + \frac{2R_2}{R_1} \right] \left[\frac{R_f}{R} \right] [V_+ - V_-]$$

$$(Gain)_{D\cdot A} = \frac{R_f}{R} [V_+ - V_-]$$



Advantage of I·A over D·A -

- (i) Higher Gain, Higher CMRR, Higher i/p impedance.
- (ii) More control over gain [By changing less resistor values]


* Use of Instrumentation amplifiers:-

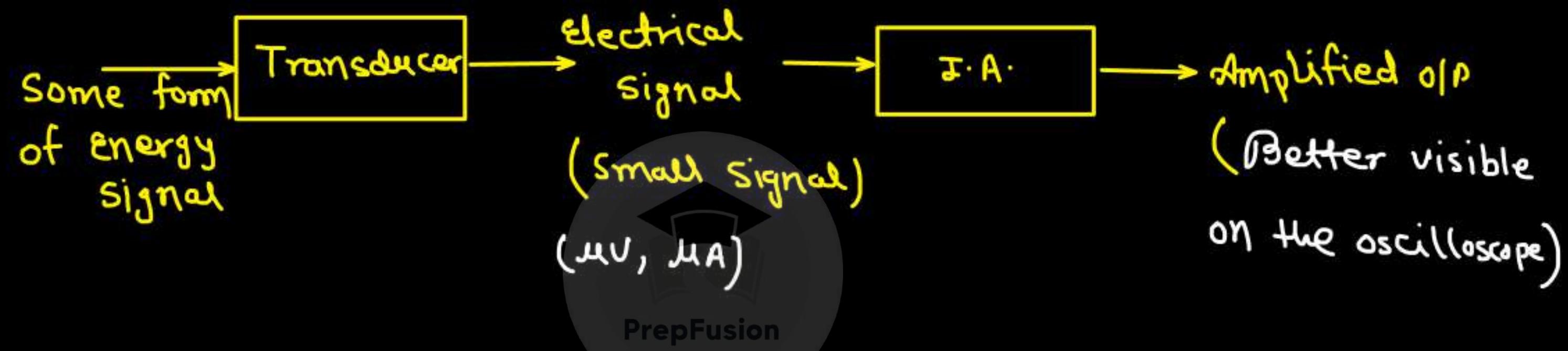

Revision Question :-

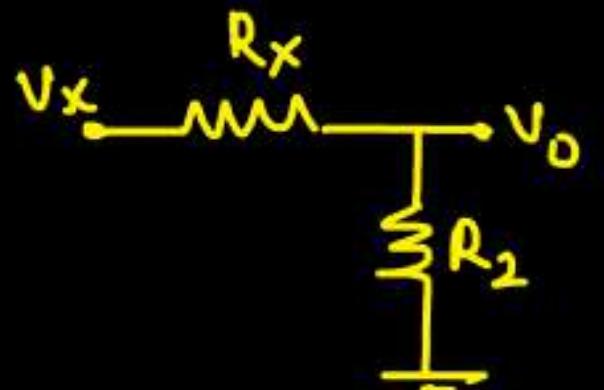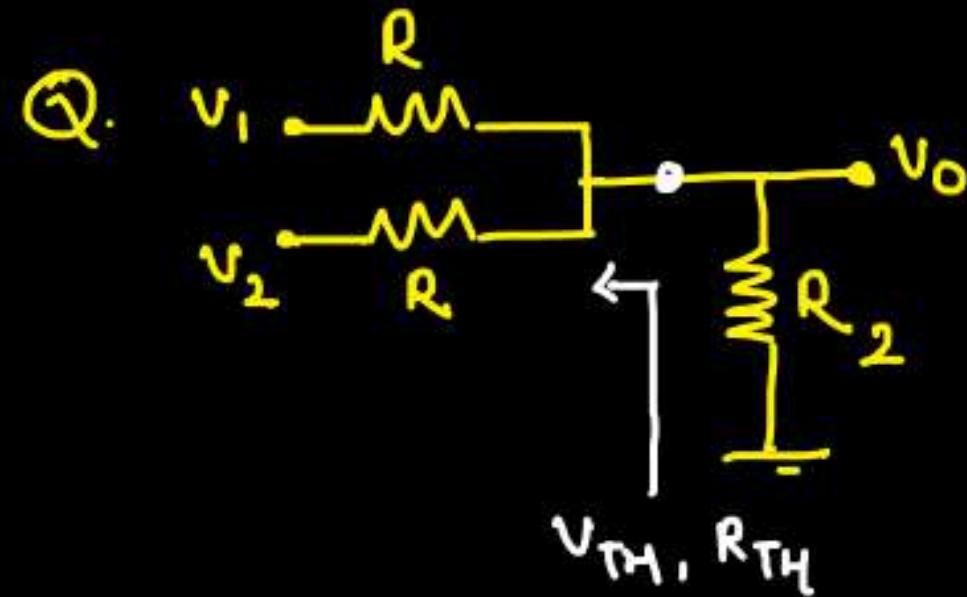


Find V_x and R_x ?

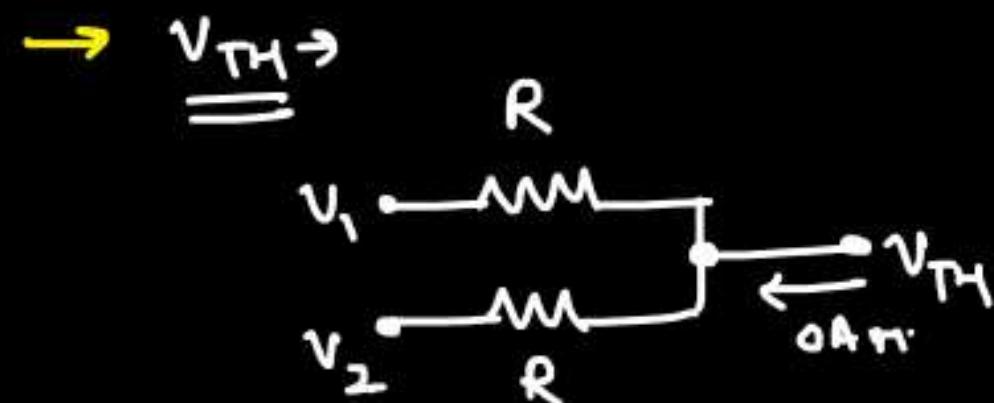



PrepFusion
 $R_{TH} \Rightarrow$
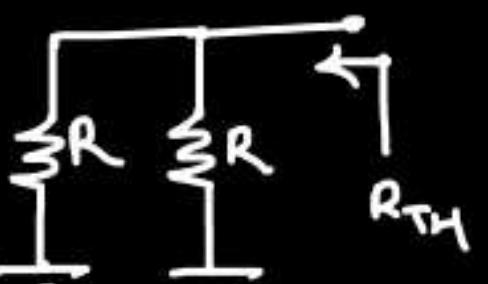
$$V_{TH} = \frac{V_1 R + V_2 R}{R+R} = \frac{V_1 + V_2}{2}$$



$R_{TH} = R_2$

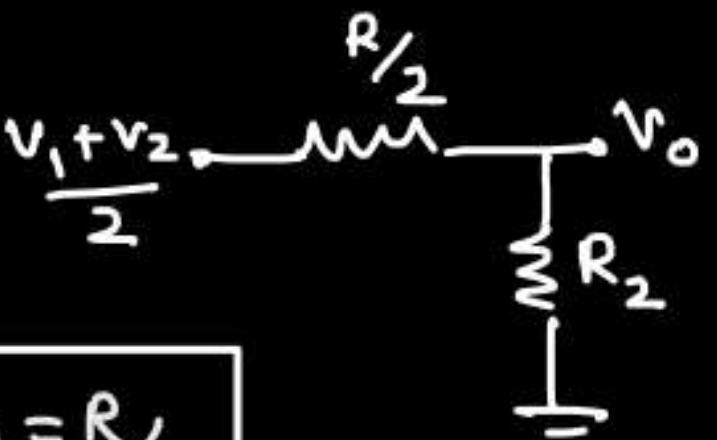

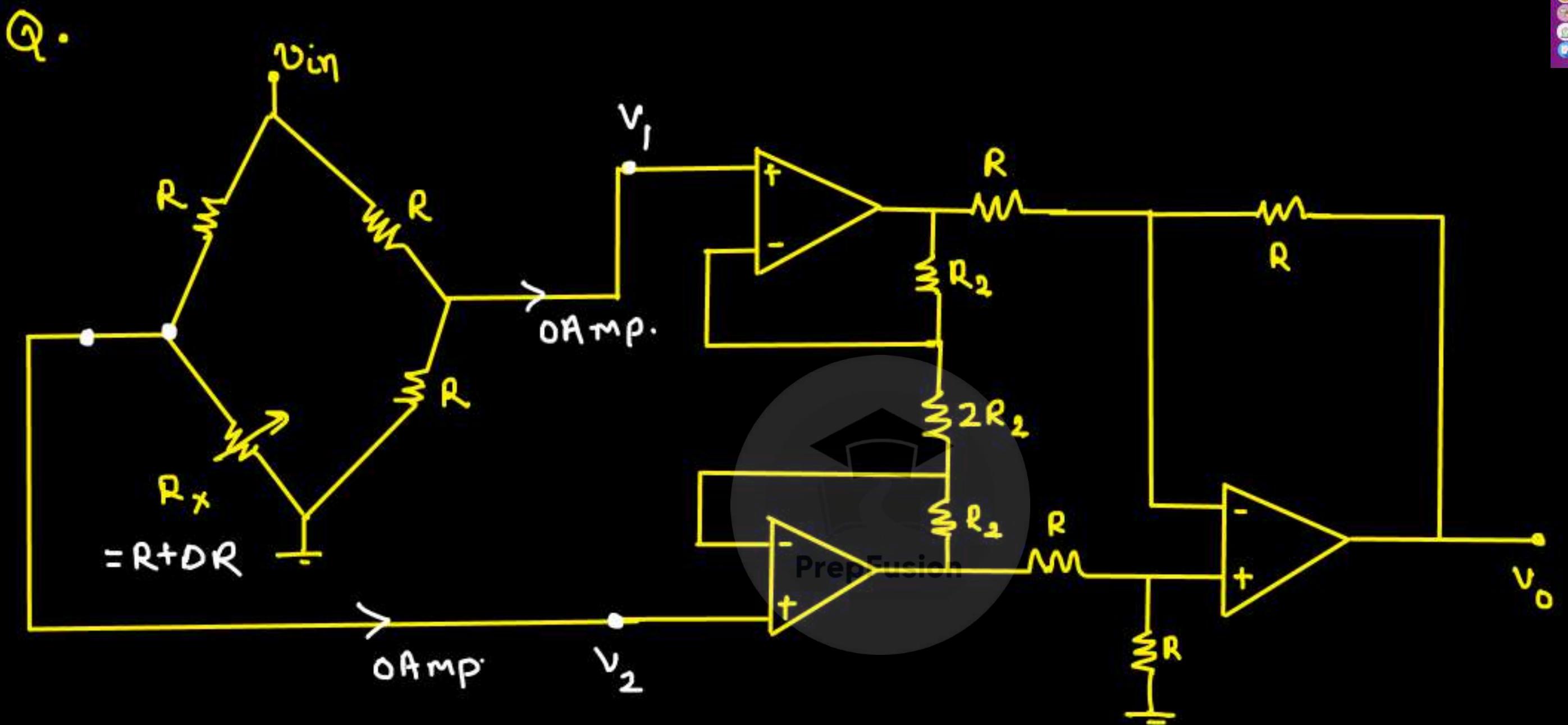


Initially $R_x = R$, but because of Temp. changes, the R_x value becomes $R + \Delta R$. Find V_0 voltage in this case.

$$V_o = \frac{R}{R} \left[1 + \frac{2R_2}{2R_2} \right] [V_2 - V_1]$$

$$V_o = 2 [V_2 - V_1]$$

when $R_x = R$

$$V_1 = V_2 = \frac{V_i}{2}$$

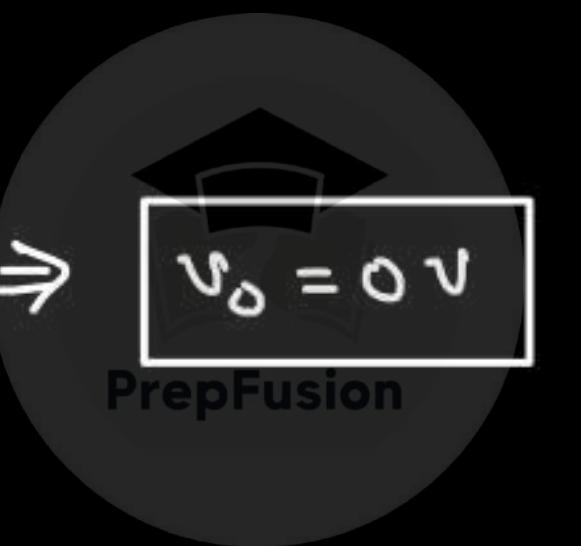

when $R_x = R + DR$

$$V_2 = \frac{R + DR}{R + R + DR} V_i = \frac{R + DR}{2R + DR} V_i$$

$$V_1 = \frac{V_i}{2}$$

$$V_o = 2 [V_2 - V_1]$$

$$= 2 \left[\frac{R + DR}{2R + DR} V_i - \frac{V_i}{2} \right]$$

$$= 2 \left[\frac{2R + 2\Delta R - 2R - DR}{2(2R + DR)} \right] V_i$$

$$V_o = \left[\frac{\Delta R}{2R + DR} \right] V_i$$



$2R \gg \Delta R$

$$V_o = \frac{\Delta R}{2R} V_i$$

O/P voltage \propto change in Resistance

$$V_o \propto \frac{\Delta R}{R}$$

⑤ Voltage to current converter :-

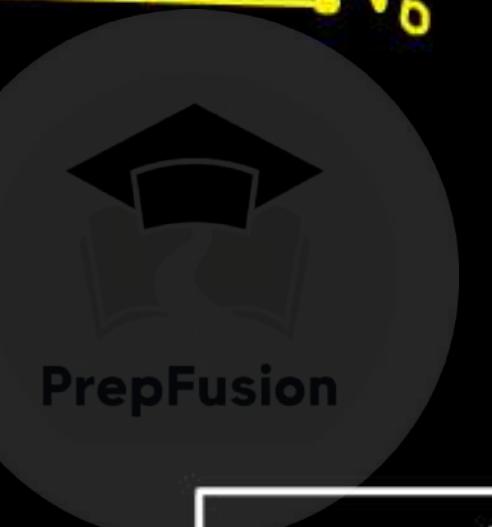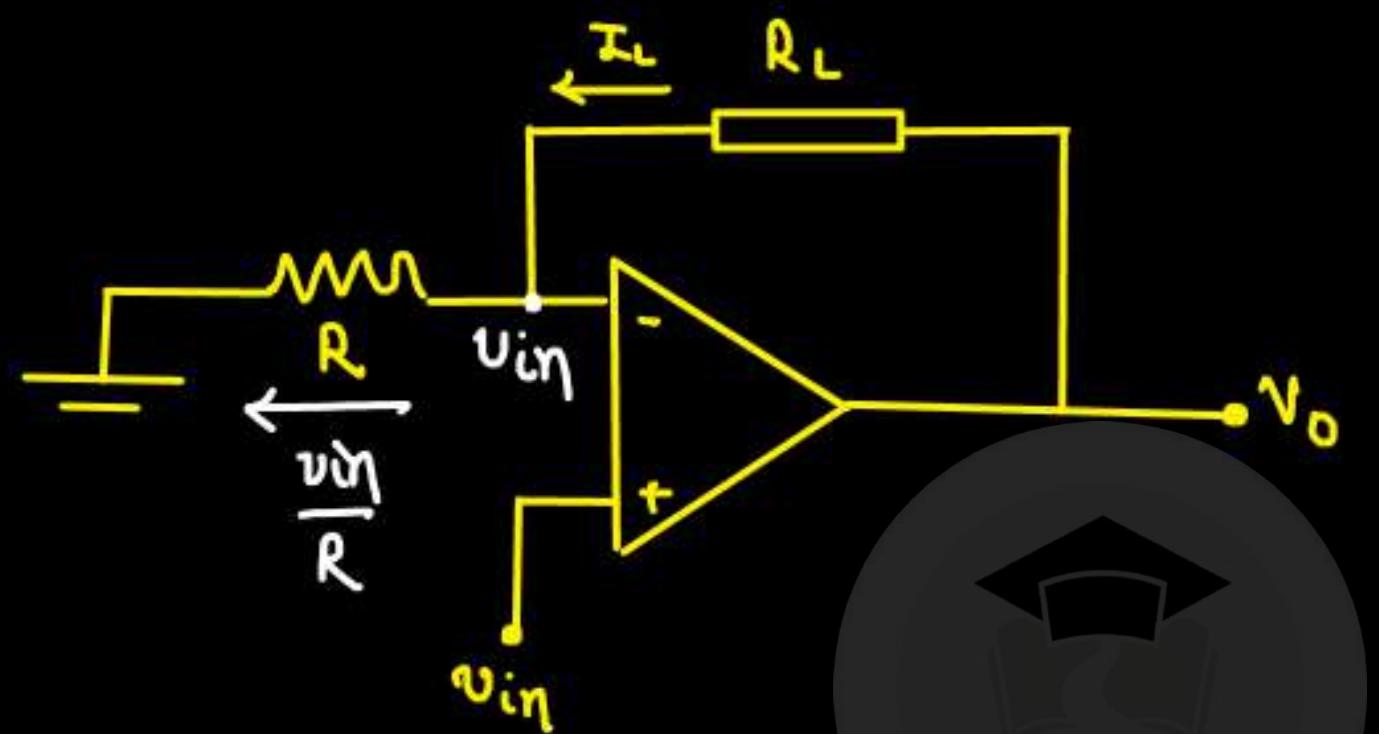


$$\frac{v_{in}}{R} = I_L$$

$$I_L \propto v_{in}$$

$$I_L \neq f(R_L)$$

$$I_L = f(v_{in})$$

⑥ Current to Voltage Converter :-

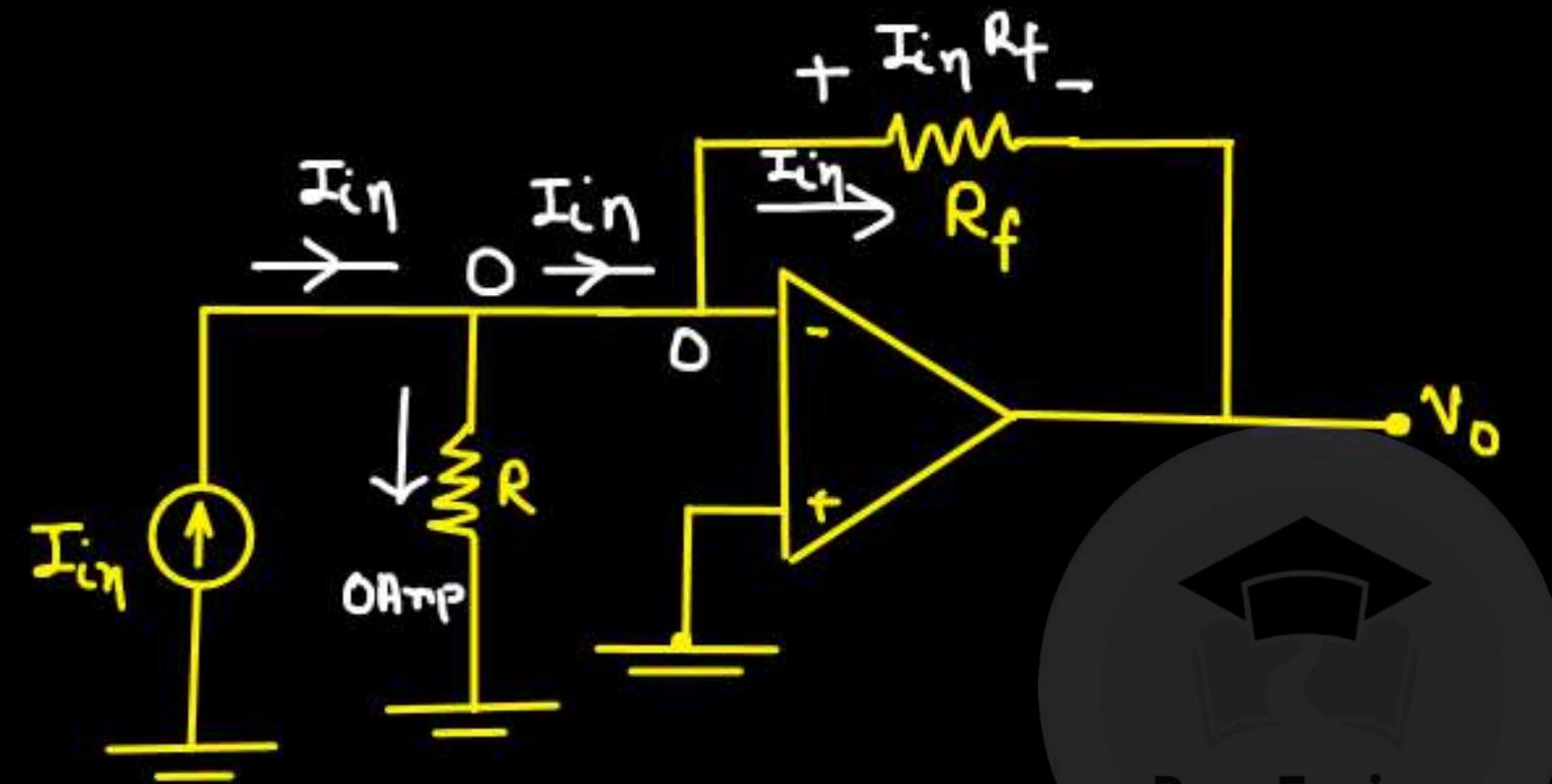


PrepFusion

$$V_o = -I_{in} R_f$$

$$V_o \propto I_{in}$$


Assignment -12

Q. 1

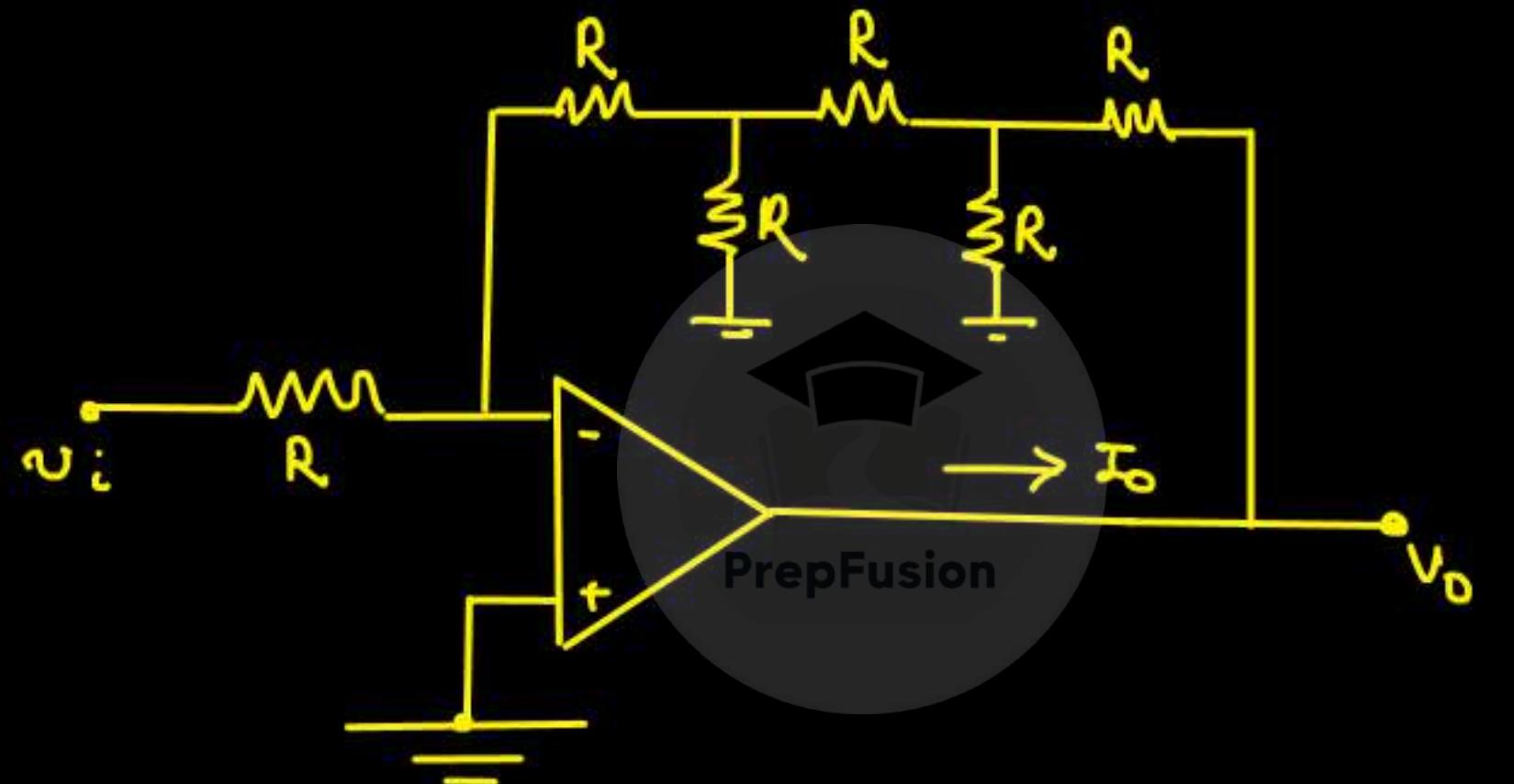


Find the gain $\frac{v_o}{u_i} = ?$


Find I_o ?

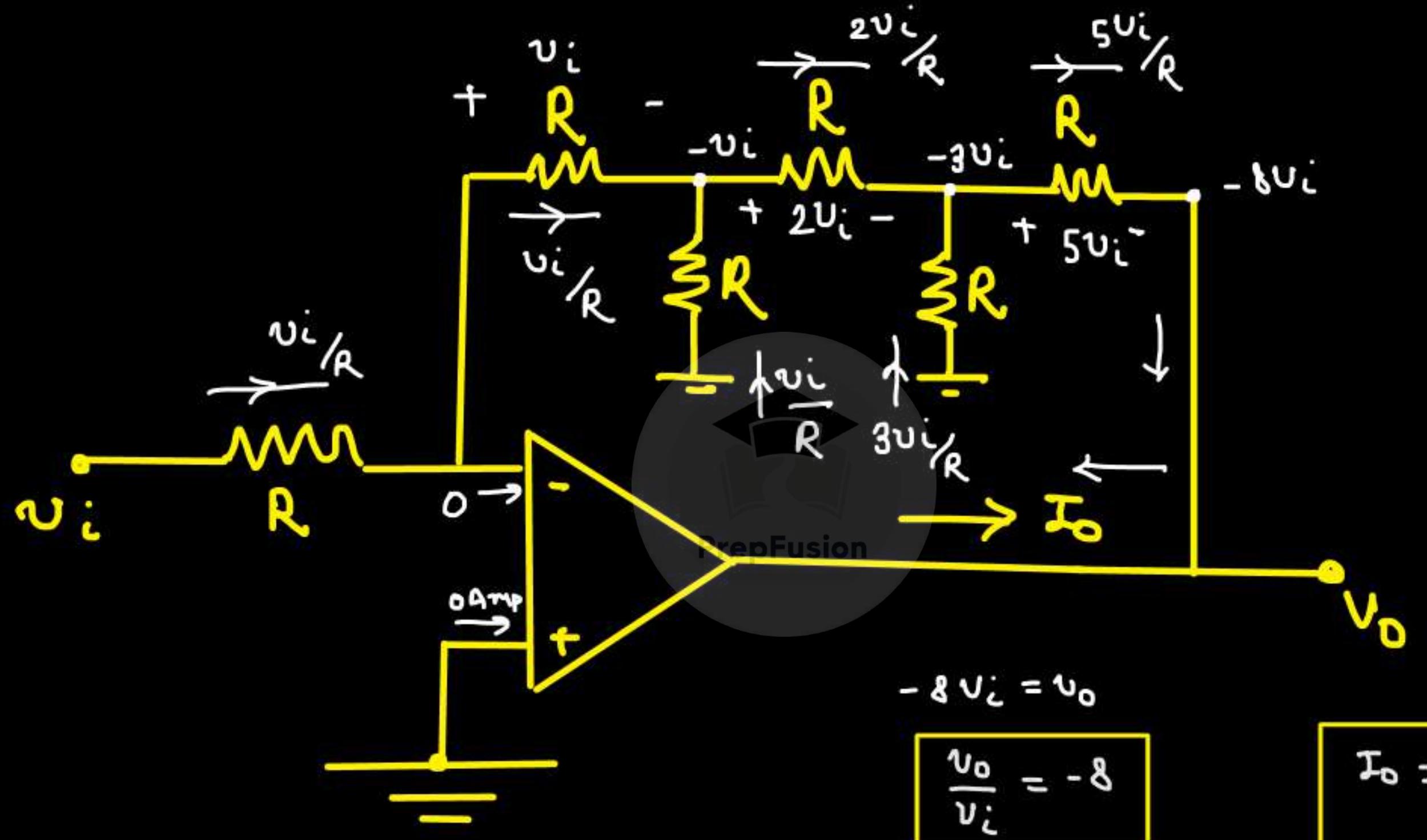

Q. 2

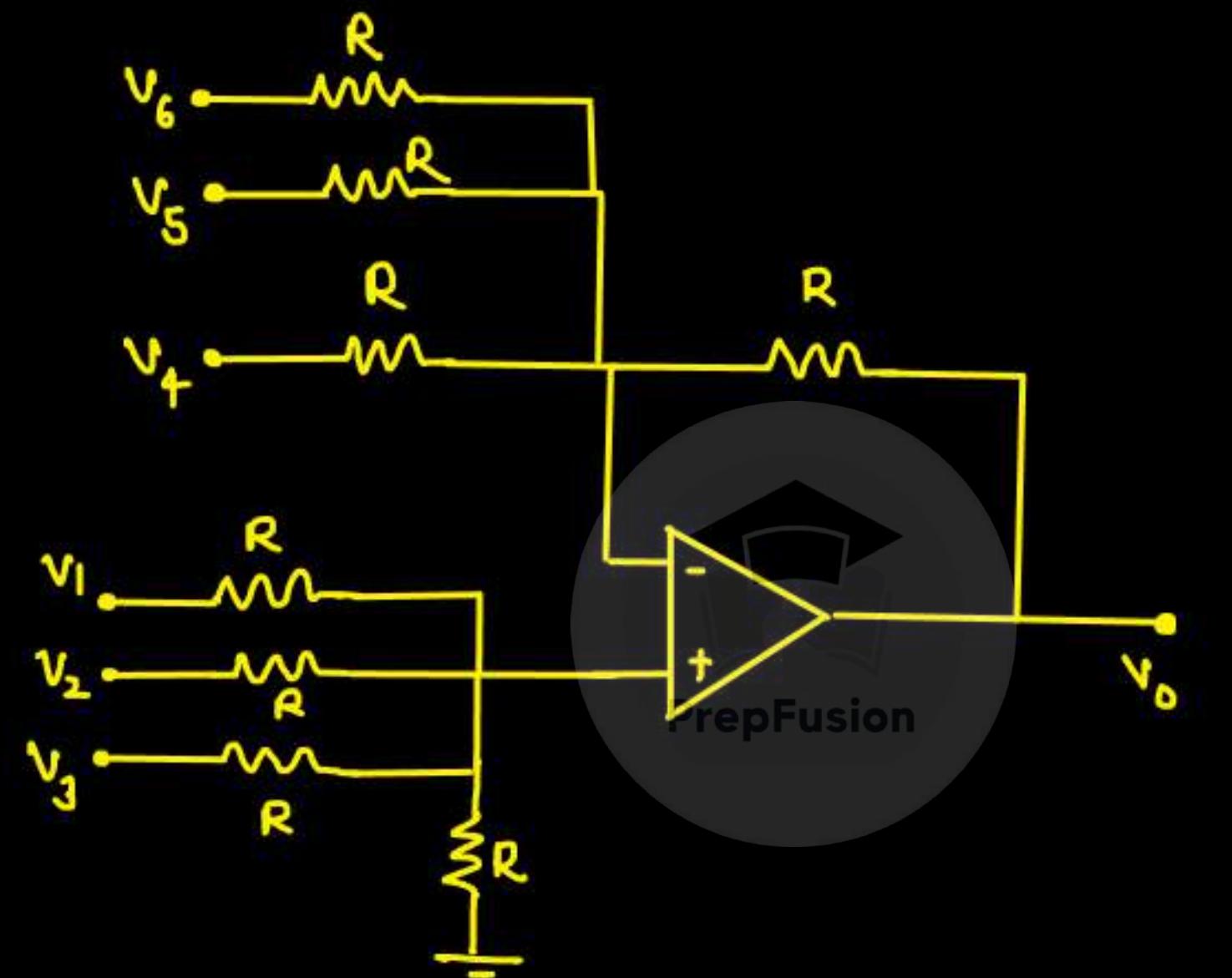


Find $v_o = ?$

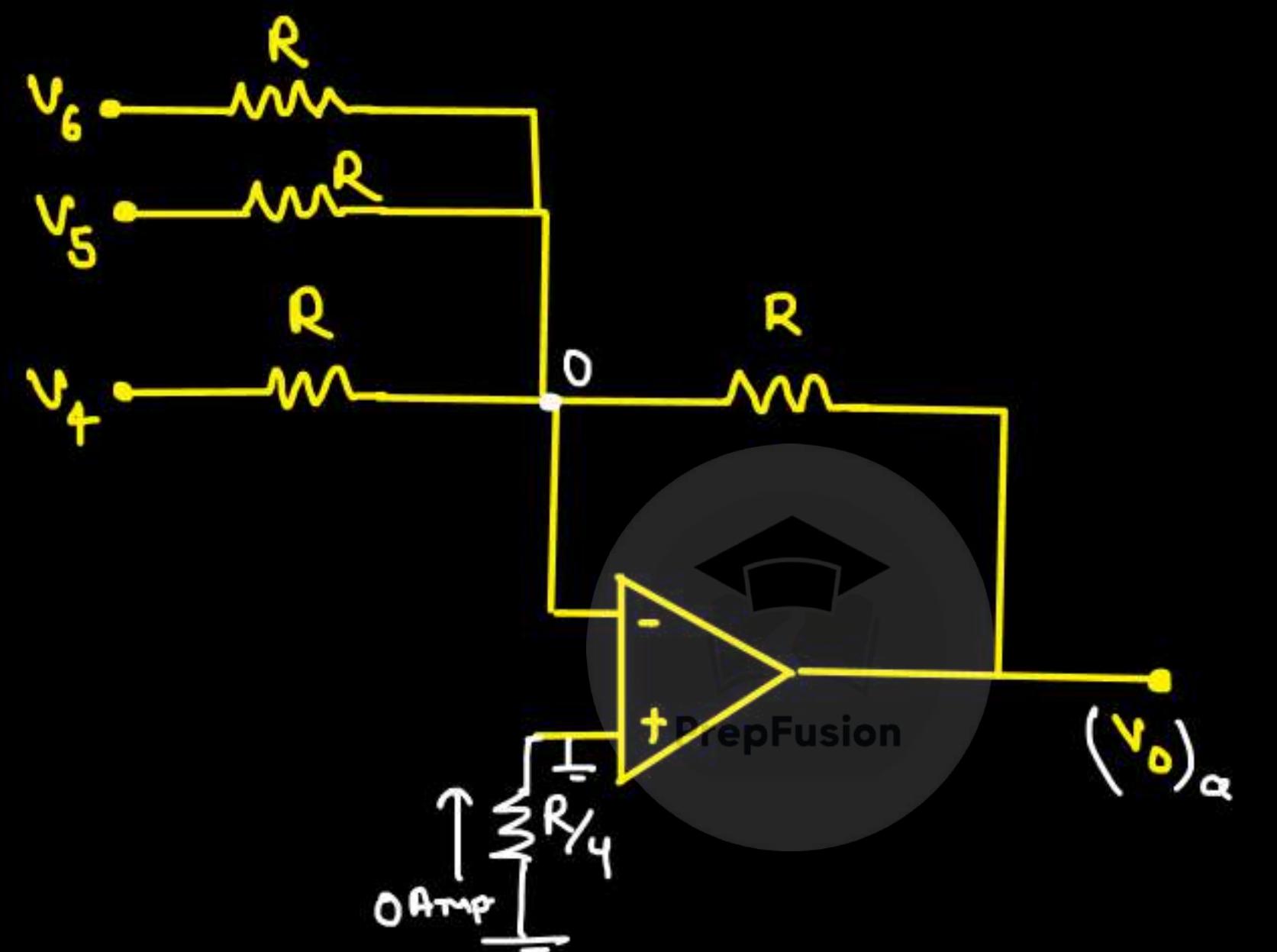

$$-\frac{v_6}{R} - \frac{v_5}{R} - \frac{v_4}{R} - \frac{(v_o)_q}{R} = 0$$

$$(v_o)_q = -(v_4 + v_5 + v_6)$$

— ①

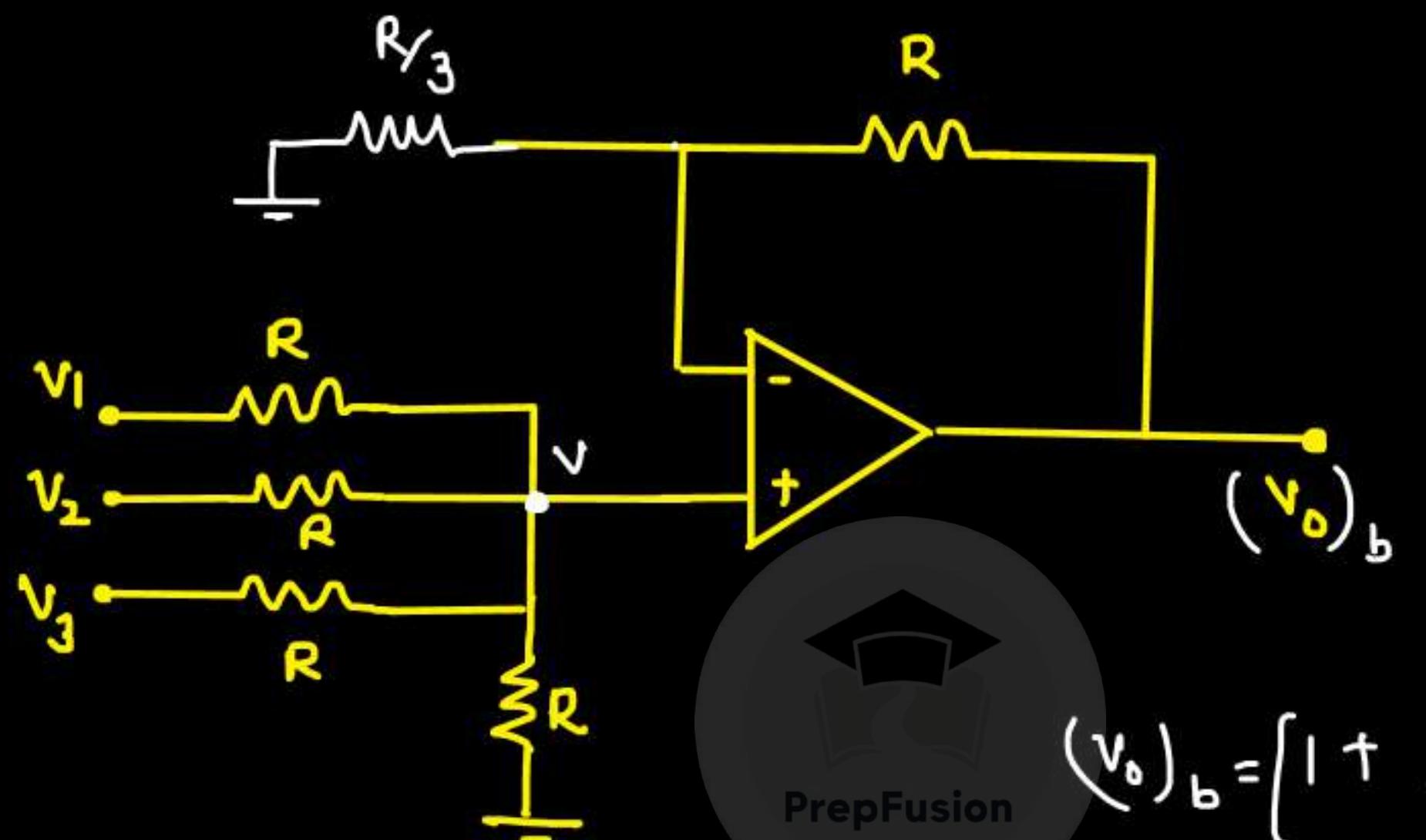

PrepFusion

$$(v_o)_b = \left[1 + \frac{R}{R_{1/3}} \right] v$$

$$(v_o)_b = 4v - \textcircled{2}$$

By eqn $\textcircled{2}$ and $\textcircled{3}$

$$(v_o)_b = v_1 + v_2 + v_3 \quad \text{--- } \textcircled{3}$$

$$\frac{v-v_1}{R} + \frac{v-v_2}{R} + \frac{v-v_3}{R} + \frac{v}{R} = 0$$


$$4v = v_1 + v_2 + v_3 \quad \text{--- } \textcircled{3}$$

$$V_o = (V_o)_a + (V_o)_b$$

$$V_o = V_1 + V_2 + V_3 - V_4 - V_5 - V_6$$



Q.

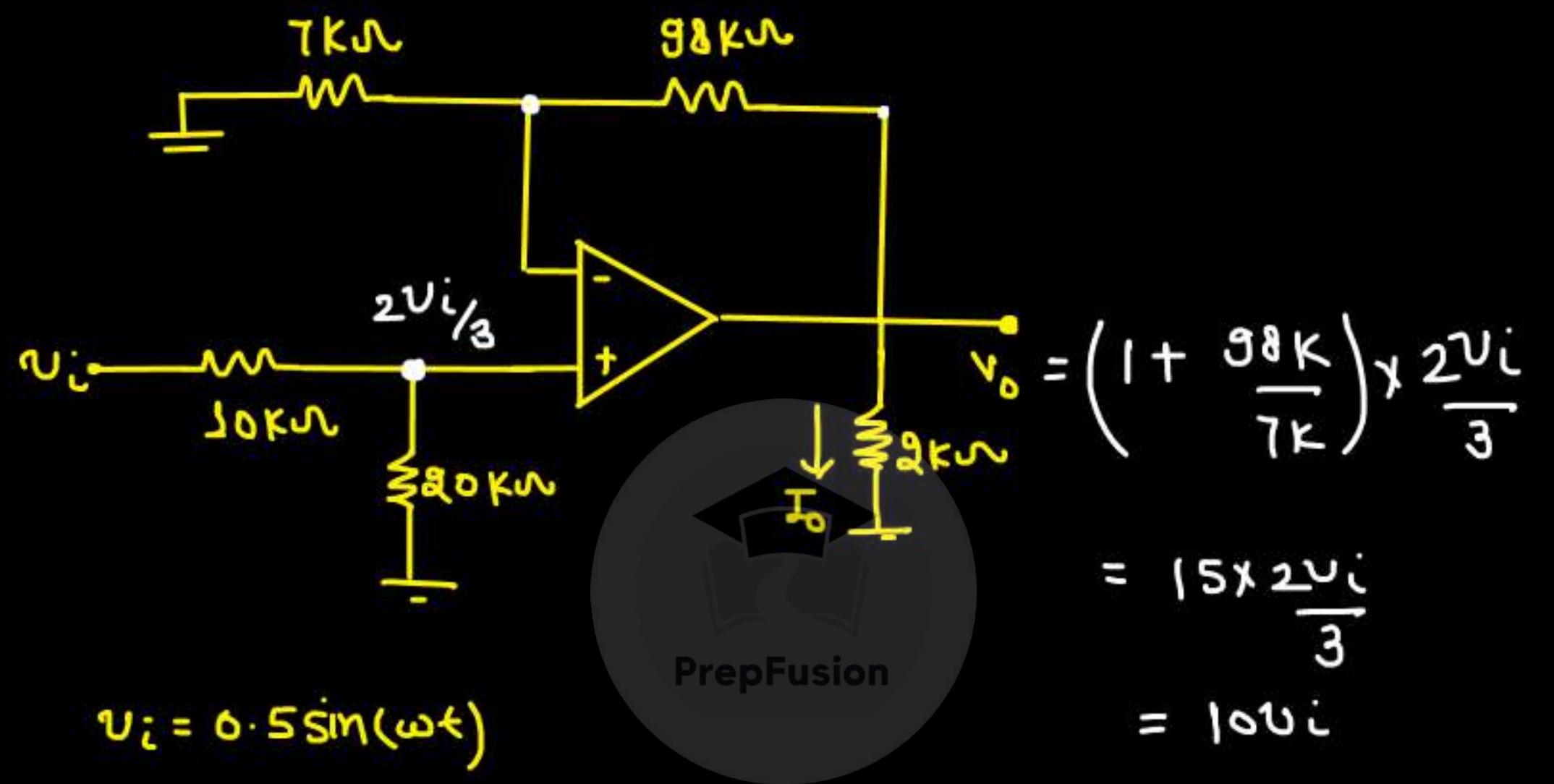


$$v_i = 0.5 \sin(\omega t)$$

Find the maximum amplitude of I_o ?

$$I_o = \frac{v_o}{2k\Omega} = \frac{10v_i}{2k\Omega} = \frac{5 \sin(\omega t)}{2k\Omega} = 2.5 \sin \omega t \text{ mA}$$

$$(I_o)_{\max} = 2.5 \text{ mA}$$

Q.

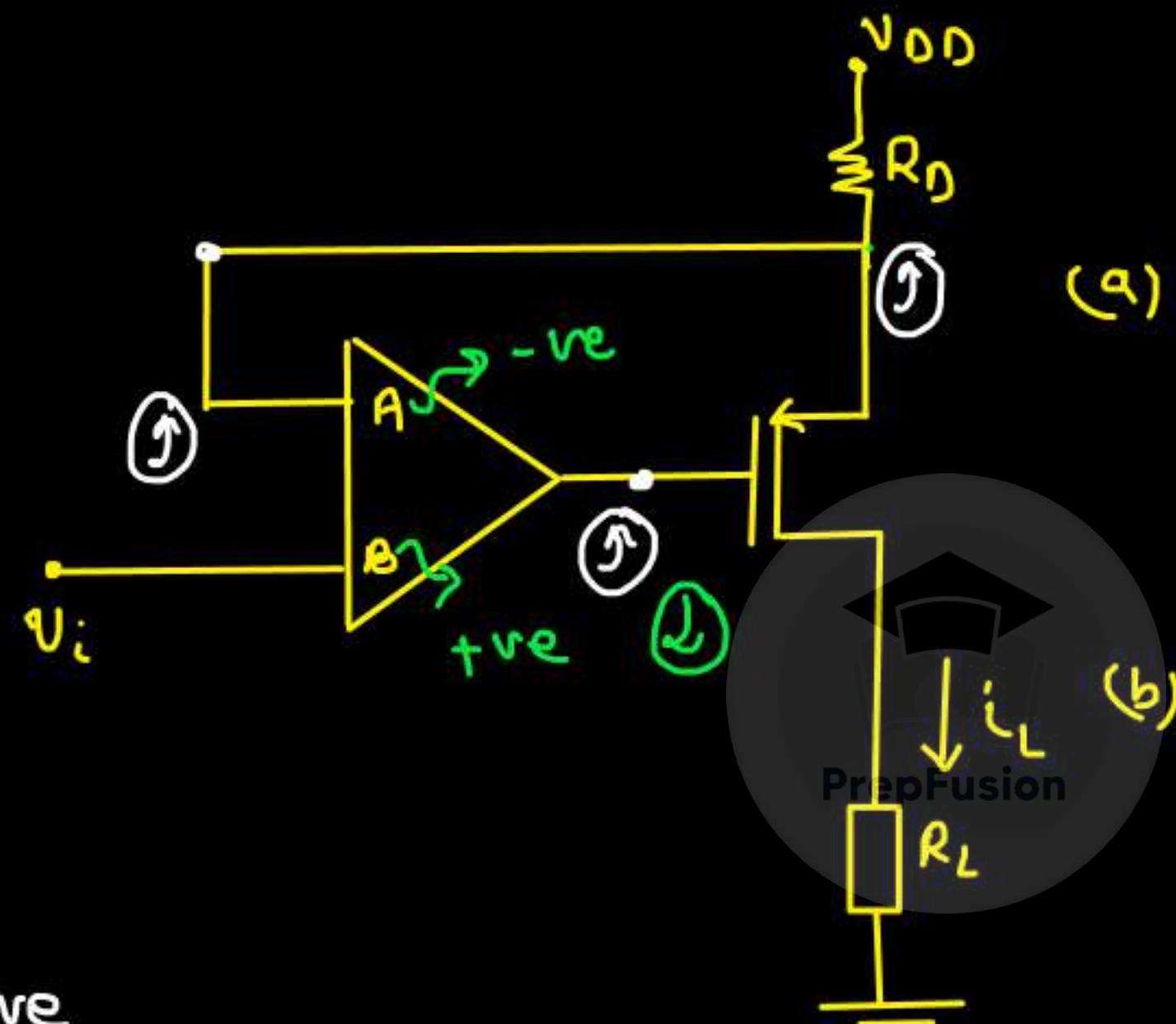



$$A = -ve$$

$$B = +ve$$

(a) Find the sign of A and B such that op-amp is working in Negative feedback.

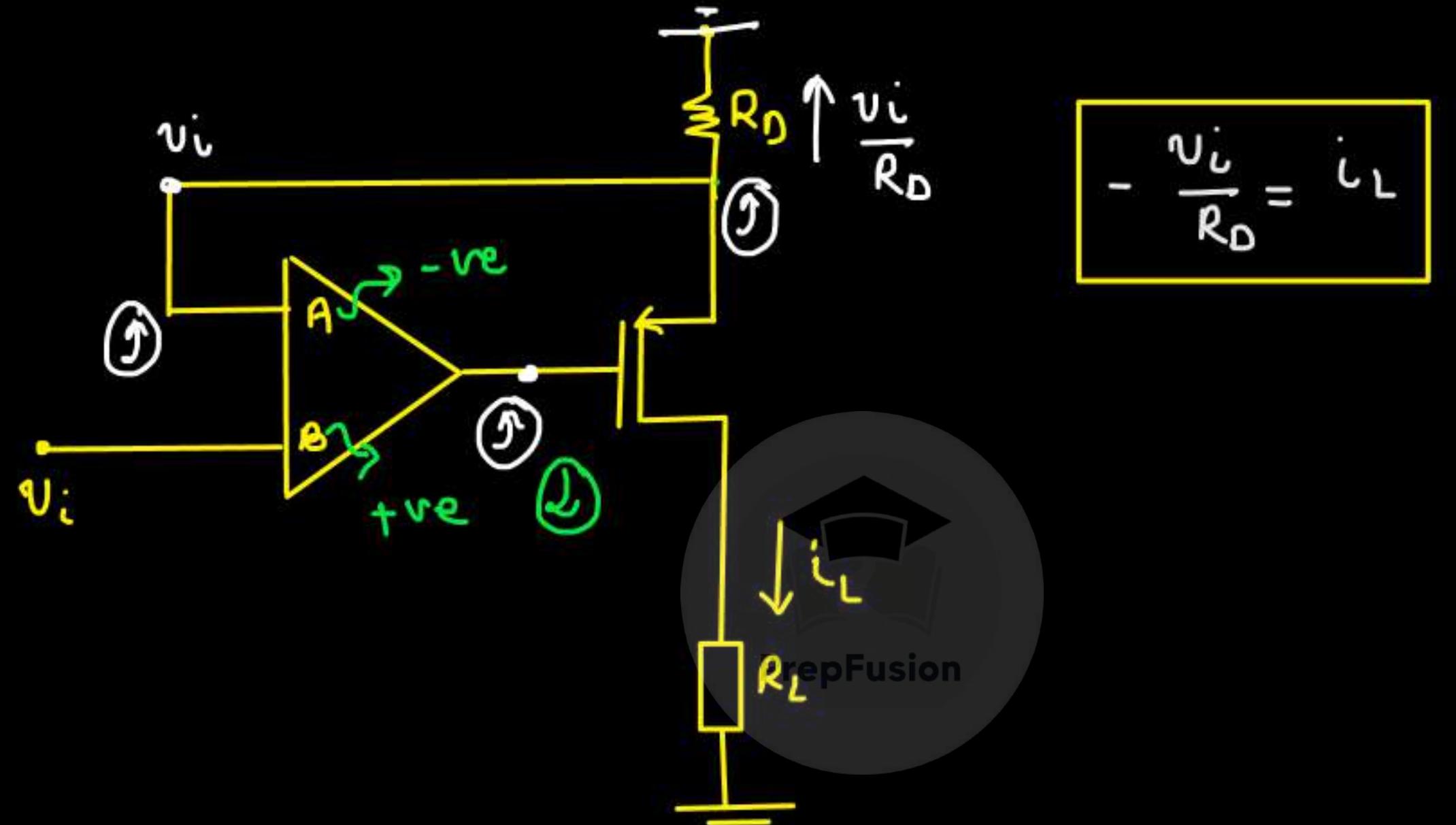(b) Find small signal current i_L in terms of small signal voltage u_i .



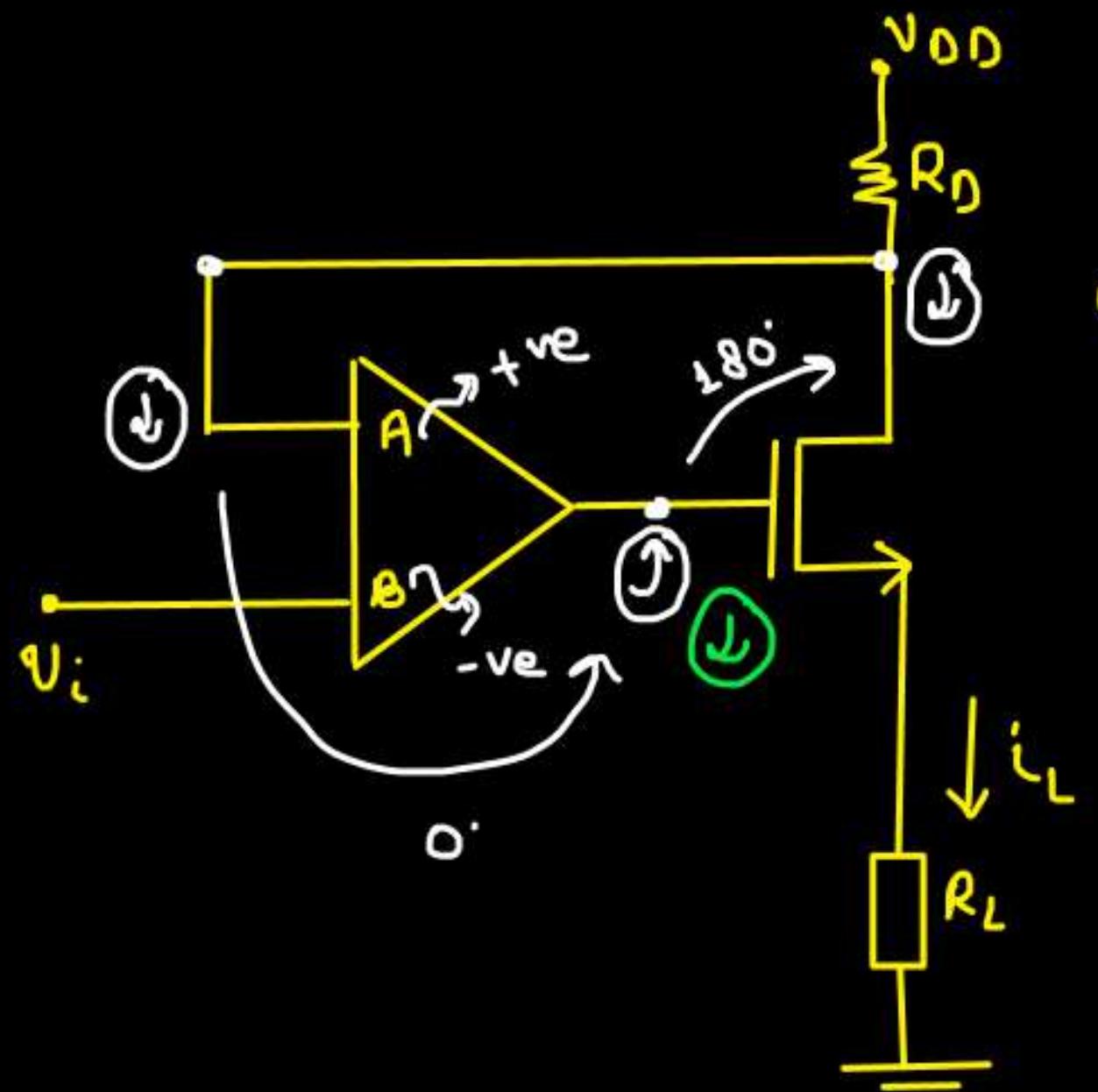


(a) $A = +ve$, $B = -ve$

$$(b) -\frac{U_i}{R_D} = i_L$$

(a) Find the sign of A and B such that op-amp is working in negative feedback.

(b) Find small signal current i_L in terms of small signal voltage U_i .


MSQ
Q.

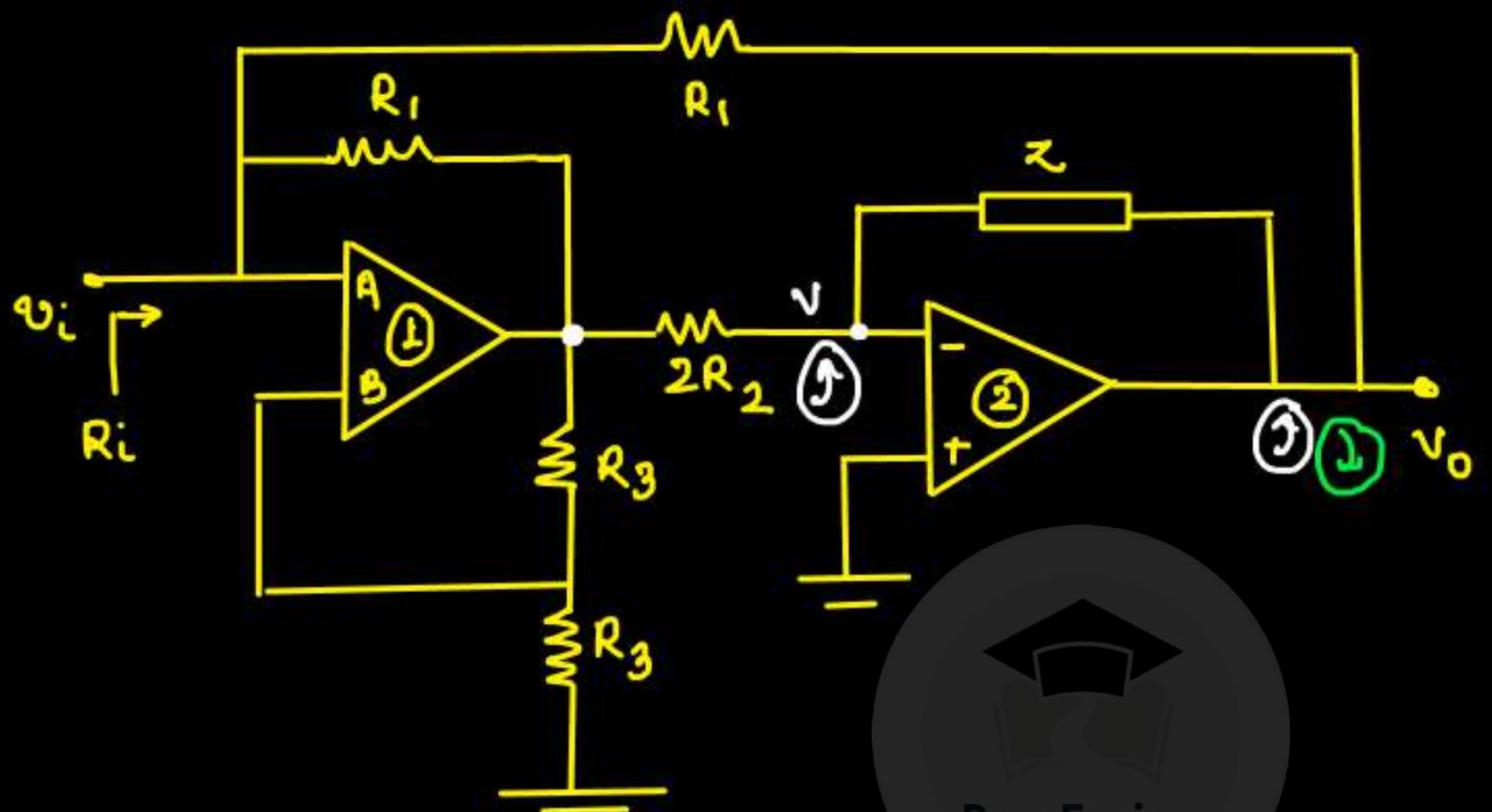

PrepFusion

Which of the following is/are correct?

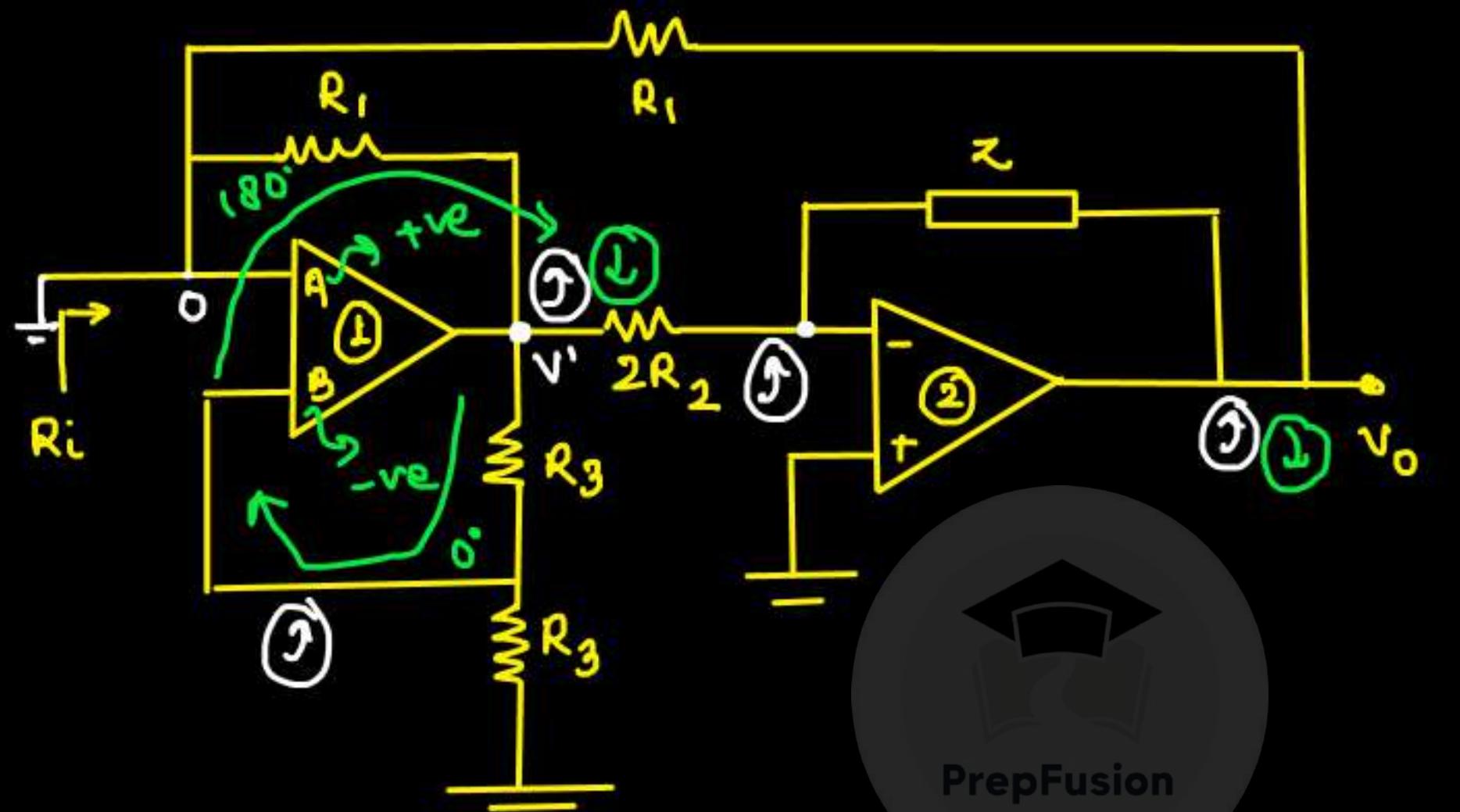- (a) For both of the OP-amps to work in Neg. f/b ; A = +ve , B = -ve
- (b) For both of the OP-amps to work in Neg. f/b ; A = -ve , B = +ve
- (c) Considering negative f/b, R_i acts as inductor if Z = inductor
- (d) Considering negative f/b, R_i acts as capacitor if Z = capacitor




PrepFusion

Node A $\rightarrow 0$

Node B $\rightarrow \text{?}$ {if v' increases}

$$B = -ve, \quad A = +ve$$

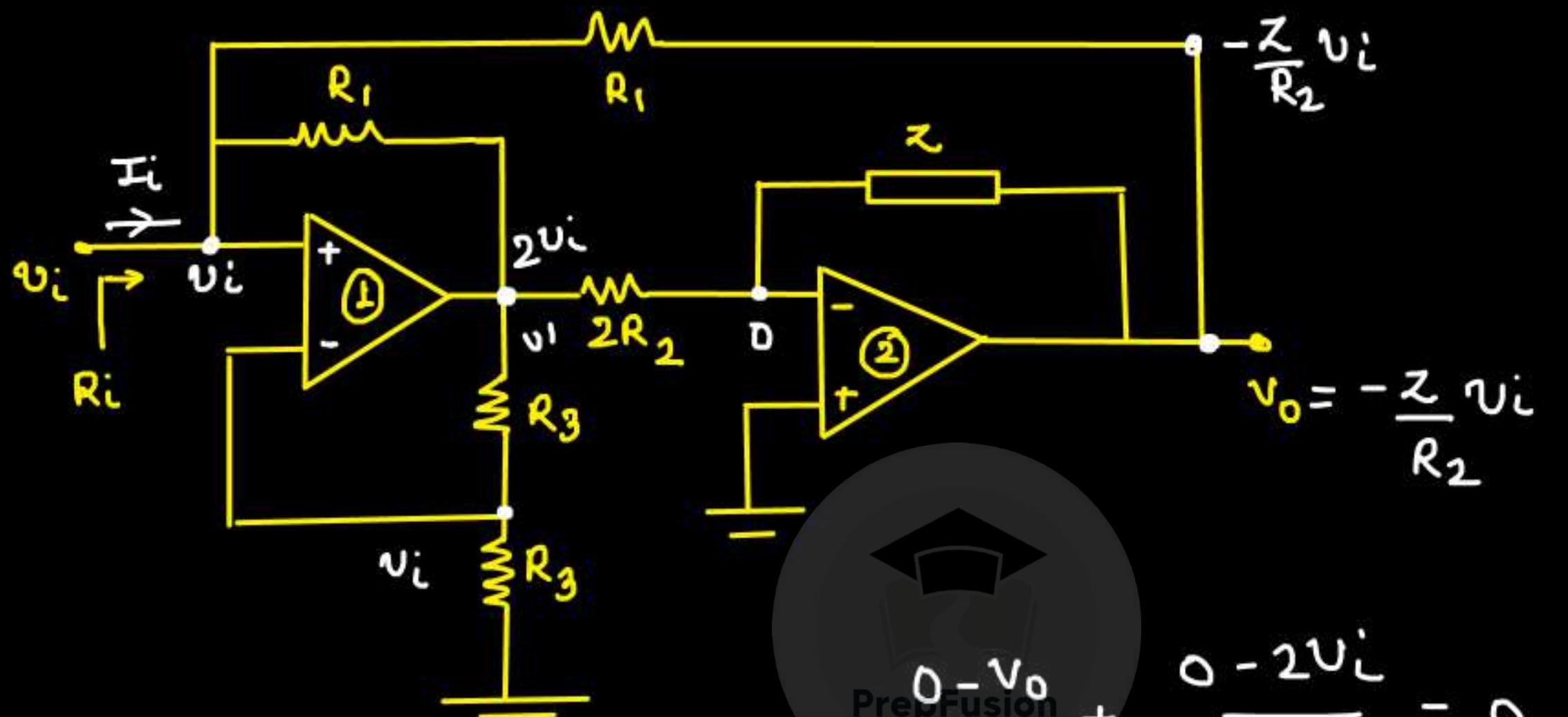

PrepFusion

$$\frac{0 - v_o}{z} + \frac{0 - 2v_L}{2R_2} = 0$$

$$\frac{v_i - 2v_L}{R_1} + \frac{v_i + \frac{z}{R_2} v_L}{R_1} = I_i$$

$$v_o = -\frac{z}{R_2} v_L \quad \text{--- (1)}$$

$$-v_i + v_i + \frac{z}{R_2} v_L = I_i R_1 \Rightarrow$$

$$\frac{v_i}{I_i} = \frac{R_1 R_2}{z}$$

$$R_i = \frac{R_1 R_2}{z}$$

$$R_i = \frac{R_1 R_2}{Z}$$

$Z \rightarrow$ Inductor ; $Z = j\omega L$


$$R_i = \frac{R_1 R_2}{j\omega L} = -j \frac{R_1 R_2}{\omega L}$$

if $Z \rightarrow$ Inductor $\Rightarrow R_i \rightarrow$ capacitor

if $Z \rightarrow$ capacitor ; $Z = \frac{1}{j\omega C}$


$$R_i = \frac{R_1 R_2}{\frac{1}{j\omega C}} = j\omega C R_1 R_2 \rightarrow \text{Inductor}$$

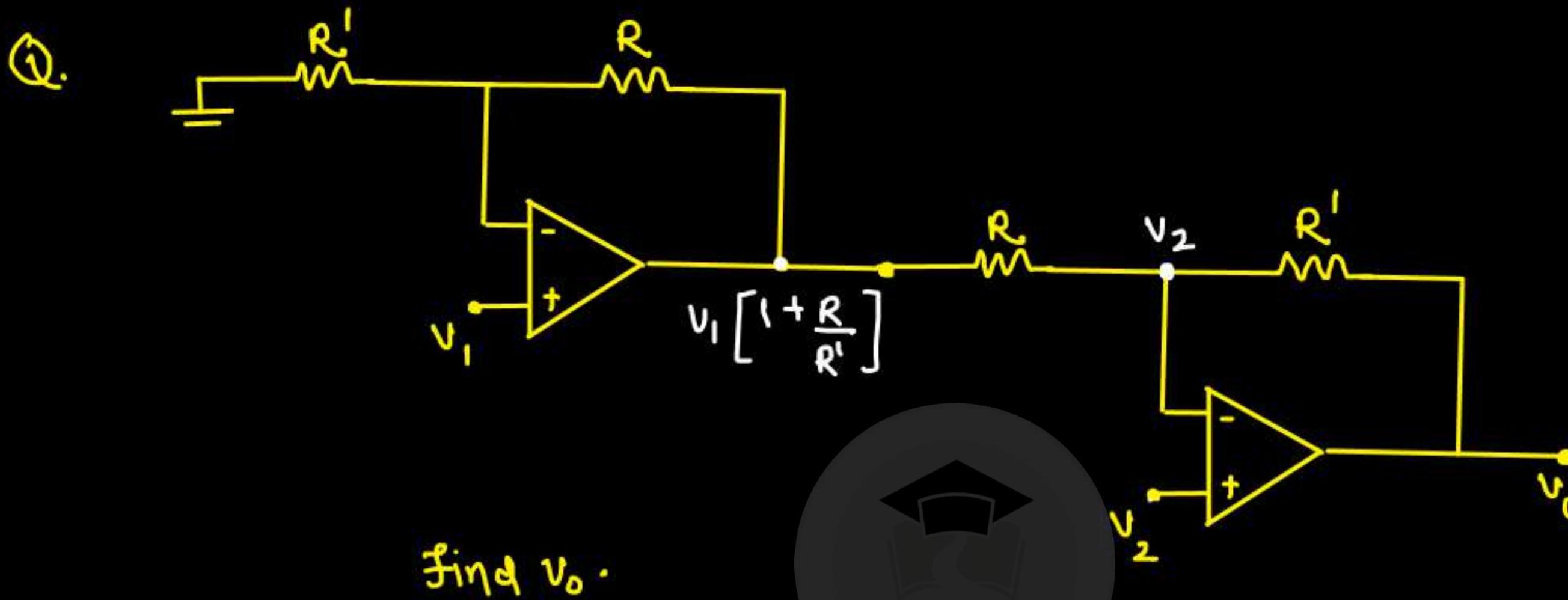if $Z \rightarrow$ capacitor $\Rightarrow R_i \rightarrow$ Inductor



find v_0 .



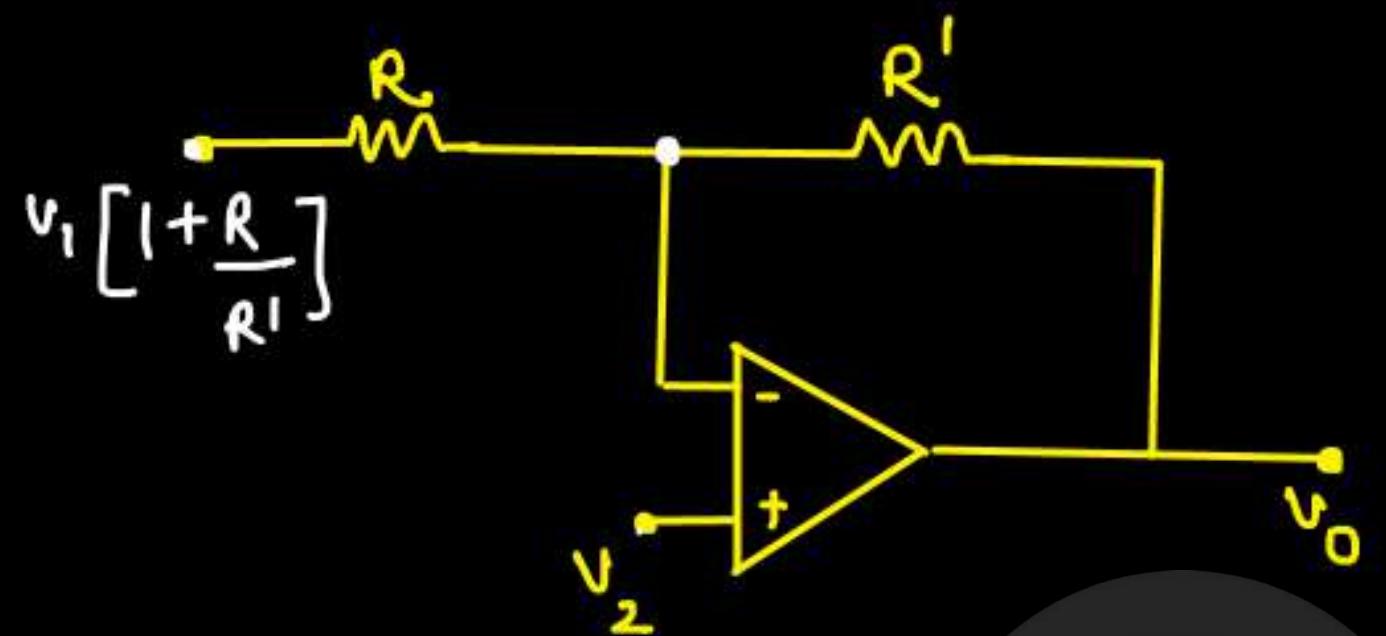

$$v_o = \left[1 + \frac{R'}{R}\right] v_2 - \frac{R'}{R} \left[1 + \frac{R}{R'}\right] v_1$$




$$= v_2 + \frac{R'}{R} v_2 - \frac{R'}{R} v_1 - v_1$$

$$= (v_2 - v_1) + \frac{R'}{R} (v_2 - v_1)$$

$$v_o = \left(1 + \frac{R'}{R}\right) (v_2 - v_1)$$

Q.


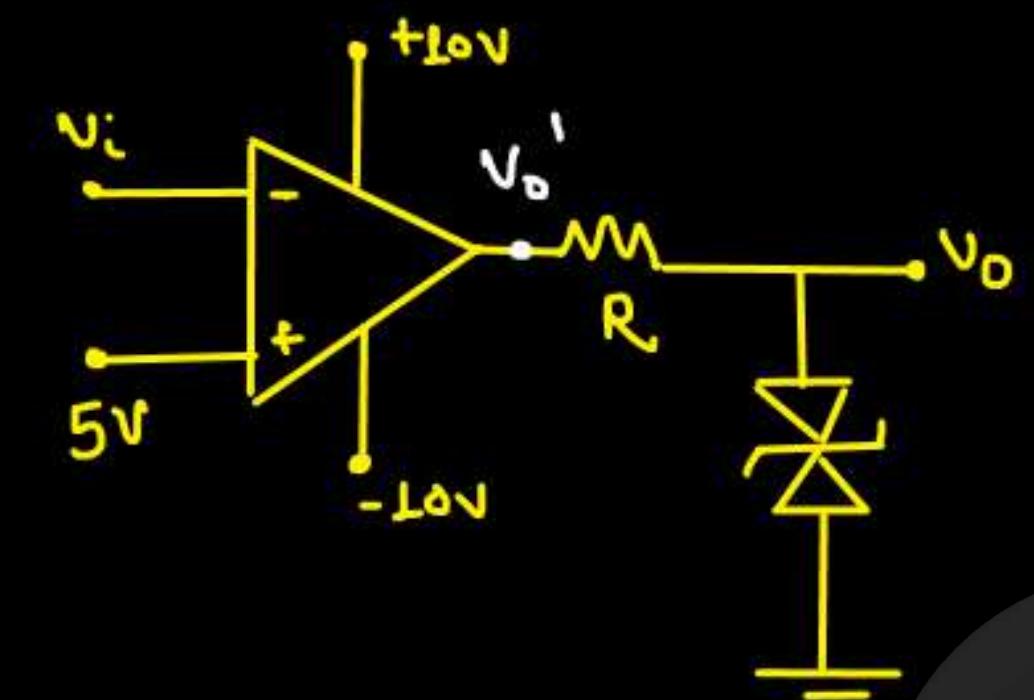


For the zener,

$$V_{ON} = 0.7V, V_Z = 6.3V$$



Draw Transfer characteristic V_o v/s v_i ?
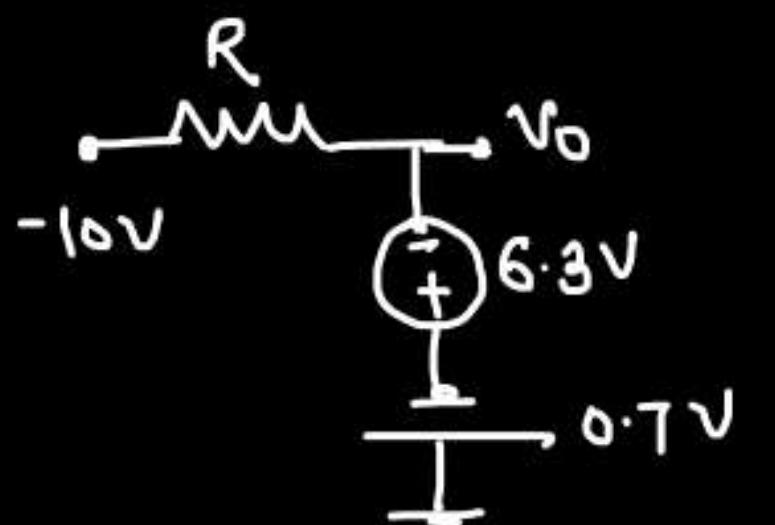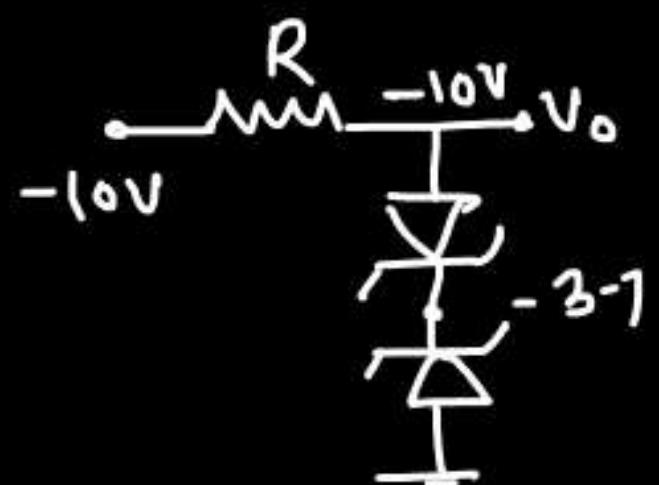
$$\rightarrow v_i > 5V \Rightarrow v_i = -10V$$




$$v_i > 5V \Rightarrow V_o = -7V$$

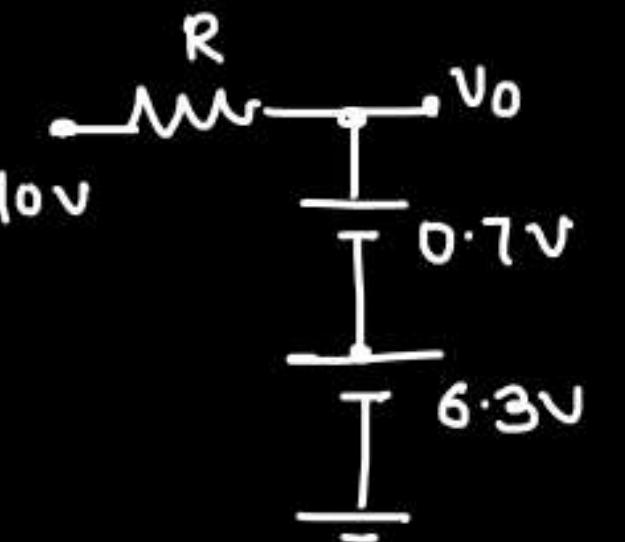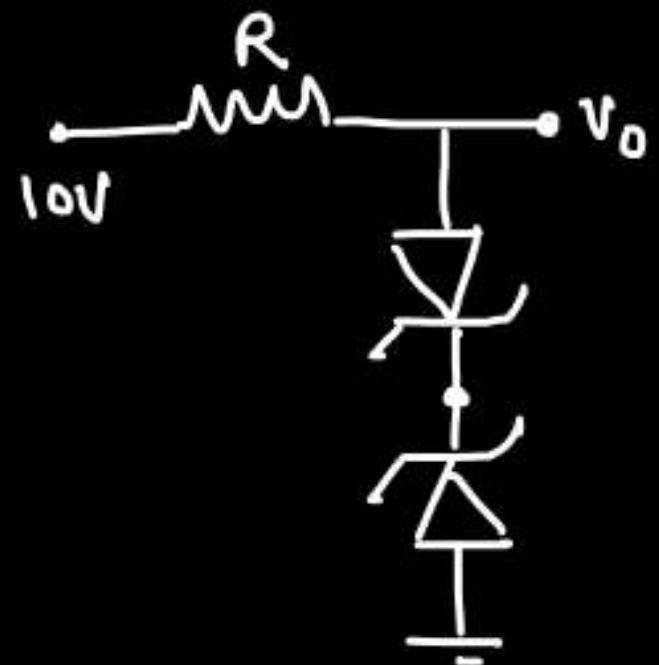
$$V_L < 5\text{v} \Rightarrow V_0' = +10\text{v}$$



PrepFusion

$$V_0 = 7\text{v}$$

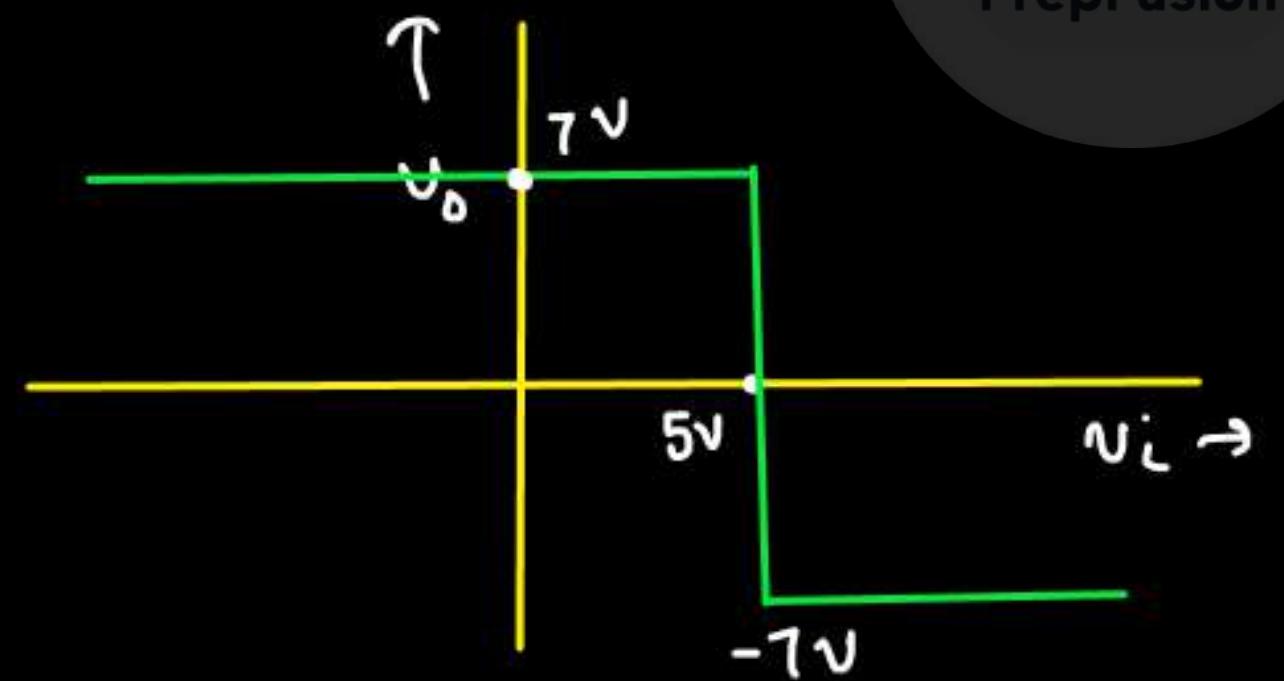

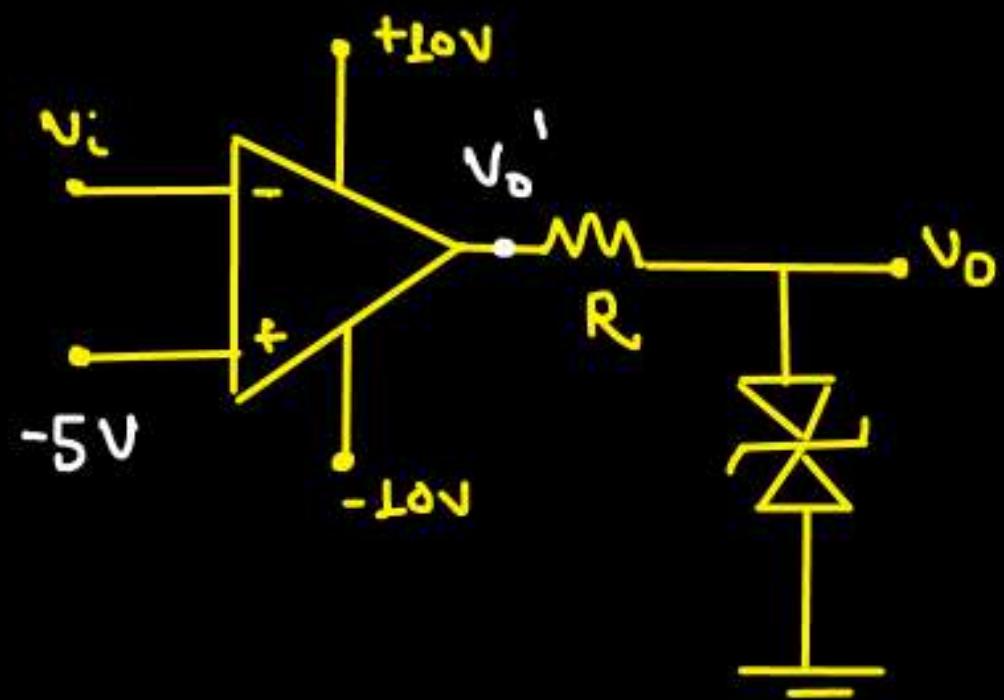

For the zener,

$$V_{ON} = 0.7V, V_Z = 6.3V$$

Draw Transfer characteristics V_o v/s v_i ?

PrepFusion

$$\rightarrow V_i > -5V \Rightarrow V_o' = -10V$$




$$V_o = -7V$$

$$V_i < -5V \Rightarrow V_o' = 10V$$





$$V_o = +7V$$

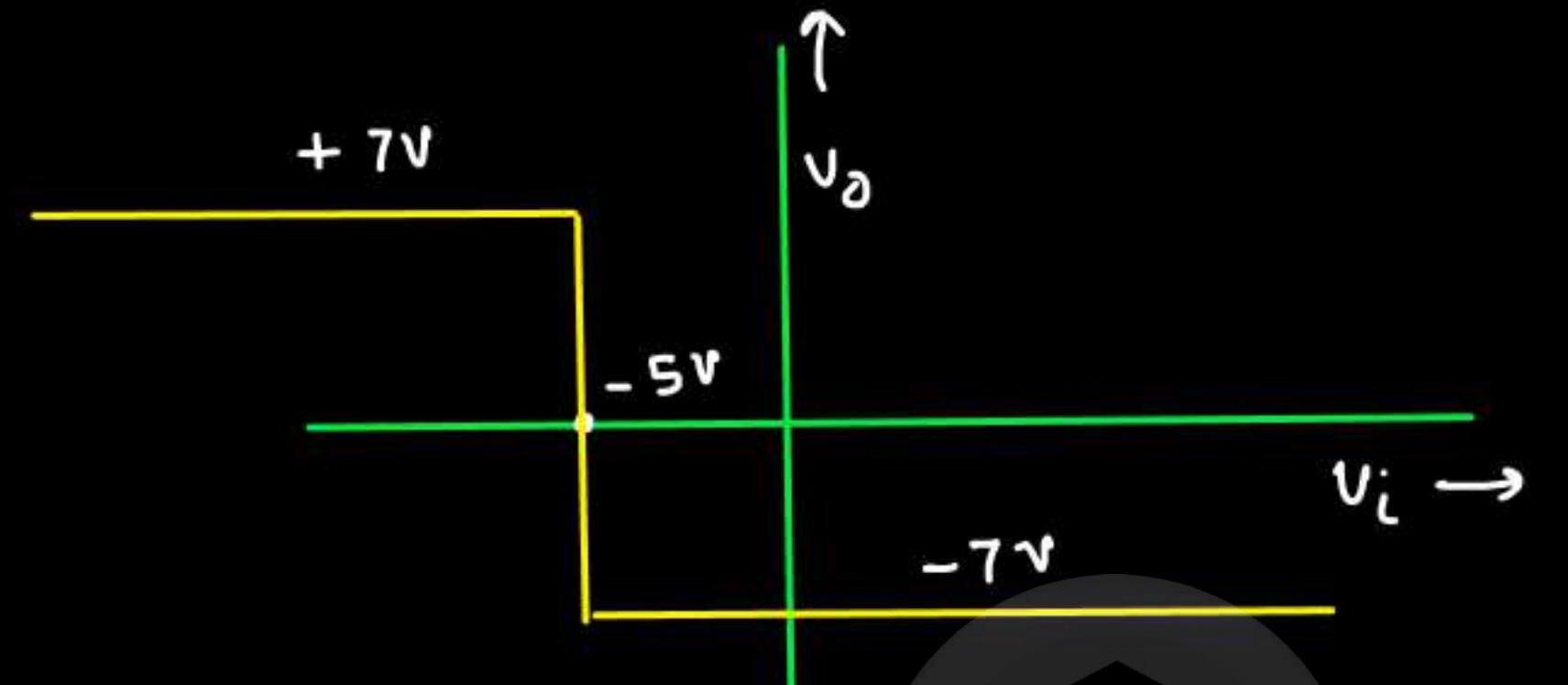

* Non-Linear Applications of OP-Amp:-

① Anti-log | exponential Amplifiers:-

$$\Rightarrow v_D = v_L$$

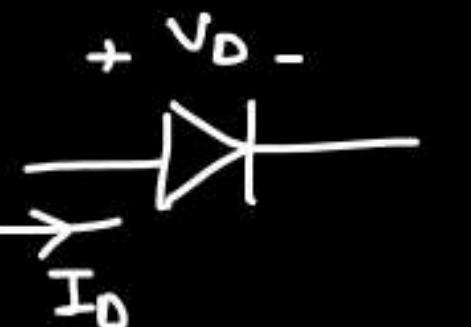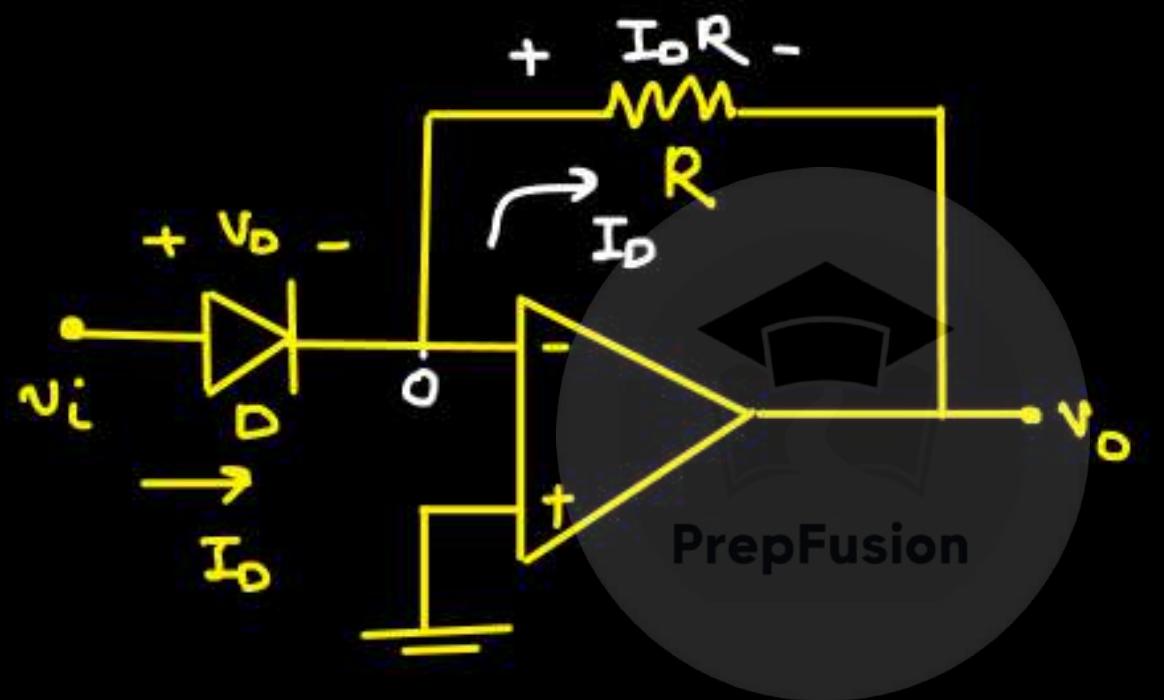

Considering, diode turns

ON for $v_D > 0$


$$I_D = I_s e^{v_D/nV_T}$$

$$\begin{aligned} v_O &= -I_D R \\ &= -I_s e^{v_D/nV_T} \times R \end{aligned}$$

$$v_O = -I_s R e^{v_D/nV_T}$$

$$\Rightarrow v_O \propto e^{v_D/nV_T}$$

② Logarithmic amplifier:-

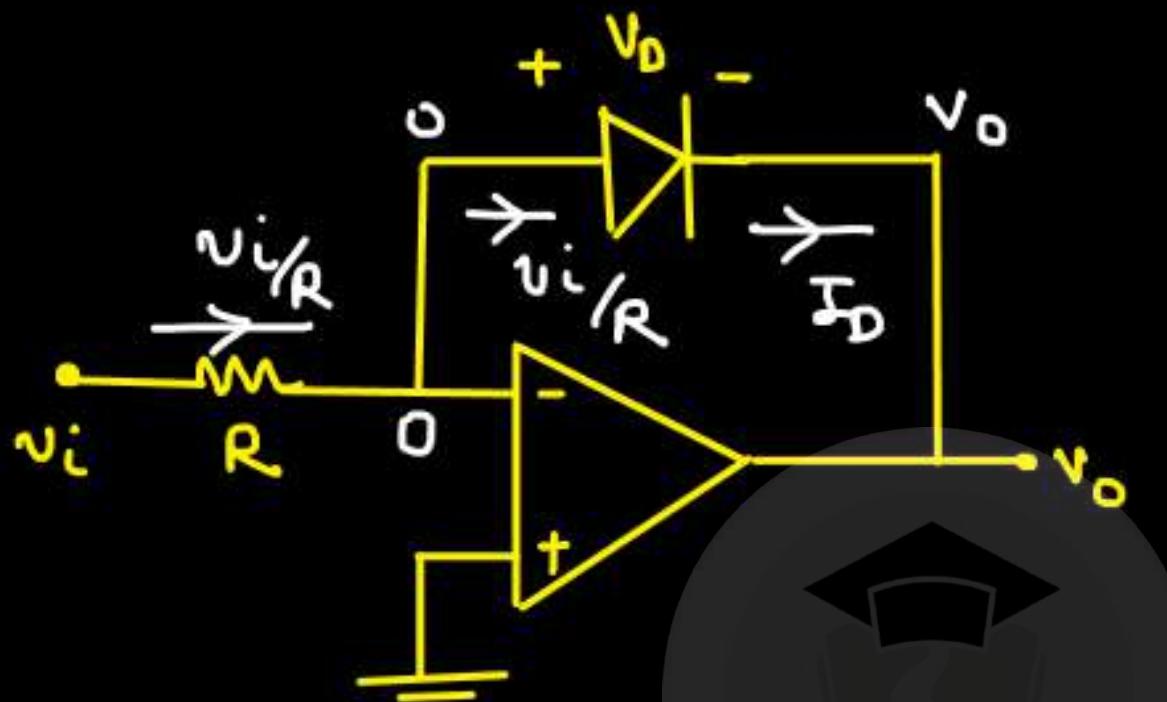

$$V_D = -V_o$$

$$I_D = I_s e^{V_D/nV_T}$$

$$\frac{v_i}{R} = I_s e^{-V_o/nV_T}$$


$$\exp\left(-\frac{V_o}{nV_T}\right) = \frac{v_i}{I_s R}$$

$$\Rightarrow -\frac{V_o}{nV_T} = \ln\left[\frac{v_i}{I_s R}\right]$$

$$\Rightarrow V_o = -nV_T \ln\left[\frac{v_i}{I_s R}\right]$$

$$V_o \propto \ln[v_i]$$

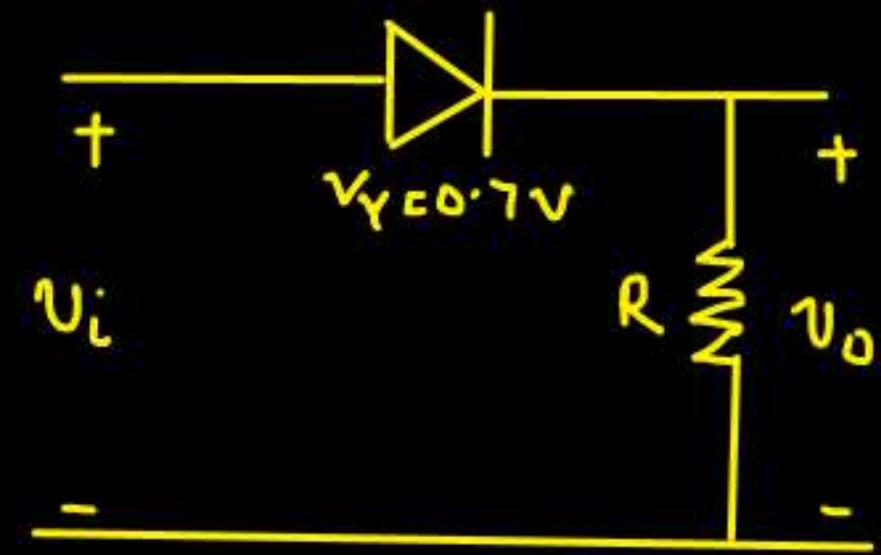* Half Wave rectifier using diode ($V_F = 0.7V$) :-




$$v_i = 20mV \sin \omega t$$

$$\text{and } V_F = 0.7V$$


⇒ diode will never turn on

$$\Rightarrow v_o = 0V$$

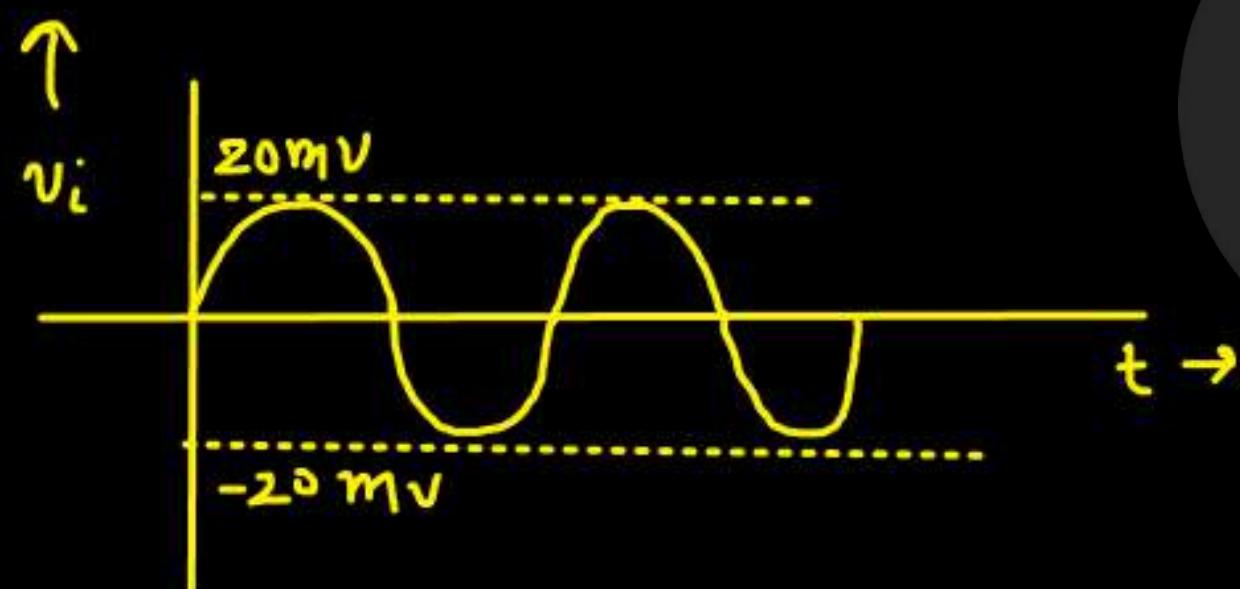

↳ Here, this ckt is not working
as HWR because $(v_i)_{\text{max}} < V_F$


③ HWR using Precision diode :-

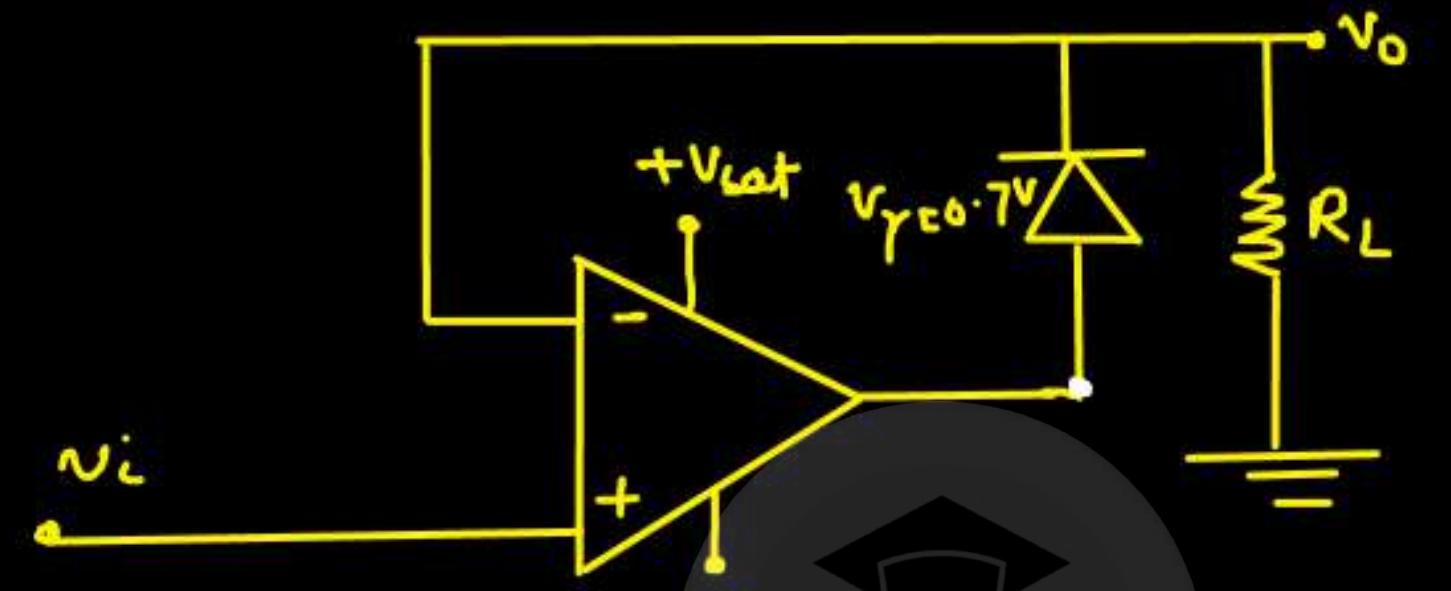


→ Apply O.C. Test :-

$$V_i < 0V \Rightarrow V_0' = -V_{sat}$$

→ diode is off
-V_{sat}

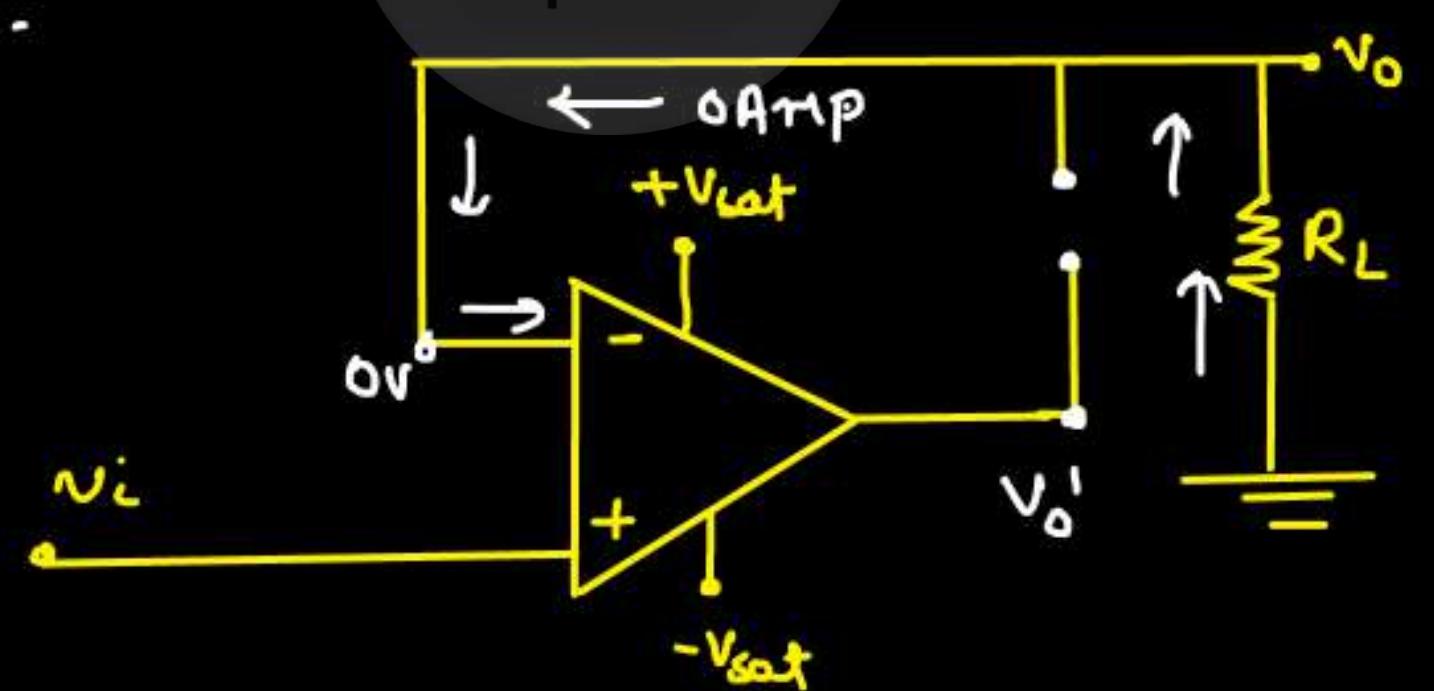

if diode is off

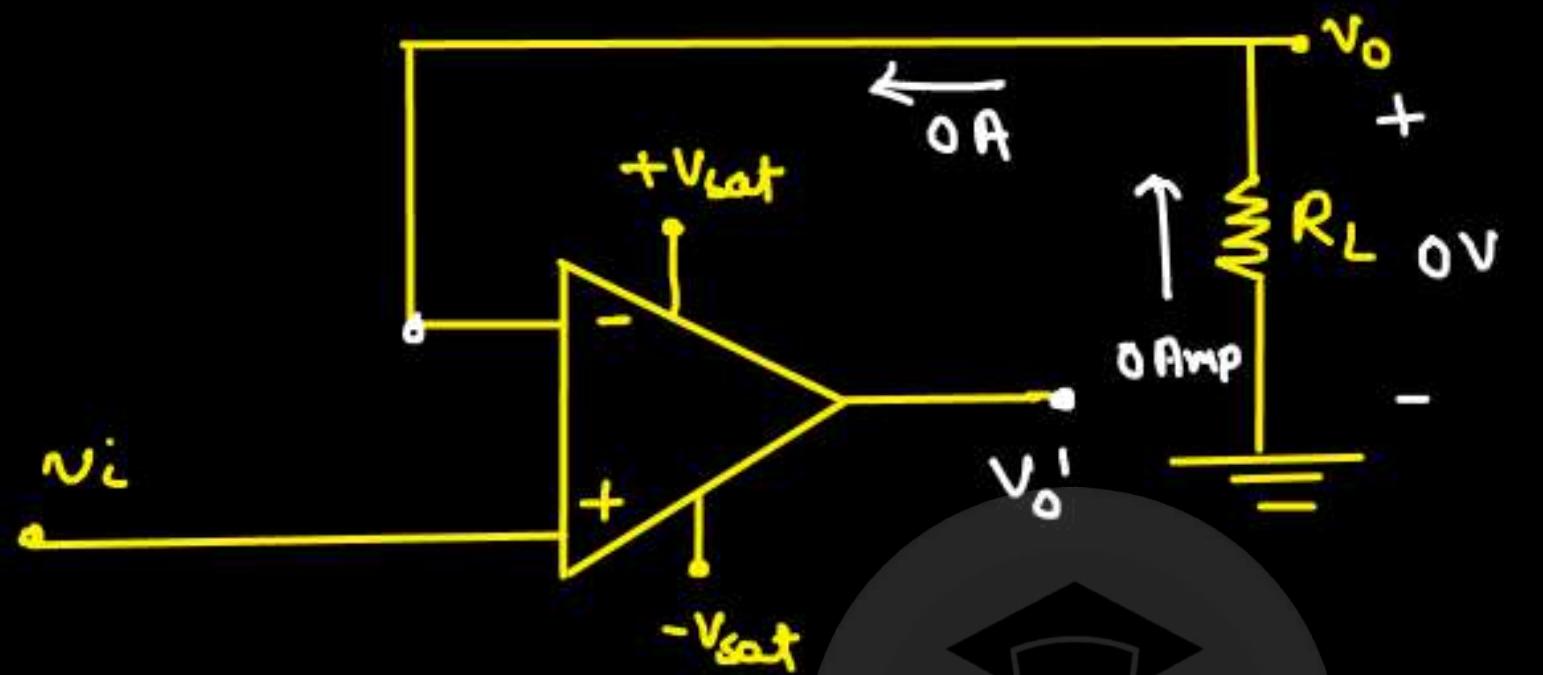



⇒ There is no f/b

$$V_o = 0V$$

{ for $V_i < 0$ }

for $V_i > 0$:-


$$V_o' = +V_{sat}$$

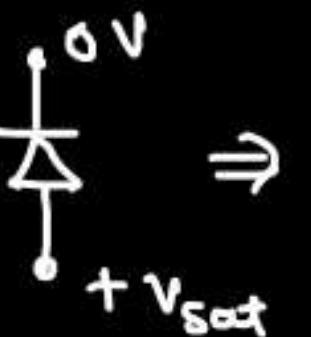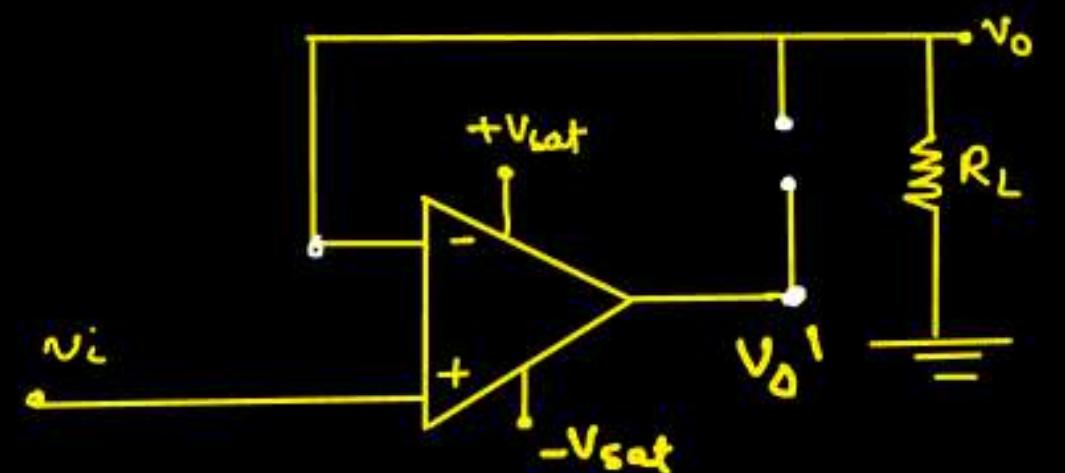

⇒ diode is ON

$$\frac{1}{e^{0.7V}}$$

$$-V_{sat}$$

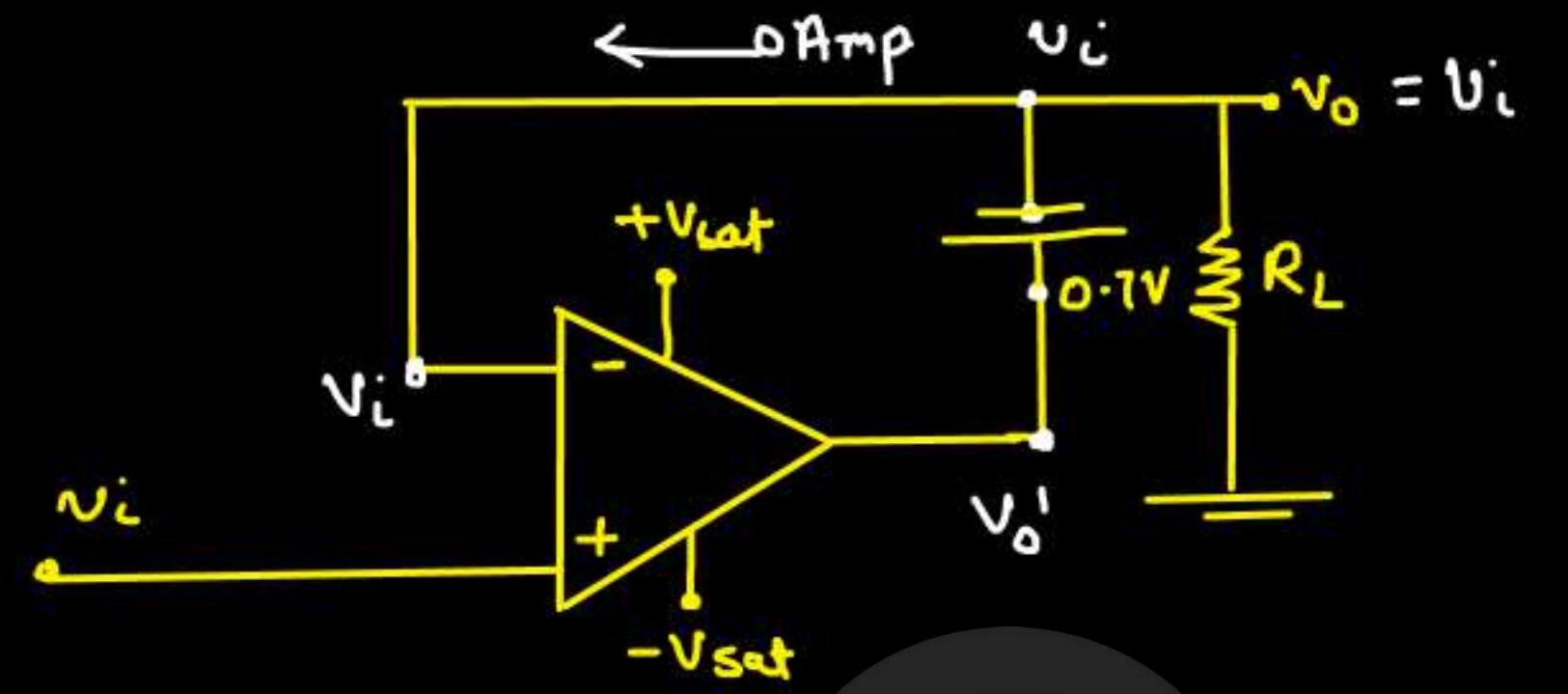




⇒ There is negative present ⇒ virtual short is valid

PrepFusion

$$V_o = V_i$$

For $V_i > 0 \Rightarrow V_o = V_i$

$V_i < 0 \Rightarrow V_o = 0$

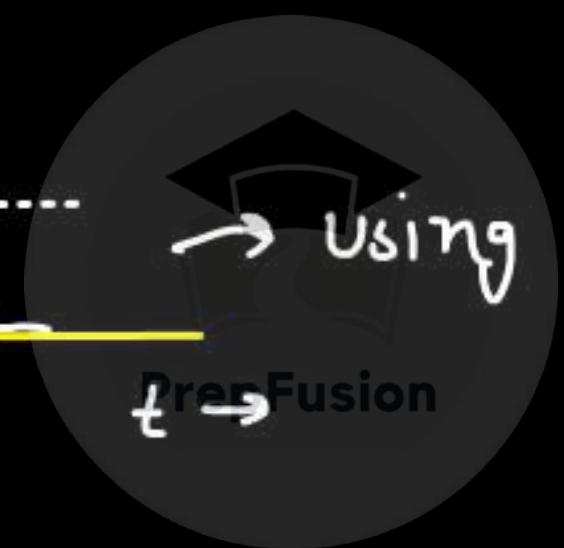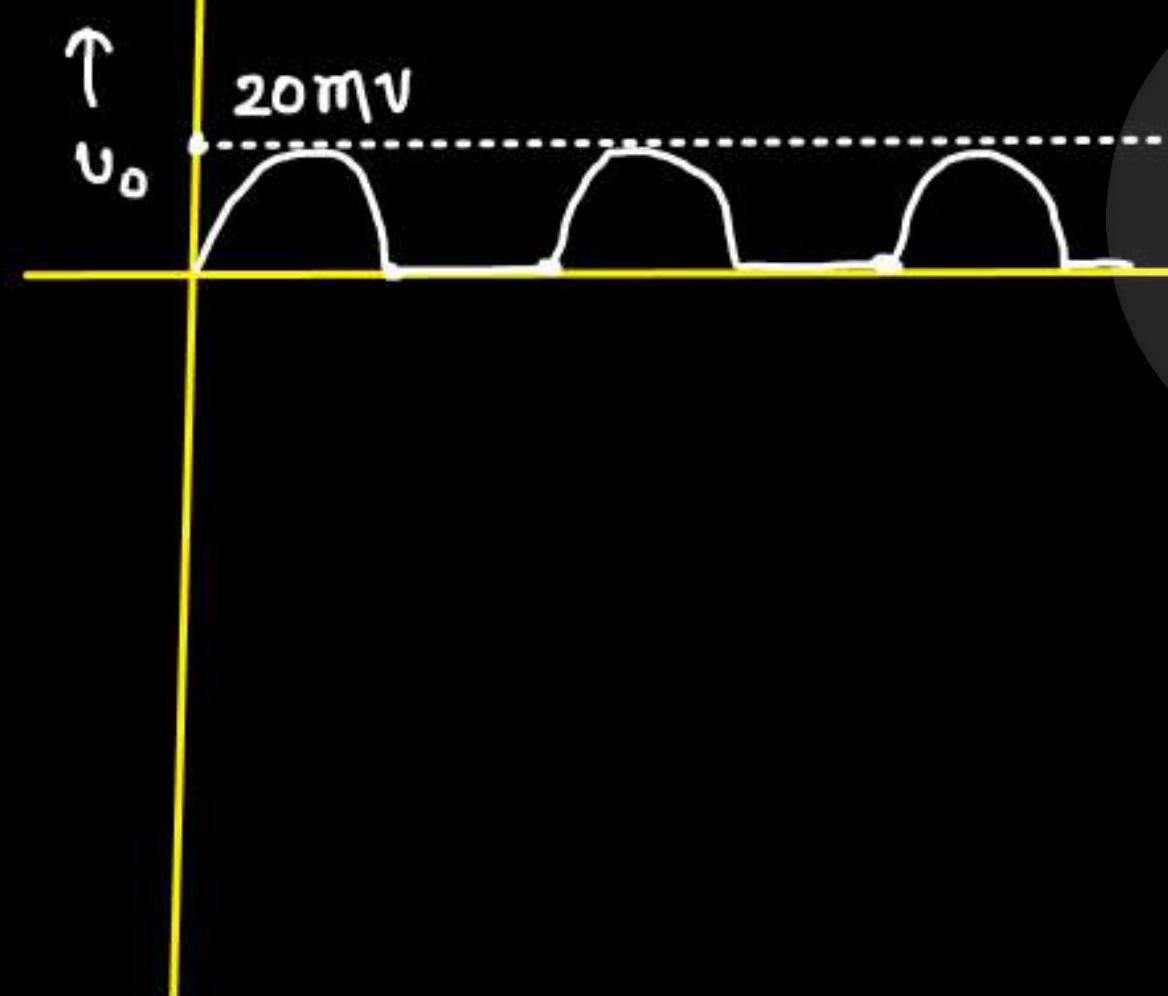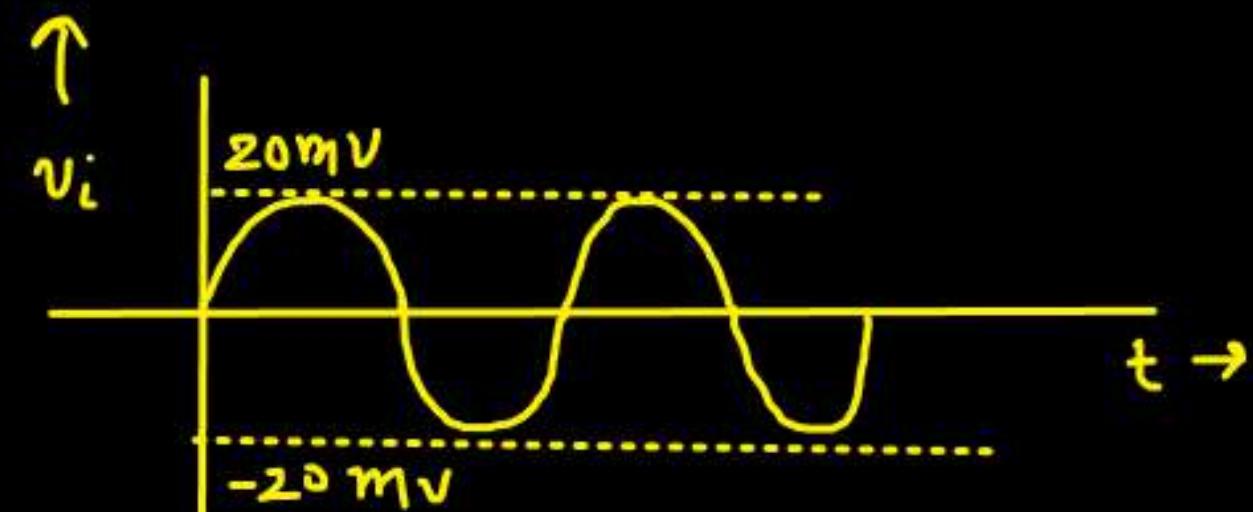


PreFusion

* OP-Amp is active element or Passive :-


- ↳ Produces High gain using external supply.
- ↳ Can deliver the energy.




④ Active Half Wave Rectifier:-

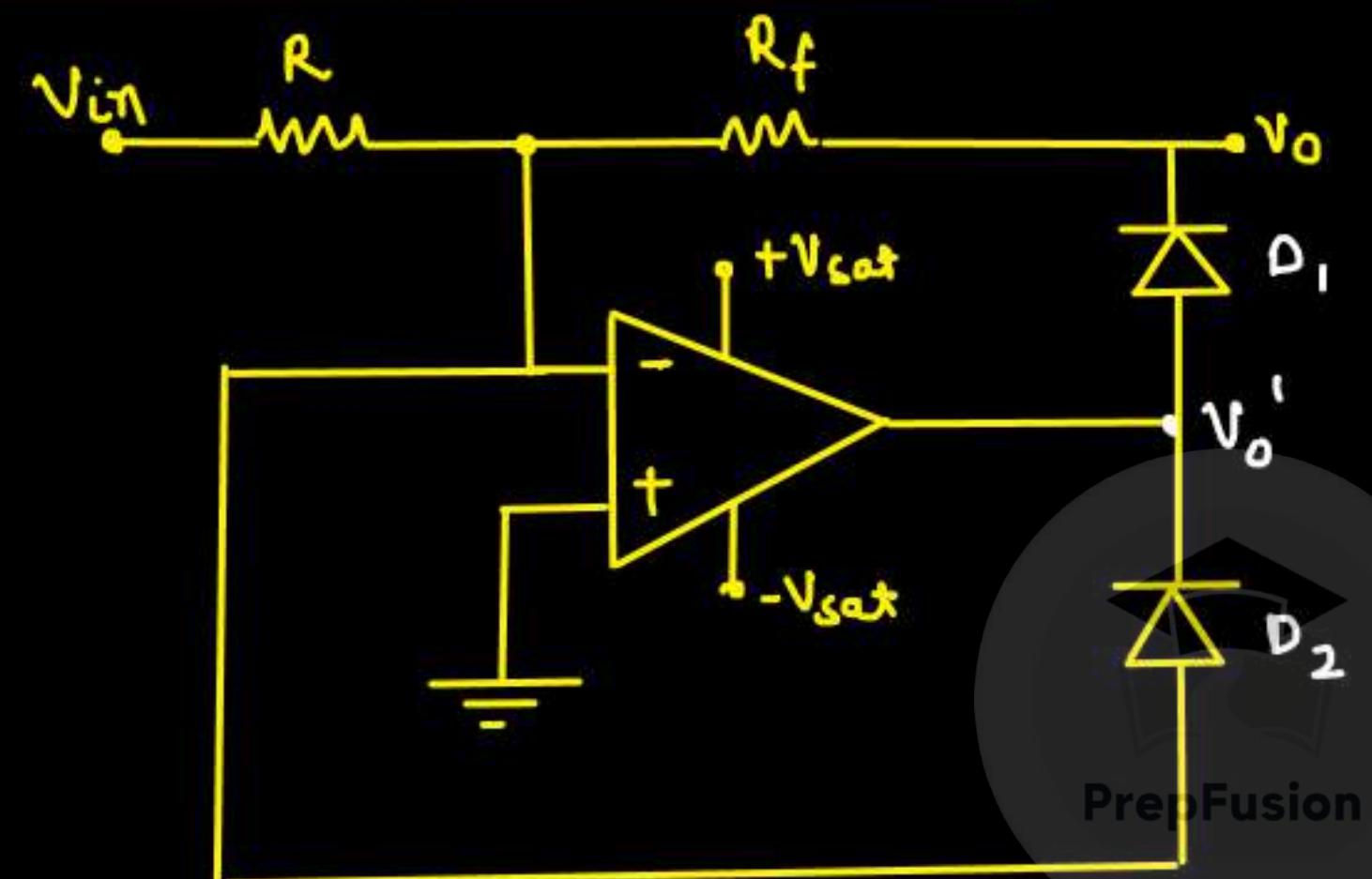

Applying o.c. Test :-

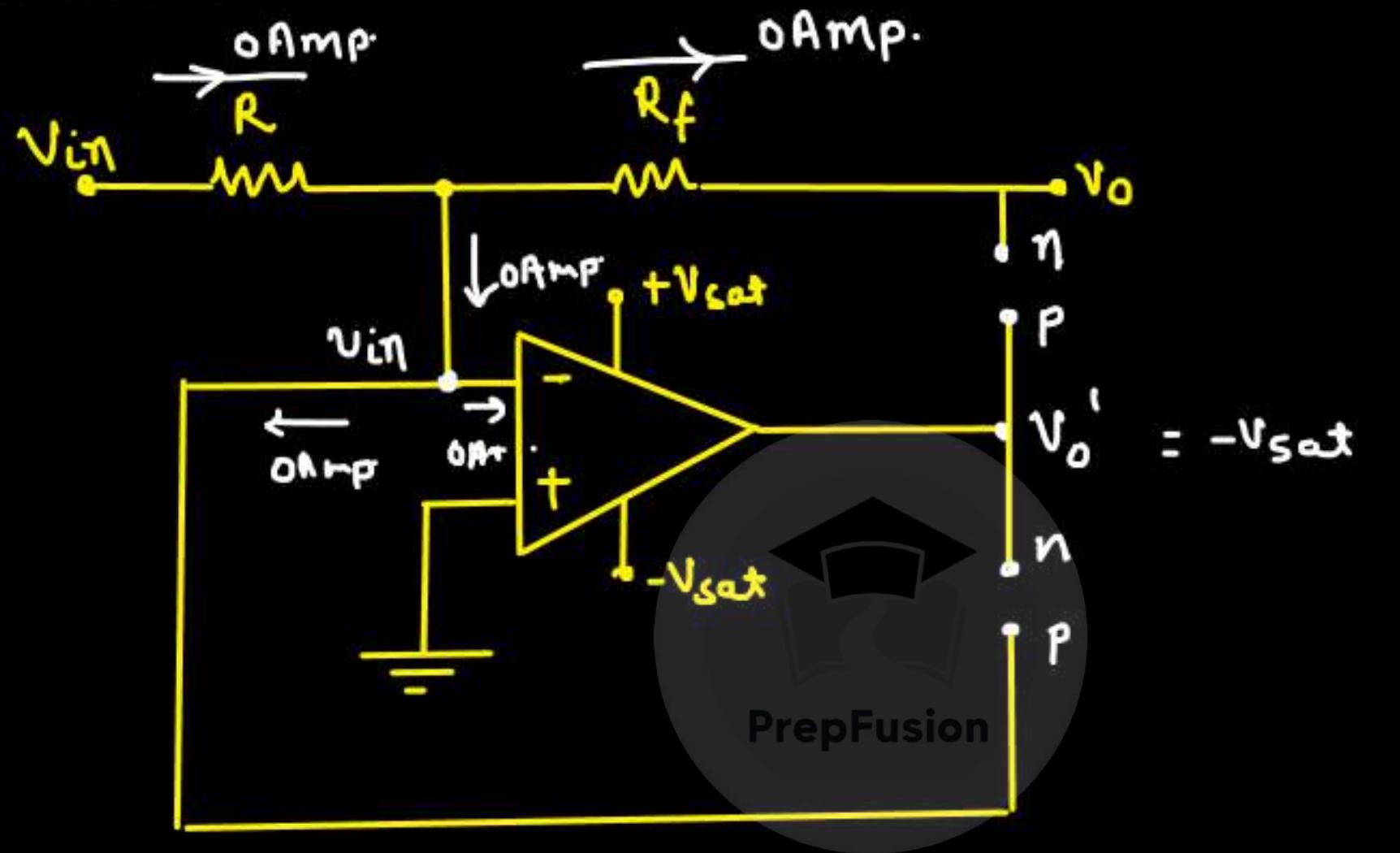

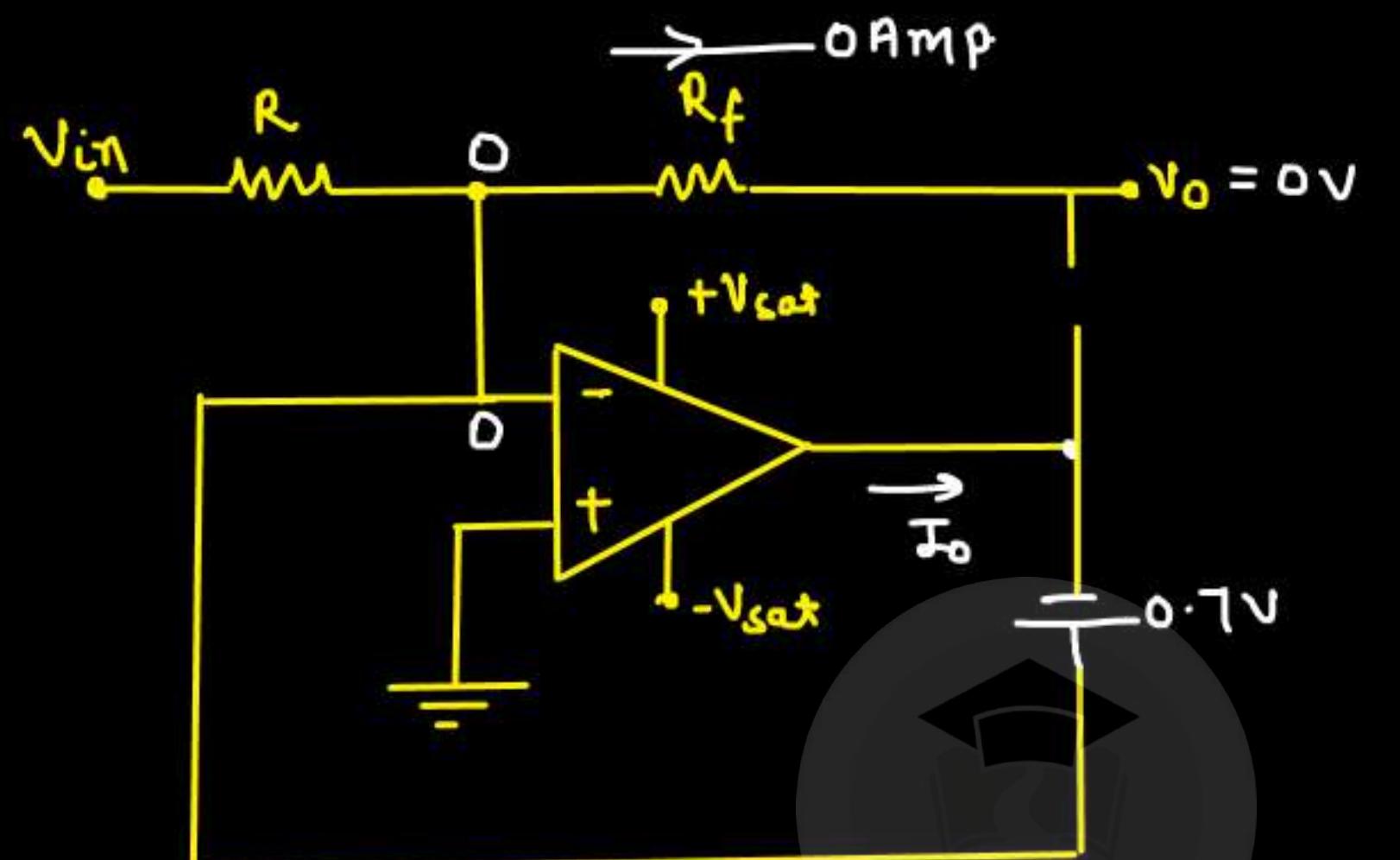① $V_{in} > 0 \Rightarrow V_o' = -V_{sat} \Rightarrow D_2$ Turns ON, D_1 is off




$$I_o = \frac{-V_{in}}{R}$$

PrepFusion


Negative f/b is present

for $V_i > 0 \Rightarrow V_o = 0 \text{ V}$

Applying O.C. Test :-

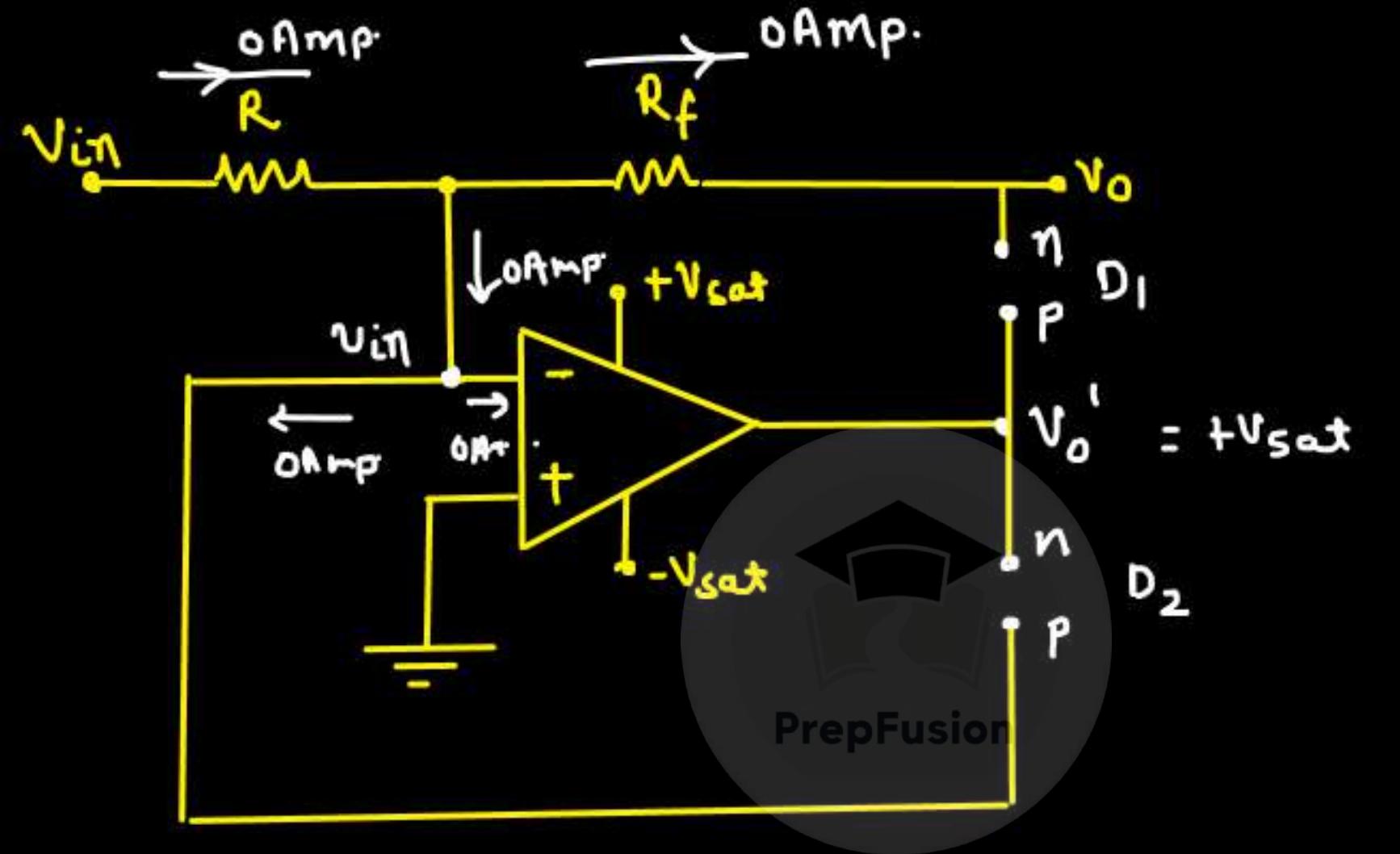

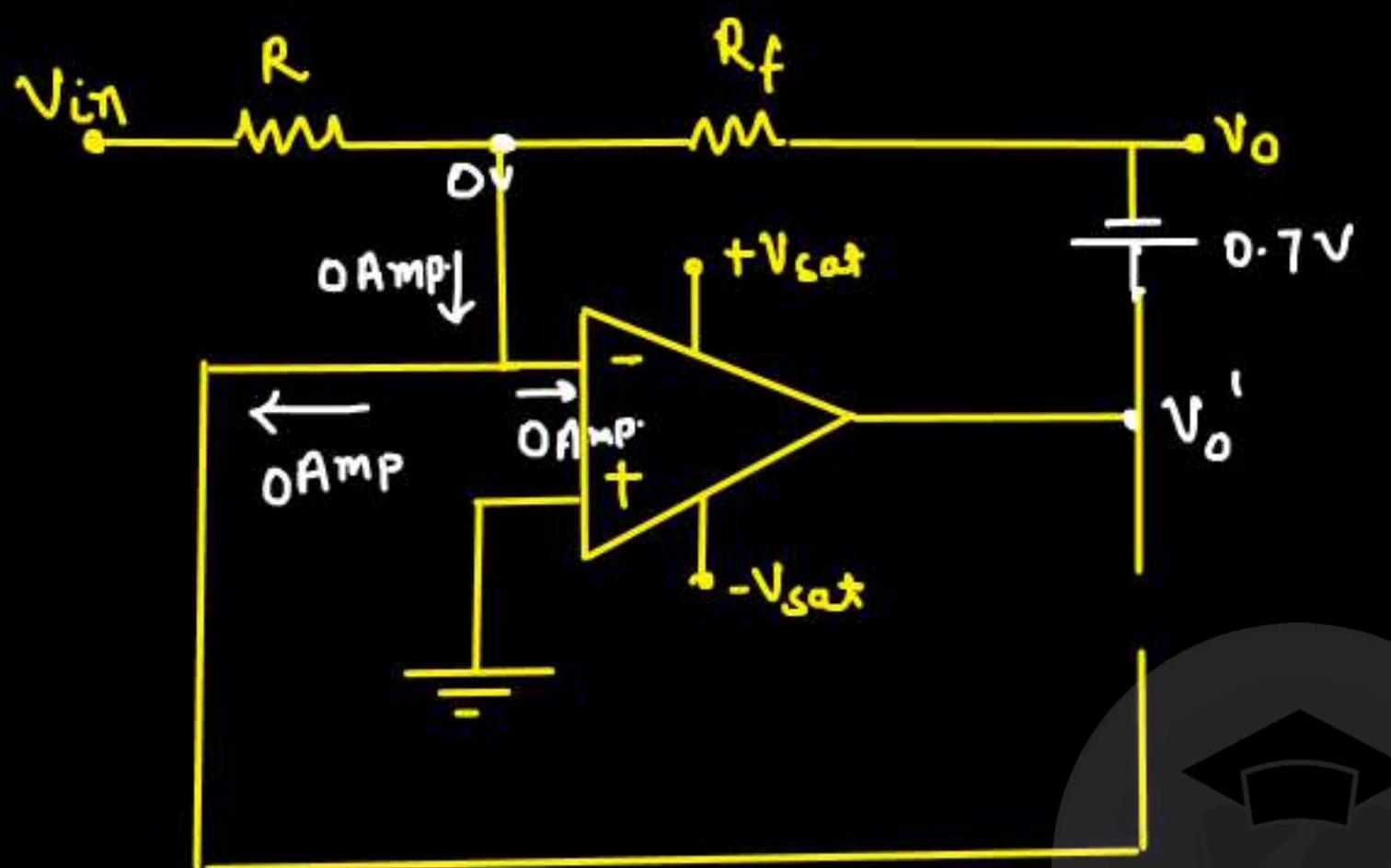$v_{in} < 0 \Rightarrow v_o' = +v_{sat} \Rightarrow D_1$ turns on, D_2 is off





$$V_i > 0 \Rightarrow V_o = 0V$$

$$V_i < 0 \Rightarrow V_o = -\frac{R_f}{R} V_{in}$$


$$0 - \frac{V_{in}}{R} + \left(0 - \frac{V_o}{R_f} \right) = 0$$

$$V_o = -\frac{R_f}{R} V_{in}$$


$\left\{ V_i < 0 \right\}$

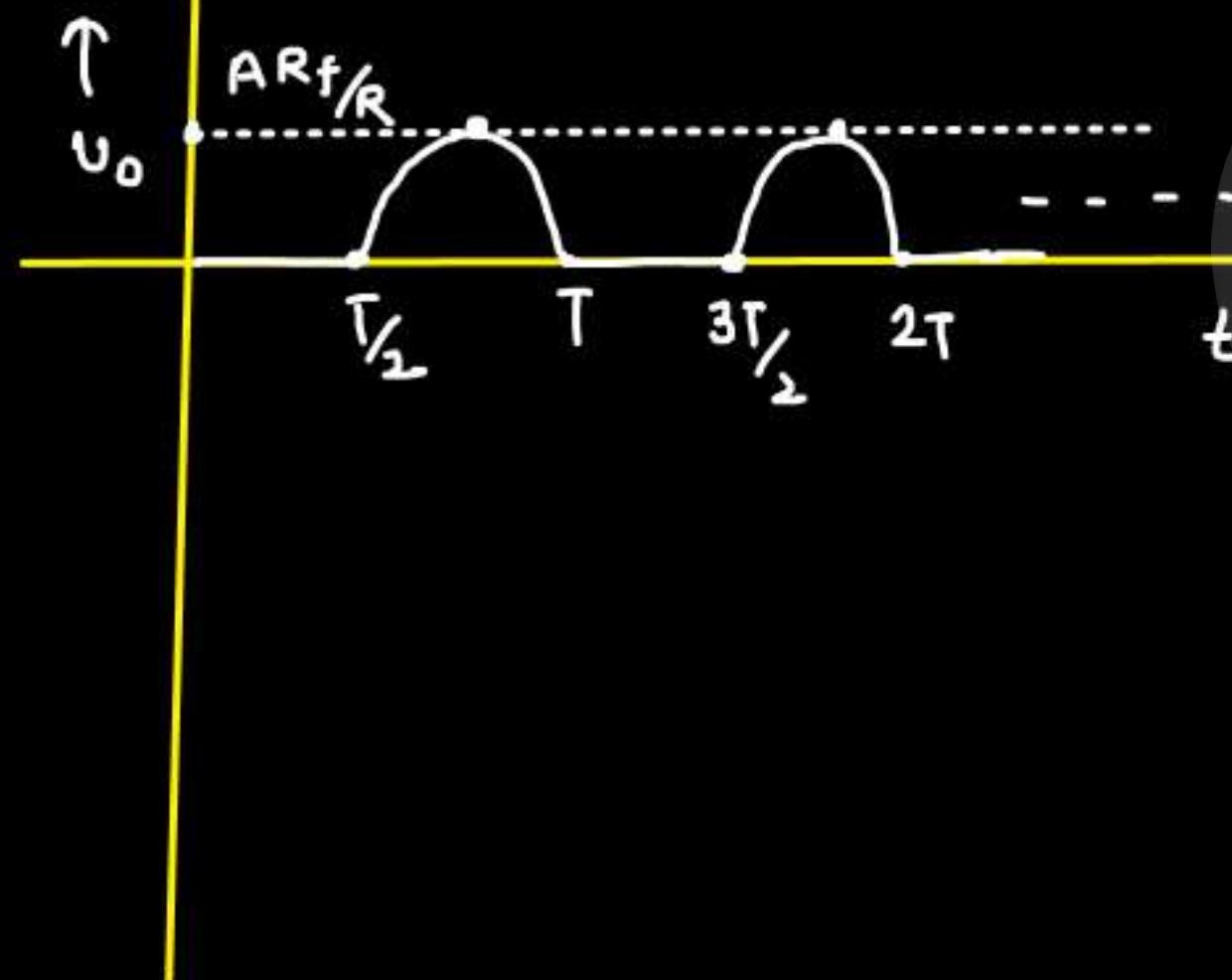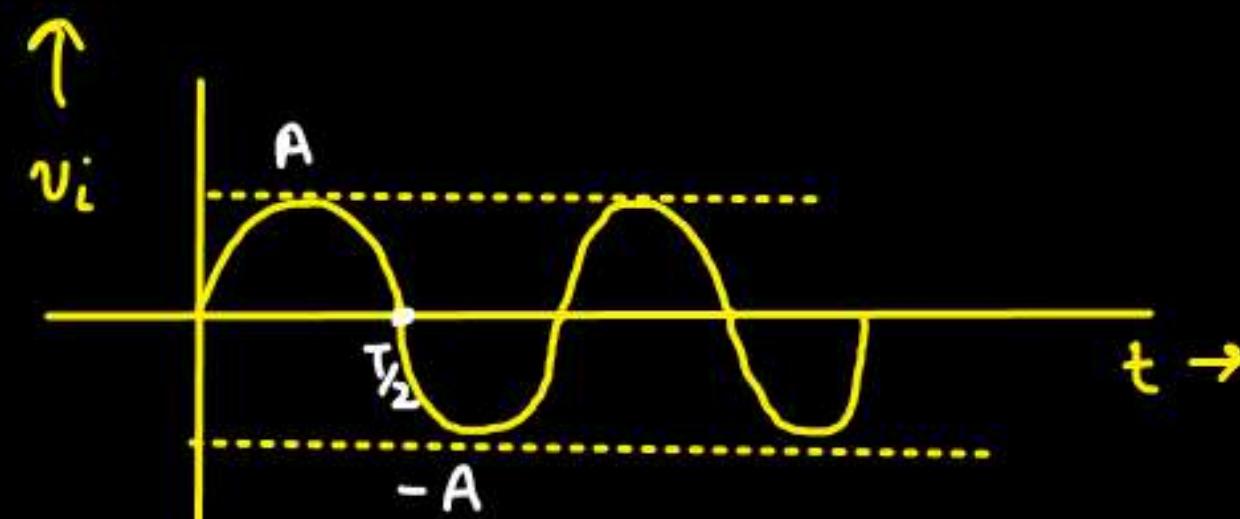


Transfer characteristics:-

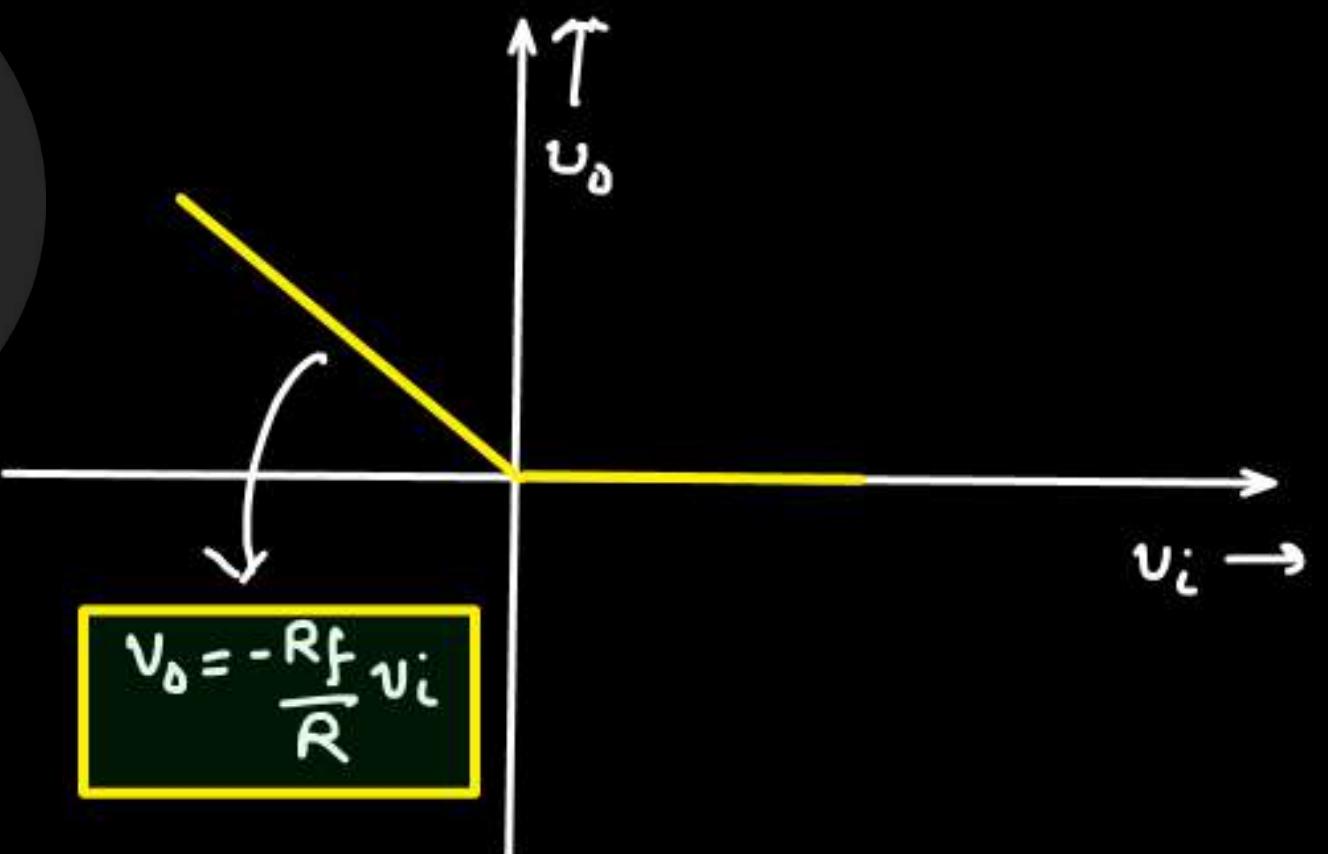

Q. Draw Transfer characteristics?

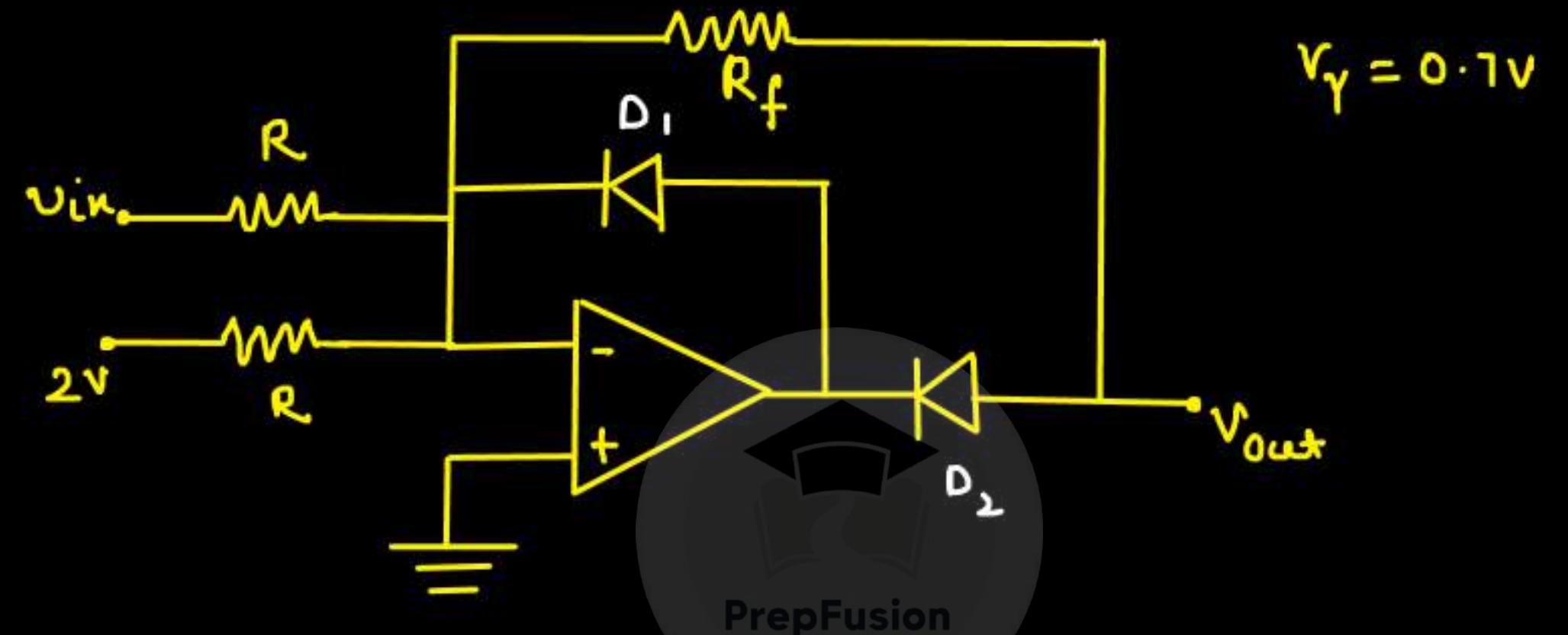

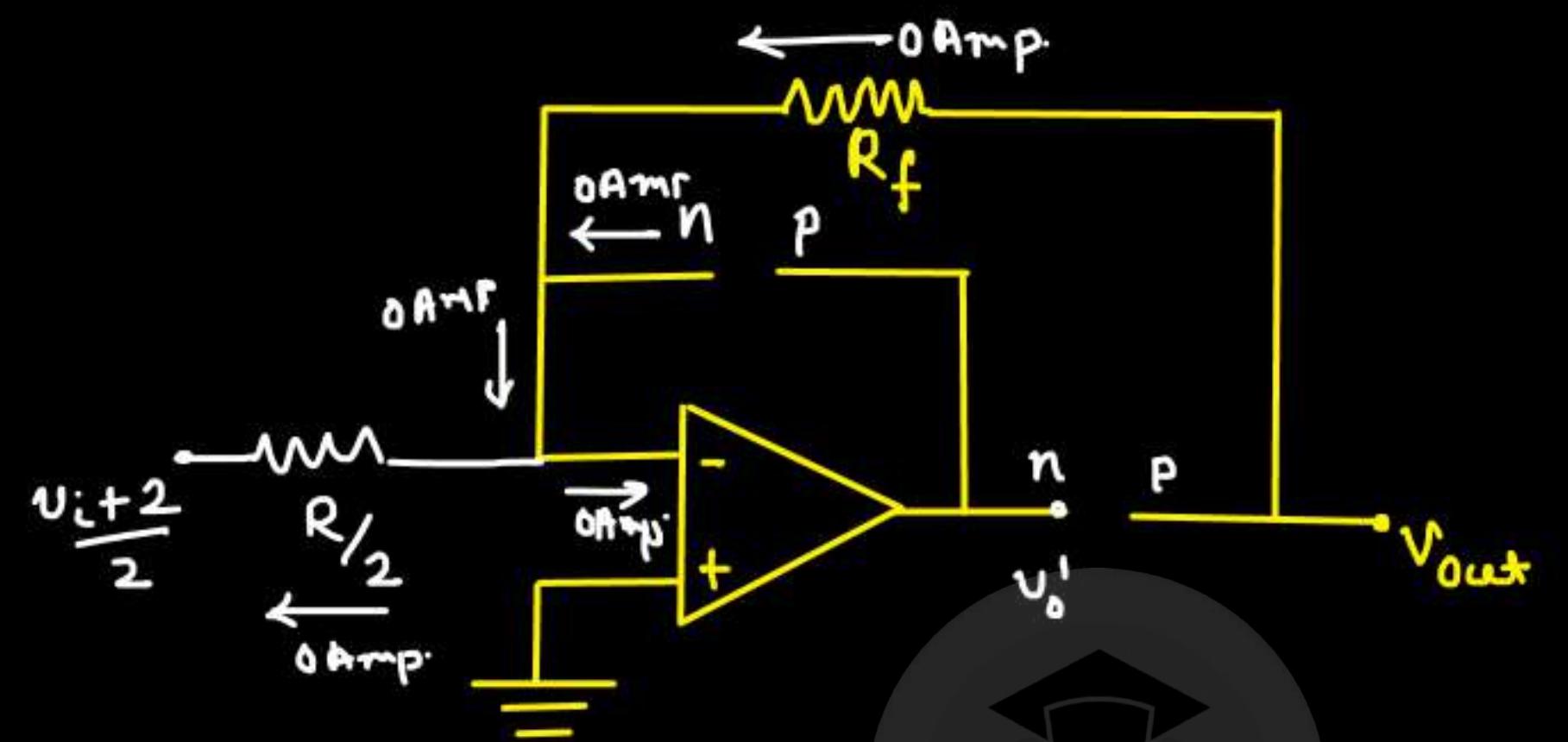


$\frac{V_i + 2}{2} > 0 \Rightarrow V_o' = -V_{sat} \Rightarrow D_2 \text{ turns ON}, D_1 \text{ is OFF}$

$V_i > -2$



$V_i > -2 \text{ :-}$

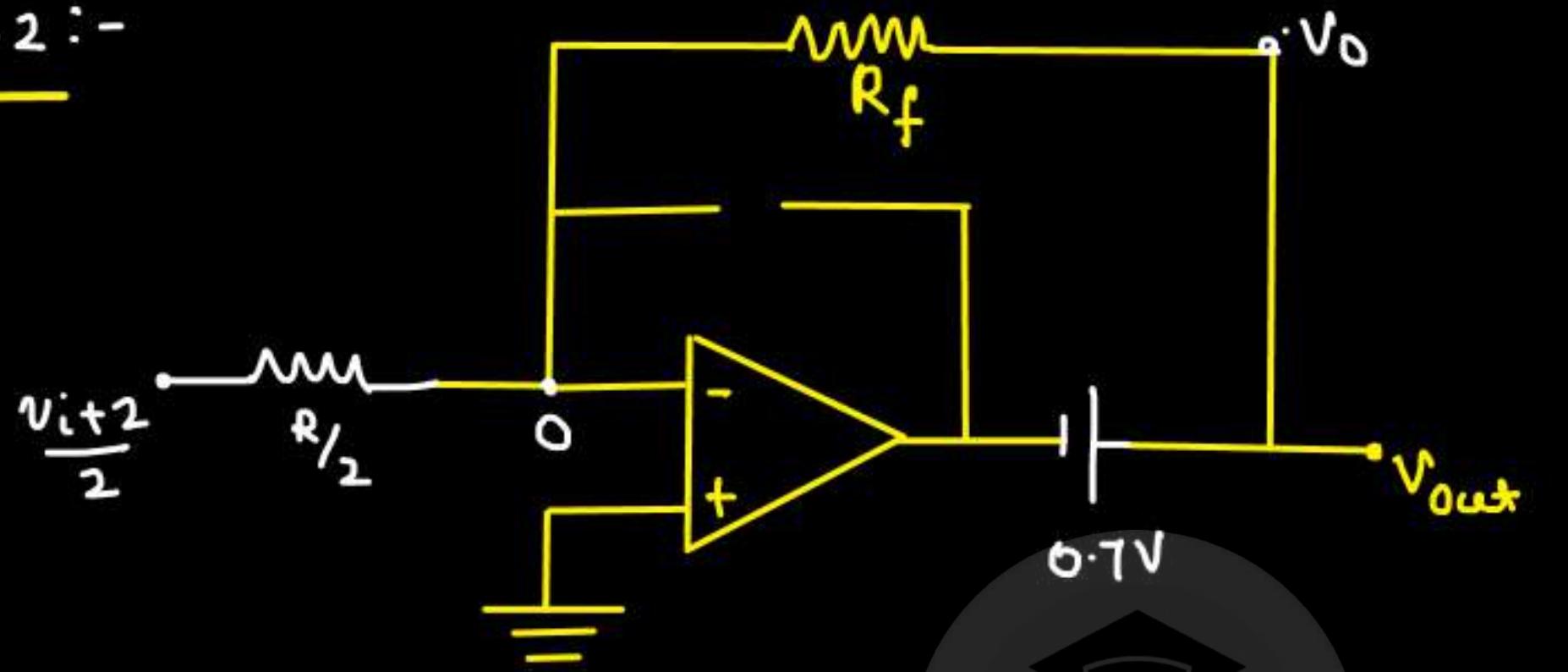


$$V_o = -\frac{R_f}{R} \left[V_i + \frac{2}{2} \right]$$

$$\{ V_i > -2 \}$$

$$V_o = -\frac{R_f}{R} [V_i + 2]$$




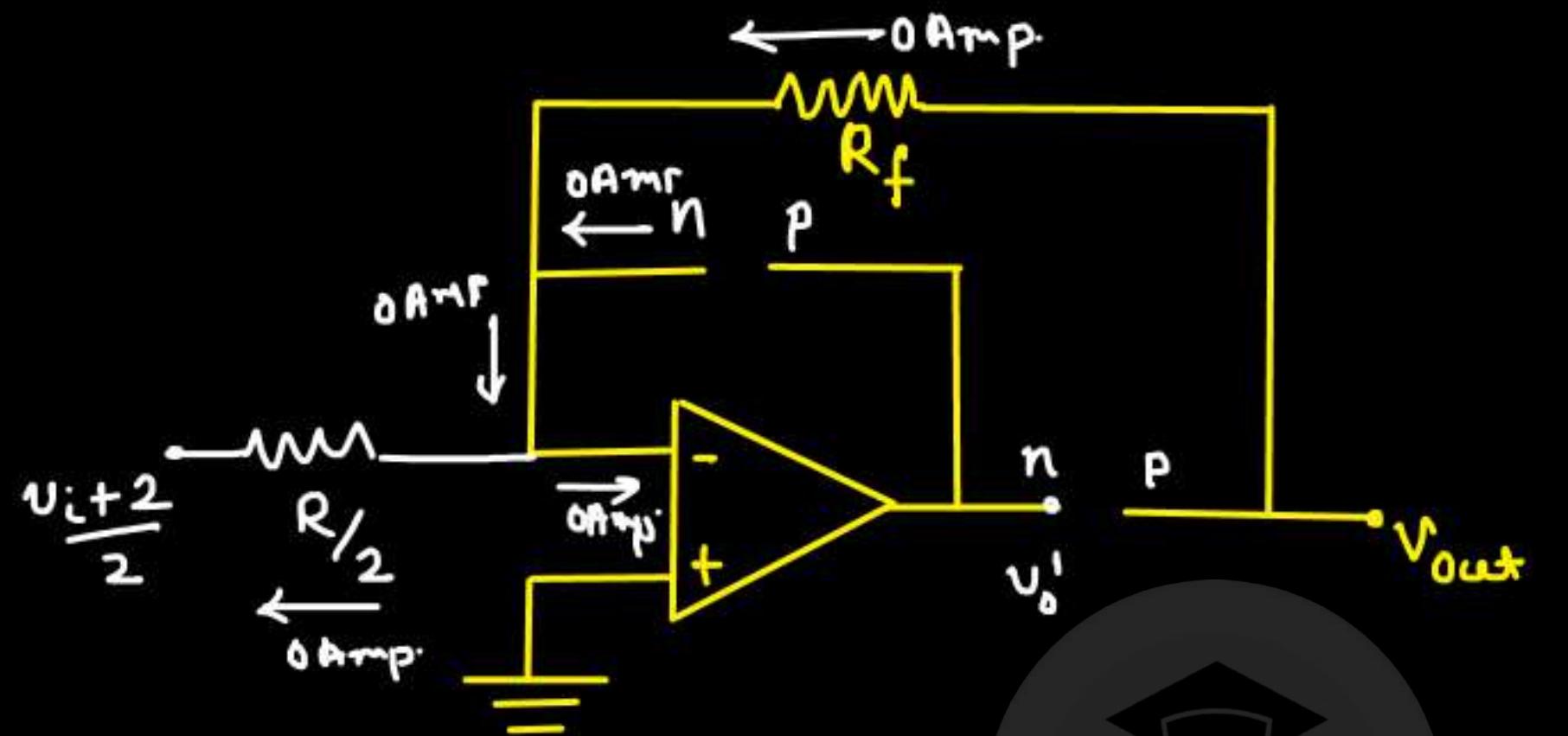

$\frac{v_i + 2}{2} < 0 \Rightarrow v_o' = +v_{sat} \Rightarrow D_1 \text{ turns on}, D_2 \text{ is off}$

$$v_i < -2$$


$V_i < -2$

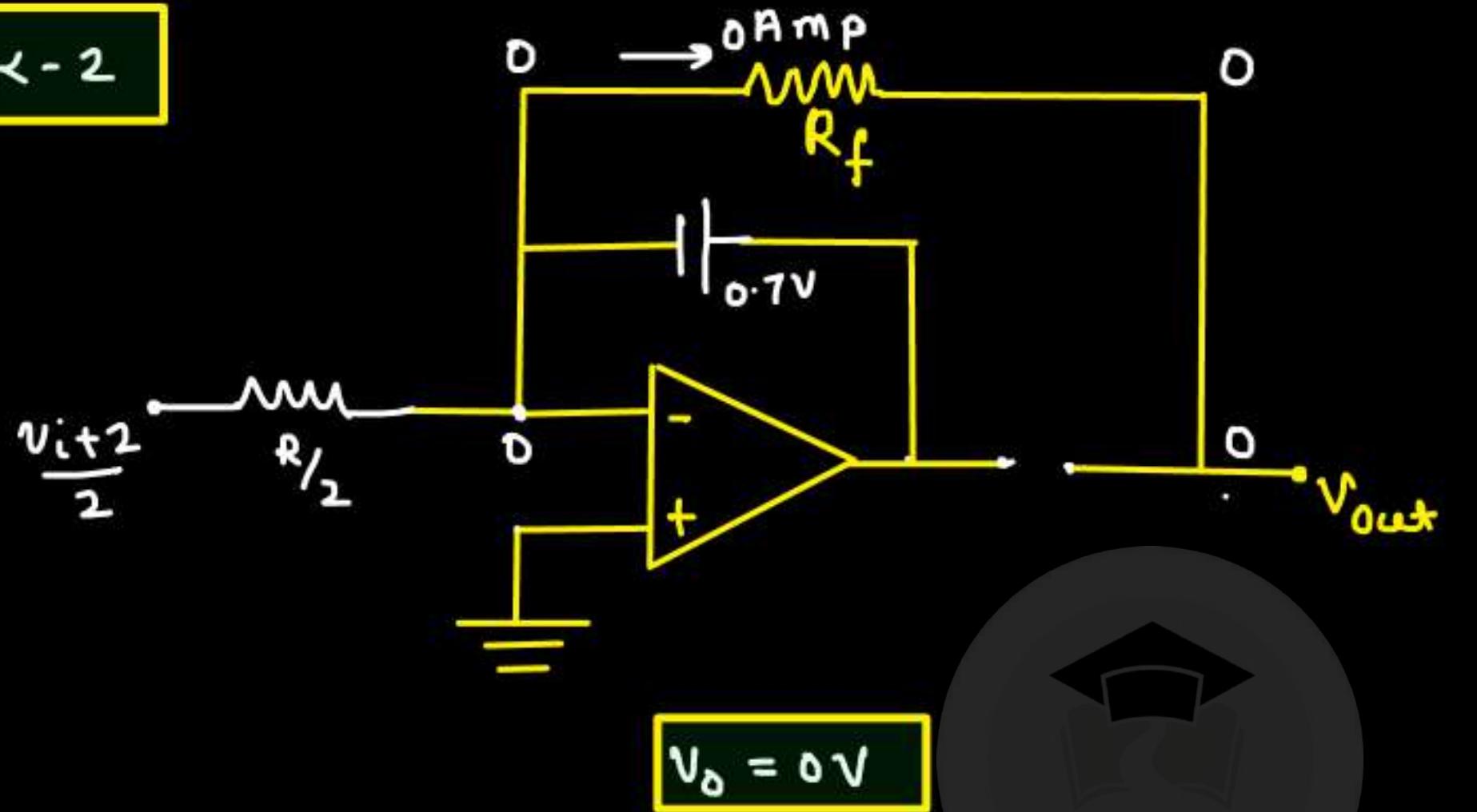


$\star \star$


$$V_i > -2 \Rightarrow V_o = -\frac{R_f}{R} (V_i + 2)$$
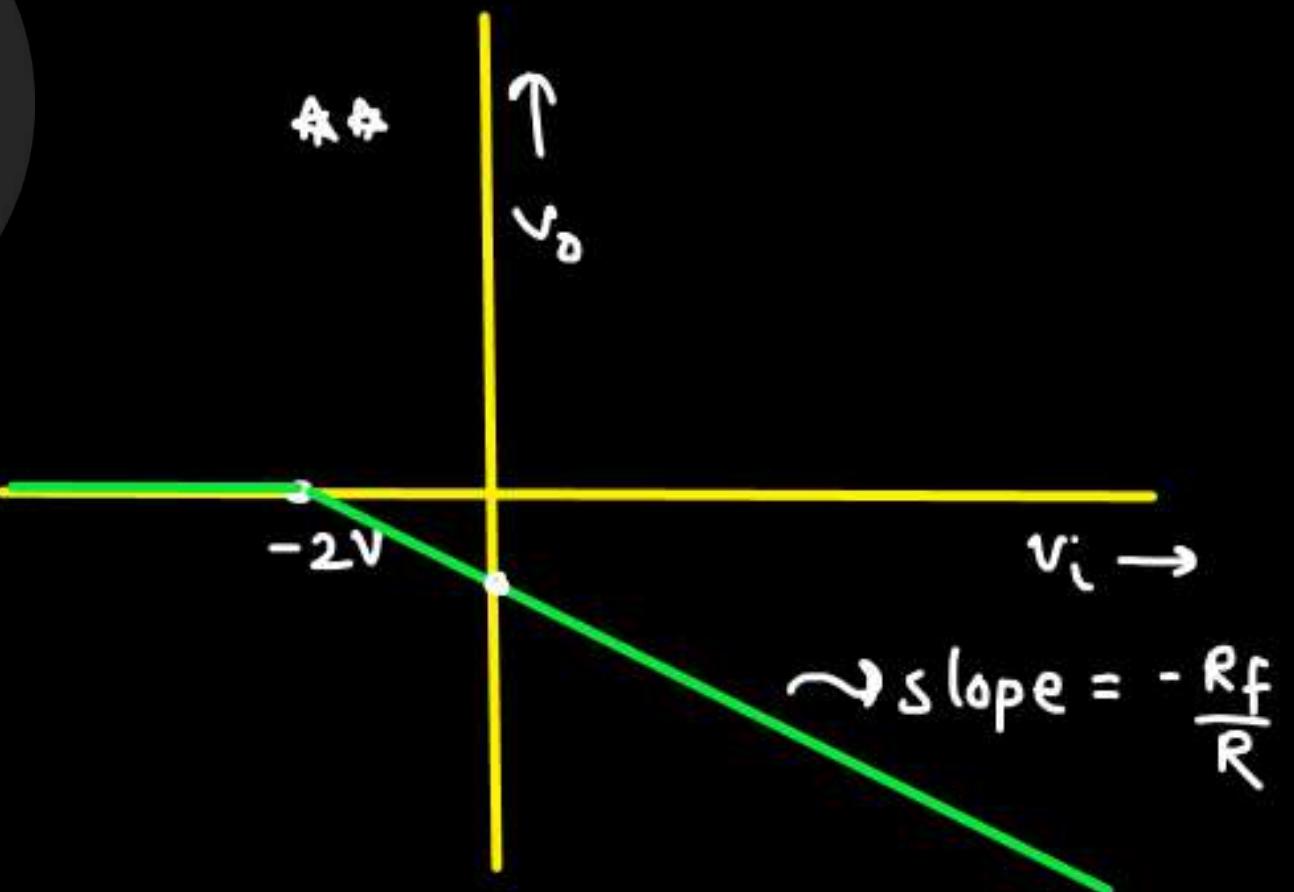
$$V_i < -2 \Rightarrow V_o = 0 \text{ V}$$



⑤ Active Full Wave Rectifier :-

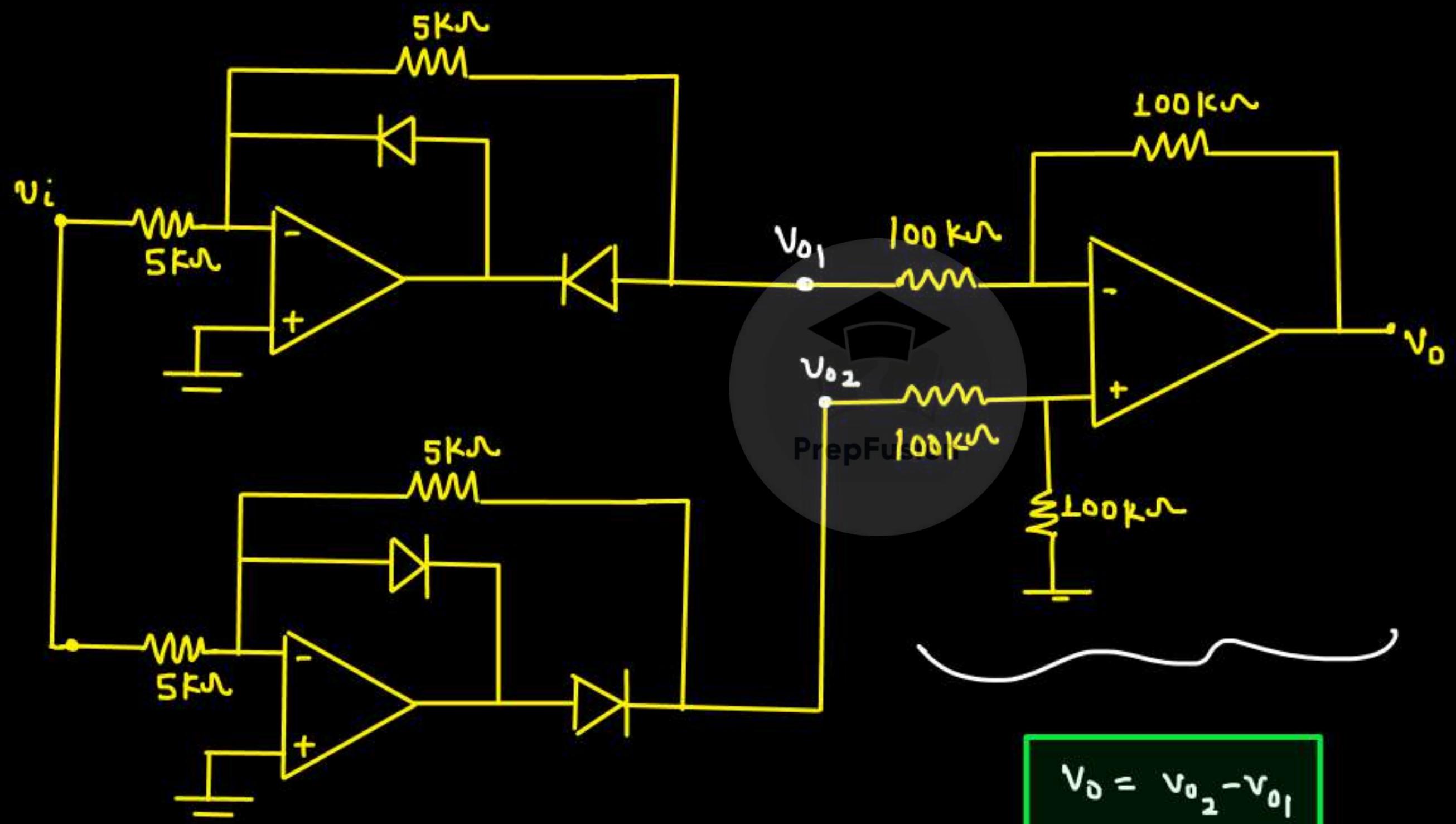

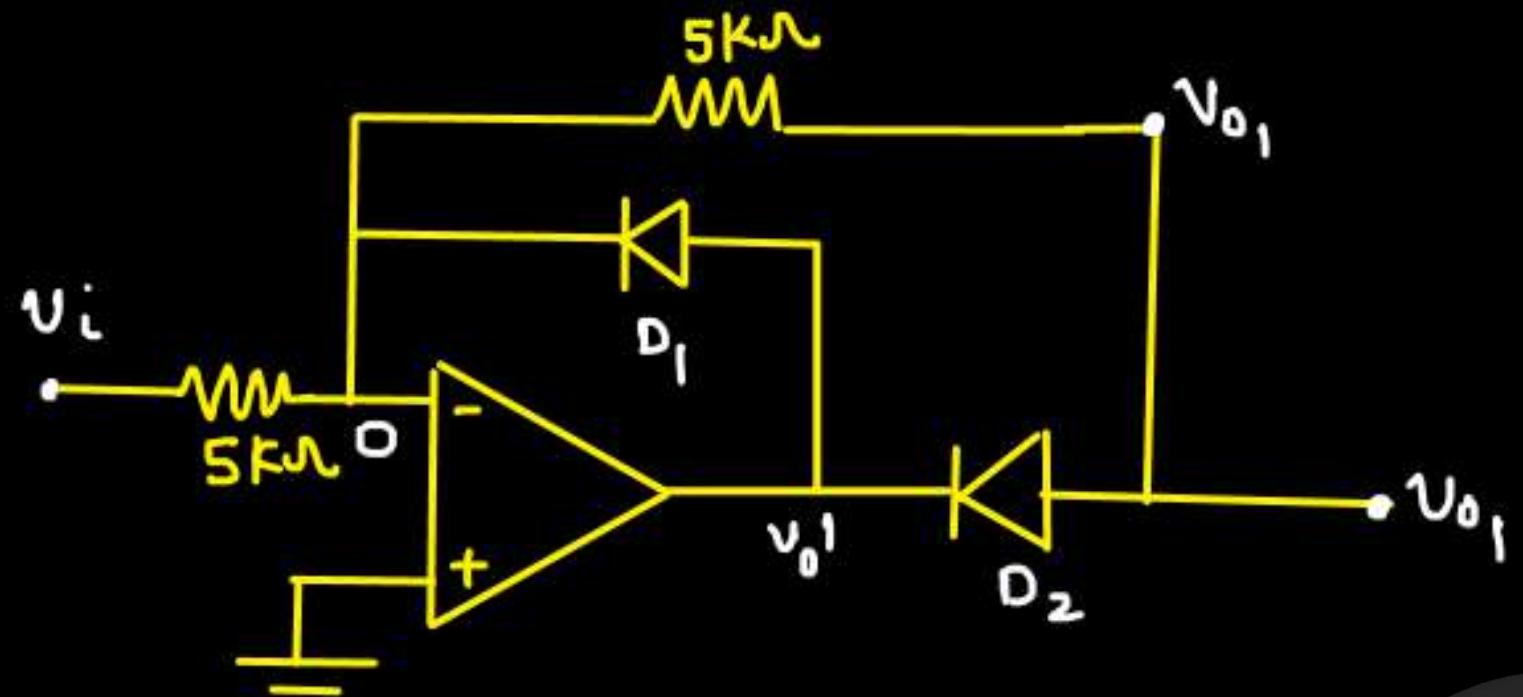


$v_i > 0 \Rightarrow v_o^1 = -v_{sat} \Rightarrow D_2 \text{ ON}, D_1 \text{ OFF}$


$$v_{o_1} = -\frac{5k\Omega}{5k\Omega} v_i$$

$v_i > 0 \Rightarrow v_{o_1} = -v_i$

$v_i < 0 \Rightarrow v_o^1 = +v_{sat} \Rightarrow D_1 \text{ ON}, D_2 \text{ OFF}$

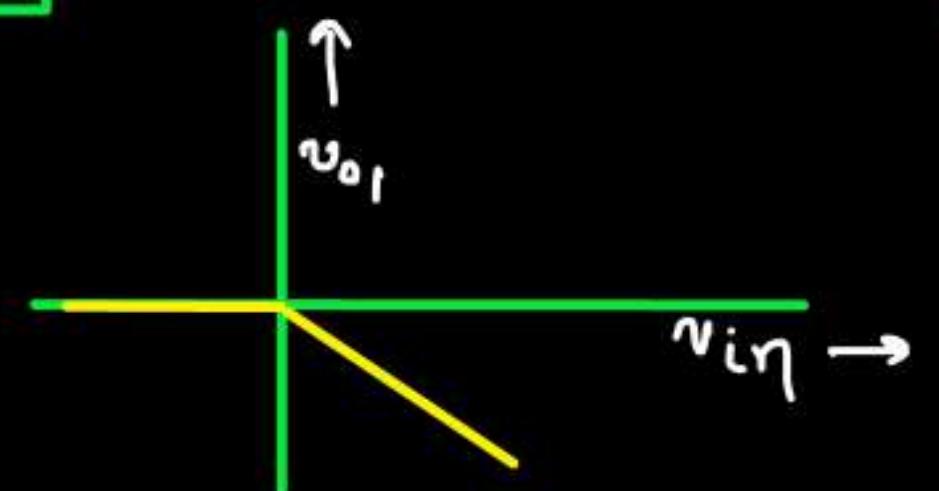$v_i < 0 \Rightarrow v_{o_1} = 0 \text{ V}$



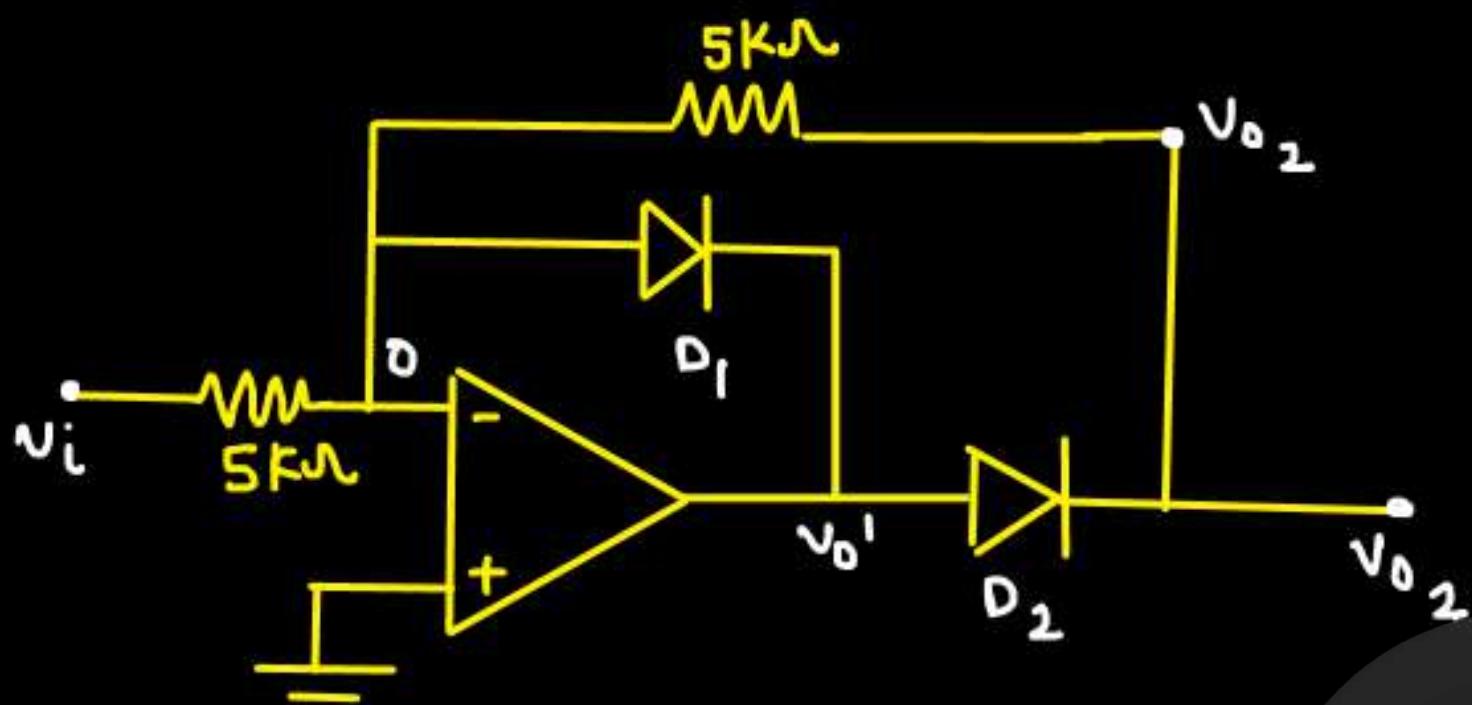


$u_i > 0 \Rightarrow v_o' = -v_{sat} \Rightarrow D_1$ turns on, D_2 is off


$$u_i > 0 \Rightarrow v_{o2} = 0V$$


$u_i < 0 \Rightarrow v_o' = +v_{sat} \Rightarrow D_2$ turns on, D_1 is off

$$v_{o2} = -\frac{5k\Omega}{5k\Omega} \times u_i$$

$$u_i < 0 \Rightarrow v_{o2} = -u_i$$

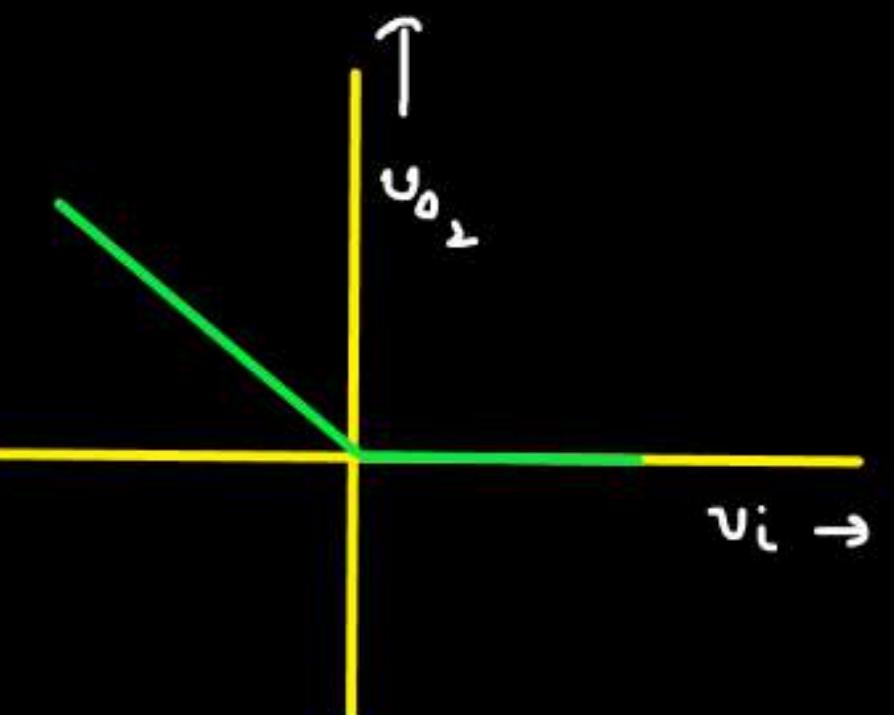


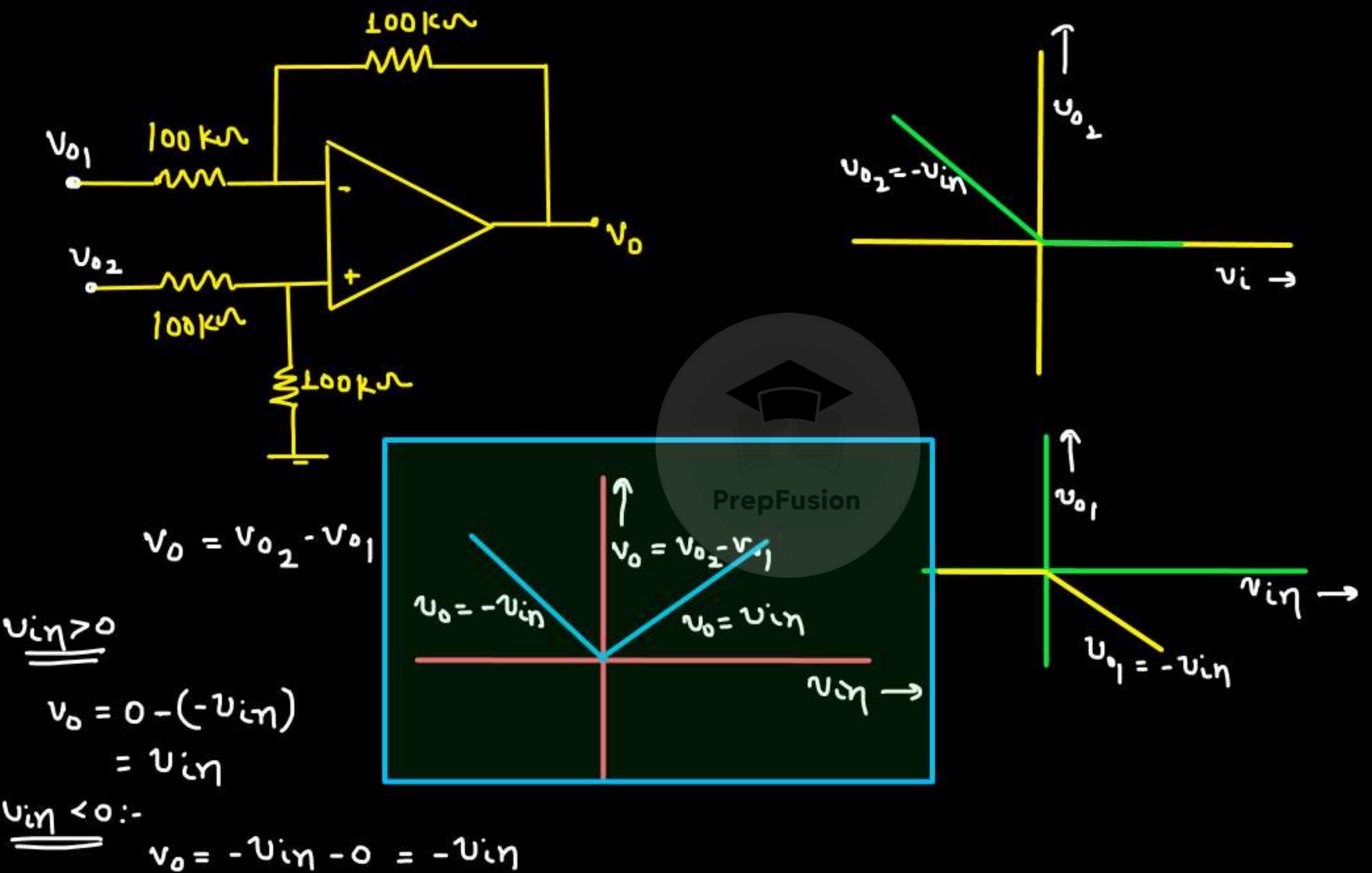

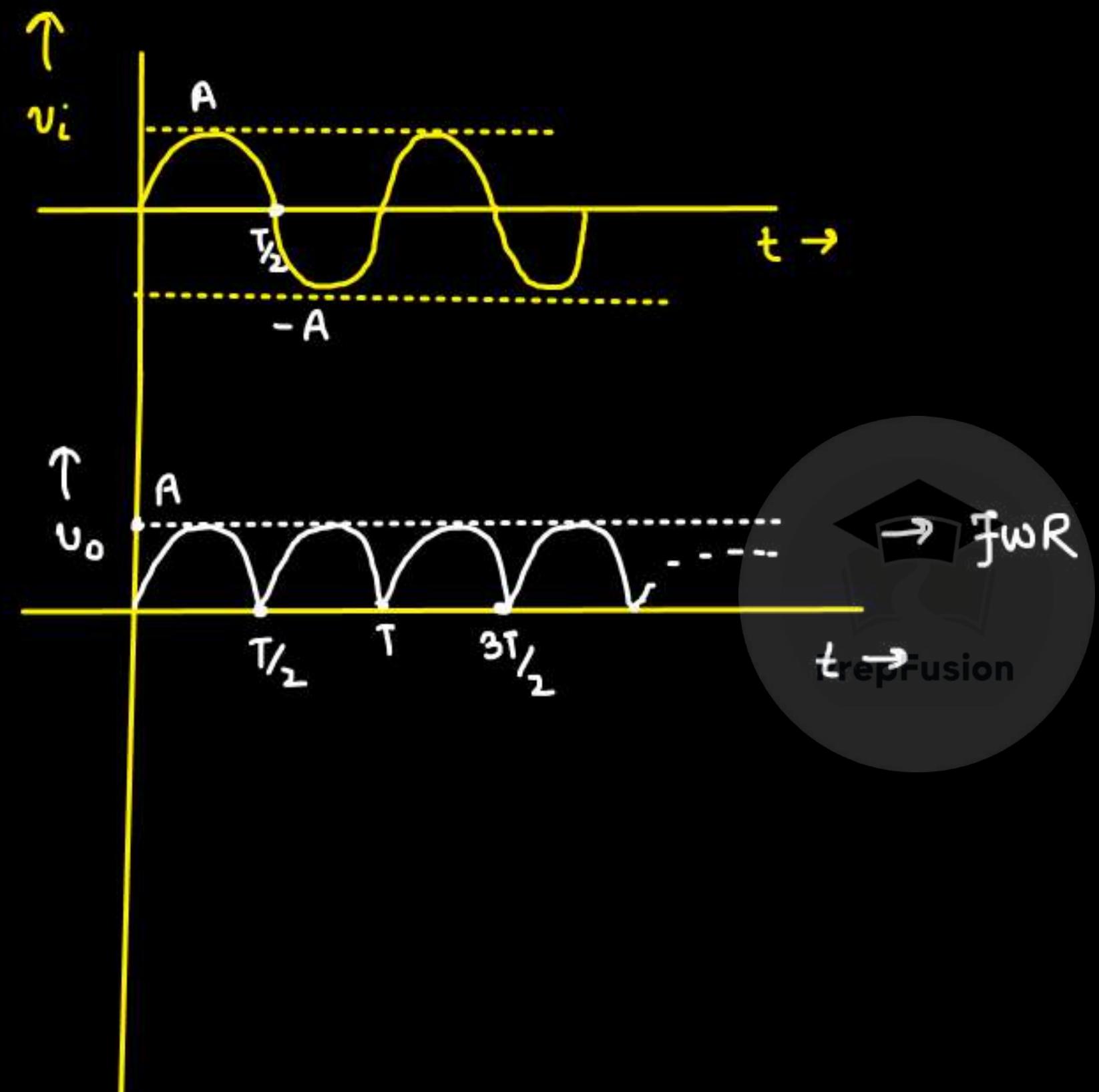

Assignment - 13

Q.

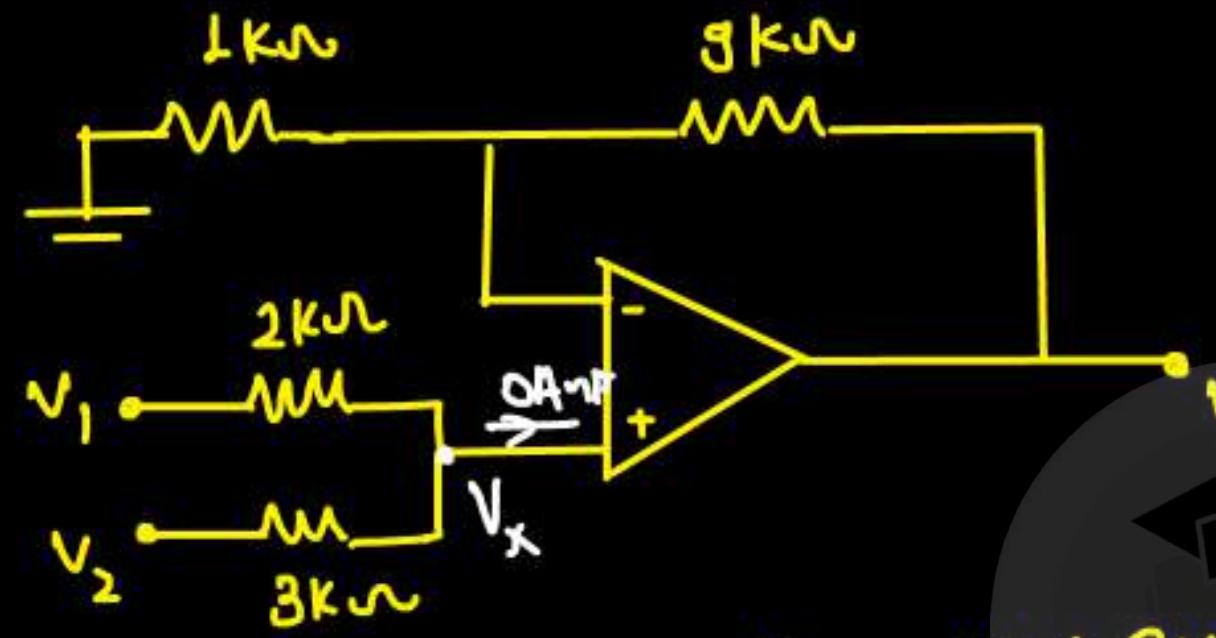

$$V_O = \alpha V_1 + \beta V_2$$

PrepFusion

value of $\alpha + \beta$ is — .

$$\Rightarrow V_O = \left[1 + \frac{9k}{1k} \right] V_L$$

$$V_O = 10V_L \quad \textcircled{1}$$


$$V_L = \frac{3V_1 + 2V_2}{5} \quad \textcircled{2}$$

$$\alpha = 6, \beta = 4$$

$$\alpha + \beta = 10$$

$$V_O = 10 \left[\frac{3V_1 + 2V_2}{5} \right] = 6V_1 + 4V_2$$

Q.

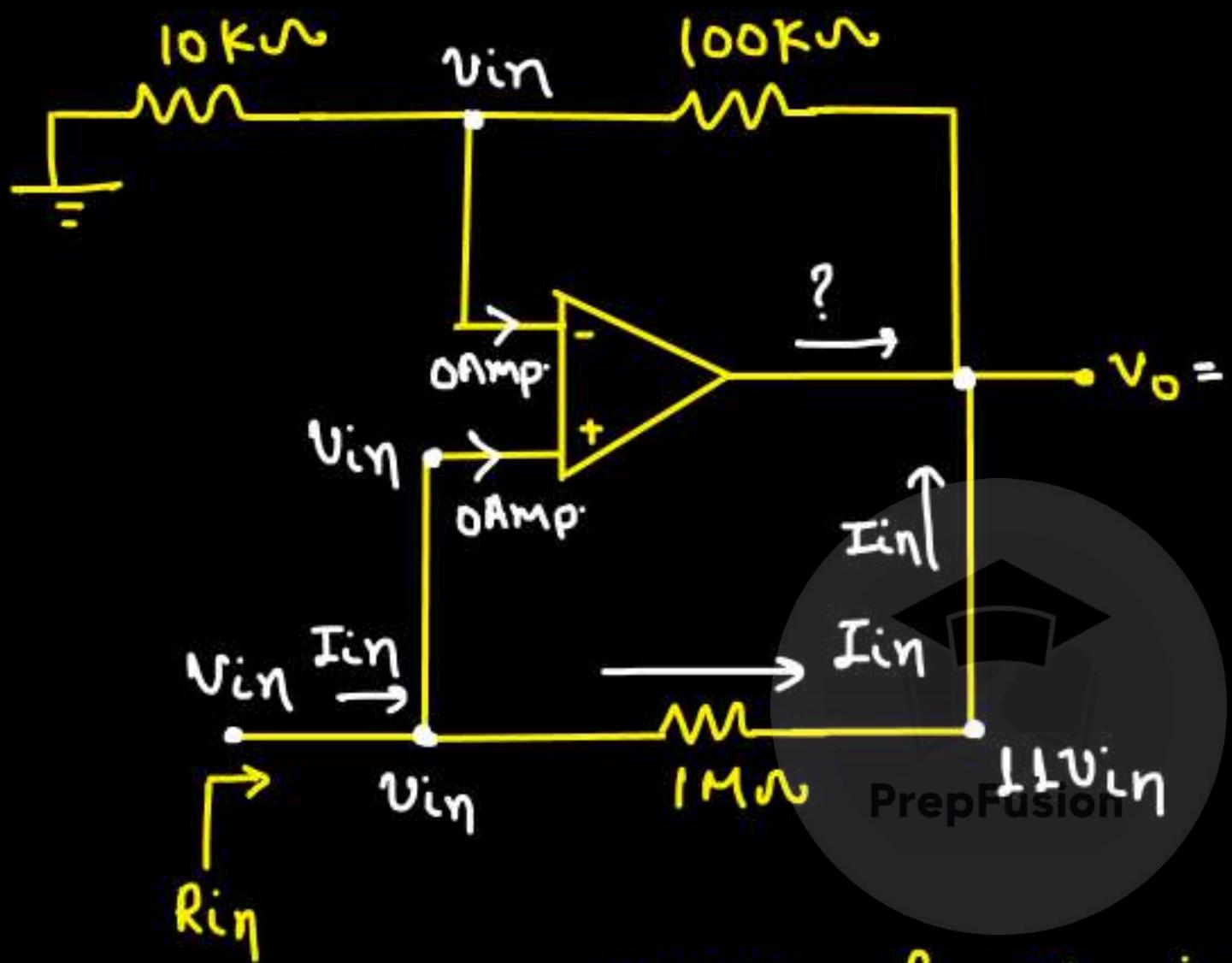

$$V_o = \left[1 + \frac{100}{10}\right] V_{in} = 11 V_{in}$$


$$R_{in} = \frac{V_{in}}{I_{in}}$$

Value of R_{in} is -100 kohm.

$$\frac{V_{in} - 11V_{in}}{1M\Omega} = I_{in} \Rightarrow$$

$$R_{in} = \frac{V_{in}}{I_{in}} = -100k\Omega$$

Q.

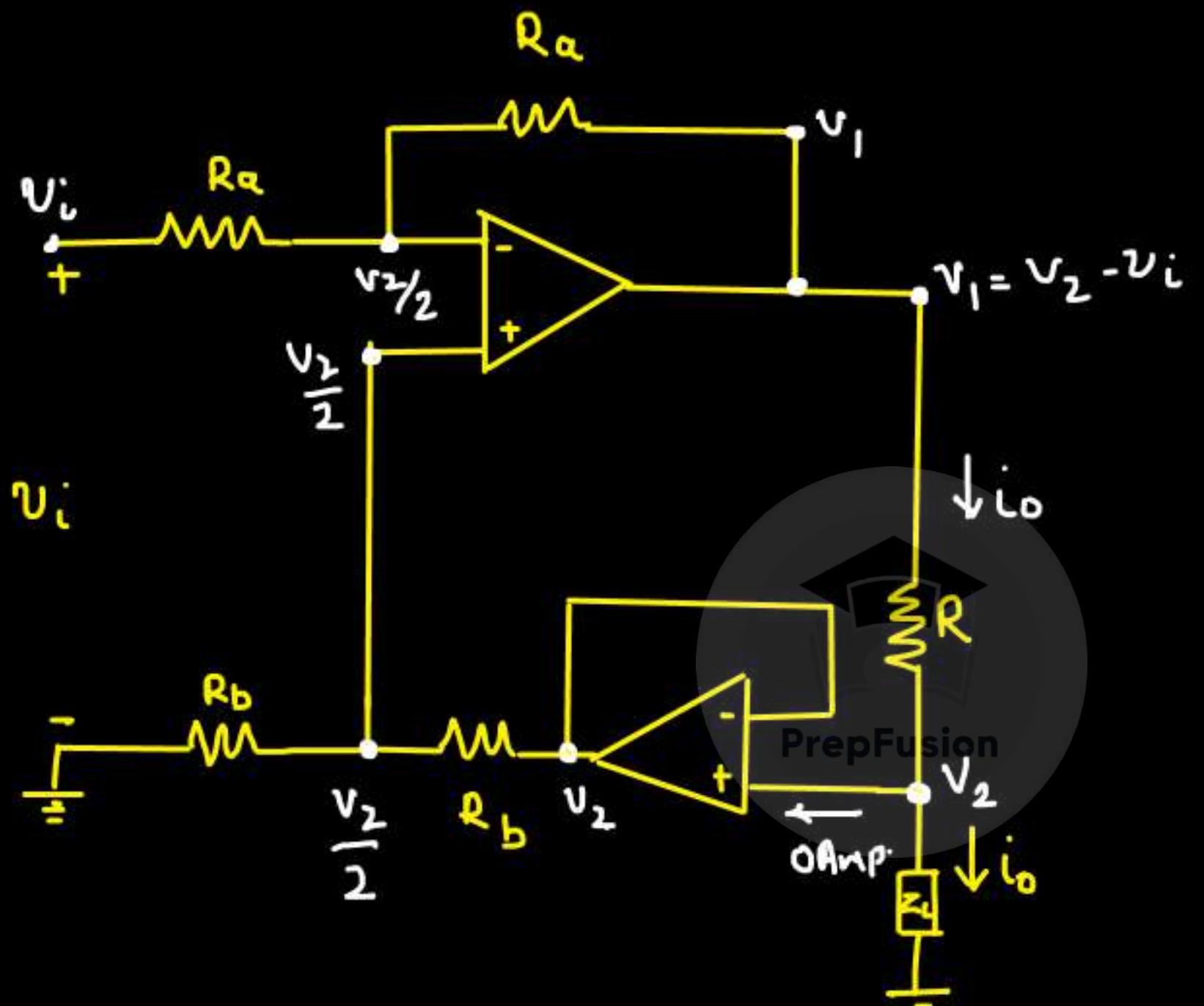

$$\frac{v_i + v_1}{2} = \frac{v_2}{2} \Rightarrow v_1 = v_2 - v_i$$

Find the expression of i_o


$$[i_o \neq f(z_L)]$$

$$i_o = \frac{v_1 - v_2}{R}$$

$$i_o = -\frac{v_i}{R}$$



Q.

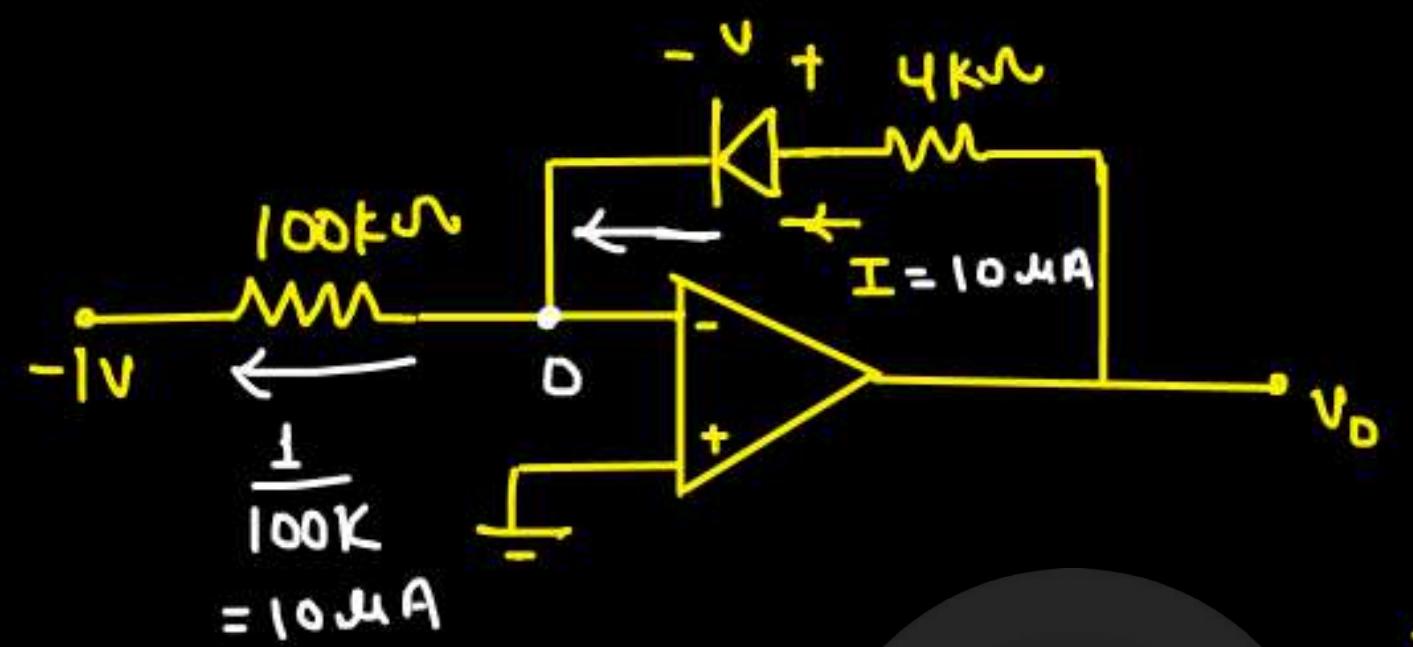

$$I = I_0 [e^{V/V_T} - 1]$$

For the diode $I = I_0 [e^{V/V_T} - 1]$


PrepFusion $V_T = 25\text{mV}$, $I_0 = 1\mu\text{A}$

Value of V_D is ____ mV.

↪ $I = I_0 [e^{V/V_T} - 1]$

$$10\mu\text{A} = 1\mu\text{A} [e^{V/25\text{mV}} - 1] \Rightarrow V = 0.06\text{V}$$

$$V = 25\text{mV} \ln(11)$$

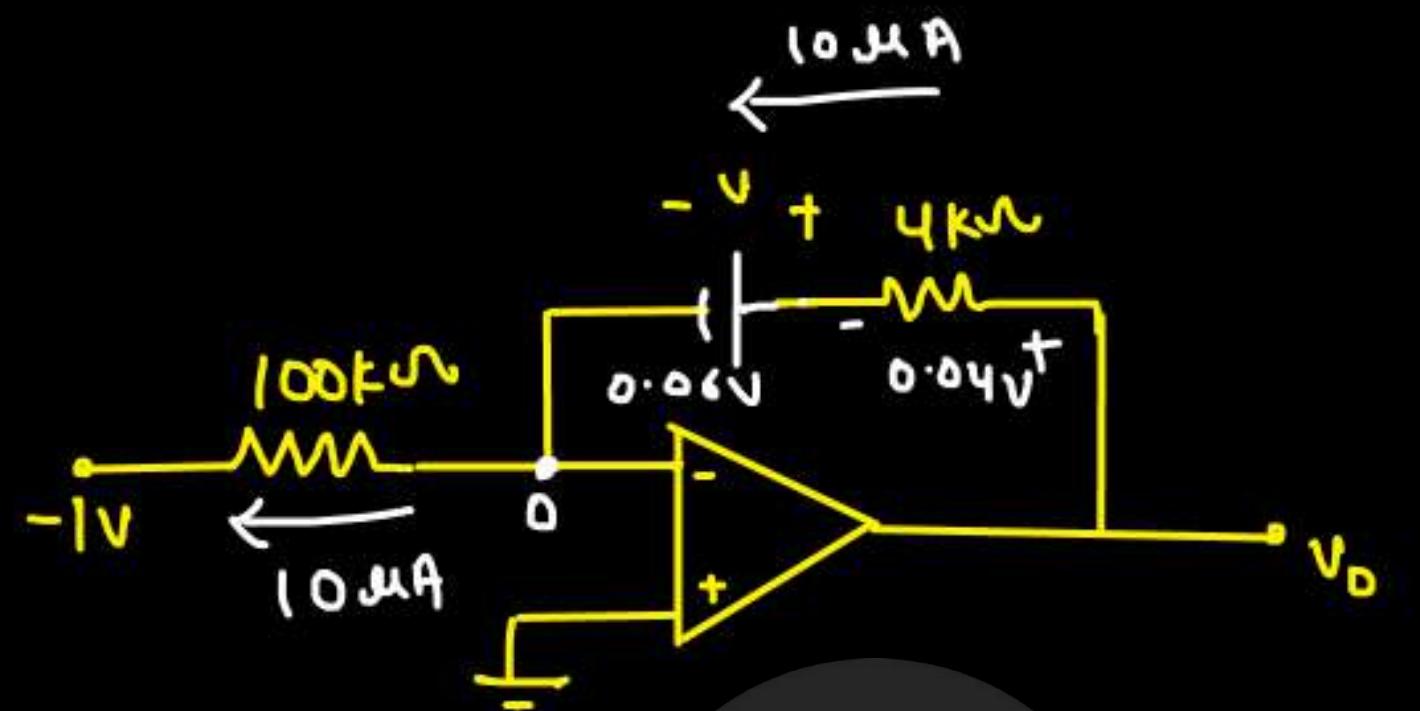


$$V_o = 0 + 0.06 + 0.04$$

PrepFusion

$$V_o = 0.1 V_o \text{ (incorrect)}$$

Q.

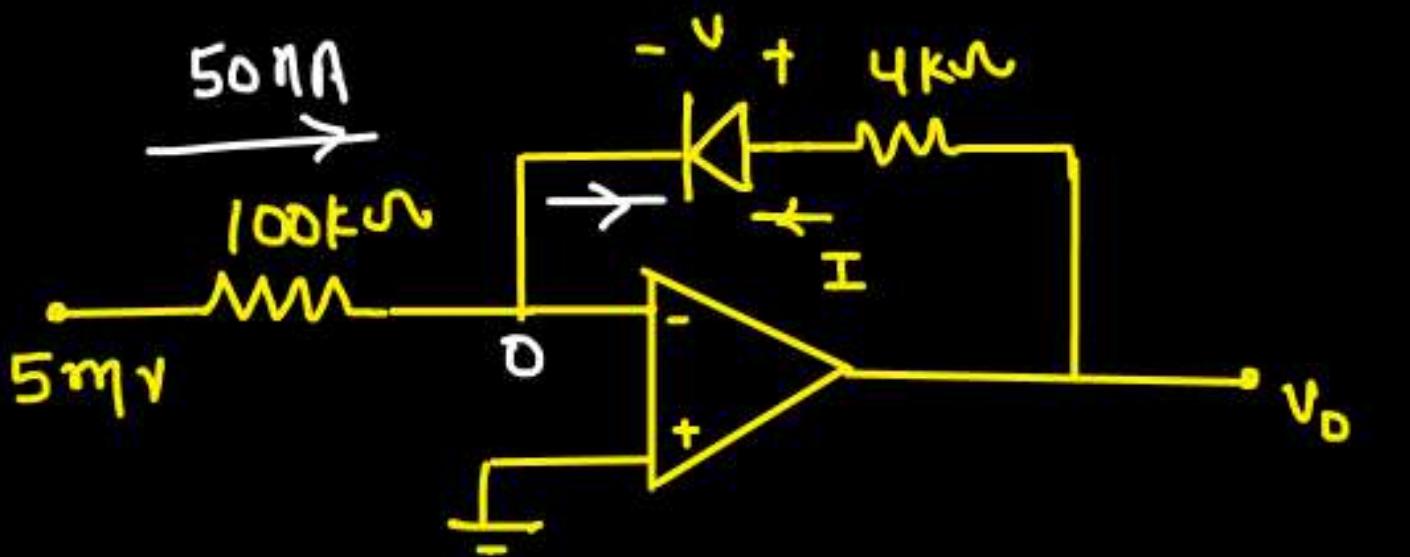


For the diode $I = I_0 [e^{\frac{v}{v_T}} - 1]$

$$v_T = 25 \text{ mV}, I_0 = 1 \mu\text{A}$$

Value of v_D is ____ mV.

→ Assuming, diode is giving me some finite voltage \Rightarrow neg feedback is true

Virtual short
is valid

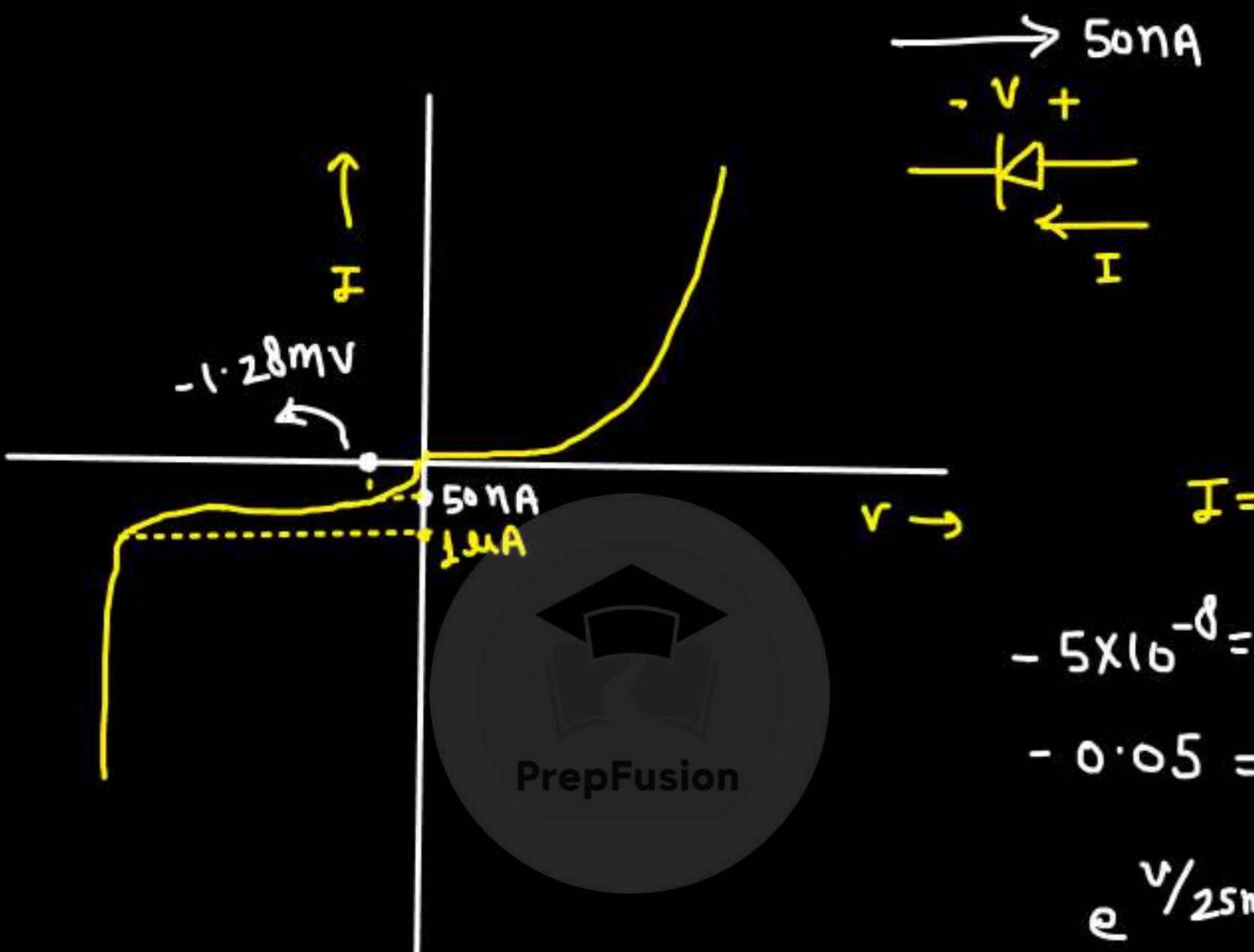



$$-5 \times 10^{-8} = 1 \times 10^{-6} [e^{V/25\text{mV}} - 1]$$

$$-0.05 = e^{V/25\text{mV}} - 1$$

$$e^{V/25\text{mV}} = 0.95$$

$$V = -1.28\text{mV}$$

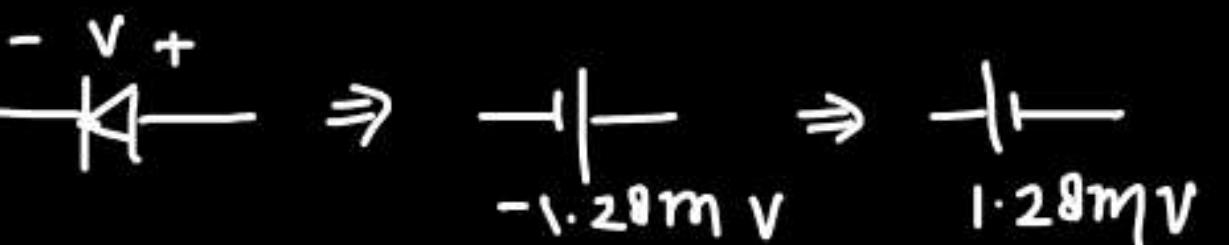


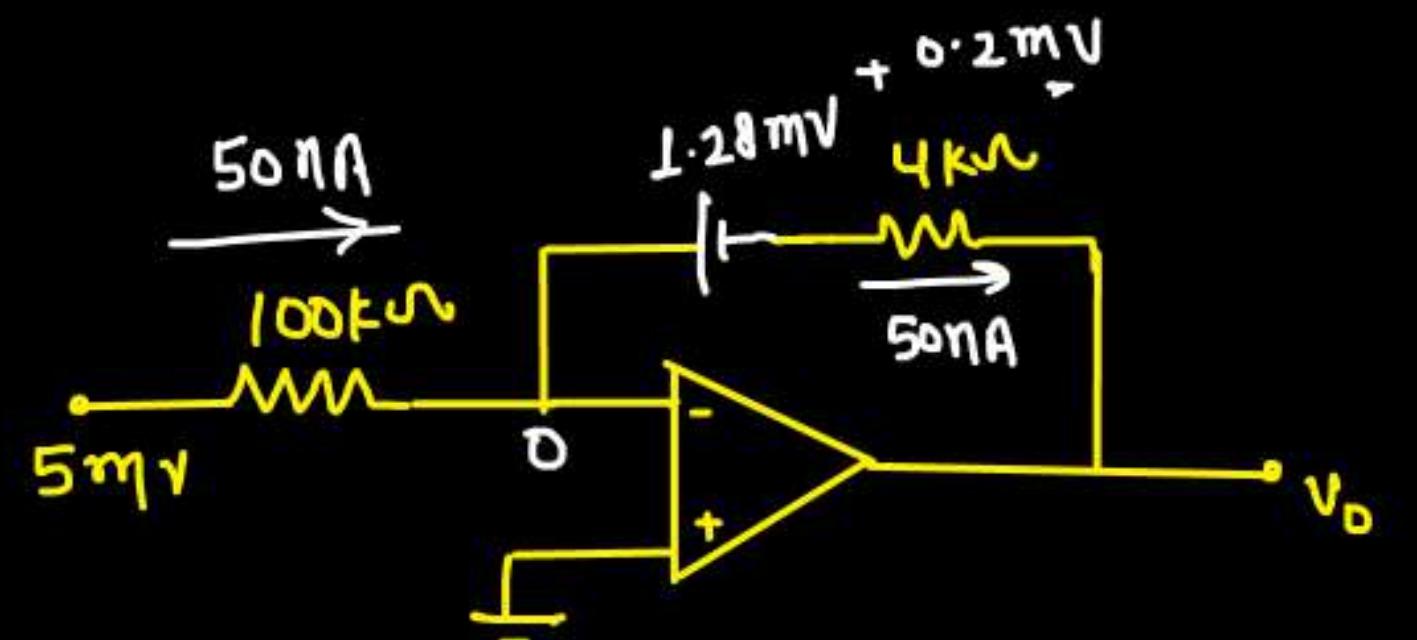

$$V_o = 0 - 1.28 \text{ mV} - 0.2 \text{ mV}$$

$$V_o = -1.48 \text{ mV}$$
PrepFusion

Q.

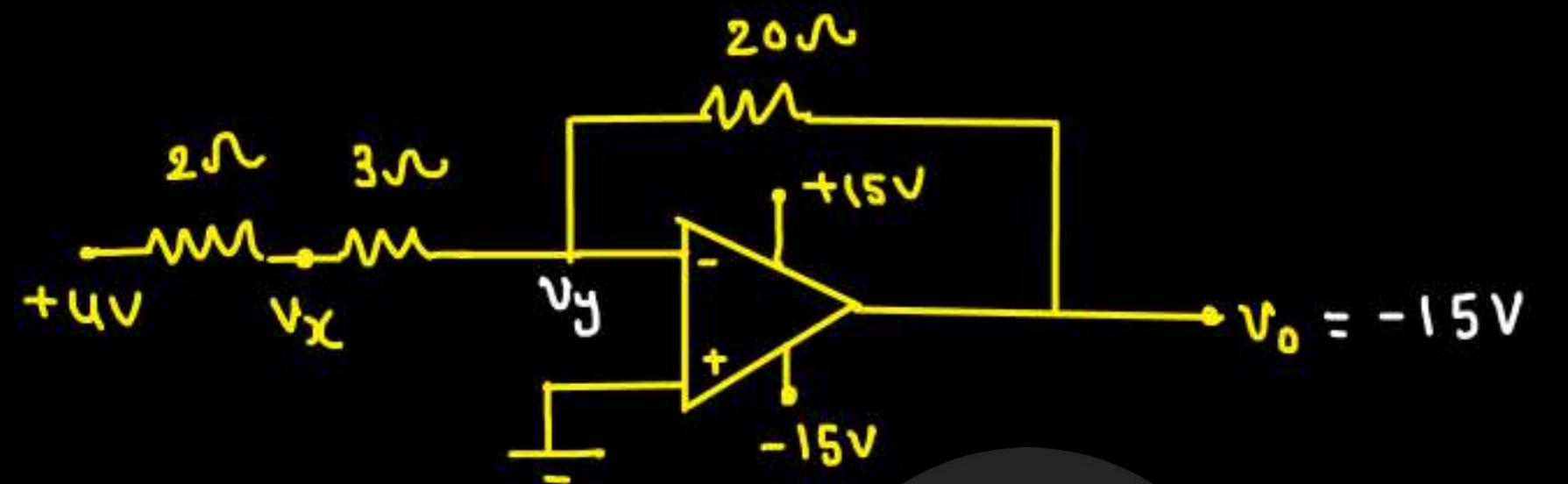


The potential @ node X is — ?

PrepFusion

$$v_o = \left(-\frac{20}{5} \right) 4 = -16V \times \underbrace{\quad}_{\downarrow}$$


virtual short not valid

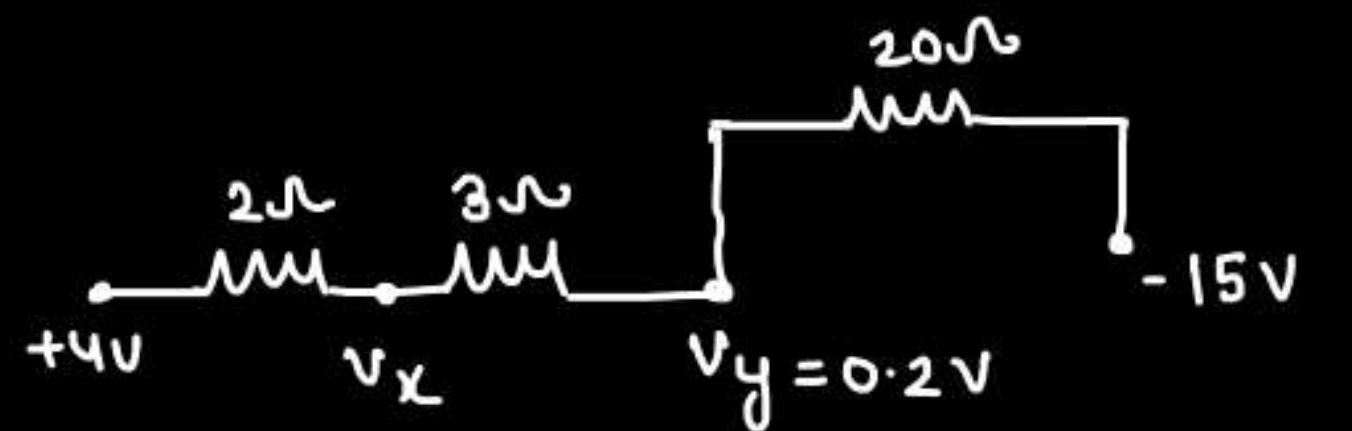

$$v_y = \frac{-15(5) + 4(20)}{25} = 0.2 \text{ V}$$


$$v_x = \frac{0.2(2) + 4(3)}{5} = \frac{(2 + 0.4)}{5} = 2.48 \text{ V}$$


Q.

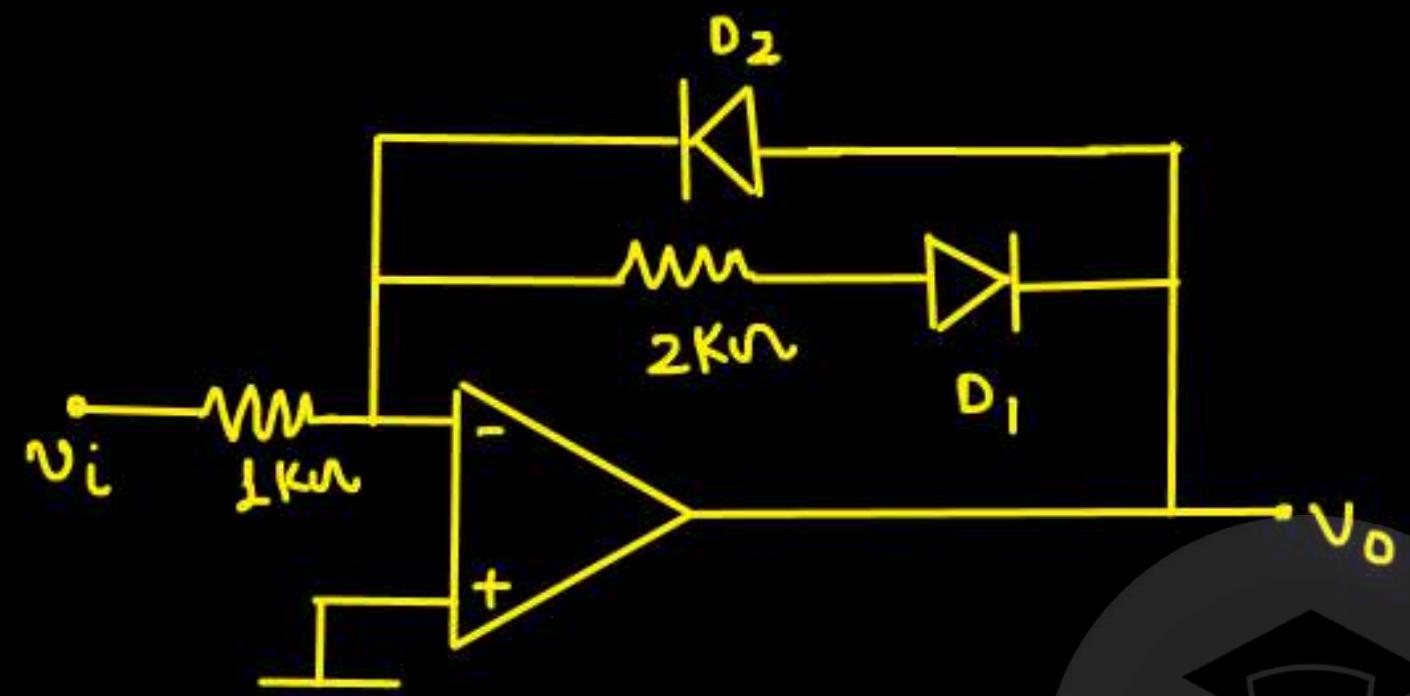



forward voltage drop for both of the diode is 0.7V.

find the avg. value of V_0 .

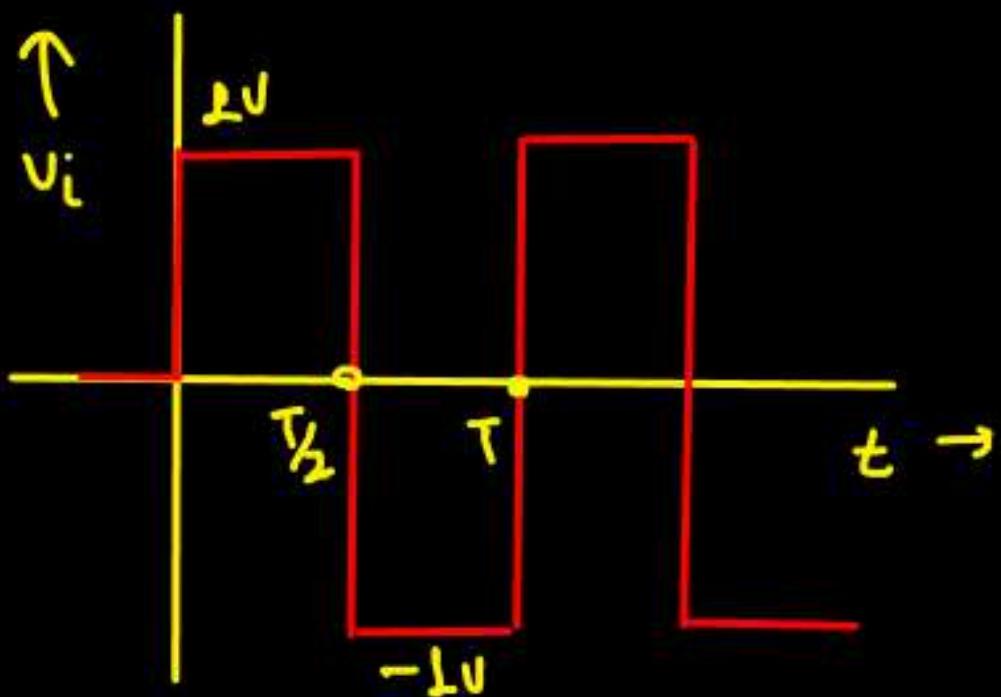

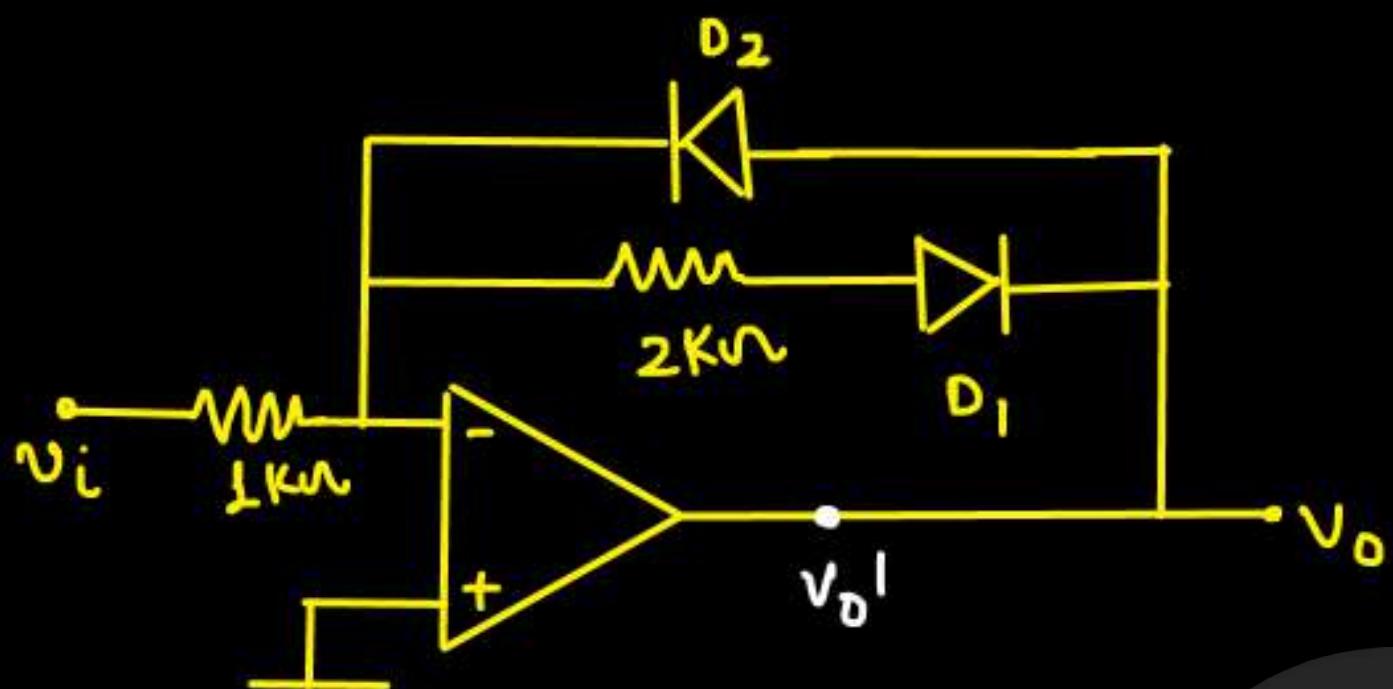
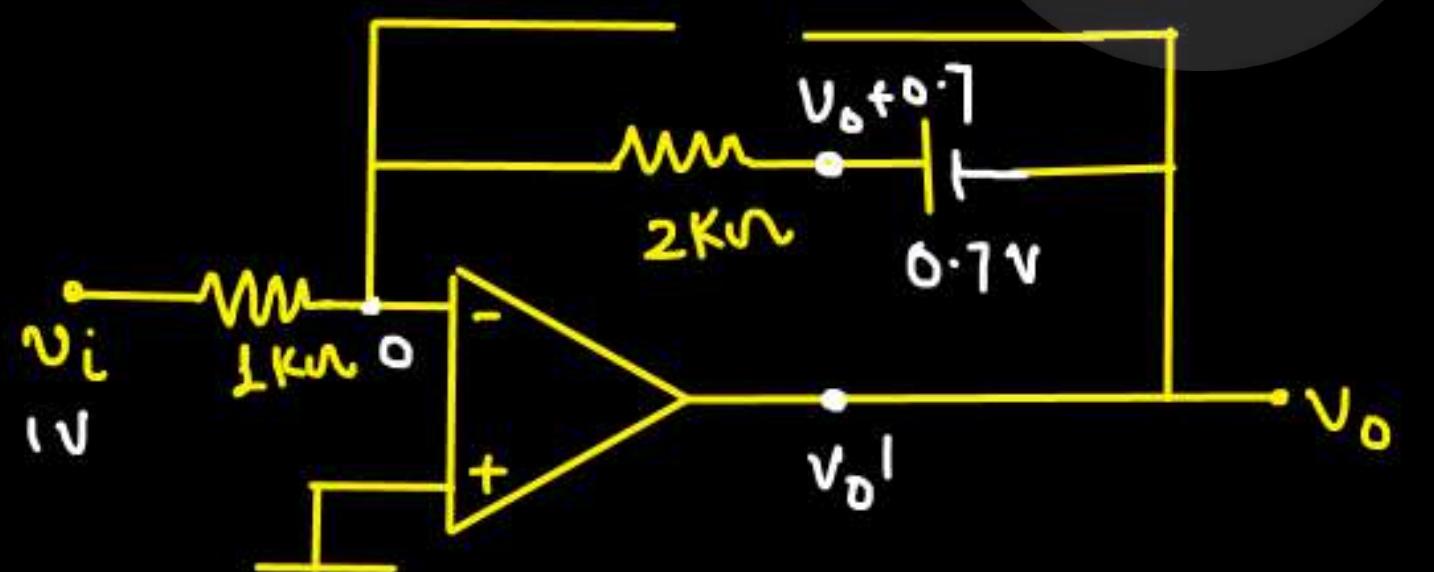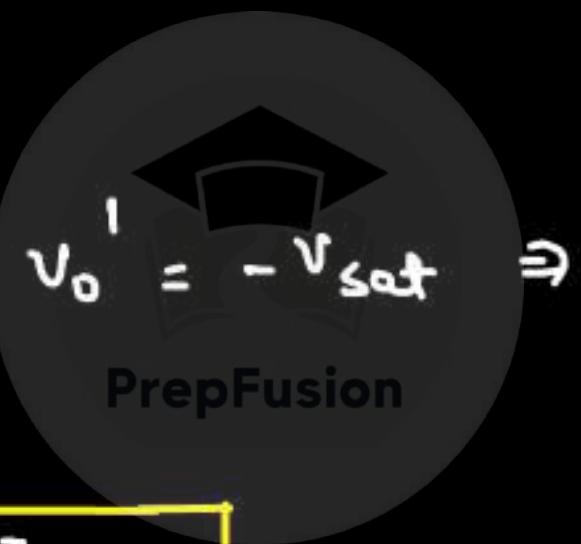
$$0 < t < T/2 \Rightarrow v_i = +1V \Rightarrow v_o' = -V_{sat} \Rightarrow D_1 \text{ ON}, D_2 \text{ OFF}$$




$$\frac{-v_i}{1k} + \left(\frac{0 - v_o - 0.7}{2k} \right) = 0$$

$$-2v_i - v_o - 0.7 = 0$$

$$v_o = -2.7V \quad \left\{ 0 < t < T/2 \right\}$$

$T/2 < t < T$:-

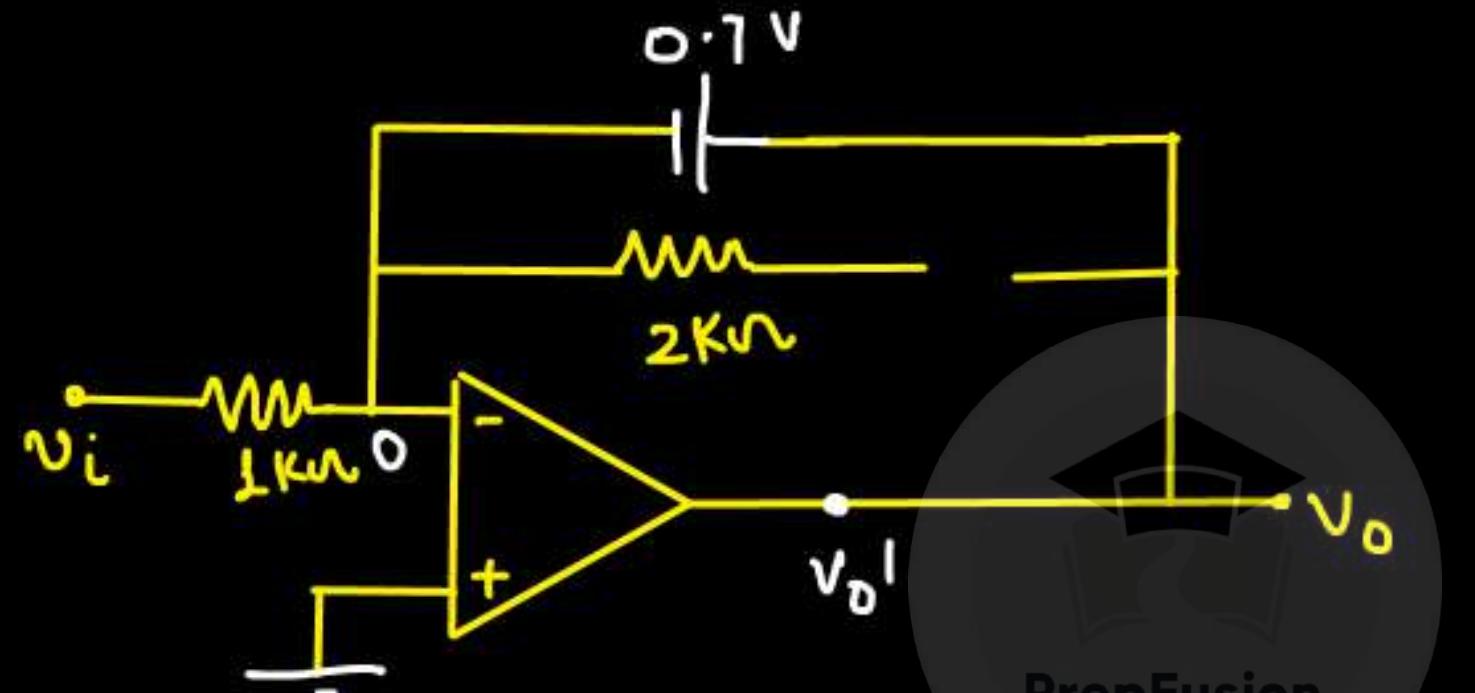
$$v_i = -1 \text{ V} \Rightarrow v_o^1 = +v_{\text{sat}} \Rightarrow D_2 \text{ ON}, D_1 \text{ OFF}$$




$$v_o = 0.7 \text{ V} \quad \{ T/2 < t < T \}$$

$$(v_o)_{\text{avg.}} = \frac{(-2.7) T/2 + (0.7) T/2}{T}$$

$$(v_o)_{\text{avg.}} = -1 \text{ V}$$

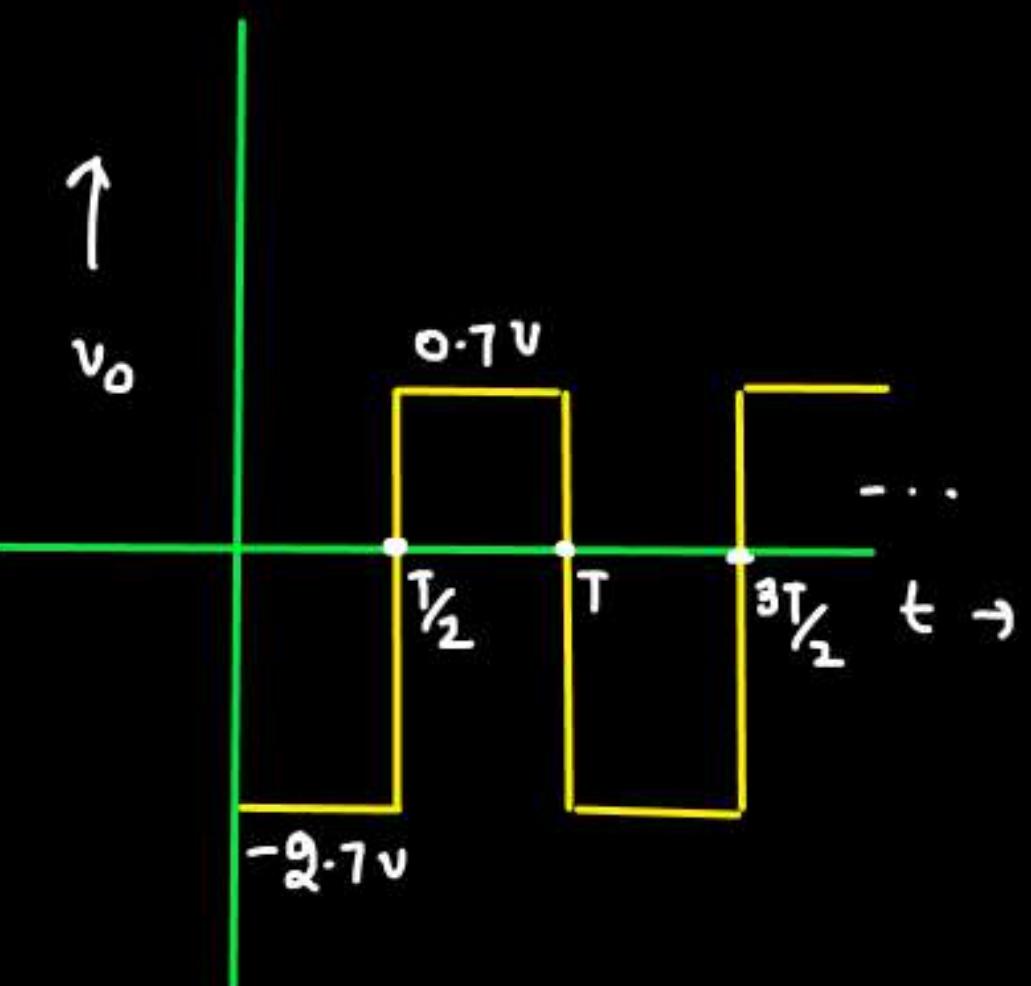

Q.


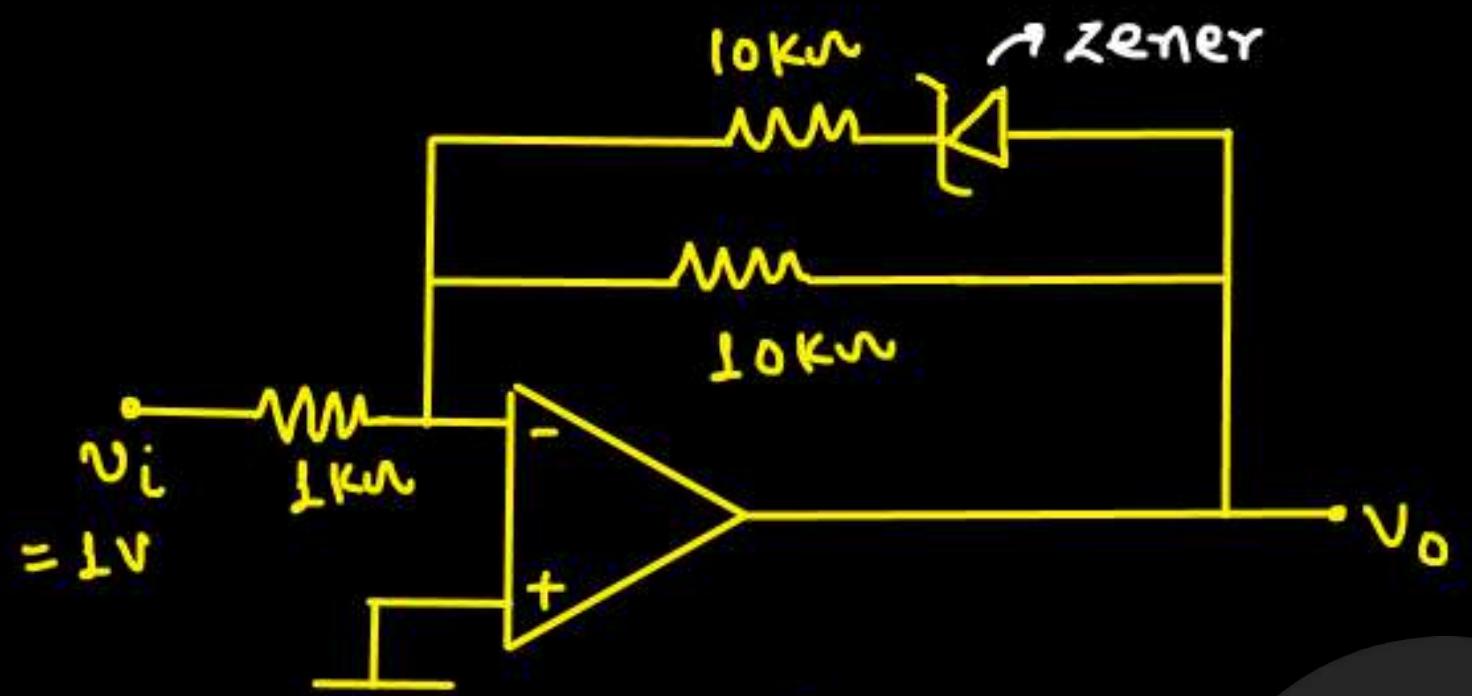



Breakdown voltage of zener diode = 3.2V

Find V_o .

PrepFusion

→ Applying O.C. Test :-

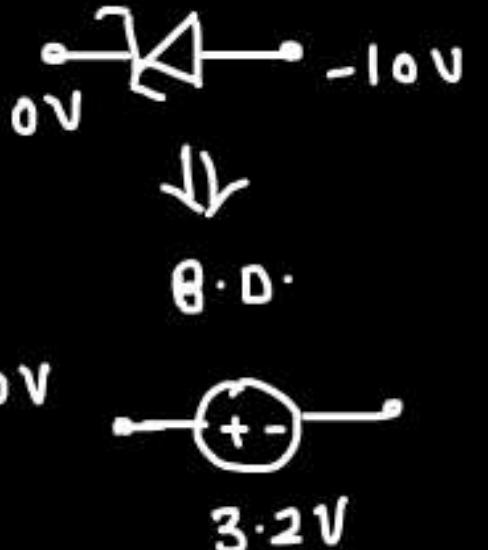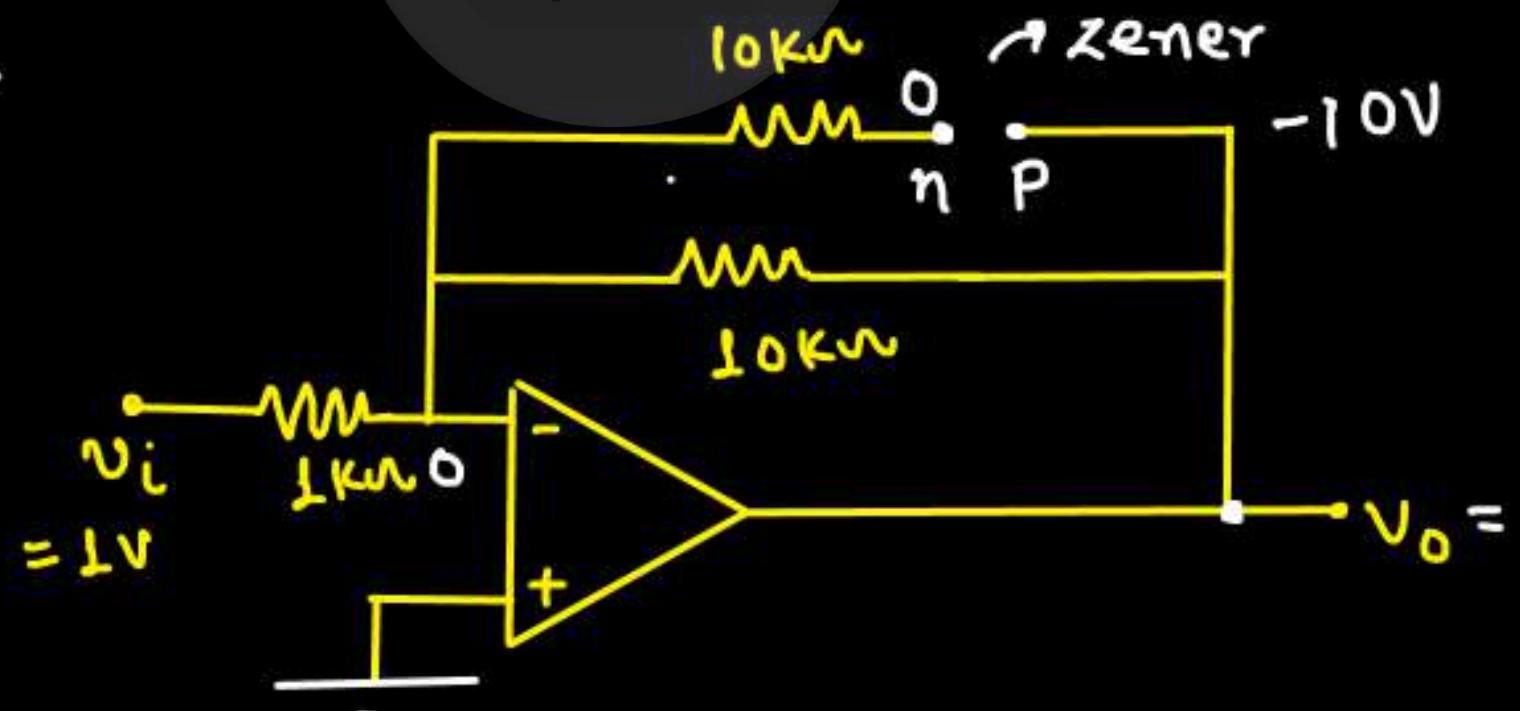

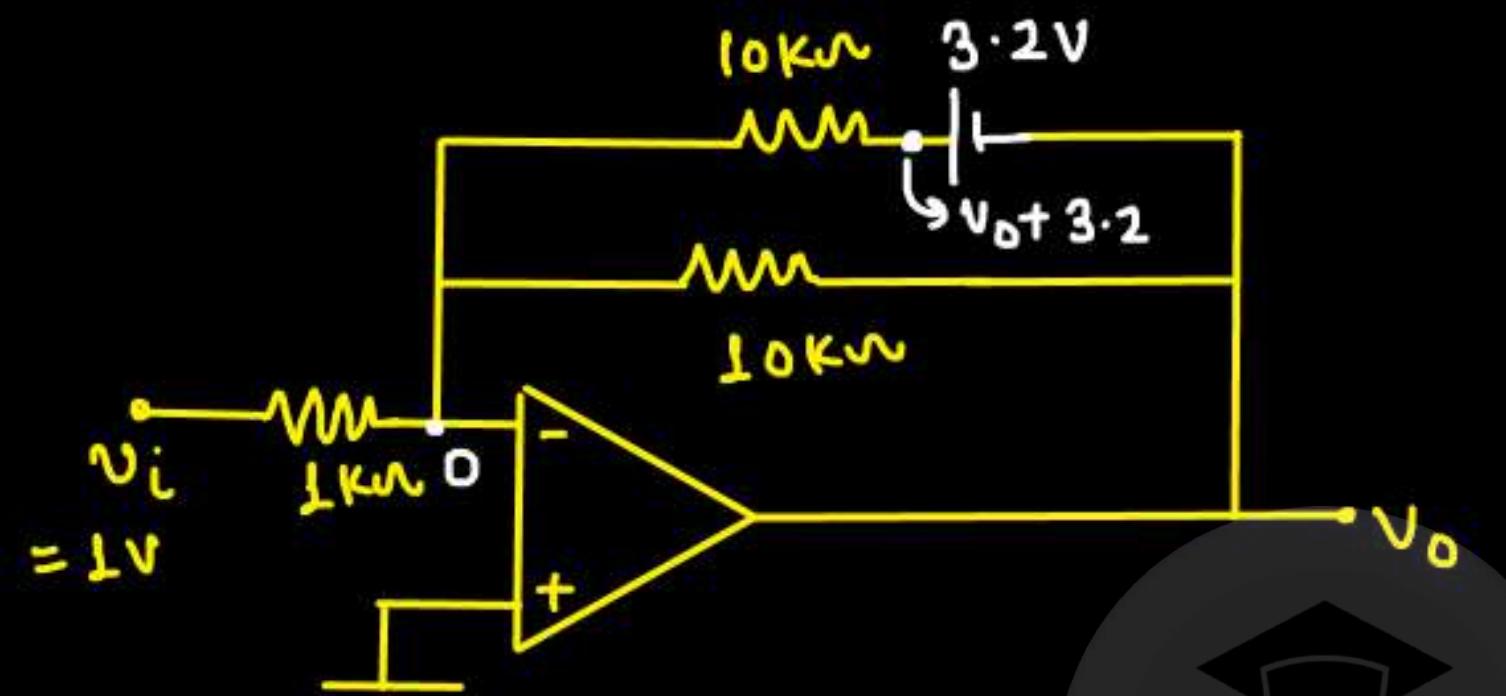

$$\frac{0 - 1}{1k} + \frac{0 - V_o}{10k} + 0 - \frac{(V_o + 3.2)}{10k} = 0$$


$$-10 - V_o - V_o - 3.2 = 0$$


$$2V_o \approx -13.2$$

$V_o = -6.6 \text{ V}$



Q.

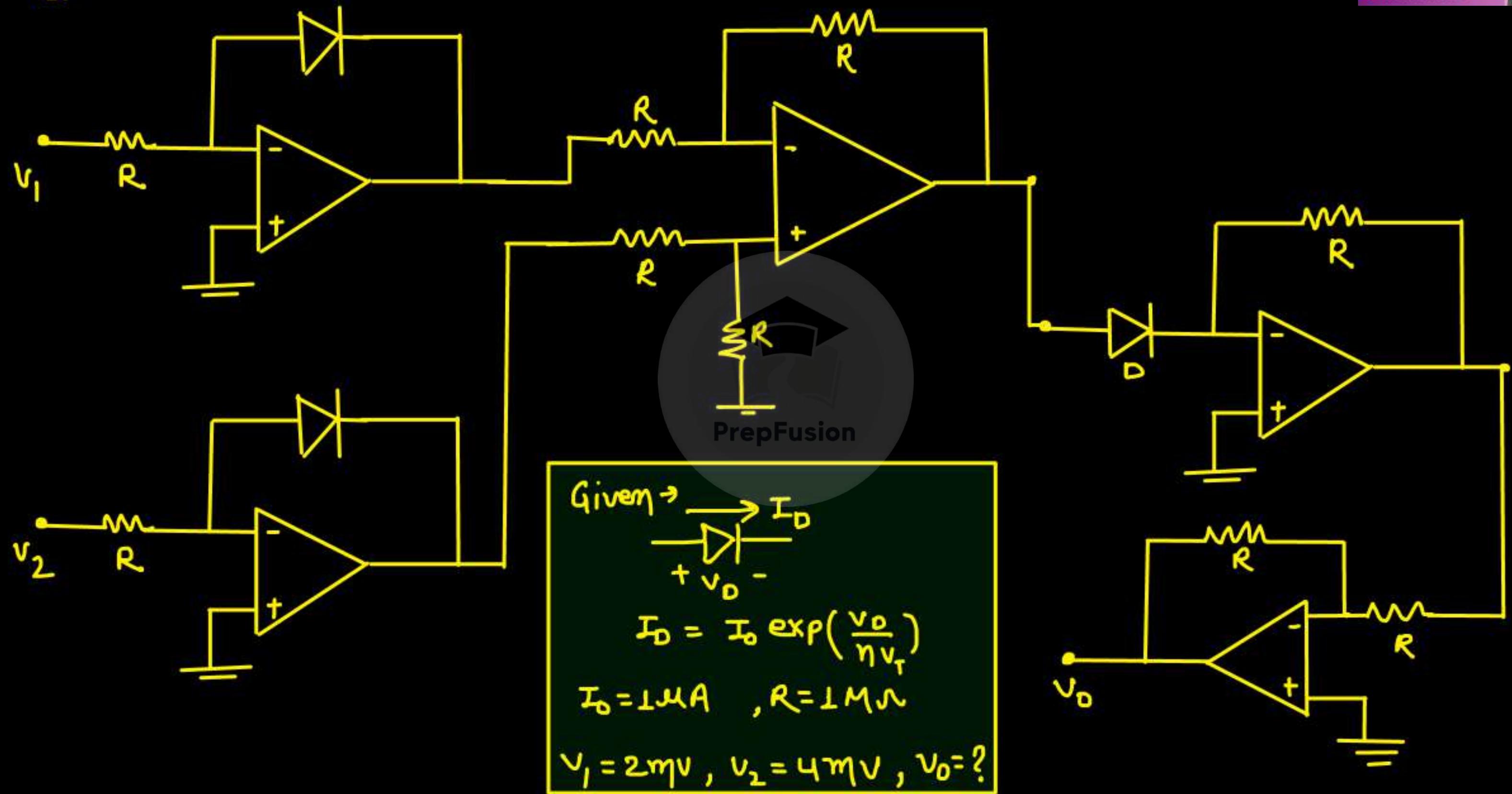

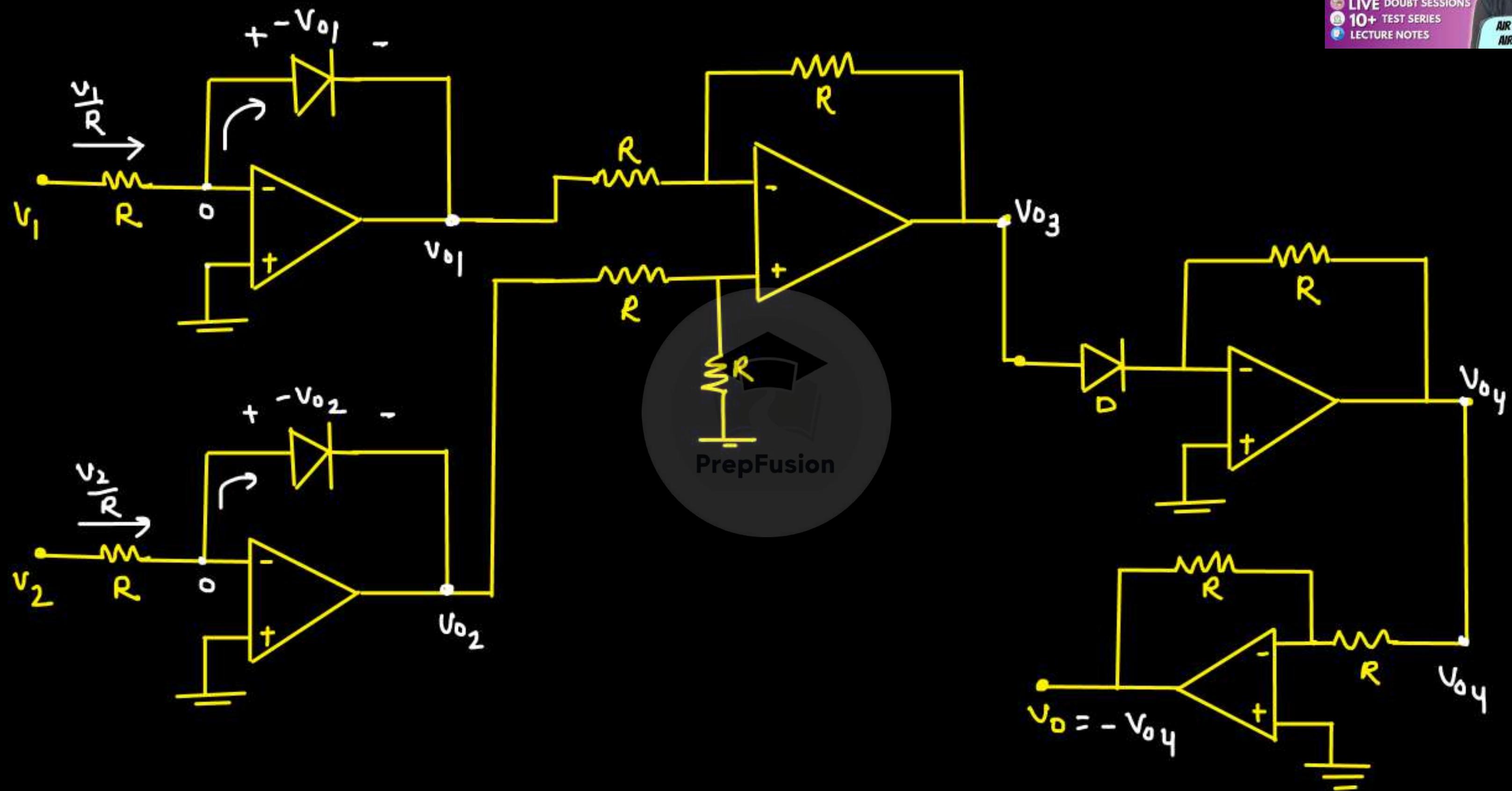


$$\frac{V_1}{R} = I_D \exp \left[-\frac{V_{D1}}{nV_T} \right]$$

$$V_{D1} = -nV_T \ln \left[\frac{V_1}{I_D R} \right] \quad \text{--- (1)}$$

$$V_{D2} = -nV_T \ln \left[\frac{V_2}{I_D R} \right] \quad \text{--- (2)}$$

$$\begin{aligned} V_{D3} &= \frac{R}{R} [V_{D2} - V_{D1}] \\ &= -nV_T \ln \left(\frac{V_2}{I_D R} \right) + nV_T \ln \left(\frac{V_1}{I_D R} \right) \\ &= nV_T \left[\ln \left(\frac{V_1}{I_D R} \right) - \ln \left(\frac{V_2}{I_D R} \right) \right] \end{aligned}$$
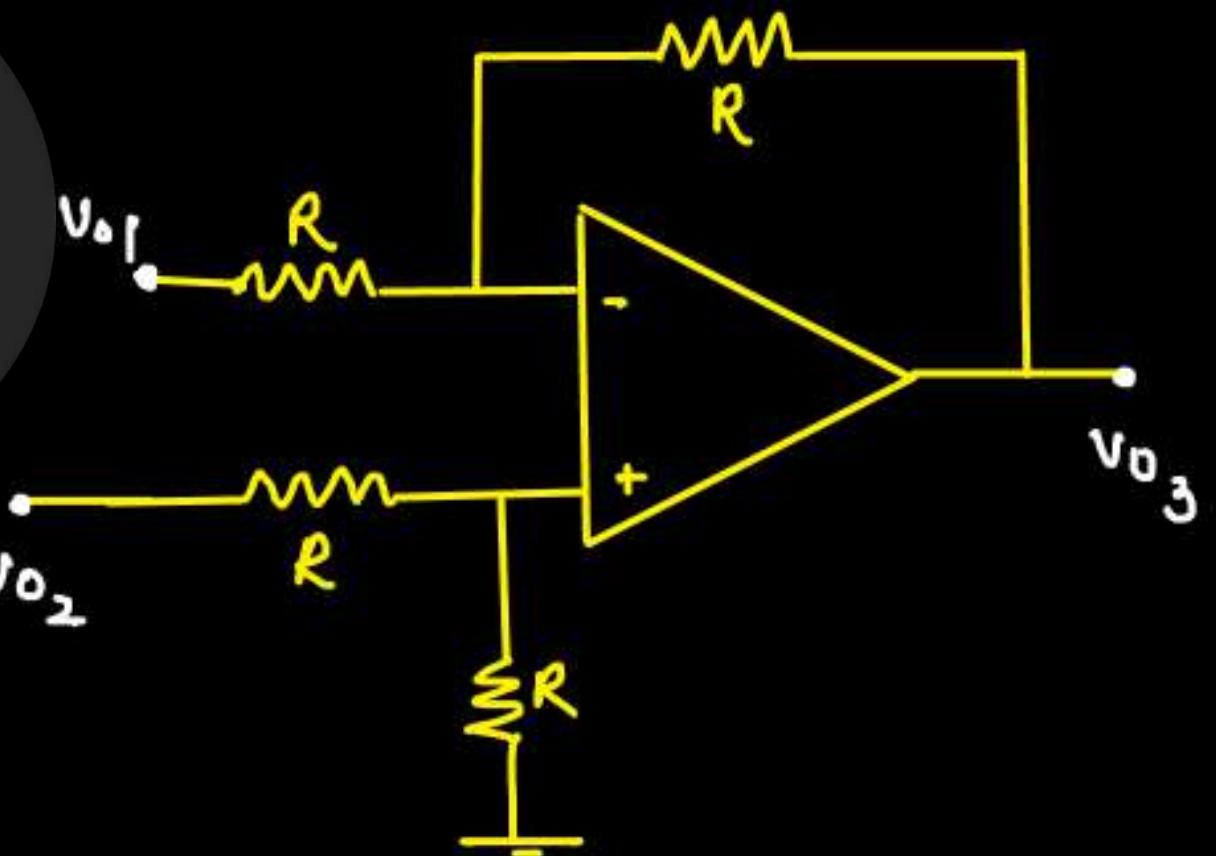
$$V_{D3} = nV_T \ln \left(\frac{V_1}{I_D R} \times \frac{I_D R}{V_2} \right)$$



$$V_{o3} = \eta V_T \ln \left(\frac{v_1}{v_2} \right) \quad \text{--- (3)}$$

$$V_{o4} = -I_D R$$

$$V_{o4} = -I_D \exp \left[\frac{V_{o3}}{\eta V_T} \right] R$$


$$V_{o4} = -I_D R \exp \left[\frac{\eta V_T \ln \left(\frac{v_1}{v_2} \right)}{\eta V_T} \right]$$

$$V_{o4} = -I_D R \exp \left[\ln \left(\frac{v_1}{v_2} \right) \right]$$

$$V_{o4} = -I_D R \left(\frac{v_1}{v_2} \right) \quad \text{--- (4)}$$

$$V_o = -V_{o4}$$
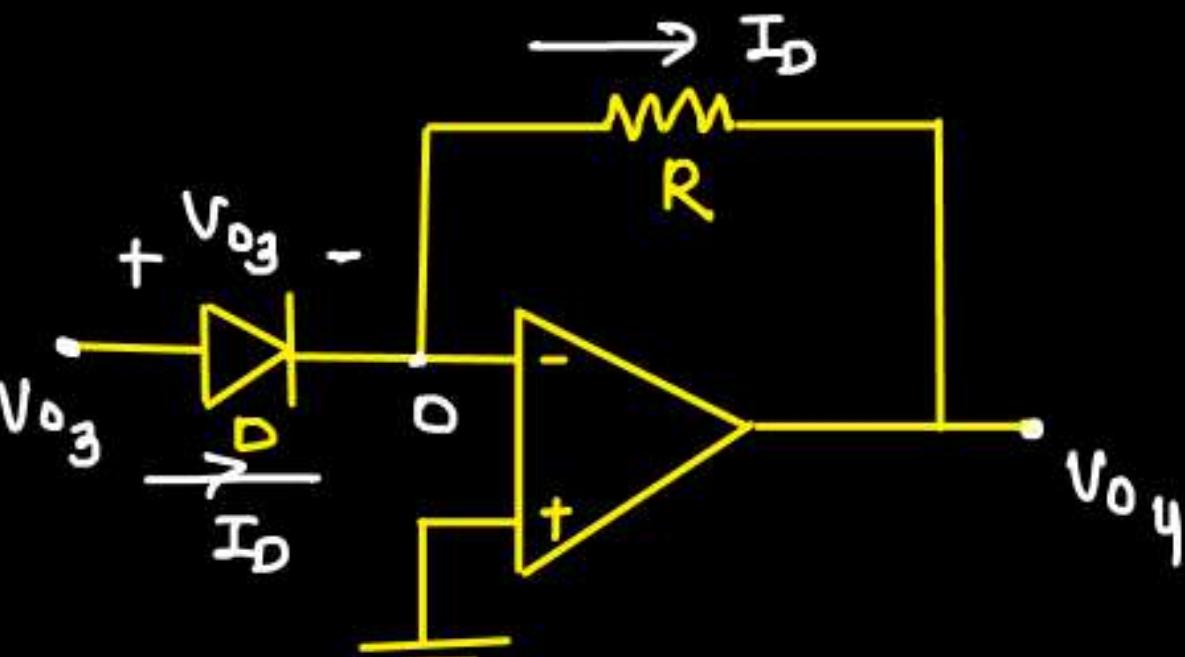
$$V_o = I_D R \left(\frac{v_1}{v_2} \right)$$



$$V_o = 1\mu \times 1m \left(\frac{2m}{4m} \right)$$

Ans
★

$$V_o = 0.5V$$



Filters:-

Passes a particular range of frequencies.

- (a) LPF
- (b) HPF
- (c) BPF
- (d) BSF
- (e) SPPF



PrepFusion

Basics of Analog Filters || Analog VLSI Mastery (Cohort 0-10) ||
Himanshu Agarwal
856 views • 3 months ago

Himanshu Agarwal

On our channel, you will get 1) Comprehensive Courses 2) Lecture Notes 3) Assignments This course is helpful for Placements in ...

4K

ANALOG VLSI MASTERY

BASICS OF CONTROL THEORY

LECTURE -49


BASICS OF ANALOG FILTERS

COHORT (0-10) BY HIMANSHU AGARWAL
GATE AIR-27 (ECE)
GATE AIR-45 (IN)
ANALOG ENGINEER AT TI

SUBSCRIBE 

1:27:19

Passive Filter:-

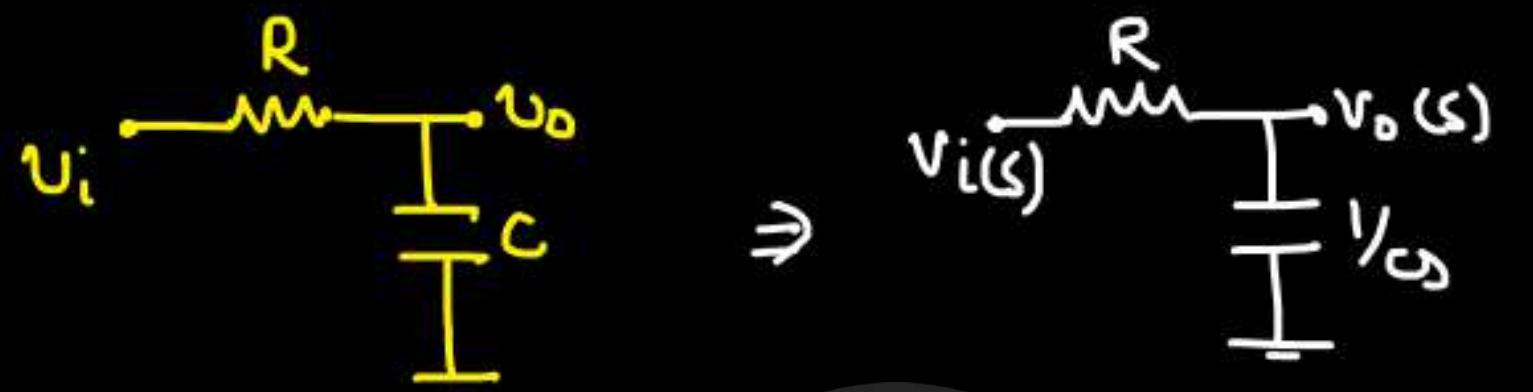


Unity gain B.W.

$$|T(j\omega)| = \frac{1}{\sqrt{1+\omega^2 R^2 C^2}}$$

$$|T(j\omega_{UQB})| = 1$$

$$\omega_{UQB} = 0 \text{ rad/sec.}$$

fixed

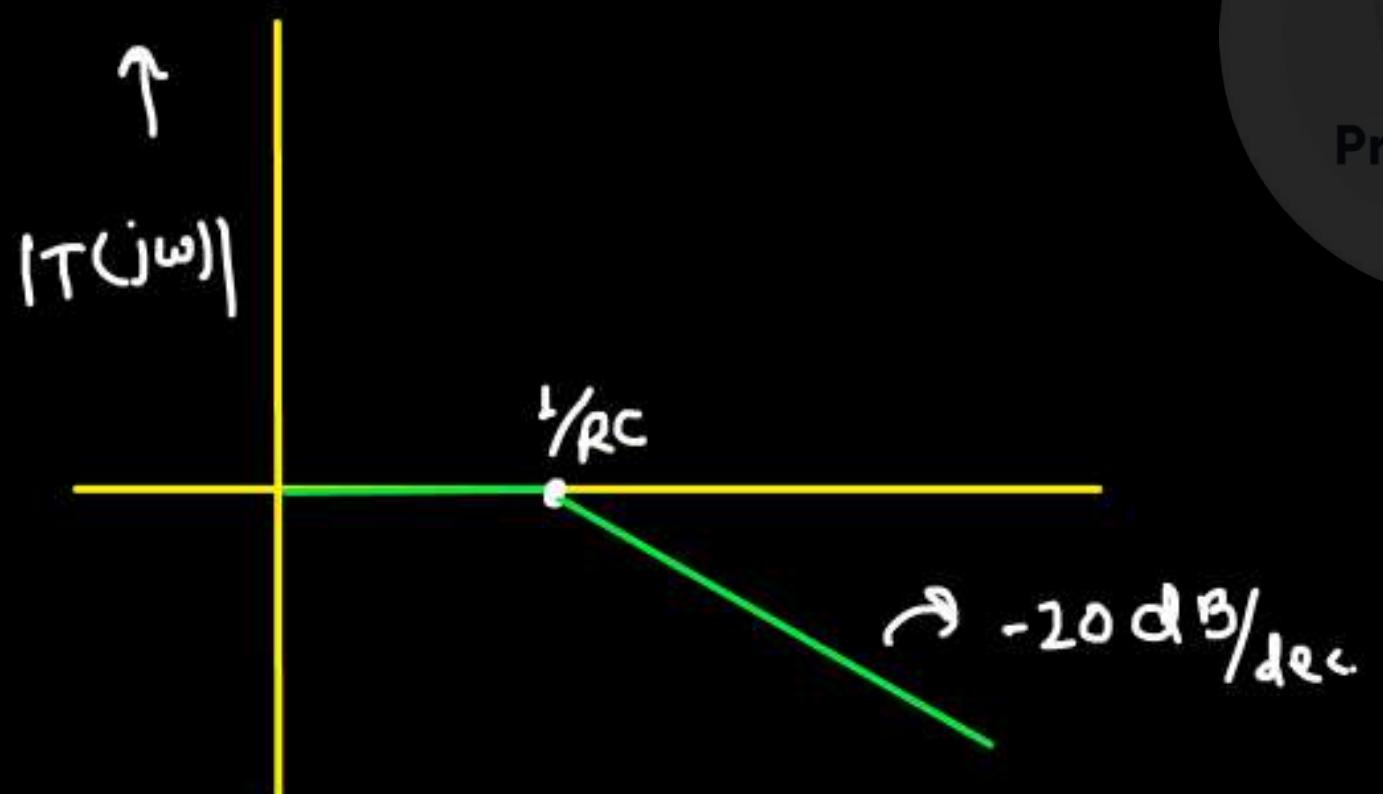

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCs}$$

PrepFusion


$$T(s) = \frac{1}{1 + RCs}$$

$$|T(j\omega)| = 1 = 0 \text{ dB}$$

Active filters:-

- ↳ filters made using active elements like op-amp.
Transistors etc.
- ↳ Using Active filters , you can adjust the dc gain and unity gain frequency of the filter.
- ↳ Using active filters, you can avoid loading effects while cascading.

① Low Pass Filter:-

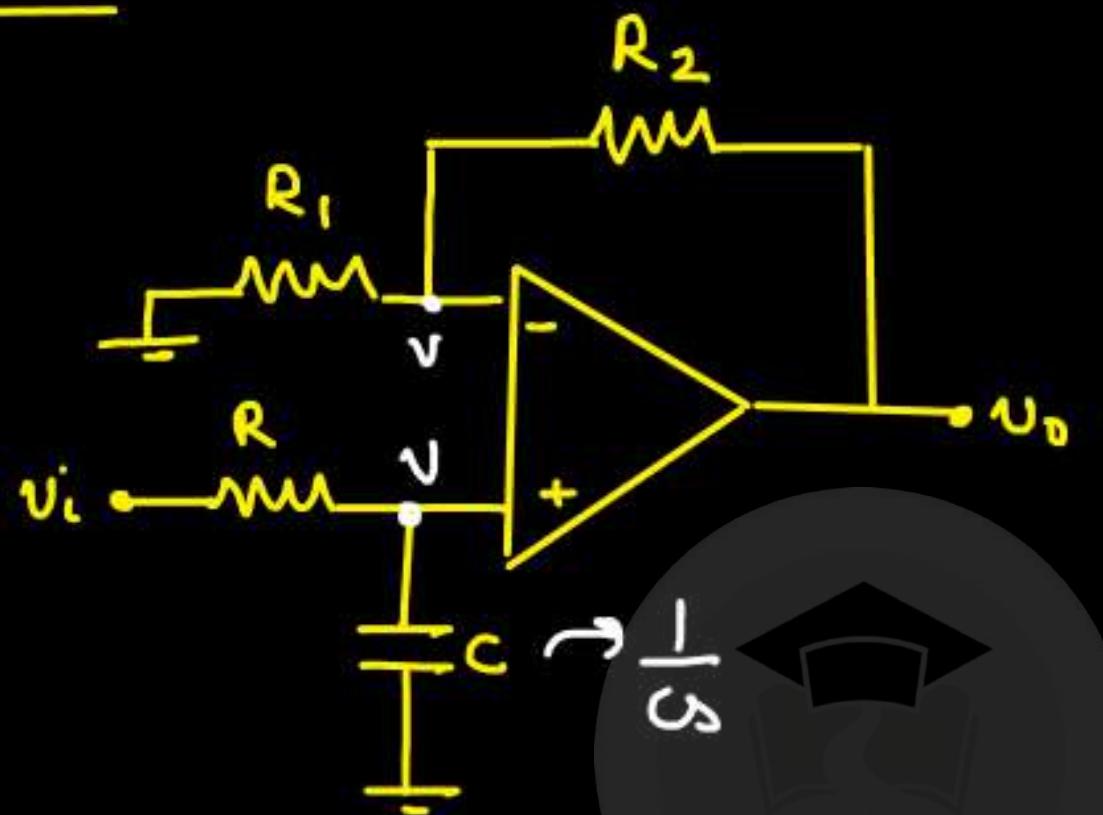

$$v_o(s) = \left(1 + \frac{R_2}{R_1}\right) v(s) \quad \text{PrepFusion} \quad \textcircled{1}$$

$$v(s) = \frac{1}{1 + RCs} v_i(s) \quad \textcircled{2}$$


By eqn ① and ②

$$\frac{v_o(s)}{v_i(s)} = \left(1 + \frac{R_2}{R_1}\right) \times \frac{1}{1 + RCs}$$

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + RCs}$$

at $\omega=0$ / dc gain

$$T(j0) = 1 + \frac{R_2}{R_1}$$

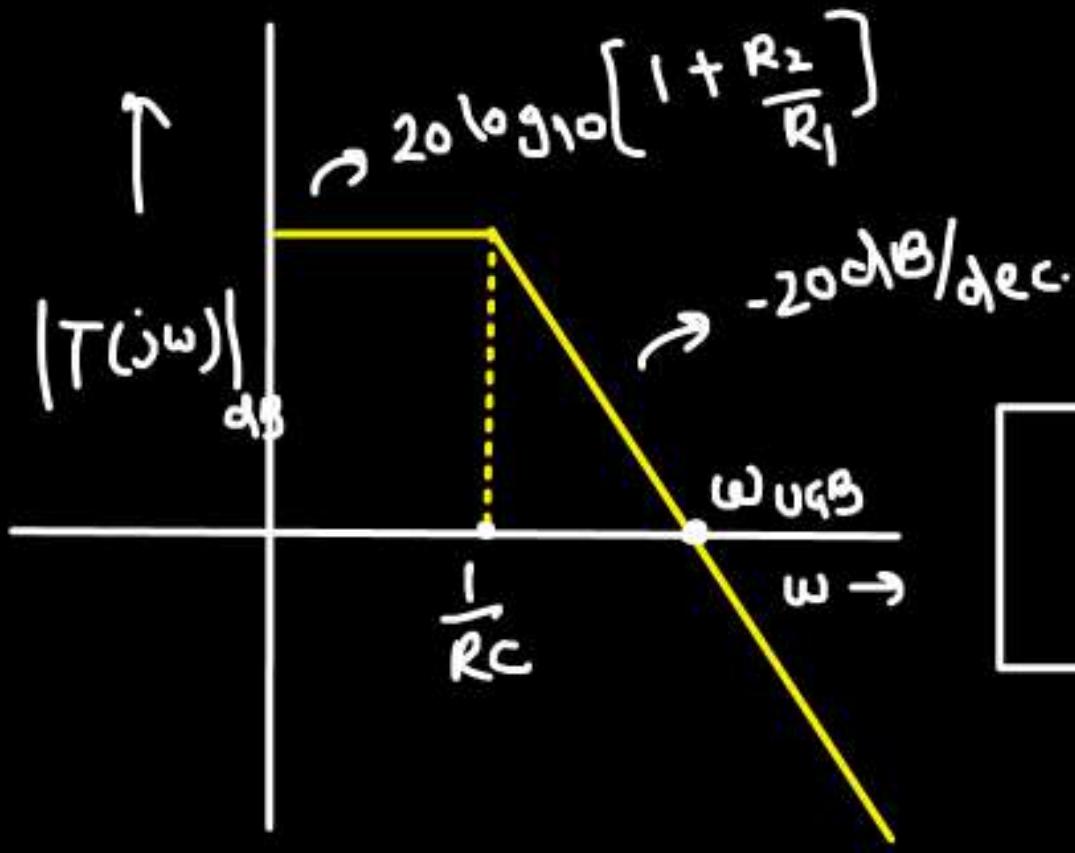


$$\omega_{3-dB} = \frac{1}{RC}$$

dc gain is adjustable by controlling R_2 and R_1 values

$$\omega_{UGB} = \text{dc gain} \times \omega_{3-dB}$$

$$\omega_{UGB} = \left(1 + \frac{R_2}{R_1}\right) \times \frac{1}{RC}$$

Ex:-

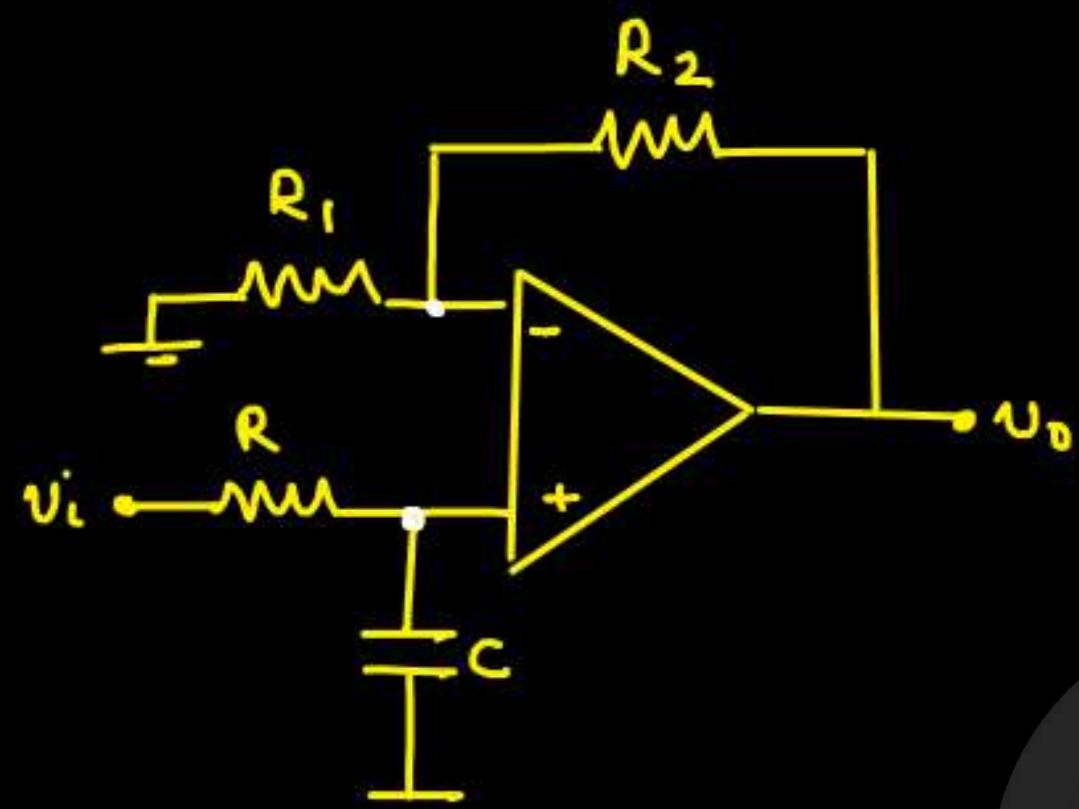

$$RC = 2 \text{ sec.}$$

$$\frac{R_2}{R_1} = 9$$

Find $\omega_{3-\text{dB}}$, ω_{UGB} and
dc gain.

$$T(s) = \frac{10}{2s + 1}$$

$$\rightarrow \text{dc gain} = 10$$

$$\rightarrow \omega_{3-\text{dB}} = \frac{1}{2} \text{ rad/sec.}$$

$$\rightarrow \omega_{\text{UGB}} \approx 10 \times \frac{1}{2} = 5 \text{ rad/sec.}$$


$$|T(j\omega)| = \frac{10}{\sqrt{1 + 4\omega^2}}$$

$$|T(j\omega_{\text{UGB}})| = \frac{10}{\sqrt{1 + 4\omega_{\text{UGB}}^2}} = 1$$

$$\Rightarrow \sqrt{\frac{99}{4}} = \omega_{\text{UGB}}$$

$$\omega_{\text{UGB}} = 4.97 \text{ rad/sec.}$$

② High Pass Filter :-

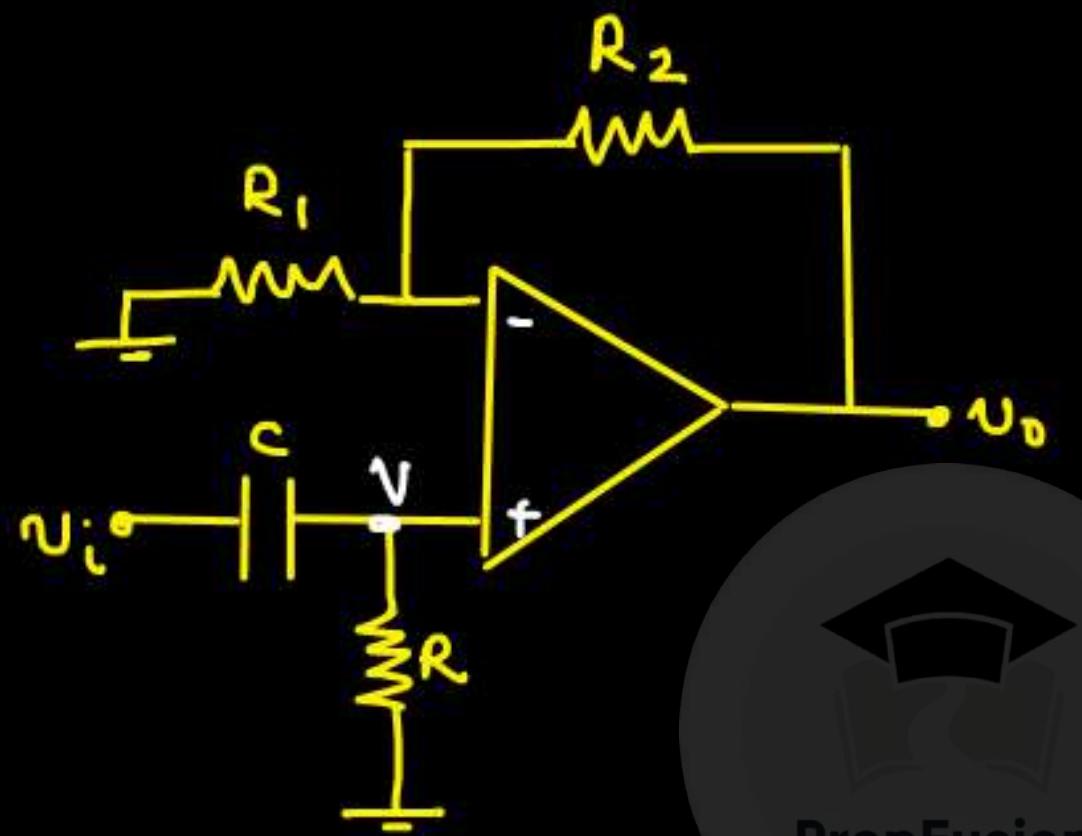

PrepFusion

$$v_o(s) = \left(1 + \frac{R_2}{R_1}\right) v(s)$$


$$v(s) = \frac{R}{R + \frac{1}{sC}} v_i(s) = \frac{RC}{RC + 1} v_i(s)$$

$$\Rightarrow v_o(s) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{RC}{RC + 1}\right) v_i(s)$$

$$T(s) = \frac{V_o(s)}{V_i(s)} = \left(1 + \frac{R_2}{R_1}\right) \times \frac{RC}{RC + s}$$

$$\omega_Z = 0$$

$$\omega_p = \frac{1}{RC}$$

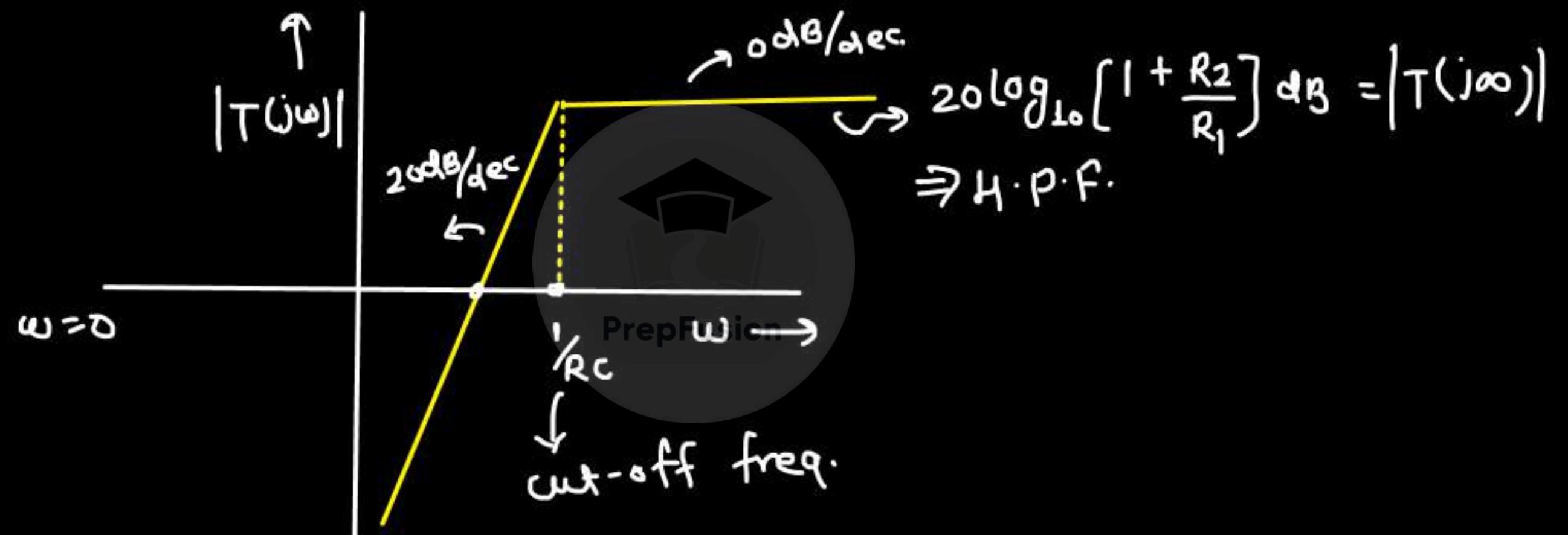

* How to check the type of filter without writing Transfer function:-

↳ Put $\omega=0$ and $\omega=\infty$

(i) if at $\omega=0 \Rightarrow V_o \neq 0$
and $\omega=\infty \Rightarrow V_o = 0$

\Rightarrow Passes only low freq. \Rightarrow L.P.F.

(ii) if at $\omega=0 \Rightarrow V_o = 0$
and $\omega=\infty \Rightarrow V_o \neq 0$

\Rightarrow Passes only High freq. \Rightarrow H.P.F.

(iii) if at $\omega=0 \Rightarrow V_o = 0$
and $\omega=\infty \Rightarrow V_o = 0$

\Rightarrow Passes some range of freq. b/w $\omega=0$ and ∞
 \Rightarrow B.P.F.

(iv) if $\omega=0 \Rightarrow v_o \neq 0$
 $\omega=\infty \Rightarrow v_o \neq 0 \Rightarrow$ Band reject / All Pass filter

↓


check Transfer f^{η}

Pole-zero symmetric about $j\omega$ axis \rightarrow APF

$0/\omega \rightarrow$ BPF



Q.

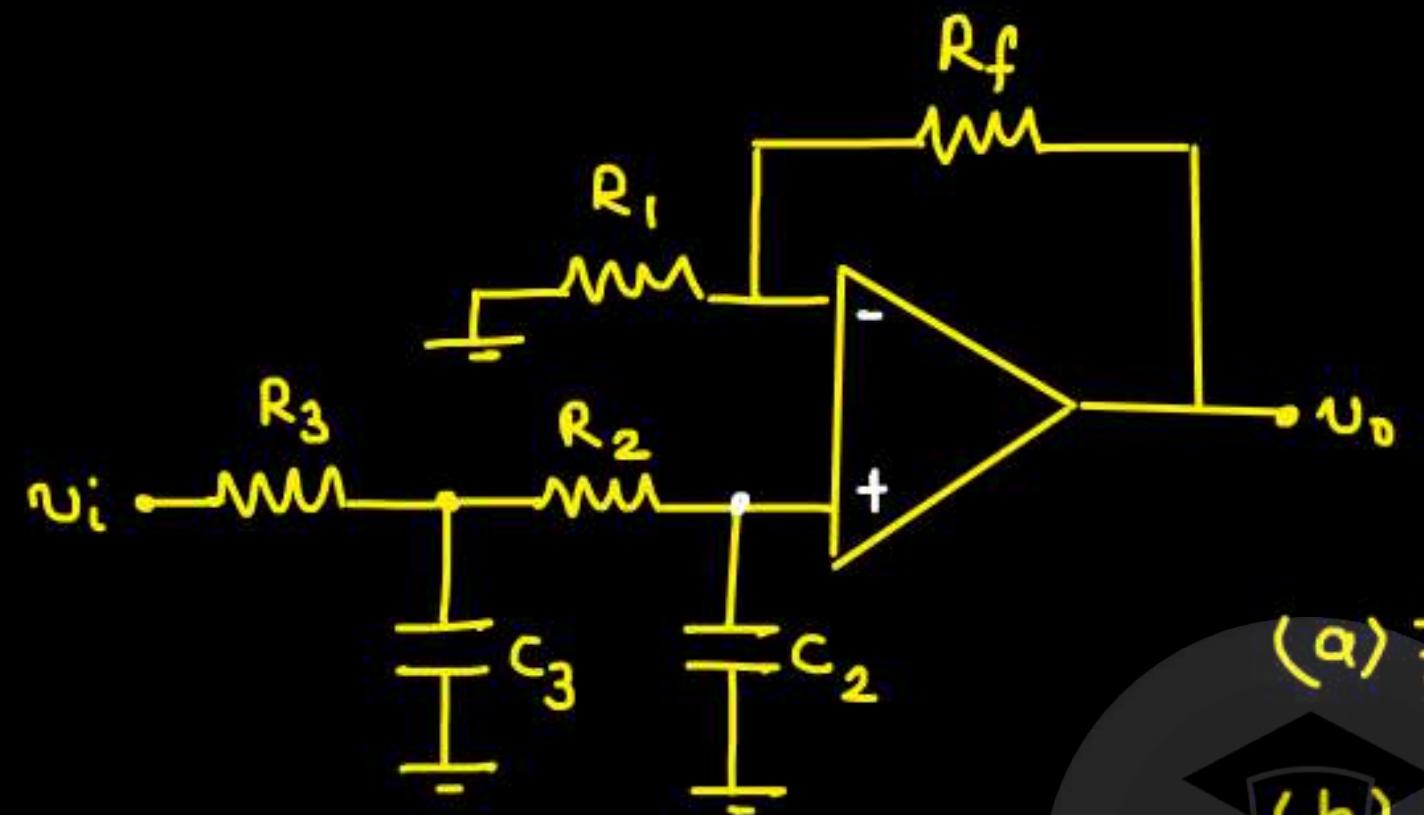

(a) Find the order of the filter.


(b) Find the type of the filter.

Prep^{Rf}ision

(a) 2nd order


(b) $\omega = 0$

$$X_C = \infty$$

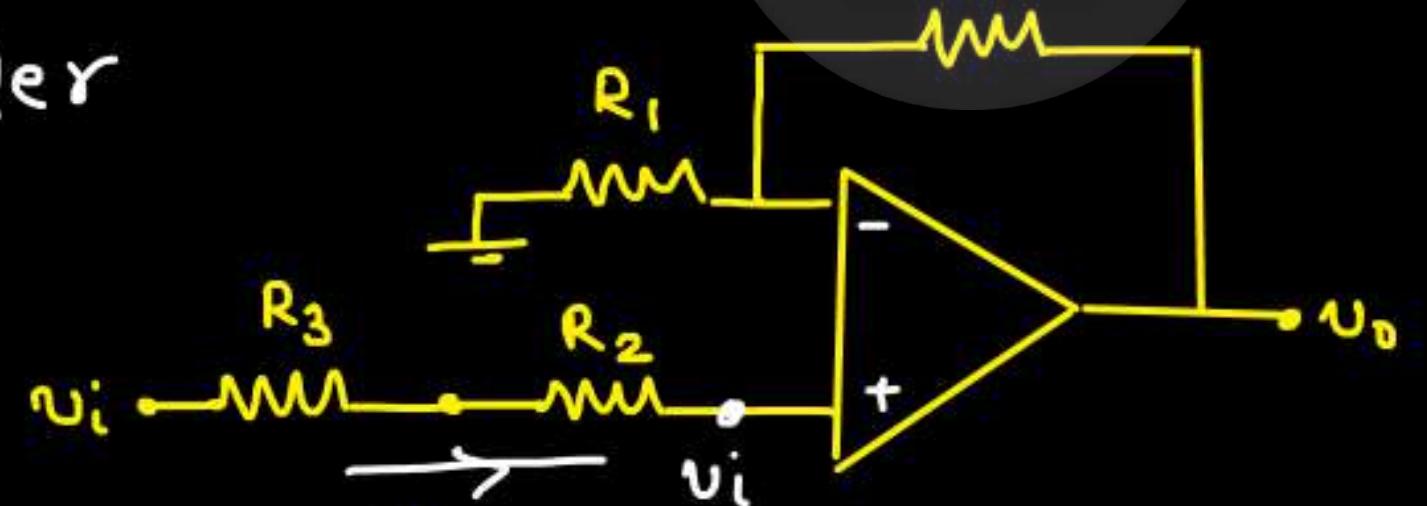


$$u_o(\omega=0) = \left(1 + \frac{R_f}{R_1}\right) u_i$$

\Rightarrow LPF

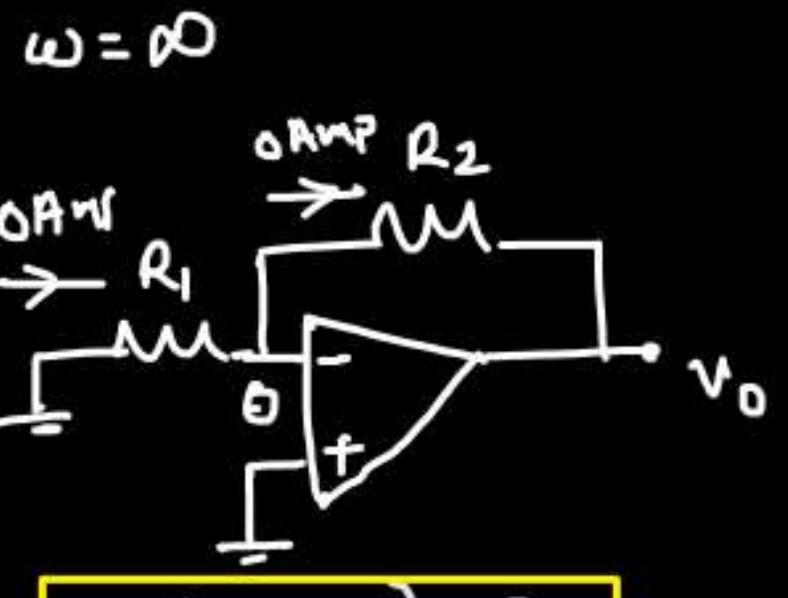


$$u_o(\omega = \infty) = 0$$

③ Band Pass filter :-

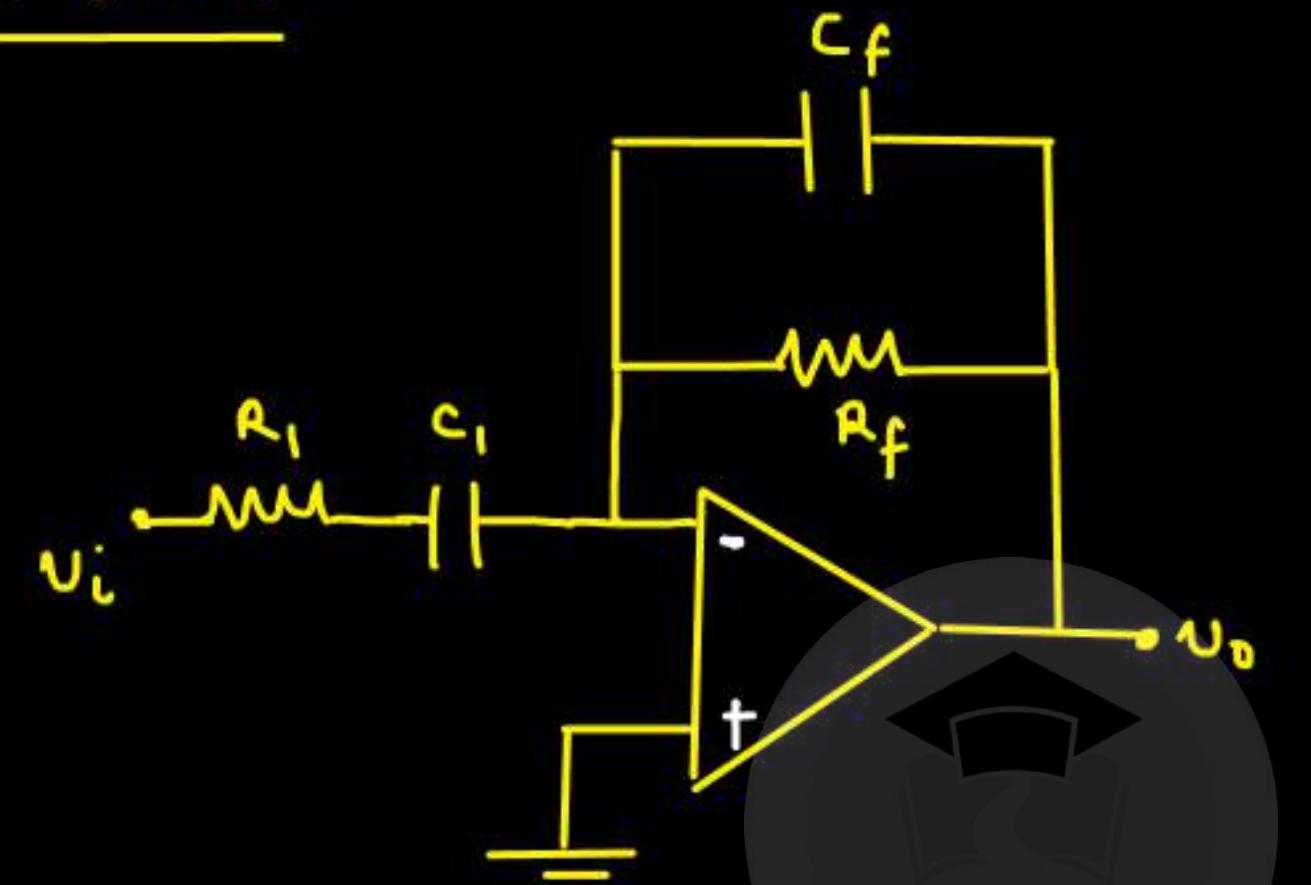


$$\omega = 0 \Rightarrow$$

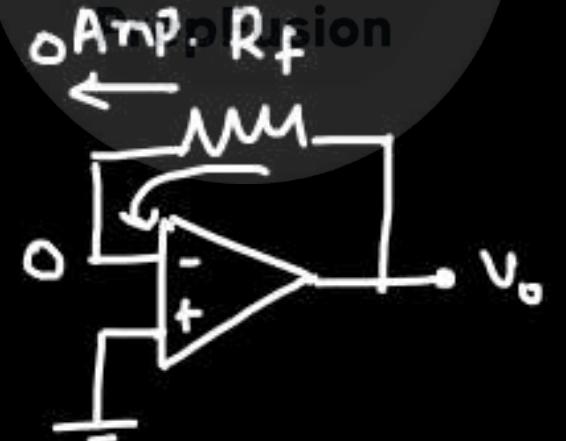

$$\Rightarrow V_0(\omega = 0) = 0 \text{ V}$$


⇒ BPF

$$\omega = \infty \Rightarrow$$

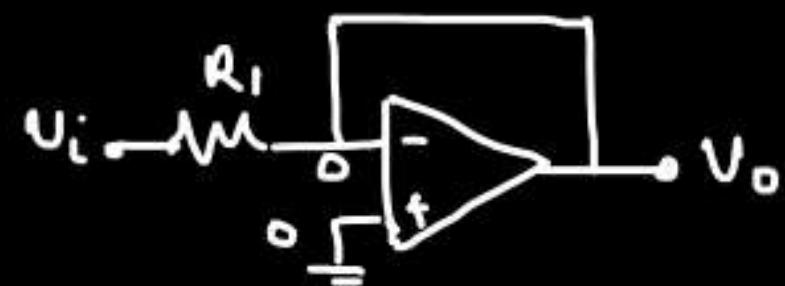


$$V_0(\omega = \infty) = 0 \text{ V}$$
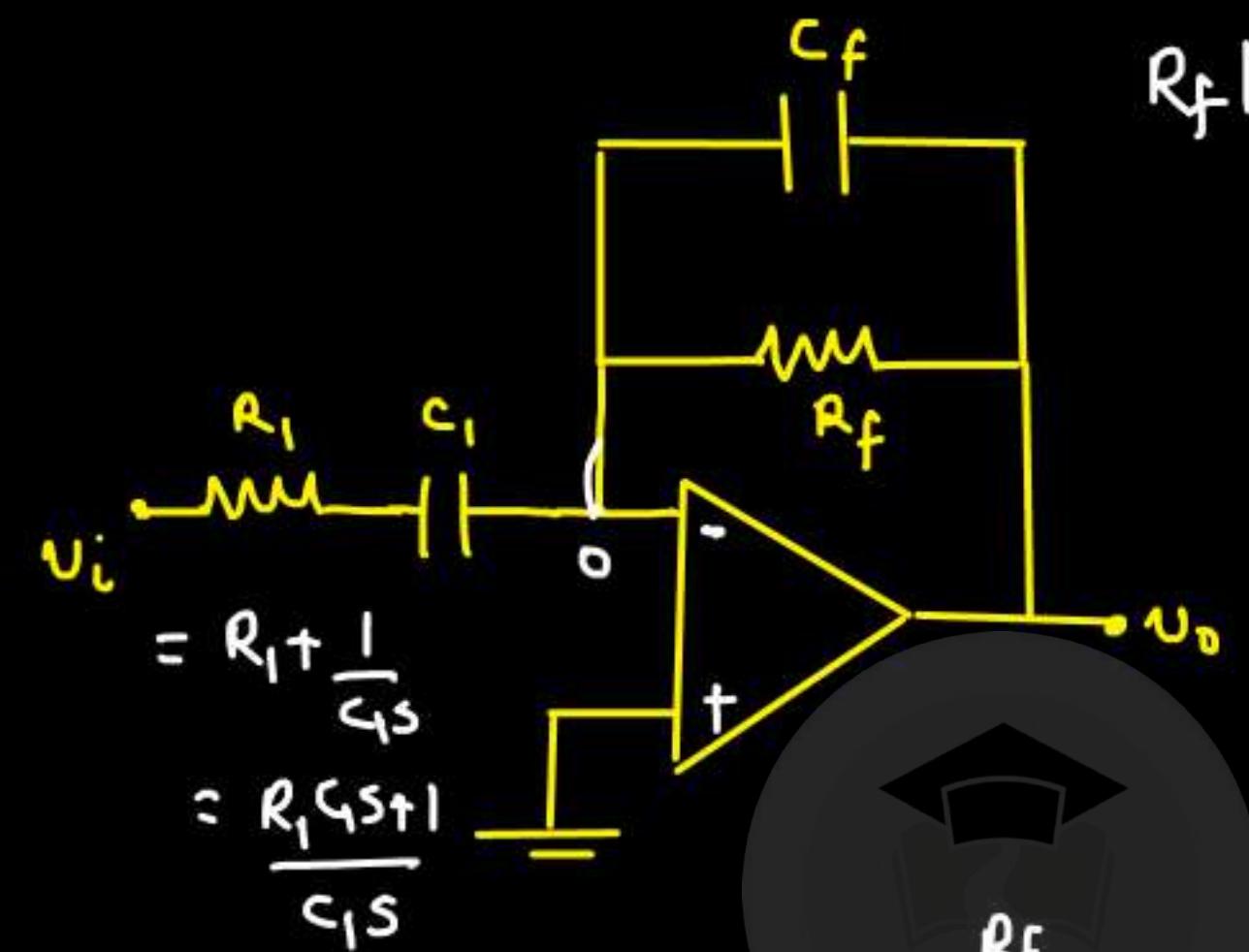
$$R_f \parallel \frac{1}{C_f s} = \frac{R_f}{R_f C_f s + 1}$$



$\frac{R_f}{R_f C_f s + 1}$

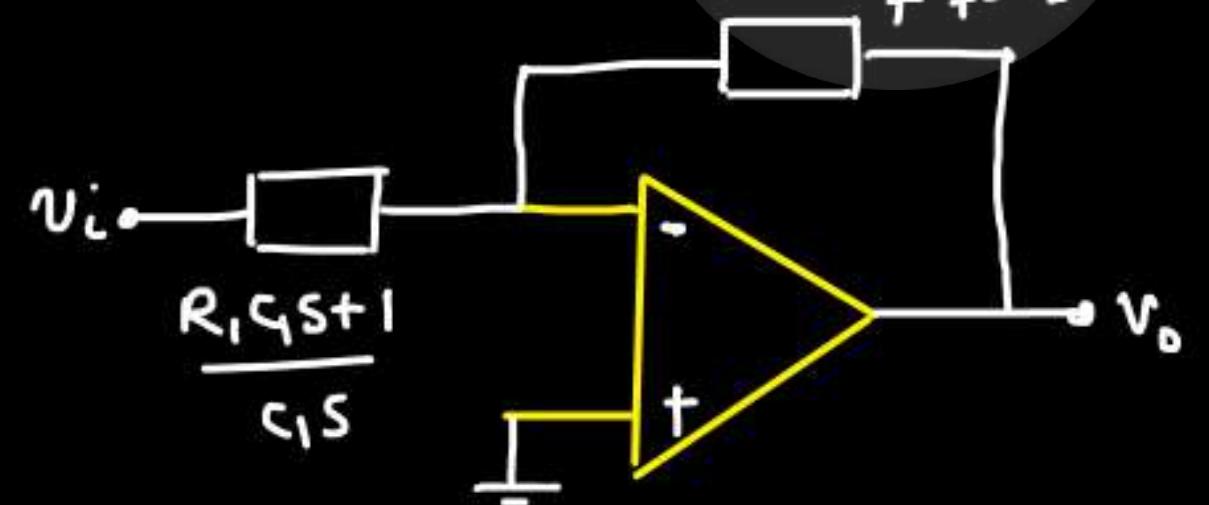


$$\frac{U_o(s)}{U_i(s)} = \frac{\frac{-R_f}{C_f s}}{\frac{R_f C_f s + 1}{C_f s}}$$


$$\frac{V_o(\omega)}{V_i(\omega)} = \frac{-R_f C_f s}{(R_f C_f s + 1)(R_i C_i s + 1)}$$

$$\omega_L = 0$$
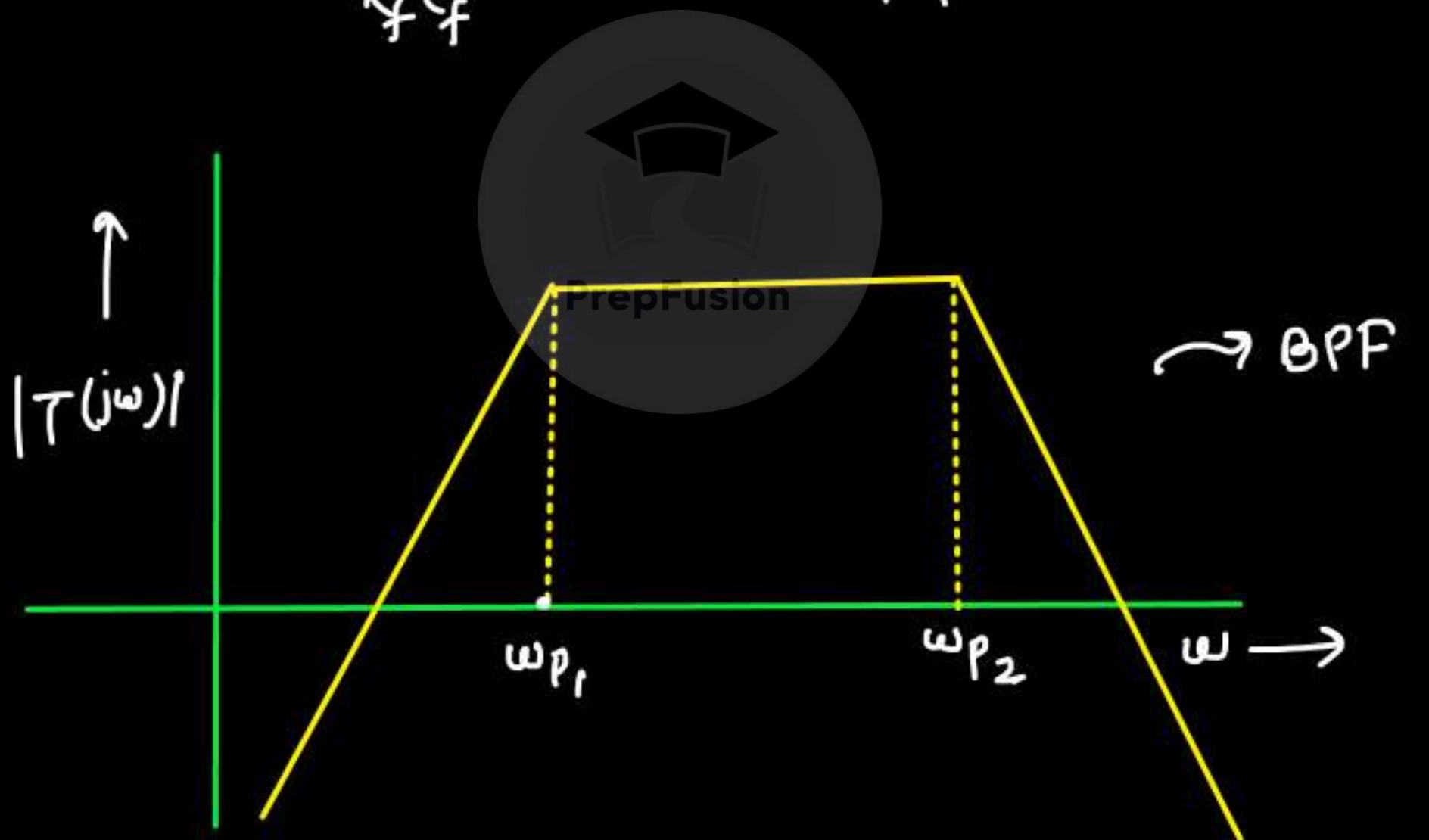
$$\omega_p = \frac{1}{R_f C_f} \quad \omega_p = \frac{1}{R_i C_i}$$




④ All Pass Filter :-

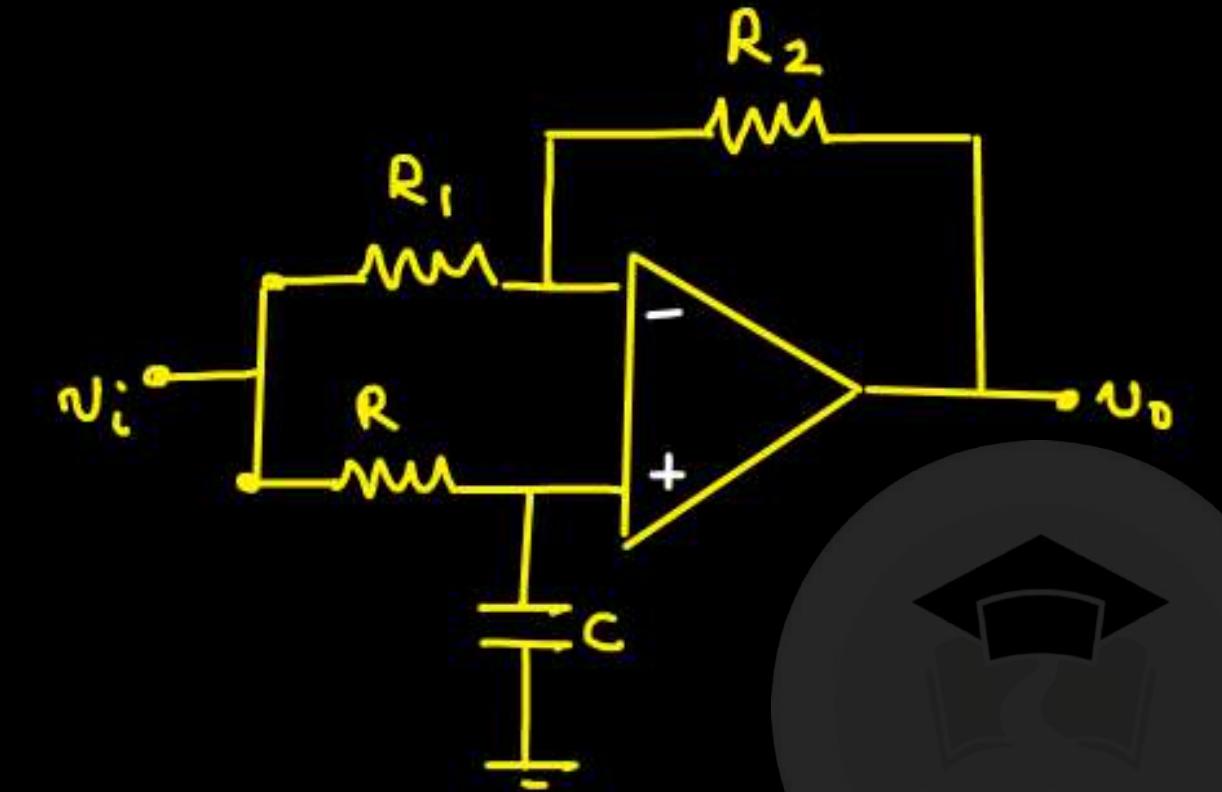


$$\underline{\omega = 0} : - X_C = \infty$$

$$V_o(\omega=0) = V_i$$

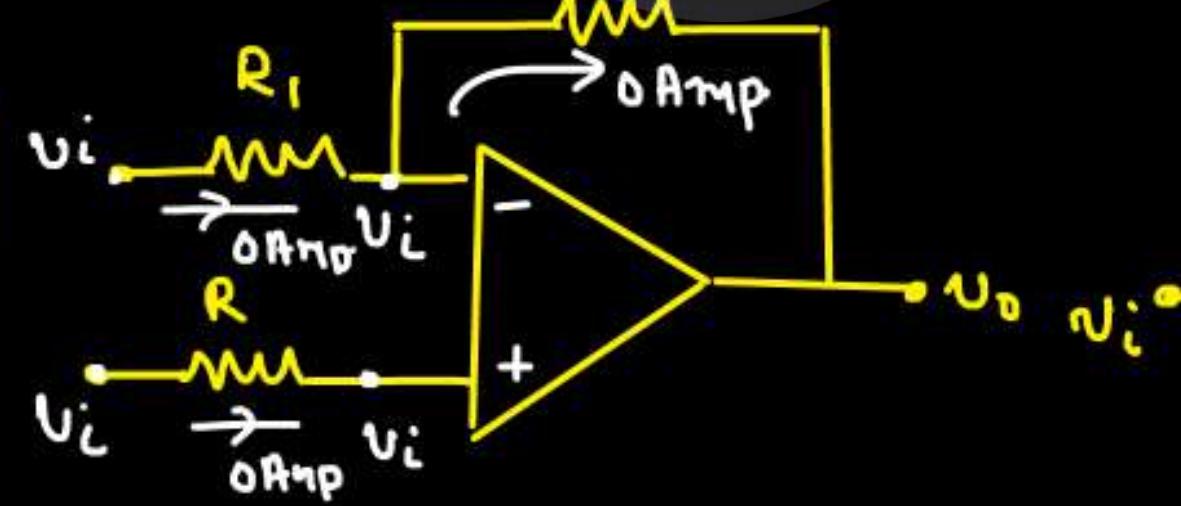

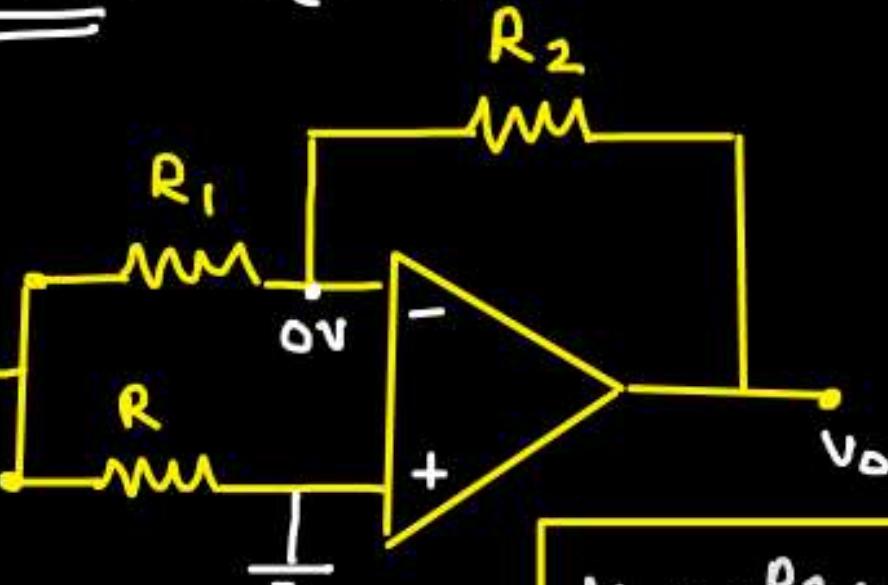
$$\underline{\underline{\omega = \infty}} : - X_C = 0$$



$$V_D = -\frac{R_2}{R_1} V_i$$

$\underline{\underline{C}}$

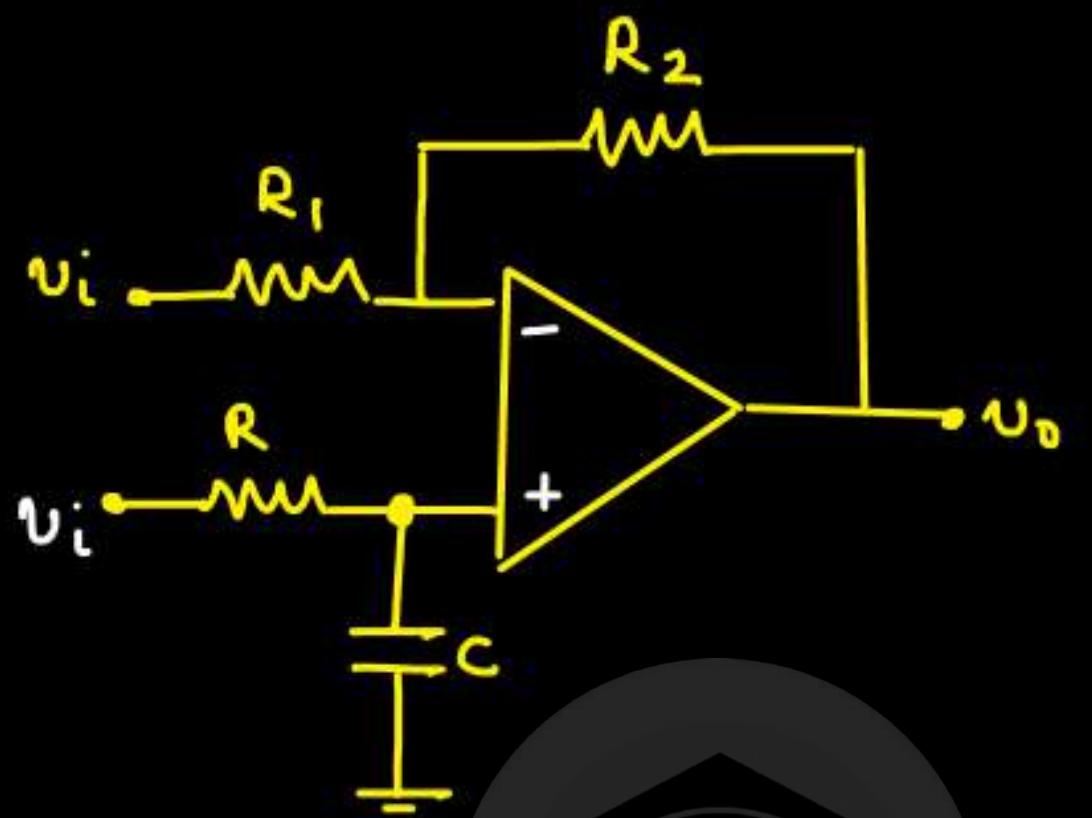

$$v_o(s) = \left(1 + \frac{R_2}{R_1}\right) \times \frac{1}{RCS + 1} v_i(s) + \frac{R_2}{R_1} v_i(s)$$

$$= \frac{v_i(s)}{1 + RCS} + \frac{R_2 v_i(s)}{R_1} \left[\frac{1}{1 + RCS} - 1 \right]$$


$$= \frac{v_i(s)}{1 + RCS} + \frac{R_2}{R_1} v_i(s) \left[\frac{-SRC}{1 + SRC} \right]$$

$$V_o(s) = \frac{V_i(s)}{1 + SRC} \left[1 - \frac{R_2}{R_1} SRC \right]$$

$$\omega_p = -\frac{1}{RC}$$


$$\omega_z = \frac{R_1}{R_2 RC}$$

→ BSF

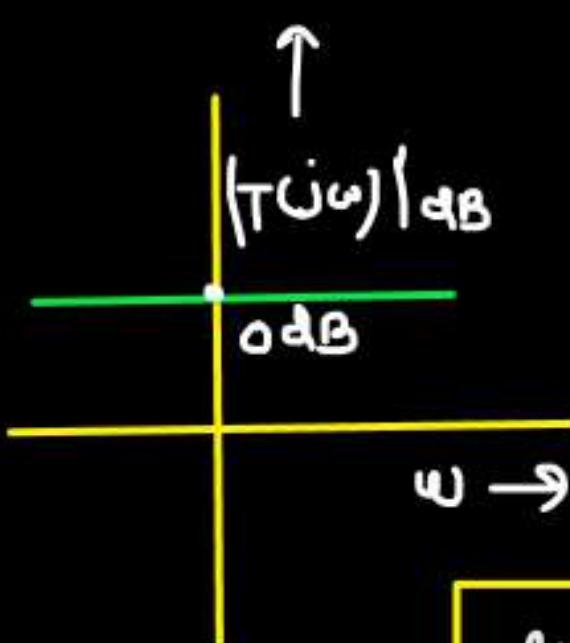

But if $R_2/R_1 = 1$
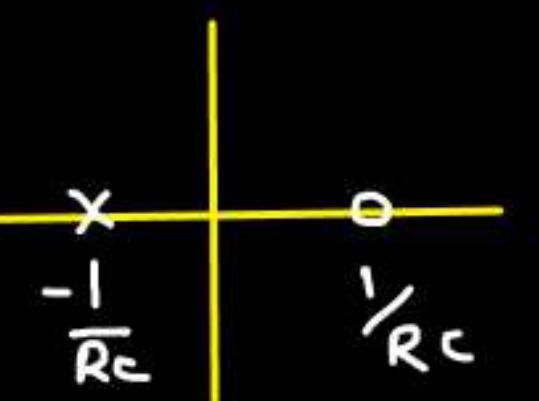
$$\omega_p = -\frac{1}{RC}, \quad \omega_z = \frac{1}{RC}$$




→ APF

$$\frac{V_o(s)}{V_i(s)} = \frac{1 - SRC}{1 + SRC}$$

$$|T(j\omega)| = \sqrt{\frac{1 + \omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}} = 1$$

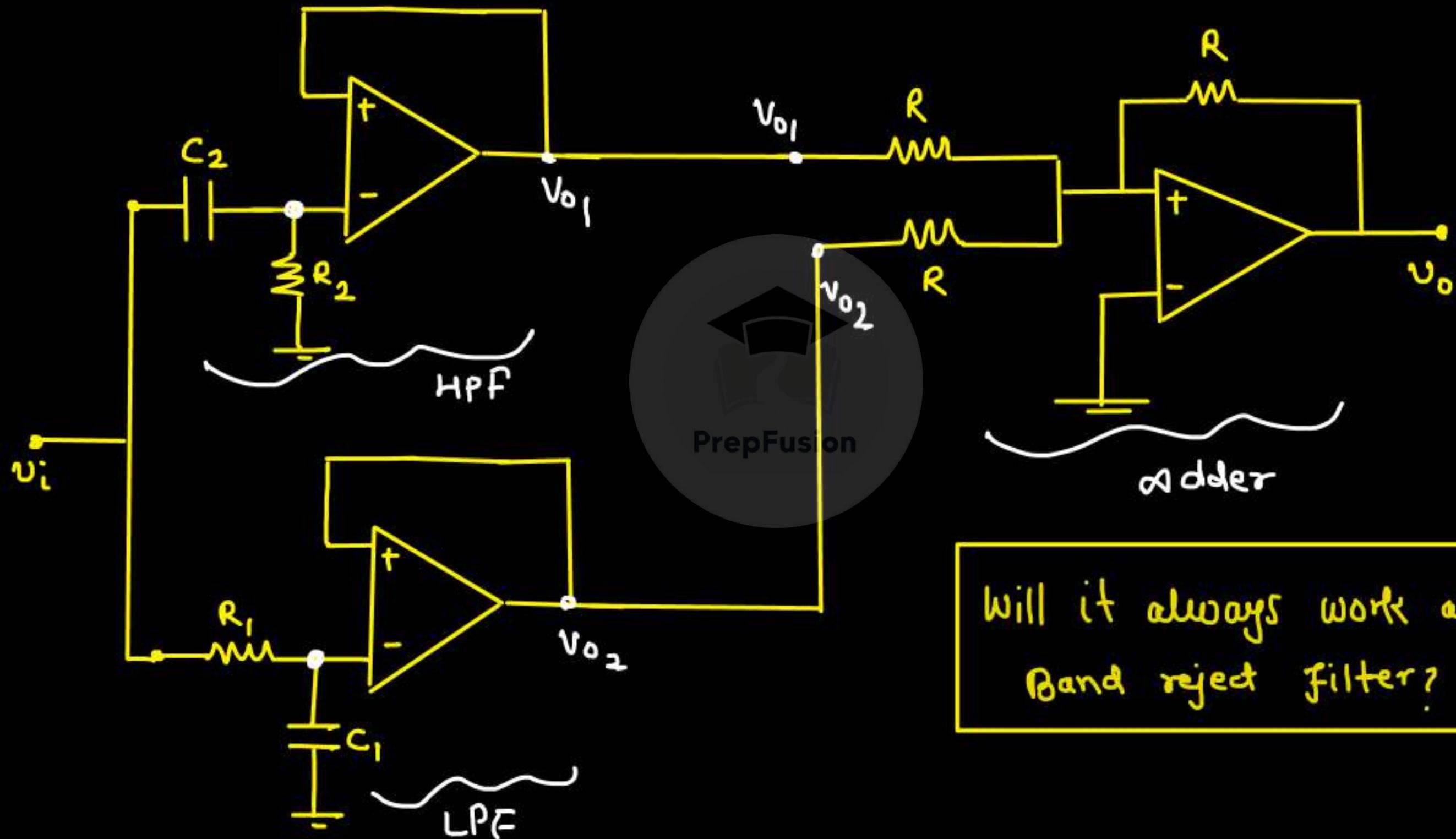⑤ Band Reject Filter :- / Band stop filter



Will it always work as
Band reject filter?

$$V_{o1}(s) = \frac{SR_2C_2}{1 + SR_2C_2} v_i(s)$$

$$V_{o2}(s) = \frac{1}{1 + SR_1C_1} v_i(s)$$



$$\begin{aligned} V_o &= -2 \left[\frac{V_{o1} + V_{o2}}{2} \right] \\ &= -V_{o1} - V_{o2} \quad = \text{PrepFus}(V_{o1} + V_{o2}) \end{aligned}$$

$$v_o = - \left[\frac{1}{1 + SR_1C_1} + \frac{SR_2C_2}{1 + SR_2C_2} \right] v_i(s)$$

$$\frac{v_o(s)}{v_i(s)} = - \left[\frac{1 + SR_2C_2 + SR_2C_2 + S^2R_1R_2C_1C_2}{(1 + SR_1C_1)(1 + SR_2C_2)} \right]$$

$$\frac{v_o(s)}{v_i(s)} = -\frac{1 + 2sR_2C_2 + s^2R_1R_2C_1C_2}{(1+sR_1C_1)(1+sR_2C_2)}$$

Two poles, Two zeros

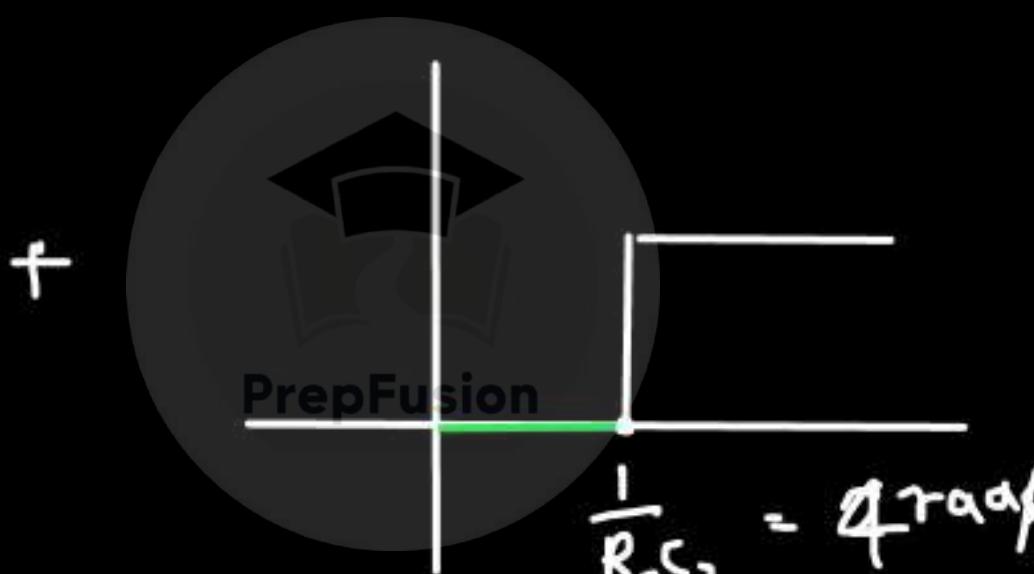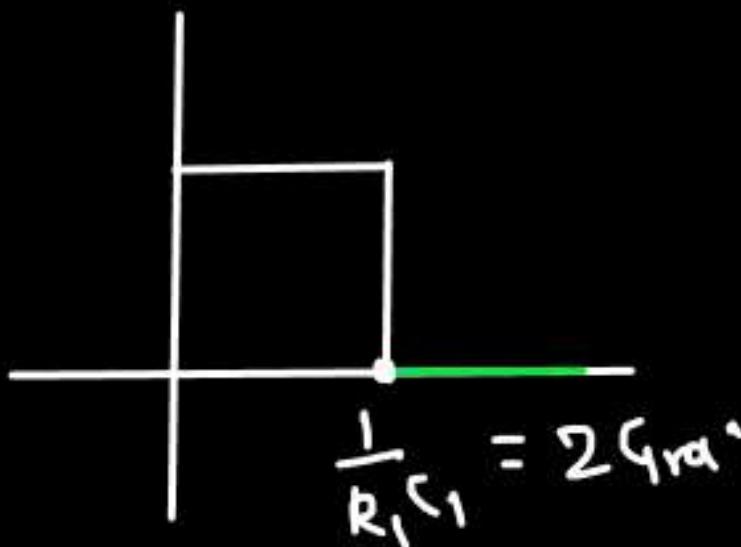


if $\frac{1}{R_1C_1} > \frac{1}{R_2C_2} \Rightarrow$ The filter doesn't act as B.S.F.

if $\frac{1}{R_1C_1} < \frac{1}{R_2C_2}$ or $R_1C_1 > R_2C_2 \Rightarrow$ The filter acts as B.S.F.

Assignment - 14


Q. 1

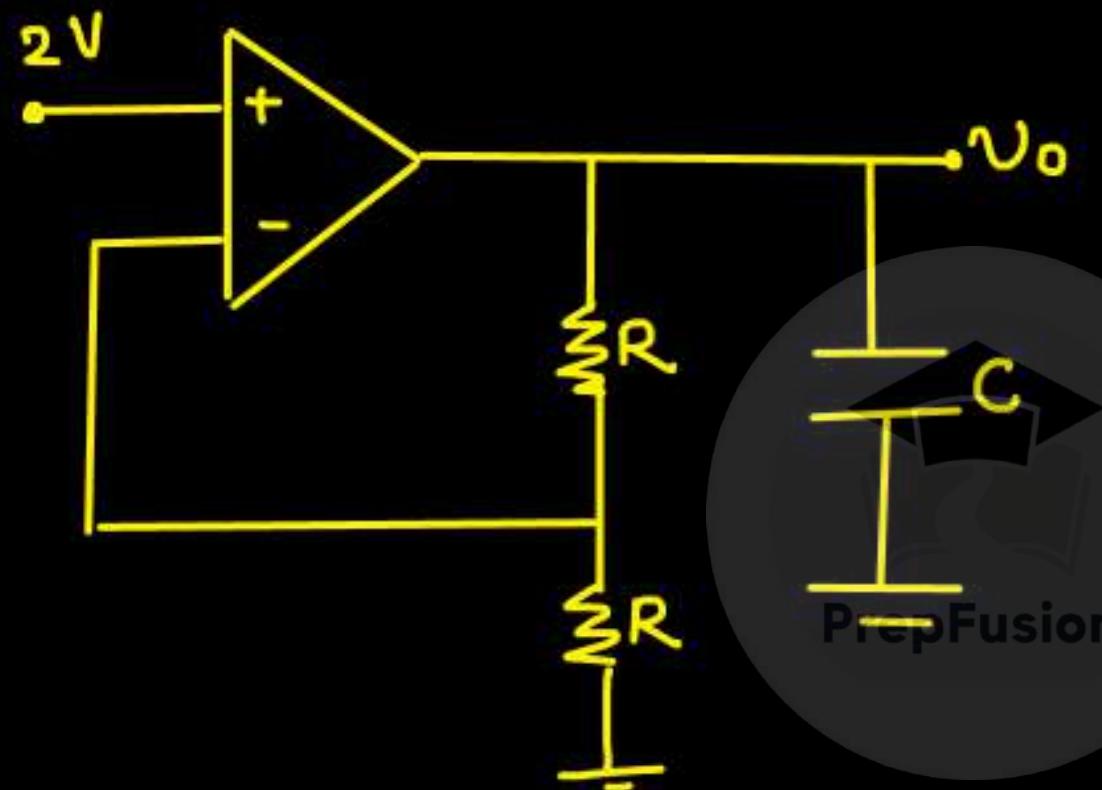

What is the time constant of
the circuit?



M-I :-

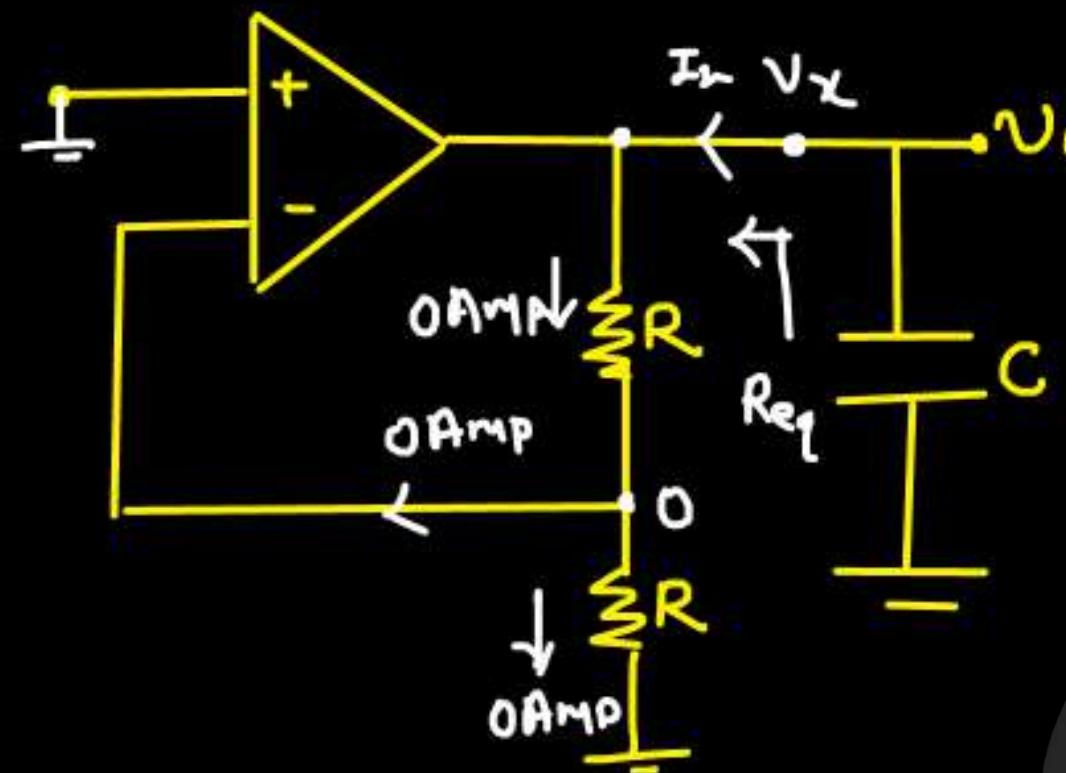


$$\tau = R_{\text{eq}} C$$

$$R_{\text{eq}} = \frac{V_o}{I_{\text{IL}}} = \frac{0}{\frac{V_o}{I_o}} = 0 \Omega$$

$$\tau = 0$$

M-II :-

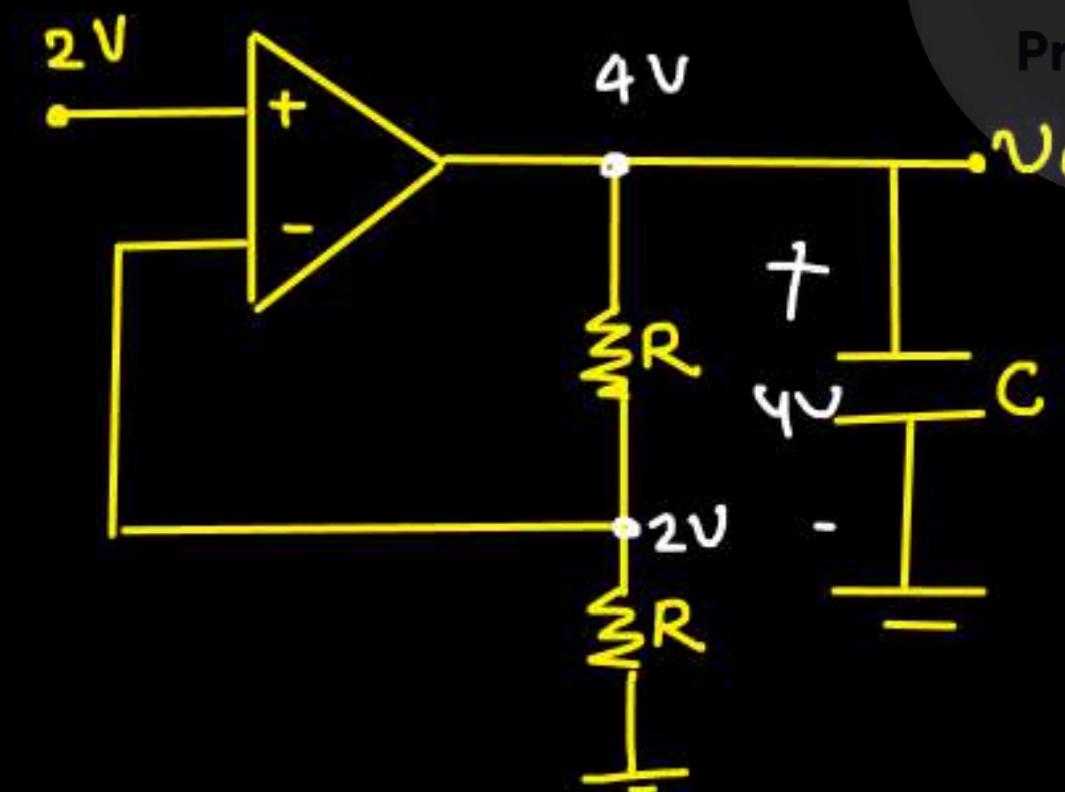


PrepFusion

$$V_o = 4V$$

$$\tau = 0$$

⇒ zero order ckt

Q.

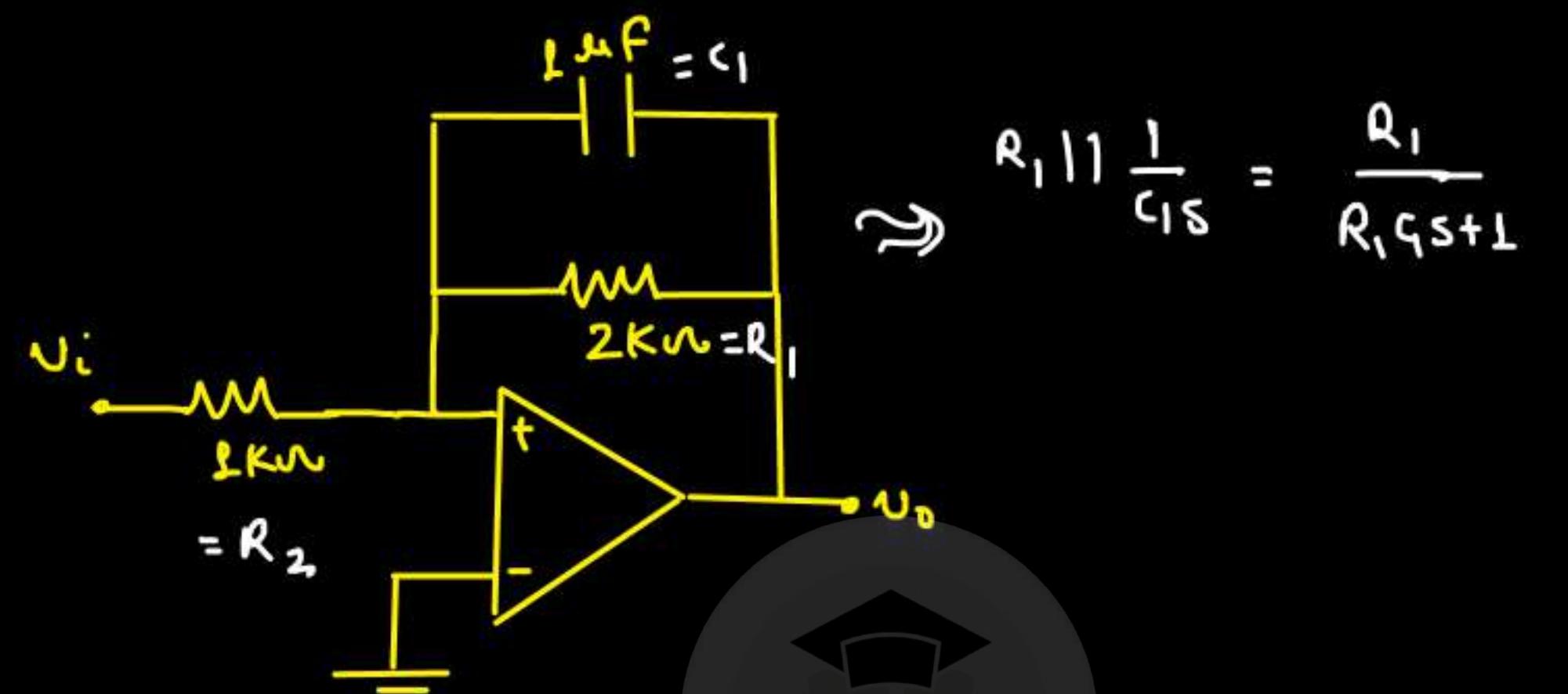

- (a) Find the type of Filter?
- (b) DC gain = ?
- (c) 3-dB Bandwidth = ?
- (d) Unity gain Bandwidth = ? (approx)

$$(a) \omega = 0 \Rightarrow V_o = -2V_i$$

⇒ L.P.F.

$$\omega = \infty \Rightarrow V_o = 0$$

(b) DC gain (gain @ $\omega=0$):-

$$\frac{V_o}{V_i} = -2$$

$$(c) \frac{V_o(s)}{V_i(s)} = -\frac{R_1}{(R_1 C_1 s + 1) R_2}$$



$$(d) \omega_{UGB} \approx |\text{DC gain}| \times \omega_{3-dB}$$

$$\approx 2 \times 0.5 \text{ rad/sec.}$$

$$\approx 1 \text{ rad/sec.}$$

↳ Approx

$$\omega_{3-dB} = \frac{1}{R_1 C_1} = \frac{1}{2 \times 1 \mu} = 0.5 \text{ rad/sec.}$$

$$(d) \frac{V_o(s)}{V_i(s)} = \frac{-R_1/R_2}{R_1 C_1 s + 1} = \frac{-2}{2 \times 10^{-3} s + 1} = T(s)$$

$$|T(j\omega)| = \frac{2}{\sqrt{1 + \omega^2 \times 4 \times 10^{-6}}}$$

at $\omega = \omega_{uqg}$


$$|T(j\omega_{uqg})| = \text{PrepFusion} \frac{2}{\sqrt{1 + \omega^2 \times 4 \times 10^{-6}}}$$

$$\omega^2 \times 4 \times 10^{-6} = 3$$

$$\omega_{uqg} = \sqrt{3} / 2 \text{ Krad/sec.}$$

$$\boxed{\omega_{uqg} = 0.87 \text{ Krad/sec.}} \rightarrow \text{exact}$$

Q.

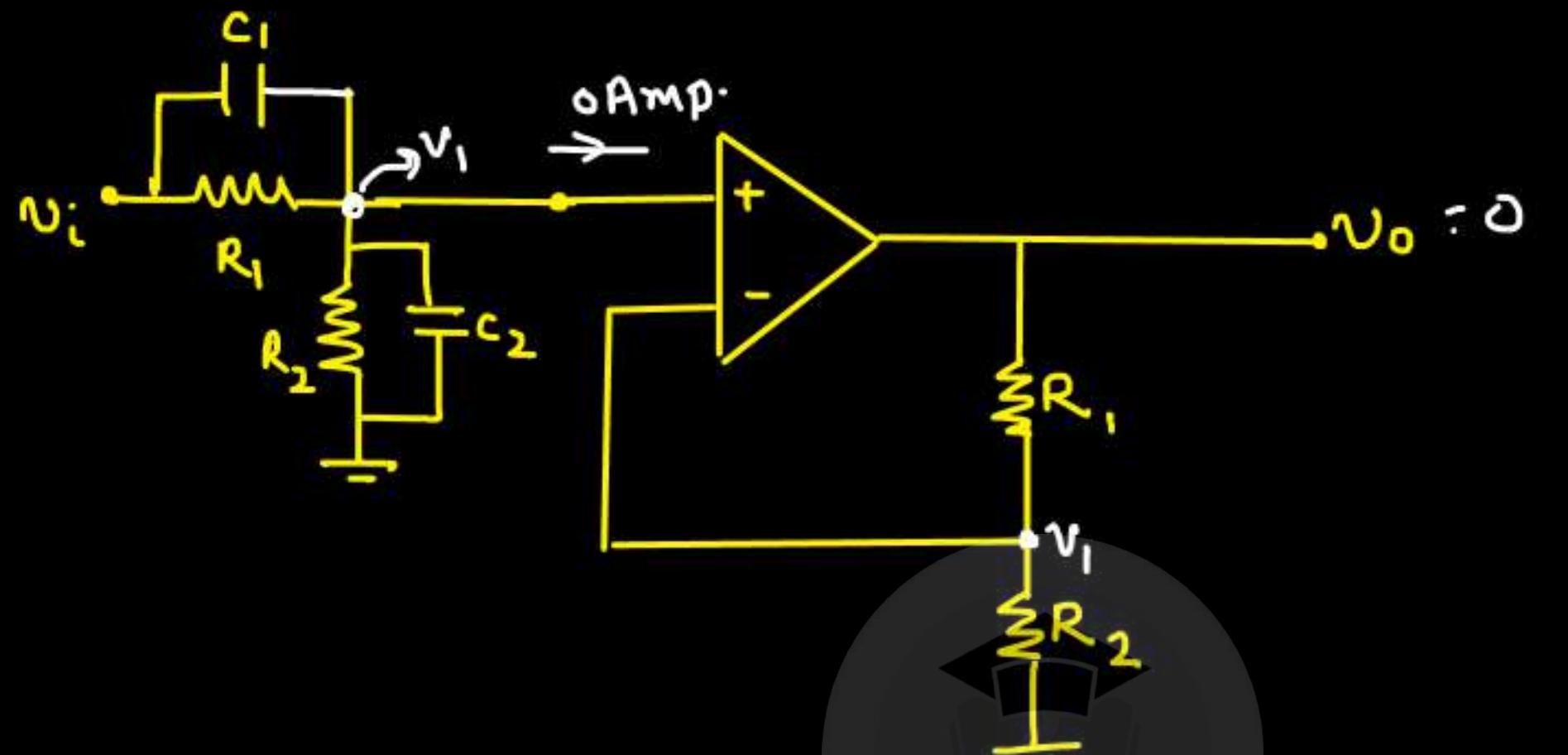

PrepFusion

- (a) What is the order of the ckt?
 (b) What kind of filter is that?

→ (a) 1st order


(b) @ $\omega = 0$, $v_1 = \frac{R_2}{R_1 + R_2} v_i$

$$v_o = \left(1 + \frac{R_1}{R_2}\right) \times \frac{R_2}{R_1 + R_2} v_i$$


$v_o = v_i$

⇒ APP or BSF ?

@ $\omega = \infty$

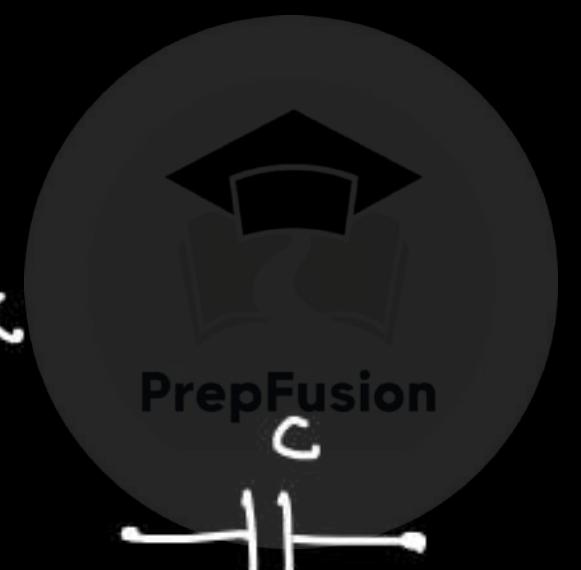

PrepFusion

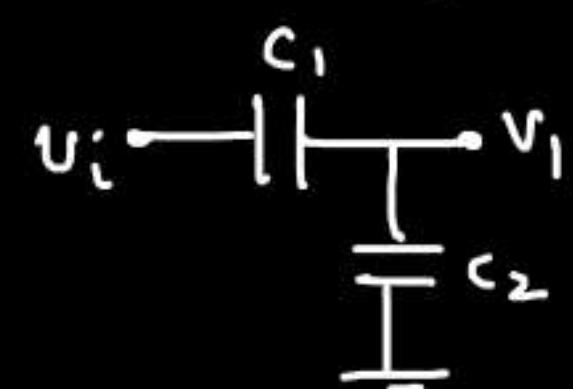


$$v_1 = \frac{C_1}{C_1 + C_2} v_i$$

$$\omega_p = \frac{1}{(R_1 || R_2)(C_1 + C_2)}, \quad \omega_Z = \frac{1}{R_1 C_1}$$

⇒ BSF

$v_o = \left(1 + \frac{R_1}{R_2}\right) \left(\frac{C_1}{C_1 + C_2}\right) v_i$

Q.

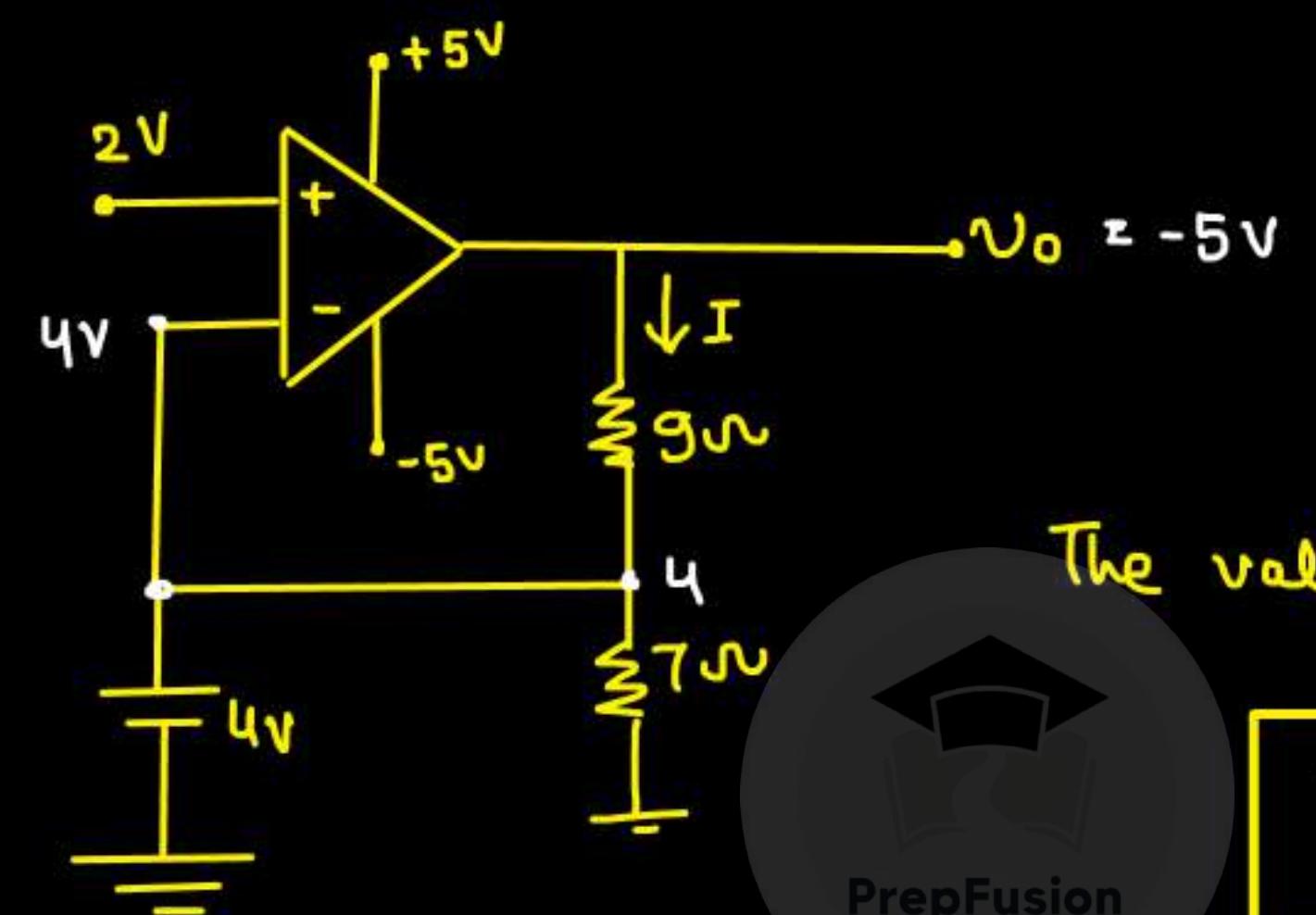


The value of current I is — ?

$$I = \frac{-5 - 4}{9} = -1 \text{ AMP}$$

PrepFusion

Q.

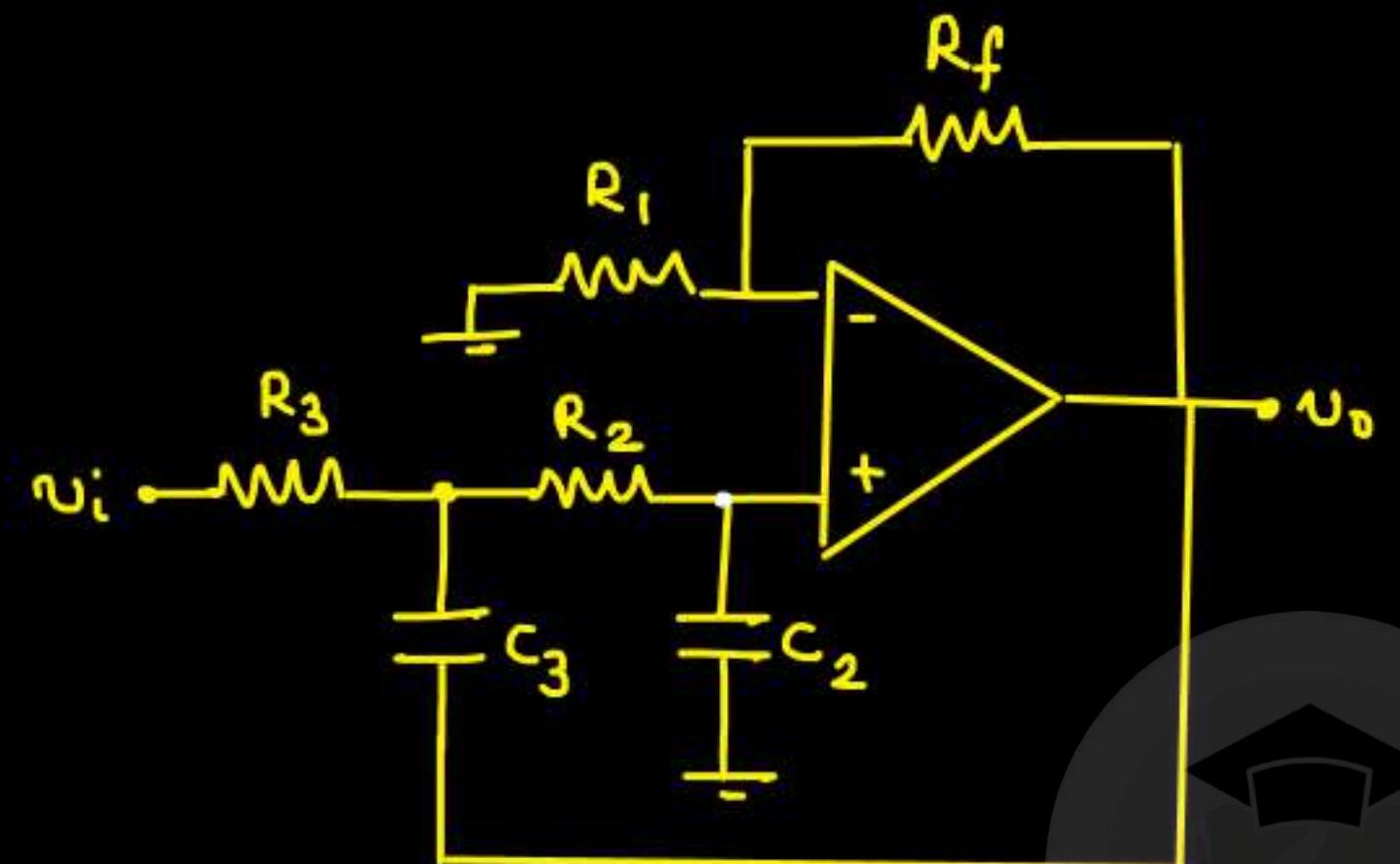

Determine the type of filter.


PrepFusion

⇒ L·P·F·

$$\Rightarrow \omega = 0 \Rightarrow v_o = \left(1 + \frac{R_f}{R_1}\right) v_i$$


$$\omega = \infty \Rightarrow v_o = 0$$

Q.

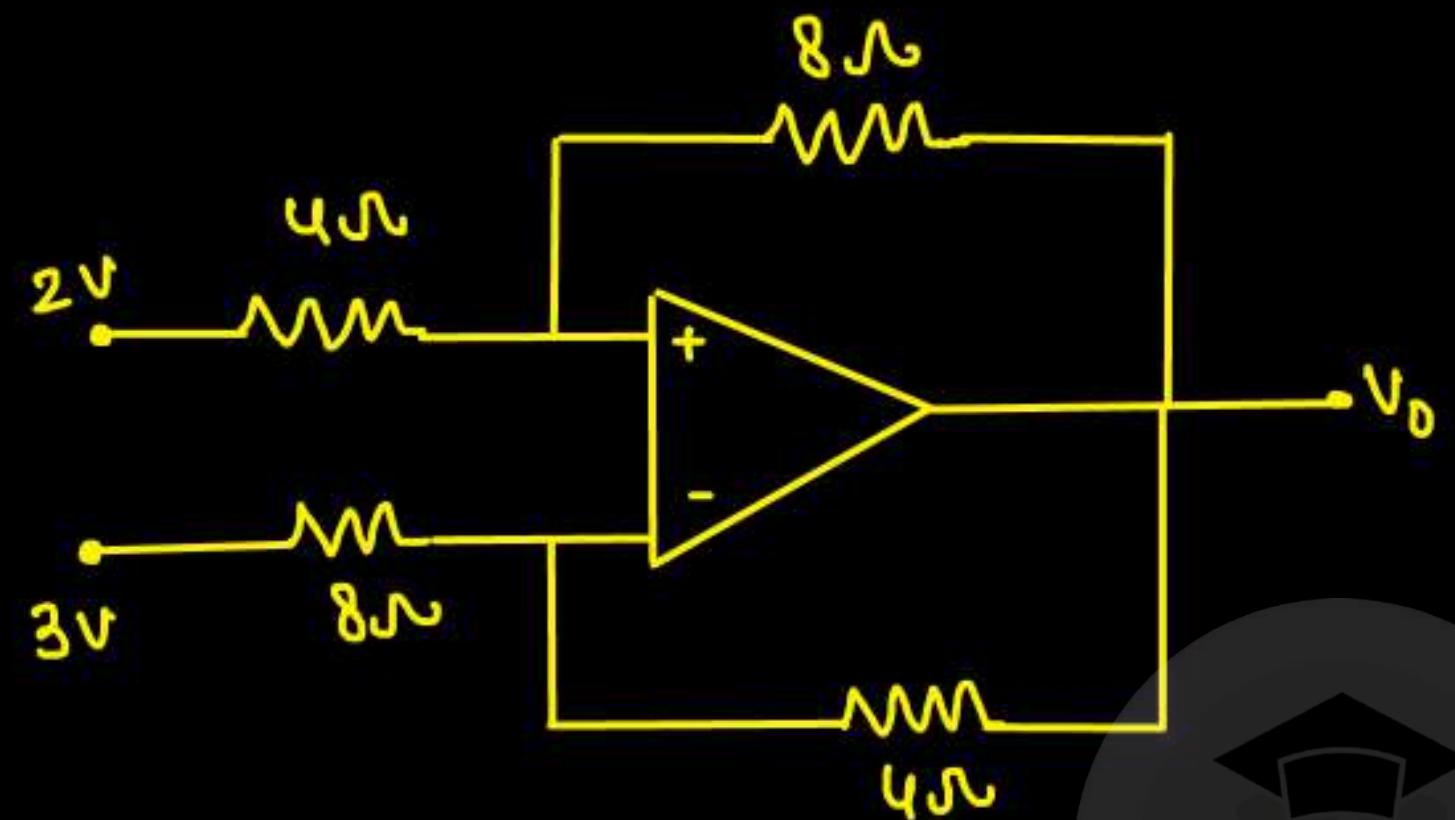

- (a) Which feedback is present in the circuit?
- (b) Find V_o .

Type of f/b:-

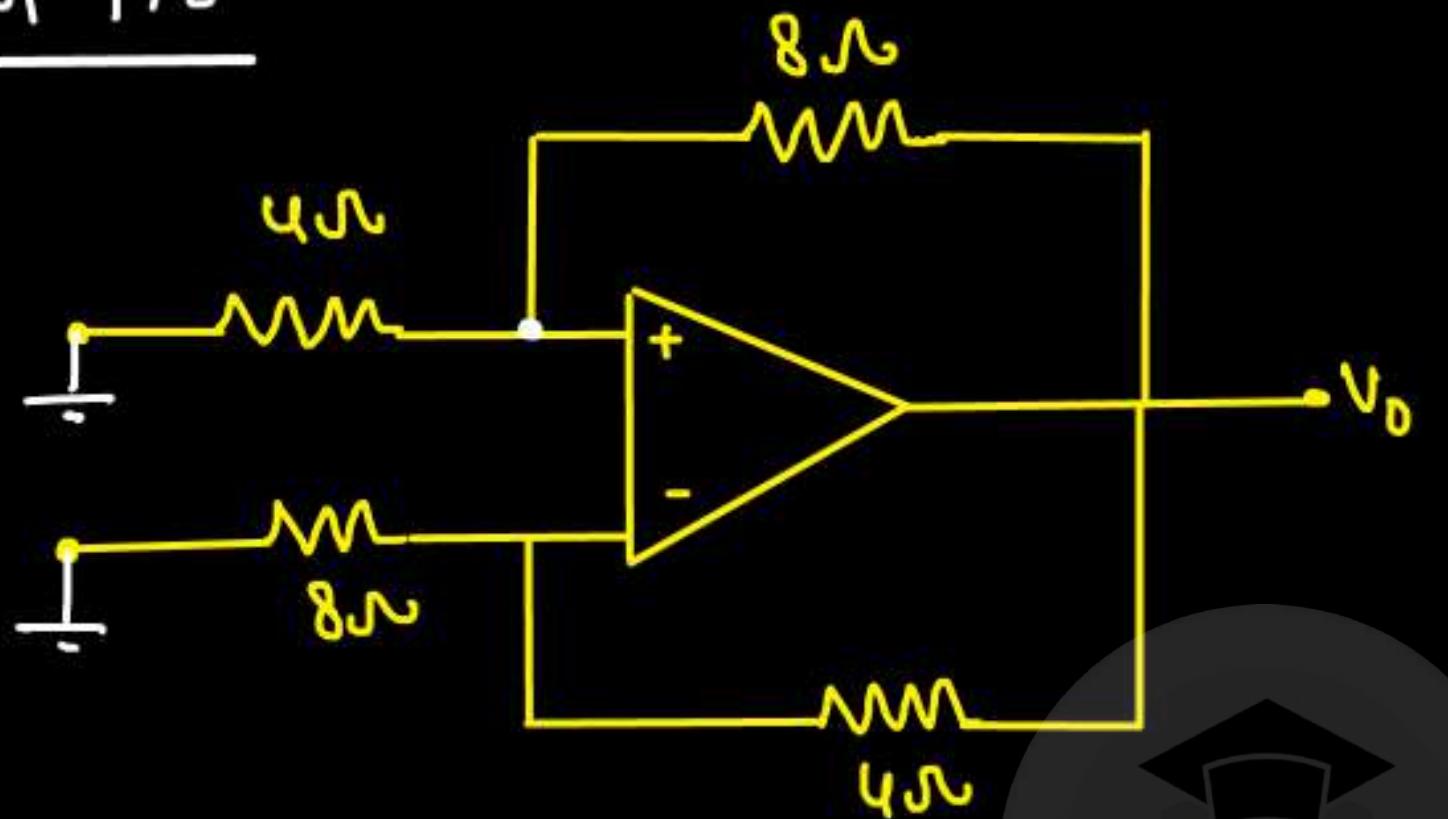


$$V_t = \frac{4}{12} V_o = V_o / 3$$

PrepFusion

⇒ Negative f/b
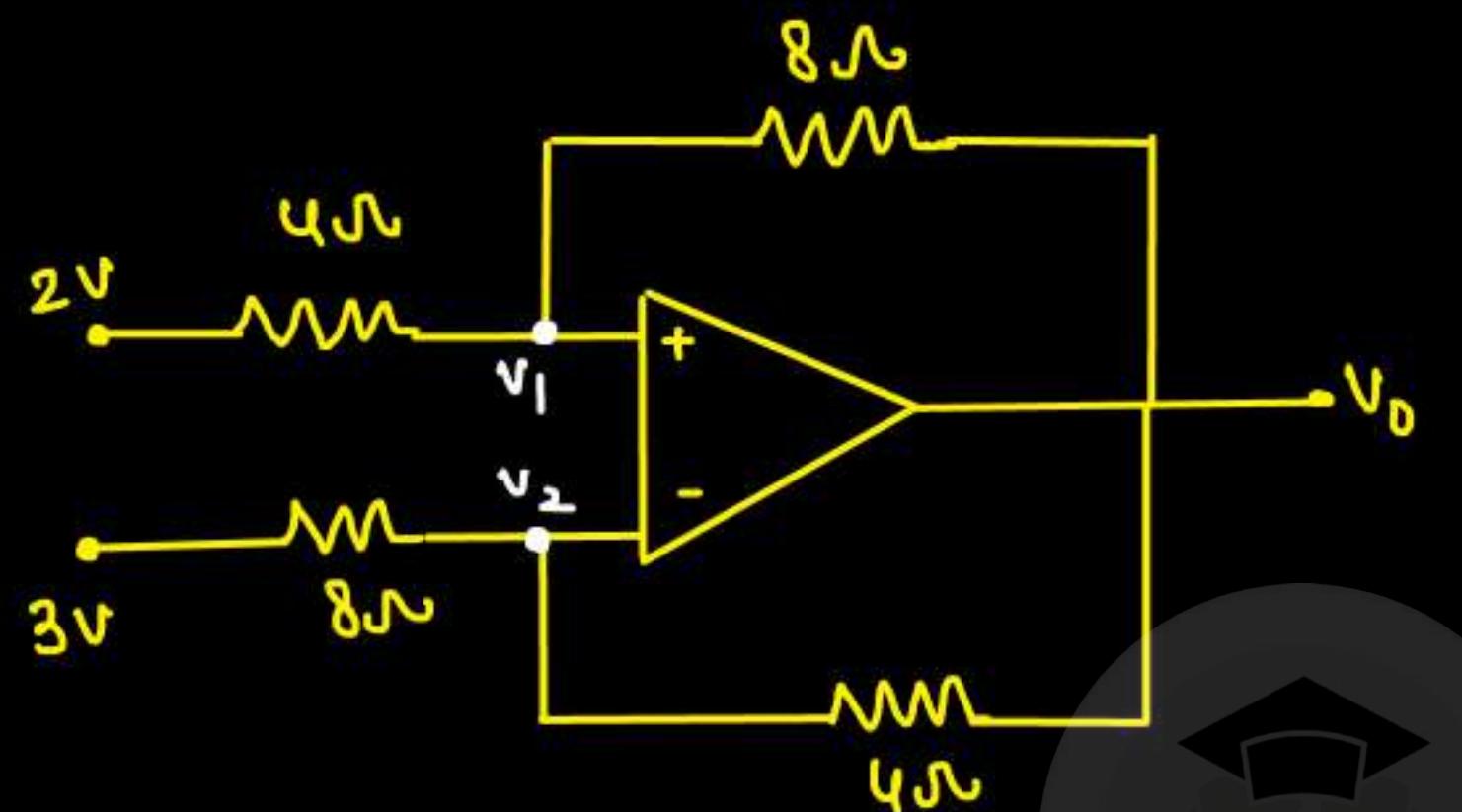
$$V_- = \frac{8}{12} V_o = 2 V_o / 3 \Rightarrow \text{dominating}$$



PrepFusion

$$v_1 = v_2$$

$$\frac{16 + 4v_o}{12} = \frac{8v_o + 12}{12}$$


$v_o = 1V$

⇒ Parameters of OP-Amp :-

- Input offset voltage
- Output offset voltage
- Input offset current
- Input bias current
- CMRR
- Slew Rate
- Frequency Response




1. Input offset Voltage:-

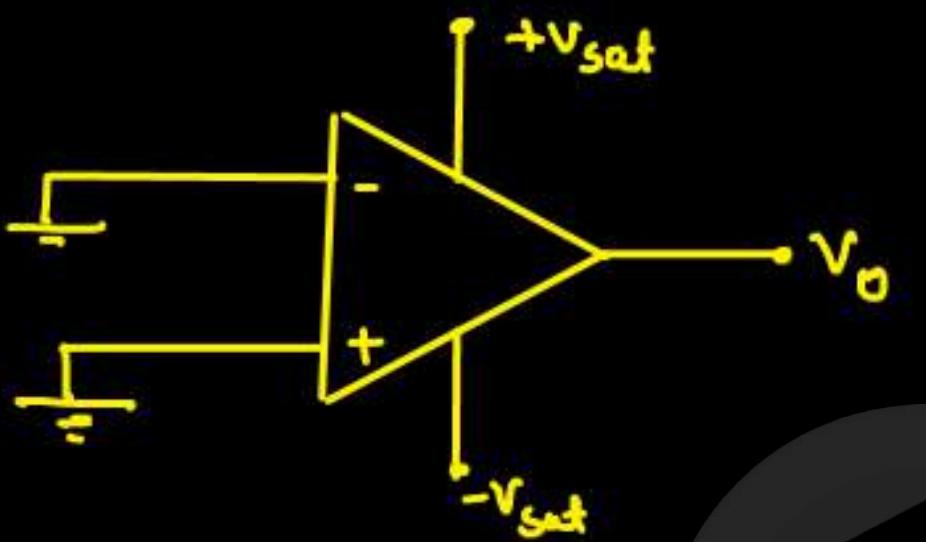


$$(V_o)_{\text{expected}} = 0 \text{ V}$$

PrepFusion

$$(V_o)_{\text{actual}} = V_{DD}$$

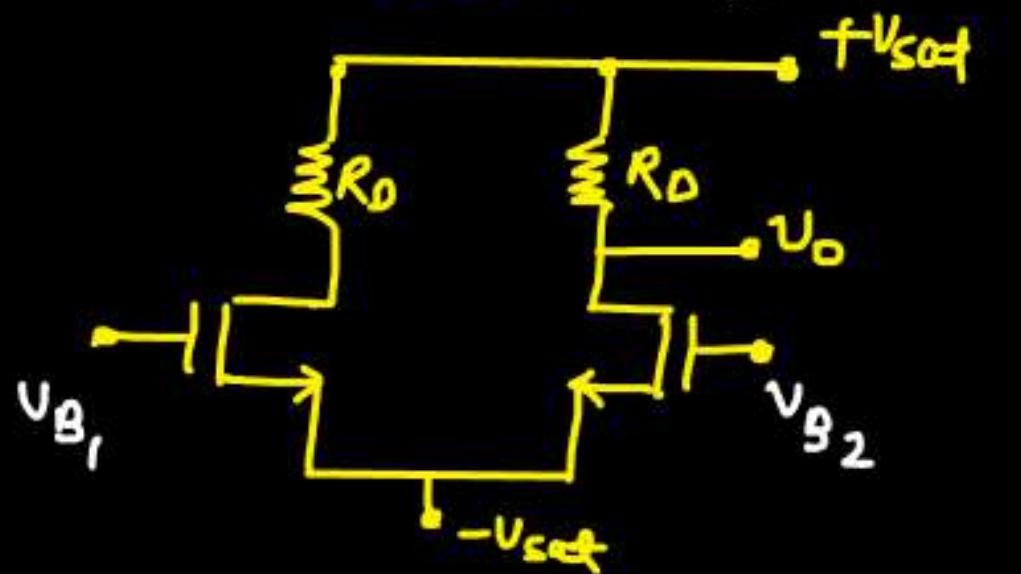

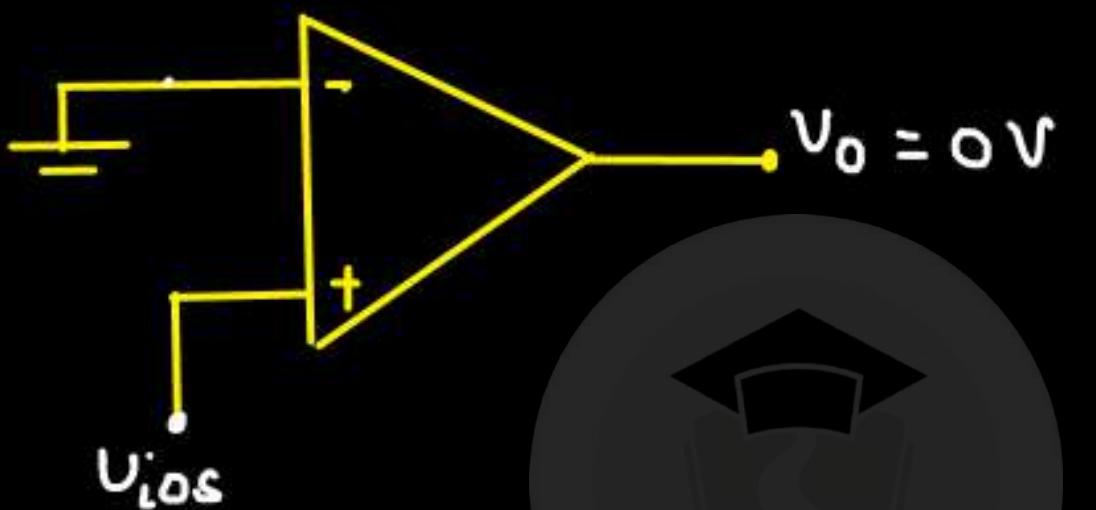So, at the input you apply a small offset voltage to make your output zero.




The amount of differential voltage that must be applied b/w two terminals of OP-Amp such that O/P of OP-Amp is zero , is known as input offset voltage.

Range :- μV to mV


It's tough to predict the polarity of i/p offset voltage.

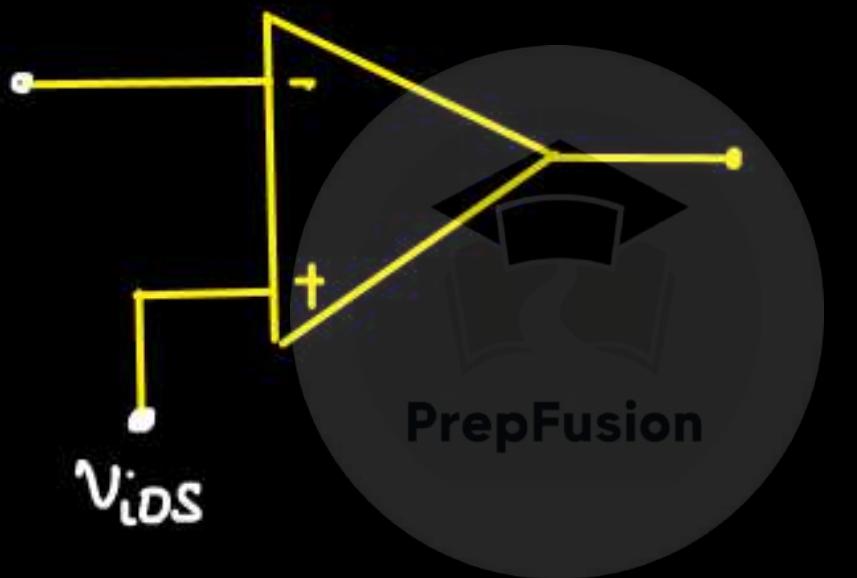Generally, offset voltage is shown by a battery @ non-inverting terminal.



⇒ Effect of input offset voltage:-

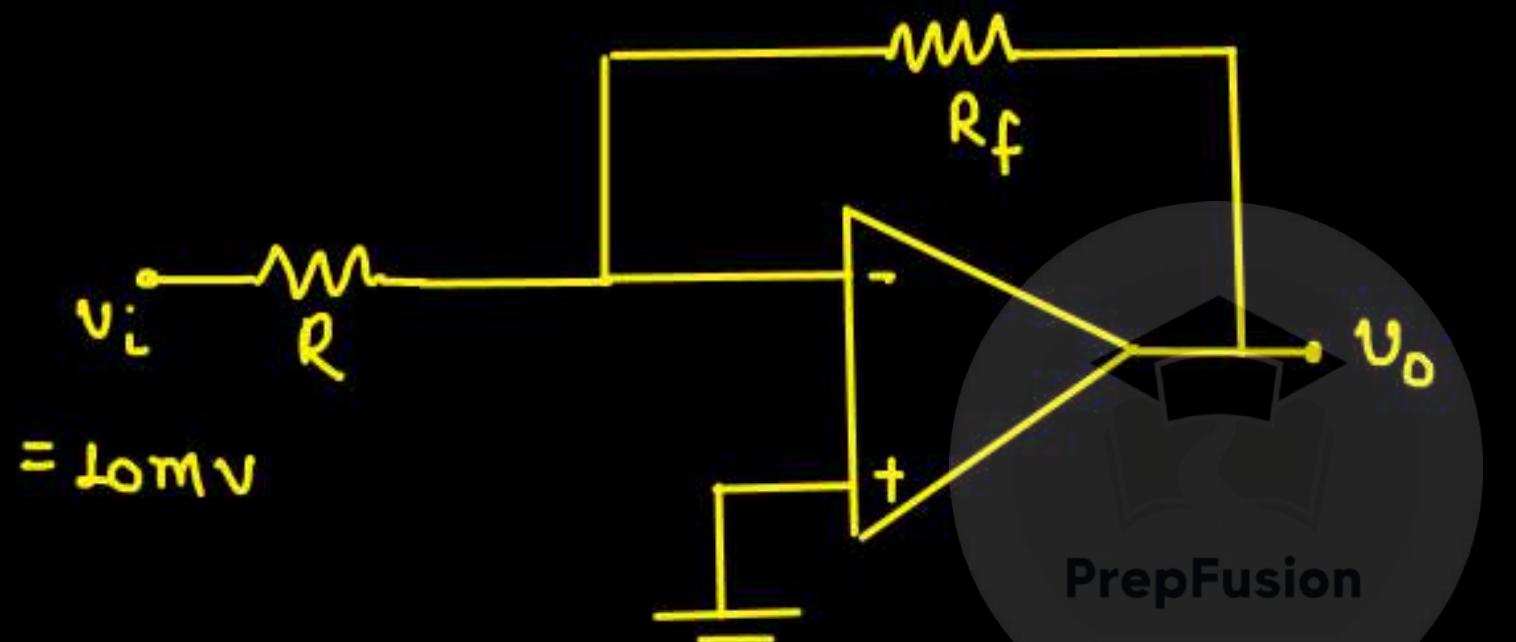* Consider an inverting OP-amp with $\frac{R_f}{R} = 100$




Considering zero offset , $\frac{U_o}{V_i} = -\frac{R_f}{R} = -100$

$$U_o = -100 \times 10 \mu V$$

$$\boxed{U_o = -1V}$$

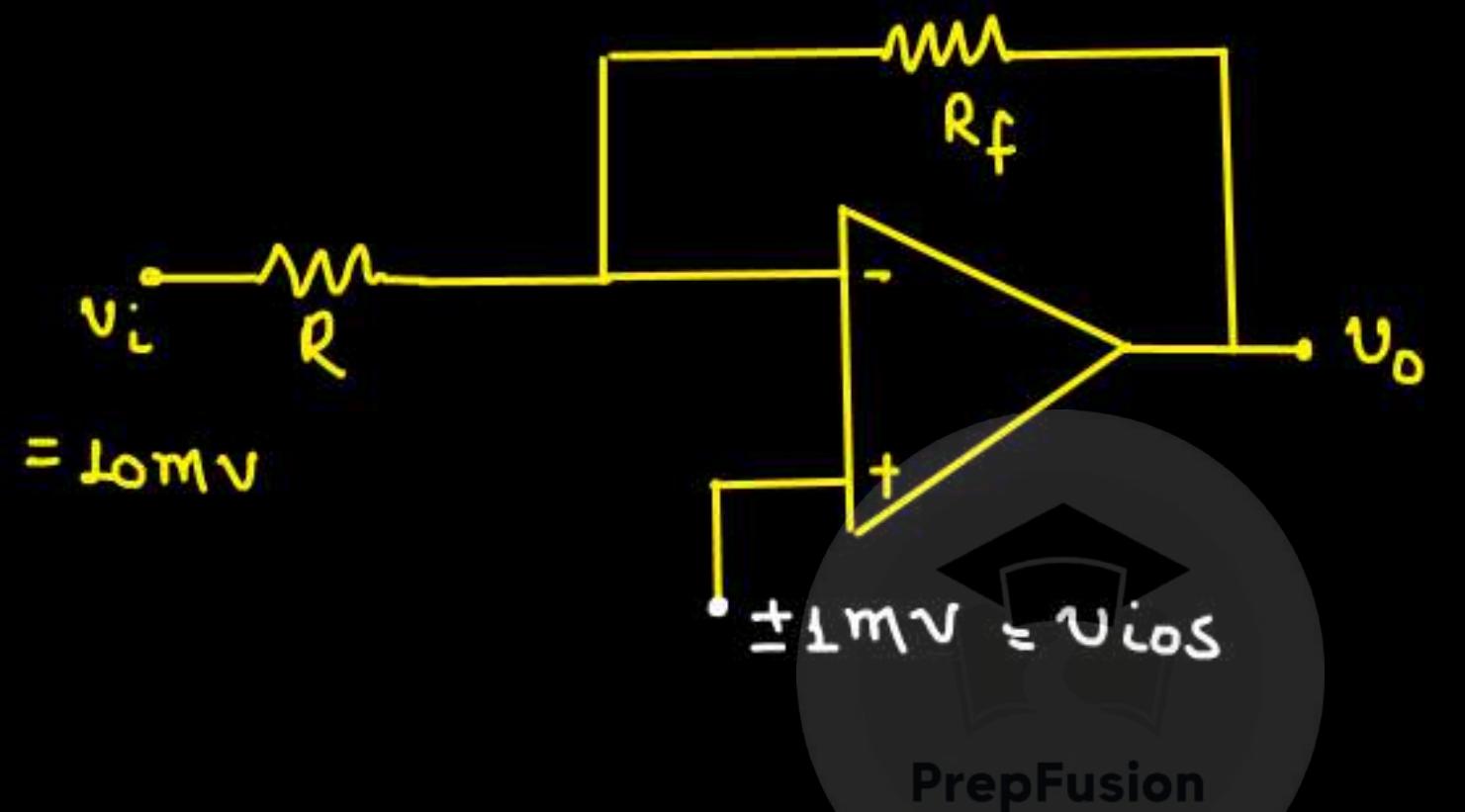
Now, let there is an offset of $\pm 1\text{mV}$.



$$\begin{aligned}
 v_o &= -\frac{R_f}{R} v_i + \left[1 + \frac{R_f}{R}\right] v_{ios} \\
 &= -100 \times 20\text{mV} + \left[1 + 100\right] [\pm 1\text{mV}] \\
 &= -1\text{V} \pm 0.101\text{V} \\
 &= -1.101\text{V}, -0.899\text{V}
 \end{aligned}$$


⇒ Input offset Current, Input bias current:-


ideally,

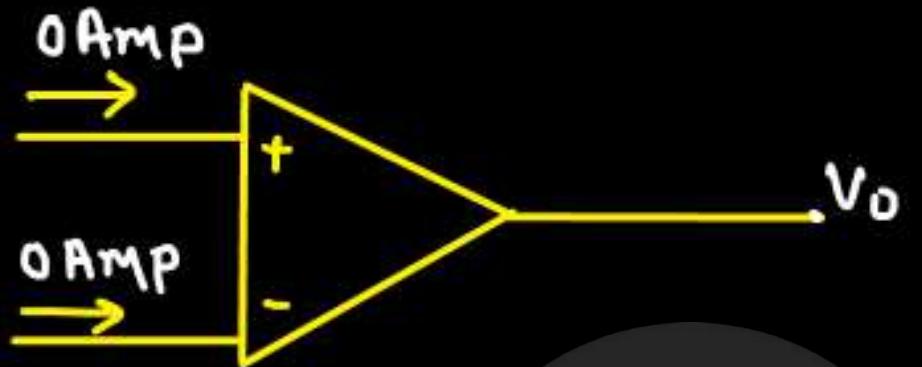

But,

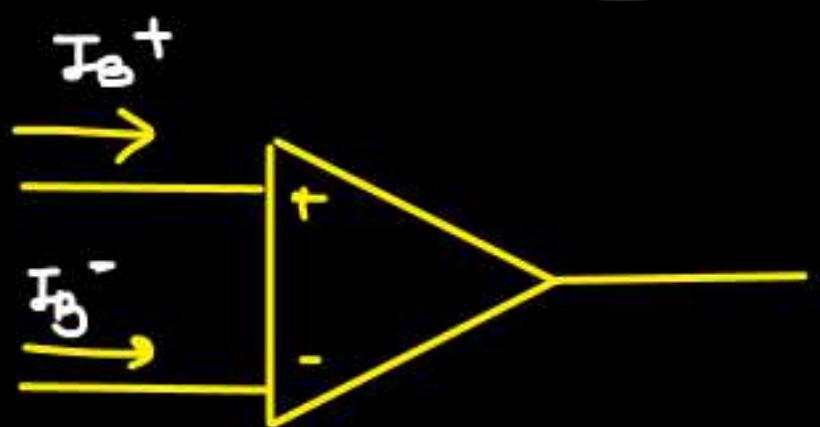There is some small amount of current that flows through the ^{PrepFusion} i/o terminals of the op-amps.



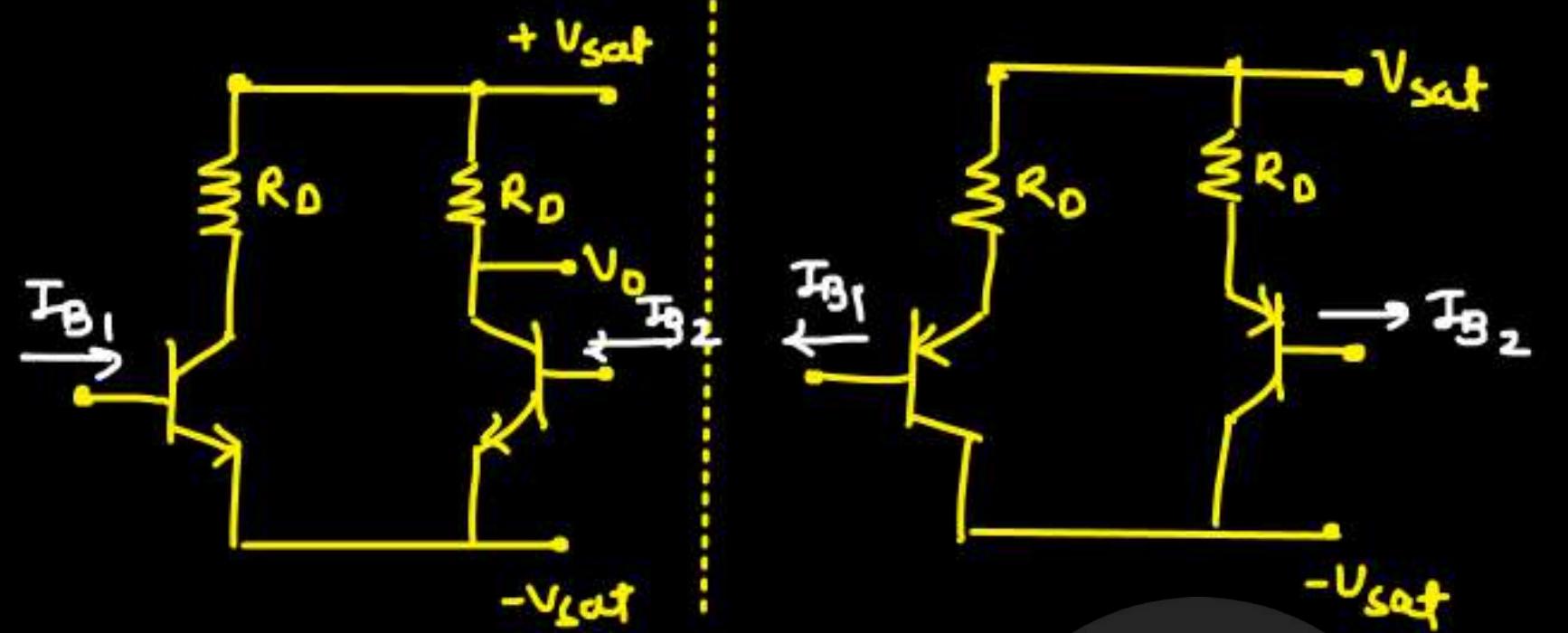

Input bias current :-

$$I_B = \frac{I_B^+ + I_B^-}{2}$$


Input offset current :-

$$I_{IOS} = | I_B^+ - I_B^- |$$

Range → μA to nA

⇒ Effect of bias current:-

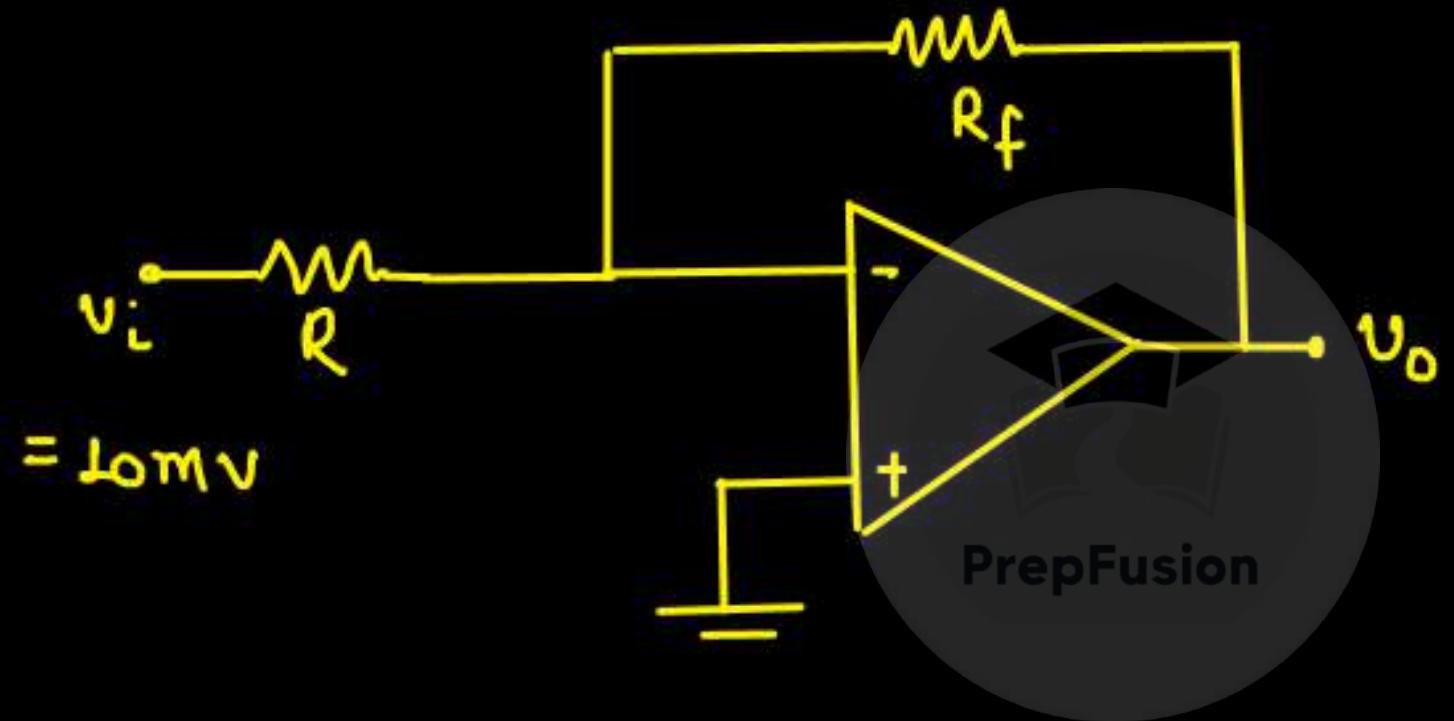
* Consider an inverting OP-Amp with $\frac{R_f}{R} = 100$



Considering zero offset , $\frac{U_o}{V_i} = - \frac{R_f}{R} = -100$

$$U_o = -100 \times 10\text{mV} = 1\text{V}$$

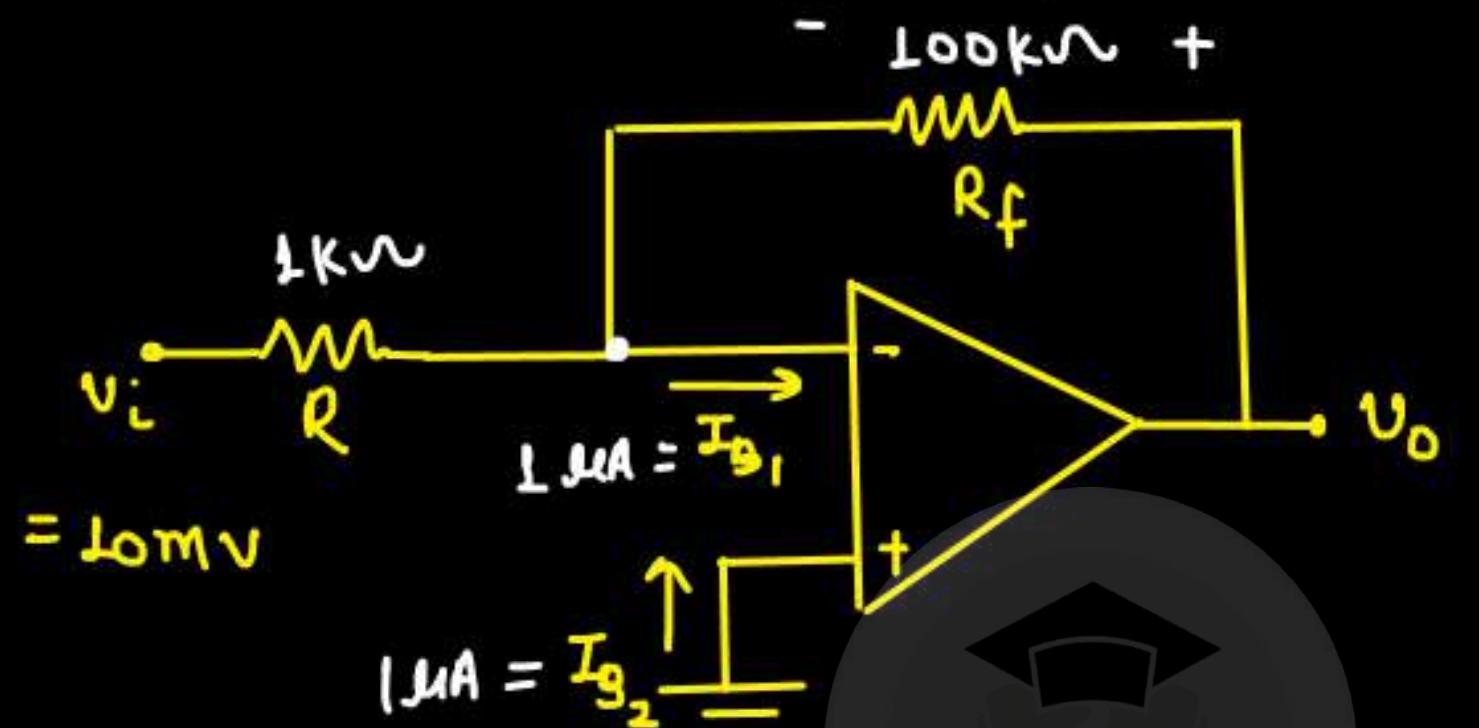
Now, Consider bias currents are present as shown.



Take $R_f = 100k\Omega$, $R = 1k\Omega$, $I_{B1} = I_{B2} = 1\mu A$

$$\begin{aligned}
 V_o &= -\frac{R_f}{R} V_i + I_{B1} \times R_f \\
 &= -(100 \times 10^3 \times 10^{-6}) \times 100 \times 10^3 + [1 \times 10^{-6}] \times 100 \times 10^3 \\
 &= -1V + 0.1 = -0.9V
 \end{aligned}$$

Q. Find v_o .

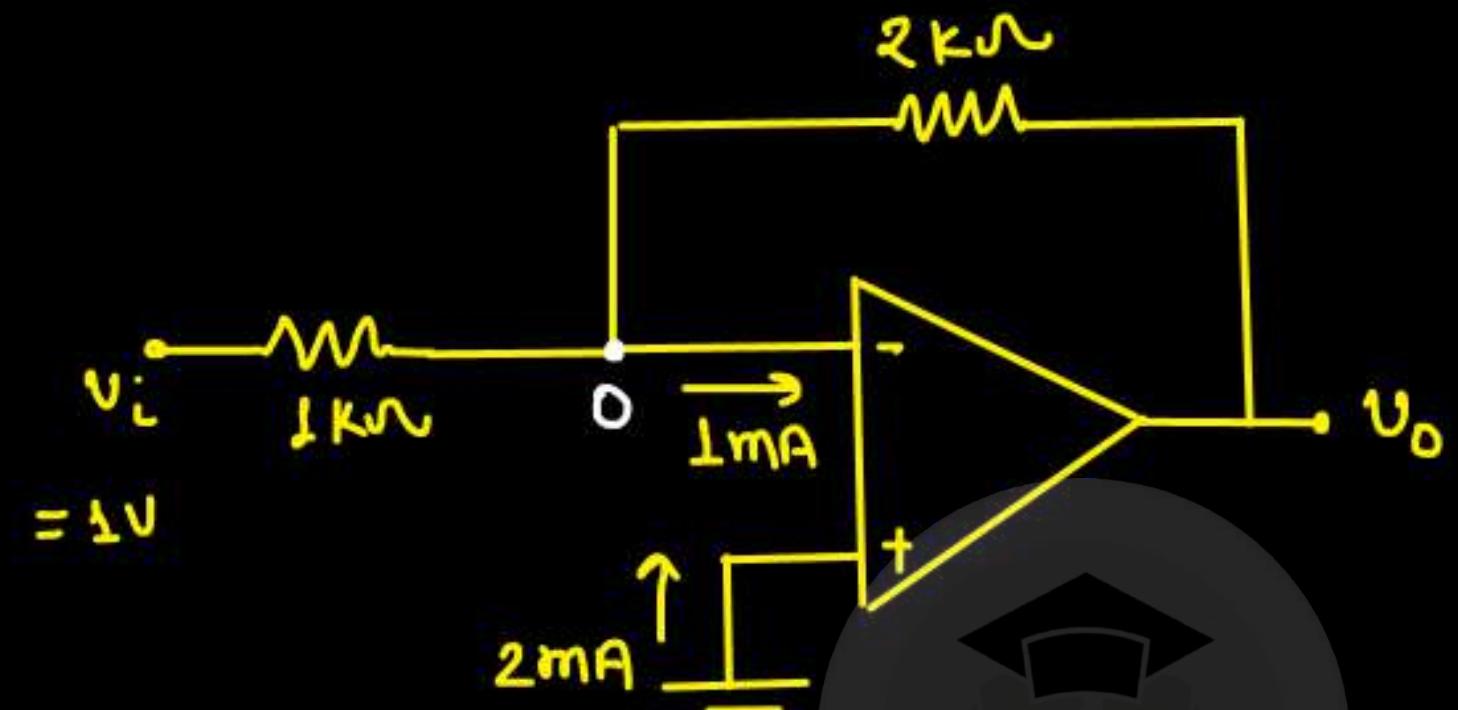

$$\frac{0 - 1}{1k} + 1mA + \frac{0 - v_o}{2k} = 0$$


$v_o = 0V$

PrepFusion

$$v_o = -2 \times 1V + 2k \times 1mA$$

$v_o = 0V$

Q.

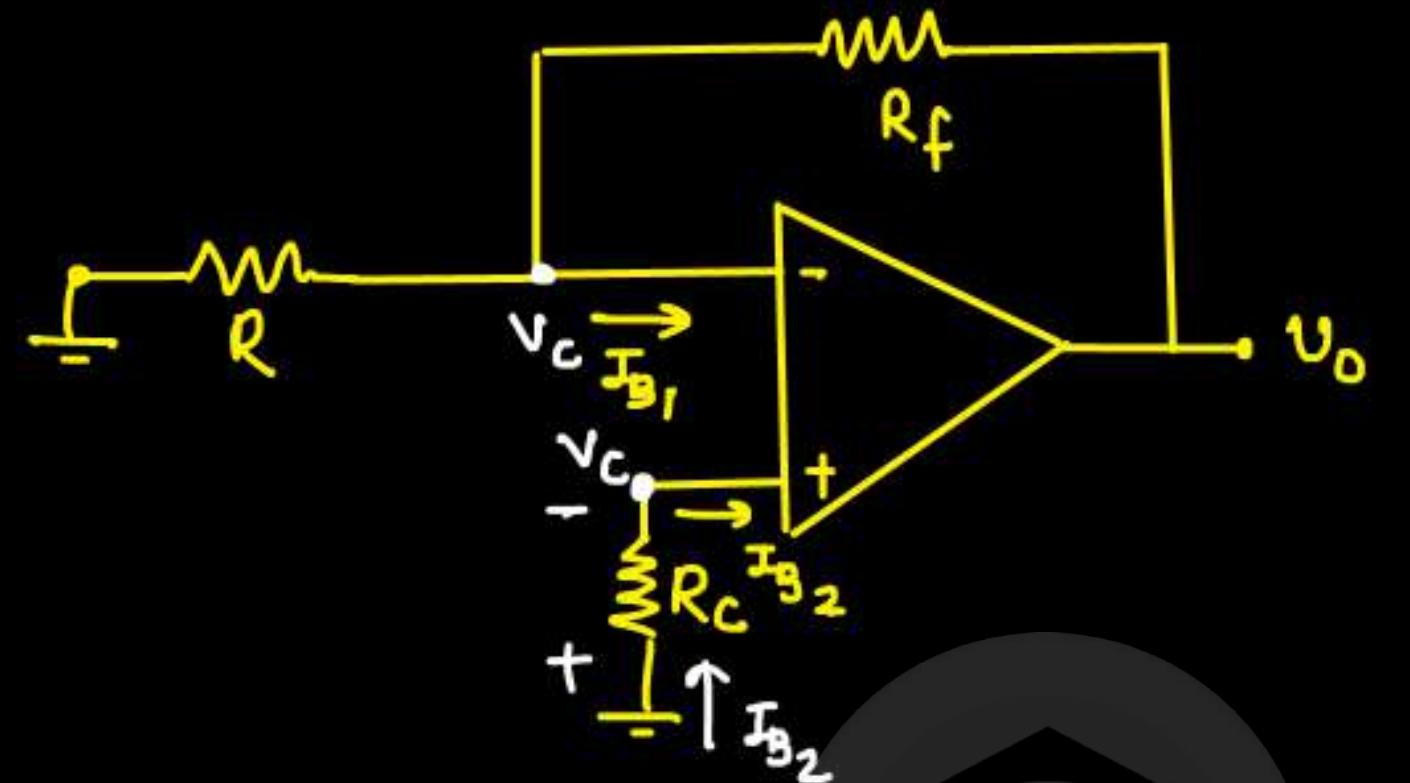

- (i) Find o/p voltage v_o .
 (ii) if $R_C = R \parallel R_f$, find v_o .

→

$$v_C = - I_B2 \times R_C - 0$$

$$\frac{v_C}{R} + \frac{v_C - v_o}{R_f} + I_{B1} = 0$$

$$\frac{V_C}{R} + \frac{V_C}{R_f} + I_{B_1} = \frac{V_o}{R_f}$$

$$R_f \left[-I_{B_2} R_C \left[\frac{1}{R} + \frac{1}{R_f} \right] + I_{B_1} \right] = V_o$$

*J

$$\text{if } R_C = R \parallel R_f$$



$$-I_{B_2} \times \left(\frac{RR_f}{R+R_f} \right) \left[\frac{R_f + R}{RR_f} \right] + I_{B_1} = \frac{V_o}{R_f}$$

$$\text{if } I_{B_1} = I_{B_2} = I_B$$


$$V_o = (0) R_f$$

$$V_o = 0V$$


$$N_o = R_f (I_{B_1} - I_{B_2})$$

$$V_o = R_f \times I_{ios}$$

Conclusion :-

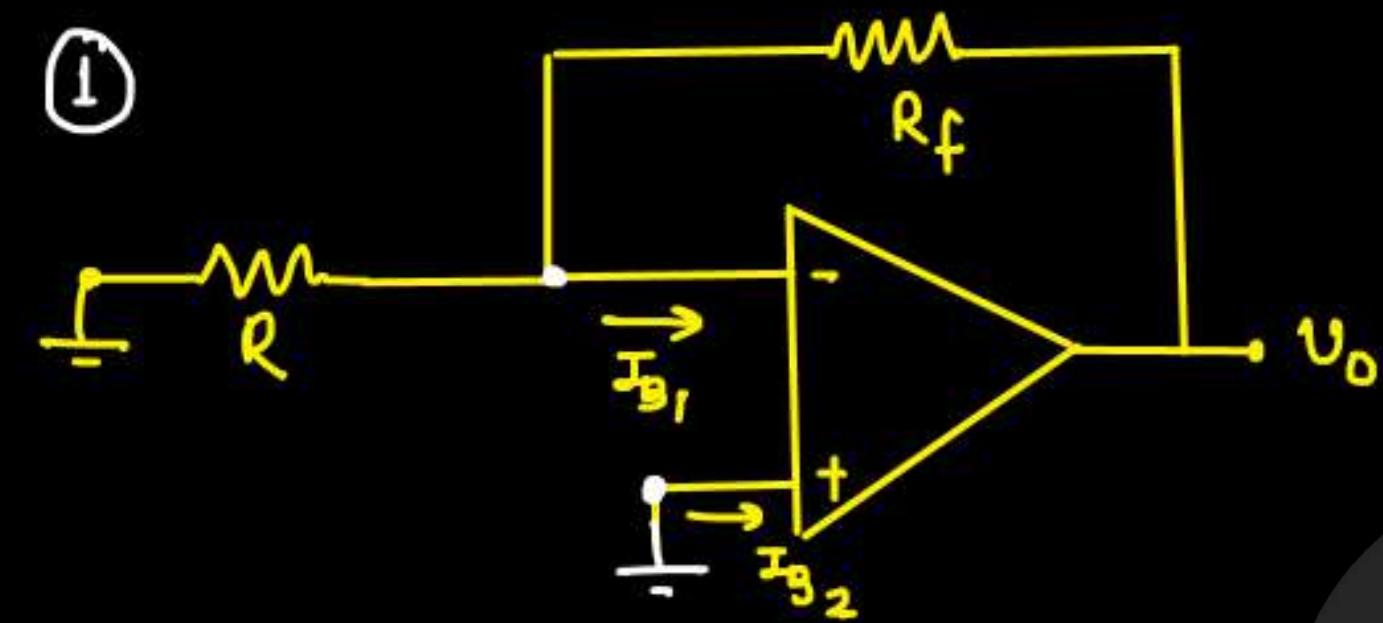

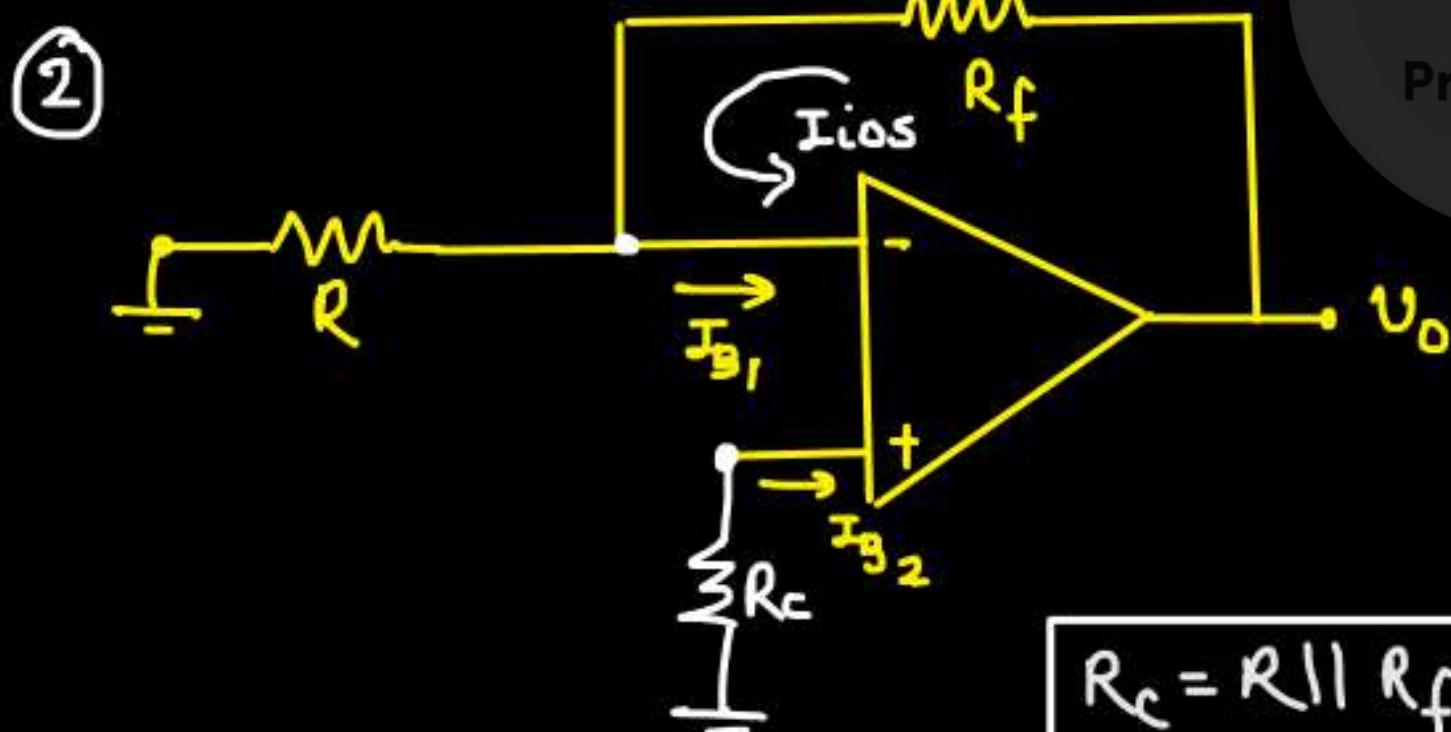
$$\textcircled{1} \quad V_o = I_{B1} R_f$$



$$R_c = R \parallel R_f$$



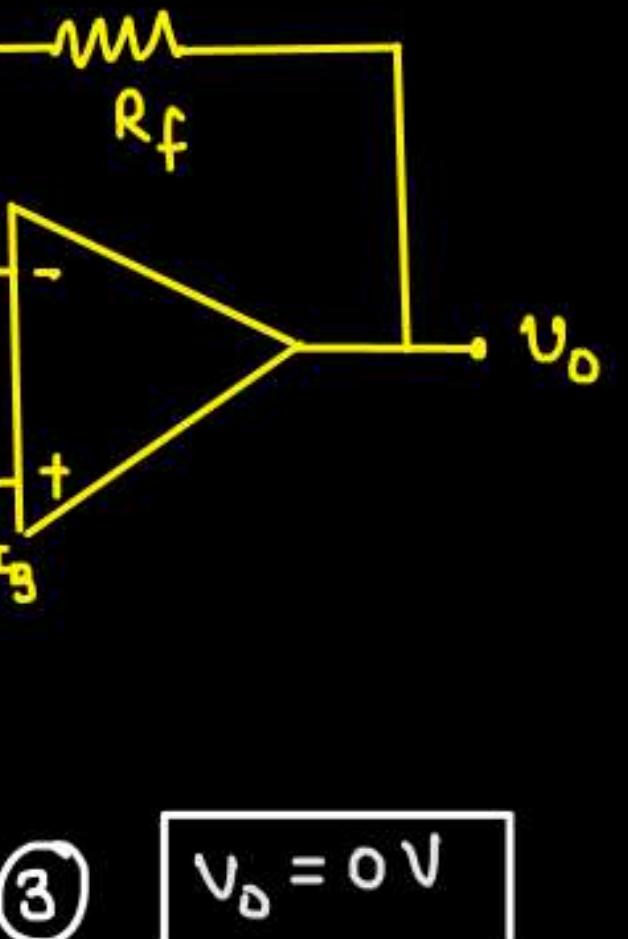
$$\textcircled{2} \quad V_o = I_{B1} R_f$$



$$\textcircled{3} \quad V_o = 0V$$

Q.

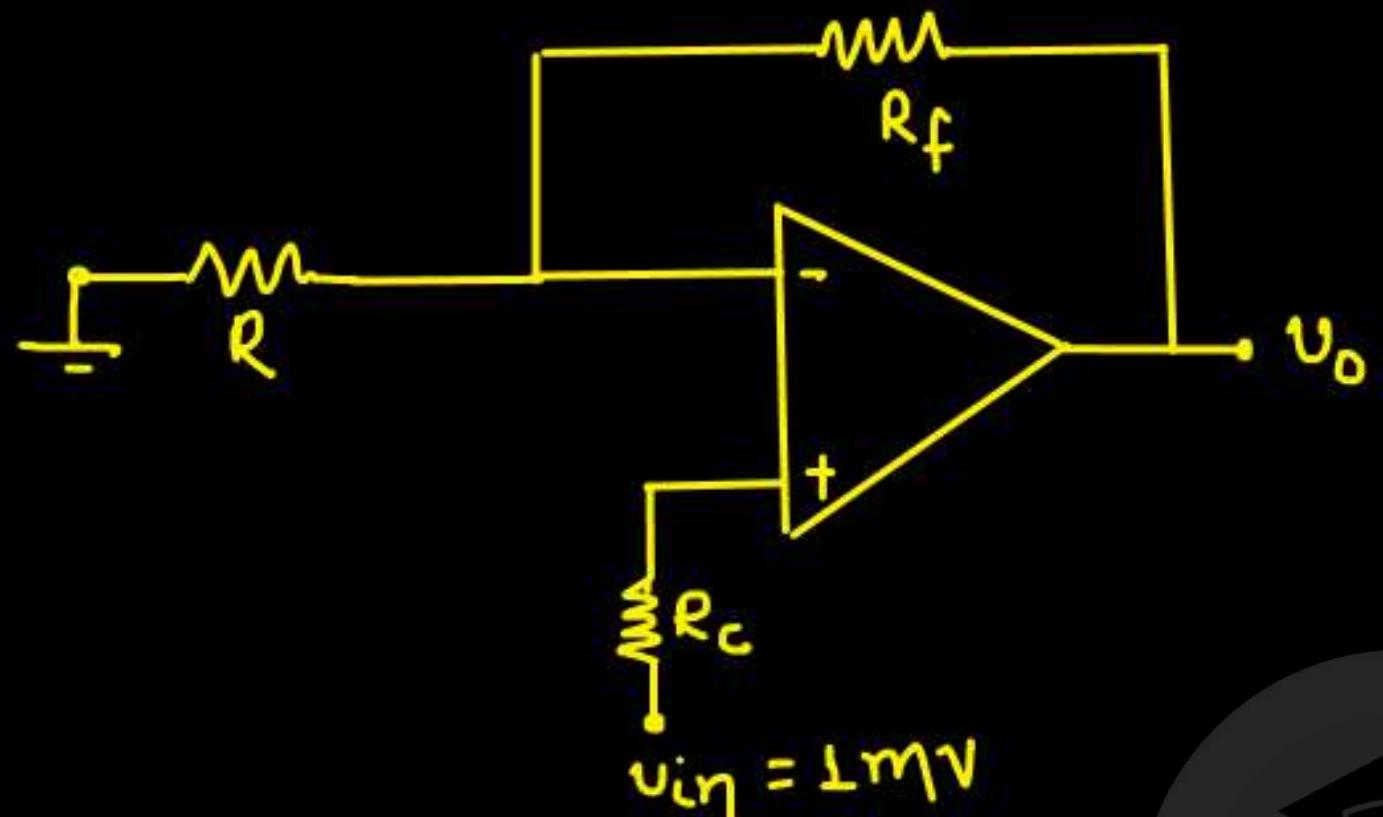

$$\rightarrow I_{ios} = 50\text{nA}$$

$$I_B = 100\text{nA}$$



For the given config,

$$R = 1\text{k}\Omega, \quad R_f = 9\text{k}\Omega, \quad R_c = 900\Omega$$

input offset voltage = 0.5mV


input offset current = 50nA

input bias current = 100nA

Find v_o .


Applying Superposition:-

(i) Considering only v_{in}

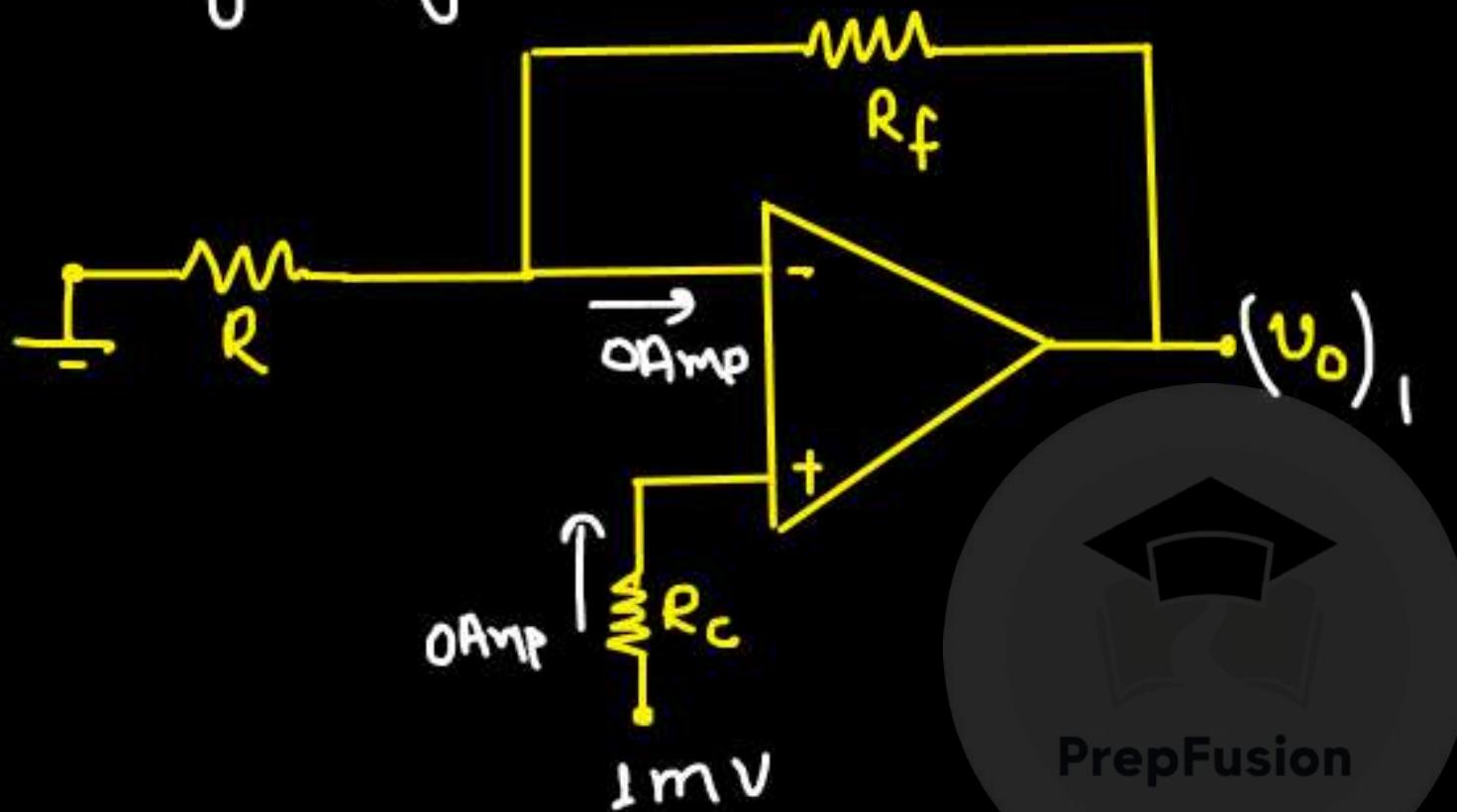

$$v_{o1} = \left(1 + \frac{R_f}{R}\right) \times 1mV = 10mV$$


considering only offset voltage:-

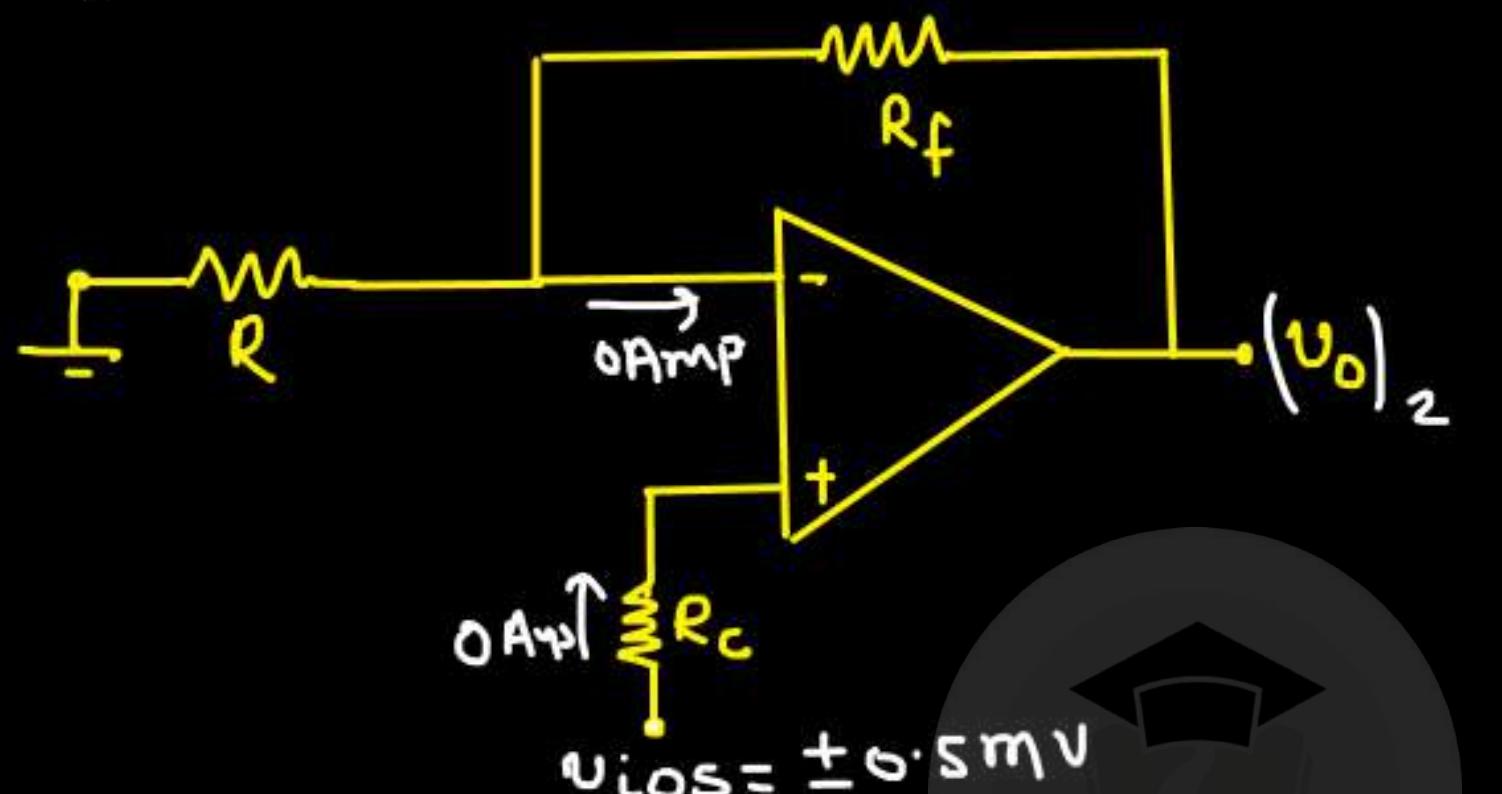

$$v_{o2} = \left(1 + \frac{R_f}{R}\right) \times (\pm 0.5mV)$$

$v_{o2} = \pm 5mV$

Considering bias and offset current :-

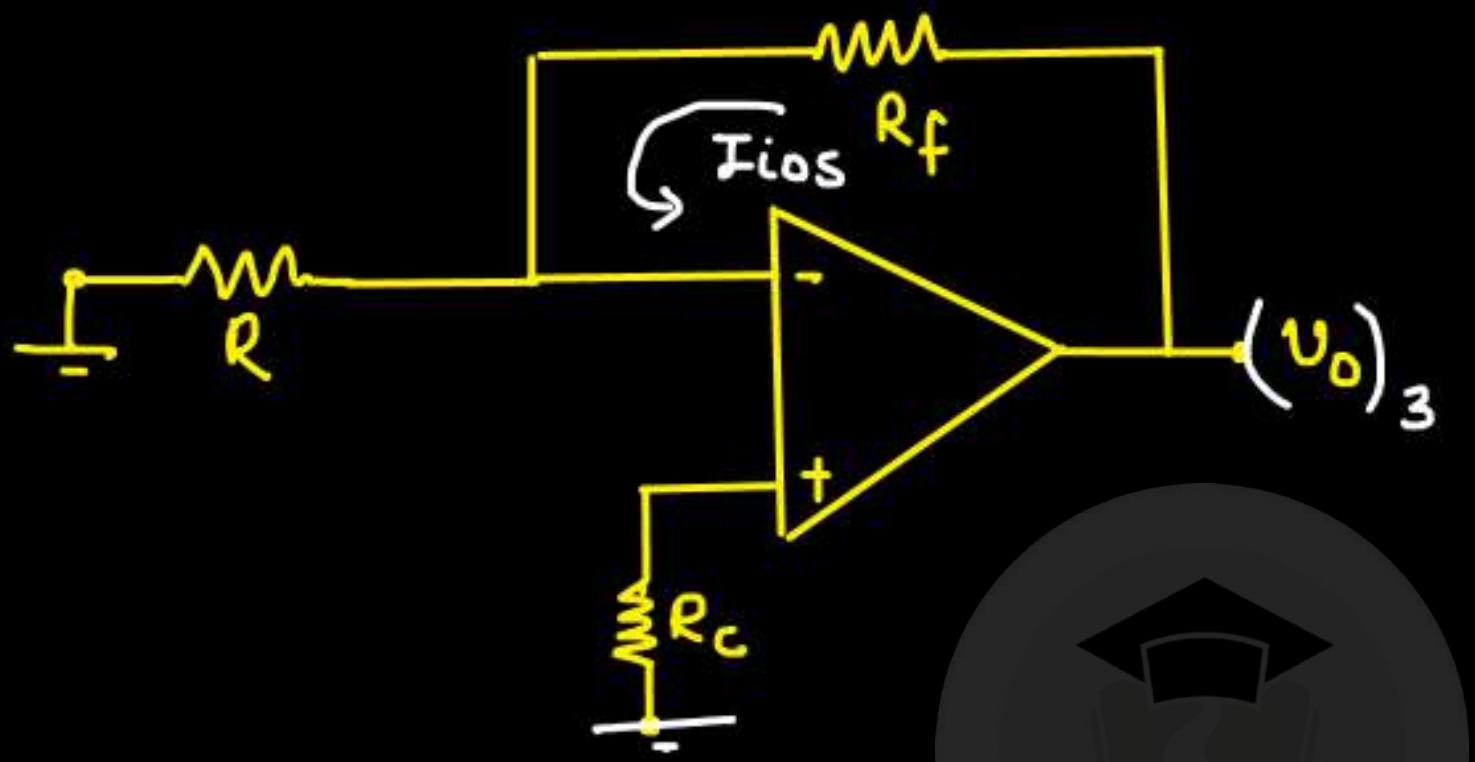

$$\begin{aligned}(V_o)_3 &= \pm I_{ios} \times R_f \\ &= \pm 50 \text{nA} \times 9 \text{k} \\ &= \pm 45 \times 10^{-5} \text{ V}\end{aligned}$$

$$(V_o)_3 = \pm 0.45 \text{ mV}$$


$$(V_o)_{\max} = 15.45 \text{ mV}$$

$$(V_o)_{\min} = 4.55 \text{ mV}$$


$$V_o = V_{o_1} + V_{o_2} + (V_o)_3 = 10 \text{ mV} \pm 5 \text{ mV} \pm 0.45 \text{ mV}$$

* Frequency Response of OP-Amp:-

ideally,

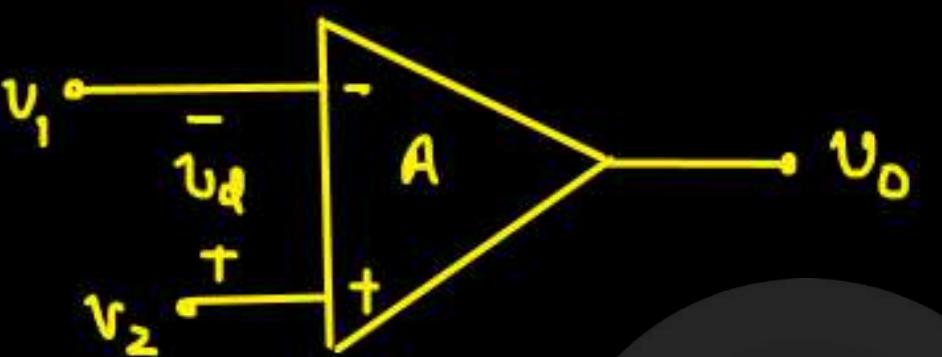


$$\frac{v_o(s)}{v_d(s)} = A$$

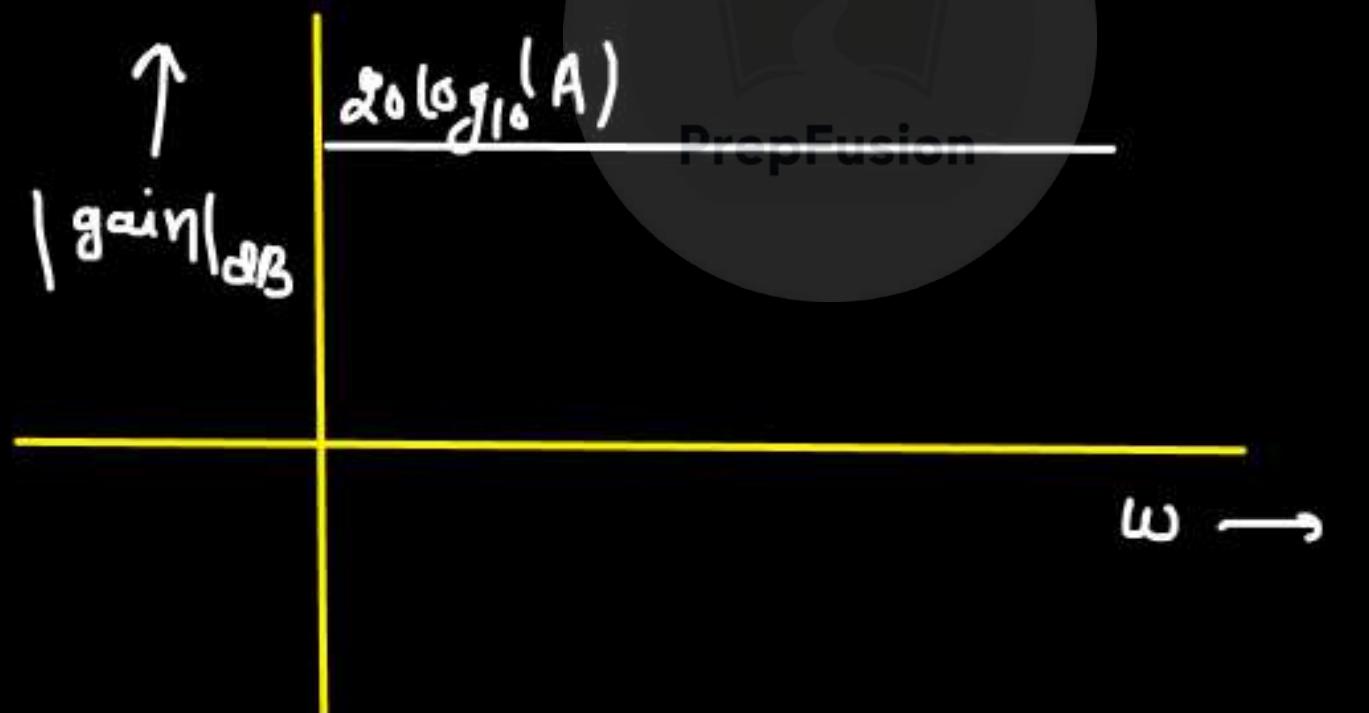

But practically,

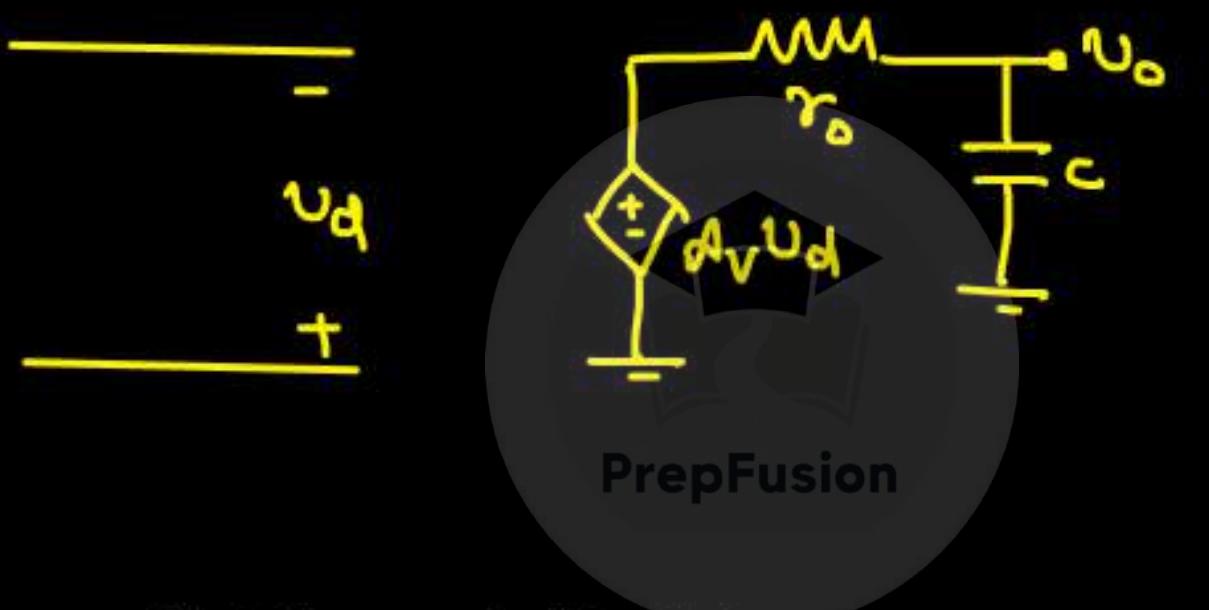The freq. response of op-amp is same as
low-pass filter.




$$u_o(s) = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + r_o} A_v u_d(s)$$

$$u_o(s) = \frac{A_v u_d(s)}{r_o s + 1}$$


$$\frac{u_o(s)}{u_d(s)} = \frac{A_v}{s/\omega_0 + 1}$$

; $\omega_0 = \frac{1}{r_o C}$

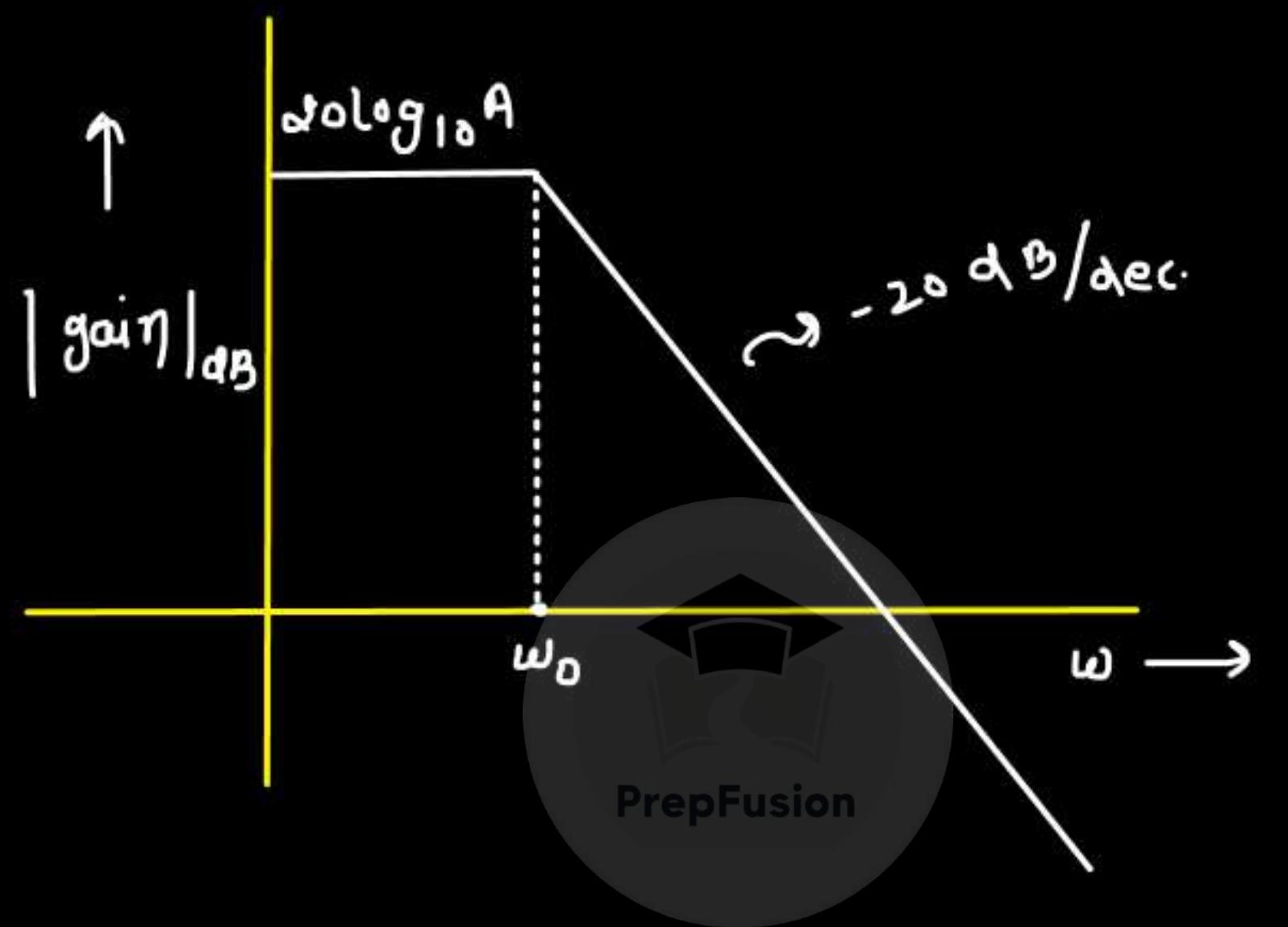


$$\frac{v_o(s)}{v_d(s)} = T(s) = \frac{\omega_v}{s/\omega_0 + 1}$$

$$|T(j\omega)| = \frac{\omega_v}{\sqrt{(\omega/\omega_0)^2 + 1}}$$

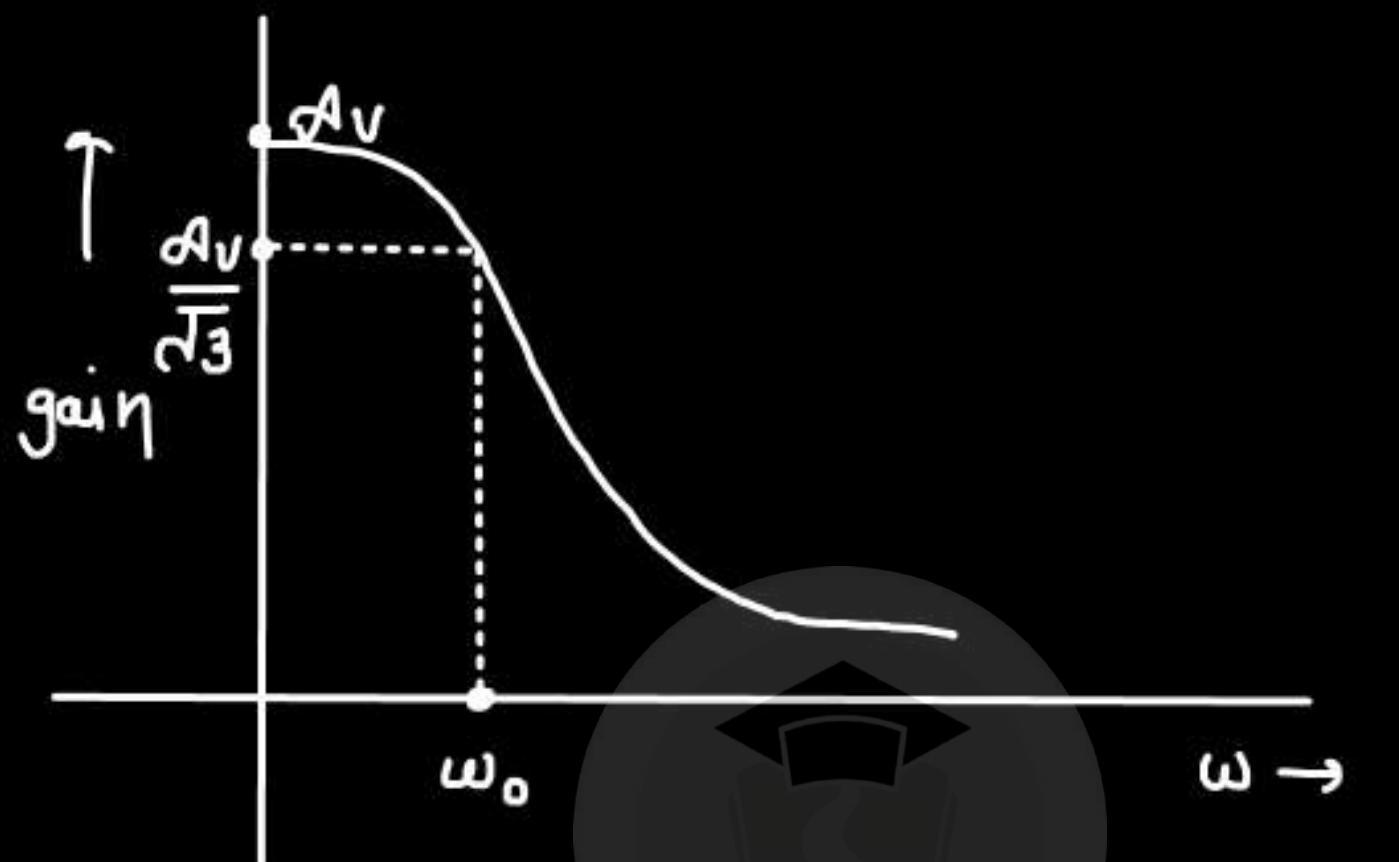

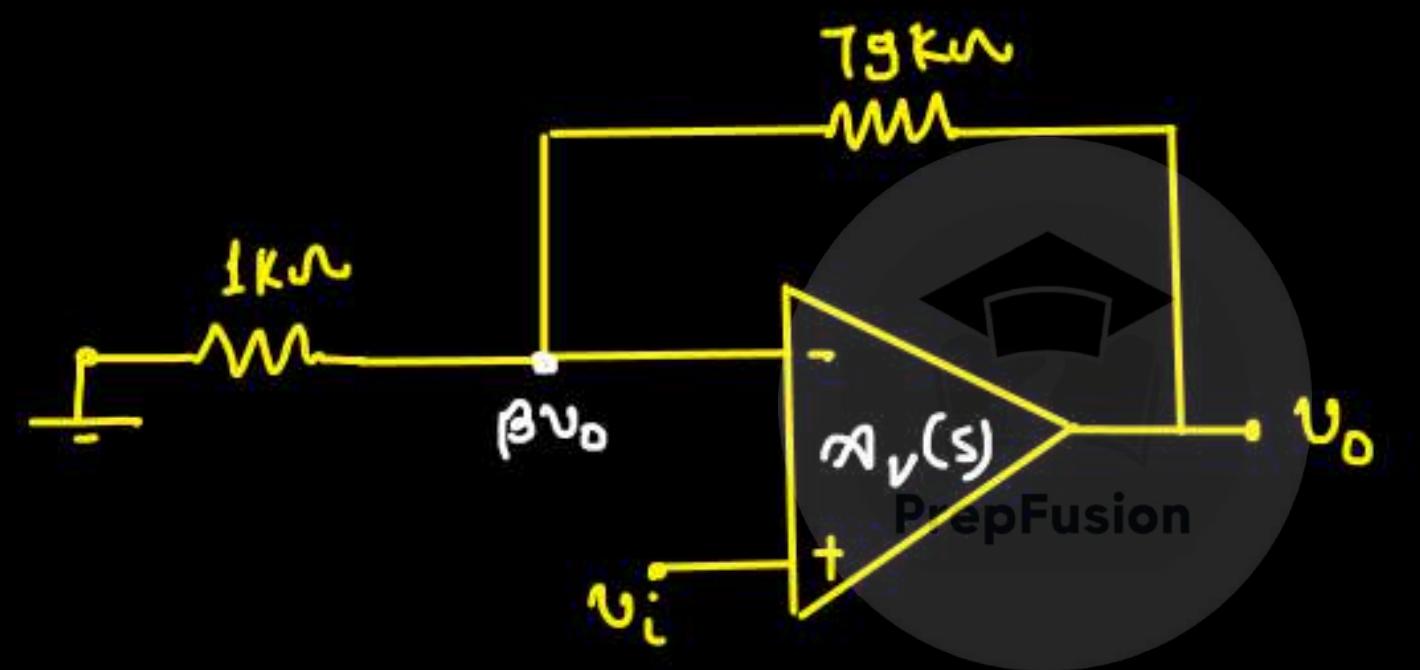Q. For the given op-amp, open loop gain is 10^5 V/V .
and open loop cut-off freq. is 8Hz.
The voltage gain of amplifier at 15KHz is ____



$$\rightarrow \begin{aligned} \infty &= 10^5 \text{ V/V} \\ f_0 &= 8 \text{ Hz} \\ \omega_0 &= 16\pi \text{ rad/sec.} \end{aligned}$$

$$A_v(s) = \frac{10^5}{s/\omega_0 + 1}$$

$$\left\{ \omega_0 = 16\pi \text{ rad/sec.} \right\}$$

$$A_V(s) [V_{in}(s) - \beta V_o(s)] = V_o(s)$$

$$\beta = \frac{1k}{1k + 79k} = \frac{1}{80}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{A_U(s)}{(1 + A_U(s))\beta}}$$

$$\frac{V_o(s)}{V_i(s)} = [A_U(s)]_f = \frac{\frac{10^5}{s/\omega_0 + 1}}{\frac{10^5}{s/\omega_0 + 1} \times \frac{1}{80}} = \frac{80 \times 10^5}{80(s/\omega_0 + 1) + 10^5}$$

$$[A_V(j\omega)]_f = \frac{80 \times 10^5}{80 \left[\frac{j\omega}{\omega_0} + 1 \right] + 10^5}$$

$$[\alpha_v(jf)]_f = \frac{80 \times 10^5}{80 \left[j \frac{f}{f_0} + 1 \right] + 10^5}$$

$$[\alpha_v(j15\text{KHz})]_f = \frac{80 \times 10^5}{80 \left[j \frac{15 \times 10^3}{R} + 1 \right] + 10^5}$$

$$|\alpha_v(j15\text{KHz})|_f = \left| \frac{80 \times 10^5}{j 15 \times 10^4 + 80 + 10^5} \right|$$

$$= \frac{80 \times 10^5}{\sqrt{(80 + 10^5)^2 + (15 \times 10^4)^2}}$$

$$= 44.36 \text{ V/V}$$

Ans.

M-II:-

$$(\alpha_v)_f = \frac{10^5}{1 + 10^5 \times \frac{1}{80}} \approx 80$$

$$(f_0)_f = f (1 + \alpha\beta) = 8 \left[1 + \frac{10^5}{80} \right] \approx 10 \text{ kHz}$$


$$[\alpha_v(jf)]_f = \frac{80}{\frac{jf}{10k} + 1}$$

$$[\alpha_v(j15k)]_f = \frac{80}{\frac{j15k}{10k} + 1} = \frac{80}{j(1.5 + 1)} =$$

gain at 15kHz = $\frac{80}{\sqrt{(1.5)^2 + 1}} = 44.31 \text{ v/v}$

④ CMRR (Common Mode Rejection Ratio) :-

For Differential Amplifier :-

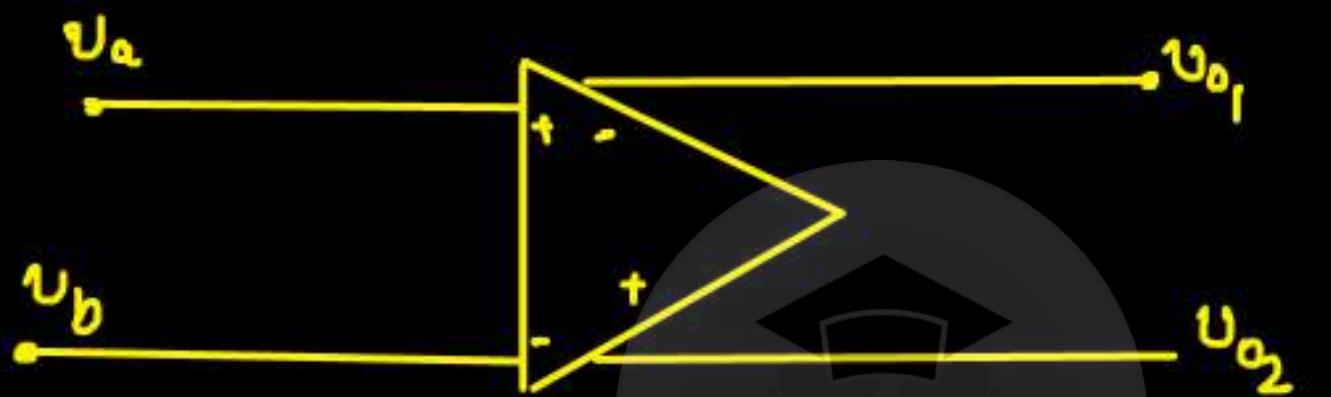

Differential gain (α_d) =
$$\frac{u_{o2} - u_{o1}}{u_{in}}$$

$$\left\{ u_a = \frac{u_{in}}{2}, u_b = -\frac{u_{in}}{2} \right\}$$


Common Mode Differential Gain (α_{CM-DM}) =
$$\frac{u_{o2} - u_{o1}}{u_{CM}}$$
 $\left\{ u_a = u_b = u_{CM} \right\}$

$$CMRR = \left| \frac{\text{Differential Gain}}{\text{Common Mode Differential Gain}} \right|$$


For Op-Amp:-

$$CMRR = \left| \frac{\text{Differential Gain}}{\text{Common Mode Gain}} \right|$$

PrepFusion

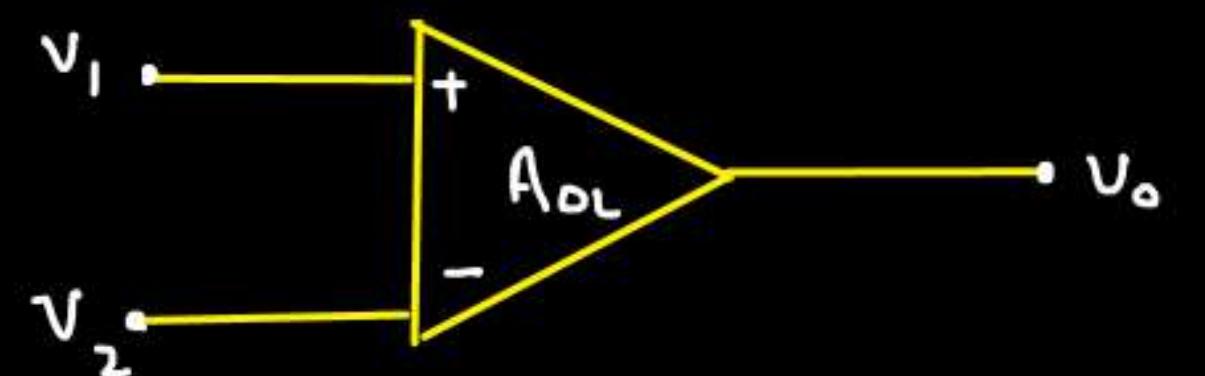


Differential Gain :-

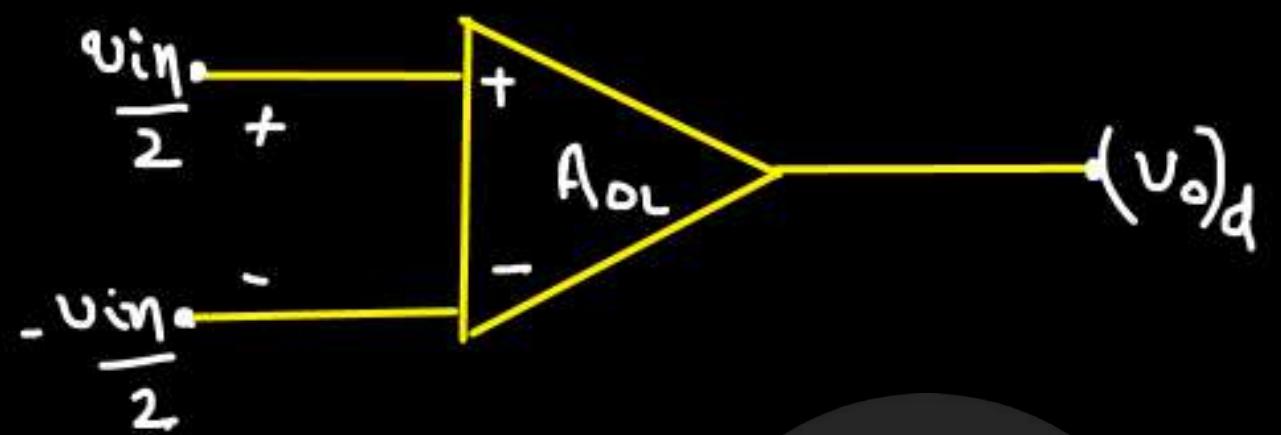

$$(v_o)_d = A_{OL} \left[\frac{v_{in+}}{2} + \frac{v_{in-}}{2} \right] = A_{OL} v_{in}$$

⇒ differential gain $\alpha_d = \frac{(v_o)_d}{v_{in}} = A_{OL}$

Common Mode Gain :-

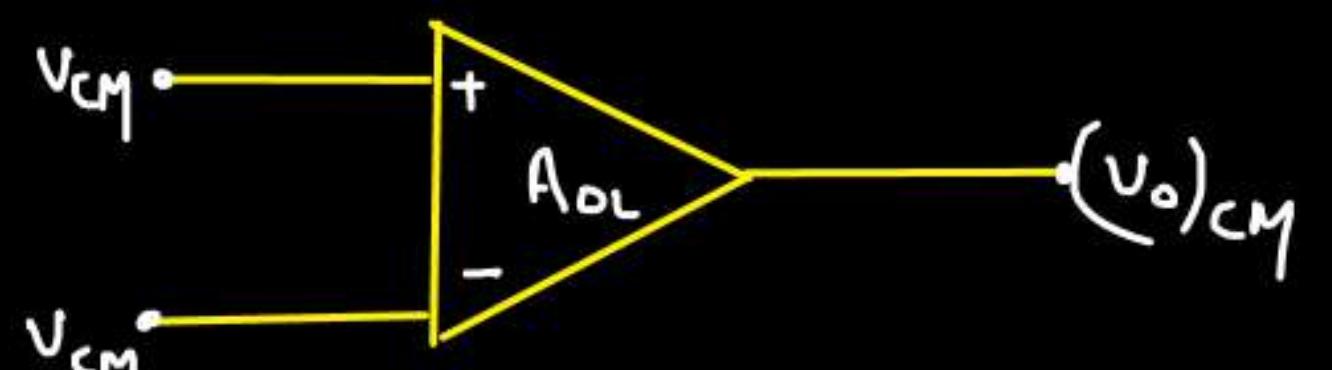

$$(v_o)_{CM} = A_{OL} (v_{CM+} - v_{CM-})$$


$$\Rightarrow (v_o)_{CM} = 0$$

$$(\alpha_v)_{CM} = \frac{(v_o)_{CM}}{v_{CM}} = 0$$

$$CMRR = \frac{A_d}{A_c} = \frac{A_{OL}}{0} = \infty$$

for an ideally op-amp $CMRR = \infty$

But, Practically

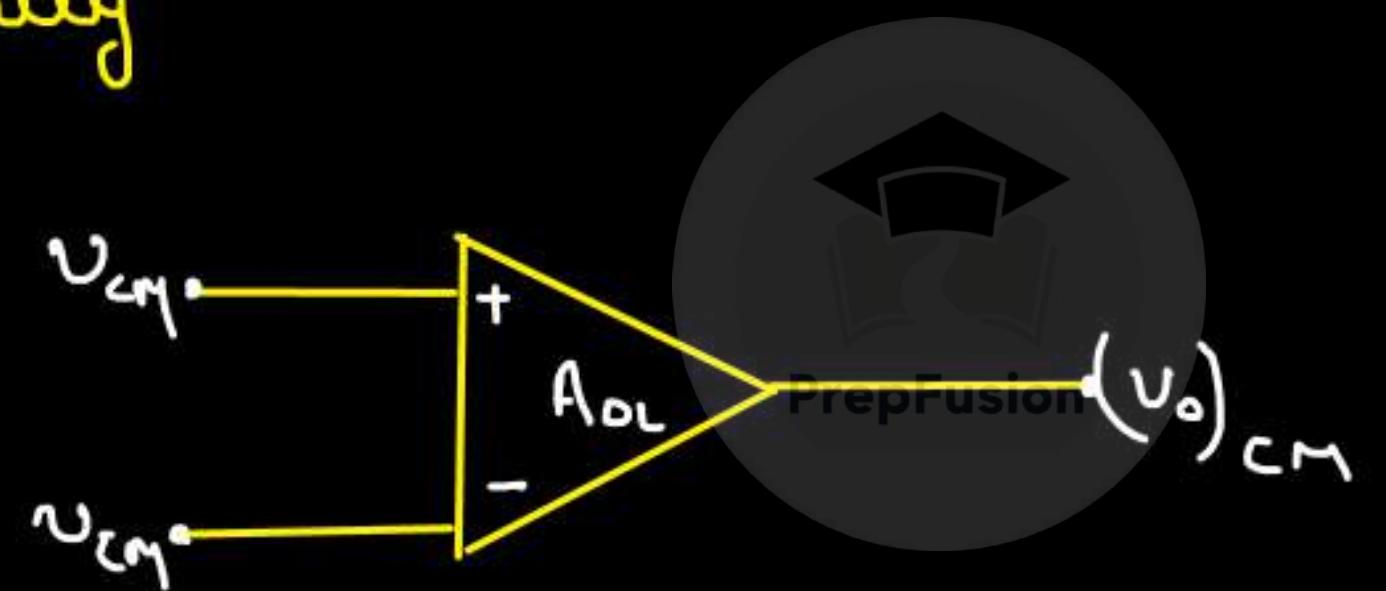


common Mode gain is by

$$(A)_{CM} = \frac{(v_o)_{CM}}{v_{CM}}$$

$$CMRR = \left| \frac{A_d}{A_c} \right|$$

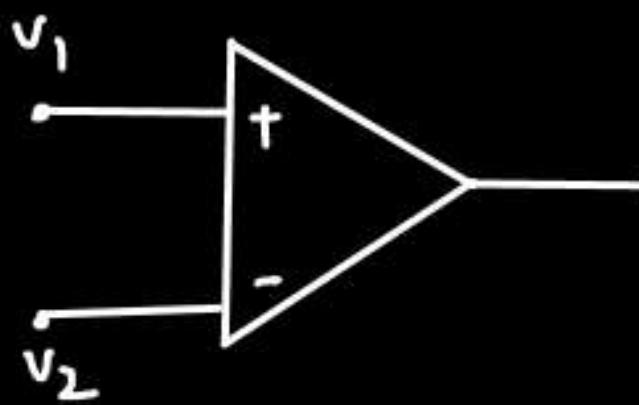So, Generally o/p of OP-Amp can be expressed as



$$v_o = A_d v_d + \alpha_{CM} v_{CM}$$


$$v_o = (\text{differential gain} \times \text{differential input}) + (\text{common Mode gain} \times \text{common Mode input})$$

$$v_o = A_d (v_1 - v_2) + \alpha_{CM} \left(\frac{v_1 + v_2}{2} \right)$$

$$CMRR = \left| \frac{\alpha_d}{\alpha_{CM}} \right|$$

↳ Generally CMRR is defined for open-loop config. of OP-Amp but when we use op-amp as Differential amplifier, we take the same CMRR value for closed loop as well.

Q.

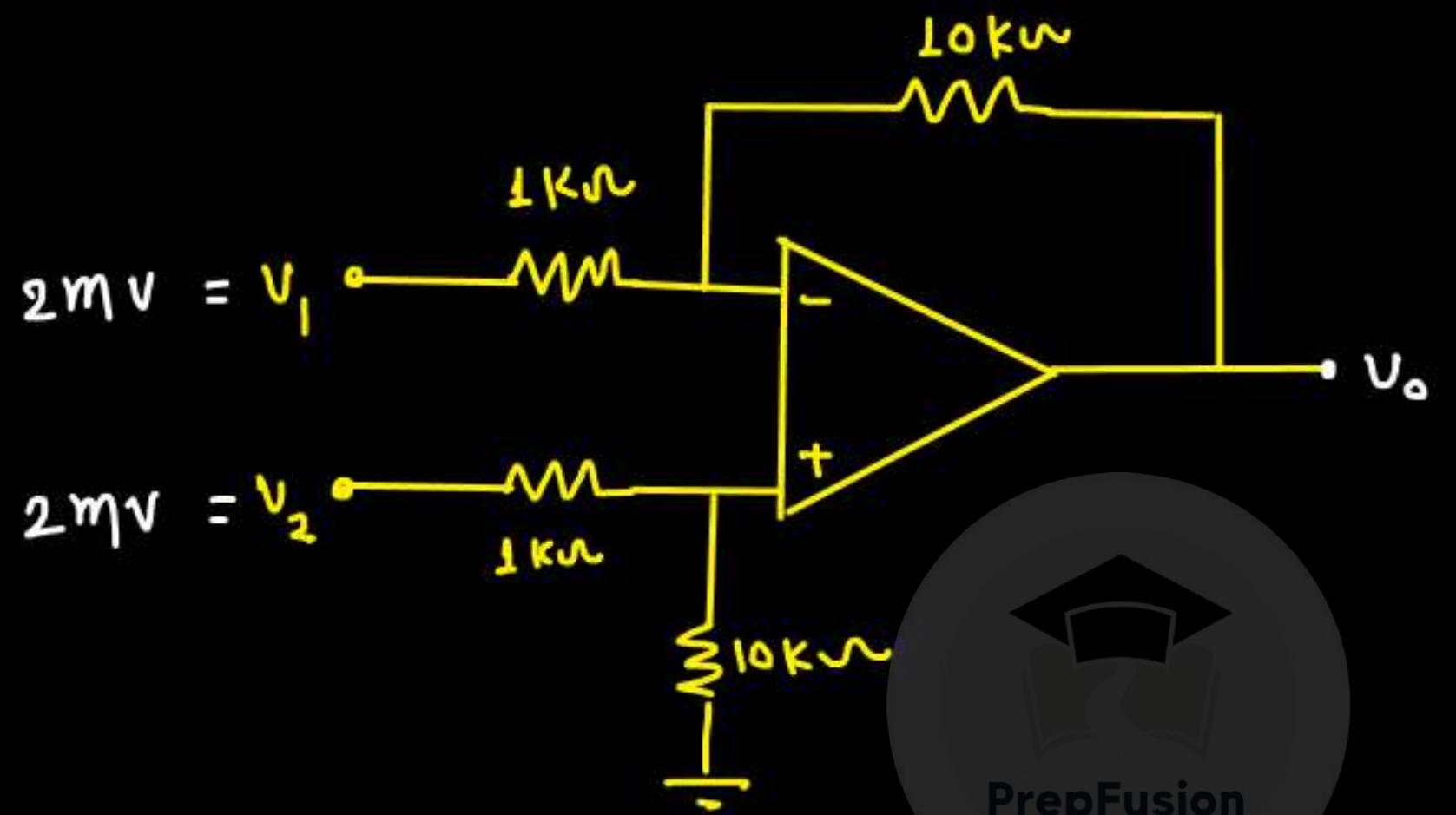

$$V_{id} = V_2 - V_1 = 5\text{mV}$$

$V_{CM} = 2\text{mV}$ (common Mode Signal)

CMRR of the op-amp = 90 dB

Find common Mode output voltage = ?

if OP-amp was ideal:-

$$(V_o)_{\text{out}} = \frac{10k}{2k} (V_{CM} - V_{CM}) = 0$$

But op-amp is having CMRR = 90dB

$$20 \log_{10} (\text{CMRR})_{\text{dec}} = 90$$

$$\text{CMRR} = 31622.78 = \frac{\text{Ad}}{\text{Ac}}$$

Differential Gain (Ad) = ?

$$\text{Differential o/p} = 10(V_2 - V_1) = 10 \times 5 \text{mV} = 50 \text{mV}$$

$$\text{Differential i/p} = V_2 - V_1 = 5 \text{mV}$$

$$\text{Differential Gain} (\text{Ad}) = \frac{50 \text{mV}}{5 \text{mV}} = 10 =$$

$$\frac{A_d}{A_c} = 31622.78$$

$$\frac{10}{A_c} = 31622.78$$

$$A_c = 3.16 \times 10^{-4}$$

⇒ common Mode gain

$$\frac{(V_o)_{CM}}{(V_i)_{CM}} = 3.16 \times 10^{-4}$$


PrepFusion

$$(V_o)_{CM} = 3.16 \times 10^{-4} \times 2 \times 10^{-3}$$

$$(V_o)_{CM} = 0.632 \mu V$$


Ans.

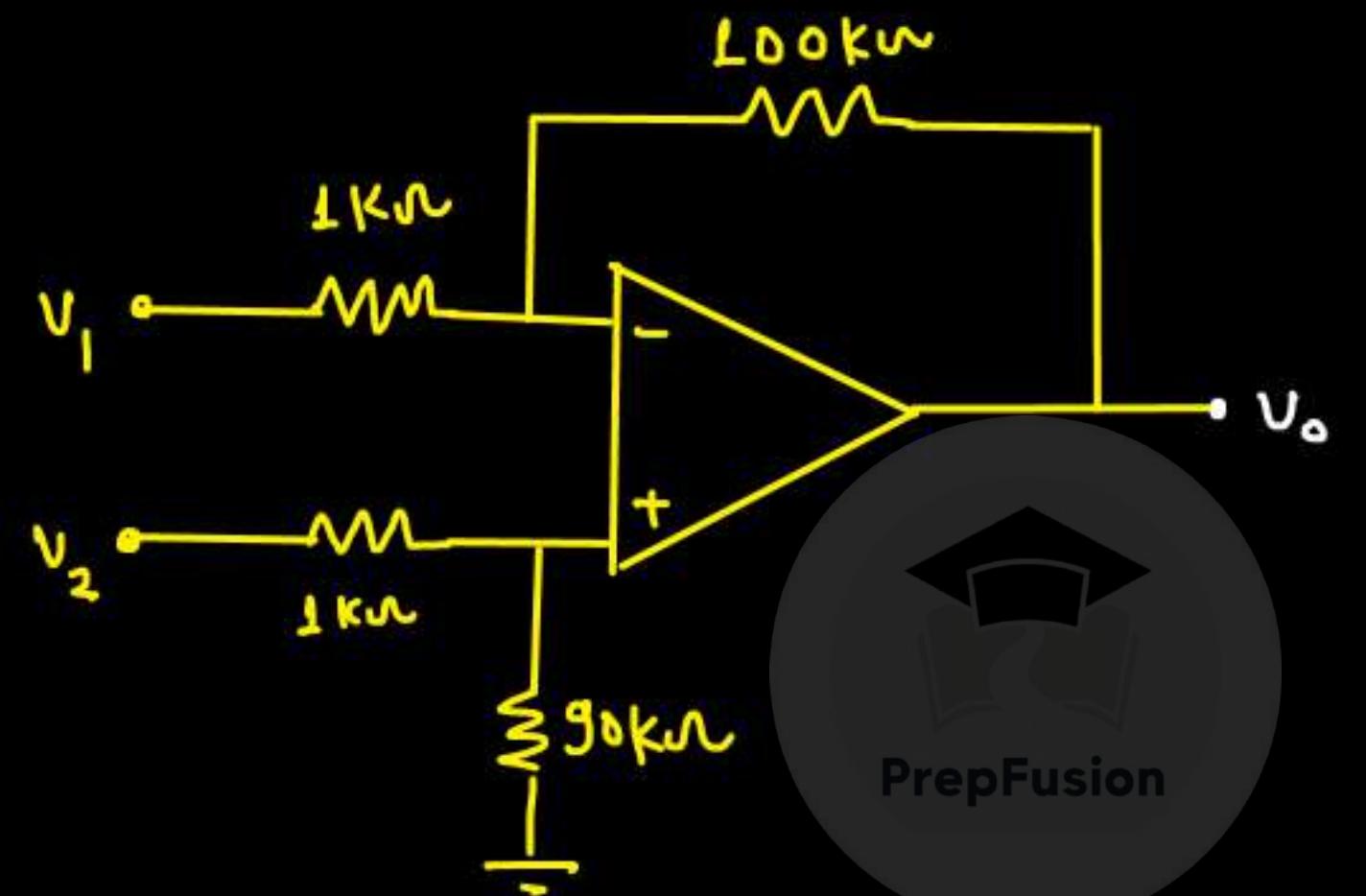Q. The given OP-amp is ideal. ($C_{MRR} = \infty$)



Find CMRR of the differential Amplifier shown:-

→ Differential Gain (α_d): -

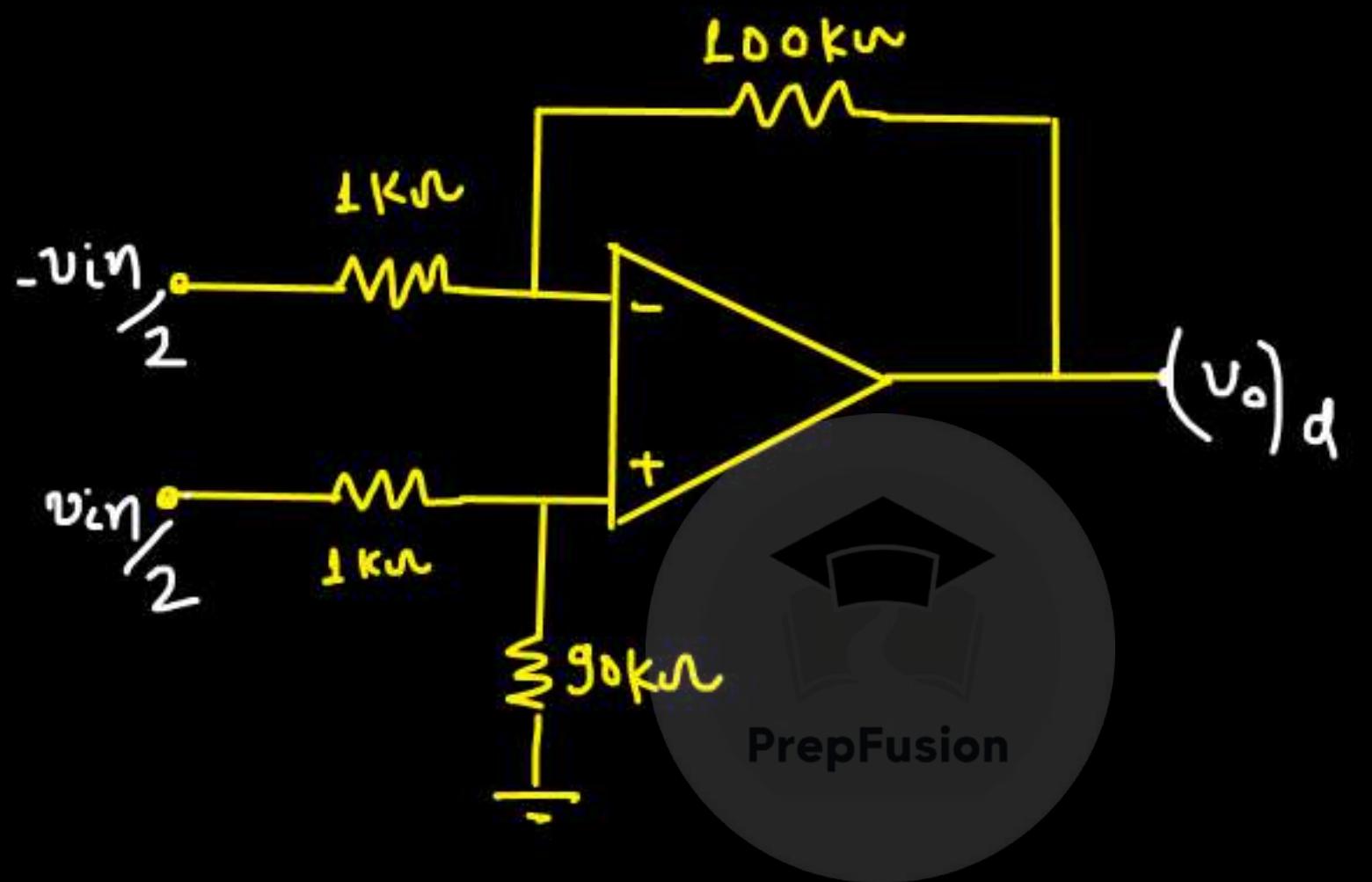


$$(v_o)_d = \frac{g_o}{g_i} \times \frac{v_{in}}{2} \times \left[1 + \frac{100}{1} \right] + \left(-\frac{100}{1} \right) \left(-\frac{v_{in}}{2} \right)$$

$$(v_o)_d = \left[\frac{g_o}{g_i} \times 101 + 100 \right] \frac{v_{in}}{2}$$

$$(\alpha_v)_d = \frac{(v_o)_d}{v_{in}} = 99.94 \%$$

Common Mode Gain:-

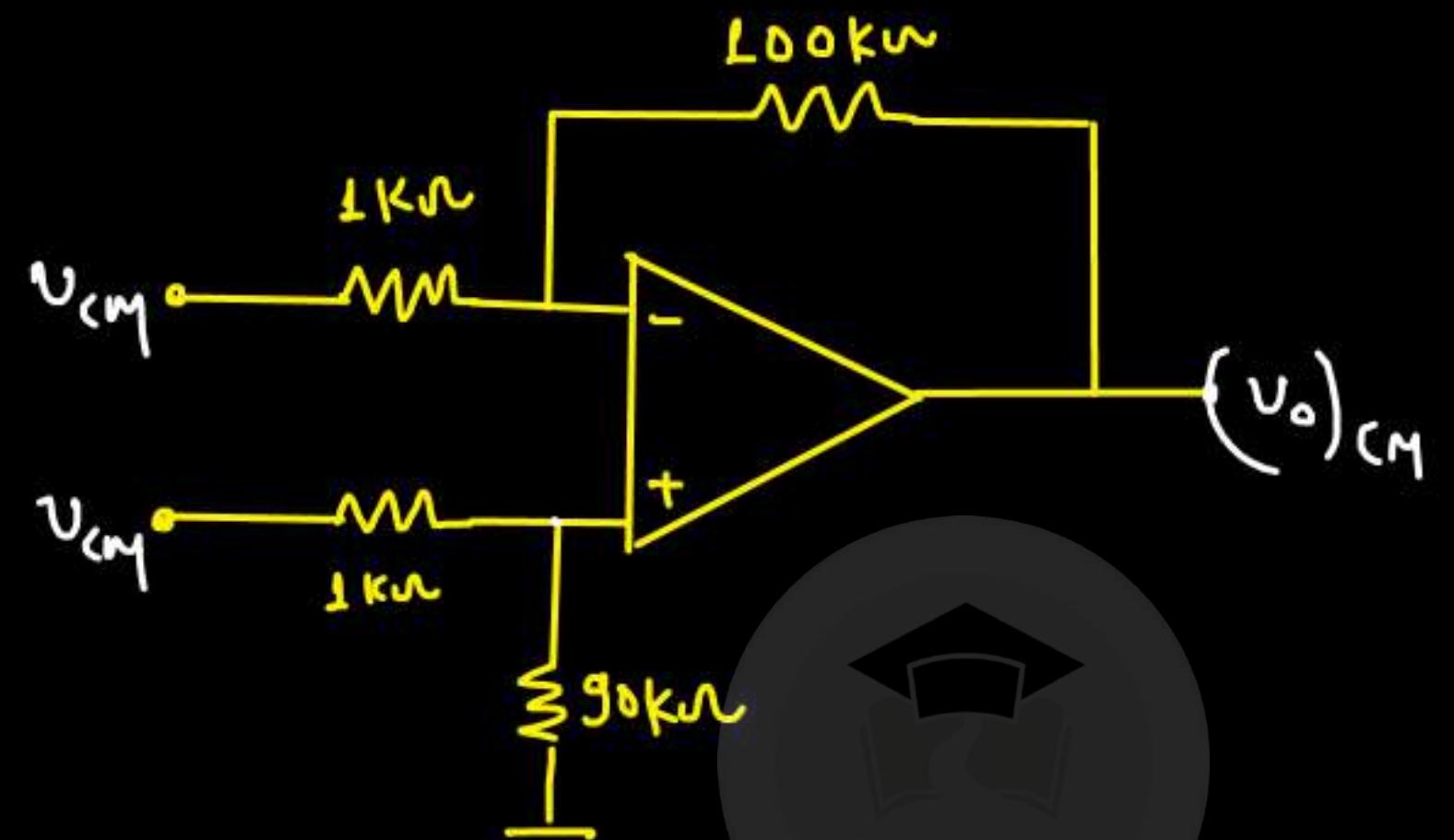

$$(v_o)_{CM} = \frac{g_o}{g_i} \times (1 + 100) v_{CM} + (-100) v_{CM}$$

$$(v_o)_{CM} = -0.109 \times v_{CM}$$

$$(\alpha)_{CM} = (v_o)_{CM} / v_{CM} = -0.109$$

$$\alpha_{CM} = -0.109$$

$$CMRR = \left| \frac{\Delta V}{\Delta C} \right| = \left| \frac{99.94}{-0.109} \right| = 909.45$$

$$\begin{aligned}
 &= 20 \log_{10} 909.45 \\
 &= 59.17 \text{ dB}
 \end{aligned}$$






⑤ Slew Rate:-

Max^m rate of change of o/p voltage.

Let slew rate = $5V/\mu s$

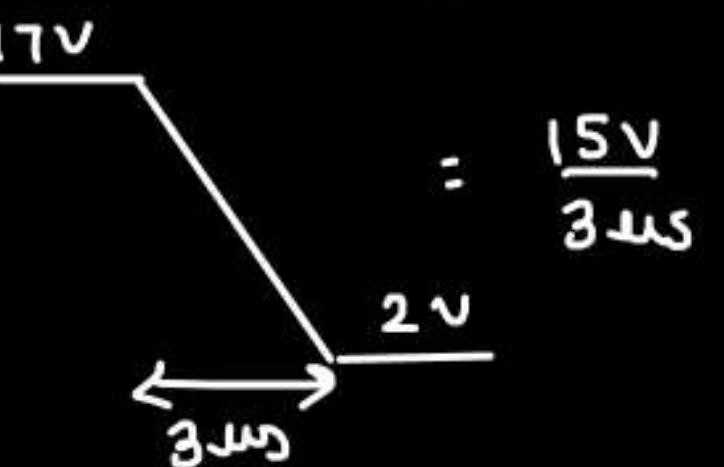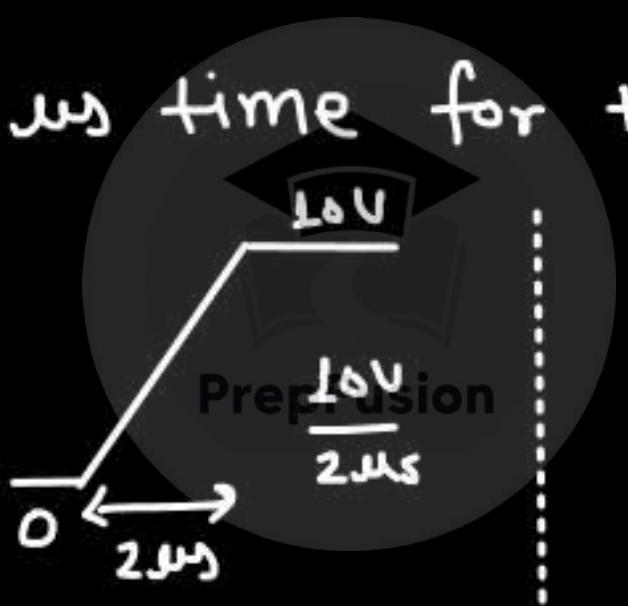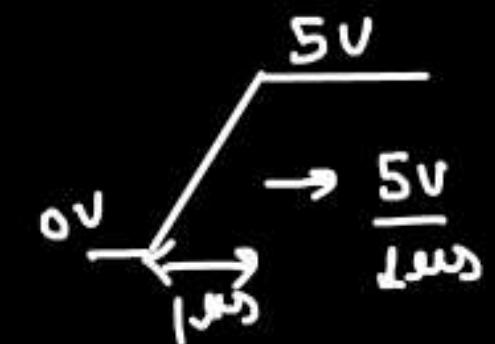
⇒ It would take 1μs time for the o/p to gain or lose 5V.



Generally, Slew Rate is defined as:-

$$S.R. = \frac{dV_o}{dt}$$

for op-amp SR unit $\rightarrow V/\mu s$

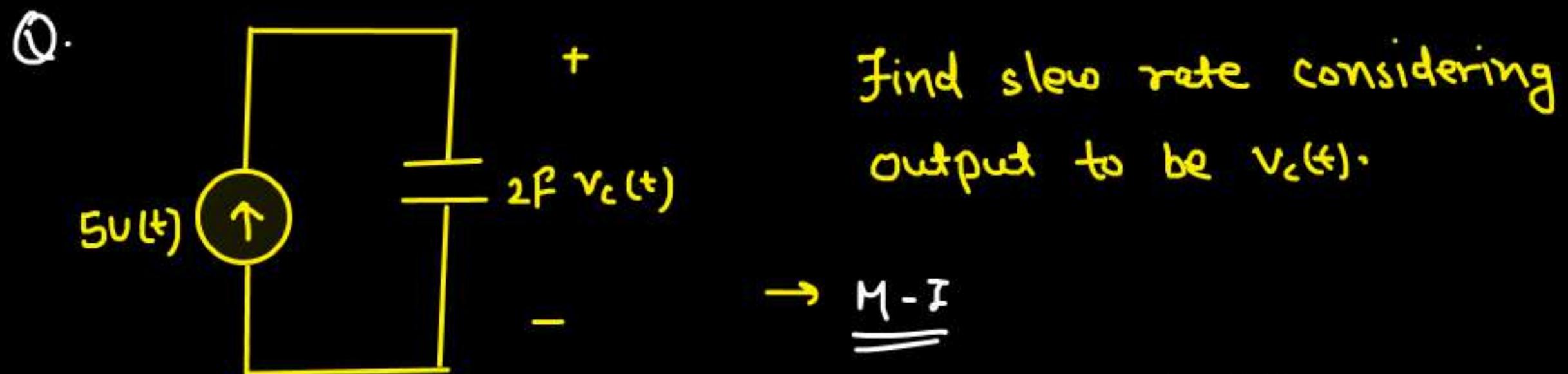

M-II

$$v_c(t) = \frac{1}{C} \int_0^t I(\tau) \cdot d\tau$$

$$= \frac{1}{2} 5t U(t)$$

$$v_c(t) = 2.5t U(t)$$


$$SR = 2.5V/\text{sec.}$$

$$S.R. = \frac{dv_c(t)}{dt} = ?$$


$$I(t) = C \frac{dv_c(t)}{dt}$$

$$\Rightarrow \frac{dv_c(t)}{dt} = \frac{I(t)}{C} = \frac{5U(t)}{C}$$

$$SR = \frac{5}{2} = 2.5V/\text{sec.}$$

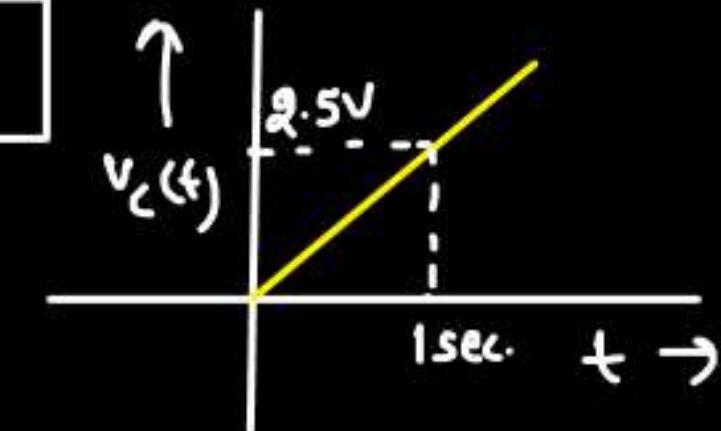

Q.

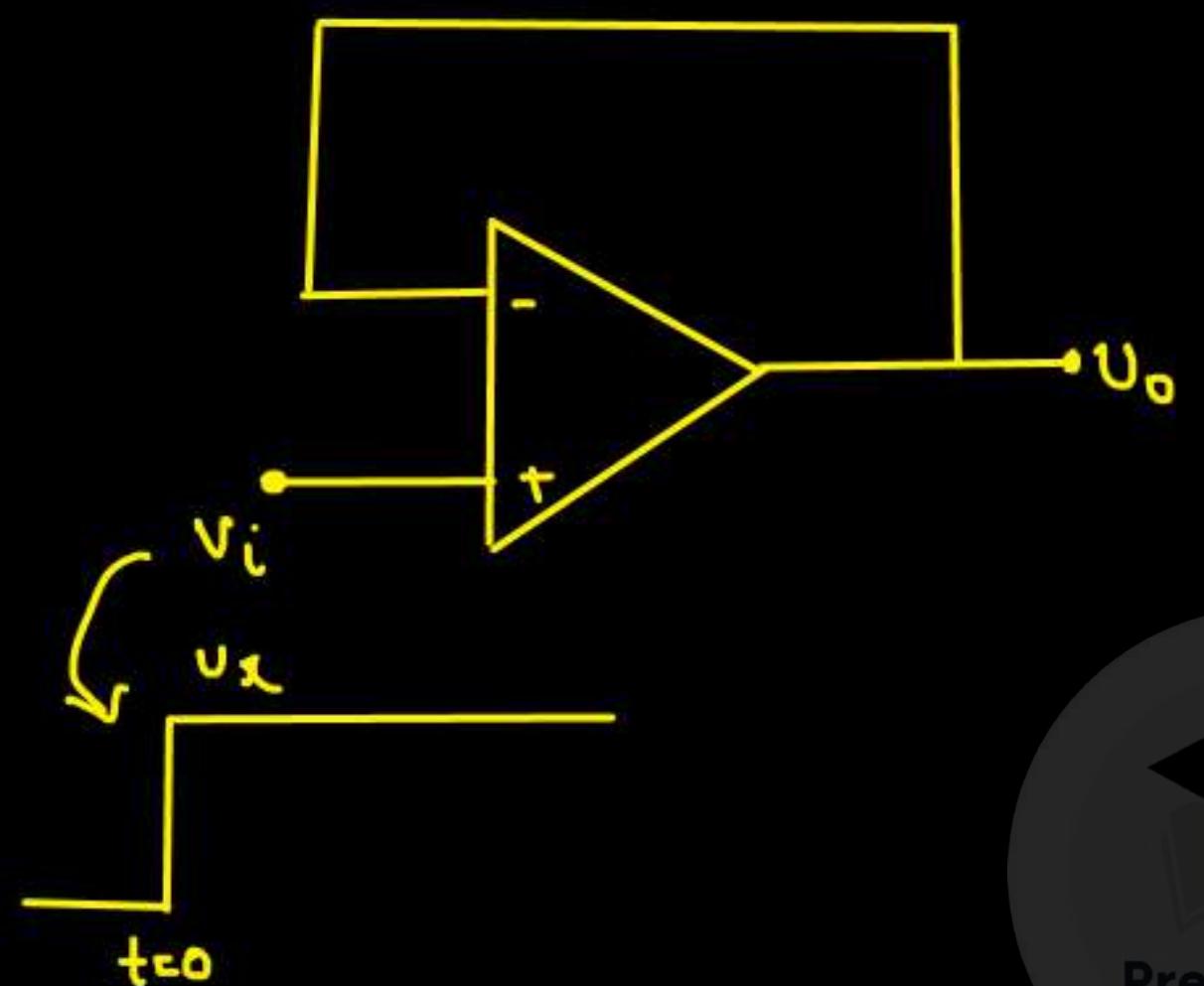


$$S.R. = \infty \text{V}/\mu\text{s}$$

$$= \frac{V}{0\mu\text{s}}$$

(a)




(b)

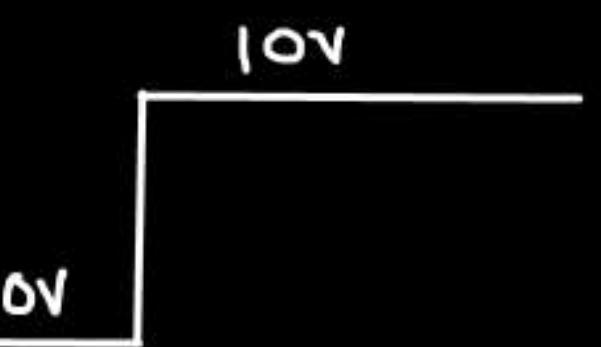

Take slew rate = ∞ [ideal op-amp]

Draw V_o for (a) $V_x = 5V$ (b) $V_x = 10V$


Q.

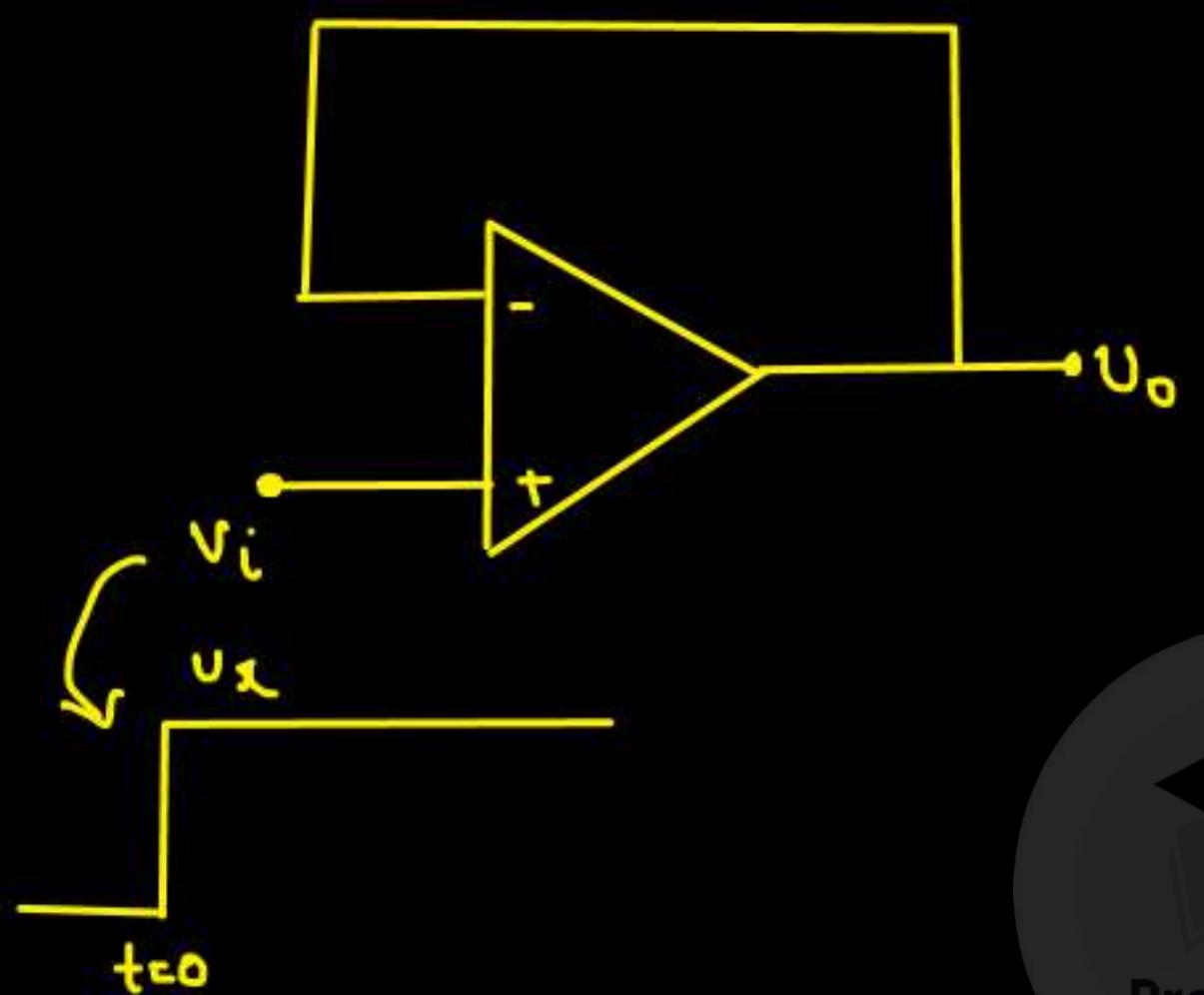

$$S.R. = 0.5V/\mu s$$

$$V_o = V_i$$


(a)

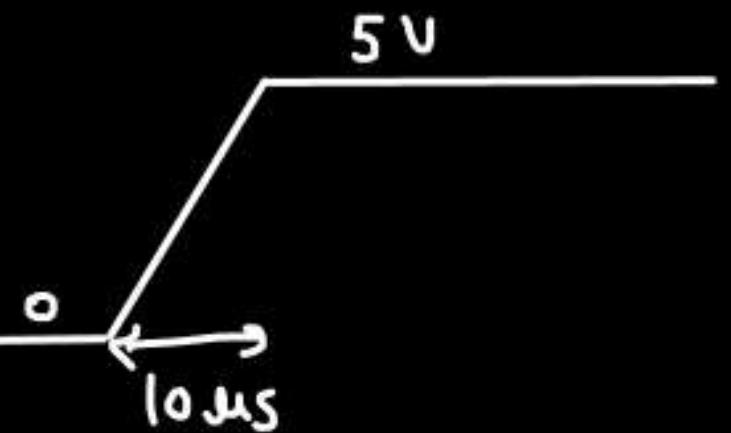


PrepFusion (b)

Take slew rate = $0.5V/\mu s$

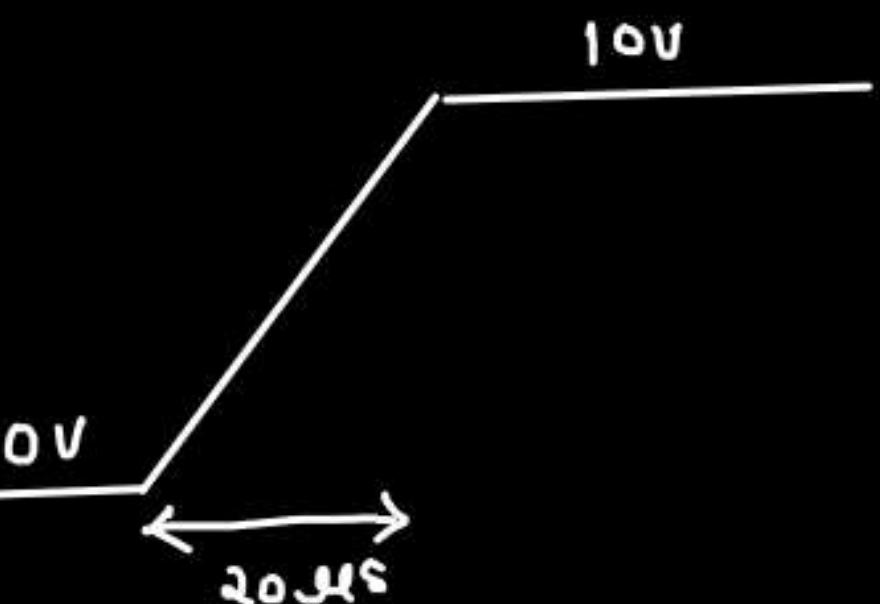Draw V_o for (a) $V_x = 5V$ (b) $V_x = 10V$






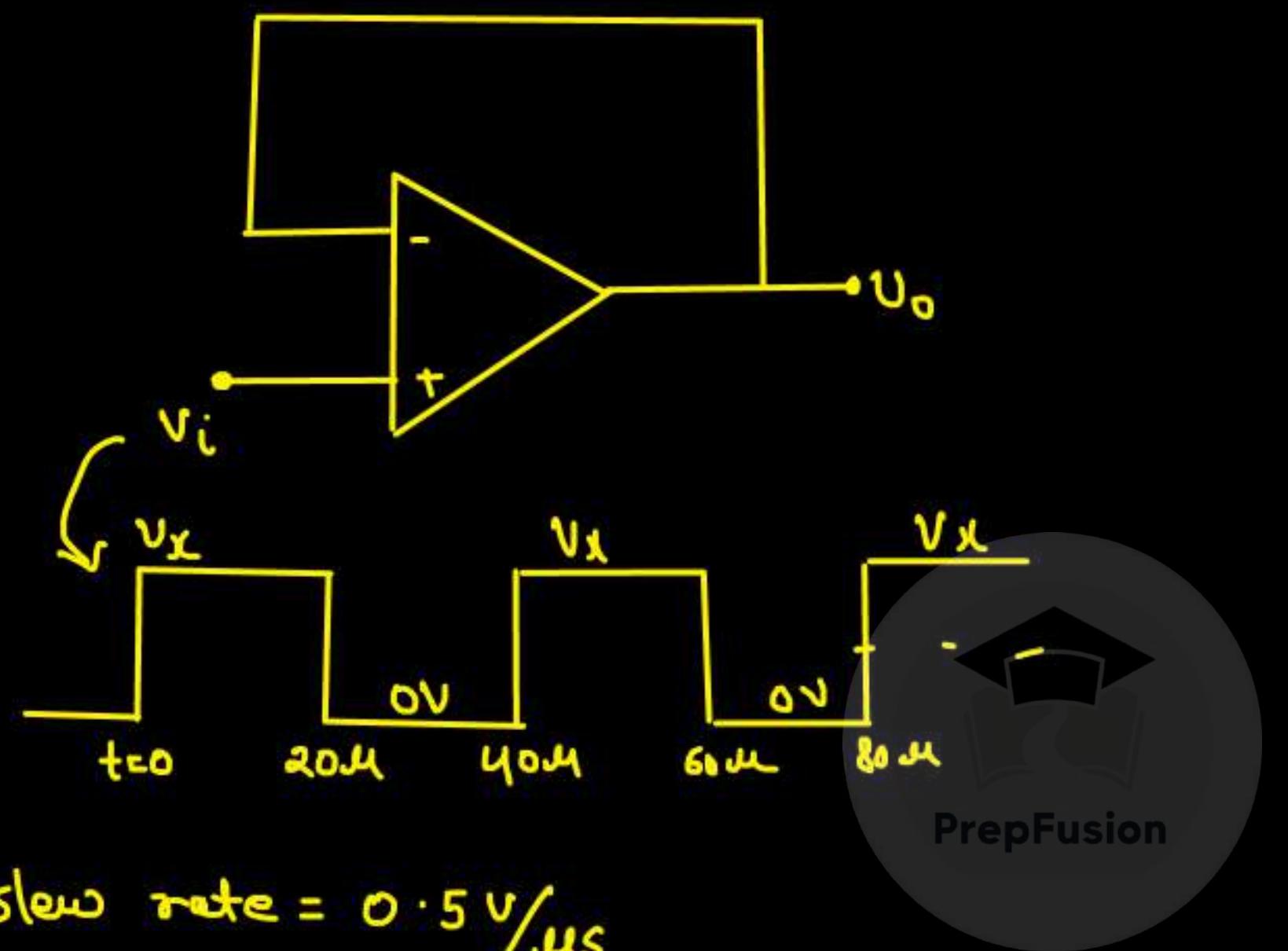

Take slew rate = $0.5 \text{ V}/\mu\text{s}$

Draw V_o for (a) $V_x = 5\text{V}$ (b) $V_x = 10\text{V}$ (c) $V_x = 20\text{V}$
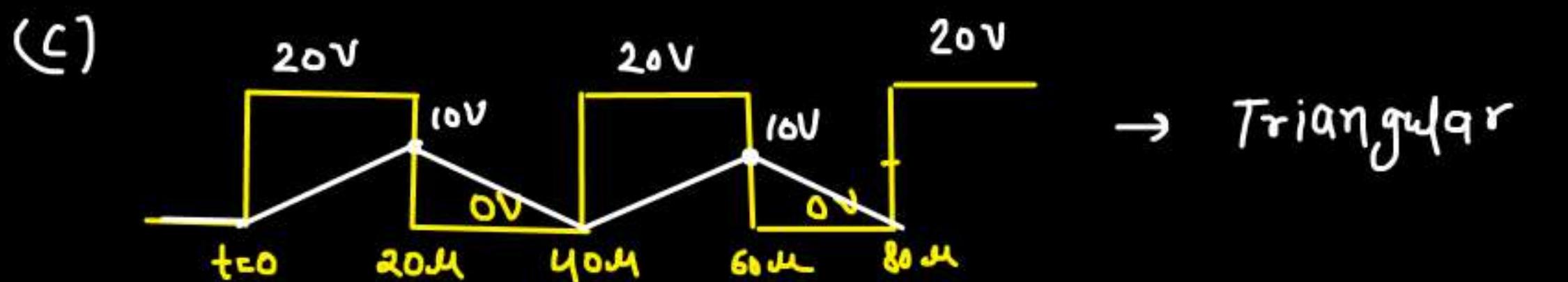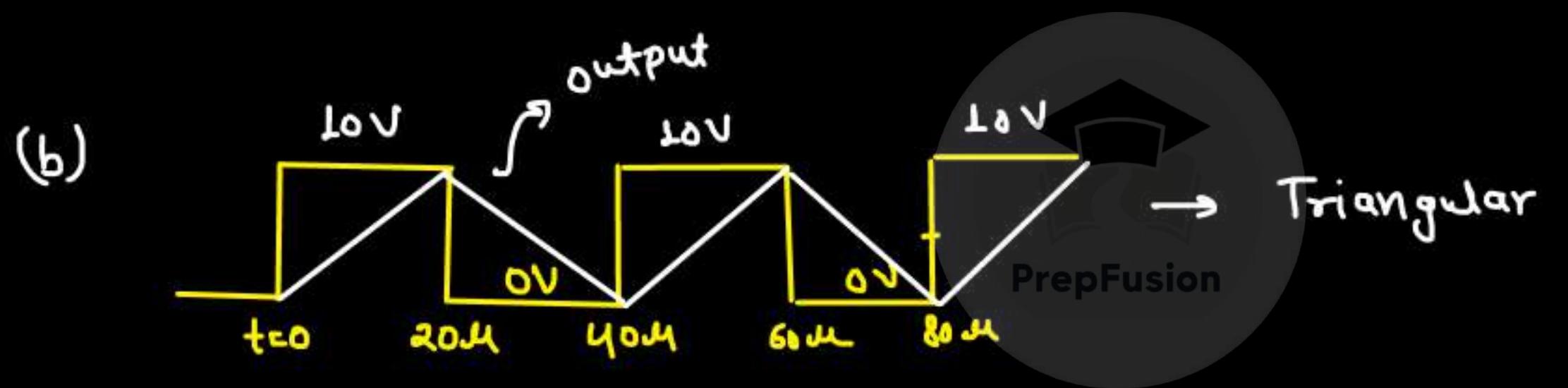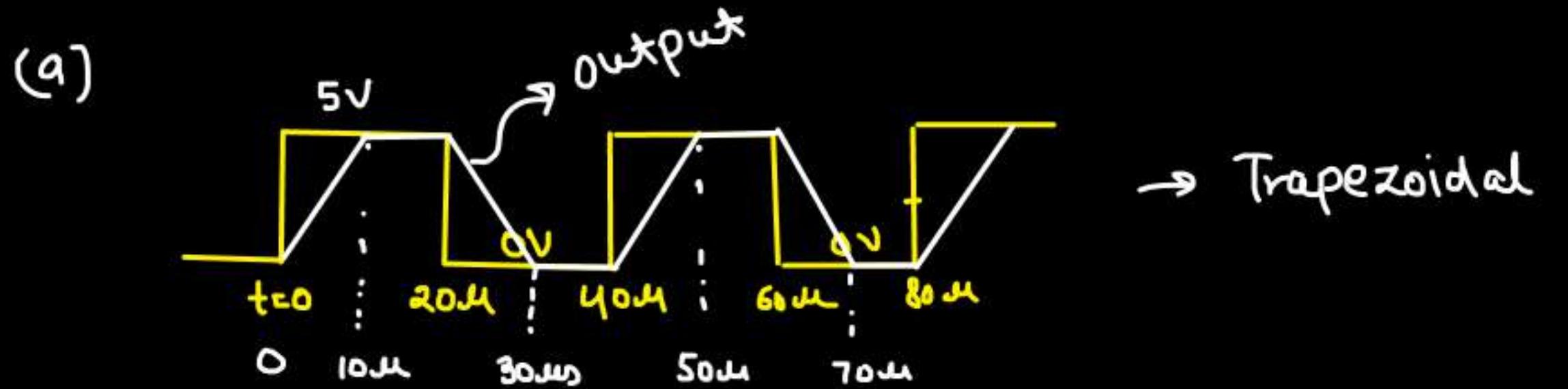
$$\begin{aligned} S.R. &= 0.5 \text{ V}/\mu\text{s} \quad \rightarrow 40\mu\text{s} = 20\text{V} \\ 1\mu\text{s} &\rightarrow 0.5 \text{ V} \quad \rightarrow 10\mu\text{s} \rightarrow 5\text{V} \end{aligned}$$



$0.5V/\mu\text{sec}$.


$2V/\mu\text{sec} \rightarrow 10\mu\text{s}$

* In case of Sinusoid i/p :-

For distortionless o/p :-

$$\left| \frac{dV_o}{dt} \right|_{\max} \leq SR$$

Remember

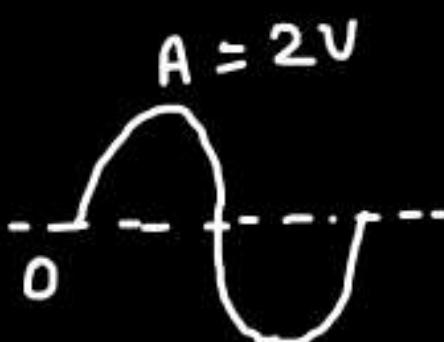

$$V_o(t) = A_m \sin \omega_m t$$

$$\frac{dV_o(t)}{dt} = A_m \omega_m \sin \omega_m t$$

$$\left| \frac{dV_o(t)}{dt} \right| = A_m \omega_m$$

$$A_m \times 2\pi f_m < SR$$

$$f_m < \frac{SR}{2\pi A_m}$$

$$(f_m)_{\max} = \frac{SR}{2\pi A_m}$$

Power Bandwidth

Q. For OP-Amp, Slew rate = $2V/\mu s$

Peak output = 12V

Maximum allowable freq. of i/p = ?

OR

Power Bandwidth = ?



$$SR = 2V/\mu \text{sec.}$$

$$\frac{dV_o}{dt} = A_m \omega_m \sin \omega t$$

$$\left| \frac{dV_o}{dt} \right|_{\max} = A_m \times 2\pi f_m \\ = 12 \times 2\pi f_m$$

$$12 \times 2\pi f_m < 2V/\mu s$$

$$(f_m)_{\max} = \frac{2 \times 10^6}{12 \times 2\pi}$$

$$(f_m)_{\max} = 26.52 \text{ KHz}$$

Q. OP-AMP SR = 5V/ μ s

Find out largest sine wave output voltage possible
at a freq. of 1MHz



$$\left| \frac{dV_o}{dt} \right|_{\text{max}} \leq SR$$

$$A_m w_m \leq SR$$

$$A_m \times 2\pi \times 1 \times 10^6 \leq 5 \times 10^6 \text{ V/sec.}$$

$$A_m \leq \frac{5}{2\pi}$$

$$A_m \leq 0.79 \text{ V}$$




$$(A_m)_{\text{max}} = 0.79 \text{ V}$$

Parameter	Ideal op-amp	Practicality
① Offset Voltage	0	μV to mV
② Bias Current	0	nA to fA
③ Offset Current	0	nA to fA
④ Bandwidth	∞	1 MHz (IC-741)
⑤ CMRR	∞	100 dB
⑥ Slew rate	∞	Some V/μs



→ Integrator Using OP-Amp :-

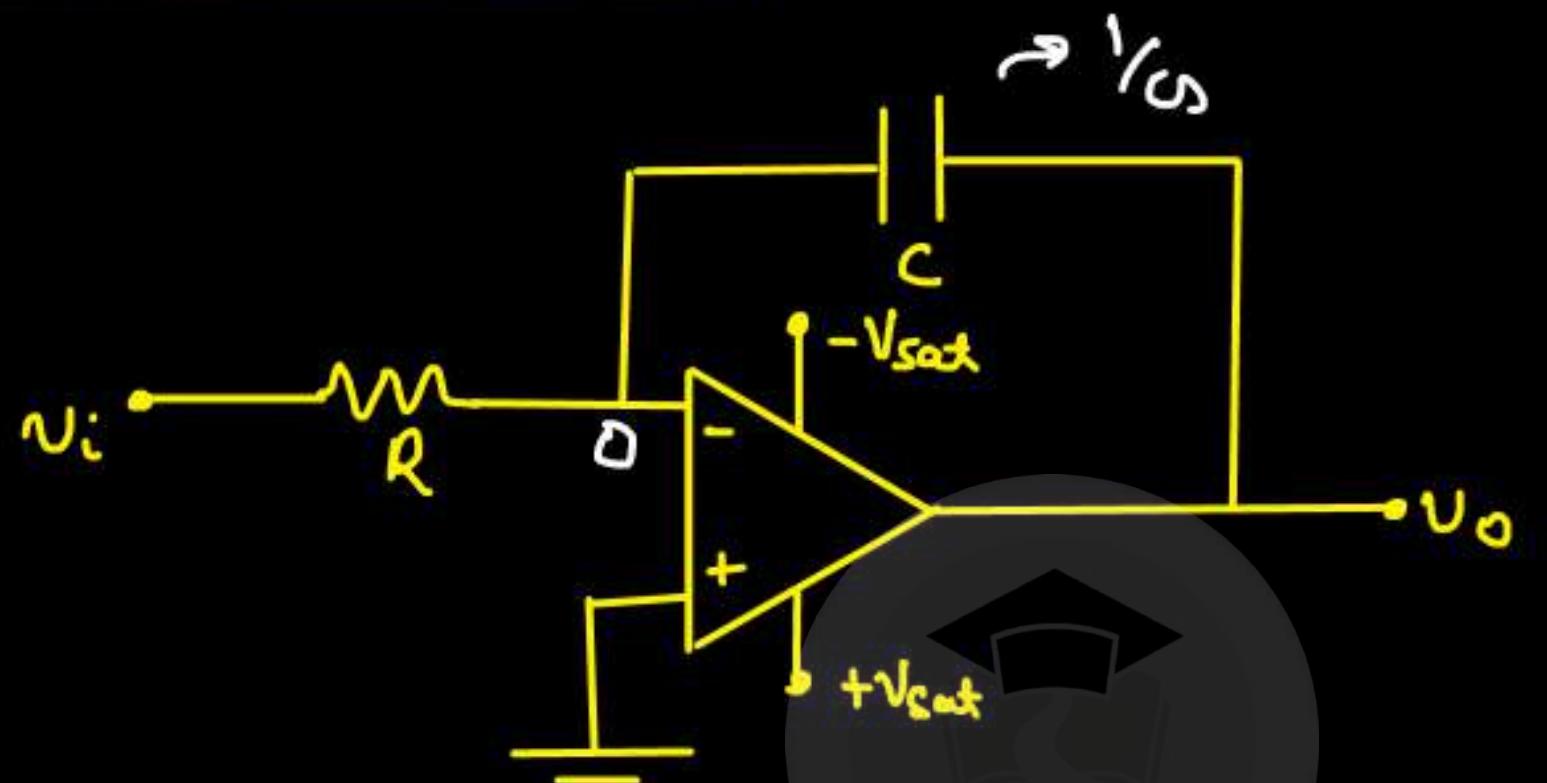


PrepFusion

$$\frac{V_o(s)}{V_i(s)} = -\frac{1}{sCR} = T(s)$$

$$V_o(s) = -\frac{1}{sRC} V_i(s) \Rightarrow$$

$$V_o(t) = -\frac{1}{RC} \int_{-\infty}^t V_i(t) \cdot dt$$

Pole @ $\omega = 0$

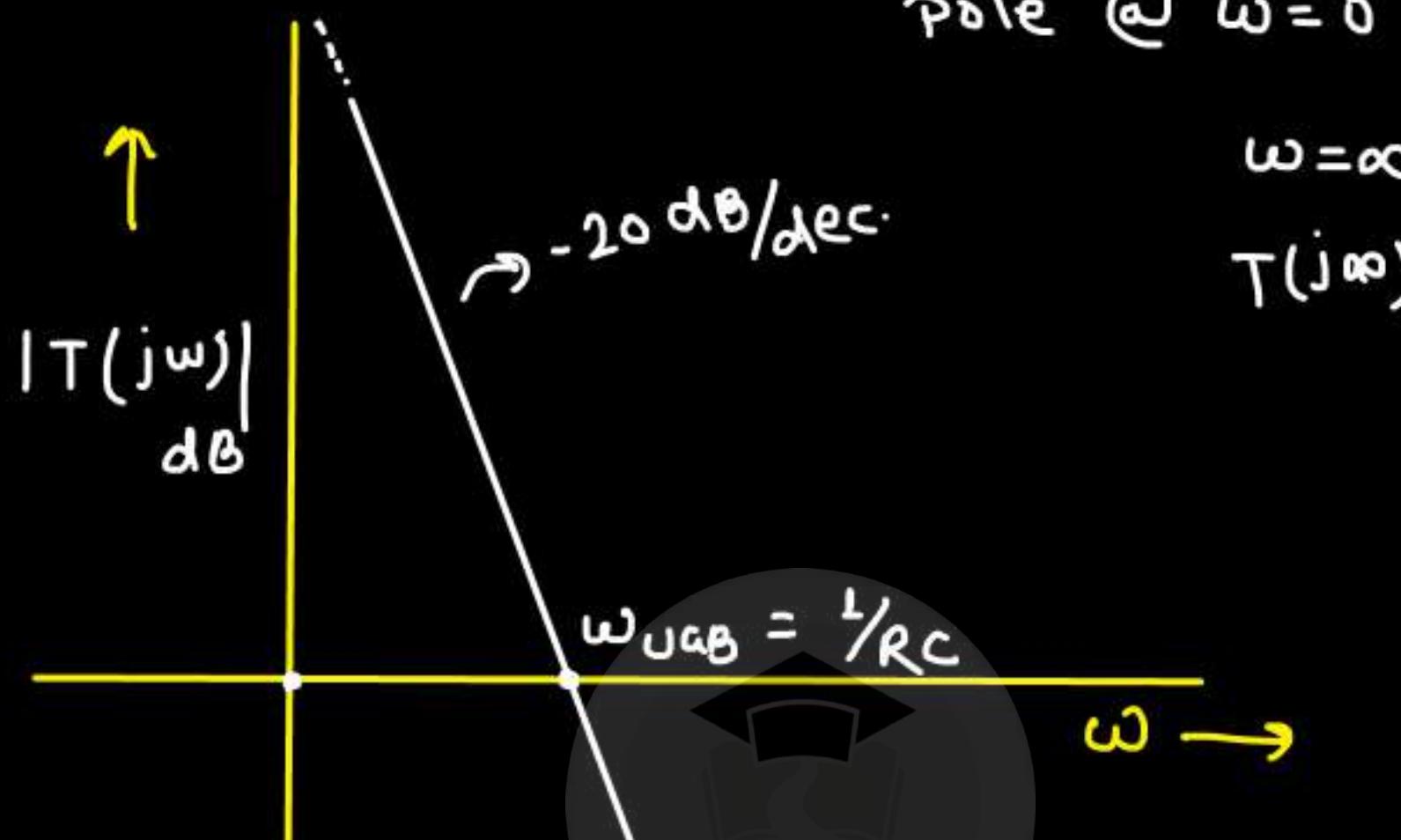

$\omega = \infty$

$$T(j\infty) = \frac{1}{\infty} = 0$$


$$= 20 \log_{10}(0)$$

$= -\infty$

Drawbacks:-


- Acts as open loop config. at low freq. (Saturated O/P).
- Very low bandwidth. The gain keeps on decreasing with increase in freq.

(c) Effect of offset:-

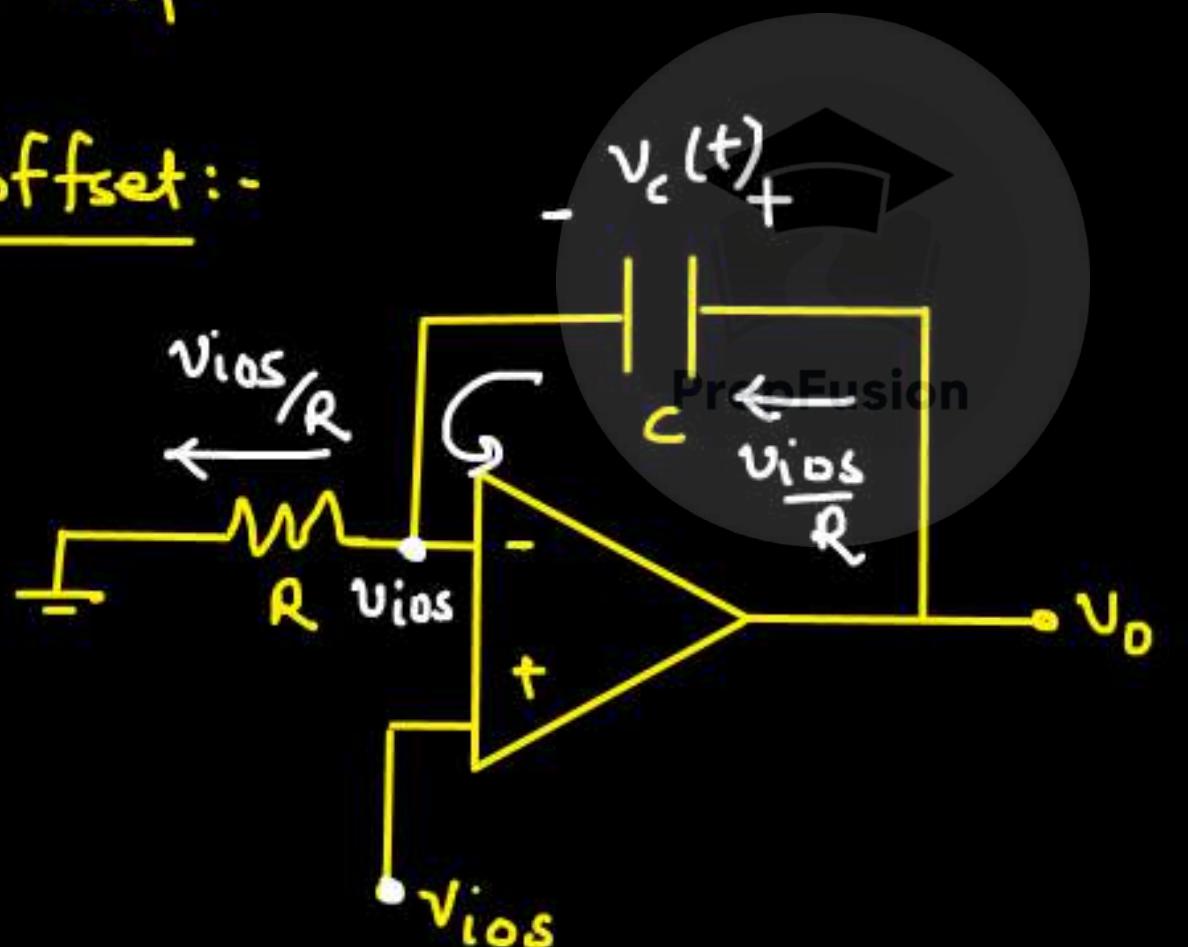

$$\begin{aligned} U_o &= V_{i0s} + V_c(t) \\ &= V_{i0s} + \frac{1}{C} \int_{-\infty}^t \frac{V_{i0s}}{R} dt \end{aligned}$$

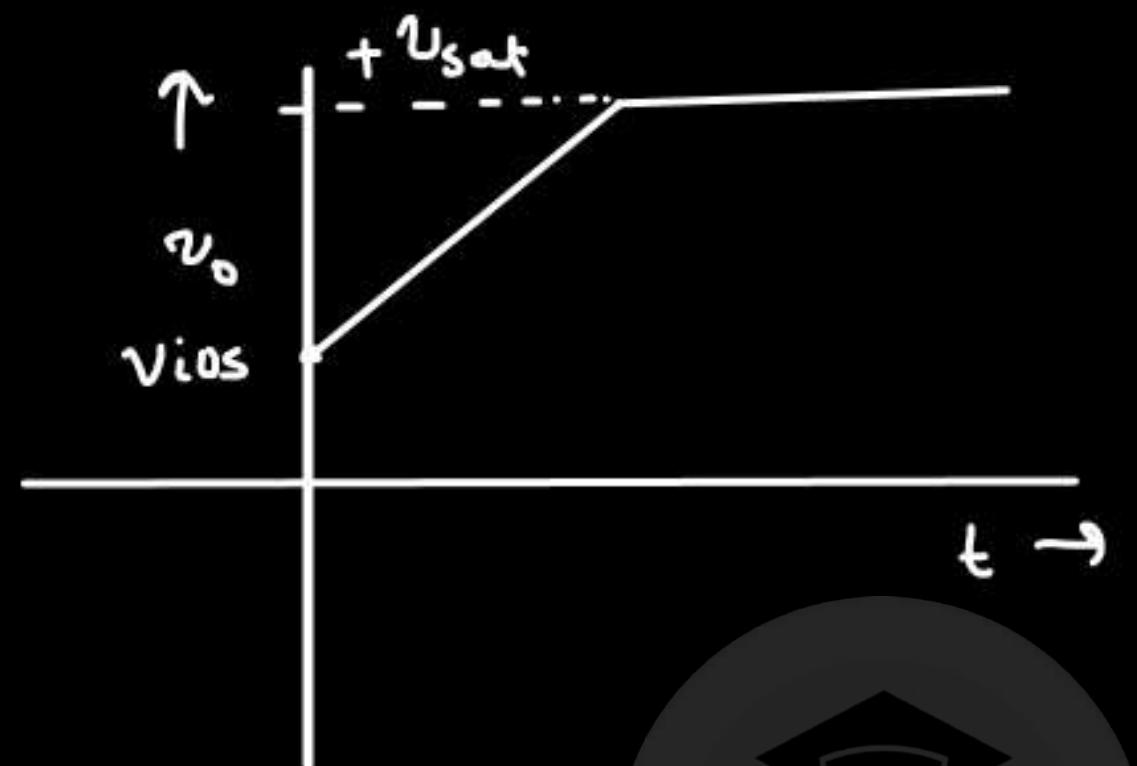
$$U_o(t) = V_{i0s} + \frac{V_{i0s}}{RC} t$$



without even applying the VP, op is saturated.


PrepFusion

Practical Integrator :-


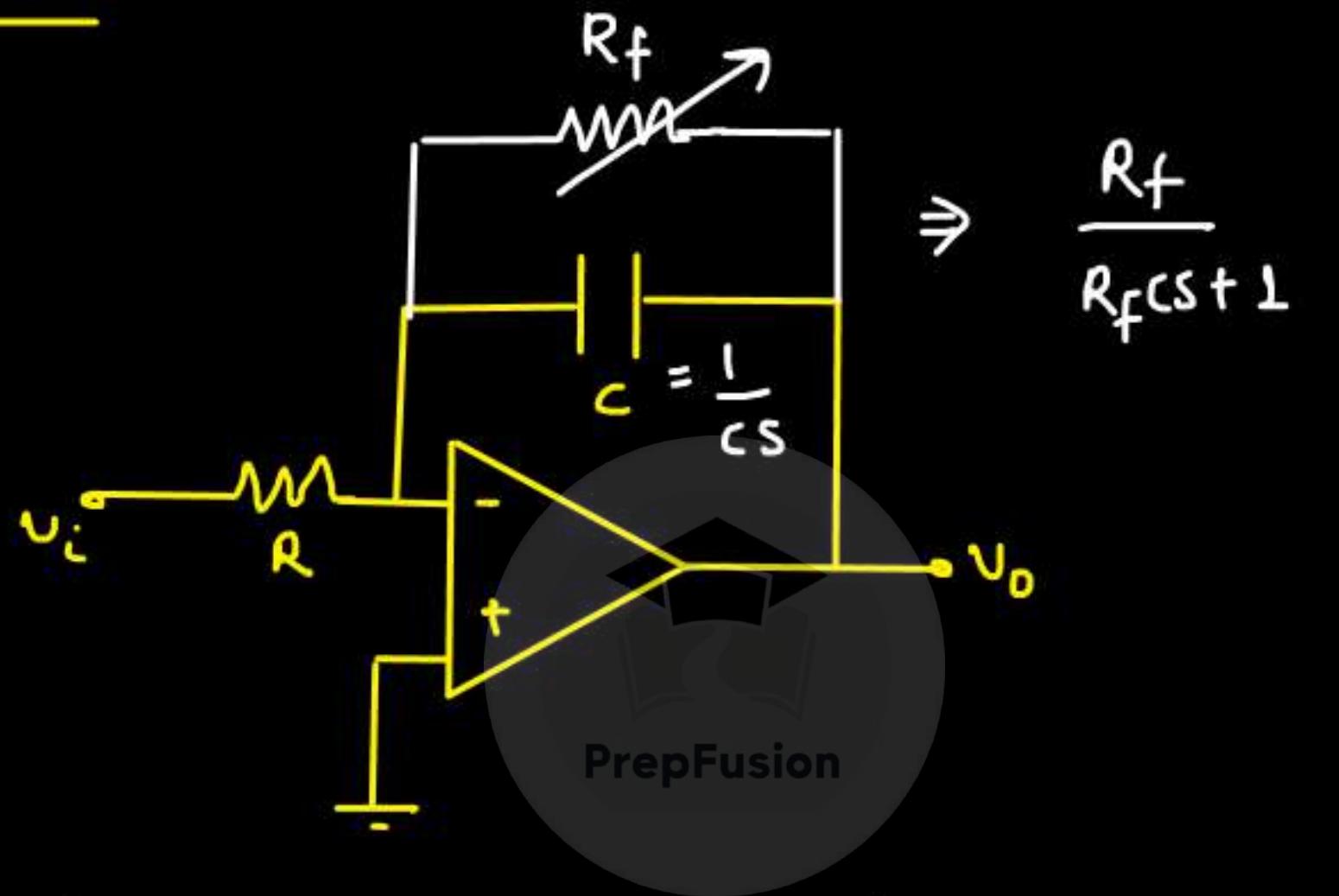


$$\frac{v_o(s)}{v_i(s)} = \frac{-R_f/R}{R_f C s + 1} = T(s)$$


$$\omega_p = \frac{1}{R_f C}$$

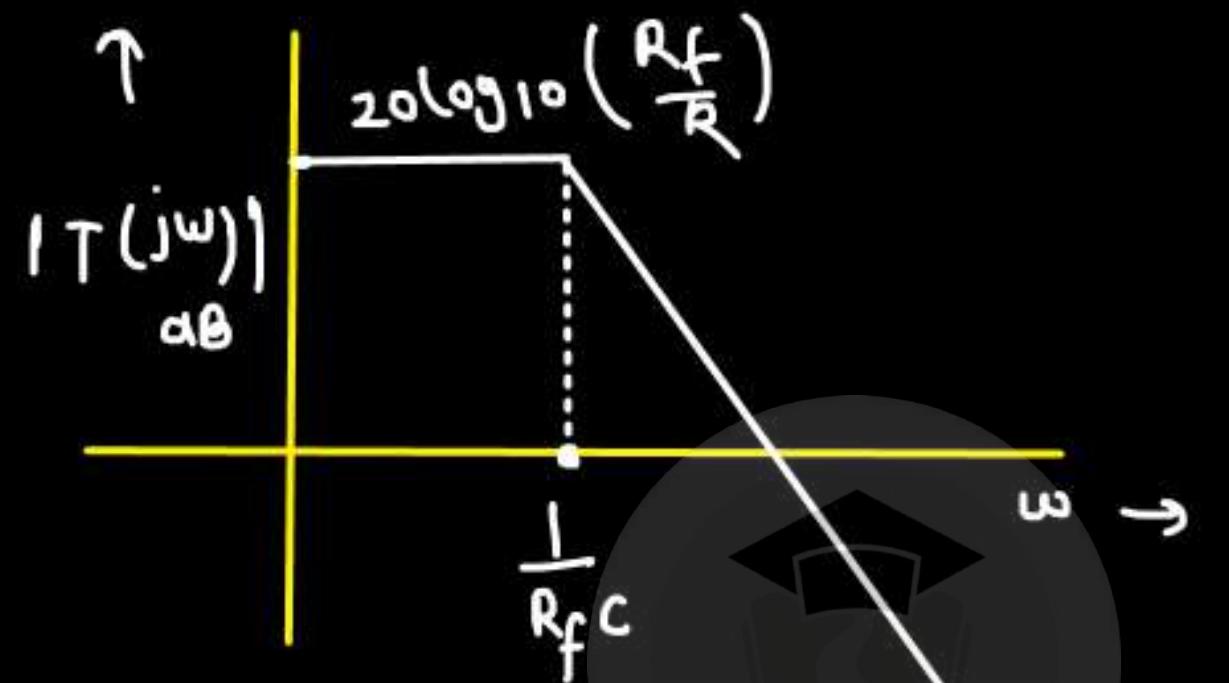

Effect of offset:-

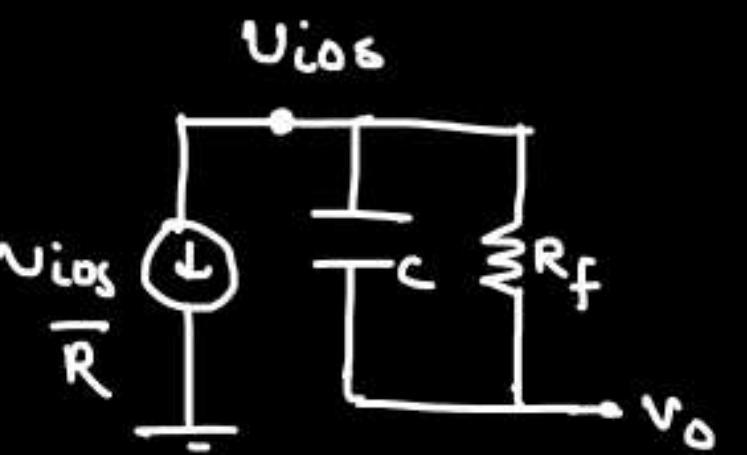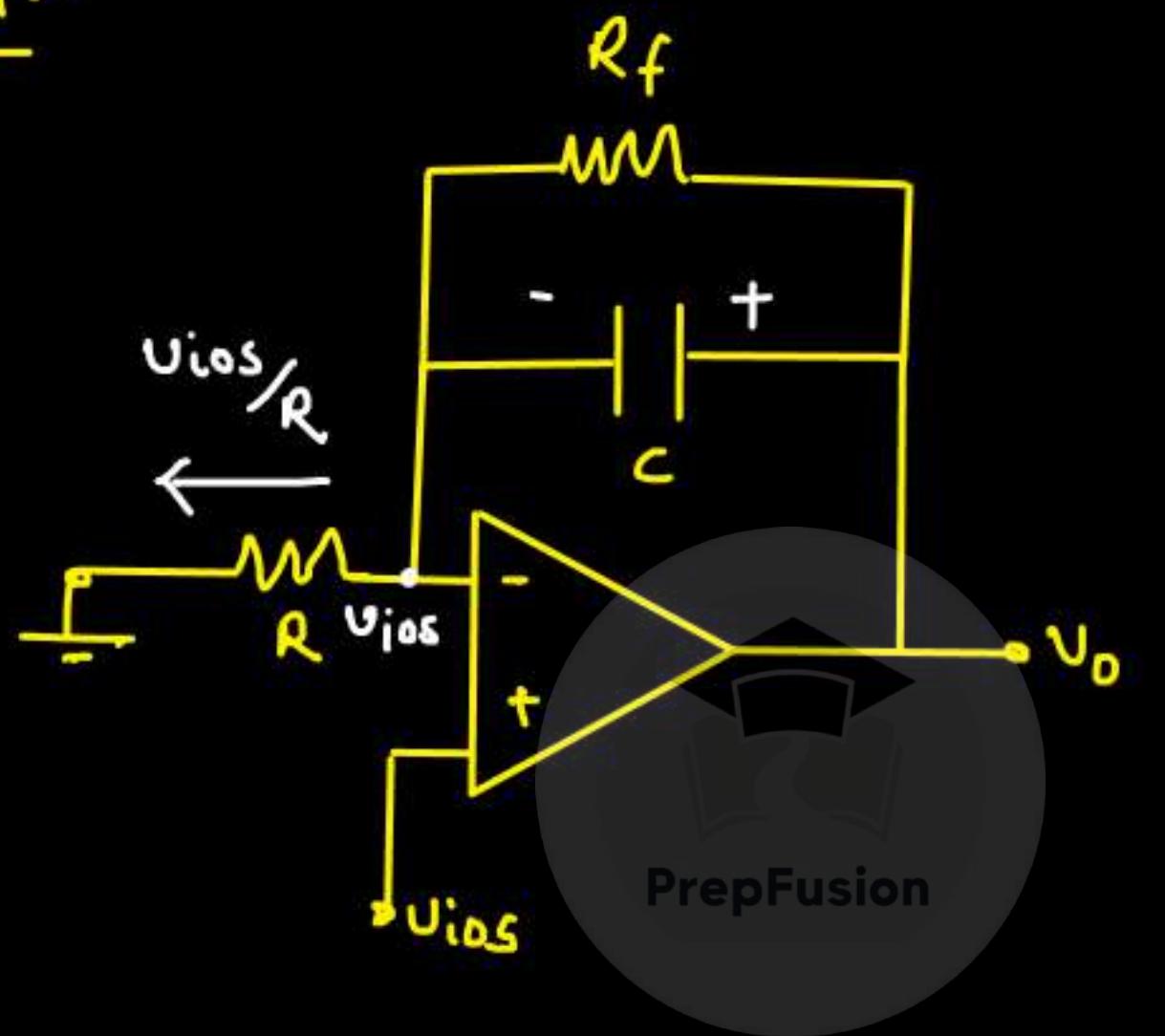


$$V_o(t=0^+) = V_{ios}$$

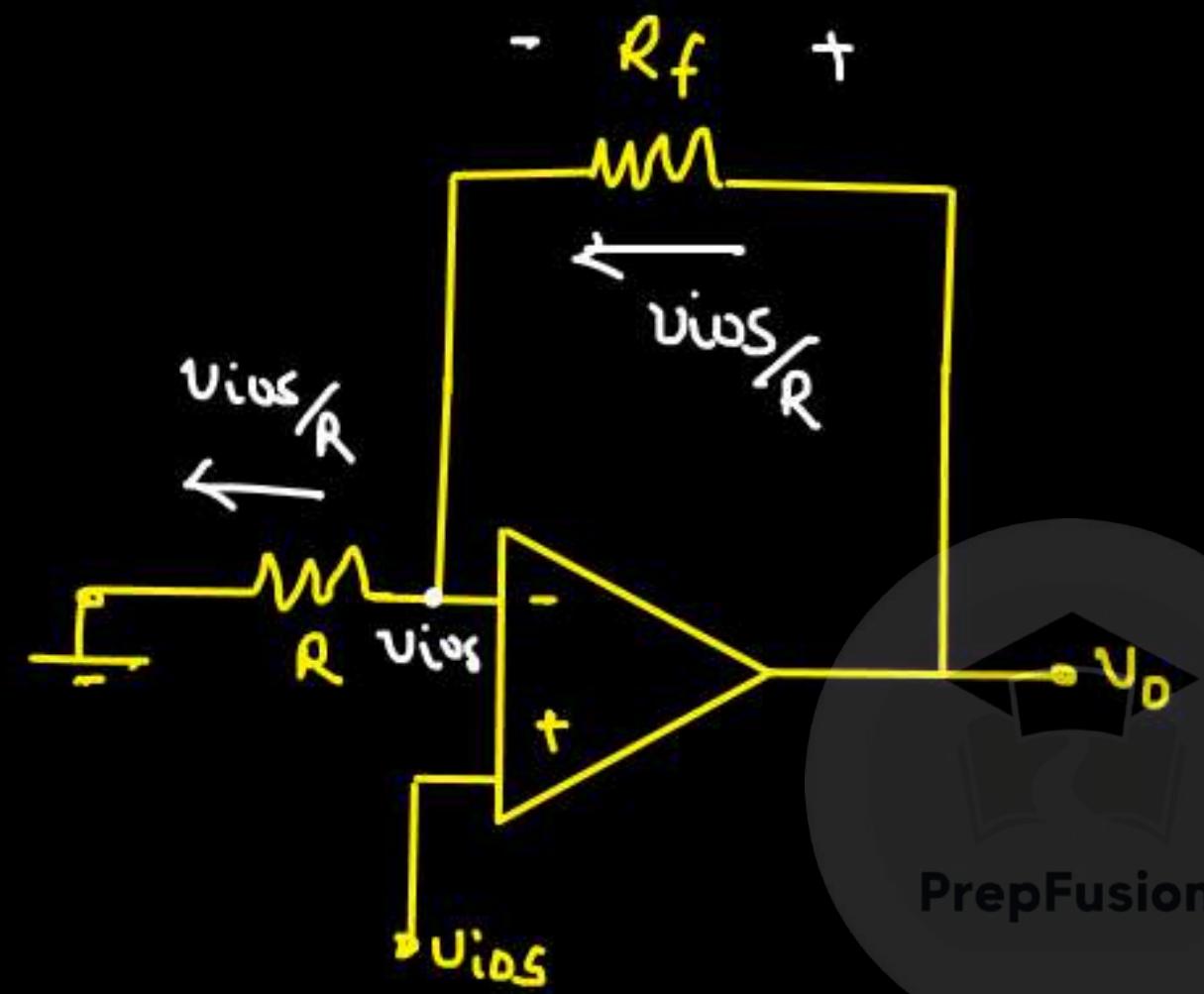


$$V_o(t=\infty) = V_{i\text{OS}} + \frac{V_{i\text{OS}}}{R} \times R_f$$
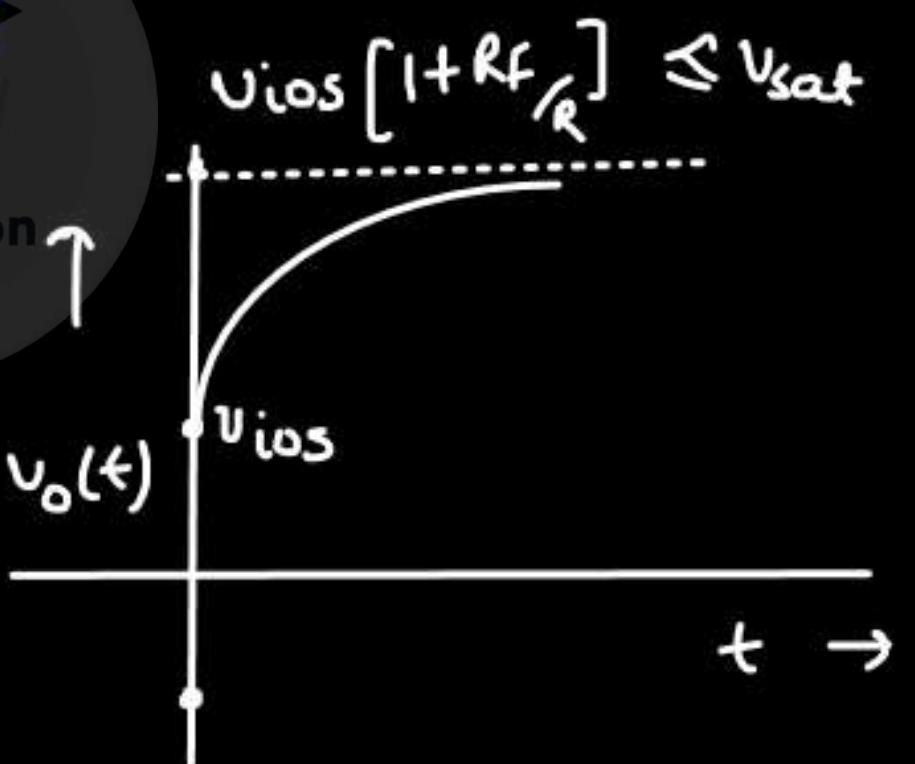
$$V_o(t=\infty) = V_{i\text{OS}} \left[1 + \frac{R_f}{R} \right]$$




★ Ideal Integrator with different inputs:-

(a)

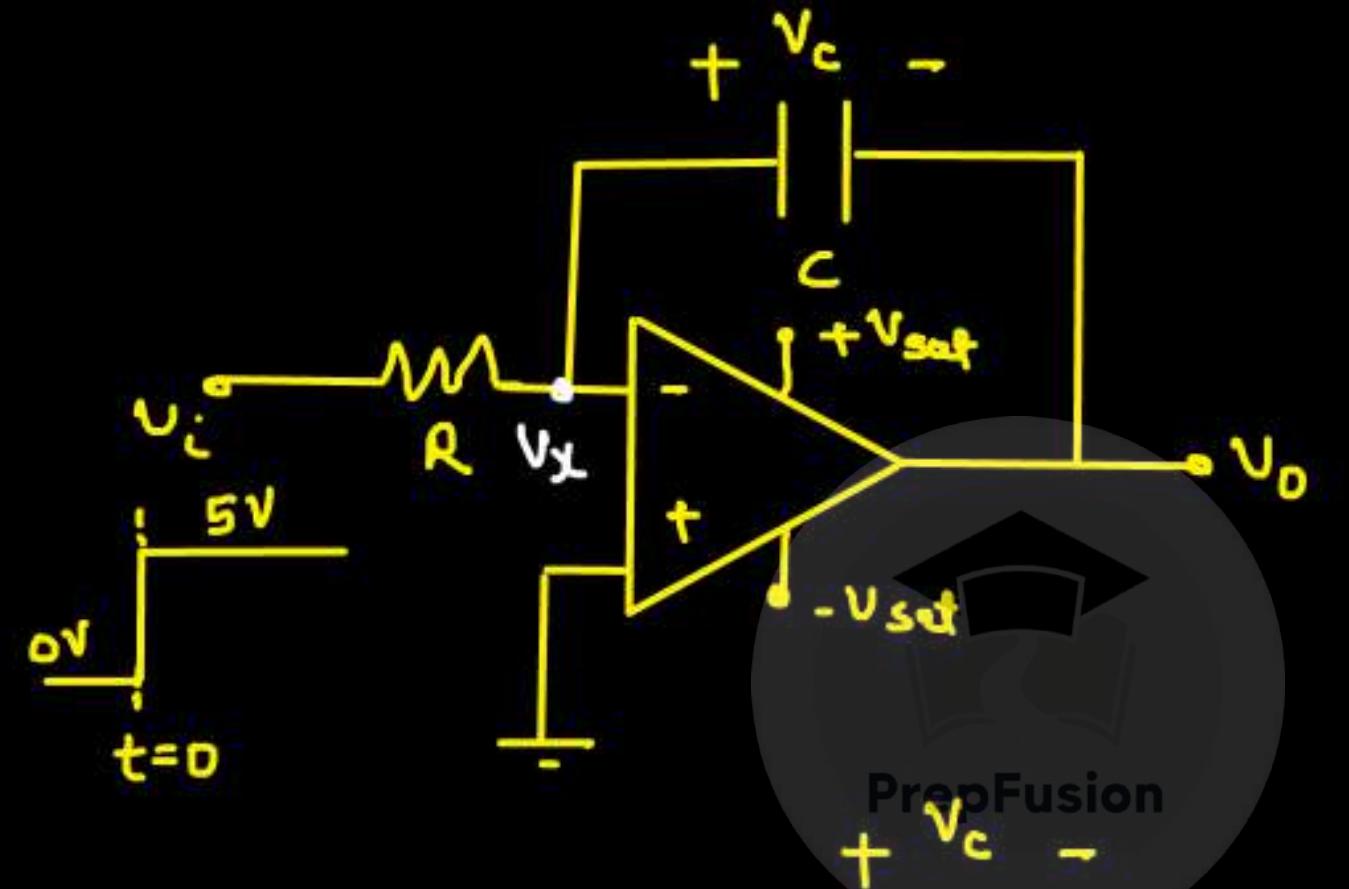

at $t = 0^+$

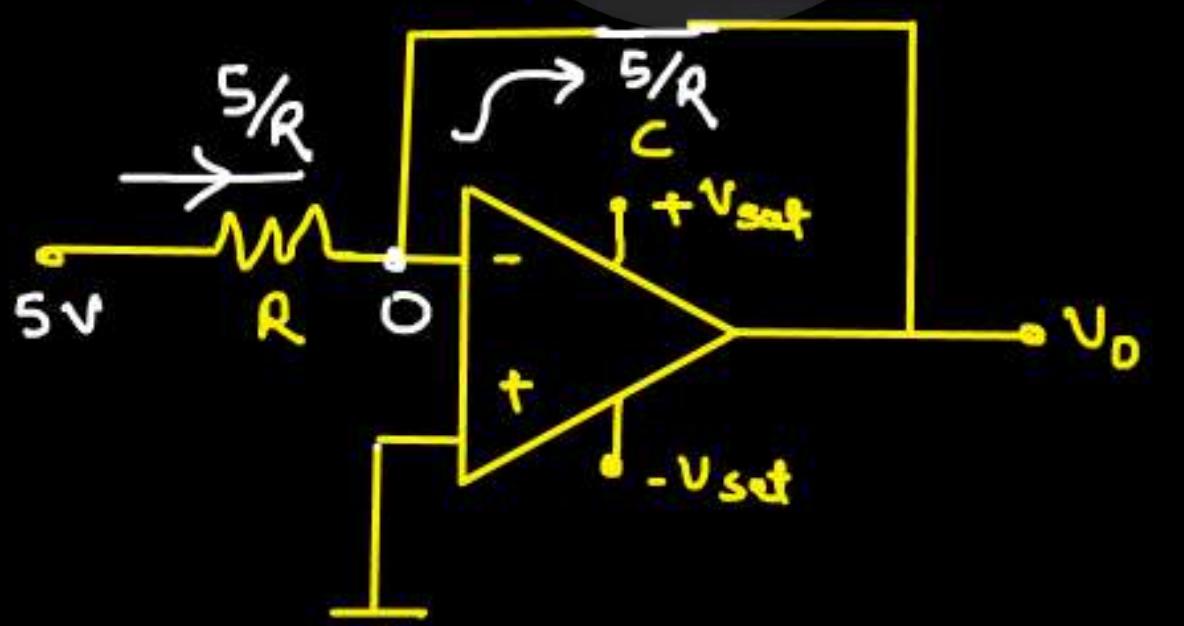


$$v_x(t=0^+) = 0$$

$$v_c(t=0^+) = 0$$

$$v_o(t=0^+) = 0$$

constant $5/R$ current is flowing through cap.

So, cap. would charge linearly

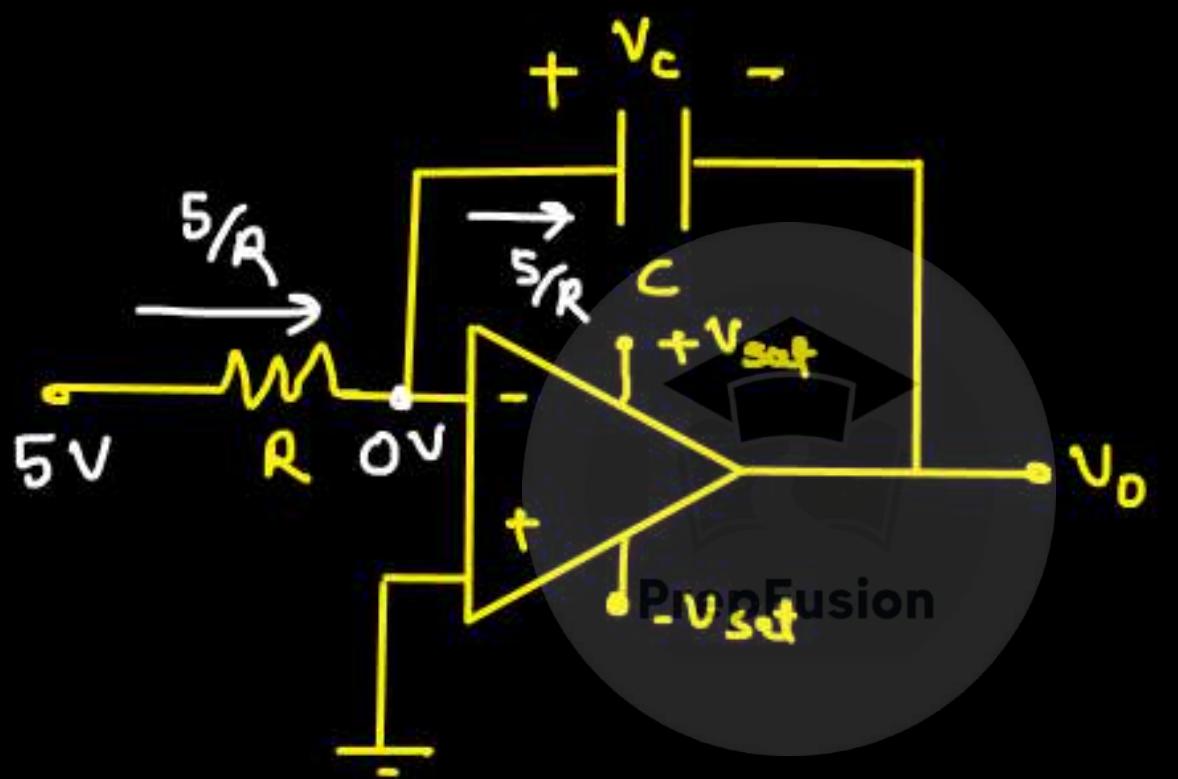




$$V_o(t) = -V_c(t)$$

$$V_c(t) = \frac{1}{C} \int_0^t \frac{5}{R} dt$$

$$V_c(t) = \frac{5t}{RC}$$


$$V_c(0) = 0$$

$$V_o(t) = -\frac{5t}{RC}$$

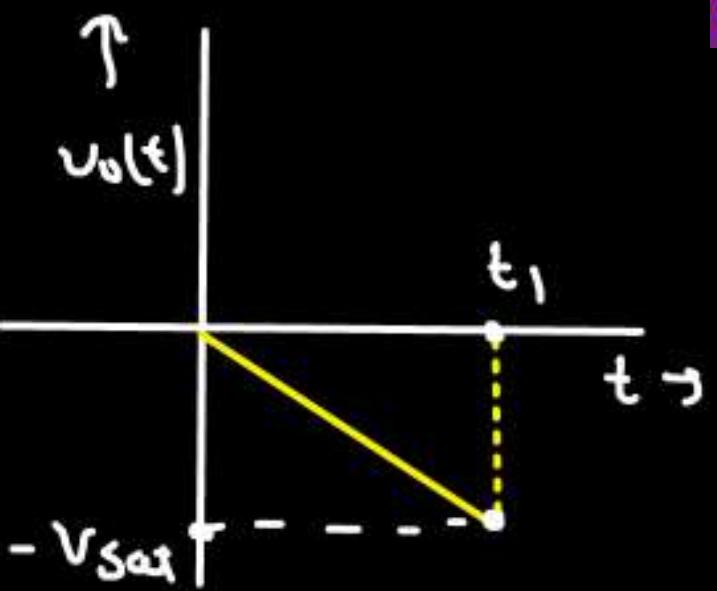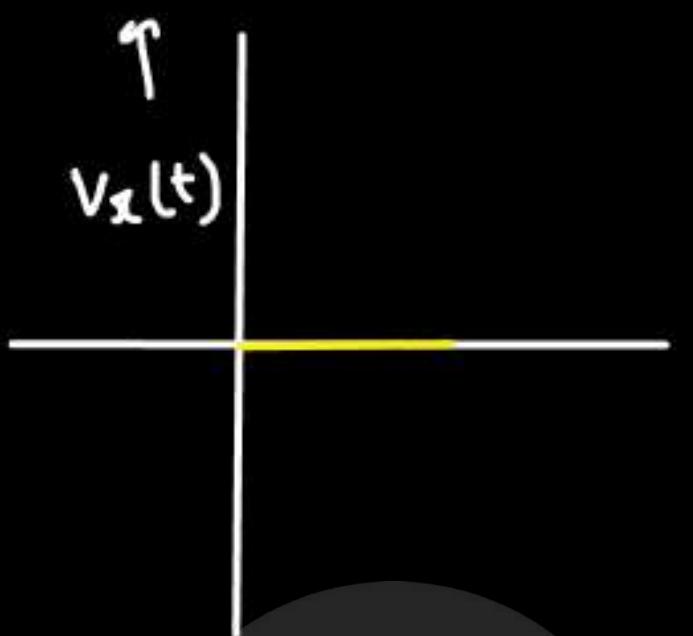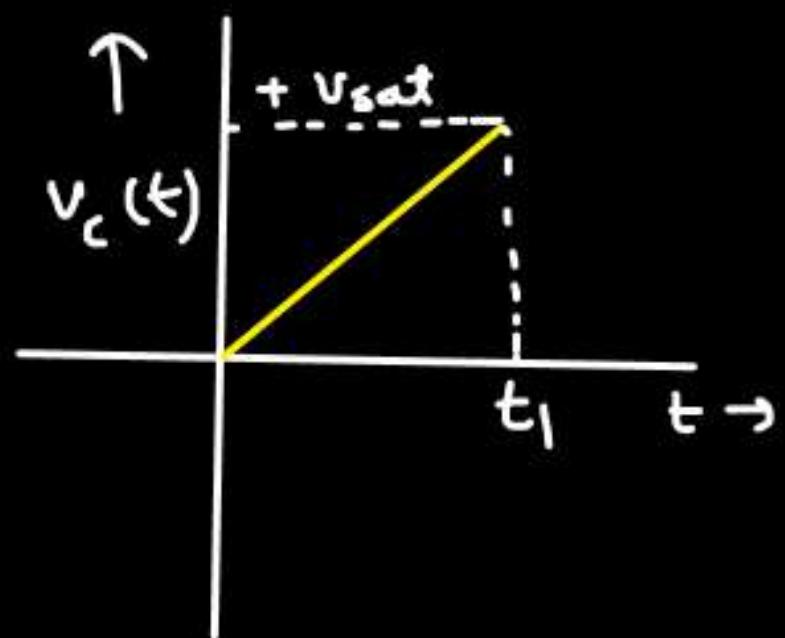


Here, $v_o(t)$ is continuously decreasing
but the minimum value it can get is $-V_{sat}$

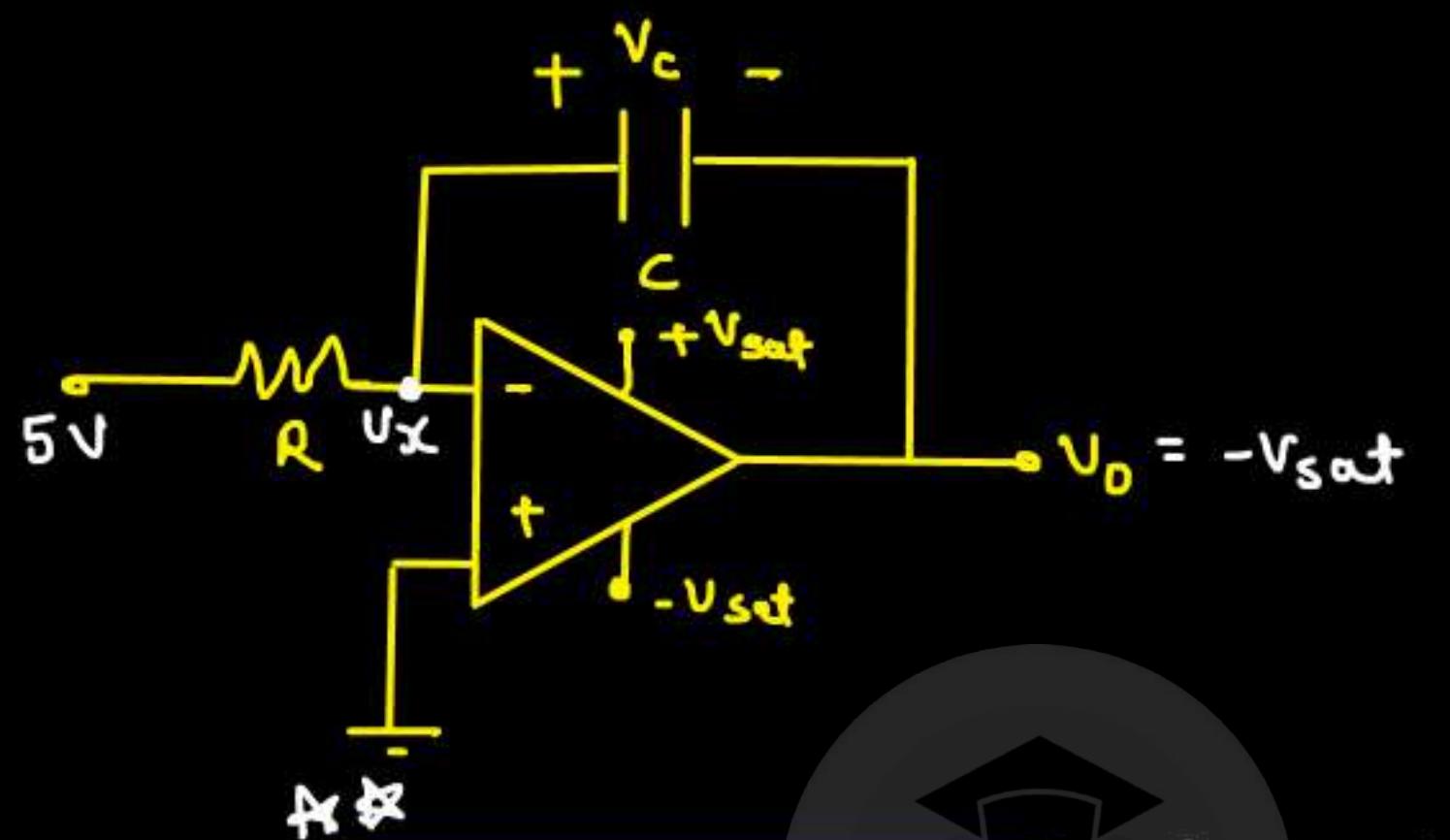at $\text{at } t = t_1 \quad v_o(t_1) = -V_{sat}$



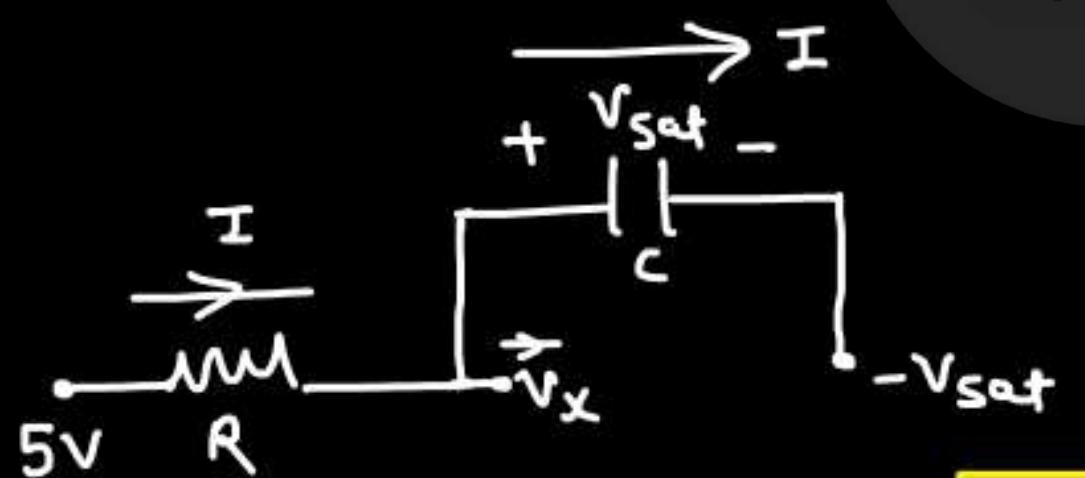
now ~~$V_x(t > t_1) \neq 0V$~~ { OpAmp is saturated \Rightarrow Virtual short
NOT valid }






$$V_o(t = t_1) = -Vsat = V_o(t = \infty)$$


$$\begin{aligned} V_c(t = t_1) &= +Vsat \\ V_c(t = \infty) &= 5 + Vsat \end{aligned}$$
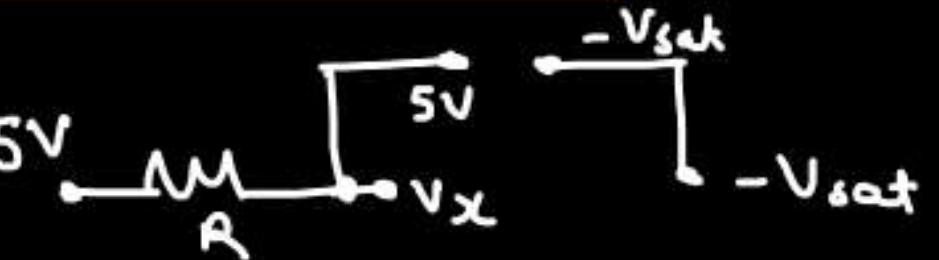
$$\begin{aligned} V_x(t = t_1) &= 0V \\ V_x(t = \infty) &= 5V \end{aligned}$$



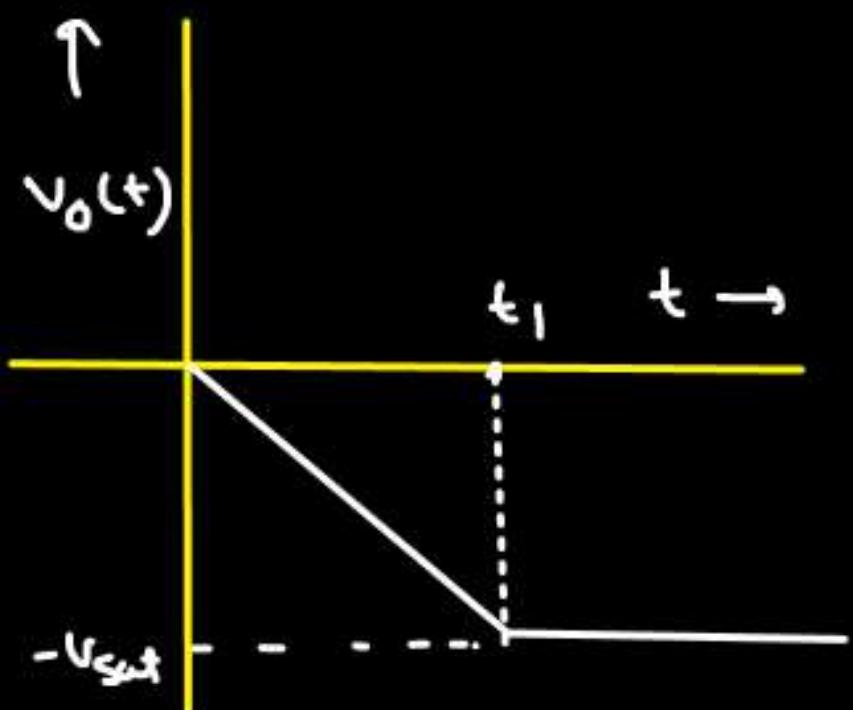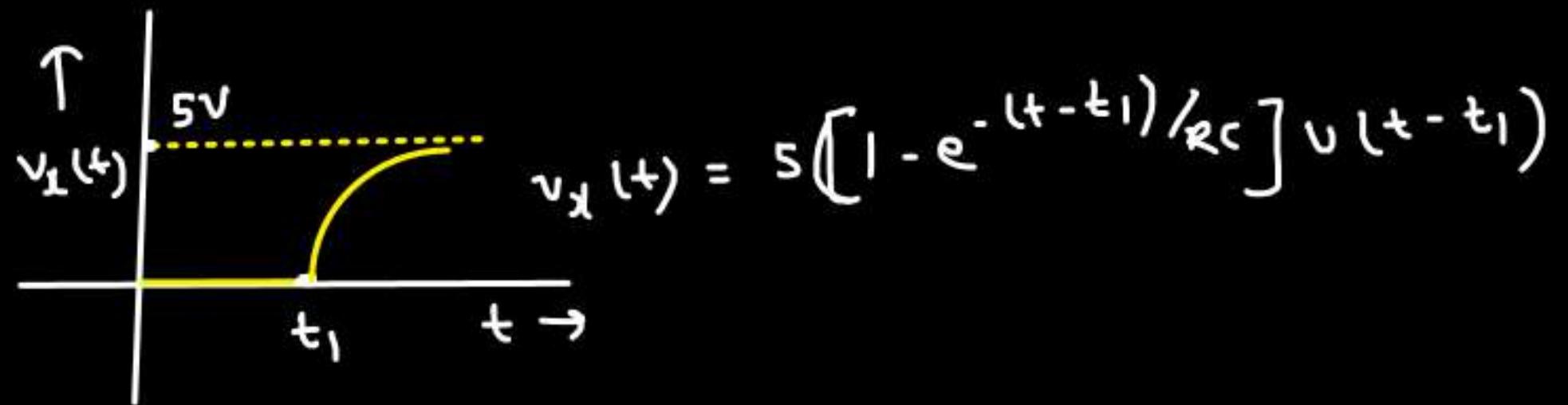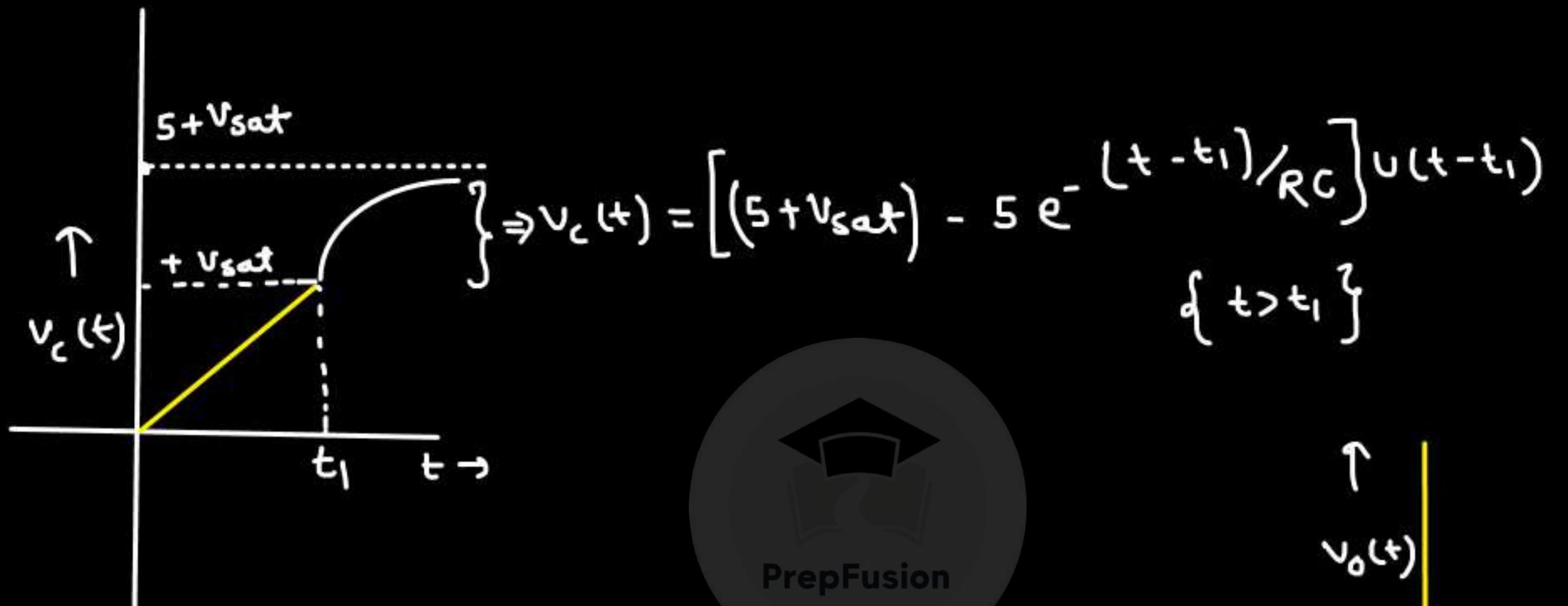

(b)

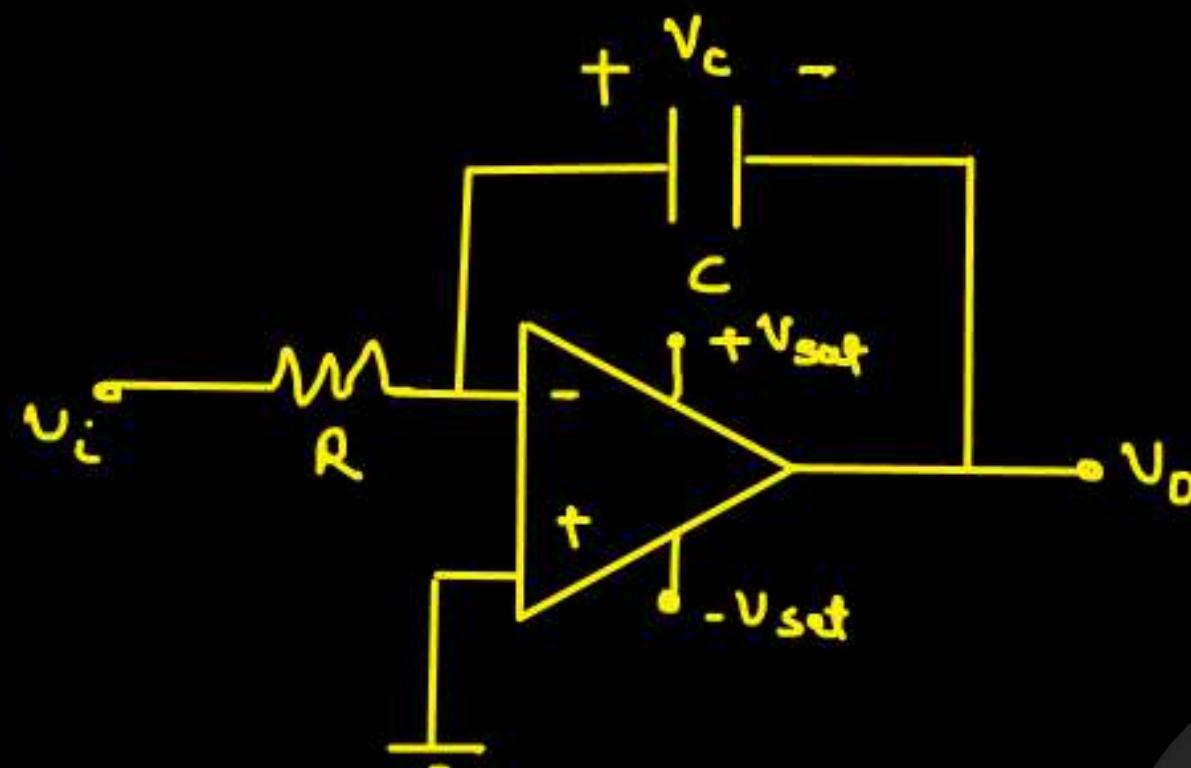

0 < t < $T_{1/2}$:-

$$v_L = 5V$$

$$v_o(t) = -\frac{5t}{RC}$$

$$v_o(T_{1/2}) = -\frac{5T}{2RC}$$

$$v_c(T_{1/2}) = \frac{5T}{2RC}$$

now, $T_{1/2} < t < T$

$$v_L = 0V$$

$$v_c(T_{1/2} < t < T) = \frac{5T}{2RC}$$


$$v_o(T_{1/2} < t < T) = -\frac{5T}{2RC}$$


now, $T < t < 3T/2$

$$v_L = 5V$$

$$v_c(t) = \frac{5T}{2RC} + \frac{5}{RC}(t-T)$$

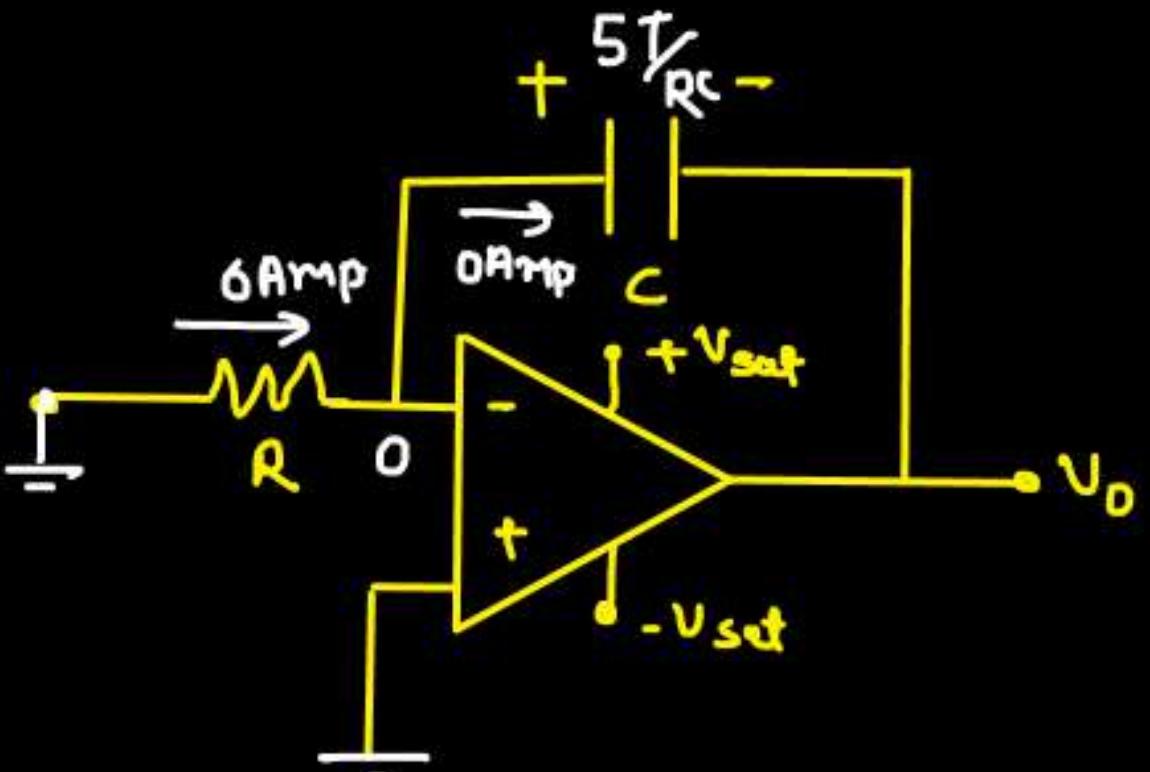
$$v_c(3T/2) = \frac{5T}{RC}, v_o(3T/2) = -\frac{5T}{RC}$$



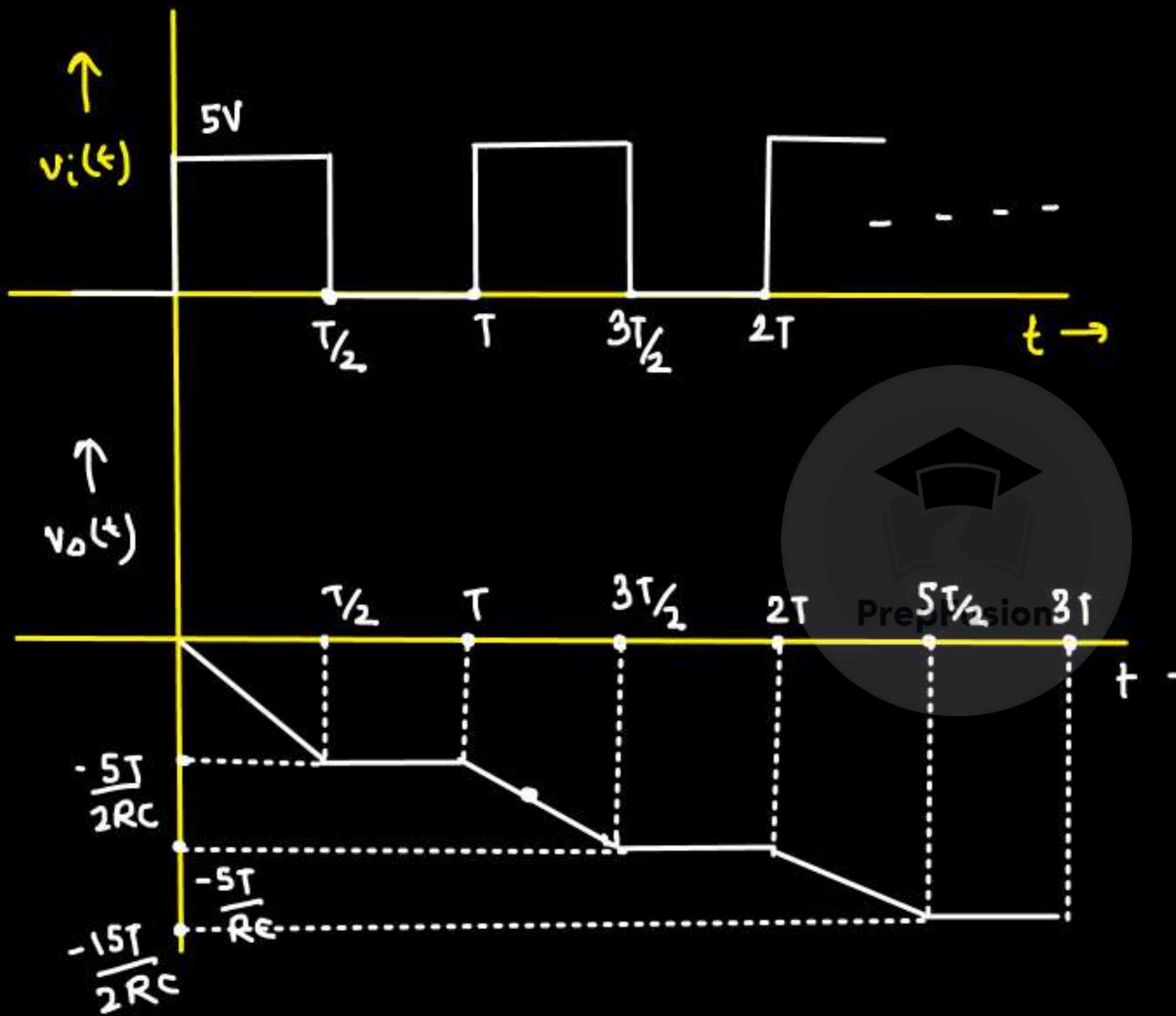


considering o/p doesn't
saturate in time window

$\frac{T}{2}$

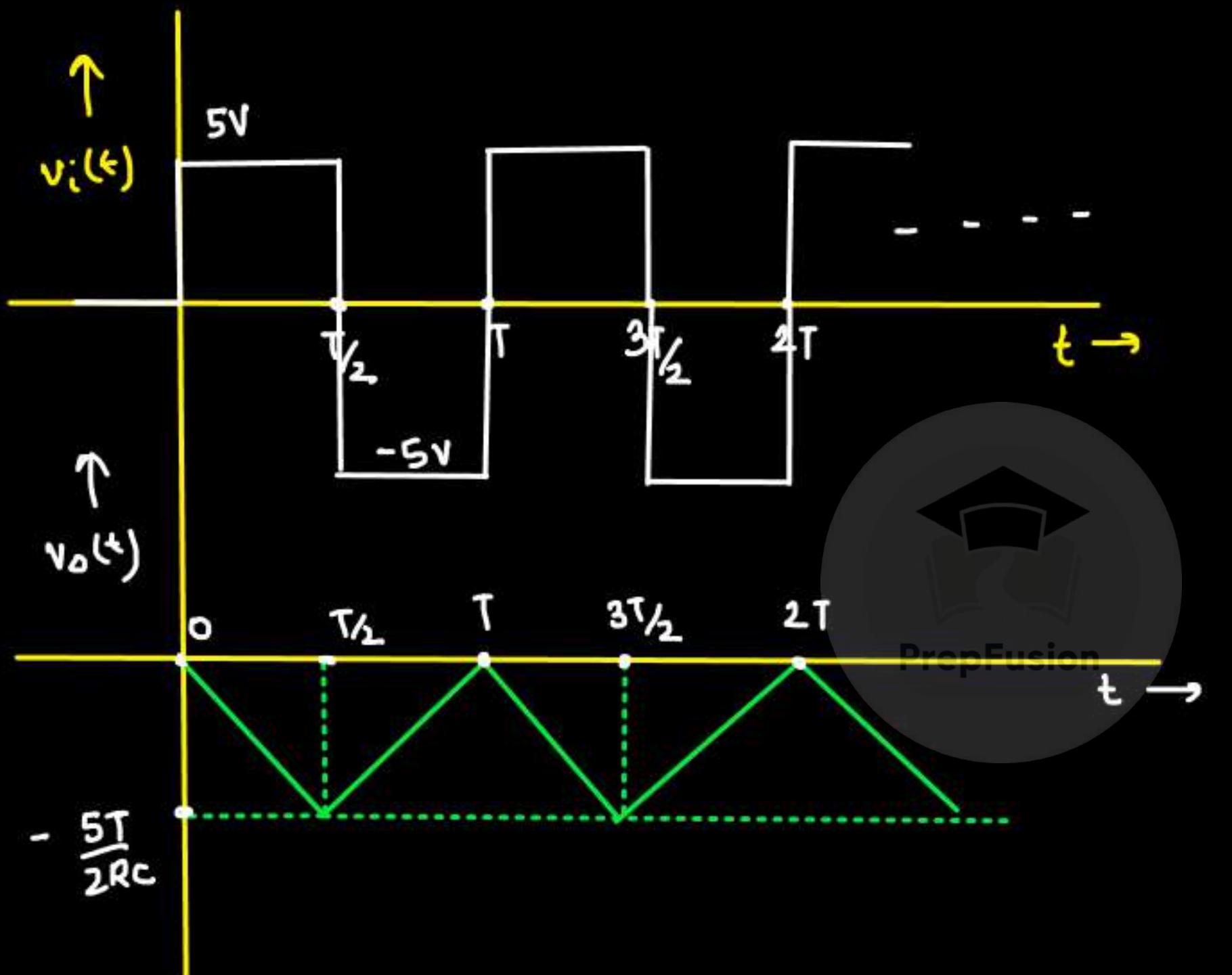

considering o/p doesn't
saturate in time window
 $T/2$

$$\frac{T}{2} < t < T \therefore$$

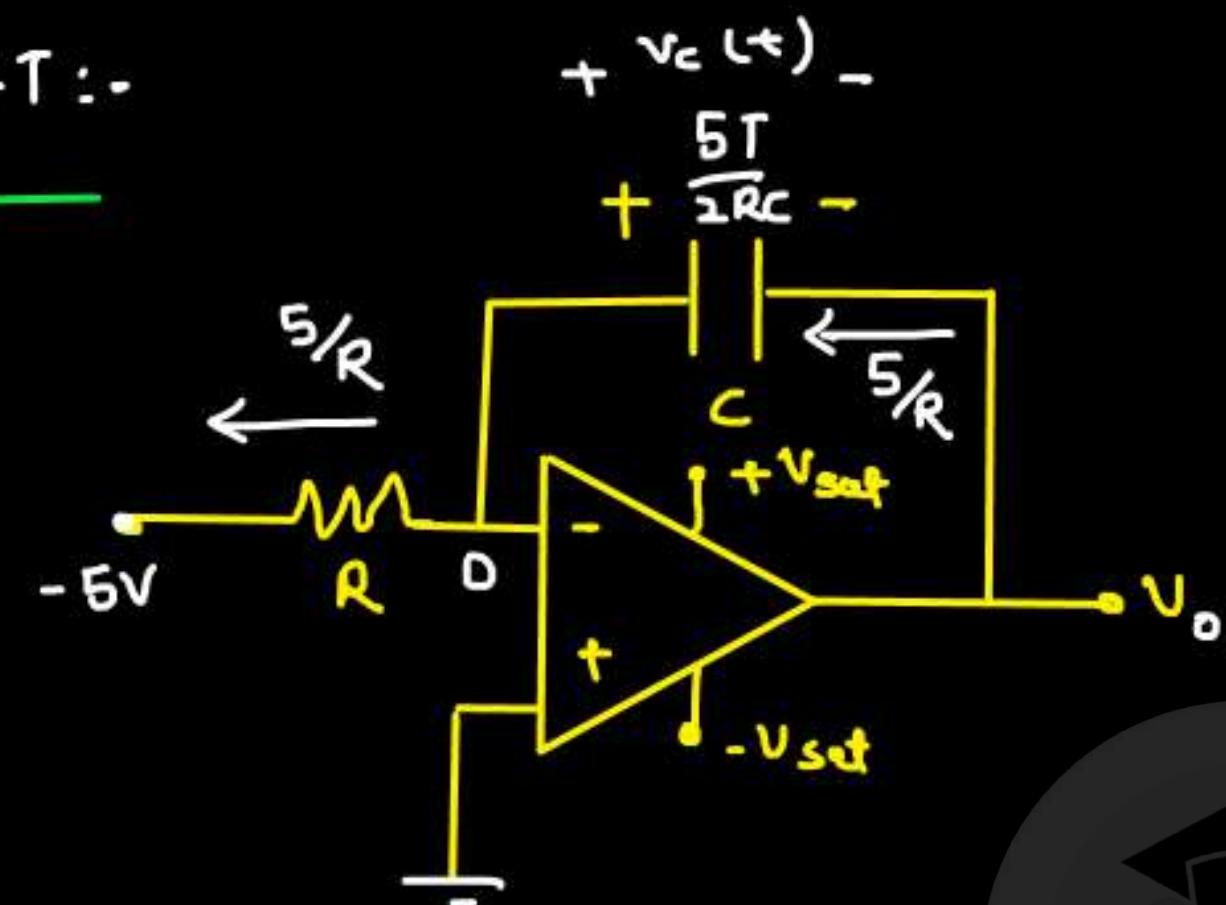


$$v_c(t) = \frac{5T}{2RC} - \frac{5}{RC}(t - \frac{T}{2})$$

$$v_c(T) = \frac{5T}{2RC} - \frac{5T}{2RC} = 0$$




Q. Draw O/P waveform for the given i/p.

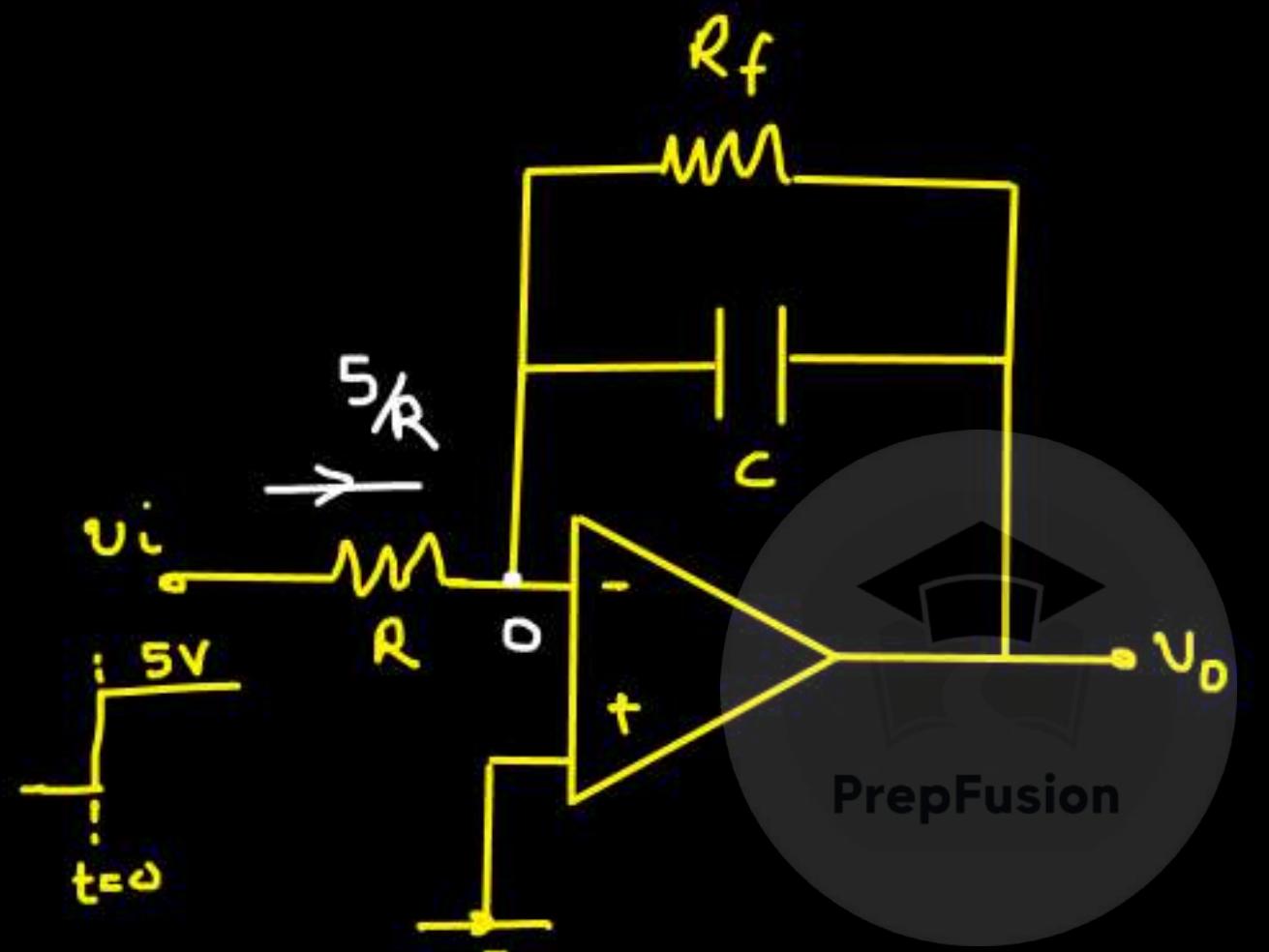


Considering OP-amp has
very High Saturation
voltage.

$$@ t = 0^+ \Rightarrow \text{Cap. S.C.} \Rightarrow v_o(t=0) = 0V$$
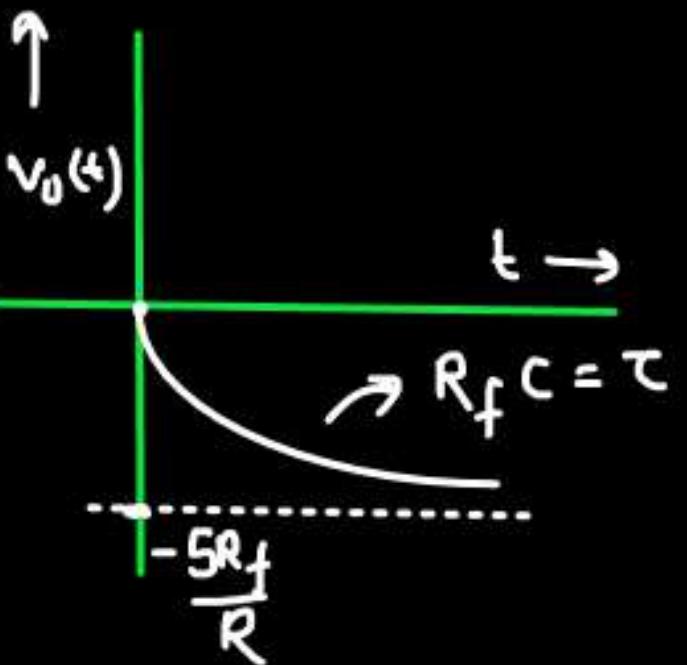
$$t = \infty \Rightarrow \text{Cap. O.C.} \Rightarrow v_o(t=\infty) = -\frac{5R_f}{R}$$




Q.


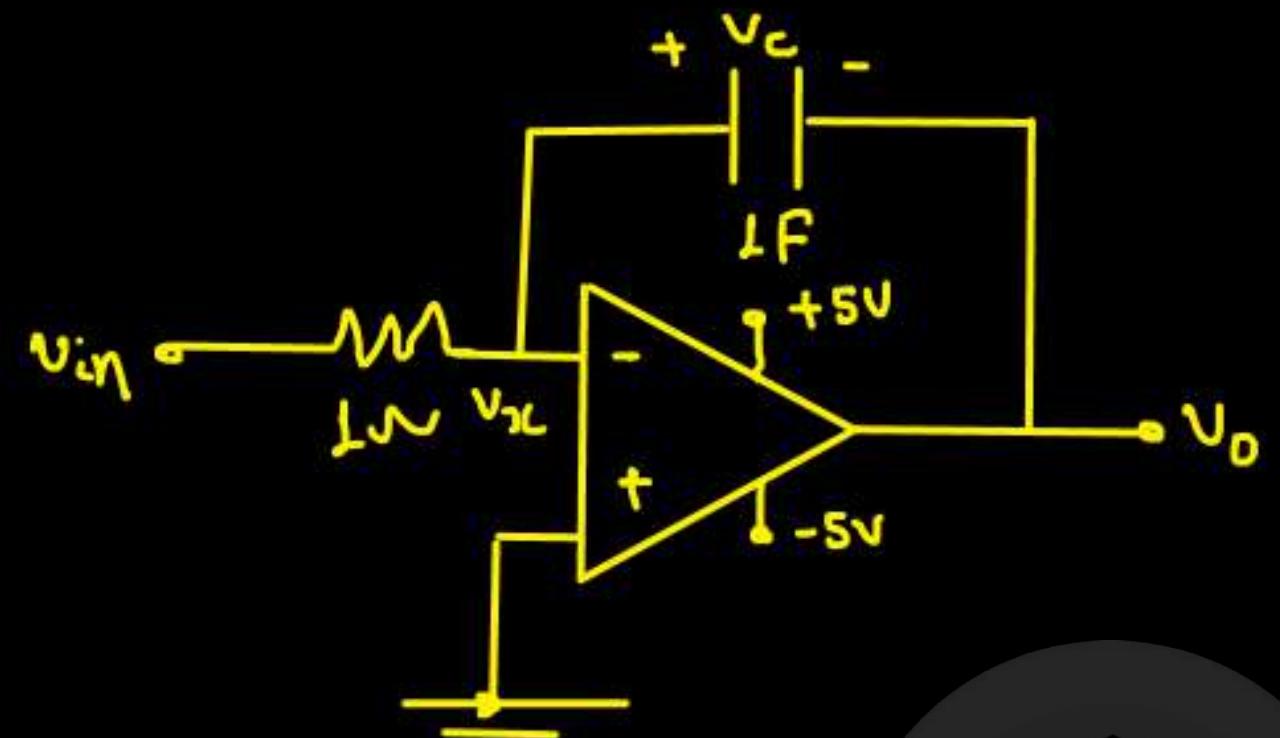


Draw v_c , v_x and v_o waveform.

Find v_o value at $t = 10 \text{ sec.}$

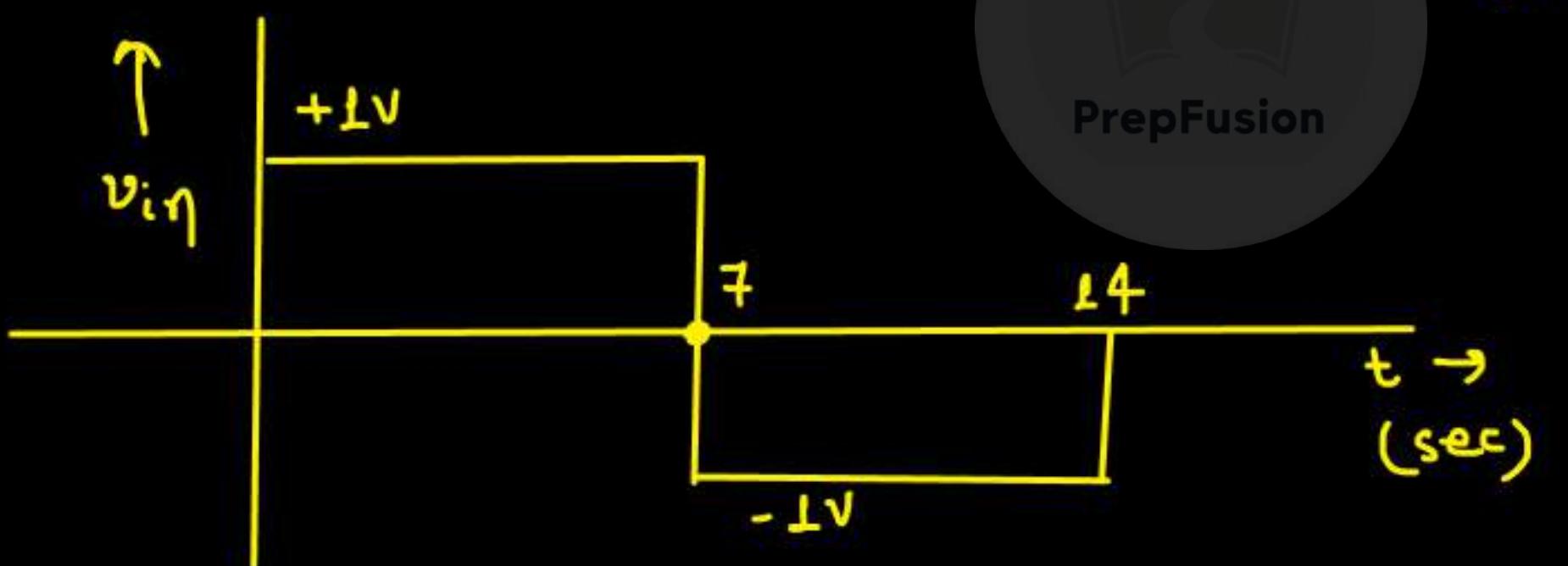



④ $t=0^+$

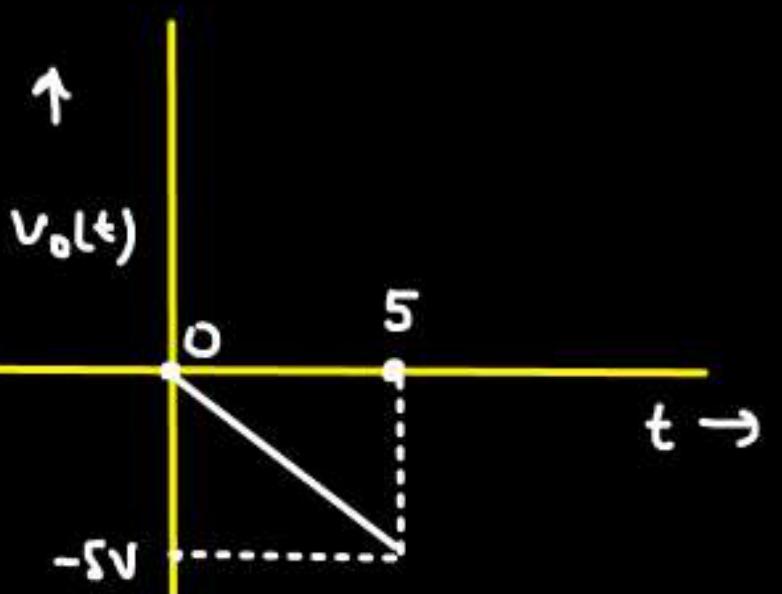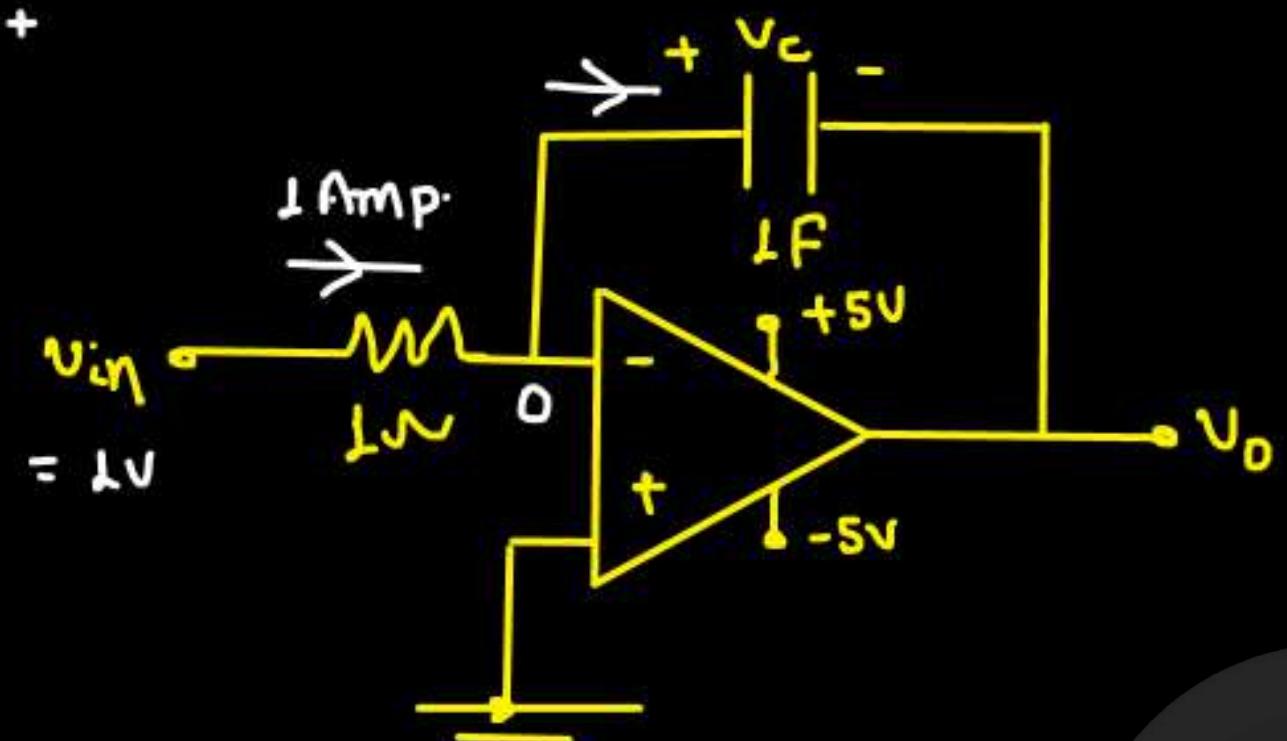

$$V_c(t) = \frac{1}{C} \int_0^t i(t) dt = \frac{1}{1} \int_0^t 1 dt = t \text{ volt}$$


PrepFusion

$$V_o(t) = -V_c(t)$$

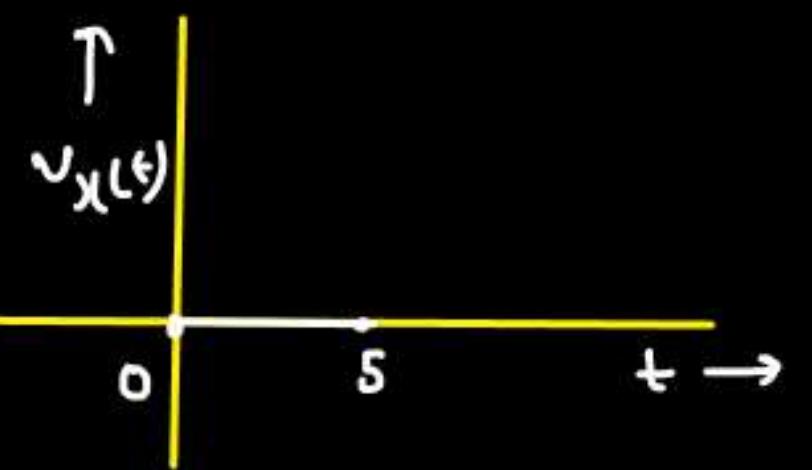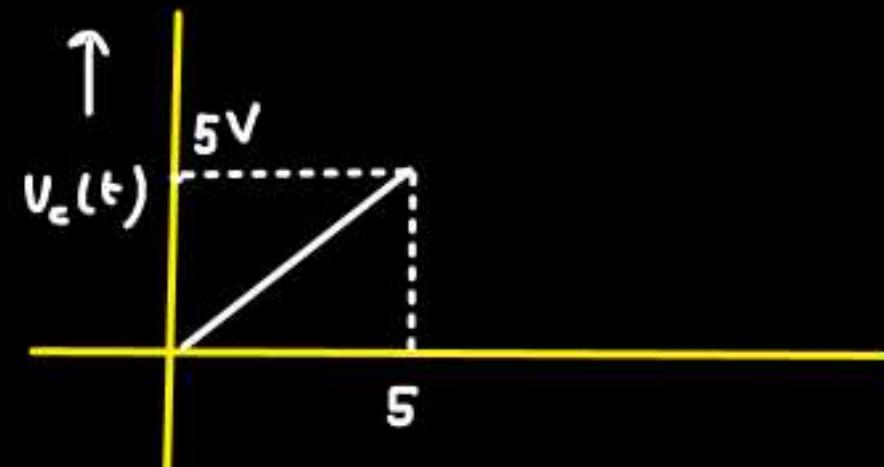

@ $t = 5 \text{ sec}$, o/p saturates \Rightarrow virtual short NOT valid

$5 \text{ sec} < t < 7 \text{ sec.}$

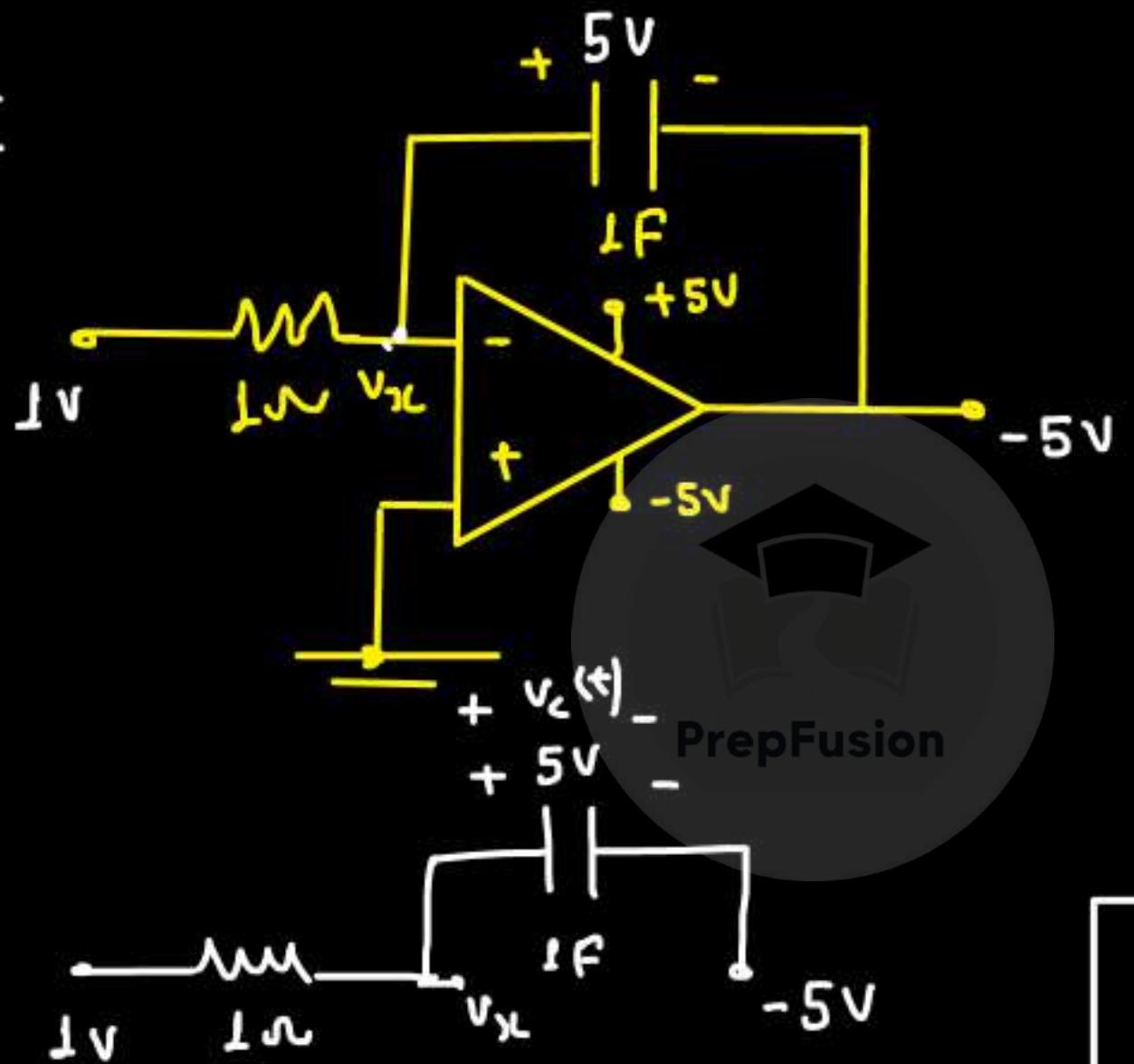

$$V_x(5 \text{ sec}) = 0 \text{ V}$$

$$V_x(\infty) = 1 \text{ V}$$

$$V_x(t) = [1 - e^{-(t-5)/1}] u(t-5)$$



$$V_c(t) = [6 - e^{-(t-5)}] u(t-5)$$

$$V_c(5 \text{ sec}) = 5 \text{ V}$$

$$V_c(\infty) = 6 \text{ V}$$

$$v_x(1\text{sec}) = L - e^{-2/L}$$


$$= 0.864 \text{ V}$$

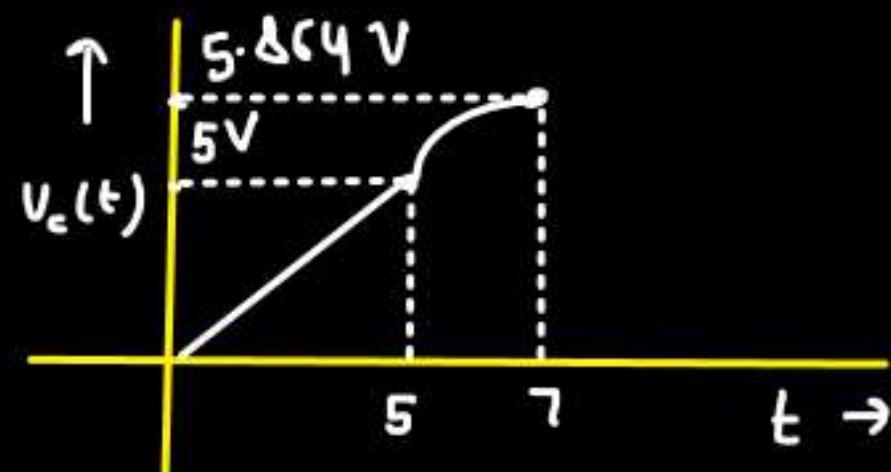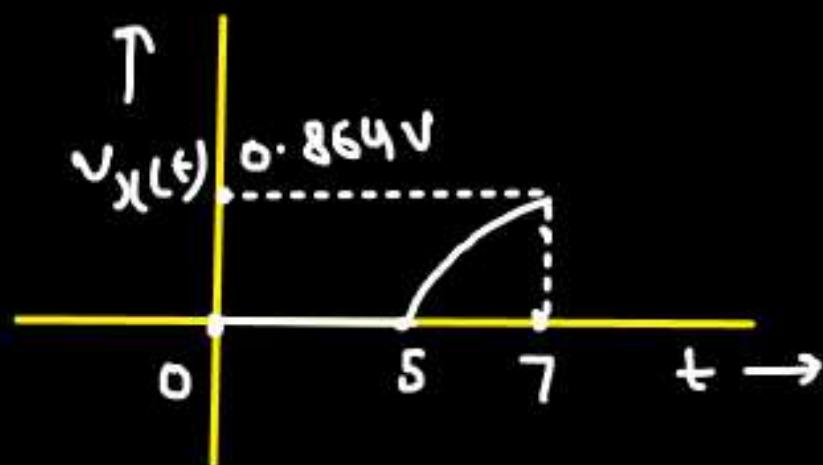


PrepFusion

$$v_c(1\text{sec}) = 6 - e^{-2}$$

$$= 5.864 \text{ V}$$

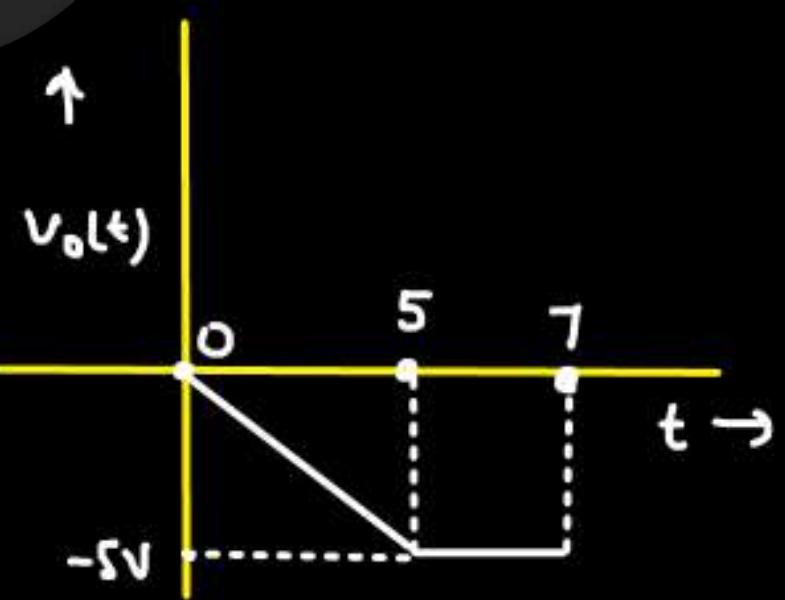


at $t = 7^+$ sec.

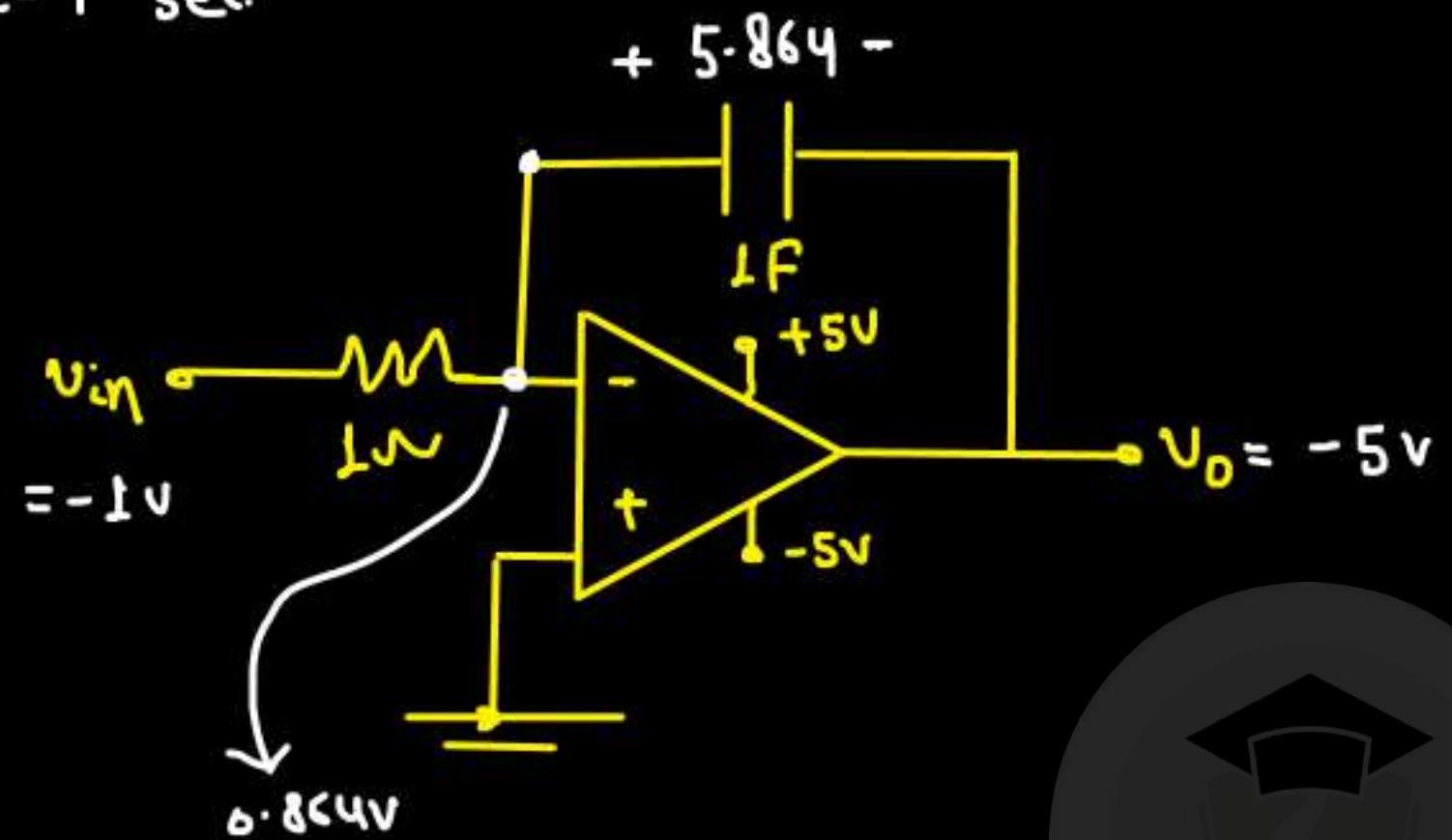

PrepFusion

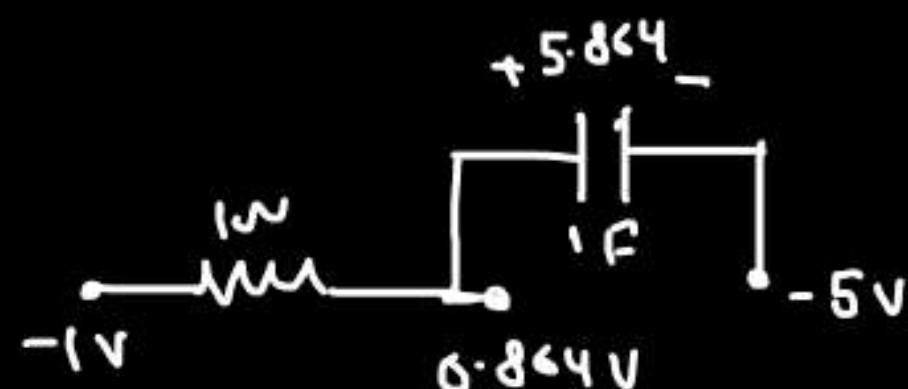O/p is still saturated \Rightarrow concept of virtual short is not valid



$$v_x(t=7^+) = 0.864V$$

$$v_x(t=\infty) = -1V$$

$$v_c(t=7^+) = 5.864V, \quad v_c(t=\infty) = 4V$$

$$v_x(t) = [-1 + 1.864 e^{-(t-1)}] u(t-1)$$

$$v_c(t) = [4 + 1.864 e^{-(t-1)}] u(t-1)$$

at $t = t_1$; $v_x(t_1) = 0$

$$-1 + 1.864 e^{-(t_1-1)} = 0$$

$$t_1 = 1.625 \text{ sec}$$

$$v_x(1.625 \text{ sec}) = 0 \text{ V}$$

$$v_c(1.625 \text{ sec}) = 5 \text{ V}$$

⇒ if v_x node goes below 0V, then cap. voltage changes instantaneously which is not possible. So, v_x node stays at 0V

