

Interview Questions – 13 May 2026

- 1 Introduce yourself.
- 2 Explain all projects briefly, focusing only on the chip working.
- 3 Explain Bandgap Reference (BGR) calibration.
- 4 What is a Sigma-Delta Modulator?
- 5 What are decimation filters? Were they provided by the designer, or did you develop them?
- 6 Explain the Sigma-Delta block diagram in detail along with its working principle.
- 7 How many integrators are used in a Sigma-Delta Modulator? Why is only one integrator used?
- 8 Explain PLL briefly with a block diagram.
- 9 How many bugs did you find, and in which block?
- 10 Have you worked in Virtuoso for schematic design?
- 11 What is the difference between a Flash ADC and a Sigma-Delta ADC?
- 12 Which model is best for development considering time constraints?
- 13 What are wreal and SystemVerilog RNM models?
- 14 How did you verify SCS versus RNM?